

NOVEMBER 1978

Australia 85c; Malaysia \$2.50; New Zealand 85c

50p

TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS

Eliminating Ghosts

Thorn 9000 Chassis Faults
Channel Display using LEDs

PHD COMPONENTS
RADIO & TV COMPONENT DISTRIBUTORS
UNIT 7 CENTENARY ESTATE
JEFFRIES RD ENFIELD MIDDX
CALLERS BY APPOINTMENT ONLY TELE 261295

ALL COMPONENTS PRICED EACH
(INCLUSIVE OF VAT AT 12½%)
NO MINIMUM ORDER CHARGE
PLEASE ADD 35p POST & PACKING

CAPACITORS

Description	
DECCA 400-400/350V	3.25
GEC 2000/200-150-50/350V	1.90
GEC 1000-2000/35	1.85
GEC/G8 600/300V	1.83
GEC/G8 600/250V	1.55
RRI 600/300V	1.83
PYE 631 200-300/350	2.69
PYE 159 1000-1000/40	0.85
RRI 823 2500-2500/30	1.03
RRI 300-300/300	2.47
ITT/K8 200-200-75-25	2.86
TCE 950 100-300-100-16/275	1.83
TCE 400 150-100-100-100-15	3.51
TCE 1500 150x 150 x 100	1.99
TCE 3000/3500 175-100-100	2.16
TCE 3000/3500 1000/70V	0.65
TCE 3000/3500 220/100	0.47
TCE 8000/8500 2500/2500/63	1.41
TCE 8000/8500 700/B00	0.93
TCE 8000/8500 400/350	0.93
300-300/350	2.82
100-200/275	1.41
100-200-60/275	1.41
200-200-400/350	3.05
200-200-100-32/350	1.41
125-300-100/350	1.41
300-200-100/300	1.41
2000-2000/40	0.70
300-300-100-32	1.41
300-300-100-50	1.41
220-100-47-22/340	1.41
200-100-100-150/350	1.41

DROPPERS

Dropper TCE 1400	1.06
Dropper TCE 1500	0.85
Dropper TCE 1600	0.89
Dropper TCE 3000/3500	0.54
Dropper TCE 8000	0.80
Dropper TCE 8500	0.85
Dropper Philips G8	0.49
Dropper Philips G10	0.25
Dropper Philips 210	0.63
Philips 210 (Link)	0.54
Dropper RRI 141	0.42
Dropper RRI 161	0.58
Dropper 27840	0.83
Dropper GEC 2000	0.71
Dropper PYE 11062	0.85
Dropper PYE	0.95

DIODES & RECTIFIERS

AA116 Diode	0.11
AA117 Diode	0.11
AA119 Diode	0.11
OA47 Diode	0.08
OA79 Diode	0.08
OA81 Diode	0.08
OA85 Diode	0.08
OA90 Diode	0.08
OA91 Diode	0.08
OA95 Diode	0.08
OA202 Diode	0.12
BA100 Diode	0.12
BA102 Diode	0.07
BA130 Diode	0.10
BA145 Diode	0.20
BA148 Diode	0.06
BA154 Diode	0.09
BA155 Diode	0.09
BA164 Diode	0.09
BA13 Diode	0.11
BAX16 Diode	0.07
BAY38 Diode	0.11
BY206 Diode	0.20
SK3F/04 Diode	0.20
IN1418 Diode	0.05
IS44 Diode	0.05
BY126 Rectifier	0.10
BY127 Rectifier	0.12
BY133 Rectifier	0.15
BY164 Rectifier	0.50
BY179 Bridge Rectifier	0.96
BY182 Bridge Rectifier	1.27
BY238 Rectifier	0.14
BYX10 Rectifier	0.16
BY187 High Voltage Rectifier	0.30
IN4001 Rectifier	0.08
IN4002 Rectifier	0.08
IN4003 Rectifier	0.09
IN4004 Rectifier	0.09
IN4005 Rectifier	0.10
IN4006 Rectifier	0.10
IN4007 Rectifier	0.11
BY142 Rectifier	0.10
BR100	0.30
BR101	0.35
BRV39	0.35
BT116	1.70
BT119	2.00
BT120	2.00
T106	1.40
2N4443	1.50
BT100A/02	1.50
OT112	3.50
BYX55/350	0.60
BYX55/600	0.60
BYX71/600	0.60
2N4444 Thyristor	1.27
BT109 Thyristor	1.27

TRANSISTORS

AC107 Transistor	0.20
AC126 Transistor	0.20
AC127 Transistor	0.20
AC127/01 Transistor	0.30
AC128 Transistor	0.20
AC128/01 Transistor	0.30
AC141 Transistor	0.20
AC141K Transistor	0.20
AC142 Transistor	0.27
AC142K Transistor	0.45
AC153 Transistor	0.45

AC176 Transistor	0.30
AC176/01 Transistor	0.45
AC186 Transistor	0.30
AC187 Transistor	0.30
AC187K Transistor	0.45
AC188 Transistor	0.30
AC188K Transistor	0.45
AC193K Transistor	0.45
AC194K Transistor	0.50
AD140 Transistor	1.50
AD142 Transistor	1.50
AD143 Transistor	1.50
AD145 Transistor	1.50
AD149 Transistor	1.00
AD161 Transistor	0.50
AD162 Transistor	0.50
AD262 Transistor	1.20
AF114 Transistor	0.45
AF115 Transistor	0.45
AF116 Transistor	0.45
AF117 Transistor	0.45
AF118 Transistor	0.45
AF121 Transistor	0.45
AF124 Transistor	0.45
AF125 Transistor	0.45
AF126 Transistor	0.45
AF127 Transistor	0.45
AF139 Transistor	0.45
AF239 Transistor	0.60
AL102 Transistor	2.70
AU107 Transistor	2.70
AU110 Transistor	2.70
AU113 Transistor	2.70
BC107 Transistor	0.15
BC108 Transistor	0.15
BC109 Transistor	0.15
BC113 Transistor	0.12
BC114 Transistor	0.12
BC115 Transistor	0.15
BC116 Transistor	0.15
BC117 Transistor	0.15
BC118 Transistor	0.12
BC119 Transistor	0.33
BC125 Transistor	0.15
BC126 Transistor	0.14
BC136 Transistor	0.14
BC137 Transistor	0.14
BC138 Transistor	0.28
BC139 Transistor	0.28
BC140 Transistor	0.28
BC142 Transistor	0.28
BC143 Transistor	0.28
BC147 Transistor	0.10
BC148 Transistor	0.10
BC149 Transistor	0.10
BC150 Transistor	0.10
BC154 Transistor	0.10
BC157 Transistor	0.10
BC158 Transistor	0.10
BC159 Transistor	0.28
BC161 Transistor	0.28
BC168 Transistor	0.10
BC171 Transistor	0.10
BC172 Transistor	0.10
BC177 Transistor	0.17
BC178 Transistor	0.17
BC179 Transistor	0.17
BC182 Transistor	0.10
BC183 Transistor	0.10
BC183L Transistor	0.10
BC184L Transistor	0.10
BC184LC Transistor	0.12
BC186 Transistor	0.18
BC187 Transistor	0.18
BC203 Transistor	0.10
BC204 Transistor	0.10
BC205 Transistor	0.10
BC206 Transistor	0.10
BC225 Transistor	0.10
BC208 Transistor	0.10
BC209 Transistor	0.10
BC212 Transistor	0.10
BC213L Transistor	0.10
BC214 Transistor	0.10
BC225 Transistor	0.10
BC237 Transistor	0.15
BC238 Transistor	0.10
BC251A Transistor	0.10
BC301 Transistor	0.30
BC303 Transistor	0.30
BC307 Transistor	0.10
BC308 Transistor	0.10
BC327 Transistor	0.11
BC328 Transistor	0.11
BC337 Transistor	0.11
BC338 Transistor	0.11
BC547 Transistor	0.11
BD115 Transistor	0.35
BD116 Transistor	0.80
BD124P Transistor	1.80
BD131 Transistor	0.45
BD132 Transistor	0.45
BD133 Transistor	0.54
BD134 Transistor	0.54
BD135 Transistor	0.54
BD136 Transistor	0.54
BD137 Transistor	0.54
BD138 Transistor	0.54
BD139 Transistor	0.54
BD140 Transistor	0.54
BD144 Transistor	2.50
BD155 Transistor	0.60
BD157 Transistor	0.60
BD158 Transistor	0.60
BD163 Transistor	0.60
BD165 Transistor	0.60
BD175 Transistor	0.60
BD177 Transistor	0.60
BD183 Transistor	0.60
BD187 Transistor	0.60
BD210 Transistor	1.24
BD235 Transistor	0.54
BD236 Transistor	0.54
BD237 Transistor	0.54
BD238 Transistor	0.54
BD239 Transistor	0.54
BD380 Transistor	0.54
BD437 Transistor	0.54
BD439 Transistor	0.54

BD441 Transistor	0.54
BD535 Transistor	0.54
BD536 Transistor	0.54
BD537 Transistor	0.54
BD538 Transistor	0.54
BDX73 Transistor	0.80
BDY201 Transistor	2.10
BF115 Transistor	0.45
BF118 Transistor	0.45
BF121 Transistor	0.45
BF152 Transistor	0.30
BF154 Transistor	0.15
BF155 Transistor	0.15
BF160 Transistor	0.15
BF163 Transistor	0.45
BF167 Transistor	0.45
BF173 Transistor	0.45
BF177 Transistor	0.45
BF178 Transistor	0.45
BF179 Transistor	0.45
BF181 Transistor	0.45
BF182 Transistor	0.45
BF183 Transistor	0.45
BF184 Transistor	0.45
BF185 Transistor	0.45
BF194 Transistor	0.10
BF195 Transistor	0.60
BF196 Transistor	2.70
BF197 Transistor	2.70
BF198 Transistor	2.70
BF199 Transistor	2.70
BF200 Transistor	0.15
BF224 Transistor	0.15
BF240 Transistor	0.15
BF241 Transistor	0.12
BF256LC Transistor	0.12
BF257 Transistor	0.15
BF258 Transistor	0.15
BF27 Transistor	0.15
BF273 Transistor	0.12
BF274 Transistor	0.33
BF326 Transistor	0.15
BF333 Transistor	0.14
BF338 Transistor	0.14
BF355 Transistor	0.14
BF458 Transistor	0.28
BF459 Transistor	0.28
BF473 Transistor	0.28
BFX23 Transistor	0.28
BFX24 Transistor	0.28
BFX85 Transistor	0.10
BFX88 Transistor	0.10
BFX89 Transistor	0.10
BFY50 Transistor	0.10
BFY5 Transistor	0.10
BFY82 Transistor	0.10
BFY90 Transistor	0.90
BDX32 Transistor	2.40
BU105 Transistor	1.50
BU105/01 Transistor	2.40
BU105/02 Transistor	2.40
BU105/04 Transistor	2.40
BU108 Transistor	1.50
BU204 Transistor	2.40
BU205 Transistor	1.50
BU206 Transistor	2.40
BU208 Transistor	2.40
BU208/02 Transistor	2.40
BU326S Transistor	2.40
BU406 Transistor	1.89
BU406D Transistor	2.66
BU407 Transistor	1.59
BU407 Transistor	2.40
2SC1172Z Transistor	2.40
R2008 Transistor	2.25
R2009 Transistor	2.25
R2010 Transistor	2.55
R2540 Transistor	3.00
ME0404 Transistor	0.15
ME0412 Transistor	0.15
ME4003 Transistor	0.10
ME6002 Transistor	0.15
ME8001 Transistor	0.12
MJ340 Transistor	0.75
MJE520 Transistor	0.60
MJE2955 Transistor	0.96
MJE3055 Transistor	0.87
MJE2955 Transistor	1.20
MJ3055 Transistor	1.20
MP8113 Transistor	0.75
MPS005 Transistor	0.11
MPS005 Transistor	0.11
MPS155 Transistor	0.11
PIP31A Transistor	0.48
TIP32A Transistor	0.48
TIP41A Transistor	0.75
TIP42A Transistor	0.75
TIP2995 Transistor	0.96
TIP3055 Transistor	0.96
TIS91M Transistor	0.21
2N2904 Transistor	0.33
2N2905A Transistor	0.36
2N2905 Transistor	0.36
2N3053 Transistor	0.36
2N3055 Transistor	0.36
2N3703 Transistor	0.88
2N3705 Transistor	0.12
2N3710 Transistor	0.12
2N5296 Transistor	0.57
2N5298 Transistor	0.57
2N5496 Transistor	0.63
2N6178 Transistor	0.90
2N6180 Transistor	0.90


INTEGRATED CIRCUITS

TA4550 Int Circuit	0.25
TA4570 Int Circuit	2.10
TA4611 B12 Int Circuit	2.00
TA4630S Int Circuit	2.50
TA4661B Int Circuit	1.60
TA4700 Int Circuit	3.75
TA0100 Int Circuit	1.50
TBA120AS Int Circuit	0.63
TBA231 Int Circuit	1.05
TBA325 Int Circuit	0.50

TBA480Q Int Circuit	1.94
TBA520Q Int Circuit	2.80
TBA530Q Int Circuit	2.25
TBA530Q Int Circuit	2.40
TBA540Q Int Circuit	2.60
TBA540Q Int Circuit	2.60
TBA550Q Int Circuit	3.15
TBA550Q Int Circuit	3.15
TBA560Q Int Circuit	3.15
TBA560Q Int Circuit	3.40
TBA570Q Int Circuit	1.62
TBA570Q Int Circuit	1.74
TBA641 BX1 Int Circuit	2.61
TBA641 B11 Int Circuit	3.18
TBA651 Int Circuit	1.75
TBA700Q Int Circuit	1.25
TBA720AQ Int Circuit	2.60
TBA730Q Int Circuit	0.50
TBA750Q Int Circuit	2.25
TBA750Q Int Circuit	2.25
TBA800 Int Circuit	1.30
TBA810S Int Circuit	1.50
TBA820 Int Circuit	1.05
TBA820 Int Circuit	3.66
TBA820Q Int Circuit	3.75
TBA890 Int Circuit	3.75
TBA990 Int Circuit	3.60
TCA270Q Int Circuit	2.00
TCA900 Int Circuit	0.87
TCA940 Int Circuit	2.25
TDA1170 Int Circuit	2.60
TDA1200 Int Circuit	2.25
TDA1270 Int Circuit	2.60
TDA1412 Int Circuit	0.90
TDA2020 Int Circuit	3.80
MC1307P Int Circuit	1.60
MC1310P Int Circuit	1.80
MC1327P Int Circuit	2.10
MC1327PQ Int Circuit	2.10
MC1330P Int Circuit	1.35
MC1351P Int Circuit	1.74
MC1352P Int Circuit	1.30
MC1358PQ Int Circuit	1.40
SN76003N Int Circuit	3.10
SN76003ND Int Circuit	2.60
SN76013N Int Circuit	2.20
SN76013N07 Int Circuit	2.20
SN76013ND Int Circuit	2.20
SN76023N Int Circuit	2.00
SN76023ND Int Circuit	2.00
SN76001N Int Circuit	3.00
SN76110N Int Circuit	1.60
SN76131N Int Circuit	1.90
SN76226DN Int Circuit	1.30
SN76227N Int Circuit	1.00
SN76532N Int Circuit	1.20
SN76533N Int Circuit	1.50
SN76544N Int Circuit	1.70
SN76650N Int Circuit	1.50
SN76660N Int Circuit	0.80
SN76665N Int Circuit	1.20
SN76666N Int Circuit	0.80
SL901B Int Circuit	7.50
SL917B Int Circuit	9.90
TBA396Q Int Circuit	0.50
TDA440 Int Circuit	2.50
SN76001N Int Circuit	2.00

VALVES

DY86/87 Valve	1.00
DY80	

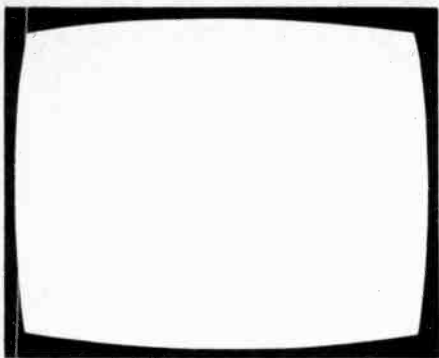

TELEVISION

November
1978

Vol. 29, No. 1
Issue 337

COPYRIGHT

© IPC Magazines Limited, 1978. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

BINDERS AND INDEXES

Binders (£2.85) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders add 60p to cover despatch and postage.

BACK NUMBERS

Some back issues, mostly those published during the last two years, are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 70p inclusive of postage and packing to both home and overseas destinations.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Your Problems Solved". Send to the address given above (see "correspondence").

this month

- 7 **Leader**
- 8 **Teletopics**
News, comment and development.
- 13 **Eliminating Ghosts** *by Bill Wright*
An aerial specialist with considerable experience of ghosting in an area plagued with this problem discusses methods of cleaning up the picture, in particular by careful adjustment of horizontally stacked arrays.
- 16 **Letters**
- 18 **Thorn 9000 Chassis Faults** *by John Coombes*
A summary of fault experiences on this unusual chassis, with its Syclops combined line output/regulated power supply circuit.
- 21 **Long-Distance Television** *by Roger Bunney*
Reports on DX reception and conditions, and news from abroad. Also notes on varicap tuners and some interesting f.e.t. circuits.
- 24 **Colour Receiver Project, Part 2** *by Luke Theodossiou*
Introducing the signals board. Complete circuitry plus a description of the pin-diode tuner and the i.f. strip.
- 32 **Twisted Tails** *by Les Lawry-Johns*
Problems this month include trouble with a Spaniel in need of trimming.
- 34 **LED Channel Display** *by Alan Damper*
A problem when using varicap tuners with rotary manual control is to know which channel is being received. This simple system not only gives channel identification but also indicates optimum tuning.
- 35 **Readers' PCB Service**
- 36 **The Language of Logic, Part 2** *by E. A. Parr, B.Sc., C.Eng., M.I.E.E.*
Start of an illustrated dictionary of terms used in connection with electronic logic systems.
- 40 **TV Servicing: Beginners Start Here, Part 14** *by S. Simon*
Fault finding in valve field timebase circuits, with particular reference to the things that go wrong in the Thorn 1500 chassis.
- 43 **Next Month in Television**
- 44 **Versatile Remote Control System** *by Brian Dance, M.Sc.*
Plessey's new remote control system for TV receivers uses pulse-position modulation and two special i.c.s. The link can be either ultrasonic or infra-red. The system and the circuitry are described. The system has already been adopted by several continental setmakers.
- 47 **Your Problems Solved**
- 49 **Test Case 191**

OUR NEXT ISSUE DATED DECEMBER WILL BE
PUBLISHED ON NOVEMBER 20

EX-EQUIPMENT SPARES

MONO TUBES (tested) 19" Rimguard £3.00 23" Rimguard £4.00 20" Rimguard £5.00 24" Rimguard £6.00 +£3.00 p.p.	MONO TUNERS 6 - button integrated all at £6.50 U.H.F. P/Button D/S £4.50 U.H.F. P/Button S/S £6.50 Rotary £3.00 + £1. p.p.	MONO LOPTS All D/Standard Lopts at £4.00 + £1. p.p. All S/Standard at £4.00 + £1. p.p.	MONO PANELS i.e. Philips, Bush etc. £3.50 + £1 p.p. Quotations for complete S/Hand chassis if required. (Diff prices)	MISC. S/Output Trans. £1 + VAT + £1 P&P F/Output Trans. £1.25 + VAT + £1. P&P Scancoils £1.50 + VAT + £1. P&P. Other spares available. please write or phone for details.
--	---	---	--	---

VALVES (MONO & COLOUR)

PCL82 0.10	PCF802 0.10	PCC86 0.10	EY86/7 0.10	30PL1 0.25	PL509 1.00
PCL83 0.25	PCF805 0.25	PC97 0.20	EY8/7 0.10	30PL13/4 0.10	PY500 1.00
PCL84 0.10	PCF806 0.10	PC900 0.10	DY802 0.10	30P12 0.10	GY501 1.00
PCL85 0.10	PCF808 0.25	EF80 0.10	PY800/1 0.10	30FL1/2 0.25	PL508 0.50
PCL86 0.10	PCF80 0.10	EF85 0.10	PL36 0.25	ECC82 0.10	PCH200 0.50
PFL200 0.10	PCC189 0.10	EF183 0.10	PL504 0.25	ECC81 0.10	PCF200 0.50
PCF801 0.10	PCC86 0.10	EF184 0.10	PL81 0.10	ECH81 0.10	CEY51 0.15
30C1 0.10	30C15 0.10	6BW7 0.10	6/30L2 0.10	ECL80 0.10	
30C17 0.10	30C18 0.25	ECC85 0.10	U26 0.10	ECL82 0.10	
PL83 0.10	PL84 0.10	EH90 0.10			

Please note there is 25p p.p. per order

D/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	EHT	REG	CON	S/OUTPUT	POWER	L/TB	F/TB
Bush/Murphy	6.50	6.50	6.50	—	—	6.50	1.50	6.50	—	—
GEC/Sobell	6.50	7.50	—	—	—	6.50	—	—	—	7.50
Philips	6.50	9.50	—	—	—	7.50	—	—	—	6.50
Decca	6.50	12.50	12.50	—	—	6.50	2.00	8.00	—	6.00
							(19" only)			
Thorn 2000	6.50	7.50	7.50	6.50	6.50	7.00	—	8.00	15.00	6.50
Pye	7.50	7.50	9.50	—	—	6.50	—	—	—	7.50
Baird	6.50	8.50	8.50	—	—	6.50	—	—	—	6.00

Postage & Packing £1.25

S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	9.50	—	20.00	—	8.00	6.00	15.00	—
GEC Hybrid	9.50	9.50	15.00	—	6.00	—	—	12.00
Philips G6 S/S	9.50	—	10.00	—	9.00	—	—	10.00
Thorn 3000	10.00	9.00	18.00	10.00	6.00	20.00	20.00	10.00
Pye 691/693	10.00	7.50	18.00	—	8.00	—	15.00	7.50
Thorn 3500	10.00	9.00	18.00	10.00	10.00	20.00	20.50	10.00

Korting and other foreign panels available on request.

Postage & Packing £1.25

COLOUR TUBES 19" 18.00 19" A49.192 £20 20" 20.00 22" 25.00 25" 18.00 26" 32.00 Plus P & P £4	COLOUR TUNERS Bush 6.50 GEC 6.50 Philips G6 S/S 6.50 Thorn 3000 6.50 Pye 691/697 7.50 Some new tuners in stock can supply on request. Many Foreign Tuners also available on request. Plus P & P £1	COLOUR LOPTS Most lopts available from £7.00. Both British & Foreign makes. Please ring or write. P & P per lopt £1	MISC. S/Output transformer from £1.50 F/Output from £1.25 Scancoils from £5.00 P & P £1 Other spares available on request.	G8 PANELS SPECIAL OFFER CHROMA £12.00 I.F. £10.00 POSTAGE & PACKING £1.25 PER PANEL.
--	---	--	--	--

MAIL ORDER TVs GOOD WORKING

COLOUR				MONO			
Pye 19"	£55.00	22"	£65.00	26"	£75.00	20" & 24" S/S	£16.00
GEC 19"	£55.00	22"	£65.00	26"	£75.00	20" & 24" D/S	£14.00
Bush 19"	£65.00	22"	£75.00	26"	£85.00	19" & 23" D/S	P/button £12.00
Philips G6	—	22"	£63.00	26"	£75.00	19" & 23" D/S	Rotary £8.00

Many other makes & models available. Please ring or write for information.

PERSONAL CALLERS WELCOME

12½% V.A.T. on all prices colour & mono.
 P & P £8.00 per colour set. P & P £5.00 per mono set.

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED.

PLEASE ADD 12½% V.A.T. TO ALL ITEMS AND OVERSEAS AT COST. CASH WITH ALL ORDERS.

BRIARWOOD TELEVISION LTD.

Briarwood House, Preston Street, Bradford, West Yorkshire BD7 1NS Tel (0274) 306018

TELEVISION SALE

DISCOUNT FOR QUANTITY

MONO

Rotaries 19" & 23"

GEC	£ 3.00
Thorn 950 etc.	3.00
K.B.	3.00
Pye	3.00
Thorn 1400	4.50

D/S P/B 19" 23"

Thorn 1400	£ 7.00
Bush 161 etc.	7.00
Baird 660 etc.	7.00
Philips 210 etc.	7.00
Pye Olympic etc.	7.00

D/S P/B 20" 24"

Bush	£ 10.00
GEC	10.00
Philips	10.00
Pye	10.00
Thorn	10.00

S/S 20" 24"

Bush 313 etc.	£ 12.00
Pye 169 chassis	12.00
Thorn 1500	12.00
GEC series 1 & 2	12.00
Decca MS series	12.00

S/S COLOUR

	19"	20"	22"	25"	26"
	£	£	£	£	£
GEC	40	45	45	45	50
Philips	-	-	45	45	50
Thorn	65	-	65	65	85
Bush	60	-	65	65	75
Kort	-	-	65	-	75
Pye	-	-	-	-	-
Varicap	-	-	60	-	70

MAINS DROPPERS

All Popular Makes now in stock e.g.

1500 @	60p	Philips 210 @	40p
8000 @	54p	Bush 161 @	40p
G8 @	36p	Pye 723 @	47p
GEC 2110-41R @ 45p			

PLEASE NOTE THERE IS
12½ V.A.T.

Please note all mono sets sold as 100% comp. No broken masks, no broken panels etc.
Colour sets sold with good c.r.t.s and 100% comp.
Working Mono £3.00 extra
Working Colour £15.00 extra
Supplied in 1's or 100's

**WE DO NOT SELL RUBBISH
AT
BRIARWOOD TV LTD
EXPORT
COLOUR & MONO T.V.s
AVAILABLE READY FOR USE
ABROAD**

BRIARWOOD TELEVISION LTD.

Briarwood House
Preston Street, Bradford, West Yorkshire BD7 1NS.
Tel: (0274) 306018.

All transistors, IC's, offered are new and branded. Manufactured by Mullard, I.T.T., Texas, Motorola etc.

Please add 12½% VAT to all items and overseas at cost.

P & P U.K. 25p per order, overseas allow for package and postage. Cash with all orders. All prices subject to alteration without notice.

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £		
AC107	0.23	BC171	0.12	BF260	0.24	1N5404	0.12		
AC113	0.17	BC172	0.12	BF262	0.28	1N5406	0.13		
AC115	0.17	BC173	0.15	BF263	0.25	1N5408	0.16		
AC117	0.24	BC177	0.14	BF271	0.20	VALVES			
AC125	0.20	BC178	0.14	BF273	0.12	DY87	0.52		
AC126	0.18	BC179	0.14	BF336	0.35	DY802	0.64		
AC127	0.19	BC182L	0.08	BF337	0.24	ECC82	0.52		
AC128	0.17	BC183L	0.07	BF338	0.29	EF80	0.40		
AC131	0.13	BC184L	0.11	BFT42	0.26	EF183	0.60		
AC141	0.23	BC186	0.18	BFT43	0.24	EF184	0.60		
AC142	0.19	BC187	0.18	BFX84	0.27	EH90	0.60		
AC141K	0.29	BC209	0.14	BFX85	0.27	PC86	0.76		
AC142K	0.29	BC212	0.13	BFX88	0.24	PC88	0.76		
AC151	0.17	BC213L	0.09	BFY37	0.22	PCC89	0.65		
AC165	0.16	BC214L	0.14	BFY50	0.18	PC189	0.65		
AC166	0.16	BC237	0.07	BFY51	0.17	PCF80	0.70		
AC168	0.17	BC240	0.31	BFY52	0.18	PCF86	0.68		
AC176	0.17	BC281	0.24	BFY53	0.27	PCF801	0.70		
AC176K	0.28	BC262	0.20	BFY55	0.27	PCF802	0.74		
AC178	0.16	BC263B	0.20	BHA0002	1.90	PCL82	0.67		
AC186	0.26	BC267	0.19	BR100	0.20	PCL84	0.75		
AC187	0.21	BC301	0.26	BSX20	0.23	PCL85	0.78		
AC188	0.20	BC302	0.30	BSX76	0.23	PCL805	0.75		
AC187K	0.34	BC307	0.10	BSY84	0.36	PCF200	1.00		
AC188K	0.34	BC337	0.13	BT106	1.18	PL36	0.90		
AD130	0.50	BC338	0.09	BT108	1.23	PL84	0.74		
AD140	0.65	BC307A	0.12	BT109	1.09	PL504	1.10		
AD142	0.73	BC308A	0.12	BT116	1.23	PL509	2.45		
AD143	0.70	BC309	0.14	BT120	2.08	PY88	0.63		
AD145	0.70	BC547	0.09	BU105/02	1.87	PY500A	1.60		
AD149	0.64	BC548	0.11	BU105/04	2.25	PY81/800	0.57		
AD161	0.41	BC549	0.11	BU126	1.40	E.H.T. TRAYS MONO			
AD162	0.48	BC557	0.11	BU205	1.97	950 MK2 1400	2.26		
AD161	1.30	BD112	0.39	BU208	2.49	1500 18" 19" stick			
AD162	0.42	BD113	0.65	BY126	0.09		2.37		
AF106	0.42	BD115	0.40	BY127	0.10	1500 24" 5 stick	2.48		
AF114	0.23	BD116	0.47	OC22	1.10	Single stick Thorn TV			
AF115	0.22	BD124	1.30	OC23	1.30	11.16K 70V	0.75		
AF116	0.22	BD131	0.32	OC24	1.30	TV 20.2 MT	0.75		
AF117	0.30	BD132	0.34	OC25	1.00	TV20 16K 18V	0.75		
AF118	0.40	BD133	0.37	OC26	1.00	IC's			
AF121	0.43	BD135	0.26	OC28	1.00	SN76013N	1.20		
AF124	0.33	BD136	0.26	OC35	1.00	SN76013ND	1.00		
AF125	0.29	BD137	0.26	OC36	0.90	SN76023N	1.20		
AF126	0.29	BD138	0.26	OC38	0.90	SN76023ND	1.00		
AF127	0.29	BD139	0.40	OC42	0.45	SN76226DN	1.50		
AF139	0.39	BD140	0.28	OC44	0.20	SN76227N	1.20		
AF151	0.24	BD144	1.39	OC45	0.20	TBA341	0.97		
AF170	0.25	BD145	0.30	OC46	0.35	TBA520Q	1.45		
AF172	0.20	BD222/T1P31A	0.39	OC70	0.22	TBA530Q	1.20		
AF178	0.49	BD225/T1P31A	0.39	OC71	0.28	TBA540Q	1.45		
AF180	0.60	BD234	0.34	OC72	0.35	TBA550Q	1.60		
AF181	0.30	BD222	0.50	OC74	0.35	TBA560CQ	1.80		
AF186	0.29	BDX22	0.73	OC75	0.35	TBA570Q	1.00		
AF239	0.43	BDX32	1.98	OC76	0.35	TBA800	1.00		
AU113	1.29	BDY18	0.75	OC77	0.50	TBA810	1.50		
BA130	0.08	BDY60	0.80	OC78	0.13	TBA920Q	1.80		
BA145	0.14	BF115	0.24	OC81	0.20	TBA990Q	1.60		
BA148	0.17	BF121	0.21	OC82	0.20	TCA270SQ	1.45		
BA155	0.10	BF154	0.19	OC80	0.13	TCA270SA	1.45		
BAX13	0.05	BF158	0.19	OC83	0.22	TCA1327B	1.00		
BAX16	0.08	BF159	0.24	OC84	0.28	E.H.T. TRAYS COLOUR			
BC107	0.12	BF160	0.23	OC85	0.13	Pye 691 693	4.50		
BC108	0.12	BF163	0.23	OC123	0.20	Decca (large screen)			
BC109	0.12	BF164	0.17	OC169	0.20	CS2030/2232/2630/			
BC113	0.12	BF167	0.23	OC170	0.22	2632/2230/2233/			
BC114	0.14	BF173	0.21	OC171	0.27	2631	5.67		
BC115	0.12	BF177	0.26	OA91	0.05	Philips G8 520/40/50			
BC116	0.12	BF178	0.24	BRC4443	0.65		5.66		
BC117	0.13	BF179	0.28	R2008B	1.50	Philips G9	5.79		
BC119	0.24	BF180	0.30	R2010B	1.50	GEC C2110	5.50		
BC125	0.15	BF181	0.34	R2305	0.38	GEC Hybrid CTV	5.40		
BC126	0.09	BF182	0.30	R2305/BD222	0.37	Thorn 3000/3500	5.50		
BC136	0.14	BF183	0.29	SCR957	0.81	Thorn 800	2.42		
BC137	0.14	BF184	0.23	TIP31A	0.38	Thorn 8500	5.23		
BC138	0.24	BF185	0.29	TIP32A	0.36	Thorn 9000	6.10		
BC139	0.21	BF186	0.30	TIP3055	0.53	GEC TVM 25	2.50		
BC140	0.31	BF194	0.09	T1590	0.19	ITT/KB CVC 5/7/8/9			
BC141	0.22	BF195	0.09	T1591	0.19		5.50		
BC142	0.19	BF196	0.12	TV106	1.09	RRI (RBM) A823	5.89		
BC143	0.19	BF197	0.10	DIODES				Bang & Olufsen	
BC144	0.19	BF198	0.15	1N4001	0.04	4/5000 Grundig			
BC147	0.09	BF199	0.14	1N4002	0.04	5010/5011/5012/			
BC148	0.09	BF200	0.28	1N4003	0.06	6011/8012/7200/			
BC149	0.09	BF216	0.12	1N4004	0.07	2052/2210/2252R			
BC153	0.12	BF217	0.12	1N4005	0.07	Tandberg (radionette)			
BC154	0.12	BF218	0.12	1N4006	0.07	Autovox	6.60		
BC157	0.10	BF219	0.12	1N4007	0.08	Grundig 3000/3010			
BC158	0.11	BF220	0.12	1N4007	0.08	Saba 2705/3715			
BC159	0.11	BF222	0.12	1N4148	0.30	Telefunken 709/710/			
BC160	0.28	BF221	0.21	1N4751A	0.11	717/2000	6.80		
BC161	0.28	BF224	0.12	1N5401	0.10	Korting	6.80		
BC167	0.13	BF256	0.37						
BC168	0.10	BF258	0.27						
BC169C	0.12	BF259	0.27						

TTLa	7490.....38p	74184.....280p	4051.....110p	BC109C.....12p	BD140.....38p	OC70.....40p	2N2219.....28p	2N5194.....90p	LM380.....95p	TBA800.....85p	★★★★★★★★★★
7400.....13p	7491.....90p	74185.....120p	4054.....120p	BC147.....38p	BD234.....70p	OC71.....48p	2N2219A.....28p	2N5245.....40p	LM381AN.....145p	TBA810S.....105p	★★★★★★★★★★
7401.....14p	7491AN.....90p	74186.....90p	4055.....140p	BC148.....38p	BF180.....32p	RF180.....32p	2N2221.....28p	2N5296.....85p	LM732.....125p	TBA820.....75p	★★★★★★★★★★
7401AN.....18p	7492.....58p	74189.....120p	4056.....130p	BC149.....10p	BF181.....32p	R2010B.....200p	2N2221A.....24p	2N5457.....40p	LM733.....100p	TBA820.....29p	★★★★★★★★★★
7402.....16p	7493.....58p	74191.....120p	4060.....130p	BC157.....10p	BF182.....32p	TP29.....50p	2N2222.....20p	2N5458.....40p	LM747.....70p	TDB05B5.....30p	★★★★★★★★★★
7403.....16p	7494.....58p	74192.....90p	4066.....80p	BC158.....10p	BF183.....32p	TP29A.....45p	2N2222A.....20p	2N5459.....40p	LM748.....95p	UA741CP.....25p	★★★★★★★★★★
7404.....20p	7495.....75p	74193.....90p	4067.....40p	BC159.....11p	BF194.....10p	TP29B.....50p	2N2368.....20p	2N5460.....40p	LM3900.....85p	ZN414.....30p	★★★★★★★★★★
7405.....20p	7496.....90p	74194.....160p	4068.....25p	BC169C.....14p	BF195.....12p	TP29C.....50p	2N2369.....18p	2N5485.....44p	LM3911.....125p	ZN424E.....130p	★★★★★★★★★★
7406.....40p	7497.....290p	74195.....110p	4069.....27p	BC172.....12p	BF196.....12p	TP30.....40p	2N2369A.....18p	2N6027.....48p	LM3911.....125p	326-5DR.....25p	★★★★★★★★★★
7407.....40p	74100.....140p	74196.....100p	4070.....65p	BC177.....17p	BF197.....14p	TP30A.....48p	2N2369A.....18p	2N6027.....48p	LM3911.....125p	326AJ.....25p	★★★★★★★★★★
7408.....22p	74104.....75p	74197.....130p	4071.....26p	BC178.....17p	BF198.....18p	TP30B.....48p	2N2369A.....18p	2N6027.....48p	LM3911.....125p		★★★★★★★★★★
7409.....22p	74105.....75p	74198.....250p	4072.....30p	BC179.....18p	BF199.....20p	TP30C.....60p	2N2369A.....18p	2N6027.....48p	LM3911.....125p		★★★★★★★★★★
7410.....18p	74107.....35p	74199.....250p	4073.....30p	BC182.....10p	BF200.....32p	TP30D.....60p	2N2369A.....18p	2N6027.....48p	LM3911.....125p		★★★★★★★★★★
7411.....26p	74109.....80p	74221.....175p	4078.....170p	BC183.....10p	BF224.....20p	TP31A.....58p	2N2905.....25p	2N2905.....25p	LM3911.....125p		★★★★★★★★★★
7412.....26p	74110.....80p	74200.....85p	4081.....20p	BC184.....11p	BF240.....18p	TP31C.....80p	2N2906.....25p	2N2906.....25p	LM3911.....125p		★★★★★★★★★★
7412AN.....28p	74111.....75p	74205.....48p	4082.....25p	BC187.....30p	BF241.....18p	TP32.....80p	2N2906A.....24p	2N2906A.....24p	LM3911.....125p		★★★★★★★★★★
7413.....40p	74118.....220p	74206.....48p	4093.....94p	BC212.....11p	BF248.....38p	TP32A.....80p	2N2907.....25p	2N2907.....25p	LM3911.....125p		★★★★★★★★★★
7416.....40p	74118.....110p	74207.....48p	4096.....120p	BC212L.....11p	BF257.....38p	TP32B.....80p	2N2907A.....30p	2N2907A.....30p	LM3911.....125p		★★★★★★★★★★
7417.....40p	74119.....225p	74208.....42p	4099.....145p	BC213.....11p	BF258.....32p	TP32C.....82p	2N2908.....25p	2N2908.....25p	LM3911.....125p		★★★★★★★★★★
7420.....18p	74120.....130p	74510.....100p	4160.....105p	BC213L.....12p	BF259.....38p	TP33.....90p	2N2908A.....24p	2N2908A.....24p	LM3911.....125p		★★★★★★★★★★
7421.....43p	74121.....32p		4161.....105p	BC214.....13p	BF264.....38p	TP33A.....90p	2N2909.....25p	2N2909.....25p	LM3911.....125p		★★★★★★★★★★
7422.....28p	74122.....84p		4162.....105p	BC214L.....13p	BF337.....38p	TP33B.....90p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7423.....38p	74123.....75p		4163.....105p	BC237.....18p	BF339.....30p	TP33C.....110p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7425.....33p	74125.....75p	CM08	4174.....110p	BC237A.....18p	BF400.....30p	TP34.....90p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7426.....43p	74126.....82p	CM08	4175.....100p	BC238.....18p	BF411.....30p	TP34A.....110p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7427.....40p	74128.....82p	CM01	4194.....105p	BC238A.....18p	BF452.....20p	TP34B.....110p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7428.....40p	74130.....110p	CM06	4406.....710p	BC238B.....18p	BF479.....30p	TP34C.....115p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7430.....18p	74132.....82p	CM07	4409.....710p	BC238B.....18p	BF480.....30p	TP35A.....220p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7432.....38p	74135.....80p	CM08	4410.....710p	BC238C.....20p	BF481.....30p	TP35C.....280p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7433.....44p	74136.....80p	CM09	4419.....50p	BC238C.....20p	BF482.....30p	TP36.....280p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7437.....38p	74137.....80p	CM10	4422.....85p	BC238C.....20p	BF483.....30p	TP36A.....280p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7438.....38p	74141.....85p	CM11	4433.....220p	BC238C.....20p	BF484.....30p	TP36B.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7440.....18p	74142.....300p	CM12	4435.....80p	BC238C.....20p	BF485.....30p	TP36C.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7441.....90p	74145.....95p	CM13	4450.....290p	BC238C.....20p	BF486.....30p	TP36D.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7441AN.....120p	74147.....210p	CM14	4451.....290p	BC238C.....20p	BF487.....30p	TP36E.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7442.....75p	74150.....130p	CM15	4501.....95p	BC238C.....20p	BF488.....30p	TP36F.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7443.....120p	74151.....81p	CM16	4502.....120p	BC238C.....20p	BF489.....30p	TP36G.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7444.....120p	74153.....85p	CM17	4503.....85p	BC238C.....20p	BF490.....30p	TP36H.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7445.....97p	74154.....140p	CM18	4507.....55p	BC238C.....20p	BF491.....30p	TP36I.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7446.....110p	74155.....97p	CM19	4508.....295p	BC238C.....20p	BF492.....30p	TP36J.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7447.....75p	74158.....96p	CM20	4510.....95p	BC238C.....20p	BF493.....30p	TP36K.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7448.....85p	74157.....98p	CM21	4511.....95p	BC238C.....20p	BF494.....30p	TP36L.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7450.....18p	74159.....280p	CM22	4512.....100p	BC238C.....20p	BF495.....30p	TP36M.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7451.....18p	74160.....110p	CM23	4513.....100p	BC238C.....20p	BF496.....30p	TP36N.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7453.....18p	74161.....110p	CM24	4514.....100p	BC238C.....20p	BF497.....30p	TP36O.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7454.....18p	74162.....100p	CM25	4515.....100p	BC238C.....20p	BF498.....30p	TP36P.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7460.....18p	74163.....100p	CM26	4516.....100p	BC238C.....20p	BF499.....30p	TP36Q.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7470.....38p	74164.....120p	CM27	4517.....100p	BC238C.....20p	BF500.....30p	TP36R.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7472.....32p	74165.....150p	CM28	4518.....100p	BC238C.....20p	BF501.....30p	TP36S.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7473.....38p	74166.....160p	CM29	4519.....100p	BC238C.....20p	BF502.....30p	TP36T.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7474.....38p	74167.....320p	CM30	4520.....100p	BC238C.....20p	BF503.....30p	TP36U.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7475.....43p	74170.....260p	CM31	4521.....100p	BC238C.....20p	BF504.....30p	TP36V.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7476.....38p	74172.....80p	CM32	4522.....100p	BC238C.....20p	BF505.....30p	TP36W.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7480.....54p	74173.....190p	CM33	4523.....100p	BC238C.....20p	BF506.....30p	TP36X.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7481.....110p	74174.....110p	CM34	4524.....100p	BC238C.....20p	BF507.....30p	TP36Y.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7482.....90p	74175.....95p	CM35	4525.....100p	BC238C.....20p	BF508.....30p	TP36Z.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7483.....100p	74176.....90p	CM36	4526.....100p	BC238C.....20p	BF509.....30p	TP36AA.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7484.....110p	74177.....120p	CM37	4527.....100p	BC238C.....20p	BF510.....30p	TP36AB.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7485.....120p	74180.....110p	CM38	4528.....100p	BC238C.....20p	BF511.....30p	TP36AC.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7486.....35p	74181.....320p	CM39	4529.....100p	BC238C.....20p	BF512.....30p	TP36AD.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★
7489.....340p	74182.....180p	CM40	4530.....85p	BC238C.....20p	BF513.....30p	TP36AE.....330p	2N2909A.....24p	2N2909A.....24p	LM3911.....125p		★★★★★★★★★★

STRUTT Electrical & Mechanical Engineering Ltd., 3c BARLEY MARKET ST., TAVISTOCK, DEVON
TELEPHONE: TAVISTOCK 5439. TELEX: 45263. P & P 25p. VAT 8% unless *12%. Send 12p. large SAE for Price List.

ARE YOU

USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling **used colour televisions from home** in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial **CASH INCOME** with a starting capital of less than £20. Our new unique publication "How to Deal Successfully in Used Colour Televisions" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have "pooled" their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can **succeed immediately**.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure **certain success**. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail - for both televisions **and** new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. **Plus FREE on-going advice and FREE regular updating service.**

You can start tomorrow - but you'll need our guide. The latest big illustrated edition is out now, and costs just **£4.95** - a small price to pay for financial independence!

SAME DAY SERVICE
 CITY PUBLISHING, HAYWORTH ROAD, SANDIACRE, NOTTINGHAM NG10 5LL

To: City Publishing, Hayworth Road, Sandiacre, Nottingham NG10 5LL.
 Please send by return post "How to Deal Successfully in Used Colour Televisions".
 I enclose cheque/p.o. for £4.95.

NAME.....
 ADDRESS.....

**BIG NEW EDITION
 OUT NOW!**

QUALITY USED TV's AT GIVE AWAY PRICES

S.S. MONO FROM £12
 D.S. COLOUR FROM £25
 S.S. COLOUR FROM £40
 PRICES PLUS V.A.T.

ALL WORKERS, FRESH STOCKS WEEKLY,
 QUANTITY DISCOUNTS, DELIVERY ARRANGED.
TRY US YOU WILL NOT BE DISAPPOINTED.

TELETRADERS
 329 TORQUAY RD,
 PAIGNTON, DEVON.
 Telephone (0803) 551364.

N.G.T. COLOUR TUBES

First Independent Rebuilder with B.S.I. CERTIFICATION
 (Certificate No. 004)

Tubes are processed using high temperature pumping schedules giving high definition and long life. They are then fitted with an implosion safety system approved by the British Standards Institution.

N.G.T. ELECTRONICS LTD.,
 120, SELHURST ROAD., LONDON S.E.25
 Phone: 01-771 3535.
 20 years experience in television tube rebuilding.

ARE YOU IN THE DARK?
...ABOUT OUR



COLOUR T.V. PANEL EXCHANGE REPAIR SERVICE

FULL RANGE OF
THORN · RBM · PHILIPS
PYE · INVICTA · GEC
DECCA · TELPRO
AND MANY OTHER MAKES

90 DAY GUARANTEE ON ALL REPAIRS
SAME DAY POSTAL SERVICE

We employ a large skilled Staff, who utilise some of the most sophisticated Test equipment available, inclusive of AUTOMATIC FAULT FINDING COMPUTERS together with specially designed SERVICING JIGS which in short means to you:-

HIGH QUALITY REPAIRS - AT LOW COST



ONE OFF
OR



100 OFF · NO ORDER TOO
LARGE OR SMALL

SEND FOR PRICE LIST

SEND FOR CATALOGUE
BLOCK DISCOUNTS FOR TRADE CONTRACTS

TO

Campbell Electronics Ltd.

Factory Unit E5, Halesfield 23, Telford · Shropshire · TF7 4QX
Telephone: Telford (0952) 584373. Ext. 2. Telex 35191 Chamcon

BENTLEY ACOUSTIC CORPORATION LTD.

The Old Police Station, Gloucester Road, LITTLEHAMPTON, Sussex.

PHONE 6743

ALL PRICES INCLUSIVE OF V.A.T. AT 12½%. NOTHING EXTRA TO PAY

OA2	£1.20	6DT6A	0.85	30C17	0.90	ECC86	2.00	EZ41	1.00	PL519	3.75
OB2	0.40	6E5	1.00	30F5	0.70	ECC88	0.72	EZ80	0.42	PY33/2	0.50
IB3GT	0.55	6EW6	0.85	30FL2	2.25	ECC189/1.00	EZ81	0.45	PY81	0.60	
5CG8	0.75	6F1	0.80	30L15	0.75	ECC8072.80	GY501	1.40	PY82	0.40	
5R4GY	1.00	6F6G	0.70	30L17	0.70	ECC80	0.65	GZ32	1.00	PY88	1.12
5U4G	1.00	6F18	0.60	30P12	0.74	ECC82	0.50	GZ33	4.00	PY500A.2.05	
5V4G	1.00	6F23	1.00	30P19	0.90	ECC86	0.80	GZ34	2.25	PY800	0.60
5Y3GT	0.65	6F28	0.85	30PL1	2.20	ECH35	2.00	HN309	1.70	PY801	0.60
5Z3	1.40	6GH8A	0.80	30PL13	1.30	ECH42	1.00	KT66	3.50	PZ30	0.50
5Z4G	0.75	6GK5	0.75	30PL14	1.50	ECH81	0.55	KT88	6.75	QQV03/10	
6/30L2	0.90	6GK6	2.00	50CD6G		ECH84	0.75	P61	0.60		
6AC7	0.70	6GU7	0.90		4.00	ECL80	0.55	PC86	0.80	QV06/20	
6AG7	0.70	6H6GT	0.50	85A2	1.40	ECL82	0.60	PC88	0.80		4.70
6AH6	0.70	6J5GT	0.65	807	1.10	ECL83	1.50	PC92	0.65	R10	5.00
6AK5	0.45	6J6	0.35	5763	3.65	ECL86	0.64	PC97	0.75	R19	0.75
6AM8A	0.70	6JUBA	0.90	AZ31	1.00	EF22	1.00	PC900	0.65	UABC80	
6AN8	0.78	6K7G	0.50	AZ41	0.50	EF40	2.00	PCC84	0.39		0.45
6AQ5	0.75	6K8G	0.50	DY51	2.00	EF41	1.00	PCC85	0.47	UAF42	0.70
6AR5	1.05	6L7(M)	1.50	DY86/7	0.52	EF80	0.40	PCC89	0.49	UBC41	0.70
6AT6	0.60	6Q7G	0.75	DY802	0.50	EF83	1.70	PCC1890.60		UBC81	0.55
6AU6	0.62	6SA7	0.70	E80CF	6.00	EF85	0.45	PCF80	0.80	UBF80	0.50
6AV6	0.65	6SG7	0.70	E88CC	1.20	EF86	0.52	PCF82	0.45	UBF89	0.39
6AW8A	1.15	6SJ7	0.70	E80F	5.50	EF89	0.55	PCF86	0.57	UC92	0.50
6AX4	0.75	6U4GT	1.00	E188CC5.00		EF91	0.70	PCF200	1.55	UC85	0.50
6BA6	0.65	6V6G	0.50	E280F	12.50	EF92	0.70	PCF201	1.45	UCF80	0.80
6BC8	0.90	6X4	0.95	EAS0	0.40	EF183	0.50	PCF801	0.49	UCH42	1.00
6BE6	0.70	6X5GT	0.50	EABC80		EF184	0.50	PCF802	0.80	UCH81	0.60
6BH6	1.10	9D7	0.70		0.48	EH90	0.75	PCF805	2.25	UCL82	0.75
6BJ6	0.75	10C2	0.70	EAF42	1.00	EL34	2.50	PCF806	0.70	UCL83	1.00
6BK7A	0.85	10DE7	0.80	EAF801	1.50	EL41	1.00	PCH2001.20		UF41	1.00
6BN8	1.50	10F1	1.00	EB91	0.25	EL81	1.00	PCL82	0.62	UF42	1.00
6BQ7A	1.40	10F18	0.65	EBC41	1.00	EL84	0.48	PCL83	1.20	UF80	0.40
6BR7	1.00	10P13	0.80	EBC81	1.00	EL95	0.95	PCL84	0.65	UF85	0.50
6BR8	1.25	10P14	2.50	EBF80	1.00	EL360	2.50	PCL86	0.85	UF89	0.52
6BW6	3.75	12AT6	0.45	EBF89	0.40	EL506	2.00	PCL805.085		UL41	0.90
6BW7	0.65	12AU6	0.50	EC86	0.84	BL509	2.50	PFL200	1.35	UL84	0.90
6BZ6	1.50	12AV6	0.60	EC88	0.84	EM80	1.00	PL33	1.00	UM80	1.00
6C4	0.50	12BA6	0.50	EC92	1.00	EM81	1.00	PL36	0.80	UY41	0.70
6C9	2.00	12BE6	0.85	EC97	0.75	EM84	1.00	PL81	0.49	UY85	0.70
6CB6A	0.65	12BH7	0.68	ECC33	2.00	EM87	1.45	PL81A		U19	4.00
6CD6G	4.00	13D8	2.00	ECC35	2.00	EY51	0.80	PL82	0.50	U25	1.00
6CG8A	0.90	19AQ5	0.65	ECC40	1.00	EY81	1.50	PL83	0.50	U26	0.90
6CL6	0.75	19G6	6.50	ECC81	0.52	EY83	1.50	PL84	0.50	U191	0.50
6CL8A	0.95	19H1	4.00	ECC82	0.62	EY87/6	0.45	PL95	1.00	U301	1.00
6CM7	1.00	20P1	1.00	ECC83	0.62	EY88	1.00	PL504	1.05	U404	0.75
6CU5	0.90	20P4	0.84	ECC84	0.50	EY500	1.45	PL508	1.85	U801	1.00
6D87	0.90	30C15	1.00	ECC85	0.50	EZ40	1.00	PL509	3.10	X41	1.00

All goods are unused and boxed, and subject to the standard guarantee. Terms of business: Cash or cheque with order only. Despatch charges: Orders below £25, add 50p extra per order. Orders over £25 post free. Same day despatch. Terms of business available on request. Any parcel insured against damage in transit for only 5p extra per parcel. Many other types in stock. Please enclose S.A.E. with any enquiries. Special offer of EF50 VALVES, SOILED, BUT NEW AND TESTED £1 EACH.

Technical Training in Radio, Television and Electronics

Start training TODAY and make sure you are qualified to take advantage of the many opportunities open to trained people. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college has helped thousands of people to move up into higher paid jobs - and they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

City and Guilds Certificates:-

Telecommunications Technicians,
Radio, TV and Electronics Technicians,
Electrical Installation Work,
Technical Communications,
Radio Amateur,
MPT General Radio Communications
Certificate.

Diploma Courses:-

Electronic Engineering,
Electrical Engineering,
Computer Engineering,
Radio, TV, Audio Engineering, Servicing and
Maintenance. (inc. Colour TV)
New Self-Build Radio Courses with Free Kits.

Colour TV Servicing

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study courses which are approved by a leading manufacturer.

The ICS Guarantee

If you are studying for an examination, ICS will guarantee coaching until you are successful - at no extra cost.

POST OR PHONE TODAY FOR FREE BOOKLET.

I am interested in.....

Name

Address.....

..... Phone No:.....

ICS International Correspondence Schools,
Dept. A285, Intertext House,
LONDON SW8 4UJ. Tel 622 9911 (all hours)

TRANSISTORS, ETC.


Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
AC107	0.48	AU103	2.40	BC204*	0.56	BC377	0.29	BD234	0.29	BF222	0.61	BPX29	1.62	MPSU05	0.66	ZTX500	10.18	N3819	10.47
AC117	0.38	AU107	2.75	BC204*	0.39	BC394	0.39	BD235	0.63	BF224 & J	0.22	BR101	0.53	MPSU06	0.76	ZTX502	10.22	N3820	0.72
AC126	0.36	AU110	2.40	BC205*	0.39	BC440	0.52	BD236	0.63	BF240	0.32	BR103	0.64	MPSU55	1.26	ZTX504	10.28	N3866	1.08
AC127	0.54	AU113	2.60	BC206*	0.37	BC441	0.59	BD237	0.68	BF241	0.31	BR303	1.06	MPSU56	1.32	ZN404	1.30	N3904	1.06
AC128	0.46	BC107*	0.16	BC207*	0.39	BC461	0.78	BD238	0.68	BF244*	0.61	BRC4443	1.76	MPSU60	0.82	ZN696	0.46	N3905	10.20
AC128K	0.55	BC108*	0.15	BC208*	0.37	BC477	0.30	BD253	1.58	BF245*	0.53	BRY39	0.60	MPU131	10.89	ZN697	0.46	N3906	10.20
AC141	0.65	BC109*	0.16	BC209*	0.39	BC478	0.25	BD410	1.65	BF254	0.48	BR566	10.44	OC26	1.90	ZN706A	0.33	N4036	0.94
AC141K	0.70	BC113	10.22	BC211*	0.36	BC479	0.33	BD433	0.65	BF255	0.58	BSS27	0.92	OC28	1.49	ZN708	0.29	N4123	10.17
AC142	0.60	BC114	10.22	BC212*	0.36	BC545*	10.13	BD435	0.70	BF256*	0.49	BT106	1.50	OC29	1.20	ZN914	0.32	N4124	10.17
AC142K	0.65	BC117	10.24	BC212L*	0.37	BC546*	10.13	BD436	0.71	BF257*	0.44	BT109	1.99	OC35	1.85	ZN916	0.46	N4126	10.17
AC151	0.31	BC116*	10.25	BC213*	0.36	BC549*	10.15	BD437	0.74	BF258	0.52	BT116	1.46	OC36	1.25	ZN918	0.54	N4236	2.20
AC152	0.36	BC117	10.30	BC213L*	0.36	BC550	10.24	BD438	0.75	BF259	0.54	BT119	5.18	OC42	0.90	ZN930	0.29	N4289	10.32
AC153	0.42	BC118	10.24	BC214*	0.37	BC556	10.23	BD439	0.68	BF262	0.73	BU102	2.85	OC44	0.88	ZN1164	8.29	N4292	10.32
AC153K	0.52	BC119	10.34	BC214L*	0.38	BC557*	10.16	BD520	0.88	BF263	0.88	BU105	11.80	OC45	0.63	ZN1304	1.40	N4416	0.85
AC154	0.41	BC125*	10.30	BC225	0.42	BC558*	10.16	BD529	0.87	BF270	0.47	BU105/02	11.95	OC70	0.85	ZN1305	1.29	N4444	1.90
AC176	0.45	BC126	10.30	BC237*	0.16	BC559*	10.17	BD600	1.23	BF271	0.42	BU108	12.98	OC71	0.73	ZN1306	1.49	N4921	0.80
AC178	0.51	BC132	10.20	BC238*	0.15	BCY10	0.30	BD663BR	0.86	BF272A	0.80	BU126	12.91	OC72	0.73	ZN1307	1.32	N5042	1.65
AC179	0.55	BC134	10.22	BC239*	0.22	BCY30A	1.06	BDX18	1.55	BF273	0.33	BU204	12.50	OC81	0.83	ZN1308	1.53	N5060	10.28
AC187	0.58	BC135	10.21	BC251*	0.28	BCY32A	1.19	BDX32	2.95	BF274	0.34	BU205	12.78	OC82	0.96	ZN1711	0.47	N5061	10.30
AC187K	0.65	BC136	10.22	BC252*	0.26	BCY32A	1.02	BDY18A	0.83	BF336	0.63	BU206	13.09	OC139	1.30	ZN1893	0.52	N5064	0.83
AC188	0.61	BC138	10.30	BC253*	0.38	BCY32A	1.02	BDY18A	1.55	BF337	0.63	BU208	14.88	OC140	1.38	ZN2102	0.71	N5086	10.49
AC188K	0.61	BC138	10.35	BC261A*	0.28	BD0115	1.35	BDY20	0.85	BF338	0.68	BU207	11.38	OC170	0.80	ZN2107	0.55	N5087	10.50
AC193K	0.70	BC140	0.36	BC262A*	0.28	BD0123	1.50	BDY38	1.38	BF355	0.72	BU277	2.50	OC171	0.82	ZN2118	0.42	N5092	10.59
AC194K	0.74	BC141	0.44	BC263*	0.26	BD124	1.85	BF115	0.48	BF362	1.04	C106D	0.60	OC200	3.90	ZN2219	0.55	N5294	0.66
ACY17	1.20	BC142	0.36	BC267*	0.20	BD130Y	1.56	BF117	0.45	BF363	1.04	C106F	0.43	OC201	3.95	ZN2221A	0.26	N5296	0.68
ACY19	0.95	BC143	0.38	BC268*	0.28	BD131	0.58	BF120	0.55	BF367	1.02	C111E	10.46	OC202	2.40	ZN2222A	0.41	N5298	0.71
ACY28	0.98	BC147*	10.12	BC286	0.40	BD132	0.68	BF121	0.85	BF451	0.43	DA0N1	0.64	OC205	3.95	ZN2369A	0.40	N5322	1.16
ACY39	2.02	BC148*	10.12	BC287	0.49	BD133	0.70	BF123	0.48	BF457	0.46	E1222	0.47	OCP71	1.98	ZN2401	0.80	N5449	1.18
AD140	1.70	BC149*	10.13	BC291	0.27	BD135	10.37	BF125	0.68	BF458	0.49	E5024	10.19	ZN236A	0.94	ZN2484	0.35	N5457	10.46
AD142	1.90	BC152	10.42	BC294	10.37	BD136	10.38	BF127	0.51	BF459	0.52	GET872	0.46	R200B8	12.92	ZN2570	0.74	N5458	10.40
AD143	1.78	BC153	10.38	BC297	0.36	BD137	0.40	BF137F	0.78	BF594	10.16	MC140	10.36	R20108	12.79	ZN2646	0.82	N5459	10.58
AD149	1.92	BC154	10.41	BC300	0.62	BD138	0.42	BF152	10.19	BF596	10.17	ME0402	10.18	R2322	10.76	ZN2784	1.15	N5494	0.95
AD161	0.66	BC157*	10.13	BC301	0.38	BD139	0.46	BF155	10.25	BF597	10.27	MF0404/02	10.18	R2323	10.85	ZN2859	2.08	N5496	1.35
AD161/162	1.22	BC158*	10.12	BC302	0.86	BD140	0.50	BF159	0.53	BF599	10.30	ME6001	10.18	ST2110	0.48	ZN2904	0.45	N5602	1.75
AD162	0.71	BC159*	10.14	BC303	0.64	BD144	2.24	BF160	10.20	BF640	10.29	ME6002	10.18	ST1120	0.48	ZN2904*	0.40	N6107	0.71
AF114	0.35	BC160	0.52	BC304	0.44	BD145	0.75	BF161	0.84	BF641	10.30	MJ2955	1.30	TIC44	10.25	ZN2905*	0.39	N6122	0.60
AF115	0.35	BC161	0.58	BC307*	10.17	BD150A*	10.51	BF163	10.65	BF645	10.29	MJ3000	1.58	TIC46	10.35	ZN2906*	0.36	N6178	1.07
AF116	0.41	BC167B	10.15	BC308*	10.14	BD155	10.90	BF164	10.95	BF652	10.33	MJ340	0.68	TIC47	10.45	ZN2926G	10.15	N6180	1.39
AF117	0.42	BC168B	10.14	BC309*	10.18	BD157	0.51	BF166	0.56	BF651	10.29	MJ341	0.72	TIP29A	0.47	ZN2960	10.14	N6211	2.74
AF118	0.98	BC169C	10.15	BC317*	10.15	BD158	0.75	BF167	0.38	BF662	10.28	MJ370	0.74	TIP30A	0.50	ZN2957	10.14	ZN5337BP	4.28
AF121	0.88	BC170*	10.16	BC318*	10.16	BD159	0.68	BF173	0.35	BF679	10.30	MJ371	0.79	TIP31A	0.51	ZN2965	1.12	ZN5458C	0.78
AF124	0.38	BC171*	10.15	BC319*	10.19	BD160	2.69	BF177	0.46	BF680	10.29	MJ520	0.85	TIP31C	0.87	ZN3053	0.48	ZN5643A	2.25
AF125	0.38	BC172*	10.14	BC320	10.17	BD163	0.67	BF178	0.36	BF681	10.30	MJ521	0.95	TIP32A	0.56	ZN3054	0.86	ZN5930D	1.90
AF126	0.36	BC173*	10.22	BC321A & B	10.18	BD165	0.68	BF179	0.58	BF688	10.42	MJ2955	1.20	TIP32C	0.72	ZN3055	0.72	ZN5931	1.48
AF127	0.86	BC174A & B	10.22	BC322	10.28	BD166	0.88	BF180	0.53	BF741	0.55	MJ3000	1.95	TIP33A	0.77	ZN3250	0.52	ZN5117Z	3.58
AF139	0.58	BC176	0.22	BC323	1.15	BD175	0.90	BF181	0.53	BF743	0.55	MJ3005	1.22	TIP34A	0.84	ZN3254	0.58	ZN5234	1.48
AF147	0.52	BC177*	0.20	BC328	10.18	BD177	0.58	BF182	0.44	BFW11	1.02	MPF102	10.40	TIP41A	0.72	ZN3391A	0.38	3N128	1.60
AF149	0.45	BC178*	0.20	BC328	10.18	BD178	0.92	BF183	0.52	BFW30	2.58	MPS3702	10.33	TIP42A	0.80	ZN3633	12.70	40250	0.58
AF178	1.35	BC179*	0.22	BC337	10.17	BD181	1.94	BF184	0.44	BFW59	10.19	MPS3705	10.30	TIP2955	0.77	ZN3703	10.17	40251	1.14
AF179	1.36	BC179*	0.28	BC338	10.17	BD182	2.10	BF185	0.42	BFW60	10.20	MPS6521	10.36	TIP3055	0.58	ZN3704	10.19	40327	0.67
AF180	1.35	BC182*	10.15	BC340	0.19	BD183	1.34	BF186	0.42	BFW90	10.65	MPS6523	10.36	TIS43	10.44	ZN3705	10.17	40361	0.48
AF181	1.33	BC182L*	10.15	BC347*	10.17	BD184	2.30	BF194*	10.14	BFX29	0.38	MPS6566	10.44	TIS73	11.36	ZN3706	10.16	40362	0.80
AF186	1.48	BC183*	10.14	BC348A & B	10.17	BD187	1.20	BF195*	10.13	BFX84	0.42	MPSA05	10.30	TIS90	10.23	ZN3707	10.18	40410	0.94
AF202	0.27	BC183L*	10.14	BC349B	10.17	BD188	1.25	BF196*	10.14	BFY50	0.38	MPSA06	10.32	TIS91	10.28	ZN3708	10.17	40429	0.88
AF209	1.82	BC184*	10.15	BC350*	10.17	BD189	0.71	BF197	10.15	BFY51	0.37	MPSA55	10.43	ZTX108	10.14	ZN3715	1.70	40530	0.79
AF240	1.40	BC184L*	10.15	BC350*	10.17	BD222	0.91	BF198	10.15	BFY52	0.36	MPSA55	10.43	ZTX109	10.16	ZN3717	2.39	40595	1.38
AF279S	0.91	BC185	0.36	BC351*	10.22	BD225	0.91	BF199	10.29	BFY53	0.36	MPSA93	10.56	ZTX113	10.23	ZN3722	2.58	40603	1.13
AL100	1.30	BC186	0.25	BC352A*	10.24	BD232	0.91	BF200	10.26	BFY90	1.98	MPSL01	10.33	ZTX300	10.16	ZN3773	3.90	40636	1.25
AL103	1.58	BC187	0.27	BC360	0.59	BD233	0.62	BF218	10.42	BPX25	1.62	MPSU01	0.61	ZTX304	10.26	ZN3794	10.40	40654	0.83

Alternative gain versions available on items marked*.

For matched pairs add 20p per pair.

LINEAR IC's

Type	Price (£)	Type	Price (£)
BRC1330	10.93	SN76008KE	1.56
CAB100M	2.44	SN76013N	1.56
CA3005	1.92	SN76013ND	1.40
CA3012	1.45	SN76018K	1.56
CA3014	2.23	SN76023N	1.56
CA3018	0.71	SN76033N	2.22
CA3020	1.89	SN76110N	1.20
CA3028A	0.80	SN76115N	1.62
CA3028B	1.09	SN76116N	1.78
CA3045	3.75	SN76131N	12.10
CA3046	0.70	SN76226N	12.80
CA3065	1.74	SN76271N	11.61
CA3069	1.98	SN76282N	11.80
CA3130S	1.57	SN76502N	11.92
FCH161	12.40	SN76530P	9.97

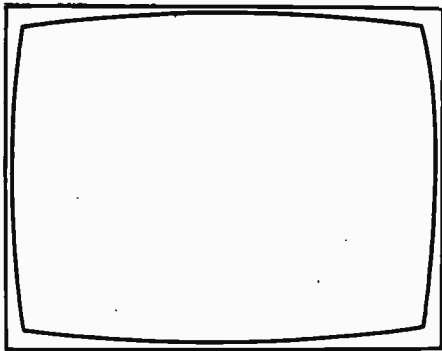

TELEVISION

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTS MANAGER

Roy Smith 01-261 6671

CLASSIFIED ADVERTS

Colin R. Brown 01-261 5762

COVER PHOTO

Test Card F shows ghosting up very well! Note that the card is the joint copyright of the BBC, BREMA, EEA and the IBA.

SUBSCRIPTION SERVICE

You can now take out an annual subscription to TELEVISION, so that copies are sent direct to your home each month. The cost is £9.50 for UK residents, and for overseas residents £10.50 or \$21 to the USA or Canada. Orders with payment should be sent to:

IPC Services,
Oakfield House,
Perrymount Road,
Haywards Heath,
Sussex.

Make money orders, cheques etc. payable to IPC Services.

Know-How

The future structure of the UK's TV industry is becoming clearer. Decca and Thorn have reduced their production capacity, with Thorn now undertaking fresh investment at its two remaining plants. The multinationals IIT and Philips seem to have survived the traumas of recent years reasonably well: Philips has absorbed Pye, and IIT is setting up new plant at Basildon to produce its new small-screen colour chassis. The most intriguing factor however is that the Japanese have ended up with a significant chunk of the industry. Sony and National Panasonic both have plants in South Wales, while Toshiba is forming a joint company with Rank to handle the audio/TV side of Rank's operations. Talks between Hitachi and GEC are continuing.

It's the Rank-Toshiba link that hit the headlines however, with questions in parliament and a brief hullabaloo. The general tenor of press comment seemed to be concerned with the UK acquiring Japanese know-how — as if no one in the UK knew how a transistor worked, or how to make a c.r.t.! In practice of course basic electronics know-how is nowadays pretty widely spread. Get together a handful of engineers almost anywhere and provide them with the necessary components and they'd have a TV set working without too much difficulty. But would it be reliable, and a sound commercial proposition? This in fact is where the required know-how lies.

In a modern mass TV assembly plant production engineering know-how is probably more important than electronics know-how. In other words, the vital ingredient today is the ability to test and assemble sets rather than to knock up circuits that work. But production know-how is expensive, and can be generated only through intensive, large-scale operations. A great deal of money is required, because whereas electronic components are comparatively cheap, the computer to check them with isn't. Nor is automatic insertion equipment, the equipment that produces reliable soldered joints, and the equipment to check panels and sets. What it boils down to is that the lack of profitability of the UK's TV industry in recent years means that instead of generating our own production know-how we're now having to buy it in. A frustrating situation for a long established industry to find itself in.

It's likely however that this sort of thing is pretty general in UK industry. In the semiconductor field for example designing the circuits is no problem: the chemistry, testing, getting the encapsulation right and so on is. Dare one mention the car industry?

It's interesting to note that the multinationals Philips and IIT have fared comparatively well in recent times, presumably because they've had international know-how to call upon. Figures of investment per employee are often quoted when making international comparisons of economic performance, the UK coming out rather badly. The figures may seem rather pointless by themselves, but take on greater significance when considered in the light of the technology required for today's mass production. The obvious reason why the necessary investment hasn't been made in the UK is shortage of funds, but other factors are involved as well. For example, the role of the engineer in industrial management. Decisions on investment are made in company boardrooms: is the engineering voice adequately represented there? International comparisons suggest not. That's one factor that requires urgent review. Another factor is education, training and the ability to get the right mix of skills. If it's production and materials engineering skills that are required, is enough training being devoted to them? Is the training of technicians and engineers unduly specialised, so that shortages keep arising because no one's adaptable enough to be able to tackle different subjects?

Another problem is industrial organisation. We don't just mean the old blue/white collar business, though that should have been sorted out long ago. Problems do seem to arise in industries such as TV and car manufacture, where products are assembled from bought in components. Who specifies what, and who's responsible for the necessary research? To put it crudely, should the capacitor manufacturer or the setmaker find out why mains filter capacitors fail so frequently? Things can easily go wrong where an industry is not integrated, a point again brought out by the comparative success of the multinationals. This is a factor that's probably by now largely been resolved however — but at what a cost in terms of a reputation for unreliable products.

Just now industry looks set for a brighter future. There's still a lot for the UK to do in getting its industrial strategy right however.

Teletopics

RANK-TOSHIBA

After many months' negotiations, Rank Radio International and Toshiba (UK) have announced the setting up of a jointly owned subsidiary, Rank Toshiba Limited, which will take over and develop Rank's television and audio manufacturing plants in the west country. Rank has been making losses on its TV making operations for several years now, and the join up with Toshiba will give it much needed cash plus access to Toshiba's technology. The project is being backed with £1.95 millions of government funds. Rank say that their colour TV output this year will amount to some 175,000 sets, and the aim is to increase this to around 350,000 by 1981, of which 40 per cent will carry the Toshiba brand name while the remainder will be sold as Bush, Murphy or Rank-Arena sets. Two-thirds of the Toshiba sets will be earmarked for export.

For Toshiba, the venture means access to large-screen TV sets, manufacturing capability within the EEC, and an interest in Rank's expertise in the fields of teletext and viewdata - Rank have been active in this area from the start, and introduced the first teletext receiver for sale to the general public. Rank will start to manufacture small-screen colour sets, and by 1981 production will be centred on the Toshiba X53 chassis. It's not clear how Mullard will be affected, and doubtless the yen-pound exchange rate will be the deciding factor here. Rank started to use Toshiba's RIS colour tubes in early 1975, with the introduction of their Z718 chassis. More recently with the introduction of the T20 chassis they have been switching over to use of the Mullard 20AX tube, and currently 85 per cent of Rank's colour sets are being fitted with the Mullard 20AX tube.

A group of Japanese technicians is to work at Plymouth for the next couple of years on getting the new production lines into operation. This gives an indication of the type of technology that Toshiba will be contributing.

RCA'S S4 PIL TUBE

RCA have announced the introduction of a new version of their PIL tube, called the S4. It will be available in both 110° and, for the smaller sizes, 90° versions. The main changes are the use of a new deflection yoke, with higher sensitivity and consequently reduced receiver power consumption, and a new high-resolution gun which gives improved focus performance. Previously announced developments such as the contoured-line screen, super-arch mask, pigmented phosphors etc. are all incorporated in the new tube.

The new saddle-toroidal yoke - saddle-wound line deflection coils and toroidally-wound field scan coils - has a significantly improved efficiency and offers optimum impedance matching to present day high-performance circuitry. The peak energy requirement is 4.3mJ for the horizontal deflection and 3.9W for vertical deflection. The series-connected horizontal deflection coils have a resistance of 1.05Ω and require a peak-to-peak current of 5.4A at 25kV. The vertical scan coils may be series- or parallel-connected. In the former case the resistance is 10Ω and the p-p deflection current required is 1.25A at 25kV; in the latter case the figures are 2.5Ω and 2.5A respectively. This enables the tube to be used with each of the popular vertical deflection systems at present used in Europe.

The new gun incorporates a larger diameter lens to give a smaller spot size and thus improved focus. The focus electrode operates at 7kV compared to the 4.6kV of current PIL tubes. In the interests of reliability, a new base and socket have been designed to accommodate this increased focus voltage.

RCA point out that the tubes have been specifically designed to meet European TV receiver requirements. Note that our colour receiver project is based on the current generation of PIL tubes and cannot be adapted to use with the new version, which is not yet in full scale production.

PRESTEL'S EXPORT SUCCESSES

The Post Office seems to be enjoying considerable export success with its Prestel (viewdata) system. An agreement in principle has been reached with Insac Data Systems Ltd., the firm set up by the National Enterprise Board to market British computing systems and software overseas, to make a Prestel service available to users in the USA late next year. This follows the signing of a letter of intent by the Hong Kong Telephone Company to purchase Prestel technology. West Germany and the Netherlands have already bought Prestel equipment from the PO. The Hong Kong Telephone Company is negotiating separately with GEC Computers Ltd for the supply of a GEC Series 4000 computer on which the service will be based. The start of the public Prestel service in the UK is now planned for the first quarter of 1979.

NEW CATALOGUES

Best Electronics have just published their largest ever TV spares catalogue, covering semiconductor devices, capacitors, resistors, e.h.t. rectifiers, picture tubes, valves, fuses, instruments, soldering equipment, tools and chemicals. Each section is thumb indexed for easy reference, and is written specifically for service engineers. Setmakers' part numbers are included, together with a semiconductor index detailing over twelve hundred device alternatives, all manufacturers' recommended ones. Copies of the new seventy-two page catalogue are available free, from Best Electronics (Slough) Ltd, Unit 4, Farnburn Avenue, Slough, Berks SL1 4XU, or telephone Slough. (0753) 39322.

A new 36-page catalogue has been published covering the entire range of Tequipment oscilloscopes and accessories. Copies are available from Tektronix UK Ltd., Beaverton House, PO Box 69, Harpenden, Herts.

We have received from Anglia Components of Burdett Road, Wisbech, Cambridgeshire PE13 2PS a copy of the latest edition of their very comprehensive components catalogue which includes resistors, capacitors, semiconductor devices, e.h.t. triplers and many other TV components. Anglia Components supply trade customers only. Telephone 0945 63286.

RELAY STATION OPENINGS

The following relay stations are now in operation:
Bellair (Antrim) BBC-1 channel 48, Ulster Television

channel 52, BBC-2 channel 56. Receiving aerial group C/D.

Box (Wiltshire) BBC-1 channel 40, HTV West channel 43, BBC-2 channel 46. Receiving aerial group B.

Fort Augustus (Scotland) Grampian Television channel 23, BBC-2 channel 26, BBC-1 channel 33. Receiving aerial group A.

Kington (Herefordshire) BBC-1 channel 39, BBC-2 channel 45, ATV channel 49. Receiving aerial group B.

Lochwinnoch (Strathclyde) BBC-1 channel 57, Scottish Television channel 60, BBC-2 channel 63. Receiving aerial group C/D. Note that horizontal polarisation is used.

Primrose Hill (Huddersfield, Yorkshire) BBC-1 channel 57, Yorkshire Television channel 60, BBC-2 channel 63. Receiving aerial group C/D.

Except for Lochwinnoch, all the above transmissions are vertically polarised.

NEW CIRCUITRY FROM RANK

Rank have introduced a new colour TV chassis, type T22A, which is initially used in the Bush Models BC6268, BC6368 and BC6468. The chassis uses the 20AX c.r.t., and has the same timebase and switch-mode power supply circuitry as the T20A chassis. There's an interesting new signal panel however. To start with, a surface-wave filter (type SW102M) is used to form the i.f. bandpass response at the input to the i.f. strip, preceded by a wideband two-transistor amplifier. The rest of the i.f. strip consists of a Mullard TDA2540 i.c., with an SGS TDA2190 i.c. combining the intercarrier sound and audio functions. The decoder consists of a TDA2560/TDA2522 combination followed by a TDA2532 matrixing i.c. This is an up-dated version of the TBA530, and drives class AB RGB output stages. These are unusual, and a simplified circuit of the R output stage is shown in Fig. 1. The R output is applied to the base of VT9, which has a very high value load resistor (R136). Positive-going signal excursions drive VT9 to saturation, the output being conveyed to the c.r.t. cathode via D39. On negative-going signal excursions VT9 is driven to cut-off, its positive-going collector voltage driving VT12 on to provide a low-impedance, emitter-follower output. R142 is included to reduce the dissipation in VT12, and the gain is set by the ratio of R139 to R116/R117 in parallel. A similar circuit is used in the B and O 3500/4000/5000 chassis and the Rediffusion Mk.III chassis. The panel incorporates circuitry for interfacing with a teletext decoder module.

THE WESSEL CIRCUIT

In our original note on the Rank small-screen colour set (*Teletopics*, May 1978) we slipped up over the system of e.h.t. regulation used. In fact the chassis uses a combined switch-mode power supply/line output stage known as the Wessel circuit. It's been talked about for some time, but this is the first time it's put in an appearance in a set sold in the UK. A simplified circuit is shown in Fig. 2. The line output/switch mode transistor T686 is fed with an unregulated 300V supply from a bridge rectifier via transformer Tr841. The rest of the supplies are obtained from the line output transformer. As with any switch-mode circuit, regulation is achieved by varying the on/off time of the control transistor. Thus a modulated squarewave drive is applied to the base of T686, the mark/space ratio varying as required to stabilise the supplies obtained from the line output transformer. When T686 is driven on, D687 also switches on and the right-hand side of the screen is scanned in the normal manner, the efficiency diode providing the initial, left-hand part of the scan. When T686 is switched off at the end of the forward scan, D725 conducts and charges C836.

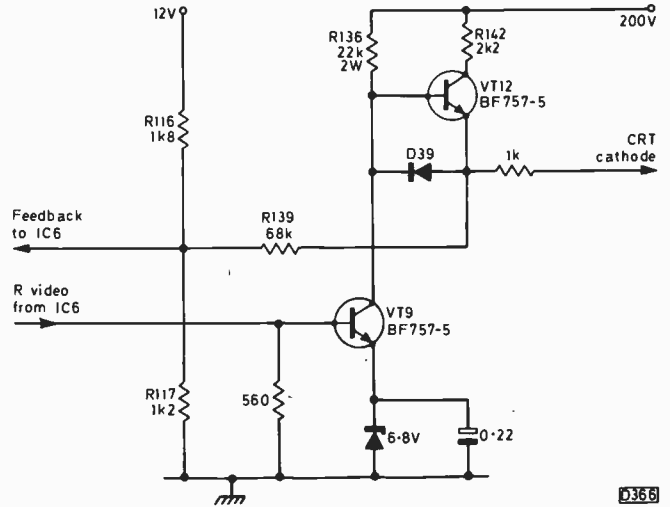


Fig. 1: Class AB video output circuit used in the new Rank T22A colour chassis.

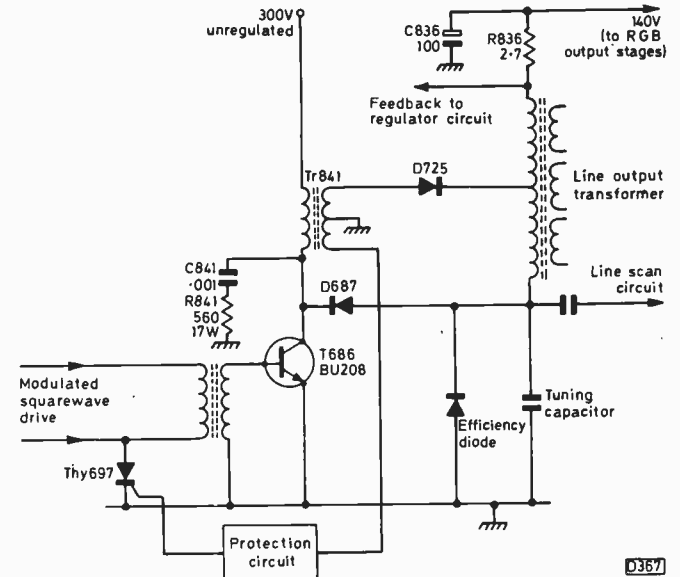


Fig. 2: Basic Wessel combined switch-mode power supply/line output stage circuit used in Rank's W. German produced small-screen colour sets. From the regulated power supply viewpoint, the stage acts as a parallel switch-mode power supply. The arrangement is such that the rectifier (D725) switches on when the transistor is switched off and vice versa however.

D725 remains conducting until T686 is switched on again. Thus the more T686 conducts, the less D725 conducts and vice versa, achieving regulation of the supplies. The voltage across R836 is fed back as the reference to a square-wave modulator circuit which is interposed between the TDA2590 sync/line oscillator i.c. and the line driver stage. A start-up circuit is required for the line oscillator i.c. A short-circuit across any of the outputs would result in excess current in T686. Under these conditions the protection circuit fires the thyristor Thy697, removing the drive to T686. Needless to say, the transformer Tr841 is a rather special one. C841/R841 are included to provide protection for T686.

SATELLITES FOR BROADCASTING

The latest IBA technical review is entitled *Satellites for Broadcasting* and must surely be the first book to be published on this subject. Full of interesting information and lavishly illustrated, the book is available from the IBA, Engineering Information Service, Crawley Court, Winchester, Hants SO21 2QA at £1.50 a copy.

SPECIAL OFFER

a Year's Subscription to

TELEVISION

**FOR
ONLY
£2**

if you order three or more gift subscriptions from any of the magazines shown below.




1 Practical Electronics
to addresses in:
U.K. £10.60
Other countries £10.60




2 Practical Wireless
to addresses in:
U.K. £10.60
Other countries £10.60



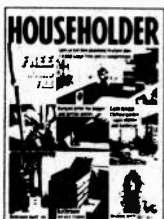3 Everyday Electronics
to addresses in:
U.K. £8.50
Other countries £9.50



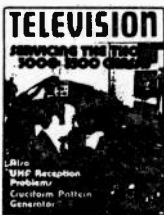4 Practical Householder
to addresses in:
U.K. £8.50
Other countries £9.50



5 Television
to addresses in:
U.K. £9.50
Other countries £10.50

Magazine subscriptions make ideal gifts. They are so easy to arrange – with no shopping and no packing – and they form a year-long reminder to friends and relatives at home and overseas. Choose a magazine suiting the interests of your recipient from the list of titles below, and if you order three or more gift subscriptions to one or more of these magazines you can claim your own annual subscription to **Television** for as little as £2 – an unbeatable price for ensuring that copies are delivered direct to your home every month. Even cheaper than waiting your turn at the newsagents'.

And for every gift subscription you order, you can instruct us to send a greetings card announcing your gift. So this year you save on Christmas cards too! *Get your order in NOW.*

Please send your order in to us in good time before the Christmas rush.



6 Practical Hi-fi
to addresses in:
U.K. £9.50
Other countries £10.50



7 Practical Woodworking
to addresses in:
U.K. £9.50
Other countries £10.50



8 Practical Motorist
to addresses in:
U.K. £9.50
Other countries £10.50



9 Practical Boat Owner
to addresses in:
U.K. £10.00
Other countries £10.00

All subscription orders must be accompanied by payment. Cheques should be made payable to IPC Magazines Limited and sent with this completed order form to Room 2613 King's Reach Tower, Stamford Street, London SE1 9LS.

Use this panel to order your own normal rate subscription to (Television) or to claim your special offer rate.

MY NAME AND ADDRESS (please print all names and addresses)

NAME

ADDRESS

Enter full rate here if less than three other subscriptions are being ordered. £

If you are ordering 3 or more other subscriptions enter only £2 here

SEND MAGAZINE NO. TO:

NAME

ADDRESS

please send a greetings card announcing this gift. £

SEND MAGAZINE NO. TO:

NAME

ADDRESS

please send a greetings card announcing this gift. £

SEND MAGAZINE NO. TO:

NAME

ADDRESS


please send a greetings card announcing this gift. £

I enclose full payment. TOTAL £

SIGNED

MANOR SUPPLIES COLOUR BAR GENERATOR

plus CROSS HATCH KIT (Mk. 4)

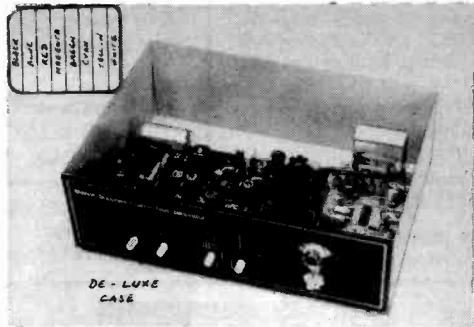

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars, all R-Y, B-Y and Lum. Combinations.
- ★ Plus cross hatch grey scale, peak white and black levels.
- ★ Push button controls, small, compact battery operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £35.00 + 8% VAT + £1.00 P/Packing.

CASES, ALUMINIUM £2.40, DE-LUXE £4.80, BATT. HOLDERS £1.50. ADD 8% VAT TO ALL PRICES!

ALSO THE MK3 COLOUR BAR GENERATOR KIT FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS. £25.00 + £1.00 p.p. CASE EXTRA £1.40. BATT. HOLDERS £1.50. ADD 8% VAT TO ALL PRICES.


- ★★ Kits include drilled P.C. board, with full circuit data, assembly and setting up instructions.
- ★★ All special parts such as coils and modulator supplied complete and tested, ready for use.
- ★★ Designed to professional standards.
- ★★ Demonstration models at 172 West End Lane, NW6.
- ★★ Every kit fully guaranteed.

MK4 DE LUXE (BATTERY) BUILT & TESTED £58.00 + 8% VAT + £1.20 P/Packing.

ALTERNATIVE MAINS SUPPLY KIT £5.78 + 8% VAT + 65p P/P. VHF MODULATOR (CH1 to 4) FOR OVERSEAS £3.50. INFORMATION ON VIDEO TAKE-OFF FOR C.C.T.V.

MANOR SUPPLIES TELETEXT KIT (incl TEXAS DECODER). Full facilities in colour. External unit. AE input to set. Write or call for further information. See working demonstration model! Easy to build and results guaranteed for every completed unit.

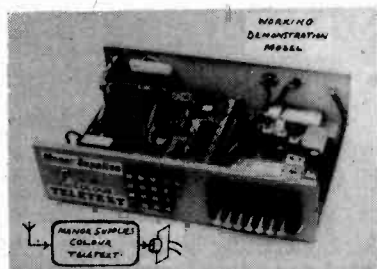Texas XM11 Decoder £130.00 p.p. £1.00.
Auxiliary Units. £88.00 p.p. £1.50
De-Luxe Case £14.80 p.p. £1.00.
Add 12½% VAT.
Separate Price List for Individual Units available.



Changes from Teletext to picture without switching aerials.

Armchair control of Teletext and T.V. stations.



COLOUR, UHF & TELEVISION SPARES

NEW SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED FOR SOUND & VISION £28.50 p.p. 95p.

NEW 'TELEVISION' COLOUR RECEIVER PARTS CAN BE SUPPLIED

T.V. PORTABLE PROJECT LOPT, SCAN COILS, DRIVER £12.50; EHT RECT. 80p; ELC1043/05 £5.50, CONTROL UNIT £1.80; VIS GAIN, VIS SELECT (TESTED) £3.80; PACKS: I.C. £5.20, CAPS TANT £2.75, ELECTROLYTICS £3.20, CERAMICS £2.00, POLY-ESTER ETC. £1.35; PRESETS 90p, TRANSISTORS £3.90, RESISTORS £2.50, SEMICONDS £3.80, BRIDGE REC. £1.95, C106 90p; BYX71/600 (2) £2.40; RELAY £2.25, CONTROLS £1.18; 6MHz FILTER 68p; COIL £1.00; AERIAL £1.00; p.p. 85p. MAINS TRANSFORMER £5.80 p.p. £1.00. OTHER PARTS AVAILABLE. WORKING MODEL ON VIEW AT 172 WEST END LANE, NW6. SPECIAL OFFER FOR SHOP CUSTOMERS, TOSHIBA 14" CRT BRAND NEW £12.50.

TV TEST GENERATOR UHF MODULATOR £3.50 p.p. 35p.*

CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £11.00 + 45p. p.p.* (ALUM. CASE £2.00 p.p. 75p.*) COMPLETE TESTED UNITS, READY FOR USE (DE LUXE CASE) £20.80 p.p. £1.00.* ADDITIONAL GREY SCALE KIT £2.90 p.p. 30p.*

UHF SIGNAL STRENGTH METER KIT £16.80 (ALSO VHF VERSION* ALUM CASE £1.40, DE-LUXE CASE £4.80 p.p. £1.00.)

CRT TESTER & REACTIVATOR PROJECT KIT £19.80 p.p. £1.30*

"TELEVISION" COLOUR SET PROJECT (1974) SPARE PARTS STILL AVAILABLE.

SPECIAL OFFER I.F. Panel, leading British maker, similar design to "Television" panel. Now in use as alternative inc. circuit and connection data, checked and tested on colour £14.80 p.p. 95p.

STABILISER UNITS, "add on" kit for either 40V or 20V, £2.80 p.p. 35p.

PHILIPS 210 or 300 Series IF Panels £2.50 p.p. £1.00.

PHILIPS 210, 300 Series Frame T.B. Panels £1.00 p.p. 65p.

PHILIPS 19TG 170 Series Timebase Panels £2.50 p.p. 90p.

BUSH A823 (A807) Decoder Panel £7.50 p.p. £1.00.

BUSH A823 SCAN CONTROL PANEL £2.50, p.p. 75p.

BUSH 161 TIMEBASE PANEL A634 £3.80 p.p. 90p.

GEC 2040 Surplus Panels, ex-rental. Decoder £5.00 p.p. 90p.

GEC 2040 Convergence Control Panel £2.50 p.p. 90p.

DECCA CTV25 Single Stand. IF Panel £3.80 p.p. 65p.

DECCA Colour T.V. Thyristor Power Supply. HT, LT etc. £3.80 p.p. 95p.

BUSH TV 300 portable Panel incl. circuit £5.00 p.p. 95p.

BUSH TV 312 IF Panel (Single I.C.) incl. circuit £5.00 p.p. 65p.

BUSH TV Portable Eleven Volt Stab. Power Supply Unit £3.80 p.p. £1.00.

PYE 697 Line T.B. P.C.B. for spares, £1.50 p.p. £1.00.

MULLARD AT1022 Colour Scan Coils £6.00 p.p. £1.20, AT1023/05 Convergence Yoke £2.50 p.p. 85p, AT1025/06 Blue Lat. 75p p.p. 35p, Delay Lines, DL1E 90p, DL20, DL50 £3.50 p.p. 75p.

PHILIPS G6 single standard convergence panel, incl. 16 controls, switches etc., and circuits £3.75 p.p. 85p, or incl. yoke, £5.00. G8 Decoder panels ex Rental £5.00. Decoder panels for spares £2.50 p.p. 85p.

VARICAP, Mullard ELC1043/05 UHF tuner £5.50, G.I. type (equiv. 1043/05) £3.50 p.p. 35p. Control units, 3PSN £1.25, 4PSN £1.50, 5PSN £1.80, Special offer 6PSN £1.00, 7PSN De Luxe £2.80 p.p. 35p. TAA 550 50p p.p. 15p. Salv. UHF varicap tuners £1.50 p.p. 35p.

BUSH "Touch Tune" assembly, incl. circuit £5.00 p.p. 75p.

VHF, ELC 1042 £4.80, p.p. 35p, on Pye P.C.B. £5.40 p.p. 85p.

VARICAP UHF/VHF ELC 2000S £8.50 p.p. 65p.

UHF/625 Tuners, many different types in stock. Lists available. UHF tuners transist. incl. s/m drive, £2.85; Mullard 4 position push button £2.50, 6 position push-button £4.50 p.p. 90p. AE ISOL 30p p.p. 20p.

TRANSISTORISED 625 IF for T.V., sound, tested. £6.80 p.p. 65p.

PHILIPS 625 IF Panel incl. circuit 50p p.p. 65p.

TBA "Q" I.C.s. 480, 530, 540, £2.20, 550, 560C, 920 £3.20 p.p. 15p.

HELICAL POTS, 100K. 4 for £1.20 p.p. 20p.

PHILIPS 19TG170 Mains Droppers, two for 90p p.p. 50p

LINE OUTPUT TRANSFORMERS. New guar. p.p. 85p.

BUSH 145 to 186SS series £6.95

BUSH, MURPHY A816 series £8.50

DECCA DR1, 2, 3, 121/123, 20/24, MS1700, 2001, 2401 £6.80

DECCA MS2000, 2400 £5.80

FERG., HMV, MARCONI, ULTRA 850, 900, 950 Mk. 1 £5.90

950II, 1400, 1500, 1590 £5.90

GEC 2000, 2047 series, etc. £6.80

INDESIT 20/24EGB £6.80

ITT/KB VC2 to 53, 100, 200, 300 £6.80

MURPHY 1910 to 2417 series £6.95

PHILIPS 19TG121 to 19TG156. £4.80

PHILIPS 19TG170, 210, 300 £6.80

PYE 11U, 368, 169, 769 series £6.80

PYE 40, 67 series (36 to 55) £3.80

PAM, INVICTA, EKCO, FERRANTI equivalents as above.

SOBELL 1000 series £6.80

STELLA 1043/2149 £6.80

THORN MONO SCAN COILS (850 to 1500) £2.80 p.p. 85p.

THORN 850 Time Base Panel. Dual Standard 50p p.p. 80p.

THORN 3000, 3500 Tripler £5.80 p.p. 85p. Others available.

6-3V CRT Boost Transformers £2.90 p.p. 75p., Auto type £1.80 p.p. 45p.

CALLERS WELCOME AT SHOP PREMISES
THOUSANDS OF ADDITIONAL ITEMS AVAILABLE NOT NORMALLY ADVERTISED

MANOR SUPPLIES
172 WEST END LANE, LONDON, N.W.6.

(Near W. Hampstead tube stn: 28, 59 159 Bus Routes) 01-794 8751

Mail Order: 84 GOLDERS MANOR DRIVE, LONDON N.W.11.

PLEASE ADD 12½% VAT TO PRICES (EXCEPT * 8%)

TV'S TV'S TV'S

THOUSANDS OF MONO TV'S IN STOCK

All makes - all sizes from £4.00.
Square screen from £8.00.

Clearance of 25" D/STD Colour Sets. (Philips 500 and GEC 2028 only) £24.00 plus £6 p/pkg.

Over 2,000 S/STD Colour TV's in stock, inc. Pye Varicaps, Bush Integrated, Thorn 3000/3500/8000, Decca Bradford, GEC 2100, Korting, Grundig, Luxor etc.
With tube tested from £48.00. Working sets from £64.00.

Earlier model S/STD i.e. Philips 511, GEC 2040, Pye Hybrid.
Quantities from £36.00 each.
Singles working from £48.00.

EX-TV SPARES

COLOUR PANELS

Only supplied for models Philips G6, RBM, GEC, EMO, Pye Hybrid varicap, Korting, Bush or Pye LTB Module.

£14.00 plus £2 p/pkg.

Chroma all models

£11 plus £1 p/pkg.

All other panels

£7.00 plus £1 p/pkg.

COLOUR TUNERS

Most makes from £5.00 plus £1 p/pkg.

COLOUR TUBES

(fully tested)

25" £16.00

19" £20.00

22" £24.00

26" (90°) £28.00

26" (110°) £32.00

Plus £4.00 p/pkg.

MONO PANELS/TUNERS

Most types from

£3.00 plus £1 p/pkg.

SPECIAL OFFER:

26" EUROSONIC COLOUR TV with 110° super slim tube, electronic varicap tuner with VHF capability, slider controls inc. tint, dark teak cabinet. Complete with circuit diagram and full spares availability.

Unserviced with tube tested £58.00

Fully serviced working £78.00

Add £6.00 p/pkg. or collect any depot (except Scotland).

PLEASE ADD 12½% V.A.T. TO ALL ORDERS.

MAIL ORDER SEND C.W.O. TO TRITEL (NORTHERN AND SOUTHERN ONLY) CASH COLLECT AT ALL OTHER BRANCHES. UNCROSSED PO'S ONLY.

QUANTITY DISCOUNTS, DELIVERIES ARRANGED.



LONDON:

Kingsley House,
Off Avonmore Rd.,
(Opp. Olympia),
Hammersmith Rd.,
London W14.
Tel. (01) 602 2982.

WEST:

Unit 4a,
Bulwark Industrial
Estate, Chepstow,
Nr. Bristol.
Tel. Chepstow,
(02912) 6652.

SOUTHERN:

Watling Street,
Hockcliffe, North
Dunstable (on A5),
Tel. Hockcliffe
(052521) 768.

NORTHERN:

Thornbury
Roundabout,
Leeds Road,
Bradford 3.
Tel. (0274)
665670.

SCOTLAND:

Peacock Cross
Industrial Estate,
Burnbank Road,
Hamilton.
Tel. (06984)
29511.

NOW OPEN

ALSO AT:
MIDLAND:
48/52 Pershore St.,
Birmingham 5.
Tel. (021) 622 1023.

TV LINE OUTPUT TRANSFORMERS

ALL MAKES SUPPLIED PROMPTLY by our

RETURN OF POST MAIL ORDER SERVICE

All Mono Lopts at the one price

£6.45
BONA FIDE
TRADE

£7.00 RETAIL
(V.A.T. INCLUDED AT 12½%)

Postage and Packing 70p

All Lopts NEW and GUARANTEED for SIX MONTHS

WE ALSO SUPPLY SEPARATE WINDINGS FOR THE FOLLOWING COLOUR L.O.P.T.S
Pye 691 or 697 Chassis.

Bush CTV25 Mk. 1-2-or-3.

Decca CTV25 Non-Tripler Version.

Philips G.6 Single or Dual (Overwind for this Model on Exchange Basis Only).

Philips K.70 Underwind Only.

EMO 90°

COMPLETE L.O.P.T.S

Philips G.8, ITT C.V.C. 5-9 and Decca Bradford.

Prices for the above Colour L.O.P.T.S and Windings on application.

S.A.E. all enquiries.

PAPWORTH TRANSFORMERS

80 MERTON HIGH STREET,
LONDON S.W.19

01-540 3955

TELEVISION ELECTRONIC DISTRIBUTION (SPARES) LTD.

412a Hanworth Road, Hounslow, Middlesex
Telephone: 01-572 4668

PANEL REPAIR/EXCHANGE SERVICE

TRADE ONLY

BERRYVISION 510

EMO

THORN 2000 Series, 3000/3500 Series, 8000/8500/8800/9000 Series.

GEC Solid State 2110 Series.

PHILIPS G8 G9

RBM A802/823

DECCA Solid State 80 Series/Hybrid 30 Series.

GRUNDIG 5010/6010 GB

VERY COMPETITIVE PRICES.

3 MONTHS' WARRANTY FROM DATE OF OUR INVOICE.

DISCOUNT FOR BULK PANEL ORDERS.

CATALOGUE AVAILABLE ON REQUEST.

Eliminating Ghosts

Bill Wright

FORTUNATE indeed is the aerial contractor who operates where good, strong signals abound. But pity the poor soul who has to live with good, strong ghosting as well. Ghosting, as all customers know, is something that can be cured by any half-competent aerial man in next to no time and at minimal cost. "The man who mended the telly said the aerial just needed moving round a bit to get rid of the ghosting." The service engineers who cover our patch seem fond of such unguarded statements! The truth, unfortunately, is often sadly different. Faced with a really good aerial installation which is nevertheless producing very ghosty pictures, the aerial contractor is very much aware that things aren't as simple as the customer (and the TV engineer!) sometimes seems to believe.

As aerial contractors in an area of generally high field strengths but often very bad ghosting, we've been much involved with the "ghost problem" over the years. In the early days of u.h.f. transmissions most of the major aerial manufacturers produced stacked arrays. These were supposedly the ultimate answer to ghosting. In practice however results were variable. No improvement at one call; a pleasant surprise at the next; and so on. The whole thing had an alarming air of unpredictability, while the time and trouble involved in each installation meant that a high failure rate was quite unacceptable.

Log-periodic Aerials

The manufacturers' next bright idea was in the shape of the log-periodic aerial. And a very peculiar shape we thought it to be (see Fig. 1). Log-periodic aerials are enigmatic, inscrutable devices. They are quite unlike more familiar aerials in that every element is driven. In other words there are no reflectors or directors, but simply a series of dipoles which are connected to the downlead via the boom. In fact there are two parallel booms. Each dipole is connected at its centre point across the two booms, and the polarity of this arrangement alternates along the boom. The ends of the booms farthest from the transmitter are shorted together, whilst the downlead is connected across the front end. Don't be misled by the appearance of the Antiference TS21: the coaxial feeder emerges from the back end of the aerial but runs along inside the boom to the connection point at the front. Log-periodic aerials generally have a characteristic impedance about 100Ω , but matching devices are not considered necessary. The coaxial inner is connected to the uppermost boom, and the outer to the lower one.

The "spread" of dipole lengths from smallest to largest determines the aerial's bandwidth and, since the gain suffers little if this spread is relatively great, log-periodic aerials designed for domestic TV reception usually cover the whole of the relevant band, be it channels 6 to 13 or 21 to 68. If the gain is plotted against frequency (within the designed bandwidth) the result is a surprisingly straight line.

This flat response is one outstanding characteristic of the log-periodic aerial. The other is its extremely clean and sharp polar response pattern (see Fig. 2): undesirable rear and side lobes are smaller than those of a conventional

aerial of comparable size. This is because the phase relationship between the voltages developed across each dipole (as they appear at the downlead having travelled varying distances along the booms) tends to favour signals arriving from the front of the aerial rather than those arriving from any other direction. The lack of parasitic elements also helps to keep the response clean.

A highly directional aerial immediately suggests itself for anti-ghosting work of course, and the log-periodic aerial begins to sound ideal. The drawback is its poor forward gain, which seems to be an unavoidable feature of aerials based on this principle. The forward gain figure usually quoted is 8.5dB, which is significantly lower than a conventional 10-element Yagi aerial's gain of about 11dB. In many locations the poor gain of the log-periodic aerial effectively disqualifies it from anti-ghosting work, which is a great pity.

Some time ago Antiference produced a version of their 21-element log-periodic aerial with an amplifier attached. This alleviated the problem to a limited extent, but the cost of the product compared very unfavourably with that of a straight 18-element Yagi aerial without amplification and the results often didn't in the customer's eyes justify the extra expense. Antiference no longer produce a log-periodic aerial for ordinary domestic use: possibly they feel that their XG8, XG14, and XG21 aerials provide a more useful combination of gain and directivity.

Log-periodic aerials are nevertheless nice, light, compact arrays with low wind resistance, and in some locations the extra height that this allows, combined with the aerial's directional properties, will do the trick.

We've used a great many log-periodic aerials over the years to combat ghosting, but we very soon became aware that they don't produce the complete answer in every case.

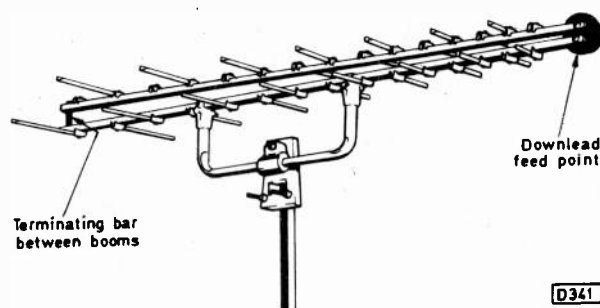


Fig. 1: The Jaybeam LBM2 log-periodic aerial.

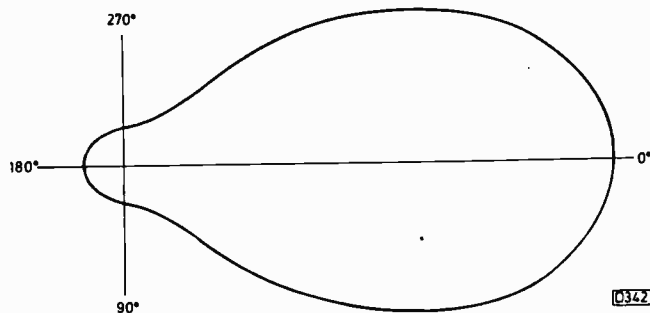


Fig. 2: Polar response of the LBM2 at 500MHz.

They were found to be at their best in areas of high field strength where, with say a combination of half a dozen factory chimneys to the rear and some local obstruction to the fore, strong multiple images are present on the screen. In this sort of place a ten or eighteen element Yagi would produce unrecognisable and unclockable images but a log-periodic aerial might, if it was your lucky day, give watchable but still very ghostly results. The fact that the customer would then appear to be unable to detect any improvement is neither here nor there.

The majority of our ghosting problems are not of this sort however. Often the problem is one solitary ghost image which can be strong enough to make the picture unwatchable. Forty-four footballers controlled by two referees... Video in stereo... In these conditions log-periodic aerials seem as unpredictable as the earlier stacked arrays. Unpredictable except that they tend to be at their least effective on the roofs of the most critical customers, just like all other aerials. Log-periodic aerials are cheaper than stacked arrays - if you can manage without an amplifier. They are quicker to assemble. Perhaps they work on average a little bit better. But they don't really solve the problem.

Back to the Drawing Board

So we started to experiment extensively, and spent a lot of time working with stacked arrays. We needed to tailor the response pattern of the array at each location to reject signals from one specific direction, that of the ghosting. At the same time, maximum forward gain must be maintained. This is important because the strength of the ghost image as it appears on the screen is dictated not by the strength of the ghost signal in absolute terms but by the ratio between it and the signal received direct from the transmitter.

In the early days we had simply fixed two aerials together and rotated the whole assembly for the best results. This was a bit hit and miss. A typical polar response diagram for a horizontally stacked array of two aerials is shown in Fig. 3. Ghosting from directions A1 and A2 will be largely rejected by the array, but ghosting from directions B1 and B2 will be rejected to a much lesser extent. We can't move the factory chimney, gasometer, or other reflecting object, so we must alter the angles of minimum and maximum signal acceptance. We must do this while still keeping the largest forward lobe pointing at the transmitter.

How? Consideration of the way stacked arrays achieve their directional characteristics lead us to realise that we have to satisfy the following conditions: (1) Both aerials must receive as much signal as possible direct from the transmitter, and these signals must be combined exactly in phase. (2) The ghost signals received by the two aerials must be of equal amplitude and must be combined exactly out of phase.

Alignment Procedure

If there's only one really troublesome ghost signal to deal with, the above conditions can be satisfied quickly and easily as follows.

Fix a horizontal boom on a vertical mast (see Fig. 4) with an 18-element aerial at one end of the boom. The aerial's supporting cradle should be roughly central on the boom. Rotate this assembly for maximum signal strength, using a field strength meter or a portable TV set with an attenuator. Ignore ghosting at this stage. The boom should now be at right-angles to the direction of the transmitter. Secure the assembly in this position.

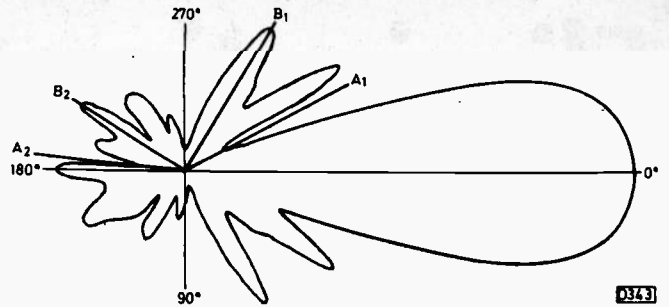


Fig. 3: Polar diagram of a stacked Yagi aerial array.

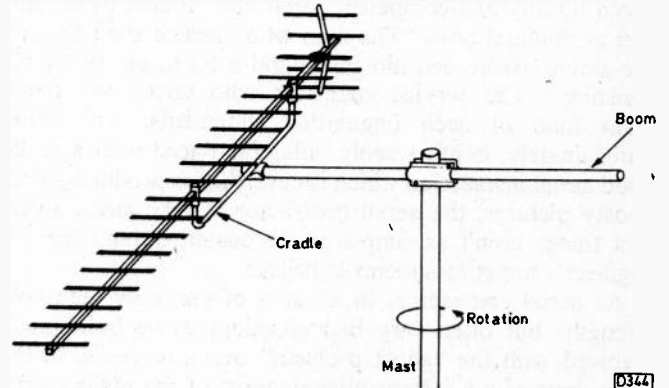


Fig. 4: Aligning the first aerial.

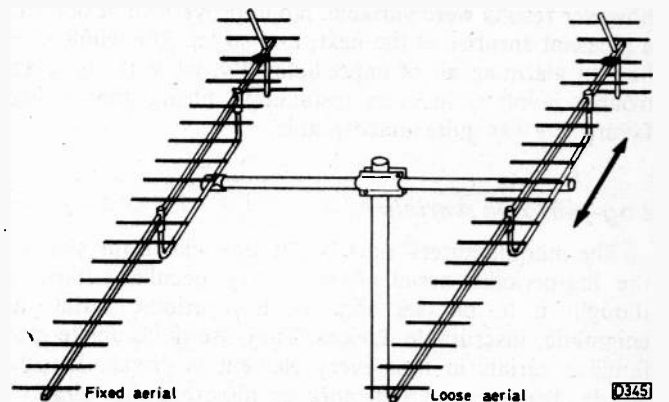


Fig. 5: Movement of the second aerial towards and away from the transmitter for correct phasing of the signals received by the two aerials direct from the transmitter. Adjust for maximum signal pickup. The phasing harness used when adjusting the aerials consists of a quarter wavelength of 50Ω coaxial lead connected between the 75Ω downlead and the equal-length 75Ω leads from the two aerials.

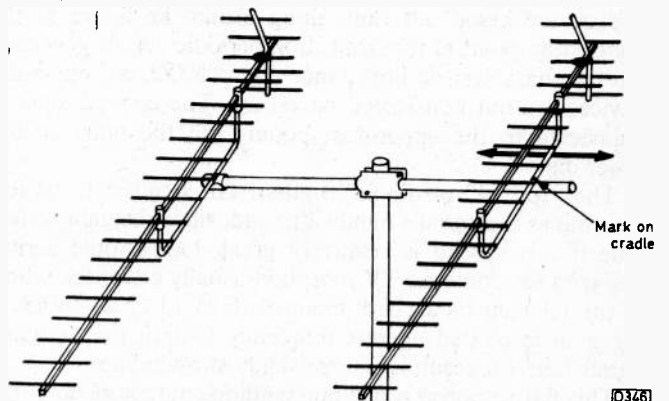


Fig. 6: Sideways movement of the second aerial. This adjustment is made so that the ghost signal pickup by the two aerials cancels out.

Connect this aerial and an identical one to the meter or TV set, using a phasing harness. Holding the second aerial in position along the boom, move it towards and away from the transmitter (see Fig. 5), carefully keeping it pointed at the transmitter. Since this movement alters the phase relationship of the two aerials, a maximum and minimum meter indication will occur. If a meter is not available and a TV set has to be used, the effect is visible but less obvious. Obtain a maximum reading, then mark on the cradle with felt pen the point where it crosses the boom. Again, ignore ghosting. Repeat this procedure several times, with the loose aerial at different distances from the fixed one. The same mark on the cradle should coincide with a maximum meter reading at all points along the boom. If not, the boom is not at right-angles to the transmitter direction. Realign it if this is the case.

You can now alter the distance between the two aerials while they remain exactly in phase. In this way the forward gain of the combined array is always at maximum. The mark on the cradle must always be kept exactly on the boom of course. Don't be tempted to skip on the adjustments leading up to this point: if there's a phase error between the two aerials at any point along the boom there will be a reduction of forward gain if the loose aerial is mounted at that point. This will make nonsense of any subsequent attempts at alignment for minimum ghosting.

With the two aerials still connected together via the phasing harness, next move the loose aerial sideways (see Fig. 6), observing the results on the TV set. It should be possible to identify a series of points along the boom where the loose aerial should be fixed for the two aerials together to produce minimum ghosting. At these points the ghost signals from the two aerials are exactly out of phase with each other. This happy condition will recur every time the loose aerial is moved through one wavelength towards or away from the source of the ghosting. If the ghosting is only slight it may be easier to find the points along the boom where the ghost is most visible: mark these, then mount the aerial mid-way between them.

If the source of the ghosting is at right-angles to the transmitter direction the points of minimum ghosting will be at one wavelength intervals along the boom. In fact the distance between the two aerials will be $\lambda (n + \frac{1}{2})$. In cases where the ghost signal comes from an angle other than 90° or 270° the optimum positions will be more widely spaced. If the ghosting originates from almost exactly the same direction as the transmitter, or from almost exactly the opposite direction, the two aerials will need to be very far apart for phase cancellation to occur. In fact if the ghosting originates 5° from the transmitter axis (that is, from 5° , 175° , 185° , or 355°), the two aerials will need to be about 140cm apart for channel group A.

Those of a mathematical bent will realise that the distance along the boom between the two arrays can be derived from the wavelength (λ) and the angle between the transmitter and ghost directions (θ). The formula is $\lambda (n + \frac{1}{2}) \sin \theta$.

Being more nimble on a roof than with a calculator we usually proceed by trial and error. The mathematical approach can help when there are two strong ghost signals from different directions however. The series of possible inter-aerial distances for each can be worked out, and a position for the second aerial chosen which approximates to one value for both. This should be regarded as a starting point for practical experiment however, not as a definitive answer. The easiest way to find the necessary angle for the calculation is to use a large-scale Ordnance Survey map and a protractor. The direction of the source of ghosting can be

found by rotating the aerial whilst observing the TV screen. There is seldom any problem here, since the highly reflective culprit can usually be seen clearly on the skyline. In the highly unlikely event of the ghosting coming from *exactly* 180° , no phase cancellation would be possible and the ghosting would triumph. Fortunately this remains for us a hypothetical case.

Final Adjustments

Because the final adjustments are extremely critical, and involve moving a fairly large aerial accurately through small distances, great care should be taken. It's impossible to eliminate ghosting if it can't be seen properly in the first place, so the right sort of programme must be on the air. If you find yourself trying to do this job with a rapidly changing selection of cluttered shots on the screen, well, go down the ladder and have a cuppa, and admire the customer's new microwave oven for a bit. This problem brings the writer dangerously close to his number one hobby horse, which concerns the lack of BBC-2 test transmissions for most of the working day. 'Nuff said!

If the ghosting cannot be eliminated completely the reason may be that the ghost signals received by the two aerials are not of equal amplitude. If one aerial appears to be screening the other in this respect they can be mounted at different heights by simply inverting one cradle. The aerial itself should remain the same way up of course. Remember that it isn't essential for the two aerials to receive exactly the same amount of signal direct from the transmitter (although this is usually the case): it's the ghost signals that need to be exactly equal.

When a satisfactory picture has been obtained it will probably be found that the two aerials are at different distances from the mast. You can't move the mast sideways because it's attached to the chimney, but fortunately the two aerials and the boom can be moved sideways without the previous critical adjustments being invalidated. The distance between the two aerials must be kept exactly the same of course, so it's usually easiest to keep them clamped to the boom and move the whole thing in one piece. Check orientation by visual sighting along one aerial before and after moving.

Bandwidth Requirements

In theory the correct inter-aerial spacing for one channel will not be correct for the other two. In practice this doesn't seem to be a problem. We usually carry out the alignment procedure on the most ghostly channel of the three or on the middle one. Minor adjustments can then be made if necessary after the pictures have been scrutinised. Reducing the distance between the aerials will favour the higher channels and vice versa. These adjustments are small: the theoretically correct positions for each channel may be only 2-3cm apart if the two aerials are reasonably close together. This makes it easier to find a position which works on all channels however, and for this reason the two aerials should not be mounted unnecessarily far apart. We usually start with the aerials about one wavelength apart, and use the first optimum position greater than this distance.

Connecting the Aerials Together

An ordinary splitter can be used to connect the aerials together. Both inductive and resistive types are suitable. The split must be exactly equal, otherwise complete cancellation

of the ghost signals will be impossible. Commercially available splitters are generally satisfactory in this respect, but a check can be performed quickly with the field strength meter. Connect the common terminal of the splitter to a signal source, and measure each output. The other output should have a dummy load connected.

We use splitters for this purpose because they give us an accurate impedance match in a simple and straightforward way. We haven't worried much about phasing arrangements, which might give better gain, because we are rarely troubled in our area by weak signal problems. With an ordinary resistive splitter the gain, as you might expect, is about the same as the equivalent single aerial. Those who wish to experiment with phasing harnesses of greater efficiency are referred to Nick Lyon's article on *Removing Ghosts* (March 1978) and to *Long-Distance Television* (March 1977).

Don't be tempted to connect the two feeders to the downlead without any impedance correcting device. The resulting mismatch will cause all sorts of unpredictable effects.

The two feeders which take the signal from the aerials to the splitter should be of exactly the same length. If not it will still be possible to carry out the alignment procedure but one aerial will end up slightly forward of the other, which looks odd. There is also the possibility of unbalanced standing waves or some other inequality affecting the overall performance.

Choice of Aerial

The two aerials must of course be identical. After some experimentation we now always use Antiference 18-element aerials for the job. When used singly these aerials seem to us to be as directional as any on the market within the price range. We have not used large, high-gain aerials in the stacked mode – as already mentioned, we have few field strength problems to contend with. The cost of two XG21s might also have something to do with it! We can see no reason why these very large aerials should not be efficient when used in this way, though they would need a well thought out mounting and stacking arrangement. We've removed many a nasty ghost simply by replacing the

existing cheap 18-element aerial with an Antiference TC18 incidentally.

Co-channel Interference

From the aerial rigger's point of view co-channel interference presents exactly the same problem as ghosting: how to achieve maximum gain in one direction with minimum gain in another. Stacked arrays can do a really good job here, because the signal rejection is usually required on only one channel of the three. Alignment can thus be carried out on this channel, with no need to worry about the others. Co-channel interference disappears in a much more definite and obvious way than ghosting when the final adjustments are made, so finding the exact position along the boom for the second array is that much easier.

Mounting the Array

Rigid mounting is essential if the results are to be reliable. The mast should be of $1\frac{1}{2}$ or 2in diameter, with a 12in chimney bracket or the equivalent wall bracket. A 6ft x 1in heavy gauge mast is ideal for the boom, which should be cut to length when all adjustments have been made. All cables, splitters, etc. should be well secured. The feeders should be brought away from the aerials as neatly and cleanly as possible, and in an identical manner on both sides of the array.

As already stated, the technique depends for its success on each array receiving an identically strong ghost signal. For this reason the field strength of the ghost signal must be uniform over the area of the array. When considering where to mount the array therefore, keep it away from other aerials or anything else that might obscure or reflect the signal.

With a single aerial, it's often possible to find a place for the installation where the ghost signal is attenuated by intervening brickwork, stone or trees. Unfortunately this normally useful wheeze doesn't combine well with the use of stacked arrays, presumably because the ghost signal is of an uneven and irregular nature in such a location. Stacked arrays seem to be happiest nice and high and as far away from other objects as possible. ■

Letters

STANDARDS OF SERVICE

The question of what constitutes good service doesn't seem to have come up for discussion recently, though in the fast changing world of TV I think it's very important. If the customer phones to say his TV set has gone wrong and a technician calls within a few hours it's assumed by all concerned, including the customer, that the service was excellent, regardless of whether the technician left the set in a satisfactory condition. Suppose the set concerned suffered from intermittent sound or loss of one colour. Unless the cause was readily identifiable on the spot, the chances are that the technician left with one or other of the following comments: "It should be all right now I've adjusted it; let us know if not." "It should be all right now I've put in a new valve." "I can't find any fault, let's see how it goes..." "It needs a new panel: I'll bring one in a day or so." "We'll arrange to take it to the workshop for a soak test."

This sort of vagueness does not amount to good service, because the repair may or may not have been completed and more calls may be required until either the staff or

customer become so tired of the situation that more drastic action is taken. The problem mainly concerns large service organisations and rental companies, where technicians may have a dozen or more calls to make in a day, inadequate records of calls and the action taken are kept, and perhaps a different technician calls on each occasion. This situation means that each service call is a potential problem to the technician, impeding his progress through the day, with the result that he hasn't the time to get involved or to deal with an interesting problem from beginning to end – if he fails to find the cause of the trouble in the limited time available, it's back to the bench engineer.

Provided the number of complaints reaching head office are few and the usual credit-debit figures show a healthy profit, no concern is shown and the illusion of good service is maintained. One solution would be to enable the field technician to do his own bench work as well. He then won't get tired of and waste time making repeated calls to faults he can't find, but will be able to get to know a number of sets thoroughly and ensure that their performance standards are maintained. He'll be able to carry out preventive maintenance and safety checks, thus reducing his future workload.

This brings us to the quality of work carried out in the workshop. The preoccupation of large concerns with time sheets and figures leads to the dangerous situation where the main consideration is the number of "completed" outgoing sets. The pressure from sales staff in rental companies can be such that incoming decontrolled sets from other subscribers are sold before they are checked, or re-rented without any form of inspection other than a cursory glance by the non-technical installer – who's often underpaid and dependent on commission.

It amazes me that companies so run have any customers at all. It's interesting to look at the sets working in the show-rooms. In some the standards are high, but in others one sees sets with dim pictures due to failing tubes, weak or no colour, incorrectly centred pictures, intermittent rolling, and a truly amazing variation in colour fidelity. One can't expect the performance of an early design to come up to the standards of more recent times of course, but it's not unreasonable to expect old sets to perform as they were designed to do. There seems in particular to be very little appreciation of colour pictures. Setting up each receiver on a vectorscope would be expecting too much, but decent reproduction of test card F by all sets should be possible.

In conclusion, it seems to me that reappraisal of the basic approach to service is needed. There should be standard checks on sets in the workshop for safety, then assessment of the picture under various conditions to show up faulty colour reproduction, poor synchronisation, picture geometry faults and, in addition, a check on anything that to an experienced hand doesn't "feel" right, such as a badly operating on-off switch or worn tuner buttons. This should be coupled with extensive soak testing and checking to ensure that as far as possible the sets are working in peak condition. By adopting such standards, engineers will achieve greater job satisfaction, and there'll be more time too for the numerous obscure faults which increasingly complex technology is building into sets. – **Malcolm Burrell, Halstead, Essex.**

THE COMMON-EMITTER CIRCUIT

I've read with interest the correspondence in the September issue on the common-emitter circuit variant, and feel that any confusion is mainly due to the statement that a common-emitter stage imparts a 180° phase shift. In fact a common-emitter stage at normal signal frequencies provides a signal at its collector in phase with, but the inverse of, that at its base. Although the effect with a symmetrical waveform can be considered to be the equivalent of a 180° phase shift, consider what happens with an asymmetrical waveform as shown in Fig. 1(a). This shows that the phase relationship between the input and the output is maintained.

The "unconventional" common-emitter circuit shown in Mr. Amos's Fig. 1(c) appears rather more conventional when the a.c. conditions only are considered and, as shown in Fig. 1(b), the supply impedance is regarded as being zero. It can be seen that all the terminals are now connected to either the input or the output in the usual manner. It can



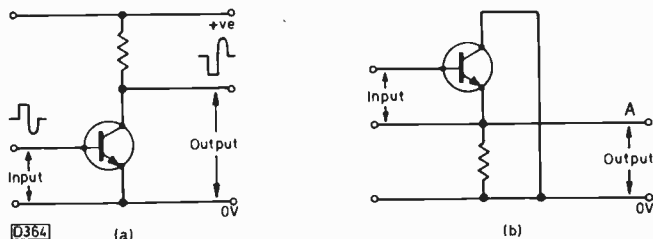


Fig. 1: Common-emitter arrangements.

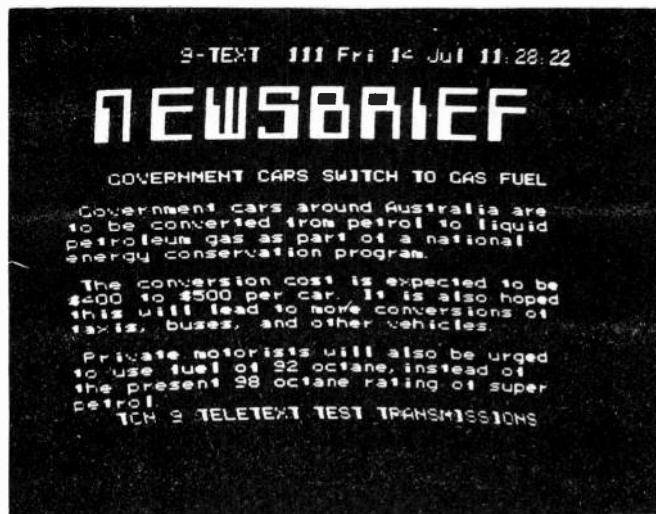

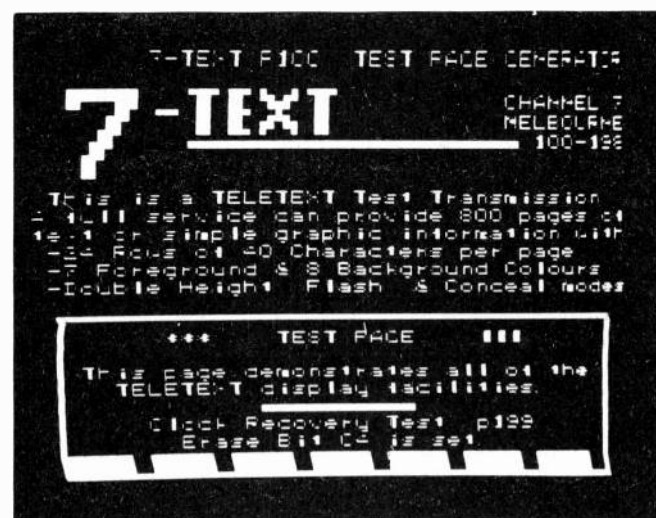Australian teletext reception. Sydney channel 9 relayed by coaxial cable to Melbourne and transmitted by Melbourne channel 9. Received by P. Izzard in Niddrie, Victoria.



Teletext transmitted on Melbourne channel 7.

also be seen that with respect to the common line A the output will be in phase with but the inverse of the input, as in the conventional way of showing the circuit. – **H. Evans, Crewe, Cheshire.**

AUSTRALIAN TELETEXT RECEPTION

I have recently completed construction of the *Television* teletext decoder and thought you might be interested in the results obtained here. The decoder was built to gain experience with teletext. The input logic, memory and display boards are as published, but for various reasons the front end differs. I chose to pick off the detected video from a standard Japanese (National) monochrome portable, passing the signal through a simple two-transistor video amplifier to the input of the CA3046 i.c. The output from the display board is then returned via a transistor back into the set's video circuitry.

The results, after some fault finding, are very encouraging. Melbourne channels 7 and 9 transmit a teletext test service, and I was able to produce stable, clear teletext from both sources. No doubt the results would have been even better following the front end as published. The accompanying photos show the reception, and I'd like to thank all those involved in the project. – **P. Izzard, M.T.E.T.I.A., Niddrie, Victoria, Australia.**

Thorn 9000 Chassis Faults

John Coombes

THE 9000 colour chassis was introduced in early 1975 and was another Thorn innovation, for two reasons. First, it's fitted with the 20in., 90° version of the RCA PIL self-converging c.r.t. And secondly the single R2540 "Syclops" transistor acts as both a parallel chopper transistor for h.t. regulation and as the line output transistor, driving two transformers. Because of the latter feature a fairly comprehensive over-voltage/excess current trip circuit is incorporated. There's NS and EW raster distortion correction, and a rather complex eight-transistor field timebase which owes something to the RCA influence, being designed to drive the low-impedance toroidal scan coils. The signal side is fairly conventional, with a varicap tuner, three-chip decoder, and cascode RGB output stages driving the c.r.t. cathodes.

No Results

As with all sets, no results is the most common fault. It's necessary first however to decide whether the set is actually dead or tripping, since the observable symptoms will be the same. A voltage check at pin 7 or 8 of socket 16 on the bottom PC752 switch-mode power supply/line output panel will show a fast flicker if the set is tripping – with the meter on the 10V or 30V range.

If the set is completely dead, the first thing to check is the mains fuse F1 (2.5AT) which, being BEAB approved, must be replaced with the same type. If it's found to be open-circuit, first check the mains filter capacitor (1 μ F, no circuit reference number, on the PC752 panel), then the mains rectifier W701 (MR510). Another possibility is the Syclops transistor VT701.

W714 Defective

If you find that VT701 is being ruined at an alarming rate, though there doesn't seem to be any apparent reason, check diode W714 (1S44) which may be open-circuit – the set will continue to operate, but the Syclops transistor will be without protection since W714 senses its emitter current, operating the overload trip if this is excessive. W714 can also be responsible for intermittent tripping. To provide increased protection for the Syclops transistor, W729 (ITT44) is added in parallel with W714 in later sets.

Set Tripping

Before dealing with the causes of tripping, it's important to emphasise that the set should not be operated with any of the trips disconnected – five factors are monitored, the Syclops transistor's collector voltage (via W703), its emitter current (W714), the mains input (W716 in the thick-film unit on panel PC752), the field timebase h.t. supply (W723) and the 240V video supply (W724).

One cause of tripping is excessive e.h.t. If R606 (set

e.h.t.) is not incorrectly adjusted (see later), check the efficiency diode W705 (MR510) which can cause this trouble. Other diodes which can cause tripping when faulty are W723 (BZX83C30, one of the trip sensors) and the 90V supply rectifier W706 (F247). The line oscillator transistor VT411 (BC212C) can be responsible for tripping, while another cause is a defective thick-film unit (R704-7/W716) which must be replaced as a complete unit – very often it will seem to check o.k. but a replacement unit will cure the fault. Other transistors which can cause tripping are the line driver VT412 (TCE527) and the 12V regulator transistor VT413 (BC182L) which is in series with the line driver. The correct type must be used when replacing the line driver transistor, otherwise you can get a white line, like a striation, down the side of the screen.

If the set keeps tripping the best course of action is to remove fuse F4 (1.6A), thus disconnecting the supply to the field timebase. If the tripping persists, remove F2 (1A), disconnecting the 30V supply. If the tripping then stops, the 30V supply rectifier W708 (BY210/400) is suspect.

If the raster appears and the set just trips out, check C602 (0.068 μ F) and the voltage comparator transistor VT601 (BC212L) on the Syclops control panel PC756.

Intermittent tripping can be the result of incorrect e.h.t. adjustment which should first be checked. R606 should be adjusted for 720V at TP708, using a 10k Ω /V or higher sensitivity meter. To make the reading, connect the meter to TP708 via a BY127 or 1N4007 rectifier diode (anode to the test point) and shunt the meter with a 1kV d.c. 0.01 μ F capacitor. If the trouble persists, change C741 (1 μ F) which decouples the emitter of the Syclops transistor.

Tripping with hum from the speaker is caused by a defective mains rectifier reservoir capacitor C702 (400 μ F).


Sound, No Raster

The most likely cause of sound but no raster is a faulty e.h.t. tripler. The line output transformer can also be responsible, often due to dry-joints – on the transformer itself, between the coil leads and connecting pins, not where the pins are connected to the board. If the e.h.t. tripler is faulty, check whether the efficiency diode W705 (MR510) is open-circuit.

No Sound or Raster

No results due to failure of the Syclops circuit to operate (set not tripping, F1 o.k.) can be due to a defective ramp reset transistor VT602 (BC182L) on the Syclops control panel. Alternatively the ramp charging capacitor C604 (0.0039 μ F) may be faulty. Other semiconductor devices on the panel may have to be checked.

The EW modulator diodes are W711 (MR814) and W712 (MR854, later MR914). The supplies for the field timebase, the decoder and the i.f. strip are derived from this circuit (though in early production sets the decoder/i.f.

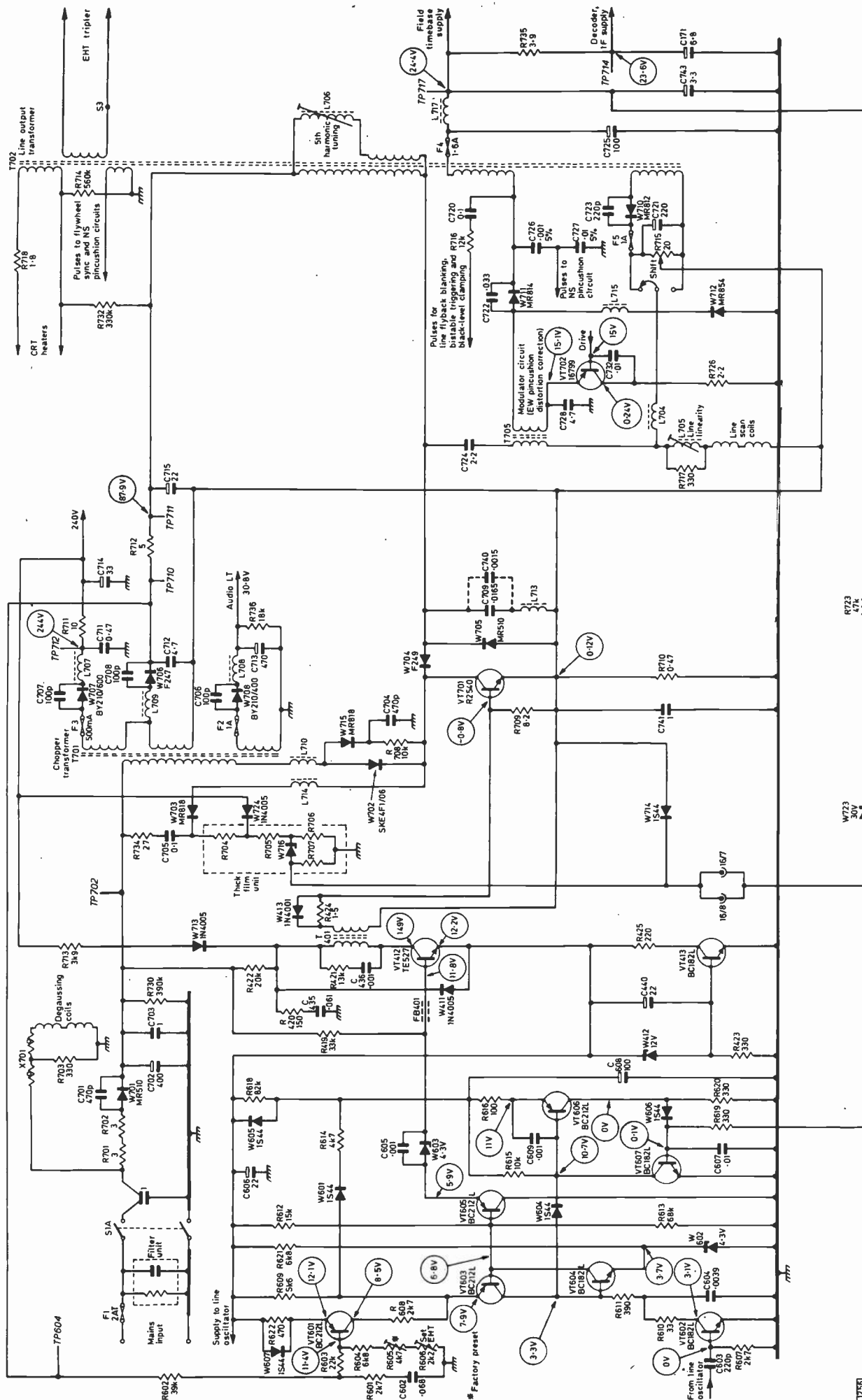

VT530

Fig. 1: The Syclops switch-mode power supply/line output stage circuit used in the Thorn 9000 chassis, including the line driver and Syclops control circuits. Components prefixed 4 are on the timebase panel (PC751), those prefixed 6 are on the Syclops control panel (PC756) while those prefixed 7 are on the Syclops audio panel (PC752). There have been several modifications. In early sets the decoder/i.f. supply was obtained from a 24V regulator fed from the 30V audio supply. Early sets use an OVB AB thick-film unit with W724 omitted, later sets an OVB B AB or OVP-B unit. Don't use the early type if W724 is present. F1 changed to 2.5A anti-surge.

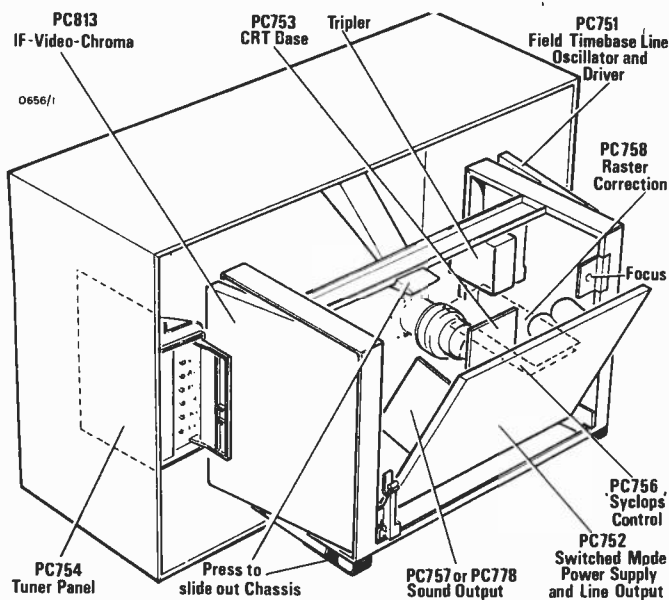


Fig. 2: Locations of the printed panels, with the bottom panel shown in the raised position for access to the print side. If the 24V field timebase supply rises excessively, the over-voltage trip operates. Check by removing F4. If this clears the trouble, connect a 120Ω 5W resistor across the field timebase supply, replace the fuse and check the field timebase circuitry.

supply is obtained from a regulator fed from the audio supply line). When W711 or W712 is open-circuit the tube heaters will be alight and e.h.t. will be present but the 24V supply will be lost and there'll be no sound or raster (c.r.t. cathode voltages high). First check fuse F4 (1.6A) however. If it's open-circuit, C196 on the i.f./video/chroma panel PC813 may be faulty. Change it to an electrolytic if it's a tantalum type. Check the field timebase supply line.

No sound or raster with no e.h.t. and the c.r.t. heaters out will be the symptom when the 90V supply to the line output transformer is absent. Check whether R712 (5Ω) or alternatively W704 (F249 between the Syclops transistor and the line output transformer) is open-circuit.

Excessive Width or Line Jitter

The symptom when W712 in the EW modulator circuit goes short-circuit is excessive width. W712 can also be responsible for line jitter: to prevent this, it was changed from type MR854 to type MR914.

R736 (18kΩ) has been added across the 30V supply reservoir capacitor C713 to prevent this voltage rising if the sound output panel PC757 or PC778 is removed. It's worth adding this resistor on all sets.

Excessive Brightness

Loss of the 240V supply to the RGB output stages will result in excessive brightness. Check whether fuse F3 (500mA) has blown. If it has, the filter capacitor C711 (0.47μF) could well be short-circuit. If the fuse is in order, the 240V rectifier W707 (BY210/600) is probably open-circuit. Excessive brightness with the 240V supply present is usually due to a defective i.c. – the SN76227N-07 demodulator/matrixing i.c. which drives the RGB output stages (IC4).

Unstable Grey Scale

Since the first anodes are internally connected in the PIL

tube, the grey scale is entirely dependent on the RGB output stages. Unstable grey scale can be caused by one or other of the three emitter circuit decoupling capacitors C174/5/7 (560pF) being defective.

Crinkley Verticals

Returning to the line timebase before going on to the field timebase, the only other trouble we've had is C431 (10μF) drying up. This decouples the emitter of the line oscillator transistor, and the result is crinkley verticals.

Field Timebase Faults

Common causes of field collapse are VT407 (16801) which is one of the field output transistors, VT408 (BC327) which drives it, the field output stage driver transistor VT404 (BC182LB) and the source-follower f.e.t. VT403 (BF256L). We've also had one of the transistors in the field oscillator circuit, VT402 (BC182L), cause field collapse.

VT407 and VT408 can also be responsible for lack of height, or bottom cramping.

The other output transistor VT406 (16802) generally causes excessive height when it goes faulty. This fault can also be due to diode W406 (1N4001) being leaky.

The components which cause field collapse can also do so intermittently. This is harder to track down of course, but a freezer spray and hairdryer help. Don't apply excessive heat however as this can cause more trouble.

Signal Board Faults

In addition to causing excessive brightness, IC4 (SN76227N-07) can be responsible for loss or intermittent loss of colour. The luminance and chrominance signal processing i.c. IC3 (SN76226DN-07) can also cause loss or intermittent loss of colour. It can also be responsible for loss of colour on various parts of the screen. Other causes of no colour are a defective chroma coupling capacitor C181 (22pF) or C186 (6.8μF) which decouples the supply to IC5 (pin 2) going short-circuit or leaky.

A ghost or a weak signal can be responsible for intermittent colour drop-out. There's a modification that can help here – adding a 12kΩ, ¼W resistor (R270) in series between C194 (1μF) and pin 13 of IC5. The fault affects only a small number of sets however.

The PAL switch is in IC4, which can be responsible for PAL switching faults.

Slow colour drop-in may be due to incorrect adjustment of the reference oscillator frequency control R210 (10kΩ) associated with IC5 (TBA395). In later production sets a zener diode W107 (BZX83C8V2) is added from pin 2 of this i.c. to chassis to eliminate hum effects on some areas of the picture.

Striations can be caused by capacitor troubles in the a.g.c. circuit. In later production C125 is changed to 100μF and C116 to 0.001μF to counter this problem.

Loss of colour can be due to incorrect tuning or a defective tuner. The tuning capacitors associated with the TCA270 vision demodulator i.c. can also be responsible. These are C136 (47pF) which tunes the a.f.c. circuit coil and C138 (75pF) which tunes the detector tank coil.

The tuning voltage stabiliser i.c. (TAA550) can cause this trouble or drifting completely off signal.

On one or two rare occasions we've found the TCA270 i.c. to be the cause of drifting, where it's been very difficult to tune the receiver to the station correctly. ■

Long-Distance Television

Roger Bunney

TWO firsts to report this month. On Wednesday, August 9th the first European television signals at 12GHz were received at the IBA's Crawley Court, Winchester engineering centre, from Italy via the OTS-2 satellite. The IBA reported that the vision quality was good, confirmed by subsequent tests which occur on various days during the periods 1200-1400 and 1700-1900 BST (normally, that is). Steve Birkill, of ATS-6 fame, is working on an installation which he hopes will enable him to receive the signals successfully.

The second and rather startling item, a first in the DX-TV field, occurred on July 30th, yours truly participating. RUV Iceland ch. E4 was being received at good strength at 1830, with the aerial pointing north west. There was no ch. E3 RUV signal however, so I tuned in to this channel and hopefully awaited the RUV "ISLAND" test card. Signals appeared at 1845, but did not lock. Adjustment of the line and field hold controls enabled the picture to be locked, displaying a picture of a variety show but lacking in height. Tuning back to ch. E3, I passed through American speech: it then became clear that the ch. E3 signal was actually a ch. A2, System M, 525-line one. Tuning back up to the sound, another System M vision signal became apparent, just above the sound frequency but slightly below the ch. E4 vision - obviously ch. A3! A hurried call was made to David Martin at Shaftesbury, and some ten minutes later he logged both signals.

Efforts were made to record the ch. A2 sound, which at 1925 went on to commercials, then to what at first seemed to be a station identification but subsequently seems could have been a promotion for a radio station. We've been unable so far to trace the source of the signals, but are awaiting information from the US. After several commercials, the following was resolved at about 1925: ".?. News Service, coming your way with stereo .?. coverage promptly at 7.30 here on ??? TFL. More coverage, better than ever. This is coast to coast action, ??? TFL MV. You'll enjoy better coverage in Telfor (Telford?) 10.30 ????? A is for astronaut." A characteristic background musical accompaniment was noted. So far, a small town called Telford has been located near Philadelphia, but no matching call letters WTLF. The investigation continues.

Hugh Cocks, some 70 miles to the west of Romsey, was contacted but RUV ch. E3 was so strong there that nothing could be resolved through it. As far as I know, this is the first time that North American ch. A2 and A3 signals have been received in Europe. They came via double/triple hop Sp.E.

As regards more conventional reception, August remained a very active month, with a high level of Sp.E activity. There was an aurora on the 4th, and improved tropospheric reception during the last week. There was continued F2/TE reception, with Gwelo, Rhodesia ch. E2 putting in an appearance on several dates - in fact its reception is becoming rather a common event in the south of England, though it hasn't reached very far north.

Sp.E signals have arrived from most of Europe, with

prolonged reception of RTVE (Spain) and NRK (Norway). Excellent Sp.E conditions were noted here on the 1st, 2nd (including Finland), 3rd, 8th (RTVE were using a variety of patterns), 10th (Rhodesia), 11th, 12th (Rhodesia), 14th, 15th, 16th, 17th (Rhodesia), 22nd, 23rd, 24th (Rhodesia again), 26th and 27th. Altogether an eventful and interesting month.

News Items

Jordan: Reports suggest that JTV is to transmit a daily one hour programme in French - so take care on ch. E3.

Canada: An unlicensed TV transmitter has been established in the North West Territory, radiating programme material recorded in the Buffalo NY area (USA), including commercials. The output comes from two stations in Buffalo. Transmissions last for some 20 hours daily. The radiated power is low, and it's expected that other transmitters in isolated areas will follow.

Sunspots: Sunspot activity may peak towards the end of 1979, not in early 1980 as earlier suggested. The Swiss Solar Observatory expects the smoothed numbers to reach 103 in November, 107 in December and 111 in January 1979.

United Kingdom: The IBA is transmitting a new experimental test pattern from its Rowridge, Isle of Wight transmitter (and its relays). The pattern generator was constructed and designed by the IBA.

New EBU Listings


France: Saint Etienne TF1 ch. E35 10kW horizontal; Limoges TF1 ch. E56 1000kW horizontal; Niort FR3 ch. E58 310kW horizontal.

Eire: Cairn Hill RTE-2 ch. E43 800kW horizontal.


Morocco: Boukhoul RTM ch. M5 520kW horizontal. Ch. M5 vision is at 171.25MHz - a good one for MS reception.

Astra Aerials

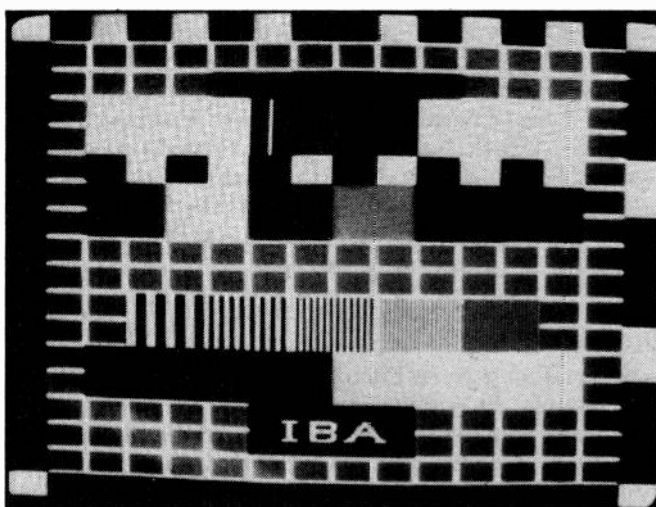Having noticed the Astra (D.I.Y.) Aerials advertisement alongside this column for several months, I decided to contact the Dwyer family - who are Astra Aerials! The business was started in 1954 and currently stocks a vast range of aerials and associated equipment, both of UK and continental manufacture. It's very obvious that they've gained a great deal of practical experience over the years,



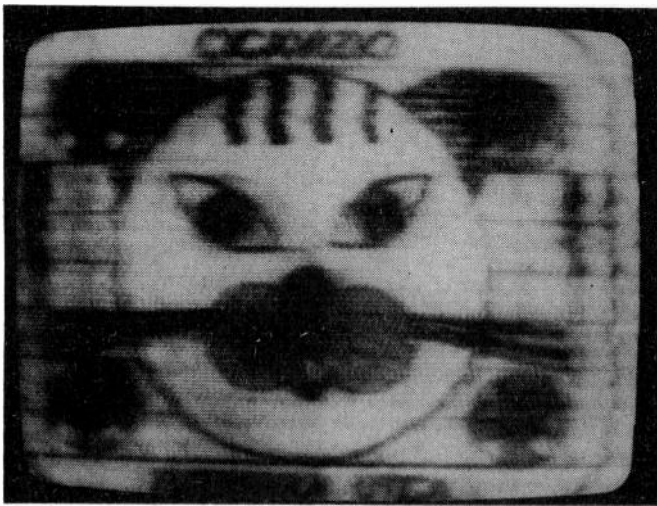The IBA's new electronic test pattern, which is undergoing evaluation. A sixth set of frequency gratings has since been added - sinewaves, same frequencies as Test Card F.



Italian "free" TV test card received by D. F. Browne.

and are consequently well qualified to advise upon and undertake even the most difficult reception projects and installations. Aerials stocked include the wideband v.h.f. Antiference MH308 and MH311. An aerial rigging crew specialises in large masts and rotor systems. Enquiries should be accompanied by an SAE.

From Our Correspondents . . .

We've had a vast pile of mail this month! Cyril Willis (Cambridge) sent in a long list of tropospheric successes at u.h.f., using a group A aerial with a Labgear 6040/WB amplifier, feeding a 22in. Pye colour receiver and an Ekco monochrome dual-standard set. Though Cambridge is low, he managed to resolve Dutch and French signals.

Des Walsh (Co. Tipperary) reports that he's received ch. 40/43 signals from Cairn Hill, a distance of some 140 miles, at up to $50\mu\text{V}$, despite intervening hills. Des is using a Wolsey Colour King and suggests that much of the signal is due to diffraction. Apparently reception in the Cork area is more difficult, due to it's suspected to the more rounded hills there than the rugged Tipperary terrain. Des goes on to say that in December 1977 Harlech TV signals at about 860MHz were received along the Waterford coast, from the NE. This is above any allocated frequency at present, and could possibly have been the result of activity by a commercial relay company. The signals were "very clear".

Garry Smith (Derby) has received the normal electronic RTVE (Spain) test pattern, but including a black bar. Since the reception was on ch. E3, it's thought that the signal could have come from the Canary Islands, the pattern relayed via Intelsat 4a with the Madrid time removed (the Canary Islands' time is an hour later than mainland Spain).

Finally Derick Browne (Portslade) reports a most remarkable reception, on July 8th on ch. E3 for about two minutes, at 1925. He thinks the signal was from an Italian "free" transmitter (see accompanying photo) as the test card is not one of the recognised ones.

Interference

In a recent column I went into the subject of electrical interference in some detail, including arcing from thermostat contacts. It's been pointed out that Radiospares have a reasonable selection of mains suppression and contact filters, one of particular interest being called a "contact suppressor". This is a small, encapsulated component containing an $0.1\mu\text{F}$ capacitor and a 100Ω resistor in series, with a maximum voltage rating of 250V

a.c. The filter is connected across the switch, relay contacts etc. to suppress interference caused when switching reactive loads.

Varicap Tuners

Quite a number of v.h.f., u.h.f., and v.h.f./u.h.f. varicap tuners are now available, and selection of a suitable one for DXing can be a confusing business. Regular advertisers Sendz Components seem to have a vast number of tuners, many of Telefunken manufacture. Those I've obtained from them have generally proved to be extremely useful, a good example being the "new v.h.f. varicap tuners covering 49-219MHz". These were apparently made for use in Australian receivers, and normally cover chs. E2-4 and up to 110MHz in Band I (ideal for sweeping through the European Bands I/II), and approximately 135-225MHz in Band III. Excellent value at £1.50. Sendz can usually supply a circuit on request with order, and exchange faulty units.

The first Mullard varicap tuner with full Band I/III coverage was the ELC1042, which requires a 12V i.t. supply and Band switching voltage and an 0.3-28V tuning supply. A noise figure of 7dB in both Bands is quoted, with power gains of 20dB and 22dB in Bands I and III respectively. Signal handling capability without overloading is 20mV in Band I and 13mV in Band III. The later ELC1042/05 has a slightly improved performance, with a 2dB higher Band III power gain.

The Mullard V311 is a late production v.h.f. tuner featuring improved overload performance, lower noise and a higher gain at 25dB in Band I and 26dB in Band III.

The Mullard u.h.f. range is larger. The partner to the ELC1042 is the ELC1043, which requires the same supplies. The later ELC1043/05 has a 2dB higher gain at 22dB and an average 1.5dB lower noise figure at 6.5dB. The /06 version has a lower gain than the /05 due to the i.f. output coil being damped by a 680Ω resistor. The overload figure is given as 15-20mV compared to the 8mV of the original ELC1043.

The new U321 u.h.f. tuner features pin diodes for gain control. It's designed for good overload performance, and can handle in excess of 20mV throughout the range. The average power gain is 22dB with a noise figure of 7dB. The U321-LO is similar but modified for use with digital tuning systems. The U322 is also similar but has a higher gain at the h.f. end of the u.h.f. band - a 26dB power gain is quoted at ch. E69. For further details of these new tuners see Part 2 of the colour receiver project elsewhere in this issue.

Undoubtedly the most sought after Mullard varicap tuner for DX purposes is the ELC2000S, though it's usually difficult and expensive to obtain. The ATS-6 satellite was received here at Romsey using one of these tuners, the other tuners available here not quite reaching 860MHz. The coverage is 47-88MHz in Band I (ideal for Sp.E, covering all channels from E2 to IC inclusive), 170-230MHz in Band III, and 470 to over 860MHz at u.h.f. The supply voltages required are the same as for the other Mullard tuners. The power gain in Band I is 29dB, Band III 28dB, u.h.f. low 32dB, high 33dB, and the noise figures are 6.5dB in Bands I/III and 9.5dB at u.h.f. Altogether a reliable, high-gain tuner which I thoroughly recommend.

FET Circuits

Our Abu Dhabi correspondent Allan Latham recently sent in a couple of interesting circuits using f.e.t.s. They've proved to be most successful apparently. The masthead amplifier (see Fig. 1) uses a dual-gate, n-channel MEM680 to give wideband Band I coverage. My own previous

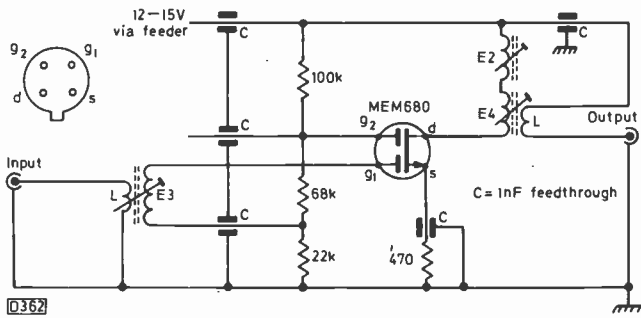


Fig. 1: Wideband f.e.t. amplifier covering chs. E2-4 inclusive. Coil data: E2 12 turns, E3 10 turns, E4 eight turns 24 s.w.g. close spaced $\frac{1}{4}$ in. diameter. L 3 turns wound at dead end. For non-masthead use connect earthy end of output coupling coil to chassis. Observe normal v.h.f. constructional practice.

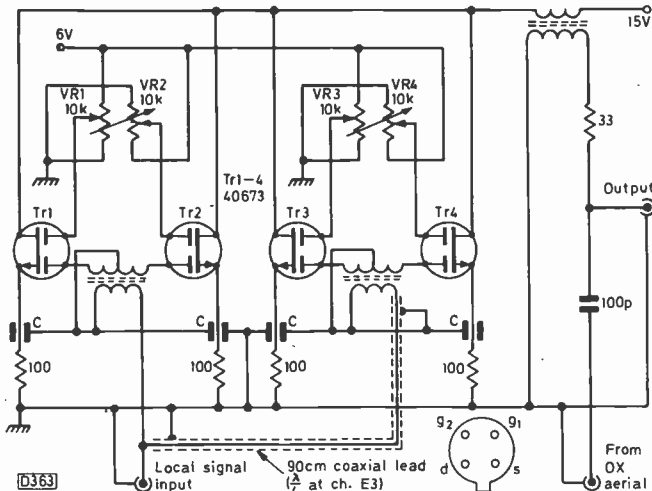


Fig. 2: Electronic phasing unit for Band I use. Coils wound on ferrite beads, primary 3 turns, secondary 5 turns with centre taps where indicated.

experiments using E300 f.e.t.s revealed that they worked well in the narrow-band mode but didn't like wideband operation. Allan's circuit with the double-tuned load seems to work well however - the power is fed to the amplifier via the downlead.

The second circuit (Fig. 2) should help all those Band I enthusiasts plagued with "interference" from a strong local signal. Previous experiments feeding a phasing circuit with the signal from the DX aerial (containing both the DX and local signals) and a signal from an aerial orientated for maximum local signal pick-up, adjusting the phase and amplitude of the latter so as to cancel out the local signal picked up by the DX array, met with fair success but needed careful adjustment for good results - while any rotation of the DX aerial meant that the phasing unit's two controls required retuning. The circuit Allan has devised is by all accounts a successful electronic equivalent using f.e.t.s and providing easy tuning with carbon potentiometers.

Basically, the local signal is fed to two balanced pairs of 40673 dual-gate n-channel f.e.t.s, with a 90° phase shift in one feed, the ganged potentiometers (of the type used for stereo amplifiers) being used to adjust the gain and phasing relative to the signal from the DX array. The result is virtual elimination of the unwanted signal, with very easy adjustment. Allan comments that he's used the circuit with great success over many months, but wishes to stress that it's purely experimental. We'd like to hear from anyone who tries it. Adjustment to phase out the local signal takes only a few seconds.

WE OFFER A UNIQUELY HELPFUL AERIAL SERVICE TO PUBLIC AND RETAILERS. WE WILL ADVISE, RECOMMEND AND EXCHANGE EQUIPMENT. WE GUARANTEE ALL CONTINENTAL AERIALS FOR FIVE YEARS FAIR WEAR & TEAR 10% OFF AERIAL MAIL ORDER SALES ONLY.

9" x 4" S.A.E. Dept TM for mail order lists. For specific advice please phone or call.

LONDON AGENTS FOR FUBA & PLEMI

Stockists of the finest aerials available in Britain:

FUBA TV & FM aerials (W.Ger.)
PLEMI TV aerials (Hol.)
UKW FM aerials (E.Ger.)
ANTIFERRECE TV & FM aerials (U.K.)
JAYBEAM TV & FM aerials (U.K.)



The fabulous golden anodised FUBA XC391

We specialise in Rotator & DX work.

ASTRA (D.I.Y.) AERIALS

A friendly family firm. Now Established 24 years

D.I.Y. AERIAL SPECIALISTS FOR ALL DOMESTIC TV & FM RECEPTION

Weather exposed part of U.K.? Scotland, Wales, West Country etc. Gales, salt air corrosion problems? Want to install your aerial and forget it? The continental aerial range from Germany and Holland having proved so fantastically successful, we are in future recommending continental aerials (especially Fuba) as our first choice for customers. In short we offer quality in a plastic age. Anodised against corrosion, guaranteed for five years, robust, high gain, easy to assemble, eye-catching superb aerials, what else, in truth could we recommend?

AERIALS & PARTS EXCHANGEABLE UNTIL SATISFIED. BONA FIDE TV/FM TRADE. COUNTER SALES ONLY.

Over 3,000 aerials stocks: All Bands: Masts: Lashings: Wall Brackets: Rotators: Televertas: Diplexers and Triplexers: You can now mix Band 4 and Band 5, or lower Band 5 with higher Band 5, or mix FM with either, 1.5db loss approx.: Padded outlets: Directional splitters: Coax, white or brown: 300 ohm cable.

Many of our customers come from recommendation.

53 WHITEHORSE ROAD, CROYDON, SURREY.

Nr. Gloster Pub & Garage
Open 9.00-5.30 MON-SAT.
Closed 12.30-1.30 But Open ALL day Sat.
Tel: 01-684 4300
01-684 5262
24 hr. answering service

FM & TV AERIALS AND ROTATORS ON DISPLAY

LOOK!

Phone: LUTON, BEDS. 38716

OPPORTUNITIES TRADE SALES

START AT £25 INC. VAT!!

FOR D/S COLOUR TV's

G.E.C., Philips, Murphy, Decca, Ferguson

S/S COLOUR TV's

Philips, G.E.C., Telefunken, Decca, Ferguson

FROM £40 INC. VAT!!

MONO TV's, all makes from £5 INC. VAT

SQUARE SCREEN, all models £12 INC. VAT!!

Deliveries arranged if necessary.

HUNDREDS OF SETS EACH WEEK TO BE DISPOSED OF AT GIVE-AWAY PRICES.

OPPORTUNITIES

9A, Chapel Street, Luton, Beds.

LUTON 38716

9.30-6.00 p.m. Weekdays, 10.30 1.00 p.m. Sundays.

Colour Receiver Project

Part 2

Luke Theodossiou

Introducing the signal board

FOLLOWING last month's very simple power supply board, we now get our teeth into some real circuitry. For a while the author was tempted to design a modular signal board – there's such a big song and dance about modules these days. The idea was finally rejected on the grounds of expense and unnecessary complexity. It's true of course that modular construction makes for more instant servicing – but only if you have replacements ready to hand: how many constructors would be prepared to go to the trouble and expense of building spares? You should have no difficulty in servicing the design adopted however. By the end of the project you should also be so familiar with the circuitry and layout that diagnosis and cure will be fairly simple should faults develop.

The board we start to deal with this month contains the signals side of the receiver. It takes the aerial signal and delivers R, G and B outputs to drive the c.r.t. cathodes – also an audio signal to drive the speaker. It could be called a "five-in-one" panel, i.e. tuner, i.f., chroma decoder, video output stages and sound channel. We'll try to describe the circuit in a logical manner (allowing for the author's shortcomings), starting with the tuner.

The tuner

The tuner was first mentioned over a year ago as a new product from Mullard, destined eventually to replace the ELC1043 and its derivatives. The new unit, the U321, is smaller than its predecessor, boasts improved performance, and has already put in an appearance in the Philips G11 chassis and the ITT CVC40 16in. portable chassis. We'll probably see more of it elsewhere in the future. Since we haven't to date described the unit, a fairly close look at it is in order.

R.f. stage and a.g.c.

The circuit is shown in Fig. 1. The r.f. stage consists of a BF480 high-current, low-noise transistor which is preceded by a pin diode attenuator using two BA379 diodes (D7004 and D7005). The receiver a.g.c. system controls the current through these diodes, which behave as a virtually linear u.h.f. attenuator. Current flows out of the tuner and is "sunked" by the TCA270S i.c. in the detector module. At maximum a.g.c. current (this is externally limited to 9mA), D7004 is hard on, while D7005 is switched off (high

impedance). This results in minimum attenuation and therefore maximum gain. As the current decreases, the d.c. bias on the diodes is such that at minimum a.g.c. current (1mA) D7004 is switched off and D7005 is hard on. This shunts the signal to earth via C2007, and leads to minimum gain.

Signal handling

Since signal attenuation occurs at the input of the tuner, the signal handling capability is increased compared to previous designs in which the gain of the r.f. amplifier was controlled by the a.g.c. potential. There's a dip in the in-band cross-modulation characteristic however, due to the influence of the BF480's emitter current variations – the emitter is d.c. coupled to the pin diode attenuator to optimise the a.g.c. characteristic. Overall, the cross-modulation performance of the U321 tuner is something like ten times better compared to other tuner units in current use. This is a direct result of using a pin diode attenuator and a high-current r.f. stage.

Mixer stage

The oscillator is conventional, using a BF480 (Tr7002) transistor and its associated components. The mixer stage is somewhat unusual though. It uses a Schottky diode, type BA280 (D7006). The conventional transistor mixer can suffer from signal handling problems due to its non-linear characteristic. The result is poor cross-modulation performance. Using a diode improves the performance but results in a conversion loss (unlike the transistor mixer, which is why the latter is normally used). In this design, the loss is made up by the additional common-base i.f. amplifier stage built around the BF324 transistor (Tr7003). Note that there is no d.c. return path for this transistor – it's provided by R410/R412/L411 in the vision gain/selectivity module. This arrangement makes the output circuit more flexible so that it can be readily interfaced with a variety of i.f. strip designs. Needless to say, tuning is performed by varicap diodes.

Incidentally, the Schottky barrier diode (to give it its full title) may be a newcomer to some readers. It consists of a semiconductor (silicon) to metal rectifying junction which eliminates charge storage effects since the offending semiconductor junction capacitance is not present. Other properties include a lower forward voltage drop, which results in lower power dissipation, low reverse leakage current and fewer reflection problems.

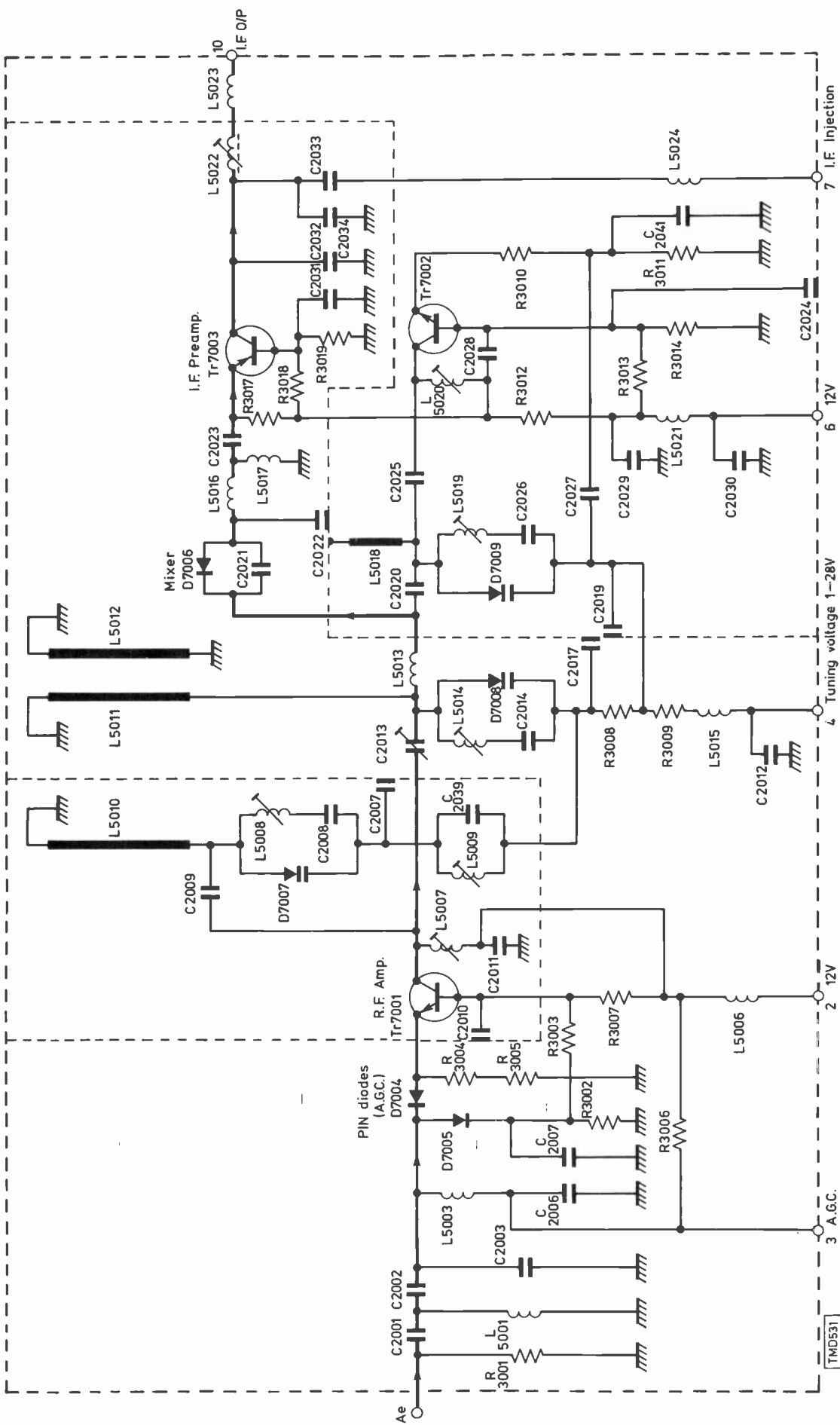


Fig. 1: Circuit diagram of the Mullard U321 tuner. The bold line shows the main signal path, whilst the dotted lines indicate metal screening.

Last month in the components list for the power supply we neglected to mention the regulator i.c.s: IC1 is a 7824 and IC2 a 7805. They are each mounted on a 10.5° C/W heatsink (FS Components stock no. 401-964). Most of the connectors we have used in the project are the Molex 0.2in. p.c.b. mounting types. They come in strips which can be very easily cut to the required number of ways. The reference no. is 3003-x, where x is the number of pins. We have found that the 15-way is probably best, since it results in little waste. We shall deal with the mating connectors when we come to the interconnections.

The i.f. output from pin 10 of the tuner is directly coupled to the Philips vision selectivity and gain module (from the G11 chassis). This and the following vision detector module are prealigned, ready-made units and were chosen for a number of reasons. First, using these units cuts out all i.f. strip alignment, making the construction of the signal board wholly uncritical. This would not have been so had we decided to design our own i.f. strip, even if a surface acoustic wave filter (SAWF) had been used. The detector, a.f.c., 6MHz attenuator and 4.43MHz subcarrier trap would still have needed setting up – and the first two of these adjustments are very critical. A glance at the signal board circuit (Fig. 3) shows the simplicity of the i.f. strip as a whole.

Secondly, since all alignment has been dispensed with, consistent receiver performance is assured. If the board is correctly built, the least that can be guaranteed is that a video signal will be present at the output of the i.f. strip – in many cases both sound and a picture should appear on switching on, without any adjustments whatsoever. This would not have been the case if the constructor had to build his own i.f. strip!

Thirdly, the author loathes winding all those damn coils! If coils had been bought in they would have been rather expensive – also the signal board would have had to be larger to accommodate a “flat-on-your-back” i.f. strip p.c.b. design.

The modules win!

Overall then, and not forgetting their reasonable price, these modules offer the constructor distinct benefits, while the quality of the signals is very good. We understand that Philips are in the process of updating the two modules, with the incorporation of a SAWF and an up-to-date i.f. i.c. Should this happen, the new modules are likely to be plug-in replacements for the current ones. As soon as we have more definite information on the introduction of the new modules we will let you know. There's no need to wait for the new modules on performance grounds however, as we don't

think they will offer any improvement. We believe that the aim of the exercise is to simplify production, since the performance of the current circuits is very high indeed.

Selectivity and gain

The circuit of the vision selectivity and gain module is shown in Fig. 2. It's quite conventional, consisting of a medium-gain, three-stage amplifier with little selectivity. The first two stages are choke-capacitor coupled, the final stage being RC coupled to the synchronous vision demodulator i.c. in the following module. The bandpass response is determined mainly by the selectivity filter between the tuner and the i.f. amplifiers. The i.f. coil in the tuner is part of the selectivity filter.


Forward gain control is applied to the second i.f. amplifier stage. The a.g.c. crossover characteristic is modified by the action of the external zener diode D1, which is used to “catch” the i.f. gain control voltage.

Vision detector

The amplified i.f. signal appears at pin 17 of this module and is directly linked to pin 1 of the vision detector module. The circuit for this module is shown in Fig. 4. The signal first passes through a double bridge-T filter which rejects the channel 1 vision and sound carriers which can be picked up by the vision selectivity and gain module (due to the use of untuned gain stages) in areas of high signal strength such as Crystal Palace.

The TCA270S i.c. is too well known to warrant much comment. Suffice to say that it produces both negative- and positive-going video signals; an a.f.c. signal; and i.f. and tuner a.g.c. signals. There are two quadrature coils, L626 for the vision synchronous demodulator and L630 for the a.f.c. synchronous demodulator. The a.g.c. detector is gated by negative-going line pulses which are fed in at pin 16 of the module.

Fig. 2: Circuit diagram of the i.f. selectivity and gain module from the Philips G11 chassis.

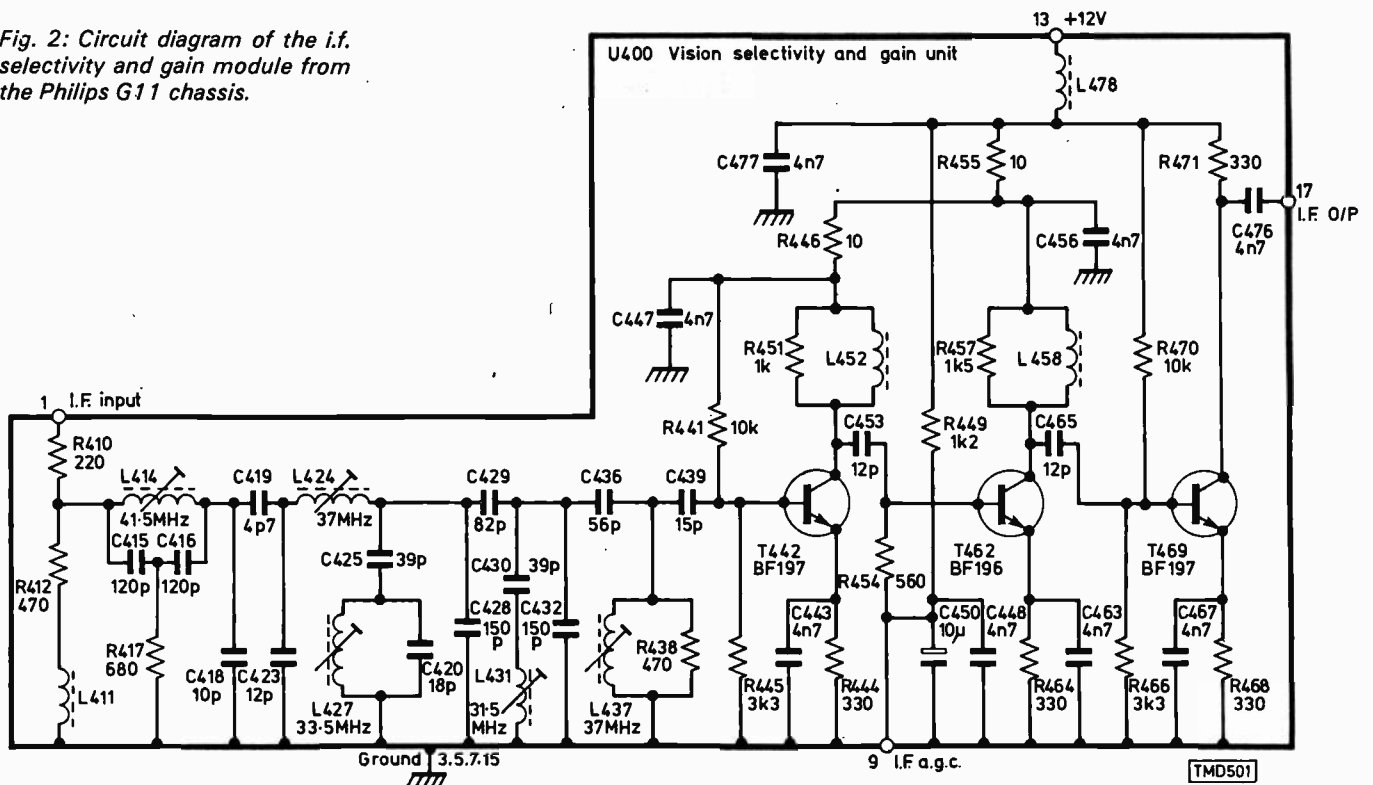

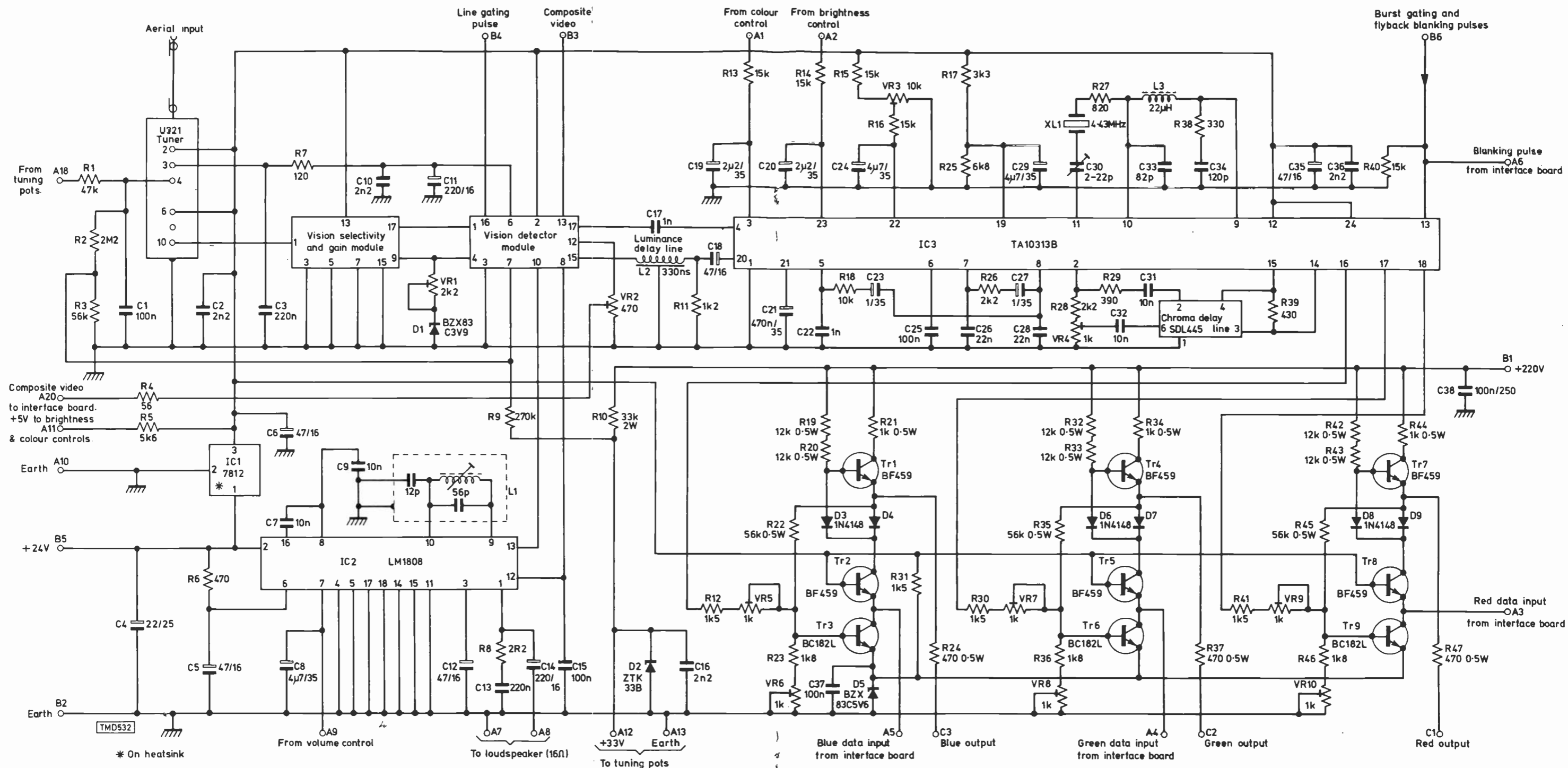


Fig. 3: Complete circuit diagram of the signal board.

The positive-going video signal appearing at pin 9 of the TCA270S passes through a 6MHz trap (L641) to remove the intercarrier sound from the video signal which is then applied to the emitter-follower T653. The load resistor for this stage is R654, which must be removed from the module before this is soldered to the p.c.b. The reason for this is that the Tifax module we shall be using to decode the teletext signal needs a positive-going video signal whose amplitude must be adjusted between 1V and 3V peak-to-peak to obtain optimum performance from the data slicer circuit on the Tifax module. We therefore remove this resistor and replace it externally with a 470Ω preset (VR2). The operation is quite straightforward, but be careful with the soldering iron as the module's component density is very high. The connection from the emitter of T653 is brought out to an unused pin (pin 12), using an insulated wire.

From this point the signal goes two ways. First through a high-pass filter consisting of C651 and L650, which removes the sync pulses and luminance signal. The resultant chroma signal is then applied to the emitter-follower T668, appearing at pin 17 of the module. It's then coupled to the luma/chroma processor i.c. (IC3) via C17.

Luminance

Secondly, from the emitter of T653 the video signal passes through R661, after which the 4.43MHz trap C656/C657/L658 removes the chroma signal, then through R665, the resulting luminance signal appearing at pin 15 of the module. It's then applied to the luminance delay line. Note that the series combination of R661 and R665

matches the delay line impedance, so no external matching resistor is necessary.

The tuner a.g.c. voltage appears at pin 4 of the TCA270S, then at pin 6 of the module. After decoupling at both low and high frequencies by C11 and C10 respectively, it's limited to 9mA by R7, further decoupled by C3 and applied to the tuner. The a.g.c. crossover point is determined by VR1.

A.f.c.

The a.f.c. voltage appears at pin 7 of the module. The centre point voltage is determined by the potential divider consisting of R3 and R9 from the +33V stabilised tuning supply. With the values used, this is 6V; i.e. when there is

no a.f.c. correction voltage from the TCA270S, this is the reference a.f.c. voltage. When the i.c. provides a correction voltage, the reference voltage either increases or decreases (depending on the output from the i.c.) and this information is added to the tuning voltage via R2. The "fierceness" of the a.f.c. action is determined by this resistor.

The negative-going video signal from the TCA270S appears at pin 13 of the module. This is connected to the sync separator i.c. on the timebase board.

6MHz extraction

The 6MHz intercarrier sound signal is extracted from the video signal by a top-coupled bandpass filter, using

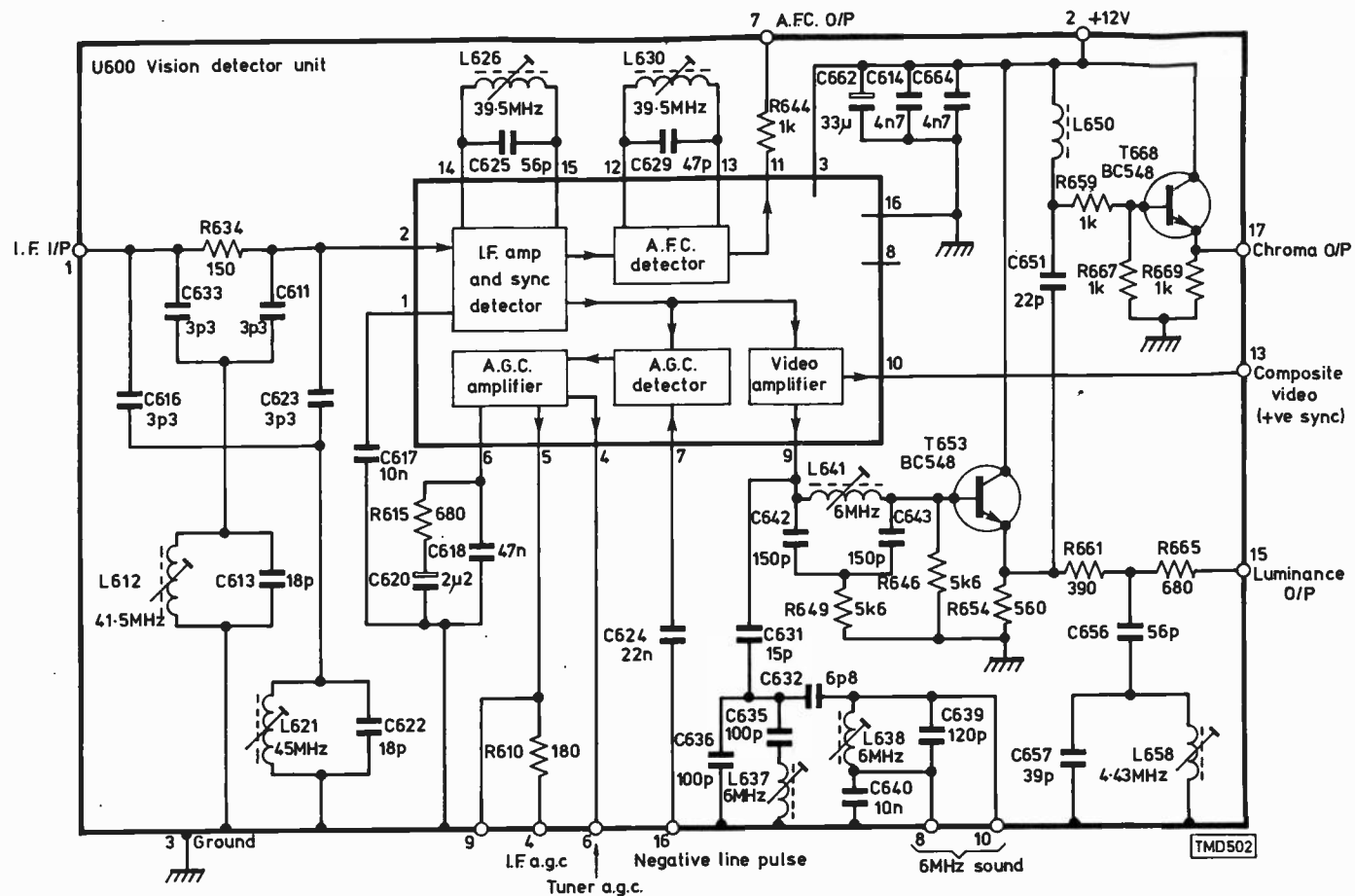


Fig. 4: Circuit diagram of the i.f. vision detector module from the Philips G11 chassis. See text for details of minor operation required to enable teletext reception.

inductors L637 and L638. The primary of this filter also incorporates a broad 4.43MHz notch filter. The 6MHz signal appears at pin 10 of the module. Pin 8 of the module is decoupled, both inside the module by C640 and outside by C15, and is at the same d.c. potential as pin 10 (via L638). This potential is used to provide bias for pin 13 of the LM1808 sound channel i.c. (IC2), coming from pin 12 of the i.c.

The LM1808

The sound channel i.c. has been described in a previous issue of *Television* (see December 1976) but a brief mention is included for completeness. There are a number of such i.c.s now on the market, but we chose this particular one for two main reasons. First it uses the least number of external components; secondly it doesn't need a heatsink.

A block diagram of the device is shown in Fig. 7, while Figs. 5 and 6 show the circuits of the i.f./detector and the power amplifier sections respectively. The i.c. provides a minimum of 2W output (although the typical figure is 3.5W) which we considered ample for all domestic listening conditions. The i.f./detector section is very similar to the LM3065. The main difference is in the volume control circuit, which is now a linear function of the volume control potentiometer (a logarithmic potentiometer is therefore required).

The audio power amplifier is similar to that of the popular LM380. Both short-circuit and thermal protection are featured, so it's pretty difficult to destroy (the author managed it once though!). The device is housed in a standard 18-pin d.i.l. package. The main reason for the very

low external component count is that the power amplifier has fixed gain, which is certainly an advantage when one of the prime objectives is to produce a simple design.

Audio quality

Some purists may disagree with the author's view that 2W is adequate. More to the point, the limitations of a speaker housed in a TV cabinet certainly degrades the audio quality. Two options are possible to obtain improved results. One is to include a socket so that an external speaker can be connected. If a standard DIN socket is used, the internal speaker will be disconnected when the plug for the external speaker is inserted. The other possibility is to extract the audio signal after the detector and feed it into the auxiliary socket of your hi-fi system.

Extracting an audio signal

Around 500mV of audio is available at pin 8 of the i.c. It should be connected to an amplifier input whose impedance is 47k Ω or greater. Two points here. Unfortunately the signal level at pin 8 is determined by the volume control (it cannot be extracted prior to the volume control circuit). Secondly, the use of a screened cable is essential, but the results may still be poor. The reason for this is that the timebases of the receiver cause high peak currents to flow through the receiver's earthing system. This can give rise to all sorts of additions to the audio signal. These are not normally audible through the receiver's speaker, but when the signal goes through a hi-fi system all the warts start showing. This approach has not been tried



SOLUS, the name on the finest colour picture tube.

With the co-operation of 'TELEVISION' and R.C.A. Solus offer the most advanced 110° PIL colour cathode ray tubes to all readers who join the magazine's colour receiver project. Solus will deliver either the A67-611X or A56-611X direct to you. Please send either a Cheque or Postal Order direct to:

SOLUS (ELECTRONICS) LTD.,
KIRKWOOD ROAD, CAMBRIDGE CB4 2PF.

The A67-611X costs £128.00 + £16.00 V.A.T. Total £144.00.
The A56-611X costs £98.00 + £12.25 V.A.T. Total £110.25.

Tubes are covered by a 1 year guarantee which can be extended to 4 years for a single payment of £9.00 plus 12½% V.A.T. (current rate).

Solus also supply a comprehensive range of quality colour tubes, monochrome tubes, valves, multipliers, integrated circuits, semiconductors, tuners and other components to the trade.



It had to happen... the NEW 1000 series

a new generation of easy-to-use, economy line scopes offering the flexibility that you the customer demanded and from who else but Telequipment, world leaders in low cost scopes.

Before introducing the 1000 series, we conducted an intensive market survey throughout Europe, the results of which were analysed by our engineering and marketing teams; from this a definite set of parameters emerged. These have all been embodied in our new 1000 series.

A choice of bandwidth: 10 or 15MHz, 5mV sensitivity at full bandwidth and 1mV sensitivity at 4MHz and a choice of modes; Algebraic Add, true X-Y, and X5 gain switching; remember we told you it was flexible.

Easy-to-use: this it certainly is; note the minimum number of controls on the front panel, probably less than any other competitive scope available and, of course, all colour coded for easy reference.

Easy-to-read: note the five inch CRT.

Easy-to-service: primary circuits are constructed on only three boards in a "u" configuration. The amplifier and time base boards pivot around the regulated power supply making for excellent accessibility. Wherever possible, standard commercial components have been utilised throughout, simplifying acquisition.

Lightweight: only 8kg (approx. 17.5lb).

Reliable: here we have called on our many years' experience in the manufacture of low cost scopes. Components are rated in excess of their required values. Automatic insertion and testing reduces human errors. Flow soldering ensures maximum reliability of soldered joints.

Low cost: just check our price list and remember there is a lot more to cost than just the price.

We made it happen, so if you would like to know the full spec., send for our colour leaflet.

TELEQUIPMENT

Tektronix UK Ltd., PO Box 69, Coldharbour Lane, Harpenden, Herts.
Tel: 05827 63141. Telex: 25559. Regional Offices: Dublin 500979, Livingston 32766,
Maidenhead 71555, Manchester 061-224 0446
Also available from Electroplan Ltd., PO Box 19, Orchard Road, Royston, Herts.
Tel: Royston 41171

Tektronix UK Ltd., P.O. Box 69, Coldharbour Lane, Harpenden, Herts. AL5 4UP.
Tel: Harpenden 63141.

Name _____
Company _____
Position _____
Address _____

Telephone No. _____

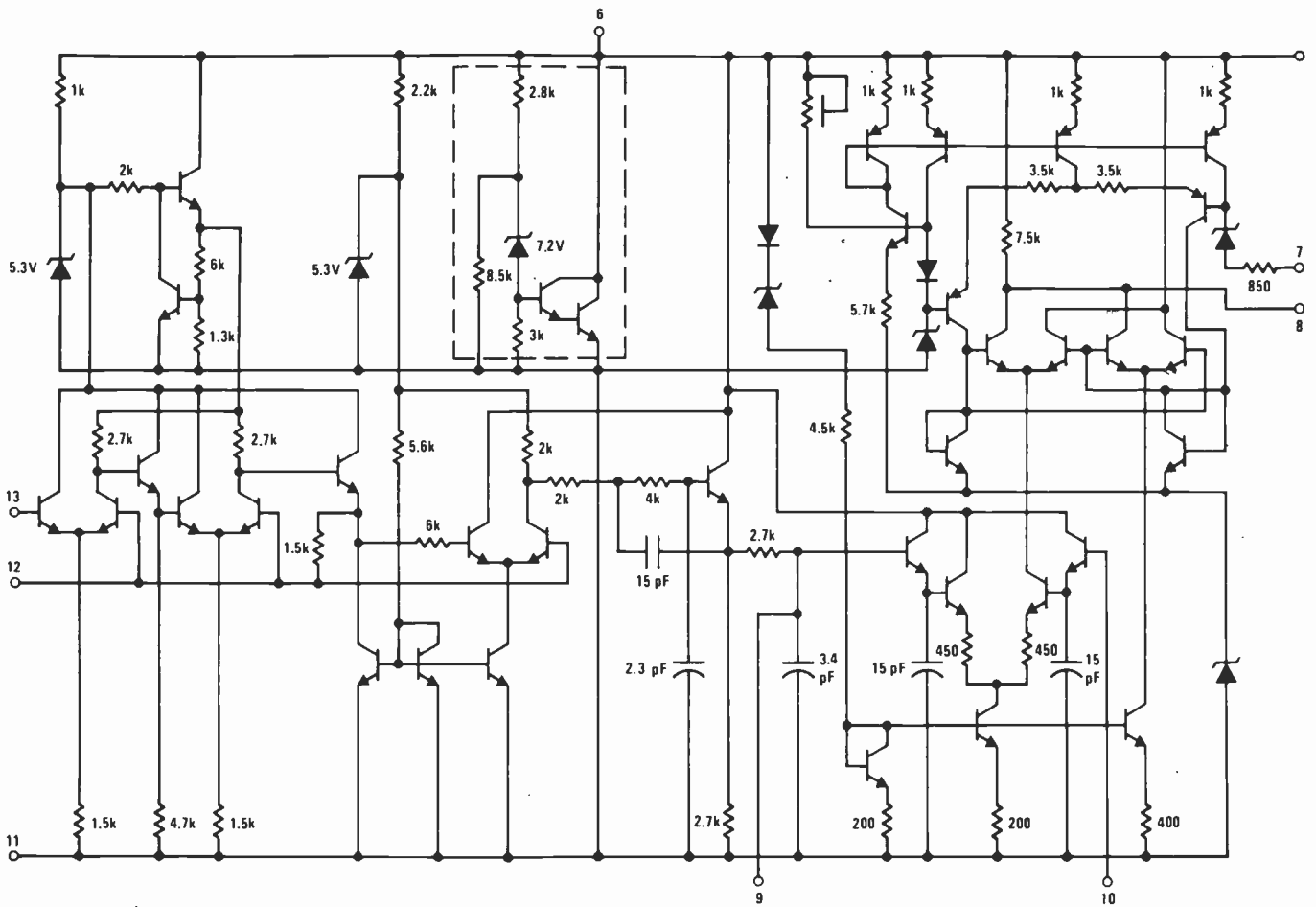


Fig. 5: Circuit diagram of the i.f. amplifier, detector and volume control sections of the LM1808 sound channel i.c.

by the author, but he would be interested to hear from any reader who may finally manage it. Incidentally, the positioning of the cable will prove critical, as will the position of the socket. This second method cannot be used unless the set is isolated from the mains.

Capacitor C9 provides de-emphasis; the audio signal is coupled to the power amplifier via C7. Resistor R6 feeds the i.f. section of the i.c., whose supply is stabilised around 11.5V (pin 6). The network comprising R8 and C13 ensures

h.f. stability.

Supply Rails

All the small signal circuitry runs on +12V, which is provided by IC1 from the +24V rail used for the audio power amplifier of the sound channel i.c. The +33V tuning voltage is stabilised by regulator diode D2 from the +220V video supply rail via dropper R10.

Note that the RCA TA10313B decoder chip is still a development device. The decision to start quantity production has unfortunately been delayed, and it may therefore be necessary to use an alternative solution. The situation is being reviewed at the time of going to press.

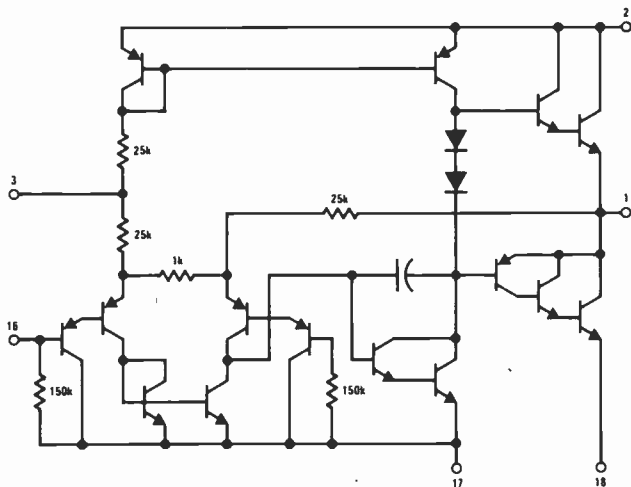


Fig. 6: Circuit diagram of the audio power amplifier section of the LM1808. This is very similar to the LM380.

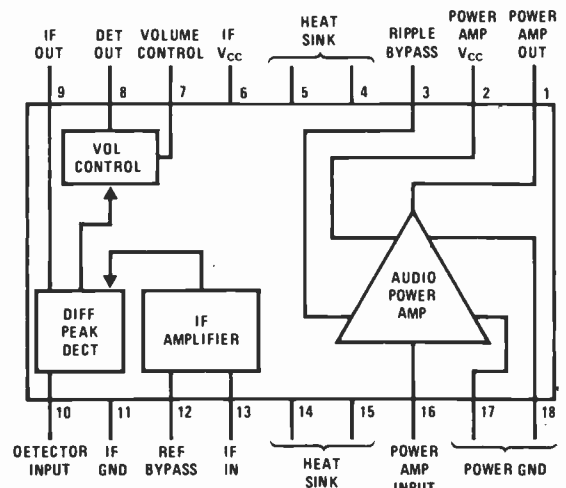


Fig. 7: Functional block diagram and pin-out of the LM1808.

Twisted Tails

Les Lawry-Johns

WE'VE had hot Pyes and burning Bushes, but the one we came across the other day takes the cake (Alfred's). You could call it a cooked up cake.

A nice young lady came in to pick up a few bits and pieces and casually mentioned that the next time she passed she would pop in a portable TV set which had been involved in a fire and could possibly be of some use for spares.

Sure enough, a couple of days later she popped in and left a twisted mass of plastic with us. Unfortunately, we didn't know her name or address and just accepted the mangled mass as a kind of burnt offering. When time permitted, we did a cut away job to see what was left inside. Much to our surprise the inside was practically untouched and was obviously almost new. If the on/off knob had not been welded to the front panel it could have been used.

Carefully arranging the component pieces on the bench we switched it on and everything functioned as it should, so we thought it worthwhile ordering a new cabinet from the makers.

On the phone this proved to be somewhat more difficult than we had anticipated. We explained that the set had been in a fire not of its own making, and that the complete outside shell was required.

A verbal tussle then ensued. We would have to specify exactly which parts were to be ordered. I never, in my ignorance, realised how many bits and pieces go to making up the cabinet of a portable TV set. Each piece was the subject of earnest discussion and apparently would be dispatched separately. So far four pieces have arrived, and by the time the rest have been accounted for the postage and packing will have cost more than the new one of the same type we have for sale. It would also appear that somehow we have ordered two of each piece!

Anyone want a £70 portable for £140?

We are never without a hybrid Pye colour receiver for very long. The report on this one said that for some time there had been a sparking noise from the back, the picture had been blurred and that finally there was lots of smoke and off it went.

Inspection showed that the long gondola type focus unit (697 chassis) was just a mass of twisted plastic which could not be separated from the VDR rod inside. This had broken anyway (hence the sparking from the rear, as the excessive voltage hopped across the focus spark gap with the slider wire contacting the rod above the break . . . I think). The final demise came when the first anode supply $0.1\mu\text{F}$ decoupling capacitor shorted and the associated $100\text{k}\Omega$ resistor cooked, as usual.

Replacing these items necessitates access to the component side of the panel, and a glance down inboard of the line output transformer showed R203 (the $47\text{k}\Omega$ reference pulse integrating resistor) to be in no fit state to be left in. In fact it just crumbled to dust when touched, so how the line hold had been locked we'll never know.

With these itmes in we were ready to check through the rest of the supply lines. These seemed to be in order. We could not check the thing however because we were out of the long VDR focus units. Phoning around proved that Don, Ray, Fred and Harry didn't have one either, which meant a delay.

Ever the impulsive type, we decided to hook up one of the square, thick-film types to a point of lower potential.

Now I don't know if you've ever looked at the tripler units used in these Pye group hybrids, but one of the three outlets is marked "focus" and connects to C226 on the transformer. Connecting the high end of the thick-film focus unit to this point, the centre to the focus lead and then earthing the low end produced just the right potential. The set was back in action and fit to fight another day.

Nothing to do with TV (as usual), but what is the answer to this one?

We ordered and received from a wholesaler some clock radios (UK made). One when unpacked was obviously not new, and on close inspection the guarantee card had been filled in and dated December 1977. We contacted the wholesalers (and their rep) who said they would collect it. Some time later they did. Some further time later a replacement was received. When unpacked, it proved to be the same set with the same filled in guarantee card.

We again contacted the wholesalers. "Good Lord" they said. "Fancy that!"

Will you collect it and supply us with a new one or give us a credit note for it?" we asked.

"Well, it's not really our pigeon. It's really between you and the makers you know. We have a directive from our head office that our responsibility ends when we have supplied goods to the dealer."

"Second-hand goods?" we queried.

"As far as were were concerned, all goods supplied by us are new."

So we thought about this and taxed the rep on his next visit. He said he knew how it had happened. When his branch were out of stock on some items they obtained them from another. It was obviously not intentional on their part, but they had sent one which had previously been returned to the makers for service by them instead of by the dealer who had given the customer a new set instead of loaning them one until their own was returned.

This left one used set which was now with us, and still is. The makers say they have discharged their obligations and have serviced the set, and that it is up to the wholesalers to put things right.

Back on the phone to the wholesalers who have now closed the branch where we obtained the set and are no longer trading in this part of the country. . . . Anyone want a new-used clock radio?

We called upon some friends to put their set right — an ageing ITT/KB VC4 used as a second set but still in mint condition except that the picture was dark and lacking width. Whilst we worked on the set, the lady of the house (a

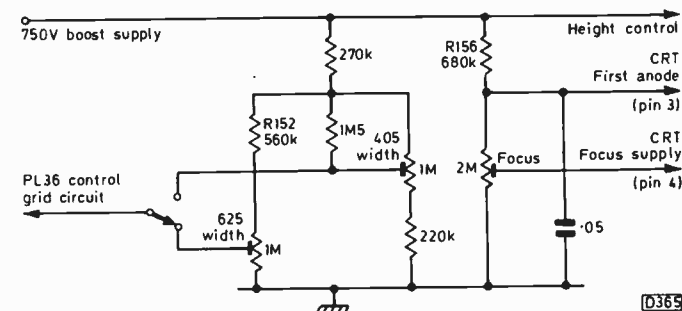


Fig. 1: Boost supply feeds in the ITT/KB VC4 and similar dual-standard monochrome chassis.

PHD COMPONENTS
RADIO & TV COMPONENT DISTRIBUTORS
UNIT 7 CENTENARY ESTATE
JEFFRIES RD ENFIELD MIDDX
MAIL ORDER ONLY TELEX 261295

ALL COMPONENTS PRICED EACH
(INCLUSIVE OF VAT AT 12½%)
NO MINIMUM ORDER CHARGE
PLEASE ADD 50p POST & PACKING

**SPECIAL OFFER OF DIRECT REPLACEMENT PARTS. ALL PARTS GENUINE
 MANUFACTURERS PARTS AND BRAND NEW.**

GEC MONOCHROME 2000

AUTOVOX 2282

Description	Manuf. Pt. No.	Price	Description	Manuf. Pt. No.	Price
VHF/UHF TUNER	M96981	4.00	LOPT	—	6.00
SCAN COIL	—	2.00	DECODER PANEL	3431 0443	12.00
TIMEBASE PANEL	M96772	4.00	DÉGAUSSING PANEL	3431 0497	2.50
LOPT	94209	3.00	SOUND O/P PANEL	3431 0414	5.00
MAINS DROPPER	27837	0.55	POWER SUPPLY PANEL	3431 0494	7.50
ELECTROLYTIC 200-200-150-50		2.00	COMPLETE CONTROL UNIT	2138 0301	3.75
			FIELD T/B O/P PANEL	3431 0499	6.25
			CONVERGENCE PANEL	3431 0503	4.25
			IF TUNER ASSEMBLY	3431 0495	9.00
			TRIPLER	—	5.00

formidable character henceforward referred to as “our Glad”) worked on the dog, an inoffensive black spaniel named Soot. In fact the set responded to our labours quite well, which was a good deal more than Soot did a short time later.

The lack of width turned out to be due to no more than a high-value resistor (R152, 560kΩ, see Fig. 1) in series with the 625-line width control, while the dark aspect was due to low voltage on the tube’s first anode (pin 3 – there was also low voltage on the focus pin 4 with the control fully up). Following the supply lead back, we came to R156 which is a 680kΩ resistor going to the boost line. This had also gone high, and being in series with the focus control (to chassis) the result was that the voltage available at the top of the focus control had got lower and lower as R156 went higher and the focus control’s value remained the same. So in went another 680kΩ resistor and the set then gave a full-width picture with plenty of brightness to spare.

While all this was going on, our Glad laboured with Soot.

The idea was to comb out the tangled fur and clip off the surplus. Soot was becoming more and more anxious as Glad approached his rear end, and when Glad picked up the scissors his nerve snapped. It’s one thing to have your sensitive areas combed, but when they are in danger of being clipped it is time to take action.

Giving a yelp of protest, Soot made for the door but found it closed. With his back to the door he prepared to do battle. He was not going to give up his vital organs without a fight. Glad was not used to dissent in the ranks however.

“Come here you stupid hound” she bawled in a voice which nearly shattered the windows. At the sound of that familiar trumpet Soot’s courage deserted him. He slunk

back to the spread newspapers and Glad’s clutches. Just then Glad realised that I was ready to go.

“Sorry Les” she hollered. “This dozy dog made me forget you. How much do I owe you?”

I told her, but apparently her purse was in the kitchen.

“Hold on to him for a minute love she said more quietly. “Comb his ears or do something to keep him happy. They need clipping too.”

So off went Glad and I soothed Soot.

“Has he got beautiful ears then?” I murmured, combing the long silky ears. “Does he want the naughty fur cut off? Yes, ’course he does.” Being an expert on dogs, I grabbed the scissors and snipped at the long fur.

Soot gave an almighty scream and belted off dripping blood all over the carpet. At the same time I was surprised to find that as well as the fur I was also holding about half an inch of Soot’s left ear in my hand.

Glad grabbed Soot as he shot through the kitchen and her scream rent the afternoon air.

“Ahhhh, Ahhhh, look at his bleeding ear. You’ve cut the end off.”

I stood struck dumb for a moment, desperately searching for words.

“Er, well, you have to clip their ears Glad. Otherwise they dangle in the dirt and pick up all sorts of things: a vet told me.”

Glad glared at me in disbelief. “You’re supposed to clip the fur, not the ear, you bloody fool. Poor old Soot’s going to look lop sided now until his fur grows.”

“Sorry Glad, sorry Soot.” And with the score at one TV set repaired and one dog with a clipped ear (neither chargeable) we beat a hasty retreat. Anybody want their dog groomed?

Tr7. If the slider voltage is below this value both these transistors will be switched off, and although Tr5 is biased "on" no current will flow via the LED. As the potential rises above 0.6V, Tr6 will conduct and the LED will start to glow, increasing in brightness as the potential increases further. At around 1.2V (the sum of the forward voltage drops across Tr7 and D3) however Tr7 will start to switch on. Tr5 thus starts to switch off, depriving the LED of current. A point of maximum brightness occurs, and this can be used to indicate the exact tuning point.

In practice the emitter potential of Tr6/7 varies with the setting of VR1 and VR2, as does the rail (A) supplying the display circuit with a constant 5V. The setting of VR3 determines the point at which the LED lights.

Modifications

The prototype was built solely to provide a tuning voltage and a display, the other supplies needed for the tuner being available within the receiver. It would be a simple matter to derive a 12V supply from the 50V rail, together with a 0-8V "manual a.g.c." voltage, if these are not already available. Similarly, the 50V supply obtained from a transformer in the prototype could possibly be obtained from the receiver's own supplies, reducing the cost considerably.

When provided with adequate heatsinks, Tr3 and Tr4

can dissipate up to 11W. With the circuit values shown it's possible to drive many more than the twelve display circuits used in the prototype. A quick calculation suggested a limit of around 400 (well you never know - you might need them!!!) providing only one LED is lit at any time.


Construction

The method of construction is not critical. In the prototype the power supply section and the display circuits were built on two separate printed boards, but there's no reason why Veroboard should not be used throughout. The unit was built into an aluminium box, with the tuning voltage output available from a socket at the rear. Tr1, Tr3 and Tr4 should have heatsinks fitted.

Whether a separate transformer is used or the 50V rail is obtained from the receiver, all circuits *must* be isolated from the metal case which should be earthed.


Setting Up

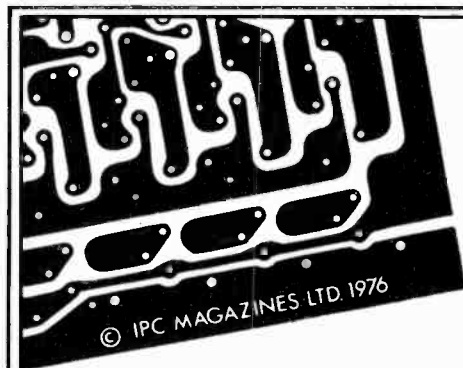Once the power supply has been built it should be tested by monitoring the tuning voltage output whilst varying VR1 and VR2 to check that the full tuning range is available. The displays are set up by tuning in the appropriate channel and adjusting the relevant preset (VR3 etc.) for maximum brightness of the associated LED. ■



All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.

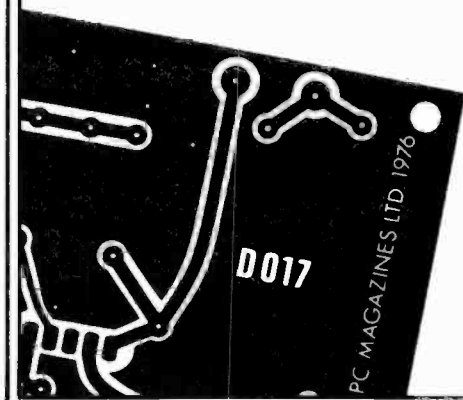Any correspondence concerning this service must be addressed to READERS' PCB SERVICES LTD, and not to the Editorial offices.



TELEVISION

READERS PCB SERVICE

Issue	Project	Ref. no.	Price
November 1976	Ultrasonic Remote Control	D007/D008	£2.95 per set
December 1976	IC Sound Circuits for the Constructor	D009	£1.25
		D017	£1.25
Jan/Feb/March 1977	TV Pattern Generator	D018 + u.h.f. mod. board	£3.90 per set
March 1977	Teletext Decoder Power Supply	D022	£2.95
May 1977	Teletext Decoder Input Logic	D011	£9.80
May 1977	Single-chip SPG	D030	£3.00
June 1977	Wideband Signal Injector	D031	£0.65
June 1977	Teletext Decoder Memory	D012	£7.90
July/Aug 1977	Teletext Decoder Display	D013	£8.00
July/Aug 1977	TV Games in Colour	D034	£3.80
August 1977	Logic State Checker	D038	£1.50
September 1977	Teletext Decoder Switch Board	D021	£1.25
September 1977	Teletext Decoder Mother Board	D027	£4.00
September 1977	Touch Tuning System	D051/D052	£4.00 per set
October 1977	Teletext Decoder IF Board	D041	£6.00
December 1977	Monochrome Portable Receiver	D032	£15.00
Feb/March 1978	On-Screen Clock	D045	£6.50
April/May 1978	CRT Rejuvenator	D046	£2.50
May/June 1978	Test-Pattern Generator	D048	£8.50
Aug/Sept 1978	Diagnostic Pattern Generator	D051	£8.00
October 1978	Colour Receiver PSU Board	D052	£3.50

To:— Readers' PCB Services Ltd. (TV), Fleet House, Welbeck St., Whitwell, Worksop, Notts.

Please supply p.c.b.(s) as indicated below:

Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME _____
 ADDRESS _____
 Post Code _____

The Language of Logic

Part 2

E. A. Parr, B.Sc., C. Eng., M.I.E.E.

IN Part 1 we introduced the basic ideas of electronic logic, and explained how the basic circuitry used operates. We also saw how basic electronic logic systems operate. Since the groundwork has now been covered, the most compact way of taking the subject further is by way of a dictionary of terms used in electronic logic.

To keep within limits we've kept to common terms, omitting the more obscure and rare ones. Inevitably there's a lot of cross-referencing to other terms in the dictionary and Part 1. Cross-referenced terms are set in italics.

Access time: A measure of the performance of a *store* such as a *ROM* or *RAM*. It's the time between applying the *address* to the address lines until the data is available at the output lines.

Accumulator: A collection of *flip-flops* used to store one binary *word*.

Adder: A device or circuit for adding two binary numbers (see main text).

Address: In a *memory* such as a *RAM* or *ROM*, data is stored in the form of *words* (usually multiples of four bits). Each word is held in a specific location, which has a unique address. See Fig. 1.

The memory uses binary addresses, but it is usual to use *octal* or *hexadecimal* for convenience.

The address of a location is very similar to a postal address.

Analogue-to-digital converter (ADC): A device for converting an analogue signal to a digital form suitable for processing by a digital circuit. There are three main types of ADC, ramp, successive approximation, and parallel conversion.

A ramp converter is shown in Fig. 2. A free-running oscillator feeds a counter which in turn feeds a *DAC*. The counter cycles from 0 to full house, generating a ramp

output from the *DAC*. The ramp voltage is compared with the input voltage, and when the two are equal the counter state is gated into the output *latches*.

A successive approximation converter asks a series of questions, each of which reduces the range in which the voltage can lie. Suppose we have an input voltage range of 0–10V, and our voltage is 6V.

First question: "greater than 5V?"

Yes. Most significant bit is 1.

Next question: "greater than 7.5V?"

No. Next bit is 0.

Next question: "greater than 6.25V?"

No. Next bit is 0.

Next question: "greater than 5.625V?"

Yes, Next bit is 1.

Next question: "greater than 5.9375V?"

Yes. Next bit is 1.

Next question: "greater than 6.09375V?"

No. Next bit is 0.

And so on, each time halving the range in which the voltage can lie. This somewhat complex process is summarised in Fig. 3. The logic of a successive approximation ADC is obviously more complex than a ramp type.

Finally we have the parallel converter. This is a sledgehammer technique with the input voltage being fed to a bank of comparators. The logic sees which comparators are turned on and sets the corresponding output bits. See Fig. 4. Note that eight comparators are needed for a three-bit output. For a four-bit output 16 comparators would be needed, for five bits we would need 32. Parallel converters get complex and expensive for high resolution.

Important parameters of an ADC are resolution (the smallest voltage step we can recognise), conversion time (the time to get a result) and cost. Obviously there is the usual engineering trade-off.

Type	Resolution	Speed	Cost
Ramp	Medium (8 bits 0.5%)	Slow (10mS)	Low
Successive Approximation	Excellent (14 bits 0.01%)	Medium (1µS)	Medium
Parallel	Poor (5 bits 3%)	Very Fast (0.1µS)	Expensive

ADCs are widely used to convert TV signals to digital form for digital transmission between studios and transmitters.

And gate: A logical gate. See Part 1

ASCII: American Standard Code for Information Interchange. An eight-bit code for transmission of alphabetic, numeric and control characters. It uses seven data bits and one *parity* bit for *error checking*.

Asserted: A quick way of defining a particular digital signal. If we have a digital signal that represents oil level,

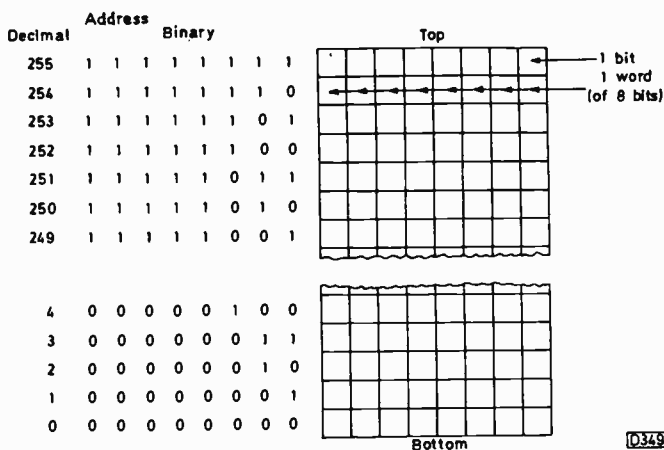


Fig. 1: A 256-location store, each location holding an eight-bit word.

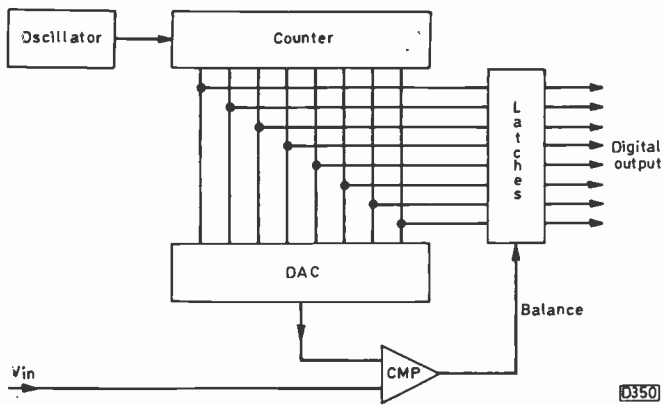


Fig. 2: Block diagram of an eight-bit ramp ADC.

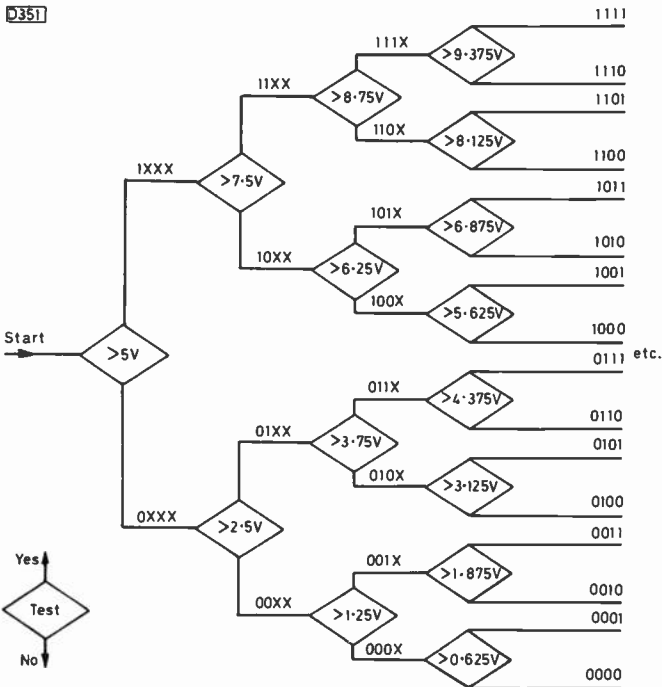


Fig. 3: Operation of a successive approximation ADC.

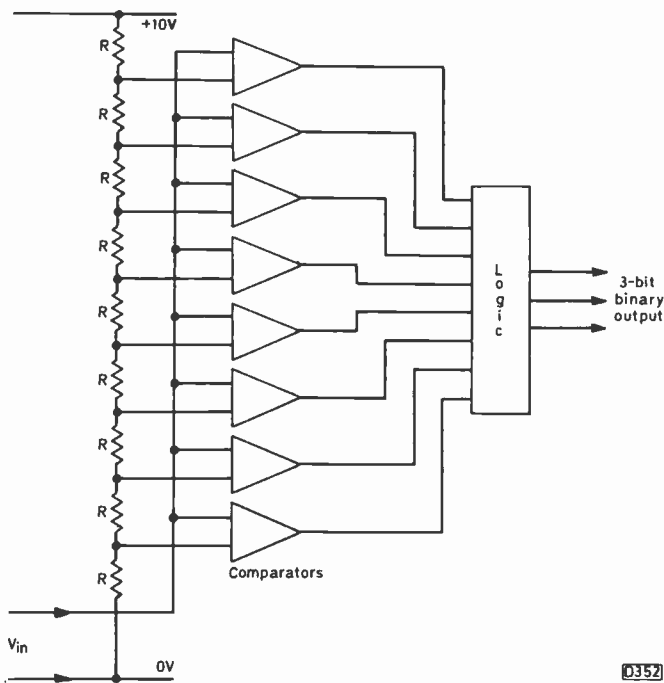


Fig. 4: The parallel ADC.

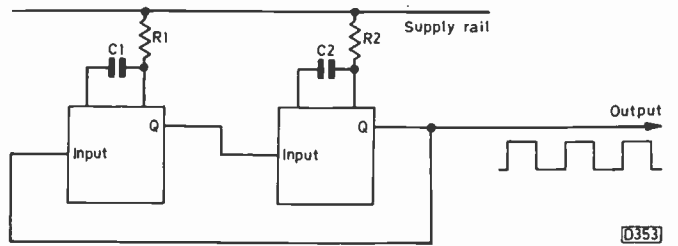


Fig. 5: Two monostable i.c.s connected to form an astable oscillator.

say, and is a 1 for oil level low, we describe the signal as "oil level low, 1 in the asserted state."

Astable: A digital oscillator giving a continuous stream of 1 and 0 signals. See Fig. 5. The astable can be made from a conventional multivibrator, or two *monostables* connected as shown.

Asynchronous: Large digital systems can be asynchronous or *synchronous*. In a synchronous system all operations are performed at a regular rate controlled by a central *clock* which acts like an orchestra conductor. In an asynchronous system each part of the system does its own thing in its own time, and there is no synchronisation of operations.

Baud: A measure of the speed of a digital transmission network. A baud is a rate of one-bit/second. A 300 Baud line can thus pass 300 bits per second.

Binary-coded decimal (BCD): BCD is a halfway house between our decimal system and pure binary. Each decimal number is encoded into a four-bit binary number, e.g.:

4	0	5	9
0100	0000	0101	1001

the resulting BCD number being 0100000001011001.

BCD is a slightly inefficient use of digital techniques. A true binary representation of 4059 is 111111011011 which uses 12 binary digits as opposed to the 16 of BCD. BCD is useful though where the digital logic is required to do only simple arithmetic operations (e.g. channel displays).

Note that each four binary bit group in BCD can only assume states 0000 to 1001. States 1010 to 1111 representing 10 to 15 are not allowed.

Binary: A number system based on base two. States 1 and 0 are the only states allowed, hence counting goes:

0	1	2	3	4	5	etc.
000	001	010	011	100	101	etc.

See Part 1 for further details.

Bistable: A circuit having two stable binary states. See *flip-flop*.

Bit: A shorthand way of writing binary digit, i.e. a signal with only two possible states, 1 and 0.

Buffer: A store for a binary *word* (which is usually 1, 4, 8, 12, 16, etc. bits long). A buffer is an isolating device, and stores a word between devices such as an *ADC* and the rest of the system.

Bus: A shorthand version of busbar. In digital systems a binary signal goes to several places, e.g. an *adder*, a *RAM*, an *ADC* and an output device. These are all connected by a common ribbon cable called a bus, which carries all the

data. See Fig. 6. Signal flow along the bus is bidirectional, e.g. RAM to ADC and ADC to output. The actual transfer is controlled by the control logic. See *tri-state gate* and *open collector*.

Byte: A binary word of eight bits. Experience has shown that this is a convenient size for a binary number. A few years ago there was a suggestion that a four-bit word should be called a "nybble", but this was not adopted!

Clear. A term used with *flip-flops*. To clear a flip-flop is the same as to reset it, i.e. set $Q=0$ and $\bar{Q}=1$.

Clock: In a *synchronous* system, events are sequenced by a clock waveform which is connected to all units. The clock waveform is usually generated by an *astable* oscillator. See also *D-type flip-flop* and *J-K flip-flop*.

CMOS: A form of digital integrated circuit using integrated field-effect transistors (f.e.t.s). These are in theory the perfect digital circuits: they operate on a wide supply range (3-15V), have excellent noise immunity, and take a very small

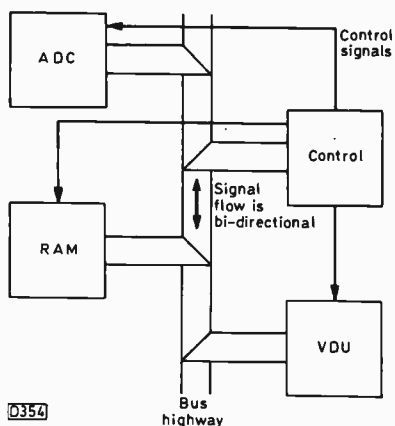


Fig. 6 (left): Digital system using a data bus.


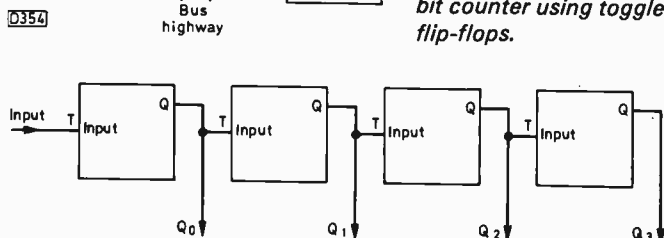


Fig. 7 (below): A four-bit counter using toggle flip-flops.

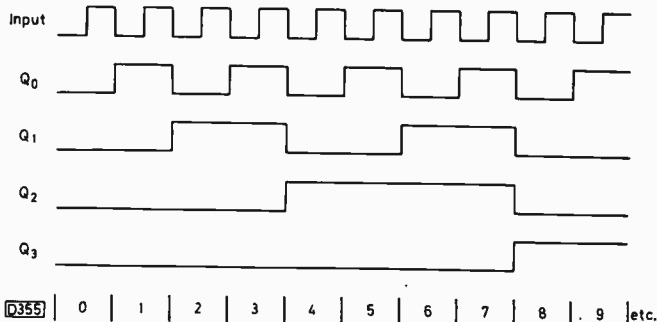

0 1 2 3 4 5 6 7 8 9 etc.

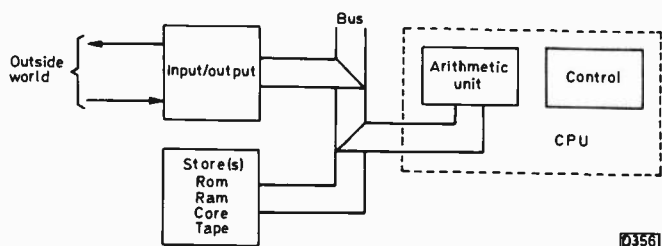


Fig. 8: Basic computer block diagram.

supply current (typically a few μA). In practice early CMOS acquired a bit of a bad reputation, as it was prone to die for no apparent reason. The cause of this was found to be static electricity. CMOS has an input impedance measured in megohms. As a result static electricity from nylon clothes or a soldering iron bit easily blasts a CMOS gate. This has now been cured, later CMOS having input protection. CMOS gates are designated by a 4 digit number in the 4000 range (e.g. 4016).

MOS stands metal-oxide-semiconductor, i.e. the f.e.t.s are of the insulated-gate type. C stands for complementary, i.e. both n- and p-channel devices are used.

Complement: (1) The \bar{Q} output from a *flip-flop* or *monostable* is sometimes called the complement output.

(2) The act of inversion is sometimes called complementing (see Part 1).

Counter: A binary counter in its simplest form is constructed from *toggle* flip-flops as shown in Fig. 7.

If the toggle flip-flops change state on the 1 to 0 edge, this simple circuit will count input pulses with the Q outputs showing the correct state. Note that Q_0 is the least significant end of the counter.

It's unusual to find a constructed counter in a digital system, as counter chips are available (usually a 4-bit counter, but chips can drive each other to give 8-, 12-bit counters).

The above counter is called a ripple through counter. Suppose we have a 4-bit counter and it holds a count of 7, i.e. 0111. We give it one pulse and the counter goes to 8, 1000, but along the way we get other numbers:

Q_0 changes to 0,	counter state 0110
this changes Q_1 to 0	0100
this changes Q_2 to 0	0000
this changes Q_3 to 1	1000 (final state).

For a very brief time, the counter gave an output of 7, 6, 4, 0, 8. In many applications this would not matter (the whole *glitch* probably lasts 10 nanoseconds) but if it's likely to cause trouble *synchronous* counters are available. These are glitch free.

Counters are available that can count up or down as desired, be preset, or count to bases of 10 (BCD) or 12.

CPU (central processor unit): A computer system has three parts (see Fig. 8). These are the store, the input/output interface, and the central control unit which does all the number crunching and control.

The central unit is called the CPU. In a *microprocessor* system, the actual microprocessor chip is the CPU. Other chips need to be added to provide the store and input/output interface.

D-type flip-flop: A form of *flip-flop* with two inputs, labelled D and Clock, and the usual two outputs Q and \bar{Q} , see Fig. 9. The operation is *synchronous*. The Q output assumes the same state as D when a pulse is applied to the clock input (see Fig. 10). Data sheets specify the polarity of the clock pulse.

Note that the D input cannot be allowed to change during the clock pulse. D-type flip-flops usually have S and R inputs as well (often labelled preset and clear, or load and clear).

Decimal: A number to base ten (see Part 1).

Decoder: A device for going from one number system to

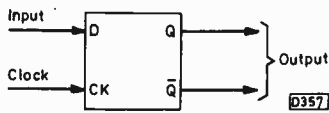


Fig. 9: D-type flip-flop.

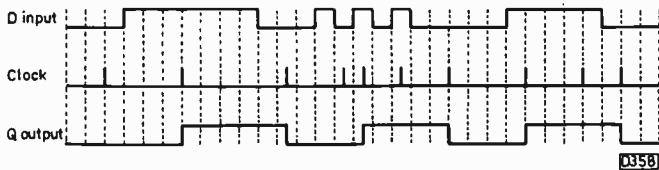


Fig. 10: How a D-type flip-flop operates.

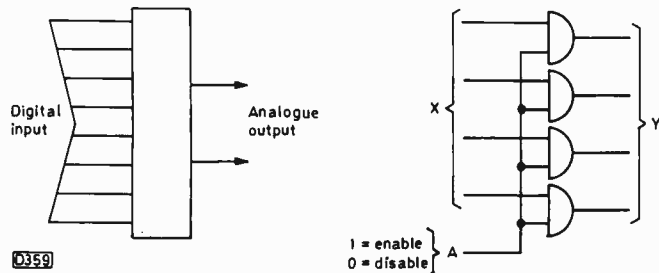


Fig. 11 (left): Digital-to-analogue converter.

Fig. 12 (right): Disabling or enabling a group of gates.

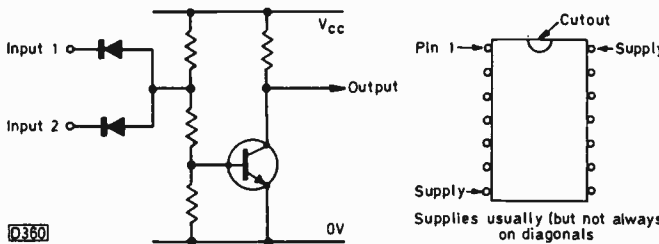


Fig. 13 (left): A two-input DTL nand gate.

Fig. 14 (right): The dual-in-line i.c. pack.

another. Usually the change is from binary to decimal. See Part 1 for details and encoders.

Decoupling: Digital integrated circuits operate at very high speeds (in excess of 20MHz). Combined with this we have 0 to 1 transitions measured in nanoseconds. The effect is to produce sharp spikes on the supply rails, causing subsequent problems with *counters* or *flip-flops*.

The conventional 10,000 μ F capacitor is of no use here, as it's the inductance of the supply leads that causes the trouble. The problem is overcome by liberally sprinkling 0.01 μ F capacitors between the supply and 0V. These are added at a density of one capacitor to two integrated circuits. *TTL* is particularly prone to supply problems, but liberal decoupling always works.

Decrement: To reduce by one. Thus 9 decremented is 8, and 1010 decremented is 1001.

Delay: Another term for *monostable*.

Digital-to-analogue converter (DAC): A device for converting a digital number (usually binary) into an analogue voltage (see Fig. 11). A DAC is thus the converse of an *ADC*, and the two together are used in digital transmissions of analogue signals (e.g. TV, telephone). A typical DAC is the Ferranti ZN425E i.c.p., which is widely available. Its data sheet is particularly informative.

Disable: To inhibit a gate or output. Usually applied where a common line goes to several gates (Fig. 12). A 0 on line A

disables the transfer of data from X to Y.

DTL: Diode-transistor logic. An early form of digital integrated circuit, not widely used today. Its internal circuit is along the lines shown in Fig. 13. Because the 0 to 1 transition at the output relies on a simple resistor, DTL is poor at driving capacitive loads.

Dual-in-Line (DIL): The official name for the familiar beetle encapulation used for digital integrated circuits – refers to the dual rows of in-line pins. DIL packs are available with a vast array of pins from four upwards. Pin 1 is always to the left of the package cutout (viewed from above). See Fig. 14.

Edge: Many devices are specified as responding to an edge signal, i.e. a transition from 1 to 0 or 0 to 1. *Counters* in general are typical devices behaving like this. A positive edge is a transition from the 0 to the 1 state, a negative edge is a transition from 1 to 0 (for positive logic).

Enable: To allow a gate or output. The opposite of *disable*.

Encoder: A device for converting a number (usually in decimal form) into binary form.

EPROM: An erasable *PROM*. This type of *PROM* can be changed, with some effort, by the user. The most common type of EPROM is cleared by flooding it with ultra-violet light through a transparent window in the chip. Once cleared, the chip can be reprogrammed.

Error checking codes: In digital data transmissions systems, noise can easily turn valid data into gibberish. To overcome this, check bits are often inserted with the data to indicate if an error has occurred.

The simplest error checking system is parity. We transmit the data in blocks of seven bits, with an eighth (parity) bit added. The parity bit makes the total number of bits in the eight bit word even (if even parity is chosen) or odd (if odd parity is chosen).

To see how this works, let us send the data stream 1011011101011011110110110100000110110010 using odd parity. We split this into blocks of seven, adding a parity bit each time.

Transmitter	Parity	Receiver	Parity	Check
1011011	0	1011011	0	OK
1010110	1	1010110	1	OK
1111101	1	Error 1101101	1	Wrong
1101101	0	1101101	0	OK
0000011	1	0000011	1	OK
0110010	0	0110010	0	OK

Error checking codes can be made far more sophisticated, allowing identification and correction of errors. Such codes are used in teletext.

Exclusive-or: A logical gate. See Part 1 for details.

Fan out: The number of gate inputs a gate (or other device) can drive is limited. The drive capability of a device is defined in terms of the unit loads it can drive: this is known as the fan out. Gate and other inputs are also defined in unit loads and this is known as the fan in.

For example, three D-type flip-flop clock inputs (each fan in 2) and two gate inputs (each fan in 1) can easily be driven from a gate output with a fan out of 10 since the total load is only 8.

TV Servicing: Beginners Start Here . . .

Part 14

S. Simon

WE should by now know what jobs the timebases do. The line timebase deflects the spot across the screen at a fairly high speed, then makes it fly back to the left-hand side at an even higher rate. Left to itself it would merely produce a white line across the centre of the screen. This would appear at very high intensity and would very quickly burn away the coating on the inside of the glass so that there would thereafter be a nasty dark line to forever record the event. This in fact is what can happen when the field timebase ceases to function. This timebase's job is to deflect the spot vertically twice for every complete frame (the two being interlaced, remember?). Dear oh dear you may say. If failure of the vertical scan concentrates the electron beam in the centre so as to burn the screen, what happens when both timebases fail? Surely the resultant laser like spot will push a hole clean through the glass, never mind the coating.

Not quite. The beam has lots of energy, but not enough to come through the glass. It could however completely burn away the coating in a split second, leaving a nasty spot at the centre of the screen. We say could. In fact this is not likely to happen as the line timebase is a maid of all work and supplies, along with other things, the final anode voltage (e.h.t.) for the tube. Thus line timebase failure means no e.h.t. and no beam. The only way in which an undeflected spot could appear is when the field and line deflection both fail although the line timebase continues to function. This would be the result if both sets of scan coils failed together

(unlikely), or if some donkey of an engineer left the deflection coils' plug out of its socket. But even here the makers often provide a safety link in the plug to disconnect the line timebase power (say the screen grid feed in the case of a valved circuit). Not all do however, so watch this point.

More often only one deflection is affected. So we can have a line across the screen to denote failure of the field scan, or far less common a line down the centre to denote that there is a failure of continuity from the line output transformer to the line scan coils. We say far less common though you will in fact come across this. It's usually the result of a poor contact between the line output transformer leadouts where they connect to the printed panel (perhaps marked by initial arcing), or associated with the series-connected scan-correction capacitor. So the rule in this event is to check the connections from the line output transformer to the scan coils and the capacitor and line scan coils for being open-circuit. These are the only causes of a vertical white line, as a failure earlier in the line timebase will result in a blank screen. O.K.?

Horizontal White Line

In the vast majority of cases if only a line can be seen it will be across the screen (east to west you might say). When this is encountered, take a closer look. If the line is straight, the fault is most likely to be in the oscillator/output section

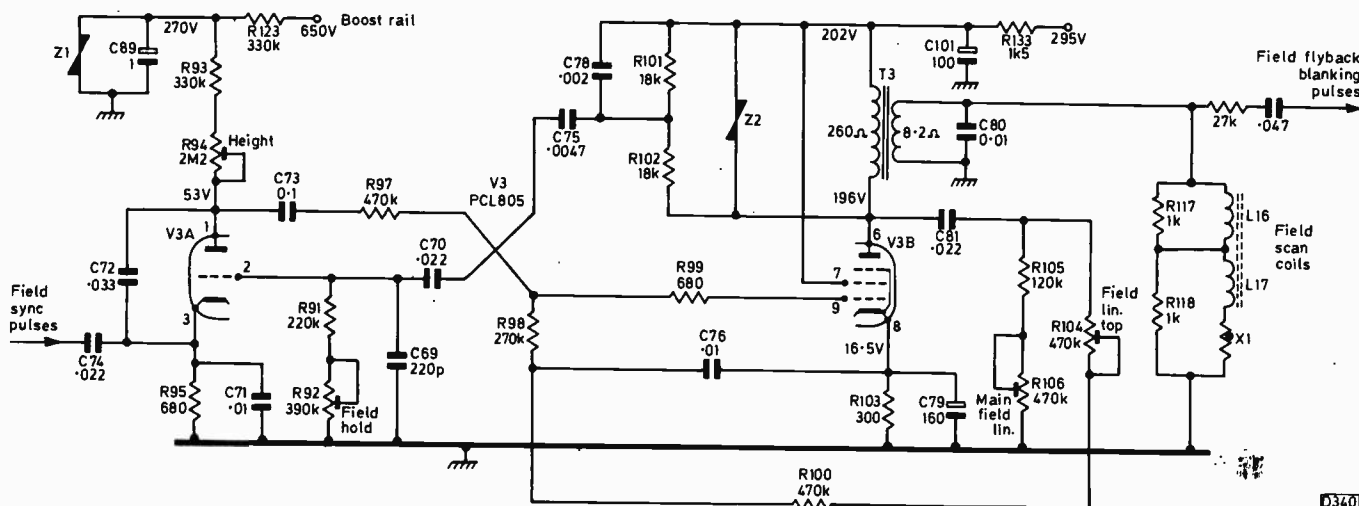


Fig. 1: The valve field timebase circuit used in the Thorn 1500 chassis. The negative-going field sync pulses are fed to the cathode of the oscillator triode section of the valve to ensure that it switches on at the right time to discharge C72. In many circuits you'll find the triode cathode connected direct to chassis, with the sync pulses applied to the control grid circuit of the pentode section of the valve, switching it off at the correct time to initiate the flyback. It's also common to find the earthy side of the field waveform generator charging capacitor connected to the cathode of the output pentode in order to provide a certain amount of linearity correction. In this circuit the same effect is achieved by returning C76 to the cathode of the output pentode. Feedback between the output pentode's anode and control grid is used to provide the main linearity correction, via C81, R104 etc. The feedback waveform is differentiated by C81/R105/R106, then integrated by R104/R100/C76, to achieve the correction required.

of the timebase. If the line has a distinct curve (a sort of depressed sinewave) however the first suspect must be the deflection coils themselves. These consist of two slabs connected in series with a little round disc thermistor (which corrects for the effect of temperature rise). Thus the fault could be an open-circuit in either winding or in the thermistor. Identify the windings, disconnect one end (to remove the shunting effect of the field output transformer secondary) and measure with an ohmmeter.

Scan Coil Identification

Identification of the windings is not difficult. The line slabs are at the top and bottom and are connected in parallel: two wires in (probably thick) and two scan coil connections to each with a pair to the top and a pair to the bottom. The field scan coils have two leads in (probably thinner), with one to the disc thermistor (tucked under a clamp?) and the other to a single lead contact. There is a double connection, but the supply leads do not connect to this as this is the series connection. The assembly may be complicated by resistors across these tags, but you should get the general idea.

Field Timebase Failure

If the horizontal white line is straight however we come to the ifs and buts. If the field timebase is valved (easier to deal with) there will be an output transformer, as in the case of the sound output stage, to match the high impedance of the output valve to the low impedance of the coils. We will deal with this arrangement first.

In a lot of sets the transformer is fixed to the printed panel, and this in itself is where the field collapse can originate. Careful examination may well show that the fixing is not all that it should be, and as the primary and secondary windings connect to the fixing pegs the search may be ended before it even got started. It's in the nature of a transformer to vibrate at the frequency at which it operates (a blinding glimpse of the obvious). This can result in fine cracks appearing around the soldered connections, and eventually all contact will be lost at this point. The process can be hastened by dropping the set. . . . It can be seen then that defects on the printed panel loom large in our quest for the cause of a horizontal white line.

The next step if necessary is to check the valve base voltages to ensure that the anode, screen grid and cathode voltages are right. We've already covered this part of the operation (valve amplifiers), so we shouldn't need to go into it in too much depth here. We will however repeat the salient points in relation to the common PCL805 field timebase valve found in most monochrome sets and some colour ones, e.g. the ITT CVC5, CVC8 etc.

We can again refer to the Thorn 1500 chassis where the output transformer T3 will be found at the top right side (check soldered contacts) and the PCL805 a little to the left and lower.

Two of the transformer contacts should have h.t. on them (the primary winding), one of these leading to pin 6 of the PCL805 valve base (anode), the other being the h.t. point from R133 which also feeds pin 7 (screen grid), see Fig. 1. If either or both voltages are absent the valve cannot start to operate. If there is no voltage at pins 6 or 7, check back to R133 which could be open-circuit. If pin 7 is about right at a little over 200V but the voltage at pin 6 is absent or very low, check up to the transformer contacts and, if these are intact, check the continuity of the primary winding as this

could be open-circuit. On a cold test the resistance should read about 260Ω.

The significant reading is at pin 8 (cathode). This records the voltage across the cathode bias resistor R103, which should have a value of 300Ω. Note that we said should. At the correct resistance value the voltage across this resistor (i.e. between pin 8 and chassis) should be 16.5V. If this figure is wrong, the valve could be faulty (assuming that the voltages at pins 6 and 7 are correct) or the resistor R103 could have changed value (which it does).

When faced with the fault of mainly top compression, most impulsive young men rush to the linearity control or circuitry when they should instead first check the value of R103. When it goes high you get top compression, when it goes low (less often) you get bottom compression. A 330Ω 2W resistor is O.K. as a replacement. More often bottom compression is due to the capacitor C79 drying up.

Once in a while one may well find that there is no or very little voltage reading across R103 (we are still looking for the reason for the horizontal white line), and although the h.t. may be present at pins 6 and 7 and the PCL805 itself has been checked the reason for the fault may begin to look illusive. A cold resistance check across R103 may show 300Ω, which means that capacitor C79 is not short-circuit (you thought it would be, didn't you?) and that the resistor is keeping its correct value.

At this point you should remember what we have said about capacitors. If one side of a capacitor is subjected to a positive potential (a positive dearth of electrons you might say) the other side or plate will become crowded with the little horrors: it's as heavily negative therefore as the other plate is positive. The electrons will stay where they are if they have nowhere to go (no d.c. path to discharge through). Now if the capacitor is C73, the control grid of the PCL805 pentode section (pin 9) will be heavily negative, thus cutting off the normal current flow through the valve. The discharge path is R97, R98, R100, R104, R105 and R106. If any of these items are open-circuit, the capacitor holds its charge and the control grid stays negative and there you have it. The fixed resistors are rarely at fault, but the preset linearity controls R104 and R106 are highly suspect and should be treated accordingly.

Oscillator Section

Now it's often the case that the output section is beyond reproach and is passing current (as denoted by the 16.5V across the bias resistor) but there's nevertheless a horizontal white line on the screen. In this event we must remember that an amplifier will amplify only if there's something for it to amplify (loud cheers). At this point we may pause for thought.

If the amplifier is willing to amplify, why not use this fact to prove that the output section and the scanning coils are in order? The output section control grid is pin 9 in the case of a PCL805. So, if we apply a signal to pin 9 there should be a variation of current through the output section of the valve and thus through the field scan coils. Ideally, this should be a 50Hz signal, and it's an amazing coincidence that this is exactly the frequency of the mains supply.

In earlier sets the heater line was derived directly from the mains, via dropping resistors. Therefore a capacitor of say 0.1μF could be touched from a heater pin (4 or 5) to pin 9, thus opening up the field scan and proving that the amplifier section is working. Where there's a diode in series with the heater circuit nearly half the a.c. waveform is snipped off, leaving a pulsed d.c. which in the 1500 series is later smoothed by C58 and C56 to provide a supply line for

the transistor stages. Even so, there's still a small ripple at the PCL805's heater pins and a capacitor from pin 5 to pin 9 will give an indication that from this point on the circuit is willing to work, given something to work on. Even a hand-held screwdriver blade will induce sufficient hum on the control grid to open up the scan slightly.

If this is so, we know that the driving force is absent. This force, applied to pin 9, should be in the form of a sawtooth voltage waveform.

Now there are many ways of producing a sawtoothed waveform. Imagine a steep approach to a cliff edge. You slowly plod up the slope, then fall straight off the top. You could say that the descent was much quicker than the ascent. Even so, it still takes time to meet your mangled end on the rocks below. Have you got the picture?

This is the shape of the current waveform required to push the tube beam (or beams in a colour receiver) from the top of the screen to the bottom. An even build up, then a sudden collapse to speedily induce the flyback to the top. Ah, you may say, what about all these magnetic fields which will want to build themselves up and collapse in the field output transformer when we don't want them to (a collapsing field induces another flow of current which induces another field and so on - ringing, you might call it). Well, this is what the VDR (voltage dependent resistor) Z2 is for, wired across the transformer's primary winding. The resistance of this device falls as the voltage across it tries to rise. So it damps the circuit's attempts to ring. Oil on troubled waters you could say.

Where were we? Oh yes. How to provide a waveform with a nice linear slope up and a rapid drop down. Well now, what about that capacitor we talked about just now. We could charge it up slowly, then discharge it quickly.

How to do this and at the right rate? Obviously the timing is of paramount importance. We need a resistor in series with the capacitor to slow down the charging rate, and the time the capacitor takes to charge will depend upon the resistance value of the resistor and the capacitance value of the capacitor (now look up $T = R \times C$ or something like that in any basic reference book).

Say we want to charge C72 through R93 and R94 (which is variable so that the charging rate can be adjusted). With V3A cut off, due to a negative charge on C70, C72 will charge up, the voltage at its "top end" rising evenly. This rise is passed on via C73 to the amplifier section (provided everything is working properly of course).

Once the voltage across C72 reaches the required figure, how do we rapidly discharge it? Well, we could have wired a neon across it so that at a certain level the neon would have "struck", conducting heavily and thus discharging the capacitor to produce the rapid fall in voltage. As a neon is none too precise in its action however we use a transistor or a valve instead, turning it on and off at the right time like an oscillator. In the 1500 chassis a valve, the triode V3A, is used.

How to turn it on and off? Well, you could use a transformer to couple the output back to the input to form a blocking oscillator, or two cross-connected transistors or valves to flip each other on and off (sorry, flipping one on and flopping the other off), or you could do much the same thing by taking part of the amplifier's output and feeding it back as is done in the 1500 chassis and many others.

You will observe two 18k Ω resistors (R101 and R102) with a connection from their junction feeding back through C75 to a timing circuit which consists of the capacitor C70 with R91 and R92, the latter being adjustable to enable the timing of the circuit to be varied. This variable resistor is termed the vertical hold, frame hold, field frequency or

something like that on various chassis, to denote that it varies the repetition frequency of the sawtooth. The size of the sawtooth thus generated is determined by the voltage applied to the charging capacitor by R94, which is termed the height, amplitude or vertical size control.

Now let's look briefly at the oscillator action. When V3A conducts (we'll come to how in a minute) C72 is discharged, the voltage at V3A anode falling sharply. This fall is communicated to V3B's control grid (pin 9) by C73, V3B thus being cut off. A positive-going voltage spike occurs at its anode, and does two things. It moves the spot rapidly to the top of the screen and, being communicated to V3A's control grid via C75 and C70, ensures that V3A turns on hard to discharge C72 fully. Now as we've seen before, when a valve is driven into heavy conduction, there's current flow in the control grid circuit. Hence the left-hand plate of C70 charges negatively, cutting V3A off again and holding it cut off until C70 can discharge via R91 and R92. This then is the timing action, that determines the "natural" repetition rate of the circuit's oscillatory action. Once C70 has discharged, V3A will switch on again. The potential divider R101/R102 determines the amplitude of the pulse fed back to the control grid of V3A to drive it into full conduction.

So there you are. Provided the components have the right value and keep the right value, the screen will be scanned at the right amplitude and at approximately the right frequency. The exact frequency is determined in the studio by the sync pulses inserted on to the transmitted signal. We talked about these last month. The field sync pulses are applied to pin 3 (triode cathode) of the valve to trigger it precisely - provided the coarse frequency setting (R92) is not too far out. If the circuit values are disturbed, the repetition rate will be outside the influence of the sync pulses and the picture will appear to roll rapidly. If on the other hand the sawtooth is not produced by this oscillatory action there will be no field scan at all and we are back to our horizontal white line. So what goes wrong and how do we tackle it when it does?

Checking the Oscillator Circuit

We have already proved the amplifier section, so this cannot be at fault. Or can it? Remember that it's also part of the oscillatory circuit, and that there are in the output stage components which determine what's fed back. Remember those 18k Ω resistors. These often change value, changing the field scanning rate and eventually causing complete field collapse. To check them, disconnect one end of one resistor and measure them both. The feedback capacitors C75 and C70 are not often at fault, and there are other things to check before these. The valve itself is most often at fault, and must come early in the checking list. This can also cause loss of field hold, particularly when the set is first switched on, i.e. the valve gets lazy and requires more time to reach its operating efficiency. If a new valve doesn't help matters, do the valve base voltage checks on pins 6, 7 and 8. If 8 is low, apply the meter to pin 9 and if this action opens up the scan suspect the linearity controls of being open-circuit as already described - the point here being that the meter itself has provided a d.c. return to chassis to "unblock" V3B's control grid.

Having ensured that the amplifier section voltages are right, check at pin 1. This is the triode anode, and the reading here should be about 50V. That is, it should be about 50V if the oscillator section is working. As we have said, the capacitors in the timebase proper don't often give trouble and it's better to concentrate on resistors if the valve is not at fault. The resistors must include the 18k Ω ones

mentioned above (R101/R102), also the height control if this has a healthy 270V at one end and precious little at the other.

If the oscillator has stopped due to some other reason (say a mangled vertical hold control, damaged by an irate user merely because the 47k Ω sync circuit resistor R44 has gone high and left the timebase floating), the triode will pass excessive current and as a result the voltage across R93, which is in series with the height control, will increase considerably, leaving a reduced voltage at both ends of the height control, thus removing suspicion from this component. Let's give this a little more thought.

A non-working oscillator draws more current than a working one. Hence its anode voltage will be low. Why?

Because a non-working oscillator doesn't develop the self-bias (in this circuit, a negative charge on C70) that cuts a working oscillator off for most of the time. It simply sits there passing a steady, increased current, hence the low anode voltage, because an increased voltage will be developed across the anode circuit resistors. It fails to develop self-bias because there's no feedback pulse to drive it hard enough for grid current to flow. O.K.?

In many chassis the feedback pulse coupling network is rather more complex than here, with extra components to shape the pulse. Obviously an open-circuit coupling capacitor or resistor or a short-circuit capacitor to chassis will result in non-oscillation.

Insufficient Height

Insufficient height is another common complaint which can originate in the oscillator stage. The cause is usually in the supply, normally derived from the boost line (line output stage), to the triode anode. The boost voltage depends upon the particular design, and will normally be found to be from around 600V to about 900V. There is usually a series resistor which reduces this voltage to the figure required at the "top end" of the charging circuit resistors. Associated with the series resistor is some sort of decoupling capacitor, usually about 0.1 μ F in value, to stabilise this point. Some designs use a higher value capacitor (say 1 μ F), so that in the event of line timebase failure the consequent collapse of the height circuit voltage is delayed – the larger capacitor takes longer to discharge thus avoiding the appearance of a concentrated spot at the centre of the screen.

Taking a look at the 1500 circuit, we find the boost line supply is via R123 which drops the 650V line down to 270V where it's decoupled by the 1 μ F electrolytic C89 (the original design used a 0.1 μ F capacitor in this position) and stabilised by the VDR Z1. When the voltage at this point tries to rise, the VDR conducts more heavily, and vice versa less heavily when the voltage tries to fall, providing the stabilisation effect. Thus Voltage Dependant Resistor.

So when the complaint is loss of height, we look for reduced voltage – provided the PCL805 is in good order and the loss of height is even at the top and bottom of the screen. C89 can (and does) leak, thus dropping the voltage, and R123 can rise in value (less often). R94 can develop a dud spot on its track, where the wiper arm contact to the track is not good (fit a new preset control), or R93 can rise in value (less often). The VDR is often suspected but in fact these little fellows are almost trouble free and can put up with a lot of mistreatment (even more so those used in width stabilising circuits). So the VDR is the last item likely to require replacement. In short, if lack of height is the problem, leap at the preset height control and then at C89 – if the valve is in order.

next month in

TELEVISION

● MULTIBURST GENERATOR

Checking the frequency response of a video circuit is greatly simplified by using a multiburst signal consisting of a series of frequencies sent consecutively along the TV line. The multiburst generator to be described provides a white bar followed by 0.5, 1.6, 3.3 and 5MHz signals. The results show up clearly on an oscilloscope and, if a dual-beam scope is used, the input and output waveforms can be compared directly.

● SERIES REGULATOR CIRCUITS

Voltage stabilisation is important in solid-state TV sets, and in the case of a mains-battery portable receiver the stabiliser circuit must be capable of working with an input voltage as low as 12V. The type of stabiliser generally used in such sets is the series regulator arrangement. Stanley Amos analyses the basic circuit and describes a number of interesting variations found in practice.

● SEMICONDUCTOR REPLACEMENTS

Sets from many parts of the globe are likely to appear on the bench today, and a bewildering variety of transistors and diodes may require replacement. Apart from the difficulty of obtaining the exact type in many cases, this also presents stock problems. It's much simpler to stick to a group of well known transistor types that can be relied upon to operate satisfactorily in the usual circuitry. Andy Denham provides useful guidance on a range of transistors and diodes that meet most requirements.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....
(Name of Newsagent)

Please reserve/deliver the DECEMBER issue of TELEVISION (50p), on sale November 20th, and continue every month until further notice.

NAME.....

ADDRESS.....
.....
.....

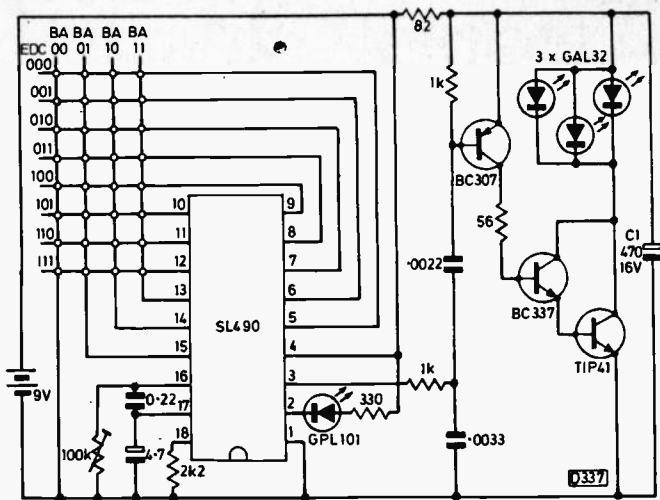


Fig. 7: Infra-red transmitter circuit.

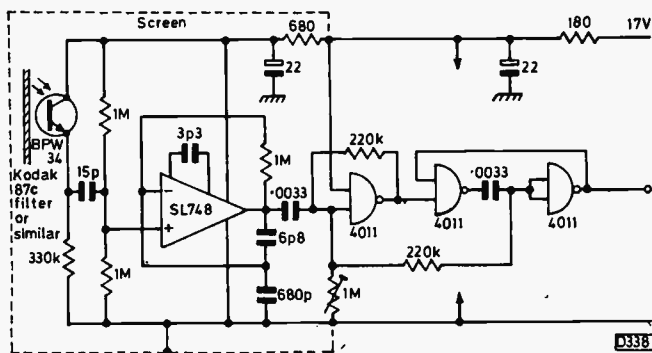


Fig. 8: Infra-red receiver circuit.

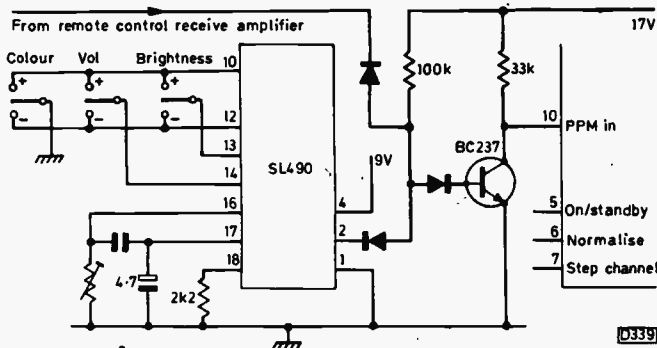


Fig. 9: Using an extra SL490 for manual receiver control.

directly control the volume, brightness and colour; as shown in Fig. 6. The circuit also has a second mute facility which instantly removes the sound without the need to reduce it over a period of a few seconds through the 32 possible sound levels. The sound returns to its original level when the mute button is pressed a second time.

The on/standby command switches the television receiver on from a standby condition. The receiver can't be switched on from the remote control unit when completely off. This prevents the possibility of a spurious signal switching the receiver on and causing a fire risk.

Infra-red linked remote control systems are slightly more complex but offer the advantages of higher data rate capability, less chance of the radiation being noticed by animals or even by humans, and less multipath interference.

The transmitter for an infra-red system must generate short d.c. pulses. These are applied to one or more infra-red emitting diodes. A typical infra-red transmitter circuit is shown in Fig. 7. The internal oscillator of the SL490 is not

required in this circuit, so it's disabled by connecting pin 18 to earth through a 2.2k resistor.

Short current pulses from pin 3 drive the BC307 pnp transistor which feeds an npn Darlington pair (BC337/TIP41). The latter provides current pulses of up to 10A for the three parallel connected GAL32 infra-red emitting diodes.

The maximum range of a circuit of this type is about 27 metres - far more than that of an ultrasonic system. A simpler infra-red system with a single npn transistor instead of the Darlington pair and a single emitter diode was found to have a range of about eight metres.

Although a current of 10A from the small battery in the hand-held infra-red transmitter unit may appear excessive, the pulse width is only of the order of 15 microsec. This pulse is drawn from the 470 microfarad capacitor C1 which must not have excessive inductance and must have short connections to the circuit if sharply rising pulses are to be obtained.

Attempts to use a pulse width of less than 15 microsec may result in a diminished response due to the response time of the phototransistor employed in the receiver.

A suitable infra-red receiver circuit is shown in Fig. 8. A light filter is employed in front of the receiving phototransistor since this is also sensitive to visible light. The filter removes the visible light but has very little effect on the 940nm infra-red radiation from a gallium arsenide emitting diode. The SL748 amplifier/filter stage in Fig. 8 must be well screened to prevent electrical interference: it's possible to include screening (in the form of wire mesh) over the phototransistor window.

The output from the SL748 is fed to one of the two-input nand gates of a 4011 CMOS i.c. (which contains four such gates). The first gate is biased for Class A operation, whilst the succeeding two gates are connected as a monostable circuit. The 1M ohm potentiometer varies the monostable threshold voltage, acting as a sensitivity control. This circuit produces very clean output pulses which are fed to pin 10 of the ML920 (see Fig. 6).

The circuits described enable up to 20 channels to be selected individually by remote control or to be stepped sequentially until the required programme is reached. If less than 20 channels are required, 6, 8, 10, 12 or 16 channels can easily be used. If the least significant bit of the transmitted word is ignored, one has a 10-channel system without any other modification.

An additional SL490 device can be used at the receiver to provide local push-switch controls. See Fig. 9.

A single transmitter can be used to control more than one receiver. In this case a switch in the pin 16 circuit of the SL490 is used to alter the RC time-constant and hence change the pulse modulation rate. If the command signal rates differ by more than 30 per cent no mutual interference or cross coupling should be found between the system. A second receiver can be incorporated in a high fidelity system so that both the television receiver and one's Hi-Fi system can be controlled from a single portable unit. A second receiver can even be used to switch on the oven.

Remote control facilities are especially important in receivers incorporating teletext decoders. The ML920 decoder can be interfaced with a teletext receiver using CMOS logic elements.

The new integrated circuits used in the remote control system described here are in production and readily available for large or small orders. It's interesting to note that they can be used not only for television remote control but also for industrial and commercial applications (such as automatic telephone answering equipment). It's understood that one TV setmaker has already adopted this remote control system. Others are due to follow.

Your PROBLEMS Solved

Requests for advice in dealing with servicing problems must be accompanied by a 50p postal order (made out to IPC Magazines Ltd.), the query coupon from page 49 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

DECCA 30 SERIES CHASSIS

With the colour control at maximum, the colour spreads over the edges of faces (particularly) and objects. Turning the brightness up fully has much the same effect. With a lower colour control setting, the faces in particular have a blue tinge. On monochrome, there are very slight red borders on all objects and people.

The first effect is usually due to the video stages operating under the wrong d.c. conditions. The luminance signal is a.c. coupled to the emitter-follower TR204 which drives pin 3 of the MC1327P demodulator/matrixing i.c. Associated with the a.c. coupling is a d.c. restorer and a preset control VR239. Reduce the brightness level by turning VR239 until the effect disappears (with the brightness control advanced), then restore normal brightness control range by means of the preset brightness control VR601 on the bottom power supply panel. If this action results in a dark picture at full brightness, advance all three c.r.t. first anode preset controls, ensuring that the grey-scale remains correct. The fringeing should be cured by adjusting the static convergence.

PYE 691 CHASSIS

The picture is good but on a normal colour transmission the red information disappears intermittently, details which should be red turning to orange over wide sections of the raster. The purity and convergence have been checked and are correct, and when the guns are separately switched, red, green and blue rasters are obtained.

The symptom is unfortunately that of a c.r.t. with a failing red gun. It would be worth checking the red output pentode's cathode decoupling capacitor C364 (0.0015 μ F) however. You could try reactivating the red gun.

GEC C2110 SERIES

When the set is switched on from cold there's inadequate field scan and foldover at the bottom of the raster. The picture corrects itself gradually, and after about six minutes is normal.

The thermistor TH451 (VA1034) in the field output stage is suspect, also the field charging capacitors C458 (22 μ F) and C457 (47 μ F). Also check the field linearity control P453. If this doesn't solve the problem, you'll have to check the semiconductor devices in the field output stage — TR454/5 and D451/2.

GRUNDIG 5010GB

The problem with this set is a line foldover of approximately half an inch down the centre of the screen. In a past issue, L515 was suggested as a possible cause. The fault remains however after replacing this coil with one from another set.

L515 is in the circuit which drives the scan thyristor. Make sure that you've used the correct coil, as it's critical in value. Also make sure that it's a good one. It's not an expensive item, and easy to replace. C515 and R515 in the same circuit tend to suffer in this chassis and should be replaced at the same time as the coil. Failing this, ensure that all joints on and around the commutator coil are sound, and if necessary check the scan thyristor and efficiency diode (Ty518 and Di518). Note that in this condition the e.h.t. will usually rise to around 30kV and at this voltage the resistors (R545/6) in series with and one or more of the c.r.t. first anode presets may fail. Other possibilities are the tuning capacitors C516/8/9 and C517. Replacements must be of the correct type, since they have to handle a ripple current of some 40A peak.

THORN 980 CHASSIS

There's an odd fault on this v.h.f. only portable. On ITV only, about a quarter of an inch of video information is being repeated down the centre of the screen, correct in every way (perhaps a line or two lower) and about 1½ in. to the right of its correct position. The contrast of both sets of information is the same. BBC-1 is excellent in every way.

If the fault is still present as say a lighter patch with no signal or a short length of wire connected to the aerial socket, there's a tendency to instability in the tuner, probably due to a faulty biscuit. If there's no sign of a fault under this condition, try reducing the signal level and see whether the fault appears at some particular signal level. If so, look around the a.g.c. line for a faulty decoupling capacitor. It would be interesting to see whether the fault is present with say a crosshatch signal applied. If not, the signal itself must be subject to some form of distortion.

PYE 697 CHASSIS

The two 100 Ω wirewound resistors R462/R463 on the convergence board were getting very hot, though the picture and sound were both o.k. before I switched the set off.

The two resistors are connected across the R/G line symmetry coil L64/5. It's unusual for this coil — which carries the line scan current — to become open-circuit, so the probability is of a break in the copper circuit around its base. The d.c. resistance of each half of the coil should be 0.5 Ω .

THORN 2000 CHASSIS

The picture is good but there's reduced height and width, varying with picture content and the brilliance control setting. Examination of the boards has failed to reveal any defective components.

It's essential to check first that the stabilised voltages from the power regulator board are correct: there should be 53V at TP3 and 55V at TP1. If these are wrong, suspect the regulator transistors VT2/3/7. If all is well here, the probable cause of the trouble will be excessive e.h.t., in which case the feedback amplifier output transistor VT6 (D1693, use type 2N3055) in the e.h.t. generator circuit may be leaky or short-circuit. Adjust R14 on the e.h.t. board for 24kV at the c.r.t.'s final anode.

DECCA 30 SERIES CHASSIS

With the slider of the set width/e.h.t. control VR451 hard over to the right (viewed from the rear) there's still lack of width. Moving the slider to the left narrows the picture. I've checked all the resistors in the width circuit, also the line drive coupling capacitor C430, and replaced the PCF802 line oscillator valve and PL509 line output valve. Before finally suspecting the line output transformer, has anything been missed?

There are several things to check before suspecting the line output transformer. First ensure that the h.t. at F1 is above 265V. If not, replace the reservoir/smoothing electrolytic block C601/2. Next try a new PY500 boost diode. Measure the resistance of the width/e.h.t. control VR451 ($2M\Omega$) – it sometimes changes value to give low width. Check the damping/tuning capacitors C433/C435 associated with the line output transformer – one or other could be open-circuit. Finally disconnect the shift choke L402 at the shift-sense tag to see whether this component has short-circuit turns.

ITT/STC VC51 CHASSIS

There is constant field slip on this set – the picture will stop for a few seconds only. The picture looks as if it would be good if only it would stop. Adjusting the height control affects the rolling, but a new PCL805 field timebase valve has made no difference.

This is a common fault with the VC51 chassis. The pentode section of a PCF80 is used as the sync separator, and its anode load and screen grid feed resistors tend to change value. They are R66 ($220k\Omega$) and R63 ($330k\Omega$) respectively. Check these, also the $390k\Omega$ and $470k\Omega$ resistors in the cathode circuit of the PCL84's triode section (field sync pulse amplifier).

KORTING 51763 SERIES

The set was left idle for several months. On switching on, it comes to life and produces a dullish raster and after 15 seconds a crackle on sound. The PY500A boost diode then starts arcing inside, followed by fuse blowing. The line output stage valves have been replaced, the set isn't damp, and no definite short-circuit can be found with a meter.

The e.h.t. tripler could be breaking down. Disconnect it and see whether the PY500A continues to arc. If it does, disconnect the $82/150pF$ high-voltage ceramic capacitors, which provide the line output stage fifth harmonic tuning, one at a time. There are usually three (C427/8/9), in the PY500A's cathode circuit.

GEC 2040 SERIES

There is no raster on this set. At the time of the failure, R705 on the raster correction panel glowed brightly – its value is not now discernable, i.e. it's thoroughly cooked. Are the two faults associated?

R705 is part of a network across the pincushion distortion correction transductor T701: the network is also in parallel with the line scan coil circuit. It's possible for R705 to become very hot should the line oscillator change frequency as a result of a component failure, then ceasing to operate. So first check whether the line oscillator is working – there should be $-60V$ at the control grid (pin 1) of the line output valve. If the line oscillator is working correctly, check the continuity of the transductor, the scan coils and the R/G symmetry coil L701.

WALTHAM W125

We're having difficulty obtaining certain components for this set and would appreciate any suggestions for suitable replacements. The components are the TS18 e.h.t. rectifier, the OA1161 diode in the line oscillator circuit, the two diodes (same type) used in the flywheel sync discriminator circuit, and the OA1160 detector diodes.

The following types are suitable:
D304 TS18 e.h.t. rectifier, use a TV18.
D101 OA1160 vision detector, use an OA90.
D102 OA1160 6MHz sound detector, use an AA119 or OA91.
D301/2/5 OA1161 line timebase diodes, use a BA129 or BA154.

MITSUBISHI CT200B

What appear to be hum bars travel either up or down the picture from time to time. They are not intrusive on bright scenes, but noticeable on dark scenes, sometimes causing a local sideways movement over a few lines.

It seems likely that one of the series regulator transistors is leaky. There are two of them, Q941 and Q943. They are on the left-hand side, with access after lowering the vertical chassis. Alternatively the mains bridge rectifier could be responsible.

BUSH TV350 PORTABLE

The sound is very distorted and the picture only faint. The screen is bright, but the brilliance control does not have much effect when turned down. There's line pairing, with a faint grey picture in the background.

The regulated l.t. line could be incorrect. Check for 11V across C609. If the supply is in order, suspect the video emitter-follower Tr9 (2SC829, 2SC838 or 2SC839 may be fitted) – the sound and sync signals are extracted from its collector circuit, so a defect here would account for the various symptoms present. There should be 7.1V at its collector, 2.7V at its base and 2V at its emitter.

THORN 3500 CHASSIS

If the brightness control setting is increased there's excessive h.t. current with the result that the excess-current trip operates, causing field foldover due to the reduced h.t. The voltages in the beam limiter and field output circuits seem to be correct. The fault occurs only when a very bright scene is displayed or the brightness control setting is increased. One other point is that when a dark scene is displayed there is progressive width cramping (pincushion shape) on the right-hand side only, the cramping increasing in proportion to the darkness of the picture, reaching a maximum of about 1in. The h.t. is stable and correct with this cramping. Neither the cramping nor the foldover occur until the set has been on for about half an hour.

We have an uncomfortable feeling that either the line output transformer or the e.h.t. transformer has one or two shorted turns. This is enough to reduce the width at low brightness and increase the line output current (though apparently the voltage across the beam limiter sampling resistor R907 is correct). The line output transistor could also be at fault, but with a fault of this nature one can never be sure. The a.c. blocking choke L504 is also not above suspicion. It might also be worthwhile checking the condition of the pincushion distortion correction transductor and its associated resistors on the convergence panel.

ELIZABETHAN T12

The trouble with this set is field slip. The picture and sound are all right and the line timebase works perfectly, but the picture rolls.

If the picture can be made to hover by adjusting the field hold control, check the $3.3\mu\text{F}$ a.g.c. reservoir capacitor C145, the two coupling electrolytics in the sync circuit (C302 and C303, both $0.47\mu\text{F}$), and the sync separator transistors Tr302 and Tr301. Otherwise a general check of components around the field oscillator transistor Tr303 will be necessary.

TEST CASE

191

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

An ASA hybrid colour receiver (of Finnish origin), Model CT5004, was working perfectly on sound but the display was marred by a small, seemingly defocused, displacement of blue with respect to the vertical picture content. The owner confirmed that the fault had developed gradually, and that before the blue started to "drift" horizontally the picture was of high colour quality.

The overall convergence adjustment is not unduly difficult on this model, and as the symptom gave a distinct impression of misconvergence steps were taken to check the adjustments while at the same time getting a feeling of how the convergence controls influenced the fault.

The convergence unit is somewhat complex (by today's standard), with diode-rectified d.c. fed through the coils for static convergence, the magnetic field in some versions (as that under investigation) being supplemented by small permanent magnets for coarse adjustment.

All the controls appeared to work and although the convergence was marginally in error the display could not be significantly improved. For a subjective test of the blue display the set was arranged so as to produce a modulated blue raster. This was well defined in terms of scanning lines, but the modulation content was of a "diffuse" nature – rather like a tube with astigmatism. Red and green modulated rasters were then similarly arranged, and both were found to be well defined in terms of picture content.

Attention was then directed to the colour drive circuits, which consist of transistor driver/output pairs for each colour, primary-colour drive being applied to the tube's cathodes. All the voltages around the blue transistor stages appeared to be correct, but when the meter probe was touched on the collector of the blue output transistor the fault condition worsened quite substantially. When the

ITT VC100

The picture and sound come on normally, but after three-four minutes a loud bang comes from the loudspeaker, followed by a chain of lesser noises. The picture appears to jolt when the bang occurs, but otherwise remains normal.

This often occurs with the VC100 and similar ITT chassis, and can usually be cured by replacing the PCL86 audio valve. If necessary, its holder may have to be changed. Very occasionally the coupling capacitor C108 ($0.01\mu\text{F}$, between pins 8 and 9) will be found to be responsible due to leakage.

probe was touched on the emitter the fault almost completely cleared!

After a short while the service technician had located the trouble, aided by the clues just described, and changing one small component restored the picture to its original high quality. What was the most likely cause of the fault, and how did the effects of the probe connections assist the technician? See next month for the solution and for a further item in the series.

SOLUTION TO TEST CASE 190

– Page 665 last month –

As in many mains/battery portables, the c.r.t. heater in the Thorn 1690 chassis is connected between chassis and the regulated l.t. rail. The small tubes used in portables tend to be more susceptible to intermittent heater-cathode shorts than the larger types used in table models, particularly if they've been subjected to excessive vibration while being carried around in a car or caravan.

The trouble was eventually traced to such a short or, rather, more of a high-resistance leak. When the tube was cold the insulation resistance was very high, but when the resistance was checked after the set had warmed up it was found to have fallen in value. This not only reduced the cathode voltage, thereby reducing the bias and causing the screen to brighten, but also attenuated the video drive signal.

The technician was presented with a good clue when his test prod inadvertently knocked the tube neck – indeed tapping the neck of the tube with a screwdriver is a good way of verifying a tube fault of this type, provided undue force is not used! (But don't do it when people like Sid and Grace are around – see page 626 last month.)

QUERY COUPON

Available until 20th November 1978. One coupon, plus a 50p (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 47.

TELEVISION NOV 1978

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Pacesetters, London SE1. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., 40 Bowling Green Lane, London EC1R ONE. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £9.50, Overseas £10.50 per annum payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Manufacturers Surplus Components

FIT THE RIGHT PART

300 mixed $\frac{1}{2}$ and $\frac{1}{4}$ watt resistors £1.50
150 mixed 1 and 2 watt resistors £1.50
200 mixed Capacitors, most types £3.30

100 mixed Electrolytics £2.20
300 mixed Printed Circuit mounting Components for various TVs, resistors, caps etc. £1.50

300 printed circuit Resistors $\frac{1}{2}$ to 4 watt £1.00
100 High Wattage TV resistors, Wirewound etc. £2.20

100 mixed miniature Ceramic and Plate Caps £1.50
25 mixed Pots and Presets £1.20
25 mixed TV Presets £1.00

20 assorted TV VDRs and Thermistors £1.20
10 assorted TV Convergence Pots £1.00

20 assorted TV knobs, includes push button, chrome, control types etc. Mostly Thorn and ITT £1.00
20 assorted Valve Bases, B9A, ceramic, EHT, etc. £1.00

20 assorted Sync Diodes blocks for various TVs £1.00
25 assorted Pulse Caps high voltage £1.00
10 Spark Gaps £1.00

20 assorted Zener Diodes 1 watt and 400MW £1.50
100 Mixed Diodes, includes zener, power, bridge, varicap, germanium, silicon, marked, unmarked etc. £3.30

New Improved Transistor Packs
100 New and Marked Transistors including: BC148, BC154, BF274, BC212L, BF200 and lots of others only £4.95

200 Transistors as above and including 2N3055, AC128, BD131, BFY50, BC238, BC184L only £9.95

Why Buy Expensive Triplers!
Repair your old 5 and 3 sticks at a fraction of the Cost.
10 Replacement Rectifier Sticks £1.00

500 untested Diodes some marked, signal, zener, sync, etc. Random checks showed over 70% good £2.95

Special TV Bargain Parcels
Lots of useful parts including damaged panels, tuners, components etc. 10lb for £7.50

Hardware Pack
Includes BA nuts and bolts, nylon, posidrive, self-tapping "P" clips, cable markers, clamps, fuse holders etc. £1 per lb.

THORN SURPLUS

3500 Series Scan Coils, new and boxed, complete with convergence yoke, purity assembly, static controls, leads and sockets £5.25

3500 Focus units with metrosil £1.00
8000 L.O.P.T windings £2 pair

1500 multi caps 150 + 150 + 100µF £1.00

3500 "625" line VHF Kit for wired systems £9.50

4 Knobs black with chrome caps to fit ITT, Thorn, GEC and most small diam. shafts 60p per set

1500 bias caps 160µF 25V 10 for £1.00

950 rotary transistor tuner with leads and slow motion drive £3.00

950 bottom panel complete with i.f.'s switch etc. £3.00

950 line transformer (not Jellypot) £2.50

Convergence Pots with knobs. 50, 200, 300, 1000 8 of 1 type £1.00. 8 of each £3.50

MISCELLANEOUS

GEC single standard, hybrid chassis. Convergence panel, Brand new, complete with plugs and leads £2.50

SPECIAL OFFER

GEC transistor rotary tuners with slow drive, AE Skt. and leads 2000 Series £2.50

KB VC3 transistor tuner £1.50
ITT CVCS power panel. New but five resistors never fitted £1.50

Pye 697 line and power panels, damaged or some bits missing but invaluable for spares £2.00

Pye mono mains droppers with fusible link. 147W + 260W 50p 3 for £1.00

Decca "Bradford" C.T.V. triplers 25KV £2.50 each 5 for £10

G8 Thyristor OT112 £1.00 3 for £2.50

Portable TV EHT Sticks "Siemens TV 18 KV". Fit most portables 50p each 3 for £1.00

White Ceramic TV Resistors 20Q 16W, 135Q 15W, 86Q 11W, 105Q 10W

10 of any one type £1.00 10 of each type £3.50

2.2k fusible, vertical mounting Screen Feed resistors 9 watt 8 for £1.00

0.47Q $\frac{1}{2}$ watt emitter resistors 40 for £1.00

Bias Caps 330µF 25v 10 for £1.00
470µF 25V 10 for £1.00
160µF 16V 10 for £1.00

Avoid Lethal Shocks Buy our specially designed EHT Probe, removes high voltage charges from tubes, caps, etc. Heavily insulated with lead and earth connector 60p each

B9A P.C. valve bases 20 for £1.00
EY87/DY87 EHT bases 10 for £1.00

PL509/PY500 ceramic bases 10 for £1.00

Out Door Triplexers Band I, II and UHF 3 for £1.00

20mm Antisurge Fuses. 800MA, 1A, 1.25A, 1.6A, 2A, 2.5A, 3-15A 12 for £1.00

DY51 EHT Rec. 50p 3 for £1.00

BR101 5 for £1.00
TBA120A 50p 3 for £1.00

SN78115N (equiv. MC1310) £1.00

TH1 thermistors 6 for £1.00
TH3 thermistors 10 for £1.50

Aluminium Coax Plugs 8 for £1.00
BC148 12 for £1.00

BF200 6 for £1.00
BD131 4 for £1.00

BC184L 12 for £1.00
ME0412 10 for £1.00

BC238 10 for £1.00
BD561 3 for £1.00

BD562 3 for £1.00

200V 1A Diodes 10D2 (equivalent to 1N4003) 20 for £1.00

600V 3A Diodes (Equiv. 1N5406) 10 for £1.00

Storage Boxes with transparent, lids can be hung up or stacked. Ideal for components 3" x 4" $\frac{1}{2}$ " high 6 for £1.00

1" high 4 for £1.00

Miniature "Terry" clips ideal for screwdrivers and small tools etc. 40 for £1.00

Low profile 14 pin quill I.C. Sockets (to fit most "O" series I.C.) 12 for £1.00

Cassette Motors self regulating, 9V, make unknown type 9FM 90p

Send 40p P. & P. on all above items send Cheque or P.O. with order to:-

SENTINEL SUPPLY DEPT. TV

149a Brookmill Rd., Deptford, London SE8
(Mail Order address only. Callers by appointment)
Trade enquiries for quantity welcome.
Surplus stocks purchased for cash.

U.H.F. GREYSCALE AND PATTERN GENERATOR-PG6RF



PRODUCES SIX INVALUABLE PATTERNS:-

- ★ CROSSHATCH GRID
- ★ DOT MATRIX
- ★ VERTICALS
- ★ HORIZONTALS
- ★ WHITE RASTER
- ★ 8 BAR GREYSCALE

ONLY REQUIRES CONNECTION TO U.H.F. AERIAL SOCKET.
9V BATTERY OPERATED.

TECHNALOGICS now gives you the opportunity to set up colour television receiver the professional way.

This pocket size, battery powered unit (consumption less than 6m.a.) based on latest CMOS technology, enables you to set up: static convergence, dynamic convergence, picture geometry, colour purity, focus, beam limiting, Grey-scale tracking, black level, clamping etc. by selecting one of the six patterns generated by the PG6RF on channel 36 (for U.K. 625-line standard T.V. sets).

Available either ready built and tested or in D.I.Y. kit form. The kit consists of all components, glassfibre p.c.b., tough plastic box with full instructions (modulator pre-built for ease of construction). Ready built and tested guaranteed for 1 year.

KIT £21.50 BUILT £28.00 + 50p p&p all subject to 8% VAT

STILL AVAILABLE:

LOGISCAN MK II COLOUR TELETEXT DECODER

YOU CAN NOW BUILD A TELETEXT DECODER TO THE LATEST BBC/IBA/BREMA SPEC. (N.B. Many other decoders are not to full spec.)

Available with full technical back-up in easy to build form for £205 Kit, £265 ready built and tested or in module form, price on request, all subject to 12 $\frac{1}{2}$ % VAT.

DISCOUNT PRICES FOR TTL LS AND LCMOS INTEGRATED CIRCUITS ON REQUEST.

DETAILS LARGE S.A.E.

MAIL ORDER ONLY

TECHNALOGICS

8 EGERTON STREET, LIVERPOOL L8 7LY

SOUTHERN IRELAND DEALERS

We are the largest stockists in the south of Ireland of clean used T.V. sets.

PYE - BUSH - PHILIPS - FERGUSON - KORTING
DECCA ETC.

UHF/VHF Mono from £15.00 each

Colour from £120

All Sets Tested & Cabinets Polished.

Over 2,000 sets in stock.

Visit our warehouse and see for yourself.

Fresh Stocks Weekly.

Delivery can be arranged.

T.V. WHOLESALE DISTRIBUTORS LTD.

E.D.I. House, Kylemore Park West Industrial Estate,
Dublin 10. Tel. 364139 or 791995.

Also at 2, Tower Street, Cork (off Barrack Street).

TRANSISTORS		DIODES		W/W RESISTORS	
ACY 20	34 *BF 198	17 *AA 119	7409 17	74123	48
ASY 66	90 BF 200	26 *BY 127	6 7413	30 74151	64
BC 107	8 BF 257	26 *IN 914	10 7420	15 74190	100
BC108	8 BF 258/9	24 IN 4001/2	4 7425	25 74190	10W Axial
*BC 147A	8 BF 324	28 IN 4004/5	4 7427	27	15W Radial
*BC 148	8 *BF 336	28 IN 4006/7	5 7430	15	
*BC 149/C	8 *BF 337	30 *14 44	6 7440	15	
*BC 158	9 *BF 370	25 *14 940	4 7445	80	
*BC 171A	10 BFY 30	1 *14 941	4 7472	25	
*BC 204B	10 BSX 19/20	16	4 7473	30	
*BC 207B	11 BT 106	130 LINEAR L.C.'s	7474	27	
BC 348	11 *BU 205	140 741 EP	19 7474	43	
BC 351	10 *BU 208	155 555 EP	25 7476	38	
BCY 70	14 *BU 208A	170	25 7480	45	
BCY 71	14 OC 201	70	7482	69	
BCY 72	14 R 2008B	175 REGULATORS	7483	72	
BD 115	43 R 2010B	175 7812	60 7486	30	
BD 131	33 TR 31A	38 7815	60 7490	33	
BD 135	34 TR 42A	62	7491	75	
BD 139	33 *ZTX 212/8	16 TTL	7491	145	
BD 695A	65 *ZTX 302	11 7400	13 7493	32	
BF 115	18 2N 930	16 7401	24 7495	60	
BF 154	24 2N 3055	28 7404	13 7496	57	
*BF 194	9 2N 3055	50 7404	27 74100	95	
*BF 195	9 *2N 3703	8 7405	27 74107	29	
*BF 197	11 *2N 3705	8 7408	17 74121	25	

QUANTITY DISCOUNTS AVAILABLE.

MIN. ORDER £200. p & p 30p. VAT PLEASE ADD 8% EXCEPT THOSE MARKED * WHICH ARE 12.5% S.A.E. FOR LISTS. EXPORT, WHOLESALE, AND INDUSTRIAL ENQUIRIES WELCOME.

K & A DISTRIBUTORS

62, BARKBY ROAD, SYSTON, LEICESTER LE7 8AF. Tel. 0633 609391.

PHILIP H. BEARMAN

(VALVE SPECIALISTS)

SUPPLIERS TO H.M. GOVT. Etc.

NEW valves by Mullard, Mazda, Telefunken, etc.

"QUALITY" BRANDED VALVES ONLY CARRY THE 90 DAY GUARANTEE, SEE OUR LISTS. IMMEDIATE POSTAL DESPATCH LISTS S.A.E. QUOTED PRICES INCLUDING 6% ALLOWANCE IN LIEU OF GUARANTEE ON BVA VALVES WHEN SUPPLIED

PRICES FROM JUNE 1978 INCL. 12½% VAT

DY86/7 75p	GY501 £1.60	PCF802 £1.00	PL36 £1.20	U25 60p	30P12 70p
DY802 80p	PC86 95p	PCF805 £1.60	PL84 70p	U26 60p	30PL13 £1.00
ECC81 75p	PC88 95p	PCF808 £1.70	PL504 £1.50	6F23 60p	30PL14 £1.20
ECC82/3 75p	PC97 80p	PCH200 £1.25	PL508 £1.55	6F28 £1.05	30PL15 £1.10
ECL80 70p	PCC84 35p	PCL82 £1.00	PL509 £3.00	20P4 70p	Etc., Etc.
EF80 65p	PCC89 75p	PCL83 90p	PL802 £2.85	30C1 90p	
EF183 80p	PCC189 75p	PCL84 £1.00	PY81/83 90p	30C17 80p	
EF184 80p	PCC89 95p	PCL85 £1.15	PY800 90p	30FL1 } £1.20	
EH90 70p	PCF86 95p	PCL85 £1.15	PY801 90p	30FL2 } £1.20	
EY51 85p	PCF200 £1.60	PD500 £3.60	PY500 £1.75	30L15 75p	
EY86/7 50p	PCF801 90p	PFL200 £1.35	PY500A £1.75	30L17 75p	

(Correct at time of going to press ONLY.)

MINIMUM ORDER 80p!

ENQUIRIES WELCOMED ON OUR VAST RANGE

TELEPHONE INQUIRIES WELCOMED

NOTE Any excess paid will be refunded.

SEND SAE FOR COLOUR & MONO TRIPLET LIST (BRC) ALSO LATEST COMPONENTS LIST. (Adjacent to Post Office) 6 & 8 POTTERS ROAD, NEW BARNET, HERTS. Tel: 449/1934-5 (Robophone on 449/1934)

STOP PRESS PC92/96, PCL200, PL95, PL519 available! Also EY500A, EL509 etc. (CLOSED 12.30-2 p.m. DAILY. OPEN SAT. A.M. ONLY)

TELEVISION TUBE SHOP

NEW TUBES AT CUT PRICES

A28-14W	£18.95
A31-19/A31-20W	£19.95
A31-410W	£17.95
CME1220/A31-120W	£17.95
CME1420/A34-100W	£18.50
CME1520/A38-160W	£17.50
CME2013/A50-120	£17.95
CME2313A59-23W	£18.95
CME24-13/A61-120W	£18.95

SPECIAL OFFER FOR K.B. FEATHERLITE VC11 TSD 282/217.....£8.50

JAPANESE etc. TUBES

9AGP4	£17.50
190AB4	£15.00
190CB4	£15.00
230ADB4	£18.95
230DB4/CT468	£24.00
CT507	£17.95
CT512	£27.79
240AB4A	£17.95
310DMB4/DGB4	£19.50
310DWB4/DJB4	£19.50
310EDB4	£18.75
310EUB4	£19.50
310EYB4	£16.50
310FDB4	£19.95
310GNB4A Equivalent	£19.95
310HCB4	£19.95
340AB4	£19.50
340AYB4	£23.00
340CB4	£24.50
340RB4	£24.50
340AHB4	£24.50

Some Rebuilt Japanese Tubes Now Available at £14 + V.A.T.

COLOUR TUBES

12VARP22	£62.50
330AB22	£67.50
470FUB22B	£85.00
A44-271X	£65.00
A47-342X	£69.50
A49-191X/120X	£52.00
A51-220X/510DJB22	£64.00
A56-120X	£69.50
A56-140X/410X	£62.00
A66-120X	£75.00
A63-11X/120X	£69.50
A67-120X	£82.00
A67-150X	£69.00
A66-140X/410X	£70.50

ALL TUBES GUARANTEED 12 MONTHS

CARRIAGE: Mono £2.00 Colour £3.00 N. Ireland £4.00

ADD 12½% VAT TO ALL PRICES

TELEVISION TUBE SHOP 52 BATTERSEA BRIDGE RD., LONDON, SW11. Tel. 228 6859/223 5088

SOUTHERN VALVE COMPANY

Second Floor, 8 Potters Road, New Barnet, Herts.

Telephone 01-440/8641 MAIL ORDER ONLY MINIMUM ORDER 80p

ALL NEW & BOXED, "QUALITY" BRANDED VALVES GUARANTEED 3 MONTHS. BVA ETC. HAVE 6% ALLOWED IN LIEU OF GUARANTEE! ALREADY DEDUCTED FROM OUR PRICES!

NOTE: PLEASE VERIFY CURRENT PRICES. Correct only at time of going to press.

Some leading makes available. VAT invoices issued on request.

DY86/7 53p	EF86 54p	GY501 £1.40	PCF802 80p	PL36 90p	PY500A £1.75
DY802 53p	EF89 55p	PC86 75p	PCF805 £1.60	PL81A 65p	UBF89 41p
ECC81 54p	EF183 55p	PC88 75p	PCF806 75p	PL82 30p	UCC85 50p
ECC82 60p	EF184 55p	PC97 72p	PCF808 £1.70	PL83 46p	UCH81 58p
ECC83 54p	EH90 60p	PC900 65p	PCL82 63p	PL84 50p	UCL82 70p
ECC85 52p	EL41 90p	PCC84 35p	PCL83 80p	PL500 } £1.10	UCL83 90p
ECH81 55p	EL309 £2.90	PCC85 52p	PCL84 65p	PL504 } £1.10	UF89 52p
ECH84 85p	EM84 90p	PCC89 50p	PCL85 } 70p	PL508 £1.50	UL41 85p
ECL80 52p	EY86/7 46p	PCC189 55p	PCL85 } 70p	PL509 £3.00	UL84 70p
ECL82 62p	EY500A £1.50	PCF80 80p	PCL86 80p	PL802 £2.90	UY41 55p
ECL86 70p	EZ80 42p	PCF86 60p	PCL200 £1.40	PY88 75p	UY85 60p
EF80 41p	EZ81 44p	PCF200 £1.50	PD500 £3.60	PY800 60p	U25 60p
EF85 45p	PCF801 55p	IPFL200 £1.35	PY801 60p	U26 60p	

One valve post 13p, each extra valve 6p. Large valves 2p, each extra. MAX 80p LISTS & ENQUIRIES, S.A.E. PLEASE! ALL PRICES INCLUDE VAT @ 12½%. ENQUIRIES WELCOMED FROM TRADE & RETAIL (same prices)

EMO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES ETC., ETC. • ALL SPARES READILY AVAILABLE • PANEL REPAIR SERVICE REBUILT TUBES — TWO YEAR GUARANTEE

Almost any TV Component supplied by return "off the shelf" e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc., etc. NEW - COMBI LOPTX NOW AVAILABLE.

YOU CAN BE 95% SURE WE CAN SUPPLY ANY TV COMPONENT BY RETURN IF YOU NEED SPARES FAST - RING NOW!

ACCESS AND BARCLAYCARD ACCEPTED. S.A.E. FOR FREE SERVICE CATALOGUE.

TELE-PORT (WTON) THE TELECENTRE, WORCESTER ST., WOLVERHAMPTON (0902) 772293


PHILIP H. BEARMAN 6 & 8 POTTERS ROAD, NEW BARNET, HERTS. Tel: 01-449 1934/5

NEW MONO TUBES, Usually 2 Year Guarantee. Tested prior sale.

A31/410W Mullard	£18.00
A31/120 - CME1220	(A31/300)* £19.50*
A34/100 - CME1420	£21.00*
A38/160 - CME1520	£21.00*
A44/120WR - CME1713	£21.00
A50/120WR - CME2013	£18.00*
A61/120WR - CME2413	£21.00*

Note* less £1 for 1 year guarantee. PRICES INCLUDE 12½% VAT. MAKES INCLUDE TOSHIBA, MAZDA, BRIMAR & MULLARD. CARRIAGE £1.50 (Mainland); £1.25 Extra Short Sea Journey. Eire Extra

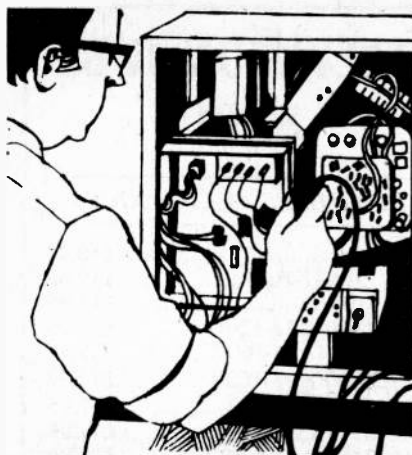COLOUR TUBES. Prices on application. SAE all enquiries please! Prices correct at time of going to press but subject to alteration without notice. Telephone enquiries welcomed. 19", 20" £60; 22" £68.00 £5 allowance old CRT.



SETS & COMPONENTS

TUNER REPAIRS

Repair Service for most types of U.H.F. Tuner.
Prompt turnaround. C.O.D. or Proforma.

R. A. ASSEMBLIES

66 Bohemia Road, Hastings SX (0424) 434932.

TIRRO ELECTRONICS the mail order division of RITRO ELECTRONICS UK offers a wide range of components for the amateur enthusiast. Large SAE or 20p brings list. GRENFELL PLACE, MAIDENHEAD, BERKS. SL6 1HL.

MAINS DROPPERS AND CAN CONDENSERS

Philips G8 47Ω	40p
Philips G8 2-2-68Ω	60p
Philips 210 118-148-LoopΩ	60p
Philips 210 30-125-2K85Ω	70p
Philips GT23 6-124-84Ω	70p
Thorn 3500 6-1-100Ω	70p
Thorn 1500 350-20-148-1500-317Ω	85p
Thorn 8000 56-1K-47-12Ω	85p
Pye 725 27-56Ω	60p
R.B.M. TV161 250-14-156Ω	65p
GEC 2010 8-15-17-70-63-188Ω	85p
2010 Covers 2013 2014 2017 & Sobell 1010 10A 13 & 1014	
Bush TV165-166-171-175-176-178	65p
Murphy V1910-1913-1914-2014-2310-2311-2312-2314	65p
TV Condensers: - 200 + 200 ± 100 mfd 300V	42p each
150-100-100-100-150M 325V	£1.90
150-150-100M 300V	£1.50
175M 400V 100-100M 350V	£1.95
400-400M 350V	£2.50

Post Free, Cash with order, VAT paid.

Durham Supplies

367 Kensington Street, Bradford 8, West Yorkshire

KORTING COLOUR T.V.s 22" and 26" screen size available. Perfect working order £80 each, non workers from £50. Full back up spares available. Tel: Mr. Wilson, Bradford (0274) 665670.

PL802/T Top Quality

Solid State Replacement Valve

£2.50 each

C.W.O.

Lloyd Electronics,
63 North Parade,
Grantham,
Lincs.

SMALL ADS

The prepaid rate for classified advertisements is 18p per word (minimum 12 words), box number 80p extra. Semi-display setting £3.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

TELEVISIONS to the Trade. Large quantities of Mono from £4, square screen from £8. Colour TVs working from £65. R.B.M. GEC, Pye, Thorn, etc. Phone Scarborough 0723 - 68087 - 65451. Scarborough TV Trading, Ridings House, Depot Lane, Seamer Road, (A64), Scarborough.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact Coles-Harding & Co., 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

American Dynascan Tube Restorer & Analyzer,

Now available in this country.
For full details write or telephone:-
T.V. WHOLESALE,
12 Front Street, Whitley Bay.
Tel: 532561 or 512276.

VALVE BARGAINS

ANY 1-20p, 5-80p, 10-£1.25, 50-£5.50

ECC82, ECH84, EH90, DY86/7, EF80, EF183, EF184, PC86, PC88, PCF80, PCF802, PCL82, PCL84, PCL85/805, PCL86, PY81, PY800, PY88, PL36, PL504, 6F28, 30PL14.

COLOUR VALVES 50p EACH
PY500/A, PL508, PL509, PL519.

Postage & Packing 30p, no VAT

VELCO ELECTRONICS

9 Mandeville Terrace, Hawkeshaw, Via Bury, Lancs.

TV SPARES PHILIPS TCE GRUNDIG TELEVIEW

01-994 5537 194 ACTON LANE, LONDON W.4.

RE-BUILT COLOUR TUBES

19" £29.50 20" £30.50
22" £32.50 25" £34.50
26" £38.50

One Year Guarantee. Tel: 226 1111
MATRIX TV LTD.,
112 Essex Road, London N1.

RCA 110° PIL TUBES For "TELEVISION" COLOUR RECEIVER Project

22" A56-611X£101.50 inc. VAT.
26" A67-611X£127.65 inc. VAT.
Neck Components included and preset at Factory.
Carriage £3.00.

B. J. BUCKLE, 14 Park Crescent, Metheringham, Lincs. Telephone (0628) 20031.

Colour T.V. Spares

Brand New Top Quality Components

E.H.T. Triplers

Philips G8 £6.50; Pye 691 £6.00; Thorn 3000 £6.50; 3500 £6.50; 8000 £4.00; Thorn 8500 £7.00; 9000 £7.00; Korting Hybrid £6.80; Grundig Hybrid £9.00.

Mains Capacitors

Philips G8, RRI, GEC, 600MFD, 300V £2.25; Pye 691 200-300MFD, 350V £3.00; Thorn 3000/3500 175-100-100 £3.00; Thorn 1000MFD, 70V 80p; RRI, 2500+2500 30V £1.25.

Semiconductors

BT119 £4.00; BT120 £4.00; TV106 £1.70; BU208 £2.80.

All prices inclusive. Please add 30p for p. & p. Thousands of parts in stock for British and Foreign TVs.

Terry Gallagher,

TV Spares Specialist
20 Oakworth Green, Beechwood,
Middlesbrough,
Cleveland TS4 3ES.

Office Only, No Callers, Thank You.
Enquiries Please Tel: (0842) 85686

INGERTONE

For ex-rental colour and mono televisions

De-controlled sets suitable for re-rent or sale.
A good selection always available, many working.
Good testing conditions.
Trade only.

LONDON

24 Dames Road
London E7
01-555-5569 01-555-2200

BRISTOL

28 St. Thomas Street
Bristol 1
0272-211179

VALVE LIST

ALL VALVES FULLY TESTED

Five valves or over postage paid
Under five valves postage 6p each

DY86/87	15p	PC900	8p	PCL85/805	20p
EB91	12p	PCC84	8p	PL36	20p
ECC82	10p	PCC85	20p	PL504	25p
ECL80	8p	PCC89	8p	PY32/33	15p
EF80	8p	PCC189	8p	PY81/800	15p
EF85	8p	PCC805	15p	PY801	20p
EF183	10p	PCF80	8p	U191	15p
EF184	10p	PCF86	15p	6F23	15p
EH90	13p	PCF805	20p	6/30L2	15p
EY86/87	13p	PCL82	15p	30F5	10p
PC86	15p	PCL83	15p	30FL1	20p
PC88	15p	PCL84	15p	30PL14	15p

S. W. ELECTRONICS

114 Burnley Road, Rawtenstall, Rossendale, Lancs.

BRC 2000, 3000, 8000, 9000.
Phillips G8, Pye 691, 697, 713
Bush Murphy 802, 823.
G.E.C. 2100 Single Standard Hybrid
 Panel Repair/Exchange Singles or Bulk.
MODULAR ELECTRONICS
 160 Brabazon Road, Hounslow, TW5 9LP.
 Telephone 01-897 0976.

EX RENTAL TV
 19" UHF 625 £4.50
 23" UHF 625 £6.00
 Colour from £40.00
EDWARDS & SONS
 103 Goldhawk Road, London W12
 Tel: 01-743 6996

BREAKING TV'S
 Over 200 TV's to be disposed of, for Spares or Complete. Almost any Mono spare available (Tested). Any Mono Tube £5 + £1.25 p & p.
SPECIAL OFFER:- BRC 1400 Chassis, complete, working order, incl. valves, less tuner, £6 + £2 p & p. Many colour spares available. S.A.E. please with enquiries.
KNAVESMIRE T.V.,
 74, Albermarle Road, York.
 Tel: York 31237.

SERVICE SHEETS

LARGE SUPPLIERS OF SERVICE SHEETS AND COLOUR MANUALS
 TV, Radio, Tape Recorders, Record Players, Transistors, Stereograms, Radiograms.
 All at 75p each except Colour TV & Car Radios
 TV Sheets full-length, not in bits and pieces, 24 x 12. All other sheets also full-length.
 Please state if circuit will do if service sheet is not in stock, large s.a.e. with all enquiries and orders otherwise cannot be attended to. Uncrossed P.O.'s or crossed Cheques returned if service sheets are not available. Mail order only or 'phone 01-458 4882. Free TV fault tracing chart OR TV CATALOGUE WITH ORDER.
C. CARANNA, 71 BEAUFORT PARK, LONDON, NW11 6BX NO CALLERS PLEASE

SERVICE SHEETS, Radio, TV, etc., 10,000 models.
 Catalogue 24p plus SAE with orders/enquiries.
TELRAY, 154 Brook Street, Preston, PR1 7HP.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc., with Free fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS
 COVERING COLOUR & MONO TELEVISIONS, RADIOS, RECORD PLAYERS, TAPE RECORDERS, ETC.
SERVICE SHEETS 75p PLUS S.A.E. SERVICE SHEET CATALOGUE 50p

BOOKS
 PRICES INCLUDE POSTAGE U.K. ONLY
 TVT '77 TRANSISTOR EQUIVALENT & DATA BOOK. (A TO Z). 272 Pages.....£2.25
 TVT '78 TRANSISTOR EQUIVALENT & DATA BOOK. (2N. 2S. ETC.). 392 Pages.....£3.30
 NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 1.....£7.20
 NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 2.....£7.20
 NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 3.....£8.60
 COLOUR TELEVISION SERVICING by G. J. King. 2nd Edition.....£7.30
 COLOUR TELEVISION THEORY by G. H. Hutson.....£6.80
 COLOUR TELEVISION PICTURE FAULTS by K. J. Bohlman.....£2.90
 COLOUR TV WITH REFERENCE TO THE PAL SYSTEM by G. N. Patchett.....£6.20
 TELEVISION (COLOUR & MONOCHROME) Part 3 by G. N. Patchett.....£4.35
 TELEVISION SERVICING HANDBOOK by G. J. King. 3rd Edition.....£6.10
 BEGINNERS' GUIDE TO TELEVISION by G. J. King. 5th Edition.....£2.65
 BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King. 2nd Edition.....£2.65
 CATHODE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett.....£4.00
 SERVICING WITH THE OSCILLOSCOPE by G. J. King. 2nd Edition.....£5.35
 TOWERS' INTERNATIONAL TRANSISTOR SELECTOR. Revised Edition.....£5.95
 (SEND LARGE S.A.E. FOR FREE BOOK LISTS)

COLOUR TV MANUALS
 COVERING FOLLOWING MAKES
 ALBA, BRC, BUSH, DECCA, GEC, DEFIANT, MARCONI, EKCO, PYE, FERGUSON, DYNATRON, NATIONAL, HITACHI, INVICTA, ITT/KB, RGD, GRUNDIG, SOBELL, STELLA, SONY, MURPHY, PHILIPS, HMV, ULTRA.
 PLEASE SEND S.A.E. FOR QUOTATION
"COMPREHENSIVE TV REPAIR MANUALS"
 by McCourt. In six Volumes
 These unique Books save time and money on repairs and cover most British Colour & Mono sets. Price £4.50 per volume plus 40p POST, or complete 6 volumes for only £27.00 POST FREE.

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS.
 FROM 1965-66 EDITION UP TO DATE. PRICES ON REQUEST.
 BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 20p POSTAGE PER COPY.
 P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, R. CONSTRUCTOR, ELECTRONICS TODAY, ELEKTOR.

BELL'S TELEVISION SERVICES
190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885
 OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

Reg. Office: 148 Queen's Parade, North Ealing, W5
SERVICE SHEETS - COLOUR TV SERVICE MANUALS
 Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p.
 Please send large Stamped Addressed Envelope.
 We can supply manuals for most makes of Colour Television Receivers by return Post.
B.R.C. PYE EKCO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON H.M.V. MARCONI AND MANY MORE. LET US QUOTE YOU.
 Please send a Stamped Addressed Envelope for a prompt reply.
COMPREHENSIVE TV REPAIR MANUALS BY J. MCCOURT
 Mono Volumes 1, 2, 3 and 4. Colour Volumes 2, 3 and 4.
 A must for the repair man, loaded with faults and cures, all at £4.00 each plus 40p post.
 Build yourself "The Colour TV Signal Injector", manual £1.45. Manual with printed circuit £2.45 post paid.
 The McCourt circuit diagram manuals Mono and Colour. Send S.A.E. for full details.
 Export enquiries welcome. International Reply Coupon please. Mail only to:
G. T. TECHNICAL INFORMATION SERVICE
 10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA

BOOKS & PUBLICATIONS
SIMPLIFIED TV Repairs. Full repair instructions individual British Sets £4.50, request free circuit diagram. Stamp brings details unique. TV Publications, (Auset), 76 Church Street, Larkhall, Lanarkshire.

LADDERS
 ALUMINIUM Roof Crawlers. Sizes 12ft.-24ft. Also aluminium ext. up to 62½ft. Leaflet. Ladder Centre (TEL2), Halesfield (1), Telford. Tel: 586644. Callers welcome.

FOR SALE

NEW BACK ISSUES of "TELEVISION" available 70p each post free. Open P.O./Cheque returned if not in stock - Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

PROJECTION T.V. Decca 1000 C/P Manual. Excellent condition. Working £35. Tel: 0952 584910.

PYE 697 Panels, Good, Cheap, S.A.E. Details. Neilson, 70 Falcon Avenue, Edinburgh.

"TELEVISION" 22" CTV needs setting up. Complete, will separate. Carefully constructed with specified components. I.F. professionally aligned. Cost over £200. Offers - Rapley, 116 Pine Gardens, Eastcote, Ruislip, Middlesex.

**NOW YOU'VE SEEN THE REST, COME AND SEE THE BEST
IN REBUILT TUBES**

CONTACT Trent Tubes

31a Radcliffe Road, West Bridgford, Nottingham.
Tel 0602 813329

Most types available Ex. Stock at very competitive prices.

SOLARTRON OSCILLOSCOPE CD1400 dual beam 15MHz with 2XCX1441 1XCX1443 £140. Tel: 874 8779.

CATRONICS TELEVISION TELETEXT, excellent working order with Catronics manual. £145 o.n.o. Congleton (026 02) 6281 after 6 p.m.

TV TUBE REBUILDING - for all supplies, equipment, plant and training - Western-Whybrow Engineering, Praa Sands Cross, Penzance (073-676) 2265.

VHF/UHF inverters less power unit samples £6.30. With power unit £11.81 inc. VAT and postage. CLEARLINE (Bampton) 21, Brook Street, Bampton, Tiverton, Devon. Phone Bampton 204.

**Colour Televisions From £30.00 VAT inc..
D/S Mono From £4.00 VAT inc.
Square Screens From £10.00 VAT inc.**

VISIT OUR WAREHOUSE AND SEE FOR YOURSELF.
WE HAVE DELIVERIES OF FRESH STOCK WEEKLY.

TELECARE
BRITAIN'S LARGEST USED T.V. DISTRIBUTOR.
Unit B.3, Eley Road, Eley Estate,
Edmonton, London N18.
Tel: 01-807 5908/9, 807 5900.

MISCELLANEOUS

COLOUR TUBES

Rebuilt with new electron gun, to British Standard. High temperature pumping.

Here is what you pay.

17-18-19 inch	£29.00
20 inch	£30.00
22 inch	£32.00
25 inch	£34.00
26 inch	£38.00

Guarantee 1 year.
Exchange basis.
Prices negotiable for contracts.
Old Colour tubes purchased.

TELESTAR TUBES
575c Moseley Road,
Birmingham B12 9BS.
Tel: 021-440 5712.

EDUCATIONAL

TELEVISION TRAINING

18 MONTHS full-time course for beginners to include all the undermentioned subjects. Short courses, combining, one or more subjects, for applicants with suitable education and electronics background such as C & G, HND, BSc etc.

- 13 WEEKS TECHNICAL MATHEMATICS & ENGLISH
- 13 WEEKS ELECTRONICS & RADIO
- 13 WEEKS MONOCHROME TELEVISION
- 13 WEEKS COLOUR TELEVISION
- 13 WEEKS VIDEO CASSETTE RECORDING & CCTV

The training incorporates a high percentage of practical work.
Next session starts on Jan 8th.
(Also available 2½ year course in Marine Electronics & Radar for employment as ships Radio Officer.)
Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept. BTT11, 20 Penywern Road,
London SW5 9SU. Tel. 01-373 8721.

**BETTER JOB!
BETTER PAY!**

GET QUALIFIED WITH ICS IN:
COLOUR & MONO TV SERVICING
COLOUR & MONO TV ENGINEERING
COLOUR & MONO TV MAINTENANCE
PLUS: Telecommunications, radio, electronics, electrical engineering, technical communications, radio communications, etc., etc.,
NEW: Self-build radio courses with free kits

Train in your own home, in your own time with ICS, the world's most experienced home study college.

**RETURN THIS COUPON TODAY
FOR FREE BROCHURE!**

ICS Int Correspondence Schools
A284 Intertext House Stewarts Rd.
London SW8 4UJ. Tel: 01-622 9911

Name

Address

WANTED

NEW VALVES and CRT's required, PCL805, PL504, PL509, PY500A etc. Cash waiting. Bearman, 6/8 Potters Road, New Barnet, Herts. Tel: 01-449 1934/5.

WANTED: Clean new semiconductors, I.C.'s etc. Good prices paid. Hewitts, 52 Barkley Road, Suston, Leicester.

UP TO £75 paid for repair information on British/foreign TV Sets. Full details from TV Technic, 76 Church St., Larkhall, Lanarkshire ML9 1HE.

PROTECT YOUR SERVICING VAN!

Do you own a television servicing van or similar light vehicle? If so, have you thought how many hundreds of pounds-worth of equipment it contains just waiting to be stolen??

Protect your van/car now with the electronic Anti-Theft Car Security System for the fully inclusive price of only £19.95 (UK only).

- ★ Ignition immobilization.
- ★ Uses existing courtesy light door switches; extra switches may be fitted to rear doors, bonnet etc. for added security.
- ★ Dual Positive or Negative chassis capability (12 V).
- ★ Includes all necessary switches, wire, connectors etc. with full installation instructions.

PLUS MUCH MORE!

Generous discount given to bona-fide companies operating servicing fleets. Trade and Overseas enquiries most welcome.

If you require further details, please send SAE/one IRC for our free leaflet.

DERWENT ELECTRONICS
Dept. T/F, 7 Epping Close, Derby DE3 4HR.

COMPREHENSIVE TV Repair Instructions for your set £4.50 with circuit (if requested). Free catalogue unique T.V./other publications. AUSE (T), 76 Church Street, Larkhall, Lanarkshire ML9 1HE.

G.E.C. Solid State Colour Panel exchange service. S.A.E. Details. Baker, 12 Hampton Gardens, Blackfield, Southampton.



6 to 12V D.C.

BELLS AND SIRENS
 Carters Siren £5.53
 Industrial Six Inch Bell £8.27
 Prices inclusive
 Send Cheque, P.O. to
CWAS ALARM
 11, Denbrook Walk
 Bradford BD4 0GS
 S.A.E. for full Price List



12V D.C.

QUALITY REBUILT TUBES

Colour (2 year guarantee) from £30
 Mono (including thin necks) from £10
 Send or phone for full list and terms

WELTECH PICTURE TUBES

5 Masons Avenue, Wealdstone, Harrow, Middx.
 01-427 5063.

COLOUR PANEL EXCHANGE SERVICE

BRC 3000 - 3500 8000 - 8500
 Philips G8 and GEC 2110 series.

Free delivery in London area on Exchange Panels. Large stock of BRC 3500 series spares. New and S/H BRC Panels for sale. Immediate exchange on repairable panels.

Catalogue available on request.

KAY JAY TV SERVICE

34, Clauson Avenue, Northolt. Phone 864 0360.

FOR EX RENTAL COLOUR AND MONO TELEVISIONS

Why not call in and see us - a relaxed friendly atmosphere, together with a choice of hundreds of sets at low, low prices. Colour from £15, Mono from £2. Also stands, spares etc. Send an S.A.E. or phone for our current price lists and area map showing how to find us.

Export enquires welcome

West Midlands TV Trade Sales

92 High Street, Kings Heath, Birmingham B14 7JZ.
 021-444 6464

DISPLAY ELECTRONICS

COLOUR TUBES
 MONOCHROME TUBES
 VDU/RADAR TUBES

REBUILT IN OUR OWN FACTORY IN N.W. LONDON

Customers are asked to note that as a result of the continuing high demand for our products we shall be moving into a new purpose built factory towards the end of the year. Until that time we shall be pleased to deal with enquiries on

WEST DRAYTON 43904

When we move our new number will be

UXBRIDGE 55800

ELECTRONIC MAILORDER LTD.

VALVE BARGAINS

Any 5-80p, 10-£1.50, 50-£6.00 Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PL504, PY81/800, PY88, 30PL14, 6F28, PFL200.

Colour Valves - PL508, PL509, PL519, PY500/A. All tested. 55p each.

Aerial Splitters: - 2 way, 75 OHMS, Inside Type, £2.50

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11 - For the stereo and standard VHF/FM radio.

B12 - For the older VHF television - Please state channel numbers.

B45 - For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. Price £4.70 each.

600V - 1 AMP.

SILICON RECTIFIERS

PRICE 10 - 50p 100 - £4.00

ALL PRICES INCLUDE VAT. P & P 30p PER ORDER. EXPORTS WELCOME AT COST.

62 BRIDGE STREET, RAMSBOTTOM, BURY, LANCs.
 TEL: RAMS (070 682) 3036.

REBUILT TV TUBES

MONO, WITH TWO YEAR GUARANTEE

A 28 - 14W; A 31 - 410W.
 And all thin neck tubes for portable TVs, including Japanese types

£14.00

CME 1601/2, CME 1713, CME 1908, CME 1913, CME 2013, CME 2313, CME 2413.

A 44 - 120W, A 47 - 11W, A 47 - 26W, A 50 - 120W, A 59 - 11W, A 59 - 23W.
 And similar types all available, only two prices.

Up to and including 20"

£11.50

23" & 24"

£12.75

COLOUR TUBES

Normal Guarantee 1 year, extendable for 4 years (details on Guarantee cards).

All types except Sony, Trinitron & P.I.L.

12" - 20" inc. Japanese £29.50

22" £33.00

25" & 26" £37.50

Please add 12½% V.A.T. to all orders. Cash or cheque and old CRT with order

Carriage £3.75 inc. V.A.T. anywhere on mainland.

All prices quoted assume the return of your old tube in rebuildable condition.

Same day despatch. Advance replacements for some types against deposit. Please enquire.

CALEY TUBES

17-35 Bangor Road, Edinburgh EH6 5JY.

031-554 4200.

Callers Welcome.

NOW leap forward with the new generation IN KIT FORM Forgestone '500



high quality
colour television receiver
the successor to the highly successful 400 Series.

- *Pin diode tuner
- *Glass epoxy printed circuit panels
- *Full technical construction manual

- *20AX Hi-Bri tube
- *Eleven integrated circuits
- *Ready built and aligned IF module
- *High quality components
- *Modern and period cabinets

- *All solid state
- *Fully isolated and protected power supply
- *Diode split L.O.P.T.
- *Low consumption

TELETEXT DECODER KITS available for Forgestone 400 and 500 models, include assembled and tested LSI Module, power unit, interface panels, keypad and complete instructions.


Buy as you build. All Forgestone Kits are for the constructor of today, sections of the Kit are available separately. Please send stamp for further details of these quality products.

Forgestone Colour Developments Limited

Ketteringham, Wymondham, Norfolk, NR18 9RY

Telephone: Norwich 810453 (STD 0603)

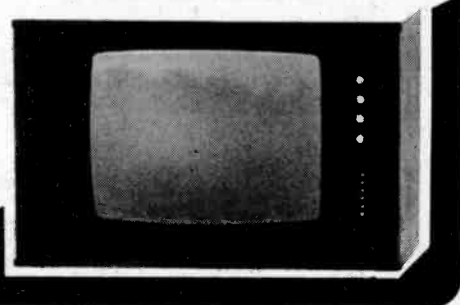Telephone or Mail Orders accepted on Access/Barclaycard



FOR YOUR GUIDANCE

VALUE ADDED TAX

Unless otherwise shown, all prices in advertisements are inclusive of VAT. Where prices are exclusive, readers should ensure that they have added the correct amount of VAT before ordering.

Export orders are not subject to the addition of Value Added Tax.

COLOUR T.V. SPARES

Are you repairing a Decca or Thorn?
We can supply most spares - fast!

Here are some examples:-

DECCA All parts stocked for the 10, 30, 80 and 100 series. LOPT £10.50. Tuner control units, 4 Butt. £6.50, 6 Butt. £8.65. 3R9 R603 52p. Cut-out £1.55. Focus £3.50. Fusibles 61p. Vol/switch £1.45. Tripler £9.00. Converg. pots 48p. Line osc. coil 95p. Mains Tx. £7.30. Mono Dropper £2.05. Mono LOPT £11.75.

THORN 3000. Tripler £9.90. PSU Dropper £1.32. 1000mfd £1.20. Mains Tx £10.44. Cond. can £3.57. Focus £3.98. Cut-out £1.48. 1500. Dropper £1.30. E.H.T. Tray £4.15. 8500. 9000 Triplers £8.50 each. 12" Portable (1590) Speaker £4.50. Batt. Socket £2.50. Vbl/Sw £2.60.

Most Makes:- Triplers, Droppers and Condenser Cans, prices on application.

One only - **THORN 2000** 25 inch. First caller with £40 gets it.

All orders are processed on day of receipt. Send 14p stamps for our catalogue (free with an order). Prices include VAT (12½%). Please add 25p for P. & P.

BOTTOMLEY'S TELEVISION

11 Leeds Road, Hipperholme,
HALIFAX

Phone HX (0422) 202979.

CALLERS - Phone first
NEW ENLARGED CATALOGUE NOW
READY

COLOUR TUBES

STANDARD TUBES

METAL BAND TUBES

Rebuilt with new Electron
Guns to British Standard
415/1972. Clause 18.2.

SUFFOLK TUBES LIMITED

214, PURLEY WAY
CROYDON, SURREY
01-686 7951

Britain's Largest Independent
TV Tube Rebuilder

40V, 2A O.P. Trans NPN PNP BD375-6 Pair 20p	£2.50 Each 10 Watts Mullard Modules LP1173	Convergence Panel for GEC 2040 £2.00	BT106 Special Type 60p Y827 Diodes 30p SN76227 50p
AD161 - 162 Pair 60p	£2.50 New	11 Pots 5 Coils & Resistors etc	TBA 510 £1.00 TBA 540 £1.00 TBA 396 50p
For Varicap 7 Push Button Units with Variable Resist- ance, Fascia Plate & Lamps £2.00	BF258 20p BC303 20p BD207 30p BF157 15p BC238A 10p BC148B 10p TIP31A 20p TIP2955 50p BF195 10p	220 MFD 450V 50p	Bridge Rectifiers B30C600A6 15p B30C500P 15p
6 Push Button Units with Variable Resist- ance for Varicap with Fascia Plate £2.00	8A 800V Thyristors 35p 2N6399A	MODULES Reject Units VHF ELC1042 50p	RCA Line Output Transistor for use in Low Impedance Line Output Circuits 75p
For Varicap 4 Push Button without Fascia Plate 20K 75p	7A/Thyristors 400V S2600D 35p	10 Watt LP1173 £1.00 I.F. LP1170 50p AM/FM LP1179 50p	BT119 £3.00 BT109 60p BT146 60p
Transistor BF180-1 UHF Tuner Unit with AE Socket & Leads. G.E.C. Rotary Type £1.35 New	16172 RCA BT119 Type £1.00	IN2069A 5p	TBA 641 BX1 £1.50 BFT 43 15p
New VHF/UHF Varicap Units AEG £3.00	AT1025/08 Blue Lateral Ass. 25p E1222 15p BSY95A 7½p 2N930 7½p 4.7NF 5kV 10p	Triple LP1174 Mullard £3.00 TIP 29A 25p TIP 32 25p	

SENDZ COMPONENTS

2 WOOD GRANGE CLOSE,
THORPE BAY, ESSEX.

Reg. Office only -
Callers by appointment only. Thank you.
Free Postage applies in U.K. only.

PLEASE ADD 12½% VAT

TV	LINE OUTPUT TRANSFORMERS All items new and guaranteed	MONO TRANSFORMER £7.45 <i>(No Extra for Carriage)</i>
		VAT @ 12½% .93
	DISCOUNT FOR TRADE.	TOTAL £8.38
BUSH TV102C TV128 TV183 or D TV103 or D TV134 TV183S TV105 or D TV135 or R TV183SS TV105R TV138 or R TV185S TV106 TV139 TV186 or D TV107 TV141 TV186S TV108 TV145 TV186SS TV109 TV148 TV191D TV112C TV161 TV191S TV113 TV165 TV193D TV115 or C TV166 TV193S TV115R TV171 TV198 TV118 TV175 TV307 TV123 TV176 TV313 TV124 TV178 TV315 TV125 or U TV181 or S	DECCA DR1 DM35 DR123 DR2 DM36 DR202 DM3 DM39 DR303 DR3 DR41 DR404 DR20 DM45 DR505 DR21 DR49 DR606 DR23 DM55 666TV-SRG DR24 DM56 777TV-SRG DR29 DR61 MS1700 DR30 DR71 MS2000 DR31 DR95 MS2001 DR32 DR100 MS2400 DR33 DR101 MS2401 DR34 DR121 MS2404 DR122 MS2420	MURPHY V843 all models to V979 V153 V159 V173 V179 V1910 V1913 V1914 V2014 or S V2015D V2015S V2015SS V2016S V2017S V2019 V2023 V2027 V2310 V2311C V2414D V2415D V2415S V2415SS V2416D V2416S V2417S V2419 V2423 A816 Chassis £11.00
BUSH A816 CHASSIS £11.00 BAIRD PLEASE QUOTE PART NO. NORMALLY FOUND ON TX. BASE PLATE 4133, 4123, 4140 OR 00062. COLOUR TRANSFORMERS ITT CVC1 TO CVC20 CHASSIS PHILIPS G8 CHASSIS DECCA CS1730 GS1830 DECCA 30 SERIES BRADFORD CHASSIS £9.50 + £1.19 VAT. TOTAL £10.69	EKCO T418 TO T546 GEC BT454 BT455 BT455DST 2000DST... all models to 2044 2047... all models to 2084 2104 or /1 2105 or /1 KB-ITT By Chassis: VC1 VC52 VC2 VC52/1 VC3 VC100 VC4 VC100/2 VC11 VC200 VC51 VC300 Or quote model No. INDESIT 20EGB 24EGB EMO WINDING 90%	PHILIPS 17TG100u 19TG170a... 21TG106u 17TG102u all models to 21TG107u 17TG106u 19TG179a 21TG109u 17TG200u G19T210a 17TG300u G19T211a 23TG111a... 17TG320u G19T212a all models to G19T314a 23TG164a G19T215a 19TG108u... 23TG170a... all models to all models to 19TG164a G20T230a... 23TG176a all models to G20T328 G24T230a... 21TG100u all models to 21TG102u G24T310
		PYE 11u 40F 58 64 81 93 161 31F 43F 59 68 83 94 150 170 32F 48 60 75 84 95/4 151 170/1 36 49 61 76 85 96 155 171 37 50 62 77 86 97 156 171/1 39F 53 63 80 92 98 160
		SOBELL ST196 or DS ST197 ST290 ST297 1000DS... all models to 1102 THORN GROUP Ferguson, H.M.V., Marconi, Ultra. By Chassis:- 800, 850, 900, 950/1, 950/2, 950/3, 960, 970, 980, 981, 1400, 1500, 1500 (24"), 1580, 1590, 1591, 1592, 1600, 1612, 1613. Or quote model No.
Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702	MON-FRI 9 am to 12.30 pm. 1.30 pm to 4.30 pm.	Hamond Components (Midland) Ltd., 416, Moseley Road, Birmingham B12 9AX. Phone: 021-440 6144. MON-FRI 9 am to 1 pm. 2 pm to 5.30 pm.
Contact your nearest depot for service by-return. Callers welcome. Please phone before calling.		
COLOUR TV LINE OUTPUT TRANSFORMERS E.H.T. RECTIFIER TRAYS (Prices on application)		

AD 161-162	PAIR 60p	BD116	30p	SN76533N	£1.00	160PF 8Kv	100M 50v
40 M/A	20MM Fuses Mixed Values Anti Surge and Quick Blow 30 for £1.00	TIP115	25p	TBA990	£1.00	270PF 8Kv	330M 10v
160 M/A		TIP117	25p	SN76660N	50p	1000PF 10Kv	330M 25v
250 M/A		TIP120	20p	SN76650N	£1.00	1200PF 10Kv	330M 35v
800 M/A		100 Mixed Electrolytics		TBA560Q	£2.00	1000PF 12Kv	330M 50v
1 Amp		1000 MFD to 4 MFD	£2.50	TBA540Q	£1.00	160M 25v	330M 63v
1-15 Amp		120 Mixed Pack of Electrolytics & Paper Condensers	£1.20	TBA54Q	£1.00	220M 25v	470M 25v
1-6 Amp		BYX 38/600R	50p	TIS91	25p	1000M 16v	470M 35v
2 Amp		.1 MFD 400	5p	TAD100	£1.00	220M 35v	470M 40v
2-5 Amp		.1 MFD 2000v	15p	SAB550	£1.50	220M 40v	47/63
3 Amp		.1 MFD 800v	8p EACH	TBA530	£1.00	220M 50v	300PF 6Kv
3-15 Amp	.01 MFD 1000v			RCA40506 Thyristors	50p	470M 25v	8M/350v
4 Amp	.047 MFD 1000v			BC108	7p	22M 315v	10p EACH
3500 Thorn Triplers	.47 MFD 630v			BD610 }	50p	BC365	10p
LP1193/1 Mullard	.0047 MFD 1500v			BD619 }	50p	BD561-2	PAIR 30p
TK 25KC15BL	.0022 MFD 1500v		MJE2955	50p	BD183	50p	
Ex Panel Pye	200+200+100M 325v	40p	TIP2955	50p	TDA2680	£1.00	
ITT11TDL CVC 20/25/30	470+470 250v	40p	AC188	10p	TDA2690	£1.00	
TS2511TDT Thorn	100+200M 325v	30p	BC149C	7p	SN16862	£1.00	
TS2511TBQ Pye	200+200+100+32M 350v	70p	Aerial Amp Power Supplies 15 volts	£1.00	MC1352PQ	£1.00	
TS2511TCE	150+200+200M 300v	50p	BC158	8p	SN76131N	£1.00	
TS2511TCF	800M 250v	20p	BC213LA	6p	TBA651	£1.00	
1730 Decca	600M 300v	£1.00	BF594	6p	TBA750Q	£1.50	
Mains Droppers	400M 400v	£1.00	BC147C	7p	TBA920Q	£2.00	
69R + 161R Pye	800+800M 250v	60p	BC212LT	7p	SN76003N	£1.50	
Rank/Bush Mains Dropper	300+300+100+32+32 300v	£1	BC182L	7p	SN7660N	£1.00	
302R/70R/6R2	200+100+100M 350v	70p	BC148B	7p	SAS570S	£1.50	
147R + 260R Pye	100M 450v	25p	BD131	25p	1N4148	3p	
Thorn Mains Dropper	33/450v	25p	Thorn 1590 Mains Lead & On/Off Switch & Control Panel with 3 Slider Pots	£1.00	BF198	7p	
80R/6R/054R/720R/317R	47M 450v	25p	Reject VHF Varicap Units UHF	50p	BF274	5p	
Thorn Mains Droppers	680M 100v	25p	AE Isolating Socket & Lead	45p	BA159	10p	
6R + 1R + 100R	6800M 40v	35p	6 Position 12.5k V/Resistors Units for Varicap	50p	BY184	25p	
Thorn Mains On/Off Switches, Push Button or Rotary	100M 350v	20p	EHT Rectifier Sticks Used in Triplers x80/150	10p	BY187	50p	
100 Mixed Diodes	22M 350v	20p	CSD118xMH }	EACH	TAA550	20p	
1N5349 Diode }	33000 10v	30p	CSD118xPA	12p	TBA396	£1.00	
12V Z/Diodes }	15000 40v	35p	3 Off G770/HU37 EHT Rec. Silicone, used in Tripler	15p	TBA510Q	£1.00	
400 MFD/350V	22M 100v	20p	Bridge Rectifiers 3 Amp	40p	TBA480Q	£1.00	
Mullard UHF T/Units	4-7M 63v	5p EACH	1A 100v	20p	TBA550Q	£1.50	
300 Mixed Condensers	MJE2021 90v 80v }	15p	2A 100v	25p	TBA720A	£1.50	
300 Mixed Resistors	SJE5451 5A }	EACH	W005M	20p	TBA 790B131	£1.00	
30 Pre-sets	90V 661 NPN }	28p	BY127	10p	TBA 800	95p	
100 W/W Resistors	80W 5A 660 PNP }	PAIR	1N4005	20 for £1.00	SN76115N	£1.00	
40 Mixed Pots	EHT lead & anode cap	25p	1N4006	20 for £1.00	TAA700	£1.50	
20 Slider Pots	Thorn 1500 EHT Rec Sticks	10p EACH	1N4007	20 for £1.00	TBA530Q	£1.00	
470M/100v	BRC2108	10p	BYX94 1200v 1 Amp.	15 for £1.00	TBA550	£2.00	
Focus Unit 3500 Thorn	100 Mixed Transistors	£1.50	BB105 UHF		SN76227N	£1.00	
Thorn 8500 Focus Unit	3 amp Diodes	10p	BA 182 Varicap Diodes		SN76544N	50p	
4 Push Button UHF Unit			BB103 VHF	12 for 60p	SN76640N	£1.00	
1400 - 1500 Series and 8500			BY176	50p	SN76033N	£1.00	
D.P. Audio Switch			BA248	7p	TBA120A	50p	
RIZ243619 Replacement for ELC 1043			BY133	10p	TCA270Q	£2.00	
UHF Varicap new			BYX55/350	10p	TCA270SQ	£1.00	
BF127 BC350 BF194			BY210/400	5p	Star Aerial Amps	£4.00	
BF264 BF178 BF184			BY206	15p	CHANNEL B+C	EACH	
BF180 BF257 BC460			BT106	95p	TV18	40p	
BF181 BF137 BF395			BT116	95p	TV20 BYF3214	50p	
BF182 BC161 BC263B			BY212	15p	Rectifier Sticks & Lead		
BC300 BF185 BF273			12 Kv Diodes 2 M/A	30p	R2010B	£1.25	
AC128 15p EACH			18 Kv BYF3123 Silicone	30p	R2008B	£2.00	
3300/40v 680/40v					BU105	£1.00	
680/50v 220/63v					BU105/04	£1.00	
2200/10v					BU205	£1.00	
2N930 BC183					BU208	£1.75	
2N2222					BU108	£1.75	
2N3566 7½p EACH					BD130Y	20p	
BF336 30p					2N3055	40p	
TIP41A - 42A PAIR 40p					BRC1693 Thorn	60p	
G11 Philips Thyristors					BD138	20p	
GEC112M 60p					BD252	20p	
Pye Thyristors					Audio O/P Trans.		
2N4444					RCA16572 }	40p	
BT116 85p					RCA16573 }	PAIR	
Mixed Components 1lb for £1.50					SCR957	65p	
					BRC4443	65p	
					5A 300	25p	
					TIC106 Thyristors }	EACH	

LONG WIRES
300 Mixed Carbon Film
5 of each type ¼ Watt
1R to 2 meg. £1.50. ITT

SENDZ COMPONENTS
2 WOOD GRANGE CLOSE,
THORPE BAY, ESSEX.
Reg. Office only -
Callers by appointment only. Thank you.
Free Postage applies in U.K. only.
PLEASE ADD 12½% VAT