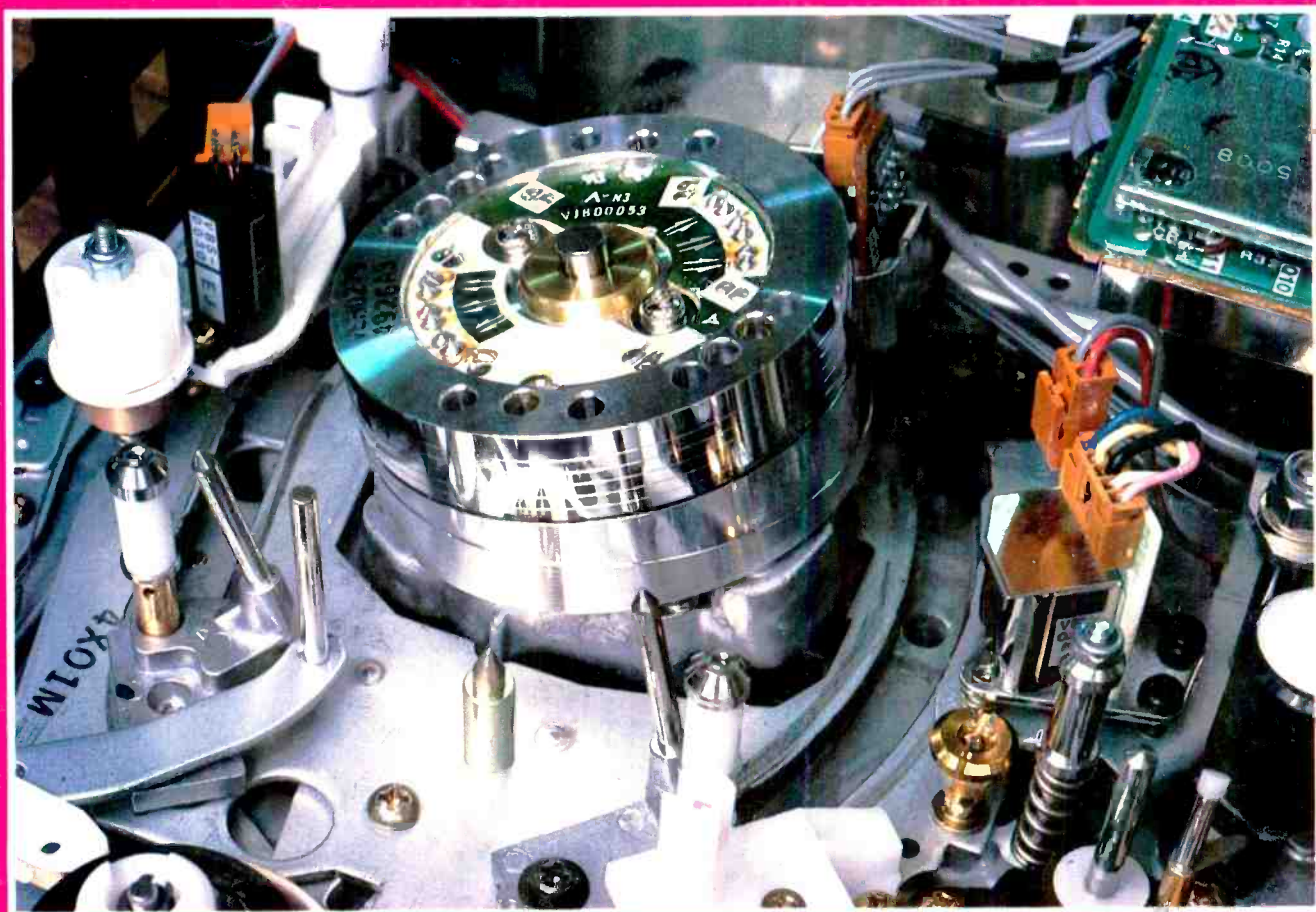


FEBRUARY 1986

Australia \$2, New Zealand \$2.50, Malaysia \$5.75 **£1.20**

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS




Developments in VCRs
The Decca-Tatung 160 Chassis
Amstrad CPC462 Servicing Notes
TV Fault Finding • DX-TV
Video Scrambling Techniques
VCR Clinic • Test Report

MANOR SUPPLIES

MKV PAL COLOUR
TEST GENERATOR FOR TV & VCR.

TEST
DEMONSTRATIONS
AT 172
WEST END LANE

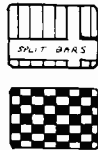


- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**
Case (10"×6"×2¼") app. **£7.40**
Optional Sound Module (6MHz or 5.5MHz) **£3.90**
Built & Tested in Case including Sound Module **£105.00**

SPECIAL TEST
REPORT
'TELEVISION'
DEC. 1982

Post/Packing £2.50
Add VAT 15% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)

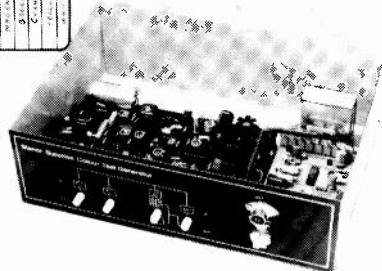

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT £30.00. CASE £7.40. BATT HOLDERS £4.20. MAINS SUPPLY KIT £4.20 (Combined P&P £2.20).

MK 4 (BATTERY) BUILT & TESTED **£58.00 + £2.20 P & P.**
MK 4 (MAINS) BUILT & TESTED **£68.00 + £2.20 P & P.**
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£5.75.**
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

GEC TELETEXT EXTERNAL ADAPTOR UNIT
Complete & ready for use. Converts any TV into a Teletext Receiver with Infra-Red Remote Control (incl. 25 Button Handset) new, boxed and fully tested. **£130.00** p.p. **£3.00.**
THORN TX9 MK2/3, TX10, teletext
Mullard Decoder panel + Interface **£35.00** p.p. **£1.80**
THORN TX10, PHILIPS G11 PRESTEL
Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£48.00** p.p. **£2.50**

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order). ADD VAT 15%

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF
TECHNICAL EXPERTS

LOPTs, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.

- PHILIPS G11 PANELS** (tested).
Power, frame, IF, decoder **£18.00** each p.p. **£2.00.** Scan Panel **£28.00** p.p. **£2.80.**
PHILIPS G11 PANELS ex rental (untested).
Power, frame IF, decoder **£10.00** each p.p. **£2.00.**
SPECIAL OFFER Philips, Pye KT3 Series infra-red remote control handsets ex rental (untested) Teletext or normal versions available **£2.50** p.p. **80p** (5 for **£10** p.p. **£1.50**). CTX, K35 Teletext + Video **£5.00** p.p. **80p.**
THORN 9000 Fault Finding Guide **£1.00** p.p. **30p.**
THORN REMOTE CONTROL HANDSETS
8800/9800 (2-button) **£10.00**; **TX9 ULTRASONIC** (3-button) **£15.00**; **TX9, TX10** Infra red **£18.00**; **TX9, TX10** Infra red Teletext **£20.00**, p.p. **£1.20.**
TX10 Remote & Tuning control panel (1515) **£9.40** p.p. **£1.50**
THORN TX10 Facia Control Panel incl. Infra Red Remote Control receiver **£7.50** p.p. **£1.50.**
THORN TX10 Series Facia Control Panel with 8 position Channel Selector **£6.50** p.p. **£1.50.**
PHILIPS UHF Modulator (Audio & Video Input) **£15.00** p.p. **£1.00.**
SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision. **£28.50** p.p. **£1.20.**
THORN TX9, TX10 Saw Filter IF Panel. **£7.50** p.p. **80p.**
PAL DECODER KIT (Video to RGB) for Monitors **£27.00** p.p. **£1.00.**
PAL ENCODER KIT (RGB to Video) **£18.50** p.p. **£1.30.**
TELETEXT DECODERS New & Tested Mullard VM 6101 **£30.00**, Texas XM11 **£40.00**, KT3 Tested **£30.00**, Untested **£5.00** p.p. **£1.60**
CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. **80p.** (Alum. Case **£2.55**, De Luxe Case **£6.80** p.p. **£1.40**.) **ADDITIONAL GREY SCALE Kit** **£2.90** p.p. **45p.**
UHF SIGNAL STRENGTH METER KIT **£22.00** (VHF version **£24.00**). Alum. Case **£2.55**, De Luxe Case **£7.40** p.p. **£1.80.**
CRT TESTER & REACTIVATOR KIT For Colour & Mono with Panel Meter Indicator - can be adapted for latest CRTs **£28.60** p.p. **£2.80.**
BUSH A823 Convergence, Time Base Panels **£5.00** each. p.p. **£1.80.**
BUSH Z718 BC5100 series IF Panel **£5.00** p.p. **90p.**
BUSH A816 IF Panel (Surplus) **£1.00** p.p. **90p.** 5 for **£4.00** p.p. **£1.40.**
GEC 2040 Decoder Panels, **£1.50** p.p. **£1.80.**
GEC 2110 PANELS Frame **£8.50** p.p. **£1.40.** Sound **£2.50** (tested) p.p. **80p.**
GEC 20AX Switch Mode Power Supply **£5.00**, IF-Decoder **£12.50** p.p. **£1.80.**
PYE 691-7 CDA Panels. Makers tested stock. **£6.00** p.p. **£1.45.**
THORN TX9 Panels ex factory for small spares. Includes I.C.s & Semicconductors etc. **£3.00** p.p. **£1.80.**
THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00** p.p. **£2.80.**
THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. **£2.80.**
THORN TX10 T.B. Panels salvaged ex factory. **£15.00** p.p. **£3.00.**
THORN 3000/3500 Power supply P.C.B. **£3.50** p.p. **£1.00.**
THORN 8000, 8500, 8800 IF Decoder Panels Tested **£10.00** p.p. **£2.30.**
THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. **£1.80.**
THORN 9000 IF/Decoder Panels Salvaged. **£5.00** p.p. **£1.60.**
PHILIPS G8/G9 IF/Decoder Panels for small spares incl I.C.s **£2.50** p.p. **£1.60.**
G11 PANELS, Ex Rental SCAN (incl LOPT) **£28.00** p.p. **£2.50** (tested).
G11 PANELS, Power, Frame, IF, Decoder, **£18.00** each. p.p. **£2.00** (tested).
GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. **£1.00.**
VARICAP, ELC/043/5 **£7.80** p.p. **80p.** Makers Controls **PYE CT200** 4PSN **£7.50**, **BUSH 4PSN** **£4.80**, **DECCA 4PSN** **£5.80**, **6PSN** **£6.80** p.p. **80p.** etc.
BUSH "TOUCH TUNE" Varicap Control Z585, 710 **£3.80** p.p. **£1.00.**
VARICAP UHF-VHF ELC2000S **£9.80**, **BUSH** **£7.80** p.p. **90p.**
VARICAP VHF PHILIPS, **£6.90**, **ELC 1042** **£7.90** p.p. **80p.**
UHF/625 TUNERS, many different types in stock. **DECCA** Bradford 5 position, **MULLARD** 4 position **£2.50**, **JAP** Rotary **£4.80** p.p. **£1.80.**
TV SOUND IF Panels **£6.80** p.p. **£1.00.**
LOPT TESTER, Service Dept approved **£15.90** p.p. **£1.20.**
LOPTS New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins **80p.**
- | | | | |
|--|--------------|---|---------------|
| BUSH MURPHY 774 series..... | £9.80 | R.B.M. T20, T22 | £9.80 |
| BUSH MURPHY A816 series..... | £9.80 | R.B.M. T20, T22 Bobbin..... | £5.60 |
| FERG., HMV, MARCONI, ULTRA | | DECCA Bradford (state Mod No)..... | £8.80 |
| 1400, 1500, 1590, 1591..... | £5.90 | DECCA 80, 100..... | £8.80 |
| THORN 1600, 1615, 1690, 1691 | £9.15 | FIDELITY ZX2000, 3000 | £14.50 |
| GEC series 1 & 2..... | £8.00 | GEC 2110 series..... | £10.60 |
| INDESIT 20/24/EGB | £7.65 | ITT CVC 5 to 9, CVC20 | £9.80 |
| ITT/KB VC 200, 300 | £7.65 | ITT CVC25, CVC30 series..... | £8.80 |
| PHILIPS 170, 210, 300 series..... | £7.65 | ITT CVC45 | £9.80 |
| PYE, INVICTA, EKCO | | PYE 691-697 (state model no.)..... | £10.00 |
| 368, 169, 569, 769 series..... | £7.65 | PYE 725 (90P) 731 to 741 | £9.20 |
| | | PHILIPS G8 | £8.80 |
| | | PHILIPS G9 | £10.80 |
| | | GEC 2114/3 Junior FineLine..... | £2.80 |
| | | PHILIPS KT3 | £9.80 |
| | | THORN 3000/3500 SCAN, EHT..... | £6.90 |
| | | RBM A823 | £4.80 |
| | | THORN 8000, 8500, 8800 | £12.80 |
| | | GEC 2028, 2040, 2100 | £4.80 |
| | | THORN 9000 to 9600 | £12.90 |
| | | PYE 713, 715 | £6.80 |
| | | THORN 9800 | £19.80 |
| | | PHILIPS 570, 571 | £6.80 |
| | | THORN TX9 | £14.80 |

OTHERS AVAILABLE. PRICES ON REQUEST.
TRIPLERS Full range available. Mono & Colour.
Special Offer: **GEC 2040/2100** EHT Tripler **£2.50** p.p. **£1.30.**
THORN 8000 EHT TRAY (2 lead) **£2.80** p.p. **£1.00**
6-3V CRT Boost Transformers for Colour & Mono **£5.90** p.p. **£1.40.**
THORN TX10 focus control **£8.80** p.p. **80p.**
THORN 8000 mains input choke **£6.80** p.p. **£1.40.**
CALLERS WELCOME AT SHOP PREMISES
THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS
TELEVISION MAGAZINE PROJECT PARTS & REPLACEMENTS
STILL AVAILABLE


Telephone 01-794 8751, 794 7346

MANOR SUPPLIES

172 WEST END LANE, LONDON, NW6 1SD

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
W. Hampstead Brit. Rail Stn. (Richmond, Dalston, Stratford, N. Woolwich)
W. Hampstead Brit. Rail Stn. (St. Pancras, Bedford)
Access from all over Greater London.

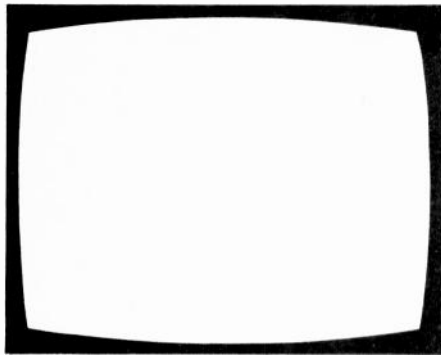Mail Order: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT
PLEASE ADD VAT 15% TO ALL PRICES INCL. P+P



TELEVISION

February
1986

Vol. 36, No. 4
Issue 424

COPYRIGHT

© IPC Magazines Limited, 1986, Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £13 in the UK, £15 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 221 Leader**
- 222 Teletopics**
- 224 Teamwork** *Anne Avis*
The husband-wife approach to running a radio/TV business.
- 227 Decca-Tatung Chassis Up-date, Part 2** *Ray Wilkinson*
Technical features of the 160 and 165 series chassis.
- 230 Quick Tests: Philips Solid-state Chassis** *S. Simon*
Tackling common faults on the G8, G9 and KT3 series chassis.
- 231 Next Month in Television**
- 232 Developments in VCRs, Part 1** *Steve Beeching, T. Eng.*
Dual-speed operation and helically-recorded hi-fi sound are features of the JVC HRD725 VCR, which is taken as an example of recent developments.
- 237 TV Fault Finding**
Reports from Alan Shaw, Philip Blundell, Eng. Tech., Steve Illidge, Hugh MacMullen, Jeff Herbert, J.G. Grieve, Malcolm Burrell and Steve Leatherbarrow.
- 239 The Human Element** *Nick Lyons*
This aspect plays a large part in servicing: some people are decidedly helpful, others can leave a set in a very dangerous condition.
- 240 Letters**
Including more on the NordMende Flv/FC25 chassis.
- 242 Test Report: The Portasol Soldering Iron** *Eugene Trundle*
- 243 And There's Another Funny Thing** *Les Lawry-Johns*
Some sets can do some very odd things – like Miss Converge's little portable.
- 246 Long-distance Television** *Roger Bunney*
Reports on DX reception and conditions and news from abroad. The new Tandy dual-standard portable is reviewed.
- 249 Servicing Notes on the Amstrad CPC464** *Christopher Holland*
- 250 Video Scrambling Techniques** *Andy Emmerson, G8PTH*
- 252 Vintage TV: The Bush T91** *Chas E. Miller*
The first post-war Bush TV set. Comments on the vintage scene.
- 254 VCR Clinic**
Reports from Christopher Holland, Les Harris, Philip Blundell, Eng. Tech., John Cahill and Eugene Trundle.
- 256 Servicing Teletext Receivers, Part 2** *Mike Phelan*
- 258 Computer Aided PCB Design** *Malcolm Burrell*
- 259 Service Bureau**
- 260 Test Case 278**

OUR NEXT ISSUE DATED MARCH WILL
BE PUBLISHED ON FEBRUARY 19

P. V. TUBES

104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.

Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

HOW TO ORDER

ADD 87p per order P+P (U.K.). Heavier parcels e.g. cable, service aids, degaus, coils please allow £1.50 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible; Add 15% VAT to total except where it states zero rate.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. V.A.T. invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice. In some cases we may have to supply an equivalent.

SEMICONDUCTORS

AC107	35	BCY72	13	BF371	30
AC126	34	BD115	45	BF392	35
AC127	34	BD116A	90	BF422	34
AC128K	34	BD124P	84	BF423	46
AC141K	40	BD131	50	BF435 = BF491	35
AC142K	39	BD132	49	BF457	35
AC176	35	BD133	60	BF458	43
AC176K	35	BD135	38	BF459	58
AC186	41	BD136	38	BF460 = BF462	86
AC187	38	BD137	38	BF469	63
AC187K	46	BD138	35	BF470	66
AC188	35	BD139	35	BF597	16
AC188K	46	BD140	44	BF757	54
AD143	82	BD144	1.70	BF758	54
AD161	54	BD150	60	BF759	27
AD162	54	BD159	65	BF779	85
AD161.62 MP	1.15	BD166	52	BF790	1.74
AF106	49	BD179	70	BF742	42
AF114	89	BD182	1.20	BF743	42
AF118	1.20	BD183	1.18	BF744	60
AF121	48	BD201	85	BF745	42
AF124	48	BD202	91	BF746	40
AF125	63	BD203	80	BF747	30
AF126	53	BD204	99	BF748	30
AF127	53	BD222	46	BF749	46
AF139	63	BD223	56	BF750	32
AF178	1.54	BD225	47	BF751	32
AF239	60	BD232	82	BF752	32
AL102	4.90	BD233	60	BF790	95
AU106	7.50	BD234	63	BR100	34
AU113	5.20	BD235	60	BR101	95
BA157	20	BD236	65	BR103	63
BC107	20	BD237	67	BR303	1.46
BC108	20	BD238	65	BRC4443	94
BC109	20	BD243	85	BRC4444	98
BC114	17	BD244	85	BRV39	55
BC115	12	BD410	79	BRV55	46
BC116A	35	BD434	74	BRV56	57
BC117	30	BD437	86	BSR99	1.80
BC118	24	BD438	84	BSV57B	89
BC119	36	BD507	69	BT100	1.65
BC138	32	BD508	80	BT101	1.20
BC140	32	BD509	86	BT102/500	1.20
BC141	30	BD510	86	BT106	1.60
BC142	30	BD278A	81	BT108	1.69
BC143	31	BD517	60	BT109	1.31
BC147	13	BD520	75	BT116	1.87
BC148	9	BD535	82	BT119	3.66
BC149	12	BD536	91	BT120	3.66
BC157	16	BD696A	1.49	BT151.800	2.07
BC158	16	BD697	1.24	BU104	2.00
BC159	15	BD698=702	1.50	BU105	1.58
BC160	52	BD707	95	BU108	1.80
BC161	32	BDX32	2.10	BU124	1.90
BC170B	15	BF115	38	BU126	1.75
BC171	15	BF117	36	BU204	1.50
BC172	15	BF125	26	BU205	1.87
BC173	16	BF127	47	BU206	1.80
BC174	10	BF154	15	BU208	1.60
BC177	27	BF158	18	BU208A	1.65
BC178	26	BF160	27	BU208D	2.20
BC182L	15	BF167	24	=BU800	
BC183L	15	BF173	36	BUW81A	3.84
BC184L	15	BF177	52	BU208Q2	2.10
BC186	35	BF178	46	BU326A	2.00
BC187	25	BF179	42	BU407	1.70
BC204	10	BF180	39	BU426	3.07
BC208	13	BF181	39	BU500	2.50
BC209	10	BF182	36	BU526	2.46
BC212	10	BF183	29	BU508	3.20
BC212L	15	BF184	42	BU806	1.40
BC213	15	BF185	36	BU807	2.94
BC214	15	BF194/394	16	BUW84	1.45
BC237	14	BF195	16	BUX84	1.50
BC238	14	BF196	16	E1222	45
BC251A	18	BF197	16	MCR101	45
BC252	12	BF198	12	MCR220	1.50
BC261	33	BF199	21	ME0411	20
BC262	30	BF200	35	MJE340	68
BC300	50	BF224	40	MJE520	50
BC301	53	BF225	20	MJ3000	1.98
BC303	33	BF241	38	MPSA92	35
BC307	20	BF256	60	MR814	90
BC308	25	BF257	34	MR854	45
BC323	99	BF258	34	MR475	2.46
BC327	22	BF259	34	MR479	2.60
BC328	18	BF262	84	OT112	1.91
BC337	18	BF263	81	OT121	1.91
BC338	18	BF271	24	R2008B	1.90
BC461	42	BF273	24	R2101B	1.92
BC547	13	BF274	24	R2265	1.50
BC548	13	BF336	40	R2322	84
BCX32 = BC637	39	BF337	41	R2323	67
BC549	10	BF338	41	R2461	1.50
BC550	10	BF355	56	R2540	6.00
BC557	10	BF362	68	RCA4558	2.20
BC558	9	BF363	72	RCA16334	90

INTEGRATED CIRCUITS

AN214Q	3.91	SN76650N	1.24	RCA16029	1.18
AN240	3.84	SN76660N	80	RCA16039	1.18
AN318	6.37	SN76666N	1.52	RCA16092	1.18
AN262	4.10	SN76530A	1.47	RCA16040	96
AN301	5.15	STK015	1.36	RCA16041	84
AN715Q	3.97	STK032 = STK078	7.85	RCA16334	90
AN6340	7.85	STK043	15.25	=DN447	
AN6341N	8.97	STK433	5.65	RCA16335	90
AN6344	7.85	STK435	9.06	=DN448	
BA521	2.80	STK436	6.50	RCA16957	2.88
BA536	3.00	STK437	7.85	TIC45	90
CA555	46	STK439	8.40	TIC46	60
CA556	84	STK459	9.50	TIL32	65
CA741	25	STK441	11.57	TIP29C	43
CA748	45	STK461=465	12.60	TIP30A	47
CA3065	1.80	STK463	14.30	TIP30C	43
HA1151	3.89	STR441	6.50	TIP31C	55
HA1342	2.49	STR451	6.50	TIP32C	42
HA1366N	2.60	STR6020	8.90	TIP33B	75
HA1366WR	2.80	TA7050P	95	TIP34B	1.06
HA1417	3.95	TA7051P	2.20	TIP41C	47
HA11219	4.21	TA7063P	9.50	TIP42C	50
HA11244	4.04	TA7074P	3.46	TIP47	93
LA4031P	3.21	TA7108P	3.43	TIP120	65
LA4032P	3.15	TA7120P	2.43	TIP2955	90
LA4102	3.37	TA7129AP	3.76	TIS91	32
LA4400	3.05	TA7130P	1.93	TU106/02	1.80
LA4422	3.28	TA7146P	4.67	2N696	21
LC7130	5.93	TA7193P	5.67	2N918	82
LC7120	5.87	TA7171P	8.90	2N2904	51
LC7137	5.50	TA7172P	8.90	2N2905	28
LM1011	3.25	TA7173P	8.90	2N3054	60
LM1340T	7.5	TA7176P	2.50	2N3055	79
MB3712	2.60	TA7202P	4.27	2N3072	16
MC1307	1.99	TA7204P	3.77	2N3073	16
MC1310P	1.84	TA7205AP	3.72	2N3075	10
MC1327	1.70	TA7208P	3.40	2N3076	10
MC1351P	2.93	TA7210P	6.60	2N3708	17
MC1349	1.99	TA7222	2.42	2N5294	48
MC1350	1.50	TA7223P	3.74	2N5296	69
MC1352	1.75	TA7227P	5.98	2S837	1.86
MC1358P	1.50	TA7228P	5.98	ETTR6016	53
MC1495L	6.6	TA7310P	2.78	ML232	2.20
MC1401BCP	4.3	TA7609P	4.39	ML236	5.35
MC14049UB	4.3	TA7611AP	2.92	ML237	2.50
MC7742	1.35	TA8570	3.98	ML238	2.50
MC7812	1.35	TAA310	2.83	ML239	2.50
ML231	2.20	TAA320	2.00	ML920	4.12
ETTR6016	2.20	TAA550	55	ML922	3.29
ML232	2.20	TAA630	3.90	ML928	2.18
ML236	5.35	TAA8400S1	1.96	MMS387ANN	4.15
ML237	2.50	TAA661B	1.20	MRF475	2.50
ML238	6.00	TAA120A	1.49	MRF477	10.00
ML239	2.50	(A),(S),(AS),(SA),	2.75	MMS5807	7.87
ML920	4.12	TA120B	1.30	MS1513L	2.80
ML922	3.29	TA120SB	1.37	MS1515L	3.28
ML928	2.18	TA120T	1.49	SAA1025	8.50
MMS387ANN	4.15	TA120U	1.49	SAA1124	5.34
MRF475	2.50	TA1395	1.75	SAA1250	4.99
MRF477	10.00	TA396	1.75	SAA1251	5.75
MMS5807	7.87	TA440N	2.75	SAA5000	6.15
MS1513L	2.80	(TBA1441)	2.50	SAA5010	6.30
MS1515L	3.28	TA440P	2.50	SAA5012	6.50
SAA1025	8.50	TA480Q	1.82	SAA5020	5.90
SAA1124	5.34	TA510	3.00	SAA5030	8.25
SAA1250	4.99	TA520(Q)	1.68	SAA5050	8.50
SAA1251	5.75	TA530(Q)	1.38	SAA3210	2.93
SAA5000	6.15	TA540	1.76	SAS560S	2.07
SAA5010	6.30	TA550	3.20	SAS570S	2.07
SAA5012	6.50	TA560(Q)	4.21	SAS660	3.25
SAA5020	5.90	TA570	1.79	SAS670	3.25
SAA5030	8.25	TA690	1.50	SAS80	2.90
SAA5050	8.50	UBA618X1	3.50	SAS590	2.90
SAA3210	2.93	TA673	2.45	SL9018	7.00
SAS560S	2.07	TA700	2.12	SL917B	9.25
SAS570S	2.07	TA720	2.64	SL1310	1.80
SAS660	3.25	TA750	2.98	SL13270	1.20
SAS670	3.25	TA800	1.62	SL1430	1.58
SAS80	2.90	TA810AS	1.38	SL1432	3.36
SAS590	2.90	TA820M	1.75	SL76544	2.05
SL9018	7.00	TA820M	1.20	SN76023N	2.00
SL917B	9.25	TA890	3.94	SN76110N	1.42
SL1310	1.80	TA920(Q)	3.00	SN76115N	2.27
SL13270	1.20	TA950(2X)	3.25	SN76131N	2.00
SL1430	1.58	TA970	4.09	SN76226DN	2.72
SL1432	3.36	TA990	1.90	SN76533N	1.70
SL76544	2.05	TA14406	2.44	STR451	6.50
SN76023N	2.00	TA760	2.30	STR6020	8.50
SN76110N	1.42	TA2705Q	2.50		
SN76115N	2.27	TA800	5.95		
SN76131N	2.00	TA830	3.44		
SN76226DN	2.72	TA900	2.20		
SN76533N	1.70	TA910	2.20		
STR451	6.50	TA940	1.95		
STR6020	8.50	TA440	2.20		
SN76544N	2.35	TA1002	1.95		

DIODES

UPC1190G	1.20	AA119	9
UPC1198C	4.00	BA102	17
UPC1200V	1.18	BA115	13
UPC1211V	2.70	BA145	17
UPC1212V	1.34	BA148	17
UPC1215V	1.66	BA154	6
UPC1216V	1.20	BA155	14
UPC1217G	2.24	BA156	15
UPC1218H	1.80	BA317	26
UPC1223C	2.20	BAX13	4
UPC1225H	2.00	BAX16	8
UPC1226V	1.50	BB105G	30
UPC1227V	1.20	BY126	

P. V. TUBES

104 ABBEY STREET, (0254) 36521
ACCRINGTON, LANCs BB5 1EE. 32611

SONY PARTS

SEMICONDUCTORS		
Diode CV12E	GEN	2.34
Diode GH3F	KV-GEN	1.42
Diode IS1555	GEN	25
Diode UO5G	KV1810UB	96
Diode V11N	KV1810UB	96
Diode 10E2	GEN	25
Thyristor SG-264A	KV-GEN	4.08
Thyristor SG629	KV1810UB	6.42
Thyristor SG-6533	KV-GEN = SG613	13.20
BX342	SLC7UB	4.08
CX104A	KV1810UB	5.28
CX136A	VTR-GEN	7.74
CX143A	SLC57UB	7.20
CX186	SLC5UB	5.28
M51231P	KV2200UB	2.34
STK2129	STRYK50L	13.20
TCP4621AF6	SLC6UB	13.87
TDA2578A	TK2752UB	3.24

Please ask for any part not listed.

UPC 1394C	KV2060/62U	2.34
UPD 546C107	SLC7UB	16.98
UPD 547C049	SLC7UB	8.94
TL494CN	SLC7UB	5.28
2SA 771	TAFA5A	2.34
2SA 835	GEN	1.42
2SA 1027R	ICF-C820L	25
2SA 1175	SLC7UB	89
2SB 733	KV2204UB	96
2SB 740C	TCX88B	96
2SB 856	GEN	1.42
	SY8-724-375-01	
25C 403C	GEN	25
25C 867A	GEN	2.34
25C 1034	GEN	5.28
25C 1061	GEN	46
25C 1114	GEN	5.28
25C 1124	GEN	96
25C 1136	GEN	3.18
25C 1362-7	GEN	25
25C 1364	GEN	25
	SY8-729-341-34	
25C 1413A	KV-GEN	7.38
25C 1475	KV1810UB	25
25C 1982	GEN	1.42
	SY8-725-800-00	
25C 2009	GEN	25
25C 2278	GEN	96
25C 2335 Kit	SLC7	7.38
25C 2369	SLC57UB	3.18
25C 2551	KV-GEN	98
25C 2785	AG-7UB	25
25C 3153	KV2060UB	4.08
25D 257	ST5150	2.34
25D 725	KV2204/2704	8.94
25D 773	BM715T	25
25D 774	SL/HMK	96
25D 870	KV2704E	6.42
25D 1164	SLC6UB	96
25D 1497-02	KV2252/2752	4.08
25D 1497-06	KV2252/2752	4.08

SUNDRIES

UHF Tuner BT-871	KV1810UB	37.20
Booster Antenna	SLC7UB	31.38
RF Modulator	SLC6UB	60.38

SONY REMOTE CONTROLS

SLC5UB		19.80
SLC6UB		17.40
SLC7UB		42.00

VIDEO/AUDIO HEADS

Ace Assembly	SLC7UB	24.10
Ace Assembly	SLC6UB	47.22
	SYA-676-104-6A	rep
	SYA-676-205-5A	rep
Video Head ORS-21R	SLC9UB	43.20
Video Head DSR-35A	SLC20/30/40UB	41.34
Video Head DSR-36R	SLC5/C6/7UB	42.00
Video Head DSR-43A	SL8000UB	46.74
Head Record-Play-back	PP128-3602C/GEN	13.87
Head Record-Play-back	181-3602D/TC/HMK3000	4.12

SPECIFIC COMPONENTS

Philips G8 knobs sm/1g		50
90° transistor		2.60
Thom 1591 speakers sm		6.20
lg		6.20
Thom 1500 controls		59
390K frame 470K line contrast 1k5		each
Focus control Thom/GENC		2.95
Thom 9000 focus unit		8.40
Thom 8500 focus unit		4.75
Thom Tx10 focus cont.		10.20
Decca bridge trans.		1.97

MECH. REPLACEMENT PARTS

Drum Assembly Main	SLC7UB	192.52
Idler Kit/Rewind Kit	SLC7/CSUB	5.95
Idler Kit/Rewind Kit	SLC8UB	3.95
Forward Assembly	SLC8UB	3.18
Gear Kit	SLC9UB	8.94
Guide Pin Kit	SLF1/C9UB	5.28
Pinch Roller	TC-GEN	96
Pinch Roller	TC204SD	1.42
Pinch Roller	HMK44/44B	96
Pinch Roller	TCK55	96
Cassette Holder		
Assembly	TCK44	1.42
Lever Forward		
Assembly	WM2	96
F/Wheel Assembly	WM2	3.18
Limiter Assembly	SLC7UB	2.34
Idler Assembly	SLC7UB/CS/3000	96
Brake Assembly	SLC7UB	1.42
Pulley Loading		
Assembly	SLC6UB	96
Thrust Bearing		
Assembly	HMP70	3.18
Screw Cassette Lid	WM2	25
Coil Spring	WM2	25
Battery Lid	WM2	96
Lid Timer	SLC7UB	96
Gear Kit	SLC9UB	96
Threading Gear	SLT6ME	96
C5 C7 Capstan Motor		34.00
C7 Drive Motor		32.95

BELTS

Belt	WMR2	96
Rubber Belt	TC-GEN	96
Take Up Belt	TC-GEN	96
Drive Belt	TC-GEN	96
Midway Pull Belt	TC-GEN	96
Capstan Belt	TC92	96
Capstan Belt	TC135/136SD	96
Flat New Belt	TC186SD	96
Capstan Belt	TC-GEN	96
Capstan Belt	HST300	96
Take Up Belt	HMK3000UK	96
Belt Capstan	HMK3000UK etc	96
Fast Forward-Rewind		
Belt	V02850P	1.62
Forward Belt	V02850P	1.02
Motor Belt	V02850P	1.62
Capstan Belt	VP2000	4.32
Forward Belt	SLC7UB/SLC5UB	25
Capstan Belt	SL8000UB	96
Extension Belt	SL8000UB	2.34
Orum Belt	SL8000UB	1.52
Fast Forward Idler Belt	SLC7UB	96
Threading Belt	SLC7UB	25
Capstan Belt	SLC7UB/CS	96
Eject Belt	SLC7UB	25
Counter Belt	SLC7UB	25
Fast Forward Belt	SLT7ME	96
Forward Belt	SL8000UB	96
SLC6UB		96
Fast Forward Belt	SLC6UB	96
Counter Belt	SLC6UB	96
Threading Belt	SLC6UB	96
Relay Belt	SLC6UB	96
Capstan Belt	SLC6UB	96
Belt	PS-5520 etc	3.18

SWITCHES

Switch, Filter	KV2022UB	96
Switch, P. B. Channel	1820/2 & 1340	18.86
Switch, Push Power	KV-GEN	1.20
Switch, Push	SL8000UB	96
Switch, Push Button		
Power	KV14/2060UB	3.68
Switch, Power	KV2022UB	4.08
Switch, Slide Record	SL8000UB	96
Switch, Slide Record-Playback	SL8000UB	1.42
Switch, Push	KV1612UB	4.08
Switch, Power	KV-GEN	5.50
Button, Stop/Eject	WM4	96
Knob, Control	SLC7UB	96

MANUALS (Zero VAT)

Instruction Manual	SLC9UB	2.00
Instruction Manual	SLC6UB Mk 2	2.00
Instruction Manual	SLC7UB	2.00
Instruction Manual	SLC5UB	2.00
Instruction Manual	SL6UB	2.00
Instruction Manual	KV2212UB/e2	2.00
Instruction Manual	KV2705UB	2.00
Service Manual	HMK3000	8.25
Service Manual	KV1810UB Mk 1	8.25
Service Manual	KV1400UB	8.25
Service Manual	SLC7UB	8.25
Service Manual	SLC5UB	8.25
Service Manual	SLC6UB	8.25
Service Manual	SLC9UB	8.25
Service Manual	SLC6UB Mk 2	8.25

THORN/FERGUSON SEMI-CONDUCTORS

Diode GL4850	TX10	74
Thyristor TIC45X	TX9	1.18
Diode 19022W	TX9	43
(Thyristor T9053V)	TX9 = T9054V	1.10
(Thyristor T9054V)	TX9	1.10
AN6360	3V29	6.81
HA11741	3V32	23.22
M293	TX90	7.10
M50790SP	3V35	6.98
M54544L	3V32	3.80
MC13002	38030	4.98
MC14493	TX9/TX10	2.74
MN1219	3V36	11.43
TDA1236	TX10	3.44
TDA3652	TX10	6.00
TDA4500	TX90	5.84
SL490	TX9/TX10/TX100	1.89
DTC144WF	3V35	6.00
RZ540	ICE9000	6.0
TIP112H	TX90	6.9
T5051V	TX9	3.43
T609V	TX9	3.8
T6071	TX130	1.46
T9063V	TX9	3.64
19064V	TX90	1.14
UP0553C 164	3V29	20.76
UP075196 031 036	3V36	17.13
UP07538C 020	3V38	11.06
10 Volt T05	3V29	8.74

MANUALS

Service Manual	TCE1690/1691	5.60
Service Manual	TCE1790	1.14
Service Manual	TCE9000	3.56
Service Manual	TCE9600	10.05
Service Manual	TCE9800	7.54
Service Manual	TX9	29.04
Service Manual	TX10	40.00
Service Manual	TX90	11.30
Service Manual	TX100	11.20
Service Manual	3V00	17.50
Service Manual	3V16	26.24
Supplement to 3V00	3V22	1.28
Service Manual	3V23	30.62
Service Manual	3V24	28.42
Service Manual	3V29	29.00
Instruction Manual	3V29	3.28
Service Manual	3V00	17.50
Instruction Manual	3V29	3.28
Service Manual	3V30	14.91
Instruction Manual	3V30	2.65
Service Manual	3V31	25.84
Instruction Manual	3V35	1.63
Service Manual	3V35/3V36	27.20
Supplement to 3V35	3V38	1.24
Supplement to 3V35/3V38	3V39	90
3V42		23.94
3V43		30.72

V.C.R. BELTS

Counter Belt 1	3292/3V00/3V16/3V22	60
Counter Belt 2	3292/3V00/3V16/3V22	60
Relay Drive Belt	3292/3V00/3V16/3V22	1.00
Capstan Belt	3V00	2.79
	3292/3V00/3V01/3V16/3V22	3.28
Unloading Belt	3292/3V00/3V16/3V22	60
Drum Motor Belt	3292/3V00/3V16/3V22	2.79
Cassette Drive Belt	3V23	60
Capstan Belt	3V29/3V30	1.82
Loading Belt	3V23	60
Loading Belt	3V29/3V30	60
Loading Belt	3V35/3V36/3V38	60
Tape Spool Drive Belt	3V35/3V36/3V38	60
Take Up Clutch Belt	3V29/3V30/3V35/3V36/3V38	60
Capstan Belt	3V35/3V36/3V38	1.21

VIDEO HEADS

Upper Drum Assmb	3292/3V00	35.94
Upper Drum Assmb	3V22	35.94
Upper Drum Assmb	220D/3660/3V16/3V23/3V24	35.94
Upper Drum Assmb	3V31/3V35/3V36/3V38/3V39	35.94
Upper Drum Assmb	3V29/3V30	35.74

VIDEO LAMPS

Tuning Indicator Lamp	TX9	62
Cassette Lamp	3292/3V00	3.56
Cassette Lamp	3V16	1.53
Cassette Lamp		
Holder	3V16	60
Cassette Lamp	3V23	1.95
Cassette Lamp		
Holder	3V29/3V30/3V31/3V32	60
Cassette Lamp	3V29/3V30	1.41
Cassette Lamp	3V31/3V32	1.60

PHILIPS KT3/K30 PARTS

KT3 positor		1.50
Mains electrolytic 225.25 380V		2.50
Selector unit Mod. 933		13.42
On/off switch Mod. 933		3.20
Tripler		10.65
Luminance chroma panel		24.00
2003 UF module		14.95
U321 IF module		13.50
R.G.B. panel		10.30
Sound panel		8.50
Power panel		10.60
Mains input panel		14.30
Line sync panel		10.20
Mark I/ chroma panel		16.50
Sound module		8.50
LOPT		9.70
Focus unit		3.50

V.C.R. MOTORS

Capstan Motor	3292/3V00/3V01/3V16	57.45
Drum Motor	3292/3V00/3V01/3V16/3V22	43.49
SMP Reel Motor	3V23	32.79
Cassette Housing		
Motor Assembly	3V23	16.32
Capstan Motor	3V23	52.81
Loading Motor	3V23/3V24/3V29/3V30	3.56
Capstan Motor	3V29/3V30	27.32
Reel Motor	3V29/3V30	32.79
Lower Drum Motor		
Assembly	3V29/3V30	78.72
Cassette Motor	3V35/3V36/3V38	6.92
Mode Control Motor	3V35/3V36/3V38	5.95
Capstan Motor	3V35/3V36/3V38	23.90

REMOTE HANOSETS

7723 Non Text	3767/3788	38.60
7725 Non Text	20A2/2282/3781/3704/1/37081/37101/3714/37351/37361/37371	19.40
7731 Text and Stereo	20A4/2284/37063/37093/37463/37493	20.01
7736 Text	20A3/2203/3795/3796/37003/37103/37353/37363/37373/37953/37963	31.60

SWITCHES

On/Off Switch	TX9	2.98
On/Off Switch	TX10	2.74
Focus Unit	TX10	10.20
8 Way Tuner Unit (Not Drawer)	37141	12.88
8 Way Tuner Unit (Not Drawer)	37360	13.50
8 Way Tuner Unit (Not Drawer)	37340/37370	20.44
Volume Control	38030	1.74
6 Button Switch Assmb	3722/4722/6722/8000	20.70

TRANSFORMERS & INDUCTORS

Line Output Transformer	TCE9000	25.53
FHT Transformer	TX10	33.80
Line Output Transformer	TX10	15.00
Line Output Transformer	TX9	23.85
Line Output Transformer	38030	6.18

P. V. TUBES

104 ABBEY STREET, ACCRINGTON

TEL: 0254
36521/32611

SUNDRY EQUIPMENT	FILAMENT LAMPS	PANASONIC VCR MECHANICAL SPARES	SUNDRY VIDEO ACCESS.	WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER AERIAL EQUIPMENT
Test Lead Set 4.20 Degaussing Coil Stick 19.00 Signal Ejector 4.00 Elect. Circuit Tester 1.50 5A Choc Bloc (12) 40 Fuse Wire 5A, 15A, 30A 05 4-way 13A Mains Conn. 5.00 Safe Block (mains) 8.50 13A Plug Top (box 10) 4.80 Probes (x10) 10.90 Probes (x1) 10.90 Micro Pliers 4.20 Micro Cutters 5.00 13.25 Factory recon. Avo meters 119.00 Avo Battery 2.95 Vero Board 2.59 LG Solder Sucker 6.20 Solder 500g 7.00 D.I.Y. Solder 45 Solder Sucker Antistatic 5.40 Nozzles 81 Trim Tools 30 Metal End 74 Solda Mop Stand 70 Sidecutters sm. 1.20 Long Nose Pliers 1.20 Surge Protector Plug 12.50 Quick Set Adhesive 75 Sm. Neon Screwdriver 40 Lg. Neon Screwdriver 65 I.C. Inserters 1.18 Automatic Wire Strippers 5.95 Scarf Plugs 2.95 Scarf Leads 3.50 TAB1 Car Battery Leads/port. TV 1690/91 4.47 TA51 Car Battery Leads/port. TV 1613/1615 3.66 Car Battery Leads/port. TV Philips 3.95 Universal Car Accessory Cable 1.99 Dynascan 467 Rejuv. 3.99 Dynascan 470 Testers 2.99 B+K tube bases Dynascan No. 3 9.50 No. 15 16.44 No. 5 9.09 No. 19 10.83 No. 6 11.08 No. 21 14.40 No. 8 10.08 No. 23 13.86 No. 13 11.11 No. 24 27.07 No. 14 16.63 No. 25 12.57 C15 computer cass. 30 C20 computer cass. 33 5 1/4" floppy disc s/s/s/d 1.61 2M Fly Lead 70 4M Fly Lead 1.20 10M Fly Lead 1.90 Figure 8 Mains Lead 62 Computer to TV 97 7 pin din to 5 pin din 98 5 pin din to 5 pin din 98 Fluorescent Starter 4-80W) 15p Tinned Copper Wire 14SWG 2.73 16SWG 1.86 18SWG 1.86 20SWG 2.75 22SWG 2.90 Insulated Copper Wire (0.4mm dia.) 9.11 Battery Press Studs Min. 11 Std. 15	HES ROUND BULBS 15p L23m x D11mm 6.5V 0.3A 12V 2.2W LILLIPUT (L.E.S.) BULBS 12p L20m x D5mm 6V 0.025A 12-14V 0.1A CAPLESS LAMPS 28p L11mm x D4mm 6V 0.04A 12V 0.04A TUBULAR LAMPS CAPPED 31p L31mm x D6.3mm 6.3V 0.15A 6.3V 0.25A 6.3V 0.3A 8V 0.15A 8V 0.25A 8V 0.3A 12V 0.15A 12V 0.25A 12V 0.2A WIRE NEONS 9p 65VAC/90VDC Series res 100K for 110V - 330K for 240V WIRE ENDED LAMPS 25p D3.2mm 6V 0.04A 8V 0.04A 12V 0.04A 14V 0.025A 14V 0.04A D4.2mm 4.5V 0.06A 6V 0.06A 6.3V 0.025A 6.3V 0.08A 8V 0.04A 8V 0.06A 8V 0.08A 12V 0.04A 12V 0.06A 14V 0.06A 14V 0.08A TUBULAR LAMPS (Wire ended) 31p L22m x D4.25m 3V 0.06A 6V 0.05A 8V 0.05A 9V 0.045A 12V 0.05A 14V 0.05A	Idler Unit VXP0401 1.08 Idler Unit VXP0344 1.22 Idler Unit VXP0331 1.28 Idler Unit VXP0329 1.32 Idler Unit VDG0141 1.08 Play Idler VXP0243 1.10 Play Idler Unit VXP0433 4.80 Idler Arm Unit VXP0521 4.08 Loading Gear VXP0325 1.63 Loading Gear Unit VXP0520 1.36 Action Gear VDG0016 46 Cam Gear VDG0069 70 Intermediate Gear VDG0017 43 VIDEO PINCH ROLLERS PANASONIC NV7000 4.35 PANASONIC NV8300-333-370-777 4.35 SANYO VTC9300/VBS7000 4.35 SONY C7J7:SL7 4.35 JVC TCE 3V00-01-06-16-23-24 4.35 JVC HR2200-3320-3330 4.35 3660-1100-7700 4.35 VS9700 4.35 HITACHI VT5000 4.35 SHARP VC6300-6500 4.35 VIDEO BELT KITS 4.50 VEKIT 1 AKAI VS9300/V9500/V9800 4.50 JVC HR3300/HR3320/HR3330/HR3360 4.50 TCE 8903:3V00:3V16:3V22 4.50 VEKIT 2 PANASONIC NV7000B/NV7200B 4.50 VEKIT 3 SONY SLC5:SLC5EC:SLC5CH:SLC5E1:SLC5E:SLC5SA:SLC5UB:SLC7E:SLC7U8:SLC7EC:SLC7F:SLC7:SLC5:SLC7:SL79MER:SL8000AS:SL8000E:SL8000S:SL8000A:SL8500:SL8500B:SL8600A:SL3000UB 4.50 VEKIT 5 SONY V1011 4.50 VEKIT 6 PANASONIC NV3000B 4.50 VEKIT 7 SONY 9300P 4.50 VEKIT 8 PANASONIC NV2000B 4.50 VEKIT 9 PANASONIC NV8600B/NV8610B: 4.50 VEKIT 10 TOSHIBA V6600 4.50 VEKIT 11 SHARP VC7300 4.50 VEKIT 12 SHARP VC6300/VC6600 4.50 VEKIT 13 SANYO VTC5000 4.50 VEKIT 14 SANYO VTC5000 4.50 VEKIT 15 JVC HR7650 4.50 VIDEO IDLER TYRES O Dia L Dia Width SONY 23.7 17.4 4.9 50p SONY 24.2 18 5.1 50p HITACHI 31.8 25 4.9 52p HITACHI 39.5 30 4.2 52p PANASONIC 31.2 25 3.1 50p PANASONIC 37 27 3.9 52p PANASONIC 34.5 27 3.1 50p AKAI 26 20 3.9 50p JVC 32.8 3.4 3.9 50p JVC 23.9 4.8 4 50p	VHS Drum Motor 25.50 VHS Capstan Motor 25.50 Sanyo 5000 Reel Motor 20.00 VHS Idler 5.95 Video Lamps 1.41 3V23 Lamps with Plug 1.95 Video Care Kit 3.50 Universal Copying Kit 5.50 Video Head Cleaner 86 Sharp Reel Motor 13.13 Reel Idler (Sharp) 2.48 381/383/386/9100/9300/9500 VIDEO HEADS 3HSS UHS 32.50 4HS VHS 32.80 PS3B Beta/Sony 37.00 Philips V2000 57.00 Philips 1700 64.00 Sanyo 9300/9455/9500 53.00 Sanyo 5000/5300/5400 53.00 Toshiba V5470A BDP 50.00 Toshiba 9600 Upper Ass. 12.50 Toshiba 9600 50.00 Sharp 2300 58.00 Sharp 6300 58.00 Sharp 7300/7700/7750 58.00 Sharp 8300 58.00 Sharp 3300/9700 56.00 VIDEO TAPE SKC E180 3.20 L750 3.20 Scotch E30 3.66 E60 4.00 E120 5.00 E180 4.50 Beta L750 5.80 VCC 240 6.20 360 8.30 480 10.21 LVC 1700 Philips 1200 17.50 NEW LABGEAR * CM7271-MHA 15db 8.25 * * CM7274 4 Way Dist. 21.45 * SERVICE AIDS SERVISOL Freeze-It 1.20 SUPER SERVISOL 1.04 SERVISOL Foam Cleanser 1.02 SERVISOL Plastics Seal 1.14 SERVISOL Silicone Grease 1.30 SERVISOL Tubes Silicone Grease 1.66 SERVISOL Aero Klene 94 SERVISOL Aero Duster 1.28 SERVISOL Excel Polish 96 SERVISOL Video Head Cleanser 90 Super 40 1.66 Fire Extinguisher 640G 3.08 Heat Sink Compound 25G 1.08 Silicone Rubber Tube 110G 2.98 Solda Mop standard reel 77	Outdoor Splitter 5.50 Plastic Tape 50 F.M. Plugs 25 Set Top Aerial 2.30 Loop Aerial 1.00 Aerial Isolator Kit 2.08 Attenuator 6dB, 12dB, 16dB 1.80 27MHz Filter 50dB 2.10 Cable Clips 7mm per 100 1.18 Single Outlets 80 Surface Splitter 1.70 A Splitter 70 100M Coax 15.00 Coax Plugs per 10 1.80 1" U Bolts 30 J Bolts 25
SOCKETS ELECTRICAL BA 320A Single Gang 1.30 320B Single Switched 1.95 320C Two Gang 2.53 320D Two Switched 3.92 Switches 320E One Gang/One Way 80 320F One Gang/Two Way 1.05 320G Two Gang/Two Way 1.78	PLUGS AND SOCKETS 5 pin DIN plugs 180° 20 5 pin DIN chassis sockets 180° 28 5 pin DIN line sockets 180° 28 5 pin DIN plugs 360° 20 5 pin DIN chassis sockets 360° 28 5 pin DIN line sockets 360° 28 6 pin DIN plugs 28 6 pin DIN chassis sockets 36 36 6 pin DIN line sockets 28 7 pin DIN plugs 35 7 pin DIN chassis sockets 36 7 pin DIN line sockets 30 8 pin DIN plugs 56 8 pin DIN chassis sockets 64 8 pin DIN line sockets 55 Phono plugs 12 Phono chassis sockets 10 Phono line sockets 20 2.5mm Jack plugs 11 2.5mm Chassis sockets 17 2.5mm Line sockets 14 3.5mm Jack plugs 15 3.5mm Chassis sockets 24 3.5mm Line sockets 24 3.5mm Stereo Jack plugs 35 3.5mm Stereo chassis sockets 38 3.5mm Stereo line sockets 28 6.3mm Stereo Jack plugs 36 6.3mm Stereo chassis sockets 35 Standard mono jack plugs 20 Loud speaker plugs 2 pin 10 I.D.C. plugs 36 conn. 5.90 I.D.C. sockets 36 conn. 6.90 BNC plugs 1.15 Coax plugs Each 18p Pack of ten 1.80 Line connectors 16 Double ended female sockets 1.20 Car aerial plugs 18 PL259 with reducer 1.30 Reducers for the PL259 1.30 FM plugs 25 Crocodile Clips 25 In Line Socket (Metal) 25	DATA BOOKS (Zero VAT) Pair of A-Z/N2S TV180 8.50 LIN IC Books (data only not Equiv.) 16 LINI 5.95 IC equivalent booklet £3.25 and transistor equivalent booklet £3.25 REMOTE CONTROL HAND UNITS Some are original some are compatible types. DECCA 100/101 US Non T Text 23.80 GRUNDIG TELEPILOT 12 IR RTP20 13.87 GRUNDIG TELEPILOT 8 IR RTP05 25.10 GRUNDIG TELEPILOT 160 IR RTP06 25.10 GRUNDIG TELEPILOT 300 IR RTP07 18.87 PHILIPS G11 US Non Text US8263 22.00 PHILIPS G11 8 way IR Text IR8435 22.00 PHILIPS G11 US 31 Button 69117187 27.00 PHILIPS G11 US 2 function US8518 21.00 PHILIPS KT3/30 IR Text 1234 19.87 PHILIPS KT3/30 IR Non Text 1201 19.87 THORN TX10/JVC IR Text TP8431R 18.00 Remote Control Tester 29.94	ANTIFERRENE SB11 Splitter 2.37 COB11 Outlet 96 CS1000 Combiner/Splitter 6.15 PU1240 Power Unit 11.65 UP1300 MHA 9.99 XS2J Xtraset 14.58 4 way VHF/UHF Amp 40.71 4 way VHF/UHF Amp 50.88 XGB High Gain Aerial A-B-CD-WB 17.10 LABGEAR CM7261 Power Unit 12V 11.24 CM7262 Reg. Power Unit 12V 12.25 CM7060 MHA 10db 12V WB 9.86 CM7065 VHF/UHF MHA W/B 12V 14.34 CM7066 13.38 CM7067 UHF 12V MHA (Specify A-B or C/D) 10.72 CM7068 UHF 12V MHA High Gain (Specify A-B or C/D) 15.95 CM7053 Behind Set UHF Amp. (Mains) 13.01 CM7054 Behind Set UHF Amp. (Battery e.g. Caravans) 10.42 CM7043 Second Set Amp. UHF 12.12 CM7093 Behind Set UHF Amp. 3 Sets 15.27 CM7063 Dist. Amp. VHF/UHF 17db/output 12V 22.17 CM7108 VHF/UHF 8+1 Dist. Amp. 43.26 CM9700 27MHz CB Suppress. 4.05 CM6011 Outdoor Splitter (2 way) W/B 7.83 CM9003 Flush Single Outlet 1.47 CM9010 Flush Twin Outlet 1.95 CM9034 UHF Group Filters with CD Through Pass (state A/B/C/D) 7.69 CM6006 6 Way Passive Splitter 10.87 CM7042 TV Games Combin. 2.95 CM9009 Flush TV/FM Outlet 3.05 CM7091 Col. Bar Gen. 121.80 CM9006 VHF/UHF Diplexer 3.60 Televerta up converta 37.20	ANTEX SOLDERING EQUIPMENT C15W Iron 240V 6.20 C240 Element 2.75 Bits 102 1.10 96 1.10 106 1.10 820 1.10 821 1.10 CS17W Iron 240V 6.40 CS240 Element 2.75 Bits 1100 1.10 1101 1.10 1106 1.10 XS25W Iron 240V 6.50 XS240 Element 2.75 Bits 50 1.10 51 1.10 Temp. Controlled 30W Iron CSTC 16.95 40W Iron XSTC 16.95 Unit for above TCSU1 68.95 Stand 2.10 MLXS Auto Repair Kit 8.40 ORYX Gas Cordless Iron 19.50 Tips for Gas Iron 5.00
CABLES 100m FO31 2 Core Round .75mm ² 15.47 FO32 3 Core Round .5mm ² 15.75 FO35 3 Core Round 1.25mm ² 28.21 FO41 Speaker 7/0 2mm 3.90 Coaxial 75R 13.50 FO51 Multicore 8x7/0 9.75	We have a fully equipped computer store - Come and visit us -	RECHARGEABLES Ever Ready RX6 (HP7) 1.29 RX14 (HP11) 2.22 RX20 (HP2) 2.45 RX22 (PP3) 4.55 Universal Charger 7.50	AUDIO HEADS AND MOTORS Mono record/playback 4.32 Stereo playback 4.79 Stereo record/playback 4.99 Stereo record/playback (Dolby) 6.90 Mono/stereo erase 2.25 Electronic/rotation clockwise motors 6V MD6515 4.95 9V MD9516 4.95 12V MD12517 4.95 CASSETTE DRIVE BELTS 35m 35 46mm 37 57m 37 66m 39 110m 59 76m 43 90m 43	

HUSSAIN CENTRAL T.V. LTD.

TRADE ANNOUNCEMENT

NEW BRANCH NOW OPEN AT

PRESTON

TO OFFER YOU TOP QUALITY VIDEOS & T.V.s

JUST LOOK AT WHAT WE CAN OFFER YOU!

VIDEO

- | | |
|------------|---|
| HITACHI | — 9700 - 9500 - 8700 - 5000 - 5500 - 8000 - VT17E |
| PANASONIC | — NV2000 - NV7000 - NV7002 |
| J.V.C. | — HR7655EK - HR7700EK - HRD120EK - HR7200EK |
| SHARP | — 8300 - 9300 - 7300 - 7700 |
| FERGUSON | — 3V31 - 3V29 - 3V23 - 3V22 - 3V16 |
| MITSUBISHI | — SH303B - SH304B - SH310B - R00302 - SOH300 -
SS300B - VO320B - V330FR |
| NORMENDE | — RO500 - VOV100 - VOV101 - VOV500 |
| G.E.C. | — VO4001 - SO4000 |
| TATUNG | — SO8300 - FISHER - VOO615 - VOO520 |
| AKAI | — RVS5EK |
| BETAMAX | — SONY - C9 - C7 - C6 - C5 - FLC9UB - RO8080 - SO8000 -
SCC6UB - VC40UB - VOC6UB |
| SANYO | — VTC500 - VTCM10 - TO5150 |
| TOSHIBA | — TO9600 |

ALL PRICES ARE BASED ON QUANTITY AND + 15% VAT.

UNIT 439
OAKSHOTT PLACE
WALTON SUMMIT IND. EST.
PRESTON (M6 Junc. 29)
0772 312101

48-52 PERSHORE STREET
BIRMINGHAM
021-622-1023
021-622-1517

HUSSAIN CENTRAL T.V. LTD.

THE LARGEST RANGE AT THE LOWEST PRICES IN THE U.K.

B GRADE T.V.s – REMOTE – TEXT & STEREO TEXT

LATE LATE MODEL T.V.
GRUNDIG TEXT 7400, 6400, AND 16" TEXT
100's in stock

VIDEO CAMERA, CAMCORDS, VRC100P, SANYO
LATE LATE TANDBERG - PANASONIC - SONY - SANYO -
ITT - FERGUSON TX - G11 TEXT
20-20 VIDEO, working £30, untested from £8
V.H.S. VIDEO, untested – *100's in stock*

STILL THE No. 1 FOR EX-RENTAL T.V.s

LARGE STOCKS OF QUALITY T.V.s

200 T.V.s A DAY ARRIVING AT OUR PRESTON BRANCH.
WHY NOT COLLECT STRAIGHT FROM OUR LORRY? RING
FOR DETAILS AND DELIVERY ARRANGEMENTS OR
LOADS DIRECT FROM SOURCE TO YOUR DOOR.

ALL PRICES ARE BASED ON QUANTITY AND + 15% VAT.

01-807-4090
01-884-1314
CEDAR HOUSE
NOBEL ROAD
ELEY ESTATE
EDMONTON
LONDON N9.

0291-271000
UNIT 4
BULWARK INDUSTRIAL EST.
CHEPSTOW
GWENT.

FREE

★ 10 YEAR ★
GUARANTEE

CHROMOVAC

QUALITY REBUILDS

**SPECIAL
OFFERS**
ON
INLINE

Get on the hot-line today!

SUPERIOR QUALITY TUBES **051**
DELTA RE-BUILDS 428 8777
most types of Inline Re-builds or
new ex-stock ★ FREE 10 YEAR GUARANTEE
ON ALL OUR TUBES

Delta Rebuilds

Up to 19"	£28
Up to 22"	£30
Up to 26"	£34
110° up to 22"	£34
110° up to 26"	£38
Low focus	+£2
A47 342 New	£28
17FHP New	£30
470EHB New	£30
Delta only. Less 5% 5+	

Inline Rebuilds

Up to 22"	£40
Up to 26"	£45
A56 - 540x	£56
A66 - 540x	£58
Bonded Coil	+£5

ALL SIZES OF
NEW MONO TUBES
AT COMPETITIVE PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

Please enquire types not listed

370 HFB-A37-590.....	£45	560 DMB	£62
370 HUB	£45	AXT 56-001	£62
AXT 37-001	£45	660 AB	£65
420 CSB	£45	A67-701	£65
420 EDB-A42-590	£45	670 CZB	£65
420 EZB	£45	A66-540	£65
420 ERB	£45	420FSB	£55
470 KUB	£50		
510 UFB/A51-590.....	£55		
510 VSB	£60		
AXT 51-001	£60		
560 DYB-560 DTB	£62		
560 EGB	£62		
560 CGB	£62		

CARRIAGE
£5 Singles. 2-3 £10. 4 £12
10 £15. 10+ Carriage paid
EXCLUSIVE OF VAT
TERMS
Cash with order

QUANTITY
DISCOUNT
AVAILABLE
Ask for details

★ ASK FOR DETAILS. OUR TECHNICAL DEPT.
WILL ADVISE YOU ON PROBLEMS YOU MAY
ENCOUNTER ON FITTING INLINE TUBES

DELIVERY: Ex stock items immediate dispatch on receipt of order.
Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

CHROMOVAC

CHROMOVAC LTD. UNIT 7, BEAR BRAND COMPLEX,
ALLERTON ROAD, WOOLTON, LIVERPOOL 25

Ask for Mr Butterworth or Betty Ford ON: 051-428 8777

SPECIAL OFFER THIS MONTH

PHILIPS YEARS AHEAD
THE CREDIT CARD CALCULATOR
SOLAR POWERED £6.00

NEW PANELS

THORN 4000 LOPT Panel	£15.00
G11 IF Panel	£8.00
THORN 9600 Line Panel	£12.00
G11 Decoder Panel	£12.00
POWER SUPPLY 731	£6.00
G11 611 Condenser 470/250V	89p
G9 Power Panel	£3.50
G9 Frame	£8.00
KT4-KT3-K30 Hands. Replacement	£8 set.
HT520 METER 20,000 Fuse Diode Protector Logic Test Facility	£15.90
9000 SERIES Decoder 01 929 014 080 Thorn	£5.00
THORN TX remot panel. 5I.C. ML923-SL490-MC14528B-MC14493P-SL470 & Main Trans	£5.00
HITACHI LOPT Split Diode 2432871	£7.00
RANK T20 Fouces Pot	75p
RANK 718 Fouces Pot	£1.00
THORN 9000 LOPT Panel	£12.00
26" HITACHI LOPT Split Diode 2432301	£8.00
16" HITACHI LOPT Split Diode 2433481	£6.00
HITACHI Transformer P2270851	50p
HITACHI AE Socket	30p
1 CONDENSER Axial Leads 450 A/C 1200 D/C	15p
MAINS TRANSFORMER 240v in/20v/8v	£1
GREEN LED Flat 1000	£20. Type
CANON Tape Motor 6v	35p
MICROPHONE with Switch	25p
HITACHI 6 x 4 - 8Ω Speaker	50p
ET596 UHF V/CAP Tuner, small	£2.50
FIDELITY Panels with I.C.	£1.00
FIDELITY LOPT Split Diode AT2076/80	£3.00
FIDELITY FBS 1245AE LOPT Mono	£1.00
FIDELITY Split Diode FCC2015BE	£5.00
HI-FI MICROPHONE N8501 Philip	£8.00
G8 TUNER V/CAP on Panel	£3.50
THORN 9000 Sound OP Panel	£30p
THICK FILM, Hitachi RB-32 4A	£2.00
THICK FILM, Hitachi Frame	£5.00
K9 THORN Tuner Panel with ICS Pots	£3.00
80 Ω THORN Speaker	15p
9000 Speaker	£1.00
HITACHI Split Diode 2433752	£6.00
THORN CHASSIS 1600-1700 Series Mono	£10.00
THORN 1600 Rec- & Anode Cap	50p
ET-614 UHF V/CAP Tuner	£2.00
6 x 2 1/4 SPEAKER 5W Hitachi 8Ω	50p
K35 20 Turn Pots	6p each
K35 12 way Push Button Unit	£1.50
K35 L.O.P.T. Split Diode	£6.00
RANK T20 Front Panel	£6.00



SENDZ COMPONENTS

63 BISHOPSTEIGNTON,
SHOEBURYNNESS, ESSEX SS3 8AF.
SAME DAY SERVICE

All items subject to availability.
No Accounts: No Credit Cards.
Postal Order/Cheque with order
Add 15% VAT, then £1 Postage.
Add Postage for Overseas.

Callers: To shop at
212 LONDON ROAD, SOUTHEND.
Tel. 0702-332992

Open 9-1/2.30-6. GVMT + school orders accepted on
official headings. Add 10% handling charge.

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US			G.G.L. COMPONENTS 108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY PHONE (0228) 20358/39693			BUY WITH 		E.H.T. TRAYS	
								OECCA 80..... 7.29 OECCA 100..... 7.35 ITT CVC 20/30..... 6.85 PHILIPS G8-550..... 7.90 PHILIPS KT3..... 9.75 RBM T20/T2ZA..... 7.35 THORN 8500/8800..... 7.60 THORN 9000..... 8.70 Universal..... 5.95	
INTEGRATED CIRCUITS			TRANSISTORS			THORN/SONY		DIODES	
TYPE PRICE (£)			TYPE PRICE (£)			TYPE PRICE		TYPE PRICE	
AN214..... 1.95	SAS570S..... 1.95	TDA440..... 3.25	BC107..... 14	BD439..... 70	2N3055..... 50	LARGE RANGE OF SPARES FOR ABOVE MAKES OF TV/VIDEOS INCLUDING INSTRUCTION AND SERVICE MANUALS. PHONE OR WRITE FOR NEW LISTS. WE CAN ALSO SOURCE & SUPPLY OVER THREE THOUSAND VCS & SEMI CONDUCTORS.			
AN301..... 3.45	SAS580S..... 2.40	TDA1002..... 1.50	BC108..... 14	BD707..... 1.05	2N3773..... 3.45	SONY SPARES C5/C7 Rewind Kit... 4.65 C5/C7 Belt Kit..... 3.50 C6 Rewind Kit..... 4.35 C7 Pinch Roller..... 4.85 SG 613/6533..... 8.95 CX 143A..... 6.95 TDA 3652..... 4.35 Large range of Sony spares available			
AN303..... 3.45	SAS590S..... 2.40	TDA1003..... 2.80	BC109..... 14	BF337..... 28	15/80H..... 2.25	HITACHI VCS STR 441..... 8.95 STR 451..... 8.95 STR 6020..... 7.90			
AN305..... 3.50	SL1430..... 1.95	TDA1006A..... 2.95	BC141..... 26	BF338..... 30	15/85R..... 2.25	SUNDRIES G8 TRANSOUCTOR 2.25 G8 ON/OFF SW. 1.40 G11 E/W Coil 1.65 G11 n Coil 1.80 G11 EHT Lead 1.35 G11 EHT Lead 2.25 PYE IF Gain MOD 7.85 ITT On/Off SW 1.10 THORN On/Off SW 1.00 CUT OUT 2A 1.95 TX10 FOCUS UNIT 8.95 VCR Pilot Bulb 7.90			
AN7110..... 1.93	SL1432..... 1.75	TDA1035T..... 2.75	BC142..... 23	BF458..... 30	2SA 771..... 2.35	VALVES PCF802..... 1.09 PCL82..... 97 PCL85..... 1.03 PCL86..... 1.07 PLS04..... 1.59 PLS08..... 2.39 PL509/519..... 5.99 PY500A..... 2.25			
AN7114E..... 2.33	STK0039..... 6.45	TDA1037..... 1.95	BC147..... 09	BF459..... 36	2SA 835..... 1.55	LINE O/P TR. DECCA 80..... 7.95 DECCA 100..... 8.50 ITT CVC 20..... 7.75 ITT CVC 25/30/32..... 8.00 ITT CVC 45..... 8.45 PHILIPS G8..... 8.75 PHILIPS G11..... 13.50 PHILIPS KT3..... 9.95 PHILIPS K30..... 16.50 RBM T20A..... 11.50 THORN 1615..... 12.35 THORN 1690/1..... 9.65			
AN7115..... 2.37	STK0050..... 5.95	TDA1044..... 3.10	BC149..... 09	BF757..... 75	2SB 618..... 2.45	Available also a range of 2SA/B/C/D Transistors. Phone or write for lists.			
AN7116..... 2.37	STK0077..... 7.25	TDA1170..... 1.80	BC152..... 10	BFR90..... 1.60	2SC 867A..... 3.25	ORDERING Please Add 50p For P/P U.K. Add 15% VAT To This Total. Export Orders — Cost. DELIVERY BY RETURN ON ALL STOCK ITEMS.			
AN7116E..... 2.35	STK0078..... 7.45	TDA1270..... 2.20	BC157..... 10	BR100..... 18	2SC 1034..... 4.35				
AN7145..... 3.25	STK082..... 9.75	TDA1470..... 3.65	BC158..... 11	BR101..... 32	2SC 1061..... 1.15				
BA312..... 1.25	STK415..... 9.66	TDA2002..... 1.85	BC159..... 11	BR103..... 55	2SC 1114..... 4.75				
BA511A..... 1.95	STK430..... 7.75	TDA2003..... 2.33	BC237..... 11	BR303..... 2.95	2SC 1124..... 97				
BA521..... 1.85	STK433..... 6.50	TDA2004..... 3.15	BC327..... 11	BT106..... 1.15	2SC 1316..... 3.20				
BA532..... 1.95	STK435..... 6.75	TDA2006..... 2.25	BC328..... 12	BT116..... 1.30	2SC 1413A..... 3.95				
BA536..... 2.55	STK437..... 7.25	TDA2020..... 2.95	BC337..... 11	BT151/800R..... 1.10	2SC 1739..... 2.45				
HA1166..... 2.65	STK439..... 7.55	TDA2190M..... 4.95	BC338..... 10	BU126..... 1.78	2SC 1942..... 2.95				
HA1322..... 2.10	STK459..... 7.35	TDA2522..... 1.80	BC547..... 10	BU205..... 1.42	2SC 1962..... 1.65				
HA1338..... 2.40	STK461..... 7.95	TDA2523..... 2.25	BC548..... 10	BU208A..... 1.45	2SC 1969..... 1.95				
HA1339..... 2.40	STK463..... 8.30	TDA2530..... 2.10	BC557..... 10	BU208D..... 1.85	2SC 2078..... 1.55				
HA1342A..... 2.20	STK465..... 9.95	TDA2532..... 2.20	BD124M..... 1.05	BU326A..... 1.48	2SC 2335 (Kit)..... 7.55				
HA1366 W/W/R..... 1.95	TA7193P..... 4.30	TDA2540..... 1.95	BD131..... 33	BU407..... 1.12	2SC 2369..... 3.25				
HA1370..... 2.75	TA7202..... 2.25	TDA2560..... 1.80	BD132..... 33	BU407D..... 1.45	2SD 588A..... 1.97				
HA1374..... 3.80	TA7204P..... 1.90	TDA2578A..... 3.25	BD201..... 80	BU500..... 1.80	2SD 725..... 7.95				
HA1377..... 3.80	TA7205AP..... 1.40	TDA2581..... 2.15	BD202..... 70	BU508A..... 1.95	2SD 870..... 5.95				
HA1388..... 4.20	TA7208P..... 1.95	TDA2582..... 2.20	BD222..... 50	BU526..... 2.00					
HA1397..... 3.90	TA7222AP..... 1.85	TDA2591..... 2.30	BD225..... 55	BU807..... 1.30					
LA1201..... 1.75	TA7223P..... 2.85	TDA2593..... 2.30	BD235..... 32	BU826A..... 3.20					
LA1230..... 2.30	TA7277P..... 2.95	TDA2594..... 2.95	BD236..... 43	R2010B..... 1.45					
LA1365..... 2.45	TA7310..... 1.55	TDA2600..... 5.95	BD237..... 40	R2540..... 2.35					
LA350..... 1.65	TA7313..... 1.45	TDA2611A..... 1.50	BD238..... 39	TIP31C..... 46					
LA4031..... 2.45	TAA550..... 4.43	TDA2640..... 2.40	BD410..... 50	TIP32C..... 47					
LA4032..... 2.30	TBA120AS..... 95	TDA3561A..... 5.35	BD434..... 50	TIP33..... 80					
LA4101..... 1.50	TBA120SB..... 90	TDA3562A..... 5.50	BD437..... 70	TIP34..... 95					
LA4102..... 1.95	TBA120U..... 1.25	TDA4600..... 2.85	BD438..... 78	TIP42C..... 48					
LA4400..... 2.50	TDA9503..... 2.35	TDA9503..... 2.35	UPC555C..... 70	TIP47..... 75					
LA4430..... 2.45	UPC566C..... 2.10	UPC566C..... 2.10	UPC585C..... 1.40	TIP2955..... 70					
LA4440..... 3.55	UPC1031H..... 2.95	UPC1031H..... 2.95	UPC1032H..... 95	TIP3055..... 70					
LA4460..... 2.95	UPC1156H..... 2.45	UPC1156H..... 2.45	UPC1181H..... 2.20						
LA4461..... 2.95	UPC1182H..... 2.20	UPC1182H..... 2.20	UPC1185H..... 3.30						
MB3712..... 2.30	UPC1230H..... 3.95	UPC1230H..... 3.95	UPC1230H..... 3.95						
MB3713..... 2.25	UPC1238H..... 2.35	UPC1238H..... 2.35	UPC1350C..... 4.50						
ML2318..... 2.35	UPC1350C..... 4.50	UPC1350C..... 4.50	UPC1353C..... 2.60						
ML2328..... 2.55	UPC1365C..... 5.05	UPC1365C..... 5.05	UPC2002H..... 1.85						
ML2328..... 2.55									
SAA1124..... 3.45									
SAA1125..... 4.70									
SAA1250..... 3.85									
SAA1251..... 4.95									
SAA5010..... 5.10									
SAA5012..... 5.70									
SAF1032P..... 3.25									
SAF1039P..... 4.55									
SAS560S..... 1.95									

TELEPART



Telegen-1
 PRICE £18.35 (Inc. VAT)
 * EXCEPTIONALLY LIGHT AND DURABLE
 * POCKET SIZE FOR OUTSIDE SERVICE
 * P3 BATTERY POWER SOURCE
 * FIVE DIFFERENT TEST PATTERNS FOR COLOUR & MONO TV
 * CROSSHATCH GRID * DOT MATRIX
 * WHITE RASTER
 * HORIZONTALS * VERTICES
 * 3.5mm JACK SOCKET FOR OPTIONAL P.S.U.

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.



Telegen-2
 PRICE £34.45 (Inc. VAT)
 * EXCEPTIONALLY LIGHT & DURABLE
 * COMPACT 10 x 12 x 4.5 cms
 * RED RASTER * GREEN RASTER
 * BLUE RASTER
 * COLOUR BARS
 * 3.5 mm JACK SOCKET FOR P.S.U.
 * PROVIDES UHF SIGNAL APPROX. CHANNEL 35

Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect complement to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

Power Supply
 A switchable power supply ideally suited to both Telegen 1 and Telegen 2.
 PRICE £4.55 (Inc. VAT)
 ALL ITEMS POST AND PACKING £1.44 (Inc. VAT)
 All goods should be delivered within 4 working days.
32 TEMPLE STREET, WOLVERHAMPTON
WV2 4AN. TEL: (0902) 773122

MAKE YOUR INTERESTS PAY!!

Train at home for one of these Career Opportunities

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE INFORMATION PACK on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/>	Radio, Audio & TV Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds)	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Elec. Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>

GCE over 40 'O' & 'A' level subjects

Name: _____
 Address: _____
 P. Code _____

ICS International Correspondence Schools,
 Dept. EGS26, 312/314 High St., Sutton, Surrey
 SM1 1PR. Tel: 01-643 9568 or 041-221 2926
 (both 24 hours).

INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT

**LEADER LCT-910A
C.R.T. TESTER-REJUVENATOR**

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.


- ★ Tests for shorts and leakage between electrodes.
- ★ Tests cathode emission characteristics.
- ★ Separately checks condition of guns.
- ★ Removal of shorts and leakage between electrodes.
- ★ Checks heater warm-up characteristics.
- ★ Rejuvenation of low emission cathodes with automatic timing.
- ★ Super rejuvenation with manual control.
- ★ Complete with tube base adaptors.

Size: H 230mm W 330mm D 120mm.



PRICE £210 + £31.50 VAT

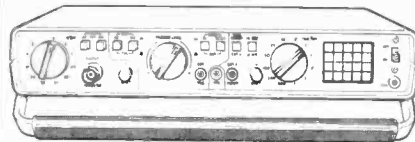**THE VERY LATEST SC110A LOW POWER,
FULLY PORTABLE OSCILLOSCOPE.**



The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope.

FITS IN A BRIEFCASE

Full Sized Performance

- 10 MHz bandwidth.
- Full trigger facilities are provided including TV frame, or TV filtering.
- Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
- Size 255mm x 148mm x 50mm.

PRICE £165.00 + £24.75 VAT

Accessories: Carry Case £5.95 + £0.89 V.A.T.
 x 1 Probe £7.50 + £1.13 V.A.T.
 x 10 Probe £8.50 + £1.28 V.A.T.
 x 1/x 10 Switched Probe £10.50 + £1.58 V.A.T.
 AC Adaptor £6.95 + £1.04 V.A.T.

ALSO AVAILABLE
 Analogue Multimeters
 Digital Multimeters
 Oscilloscopes
 Signal Generators
 Digital Frequency Meters
 Pattern Generators
 CRT Tester/Rejuvenator
 T.V. Field Strength Meter
 Digital Capacitance Meter
LARGE S.A.E.
FOR COMPLETE LIST.


LOPT TESTER

**BK's REVOLUTIONARY DYNAMIC
'LOPT' TESTER**
 Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal.
 Size 75x100x40 mm. Supply 240V AC


PRICE £25.99 + £3.VAT

**LEADER HIGH VOLTAGE
METER EHT PROBE**

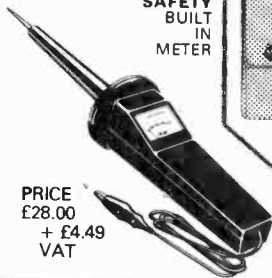Measures up to 40 K.V. D.C. with **SAFETY BUILT IN METER**




PRICE £28.00 + £4.49 VAT

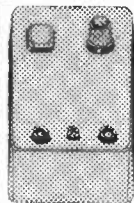

CRT TESTER-REJUVENATOR

BK's C.R.T. TESTER-REJUVENATOR
 Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC


PRICE £32.00 + £4.80VAT

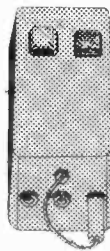

**HAMEG HM 203-5 20MHz
DUAL TRACE OSCILLOSCOPE**

SPECIFICATION:

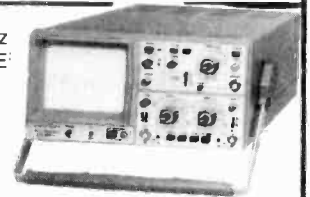- BANDWIDTH DC-20MHz
- SENSITIVITY CH1, CH2 2mV-50V/DIV
- TIMEBASE 40ns to 0.2S CM
- TRIGGER DC-40MHz Auto-Normal-TV
- CALIBRATION OUTPUT
- CH1 ADD AND INVERT FACILITY
- ALT/CHOP SWITCH
- LARGE RECTANGULAR SCREEN 8 x 10 cms.
- BUILT IN SEMICONDUCTOR COMP. TESTER
- SIZE 285mm x 145mm x 380mm.
- SUPPLY 110-125-220-240V AC 50-60Hz



**WITH COMPONENT
TESTER**

PRICE £270.00 + £40.50 VAT
 Optional probes as above

2 YEAR WARRANTY

*** FULLY
GUARANTEED**

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.



B. K. ELECTRONICS Dept. 'T'

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,
 ESSEX, SS2 6TR TEL: 0702-527572




Satellite TV System

Satellite TV is now available in the U.K. This heralds the start of a new television era. Connexions have now available the first low cost satellite signal receiving system designed for the consumer market.

With this equipment up to fourteen new channels of entertainment and information are available to the consumer - whether private home, pub, club, disco, hotel, restaurant or educational establishment.

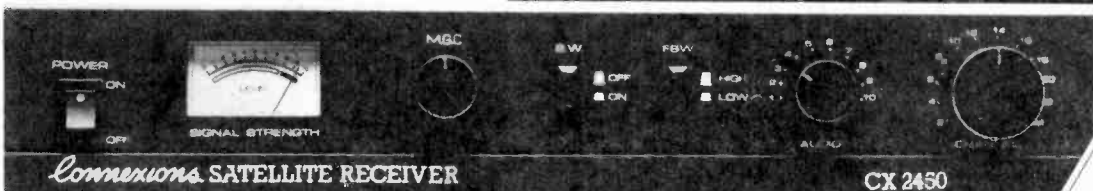
The channels currently available are broadcasting a wide range of top quality material including current cinema films, national/international and minority sports, pop videos, childrens programmes, news channels and general entertainments.



Connexions SATELLITE RECEIVER

CX 2450

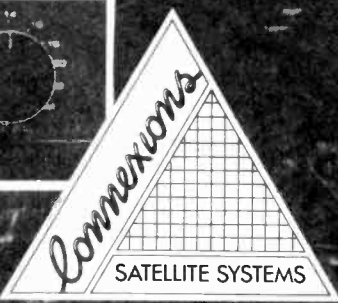
Full Band satellite systems are available at £1295 plus VAT & carriage. Trade and dealership enquiries welcome.



Connexions Satellite Systems Ltd

125 East Barnet Road, New Barnet, Herts. EN4 8RF Telephone: 01-441 1282 (5 lines) Telex: 295181 SMC G

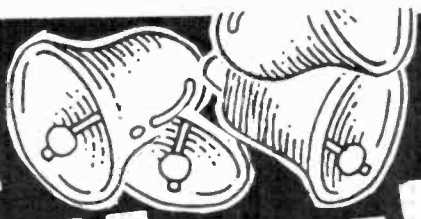**We've Rung
out the Old
& we're
Bringing in the New!**



Due to the tremendous success of our Christmas
Clearout Sale, we have now made way for

MASSIVE STOCKS

**OFF VCR'S
VCR'S
CTV'S
CTV'S
CTV'S
AUDIO**

Quantity Consistent
with Quality



etc



SO WHY NOT BUY FROM THE BEST?
OPEN 6 DAYS WEEKLY AND SUNDAY BY APPOINTMENT AT
Kent Ledgerwood Wholesale Ltd.

BRADFORD
TRITEL TV
1043 Leeds
Road
Thornbury
Roundabout
BRADFORD

LEEDS
TRITEL
DISCOUNT
STORES
Long Row
Horsforth
LEEDS

LUTON
WESTSIDE TV
29/31 West Side
Centre
LUTON

SCOTLAND
TRITEL TV
Unit 4
Peacock Cross
Industrial Estate
Burnbank Road
HAMILTON

LONDON
WEMBLEY TV
Unit 4
Fourth Way
Off South Way
Behind Wembley
Stadium
WEMBLEY

Tel: 0274 665670

Tel: 0532 590252

Tel: 0582 24177

Tel: 0698 282141

Tel: 01 903 7587

EAST CORNWALL COMPONENTS

NEW 1986 CATALOGUE is now available - range of components greatly increased - over 136 pages fully illustrated. Price £1.00 per copy (free upon request with orders over £15). Includes 50p Credit Note, Special Offer Sheets, Order Form and Pre-Paid Envelope. Order your copy now - will be despatched within 7 days.

VALVES		TRANSISTORS + DIODES				Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
Type	Price (£)	Type	Price (£)	Type	Price (£)	BC327	0.16	BF117	0.50	BFY52	0.22	BV199	0.72	TIP33A	0.55	2SC2029	2.70	74LS112	0.44
DY802	0.95	AC127	0.28	BC117	0.22	BC328	0.16	BF119	0.82	BFY90	1.34	BY206	0.16	TIP44	0.70	2SC2078	1.05	74LS113	0.40
DC887	0.66	AC128	0.30	BC118	0.16	BC338	0.12	BF125	0.42	BR100	0.25	BY210/600	0.21	TIP42	0.42	2SC2091	0.70	74LS114	0.39
YYB1	1.00	AC128K	0.34	BC119	0.28	BC350A	0.24	BF127	0.41	BR101	0.40	BY210/600	0.21	TIP47	0.42	2SC2094	2.80	74LS122	0.68
EC282	0.92	AC141	0.58	BC125	14	BC351	0.16	BF154	0.14	BR103	0.50	BY210/800	0.28	TIP211	0.63	2SC2314	0.80	74LS124	1.15
EC083	1.00	AC141K	0.38	BC140	0.27	BC440	0.36	BF157	0.46	BR303	0.25	BY228	0.46	TIP2955	0.70	2SC2335	1.50	74LS126	0.50
CC884	0.80	AC142	0.56	BC141	0.24	BC441	0.40	BF158	0.30	BR339	0.50	BY238	0.65	TIP3055	0.58	2SK135	3.80	74LS132	0.60
CC885	0.95	AC142K	0.38	BC142	0.24	BC461	0.58	BF160	0.23	BRV56	0.42	BY238	0.65	TIP3055	0.58	3N211	3.52	74LS135	0.26
CC888	1.25	AC151	0.45	BC143	0.26	BC478	0.24	BF167	0.32	BSY19	0.32	BY310	0.20	TSI43	0.88	3N211	3.52	74LS136	0.42
ECF80	1.20	AC152	0.45	BC147	0.18	BC516	0.48	BF177	0.42	BSX20	0.70	BYX36/150	0.40	TSI90	0.27	3SK88L	1.60	74LS138	0.44
ECF81	1.40	AC153	0.57	BC147B	0.14	BC547	0.12	BF178	0.28	BSX59	0.38	BYX36/600	0.48	TSI20	2.45	40636	1.85	74LS139	0.58
ECF84	0.80	AC153K	0.46	BC148	0.10	A or B	0.10	BF180	0.27	BSX76	0.65	BYX48/300	0.70	Y278	0.14	40673	1.80	74LS145	1.64
ECF88	1.50	AC176	0.30	BC148B	0.12	A or B	0.10	BF181	0.27	BSY52	0.35	BYX54/600	0.30	Y969	2.80			74LS147	0.93
ELC82	1.10	AC176K	0.38	BC149	0.10	A or B or C	0.10	BF182	0.32	BSY54	0.25	BYX71/600	1.18					74LS148	1.28
ELC86	1.75	AC187	0.28	BC149C	0.14	BC549	0.10	BF183	0.32	BT100A/02	0.90	Y212	0.78	Z7107	0.14	74LS00	0.24	74LS148	1.28
EF80	0.75	AC187K	0.38	BC157	0.10	A or B	0.10	BF184	0.30	BT101/300	2.75	C106D (400V)	0.48	ZX502	0.22	74LS01	0.24	74LS149	0.70
EF86	1.80	AC188	0.28	BC158	0.12	BC550	0.10	BF185	0.18	BT101/500	3.25	C106F (50V)	0.36	IN4001	0.04	74LS02	0.24	74LS155	0.55
EF183	0.90	AC189K	0.38	BC159	0.12	A or B	0.10	BF190A	0.25	BT102/300	3.60	D40N11	1.08	IN4003	0.05	74LS03	0.24	74LS157	0.45
EF184	1.00	AC272	1.50	BC160	0.14	BC557	0.10	BF195	0.12	BT108	1.15	E5202	0.30	IN4004	0.05	74LS04	0.24	74LS158	0.58
EH90	0.98	AD142	0.88	BC160	0.30	BC558A	0.10	BF200	0.30	BT108	1.25	E5204	0.30	IN4006	0.07	74LS05	0.24	74LS160	0.62
KT66(G.E.C.)	16.00	AD143	1.10	BC161	0.30	BCY70	0.16	BF222	0.38	BT109	1.15	E5204	0.30	IN4007	0.07	74LS06	0.24	74LS161	0.68
KT88(G.E.C.)	19.00	AD149	0.72	BC168B	0.20	BCZ10	3.21	BF224	0.16	BT116	1.20	ET872	0.60	IN4148	0.04	74LS09	0.24	74LS161	0.68
EL34	3.25	AD167	1.20	BC169C	0.12	BCZ11	2.60	BF224J	0.20	BT119	3.30	ET881	1.70	IN5400	0.12	74LS10	0.24	74LS163	0.68
EL84	1.00	AF102	0.52	A or B or C	0.10	BD124P	0.70	BF240	0.30	BT120	3.50	ET882	1.90	IN5402	0.13	74LS11	0.24	74LS164	0.74
EL509	7.85	AF115	2.10	BC171	0.10	BD130Y	0.68	BF244	0.34	BT121	2.99	IT2201	0.44	IN5403	0.16	74LS12	0.24	74LS165	1.10
EM87	2.55	AF116	2.10	A or B	0.10	BD131	0.36	BF244A	0.30	BT121	2.99	IT2203	0.34	IN5406	0.16	74LS13	0.24	74LS166	1.50
EV86/87	0.67	AF121	0.56	BC172	0.12	BD132	0.36	BF257	0.22	BT121	2.99	IT2203	0.34	IN5408	0.16	74LS14	0.33	74LS168	1.48
EV900A	2.50	AF124	0.42	A or B	0.12	BD135	0.26	BF258	0.26	BU100A	2.30	MEU021	0.62	IN5920	0.07	74LS19	0.44	74LS173	0.98
PC084	0.95	AF125	0.58	BC177	0.24	BD136	0.26	BF259	0.26	BU101	1.40	MJ2955	1.00	2N2122A	0.34	74LS20	0.24	74LS174	0.75
PC085	1.75	AF126	0.58	A or B or C	0.24	BD137	0.26	BF262	0.26	BU105	1.20	MJ2955	1.00	2N2222	0.30	74LS22	0.24	74LS175	0.82
PC089	0.75	AF127	0.38	BC182	0.10	BD138	0.30	BF263	0.38	BU105/02	1.75	MJ3000	1.80	2N2904A	0.48	74LS24	0.24	74LS179	0.80
PC8189	0.85	AF139	0.40	A or B or C	0.10	BD139	0.30	BF270	0.10	BU108	1.20	MJ3440	0.46	2N2926G	0.14	74LS26	0.24	74LS182	0.98
PCF80	0.95	AF178	2.28	BC182L	0.10	BD140	0.28	BF271	0.28	BU124E	1.98	MJE250	0.44	2N3053	0.30	74LS27	0.24	74LS194	0.75
PCF86	1.25	AF239	0.50	LA LD LC	0.10	BD142	1.26	BF273	0.22	BU126	1.40	MJE2955	1.60	2N3054	0.60	74LS28	0.24	74LS195	0.74
PCF200	0.95	AF295	1.40	BC183	0.10	BD145	1.82	BF274	0.34	BU133	1.90	MJE3055	1.60	2N3055	0.65	74LS30	0.24	74LS196	0.84
PCF801	1.05	AL100	5.40	A or B	0.10	BD150A	0.28	BF284	0.46	BU204	1.30	MPSA05	0.30	2N3703	0.10	74LS32	0.24	74LS197	0.84
PCF802	1.05	AL102	4.40	BC183L	0.10	BD160	1.58	BF336	0.32	BU205	1.30	MPSA10	0.30	2N3904	0.20	74LS37	0.24	74LS221	0.85
PCF806	1.20	ASV80	5.20	LA LB LC	0.10	BD165	0.45	BF337	0.28	BU206	1.50	MPSL01	0.34	2N3904	0.20	74LS37	0.24	74LS240	0.80
PCL82	1.00	ASZ17	2.00	BC184	0.10	BD183	0.70	BF338	0.28	BU208	1.40	MPSU05	1.05	2N3906	0.20	74LS38	0.24	74LS241	0.80
PCL83	2.50	AU110	2.80	A or B or C	0.15	BD201	0.52	BF355	0.35	BU208A	1.05	MPSU06	1.18	2N5294	0.80	74LS40	0.24	74LS242	0.94
PCL84	1.40	AY102	4.40	BC212	0.15	BD204	0.50	BF357	0.27	BU326S	1.75	MPS502	0.40	2N6107	0.80	74LS42	0.50	74LS243	0.94
PCL86	1.00	B40C200	1.03	BC212 L	0.10	BD204	0.50	BF371	0.24	BU407	1.10	MR854	0.07	25C1098	0.84	74LS44	0.85	74LS247	1.20
PCL805/85	1.05	BA110	0.68	A or B	0.10	BD222	0.80	BF422	0.20	BUX80	3.70	OA91	0.07	25C1172Y	1.70	74LS51	0.24	74LS251	1.20
PD500	2.90	BA115	0.14	BC212 C	0.09	BD225	0.40	BF450	0.38	BUV20	2.75	OC26	2.65	25C1173Y	0.88	74LS52	0.30	74LS252	0.75
PFL200	1.85	BA121	0.40	LA LB	0.10	BD232	0.45	BF450	0.38	BUV20	2.75	OC35	1.75	25C1279	0.50	74LS73	0.30	74LS257	0.75
PL33	1.50	BA129	0.38	BC213	0.10	BD234	0.30	BF457	0.30	BUY69A	2.60	OC36	4.75	25C1306	0.92	74LS74	0.33	74LS258	0.73
PL36	1.75	BA148	0.16	A or B or C	0.24	BD235	0.30	BF458	0.35	BUY69B	1.98	OC72	0.70	25C1307	1.50	74LS75	0.44	74LS259	1.20
PL81	0.85	BA155	0.12	BC213L	0.10	BD237	0.38	BF458	0.35	BUY71	0.80	OC73	0.70	25C1317	0.50	74LS76	0.38	74LS266	0.55
PL82	0.75	BA157	0.28	LA LB LC	0.10	BD237	0.38	BF458	0.35	BUY71	0.80	OC81	0.68	2AC1449	0.60	74LS82	0.82	74LS279	0.70
PL83	1.20	BB105G	0.30	BC237	0.11	BD410	0.76	BF461	0.32	BY122	0.60	OC81	0.68	2AC1449	0.60	74LS82	0.82	74LS279	0.70
PL84	0.75	BB105G	0.48	BC238	0.12	BD434	0.58	BF461	0.32	BY126	0.60	ORP12	0.85	25C1507	0.60	74LS85	0.25	74LS283	1.20
PL95	2.00	BB110B	0.42	BC251	0.14	BD438	0.58	BF471	0.68	BY127	0.60	ORP12	0.85	25C1507	0.60	74LS85	0.25	74LS283	1.20
PL504	1.40	BC107	0.16	A or B or C	0.10	BD439	0.85	BF473	0.68	BY133	0.06	R2008B	1.20	25C1678	1.00	74LS86	0.35	74LS289	0.80
PL508	2.70	A or B	0.12	BC262	0.20	BD441	1.00	BFV13	0.84	BY135	0.35	R2540	0.45	25C1758	0.68	74LS90	0.40	74LS335	1.10
PL509/519	5.25	BC108	0.10	A or B	0.28	BD507	1.05	BFV44	0.88	BY164	0.48	TC45	0.45	25C1923	0.30	74LS92	0.30	74LS366	0.58
PV88	1.80	BC109	0.10	BC301	0.30	BD520	1.20	BFX29	0.28	BY179	0.56	TC47	0.40	25C1945	2.88	74LS93	0.54	74LS367	0.50
V7500A	2.20	BC109	0.10	BC303	0.30	BD707	0.88	BFX90	6.78	BY184	0.38	TCI29	0.30	25C1953	0.70	74LS95	0.60	74LS368	0.50
J26	1.95	BC113	0.14	BC303A	0.14	BFZ85	0.35	BFY17	0.65	BY187	0.35	TIP30A	0.32	25C1957	0.70	74LS96	1.20	74LS373	1.00
UCH81	2.00	BC113	0.12	BC307A	0.18	BFV51	1.48	BFY21	0.65	BY188	0.75	TIP31C	0.35	25C1969	2.80	74LS97	0.40	74LS374	1.00
ULC82	1.80	BC115	0.12	BC317A	0.12	BDX32	0.12	BFY25	0.12	BY198	0.64	TIP32	0.35	25C2028	0.73	74LS109	0.44	74LS375	0.70
30FL12	1.60	BC116	0.12	BC323	0.90	BF115	0.32	BFY51	0.22	BY198	0.64								

CHART RECORDER SPECIAL

Brand new 3 channel pen recorders with charts with complete. Full spec. upon request.
Once only price **£40 + £10 p&p + VAT.**

Fuseholders

- 20mm Panel Mounting 0.28
- 20mm Chassis Mounting 0.06
- 1 1/4" Panel Mounting 0.35
- 1 1/4" Chassis Mounting 0.12
- Carline 1 1/4" holder 0.10

SOLDERING SECTION

Soldering Station complete with 30W or 40W Iron (state which) **67.95**

XS25 W Iron kit complete with steel & plug attached **10.00**

CS 18W, as above

Antex 15W iron 9.90

Antex 18W iron 5.75

Antex 25W iron 5.50

Antex elements 2.75

Antex bits 0.90

Antex stands 2.10


Soldersucc 4.50

Spare nozzles for Soldersucc 0.65

CAPACITORS

Metalised Paper

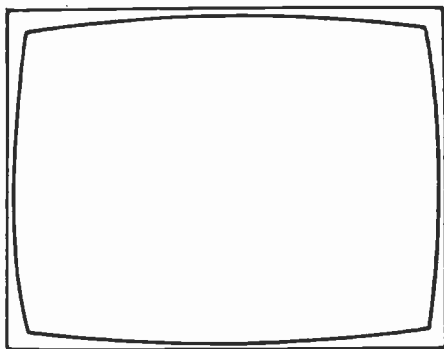- 22F 600V AC 24p
- 10nF 100V DC 22p
- 10nF 500V AC 30p
- 15nF 300V AC 30p
- 22nF 100V DC 32p
- 100nF 300V AC 46p
- 470nF 50V DC 69p



TELEVISION

Here We Go Again

Ever since TV has been a practical proposition there's been debate about standards. As is well known, the debate in the UK had not been resolved by the time TV broadcasting started in November 1936. The Selsdon Committee, which had been appointed by the government to advise on TV standards, had been unable to come to a conclusion. So we started off with dual-standard operation, using the Baird 240-line and EMI 405-line systems on alternate weeks. It didn't take long for the operational advantages of the EMI system to become apparent: the Baird system was dropped in February 1937.

The debate in the USA went on rather longer. In early 1933 RCA demonstrated all-electronic TV, using a 240-line system. As the depression was at its height there was no great urgency to get TV broadcasting started. By June 1936 however the FCC, which had been set up two years previously, started to take an interest. The Radio Manufacturers Association (RMA) proposed to the FCC a 441-line system. In October 1938 the FCC assigned channels for TV use and the RMA put forward slightly revised proposals (vestigial-sideband operation came in). TV broadcasting started on April 30th, 1939 – but on an experimental basis only, using the RMA system. The FCC still couldn't make up its mind and held further hearings in June 1940. In addition to the RMA standard Philco proposed a 605-line system and Du Mont a 625-line system. The industry became involved in a standards battle and the FCC wouldn't come to a decision (the same thing was to happen with teletext and stereo TV sound many years later). To end this unhappy situation – since a full, commercial service couldn't start without an agreed standard – the RMA set up the National Television Standards Committee which held its first meeting on June 31st, 1940. The debate continued and it wasn't till January 1941 that the NTSC made its first report to the FCC. It favoured a 441-line system, with f.m. sound. The FCC wasn't happy with a line standard dating from 1936 and asked the NTSC to have a further think. Two months later the NTSC came up with the 525-line system.

It wasn't long before standards debates were to be with us once more. In the UK the problem was what standard to adopt for post-war TV. In the event 405-line transmissions were restored, though other proposals were put forward. The decision seems to have been taken on the grounds that the public had already invested in 405-line sets (about 20,000 of them!) and that the BBC was ready to go with its 405-line equipment. It was left to Europe to take up the argument about standards. France adopted 819 lines while the rest of Europe eventually adopted 625 lines.

The only time when there appears to have been little debate on standards was the start of colour broadcasting in the USA. An experimental field sequential system had been tried in 1948 but had not been a commercial success. The sets were unreliable and the programmes few. In particular the system was non-compatible – you couldn't see the programmes in monochrome on a black-and-white set. RCA had been working on colour since before the war and by the late forties had notched up a series of advances: it demonstrated the shadowmask tube to the FCC in March 1950. During July and October 1951 RCA publicly demonstrated compatible colour TV and by November of that year had agreed a set of specifications with the NTSC. There was no competing colour TV system in sight and when RCA petitioned the FCC in June 1953 the RCA/NTSC system was accepted.

When it came to colour for Europe we were back with standards battles once more. During the mid-sixties the argument raged over NTSC, PAL, SECAM – all in various forms – and a few other proposals. It was never resolved. Today one can perhaps say that neither PAL or SECAM has any particular advantage over the other – technological advances have made the earlier disputes seem almost irrelevant.

The field of TV and video has been dogged by debates on systems and standards ever since. Which VCR standard to use, which disc system and what standard for satellite TV? The VCR and disc battles have differed from previous ones in that the broadcasting authorities have not been involved. While it's sometimes said that Beta gives a better picture, once again technical developments have ensured that no system has any great advantage in the longer run.

The debate over a system for European DBS broadcasting seems to have been decided in favour of the IBA developed MAC system – in conjunction with sound systems of continental origin. One can't be too sure until DBS services actually start – variants on PAL and SECAM have also been proposed.

We're by no means at the end of the road however. High-definition TV with an aspect ratio change is the next step being considered and here there are already the makings of a hot dispute. The Japanese developed a 1,125-line, 60Hz system some while back. It provides superb results and has received the backing of the Americans. The Japanese and Americans are now pushing for its acceptance as a world-wide HDTV standard. This would of course overcome the old problems of standards conversion and simplify the provision of studio/broadcasting equipment. But it's not compatible with existing services – we're back with the old compatibility problem. The alternative "Enhanced MAC" system developed by the IBA has the great advantage of compatibility with basic MAC. The additional picture information required for a 5:3 aspect ratio display is incorporated in some of the space otherwise devoted to sound signals: higher resolution is achieved by using some IBA developed techniques about which little has been publicly said.

A decision about HDTV standards will not be essential for some while, though the issue is to be considered by the International Radio Consultative Committee in May. The argument is hotting up. Oh yes: we forgot to mention the various (at least four) competing stereo TV sound systems and the arguments about teletext systems . . .

EDITOR

John A. Reddihough

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Pat Bunce
01-261 5942

Please note that the telephone numbers above are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 209.

COVER PHOTO

This month's front cover photo shows a close-up view of the head drum assembly used in the Panasonic Model NV870, which features VHS hi-fi sound. The cassette housing – it's a front loader – was removed to obtain a better view.

HELP WANTED

Does any reader know where spare parts/service data can be obtained for Nikkai colour sets, also the Perdio monochrome portable Model RP206?

Teletopics

JAPANESE-EEC AND INTERNATIONAL TRADE

The EEC Commission has increased the customs duty levied on imported VCRs (other than for professional use) from 8 to 14 per cent, effective from January 1st. To conform with GATT regulations, balancing cuts have been made on semiconductor device duties (down from 17 to 14 per cent) while duties on electronic calculators, portable radios, portable cassette decks and alarm radios have been completely removed. Most imported VCRs come from Japan of course though some are now coming from S. Korea. Talks with Japan on the extension of former agreements on export limitation to the EEC continue, though the Japanese Ministry of International Trade and Industry (MITI) has announced that these will be maintained – MITI will continue to monitor shipments of VCRs, also CTVs and tubes, cars, light commercial vehicles, forklift trucks and numerically controlled machine tools. For VCRs, MITI suggests that 1.5 to 1.7 million machines would be the appropriate export level for 1986. Japanese VCR exports to Europe during 1985 are expected to have been some 1.8m, well within the 2.25m level set by the previous voluntary export restraint agreement.

The next sensitive trade item is likely to be the compact disc player, which at present carries a 19 per cent import duty in the EEC. Japanese production capacity is understood to have grown by a factor of four last year to 4.3m units and is expected to more than double to 8.7m this year. A report by stockbrokers Vickers da Costa points out that such production levels are in excess of current demand: as a result price cutting is expected, especially in the EEC where prices are "relatively high". As if to emphasise the point, Sharp recently announced the first CD players in the UK at under £200. There are two models that differ only in styling: they both have a suggested retail price of £199. In the USA the price of CD players has fallen from around \$1,000 in 1983 to just under \$300.

Philips has doubled its share of the European VCR market since starting to produce and sell VHS machines. It claims to have 12 per cent of the UK market, which puts Philips in second place to Thorn EMI. Philips' share of the European market is estimated to have risen to 14 per cent last year. Its video business is understood to be close to break even point after past heavy losses. Production of V2000 system VCRs has now ceased – sales are expected to continue for a further six months or so while stocks last. Philips has also announced that the LaserVision disc player has been withdrawn from the W. German market. Its sale in the UK will continue.

NEW PLANTS

The S. Korean based Samsung Electronics group is understood to be close to a decision on where to establish a manufacturing facility in the UK. Sites in the NE and in the West Midlands have been under consideration. Samsung proposes to start manufacturing VCRs, television sets and microwave ovens in the UK. At present Samsung imports VCRs and microwave ovens from its Korean plants and 14in. colour sets from a plant in Portugal. Samsung has a 4.5 per cent share of the UK microwave oven market. The aim in the TV field would

be to develop and manufacture in the UK large-screen sets for the European market.

Hitachi has announced plans to convert part of its CTV plant at Anaheim, California to manufacture of VCRs. Initial capacity will be 100,000 VCRs a year, rising to 5-600,000 machines annually within two years if market conditions justify this.

GIANTS PLAN MERGER

The US General Electric Company (GE) has signed a £4.46bn agreement to take over the RCA Corporation. The aim of the deal is to strengthen the competitive position of the companies in high-technology manufacturing. It will be the largest non-oil merger in US company history, creating a corporation with annual sales approaching \$40bn, a workforce of over 400,000, and interests in aerospace, broadcasting, financial services, consumer and industrial electronics and heavy electrical manufacturing.

Both GE and RCA have a long history in consumer electronic equipment manufacture while RCA has broadcasting interests that include ownership of the NBC network. RCA demonstrated electronic TV broadcasting, using a 240-line system, in the early months of 1933 and in the forties developed the colour system that came to be known as the NTSC system. GE and RCA have both been major TV receiver manufacturers. GE now sells sets produced by Matsushita (see Teletopics, December 1985) while RCA assembles sets from parts imported from Mexico and Taiwan.

Both companies became conglomerates when this was fashionable in the sixties and seventies. GE's interests extended to cover coal mining and energy while RCA's extended to greetings cards, frozen foods and the Hertz car rental business. During the last few years both companies have been selling off businesses not related to their core activities. In 1984 GE had sales of \$28.9bn (13 per cent consumer products) and RCA \$10.1bn (22 per cent consumer products, 23 per cent broadcasting and 6.1 per cent records and video).

PHILIPS-DU PONT DISC VENTURE

Philips and the Du Pont Company of the USA have established a 50/50 joint venture company which combines their interests in optical information storage discs for the audio, video and data markets. The new company, called Philips/Du Pont Optical (PDO), aims to capture a major share of the world optical disc market, which is expected to exceed \$4bn a year by 1990. It's expected to generate annual sales of about \$900 within five years. Initial assets of the new company include 50 per cent of the PolyGram CD factory (the world's largest) in Hanover, W. Germany, and the LaserVision disc operation at Blackburn, Lancs. The company has announced plans to introduce a combined audio/video optical disc player to boost the consumer section of the optical electronics market. In addition to playing CD and video discs it will be possible to use the player with a microcomputer for data storage. The price of the player is expected to be around £370 initially.

THORN EMI TO SELL CABLE TV INTERESTS

Thorn EMI plans to sell off its cable TV interests which include the satellite delivered cable TV channels Music Box (50 per cent stake), Premiere (41.2 per cent stake) and The Children's Channel (wholly owned), also the cable franchises at Swindon (wholly owned), Coventry (51 per cent stake) and Ulster Cablevision (20 per cent stake).

It seems that all these operations are at present loss making, though Thorn EMI say that the decision to sell out is strategic – in order to concentrate on the firm's core business interests of technology, lighting, domestic equipment (including Ferguson) and the rental/retail outlets. Since our last column Thorn EMI has sold its cinema and film making business to a management-based group, leaving the cable interests rather out on a limb.

UK SATELLITE TV

The IBA's report on the prospects of establishing a UK DBS TV service was due to be presented to the government by the end of December. One of the companies that put forward proposals to the IBA is Carlton Communications, whose managing director Michael Green comments that he could put together a consortium of "significant companies" to run such a service – provided the operator could use a satellite system of his own choice and be given freedom over financing arrangements and programme scheduling (subject to normal decency standards). The IBA is expected to emphasise the need for an early start to DBS broadcasting and a completely commercial approach.

According to a Goodall Partnership survey sales of satellite TV receiving installations in the UK during the latter half of 1985 totalled some 1,800 – nowhere near this number of licences have been issued by the DTI however. It expects sales of about 30,000 installations over the next two years. The government has announced that from March planning permission will no longer be required to instal dish aerials of up to 0.9m at the front of a house – planning permission will still be required in national parks, conservation areas and areas of outstanding natural beauty.

THE 50MHz BAND

Terms for allocating the 50-50.5MHz band for use by radio amateurs have been finalised by the Department of Trade and Industry and become effective from February 1st, 1986. The conditions are as follows: the allocation shall be primary within the UK; class A licensees only will be permitted use of the band initially; maximum transmitting aerial height to be 20m above ground level, with horizontal polarisation; no mobile, portable or temporary-premises operation will be allowed; there will be no restriction on modes or hours of operation; no repeaters will be allowed; existing permits will be withdrawn. Use of the band by radio amateurs is based on non-interference to European broadcasting services.

FIFTH UK TV CHANNEL?

The Peacock Committee, which was set up to consider the future financing of the BBC, is to investigate the feasibility of starting a fifth TV broadcasting channel in the UK, also local city TV stations. The decision to commission independent research on the possibility of such services was made by the Committee on the basis that TV financing in the UK is related to the number of services available.

MULLARD SECAM-PAL TRANSCODER IC

Mullard have introduced a Secam to PAL transcoder i.e., type TDA3592A, which is able to convert a Secam input to a PAL signal. The input is identified by a built-in circuit. If a PAL signal is received this passes directly to the chroma output. If a Secam signal is received the PAL path is automatically switched off: the signal then passes

via limiting/amplification, demodulation, clamping, de-emphasis, blanking and reinsertion circuits to a PAL modulator which produces a true PAL output.

A power-saving feature operates when the supply voltage falls below 5V. In this event the Secam processing shuts down but the non-Secam (PAL/monochrome signal path) remains active. The 24-pin chip operates from a 12V supply and requires typically 90mA.

NEC SATELLITE TV EQUIPMENT

According to Simon Orme of NEC Business Systems (Europe) Ltd. "everything is now in place" to deliver significant quantities of the NEC NESAT satellite TV receiver system to the UK market. The system is designed to plug into an existing TV set and is available through master distributors who will be responsible for installing the equipment, including the aerial. It's also available on rental through some branches of DER.

The NESAT system comprises a dish aerial to suit the location, a low-noise converter and an indoor tuner unit. Gallium arsenide devices are used in the LNC, which has been designed so that two units can be stack-mounted for reception of signals of either polarity. These are fed to an i.f. (0.7-1.7GHz) combiner unit before going to the tuner via a single cable. The approximate price of the NESAT system is £1,500. For further details contact Simon Orme, NEC Business Systems (Europe) Ltd., 35 Oval Road, London NW1 7EA (01-267 7000).

NEW BRAND

Judging by our post bag, one of the things that causes readers most problems is unknown brand names. So note Questar, which has just been launched by Asda for use on small appliances and brown goods sold in their ninety electrical departments nationwide. No TVs yet, but a VCR is promised. Servicing of Questar products, which come from Japanese and other Far Eastern suppliers, is carried out by Serviscope, a national organisation owned by Visionhire.

PUBLICATIONS/CATALOGUES

This year's IBA Yearbook of Independent Broadcasting (*Television and Radio 1986*) takes a new look in a larger format with 224 pages lavishly illustrated in colour. It's available from bookshops at £4.90 or direct from Independent Television Publications Ltd., Circulation Department, Whippendell Road, Watford, Herts at £7 including postage and packing.

Tandy's 1986 catalogue is available from Tandy Corporation (Branch UK), Tameway Tower, Bridge Street, Walsall, West Midlands WS1 1LA. Tandy claim to be the world's largest electronics retailer, with 215 stores and 135 dealers in the UK. The catalogue contains a vast array of equipment and components including two monochrome portable TV sets with LCD displays and a full-feature VHS VCR which is priced at £379.95.

VISNEWS ARCHIVE MATERIAL

All material in the Visnews Library is now available on one inch video tape. During the last three years technical experts at Visnews Facilities have been working their way through four million feet of historic archive material held at the library: the process, using the latest technology, has greatly enhanced the picture and sound quality. The material includes coverage of the coronation of Tzar Nicholas II (1896), the diamond jubilee of Queen Victoria (1897) and the 1911 Delhi Durbar.

Teamwork

Anne Avis

"What's it like to live over a TV repair shop?" ask new visitors to our home, their curiosity aroused by the constant sound of the shop bell and the persistent telephone calls. I suspect that they have their doubts, but for Chris and I as married business partners the arrangement has worked very well. I've noted a lack of contributions in *Television* from the many "other halves" of small businesses like ours – wives who've become business partners not only because the accountant thinks it expedient but because we have our own contribution to make, quite apart from feeding the engineer. Even Honeybunch doesn't say how she copes with Les Lawry-Johns.

Opening Shop

Our business partnership started three years ago when Chris had the opportunity to buy the business he'd worked in for ten years. We'd married three years previously and though we'd hoped for our own business eventually this unexpected chance seemed at first a less inviting "wedding". We had to sell our much loved and worked on first home in order to buy suitable business/domestic accommodation, and the more I saw of available property within our price range the more despairing I became. But at last we found a place I knew could be home and Chris knew was ideal for business. Despite the surveyor's opinion that it was a "rattlebag old property", despite nerve-racking planning permission delays and frustrating missing links in house purchase chains, we finally harnessed the muscle power of friends and family, hired a van and moved house and business in two chaotic weeks. Our ten month old daughter found the packaging and paraphernalia a marvellous adventure playground, but our pleasure and relief came when I was able to photograph Chris at the shop door with the "open" sign. Since then a lot more emulsion paint has flowed and we've suffered a heartbreaking family tragedy, but the partnership has survived and developed into a comfortable way of living.

What's Involved

My major contribution is bookkeeping. This was no easy task for an ex-nurse with an aversion to maths, but I have a good friend and teacher in the lady who previously worked part-time for the business and bequeathed me a sensible system when she retired. I've nevertheless endured hours of frustration chasing odd pence that won't balance, and suffered an anxious day trying to look busy with housework while the VAT inspector politely but persistently combed the books at the end of our first year. Thankfully the errors were small, but the whole process reinforced my resentment of the unrewarding time spent on VAT.

Books, cleaning and coffee-making apart, there are plants in the shop window to be tended (not geranium diodes, as Chris suggested) and well-meaning but time-wasting acquaintances to be siphoned off when they "pop in for a chat" – as well as the occasional lifting assistance required when a giant 26in. Dynatron in a fancy cabinet

puts in an appearance (perhaps the hospital training helps with that, though the patients had softer edges).

And of course I have to hold fort when Chris has to answer an outside call. His absence guarantees the appearance of someone wanting an obscure part or technical assistance. I can manage plugs, batteries and fuses now, and can even demonstrate reconditioned sets, but have yet to graduate in styli, belts and semiconductors. It's sometimes difficult to stem the flow of a customer's technical jargon, though I suppose I should feel flattered when they assume I know about using TVs with computers and why their picture goes bright green. However falsely, I can actually sound quite knowledgeable on things like field collapse and ghosts.

Working on the spot meant that I didn't have to "give up work" to have our new baby girl and that we don't have to employ a child minder as we would if I'd resumed my old career – quite an advantage over some of my ex-colleagues who keep asking "when are you coming back?".

Snags

There are inevitable snags, like the customer who interrupted the Queen's Christmas Day broadcast and the intrusion of shop into house. I endeavour to limit the latter as gently as possible, but the dining table frequently has sets nestling beneath it and the coat cupboard recently housed a large TV set for two months while it awaited a guarantee-replacement part (thanks, Disastercare). My nest of tables spends more time displaying sets in the window than it does in the sitting room, and I nearly lost one to a passer-by who thought it was for sale.

Summing Up

Some might find themselves too much under each other's feet, but during the day we usually meet properly only for snacks, and even those are likely to be interrupted by the telephone or shop bell. Working so closely makes it almost impossible not to understand each other's problems, so there's no argument about Chris spending an extra hour or two in the workshop when the jobs waiting clip is bulging, nor about some help for me when the baby's been very demanding and visitors are expected.

We are fortunate to share common goals and to have our living in our own hands – so far as the government allows. What's more I get my TV mended for nothing – when there's time . . .



Chris and Anne Avis at RadioVision Exeter.

POST A PART ELECTRONICS
6 CHAPMAN COURT, CHARFLETS ROAD,
CANVEY ISLAND, ESSEX SS8 0PQ.
Telephone 0268 690868
Telex 99305



TRADE COUNTER OPEN

ORDERS DESPACHED SAME DAY
ADD 75p P&P, THEN 15% VAT.

ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thorn 10C 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 70C	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
Pye 725 Complete Tube Base Panel	1.25
TX9 Complete Tube Base Panel	2.75
TX10 Complete Tube Base Panel	3.75
TX90 Complete Tube Base Panel	4.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket ITT CVC32	45p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Inserter 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lept	90p
Anode Cap	47p
Sanyo Anode Cap Assy + Lead. 127CD-CT-1G	65p
Degauss VDR E2990/HP230 3000/8000	25p
Degauss Thermistor CB-RDH (TX90)	1.80
Control Knob Thorn TX90	4 for 2.00
On/Off Knob Thorn TX90	65p
Push Button Assy Thorn TX90	9.80
Tube Neck Connection Assy. 20AX AT1081	5.00
EHT Cable	Metre
BF259 with Heatsink	14p
TI110 with Heatsink	10p
L129/130/131 Coil	40p
6MHz Ceramic Filter	25p
DL700 (Philips) Chroma Delay Line	1.00
DL500 Chroma Delay Line	1.00
T9006A Lum Delay Line	1.00
8K5/9K Lum Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100R	15p
Thorn 2000 Focus Pot	1.00
Thorn 3000 Focus Pot	3.75
Thorn 9600 Focus Pot	2.40
Thorn 8K5 Focus Pot	2.40
Thorn 4000 Focus Pot	2.75
Thorn TX10 Focus Pot (New Type)	9.00

SERVICE AIDS

Ambersil M54 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Amberron	6oz 2.25
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Ambracens Foaming Cleaner	13oz 1.26
Ambersil Circuit Lacquer	14oz 2.15

THICK FILM RESISTOR UNITS

3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.30
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

FUSES

50MA	10 for 70p	250MA	10 for 65p
250MA	10 for 50p	750MA	10 for 65p
315MA	10 for 50p	7A	10 for 50p
500MA	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn Mains TX 9000 (T701)	10.00
Thorn Mains TX 9600 (T512)	10.00
Thorn S.O.P.T 8000/8500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LOPT 9000	10.00
Thorn LOPT 9600	12.00
Thorn LOPT 1590/91	7.25
Thorn LOPT 1690/91	7.25
Thorn LOPT 8000	9.80
Thorn LOPT 8500	9.80
Thorn LOPT TX9	9.85
Thorn LOPT TX10	19.00
Thorn LOPT TX90	13.75
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT G9	8.80
Philips LOPT G11	13.75
GEC LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT CV21 4-2751-44700	3.50
ITT LOPT CVC5-9	9.50
ITT LOPT CVC30	8.75
ITT LOPT CVC45	9.75
Baird 8750	10.25
Baird 8752	10.25
Thorn Line Drive TX TX9 (T2)	3.00
Thorn Line Drive TX 8K etc (T402)	1.85
Thorn Line Drive TX 9K (T705)	3.75
Thorn Switch Mode TX 9K6 (T511)	3.75
Thorn Input Choke TX9 (L64)	4.00
Thorn Choke TX90 (L120)	2.95

300 Mixed Resistors	1.50	10 Spark Gaps	1.00
300 Mixed Capacitors	1.50	10-16 pin Quil IC Socket	90p
150 Mixed Electrolytics	2.00	20 Assorted TV Knobs	1.00
100 W/W Resistors	1.00	10-16 pin Quil to Dil IC Socket	90p
20 Mixed Conv Pots	1.00	100 Mixed Diodes	1.00
40 Mixed Pots	1.50	50 Mixed Mica Washers	65p
20 Mixed Sliders	1.00	300 Mixed Resistors & Capacitors	1.50
40 Mixed Presets	60p	100 Mixed Dil to Dil IC Socket	1.00
20 Mixed VDR & Thermistors	1.00	50 Electrolytics & 50 Capacitors	1.00
100 Mixed Ceramic Discs	1.00	50 Mixed Poly Capacitors	1.00
20 Mixed Valve Bases	1.00	20 Mixed Valve Bases	1.00

AC128	39	BC174B	23	BCX33	22	BF173	25	BFR52	31	NKT276	20
AC131	40	BC177	24	BCX34	21	BF174	24	BFR62	29	NKT453	1.65
AC138	40	BC182LB	12	BD115	49	BF179	29	BFR81	29	DT112	1.92
AC141K	39	BC183L	12	BD131	30	BF181	32	BFR87	25	DT121	2.08
AC142K	38	BC184L	13	BD132	46	BF184	30	BFR91	2.08	R1039	1.80
AC153	39	BC187	24	BD133	58	BF185	30	BFT42	30	R2008B	1.10
AC176	33	BC204	15	BD139	36	BF194	16	BFX38	40	R2030	70
AC176K	38	BC208	9	BD140	38	BF195	16	BFY50	30	R2265	1.30
AC128K	93	BC212L	9	BD144	1.70	BF196	16	BFY51	34	R2305	80
AC188	38	BC213L	12	BD150	50	BF197	15	BFY52	34	R2322	50
AD142	1.18	BC237	12	BD161	96	BF198	19	BRC116	1.50	R2443	25
AD143	1.06	BC238B	8	BD201	74	BF199	15	BRC1693	1.33	RCA16446	30
AD149	96	BC238L	8	BD203	78	BF223	18	BU105	1.00	RCA16599	1.25
AD161	32	BC250A	15	BD204	96	BF224	19	BU126	1.10	RCA16600	1.40
AD162	32	BC251	8	BD222	48	BF238	20	BU207	1.35	RCA16799	1.13
AD263	1.05	BC252A	20	BD225	52	BF240	9	BU208	1.15	RCA16800	1.42
AF127	45	BC294	37	BD232	50	BF241	21	BU208A	1.15	RCA16802	1.38
AF139	38	BC301	32	BD233	60	BF255	10	BU226A	1.20	RCA16815	1.20
AF239	41	BC303	31	BD234	60	BF256LB	38	BU407	1.70	SP8385	2.65
BC107	15	BC307	10	BD237	55	BF265S	20	BU408	2.76	ST299	2.25
BC108	15	BC308	8	BD238	65	BF267	28	BU500	2.30	ST8000	1.25
BC109	15	BC309	14	BD241	59	BF259	28	BU526	2.46	T6050V	1.30
BC115	16	BC327	18	BD244	85	BF274	25	BU806	1.80	T6052V	1.30
BC117	21	BC328	18	BD278A	81	BF274	11	BU807	2.94	T9003V	1.25
BC125	26	BC337	17	BD386	68	BF337	29	CI129	9	T9010V	1.45
BC126	23	BC338	17	BD433	71	BF338	34	CI172B	9	T9053V	1.30
BC139	27	BC347	8	BD437	83	BF355	40	E5386	54	T9054V	1.00
BC141	34	BC394	8	BD592	1.20	BF361	50	E9003	29	T9059V	1.10
BC142	30	BC454	8	BD589	1.20	BF369	21	E9005	25	TIC45X	50
BC143	31	BC455	8	BD617G	1.35	BF394	16	ME0404	10	TIC46	48
BC147	12	BC456	10	BD679	1.42	BF422	47	ME0412	10	TIC106C	40
BC148	12	BC460	40	BD701	1.04	BF423	53	ME6002	10	TIP29	42
BC149	12	BC463	22	BD702	1.12	BF450	43	MJ2501	2.36	TIP30	42
BC153	16	BC546	8	BD707	95	BF453	53	MJ3001	2.21	TIP31	35
BC1540R	16	BC547	12	BD708	95	BF458	37	MJE340	50	TIP32	43
BC154YL	16	BC548	12	BD839	1.30	BF459	35	MJE520	50	TIP33	61
BC157	12	BC549	8	BDX10	93	BF461	59	MJE2955	1.40	TIP41	42
BC158	12	BC557	10	BDY20	1.09	BF566B	58	MJE3055	1.50	TIP42	45
BC159	15	BC558	10	BDY82	99	BF596	15	NKT241W	8	TIP110	61
BC171	9	BC559	8	BF137	20	BF594	16	NKT241G	8	TIS91	25
BC172	9	BC595	8	BF153	20	BF575	62	NKT241Y	8	ZTX550	30

INTEGRATED CIRCUITS

BRC1330	1.40	SN7613ND	1.80	TBA530	1.26	TDA2030	2.10
BRC3064	1.00	SN76023N	1.80	TBA544	1.00	TDA2522	2.10
BRCM/200	1.00	SN76033N	2.00	TBA550Q	1.82	TDA2530	2.61
BRCM/300	1.00	SN76115	2.00	TBA611	1.50	TDA2540	3.50
CA306	1.58	SN76131N	1.58	TBA651	2.05	TDA2560	3.50
LM1303P	1.48	SN76226N	1.25	TBA651	2.05	TDA2581	3.00
ML231B	2.20	SN76227N	1.00	TBA720A	2.49	TDA2591	1.96
ML237B	2.00	SN76530P	1.30	TBA750	2.20	TDA2611A	1.95
ML239B	2.06	SN76622N	1.00	TBA800	1.62	TDA2640	2.50
MC1327AP	1.25	SN76660N	80p	TBA810S	1.00	TDA2690A	6.00
MC1358P	1.30	SN76666N	75p	TBA920	2.08	TDA5903	2.80
MC1455P	18p	SN76744	1.32	TBA950	2.54	TCEP100	3.48
MC14516BCP	60p	SY153A	2.50	TB41440	1.92	TCA1009	1.95
SAA1025	7.20	TA7117P	1.00	TCA270SA	1.05	TDA4269A	4.80
SAA1124	4.50	TA7109AP	2.80	TCA270C	1.05	MC14429P	4.50
SAA5010	6.00	TAA611	1.40	TCA270CQ	1.05	MC14514	5.00
SL432A	1.80	TBA120B	1.20	TDA1035T	3.50	UA758PC	2.50
SL1430	2.50	TBA120C	1.20	TDA1037	2.12	UA4008A	2.86
SL1432	2.50	TBA120CQ	70p	TDA1170	2.75	ULN2216A	1.30
SN15846N	60p	TBA120S	70p	TDA1170S	1.76	UPC1365C	5.75
SN74123N	65p	TBA120U	70p	TDA1200	2.42	SC3488P	1.40
SN74154N	1.40	TBA395	1.00	TDA1270	2.76	SC3511P	1.40
SN76001N	1.40	TBA480Q	1.40	TDA1327	2.53	SW153	2.50
SN76110N	1.14	TBA510	1.90	TDA2002	2.80		

Thorn 8/8K5 ex equip panels	untested	Thorn 3/3K5 ex equip panels	untested	Thorn 4000 Convergence panel ex-factory	3.75
PSU	2.88	PSU	3.75	Thorn 4000 PSU panel ex-factory	2.50
FTB	3.75	LTB	3.75	Thorn 3K5 beam limiter board	2.00
Decoder	4.00	Video	2.50	new	1.75
Thorn 9K ex equip panels	untested	Chroma	2.75	Thorn 3.3K5, EHT & scan TX + X	1.80
PSU	12.00	IF	1.75	R2008B on alum chassis ex-spares	1.80
Decoder	5.00	Conv. 3K	3.00	equipment	1.80
Thorn 9K6 ex equip panel	untested	Conv. 3K5	3.75	Thorn 8/8K5 damaged FTB for spares	1.25
Decoder	5.75	Autovox Decoder FG01 boxed</			

LINEOUT TRANSFORMERS

Table listing various electronic components such as transformers, capacitors, and resistors with their respective part numbers and prices.

GEC SPARES

Table listing GEC spares including various electronic components like resistors, capacitors, and diodes.

PHILIPS G11 CHASSIS

Table listing Philips G11 chassis components including various electronic parts and their prices.

THORN VIDEO SPARES

Table listing Thorn video spares including various video-related components and their prices.

THORN VIDEO SPARES (OVER 450 PARTS)

Table listing Thorn video spares (over 450 parts) including various video-related components and their prices.

QUICK SALES TV SPARES THE COACH HOUSE, BRUXTON LANE, TELFORD, SALOP
FULL LIST OF OVER 3000 ITEMS SENT WITH ORDER OR SEND 9" x 4" SAE. PLEASE USE STOCK NUMBER WHEN ORDERING, OR USE SET MAKER'S PART NUMBER. ACCESS AND VISA ACCEPTED. OFFICIAL ORDERS FROM GOVERNMENT OR SCHOOLS WELCOMED. ALL GOODS ARE STOCK ITEMS.

Decca-Tatung Chassis Up-date

Part 2: The 160 Series

Ray Wilkinson

The introduction of the 160 series chassis marked a number of milestones for Deccacolour/Tatung CTVs. It was intended to drive 90° tubes in screen sizes from 14 to 22in. and the original concept included neither remote control nor export versions. In the event the chassis proved to be so successful that such versions were subsequently called for.

In conjunction with the Production Engineering and Test Instruments departments in the factory the PCB size and shape were carefully worked out so that a new in-line production line could be designed specifically for the chassis. The test equipment is even more automated than before to increase the reliability and consistency of the sets.

As with the 140/145 series all the circuitry apart from that on the tube base panel is arranged on a single PCB. Two tube base layout designs are required however: while the 20 and 22in. tubes have standard necks, as in the 140 series, the 14 and 16in. tubes have mini-necks and different pin connections. The bare PCB has both types of tube base panel attached with perforations, like postage stamps. The production schedule determines which model is to be made at any particular time. After assembly, test and alignment of the whole panel and the appropriate tube base section the base sections are broken away and the main panel is fitted in the cabinet. The unwanted base section is either discarded or used for spares.

Test Equipment

All the test equipment used in the production of the chassis was designed and built by the factory's Test Instruments department. It consists of six sequential in-

line stations placed after the flow-solder and inspection sections. Each station carries out component checks, voltage or current measurements, waveform checks and adjustments to coils or preset potentiometers. Most of these tests are carried out automatically under microprocessor control. Where an operator is required, for example to check a critical waveform, the test gear will be making other checks at the same time.

The chassis is supported by a pair of tapes as it moves along the assembly line. These tapes carry the chassis to each test station in turn. As the chassis stops over the test equipment the pin bed beneath is raised by pneumatic rams so that the pins contact the appropriate test points on the copper track.

Automatic Adjusters

Each automatic adjuster for a coil or preset potentiometer is driven by a precision motor and gearbox included within a servo feedback loop, the motors and gearboxes being supported above the chassis in a transparent plastic safety cover. It's fascinating to watch one of these adjusters in operation. For example, to adjust the coupling between the tuner and the i.f. strip the system injects a frequency sweep at the tuner test point and displays the response on the monitoring oscilloscope. Then, as the system measures the amplitude of the response at four critical frequencies, the adjuster automatically tweaks the core of the coupling coil in the tuner. You can see the result on the scope, as the response curve gradually takes on the correct shape.

The tests are split up so that the time spent at each test station is the same. This is essential since the assembly line


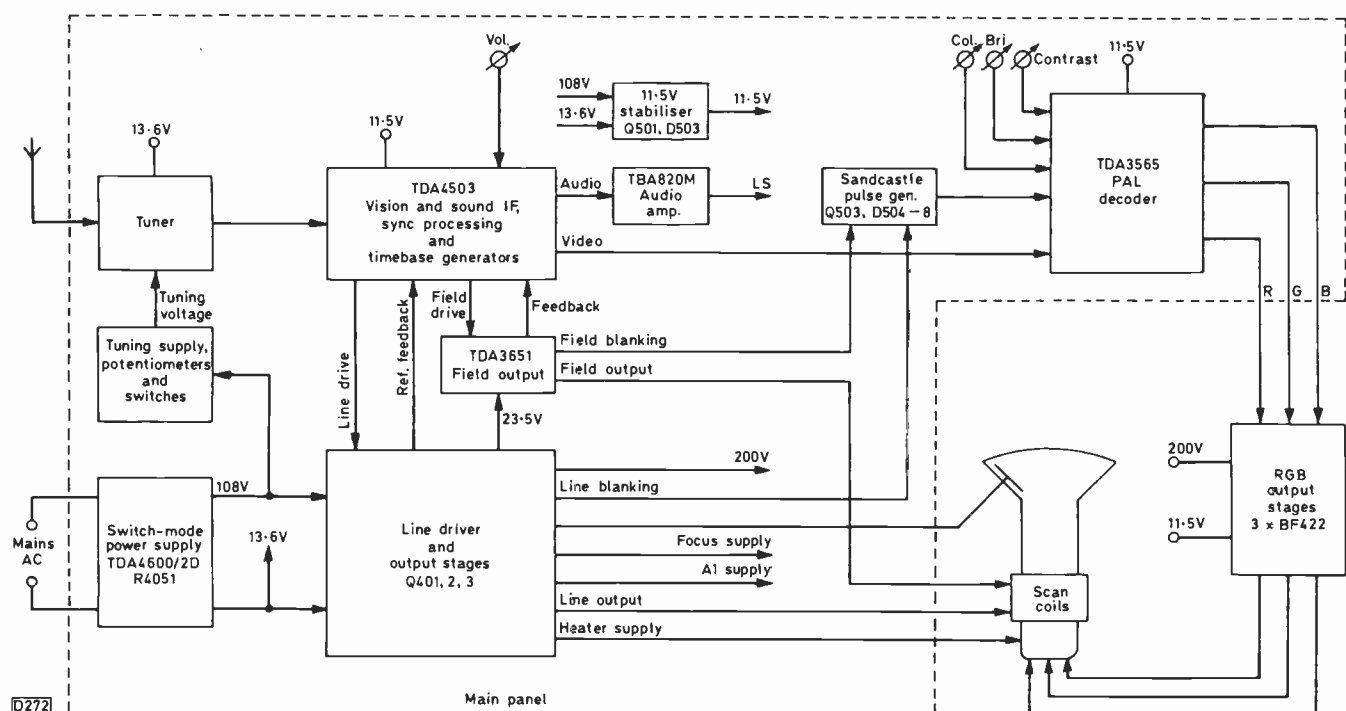


Fig. 1: Simplified block diagram of the 160 series chassis.

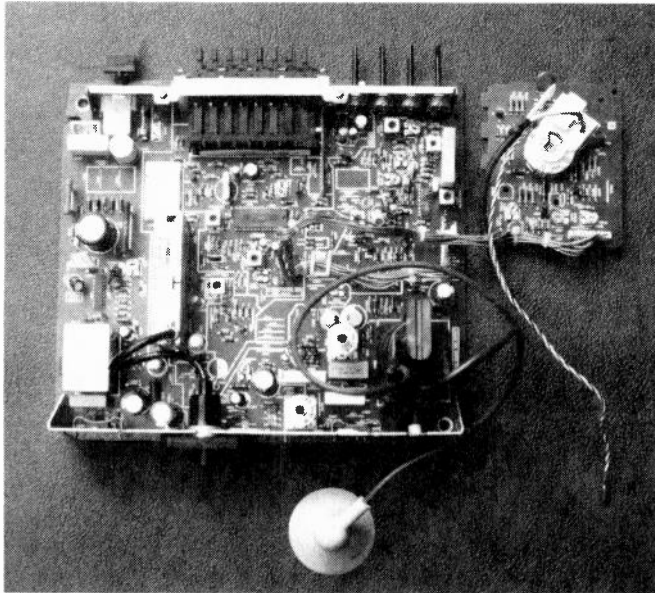

The basic 160 series chassis.

moves continuously.

The 160 Chassis

Now to the 160 chassis itself. If you compare the accompanying photo with the 145 chassis shown last month you can see the simplification that's been achieved. The main contributory factor to this simplification is the TDA4503 chip that became available at the time we started to design the chassis. You can see from Fig. 1 how many circuit sections are incorporated within this chip.

The vision i.f. section of the chip is based on the TDA2540/1 series chips we used previously, so we were able to make use of our earlier experience in the development of this part of the set. A significant difference however is that there is only a single coil to serve the dual purpose of detector tank and a.f.c. coil. The phase shift required for a.f.c. operation is generated within the i.c.

The sync processor section of the chip is based on the TDA2578, but the second phase-locked loop is not present. This is the loop that would control the possible shift in flyback pulse phase as the beam current, and hence the collector current and switch-off time of the line output transistor, change. In other words you could get sideways kinks in the picture as the brightness varies. We've minimised this effect by ensuring that the line output transistor just stays out of saturation, making its switch-off time much more consistent.

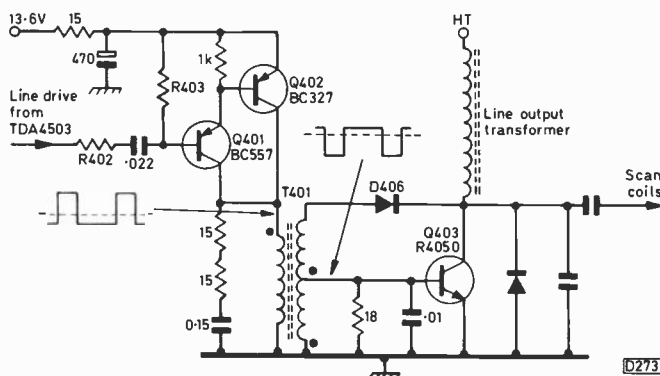


Fig. 2: The line driver stage and the line output transistor's base circuit. The values of R402 and R403 depend on the size of the tube.

Fig. 2 shows the line output transistor's base drive circuit. The line driver transformer T401 drives the line output transistor Q403 hard on but the combination of D406 and the few extra turns on T401 prevent its collector voltage going too low – the extra turns provide enough voltage to turn on D406. This extra winding is designed so that Q403 remains just on the edge of saturation during the scan period, thus reducing its dissipation to a minimum.

The other main simplifications achieved are in the colour decoder and RGB output stages. The TDA3565 PAL decoder chip is an 18-pin version of the TDA3561A (used in the 145 chassis) without provision for RGB inputs or teletext. We've removed the preset adjustments we had on the customer controls in the 140/145 series. This means that we can't adjust for spreads between i.c.s, but with care in the design and the choice of test limits this hasn't been a problem – and it does simply the test procedure.

Another alignment operation that's been simplified is the previously mentioned tuner coupling. In earlier designs we always had an adjustable coupling coil in addition to the one in the tuner: it formed part of a bottom-capacitance coupling between the tuner and the SAWF driver transistor – this arrangement was explained in detail in my previous series of articles. In the 160 chassis the second coil is fixed – it forms part of the printed circuit track. Its value is thus very consistent between sets. A screen is necessary to reduce interference but this is simply fitted as a hand-inserted component.

The PAL decoder has no luminance delay line. This is because we were able to use a SAWF that incorporates the required delay.

Two other features that ease assembly are the single heatsink/strengthening rail at the back of the chassis and the use of a mains switch that fits straight on to the PCB.

Remote Control – the 165 Chassis

The success of the 160 chassis in its basic form prompted the marketing department to ask for a remote control version that would complement the existing range of remote control chassis described last month. The i.c. chosen for this purpose is a single-chip version of the M104/M293 combination used in the 145 series.

From the system block diagram shown in Fig. 3 you can see that most of the circuitry, including the display driver, is contained in the M491, a 40-pin NMOS LSI chip. This i.c. provides voltage-synthesis tuning for sixteen programmes, in a similar manner to the System 40 arrangement, with remote control of channel selection, volume and on/off (standby).

The TDA8160 infra-red remote control receiver chip is a small 8-pin device we've been able to fit on the main PCB with its own screen around it.

The system's mode of operation is very similar to the M104/M293 arrangement described last month but the action of some of the circuitry may not be immediately apparent.

Diodes DR02/3/4 decode some of the seven-segment display driver lines so that on channels 14/15/16 QR04's collector voltage falls. The collector of this transistor is connected to the coincidence detector pin in the sync processor section of the TDA4503 chip to give a short line time-constant for VCR use.

When you switch the set on you normally want it to come on fully rather than in standby. If pin 25 is connected to 0V the standby output at pin 26 will be set to

already used for the basic 160 chassis.

In Conclusion

With its reduced component count and more automated production the 160 series has proved to be a popular chassis within the factory. It's giving even more consistent

performance and reliability in the field than its predecessors – and we thought they were good!

Finally, I would like to take this opportunity to thank all my colleagues at the laboratory and the factory for their help and friendship over the years. Also my thanks to the management of Tatung (UK) Ltd. for their permission to publish these articles.

Quick Tests: Philips Solid-state Chassis

S. Simon

This time we'll report on some of the solid-state Philips CTV chassis that often come into the workshop – the G8, G9 and KT3. We'll skip over the G11 (20AX chassis) since it was thoroughly covered in these pages quite recently – see the October 1985 issue.

THE G8 CHASSIS

The G8 has also been extensively covered in the past, so we'll just provide some notes that may be of help.

As the tube's heaters are supplied by the mains transformer the first check to make is a visual one – are the heaters alight? If they are we know that the mains supply to the set is intact and that the 3-15A mains fuse (anti-surge type) is o.k. If the tube's heaters are not glowing, check the mains supply to the on/off switch and the condition of the mains fuse. It's on the extreme left side, under a cover. Remove this and check the appearance of the fuse. If it's blackened, check the mains rectifier thyristor. This is roughly in the centre of the power panel (left side) and is usually a BT106 on a stud mounting though occasionally a flat type, e.g. a BT116, will be found. Check for shorts. The mains filter capacitor is rarely at fault in this chassis: it's located bottom left, on the inside (C1366).

Also check the condition of the large h.t. reservoir capacitor (600 μ F – C1385) at the bottom left. The tags are to the front and a mirror can be used to check the appearance of the business end. Any burn marks, corrosion or bumps should condemn it to the waste bin. This capacitor is now failing more regularly and should be a "first check" in these sets.

Very often no shorts or other reasons for fuse failure will be found and a replacement will bring the set back to life. Suffering from the rigours of a spiky mains supply over a long period of time tends to kill off these fuses.

If the mains fuse is intact and the tube's heaters are alight but the set is otherwise dead, check the voltage at the rear edge h.t. fuses. Some 200V should be found here. If this voltage is present, transfer attention to the right side line output panel and check the 800mA fuse roughly half way up the rear edge. If this fuse is intact (200V at both ends) proceed to the front end and locate the large 47 Ω wirewound, vertically mounted anti-breathing resistor R5535. There may be 200V at one end but not at the other. If this is so you're lucky, a replacement being all that's necessary. If however there's 200V at both ends you will probably have to look for a dry-joint. Most often the poor contact will be found on the top line drive panel where the black wires join to the earth tag. It may be necessary to remove this small panel in order to resolder the contacts on the print side. This will normally restore the operation of the set.

If the 800mA line scan panel fuse has failed – and this is the usual situation – the chances are that the line output transformer has failed. This must not be assumed however. Disconnect the tripler – remove the plug from the nipple on top of the transformer – and check the current drawn (meter across the fuse). If the current is still over 500mA, switch off and check the resistance to chassis from the top end of the 47 Ω resistor previously mentioned. If the reading is low, check the line shift control (shorted to case?) and the two line output transistors. Check these anyway.

If the transistors are o.k., examine the transformer to see if there are any signs of burning on the top (not essential) winding. If so, cut the winding out and run the nipple from the original feed tag. Check the current drawn and if this is normal refit the tripler plug and try again (in case the tripler was the cause of the failure in the first place). The top winding is not usually at fault however. The majority of transformer failures are due to shorts in the main winding. This necessitates a new transformer – an extremely common occurrence with the G8, as most of us in the trade know only too well. The imported type of replacement transformers (brown) seem to be more reliable than the original ones.

If the tube's heaters are alight but there's no voltage at the left-hand h.t. fuses, note the front end, long vertical dropper resistor. There should be a.c. at the two bottom tags and h.t. (d.c.) at the upper two. It's common for a section to fail. The value of the bottom, surge limiter section is 2.2 Ω while the upper, h.t. smoothing section is 68 Ω . If the lower section is intact, don't put the meter across the upper two tags to check it. Switch the meter to 250V or so and then apply the leads. The reason for doing this is that if this section has gone open-circuit one tag may still be fully charged by the 600 μ F reservoir capacitor which must be discharged before risking an ohmmeter check. If in doubt connect a resistor of say 50 Ω value across the tags to discharge the electrolytic. You've been warned! If both sections are intact check the print side of the lower panel – poor connections here are not unknown.

So much then for dealing with a "dead" G8. For further information on servicing this chassis refer to the May and July 1985 issues.

THE G9 CHASSIS

The G9 chassis can be looked upon as a 110° version of the G8. The signals panel is the same and the power supply panel follows similar lines but the rest is quite a bit different. The approach required is also different.

The left side power supply panel is obscured by the convergence board and some care is required if this is moved with the set on. Be very careful – don't let it flop

around. The mains fuse is the one at the bottom of the power supply panel and is again a 3·15A anti-surge type. The h.t. fuse is the 1A one near the top of the panel. The voltage here should be 205V and usually is.

The main source of trouble in these sets is over to the right, on the line output panel. You'll find a 2,200 μ F capacitor here, C5138. It's subject to the strain of trying to hold a steady supply of about 45V across the two resistors in series with the emitter of the line output transistor. This 45V supply is available only when C5138 is in good order. All too often it isn't, and it should be the first suspect when a variety of symptoms present themselves – rapid variations in picture size etc. Much time in the past has been spent in checking the power supply for a fault only to find that the culprit was this large electrolytic over on the line output panel. The associated zener diode D5134 is also a possible suspect – type BZX79/C51. Dry-joints here are a bit of a pain and can occur on both sides of the panel. The audio output stage feed resistor R3141 (39 Ω) takes its supply from C5138 and can suffer when the electrolytic is defective – it's on the signals panel.

The G9's line output transformer is also suspect, but not to the extent of the one on the G8. It's smaller but retains the tripler nipple which makes disconnection easy if this item is suspect – note that the G8 and G9 use a different type of tripler.

Just one word about the power supply. There's no surge limiting resistor in the feed to the thyristor (which has a soft-start circuit), just the bottom right filter choke. The front end "dropper" is the h.t. smoothing resistor and has a value of 56 Ω .

Sorry, but that's all I have to say about the G9. Further information on the chassis can be found in the August 1981 issue.

THE KT3 CHASSIS

Finally this month a few words on the KT3 chassis. Not many because this is a reliable design spoilt by the tendency of just one item to fail. Had the design of the KT2 (the earlier 14in. chassis) been followed this one item would not have been included. The KT2 had a surge limiter in the supply to the h.t. rectifier: it consists of two 10 Ω resistors in parallel. The KT3 has a single 4·7 Ω surge limiting resistor that follows the main bridge rectifier. It fails time and time again. The circuit reference number is R6191 and it's on the bottom right subpanel.

The KT3 chassis was used in a variety of models ranging from 14 to 20in. sets. The K30, used in larger screen sets with 110° scanning, is similar. Later came the CTX chassis with its single, horizontal board. All these chassis have the devilish 4·7 Ω resistor, so be prepared to find it open-circuit in the various models in this range.

Three sixteen-pin i.c.s that have control over the twelve channels are to be found at the rear of the selector drawer used in some of these models. If some channels can be selected and perform well but some can't, one of the i.c.s is usually responsible. Care is required when handling these i.c.s – fingers and tools should be discharged to earth to prevent any i.c. touched being ruined by static. Most standard models have a tuning assembly in the side of the cabinet. Access is by removal of a panel. This is pretty obvious however: most of the troubles are caused by plug and socket contacts and the occasional dry-joint.

Some servicing notes on the KT3/K30 chassis appeared in the November 1983 issue (where R6191 was incorrectly shown in Fig. 1 as R6291).

next month in

TELEVISION

● SERVICING THE HITACHI NP6C CHASSIS

This chassis was used in a number of Hitachi models with tube sizes from 13 to 20in. It's hard to believe that some of these sets are now ten years old! There are still a lot of them around and while the circuitry is fairly conventional some fault conditions can cause problems. John Coombes provides a detailed guide to fault finding.

● VHS THE PHILIPS WAY

Philips' position in the European VCR market has improved significantly since the firm adopted the VHS system. But Philips always like to do things their own way. As a result, the operation of Philips manufactured VHS machines differs from that of Japanese produced machines. This can cause some confusion, as Harold Peters explains.

● THE NETWORK NW1402R WITH EMS

A Korean set using European technology! No wonder that engineers can be puzzled when they have to deal with it. EMS stands for Electronic Memory System – the SGS M193 non-volatile programme/channel memory chip. Information on the system seems difficult to come by so Denis Mott provides an explanation of how it works – also details of a simple modification to overcome the problem of tuning drift.

● MORE ON VCR DEVELOPMENTS

In the second part of his article on VCR developments Steve Beeching describes the half-speed system and the techniques that were evolved to make it possible. A "jump" circuit is required for stable colour in the search mode, and a video noise reduction system is used to improve the signal-to-noise characteristics – this employs carrier shift during recording and a CCD delay line circuit for playback. Picture sharpening is also described.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO
(Name of Newsagent)

Please reserve/deliver the March issue of TELEVISION (£1·20), on sale February 19th, and continue every month until further notice.

NAME

ADDRESS

.....

.....

.....

Developments in VCRs

Part 1

Steve Beeching, T.Eng.

Two major developments in VCRs over the last year or so have been dual-speed operation, giving up to eight hours of recording and playback, and hi-fi stereo sound, with the sound signals laid down on helical tracks along with the video signal. These and other features are all part of the specification of the JVC Model HRD725 which we'll use as an example in describing recent VCR developments.

With the HRD725 JVC came up with not just a hi-fi VCR but one that has other capabilities above and beyond previous models. Apart from the hi-fi sound there are normal stereo sound tracks with Dolby, as in previous models. These tracks can be post-dubbed together as a stereo pair, or individually for bilingual use, or used to keep the original background sound with a post-dubbed commentary added.

Six-head Drum

The HRD725's head drum has six head tips, two for hi-fi audio, two for standard video recording/playback and two for long-play video. Considerable thought was put into the use of the long-play (LP) and standard-play (SP) heads to provide noise-free visual search, still field and step-field variable playback. We'll look into all these modes of operation in some detail. I'd like to make the point at the outset that various low-cost "equivalents" of the HRD725 don't incorporate the full electronic playback processing: because of this they have noise bars in visual search and omit the variable-speed playback feature. Another point worth noting is that several machines with hi-fi sound have monaural standard audio tracks, making them non-compatible with previous stereo sound modes.

The positions of the six heads in the drum are shown in Fig. 1. The audio heads are mounted 138° in advance of the following video heads. Each is $26\mu\text{m}$ thick, so the audio tracks are $26\mu\text{m}$ wide. In addition the audio heads are mounted on a plane higher than the video heads, so that the $26\mu\text{m}$ wide audio track lies within the $49\mu\text{m}$ wide

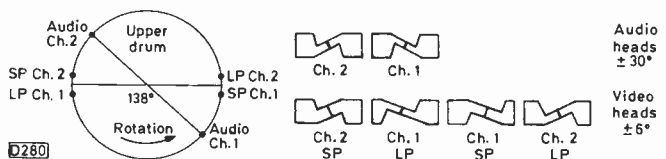


Fig. 1: Arrangement of a VHS head drum for standard/long play and hi-fi audio record/playback.

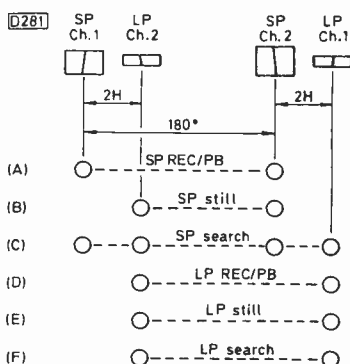


Fig. 2: Use of different heads in the various modes of operation. For SP stills one LP and one SP head is used. All four video heads are used in the SP search mode.

track traced by the following video head. The audio heads record the audio tracks prior to these being traced over by the video heads. This is one of the principles of the depth multiplex recording system used for video hi-fi sound.

The pairs of video heads are constructed as a single unit, each head having its own winding. For a reason that will become clearer later, an LP and an SP head of opposite azimuth are mounted together: they are precisely two lines apart when recording or playing. The Ch. 1 SP head is slightly thicker than $49\mu\text{m}$ while the Ch. 2 SP head is much thicker – more like $56\mu\text{m}$ (an estimate) – though each records a standard $49\mu\text{m}$ track since one head over records the excess track of the other head. To ensure this, the tape speed is such that the tape moves $49\mu\text{m}$ along during each head scan. The LP video heads are $25\mu\text{m}$ thick and record $25\mu\text{m}$ wide tracks. The advantages of having a thicker Ch. 2 SP head to get noise-free still pictures will become clearer later.

Visual Search and Still Picture Modes

Before getting involved in the electronics, let's consider the use of the multiple heads to read the recorded video tracks in the visual search and still picture modes. Slow motion is simply the use of the capstan motor in the stepping mode to provide sequential frame displays, forward or reverse.

The head selection chart (Fig. 2) shows the differences in head thickness and gap tilt (azimuth offset). (A) shows normal record/playback, using the Ch. 1 and Ch. 2 SP heads alternately. (D) shows slow-speed record/playback, using the Ch. 1 and Ch. 2 LP heads alternately. The LP heads are also used for LP still pictures (E) and picture search (F). Noise bars are apparent therefore during the LP picture search and still frame modes. Note that it's still frame as opposed to still field.

In the SP still picture mode (B) the thicker Ch. 2 SP head is used in conjunction with the Ch. 2 LP head. The result is a still field with the same track read alternately by these two heads. This is illustrated in Fig. 3, where the advantage of using the thicker Ch. 2 SP head to cover the Ch. 2 track without missing any f.m. video signal can be seen. With the tape stationary the heads scan the tape at a more acute angle than when the tape is moving during record. The replay path is thus longer, covering at least some portion of three adjacent tracks, though the head azimuth matches only the central track. The adjacent tracks are ignored. Since it's thinner, the Ch. 2 LP head doesn't cover so much track. It can lose out at the very top and introduce noise if the tracking is not spot on. For this reason the machine's still picture quality is perfectly noise free only with its own recordings and is not necessarily clean with a library tape. This is true of most machines with still-picture and slow-motion modes.

All four heads are active in the SP picture search mode (C), in forward or reverse. At nine times normal speed each head crosses a number of tracks, some eight-nine (see Fig. 4). Each head can replay only alternate tracks since those between have the wrong azimuth. Hence the noise bar with traditional machines. The HRD725 how-

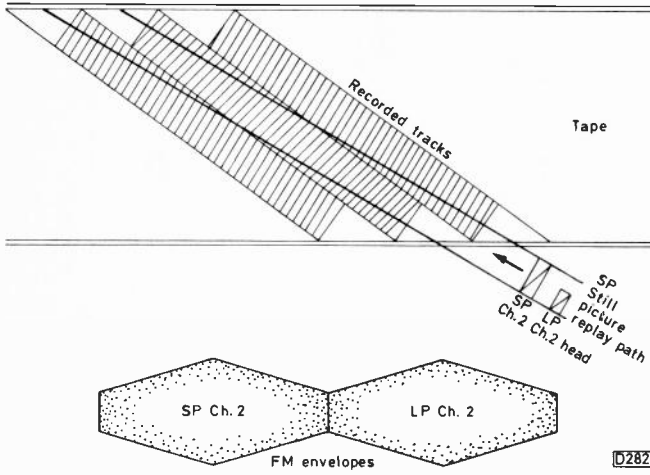


Fig. 3: SP still playback.

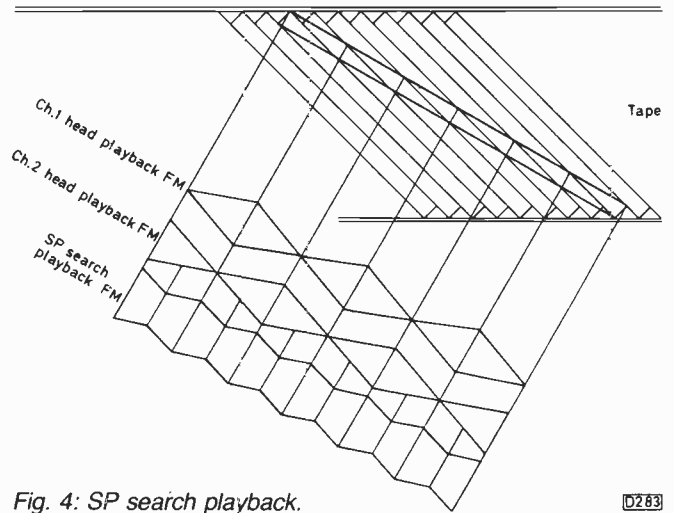


Fig. 4: SP search playback.

ever incorporates a circuit that selects the best f.m. carrier of the four at all times during the visual search mode, giving noise-free SP visual search.

Noise-free SP Search

Fig. 5 shows how this is achieved. Transistor switches Q1 and Q2 switch off the SP heads in the LP mode or earth the playback side of the windings in record. Q5 and Q6 provide the same action with the LP heads. For SP visual search Q1, Q2, Q5 and Q6 are all open. Selection of the outputs from the preamplifiers in IC1 and IC2 is done by the drum flip-flop signal. This is in antiphase between the LP and SP heads. IC3 selects the outputs from the SP or LP heads and routes the signal to the

playback f.m. demodulator circuitry. IC4 monitors the f.m. signals from each set of LP or SP heads: its output at pin 7 is low if the signal level from the SP heads is greater than that from the LP heads and vice versa. IC405 produces a pulse that corresponds to the peak f.m. carrier from the LP or SP heads, this pulse being used by the automatic tracking system to detect the position of the noise bar within a still picture and remove it.

The microcomputer chip IC413 controls the head switching and selection. During visual search it selects the LP or SP heads via IC419 according to the highest value of f.m. signal detected by IC4. As IC419 is clocked by the playback line sync pulses switching between heads occurs at the start of a line. The result is a noise-free SP visual search – only thin switching lines with a slight horizontal

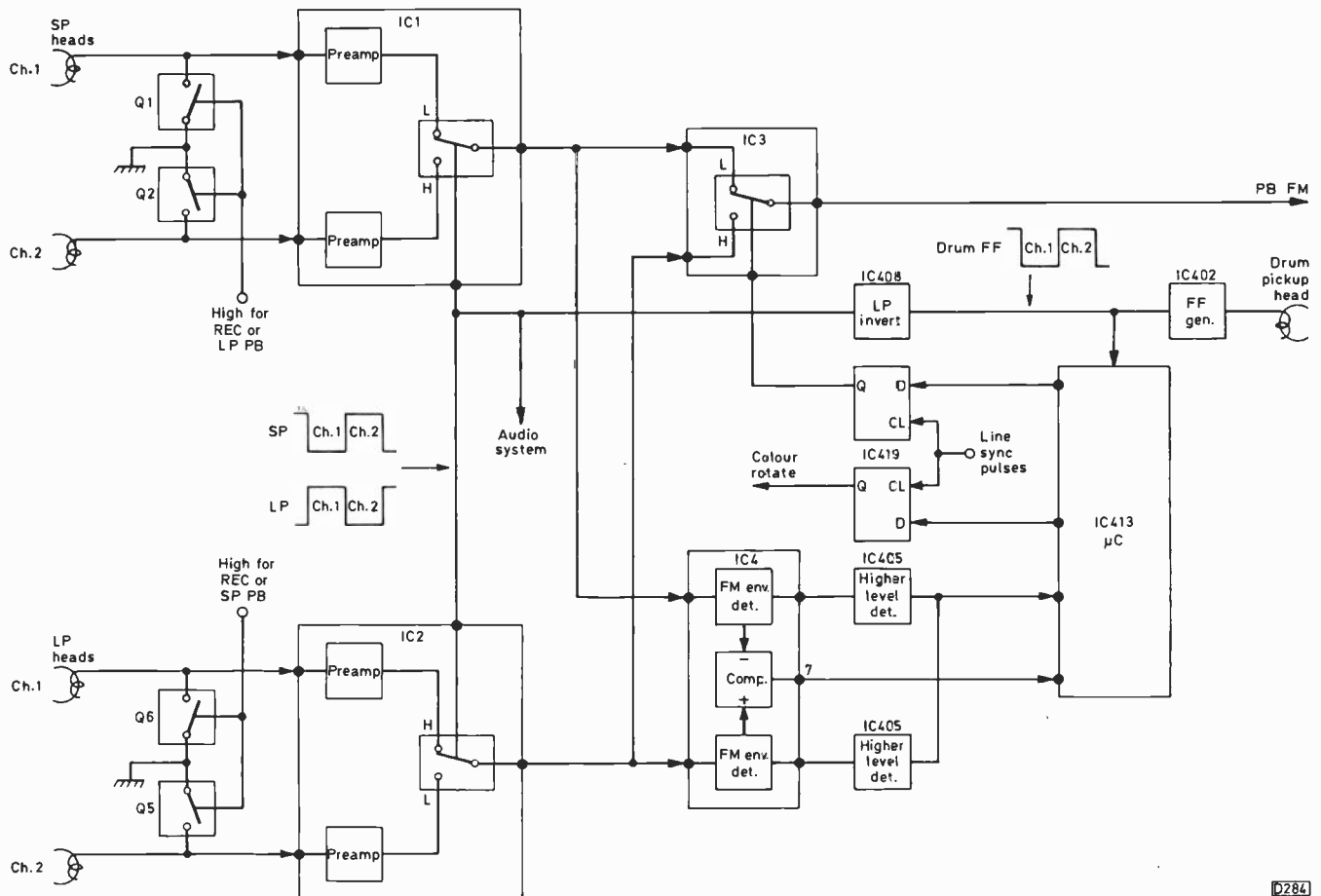


Fig. 5: Block diagram of the video head selection system.

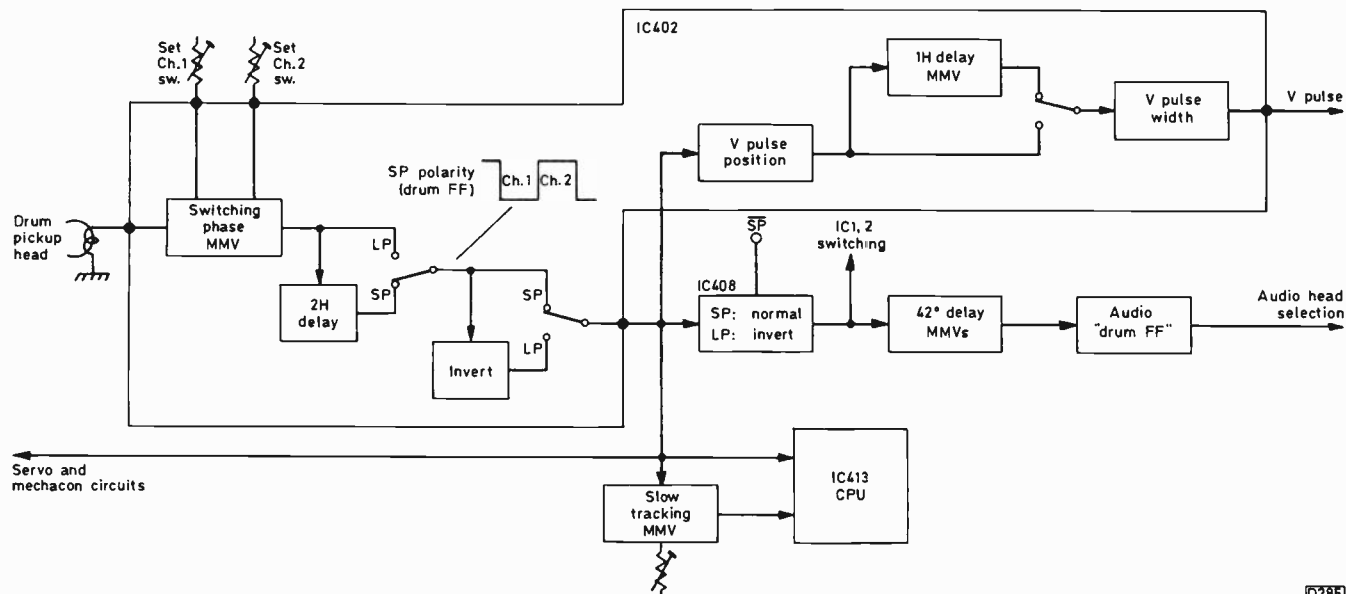


Fig. 6: Block diagram of the switch timing system.

displacement can be seen. IC413 also controls the colour phase via IC419, by issuing a colour rotate signal to the chroma circuits when head switching occurs.

Head Switching Control

In a standard VCR the video heads are mounted 180° apart and take 40ms to complete a single revolution. Thus each head scans the tape during half a revolution, i.e. 20ms. It follows that 40ms = 360° of drum rotation and any scan angle can be expressed as an equivalent time period. The r.f. switching pulse, or drum flip-flop as I prefer to call it, is generated by the drum servo as a symmetrical squarewave. In a hi-fi/LP VCR three flip-flop trains are required – for the SP, LP and hi-fi head switching. As we saw earlier the LP heads are displaced from the SP heads by two TV lines (2H). Thus a two-line time shift is required between the SP and LP head switching flip-flops. The audio heads are displaced by a 138° advance, so a 42° delay will bring the flip-flop switching edges to the correct time.

Fig. 6 shows in block diagram form the circuitry used for this. The LP heads are the most advanced and coincide with the primary timing edges from IC402. The SP timing edges are delayed by 2H. Since the azimuths of the SP heads are opposite to those of the LP heads, inverted flip-flop pulses are required for one lot with respect to the other: the LP flip-flop pulses are taken via the inverter.

From this point the flip-flop pulse train is distributed to the other parts of the system that require head timing information. For the audio head selector circuits the flip-flop is given a 42° delay to time the edges correctly. There is also an inverter to get the switching polarity correct for audio in the LP and SP modes.

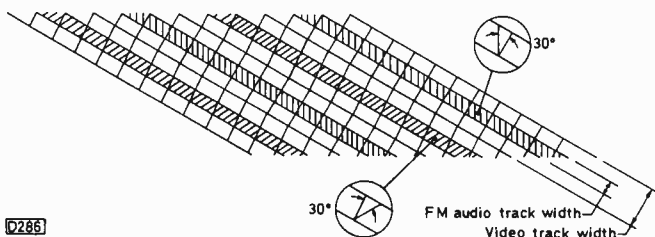


Fig. 7: VHS hi-fi track pattern.

The V-pulse output circuit provides synthesised field sync pulses for use in the slow/still and visual search modes to ensure stable field locking with the tracking noise bars out of the picture area, i.e. pushed into the field sync period.

Hi-fi Audio

For hi-fi audio recording the two left and right channel signals are frequency modulated on to two carriers at 1.4MHz and 1.8MHz respectively, the heads (see Fig. 1) having an azimuth offset of ±30°. The 26μm wide audio track is centred on (beneath) the corresponding video track as shown in Fig. 7.

Fig. 8 illustrates the depth multiplex recording principle. As the audio head has a wider gap (not track) than the video head its recording penetrates the 4μm magnetic layer on the tape to a greater depth than the corresponding video signal. The surface portion of the audio recording is then erased by the following video head as this records to a depth of only about 1μm. This leaves a two-layer magnetic recording with the audio signal below the video signal. The attenuation of the audio signal by the erasure of its top layer is only some 12dB – this varies depending on the tape energy level. Separation of the audio and video carriers during playback is achieved through the azimuth difference between the audio and video heads – the video heads at ±6° and the audio heads at ±30° “see” only their own carriers.

The f.m. deviation for hi-fi audio recording is ±150kHz. Incidentally, for Beta hi-fi the carriers are at 1.44MHz and 2.1MHz, the deviation being ±500kHz. Fig. 9 shows the VHS video and audio signal spectrums with hi-fi sound.

Record/Playback System

The basic hi-fi record/playback system is shown in Fig. 10. The input is selected by IC5 which can accommodate simultaneous TV and f.m. radio broadcasts by allowing the machine to record TV from its tuner and hi-fi audio via an external f.m. radio input. There's a choice of a.g.c. or manual recording level, selection of the latter being indicated on an LED ladder array. The a.g.c. is of the limiter type so that noticeable variation in level with

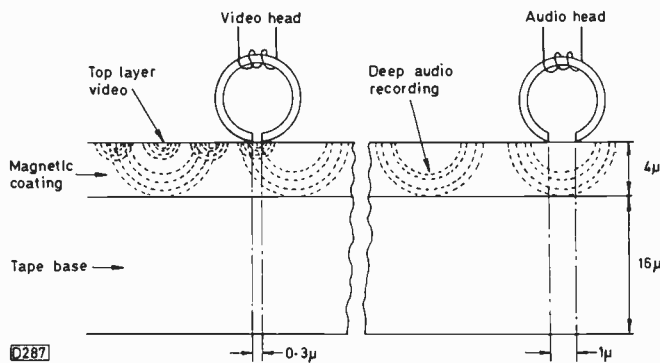


Fig. 8: The principle of depth-multiplex recording.

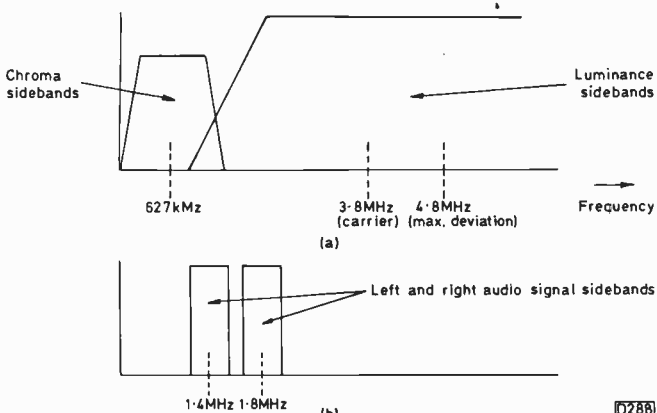


Fig. 9: Frequency spectrum for VHS hi-fi: (a) video signals, (b) the two f.m. audio signals.

sudden changes in input level – often called “breathing” – is avoided.

IC9 provides muting on power up and power down to prevent spurious noise. IC13 also contains muting control, mainly for playback purposes.

In the record mode the dynamic range of the signal is reduced by a compressor arrangement in IC15 – we'll return to this later. Pre-emphasis is next carried out by IC12 in conjunction with the RC network connected to pin 6. The signal is then limited and passed via a low-pass

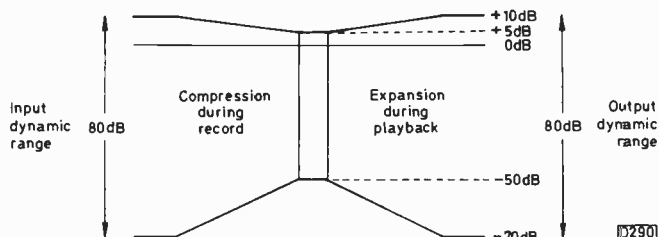


Fig. 11: Audio compression/expansion for noise reduction.

filter to the f.m. modulator in IC13. A voltage-controlled oscillator is used as the f.m. modulator. The record level control is incorporated to prevent over-recording (the f.m. modulator being driven to a deviation in excess of 150kHz). The low-pass filter cuts off at 20kHz – this reduces harmonic intermodulation, particularly from the f.m. broadcast stereo pilot tone at 38kHz. After modulation the left signal at 1.4MHz is added to the right 1.8MHz signal. The two signals are then sent to the audio heads via the record drive amplifier.

In playback the 1.4MHz and 1.8MHz signals are amplified, with a.g.c., by IC1, Q4 and Q13 and are then separated by bandpass filters before passing to their respective demodulator and dropout compensator circuits. Demodulation is performed by making use of the voltage-controlled oscillator as part of a phase-locked loop – the error signal produced by a phase comparator is the recovered audio signal. The following hold circuit eliminates audible glitches caused by dropouts and the head switching pulses – we'll return to this. De-emphasis is then applied before the signal goes to the expander circuit to correct for the compression applied during recording.

Signal Compression/expansion

Signal compression/expansion (see Fig. 11) is used to improve the signal-to-noise ratio significantly while maintaining an 80dB dynamic range. Compression is applied during the recording process, the playback signal being subjected to a corresponding expansion. The processes are logarithmic and a special i.c. has been developed to

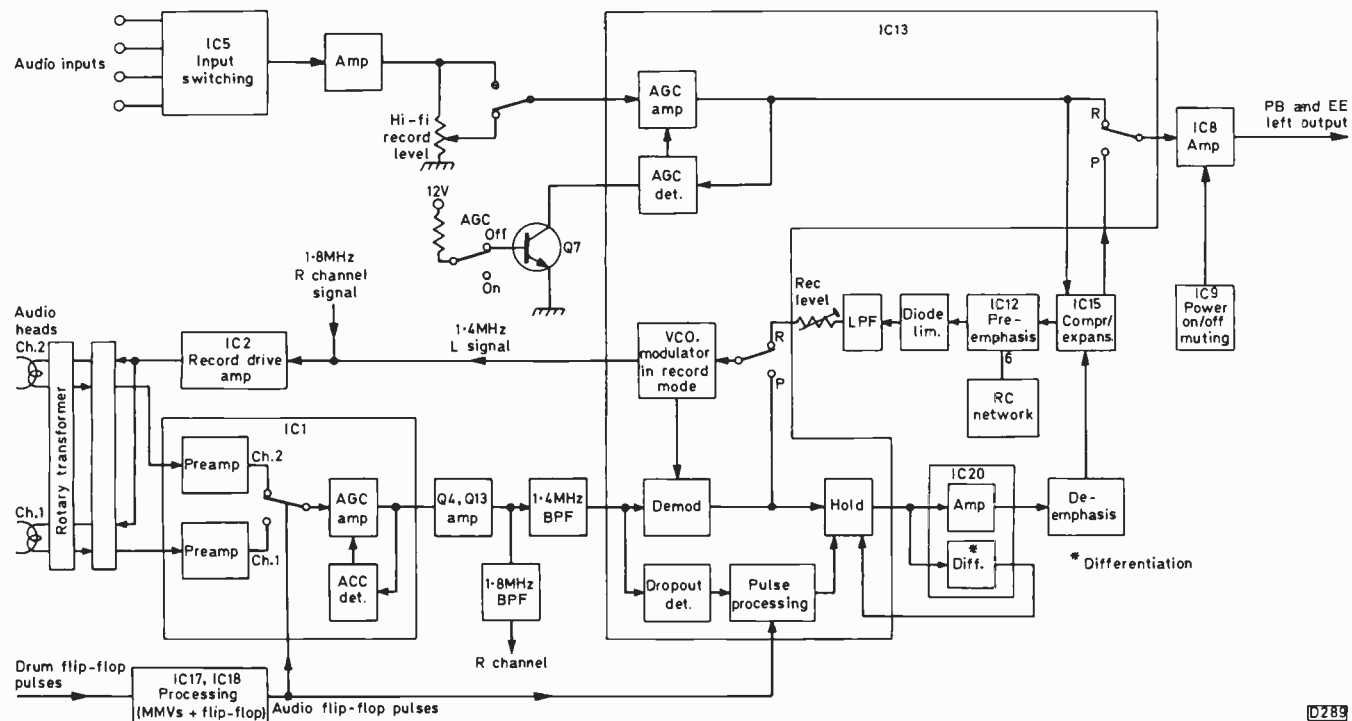


Fig. 10: Simplified block diagram showing the audio signal processing – one channel only.

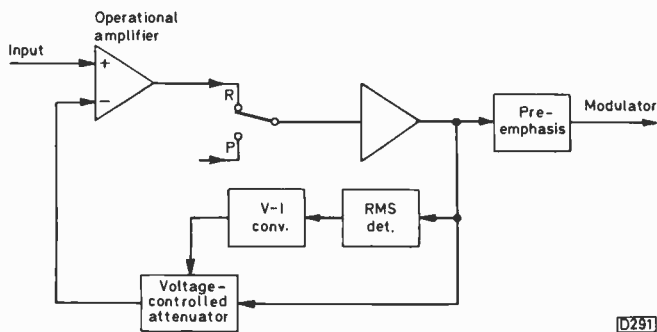


Fig. 12: Block diagram of the record compression system.

perform these operations.

In the Dolby noise reduction system only the high-frequency components of the signal are modified during record/playback. Low-level, high-frequency signals are amplified before being recorded then attenuated during playback. This reduces the tape noise level during playback. The compander/expander used in the JVC HRD725 works at all frequencies and signal levels, the frequency response being tailored by the pre-emphasis/de-emphasis networks. It provides a 10dB compression/expansion of the signal for every 60mV change with respect to a set 0dB level.

A block diagram of the record compression system is shown in Fig. 12. The input signal is applied to the non-inverting input of an operational amplifier, then to a further amplifier, before being subjected to pre-emphasis. Compression is carried out by applying feedback to the inverting input of the operational amplifier. A voltage-controlled amplifier/attenuator (VCA) is included in the feedback circuit. It's controlled by an r.m.s. detector which converts the level of the audio signal to a d.c.

control voltage. This is transformed to a control current to control the gain of the VCA.

During playback the VCA is in series with the signal path (see Fig. 13). It works in reverse to the record mode. All frequencies that were compressed are expanded with the result, in conjunction with the pre-emphasis/de-emphasis applied, that tape noise is reduced over a much wider frequency range than that achieved with Dolby. It's not unlike the DBX system.

An r.m.s. (root mean square) detector is used since neither a mean-level nor a peak level detector will give an accurate output when a complex signal input is applied. What the r.m.s. detector does is to take the peak value of the input, square it, then take the square root of the mean value of successive squared peaks to produce an "effective value" output.

Audio Head Switching

The drum flip-flop pulses are used to switch between the outputs from the two heads during playback. This is done to eliminate noise from the head not actually scanning the tape. As the audio heads lag the video heads by 42° the drum flip-flop pulses cannot be used directly to carry out the switching. Two monostables triggered by the drum flip-flop pulses are used in conjunction with a flip-flop multivibrator to introduce the 4.7ms delay required for the switching pulses.

Dropout System

If a tape dropout occurs the level of the playback audio f.m. carrier falls to a level where it's insufficient to recover the audio without distortion or noise. Further noise and distortion occur during the switching between the outputs

3 WEEK FULL-TIME



Next four courses commence on JAN. 27th, MARCH 17th, MAY 12th & JUNE 30th

VIDEO CASSETTE RECORDER SERVICING COURSE

INTENSIVE COURSE INTENDED FOR QUALIFIED TELEVISION SERVICE ENGINEERS OR APPLICANTS WITH SIMILAR BACKGROUND. THE COURSE COMBINES THE ADVANTAGES OF INDUSTRIAL AND ACADEMIC TRAINING WITH A HIGH PERCENTAGE OF PRACTICAL WORK.

Further details from:

LONDON ELECTRONICS COLLEGE (VCR Dept.)
20 Penywern Road,
Earls Court, London SW5 9SU
Tel: 01-373 8721

of the two heads. Both dropout and switching noise must be removed without affecting the quality of the sound reproduction. This is done in IC13 (see Fig. 10). A switched hold circuit is used. In the event of a dropout the hold circuit, activated by a pulse from the dropout detector, holds the demodulated audio level at about 75 per cent of peak level for the duration of the dropout. De-emphasis and filtering smooth the effect of this hold action. Filtering is assisted by differentiating the audio signal and feeding the result back to the hold circuit. The audio flip-flop pulses are used to activate the hold circuit during the head switching periods.

As a check on the quality of the sound I've recorded the output from a compact digital disc on the tape. It's

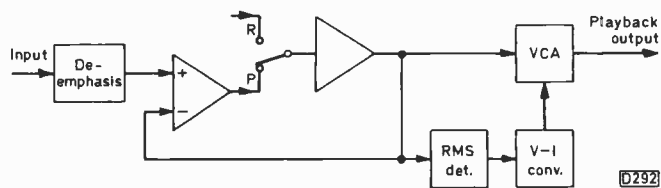


Fig. 13: Block diagram of the playback expansion system.

difficult to tell the difference between the output from the disc itself and that obtained from tape playback. In fact the system works very well.

Next month we'll look at the long-play system in more detail.

TV Fault Finding

Reports from Alan Shaw, Steve Illidge, Philip Blundell, Eng. Tech., Hugh MacMullen, Jeff Herbert, J. G. Grieve, Malcolm Burrell and Steve Leatherbarrow

Toshiba FST Sets

We've had the following faults with the latest Toshiba sets with FST tubes.

First there was a Model 211E with tuner drift. A common enough fault maybe, but when we removed the 33V stabiliser i.c. DA05 it was found to be a 1N4148 diode. Fitting a ZTK33B cured the fault. Over the next few weeks we came across many new sets with the wrong part fitted in this position. A phone call to Toshiba confirmed that there had been a production boob – maybe the symptom shows up only when a set is tuned to the higher channels?

The second problem we had with this model was purity errors. The set would degauss, but a few days later there would be another service call for the same complaint. The degaussing arrangement in this set consists of just one coil around the c.r.t.: Toshiba now supply a conventional pair of coils with connecting leads and plugs – fitting this completely overcomes the problem.

A blown mains fuse is usually caused by the 2SC3409 chopper transistor Q802 but beware – the SI8100D control chip IC801 will probably also be dud.

Video faults such as a smeary, negative-looking picture should cast suspicion on the TA7699AP chip IC501, though we did have one very peculiar negative-looking picture due to R210 (1.6kΩ) being open-circuit.

Overall the FST Toshibas give an excellent picture but the 211E's sound quality leaves something to be desired as a result of its rather small loudspeaker. The plate glass screen needs to be removed quite frequently for cleaning. Be very careful when transporting these CTVs as the light grey cabinet finish on some versions is easily damaged. A.S.

Tandberg/Lowe-Opta CTV4

This example of a rare breed had been fitted with a new tuner the week before. Now when switched on from cold it wouldn't tune in a station though the frequency-synthesis circuit was trying very hard to find something. For the first ten minutes the tuning voltage ramped furiously, then suddenly the picture would appear and would be fine for the rest of the day.

Freezing the tuner and the frequency-synthesis tuning module had no effect but the frequency divider module was found to be temperature sensitive: freezing the BC557

in this can brought the fault on, but replacing this transistor had no effect. Scope checks then revealed that the divided signal was being modulated by a line-frequency component which was coming in on the 5V line. This supply comes from a winding on the line output transformer: the associated reservoir capacitor had dried up. P.B.

ITT CVC820 Power Board

The problem with this set was no sound or vision and a quick check showed that the chopper output was very low at 40V instead of 124V. When the line output transistor was unplugged and a dummy load was connected the 124V line returned to normal, so battle commenced in the line output stage. The diodes fed from the line output transformer were all blameless, so in went a new transformer (diode-split type). This failed to restore normal operation and the cause of the trouble was eventually found to be the horizontal shift transformer TR404. P.B.

Bang and Olufsen 7530/7802

Several of these sets have come to our attention with a faulty character generator chip (IC3). The fault shows up as horizontal green lines in the bottom right-hand corner of the screen – in one case it built up over a few minutes to a green square that covered the lower right-hand corner. S.I.

Grundig 5010

The unusual fault with this set was field collapse after about ten minutes. As a first check we found that by just moving the field collapse service switch the fault would clear, only to return some ten minutes later. So we shorted out the switch, which quite often becomes intermittent due to dirt, but after the same period we had field collapse again. Whilst checking voltages under the fault condition we found that touching almost any point in the field timebase circuit with the meter probe restored the field scan. By being very careful we noted that under the fault condition the two GD241 output transistors were cold and had 30V at their collectors. We eventually found that a gentle squeeze on the BD135 emitter-follower driver

transistor would restore the field scan. Changing this transistor cured the trouble, though no fault could be found with it. **H.MacM.**

Hitachi CPT1471

This set had all the usual faults involving the chopper and field output chips and the field flyback transistor, with burnt resistors. But after exactly four hours the set would switch off with the customary chopper chip symptoms. After lengthy checks with the cabinet on and off heat was found to be the basic cause of the problem, mainly on the long, thin tin heatsink for the chopper and the line output transistor. By bolting on a fairly heavy piece of 5×2 in. aluminium above the chopper itself to spread the heat upwards the fault was completely cured. The chopper chip is much too expensive to keep on having to change it, and the manufacturers don't take kindly to the return of solid-state components. **H.MacM.**

Purity Problem

Despite checking the auto-degaussing circuit and manually degaussing this set (a Sony KV2020UB) there were intense purity errors. On a red raster test signal ninety per cent of the screen was blue, with lighter bands at the top and bottom – the only red was a small round blob on the right-hand edge of the screen. I concluded that the tube's shadowmask must have become detached but on fitting a replacement almost identical results were obtained.

Sony technical suggested that there was a scan coil fault and mentioned that they'd come across a case where a lightning strike had left the metal shield around the tube heavily magnetized. Sure enough by manually degaussing the shield, taking the coil over the top, sides and bottom of the cabinet, good purity was restored. The normal method of degaussing with the coil in front of the set had no effect on the purity, so the shield must have become permanently magnetised. Be sure to degauss the shield before suspecting the tube itself if there are persistent purity errors – it turned out to be an expensive lesson! **J.H.**

Philips CTX-S Chassis

This set suffered from low voltages – the e.h.t. was only 10kV and the chopper's 125V output was low, as was the line output transformer derived 150V supply. The supply to the chopper was high. Replacing the two transistors in the chopper control circuit restored normal operation – Tr7322 (BC548) and Tr7323 (BC558). **J.G.G.**

Some Quickies

Rank T20 chassis: A two-inch high picture was found to be due to one of the field output transistors being open-circuit. Fortunately they're easy to change.

Sony KV1810UB: This one had a bright, smeary display. The $4.7\mu\text{F}$ reservoir capacitor for the h.t. supply to the RGB output transistors was found to be the cause (C543 in earlier sets, C596 in the Mk. II version).

Körting hybrid CTV chassis: An intermittently dark picture was found to be the result of varying c.r.t. first anode supplies. These arrive at the tube base via a plug and socket arrangement at the front of the chassis (from rear). The Paxolin panel here was discoloured: scraping the carbonised sections provided a cure.

Recent Finlux chassis: This set was dead with a short-

circuit chopper transistor. A circuit wasn't available but visual examination revealed a discoloured $270\text{k}\Omega$ resistor that read $1.5\text{M}\Omega$. Replacing this produced some of the best pictures we've ever seen on the face of a c.r.t. The resistor was of course the usual one that gives this symptom in a power supply of this type – for example the $150\text{k}\Omega$ resistor in the GEC 20AX chassis and the ITT CVC20 etc. chassis. **S.L.**

GEC C2110 Series

We still have a number of these sets out on rental, many still giving good results. Whilst field roll is usually due to C452 ($4.7\mu\text{F}$) we recently had a case where it was due to the oscillator timing resistor R455 ($470\text{k}\Omega$). Incidentally, opening of the thermal resistor R601, giving a bright raster with flyback lines and no sound, has in our experience always been due to a power supply fault – usually the thyristor giving a high h.t. voltage. **S.L.**

Decca 30 Series Chassis

Slowly decreasing width with a Decca 30 series chassis, coincident with brightness reduction and eventual springing of the line output valve's screen grid feed resistor, was caused by two old favourites – the line oscillator valve's $33\text{k}\Omega$ anode load resistor and the $330\text{k}\Omega$ resistor in the width circuit. **S.L.**

Sony KV2704UB

One day this set developed what seemed to be a standby fault. When standby was pressed on the remote control unit the set went completely dead and the red LED at the front went out. Repeated operation of the on/off switch could bring the set to life but this required a certain knack. I lived with it for about a year (it's my own set) but friends found the set impossible to use. Investigation on board M (remote control etc.) showed that there were no supply voltages in the standby mode. This suggested a fault on power supply panel F2, which was removed for investigation. Since most modern sets are fairly reliable I tend to suspect high-value resistors. The circuit is the Siemens self-oscillating type chopper, with the start-up circuit consisting of D605, R605 ($330\text{k}\Omega$), R606 ($470\text{k}\Omega$), C609 and R607 (100Ω). A check on the values of R605 and R606 showed that they were both open-circuit. It was a relief to find that the set was fully operational once these resistors had been replaced and the board refitted. **M.B.**

Sony KV1810UB

I'm sure we all know these sets, by reputation if not by experience. It was with some trepidation that I received a call from a friend to look at one of them. "It smoked" he said, "so we switched it off". R608 in the start-up circuit and R642 in the switch-off protection circuit were clearly distressed, but the associated components D604, D605 and Q602 read o.k. when checked with a meter. Replacing the defective resistors and powering up resulted in a burst of smoke from R642, which disintegrated, leaving the set apparently working happily though R608 was noticeably hot.

There's not a lot in this part of the circuit. The start-up GCS Q602 also turns on when the set is switched off so that the pulse-width modulator monostable in the chopper power supply continues to operate to the very last – otherwise the line output GCS Q510 can suffer. Q602 is

switched on and off by Q601. It's also necessary to keep the line oscillator running as long as possible at switch off, again to protect Q510. To this end D604, which is reverse biased during normal operation, is connected between the chopper output and the anode of Q602 to maintain the 19V rail from which the line oscillator is run.

In normal operation the voltage at the anode of Q602/cathode of D604 should be high – about 280V. In this case however the voltage was very low. Clearly Q602 was not

being switched off as it should have been following the start-up action. Its base resistor R609 was found to be open-circuit while Q601 itself was short-circuit. A BC184 was found to work well in this position – Q602 was replaced as a precaution. This restored normal operation after a check for other impending troubles in the power supply and replacement of C605 (22 μ F) in the chopper driver start-up circuit – it had lost some of its capacitance. **M.B.**

The Human Element

Nick Lyons

Who said “we’re all in this together”? I can’t remember, but he should have been in the TV trade. Now we can all make mistakes (like criticising PCL86s for example) and I’m not alone in this respect. We humans also tend to get into jams not of our own making – when wholesalers for example don’t have in stock the parts they should. The individual dealer can’t keep in stock every obscure part for every set, but the importers/agents for the relevant specimens might have the decency to do so – always assuming that you can find out who they are. When one’s own and the agent’s stock control and competence fail, what’s one to do?

Help with a Decca 100

Sometimes on the other hand one gets unexpected help. One Saturday morning some time ago I was in attendance on a Decca 100. I found myself caught short on high-voltage zeners – there’s a 186V one on the power panel. No wholesalers were open of course so it looked like a loan set for the weekend. It then occurred to me that I could perhaps prevail on the chaps on Burley Road. Now it’s a little bit off my patch and I’d never set foot in the place before, much less did I know any of them.

I strode into the shop and explained my predicament to the chap who said he didn’t repair many Deccas and didn’t have one of them in stock. But he did have an 80 “on the pile” and I was welcome to anything off that. He then proceeded to remove the relevant component from the set and point blank refused any payment for it.

The day was saved and they have my thanks: what a pity not everyone subscribes to the same ideals! On the phone the other day to a rather close neighbour in the business I was lectured in the most haughty manner on my naivety in expecting any such assistance and was made to feel rather like something you might tread in whilst walking the dog. Never mind, next time they want something – every dog has his day!

An Ageing Rank A823

Later that week an ageing (aren’t they all?) Rank A823 chassis appeared, bearing Co-op livery and attempting to display a picture on its 19in. tube. The owner said it made loud cracking noises. He realised that the picture was poor but said it would do. The cracking worried him however.

Well, in the dry atmosphere of our workshop it never murmured for hours on end. While I was waiting for something to happen I thought it might be an idea to cure some of the more obvious faults. The poor convergence was easily put right by replacing the relevant potentiometers. In fact the convergence was so good that I decided to “blast” the tube.

At this point I should say that on the appearance of my home-brew “blaster” the other members of the staff are usually to be seen cowering behind substantial pieces of furniture. The blaster has an enviable record of success however, and this set was no exception. I was confronted with an A823 displaying one of the finest pictures I’d ever seen on one of these sets. My mind began to tick over: what had caused that original cracking? Perhaps, I surmised, the customer’s living room suffers from a lot of condensation due to a gas fire, or maybe the kitchen is close by? If I cleaned around the cavity connector and dried it off well it should be all right.

So I reached forward to pull off the cavity connector. Zapp – a very nasty shock. After recovering from this I came to the conclusion that the cavity connector had decomposed. It seemed wise to prod around the cavity with a shorting lead to deck. Touching the plastic didn’t produce any response, but when the lead strayed near the Aquadag – crack!

Having made sure that the ‘dag and the cavity proper were fully discharged I set about examining the tube. The Aquadag earthing had all been removed. On trying to clean around the cavity connector I found that the glass was cracking in zig-zags for about two-three inches from the cavity while chips of glass were missing from the surface. Clearly the tube had been severely tracking across from the cavity to the Aquadag and some lunatic had thoughtfully “cured” the problem by disconnecting the earth from the ‘dag and just allowing it to charge to the e.h.t. potential. The loud cracking noises the customer had heard were not actually the tube itself flashing over but the charged Aquadag flashing across to the metal tube shield!

On explaining the situation to the customer he said that as he had two small children who often played around near the set the possibility of the tube imploding was not something he could risk. Could we dispose of the set as we thought fit?

Well, the more we looked at the cracks in the tube’s glass cone the more nervous we got. Ken said he didn’t fancy having to carry it outside as it was somewhat colder there and the glass contracting suddenly might finish the thing off whilst he still had hold of it. In the event we dispatched the tube in the workshop, with a couple of old coats thrown over it and a length of Dexion – a long length.

The most worrying aspect of this little tale is that there are people who will carry out such work as was performed on this set, leaving the potential (no pun intended) risk of death or serious injury from severe shock and/or the effects of the tube imploding. In my view “cowboy” is not a strong enough term for such people.

Letters

THE NORDMENDE FIV CHASSIS

Pete Saunders' article on the NordMende FIV chassis (December issue) was comprehensive but I'd like to add a few notes – incidentally, the FC25 is the later version incorporating a Full Check 25 point diagnostic connection system.

The first step when working on one of these sets should always be to check the mains connection. Ensure that the neutral lead goes to chassis and the live lead to the fuse. Earlier sets have black and blue leads but the later ones with brown and blue are as often as not incorrectly connected.

In a technical circular NordMende stated that the M010 protection module must always be removed. At the same time D532, which is not present in early sets, must be added in series with the mains rectifier thyristor. It's type SSC1C0880. Whilst I was told by NordMende that a 3A, 1kV type would do a number of 1N5408s I fitted subsequently failed, leaving a charred mess and often damaged print. I now use a BY223. To fit, cut the print adjacent to the thyristor's anode and drill one hole: fit the anode leg of the diode through the hole and bend the cathode leg up to solder it to the thyristor's heatsink.

A more reliable replacement for the EW modulator driver transistor T410 when this fails is the TIP42. Mount it upside down on the heatsink, with extension wires down to the PCB for the base and emitter. The collector lead can be snipped off – the heatsink will make this connection.

I've found that a full linear scan is seldom obtainable when a 2N3055 is used as a replacement for the SM5C field output transistor. A TIP35C always works satisfactorily in this position. Intermittent height variation was traced to a dry-joint on R408 in the U2 supply circuit.

Loss of sound is occasionally caused by short-circuit turns in the sound output transformer. Intermittent sound has also been caused by the loudspeaker – this is annoying after confidently replacing the audio module only to hear the phone ring next day with the same complaint!

In common with some other continental TV sets tuning drift is made worse by having the tuning supply stabiliser (TAA550/ZTK33) dissipate too much power. NordMende changed the feed resistor (R219) from 11k Ω to 16k Ω . I always use an 18k Ω resistor but then I've plenty of these removed from Grundig sets – I replace these with a 27k Ω resistor. A green or grey metal-oxide type must be used.

Sticking on a particular channel can be caused by CB31 (0.01 μ F) in the case of channel one or the equivalent 0.0033 μ F capacitor in the case of channels 2-8 (CB35/41/45/51/55/61/65) going leaky. This will show up using an Avo on the high ohms range.

If R128 in the 24V supply fails replace it with a 27 Ω resistor as in later sets – I use the 1/3W metal-film type.

That loud buzz, generally due to the mains filter choke L531 being in need of replacement, foxed me once. A new choke provided no cure and I eventually found that R557 (470k Ω) in the active filter circuit was open-circuit. Remove to test. R557 has also been found to be responsible for ripple on the U1 h.t. line, though the more common cause of this is the active filter transistor T506

(MJ3000 in earlier sets, MJ3001 in later ones).

Occasionally a set won't start up due to a "lazy" thyristor: the same thyristor will normally work perfectly in another set . . .

A moiré like patterning, sometimes with colour running through, has been traced to the 11.5V stabiliser transistor T203 – d.c. conditions o.k. but a scope check will show "grass".

Instant BU208 line output transistor deaths have cost me on occasions. No definite reason for this has been traced but the cause is probably poor plug-socket contact in the line scan circuit. As well as the BU208, D543 (TAA550/ZTK33), T501 (S6002), T506 (MJ3000/MJ3001) and sometimes the mains rectifier thyristor D538 (TAG6-600 recommended replacement) are simultaneously killed.

A spare male pin stuck in a wooden handle can be used to check for a good fit of all the females in the line scan plug/socket connections. If you find a bad one, don't attempt to tighten it by squeezing. Find a better one – there are dozens of unused connectors on the various cables running round the set.

Another warning: note if any of the plastic location spades are missing when plugs are removed. If they are, mark them with a dab of paint. If you're not familiar with this chassis it's very easy with missing spades to reconnect plugs in the wrong place – it's impossible to find a place for *all* the plugs if any are wrong when the spades are present and correct.

Odd N/S correction faults can be caused by R461 (2.7k Ω) going either open- or short-circuit.

No mention was made of the awesome remote control system used with the NordMende FIV. It has as many wires inside as the early Dynatron remote control systems (but only two screws on the back – Les L-J.). The circuitry seems frightening, with an extra nineteen integrated circuits. To read the technical description in the manual is too much. Fortunately every "funny/intermittent" fault I've encountered has been on the 5V line – due to the bridge rectifier or the 5V stabiliser i.c.

Another bloomer: some of the remote control sets have a 240:220V autotransformer to supply the remote control circuits and many of these were wired incorrectly. Instead of 220V, approximately 260V is presented to the transformer. This doesn't seem to cause problems but rewiring is obviously desirable.

Finally, while we all know that L. L-J. hates/fears NordMendes some of us think that the FII, FIII and FIV were well ahead of their time. Does anyone know where I can find one of the four-screen sets? – I want one to play with. Or a teletext adaptor for the FIV remote control sets as a pressie for my favourite typist, who prefers the NordMende to the much more modern Grundig teletext set we're now watching.

*Les Austin, Managing Director,
Ochre Mill Technical Services Ltd.,
Lower Moddershall, Stone, Staffs.*

ELECTRON PATTERN PROGRAM

Users of the Electron microcomputer test pattern program (page 96, December 1985) can solve the aspect ratio problem mentioned in your editorial note by changing line 2010 as follows:

2010 Y = 0.923*(SQR(ABS(R*R)-(X*X)))

If, like me, you prefer to work with a larger circle try R = 500 in line 1960, and for tidier text displays change line 20 to:

20 VDU 23,1,0;0;0;0;

Line 630 should read "IF INKEY . . ." of course.

Colin McLaughlin,
Harlaxton, Grantham.

SPECTRUM 48K COLOUR BARS

The following program for the Sinclair Spectrum 48K produces five colour bar patterns that fill the entire screen, including the border. Pressing and releasing the space key will sequence through them.

Lines 20-30 put the code into the memory. Line 40 checks for correct checksum but is not infallible, so save the program before trying it out. Lines 50-110 produce the patterns by using the machine code routine located at address 32976.

Poking address "A" switches the reference bar on or off (1 to 54).

Poking address "B" changes the colour of the reference bar (0 to 7).

```
10 LET A=33104: LET B=33114: LET C=0
20 FOR X=32976 TO 33177: READ N
30 POKE X,N: LET C=C+N: NEXT X
40 IF C <> 22074 THEN PRINT "CHECK DATA LINES":
STOP
```

```
50 POKE A,54: POKE B,0: GOSUB 100
60 POKE A,1: POKE B,7: GOSUB 100
70 POKE B,2: GOSUB 100
80 POKE B,1: GOSUB 100
90 POKE B,4: GOSUB 100: GOTO 50
100 IF INKEY$ = CHR$32 THEN GOTO 100
110 RANDOMIZE USR 32976: RETURN
120 DATA 33,251,201,34,34,128,62,7
130 DATA 50,141,92,50,72,92,205,178
140 DATA 13,62,10,237,71,237,94,33
150 DATA 0,88,62,7,14,1,205,7
160 DATA 129,61,6,6,197,14,5,205
170 DATA 7,129,61,193,16,246,14,1
180 DATA 205,7,129,205,31,129,201,245
190 DATA 203,39,203,39,203,39,17,32
200 DATA 0,229,6,24,119,25,16,252
210 DATA 13,225,35,32,241,241,201,118
220 DATA 6,27,16,254,6,62,205,116
230 DATA 129,221,35,134,16,248,14,192
240 DATA 62,7,211,254,6,9,16,254
250 DATA 62,0,211,254,6,3,16,254
260 DATA 237,68,13,32,235,35,205,16
270 DATA 129,14,0,237,68,237,68,6
280 DATA 54,205,116,129,221,35,78,16
290 DATA 248,62,7,211,254,62,127,219
300 DATA 254,31,48,2,24,185,62,62
310 DATA 237,71,237,86,62,0,211,254
320 DATA 205,107,13,201,62,7,211,254
330 DATA 211,254,62,6,211,254,62,5
340 DATA 211,254,0,62,4,211,254,62
350 DATA 3,211,254,0,62,2,211,254
360 DATA 62,1,211,254,0,62,0,211
370 DATA 254,201
```

M. J. Edis, G4RPT,
Broughton, Nr. Kett, Northants.

G9AED - POSTSCRIPT

I think I can provide some information of interest to Andrew Emmerson whose article on G9AED appeared in the December issue. If I'm right, the vehicle is still in everyday use.

Its last operational job for the IBA was at the Dover transmitter site (Church Hougham). In about 1964/5 my friend and mentor Geoffrey Hutson was instrumental in

TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

RANK BUSH MURPHY		ITT: VC200 to VC402	9.20
A774 with stick rectifier	9.78	CVC1, CVC2 (FORGESTONE)	11.50
A816, T16, T18, Z712, Z715	10.35	CVC5, CVC7, CVC8, CVC9 series	9.20
T20, T22, T26, Z179, A823	11.50	CVC20	10.35
Z718 Basic unit	13.50	CVC25, CVC30, CVC32, CVC45	9.20
T24e, T24h split diode	P.O.A.	CVC40, CVC1200, 1210, 1215	P.O.A.
		FT110, FT111. P/no AT2063/02	11.50
DECCA: 1210, 1211, 1511	11.50	PYE: 169, 173, 569, 368 series	9.20
1700, 2001, 2020, 2401, 2404	9.20	CT200, CT200/1, CT213 series	10.35
CS1730, 1733, 1830, 1835	9.20	725-731, 735, 737, 741 Series	9.78
30, 70, 80, 90, 100, 130 Series	9.20		
FERGUSON, THORN: 1590, 1591	9.20	PHILIPS: 170, 210, 300 series	9.20
1690, 1691. built in rect.	9.78	320 series	9.78
1600, 1615, 1700 series	P.O.A.	TX, T8 mono	P.O.A.
1790 mono portable	P.O.A.	G8 and G9 Series	9.20
3000, 3500, 8000, 8500, 8800	P.O.A.	KT2, KT3. series colour	9.20
9000, 9200, 9300 series	12.00	G11. K30. split diode	P.O.A.
9500, 9600, 9650 series	10.99		
9800, TX9, TX10 series	P.O.A.	BINATONE: 9909, 9798, 9860	P.O.A.
MOVIESTAR 3781, 3787	12.00	DORIC Mk3	11.50
		FINLUX 9560, 9670	P.O.A.
FIDELITY: FTV12 mono	10.35	GRUNDIG: most models in stock	
CTV14R, CTV14S colour	15.83	NORDMENDE: FC125, Z206, Z306	11.50
		SANYO: 5101, 5103, 7118, 7130	P.O.A.
G.E.C. 2047 to 3135 mono	9.20	SHARP: C1851H, C2051H	P.O.A.
1201H, 1501H, 2114, 3133, 3135	9.20	TOSHIBA: C800, C800B	19.45
DUAL & SINGLE hybrid col.	10.00	TANDBURG: 190, CTV2-2, CTV3-3	P.O.A.
SINGLE STD solid state	12.00	TELEFUNKEN: most models in stock	
SINGLE STD split diode	P.O.A.	LINE OUTPUT TESTER	16.79
INDESIT: 24EGB hybrid	9.50		
12LGB, 12SGB mono portables	10.35		
		Tidman Mail Order Ltd.,	
WINDINGS		236 Sandycombe Road,	
TYNE: main winding	6.80	Richmond, Surrey.	
RBM: T20, T22, T26, Z179	6.33	Approx. 1 mile from Kew Bridge	
WALTHAM: W125 eht winding	2.37	Phone: 01-948 3702	
WALTHAM: W190, W191 eht coil	£6.00	Mon-Fri 9 am to 12.30 pm &	
KORTING: hybrid winding	6.90	1.30-4.30 pm	
		Sat 10 am to 12 noon.	

persuading the IBA to donate the caravan to the Canterbury College of Technology where Geoff used it to run the first colour TV courses in Kent. Eventually, when a colour TV laboratory became available, "The Caravan" became a development laboratory and office for members of the Electronics Section.

In about 1978/9 the caravan was donated to the Canterbury and District Model Engineering Society at Sturry near Canterbury, where it's in regular use as a store and committee room cum tea-bar.

Geoff Lewis,
Canterbury, Kent.

VIDEO FADER CORRECTION

Here's a correction note on the video fader unit featured in the May 1985 issue, page 376. The sync separator transistor Tr9 is shown as type BF178 in the components list. This is an npn type, while the circuit shows that a pnp transistor is required in this position. I've found that a BFX88 works all right - the base connections are the same.

Mark Lamb,
Birkenhead, Merseyside.

RANK Z718 CHASSIS

Reader J. Thomas of Durham (full address not supplied) asks if we've published anything on servicing the Rank Z718 chassis, pointing out that information is difficult to obtain since Rank withdrew from the domestic radio/TV field. Readers with this problem will find a detailed article in the August/September/October 1982 issues of *Television*.

Test Report: The Portasol Soldering Iron

Eugene Trundle

The denigrators of sound broadcasting often refer to it as "steam radio". What would they make of the subject of this review – a gas soldering iron, in portable and rechargeable form? It works with ordinary butane gas, dispensed from the sort of pressurised refill cylinder you can buy at a tobacconist: one fill of gas is sufficient to run the iron for up to an hour, depending on the heat setting used.

The Portasol iron is 173mm long and 19mm in diameter. It has a removable protection cap incorporating a pocket clip and uses an ignition system that consists of an abrasive wheel and an ordinary cigarette lighter type flint. Replacing the cap automatically shuts off the gas valve and shrouds the bit to prevent risk of burn damage when the iron is put down.


The bit is nickel plated and incorporates the burner system and three cooling fins to prevent heat conduction to the plastic body. It screws in for easy replacement and is available in two tip sizes, 3.2 and 2.4mm – the latter is supplied as standard. Bit life is quoted as up to thirty hours. At the opposite end is the filler valve and regulator wheel to control the heat output. The instrument is finished in bright orange and weighs about 65 grams when fully charged.

On Test

I started at the newsagents where seventy odd pence bought me a big refill – enough I would think to run the iron for many months in normal use. This dispenser came with several adaptors, one of which fitted the Portasol. The fuelling time was four seconds.

It's easiest to light the tip with the iron's regulator at maximum. This also gives the fastest warm-up time of course. From lighting to reaching the melting point of solder took about seventeen seconds at normal room temperature. I found that the heat regulator's range was quite wide, and would agree with the quoted equivalent dissipation range of 10-60W.

When used flat out the heat developed was sufficient to make a good hot puddle of molten solder on the top casing of an ELC1043 varicap tuner – this is the most practical and familiar illustration I can make of its capabilities. When turned to minimum the iron was well able to deal with small work on fine PCB tracks etc. – I did some repairs to a cracked panel at the minimum heat setting with good results, bridging the cracks with 5A fuse wire.

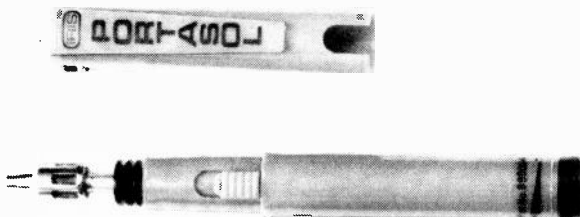

The Portasol soldering iron.

Out of doors next to see how it performed in the open. Once lit even a howling gale (simulated on this still evening by running round the garden with the iron held aloft in Olympic style) failed to extinguish it. The great outdoors did not diminish its soldering capability, though higher heat regulator settings were required. The man next door, already suspicious of my eccentricity, must have become convinced that I'm ready for the Funny Farm – he's probably right.

Applications

The iron wouldn't be used for bench repair work in normal circumstances because of the need to refuel it, ignite it and wait for warm up. Since it has no element or electrical connections however it can't cause trouble with voltage spikes or current surges, while the absence of an earth permits its use on floating or isolated components. These are points worth remembering. The Portasol really comes into its own for outdoor work where no convenient electric power source is available. Such pastimes as maintenance of cable TV distribution networks, mending TV surveillance cameras in situ, dealing with masthead and microwave dish mounted amplifiers and terminations, and telecommunications field work suggest themselves.

The iron should be a boon to those who deal with in-car or marine electronic equipment. Irons that operate at 12 and 24V are available, but it's not always easy or convenient to hook up to the battery and the high current connecting wire required for low-voltage irons is heavy and inflexible. It's not easy to trail a wire to the car's rear speaker mountings, down to the cruiser's bilge or up to the cabin roof! Perhaps it's me, but operation from a large lead-acid battery seems to produce more spitz-and-sparken, bangs and burns per hour than the average Guy Fawkes night . . . The other advantage of the Portasol in these situations is that its wide 10-60W capability enables it to replace two sizes of conventional soldering irons.

Conclusion

While it's not suited to bench work the gas iron seems to me to be excellent in all other situations. It's far cheaper in first cost than a rechargeable electric soldering iron, needs less maintenance, is lighter and has a greater thermal capacity than most. It's the most "ready" soldering iron possible, with little to go wrong and an ability to work anywhere from the chimney stack to the river bank or down a mine if required. Provided it never develops a gas leak – as cigarette lighters sometimes can – it should have a long service life.

A lot of thought and ingenuity has gone into this patented design, and it shows. At its cost of about £17.50 plus VAT to the trade it's well worth considering – unless you're tied hand and foot to the indoor bench. The price quoted includes two interchangeable bits, 3.2 and 2.4mm: replacement bit-burner assemblies cost about £2.70 each plus VAT. Wichita and Watford linemen, ICE vendors and mobile menders take note! I can also thoroughly recommend this iron to aerial erectors and dish riggers,

field engineers and cablepersons.

The review iron was lent to me by SEME Ltd., Units 2E and 2F, Saxby Road Industrial Estate, Melton

Mowbray, Leics. LE13 1BS (0664 65 392). The Portasol is also available from Anglia Components and Phab Electronics.

And There's Another Funny Thing

Les Lawry-Johns

What strange things some sets can do. When Miss Converge brought in her Pye T194 portable (Philips TX chassis) I thought it would be another quick job. So she stood there while I fumbled about. She said it was the on/off switch and I wanted to show her that it wasn't. The supply was reaching the series regulator transistor but its output was only about 2V. So I checked the control circuit and everything seemed to be o.k. I took the tube base off to check for shorts or heavy loading but found nothing.

"Try the switch again" said Miss Converge.

"It won't make any difference" I growled.

Just to show her I switched the set on again and the sound burst out loud and clear. The only thing that was different was the disconnected tube base. I put this back on and the heater glowed merrily, followed by a raster. She smirked.

"It's not the switch" I insisted.

"All right then, try it again."

So I switched off, waited a while and switched on again. Nothing happened. I removed the tube base and the sound burst out. Put the tube base back on again and a picture appeared.

"If you fit a switch it'll be all right."

"Yes dear, if I fit a switch to turn the tube's heater off until the set has started up it'll be all right."

"Well do that then."

I was in no mood to argue, so I fitted a single-pole switch on the back cover and wired it in series with the tube's heater. I realised I was doing something wrong, but if that's the way she wanted it at least this would save me having to think. We could now switch the set on with the rear switch off, then close the rear switch and the tube would light up and everything was fine. I made sure she understood the procedure – keep the rear switch in the off position until the sound comes through.

After she'd departed, feeling satisfied that she'd been right all along, I was left to wonder what part of the control circuit had been at fault. I'd checked everything (I thought). Have you had a funny feeling like that? You probably found out what it was, like I should have done.

To Sweat or Not to Sweat

It's not often that a G11 makes me sweat, but one did the other day. The chap said he didn't want to spend more than twenty quid on it and I told him I didn't think that would be necessary.

I checked the h.t. line for a start. There was a short that disappeared when I removed the BU208A's plug, from the top. So I removed the line output transistor subpanel, fitted a new one and also a 1A fuse in the h.t. fuseholder (the one in there was 2.5A). Both the 3.15A mains fuses were intact.

With the new panel fitted I switched on. There was a flash from the 3.15A mains fuses and I found that two of the bridge rectifier diodes were dead short. I wondered

about this but fitted two BY127s and new fuses and tried again. There was a brief rush of sound and a spark from the tube base, then nothing. The glow switch on the power panel glowed and some smoke came from a resistor. The 1A fuse had failed and the new BU208A was short-circuit. Oh yes, I'd also taken out the green 470 μ F h.t. reservoir electrolytic and fitted a nice blue one.

The price was beginning to escalate so I thought I'd better check the tube. It was cracked. I took my blue 470 μ F electrolytic out and wrapped the whole thing up.

"Sorry sir, it'll be a lot more than twenty quid I fear."

Sam Boy

Sam is a local character who is slipped the odd pound by everyone who receives his "Morning Guv" greeting. This enables him to live comfortably without the need to work – except to clean the occasional car or something. He reminds me of a song we used to sing during the last war.

"Sam boy was a lazy goon
who never would work in the afternoon,
too tired was he, too tired was he.
Into the woods he used to go
just to get his head down low
under a tree.
When along came a bee
making this noise
bzz, bzz, bzz, bzz.
Go away you bumble bee
I ain't no rose, no silly little flower,
get off my (censored) nose, away from here.
If you want a bit of
you can
but you'll get no here.

A silly song maybe, but an evocative one. It brings back memories of the pubs in Gib (Main Street) and Alex (Beer Street) . . .

Prodnose: I don't see the point of all this and suspect you're merely trying to be vulgar. Your editor has been consulted and you are asked to stick to TV matters.

Myself: I'm sorry. I'll try to do just that.

Nobody Told Me

So where do all the turkey eggs go? The question occurs to me at this time of year and no one's ever been able to shed any light on the matter. Until the other day – in the pub this Sunday lunchtime.

"I asked him why you can't buy turkey eggs. The farmer said they only lay fertile ones which are hatched. The rest of the time they just gobble."

Well I never. Not like chickens after all. I also heard it said that farmers don't know how long pigs would live if they were allowed to. Then they turned to me and asked how long a TV set lives? I had to say that after ten years it's anybody's guess.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

16181	1.04	ZSC1124	1.26	ZSD348	16.13	AN5435	3.08	BC186	0.27	B0222	0.49	BF195	0.14	BSP59	1.29	BZ79 RANGE	0.10
16182	1.04	ZSC1151A	4.72	ZSD350	5.20	AN5610	7.43	BC187	0.28	B0225	0.49	BF196	0.17	BSS38	0.59	BZ788 RANGE	0.10
16334	0.98	ZSC1152	4.68	ZSD350A	2.80	AN5612	3.51	BC204	0.16	B0228	0.63	BF197	0.16	BSTBD140G	4.98	C106D	0.46
16335	0.94	ZSC1162	1.05	ZSD353	7.90	AN5613	3.80	BC207	0.14	B0229	1.05	BF198	0.17	BSTC0146	2.48	C1129	0.58
16446	0.98	ZSC1172	2.22	ZSD389	2.41	AN6320N	4.28	BC212	0.11	B0231	0.50	BF199	0.17	BSTC0246	6.99	CA1310E	2.70
16600	1.38	ZSC1172N	2.20	ZSD401	3.55	AN6326	3.96	BC212B	0.26	B0232	0.50	BF200	0.37	BSTC0233	6.12	CA3044	3.50
16799	2.88	ZSC1195	3.26	ZSD551	2.42	AN6342	1.61	BC212L	0.10	B0234	0.42	BF216	0.36	BSTC1233	4.74	CA3046	2.06
16801	0.54	ZSC1213	0.89	ZSD588A	1.99	AN6344	5.87	BC212LB	0.26	B0237	0.47	BF218	0.36	BSTC3146	0.39	CA3060	1.65
16802	1.27	ZSC1226	1.46	ZSD600	3.25	AN6363	1.60	BC213	0.10	B0238	0.46	BF222	0.55	BSTCC0143	3.07	CA3065	1.29
16803	5.30	ZSC1306	1.98	ZSD621	12.67	AN6551	13.05	BC213L	0.10	B0239	0.46	BF224	0.17	BSTC0643	3.37	CA3089	0.83
16805	0.86	ZSC1307	1.98	ZSD636	0.40	AN6552	0.68	BC213LB	0.15	B0240	0.37	BF237	0.65	BSV578	3.49	CA3089E	1.43
17074	9.30	ZSC1316	4.10	ZSD657	2.80	AN7115	2.52	BC214	0.10	B0241	0.39	BF240	0.17	BSW68	0.60	CA3090	2.38
17127	3.51	ZSC1364	0.49	ZSD679	3.35	AN7145	2.80	BC214L	0.14	B0242	0.39	BF241	0.17	BSX19	0.34	CA3094	2.20
1N4001	0.06	ZSC1383	1.20	ZSD731	2.11	AN7146	9.90	BC214LB	0.26	B0243	0.50	BF244	0.57	BSX20	0.34	CA3131EM	3.12
1N4002	0.06	ZSC1398	0.84	ZSD787E	0.62	AN7150	2.46	BC225	0.40	B0243A	0.37	BF245A	0.37	BSX21	0.87	CAH76023N	6.60
1N4003	0.06	ZSC1410	2.39	ZSD811	5.54	AN7151	2.65	BC237	0.10	B0244	0.51	BF255	0.28	BSY79	0.51	CBF16848N-07	1.56
1N4004	0.04	ZSC1413	3.55	ZSD823	1.98	AN7156	2.78	BC238	0.10	B0244A	0.85	BF256	0.28	BSY79	0.51	CD4001	0.38
1N4005	0.08	ZSC1505	1.00	ZSD856	6.61	AN7158	6.75	BC238A	0.13	B0245C	0.99	BF256LC	0.42	BT100A	1.61	CD4002	0.27
1N4006	0.08	ZSC1578	8.74	ZSD869	7.17	AN7218	1.64	BC239	0.12	B0246C	0.89	BF257	0.34	BT106	1.55	CD4008	1.06
1N4007	0.07	ZSC1617	3.89	ZSD898 TR	5.45	AP98076	4.68	BC239B	0.25	BD253	1.05	BF258	0.36	BT108	1.45	CD4011	0.29
1N4148	0.04	ZSC1670	3.13	40408	0.50	AS5605	1.58	BC251A	0.12	BD278A	0.80	BF259	0.34	BT109	1.45	CD4012	0.24
1N4448	0.05	ZSC1678	1.98	40594	1.53	AU113	2.97	BC252	0.12	BD317	2.60	BF262	0.57	BT112	2.48	CD4013	0.47
1N5401	0.14	ZSC1810	1.70	40595	1.53	AY105K	2.08	BC256	0.25	BD318	2.59	BF263	0.57	BT113	2.48	CD4016	0.46
1N5402	0.15	ZSC1815	0.66	40636	1.43	AY106	1.06	BC261A	0.22	BD375	0.42	BF264	0.37	BT116	1.20	CD4017	0.82
1N5403	0.16	ZSC1829	2.22	40871	1.53	BA130	0.14	BC262	0.22	BD377	0.26	BF271	0.34	BT119	1.76	CD4020	1.23
1N5404	0.15	ZSC1855	1.88	40872	1.53	BA1310	1.98	BC287	0.50	BD379	0.76	BF273	0.20	BT120	2.17	CD4021	0.39
1N5408	0.35	ZSC1875	4.77	60857	1.21	BA1320	1.38	BC294	0.50	BD380	0.76	BF274	0.20	BT121	2.48	CD4023	0.28
1N914	0.04	ZSC1891	3.69	74L300	0.32	BA1330	2.75	BC301	0.45	BD410	0.52	BF324	0.23	BT122	2.48	CD4025	0.64
1S44	0.05	ZSC1893	3.02	7805 TD-Z20	0.63	BA145	0.19	BC302	0.53	BD412	6.27	BF336	0.33	BT123	1.98	CD4028	0.94
1SS012A	0.81	ZSC1929	2.25	7805 TD-3	1.16	BA148 DIDD	0.33	BC303	1.04	BD418	0.87	BF337	0.36	BT125	2.48	CD4047	1.06
1S921	0.06	ZSC1942	5.70	7806	0.73	BA154	0.40	BC307	0.18	BD433	0.47	BF338	0.40	BT126	2.48	CD4049	0.46
2N1302	0.27	ZSC1945	4.53	7808	2.39	BA156	0.05	BC307A	0.14	BD434	0.49	BF355	0.49	BT128	2.48	CD4050	0.55
2N1303	0.38	ZSC1953	1.93	7812 TD-3	2.85	BA157	0.22	BC308	0.18	BD435	0.49	BF362	0.66	BT129	3.07	CD4052	0.75
2N2218	0.42	ZSC1957	0.95	7812 TD-Z20	1.16	BA159	0.12	BC308A	0.11	BD436	0.60	BF363	0.60	TBA970	3.06	CD4053	0.80
2N2219A	0.40	ZSC1959	0.31	7815	0.64	BA182	0.19	BC309	0.17	BD437	0.49	BF371	0.49	BT151-800R	1.15	CD4069	0.29
2N2222	0.38	ZSC1962	1.93	7818	1.66	BA222	0.52	BC317A	0.13	BD438	0.40	BF391	0.25	BT151 500R	1.38	CD4081	0.25
2N2646	0.80	ZSC1969	2.92	7824	0.64	BA284/2	0.17	BC327	0.15	BD441	1.42	BF393	1.59	BT16018	2.42	CD4083	0.72
2N2904	0.36	ZSC1985	0.55	AC107	0.73	BA301	0.87	BC328	0.11	BD442	0.66	BF417	0.84	BT16218	2.51	CD4511	1.10
2N2905	0.43	ZSC1983 TR	7.00	AC117	0.43	BA302	1.24	BC337	0.09	BD507	0.60	BF418	1.87	BT18024	4.43	CP5521	17.83
2N2906	0.38	ZSC2009	0.34	AC123K	0.43	BA311	1.32	BC338	0.12	BD509	1.42	BF422	1.29	BT18124	4.89	CT12E	3.07
2N3053	0.27	ZSC2029	2.32	AC128	0.34	BA312	0.97	BC360	0.34	BD510	1.07	BF423	1.12	BT18214	5.99	CX034	11.83
2N3054	0.99	ZSC2027	1.43	AC138	0.09	BA313	0.76	BC368	0.24	BD518	1.50	BF435	0.54	BT18224	2.97	CX085D	3.14
2N3055	0.61	ZSC2028	2.11	AC141	0.29	BA317	0.40	BC440	1.09	BD519	1.50	BF450	0.35	BU105	1.50	CX104	9.64
2N3055H	0.85	ZSC2057	1.18	AC142K	0.43	BA318	0.09	BC441	0.04	BD529	1.32	BF451	0.29	BU106	2.48	CX108	9.16
2N3442	1.16	ZSC2073	1.54	AC151	0.28	BA328	4.77	BC455	0.36	BD530	1.10	BF457	0.41	BU108	1.50	CX109	7.86
2N3702	0.14	ZSC2078	2.39	AC153	0.34	BA333	1.37	BC455	0.36	BD533	0.67	BF458	0.39	BU109	2.25	CX121	11.83
2N3703	0.14	ZSC2091	1.30	AC176	0.30	BA401	0.62	BC460	0.42	BD534	0.53	BF459	0.52	BU110	5.89	CX130	8.76
2N3704	0.14	ZSC2122A	5.12	AC179	0.28	BA511 (IC)	2.94	BC461	0.47	BD535	0.77	BF460	1.56	BU111Y	4.16	CX131	11.83
2N3705	0.14	ZSC2141	1.86	AC183	0.72	BA521	2.02	BC462	0.30	BD536	0.61	BF469	0.31	BU124	1.38	CX134	11.84
2N3706	0.14	ZSC2166	1.98	AC187	0.39	BA524	8.94	BC463	0.64	BD537	0.74	BF470	0.55	BU126	0.90	CX136	11.49
2N3707	0.16	ZSC2216	0.69	AC187K	0.43	BA526	7.98	BC464	0.64	BD538	0.67	BF471	0.31	BU134S	4.57	CX137	11.83
2N3711	0.11	ZSC2233	2.20	AC188	0.25	BA532	2.67	BC465	0.64	BD548	0.83	BF472	0.33	BU1204	1.58	CX138	11.83
2N3771	2.04	ZSC2271	4.01	AC188-01	0.49	BA536 (IC)	2.95	BC477	0.32	BD580	1.17	BF479	0.61	BU205	1.08	CX157	4.84
2N3772	1.71	ZSC2278	1.14	AC188K	0.43	BA6304A	2.92	BC478	0.32	BD590	1.17	BF480	0.60	BU206	1.27	CX158	4.10
2N3773	2.29	ZSC2314	0.87	AC193K	0.65	BA843	3.96	BC479	0.41	BD598	1.25	BF491	0.32	BU207	1.65	CX170	7.62
2N3819	0.41	ZSC2335	10.41	AC194K	0.65	BAV18	0.26	BC532	0.28	BD677	0.53	BF495	0.64	BU208	1.12	CX177	6.75
2N3823	1.17	ZSC2526	1.87	AD140	1.06	BAV19	0.11	BC546	0.17	BD679	0.57	BF506	0.43	BU208/02	1.97	CX506	9.33
2N3904	0.62	ZSC2551	1.26	AD145	1.60	BAV20	0.11	BC547	0.10	BD680	0.76	BF509	0.76	BU208A	1.12	CX507	7.62
2N3908	0.62	ZSC2570	2.39	AD149	0.90	BAV21	0.34	BC548	0.10	BD681	1.48	BF523	0.20	BU208D	1.95	CX755	12.95
2N4101	1.33	ZSC2570A	1.05	AD161	0.56	BAX12	0.11	BC549	0.10	BD695	2.30	BF594	0.27	BU209	1.93	CX758	7.62
2N4240	3.30	ZSC2578	6.75	AD162	0.46	BAX13	0.11	BC550	0.10	BD696	2.47	BF595	0.27	BU226	2.95	D1693	2.59
2N4444	0.90	ZSC264A	4.82	AD262	1.05	BAX16	0.11	BC556	0.16	BD697	3.60	BF596	0.18	BU312	2.38	DEC1	2.20
2N4914	0.72	ZSC2671	1.99	AF114	2.47	BB119	0.17	BC557	0.10	BD698	1.85	BF597	0.27	BU326	2.00	DEC2	2.20
2N5064	0.71	ZSC2728	0.95	AF115	1.24	BC107	0.13	BC558	0.10	BD699	3.49	BF617	1.05	BU326A	2.20	E1222	0.40
2N5253	0.50	ZSC2785	0.75	AF117	0.50	BC107B	0.11	BC559	0.10	BD700	3.70	BF618	1.05	BU326S	2.20	E5024	0.28
2N5294	0.50	ZSC372	1.40	AF118	1.20	BC108	0.15	BC560C	0.14	BD702	3.70	BF694	0.22	BU406	1.49	E5386	0.28
2N5296	0.49	ZSC373	1.16	AF127	0.50	BC108B	0.15	BC635	0.26	BD707	1.06	BF757	0.59	BU407	0.82	E5529	0.25
2N5297	0.50	ZSC383	1.33	AF139	0.53	BC109	0.12	BC636	0.26	BD709	1.12	BF758	0.65	BU407D	1.00	E8021	1.29
2N5298	0.61	ZSC388	0.50	AF178	1.46	BC109B	0.15	BC637	0.24	BD710	0.80	BF759	0.47	BU412	5.29	E9003	0.26
2N5490	1.49	ZSC394V	0.81	AF179	0.55	BC113	0.14	BC638	0.20	BD807	0.34	BF760	0.65	BU426	1.90	E9005	0.50
2N5496	0.59	ZSC41	2.19	AF180	0.55	BC116A	0.25	BC639	0.20	BD809	0.75	BF762	0.70	BU426A	1.67	ESM432C	4.60
2N6107	0.58	ZSC45															

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

HA1338	7.50	M1130	5.35	NE646N	2.98	SAS560	1.85	SN76620	2.59	TA7109	3.71	TC4053BP	4.34	TDA2611AQ	2.98	TIP30C	0.30
HA1339	2.33	M191	6.32	NE650N	4.34	SAS560S	2.26	SN76622	1.85	TA7120P	0.64	TCA150	1.79	TDA2612Q	4.68	TIP31A	0.34
HA1342	2.65	M193	18.55	NE6548N	4.18	SAS560T	5.42	SN76623	0.69	TA7122B/P	0.92	TCA160B	1.79	TDA2620	1.96	TIP31B	0.38
HA1350	3.75	M51102L	6.35	NP1106	5.61	SAS570	1.78	SN76630	2.55	TA7124P	2.34	TCA270Q	1.71	TDA2631	1.96	TIP31C	0.50
HA1365	4.02	M5115P	5.24	OA200	0.11	SAS570S	2.61	SN76640	4.24	TA7130P	1.27	TCA270S	2.15	TDA2631	2.73	TIP32B	0.69
HA1365V	1.86	M51231P	3.04	OA202	0.11	SAS570T	5.02	SN76651	2.57	TA7136AP	1.27	TCA270SQ	1.65	TDA2640	2.59	TIP32C	0.40
HA1366VWR	4.32	M5124P	4.82	OA40	0.14	SAS580	2.85	SN76660N	2.48	TA7137P	0.98	TCA290A	2.19	TDA2643	12.12	TIP33C	0.80
HA1367	1.36	M5134-3041	4.13	OA90	0.08	SAS5800	2.09	SN76665N	1.49	TA71414P	3.87	TCA420A	2.36	TDA2651	4.65	TIP34	1.18
HA1368	1.90	M51394P	11.97	OA91	0.09	SAS590	2.85	SN76666N	1.41	TA7146P	4.23	TCA440	1.93	TDA2652	6.95	TIP41A	0.49
HA1368R	2.45	M5142P	5.49	OA95	0.09	SAS5900	2.56	SN76705N	1.34	TA7148P	1.67	TCA4500A	2.16	TDA2653	5.85	TIP41B	0.65
HA1370	3.71	M5143P	7.33	OC28	2.52	SAS5960	1.97	SN76707N	4.39	TA7149P	3.26	TCA530	2.16	TDA2654	6.18	TIP41C	0.45
HA1374	4.80	M5144P	3.77	OC29	2.15	SAS6000	2.57	SN76709	5.12	TA7161P	5.45	TCA690	10.26	TDA2655	5.44	TIP42A	0.49
HA1377	3.96	M51513L	2.55	OC35	1.06	SAS660S	1.33	SN76709N	5.45	TA7162P	2.59	TCA690B	2.04	TDA2660	2.47	TIP42B	0.79
HA1389	2.39	M51515BL	3.23	OC36	1.28	SAS6610	1.33	SN76730	3.36	TA7169	9.54	TCA690B	3.30	TDA2660	2.47	TIP42C	0.53
HA1389R	2.05	M51516L	2.95	OC44	0.35	SAS670	1.33	SN76810N	3.96	TA7171P	2.79	TCA730	3.81	TDA2670	2.48	TIP42	0.65
HA1392	3.90	M51517L	3.71	OC45	0.18	SAS6700	3.53	SN76820N	0.90	TA7172P	1.41	TCA740	2.48	TDA2670A	1.94	TIP48	0.92
HA1394	3.95	M5152L	2.88	OC75	0.44	SAS670S	1.33	SN94011	5.54	TA7176P	2.48	TCA750	2.25	TDA2680	3.20	TIP49	3.61
HA1397	3.76	M51522	4.77	ON188	1.87	SAS6710	1.33	SN94042	4.35	TA7193AP	6.67	TCA800	5.95	TDA2680A	2.65	TIP54	3.65
HA1398	3.98	M5191P	4.94	ON236	1.06	SAS6800	2.53	SP6385	0.55	TA7193P	5.50	TCA800Q	5.95	TDA2780AQ	6.14	TIP55A	3.65
HA1406	2.06	M5192	2.20	OT112	1.08	SAS6810	1.43	STAA41C	2.75	TA7201P	2.71	TCA830S	2.71	TDA2790Q	5.12	TIS43	1.34
HA1452	1.63	M5194AP	5.74	OT121	1.32	SBA550B	4.50	STK0029	5.54	TA7202P	2.47	TCA900	2.04	TDA2791	2.50	TIS90	0.28
HA17723	5.94	M53273P	1.02	PD144	2.24	SBA750	1.61	STK0039	5.35	TA7203P	2.18	TCA910	1.65	TDA2795	2.78	TIS91	0.29
HBF4030AF	8.48	M53274P	1.33	PT2014	0.89	SC488P	2.09	STK0059	7.17	TA7204P	2.16	TCA940E	2.93	TDA3000T	2.55	TMS1000L	11.86
HO38750A53	2.71	MA06	1.07	PT5006	2.48	SC9503	1.85	STK0060	7.63	TA7205	1.38	TCC300	3.89	TDA3000A	11.49	TMS3748NS	14.95
HD4480	17.16	MA8001	0.82	PT6042	1.79	SC9504P	1.95	STK0080	9.16	TA7206P	6.25	TCE527	1.86	TDA3190	2.68	TMS4116	2.06
HD44801A05	17.49	MB3705	1.81	R1038	2.19	SC9511P	2.89	STK0100	3.96	TA7207P	3.34	TCE82	1.08	TDA3300B	1.08	TM06	1.76
HEF4001P	0.67	MB3712	1.85	R1039	2.19	SC9567	1.33	STK0103	9.25	TA7208P	2.15	TCE83	1.08	TDA3500	4.25	TY6010B	2.97
HEF4001BP	0.67	MB3713	1.89	R2008B	1.33	SG264A	5.26	STK0114	8.94	TA7210P	3.58	TCE84	1.08	TDA3501	7.25	UY05G	1.14
HEF4011	0.29	MB3730	3.25	R2009	1.98	SG608	8.26	STK0115	7.75	TA7214P	3.63	TCEP100Q	10.25	TDA3506	9.98	U143M	3.08
HEF4528	0.60	MC13002	6.22	R2001B	1.33	SG613	8.75	STK0116	6.91	TA7215P	2.58	TCEP100	9.61	TDA3510	6.96	U37003	0.49
HM6231	9.81	MC1303P	2.16	R2029	1.33	SG629	10.27	STK022	5.25	TA7217AP	1.37	TD190	0.95	TDA3520	9.71	UA723CA	5.53
HM6232	8.89	MC1307P	1.92	R2030	1.33	SG6533	8.31	STK025	12.50	TA7222	1.95	TD3700H	0.60	TDA3521	13.39	UA758PC	5.29
HM9102	3.22	MC1310P	1.30	R2257	2.38	SI-1125HO	13.86	STK040	8.70	TA7227P	2.81	TD3F800H	4.86	TDA3540	2.98	UA763PC	3.38
HM9104	3.24	MC1327P	1.33	R2265	1.49	SI-1125H	7.90	STK043	10.48	TA7229P	4.45	TD3F800R	3.66	TDA3560	5.00	UA7710	2.31
HM9105	3.24	MC1330P	0.89	R2305	1.18	SKE2F 1/04	1.39	STK054	7.13	TA7233P	5.32	TD3F900H	4.16	TDA3561	6.50	UA810	2.36
HT4207	17.16	MC1349P	1.99	R2306	1.36	SKE2G 2/04	0.96	STK070	22.31	TA7240P	7.83	TD41003A	1.79	TDA3561A	7.90	U12N2216F	7.70
JTT2003	0.22	MC1350P	1.61	R2322	0.59	SKE2G 3/04	0.99	STK077	7.57	TA7245P	7.50	TD41005A	2.22	TDA3571A	6.24	U12N216F	2.15
K174YP	3.46	MC1351P	1.33	R2323	0.76	SKE4F 1/02	1.32	STK078	8.62	TA7245P	5.94	TD41006A	1.69	TDA3571Q	8.23	U12N216F	6.32
KA2101	2.92	MC1352P	1.12	R2348	2.01	SKE4F 1/06	0.73	STK082	11.86	TA7252P	3.15	TD41010	1.15	TDA3576	7.09	U1C1009C	2.75
KC581C	6.32	MC1357P	2.15	R2354A	2.01	SKE4F 2/06	0.85	STK086	13.57	TA7609	1.17	TD41011	2.40	TDA3590	6.79	U1C1026C	1.24
KC582C	3.97	MC1358P	1.30	R2354B	2.01	SKE4F 2/08	0.86	STK1201	6.66	TA7676P	2.81	TD41028	2.85	TDA3590B	1.54	U1C1028H	2.00
KC583C	5.54	MC14001	2.40	R2441	0.49	SKE4F 2/10	1.24	STK1110	7.32	TA7676P	3.33	TD41029	2.49	TDA4050A	2.87	U1C1031H	2.77
L129V	0.25	MC14013	0.41	R2443	0.88	SKE4G 2/02	1.90	STK2230	7.70	TAA310A	1.16	TD41035T	2.55	TD41180P	1.92	U1C1025H	2.90
L200CV	1.69	MC14016CP	0.84	R2461	1.50	SKE5F 3/10	1.06	STK415	1.27	TAA320A	1.27	TD41034B	2.42	TD41260	1.52	U1C1032H	0.60
LA1111AP	0.88	MC14017	0.26	R2477	1.02	SL1310	1.34	STK433	4.95	TAA350A	0.80	TD41037	3.95	TD41280	7.20	U1C1030H	2.27
LA1201	1.02	MC14025	0.60	R2501	1.28	SL1327E	3.13	STK435	5.94	TAA435	1.82	TD41037D	1.28	TD41290	4.50	U1C1031H	4.50
LA1210	1.56	MC14049UBC	1.05	R2540	1.98	SL1430	2.39	STK436	7.21	TAA570	0.37	TD41041	2.16	TD41440	4.90	U1C1031H2	6.00
LA1230	2.87	MC1438R	1.58	R2540X	3.30	SL1430T	1.31	STK437	7.00	TAA570	1.74	TD41044	2.62	TD41440	4.27	U1C154H	1.93
LA1320	2.87	MC14493P	2.82	R2615	0.67	SL1432	2.25	STK439	8.31	TAA611B12	1.30	TD41047	1.21	TD41442	3.95	U1C1156H	2.96
LA1352	1.54	MC14556CP	3.47	RCA1195NB	2.16	SL414	3.09	STK441	11.28	TAA621AX1	2.00	TD41054M	4.10	TD41442	4.20	U1C1182H	2.94
LA1357N	11.07	MC17724CP	3.48	RCA1693Z	5.30	SL432A	3.44	STK443	10.29	TAA660	4.24	TD41059B	0.80	TD41443	4.78	U1C1182H	1.82
LA1363	6.21	MC17724CP	3.48	RCA1693Z	5.30	SL437	7.43	STK459	9.40	TAA661B	1.00	TD41060	2.59	TD41443	2.27	U1C1182H	1.25
LA1364	3.02	MC17818C	2.18	RCA1633A	1.02	SL439	2.48	STK460	10.75	TAA700	2.59	TD41082	3.06	TD41443	2.27	U1C1213C	0.99
LA1365J	3.44	MC7824CP	4.68	RCA1633A	1.36	SL480	3.14	STK461	9.68	TAA840	2.59	TD41104	5.61	TD41440	2.87	U1C1217C	2.47
LA1378	6.52	MC7824CP	4.68	RCA16800	1.38	SL490	2.37	STK463	11.53	TAA930	4.87	TD41151	2.17	TD41460	2.84	U1C1217C	2.47
LA1385	1.94	MC789M12	0.83	RCA1678M12	2.38	SL901B	8.32	STK465	10.31	TAA970	2.83	TD41170	1.37	TD41461	3.11	U1C1212C	1.72
LA1387	7.60	MC789M24	0.94	RCA16801	0.95	SL917B	9.96	STK466	11.77	TAD100	2.52	TD41170S	3.25	TD41462	4.46	U1C1351C	1.81
LA3155	1.43	MCR1011	0.67	RCA16802	1.08	SL918A	11.07	STR441	9.45	TAG232-600	0.73	TD41180	3.25	TD41462	3.25	U1C1355C	1.81
LA3300	1.54	MCR106-5/6	0.85	RCA17028	2.48	SN16861N-07	2.73	STR453	8.16	TAG625-600	1.06	TD41190	2.11	TD41490	2.31	U1C1350C	1.07
LA3301	1.41	MCR207	2.28	RCA17074	6.80	SN16880N	3.62	STR6020	8.31	TBA120	1.05	TD411902	2.48	TD41490	3.15	U1C1350C	2.13
LA3301	1.23	ME0402	0.77	RCA17576	1.58	SN16896N	10.25	T6007V	0.95	TBA120A	1.05	TD41200A	1.43	TD41490	3.15	U1C1362	7.75
LA4003P	4.20	ME0404	0.26	RCA60857	4.95	SN29715N	6.06	T6007	0.62	TBA120AS	1.24	TD41220	1.95	TD41490	2.92	U1C1366	4.14
LA4031P	3.20	ME0404/2	0.47	RGF10	0.50	SN29716N	3.04	T6016	0.40	TBA120S	1.05	TD41230	3.23	TD41490	5.44	U1C1366	7.51
LA4032P	2.35	ME0411	0.28	RT402	1.58	SN29717N	7.19	T6017	0.72	TBA120SB	1.05	TD41235	3.08	TE527	1.38	U1C1360C	4.14
LA4050P	1.57	ME0412	0.24	RT905A	2.38	SN29717N	11.95	T6018V	0.40	TBA120T	0.95	TD41270	3.76	TE538	0.49	U1C1458	1.48
LA4051P	1.79	ME4102	0.58	SO280	1.14	SN29722AN	7.65	T6021	0.40	TBA120U	2.50	TD41327A	1.50	TE626	1.49	U1C302C	2.51
LA4100	1.25	ME5458	10.02	SO281	2.14	SN29744AN	2.29	T6022V	3.92	TBA1440	2.03	TD41327B	1.82	TEA1002	3.47	U1C322C	4.94
LA4101	1.30	ME6002	0.26	SI1299	4.74	SN29764AN	1.38	T6026	0.98	TBA1440G	7.20	TD41330	1.76	TEA1009	1.86	U1C341C	4.10


Long-distance Television

Roger Bunney

November was an extremely gloomy month – with reception matching the weather. Very few Sporadic E signals were received: Iain Menzies (Aberdeen) noted RUV (Iceland) ch. E4 on the 5th, late in the evening, and that's about the only item of importance. The Leonids Meteor Shower produced lively results here in the Southampton area, with many pings of miscellaneous material in Band I, particularly on the morning of the 17th. You'll get very short pings of signal via MS reflection in Band I on most mornings of course – if you're prepared to wait with a receiver on tune and with good sync locking. The lack of signals is depressing but is to be expected during the winter months, with only Belgium ch. E3 and Holland ch. E4 rising at times here above the noise level to confirm that the receiving system is actually working!

Robert Copeman (Sydney) reports that the Australian SpE season has started, with many Australian ch. 0-2 signals present, also Dunedin ch. 2. The new sunspot cycle has commenced, with a count of 32 on the 8th rising to 50 on the 14/15th then dropping towards the end of the month. Hopefully we'll in due course experience another record peak of solar activity, with world-wide reception of the low v.h.f. channels, as we experienced in the late seventies.

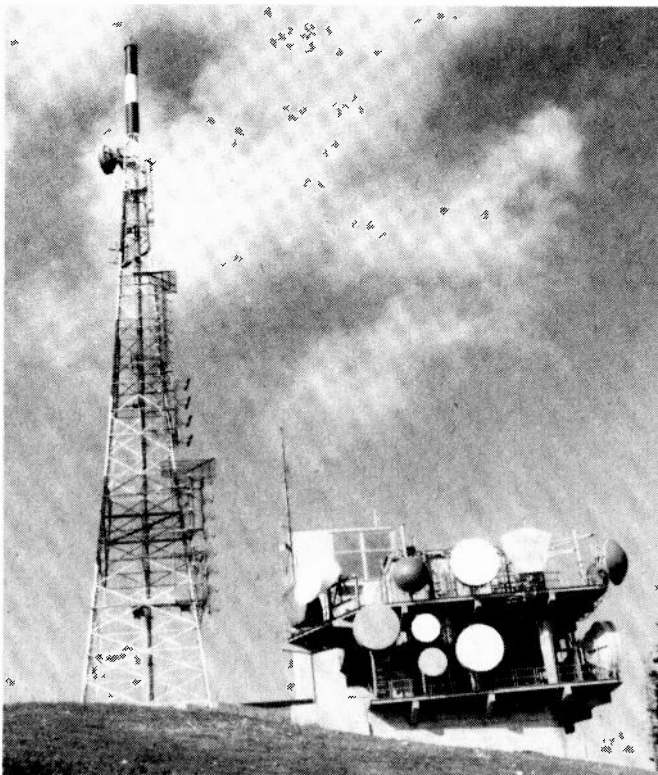During the October tropospheric openings Keith Chaplin (Barrow-on-Soar, Leics.) received a suspected MTV-1 (Hungary) signal in Band III. It was photographed at 1842 GMT on October 27th. The ch. R9 signal



The transmitting site at La Dole, Switzerland.

couldn't be identified at the time but the "Video Reklam" caption suggested MTV. It's now been identified by Igor Hajek as an advertisement for a domestic furniture factory at Kanisza, Hungary. From this information it appears that the transmitter was the 5kW outlet at Miskolc, north east of Budapest. A remarkable catch! Apparently an ARD-1 (W. German) signal faded and the stronger MTV signal came up for some two minutes before fading back again beneath ARD-1.

The log of October tropospheric reception received from Ryn Muntjewerff (Holland) is more like a list of EBU TV transmitters: 21 E. German, 9 Swiss, 2 Austrian, 15 Polish (including TVP-1 Ploc ch. R29), 11 Czechoslovakian, 17 Danish (including 2 regional), 18 Norwegian, 49 Swedish and 10 Russian stations were received in Band III and at u.h.f. The Norwegian signals all came from low-power relays. The most impressive Russian reception was from Vilnius on ch. R31 (600kW e.r.p.) at a distance of 1,350km. This was on the 17th at 0957-1120. Other transmitters received include Slonim, Kaunas, Klaipeda, Srodno and Kaliningrad, mostly on the 27th from 0630 onwards. Ryn comments that many of the signals were S5. Ducting was present since they were swamping the nearer stations. Ryn lives in an excellent, flat area of course and has a high lattice tower with stacked multiple director u.h.f. arrays for each group.

News Items

Switzerland: A correspondent recently visited the La Dole transmitting site and took the accompanying photograph of the mast. The Telecine aerial panel is just below the u.h.f. cylindrical shroud (which houses the SRG/TSI arrays), on the opposite side to the microwave dish, and appears to be horizontally polarised. There are also Band I/II/III arrays on the mast – the use of the Band III system is not known.

New Zealand: Four regional "warrants" are being offered for New Zealand's third channel, which is to be commercially financed. Three warrants will cover the North island, comprising the Auckland, Bay of Plenty and Wellington regions, while the South island will be offered as a single region. A fifth warrant is on offer to provide a news service. A Maori group, the Aotearoa Broadcasting System, which has NZBC support, is applying for one warrant and says that if successful a third of its programme output will be in the Maori language.

S. Korea: Three of the five TV networks started stereo/dual language transmissions last October, using a modified (for the system M standard) version of the W. German system. The main sound is at 4.5MHz, as usual with system M, the second carrier being at 4.724MHz. The Japanese single carrier f.m.-f.m. system was tried but dropped in favour of the W. German two-carrier system. Dual-sound receivers are available at typically £350 for a 16in. colour set, and for about £50 you can get a sound tuner for use with an older set. My thanks to Jean-Louis Dubler for this and other information on Korean TV.

Satellite news: The Orbita Technologies Corporation of New York is offering a terminal capable of tracking the Russian Molniya craft, which is in an elliptical orbit. The terminal costs some \$56,000 and is intended for use by universities to provide Russian first programme material for language studies. The system includes a 15ft dish with head electronics and standards conversion to system M for feeding to a standard US TV set. Though Gorizont is visible along the eastern seaboard no geosynchronous

Russian craft that carries TV can be seen farther west. Molniya operates in a non-geosynchronous orbit to provide TV coverage of far northerly Russian outposts that can't receive signals from a satellite in orbit over the equator.


In brief: The NOS Goes transmitter has been seen using the FUBK pattern with a "Goes" identification during the early morning period. . . . A decision on how to operate the Swedish third channel, either as a commercial or Pay-TV service, has still not been made though a start is due later this year. . . . Despite funding problems the third Egyptian channel has now opened, with two hours of transmissions on most days, four hours on Thursdays and Saturdays.

Tandy Dual-standard Portable Review

We were recently able to test the new Tandy dual-standard 5in. monochrome portable Model 16-9030 – the "Portavision". At the time of writing this set is in short supply, but it should be readily available in Tandy stores from late January. The UK version features full coverage of Bands I/III/IV/V system I (UK), with switching for system L (French standard). A variant that initially came into the UK by mistake (in very small numbers) is a 220V version for systems B/G/L.

It's an attractive set measuring $8 \times 4\frac{7}{8} \times 10\frac{7}{8}$ in. Power is from a 240V a.c. mains supply (lead supplied), an external 12V d.c. source (lead not supplied) or nine HP2(D) internal batteries. A standard 3.5mm earpiece jack with speaker muting is fitted. The seven-section telescopic aerial extends to $31\frac{1}{2}$ in. A flush, coaxial socket is fitted on the left-hand side and adjacent to this are switches for internal/external aerial selection and system changeover (I/L).

For tuning there's a vertical thumbwheel and a band switch for u.h.f., v.h.f.-H (Band III) and v.h.f.-L (Band I). The tuning control is positive in action with no backlash. Tuning indication is via vertical tuning scales and a moving centre strip – which proved accurate. The scales are marked 2, 3, 4 (chs. E2/3/4), 5 through 12 (chs. E5-12), 1 through 6 (chs. L1-6) and at u.h.f. chs. 21-68. The numbering for 1-6 is based on the provisional French channel numbering when the Band III services were being re-engineered: in practice the channels are L5-10 (L2-4 are in Band I). Since the French Band I channels have reversed sound/vision spacing, Band I reception of French signals will not work correctly (there's no reference to French Band I reception in the instruction book).

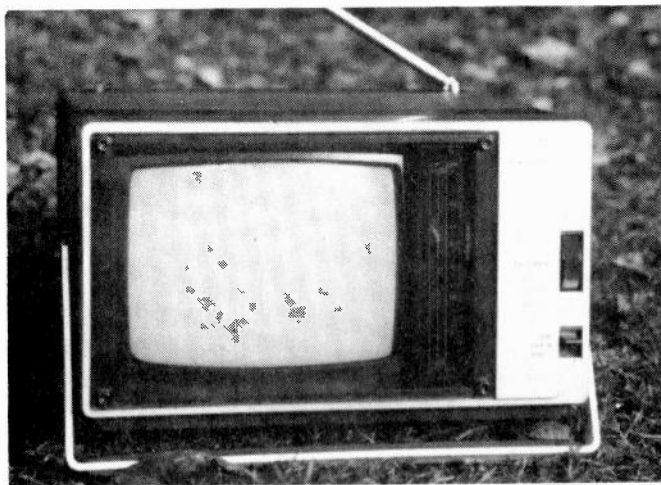

The Tandy 5in., dual-standard Portavision Model 16-9030.

AERIAL TECHNIQUES

WE
HAVE
IT
ALL
HERE



Yes indeed we have – and it's all in our **CATALOGUE FOR 1986** packed with Aerials, Amplifiers, Filters, Rotators, Hardware etc. etc. for all types of aerial installation/requirement including **TV/FM DXing** within Bands 1 to 5 inclusive. Multi-Standard PAL/SECAM colour televisions are featured for DXing, Domestic and Overseas television reception. **AERIAL TECHNIQUES** also provide a complete and comprehensive consultancy service for ALL reception queries/problems (SAE please). We can now offer an attractively priced 11GHz Satellite System for the reception of ECS 1, INTELSAT V and other Satellites, separate leaflets are available on request. For a speedy dispatch, ACCESS and VISA Mail & Telephone orders may be placed for any of the items listed in our comprehensive Catalogue. We are active TV/FM DXing specialists – your guarantee of honest and knowledgeable advice.

DXers-Special Offer:
ANTIFERRE UP1300 VHF Masthead Amplifier (40-230MHz) for Bands 1, 2 & 3 Gain 19dB, Noise figure only 2.5dB **£16.90**
Matching 12V Power supply unit for use with the above amp **£11.25**

WHETHER YOUR NEED IS FOR LOCAL OR FRINGE RECEPTION, ALTERNATIVE CHANNELS, TV/FM DXING, OR FOR A DISTRIBUTION SYSTEM, AERIAL TECHNIQUES IS THE 'ONE STOP' ADDRESS FOR ALL EQUIPMENT.

**AERIAL TECHNIQUES IS UNIQUE –
OUR HIGH QUALITY CATALOGUE COSTS ONLY 65p.**

Why not send for your copy today – please include an SAE with all enquiries. All prices inclusive of VAT and carriage. Delivery 7-10 days.



AERIAL TECHNIQUES (T)
11 Kent Road, Parkstone,
Poole, Dorset BH12 2EH. Tel: 0202 738232



Measurement showed the following coverage: Band I 46.5-70.25MHz, Band III 175-228MHz, Bands IV/V 456-872MHz. Internal (non-user) adjustments are provided for l.f. and h.f. tracking, so it's possible that the u.h.f. coverage could be extended downwards to take in the 435MHz ATV band.

The construction of the electronics is relatively good. The two tuners are minute, each measuring $1\frac{5}{8} \times 1 \times \frac{1}{2}$ in. Both have varicap tuning and three stages – r.f. amplifier/mixer/local oscillator. The u.h.f. tuner's i.f. output is taken to the v.h.f. tuner for further amplification and both tuners have a.g.c. The i.f. strip consists of a fixed-gain preamplifier, a SAW filter and an i.c. for gain/a.g.c./detection etc. Switching for positive- or negative-going vision is via a buffered phase inverter. On the sound side there's switch selection between a system I intercarrier circuit and a tuner-fed system L i.f. strip.

The gain was found to be good, the screen being very lively and the contrast adequate. The i.f. selectivity, given the wide i.f. bandpass characteristic, showed a very sharp fall at h.f., indicating an excellent SAWF skirt response. A degree of adjacent channel interference will be inevitable under strong SpE conditions with the transmitted carriers 2MHz or so apart. For fringe reception at u.h.f. the selectivity was found to be good, the gain high and the picture quality sharp. The receiver responded well to weak Band I MS signals, with immediate locking. Timebase locking showed a wide pull-in range, even on weak signals. Slightly different line lock positions were noted for positive- and negative-going vision signals.

When used for Band I reception the telescopic aerial produced instability across the entire band, but perfectly stable results were obtained with an external aerial. In any

event the telescopic aerial would not be used for efficient reception – the enthusiast would use a more conventional aerial array. There's a clear circuit diagram in the booklet supplied.

I felt that the flush-mounted coaxial socket was rather fragile – it could possibly cause intermittency in time. It might be better to use a short coaxial lead terminated in a line socket to avoid wear on the panel-mounted socket. It seems a pity that the three W. European standards (I, B/G and L) are not covered – no mention is made of the scrambled Canal Plus Band III signals.

In conclusion I was very impressed with the performance and potential of the receiver – in fact I bought one. Available from Tandy stores at £89.95 inclusive.

1986 Meteor Shower Dates

The Quadrantids Shower occurred on January 1st-6th. The rest of this year's meteor showers will take place as follows:

Lyrids, April 19-25th peaking on the 22nd.

May Aquarids, April 24th-May 20th, peaking on May 5th.

Delta Aquarids, July 15th-August 20th, peaking on July 29th.

Perseids, July 25th-August 20th, peaking on August 12th.

Orionids, October 16-27th, peaking on the 21st.

Taurids, October 20th-November 30th, peaking on November 1-10th.

Leonids, November 15-20th, peaking on the 17th.

Geminids, December 7-15th, peaking on the 13th.

Ursids, December 17-25th, peaking on the 22nd.

Our thanks to the British Astronomical Association (Meteor Section) for the above information.

An unusually high peak of intense MS activity was produced by the Draconids/Giacobinids Shower (which is not expected to produce activity this year) on October 8th, 1985 between 0730-1300 GMT. The receiver system used for monitoring (a BAA forward-scatter radar tuned to 70-312MHz) saturated over the 0915-0955 period. Dr. J. W. Mason would like to receive reports of identified reception and any observations at 51 Orchard Way, West Barnham, West Sussex PO22 0HX – not questions or requests for information please, just reports which will enable enthusiasts to contribute to original research. Send details of reception, time and location.

New Aerials

Three new aerials have become available in the UK over the past few weeks.

The South Midland Communications Ltd. (Rumbridge Street, Totton, Southampton) HS965V is a vertical, colinear sleeved receiving system housed in a fibreglass tube some 1.86m long. It clamps at the base end to a support mast while the upper end features a form of top-capacity hat. This takes the form of three horizontally positioned fins. The base stub has three ground-plane radials. It's intended to cover the range 60-950MHz (the suppliers say it provides useful gain down to below 50MHz). The gain is 3dBd over the upper part of the coverage.

Revco Electronics Ltd. (Modbury, Devon) have introduced the Radac wideband 25-550MHz system which is intended for use with scanners. Revco describe it as a "nest of dipoles" – it has twelve elements arranged around a central support insulator. The lower-frequency elements are inductively loaded.

The above aerials have SO239 terminations. The Radac can be obtained from Garex Electronics, 7 Norvic Road, Tring, Herts. – we hope to review a sample shortly.

The Wolsey Colour King and Triax BB Grid 'are familiar aerials to most TV enthusiasts, comprising four full-wave dipoles stacked one above the other with a large reflector plane. This arrangement gives a wide operating bandwidth. Jaybeam Ltd. (Kettering Road North, Northampton) have now introduced a similar system called the Aluminium Billboard (Model JBB/4). This covers 470-860MHz with a peak gain of 13dBd, a typical front-back ratio of 25dB and a horizontal beamwidth of 48° (-3dB points). A balun is fitted.

French System L Channels

The French System L channel allocations are as follows:

Channel	Bandwidth (MHz)	Vision carrier (MHz)	Sound carrier (MHz)
L2	49-57	55.75	49.25
L3	53.75-61.75	60.5	54
L4	57-65	63.75	57.25
L5	174.75-182.75	176	182.5
L6	182.75-190.75	184	190.5
L7	190.75-198.75	192	198.5
L8	198.75-206.75	200	206.5
L9	206.75-214.75	208	214.5
L10	214.75-222.75	216	222.5

French Fifth Service Channel Allocations

The following list indicates when channels allocated for the new fifth French TV service will become available for use. Actual service starts may take a considerable time but throughout the coming year we should be able to receive an increasing number of French private (commercial) TV stations, particularly during tropospheric openings.

Channels allocated at end 1985:

Lyon – 22, 25, 28	Lille – 47
Toulon – 57, 60, 63	Grenoble – 34, 37, 4
Grasse-Cannes – 63	Montpellier – 31, 37, 34
Cherbourg – 35	Nimes – 31, 37, 58

First quarter, 1986:

Paris – 33, 36, 35	Metz – 47, 50
Marseilles – 32, 38	Poitiers – 41, 44, 47
Nantes – 65, 21, 58	Perpignan – 41, 44, 47
Lens/Bethune/	
Douai/Arras – 51, 54	Sant Nazaire – 49, 52, 55
Nancy – 49, 52, 55	Besancon – 37, 21
Le Havre – 4, 53, 56	Maubeuge – 32
Dijon – 46, 57	La Rochelle – 48, 51, 54
Reims – 58, 64, 61	

Second quarter, 1986:

Bordeaux – 40, 43, 46	Caen – 38, 60, 63
Toulouse – 29, 32, 34	Avignon – 51, 54, 57
Valenciennes – 49, 37	Limoges – 38, 45
Saint Etienne – 2, 28	Amiens – 49, 52, 55
Tours – 30, 33, 36	Thionville – 59
Rennes – 31, 34, 55	Lorient – 59, 62, 65
Orleans – 35, 32, 47	Angouleme – 31, 34, 37
Brest – 57, 60, 63	Saint Quentin – 30, 33, 36
Angers – 51, 54, 39	Montlucon – 49, 52, 55
Dunkerque – 59, 62	Nevers – 41, 46, 36
Le Mans – 59, 62, 65	Bourg-en-Bresse 38, 52, 32
Le Creusot – 23, 60, 63	Pau – 57, 60, 63
Bayonne – 30, 33	Aix-en-Provence – 59, 62
Troyes – 50, 53, 56	Hagondange – 56
Valance – 65, 53	

Servicing Notes on the Amstrad CPC464

Christopher Holland

Following last year's series of articles on microcomputers, which used the Amstrad CPC464 to illustrate the techniques involved, the following servicing notes should be of interest: they are based on eighteen months' experience of this computer and its accompanying monitors, the colour CTM640 and the green screen GT64.

First, the good news for all TV technicians is the fact that the great majority of problems encountered with these units relate to the monitors and tape decks, which should be familiar territory. Microcomputer faults as such are relatively rare and tend to show up early in the warranty period. The fault-finding principles here are similar to those required with modern microcomputer-controlled VCRs, although the relationship between the symptoms displayed on the monitor's screen and the actual fault is not always obvious. The i.c.s used in the computer are very reliable, which is just as well since most of them are soldered directly into the double-sided print: a useful rule of thumb is that the i.c.s that normally give trouble are the ones the designer has decided to fit in i.c. holders.

Computer Faults

The most common computer fault is that at switch on the monitor's screen is either blank or full of garbage. The cause is usually failure of the ULA chip IC116 (20RA043) or the microprocessor chip IC111 (Z80A). If possible, substitution is the simplest check as both are pluggable. If this fails to effect a cure, try the following steps:

(1) Check the 5V supply and earth lines to the major chips, particularly the ULA, the Z80A and the ROM i.c. (IC103, TMM-23256P-1950). In the event of an intermittent 5V supply, check the socket for the supply lead from the monitor.

(2) Check the clock pulses – a frequency counter is needed for this. Note that the 16MHz crystal X101 rarely gives trouble, also that the wire link soldered across the body of the crystal is a convenient earth connection point for probes etc. (the ULA's heatsink is not earthed). Check for the 16MHz clock pulses at pin 8 of the ULA: if absent suspect the ZN7400 clock oscillator IC125. The Z80A is clocked by a 4MHz pulse at pin 6: if missing check transistor Q103 (ZTX312L – shown as TR3 on the PCB) and confirm that 4MHz pulses are leaving the ULA at pin 39.

(3) Check the reset pulse. This is fed to pin 26 of the Z80A, pin 35 of the PIO chip (IC107) and pin 37 of the ULA. Failure of these reset pulses is normally due to IC110 (74LS132).

Other problems experienced with the computer include the following.

If any of the keyboard buttons fail to respond or do so intermittently, suspect dust or dirt on the keyboard contact PCB: this is a fairly robust panel and is not prone to broken tracks.

The complaint "crashing out", or in layman's terms a program that stops at some point while it's running, accompanied by failure of the computer to respond to any instructions, is invariably caused by the ULA i.c.

Liquid spillage normally seems to occur via the printer and disc ports. While the most common liquid spilt into VCRs seems to be beer, home computer users seem to be coffee drinkers. I'm not sure what conclusions we can draw from this! While I've seen a few VCRs effectively written off by beer, the CPC464's PCB seems to be fairly tolerant of coffee and cleaning the areas affected should provide a cure.

The Cassette Deck

As previously mentioned, problems with the computer section of the CPC464 are fairly rare: much more common are faults with the tape deck causing programs not to load or to load partially or intermittently. This shows up on the monitor as "read error A" or "read error B" messages. The first steps to take are to clean the tape deck heads and to confirm that the problem is not due to poor quality tapes – watch out for distinctly second-hand looking C90 tapes that have provided years of audio use before being acquired for the computer.

Once the heads have been cleaned, check the head alignment by attempting to load a good quality prerecorded software tape – the "welcome tape" that comes with each CPC464 is suitable as it comprises eleven blocks of data. If "read error" messages appear as soon as loading commences, realign the head while monitoring the data being loaded at pin 7 of IC302 on the cassette recorder PCB.

Should the tape load perhaps seven or eight blocks of data before a "read error" occurs, or even intermittently load the whole program, suspect a faulty cassette motor. These can develop wow and flutter after a period of use – in some bad cases this can be heard from the internal loudspeaker and be seen on a scope.

"Read error A" is usually caused by a faulty motor while "read error B" is due to incorrect head alignment. This should be taken as a guide however, not as a hard and fast rule. Failure to load anything usually means that the heads are way out of alignment. Note that the heads themselves don't usually give trouble.

Monitors

Finally the area where TV technicians will feel most at home, the CTM640 colour monitor and the GT64 green screen monitor. The circuitry used is straightforward but the following notes may be of help.

With a dead colour monitor the usual culprit is the switch-mode power supply chip IC501 (SKT7308). If this should fail be sure to check all the following components unless you want to see the replacement i.c. disintegrate at switch on: resistors R501 (5.6Ω, 5W), R502 (1Ω, 3W), R511 (10Ω, 0.25W), R521 (1Ω, 0.25W) and zener diodes D507 (RD3-6FB1) and D510 (SR2M). With a dead set whose power supply is functioning normally, check zener diode D402 (RD11EB2) in the protection circuit if there's no line timebase activity.

The only other problem likely to be encountered is one of the primary colours missing. In this event check the

relevant output transistor on the tube base panel.

The only thing to watch out for on the green screen monitor is the complaint "goes into lines after a few hours". In this case check the adjustment of the line hold control L703. We've had to reset this on a number of monitors after they've been in service for about a year.

The easiest method of doing this is to centralise the picture with L703 after programming in a border of a different shade of green to the rest of the screen. Lack of line and field sync, as well as video problems, is often due to the lead that connects the keyboard to the monitor – these leads can have a hard life.

Video Scrambling Techniques

Andy Emmerson, G8PTH

The main reason for encoding or scrambling a video signal is to prevent unauthorised viewing. Whether the material is being broadcast or distributed via cable it's likely to be available to those not supposed to watch the programmes. In the USA, receiving and decoding subscription signals without payment is legally "theft of service". In addition to the commercial aspects there are also political reasons for scrambling. For example, several European governments have insisted that satellite TV signals are encoded to prevent their reception by domestic viewers – this is the reason why Sky Channel uses such an elaborate scrambling technique (Oak-Orion) which I believe has not to date been cracked by enthusiasts. Other scrambling techniques are usually less sophisticated and present little challenge to those prepared to experiment or alternatively buy a ready-made pirate decoder. It's estimated that in the USA between 25 and 30 per cent of subscription TV viewers are pirates.

To the broadcast professional any form of scrambling is a profound nuisance. Not only is the encoder another piece of equipment to go wrong, it also introduces deliberate video signal distortion. No broadcaster likes to transmit a degraded signal, particularly if he has no control over its linear restoration at the receiving end.

Basic Scrambling Arrangements

Video signal encoding systems can be classified in several ways. The simplest division is between off-air and cable-only arrangements. The former tend to be more sophisticated. Scrambling implies the need for a key or reference signal to be sent to make descrambling possible. If this signal can be sent along the same cable, disguised by being at a different frequency, the decoding circuitry can be much simplified and the cost to the operator reduced. This option is not available to off-air broadcasters however, making the decoders much more complex.

A more interesting method of classification is by the technique used. These include (1) concealed channels, (2) traps, (3) reverse traps, (4) video inversion, (5) sinewave sync suppression, (6) outband gated sync suppression, (7) inband gated sync suppression, (8) variable line delay and (9) active line rotation. These techniques can all be applied on either a static, pseudo-random or dynamic basis. In addition they can be used singly or in various combinations. The accompanying audio signal can also be handled in a number of ways.

With dynamic encoding an incomplete signal is transmitted. A complex algorithm is required at the receiving end to reconstitute the signal in its original form. The algorithm can be supplied in the form of a magnetic card which the subscriber inserts in his decoder – this "smart card" would be supplied only to paid-up subscribers. Further, the algorithm/card can be changed regularly.

Many systems use addressable decoders which require a signal supplied by the broadcaster to turn them on. Each decoder has a digital "serial number" and is activated by a code transmitted during the field blanking interval. Stolen decoders and defaulters can have their service instantly withdrawn from the broadcaster's central computer.

The Concealed Channel Technique

The concealed channel technique is simple but effective so long as viewers have normal TV sets. It involves using "mid-band" channels on cable TV networks. Many frequencies cannot be used for broadcasting since they are allocated to other radio services. There is no reason why a subscription cable TV service should not use them however. They can be made viewable to customers by means of an r.f. converter. This technique is becoming less popular as TV sets and VCRs in both Europe and the States are increasingly being supplied as "cable ready" with all-band tuners that cover the between band frequencies.

Traps and Reverse Traps

Traps and reverse traps are cable TV techniques. The trap is nothing more than an effective notch filter tuned to whatever channel is used for the premium programme. When placed in shunt across the customer's feeder cable he's prevented from seeing this programme: it's simply removed when the customer pays the subscription fee. Clearly a secure housing is required for the trap – generally a locked case.

The reverse trap is just as crude. With this technique a "spoiler" signal is injected in the guard band between the upper end of the vision bandwidth and the audio subcarrier. It distorts both signals, making the subscription channel unusable unless the cable company inserts a notch filter to remove the spoiler. In this case however the knowledgeable viewer can provide his own notch filter.

Video Inversion

Static video inversion is a simple technique and requires the decoder to turn the signal the right way up again. When performed on a quasi-random, line-by-line or frame-by-frame basis, as in the Oak-Orion system, it is much less simple to deal with. The clue to decoding this mess may be supplied by signals in the line or field blanking intervals or by an algorithm in the decoder itself.

Sinewave Sync Suppression

With a standard video signal the most negative-going part of the signal excursion is the sync section that's used to control the scanning. If a line-rate sinewave is added to

the signal – see Fig. 1 – the receiver will instead lock to the deepest part of the video waveform, with most unattractive results! The sinewave required for decoding is transmitted as low-level a.m. on the audio subcarrier. Unscrambling the video involves demodulating the sinewave, inverting it and using it to “straighten out” the distorted video signal.

Gated Sync Suppression

Outband gated sync suppression is another cable TV only technique as it requires a separate pilot frequency for the decoding signal. As we’ve already noted, a TV set relies on a negative-going sync signal to time the line and field scanning. If we suppress the sync pulses by 6dB in amplitude the receiver will lock to random video information, producing a scrambled picture (see Fig. 2).

To restore the picture to normal, the scrambling waveform is inverted and retransmitted as a.m. on a separate frequency known as the pilot frequency. This pilot frequency is generally hidden in a section of the r.f. spectrum not used for TV, often between 93-114MHz. The demodulated signal is added to the scrambled waveform to boost the sync pulses by 6dB.

The inband gated sync suppression technique is similar to that just described, only in this case the descrambling signal is contained within the bandwidth of the TV channel as amplitude modulation of the audio subcarrier, as in the sinewave sync suppression technique previously described. This makes it suitable for broadcast use.

Variable Line Delay

Variable line delay is the technique used for scrambling the French Canal Plus signals. It’s also used in N. America. The principle is to delay some lines of the TV frame to a greater or lesser extent, on a pseudo-random basis (see Fig. 3). This creates a picture with much reduced definition. The decoder has to switch in delay lines of variable length in the correct sequence in order to reconstitute a clean picture. Further information on the system used for Canal Plus and a pirate decoder design that hit the headlines was given in the December 1984 and June 1985 issues of *Television*.

Active Line Rotation

Active line rotation is a BBC technique proposed for DBS use. It’s the most ingenious of those described in this article since the TV line is sliced across its length at up to 256 points. The resultant line segments are then transmitted in quasi-random sequence. A decoder provided with the appropriate algorithm has the task of reassembling the line segments in the correct order. The algorithm would be provided by a “smart card” and the subscriber would need both the card and a personal identity number (PIN) to make his decoder work.

New Ideas

New scrambling systems are being devised all the time to defeat the signal pirates. Here’s a plaintive note from a Canadian experimenter. “They go positive and negative and put a sinewave into one of the fields. The result is that the picture flashes like hell. That’s not all. They go positive and negative with a twist: one field is all positive, the other all negative – odd and even lines are not of the

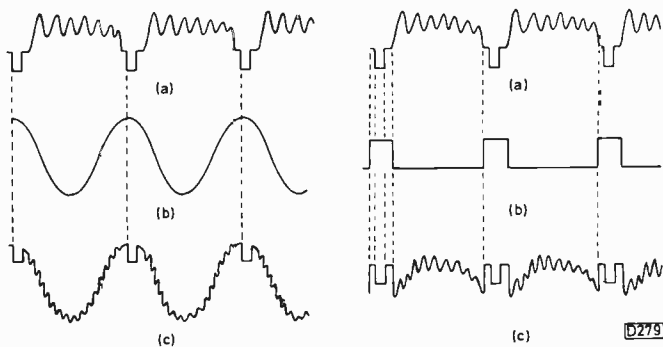


Fig. 1 (left): The sinewave sync suppression technique. (a) Normal video signal. (b) Line-frequency sinewave. (c) Result of combining signals (a) and (b).

Fig. 2 (right): The gated sync suppression technique. (a) Normal video signal. (b) Sync suppression signal. (c) Result of combining (a) and (b).

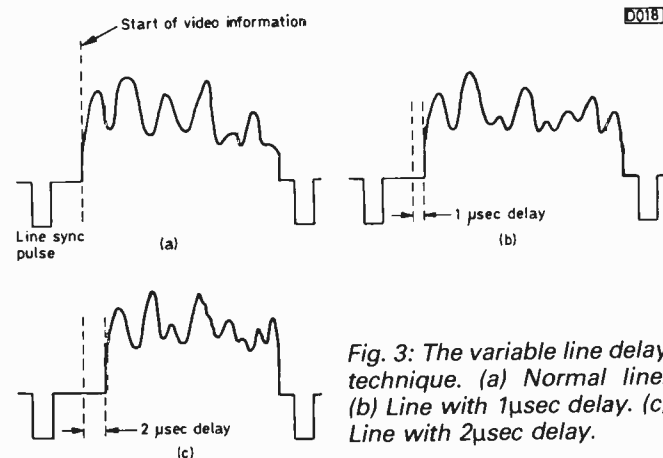


Fig. 3: The variable line delay technique. (a) Normal line. (b) Line with 1µsec delay. (c) Line with 2µsec delay.

same polarity. And they switch merrily at different speeds between all these modes.” No wonder it’s called dynamic encryption!

The Audio Signal

Several audio scrambling systems are in use. After the video signal chicanery previously described these may sound a bit tame. One system is to transmit the audio signal on a subcarrier in the same way that US f.m. radio stations transmit an auxiliary uninterrupted music service or bleeps for radiopaging. The audio signal frequency modulates a 32 or 62.6kHz subcarrier: you can’t hear 32 let alone 62.5kHz, nor can the TV speaker reproduce these frequencies, so a special decoder must be used.

Another system is to transmit the sound in the form of suppressed carrier a.m. on a 12.8kHz subcarrier – this is the technique used for Canal Plus. One dodge is to treat the audio as a stereo signal and transmit the difference between the identical left and right channels on a 19kHz subcarrier.

In all cases the normal audio channel can be used as a “barker” service, advertising what’s being missed by not subscribing to the premium service, or for community news and information.

The latest systems use digital techniques. The conventional audio subcarrier is not present: instead, two digital audio channels are carried in the line sync period. The sound is digitised into twelve-bit words which are then compressed into eight bits. This technique gives total security and enhanced signal quality at low carrier-to-noise levels.

Vintage TV: The Bush T91

Chas E. Miller

Most older engineers will remember the "Bush 9in." with affection. The small Bakelite-cabinet models from the TV12 onwards set standards of reliability and ease of servicing that were seldom equalled for many years. This vintage piece takes us back farther however, to the first post-war Bush television set, the Model T91. It was a solidly built a.c. only receiver with a number of interesting features. It had a total of eighteen valves plus the c.r.t. and employed the twin-chassis arrangement that was to become a feature of Bush sets for many years thereafter.

Vision Receiver

The vision receiver was of the t.r.f. type, using the well-known (notorious?) EF50 r.f. pentode, fresh from its triumphant or otherwise appearance in World War Two radar equipment. To be fair, apart from the poor base connections due to the short pins the valves had a useful performance, with a slope of 6.5mA/V. Stagger tuning was used to get the required bandwidth.

Four EF50s were used to provide r.f. amplification in the receiver section, the first two handling both the sound and vision signals. The strip was designed for dual-sideband reception from the Alexandra Palace transmitter, the alignment frequencies being 43MHz and 47MHz, i.e. 2MHz on each side of the vision carrier. Curiously enough there were no sound rejectors as such, the alignment instructions stipulating that the first two common r.f. amplifier stages should provide a gain of at least ten at the sound carrier frequency of 41.5MHz – if this was not achieved you had to retrim the stages until satisfactory results were obtained at the vision and sound frequencies. Thereafter we must assume that the sound take-off coil provided adequate rejection before the signal was passed to the other two vision only r.f. amplifier stages.

The arrangement of the coils in the t.r.f. strip was simplicity itself. Tuned anode, tuned grid coupling was used for all except the second stage, the coils being designed to produce the required bandwidth without being shunted by other components.

The decoupling arrangements used in the t.r.f. strip were characteristically elaborate, a forest of 500pF decouplers being connected between just about everything in sight and chassis. Following the normal practice of the time, each valve had a common earthing point to avoid spurious inductances being established via badly arranged chassis connections.

Tube Drive

The vision detector was a miniature diode, type EA50, another fugitive from radar sets. Another EF50 was used as the video amplifier, with the very low-value anode load resistance of 3.3k Ω (R22, Fig. 1). The output was d.c. coupled to the c.r.t.'s grid, so no d.c. restoration was required.

The cathode of the MW22-7 c.r.t. was strapped to the heater (no naughty heater-cathode leaks for Bush owners!) and was isolated from direct earth by a separate

mains transformer winding which was returned to an h.t. potential divider: it was set to 160-270V by the action of the brightness control. The tube's first anode was supplied with around 200V from a tap on a bleeder network across the e.h.t. supply. The latter employed a separate mains transformer which delivered 3.7kV to the anode of an HVR2 rectifier and 2V to this rectifier's highly-insulated heater. The e.h.t. obtained from this arrangement was 4.5kV, with a brace of 0.02 μ F reservoir/smoothing capacitors capable of holding a nasty shock for the unwary engineer.

The contrast was controlled by means of a potentiometer which set the cathode bias applied to the second and third r.f. amplifier. An additional local/distant switch varied and bias supplied to the first r.f. amplifier by a large factor.

Sound Receiver

For the sound strip the Bush designers decided to use a superhet circuit. The sound signal from the second r.f. amplifier was fed to a standard radio type ECH35 triode-hexode frequency changer. To prevent breakthrough of the local oscillator signal into the vision strip a rejector was fitted close to the hexode's grid coil. The i.f. was 725kHz, with an average bandwidth of 40kHz. Thus the full a.f. radiated by the transmitter could be realised with ease, and in Alexandra Palace days the sound didn't have to travel via frequency-limiting land lines (as radio programmes did!).

The ECH35 was followed by an EF39 i.f. amplifier stage, then an EBC33 double-diode-triode which provided detection, a.f. amplification and a.v.c. clamping. All akin to standard radio practice of the period. The output stage used an EL33 to provide approximately 4W of audio. A tone control was fitted, no doubt so that those unfamiliar high a.f.s could be reduced to the comfortable "mellow bellow" apparently beloved by contemporary radio listeners.

Sync Separator

The sync separator was simplicity itself (see Fig. 1), consisting of another EA50 diode (V7) which produced the line and field sync pulses at its cathode. The video signal, with positive-going sync pulses, was capacitively coupled to its anode from the cathode circuit of the video output pentode. A side benefit of this arrangement was reduced capacitive loading on the tube's video feed. In fact quite a bit of care went into the design of the video output stage. There was frequency-selective negative feedback in the cathode circuit and, in the anode circuit, a series peaking coil and l.f. boost.

Timebases

Both timebases employed thyatron oscillators, either a Mullard EN31 or Mazda T41 according to availability – minor adjustments to one or two component values were required depending on which type of valve was used. The

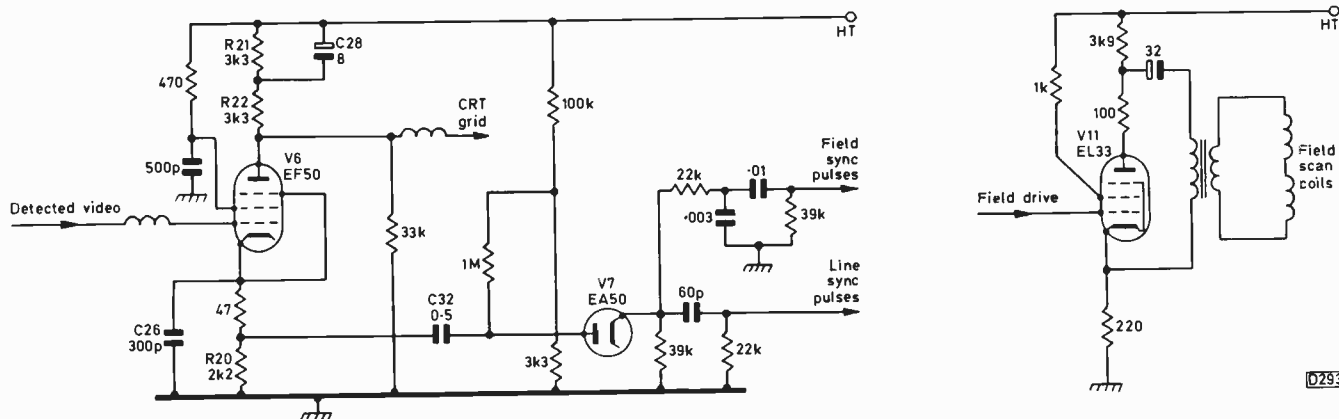


Fig. 1 (left): The Bush T91's video amplifier and sync separator circuits. A simple diode (v7) sync separator was used, the video signal developed across R20 being coupled to its anode via C32, but what a lot of trouble went into the design of the video output stage! At very low frequencies R21/C28 form part of the output valve's anode load, increasing the i.f. gain. The small-value screen grid and cathode decoupling capacitors introduce selective (medium-/low-frequency) negative feedback however. The stage's frequency response was obviously given careful consideration by the designers.

Fig. 2 (right): The T91's field output stage. Linearising negative feedback was introduced by returning the scan coupling circuit to the cathode of the output pentode.

gas-filled triode makes a simple oscillator circuit that's easy to synchronise. The problem occurs when the valve ages and becomes somewhat erratic in its firing.

An EL33 was used in the field output stage and an EL38 in the line output stage. The field output stage used RC plus transformer coupling (see Fig. 2) with negative feedback in the cathode circuit. A simple two-winding transformer was used for coupling in the line output stage, which looks particularly uncluttered to the modern eye in the absence of boost and flyback e.h.t. circuitry. Low-impedance scan coils were used for both line and field deflection.

One snag with the type of set where the e.h.t. continued unabated in the event of line timebase failure was the vertical white line that would be displayed if the set was left running in the fault condition. Fortunately the low e.h.t. voltage and the vigilance of early TV owners reduced the likelihood of a permanent burn on the screen.

The Power Supply

The hefty power supply had two mains transformers, one for the e.h.t. and the other for the h.t. and heater supplies. 310V was presented to the anodes of the two IW4/350 h.t. rectifiers which were used in a full-wave circuit. There was a great deal of h.t. smoothing employing no fewer than six large value electrolytics, two chokes and the focus electromagnet. The latter fed the h.t. to the line timebase and was shunted by a focus control network. Anyone who had experience of this type of focusing will recall that the heating-up effect of the electromagnet caused the sharpness of the picture to deteriorate frequently during an evening's viewing, calling for much adjustment. One could never bring oneself to leave the setting alone when the set was next used from cold and rely upon the warm-up to bring the picture into focus, because the programmes were so sparse one couldn't afford to miss out on anything!

Later Bush Sets

The T91 was one of the last TV designs to have a "traditional" power pack. The following TV1 (9in.) and TV2 (12in.) were of the live chassis type. While most of the circuitry remained as in the T91 an important change

was the move to flyback derived e.h.t. These sets retained the focus coil and required even more electrolytics because a half-wave mains rectifier was used. They were followed by the TV12, the first of the classic Bakelite cabinet 9in. sets, which had lots of EF50s (again) and was of the a.c./d.c. type (but still had the focus coil!). This model and its companions were followed by the TV22 series, which employed mostly miniature valves and a circuit that remained largely unchanged for many years, even when Band I/III models appeared.

A Vintage Restoration

405 may be dead but it won't lie down! Vintage sets are still being used to display vintage pictures, thanks in no small measure to articles that have appeared in *Television* on recording 405-line material. Steve Rowley tells me he's just restored a 1939 Ekco Model TA201. This was a small (7in.) table model that provided a vision display only – the accompanying sound had to be fed to the pickup sockets of an ordinary radio receiver. Steve's set up consists of a Philips VCR and a professionally made modulator. It enables him to view genuine archive material, including good old Andy Pandy and the Flower Pot Men, as well as the fondly remembered BBC Test Film of the early fifties. Congratulations Steve – may your success encourage others.

Thirty Years of Independent TV

On September 22nd last Independent Television celebrated its thirtieth birthday. It was on that day in 1955 that the then ITA came on air for the first time from the Croydon Ch. 9 transmitter. The occasion was marked by special compilations of archive material on Channel 4 and S4C, mostly of official opening ceremonies but interspersed with actual programme extracts and early commercials. This was followed by a special showing of the first episode of the made-for-TV Robin Hood series.

Sadly, the man who played the hero in this series, Richard Greene, didn't live to see this replay. He passed away earlier last year after a lengthy illness, in his 67th year. For those of us who were around when ITV started Richard Greene's Robin Hood will always typify the occasion. Episode one was shown in the Midlands area on

the very first night, 17th February 1956, and seemed to revolutionise television for us. It's difficult to believe now that this was the first filmed series to be seen on our screens, opening up a vast new dimension. Prior to this, drama productions had been made in comparatively cramped studios, with all the limitations that this implies. Technicalities alone wouldn't have made the new series succeed however: Richard Greene brought to the part the experience of nearly twenty years in films, much of his time having been spent in Hollywood – a thoroughly professional and engaging performance.

An Early Home-built Set

Reader E. Bligh has sent me details of a home-built set he made in the late forties – from the floor up, including the mains transformer. It used the well-known VCR67 radar tube which gave a green picture with a diagonal measurement of about 6in.

Much of the circuitry is reminiscent of the Bush T91 we've been considering, with EF50 vision and sound t.r.f. strips and EA50 detector diodes. The video amplifier used another EF50 while the sound was taken care of by a 6J5 driving a 6V6 output tetrode. The sync circuit was rather more elaborate, with a brace of EA50s and yet another EF50. Both timebases used T41 thyratrons followed by 6SN7 push-pull output stages.

The power supply was a most impressive piece of work

– winding the transformer must verily have been a labour of love! It provided all the voltages required in the set, including the e.h.t. – according to Mr. Bligh's notes the e.h.t. winding alone required some 12,000 turns of wire. The five other secondary windings provided 2V at 2A for the heater of the e.h.t. rectifier, 4V at 1A for the c.r.t.'s heater, 6.3V at 3A and 4V at 4A for the valve heaters, 400-0-400V at 150mA for the h.t., and 4V at 2.3A for the h.t. rectifier. The vision and sound stages were operated at 280V h.t. while the timebases received the full 400V. The loudspeaker field coil formed part of the smoothing network. A U21 was used as the e.h.t. rectifier and an MU14 as the h.t. rectifier.

Interestingly, the contrast control varied the h.t. applied to the first three r.f. amplifiers. An 0-1mA meter was wired into the video amplifier's grid circuit, presumably to monitor the strength of the incoming signal. Mr. Bligh used the set in Cricklewood, London NW2, so reception from Ally Pally must have been excellent at a distance of only four-five miles.

Comments Welcome!

One can imagine Mr. Bligh's sense of achievement when he first saw pictures on this genuinely home-constructed set. I'm most grateful to him for letting me see the circuit, and would welcome letters from other readers on such sets and vintage topics generally.

VCR Clinic

*Reports from Christopher Holland,
Philip Blundell, Eng. Tech., Les Harris,
John Cahill and Eugene Trundle*

JVC HRD120/Ferguson 3V35

With the exception of the troublesome cassette loading mechanism, mechanical problems have been virtually non-existent with this generation of JVC machines. So when I was confronted with the "no fast forward or rewind" condition I was inclined to suspect an electronic fault. On these machines fast forward and rewind drive are provided by the capstan motor, the direction being altered by reversing the polarity of the voltages at pins 1/2 of connector 28 on the main servo/mechacon panel. A check here showed that no voltage was present, and since the front indicators lighted when the relevant function was selected I felt that the operation i.c. and the microcomputer chip were probably in order. The main suspects were Q206, Q207 and IC206 which functions as a series of switches controlled by the microcomputer i.c. These switches route the capstan motor current in the required direction, the current being supplied by Q207.

Since the switching control voltages appeared to be correct the voltages at pins 2 and 8 of IC206 (input from Q207) were checked and found to be absent. Q207 was checked out of circuit and appeared to be fine so IC206 was replaced. This seemed to do the trick but while the spools turned in the fast forward and rewind modes when asked to do so they did this very slowly. It turned out to be my fault: when I replaced Q207 and refitted its heatsink I somehow managed to break the print to its collector. A few minutes spent with the soldering iron and everything was once more in order.

I've since had a further problem in this area. A machine intermittently damaged tapes because they were not being wound back into the body of the cassette during

unloading. Checks in the drive circuit just mentioned showed that adequate voltage was being made available to the drive motor at all times, so the belt that transmits this drive from the motor was checked. It turned out to be o.k. Consistent loading torque was restored only after fitting a new motor.

C.H.

Ferguson 3V29

A slow, rolling noise bar appeared every few seconds during playback. I've encountered the symptom on a number of occasions, due to the capstan servo not locking because the control pulses are missing. Cleaning the control head normally provides a cure but on this occasion a scope check showed that the problem was in the drum servo – a trapezoid with no reference pulse was present at TP4.

I'd encountered this once before and a note in the corner of the circuit mentioned that the cause had been an open-circuit tracking control. Not this time however: the control declared its innocence when checked with an ohmmeter. Checks were next made around IC3 (HA11711). This showed that pulses were absent at pin 10. So the i.c. was very carefully removed – I've falsely accused HA11711s before. Sure enough a replacement i.c. made no difference.

Further checking finally brought me to the record phase switch preset R35 – its wiper had somehow become pushed in and no longer made contact with the track. Since the video heads appeared to have been changed at some stage I can only presume that the wiper was

dislocated by someone going through the head alignment procedure. C.H.

JVC HR7200/Ferguson 3V29

The card simply said "no picture" and my immediate reaction was that a simple head cleaning job would be all that was required. At switch on I was confronted with a blank raster however. As a first step I checked the camera/TV switch – most customers seem to flick this to the auxiliary position whenever anything goes wrong – but this one was in the correct position. I then noted that the channel indicator lights were o.k., and when the monitor's volume control was turned up there was good E-E audio. Off with the top cover for a quick check for foreign objects in the mechanism, then a check with the test tape. This showed that I could forget about head cleaning – a grey, unmodulated raster appeared, similar to that in the E-E mode.

Having confirmed that Ch. 4 was showing its test pattern a scope check was made at pin 24 of IC201. A good signal was present here but it was not re-entering the i.c. at pin 13. At this point I came unstuck because the circuit ceased to resemble the diagram. Then from the recesses of my mind I recalled a modified and revised diagram that JVC had kindly supplied some while back. This soon led to Q221, which had gone open-circuit base-to-emitter. C.H.

Sharp VC9700

These machines are renowned for not recording the sound every time. Changing the relays will often effect a cure but Sharp recommend changing C648 to 0.01 μ F and R693 to 10 Ω (0.25W) as well. P.B.

Sharp VC581/2/3

The loading motor circuit in these machines has been modified to prevent intermittent system control faults such as won't play after going into search, the LED lights up when a function command is given but the machine won't carry out the command, and the mechanism won't go to a given position. The modification is simply to remove C8001 (47 μ F) which is connected across the loading motor – on PWB-W. P.B.

ITT TR3913

Rewind and fast forward were o.k. but when play was selected the play LED lit, the brake solenoid clunked and nothing else happened. The cause of the problem turned out to be the cassette lamp – the vibration when the brake solenoid pulled in interrupted the lamp's filament – but only on playback! Which fool took this machine back to the workshop for a new cassette lamp . . . L.H.

Ferguson 3V29

The machine was tried out after fitting a new cassette lamp. A recording was made and this played back all right. The machine was stopped, rewound and playback was then selected again – but this time the pause, audio dub and play LEDs lit! As the fault was found to be intermittent the mechacon panel was replaced in an attempt to speed up diagnosis. This made no difference and control via the remote handset was found to give

correct operation. So the playback switch was replaced. This cleared the fault, though an Avo check on the switch failed to show the suspected high resistance. As a check the switch was fitted to another machine – the fault then showed up on this one! L.H.

Mitsubishi HS303

No sound erase, intermittent sound recording or no sound at all seems to be a stock fault on this machine though I've not seen it mentioned in VCR clinic. The cause is plug VK: Mitsubishi recommend soldering the wires straight to the print. J.C.

Mitsubishi HS302

The fault was noise bars on the screen after about two hours use. As the machine was completely enclosed in a timber cabinet I suspected heat to be the cause of the problem. A lot of time was wasted in the workshop before I found, using a hairdryer and freezer, that IC402 was faulty. J.C.

Fisher FVHP615

This machine ejected the tape immediately and there was no rewind. Examination showed that the tape was spilling out of the take-up spool because the take-up pulley was jamming under the chassis. A drop of oil on the pulley bearing cured the problem. J.C.

Mitsubishi HS303

The customer complained of a whirring noise and wobbling picture. It turned out that the capstan flywheel has a type of rubber glued to the bottom: some of this was loose and was rubbing as the capstan rotated, causing the noise. The wobbling was due to VR4A0 in the drum servo being misadjusted. J.C.

Toshiba V57

This machine was dead and on examination the mains fuse, located in a plastic box, had shattered. The cause was a short-circuit mains filter capacitor (0.022 μ F, 250V). I later discovered that children had been switching the machine on and off continuously with the remote control unit. Presumably this had produced spikes to cause the fault. J.C.

JVC HR3660/Ferguson 3V16

This one would apply to any Ferguson/JVC piano-key machine. The problem was no colour in record or playback, first intermittent then permanent. Checks showed that the chroma signal was reaching pin 13 of IC202 (AN305) which contains, amongst other things, the a.c.c. circuit and the main mixer, but there was no output at pin 11. Burst gating pulses were present at pin 1 but there was obviously no chroma feedback to pin 15. The voltage at pin 11 was abnormally high at around 10V. A bypass capacitor connected between pins 13 and 11 didn't restore colour – until pin 11 was disconnected from the print! The chip was faulty, with a low-impedance path from pin 11 to some signal-earthly point within the device. It's important to set up R216 (converter balance) and R335 (a.c.c.) when IC202 is replaced. E.T.

Servicing Teletext Receivers

Part 2

Mike Phelan

This month we'll consider the functions of the VIP (video input processor) and TIC (timing chain) chips in the Mullard/Philips teletext decoder.

The VIP is an SAA5030 or, in earlier versions, an M913 – the pin connections of these devices are the same. A block diagram is shown in Fig. 1. The incoming video is fed to pin 16 – the input comes via a 6MHz notch filter to remove the sound carrier which would create problems in a chip containing a 6MHz oscillator! It then follows three different paths.

The shortest one leaves the i.c. at pin 12, provided pin 10 is low as it is in the G11's teletext decoder. When pin 10 is high, an AHS (after hours sync) output is obtained at pin 12 – this is generated in the TIC by division of the 6MHz signal. The G11's decoder doesn't use this facility.

The second path takes the video to an adaptive data slicer. The input to this is a.c. coupled so that the ones and zeros of the data signal become positive- and negative-going excursions. The amplitude and quality of the signal can vary enormously at this point (see Fig. 2). After rectification each half of the signal charges the capacitors connected to pins 23 and 24: these maintain the slicing level at half of each opposite-going excursion of the signal. This gives us a much cleaner signal, though still one of varying amplitude – approximately half the original data signal amplitude. What we require is a TTL compatible signal of 5V peak-to-peak, with fast rise times, suitable for driving logic circuitry. The answer to this requirement is to pass the signal through a series of limiting amplifiers to square the signal before it emerges at pin 19.

It's important to appreciate that the data signal leaving the VIP at this pin still contains the remains of any low-

level composite video as no attempt has so far been made to gate this out – this is done in the TAC (text acquisition and control) chip. The signal will not contain chroma information since this would be of sufficient amplitude to be removed by the slicer. The burst would still be present however: we'll see how this is removed later.

The data signal from the slicer/squarer is also passed to the high-*Q* tuned circuit C1/R1/L1 connected to pin 21. The clock run-in at the beginning of each row (10101010) causes this to ring – it continues to do so until the arrival of the next clock run-in – shades of the passive chroma subcarrier generator used in the Rank A823 chassis! This signal is very important: after squaring, it's fed to the TAC chip.

The final path for the video input at pin 16 is to a sync separator. The field sync output obtained at pin 13 is adjustable in phase – this is necessary because it resets the line counter in the TIC chip. The line sync output is used to phase lock the 6MHz crystal oscillator (dot clock). Part of the phase-lock loop is in the TIC which (see Fig. 3) divides the 6MHz signal by six, then by 64, to obtain a 15,625Hz output. A sandcastle pulse is produced from this – externally to the TIC. This is fed back to pin 5 of the VIP.

The sandcastle pulse is separated into its two components within the VIP. The portion between 2.5V and 5V (CBB – colour burst blanking) goes to the adaptive data slicer to remove the burst from the video signal before slicing – a low-level 4.43MHz signal with no luminance content would upset the operation of the slicer. The bottom half of the sandcastle pulse (0-2.5V – PL, i.e. phase lock) is used as the reference signal for the phase

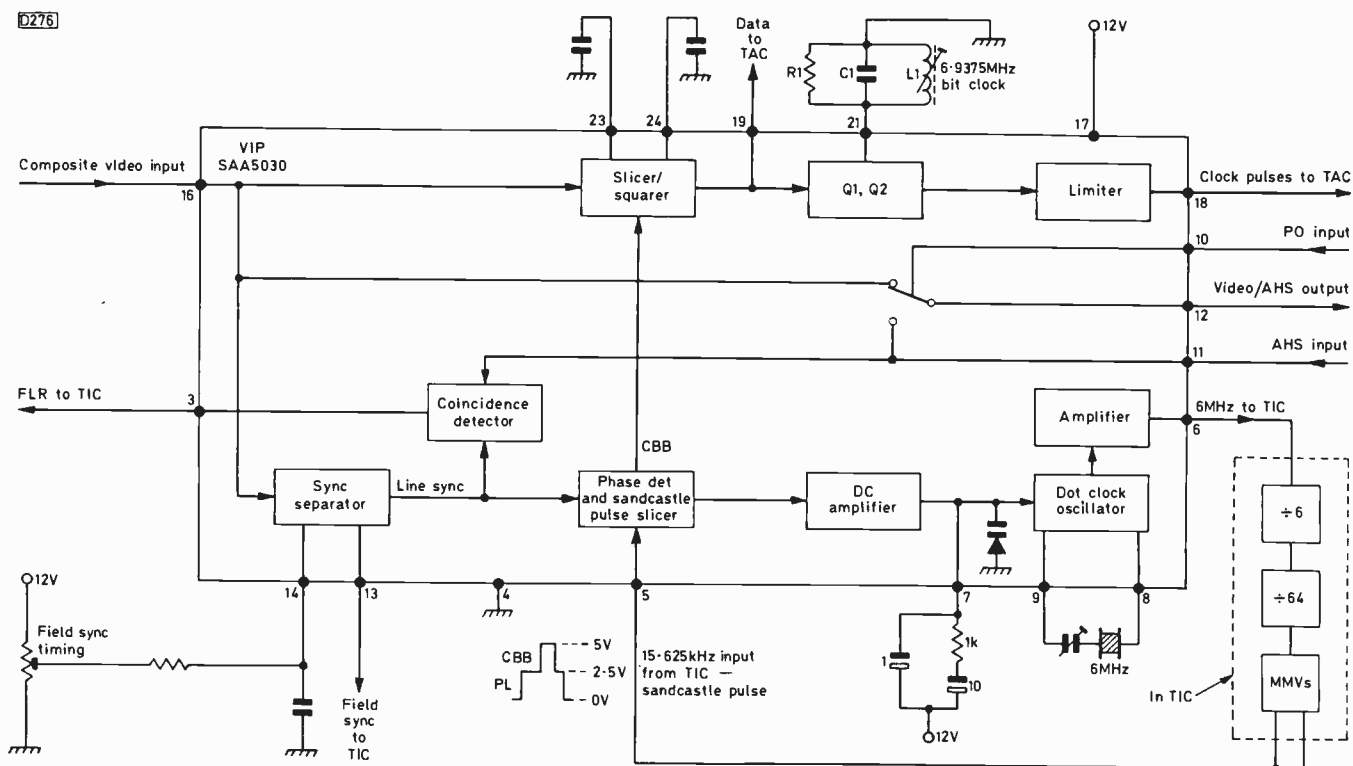


Fig. 1: Block diagram of the SAA5030 video input processor i.c.

rate) and is switched off during the DEW period when WACK (write address clock) from the TAC chip takes over. Don't forget that a teletext decoder has two functions which don't occur simultaneously – to receive and store signals, and to produce the teletext displays.

The final output, at pin 13 – LOSR enable (load output

shift register enable) – goes to the TROM chip to reset its control character flip-flops prior to the start of each line of the display. This signal also defines the character display period. At the end of this series we'll provide a glossary of all these strange mnemonics and abbreviations as a quick reference guide.

Computer Aided PCB Design

Malcolm Burrell

In the early days of electronics the components were hand wired to tagstrips which were usually mounted on a solid metal chassis. The assembly process required manual soldering of each connection, involving a large labour force, and not infrequently resulted in connections that were either left unsoldered or were badly made – dry-joints. Interconnections were made with insulated copper wire.

Enter the PCB

By the fifties the concept had evolved of preconfiguring the wiring in the form of thin copper tracks on a flat surface. The desired pattern of tracks is photographically transferred to a thin layer of copper on a paxolin or fibreglass base: etching away the unwanted areas of copper leaves what we call a printed circuit. Holes can then be drilled and the components inserted in their correct positions, with each connection made to a portion of track that links it to the other associated components. The entire assembly is passed over a bath of molten solder which can make perhaps hundreds of connections in a single operation.

Early printed circuit boards were notorious, due to hairline cracks and poor connections. They were not well suited to the high temperatures produced by thermionic valves in confined spaces, though perhaps much of the problem was basically due to the aesthetic demands made on designers of consumer electronics products at the time.

Modern techniques and solid-state circuitry, together with double-sided boards having independent wiring on both sides, have resulted in highly reliable products. Extremely complex electronic circuits can be assembled at a much lower cost.

PCB Layout

Designing the layout of a printed circuit board used to be something of a hit-and-miss process. With a fairly large number of discrete components, a certain amount of compromise was necessary. For example a supply rail might be conveniently run along one edge of the board, just out of reach of a resistor on the far side. To make contact with this one component it might be necessary to use longer connecting leads, vary the hole spacing and/or realign the tracks. Alternatively you could use additional pads with wire links between. Double-sided boards largely overcame this problem but created a design constraint similar to three-dimensional chess!

The use of integrated circuits and microprocessors changed many design concepts. Most chips don't come with long connecting leads, and although few peripheral components are needed with digital circuitry each i.c. pin will have a separate function. These connections are arranged in neat rows, with as few as eight pins on a timer chip to perhaps sixty on a microprocessor. The circuit

designer is not always aware of the problems involved in interconnecting a dozen chips, each having say sixteen connections. He designs the interconnections required to make the circuit work from a theoretical point of view. The PCB designer has to find ways of linking these 192 connection pins according to the original instructions. If an unforeseen problem or error occurs it may well be "back to the drawing board".

CAD Systems

Various CAD (computer-aided design) systems are available. They usually employ a VDU, keyboard and joystick interfacing with a computer which has a documented memory of component pin-outs and the physical profiles of the components to be used.

The designer presents his initial circuit diagram to the operator who then calls up the components by reference numbers from the data base. Having entered the information on the required interconnections between each component the operator plots the physical positions on the display and checks that the position of one component won't affect the placing of another. The autochecking facility assists in locating design errors by drawing attention to such things as any attempt to duplicate the number of a connecting pin.

Rubber Banding

Once the interconnection format has been inserted the operator moves on to the stage of "rubber banding". This gives on the VDU's screen a spaghetti-like presentation of all the component connections. By moving the cursor he can optimise the layout and separate the tracks that are to be on the top or bottom sides of the board. Since it's an interactive process, he can choose to vary the track widths to suit the circumstances – increasing the widths of supply rails for example.

Tracks can be laid vertically, horizontally or at an angle of forty five degrees. It's normal practice to run tracks vertically on one side and horizontally on the other. Where tracks on the top and bottom connect, a "via" hole is inserted.

To Final Artwork

Autochecking allows the operator to ensure that all programmed tracks have been laid. Track widths are checked and drilling information is produced. Four "films" are produced for the artwork in the case of a double-sided board: two give the top and bottom track information, a third gives the silk screen information and the fourth defines the solder resist pattern. Stored on disc or tape, the information can then be fed to a photoplotter that produces the final artwork.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.50 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

ITT CVC9 CHASSIS

There's intermittent loss of picture and sound signals, with only a blank raster and buzzing sound (occasionally sound from a foreign station is heard breaking through the buzz). The fault lasts for only about five seconds, its intermittent nature making it very difficult to make any conclusive checks.

We've had this fault on one or two occasions and have found it to be the result of one of the i.f. amplifier transistors T15/16/17 going open-circuit between the base and emitter. In view of the difficulty of diagnosis and access we'd suggest replacing all three transistors. T15/16 can be replaced with BF196s and T17 with a BF197. These lockfit types will fit directly. Ignore the original earth (screen) holes in the print – and beware of solder blobs.

PYE 725 CHASSIS

A stable picture can be obtained only with the brightness and contrast controls turned well down. Any increase in the setting of either control first affects the top two inches of the picture, where shading appears with verticals kinking at the intersection and slight hum on sound; further increase introduces field roll with the field then reducing to about half scan while the trip rate increases. The greater the white content of the picture the greater the effect. The h.t. is correct.

The earthy end of the contrast control is taken to the beam limiter sensing point in the line output stage. This point is smoothed by C573 (4.7µF), failure of which is the usual cause of this fault. It's beside the gun switches on the line timebase panel.

MITSUBISHI CT180B

The problem is lack of width – about an inch or so on either side. Initially the h.t. was slightly low with no control: replacing the 12V zener diode D901 in the error detector circuit put that right. The adjustments on the pincushion correction board have no effect on the fault.

An oscilloscope will be required to check the duration of the line flyback pulse. If it's less than 11µsec one of the bunch of flyback tuning capacitors C531/2/3/4 may have gone open-circuit. If it's correct check the boost diode D576 (SB-2) before suspecting short-circuit turns in the line output transformer.

FERGUSON TX10 CHASSIS

The mains fuse was open-circuit and the chopper transistor short-circuit. Are there any stock faults that could cause

this? Some checks have been made on the components on the primary side of the chopper transformer but everything appears to be o.k.

We don't know of any stock faults for this condition but we did have the same fault on one occasion and spent a lot of time before we found that the TDA2582 chopper control i.c. was faulty. Check also for shorts on the h.t. line. It's always worth replacing the focus control assembly on these sets. It tends to flash over, with dire consequences in various parts of the set. An improved type is now supplied.

SHARP VC6300

First the machine switched itself off during a recording. Now every time it's switched on it goes off again after the tape has moved about six inches.

There's either no take-up reel rotation or the machine thinks so. Check that the reel isn't stopping – if it does clean all belts and tyres and if necessary replace the clutch. If the reel isn't stopping check the output from the sensor at socket AF4: it should be 5-10V peak-to-peak – if not replace the opto unit under the take-up reel.

PYE V2000 VCR

This machine is working but produces a rather grainy picture with new tape and cleaned heads. A good service would seem to be required: any suggestions about what should receive attention?

Little preventive maintenance is possible with these machines, a good motto being to leave well alone! The symptoms of a worn head are snowy recordings while known good tapes are played back satisfactorily. To clean the heads properly, use isopropyl alcohol on chamois leather. Press the moistened leather against the heads on the drum and, keeping the finger still, rock the drum to and fro across the leather. Ingrained base material sometimes takes a long time to shift.

GEC V4000H

This machine is basically the same as the Hitachi VT8000-8500 series. It has the following intermittent fault. Whatever mode is selected – play, record, fast forward or rewind – the machine goes to stop after five-ten seconds (in play or record the machine first unlaces).

First check the operation of the after-load switch, which is not the most accessible of components in this machine. Towards the end of the loading sequence the load on the threading motor increases considerably and a loading belt that slips will prevent load completion – check visually that the loading poles go fully home. If the loading belt is in good condition it should be possible to stall the loading

QUERY COUPON

Available until 19th February 1986.
One coupon, plus a £1.50 (inc. VAT) cheque or postal order, must accompany EACH PROBLEM sent in accordance with the notice above.

TELEVISION FEBRUARY 1986

motor by grasping the large white nylon pulley. If the above points are in order a scope will be required to check for the presence of drum tacho pulses to the mechacon: absence of these shuts the machine down as a safety feature.

TEST CASE

278

Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

Current TV technology has greatly improved the performance and reliability of today's sets while considerably reducing their cost in real terms. What it hasn't done is to ease the difficulty of diagnosis when something goes wrong. A self-destruct situation is often present, particularly in power supplies and timebases, giving rise to the problem of how to attempt a diagnosis in the milliseconds (microseconds?) that it takes for a semiconductor device – often a large/elusive/expensive one – to be destroyed.

There are ways of countering this situation – cold checks, the use of external power supplies/variacs, dummy loads and current-limiting resistors – but occasionally a set that seems to defy all attempts at logical diagnosis comes along. This month's test case is one such example.

The guilty party was a Decca set fitted with the 70 series chassis. It arrived in the workshop with a job ticket bearing the single word "dead". And dead it was, with the 1A fuse F601 (in series with the chopper transformer's primary winding) shattered and blackened. It was no surprise to find that the BUW81A chopper transistor was dead short. This sometimes happens in these sets for no particular reason, so a new BUW81A was fitted. The items in series with its emitter – diodes D608 and D610 and resistor R636 (0.39Ω) – were also faulty and had to be replaced. Quick in-circuit checks on the driver pair Tr603/4 then proved that neither was short-circuit, so in with a new 1A fuse and switch on.

Pow! Bang! went the fuse, a wisp of smoke arose from the new R636 and the technician's morale plummeted. He'd enough problems without this! Diodes D608 and D610 (1N4007) had this time survived but were nevertheless replaced, along with the still gleaming BUW81A and R636. A more careful check on the chopper driver transistors revealed that the top one, Tr603, had some leakage. A new driver pair was fitted and L601, the coil in series with the base of the chopper transistor, was checked for continuity and good jointing. Since it was o.k. the decision was taken to apply the mains power – from a safe distance! It was a relief to hear the e.h.t. rustle up and the

loud sound (why do people always turn the sound and brightness up when a TV set fails?).

It would be nice to think that that was the end of the story, but that's not the stuff of a test case item, is it? Here's the nasty sequel. The receiver was set up and put on soak test, displaying a nice Ch. 4 test pattern. The next patient (a Ferguson camcorder, such is the variety of workshop life) was being anaesthetised on the operating table when a sizzling noise attracted our technician's startled gaze. He just had time to register that the picture on the screen of the Decca set had expanded to about 120 per cent of normal width before the splat of the blowing fuse signalled disaster.

After some totally undeserved comments about the parentage of the Decca design team, the shortsightedness of the storesman in having only three BUW81As in stock and the state of the world in general our harassed repairman went back into the Decca. The only clue he had to go on was that a vast increase in the 120V h.t. line voltage obviously occurred when the fault condition arose. This removed several possible suspects – it was unlikely for example that any of the rectifier diodes (D614/5/6) connected to the chopper transformer's secondary windings were faulty. Why wasn't the over-voltage facility in the highly intelligent TDA2581 chopper control chip being invoked? This depends on the action of zener diode D602, which was tested and exonerated. So what was going on? We'll explain next month.

ANSWER TO TEST CASE 277 – page 187 last month –

The diagnostic procedure adopted to track down what appeared to be a straightforward fault in a Fidelity CTV14 was somewhat shaky. The set had no line lock, and no amount of adjustment and component replacement in and around the line oscillator circuit had any effect on the display.

Careful study of the circuit diagram at the outset would have revealed that the line oscillator in the TDA1180 i.c. is not used to drive the line output transistor directly, and here lay the key to the solution to the fault. The line drive output from the TDA1180 is used to synchronise the oscillator in the TDA2581 chopper control i.c., the line output transistor being driven by a secondary winding on the chopper transformer. If for some reason the TDA2581 chopper control chip doesn't lock to the sync from the line oscillator the scan frequency depends on the timing components R816 and C818 connected to pin 13 of this i.c. Though the problem could have been caused by failure of one of the line drive/sync coupling components R616/C811, the cause of the trouble actually lay within the TDA2581 itself. This was the item that had to be ordered, the replacement providing a complete cure.

To think that every time we wound the line hold control to and fro everything was happening correctly within the TDA1180 – a scope or counter connected to pin 3 (line drive output) of this i.c. would have revealed all!

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £13, overseas (surface mail) £15 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

AN1270	£1.75	CX143A	£7.50	HA11788	£4.50	M54543L	£2.75	TA7136P	£1.00	UPC1028H	£0.90	2S4899	£0.70	ZSC1427	£0.30	VIDEO BELT KITS		LATE EXTRA	
AN203	£2.20	CX157	£3.95	HA11816NT	£0.50	M54548L	£8.75	TA7137P	£0.80	UPC1031H	£1.80	2S4940	£0.60	ZSC1505	£0.30	AKAI VS-2EG/SEG (5)	£1.50	AN5033	£5.25
AN210	£1.75	CX158	£3.50	HA11828NT	£0.50	M63705	£1.60	TA7139P	£1.50	UPC1032H	£0.50	2S4952	£0.35	ZSC1546	£0.30	AKAI VS 9700EG (6)	£1.75	AN5620X	£6.25
AN211A	£2.25	CX160	£2.50	HA12035	£0.50	M63712	£1.50	TA7145P	£1.80	UPC1035C	£0.20	2S49105	£0.30	ZSC1664	£0.30	FISHER VBS 7000 (6)	£2.50	AN6387	£5.63
AN214Q	£1.80	CX161A	£2.50	HA12413	£2.50	M63730	£1.75	TA7146P	£2.50	UPC1037H	£0.20	2S49102	£1.90	ZSC1682	£0.30	FISHER VBS 9000 (3)	£1.00	HA11440A	£3.75
AN217B	£2.20	CX162	£3.40	HA13402	£3.50	M63731	£2.50	TA7150P	£1.80	UPC1043C	£1.00	2S49103	£1.40	ZSC1741	£0.30	HITACHI VT5000 (7)	£1.70	HA12001W	£6.50
AN228W	£2.75	CX170	£3.50	HA13403	£1.50	M63756	£2.80	TA7152P	£1.70	UPC1049C	£1.00	2S49104	£1.90	ZSC1815	£0.25	JVC HR3300/3600 (9)	£2.00	HA12038	£6.75
AN232	£1.50	CX180	£1.50	HA13430A	£0.80	M88719	£3.50	TA7176P	£1.50	UPC1158H	£0.60	2S49105	£0.25	ZSC1826	£0.30	JVC HR3360/3660 (7)	£2.00	LA1140	£1.75
AN239Q	£3.80	HA1124A	£2.75	LA1111P	£0.80	PLLO1A	£2.30	TA7193P	£3.50	UPC1161C	£0.30	2S49106	£0.25	ZSC1849	£0.30	PANASONIC NV333 (5)	£1.40	LA3370	£2.80
AN240P	£1.50	HA1125	£1.50	LA1201	£0.85	PLLO3A	£4.95	TA7200	£2.00	UPC1167C	£0.70	2S49108	£0.35	ZSC1892	£0.30	PANASONIC NV2000 (5)	£1.40	LA4126	£2.50
AN241P	£1.50	HA1137	£1.75	LA1222	£0.80	SK1125H	£7.50	TA7201	£2.00	UPC1168C	£0.90	2S49109	£0.40	ZSC1957	£0.30	PANASONIC NV7000 (5)	£1.25	LA4507	£4.85
AN247P	£2.50	HA1149	£1.40	LA1230	£1.50	SK1125H	£7.50	TA7202P	£2.00	UPC1170A	£1.00	2S49110	£0.40	ZSC1969	£0.30	PANASONIC NV8600 (7)	£1.75	LA7016	£2.50
AN259	£2.75	HA1151	£1.50	LA1240	£1.75	SK1125H	£7.50	TA7203P	£2.00	UPC1171C	£1.00	2S49111	£0.40	ZSC2021	£0.30	SANYO VTC5500 (3)	£1.00	LA7215	£2.75
AN262	£1.50	HA1156	£1.10	LA1241	£1.50	SK1125H	£7.50	TA7204P	£1.10	UPC1172C	£1.00	2S49112	£0.40	ZSC2026	£0.30	SHARP VC3300 (4)	£2.25	LA7521	£4.50
AN271A	£2.50	HA1166	£1.60	LA1241	£1.50	SK1125H	£7.50	TA7205P	£1.10	UPC1177C	£1.00	2S49113	£0.40	ZSC2078	£0.75	SHARP VC3300 (5)	£1.75	LA7751	£4.75
AN274	£2.50	HA1196	£3.75	LA1365	£2.20	SK1015	£5.00	TA7206P	£1.00	UPC1183H	£1.20	2S49114	£0.70	ZSC2091	£0.60	SHARP VC3300 (7/00)	£1.30	LA7755	£2.95
AN295	£3.25	HA1197	£1.50	LA1460	£1.95	SK1016	£4.75	TA7207P	£1.50	UPC1185H	£1.20	2S49115	£0.60	ZSC2092	£0.95	SHARP VC3300 (5)	£1.50	LA7801	£2.95
AN303	£3.50	HA1199	£1.40	LA2200	£1.50	SK1020	£4.20	TA7208P	£1.50	UPC1186	£0.80	2S49116	£0.80	ZSC2098	£0.95	SHARP VC3300	£1.30	LA7808	£2.50
AN313U	£2.75	HA1366W	£1.60	LA3101	£1.75	SK1022	£5.25	TA7209P	£2.00	UPC1187C	£1.40	2S49117	£0.60	ZSC2166	£0.95	SONY SLT7ME/T7 (6)	£1.60	LA7910	£1.95
AN315	£1.50	HA1367	£1.10	LA3101	£1.75	SK1022	£5.25	TA7210P	£2.00	UPC1188C	£1.40	2S49118	£0.60	ZSC2166	£0.95	SONY SLCT/J7 (6)	£1.70	LC4066B	£2.50
AN318	£4.75	HA1339A	£1.60	LA3160	£0.90	SK1025	£6.75	TA7214P	£2.50	UPC1189H	£1.20	2S49119	£0.60	ZSC2228	£0.85	SONY SL800/8080 (6)	£2.00	M51102L	£4.95
AN331	£2.75	HA1342A	£1.70	LA3201	£0.95	SK1077	£5.95	TA7217A	£1.20	UPC1190C	£1.00	2S49120	£0.60	ZSC2278	£0.70	TOSHIBA V547 (5)	£1.70	TA7140P	£1.75
AN360	£1.20	HA1366W	£1.50	LA3300	£1.40	SK1078	£5.50	TA7220P	£1.75	UPC1191V	£0.95	2S49121	£0.50	ZSC2335	£1.25	TOSHIBA V7540 (5)	£1.75	UPC1387C	£2.50
AN362L	£1.30	HA1366WR	£1.50	LA3301	£1.20	SK1080	£7.20	TA7222A	£1.90	UPC1192C	£1.00	2S49122	£0.50	ZSC2365	£1.50	UPC1391H	£2.50		
AN366P	£1.50	HA1367	£1.50	LA3350	£1.20	SK1082	£7.75	TA7223P	£1.90	UPC1211H	£1.90	2S49123	£0.90	ZSC2540	£1.90	UPC1397C	£2.50		
AN610P	£1.75	HA1368	£1.60	LA4030P	£2.00	SK1430	£4.75	TA7225P	£2.50	UPC1215V	£1.60	2S49124	£0.80	ZSC2570	£2.00	UPC1400C	£2.50		
AN612	£1.75	HA1368R	£1.65	LA4031P	£1.50	SK1433	£4.50	TA7226P	£2.50	UPC1216V	£1.60	2S49125	£0.80	ZSC2579	£2.20	UPC1401C	£2.50		
AN5722	£1.50	HA1370	£2.75	LA4032P	£1.50	SK1435	£6.00	TA7227P	£3.00	UPC1217G	£1.60	2S49126	£0.80	ZSC2580	£2.20	UPC1402C	£2.50		
AN5730	£1.85	HA1374	£2.50	LA4051P	£1.50	SK1436	£5.80	TA7229P	£3.50	UPC1218H	£1.30	2S49127	£0.80	ZSC2580	£2.20	UPC1403C	£2.50		
AN5732	£1.85	HA1377A	£2.20	LA4100	£1.80	SK1437	£6.30	TA7230P	£3.50	UPC1219H	£1.30	2S49128	£0.80	ZSC2580	£2.20	UPC1404C	£2.50		
AN5753	£1.95	HA1388	£2.40	LA4101	£1.80	SK1438	£6.30	TA7231P	£3.50	UPC1220C	£1.30	2S49129	£0.80	ZSC2580	£2.20	UPC1405C	£2.50		
AN590	£1.80	HA1389	£1.70	LA4102	£1.80	SK1441	£6.80	TA7232P	£3.50	UPC1222C	£1.30	2S49130	£0.80	ZSC2580	£2.20	UPC1406C	£2.50		
AN6344	£4.75	HA1389R	£1.40	LA4110	£1.40	SK1443	£6.95	TA72312P	£3.50	UPC1223C	£1.75	2S49131	£0.80	ZSC2580	£2.20	UPC1407C	£2.50		
AN7105	£2.20	HA1392	£2.30	LA4112	£1.30	SK1457	£5.50	TA7313AP	£1.30	UPC1225C	£1.75	2S49132	£0.80	ZSC2580	£2.20	UPC1408C	£2.50		
AN7110	£1.40	HA1394	£2.75	LA4120	£2.50	SK1459	£5.75	TA7315AP	£1.75	UPC1226C	£1.75	2S49133	£0.80	ZSC2580	£2.20	UPC1409C	£2.50		
AN7114E	£1.80	HA1397	£2.50	LA4125	£2.00	SK1461	£7.50	TA7325P	£1.50	UPC1228C	£1.75	2S49134	£0.80	ZSC2580	£2.20	UPC1410C	£2.50		
AN7115E	£1.80	HA1398	£2.40	LA4140	£0.70	SK1461	£7.50	TA7328P	£1.50	UPC1229C	£1.75	2S49135	£0.80	ZSC2580	£2.20	UPC1411C	£2.50		
AN7120	£1.40	HA1457W	£0.90	LA4182	£2.00	SK1463	£7.40	TA7607AP	£2.75	UPC1229C	£1.75	2S49136	£0.80	ZSC2580	£2.20	UPC1412C	£2.50		
AN7130	£1.50	HA11215A	£4.25	LA4192	£1.95	SK1465	£8.50	TA7609P	£3.50	UPC1230H	£1.80	2S49137	£0.80	ZSC2580	£2.20	UPC1413C	£2.50		
AN7145M	£1.80	HA11221	£3.30	LA4200	£1.50	SK10025	£4.95	TA7609P	£3.50	UPC1238V	£1.00	2S49138	£0.80	ZSC2580	£2.20	UPC1414C	£2.50		
AN7146M	£1.85	HA11223W	£2.80	LA4220	£1.20	SK10029	£4.35	TA7611	£2.75	UPC1245V	£1.00	2S49139	£0.80	ZSC2580	£2.20	UPC1415C	£2.50		
AN7154	£1.75	HA11225	£1.95	LA4230	£1.75	SK10039	£4.25	TA7658P	£1.50	UPC1277H	£2.75	2S49140	£0.80	ZSC2580	£2.20	UPC1416C	£2.50		
AN7156N	£2.40	HA11235	£2.00	LA4250	£2.50	SK10040	£4.50	UHC001	£4.80	UPC1278H	£2.50	2S49141	£0.80	ZSC2580	£2.20	UPC1417C	£2.50		
AN7159N	£3.25	HA11423	£4.50	LA4400	£1.90	SK10049	£5.75	UHC004	£4.80	UPC1350C	£1.20	2S49142	£0.80	ZSC2580	£2.20	UPC1418C	£2.50		
AN7168	£2.50	HA11701	£4.50	LA4420	£1.40	SK10059	£5.00	UPC16C	£1.30	UPC1353C	£1.30	2S49143	£0.80	ZSC2580	£2.20	UPC1419C	£2.50		
AN7310	£0.80	HA11702	£4.90	LA4422	£1.20	SK10080	£5.50	UPC20C	£2.20	UPC1356C	£1.20	2S49144	£0.80	ZSC2580	£2.20	UPC1420C	£2.50		
AN7311	£1.00	HA11703	£4.50	LA4430	£1.80	SK10208	£6.50	UPC30C	£1.80	UPC1358H	£1.80	2S49145	£0.80	ZSC2580	£2.20	UPC1421C	£2.50		
BA301	£0.75	HA11704	£4.75	LA4440	£2.20	SK12029	£3.75	UPC41C	£2.00	UPC1360C	£1.60	2S49146	£0.80	ZSC2580	£2.20	UPC1422C	£2.50		
BA311	£0.95	HA11705	£5.50	LA4460	£1.75	SK12240	£6.00	UPC54C	£1.25	UPC1363C	£1.60	2S49147	£0.80	ZSC2580	£2.20	UPC1423C	£2.50		
BA313	£0.75	HA11706	£1.25	LA4461	£1.75	SK12242	£6.75	UPC55C	£2.00	UPC1365C	£1.60	2S49148	£0.80	ZSC2580	£2.20	UPC1424C	£2.50		
BA318	£1.30	HA11710	£5.50	LA4500	£2.50	SK13040	£6.50	UPC561C	£2.00	UPC1366C	£1.60	2S49149	£0.80	ZSC2580	£2.20	UPC1425C	£2.50		
BA402	£0.75	HA11711	£3.50	LA6458	£0.90	SK15211	£6.75	UPC566H	£0.60	UPC1367C	£1.60	2S49150	£0.80	ZSC2580	£2.20	UPC1426C	£2.50		
BA511A	£1.80	HA11713	£3.50	LA7800	£1.95	SK15411	£6.50	UPC571	£1.95	UPC1368H	£1.60	2S49151	£0.80	ZSC2580	£2.20	UPC1427C	£2.50		
BA514	£1.75	HA11714	£3.75	LA7806	£2.50	SK15451	£6.75	UPC573C	£2.20	UPC1370C	£1.60	2S49152	£0.80	ZSC2580	£2.20	UPC1428C	£2.50		
BA521	£1.75	HA11715	£3.25	LC7120	£3.50	SK15720	£6.80	UPC574J	£0.35	UPC1373H	£1.60	2S49153	£0.80	ZSC2580	£2.20	UPC1429C	£2.50		
BA527	£2.50	HA11727	£3.50	LC7130	£3.50	SK15750	£6.75	UPC575C	£1.00	UPC1378H	£1.60	2S49154	£0.80	ZSC2580	£2.20	UPC1430C	£2.50		
BA532	£1.50	HA11717	£6.25	LC7131	£3.75	TA7050P	£0.80	UPC576H	£1.75	UPC1382C	£1.75	2S49155	£0.80	ZSC2580	£2.20	UPC1431C	£2.50		
BA536	£2.25	HA11718	£4.75	LC7136	£3.75	TA7051P	£0.80	UPC577H	£0.70	UPC1384C	£1.70	2S49156	£0.80	ZSC2580	£2.20	UPC1432C	£2.50		
BA612	£1.80	HA11724	£18.25	LC7137	£2.75	TA7054	£1.70	UPC580	£2.75	UPC1458C	£0.90	2S49157	£0.80	ZSC2580	£2.20	UPC1433C	£2.50		
BA1310	£1.75	HA11725	£16.00	M5106P	£2.25	TA7063	£0.80	UPC585C	£0.85	UPD777	£4.50	2S49158	£0.80	ZSC2580	£2.20	UPC1434C	£2.50		
BA1320	£1.25	HA11726	£15.00	M5115P	£3.50	TA7066	£1.50												

Come along and explore the fascinating world of wood from beautiful hand carved figures to cabinet making.

See craftsmen demonstrating techniques such as hand carving, marquetry, woodturning – get a few tips on improving your own skills!

You'll find the widest possible choice of the very latest power tools, woodworking machinery and sophisticated lathes to traditional hand tools.

Or perhaps you're interested in old woodworking tools or antiques. Experts from **Christies** will be on-hand to provide a **FREE VALUATION SERVICE**. Bring along your old woodworking tools or photographs of antique furniture.

Or maybe you'll want to buy something from the craft market. Choose from a simple wooden toy to a ready to assemble kit – there's something for everyone.

For safety reasons both pushchairs and dogs (except guide dogs) cannot be admitted into the exhibition.

The 5th Annual PRACTICAL WOOD WORKING EXHIBITION

WEMBLEY CONFERENCE CENTRE
JANUARY 30-FEBRUARY 2 1986

Thursday to Saturday 10am-7pm

Sunday 10am-6pm

Tickets are available
at the door.

Adults £3

Children

under 16

and Senior

Citizens

£2.

LOOK OUT FOR THE 50p REDUCTION VOUCHER
IN THE JANUARY AND FEBRUARY ISSUES OF
**PRACTICAL
WOODWORKING**

CELTEL

NOW OPEN AT

M25 JUNCTION 30

EX RENTAL TVs AND VIDEOS.
TELETEXT PORTABLES,
B GRADE AUDIO ETC.
PANELS, REMOTES AND
FRIENDLY SERVICE.
ONLY 2 MINUTES FROM
DARTFORD TUNNEL.

THORN TELETEXT HANDSETS

£12 + VAT

9600 LINE PANEL **£8+**.

JVC VIDEO BELT SET **£4+**

2 BREACH ROAD

WEST THURROCK

PURFLEET 0708
861404

CREWE WHOLESALE TV

77 COLERIDGE WAY, CREWE

TEL: (0270) 582924

SPECIAL OPENING OFFER

G11s working **£47** in lots of 5
Decca 80s and 100s working **£33** lots of 5
Philips G8s working **£22** lots of 5
GEC 2111 working **£25** lots of 5
GEC Starline and 8 channel
working **£30** lots of 5
Thorn 9000 working **£30** lots of 5

MANY OTHER MAKES IN STOCK
ALL WORKING

★ ★ ★

VHS VIDEOS TO ORDER P.O.A.

★ ★ ★

PANELS AVAILABLE

★ ★ ★

REMOTE CONTROL SETS AVAILABLE

Delivery available on lots of 10 or more

AA117	9p	BC337	6p	BF184	20p	BFY57	25p	TIP32A	24p	2N1131	28p	BY296	20p	7818	35p	PCL805	55p	LA-4461	180p	TBA560	100p	74LS22	17p
AA119	9p	BC338	6p	BF185	20p	BFY58	25p	TIP32B	24p	2N1132	28p	BY298	20p	7824	35p	PCL806	55p	LA-5112	120p	TBA600	100p	74LS24	38p
AA132	9p	BC357	6p	BF194	5p	BFY59	45p	TIP33	60p	2N1613	24p	BY299	28p	7905	35p	PCL807	85p	LM301	26p	TBA800	35p	74LS26	17p
AC107	28p	BCV32	150p	BF195	5p	BFY48	85p	TIP34	60p	2N1711	24p	BY476	90p	7812	40p	PCL808	85p	LM311	35p	TBA105	90p	74LS27	17p
AC126	17p	BCV33	150p	BF196	6p	BFY49	85p	TIP41A	22p	2N2102	22p	BY477	90p	7813	40p	PCL809	85p	LM312	35p	TBA200	100p	74LS28	17p
AC127	17p	BCV34	150p	BF197	7p	BR101	43p	TIP42A	22p	2N218A	24p	BYX55-650	30p	7918	40p	PCL810	85p	LM313	35p	TBA250	100p	74LS30	17p
AC128	17p	BCV42	20p	BF198	7p	BR103	43p	TIP42C	25p	2N2219	24p	BYX55-800	32p	78L05	28p	PCL811	85p	LM314	35p	TBA300	100p	74LS31	17p
AC129	17p	BCV46	20p	BF199	8p	BSK20	15p	TIP48	40p	2N2221	23p	BYX70-500	32p	78L12	28p	PCL812	85p	LM315	35p	TBA350	100p	74LS32	17p
AC128K	23p	BCV56	16p	BF200	16p	BSK26	18p	TIP50	60p	2N2369	15p	BYX70-800	36p	78L15	28p	PCL813	85p	LM316	35p	TBA400	100p	74LS33	17p
AC141K	30p	BCV71	16p	BF240	10p	BT106	90p	TIP51	120p	2N2484	20p	BYX71-600	30p	78L18	28p	PCL814	85p	LM317	35p	TBA450	100p	74LS34	17p
AC142K	30p	BCV72	16p	BF241	10p	BT109	90p	TIP52	120p	2N2646	40p	OA47	6p	78L24	28p	PCL815	85p	LM318	35p	TBA500	100p	74LS35	17p
AC153K	30p	BD115	26p	BF255	12p	BT119	80p	TIP53	120p	2N2647	40p	OA47	6p	78L28	28p	PCL816	85p	LM319	35p	TBA550	100p	74LS36	17p
AC176	15p	BD124P	50p	BF256	12p	BT119	80p	TIP54	120p	2N2648	40p	OA47	6p	78L31	28p	PCL817	85p	LM320	35p	TBA600	100p	74LS37	17p
AC176K	20p	BD124	110p	BF257	18p	BT120	100p	TIP105	65p	2N2906	18p	OA200	7p	78L32	28p	PCL818	85p	LM321	35p	TBA650	100p	74LS38	17p
AC187	15p	BD128	35p	BF258	18p	BT120	100p	TIP106	65p	2N2907	18p	OA202	7p	78L35	28p	PCL819	85p	LM322	35p	TBA700	100p	74LS39	17p
AC187K	20p	BD131	25p	BF259	18p	BT120	100p	TIP107	65p	2N2908	18p	OA204	7p	78L38	28p	PCL820	85p	LM323	35p	TBA750	100p	74LS40	17p
AC188	17p	BD132	25p	BF260	18p	BT120	100p	TIP108	65p	2N2909	18p	OA206	7p	78L41	28p	PCL821	85p	LM324	35p	TBA800	100p	74LS41	17p
AC188K	23p	BD133	25p	BF261	18p	BT120	100p	TIP109	65p	2N2910	18p	OA208	7p	78L44	28p	PCL822	85p	LM325	35p	TBA850	100p	74LS42	17p
ACY18	48p	BD135	20p	BF262	25p	BT120	100p	TIP110	65p	2N2911	18p	OA210	7p	78L47	28p	PCL823	85p	LM326	35p	TBA900	100p	74LS43	17p
ACV19	48p	BD136	20p	BF263	25p	BT120	100p	TIP111	65p	2N2912	18p	OA212	7p	78L50	28p	PCL824	85p	LM327	35p	TBA950	100p	74LS44	17p
AD125	45p	BD137	20p	BF264	25p	BT120	100p	TIP112	65p	2N2913	18p	OA214	7p	78L53	28p	PCL825	85p	LM328	35p	TBA1000	100p	74LS45	17p
AD145	45p	BD138	20p	BF265	25p	BT120	100p	TIP113	65p	2N2914	18p	OA216	7p	78L56	28p	PCL826	85p	LM329	35p	TBA1050	100p	74LS46	17p
AD161	45p	BD139	20p	BF266	25p	BT120	100p	TIP114	65p	2N2915	18p	OA218	7p	78L59	28p	PCL827	85p	LM330	35p	TBA1100	100p	74LS47	17p
AD162	22p	BD140	20p	BF267	25p	BT120	100p	TIP115	65p	2N2916	18p	OA220	7p	78L62	28p	PCL828	85p	LM331	35p	TBA1150	100p	74LS48	17p
AF124	25p	BD144	90p	BF337	20p	BU204	78p	TIP120	40p	2N3442	58p	IN4007	5p	78L65	28p	PCL829	85p	LM332	35p	TBA1200	100p	74LS49	17p
AF125	25p	BD150	30p	BF338	20p	BU205	78p	TIP121	40p	2N3443	58p	IN4008	5p	78L68	28p	PCL830	85p	LM333	35p	TBA1250	100p	74LS50	17p
AF126	25p	BD151	30p	BF339	20p	BU206	78p	TIP122	40p	2N3444	58p	IN4009	5p	78L71	28p	PCL831	85p	LM334	35p	TBA1300	100p	74LS51	17p
AF127	25p	BD152	30p	BF340	20p	BU207	78p	TIP123	40p	2N3445	58p	IN4010	5p	78L74	28p	PCL832	85p	LM335	35p	TBA1350	100p	74LS52	17p
AF128	25p	BD153	30p	BF341	20p	BU208	78p	TIP124	40p	2N3446	58p	IN4011	5p	78L77	28p	PCL833	85p	LM336	35p	TBA1400	100p	74LS53	17p
AF129	25p	BD154	30p	BF342	20p	BU209	78p	TIP125	40p	2N3447	58p	IN4012	5p	78L80	28p	PCL834	85p	LM337	35p	TBA1450	100p	74LS54	17p
AF130	25p	BD155	30p	BF343	20p	BU210	78p	TIP126	40p	2N3448	58p	IN4013	5p	78L83	28p	PCL835	85p	LM338	35p	TBA1500	100p	74LS55	17p
AF131	25p	BD156	30p	BF344	20p	BU211	78p	TIP127	40p	2N3449	58p	IN4014	5p	78L86	28p	PCL836	85p	LM339	35p	TBA1550	100p	74LS56	17p
AF132	25p	BD157	30p	BF345	20p	BU212	78p	TIP128	40p	2N3450	58p	IN4015	5p	78L89	28p	PCL837	85p	LM340	35p	TBA1600	100p	74LS57	17p
AL112	70p	BD175	30p	BF371	13p	BU220	100p	TIP141	65p	2N3705	9p	IN5403	11p	78L92	28p	PCL838	85p	LM341	35p	TBA1650	100p	74LS58	17p
AL113	80p	BD179	32p	BF420	18p	BU246	85p	TIP142	65p	2N3706	9p	IN5404	11p	78L95	28p	PCL839	85p	LM342	35p	TBA1700	100p	74LS59	17p
AS215	100p	BD181	45p	BF421	18p	BU247	85p	TIP143	65p	2N3707	9p	IN5405	12p	78L98	28p	PCL840	85p	LM343	35p	TBA1750	100p	74LS60	17p
AS216	100p	BD182	45p	BF422	21p	BU248	85p	TIP144	65p	2N3708	9p	IN5406	13p	78L101	28p	PCL841	85p	LM344	35p	TBA1800	100p	74LS61	17p
AU110	110p	BD183	30p	BF440	16p	BU249	85p	TIP145	65p	2N3709	9p	IN5407	13p	78L104	28p	PCL842	85p	LM345	35p	TBA1850	100p	74LS62	17p
AY102	180p	BD187	30p	BF440	16p	BU250	85p	TIP146	65p	2N3710	9p	IN5408	13p	78L107	28p	PCL843	85p	LM346	35p	TBA1900	100p	74LS63	17p
AY106	180p	BD201	33p	BF451	17p	BU251	85p	TIP147	65p	2N3711	9p	IN5409	13p	78L110	28p	PCL844	85p	LM347	35p	TBA1950	100p	74LS64	17p
BA145	10p	BD202	38p	BF455	14p	BU252	85p	TIP148	65p	2N3712	9p	IN5410	13p	78L113	28p	PCL845	85p	LM348	35p	TBA2000	100p	74LS65	17p
BA148	10p	BD203	42p	BF459	19p	BU253	85p	TIP149	65p	2N3713	9p	IN5411	13p	78L116	28p	PCL846	85p	LM349	35p	TBA2050	100p	74LS66	17p
BA154	6p	BD204	42p	BF459	19p	BU254	85p	TIP150	65p	2N3714	9p	IN5412	13p	78L119	28p	PCL847	85p	LM350	35p	TBA2100	100p	74LS67	17p
BA157	12p	BD222	31p	BF461	60p	BU255	85p	TIP151	65p	2N3715	9p	IN5413	13p	78L122	28p	PCL848	85p	LM351	35p	TBA2150	100p	74LS68	17p
BB101	13p	BD225	31p	BF462	62p	BU256	85p	TIP152	65p	2N3716	9p	IN5414	13p	78L125	28p	PCL849	85p	LM352	35p	TBA2200	100p	74LS69	17p
BB103	16p	BD232	31p	BF463	62p	BU257	85p	TIP153	65p	2N3717	9p	IN5415	13p	78L128	28p	PCL850	85p	LM353	35p	TBA2250	100p	74LS70	17p
BB105B	16p	BD234	31p	BF470	28p	BU258	85p	TIP154	65p	2N3718	9p	IN5416	13p	78L131	28p	PCL851	85p	LM354	35p	TBA2300	100p	74LS71	17p
BB205B	24p	BD235	28p	BF471	28p	BU259	85p	TIP155	65p	2N3719	9p	IN5417	13p	78L134	28p	PCL852	85p	LM355	35p	TBA2350	100p	74LS72	17p
BC107	7p	BD236	30p	BF479	30p	BU260	85p	TIP156	65p	2N3720	9p	IN5418	13p	78L137	28p	PCL853	85p	LM356	35p	TBA2400	100p	74LS73	17p
BC108	7p	BD237	21p	BF493	18p	BU261	85p	TIP157	65p	2N3721	9p	IN5419	13p	78L140	28p	PCL854	85p	LM357	35p	TBA2450	100p	74LS74	17p
BC109	7p	BD238	24p	BF494	18p	BU262	85p	TIP158	65p	2N3722	9p	IN5420	13p	78L143	28p	PCL855	85p	LM358	35p	TBA2500	100p	74LS75	17p
BC115	10p	BD244	50p	BF596	16p	BU263	85p	TIP159	65p	2N3723	9p	IN5421	13p	78L146	28p	PCL856	85p	LM359	35p	TBA2550	100p	74LS76	17p
BC118	11p	BD245	50p	BF596	16p	BU264	85p	TIP160	65p	2N3724	9p	IN5422	13p	78L149	28p	PCL857	85p	LM360	35p	TBA2600	100p	74LS77	17p
BC140	19p	BD433	28p	BF597	16p	BU265	85p	TIP161	65p	2N3725	9p	IN5423	13p	78L152	28p	PCL858	85p	LM361	35p	TBA2650	100p	74LS78	17p
BC141	19p	BD434	30p	BF597	16p	BU266	85p	TIP162	65p	2N3726	9p	IN5424	13p	78L155	28p	PCL859	85p	LM362	35p	TBA2700	100p	74LS79	17p
BC142	19p	BD435	31p	BF598	21p	BU267	85p	TIP163	65p	2N3727	9p	IN5425	13p	78L158	28p	PCL860	85p	LM363	35p	TBA2750	100p	74LS80	17p
BC143	19p	BD437	28p	BF669	22p	BU268	85p	TIP164	65p	2N3728	9p	IN5426	13p	78L									

HITACHI VHS COLOUR CAMERAS

Mains Only Tested/
Working

VHS VIDEOS

FERGUSON

3V00, 3V22, 3V23, 3V16, 3V29,
3V30, 3V31, 3V32, 3V35

NATIONAL PANASONIC
NV8600, 8610, 2000, 7000,
370, 333, 2010

SHARP

620, 630, 640, 2300 H T/P

BETAMAX

SANYO VTC 9300, 5000, 5300

SONY C5, C6, C7, C9
and SL F1UB T/P

Also Bush, Toshiba, Hitachi and Blau Punkt

PLUS

17" 18" 20" 22" 26" Hybrid/
Solid State CTVs

Remote Control & Teletext

Discount for Quantities

Complete loads delivered from pick up point

**JOHN CARTER
(Electrical) LTD
FURNACE ROAD,
GALLOW'S INN,
ILKESTON**

Phone: 0602 303124

D.I.Y. TV TUBE POLISHING

with our DIY Polishing Kit

The Kit includes everything you need to polish approx. 25* tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

Kit Price £49 inc P&P and VAT. Available from Luton only.
*Depends on depth and area to be polished.

TV TUBES FREE DELIVERY*

5% DISCOUNT ON TUBES COLLECTED FROM LUTON
Quality, High Temperature Reprocessing

TUBE SIZE	DELTA i.e. A51-110X A56-120X A66-120X A67-120X	DELTA SPECIALS i.e. A47-342X 470CTB22 510GLB22 A56-410X A66-410X A67-150X A67-200X	IN LINE & PIL i.e. 470ESB22 470ERB22 A51-161X A51-570X 510JKB22 560AKB22 560BYB22 A56-510X A66-510X	HITACHI IN LINE etc. AXT37-001 AXT51-001 AXT56-001 510VLB22 510VSB22 560DZB22 560EGB22 A56-540X A56-711X A66-540X A67-711X	SONY TRINITRON 330AB22 400EFB22 470BE22 470DLB22 520KB22 520SB22 570EB22 570HB22 680DB22
UP TO 20"	£30	£32	£40	£44	£58
UP TO 22"	£34	£36	£42	£46	£64
UP TO 26"	£36	£38	£44	£48	£70

All tubes sold with 1 or 2 year guarantee, with optional extension by extra 2 years. Prices shown are for 12 months guarantee.

All tubes exchange glass required.

Your good, working tubes with scratches or small chips, can be POLISHED with our purpose built polishing equipment. From £7 per tube.

Delivery charge on colour tubes: Within 40 miles of Luton.

1 or 2 tubes £6. 3 or more tubes FREE DELIVERY*

Nationwide delivery available, charges on application.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

WELL VIEW

114-134 Midland Rd,
Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-1pm. Tel. 0582-410787.

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

H. K. Television, London, E.2. Tel. 01-729 1133.

West One Distributors Ltd., Gt. Missenden, Buckinghamshire.

Tel. 024 06 3609

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933 314901

Daventry Rentals, Daventry, Northants. Tel. 03272 77436

Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562

WANTED A56/A66-510X/540X and Sony. Old glass for cash

WINTER SPECIALS

10 BUSH 2 CHIP	£50
10 GEC SOLID STATE	£150
10 GEC STARLINES	£250
10 REDIFFUSION MARK 1	
REVAMP	£120
10 THORN 8000 17"	£150

ALSO BUSH T20, G11, 9000, 9600, 9800,
GEC STARLINES

PL509 £1.50, PY500 £1
ELC 1043 Tuners Ex-panel £2.50
RING FOR QUOTE

ALL + VAT

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154

THE NO. 1 WHOLESALE IN THE SOUTH

TRADE ANNOUNCEMENT

CHROMA VISION (Manchester) NOW OPEN!!!


95 LANGWORTHY RD, SALFORD M6 5PH. Tel. No. 061-736-6333
 811 WASHWOOD HEATH RD, WARD END, BIRMINGHAM 8. Tel. No. 021-784-2561

Large range of late model TV's and Videos at low, low prices
THORN AND PHILIPS TELE-TEXT, REMOTES AND BASICS

★ PHILIPS ★		★ THORN ★		★ PYE ★		★ ITT ★		★ GEC ★	
Working		Wo-king		Working		Working		In line (Starline)	
G11 660	£45	9600	£38	G11	£55	CVC 30	£38	G.E.C. 2201	£25
G8 550 22"	£20	9000	£28	222 22"	£20	CVC 20/3	£35	And Many More,	
G8 520 22"	£15	8800	£20	725 20"	£25	CVC 20	£30	i.e. Bush T20	
G8 560 20"	£30			Chelsea 18"	£25			Decca 100	
Tested G11 Tubes		Tested Thorn 9000 Tubes		Tested 22" 26" Delta Tubes		Buy in one's or 100's		Japs, Tandburg etc.	
	£20		£15		£7				
Untested		Untested		Untested		Untested		<i>Too many to list!</i>	
G11 660	£35			G11	£45			<i>Why not come along and have a look</i>	
G8 550	£12	9600	£30	222 22"	£15	CVC 30	£30		
G8 520	£8	9000	£20	725 20"	£20	CVC 20/3	£25		
G8 560	£20	8800	£15	Chelsea 18"	£20	CVC 20	£25		

★ **WORKING & SERVICED!!! VHS VIDEOS 100's IN STOCK** ★
1000's MORE UNTESTED SETS OFF THE PILE
 ★ Lorry loads direct from source ★ Delivery arranged ★

All prices subject to V.A.T.

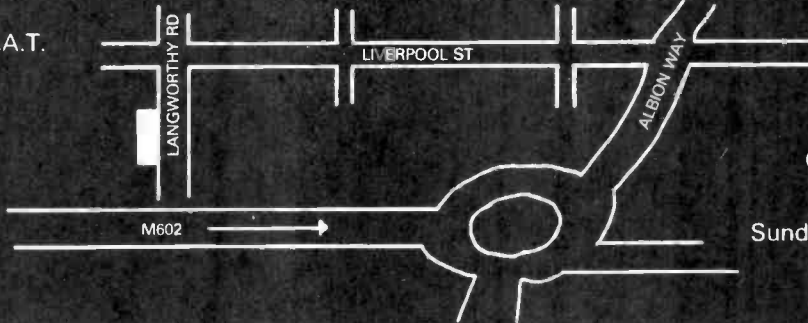

WE ARE HERE
 Only 2 minutes from end of motorway

Open 6 days a week
 9.30 a.m. - 6.30 p.m.

Sundays by appointment

Newnes Technical Books


DOMESTIC VIDEOCASSETTE RECORDERS
 a servicing guide

SECOND EDITION including fault patterns

This invaluable guide for service engineers, technicians and students has been thoroughly updated and enlarged. Along with in-depth discussion of the principles and practice of domestic machines, there is a great deal of new material on long-play machines, Hi-Fi systems and digital techniques. 160 Pages. Illustrated. 0 408 015 73X

£15.95

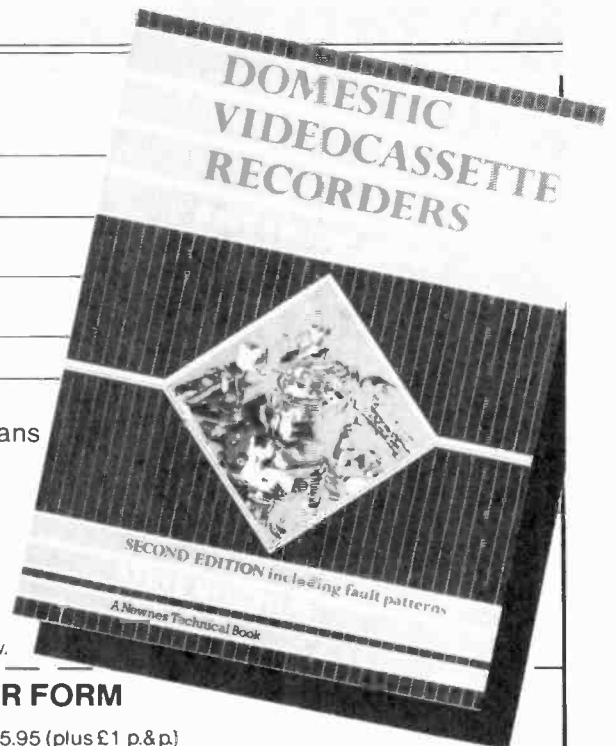Available from bookshops, but in case of difficulty fill in the order form below.



DOMESTIC VIDEOCASSETTE RECORDERS ORDER FORM

Please send me _____ copy(ies) of Domestic Video Cassette Recorders at £15.95 (plus £1 p.&p.)

I enclose a cheque/Postal Order made payable to Newnes Books for £ _____

(CAPITAL LETTERS PLEASE)

NAME _____ ADDRESS _____

Please send orders to Dept. GB, PO Box 31, Newton Abbot, Devon, TQ12 5XH.

UK offer only. Please allow 28 days for delivery. If I am not completely satisfied I may return the book/s within 14 days of delivery and you will refund my money.

UNTESTED EX-RENTAL CTVs OVER 1500 WEEKLY

WITH THIS QUANTITY WE DO NOT
HAVE TIME TO PLAY ABOUT.

NO BUMPED TUBES

BEST SOURCE IN U.K.

COLOUR TVs FROM £3

**VIDEO RECORDERS
FROM £60**

TANDBURG S/S CTVs
DUAL TUNERS IDEAL FOR
EXPORT

VIDEO RECORDERS FROM £50:
SONY C5: C6: C7 & C9
PANASONIC : SHARP
FERGUSON : GRUNDIG ETC.

CALL & SEE OUR SELECTION
DELIVERY ARRANGED FOR
BULK PURCHASES
LOAD DIRECT FROM SOURCE
AT VERY KEEN PRICES


**22"/26" TELETEXT VIEWDATA
COLOUR IN STOCK NOW**

CASH ONLY

FRANK FORD
(TV TRADE DISPOSALS)
SCHOOL LANE
GUIDE
BLACKBURN, LANCS
TEL: 0254 64489

REBUILT TUBES?

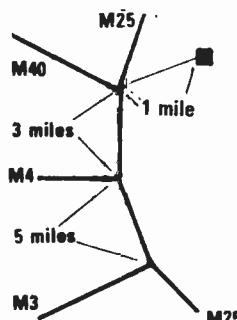Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.



**WE ARE LOCATED IN
UXBRIDGE**

At probably the most accessible part of S.E. England. The nearest junction of the M25 is only about 1 mile away and we are less than 10 minutes from the interchanges on the M25/M3, M25/M4, M25/M40. The Poyle/Colnbrook section of the M25 was completed in September with the exception of the M25/M4 interchange which will be completed soon.

**LOCAL AREA MAP AND PRICE LIST
AVAILABLE ON REQUEST**

DISPLAY ELECTRONICS LTD.
UNIT 4, SWAN WHARF,
WATERLOO ROAD,
UXBRIDGE, MIDDLESEX.
UXBRIDGE (0895) 55800.

CentreVision

TEL: 0222-44754

SLOPER ROAD

LECKWITH

CARDIFF CF1 8AB

OPPOSITE CITY FOOTBALL GROUND

5 MINS FROM M4

FERGUSON

VHS VIDEO

£75

MANY TOP QUALITY REMOTE
CONTROL WORKING TV's.

PHONE FOR LATEST PRICES

PRICES SUBJECT TO VAT

OPENING HOURS:

MONDAY - FRIDAY 9.00 - 5.30

SATURDAY 9.00 - 1.00

TOOLS OF THE TRADE

A comprehensive range of more than 30 hand-tools and pumps for electronic/manufacturing industry.

Trade Price*
from £4.50 to £5.50



• **SHEARS • SNIPPERS**



CUSHION GRIP

Spare desoldering tips available




• **ANTISTATIC CONDUCTIVE DESOLDERING PUMPS** Trade Price* from £3.60 to £6.50




• **TRIMMING KIT** Set of Five Trade Price* from £2.20 to £2.75

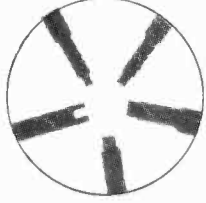• **MINI PLIERS** Long, short, smooth and knurled jaws Trade Price* from £4.70 to £5.75



• **WIRE STRIPPER • SNIPPER**
Cuts cable 10mm max
COPPER BRAID

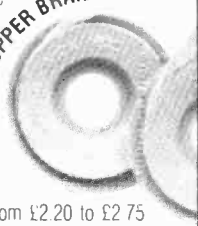• **DESOLDERING**
available in 5 sizes
Trade Price* from 75p to £1.00



For further details contact 01-631 0985

*Depending on model. Excluding VAT. Distributor/Industrial enquiries welcomed.

PHILEX

TELEVISION/COMPUTER FULL-TIME TRAINING

(FULL TIME COURSES APPROVED BY THE BUSINESS & TECHNICIAN EDUCATION COUNCIL)

2 YEAR
BTEC National Diploma (OND)
ELECTRONIC & COMMUNICATIONS ENGINEERING

(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

15 MONTHS
BTEC National Certificate (ONC)
ELECTRONIC EQUIPMENT SERVICING

(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

15 MONTHS
BTEC National Certificate (ONC)
COMPUTING TECHNOLOGY

(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

9 MONTHS
BTEC Higher National Certificate (HNC)
COMPUTING TECHNOLOGY & ROBOTICS

(Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

THESE COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

SHORTENED COURSES OF FROM 3 TO 6 MONTHS CAN BE ARRANGED FOR APPLICANTS WITH PREVIOUS ELECTRONICS KNOWLEDGE

NEXT SESSION TO COMMENCE
ON APRIL 21st

H.N.C. SEPTEMBER 1986
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE (Dept TN)
20 PENYVERN ROAD, EARLS COURT,
LONDON SW5 9SU. Tel: 01-373 8721.

OSCILLOSCOPES

TELEQUIPMENT D67 Dual Trace 50 MHz Delay Sweep with manual £250
COSSOR CDU150. Dual Trace 35MHz Solid State. Portable 8x10cm display. With Manual £200
S. E. LABS SM111. Dual Trace 16MHz Solid State. Portable AC or External DC operation 8x10cm display. With Manual £150
TELEQUIPMENT D43. Dual Trace 15MHz. With Manual £100
TELEQUIPMENT S54A. Single Trace 10MHz Solid State. With Manual £110

PHILIPS DIGITAL MULTIMETERS

4 digit, auto ranging. Complete with batteries and leads (p&p £5)
TYPE PM2517X (LCD) £75

MULTIMETERS

AVO 8 Mk 3. Complete with batteries & leads. ONLY £60
AVO 8 Mk 4. Complete with batteries & leads £65
AVO Model 7x. Complete with batteries, leads & carrying case £40
AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads £18
BELEMIC Multimeters. Un-used. Supplied with leads & batteries
EBM 20 - 37 ranges £10
SUPER 50 - 57 ranges (incl. Carrying Case) £20
Other models available.

MARCOMI ELECTRONIC VOLTMETER TF2604 20Hz-1500MHz; AC DC Ohms AC300mV-300V. FSD £95
MARCOMI VALVE VOLTMETER TF2600 10Hz-10MHz; 1mV-300V FSD £40

PROFESSIONAL 9" GREEN SCREEN MONITORS made by KGM for RELUTERS Gives quality 80 column x 24 line display. Composite video in Cased. Good condition ONLY £40 each

DISK DRIVE PSU.240V 1N; 5V 1.6A & 12V 1.5A out. Size: W125mm, H75mm, D180mm. Cased. Un-used. Only £15.00
Various 5 1/4" Floppy Disk Drives and Stepping Motors Available.

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £12. VAT to be added to Total of Goods & Carriage.

NEW EQUIPMENT

HAMEG OSCILLOSCOPE 605. Dual Trace 60MHz. Delay Sweep. Component Tester £515
HAMEG OSCILLOSCOPE 203.5. Dual Trace 20MHz. Component Tester £270
BLACK STAR FREQUENCY COUNTERS P&P £94
Meteor 100 - 100MHz £126
Meteor 600 - 600MHz £175
Meteor 1000 - 1GHz £175
BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 £110

HUNG CHANG DMM 6010. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. P&P £4 £33.50
MULTIMETER type U4324. 33 ranges. Complete with batteries and leads. P&P £4 £16

OSCILLOSCOPES PROBES. Switched <1; x10. P&P £2 £11

RACAL 32MHz Universal Counter Timer Type 836 £50

ADVANCE AM FM Signal Generator type S663. 7.5 - 230MHz £75

ADVANCE AM Signal Generator type 62. 150KHz - 220MHz £35

METRIX WOBBLATOR type 210. 5 - 220MHz £20

LABGEAR COLOUR BAR GENERATOR CM6037 £60 P&P £2

LABGEAR CROSSHATCH GENERATOR CM6004 £15 P&P £2

LABGEAR CROSSHATCH GENERATOR CM6038 Input 240V AC or 6V DC £25 P&P £2

WAYNE KERR COMPONENT BRIDGE B521 (CT375) L 100uH - 500KHz; C 1pF - 5F; R 1 milliohm - 1000Mohm £35

AVO TRANSISTOR TESTER TT169 Handled. GO/NO GO for In-situ Testing. Complete with batteries, leads & instructions. (p&p £3) NOW ONLY £12

PLEASE NOTE - From January 1st 1986, we will be closed Saturdays. Opening times: Monday to Friday 9am-5.30pm with LATE NIGHT THURSDAY until 8pm.

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Telephone: 0734 68041



MANTEL

No 1 for Quality TVs & Videos 100s of V.H.S. Videos in stock

Large Quantities of Late Model Thorn TVs. All with first class cabinets.

TELE-TEXT/ULTRASONIC/INFRARED/REMOTES

All at UNBEATABLE PRICES for QUANTITY & QUALITY

Also Philips G11/Pye G11/Basic/Remote/TELE-TEXT

Some examples of **QUALITY** working TVs

THORN 8800 *****£25
 THORN 8800 (remote) *****£30
 THORN 9000 *****£30
 THORN 9000 (remote) *****£35
 THORN 9600 *****£40
 THORN 9600 (full feature remote) *****£45

THORN 9600 TELETEXT ***** from £75
 (VARIOUS MODELS)
 THORN 9900 *****£50
 THORN 9900 f/f remote *****£60
 PHILIPS G11 *****£55

(prices quoted are based on quantity)

NO DEALER TOO LARGE OR SMALL. SINGLES SOLD

Brand New Remote Control Hand Sets Available for the majority of British & European TV sets.

1000s of UNTESTED Colour TVs

I.E. DECCA 30s, GEC 2110, GRUNDIG, TANBERGS, G8s 520s-550s, Thorn 3500/8000/8500, TT, PYE, ETC.

(Many of these untested TVs just switch on)

ALL AT LOW LOW PRICES

VAN LOADS DELIVERED DIRECT FROM SOURCE RING FOR QUOTE

New TV Trolley Stands **£4.95** Also Video Stands **POA**
 Colour TV panels & tubes available

All prices subject to V.A.T.

CALLERS WELCOME

Export Orders Welcome for those Countries using the P.A.L. System

**419 BARLOW MOOR ROAD,
 CHORLTON, MANCHESTER M21 2ER.**

TEL: 061-861 8501

V.H.S. VIDEOS

PIANO KEY & ELECTRONIC

SONY BETAMAX VIDEOS WORKERS

£68.50 EACH + V.A.T.

COLOUR T.V.s

WORKERS OR NON-WORKERS

DECCA FERGUSON

G.E.C. DORIC

PHILIPS ETC.

PANELS AND VALVES ALSO AVAILABLE

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road
 Brent Park Industrial Estate
 Southall, Middlesex UB2 5LL
 01-574 4631 Ext. 28

VIDEO SPARE BARGAINS

Prices All Inclusive

3V00/22/16	Capstan Belt	2.50
Head	Drum Belt	36.95
Capstan Motor	Switch S1	36.95
Drum Motor	Switch S2	33.95
Aud/Control Head	Micro Switch	36.50
Takeup idler (old)	Sony C5/7 Head	5.75
Takeup idler (new)	Sony Rew. Kit	5.95
Pinch Roller	Sony Capst. Motor	5.50
		37.25

Comprehensive stock of I.C.'s, Transistors, Coils, Motors, Switches, Levers, Belts, etc. for all J.V.C., Ferguson, and Sony videos available ex stock.

Export enquiries welcome. Payment C.W.O. Min. order £7.

EURO IMPEX

31 Hyde Crescent, London NW9 7EY.

TUNERS + TUNERS

- ★ If you repair sets regularly – phone us today and we will dispatch immediately – no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TELEPART 32 Temple Street,
 Wolverhampton WV2 4LJ.
 Phone: (0902) 773122.

PHILIPS 550s	£10
PYE CHELSEA SERIES	£15
THORN 9000s	£20
DECCA 80/100s	£25
ITT S/STATE	£25
PHILIPS G11s	£25
VHS VIDEOS 3V16/22 etc off the pile	ea £75

BETA

Various makes and models.

No Minimum Quantities

Quantity Rates Available

All Prices Exclusive VAT

**Free Delivery London Area,
other areas negotiable**

SOUTH LONDON TELEVISION

Mission Hall,
Southey Road, London SW19
Tel: 01-543 5437

NOR GROVE TELEVISION TRADE SERVICES

Water Street, Snowhill
Birmingham

Tel: 021-236-9616

**SUPPLIERS OF THE CHEAPEST
T.V.'s & VIDEOS TO THE TRADE**

PHILIPS G11	From £30
THORN 9000	From £20
THORN 9600	From £20
THORN 9200	From £20
THORN 9900	From £30
PHILIPS KT3	P.O.A.
THORN TX9/TX10	P.O.A.

Many other makes in stock.

Prices available on request.

Spares available.

Quantity discounts on request.

HOCKLEY DISCOUNT TELEVISIONS

We give "The Best Deals"
that's why we have the
cleanest reputation in the
trade!!!

Prices start	Working sets
From £6.00	From £12.00

OR

Lorry loads delivered
from SOURCE

We have huge stocks of
TV's + V.H.S. Videos
to offer, including:-

Philips G8's, G11's	Thorn 8000, TX9,
Pye Solid State	9000, 9600, TX10,
Pye Chelsea	Latest Hitachi
G.E.C. Solid State	I.T.T. CVC30, CVC45,
Rediffusion Mkl, MkIII	Bush T20, T22

ALSO

VIDEO + T.V. STANDS AVAILABLE!

**DON'T HESITATE TO CONTACT US
BECAUSE YOU WILL NEVER LOOSE!!**

MIDLANDS BRANCH:-

Hockley Discount Televisions,
94 Soho Hill, Hockley, Birmingham B19 1AE.
021-551-2233 - Ask for Jazz



NORTH-EAST BRANCH:-

Northern TV Distributors, Unit 2, Pert Court,
11th Ave, Team Valley,
Gateshead, Tyne & Wear.
091-487-5389 - Ask for Joe



The World of . .
P+P 1 PANEL £1.50
2 PANELS OR MORE
£3.00

"TELEPANELS"



52 Mount Pleasant Road, Chigwell, Essex, 1G7 5ER. Tel: 01-729 0506.

	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	5.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731			10.00		18.00	10.00	7.00	8.00		4.50
BUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BUSH T/20	7.50	6.50	14.00		19.00	19.00	5.00	14.00		
DECCA BRADFORD	3.00		7.00			4.00		4.00		
DECCA 80	12.00	POA	14.00		12.00	10.00		14.00		POA

POST OFF YOUR CHEQUE NOW! AND YOUR PANELS SENT BY RETURN OF POST!!!

IRISH T.V. DEALERS

(PLEASE NOTICE)

LARGE SELECTION OF RECONDITIONED PRECISION-IN-LINE UHF-VHF COLOUR TVs, SOME WITH RE-GUN TUBES FITTED, "CABINETS RESTORED TO A1 CONDITION". PRICES START @ £60.00 VAT INCLUDED. ALSO 20" & 22" RE-GUN TUBES IN STOCK, QUANTITY DISCOUNT, DELIVERY ARRANGED. VIDEO HEADS ALSO IN STOCK.

(EXPORT SPECIALISTS)

T.V. TRADE SALES

E.D.I. HOUSE

KYLEMORE PK. WEST

DUBLIN 10.

Tel: 0001-264139 (Local calls 01-)

ALSO

T.V.T.S.

CLOVER PLACE

COLLEGE ST.

KILLARNEY.

Tel: 064-33655

VALVES
 High Quality
 Best Prices
 Large Stocks
 Rapid Delivery
Edicron
 Serving industry for over 25 years
 Tel: (1)9612020 Tlx: 265531
 1-7 Wesley Avenue, London NW10 7BZ.
 Cable: Edicron London NW10

TVS TRADE SERVICES BROMSGROVE

Large selection of quality clean TV & Video
 always in stock, including:

BUSH T20/24 DECCA 80/100

GEC STARLINE

HITACHI ITT (full remote)

PHILIPS G8

PHILIPS GII PHILIPS KT3

THORN 9600 including TELETEXT

THORN 8800 THORN 9000

(remote) (remote)

THORN TX

VHS VIDEO from £85 (working)

We specialise in working sets, fully serviced and ready to deliver to your customer's home. Spares back up service available to customers. You've seen the junk, so why not now come and pay us a visit - we think you will be pleasantly surprised by our prices and the quality of our equipment. Delivery service available.

For further details phone:

COLIN BROOMFIELD,

UNIT 7, STATION STREET,
 BROMSGROVE, WORCS.

(0527) 37037



SETS & COMPONENTS

THORN, GEC, DECCA's stripped for spares. Panels, Tuners from £2.50. Phone for prices: WELLINGTONS, Dartford 0322 337212.

PHILIPS G11 AND BUSH T20 regular supplies. For prices phone 01-845-2036.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

HITACHI, MITSUBISHI, Panasonic, Sony, Toshiba, JVC, Sharp, fully refurbished. PEARSON TELEVISION, 0484 863489. Delivery arranged.

OCHRE MILL TECHNICAL. Grundig sets, panels, manuals. TELEQUIPMENT oscilloscopes, manuals, spares. LABGEAR pattern generators. 0785-814643.

T.V PANELS

REPAIR EXCHANGE SALES SERVICE
PRICES FOR REP. EXC. AS FOLLOWS

Chassis	IF	Decoder	Line Scan	Power Supply	Frame
Philips G11	18	16	20	18	16
Bush T20	X	12	16	15	12
Bush T26	X	16	18	15	X
Bush 718	X	12	18	X	12

All panels are repaired and aligned according to rank std.

Ring for prices to buy panels. Prices shown inclusive of postage, etc.

All panels guaranteed for 3 months.

T. K. PANELS SERVICE

31 Bronte Paths, Stevenage (0438) 61567

PRECISION VISION LIMITED THE COMPANY THAT CARES

Offers for sale

- ★ Ex hotel rental colour TVs
- ★ Graded colour TVs and Audio
- ★ VHS Video Recorders

Please phone for current stock position

Unit 10, Chiltern Business Centre,
198 Garsington Road (Opposite BL works), Cowley, Oxford.

Phone: (0865) 711966.

STARLITE ELECTRONICS

WILLOWS FARM,
A13 RAINHAM, ESSEX.
Rainham 23225 also
Hornchurch 50238.

EX RENTAL TVs
UNTESTED FROM £15.00
WORKING TVs £20.00
RE-GUNNING TUBES

2 year guarantee
Most types available
including Sony



TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.78 per single column centimetre (minimum 2.5 cms). Classified advertisements 40p per word.

JANUARY SALE TIME ON

Colour TV's, Videos, Slot Meters, Stands, Legs, Panels etc.

Colour TV from £5, Videos from £25, G8's from £7, G11's from £29, Remotes from £35.

Loads of other models, makes, prices. Japanese, European, British, huge selection. (Truck loads by arrangement delivered).

AND OUR SPECIAL JANUARY DEAL

SPEND OVER £250 ON SELECTED TV IN JANUARY

AND GET A CASE OF WINE FREE

GIVE YOURSELF SOMETHING TO CELEBRATE WITH

So grab the cash £££ wagon and head in our direction

GENERAL FACTORS

UNION STREET,

DONCASTER

TELEPHONE 0777-817386

CASH ONLY, NO CHEQUES

ONLY 2 1/2 MILES FROM A1M

FOR M18 - M1

NORMAN

ENTERPRISES LTD

Weston-Super-Mare, Avon.

Tel: 413991/418545

Colour TVs fully engineered
with a special care on tubes

Hitachi 217 Remote Control £85

Thorne 9000 Remote Control £42.50

Pye G11 £47.50

Rank T20 £42.50

Pye Chelsea 6 Button £27.50

Pye 725 £37.50

Pye 721 £27.50

Thorne 9600 £45

Thorne 9200 £42.50

Bush T20 Remote Control £49.50

Bush T24 £55.50

All above prices include hand sets if available
Ready for sale.

Phone now, limited number each month. All the above off the pile, less a 3rd

WOODSDALE COMPONENTS

RANK BUSH MURPHY

TRANSFORMERS

Line Output

Z718 (T703A, T706A)

New (Complete) £19.00

Less Focus Module and Rectifier £10.50

T20, T22 (T705A) £11.00

T26 (T705B) £11.00

TDA2190 Plug-in Replacement module suitable for Bush T22/26 and any set using same device £6.00

Switch Mode

T114A £6.00

Genuine RBM Units.

Prompt Postal Service P&P Paid.

Add 15% VAT to all prices.

DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote,
Pinner, Middlesex. HA5-2QT.

Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

SERVICE PAGES

(minimum 12 words), box number 70p extra. All prices plus 15% VAT. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank PLC". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5942).

FOR THE BEST QUALITY AND BEST PRICES IN BIRMINGHAM.

TESTED AND UNTESTED
TV'S AND VIDEO'S

RING - 021-772 2733

WILTS GROVE LIMITED

(Next Door to UNCLE'S DISCOUNT STORE)

128-130 Ladypool Road,
Sparkbrook, Birmingham B12 8JA.

CASH ONLY

EAST ANGLIA SUPPLIES

For your fully serviced colour televisions ready for sale or rent at realistic prices with free delivery (just petrol charged) anywhere for sensible sized orders.

G11s from £70 + VAT
KT3s from £85 + VAT
K30s from £95 + VAT
ITTs from £50 + VAT
Decca from £50 + VAT
T20s from £50 + VAT
9000s from £35 + VAT
VHS Videos.
Ferg 3V29, 3V30
NatPan NV2000, NV2010

MANY OTHER
MAKES
REGULARLY
STOCKED AND
CHEAPIES FROM
ONLY £25 + VAT
FULLY SERVICED.

Contact John, Dave or Steve for personal friendly attention on
0223 69215 or 0353 61462

JABCO Combination Lopt Tester & full distance Infra Red Remote Control Tester
Total price inc. P.P. etc. £22 C.W.O.
Hitachi/GEC Frame module HM6251
Replacement £7.50 inc. P.P.

J. BAKER & CO.
1 Old Shoreham Road,
Southwick, Sussex BN4 4RD.
Tel: 0273 - 593315

WIZARD DISTRIBUTORS MANCHESTER TV & VIDEO SPARES

We stock spares for THORN, PHILIPS,
PYE, RANK, GEC, SHARP, SONY,
DECCA + ITT.

FIDELITY SPARES MAIN DISTRIBUTOR.

Did you know we also stock

FUSES	ICs
TUBES	TOOLS
AERIALS	VIDEO LEADS
AEROSOLS	AUDIO LEADS
RESISTORS	SEMICONDUCTORS
CAPACITORS	SERVICE MANUALS
VALVES	TEST EQUIPMENT
HANDSETS	TV/VIDEO TROLLEYS

AND MUCH MORE

Counter open Monday-Friday 9am-4.45pm

TRADE ONLY

**EMPRESS STREET WORKS,
EMPRESS STREET,
MANCHESTER M16 9EN.**
Tel: 061-872 5438; 061-848 0060.

INDEPENDENT TELEVISION AND VIDEO COMPANY

LARGE STOCKS TO CLEAR
EVERY WEEK

COMPETITIVE PRICES

EXAMPLES:

B&W 20"-24" From £1.00

COLOUR:

Bush 1-2 I.C. £4.00

Philips 520-550, 26" £6.00

Thorn 3500 £6.00

GEC-Decca-ITT £6.00

Philips 550 22" £10.00

Pye 18"-20"-22" £10.00

GEC 20"-22" 26" £12.00

Thorn 8800-9000-9800 £15.00

Many Other Modern Sets
and VHS Videos

PHILIPS G11 - ITT - Bush T20-T22-
T25, Hitachi, Nat. Pan. - Sony
Off Pile from £40

Phone Frank: Nottingham
(0602) 864627

Unit 3

Meadow Trading Estate,
Meadow Lane,
Nottingham NG2 3HQ.

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS

£4.95 inc. p&p

The UNIVERSAL TRIPLER can be used in most
G.E.C., I.T.T., Pye, Rank, Decca & Continental
sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

LOOK HEAR TV

NOW OPEN. Our new trade warehouse. For the best service and quality in the East Midlands.

- * Good quality working TV's
- * Off the pile also available
- * Low prices
- * No minimum quantity
- * Limited number of VHS videos
- * Lots of TV panels for sale

Open Mon.-Fri. 10 - 5.30, Sunday 10 - 1.00

CASH ONLY

UNIT 4, KING STREET BUILDINGS,
KING STREET, ENDERBY, LEICESTER.

Only 5 mins. from Junction 21, M1.

Ring Adrian on Leicester (0533) 867530.

MR. A. L. BALMER

N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

COLOUR TV'S AND VIDEOS H.P. REPOS AND EX. RENTALS JANUARY CLEARANCE

PYE G11 EXC CAB.....£40	BUSH 718.....£20
BUSH T20/26 CH.....£35	BUSH 2 CHIP.....£8
HITACHI 191.....£20	GRUNDIG 5010.....£10
FERGUSON TX	PYE KT3.....£50
(NOT D.E.R. Etc.).....£65	GEC 2213.....£30
GEC 2010.....£20	THORN 3000.....£7
PYE 222.....£20	GRUNDIG G415/4206
PHILIPS 550.....£15	

Best Stock in the Country — over 2000 in stock (90% of our TV's Switch on)
Special Price Quoted For Bulk Purchases From Source.

REFURBISHED TV'S



BUSH T20/T26.....£45, G11.....£50,
PYE KT3.....£70, Others done to order.

DISCOUNT FOR QUANTITY

VIDEO

SHARPS 7300, 8300, 9300, HITACHI, VT11
FERGUSON 3V29 (Not Ex D.E.R. etc.)
SANYO, SONY, BETA



100's PX HOOVER JUNIOR VACS

— All models in stock

Fully reconditioned HOOVER JUNIORS (Like new) £27

CASH ONLY

TEL. 0274 688458
UNIT 12, Wharfedale Rd
M606 Euroway Estate
Bradford

OPEN 6 DAYS
SAT 9-5.30

COLOUR TV PANELS Fully Tested & Working

	IF	CDA/ Video	Decoder	LTB	Line Board	Power
GEC 2040	3.50	3.50	4.00	5.00	—	—
DECCA 13/30	3.00	—	7.00	5.00	—	4.00
BUSH A823	4.00*	—	10.00*	5.00*	2.50	4.00
THORN 8/8j	—	—	10.00	5.00	—	5.00
PYE 205	3.00	3.50	5.00	10.00	—	—
THORN 3/3j	5.00	5.00	5.00	8.00	—	10.00
G8	6.00	—	8.00	7.00	15.00	5.00

*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.
Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

fitted with
brand new
transformer

Terms cash with order.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

GOLCAR T.V. SERVICES (formerly LAVITE LTD.),
Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273

Callers by appointment only.

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Cross-hatch, Dots, Checker Board, Black Raster, White Raster, Half Black & White, Mains Powered. **£75.90**

OUTPUTS PROVIDED

UHF OUTPUT
VIDEO OUTPUT
SOUND OUTPUT
LINE PULSE
FIELD PULSE



Same as above plus RGB output **£81.50**
Line Output Transformer Tester **£11.50**
B/W Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale UHF output **£18.50**
Same as above but with Video Output **£20.50**
Capacitance Meter measures 10pF to 1µF complete with moving coil meter **£14.75**

CRT TESTER/REJUVENATOR SEND S.A.E.

S.A.E. for details. Prices include VAT.
Postage on Colour Bars £1.75, others 75 pence.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horsey Fields,
Wolverhampton WV1 3DW.
Tel: (0902) 871563

WORKING CTVs THE BEST & CHEAPEST IN LANCASHIRE SPECIAL OFFER

Working Decca Bradford Including
Black Fronts

18" 20" 22" 26" **ONLY £20.00** each in 6
units

Working GEC Plastic & Wooden. All models
20" 22" 26" **ONLY £22.00** each in 6 units

Working Bush 20" 22" 26"
ONLY £15.00 each

Philips G8 (520) 22" & 26"
ONLY £20.00 each

Plus many more makes & sizes in stock,
inc. Tanburg, Nordmende, Thorn.
1st COME 1st SERVED

ALL SETS TESTED & WORKING

CALL

JOHN POWNEY

TRADE TV SALES & SERVICE

Unit 31 Progress Industrial Estate,
Kirkham, nr Preston
(0772) 683392

UNTESTED PANELS FOR ALL MAKES OF TV
£1.25 per panel plus post & packing

Trent Tubes

31 RADCLIFFE ROAD, WEST BRIDGFORD, NOTTINGHAM

PHONE: (0602) 813329

10 YEAR GUARANTEE NOW AVAILABLE.

APPLY FOR DETAILS
THE PROFESSIONAL REBUILDER

ALL STD DELTAS
ONE PRICE **£30.00**

SPECIAL 370 EFB 22 **£48.00**

A51-161 - A51-163 **£43.00**

A51-A56-A66/500/510 (20AX)
One price **£43.00**

A56-A66/540 (30AX) **£49.00**

560DZB22 **£46.00**

SONY TYPES FROM **£55.00**

SPECIALIST SONY SERVICE

1000's more types available. VDUs, MONDs, Industrials etc.

Suppliers to Broadcasting Authorities
& National Companies and Manufacturers

ALL PRICES EX WORKS + VAT & EXCHANGE

WE SPECIALISE IN JAPANESE TYPES

DELIVERY SERVICE AVAILABLE

QUANTITY DISCOUNTS

TECHNICAL ADVICE SERVICE AVAILABLE

IRISH T.V. DEALERS

Brand new re-gunning plant operating.

— TOP CLASS TUBES —

B/W - Delta - In-Line - P.I.L.

CHRIS KELLEHER'S T.V.

Kanturk, Co. Cork

Store open 9 to 8 pm. Sunday 10-1 pm.
029-50046.

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

BOURNEMOUTH

LARGE STOCKS OF WORKING
NON-WORKING SETS, MOST
MAKES AND SIZES.

FAIR PRICES — TRADE ONLY

WAREHOUSE OPEN:
Mon-Fri 9-1, 2-5; Sat 9-1

HILLIER'S, UNIT 2A,
11-15 FRANCIS AVENUE,
WALLISDOWN. TEL: 0202 581932

PLEASE
MENTION
TELEVISION
WHEN
REPLYING
TO
ADVERTISEMENTS

VIDEO & HI-FI ELECTRONICS

379 EDGWARE ROAD

LONDON W2

TEL. 01-258 0328

ALL VHS PARTS AVAILABLE. EXAMPLES:

VIDEO HEADS

JVC, Ferguson, Akai, Saba, Telefunken **£35.00**
Sony (Betamax) **£45.00**
National Panasonic **£45.00**
All Hitachi heads from **£42.00**

INTEGRATED CIRCUITS

UPC 1365C **£6.30**
UPD 553C **£10.20**
UPD 552C **£9.56**
HA 11711 **£10.50**

All makes of idlers, pressure rollers, clutch assembly
and motors in stock.

Many other parts available. Send SAE for list.

ALL PRICES INCLUSIVE OF VAT
ADD £2.00 FOR P&P

GEMINI TUBES

THE PRICE IS RIGHT
FOR QUALITY REBUILDS
ALL WITH 2 YEAR WARRANTY

Phone now on St. Helens 37672

Or call at Unit 3,

Delphwood Drive,

Sherdley Road Ind. Estate,

St. Helens.

TRADE TVs

Yorkshire New Outlet

Ex-Rental & Repossessed TVs

Colour From **£10**

Mono From **£2**

TRADE REPAIRS AND SPARES
WANTED VIDEOS IN QUANTITY

TELEFIX

Ellingham Street,

Wakefield Road, Bradford 4.

Phone: 0274 480281 or 733373.

C.T.V. PANEL SERVICE

Exch/repair & sales - chemically cleaned - no burned
or damaged print. 3 months g'tee, large range incl.
Decca 80 & 100, G11, G8, ITT, GEC, Rank, TCE, Jap &
euro models, despatched same day.

Send S.A.E. for lists or ring with your requirements:

Argo Services (Birmingham),
53 Lawley Street, Birmingham B4 7XH.
Tel. 021 359 3753

Telephone orders accepted using Access/Mastercard/Visa
CALLERS RING FIRST

TUBES

£29.00
£14.50

INCLUSIVE, REGUNS TWO YEAR
GUARANTEE, QUANTITY DISCOUNTS SIX
MONTH GUARANTEE SLIGHTLY USED
A56-120 A56-140 A51-110 A49-191 A47-342 or 343
A44-270-1 A66-120 A66-140 (410) A67-120
(All 26" add £5)

No need to spend £5 returning old delta tube.
Slightly used in-line tubes from £29.
Six months guarantee.

IN-LINE 1 YEAR GUARANTEE

51-575 510JKB 51-161
51-580 56-611 51-510
51-590 56-615 51-570
51-001AXT 56-001AXT 56-500

£45
inclusive

56-540 £55 TOSHIBA NEW 51-110
66-540 inclusive £29 47-342 47-343
66-500 inclusive

SONY £66 (Cash & Carry only)

HITACHI

490DKB22 £34
560DZB22 £49

DECCA 100
PROFESSIONAL STICK
DE-GAUSSING COILS
£19.50 (1 YEAR GUARANTEE)

Philips G11s

Panels from £10.00. Breaking for spares, Push button
units, Tube bases. All good working order.

RADIO and TELEVISION SERVICING BOOKS
(MacDonalds). New 74/75 £15; 75/76, 76/77, 77/78,
78/79, 79/80, 80/81, 84/85, 82/83, 83/84 £22.50.

FREE DELIVERY

Except Tubes £5 each. All prices are inclusive
U-VIEW

29, Warmsworth Road, Doncaster,
Yorkshire DN4 0RP. Tel: 0302 855017.

Callers ring first, open every day including Sunday
1/2 a mile from A1



- * Britain's most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * GEC Starline
- * Decca 80
- * Decca 88
- * Decca 100
- * Pye G11
- * Thorn 8800
- * Pye 222 Series

All working and polished.
These are not from major
companies. A lot are from
hotels and have had very
little use.
Excellent reliable sets for
rental.

Krystal Marketing Ltd,
Breedon Cross
Storage,
Dale Road, Selly Oak,
Birmingham B29 6AQ.

Phone 021-471 3023
Telex 335540-G
Ask for Les

RE-GLOW TUBES

(ESTABLISHED 1959)

INLINE TUBE

20AX SPECIALISTS 30AX
INLINE - PIL - BONDED

DELTAS FROM £28 INLINE FROM £36
(VAT EXTRA)

RE-GLOW TUBES 33-37 MILES PLACE
(OFF DELCE RD) ROCHESTER, KENT

TEL: MEDWAY 43952 (STD 0634)

TELEVISION

SCREENPLAY Your Friend in the TV Business

COLOUR SETS FROM £5.00
MONOS FROM £3.00
PANELS BY POST - PRE-CALIBRATED
WORKING SETS TO ORDER

Phone Baldock 894905
SECTION 3, UNIT 4,
SERL COMPLEX,
LONDON ROAD,
BALDOCK, HERTS.

OPEN 6 DAYS 10-6.30pm/10-5pm SAT.

TELFORD ELECTRICAL SPARES & SERVICE

GENUINE
SONY SPARES



NEW -
GENUINE
FERGUSON
SPARES

VIDEO HEADS

TESS
SERVICE

COMPUTER
SPARES

TRANS-
FORMERS

Beswick FUSES

INSTRUMENTS

E.H.T. TRAYS

UNIT 42,
HEATH HILL
INDUSTRIAL
ESTATE,
DAWLEY, TELFORD,
SHROPSHIRE
TF4 2RH.
Telephone:
Telford (0952) 501618

AERIAL
PRODUCTS

AUDIO
PRODUCTS

RESISTORS

CAPACITORS

VALVES

TUNERS
Varicap &
Push Button

TRADE
COUNTER
OPEN 6
DAYS
EACH
WEEK

SEMI-
CONDUCTORS
Integrated Circuit
& Socket

SEMI-
CONDUCTORS
Diode

TUBES
Monochrome &
Regunned Colour

SOLDERING
IRONS



SOLDER &
ACCESSORIES

S.A.E. FOR
FREE
CATALOGUE.
A4 SIZE

Try Us.

We endeavour to provide a fast delivery of top
quality components for the keenest price.

HALTON TV TRADE DISPOSAL

Wide range of TVs available.
Working and non-working.

TRADE ONLY

(We have NO retail outlet)

St Michaels Industrial Estate, Widnes
Tel. 051 423 1577

REPAIR SERVICE

BRISTOL - SOUTH WEST SOUTH WALES

Scratched and chipped CRTs
can be Re-polished.

Tel: 0454 778635 for details

PRINTED PANEL REPAIR SERVICE

Printed panels and remote control handsets
repaired. Most makes and models serviced.

RING 0934 418545
for Price List or Quotation.

SITS VACANT

VIDEO ENGINEERS

We are looking for an experienced
Video Engineer. 5 day week. Bench
work. Pleasant working environment,
salary negotiable.

CELTEL

2, Breach Road, West Thurrock
Tel: 0708 861404

EXPERIENCED, ENERGETIC Television engineer
with real ambition wanted. wonderful working area.
excellent prospects. Flat available. Tel. 0969 50227
evenings.

VIDEO

V.H.S. VIDEO'S 100's IN STOCK

Famous brands:

JVC · PANASONIC · FERGUSON

Also stockists of Grade B Units, Micro-
waves, Hi-Fi, Radio/Cassettes etc. etc.

CONTACT MICK ON:

021-772 1591

WANTED

WANTED TELEVISION MAGAZINES, ANY YEAR
Phone anytime Richardson 0332-367215.

SERVICE PAGES

FOR SALE



Sabaco

For a
great deal!

VAN LOAD DIRECT FROM SOURCES

ALL SETS OFF THE PILE

Large selection of
Ferguson TX
9600/9200/9000/
8800/4000
mainly teletext with
remote control at best
prices in UK

VHS VIDEOS

Good working
order

3V22 £95


Non-working

3V23/3V29

£100

All prices

subject to VAT
and availability

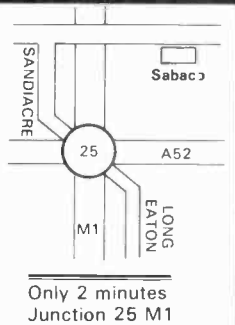

ANNOUNCEMENT TO SCOTTISH TRADERS
TOP QUALITY OF VHS VIDEO'S & TV'S

Large selection of VHS Video's
and TV's in quantities of
2's or 100's at very
competitive prices.

OPEN 6 DAYS A WEEK

9.30 am to 5.45 pm

For further details telephone:



Sabaco

75 Robertson Street, Glasgow.

Glasgow. 041-221 2146.

(2 minutes from M8).

Sabaco

46A Derby Road,

Sandiacre,

Nottingham. (0602) 397555.

2 SETS OF FULLY RECONDITIONED tube re-
running plants for sale. Training provided. From only
£3,995. Tel. 0582-410787.

DEVONICS

Quality Rebuilt Tubes
2 YEAR WARRANTY

470 ERB22	£43
510 KCB22	£45
A51-161/500/510/ 570/580/590X	£45
560 AKB/DZB/TB22	£45
A56-500/510X	£45
A56-540X	£53
A66-500/510X	£46
A66-540X	£53
670 XB22	£46

Deltas from £30

Plus carriage and VAT

2A BARTON HILL ROAD,
TORQUAY TQ2 8JH

0803 - 33035

BUSINESS OPPORTUNITES

SOUTH WEST CORNISH VILLAGE TV ELECTRICAL BUSINESS

With 25-30 Rentals, established 9 years. Large modernised
DETACHED 3 bedroomed house with adjoining shop,
double garage, workshops etc. No crime and low rates with a
good income available to you from day one. £48,500 FREE-
HOLD including van, fixtures & fittings etc.

SAE (Serious enquiries only) to:
BOX NO. 203

SUPERB WELL ESTABLISHED Television Electrical
Contracting Audio business for sale Yorkshire Dales
Market Town. Excellent profits, wonderful working
area. Box No 204.

T.V. VIDEO SALES REPAIRS & RENTAL SHOP

In pleasant Shropshire country market town. Small
growing business making good profits run at present
by engineer & wife, on a fairly leisurely 5 day week
basis. Excellent 3 bedroomed accommodation
attached, with gas c.h., walled garden.

Freehold £45,000 o.n.o. & S.A.V.
BOX NO. 205 for details

AERIALS

EVERYTHING NECESSARY for multi-outlet and
high gain installations. Cables, outlets, splitters,
channelpass filters, diplexers, masthead amplifiers,
distribution amplifiers, brackets, masts, aerials, etc.
Use trade gear and save pounds. Catalogue 75p
(refundable). Professional advice. **WRIGHTS
AERIALS**, 43 Greaves Sike Lane, Micklebring,
Rotherham.



SATELLITE T.V. RECEPTION EQUIPMENT

10.9-11.7 GHz low noise block downconverters
2-way and 4-way power dividers/2m dia GRP
dishes and polar mounts/Brass scalar feedhorns
and feed supports/indoor demodulators and in-
set demodulators.

SAE for details to:

KESH ELECTRICS LTD

MAIN ST, KESH, CO FERMANAGH, N. IRELAND
PHONE KESH (03656) 31449

AERIAL BOOSTERS

B45-UHF TV next to the set fitting. Gain 10dbs
(trebles gain), works off PP3 type battery or 8V to 14V
working. Price complete (excluding battery) £5.00.


Video Transmitter. This will transmit good qual-
ity pictures and sound more than 30ft. Price £8.90
(S.A.E. for more details).

We also make aerial boosters for VHF/FM radio £7.70,
and VHF television, prices £7.70 & £8.70. p&p 50p per
order.

ELECTRONIC MAILORDER,
62 Bridge Street, Ramsbottom,
Lancashire, BL0 9AGT.

Tel: Ramsbottom (070 682) 3036.

S.A.E. leaflets. Access/Visa Welcome.

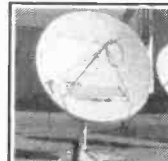

Euro-Sat

Parabolic Dish Antennas

(Parent company est. in

TV communications since 1969)

SATELLITE TVRO ANTENNAS

TOP QUALITY SOLID

GLASSFIBRE DISH ANTENNAS

TRADE PRICES

1M. DIA 11-12.4 GHZ BANDS £77.00

1.2M. DIA 11-12.4 GHZ BANDS £83.00

2M. DIA 11-12.4 GHZ BANDS £215.10

3M. DIA 11-12.4 GHZ BANDS £437.00

Trade & Export Enquiries Welcome

Prices do not include delivery

Euro-Sat

107 Cross Street, Sale, Cheshire, England.

Tel. 061-437 2631 061-881 4249

TENDERS

Mid Glamorgan COUNTY COUNCIL

REVIEW OF SELECTED LISTS OF CONTRACTORS

THE MID GLAMORGAN COUNTY COUNCIL is un-
dertaking a review of its Selected Lists of Con-
tractors over the whole range of Civil Engineering,
Building and Associated Activities.

Those interested in applying for inclusion on any of
the following lists may do so by applying for and
completing the application forms obtainable from
THE COUNTY CLERK and CO-ORDINATOR, MID
GLAMORGAN COUNTY HALL, CATHAYS PARK,
CARDIFF CF1 3NE quoting the reference PPS/MM.
The final date for applying for the forms is 31
January 1986. Completed forms must be returned to
the above address by 28 February 1986.

40 T.V. Off Air Systems

D.H. THOMAS

County Clerk and Co-ordinator,

Mid Glamorgan County Hall,

Cathays Park, Cardiff CF1 3NE.

SERVICE SHEETS

TECHNICAL INFO SERVICE – 76 Church St – Larkhall – Lanarkshire ML9 1HE

World's sole publisher of Comprehensive T.V. Repair Manuals. Largest known stocks of Service Manuals & Sheets from 1935 to latest for all kinds of equipment, espec. T.V. & Video.

Save time & expense – our big catalogues of Service Manuals & Sheets with Chassis Guide & £4 Vouchers – only £3 – updated free.
Any published Service Sheet £2.50 & I.s.a.e. except CTV/Music Centres – £3.50 & I.s.a.e.
Service Manuals from £4.50 to £39 – e.g. Thorn 8000/8004/8500/8600 only £9.50.

T.V. Repair Manuals £8.50 each. Special offers The 5 McCourt £40. The 11 Tunbridge £88.
Video Repair Manuals £4.50 per Chassis or all 10 for £25.

Comprehensive Practical T.V. Repair Manual £9.50. The Practical Radio Servicing & Repair Manual £9.50.

UNIQUE COLLECTIONS OF CIRCUITS & LAYOUTS

British CTV from hybrid to modern in 3 giant binders for only £55. Also 2 giant binders packed full for £35 pair.
Foreign CTV. Portable/Standard Mono TV. Domestic Equipment.

NEW RELEASE:- Offered to 'TELEVISION' readers for £20 (full price £25).

Giant collection of modern portable British CTV circuits and layouts.

The Integrated British CTV Repair System – 4 giant binders full of circuits & layouts with 6 big Repair Manuals. Covers 1968 to the '80s. Plus! £140.

The Integrated TV Repair System – 16 big Repair Manuals/8 giant binders plus service data and other manuals. Covers 1968-1985. Priced separately over £300. Our Offer for £250 cwo or supplied in 12 monthly sections at £25 month. Offer includes any new TV publications we publish during 1 year from placing order. Service manuals to cover our range would cost over £1,000.

The Integrated Video Repair System – 10 booklets and 4 giant binders cover the early videos, all formats to V2000, 3V30, Sanyo 9300. Only £55.

S.A.E. brings any quotes required plus free magazine, service sheet & other offers.

Phone 0698 884585 before 5 pm; 0698 883334 after 4 pm.

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European and Japanese models in stock.

Colour £3.00 Mono £2.00

Manual prices on request.

All our prices include post and packing costs.

Send stamped envelope for free catalogue and any enquiries.

SANDHURST TV SERVICES (MAIL ORDER)

57 High Street, Sandhurst, Camberley, Surrey GU17 8HB.

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

METERS

METERS. Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) LTD. (0202) 683498.

GERMAN SERVICE SHEET SPECIALISTS

We furnish any kind of German service sheet and manuals. Also thousands of different sheets and manuals available. For any enquiries:

DONBERG-ELECTRONICS
Schoolmasters House, Ranafast,
Co. Donegal, Republic of Ireland
Phone: Annagry 175

AVON METERS

We buy and sell and repair TV coinmeter. Reasonable prices, one year guarantee.

213 Cheltenham Road,
Redland, Bristol.
0272-425281

MISCELLANEOUS

GET SHARP PARTS FAST

TELEPHONE

0734 - 876444

TELEX 848953

SHARP

Main U.K. Spare Parts Distributor

Audio-TV-Video ★ Microwave ★ Photo-copier ★ Typewriter

All U.K. model spares available. Same day despatch of orders received before 1pm.

Microwave, photocopier and typewriter spares to authorised service dealers/centres only.

WILLOW VALE ELECTRONICS LTD.,

11 Arkwright Road, Reading, Berks.

TELEVISION PROJECTOR Converts TV in to 7ft screen professional assistant £25.00. Details to: NIYAAZ MOHAMMED, 10 Farm Road, Rylands 7764, South Africa.

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

SOLE SUPPLIERS TV/VIDEO Repair manuals/circuits, 1000s s/manuals supplied by return. S/sheets £2.50 except CTV/m.centres/stereos £3.50. LSAE with every order/query please brings free price list/magazine inc s/sheet – or phone 0698 884585 (883334 outside business hours) TIST, 76 Church Street, Larkhall, Lanarkshire.

GRUNDIG VIDEO Infra-red remote control VIF-K1 brand new & boxed £5.95, complete with tele-pilot TPV355 £12.95, p&p £2, these units plug strait into Grundig 2x4 super (Trade Supplied) Philips video films, ex-rental £2.99. Videos & films wanted. STAN WILLETTS, 37, High Street, West Bromwich, West Midlands. Tel. 021-553 0186.

The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes

Part 1.

The Colour Signal

Part 2.

The Receiver Decoder

Part 3.

Receiver Installation



VHS★★★V2000★★★

BETAMAX★★★UMATIC



For full details telephone

0253 725499 (Day)

0253 712769 (Night)

Or send for precis details

FLINTDOWN CHANNEL 5

339 CLIFTON DRIVE SOUTH,

LYTHAM ST ANNES FY8 1LP

(enclosing this advert)

NAME

ADDRESS

TEL:.....

SPARES/MANUALS

BURROWS SERVICE

SAE QUOTES AND CREDIT DETAILS

415a WHITEHORSE ROAD,
THORNTON HEATH, SURREY
CR4 8SD. 01-683 1911 (2 lines)

C.R.T. REBUILDING PLANT AND EQUIPMENT

Installation, commissioning, training and technical after sales assistance.

C.R.T. INTERNATIONAL

136 Badmington Road,

Coalpit Heath,

Bristol BS17 2SZ

Tel: 0454 778635

BOOKS AND PUBLICATIONS

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years usually in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

MACDONALDS R&TV BOOKS. New 74/75 £15. 75/76, 76/77, 77/78, 78/79, 79/80, 80/81, 82/83, 83/84, 84/85 £22.50. Free delivery. U-VIEW, 29 Warmsworth Road, Doncaster. 0302 855017.

A-Z LIST of manufacturer addresses. All major TV, audio etc plus many hard to get ones. Send cheques/PO for £3.75 to DOWNS ELECT. 135 Main Street, Newton Grange, Midlothian EH22 2PF.

SATELLITE RECEIVING SYSTEMS

1m and 2m Parabolic Dishes, other sizes available.

A range of other components available, eg, LNAs, Downconverters, receivers, for both 4 and 11 GHz. Complete Terminals for ECS and Intelsat, both single channel and tunable versions.

Terminals for other frequencies available.

Demonstration by appointment.

L & S Bear Electronics Ltd
Yeo Lane, Colley Lane,
Bridgwater, Somerset.

Telephone: Bridgwater (0278) 421719

T.V.'s FOR EXPORT

PHILIPS G8 and G9, DECCA, BUSH and FERGUSON

All sets with VHF/UHF Tuners and suitable for countries using the PAL system. We also supply the home market.

TELE SPARES LTD.

Unit 113, Elm Road,
Western Industrial Estate,
Dublin 12, Ireland.

Telephone: Dublin 521211/521756.

APOLLO MANCHESTER

FAST MAIL ORDER GB 3-4 DAYS ALL AREAS PLEASE PHONE FOR COST
FREE LOCAL DELIVERY SAME DAY ● FITTING SERVICE £20

2 YR GUARANTEE - QUANTITY DISCOUNTS - PILL GLASS BOUGHT

A47 342/343X - 470 BCB22/CTB22/BGB22/DHB22	£39
470-ESB22/EFB22/ERB22/FTB22	£49
A51-220X/192X	£39
A51-161X/162/163/168	£49
510-JKB22/JEB22/JDB22/JGB22/ALB22/GLB22	£49
510-VLB22(E53) DTB22/001/RFB22/RCB22/SFB22	£49
A51-590 New	£55
A51-570X/580/001/210/241	£49
A56-120X/123/140/410	£39
560-DZB22(E53)/HB22/AKB22/TB22/AWB22	£49
560-ETB22/DTB22/CSB22/DMB22/DNB22	£49
A56-611X/615X	£49
A66-120X/A67-120X/140/150/200/410	£39
20AX - A56-500X/510X - A66-500X/510X	£49
30AX - A56-540X - A66-540X	£53

If your tube type is not in stock we can arrange collection - rebuilding + redeliver

PLEASE PHONE BEFORE CALLING

061-799 0854. 24 hour answering service

43 Clarke Crescent, Little Hulton, Worsley, Nr Manchester M28 6XL

JUST OPENED

FOR

South Yorkshire/Derbyshire Dealers

Come and see our range of
Colour TVs from £6

BARGAINS GALORE

South Yorks Trade Supply, Anderson House, Cally-
white Lane, Dronfield, Sheffield, S18 6XR.

PHONE 0246 411325

Chesterfield

EMCO - EUROSonic - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●

IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf", e.g. LOPTZ - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST — RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

32 TEMPLE STREET,
WOLVERHAMPTON (0902) 773122

N.G.T. COLOUR TUBES

First Independent Rebuilder with
B.S.I. CERTIFICATION

DELTA - IN-LINE - PIL - BONDED YOKE
including

AXT Series, DZB series 20AX - 30AX
A56 610/67 610 series, A51 570/580/590X
A51 161X, Sony types etc.

- ★ Rebanded with new adhesives
- ★ Excellent high voltage clean-up
- ★ Accurate alignment of Gun and Yoke for optimum convergence

N.G.T. ELECTRONICS LTD.,
120 SELHURST ROAD, LONDON SE25
Phone: 01-771 3535.

25 years experience in television tube rebuilding.

LONDON'S LARGEST
TELEVISION WHOLESALE...
with over 4½ thousand sq. feet

"TELEMANN"

8-10 RHODA STREET (off Bethnal Green Road)
LONDON E2. FREE CAR PARK

SPECIAL OFFER!!

- Parcel of 25 Monos £1.00 each
- Parcel of 10 Philips 22" G8550 £15.00 each
- Parcel of 10 Decca Bradfords £8.00 each
- Parcel of 10 Japs Colour £20.00 each

LORRY LOADS DELIVERED DIRECT FROM SUPPLIERS
NO CHARGE FOR DELIVERY IN THE LONDON AREA!

01-739 2707 → 2 LINES ← 01-739 3123

FREE CAR PARK + NO YELLOW LINES OUTSIDE!

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Thorn Spares		KT3 Decoder £8
New 9000 Decoder £8.50	K30 Sound OP £4	
9000 Frame panel £8		
9000 Cyllops panel £1.50		
8000/8500 timebase panel £8	Hitachi 2A1500V metal case wire end FARST/REC 10p	
8800 convergence panel £6		
8500 convergence panel £6	Fidelity Tube Base with transistor & focus pot £1.50	
4000 Power supply £3	Bush Tube Base on panel £1.00	
1600 Mains lead, switch		
3500 6 push button + cable form £1.50		
7605 1NPN 1066 80V/6A 10p		
9000 Sound output panel £1		
3500 Focus unit £1.50		
3500 Mains Trans £4		
3500 cut outs 10 for £4		
3500 IF panel £3		
3500 Frame panel £3		
3500 Line panel £3		
3500 A1 Diode 20p		
Export 3500 IF panel £1		
IC board with set of SN74LS £4		
4000 Tube base £4		
3500 A1 pots 50p		
Beam limiter panel £1.50		
3500 Power panel with Y969 £1		
3 Way regulated adaptor 240V 6V/7.59V/300mA £3.50		
Rank/Toshiba preh unit £9.50		
0354 £1		
2 Banks of 3 PB unit. Pyc 731 £1.00		
4 Push button unit preh £1.00		
6 Push button VHF/UHF for v/cap. GEC-Decca type £7.00		
7 Push button for CVC5 ITT £8.00		
KT3 12 Push button unit £2.00		
KT3 (Export) 12 P.B.U £1.00		
6 Push button Unit Thorn £1.00		
6 Push button Unit hits GEC & Decca etc. £6.00		
Hearing aid unit £1		
Rank Z718 + PB/Unit MEC11 £7		
7 Button Unit GEC with Lamps £4		
Bush T151A 6 button unit with Pos. & mains lead, 6 bush buttons. Bush £6.00		
Mains Droppers		
G8 2R2+48R £1.25		
G8 47R 15 watt 75p		
Pyc 731 3+56+27R 50p		
Pyc 3R5/15R/45R 50p		
Thorn 5017/1K5 £1.00		
120/20/48/117 £1.00		
270/106 for Thorn 400 50p		
18/320/7039 £1.10		
Thorn 50-40R-1K5 50p		
Ae Socket & Lead £1		
GEC, ITT, Philips. Pyc 25p		
7x3/34 Thorn £4		
Thorn 1600/1700 £1.50		
Rank Toshiba Tube Bases 30p		
Speakers		
Pair 25 watt 4Ω speaker & tweeter in cabinet £15.00		
6x4 G11 £1.00		
5 1/2x2 1/2 £1.00		
5x3 70p		
5x3 50p		
5x3 70p		
6x4 £1.00		
7x3 £1.00		
8x5 £1.00		
8x5 £1.00		
5x3 70p		
7x3 £1.00		
5" dia £1.00		
5" dia £1.00		
6 1/2" dia £1.00		
6 1/2" dia £1.00		
2 3/4" dia 75p		
3" dia 75p		
4 1/2" sq. 75p		
KT3 speaker 75p		
3" dia 75p		
1600 5x3 £1		
K45 Philip 75p		
K30 15 watt £1		
KT3-K30		
OF-550 10p		
OF-513 10p		
OF-557 50p		
DIODES		
BY 126 10p		
BY 127 10p		
BY 133 10p		
BY 134 10p		
BY 164 10p		
BY 176 25p		
BY 179 40p		
BY 184 25p		
BY 187 10p		
BY 190 40p		
BY 196 40p		
BY 198 8p		
BY 204/4 8p		
BY 206 8p		
BY 208/800 10p		
BY 210/400 5p		
BY 210/800 10p		
BY 223 60p		
BY 224/600: 4.8A/600Ω bridge 50p		
BY 226 15p		
BY 227 15p		
BY 229/400 10p		
BY 237 5p		
BY 254 10p		
BY 255 10p		
BY 298 10p		
BY 299 10p		
BY 406 8p		
BY 527 20p		
BY 407A 10p		
BY 602 10p		
F 247 10p		
XK 3102 50p		
International Rectifier EIT Diodes 7p		
6A/600V Stud Diodes 20p		
6A/1000V Stud Diodes 20p		

NEW 1617 THORN Chassis with ICs & AU113 £8.00		
30V Power Supply 500mA 4x2/4 £2.50		
Pyc 731 Power Panel £13		
6 Diode Universal Triplers £4.00		
NEW Pyc 725 line O/P panel with L.O.P.T. & Tripler £10.00		
NEW GEC 20AX Power Supply Switch Mode £12.00		
Complete new GEC portable chassis M1201H/M1501H with P.B.U./cap/LOPTI £10		
Field + Jangle panel for GEC 3133/3135 £1.50		
GEC 2110 line panel with transformer £7.00		
GEC 2110 tuner unit + IF Panel £12.00		
Pyc/Chelsea Line op panel £7.00		
Pyc 205 T/unit £3.90		
Pyc 205 Line op panel £7.50		
Pyc 713 IF panel and tuner £7.00		
Pyc 713 Chroma £10.00		
Pyc/Chelsea Timebase panel with LOPTI £5.00		
Pyc 731 Frame Panel £5.00		
Pyc 731 Chroma £10.00		
Pyc 731 IF panel + tuner £10.00		
Pyc CIDA/205 panel £6.00		
GEC portable chassis + LOPTI 2114 New £4.00		
Thorn 1613/1713 chassis 9.75		
G9 Power Panel £6.00		
Mono RANK Chassis 127A NEW £10.00		
NEW G9 Frame Panel £10.00		
NEW G11 IF Panel £10.00		
NEW MULLARD TELETEX		
Panel 6101 £6.00	3300/70 1/100	
G8 Tuner Unit + Panel £4.00	1/100 x 10 5p	
G8 Power Supply £5.00	22/2100 25p	
G8 6 Sloping PBUs £8.00	47M/100 5p	
G8 IF & Chroma £10.00	470/100 5p	
G8 Chroma £3.00	2000/100 70p	
	4700/100 75p	
G11 IF Detector £3.00	47/160 10p	
G11 Selector gain module £2	300 300/300V 80p	
Complete CVC 825 Chassis (both panels) £40.00	800/160 50p	
AEC V/Cap Resistor Unit UHF with IC £3.00	1/250 Pulse 10p	
SA5660/SA5670 £3.00	2.2 250v 10p	
Z714 RANK IF Panels 6MHz 1 I.C. £3.00	3n3/250 A.C. 25p	
SL437F £3.00	33/250V 20p	
Z599B RANK IF Panels £2.50	4n7/250 tested 5KV 35p	
Export 5.5MHz 2 I.C.'s £2.50	91/250 35p	
TBA1205B TCA2705Q £6.00	91/400 15p	
K35 IF £6.00	22/250 10p	
Z743 RANK IF Panel £1.00	47/250 15p	
Export 5.5MHz 3 I.C.'s £1.50	100/250 20p	
TBA750+SC9504P+ £1.50	G11 470/250V £1.75	
SC9503P £1.50	GEC600/250 60p	
Pyc G11 Front panel with transducer, pots, tuner pots, 6 pb switch + lead £5.00	700/250 £1.00	
Pyc 6 button switch portable £1.00	300+300 MFD 350v 40p	
GEC V/cap VHF/UHF tuner and IF + sound O/P PC 706B3 (Export) £12.00	32/300 20p	
GFC Line O/P PC 659B3 £6.00	47/50 5p	
1110 GEC Power Panel £8.00	8/350 8p	
GEC Power Supply (Export) £10.00	4.7M/350v 10p	
G11 dynamic correction panel £6	220/350 30p	
CVC 20 Front panel with sliders + mains input panel £4	300/350 40p	
CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	400/350 50p	
CVC 9 slider pots panel £2	103/75 10p	
CVC 5 Mains on/off + 5 pots 50p	22/375 15p	
Universal Focus. Fits Pyc. Thorn and Decca Units. £10.00	220/385 75p	
T147 Rank tube base on panel £1.00	330/385 CVC 820HT 60p	
Z718 Focus Unit £1.50	330/385 CVC 820HT 60p	
T20 Focus Unit £1.00	330/385 CVC 820HT 60p	
Large Type 75p	330/385 CVC 820HT 60p	
Decca Small 75p	330/385 CVC 820HT 60p	
K13 Focus Unit 75p	330/385 CVC 820HT 60p	
K30 Focus Pot 75p	330/385 CVC 820HT 60p	
K30 Tube base on panel £1.00	330/385 CVC 820HT 60p	
TX10 Focus Units £7.00	330/385 CVC 820HT 60p	
CVC 32 Focus Unit 30p	330/385 CVC 820HT 60p	
Fidelity Focus Unit 14R-14S 30p	330/385 CVC 820HT 60p	
3500 Thorn Focus Unit £1.00	330/385 CVC 820HT 60p	
ITT Small for use with Split £2.00	330/385 CVC 820HT 60p	
Z718 Bush Focus 50p	330/385 CVC 820HT 60p	
Diode 50p	330/385 CVC 820HT 60p	
TV11 50p	330/385 CVC 820HT 60p	
Remo TV12SP 50p	330/385 CVC 820HT 60p	
1600 Thorn EHT Rec and Lead 50p	330/385 CVC 820HT 60p	
TV13 50p	330/385 CVC 820HT 60p	
TV14 50p	330/385 CVC 820HT 60p	
TV18 60p	330/385 CVC 820HT 60p	
TV20 £1.50	330/385 CVC 820HT 60p	
TV45 5p	330/385 CVC 820HT 60p	
Thorn 14/1500 rec stick 5p	330/385 CVC 820HT 60p	
G7000 Philips Video Games Packs		
11 types £5		
G11 drawer ASS 3 pots Mains switch and lead £2.00		
Line O/P panel GEC 2217/2218/221V/2214/2226/2227/2228 £10		
CLOCK DISPLAY		
4 SEG ACDM45 £1.00		
4000 thick film £2.00		
DISPLAYS		
4040 Clock £1.00		
7seg Red LED 50p		
2 digit LED 8.8 50p		
2 digit LED → 1.8 with panel + MC14511 £1.00		
4700/63 £1.50		
250/64 10p		
CVC 20-25-30 Mains Switches £3.00		
Infra Red and Ultrasonic G11 Teletext Decoder Panel £1.50		
RANK & ITT Mains Remote On-Off Switch (720R) £1.50		
RANK & ITT Mains Remote Switch 2865 ohm £1.50		
RANK & ITT Remote Switch 2800 ohm £1.50		
G11 Mains Switch 50p		
4 amp Mains Switch 50p		
GEC Mains Switch 4 amp 50p		
KT3 Mains Switch 50p		
G8 Mains Switch 50p		
Thyristor 6004 amp C106/2 24p		
G11 Preh Red LED P/Button for C.H. Change 24p		
RANK TOSHIBA Transducers TPC-2011 50p		
Mains Switch ITT Long Type Print 75p		
Mains Switch GEC Long Type TAG 75p		
Thorn 12 or 24 volt battery converter for portable colour TV £6.00		

Tube Thermpath 167 £1.00		
Rank Secam Decoder Panel UHF & VHF T115A £13.00		
Multi-Caps		
4.700/75 6 amp Rip £2.00		
350V 300M + 300M £1.00		
400V 400M 60p		
350V 400M 60p		
Thorn 3500 £1.00		
175/100/100/350v £1.00		
KT3/200/25/25/385v £1.00		
300 + 300 + 150 + 100 + 50MFD £2		
350V £2		
47/220/350v 60p		
150/150/100/100/100/320v £2.00		
2500/2500/63v 50p		
150/200/200/300v 70p		
400/400/200v £1.70		
300/100/100/16/275v £1.50		
100/200/325v 40p		
150/150/100/375v £1.50		
300/300/100/32/32/300v 2.00		
1500/2000/30v 50p		
Jelly pot Thorn 00D40/13 £3		
150/150/100/100/320v £2.00		
100/350 + 300/200/100/16/275v £2.00		
225 + 25/380 GEC 70p		
200/100/100/350v £1.50		
500/500/25v 50p		
150/150/100/300v 75p		
200/150/150/300v 1.00		
ITT Panels		
CVC 40/2 Chassis, new £30, complete with interface panel £3.00		
CVC 820 Line O/P Panel £3.00		
CVC 20 Mains Panel £3.00		
ITT 8 & 6 Push Button Unit £1.00		
CVC40/2 New Chroma Panel £10.00		
CMA 10 £2.00		
CMA 11 £2		

SENDZ COMPONENTS

63 Bishopstington,
Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE

All items subject to availability.
No Accounts - No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then £1 Postage

Add Postage for overseas
Callers: To shop at 212 London Rd.,
Southend. Tel. 0702-332992

Open 9-1/2.30-6. GVMT + school orders accepted on official
headings add 10% handling charge.

Tuner Units	
V/Cap Rank UHF Z776T/Unit	£6
V/Cap Rank VHF Z773T/Unit	£5
NEW G8 Tuner V/Cap	£5.50
ELC2000 on Panel	£2.50
GE6 6 Push Button Unit	£6
ITT 6 Push Button Unit	£6
DECCA 6 Push Button Unit	£6
GE6 or Hitachi 6 push button unit 2110 Conversion	£8
GE6 2110 V/Cap	£5
ELC1043 (Ex Panel)	£3.75
ELC1042 (Ex Panel)	£5.00
ELC2000	£4.00
ELC2004	£10.00
ELC2006	NEW £10.00
GE6 Tuner V/Cap Hitachi After 1979 ETS48, ETS47, ETS46, ETS41B	£8.00
ASTECC UM1183	£10.00
U322 (UHF)	£4.00
V314 (VHF)	£5.00
V317 (VHF)	£5
V334 (VHF)	£5
U321	£6
U341 UHF	£7.00
U342 (UHF)	£5
U411 UHF	£7.00
U.V. 411 Tuner	£10.00
U.V. 415	£7.00
U.V. 417	£7.00
ELC1043/05 Thom	£5.90
ELC1043/06 Thom	£5.00
Small V/Cap Mitsumi UHF	£4.00
VHF	£3.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
NSF-UHF/VHF Varicap (old type)	£8.00
Mosfit UHF/VHF (new type)	£8.00
UE2-B31 Fidelity V/Cap T/Unit	£6.00
UHF-VHF V/Caps on panel	£3.00
Thorn Tuner PANEL with 6x100K pots + cursors NO TUNER	£1.00
HITACHI 20 Turn Pot	40p
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR Videom MTS 900	£2.50
Mullard Video Modulator. Application, video tape recorders, TV cameras, video games, closed circuit TV, C.C.I.R. system. Data supplied.	£10.00
VT 100 Sound Tuner Kit. TV. Viosound. The latest design in low noise fitted with DNR, RF output and audio	£30.00
Sylvania UHF F4720B	£6.00
Sylvania VHF 900	£6.00
Small Tuner DX 175-220MHz Auto Changeover	£5.00
9000 Thorn Tuner on Panel	£7.00

D.P.D.T. switch Black knob: Chassis or PCB mount	
each or 40 for £1.00	4p
THORN 1400 4P.B. Mech. Tuner	40p
THORN 1500 4P.B. Mech. Tuner	40p
THORN 1500 4P.B. Mech. Tuner	40p
THORN 3500 4P.B. Mech. Tuner	40p
THORN 8000 4P.B. Mech. Tuner	40p
THORN 8500 Mech. Tuner	40p
All new & boxed.	£4.00 each
Delay Lines	
DL20A 80p	DL600 £1.00
G8 (Old Type)	£1.00
DL600	£1.00
DL710	£1.00
ULD11	30p
KT 3 Luminescence	75p
Luminescence Delay Line (CVC 45)	25p
10x1 500mA	80p
10x1 amp.	80p
Co-Ax Joint	15p
Co-Ax Belling Lee Plug	15p
Co-Ax Splitter	£1.00
UHF Modulator CCIR	£3.00
Infra Red Emitting Diode	20p
NE286H Small Neon Lamps	5p
& Philips	5p
Mullard 5 Watt Amps. LP1162	75p
New	
T.V. Tubes	
12/1107 31/510 with coils	Post £2.50 £5
4.5" tube NEC 120ANB4	£8
12" A3170W Hitachi	£10
18" Hitachi P11 Hitachi	£18
10" Black and white tube scan coils & line trans	£6.00

Integrated Circuits	
AC76003	£1.50
AM25LS23PC	10p
BAV40	40p
BC478	10p
BC527	5p
BC532	10p
BC546	10p
BC548	10p
BC556	10p
BC557	10p
BC558	10p
BC559	10p
BC635	10p
BCX32/36 Pair	25p
BCX32	25p
BD116	25p
BD124	50p
BD124 (metal)	60p
BD131	25p
BD132/238	30p
BD135	25p
BD136	25p
BD138	30p
BD140	30p
BD176	25p
BD182	£1.00
BD183	70p
BD202	60p
BD204	60p
BD207	60p
BD221	20p
BD222	20p
BD228	20p
BD226	20p
BD227	20p
BD235	30p
BD238	30p
BD239	15p
BD240	8p
BD243c	30p
BD244	30p
BD250A	8p
BD252	10p
BD253B	10p
BD331	10p
BD373b	20p
BD416	20p
BD433	25p
BD437	25p
BD439	50p
BD678	30p
BD681	30p
BD682	30p
BF761	7p
BF819A	30p
BF858	30p
BF871	30p
BF879	15p
BF879	15p
BF881	15p
BF887	10p
BF890	10p
BF952	20p
BF957	20p
BF958	20p
BF959	20p
BF960	20p
BF961	20p
BF962	20p
BF963	20p
BF964	20p
BF965	20p
BF966	20p
BF967	20p
BF968	20p
BF969	20p
BF970	20p
BF971	20p
BF972	20p
BF973	20p
BF974	20p
BF975	20p
BF976	20p
BF977	20p
BF978	20p
BF979	20p
BF980	20p
BF981	20p
BF982	20p
BF983	20p
BF984	20p
BF985	20p
BF986	20p
BF987	20p
BF988	20p
BF989	20p
BF990	20p
BF991	20p
BF992	20p
BF993	20p
BF994	20p
BF995	20p
BF996	20p
BF997	20p
BF998	20p
BF999	20p
BF1000	20p

SAS560	£2.00
SAS660	£1.00
SAS670	£1.00
SAS580	75p
SAS590	75p
SAS3210	£2.00
SL437F	£4.00
SL901B	£4.50
SL918	£4.50
TA7122	£1.15
TAA320A	75p
TAA400	£1.50
TAA570	75p
TAA611B	£2.00
TAA621	£2.00
TAA661	50p
TAA661	50p
TA7108P	£1.00
TA7120P	50p
TA7315AP	50p
TA7607AP	40p
TA7609P	50p
TBA120A	40p
TBA120AS	40p
TBA120SA	40p
TBA120B	40p
TBA120SB	40p
TBA120T	50p
TBA120SO	£1.00
TBA120U	75p
TBA120Q	30p
TBA120C	40p
TBA1441	£1.00
TBA231	75p
TBA3050	50p
TBA396Q	40p
TBA396	75p
TBA440P	£1.00
TBA440C	£1.00
TBA480Q	£1.00
TBA520	£2.00
TBA530	£2.00
TBA540	£1.00
TBA550Q	£1.75
TBA560Q	£1.00
TBA570	£1.50
TBA641	£2.00
TBA651	£2.00
TBA673	£1.00
TBA720A	£1.50
TBA750Q	£1.50
TBA780	£1.50
TBA800	50p
TBA810AP	60p
TBA810S	60p
TBA820	60p
TBA890	£1.00
TBA900	£1.50
TBA920Q	£1.50
TBA950	£1.50
TBA990Q	£1.00
TMS1000NL	£2.00
TMS1943 N2L (clockchip)	£1.00
TMS9980	£4.00
TMS9901	£1.00
TMS2708JG45	£1.00
TMS2709JL	45p
TMS3529	75p
TMS3720ANS	£3.00
TMS4014	70p
TX-012	£1.00
TMS9902	£1.20
ULN2216	75p
UPC566H	£1.00
UPC585C	£1.00
UPC1031H	£2.00
UPC1353C	£1.00
UPC1363C	£2.75
UPC1366C	£1.00
UPC2012	35p
UPD804911C	£2
SN29848	50p
SN29770BN	£1.00
SN29770AN	£1.00
SN29772BN	£1.00
SN7402N	£1
SN7472N	£1
SN74107	£1.00
SN74107	20p
SN74109	20p
SN74109	£1.00
SN76001	£1.00
SN76003	£1.00
SN76013ND	£1.50
SN76018	£1.00
SN76048	£1.00
SN76023N	£1.50
SN76033	£1.50
SN76110N	£1
SN76115AN	50p
SN76141N	£1.00
SN76226	£1.00
SN76227N	£1.00
SN76228N	£1.00
SN76270	£1.00
SN76532N	50p
SN76544N	£2.00

SN76545N	£3.00
SN76546	£1.00
SN76550	30p
SN76552	30p
SN76570	£1.00
SN76620	50p
SN76650	50p
SN76660N	40p
SN76620AN	50p
SN76666	£1.00
SN76705N	75p
SN76707N	75p
SN76708AN	75p
SN76720	£1.00
SN76709N	£2.00
UA7839C	40p
BT100A/02	40p
BT138/10A	70p
TA7116	30p
TBA540Q	£1.50
TA270	£1.00
TA270Q	£1.00
TA270R	£1.00
TA270S	£1.00
TA270T	£1.00
TA270U	£1.00
TA270V	£1.00
TA270W	£1.00
TA270X	£1.00
TA270Y	£1.00
TA270Z	£1.00
TA270AA	£1.00
TA270AB	£1.00
TA270AC	£1.00
TA270AD	£1.00
TA270AE	£1.00
TA270AF	£1.00
TA270AG	£1.00
TA270AH	£1.00
TA270AI	£1.00
TA270AJ	£1.00
TA270AK	£1.00
TA270AL	£1.00
TA270AM	£1.00
TA270AN	£1.00
TA270AO	£1.00
TA270AP	£1.00
TA270AQ	£1.00
TA270AR	£1.00
TA270AS	£1.00
TA270AT	£1.00
TA270AU	£1.00
TA270AV	£1.00
TA270AW	£1.00
TA270AX	£1.00
TA270AY	£1.00
TA270AZ	£1.00
TA270BA	£1.00
TA270BB	£1.00
TA270BC	£1.00
TA270BD	£1.00
TA270BE	£1.00
TA270BF	£1.00
TA270BG	£1.00
TA270BH	£1.00
TA270BI	£1.00
TA270BJ	£1.00
TA270BK	£1.00
TA270BL	£1.00
TA270BM	£1.00
TA270BN	£1.00
TA270BO	£1.00
TA270BP	£1.00
TA270BQ	£1.00
TA270BR	£1.00
TA270BS	£1.00
TA270BT	£1.00
TA270BU	£1.00
TA270BV	£1.00
TA270BW	£1.00
TA270BX	£1.00
TA270BY	£1.00
TA270BZ	£1.00
TA270CA	£1.00
TA270CB	£1.00
TA270CC	£1.00
TA270CD	£1.00
TA270CE	£1.00
TA270CF	£1.00
TA270CG	£1.00
TA270CH	£1.00
TA270CI	£1.00
TA270CJ	£1.00
TA270CK	£1.00
TA270CL	£1.00
TA270CM	£1.00
TA270CN	£1.00
TA270CO	£1.00
TA270CP	£1.00
TA270CQ	£1.00
TA270CR	£1.00
TA270CS	£1.00
TA270CT	£1.00
TA270CU	£1.00
TA270CV	£1.00
TA270CW	£1.00
TA270CX	£1.00
TA270CY	£1.00
TA270CZ	£1.00
TA270DA	£1.00
TA270DB	£1.00
TA270DC	£1.00
TA270DD	£1.00
TA270DE	£1.00
TA270DF	£1.00
TA270DG	£1.00
TA270DH	£1.00
TA270DI	£1.00
TA270DJ	£1.00
TA270DK	£1.00
TA270DL	£1.00
TA270DM	£1.00
TA270DN	£1.00
TA270DO	£1.00
TA270DP	£1.00
TA270DQ	£1.00
TA270DR	£1.00
TA270DS	£1.00
TA270DT	£1.00
TA270DU	£1.00
TA270DV	£1.00
TA270DW	£1.00
TA270DX	£1.00
TA270DY	£1.00
TA270DZ	£1.00
TA270EA	£1.00
TA270EB	£1.00
TA270EC	£1.00
TA270ED	£1.00
TA270EE	£1.00
TA270EF	£1.00
TA270EG	£1.00
TA270EH	£1.00
TA270EI	£1.00
TA270EJ	£1.00
TA270EK	£1.00
TA270EL	£1.00
TA270EM	£1.00
TA270EN	£1.00
TA270EO	£1.00
TA270EP	£1.00
TA270EQ	£1.00
TA270ER	£1.00
TA270ES	£1.00
TA270ET	£1.00
TA270EU	£1.00
TA270EV	£1.00
TA270EW	£1.00
TA270EX	£1.00
TA270EY	£1.00
TA270EZ	£1.00
TA270FA	£1.00
TA270FB	£1.00
TA270FC	£1.00
TA270FD	£1.00
TA270FE	£1.00
TA270FF	£1.00
TA270FG	£1.00
TA270FH	£1.00
TA270FI	£1.00
TA270FJ	£1.00
TA270FK	£1.00
TA270FL	£1.00
TA270FM	£1.00
TA270FN	£1.00
TA270FO	£1.00
TA270FP	£1.00
TA270FQ	£1.00
TA270FR	