

AUGUST 1986

Australia \$2, New Zealand \$2.50, Malaysia \$5.75 **£1.20**

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS



**Satellite TVRO Installation
Simple RGB Interface Circuit
Scan Yokes for Colour Tubes
Timebase Synchronisation • DX-TV
Operation of Electric Motors
VCR Clinic • TV Fault Finding**

THE 'TELEVISION' PHOTO SERVICE



So many readers have taken advantage of this award-winning service that the economies made are being passed on to you. Despite inflation, prices for Superprints are the same as for last year, and prices for standard size prints are even lower! Here is the price range—and remember, Superprints give you 30 per cent more picture area.

No. of Exposures	Superprints (inc. 15% VAT)	Standard size prints (inc. 15% VAT)
12—15	£1.65	£1.49
20—24	£2.20	£1.99
36	£2.95	£2.49

Plus 30p post and packing.
Extra set of prints (any size) £1.40.

RELIABILITY AND QUALITY

All our prints are made on super high-gloss Kodak paper. They are checked at every processing stage for accurate colour reproduction by the Kodak Monitoring Service—a Gold Award Winner in both 1984 and 1985. After allowing for postal and peak-period delays, you should normally expect your prints by First Class return post after seven to ten days.

ALL YOU HAVE TO DO

Send your film together with cheque or postal order in the Freepost envelope enclosed with this issue. Or fill in the coupon below and send together with your film and remittance in a strong envelope to: Readers Photo Service, FREEPOST, PO Box No. 42, Brunel Road, Newton Abbot, Devon TQ12 4XJ. All popular makes and sizes of film are accepted, and you have a full money-back guarantee. Credit is given for prints that do not come out.

PERSONALISED SERVICE

Readers know we care for their prints. If you have any queries, phone 0626 67150.

SPECIAL FILM OFFER

Even if you do not have an exposed film ready for processing, you can obtain films from us at highly competitive prices. Fresh Kodacolor VR Film for colour prints from only £1.99. Konica SR High Resolution Film for colour prints from £1.50 and when you order three you get another one FREE.

To take advantage of this offer, you must use the special order form on this page.

Sizes of Photos (Approx.)

Superprint sizes: 4" x 4" (126) 4" x 5" (110 and Disc) 4" x 6" (135)
Standard print sizes: 3.5" x 3.5" (126) 3.5" x 4.5" (110 and Disc) 3.5" x 5" (135)

USE THIS LABEL IF YOU HAVE NO ENVELOPE OR PASS TO A FRIEND. IT IS USED TO ENCLOSE YOUR PRINTS.



TO ORDER NEW KODACOLOR FILM				
Please write quantity required in the box(es) below.				
	size	each	qty	amount
Kodacolor VR film for Colour Prints	126.24	£1.99		
	110.24	£1.99		
	135.24	£1.99		
	135.36	£2.49		
	15 Disc	£1.99		
Cheque/PO payable to READERS PHOTO SERVICE				£
Name _____				
Address _____				
Post Code _____				

TO ORDER NEW KONICA FILM					
Please write quantity required in the box(es) below.					
	size	each	qty	4 for 3	amount
KONICA SR film for Colour Prints	126.24	£1.50			£4.50
	110.24	£1.50			£4.50
	135.24	£1.50			£4.50
	135.36	£2.20			£6.60
	15 Disc	£1.50			£4.50
Cheque/PO payable to READERS PHOTO SERVICE				£	
Name _____					
Address _____					
Post Code _____					

TO SEND FILMS FOR PROCESSING	
I enclose.....films for processing.	
Please send	(tick boxes)
SUPERPRINTS	<input type="checkbox"/>
Standard Prints	<input type="checkbox"/>
EXTRA SET OF PRINTS	<input type="checkbox"/>
I enclose cheque/PO for	
£.....	made payable to
READERS PHOTO SERVICE.	
ENCLOSE ORDER FORMS & PAYMENT	
FOR NEW FILMS TOO IF REQUIRED.	
Name _____	
Address _____	

Post Code _____	

COPYRIGHT

© IPC Magazines Limited, 1986. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £14 in the UK, £17 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Send orders for binders (£4.50) and indexes (75p) to the Editorial Office, Television, IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS. Prices include VAT and postage. Add 60p for overseas orders.

BACK NUMBERS

Some back issues published during the last six months are available from the Editorial Office at £1.40 inclusive of postage and packing. Address as above.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.


Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this mo

- 629 Leader**
- 630 Letters**
- 632 Single-channel**
The aim
channel
- 635 Thanks De**
The Net
Other co
blind we
- 636 Satellite T**
What to
TV receiv
finding t
- 639 VCR Clinic**
Reports f
Blundell,
- 641 Simple RG**
A simple but effective circuit for using the RGB plus sync outputs from a microcomputer to drive a standard TV receiver.
- 642 Teletopics**
News, comment and developments.
- 644 Modern Receiver Circuitry, Part 5** *J. LeJeune*
Synchronising the timebases, including a look at the complex arrangements used in a modern sync/timebase generator chip.
- 646 TV Fault Finding**
Reports from Steve Leatherbarrow, Hugh MacMullen, Philip Blundell, Eng. Tech., Keith Hamer, Garry Smith and J.K. Potts.
- 648 The Development of Colour Tubes, Part 3** *Eugene Trundle*
The design of scan yokes to produce astigmatic deflection fields and shadowmask developments.
- 654 The Operation of Electric Motors, Part 1** *Mike Phelan*
VCR electric motors can be expensive items, so it's desirable to know whether repair might be possible. The basic theory of a.c. induction motors is covered in this instalment.
- 656 Servicing Sinclair Microcomputers, Part 4** *Ken Taylor*
The rest of the Spectrum circuitry plus memory checks and fault finding.
- 659 Next Month in Television**
- 660 Saturday Plight Fever** *Chris Avis*
Saturday seems to be the day when all the problem sets come in. This was no exception.
- 661 Resistor Troubles** *Gordon Haigh*
Some resistor tips worth noting.
- 662 Long-distance Television** *Roger Bunney*
Reports on DX reception and conditions, news from abroad and details of a narrow-band i.f. amplifier circuit.
- 666 Service Bureau**
- 667 Test Case 284**

**OUR NEXT ISSUE DATED SEPTEMBER WILL
BE PUBLISHED ON AUGUST 20**

PAL COLOUR BAR GENERATOR (Mk4)

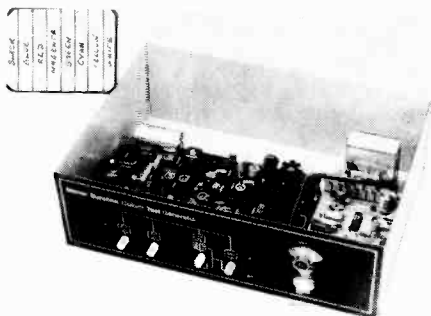

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT
£30.00. CASE £8.60. BATT HOLDERS £4.20. MAINS
SUPPLY KIT £4.20 (Combined P&P £2.20).

MK 4 (BATTERY) BUILT & TESTED £58.00 + £2.20 P & P.
MK 4 (MAINS) BUILT & TESTED £68.00 + £2.20 P & P.
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS £5.75.
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

ADD
VAT
15%

THORN TX9 MK2/3, TX10, teletext
 Mullard Decoder panel + Interface **£35.00** p.p. £1.80
THORN TX10, PHILIPS G11 PRESTEL, TELETEXT
 Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£38.00**
 p.p. £2.50

EXTERNAL TELETEXT ADAPTOR
 (RADOFIN) with cable remote control. Fully tested. **£150.00** p.p.
£3.00. Plugs into aerial socket of any T.V.

£8.50 p.p. £1.50.
SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V.
 Sound & Vision. **£28.50** p.p. £1.20.
THORN TX9, TX10 Saw Filter IF Panel. **£5.00** p.p. 80p.
PAL DECODER KIT (Video to RGB) for Monitors **£27.00** p.p. £1.00.
PAL ENCODER KIT (RGB to Video) **£18.50** p.p. £1.30.
TELETEXT DECODERS New & Tested Mullard VM 6101 **£30.00.** Texas
 XM11 **£40.00,** KT3 Tested **£30.00,** Untested **£5.00** p.p. £1.60
CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF
 Modulator, Battery Operated, also gives Peak White & Black Levels, can be
 used for any set. **£12.00** p.p. 80p. (Alum. Case **£2.90,** De Luxe Case **£6.80**
 p.p. £1.40.) **ADDITIONAL GREY SCALE Kit** **£2.90** p.p. 45p.
UHF SIGNAL STRENGTH METER KIT **£22.00** Alum. Case **£2.90.** De
 Luxe Case **£8.60** (Built & Tested **£48.00**) p.p. £2.30.
CRT TESTER & REACTIVATOR KIT For Colour & Mono complete with
 Case. Panel Meter Indicator - can be adapted for latest CRTs **£29.50** p.p.
£2.80.
BUSH A823 Convergence. Time Base Panels **£5.00** each. p.p. £1.80.
BUSH Z718 BC6100 series IF Panel **£5.00** p.p. 90p.
BUSH A816 IF Panel (Surplus) **£1.00** p.p. 90p. 5 for **£4.00** p.p. £1.40.
GEC 2040 Decoder Panels. **£1.50** p.p. £1.80.
GEC 2110 PANELS Frame **£8.50** p.p. £1.40. Sound **£2.50** (tested) p.p. 80p.
GEC 20AX Line Time Base **£18.00.** IF-Decoder **£12.50** p.p. £2.00.
PYE 691-7 CDA Panels. Makers tested stock. **£6.00** p.p. £1.45.
THORN TX9 Panels ex factory for small spares. Includes I.C.s &
 Semiconductors etc. **£3.00** p.p. £1.80.
THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains
 Transformers. **£10.00** p.p. £2.80.
THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. £2.80.
THORN 8000, 8500, 8800 IF Decoder Panels Tested **£10.00** p.p. £2.30.
THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. £1.80.
THORN 9000 IF/Decoder Panels Salvaged. For spares **£2.50** p.p. £1.80.
THORN 9000 Frame Time Base **£8.50** p.p. £1.80.
PHILIPS G8/G9 IF/Decoder Panels for small spares incl ICs **£2.50** p.p. £1.60.
PHILIPS G8 Line Driver Panel incl. Equalizing Coil. **£1.00** p.p. 60p.
G11 PANELS, Ex Rental SCAN (incl LOPT) **£28.00** p.p. £2.50 (tested).
G11 PANELS, Power, Frame, IF, Decoder. **£18.00** each. p.p. £2.00 (tested).
GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. £1.00.
U321. ELC1043/5 **£7.80** p.p. 80p. Makers Controls **PYE CT200** 4PSN **£7.50,**
BUSH 4PSN **£4.80,** **DECCA 4PSN** **£5.80,** **6PSN** **£6.80** p.p. 80p. etc.
BUSH "TOUCH TUNE" Varicap Control Z585, 710 **£3.80** p.p. £1.00.
VARICAP UHF-VHF ELC 2000S **£9.80** p.p. £1.00.
UHF/625 TUNERS, many different types in stock. **DECCA** Bradford 5
 position. **MULLARD** 4 position **£2.50,** **JAP** Rotary **£4.80** p.p. £1.80.
TV SOUND IF Panels **£6.80** p.p. £1.00.
LOPTS New and guar. P/P Mono **£1.35,** Colour **£1.50,** Bobbins 80p.
BUSH, MURPHY 774 series **£9.80**
BUSH, MURPHY A816 series **£9.80**
FERG., HMV, MARCONI, ULTRA **£4.80**
 1500, 1590, 1591, 1612, 1613, 1712 **£4.80**
THORN 1600, 1615, 1690, 1691 **£9.15**
GEC series 1 & 2 **£8.00**
INDESIT 2024EG/B **£7.65**
ITT/KB VC200, 300 **£7.90**
PHILIPS 170, 210, 300 series **£7.65**
PYE, INVICTA, EKCO.
 368, 169, 569, 769 series **£7.65**
SPECIAL OFFER
DECCA 1700, 2001, 2020, 2401, 2420 **£3.80**
GEC 2114/J Junior Fineline **£2.80**
PHILIPS 320 **£2.80**
RBM A823 **£4.80**
GEC 2028, 2040, 2100 **£4.80**
PYE 713, 715 **£6.80**
PHILIPS 570, 571 **£6.80**
R.B.M. T20, T22 **£9.80**
R.B.M. T20, T22 Bobbin **£5.60**
DECCA Bradford (state Mod No) **£8.80**
DECCA 80, 100 **£8.80**
FIDELITY ZX2000, 3000 **£16.00**
GEC 2110 series **£10.60**
ITT CVC 5 to 9, **CVC20** **£9.80**
ITT CVC25, CVC30 series **£8.80**
ITT CVC45 **£9.80**
PYE 691-697 (state model no.) **£10.00**
PYE 725 (90°) 731 to 741 **£9.20**
PHILIPS G8 **£8.80**
PHILIPS G9 **£9.80**
PHILIPS K13 **£9.80**
THORN 3000/3500 SCAN, EHT **£6.90**
THORN 8000, 8500, 8800 **£12.80**
THORN 9000 to 9600 **£12.90**
THORN TX9 **£14.80**

OTHERS AVAILABLE, PRICES ON REQUEST.

TRIPLERS Full range available. Mono & Colour.
Special Offer: **THORN 3000/3500** EHT Tripler **£2.50** p.p. £1.30.
6-3V CRT Boost Transformers for Colour & Mono **£5.90** p.p. £1.40.
THORN TX10 focus control **£8.80** p.p. 80p.

CALLERS WELCOME AT SHOP PREMISES
THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS
 Goods available if in stock immediately over shop counter (Mail order
 between 3 days and 1 week from receipt of order). **ADD VAT 15%**

Telephone 01-794 8751, 794 7346

MANOR SUPPLIES

172 WEST END LANE, LONDON, NW6 1SD
NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
W. Hampstead Brit. Rail Stn. (Richmond, Dalston, Stratford, N. Woolwich)
W. Hampstead Brit. Rail Stn. (St. Pancras, Bedford)

Access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT
PLEASE ADD VAT 15% TO ALL PRICES INCL P+P

INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT

ALSO AVAILABLE
 Analogue Multimeters
 Digital Multimeters
 Oscilloscopes
 Signal Generators
 Digital Frequency Meters
 Pattern Generators
 CRT Tester/Rejuvenator
 T.V. Field Strength Meter
 Digital Capacitance Meter
LARGE S.A.E.
FOR COMPLETE LIST.

LEADER LCT-910A C.R.T. TESTER-REJUVENATOR


Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.

- ★ Tests for shorts and leakage between electrodes.
- ★ Tests cathode emission characteristics.
- ★ Separately checks condition of guns.
- ★ Removal of shorts and leakage between electrodes.
- ★ Checks heater warm-up characteristics.
- ★ Rejuvenation of low emission cathodes with automatic timing.
- ★ Super rejuvenation with manual control.
- ★ Complete with tube base adaptors. Size: H 230mm W 330mm D 120mm.



PRICE £260 + £39 VAT

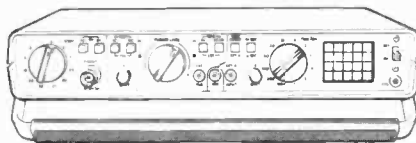THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.



The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**


- Full Sized Performance**
- 10 MHz bandwidth
 - Full trigger facilities are provided including TV frame, or TV filtering
 - Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
 - Size 255mm x 148mm x 50mm.
- 10 mV per division sensitivity.
 PRICE £165.00 + £24.75 VAT

- Accessories:** Carry Case £5.95 + £0.89 V.A.T.
 x 1 Probe £7.50 + £1.13 V.A.T.
 x 10 Probe £8.50 + £1.28 V.A.T.
 x 1/ x 10 Switched Probe £10.50 + £1.58 V.A.T.
 AC Adaptor £6.95 + £1.04 V.A.T.

LOPT TESTER


BK's REVOLUTIONARY DYNAMIC 'LOPT' TESTER
 Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal. Size 75x100x40 mm. Supply 240V AC

PRICE £25.99 + £3.90 VAT

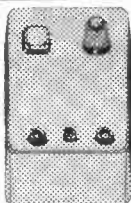

LEADER HIGH VOLTAGE METER EHT PROBE

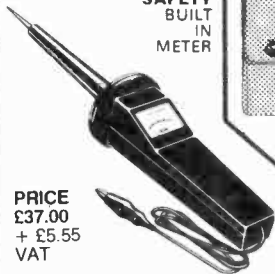Measures up to 40 K.V. D.C. with **SAFETY BUILT IN METER**




PRICE £37.00 + £5.55 VAT

*** FULLY GUARANTEED**

CRT TESTER-REJUVENATOR

BK's C.R.T. TESTER-REJUVENATOR
 Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC


PRICE £32.00 + £4.80 VAT

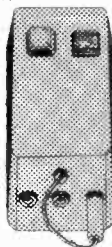

HAMEG HM 203-5 20MHz DUAL TRACE OSCILLOSCOPE

SPECIFICATION:

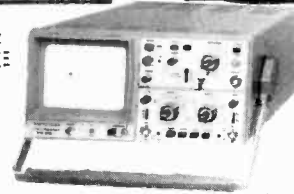- *BANDWIDTH DC-20MHz
- *SENSITIVITY CH1, CH2 2mV-50V/DIV
- *TIMEBASE 40ns to 0.2S CM
- *TRIGGER DC-40MHz Auto-Normal-TV
- *CALIBRATION OUTPUT
- *CH1 ADD AND INVERT FACILITY
- *ALT/CHOP SWITCH
- *LARGE RECTANGULAR SCREEN 8 x 10 cms
- *BUILT IN SEMICONDUCTOR COMP. TESTER
- *SIZE 285mm x 145mm x 380mm.
- *SUPPLY 110-125-220 240V AC 50-60Hz



WITH COMPONENT TESTER

PRICE £270.00 + £40.50 VAT
 Optional probes as above

2 YEAR WARRANTY

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.



B. K. ELECTRONICS Dept. 'T',

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572



TELEPART

Telegen-1

- PRICE £18.35 (Inc. VAT)
- *EXCEPTIONALLY LIGHT AND DURABLE
 - *POCKET SIZE FOR OUTSIDE SERVICE
 - *PP3 BATTERY POWER SOURCE
 - *FIVE DIFFERENT TEST PATTERNS FOR COLOUR & MONO TV
 - *CROSSHATCH GRID * DOT MATRIX
 - *WHITE RASTER
 - *HORIZONTALS * VERTICLES
 - *3.5mm JACK SOCKET FOR OPTIONAL P.S.U.



A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

Telegen-2

- PRICE £34.45 (Inc. VAT)
- *EXCEPTIONALLY LIGHT & DURABLE
 - *COMPACT 10 x 12 x 4.5 cms
 - *RED RASTER * GREEN RASTER
 - *BLUE RASTER
 - *COLOUR BARS
 - *3.5 mm JACK SOCKET FOR P.S.U.
 - *PROVIDES UHF SIGNAL APPROX. CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

Power Supply

A switchable power supply ideally suited to both Telegen 1 and Telegen 2. PRICE £4.55 (Inc. VAT)

ALL ITEMS POST AND PACKING £1.44 (Inc. VAT)
 All goods should be delivered within 4 working days.
32 TEMPLE STREET, WOLVERHAMPTON WV2 4AN. TEL: (0902) 29022 (U.K. ONLY)

MAKE YOUR INTERESTS PAY!!

Train at home for one of these Career Opportunities

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your **FREE INFORMATION PACK** on the course of your choice. (Tick one box only!)

Electronics <input type="checkbox"/>	Radio, Audio & TV Servicing <input type="checkbox"/>
Basic Electronic Engineering (City & Guilds) <input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds) <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	Car Mechanics <input type="checkbox"/>
Elec. Contracting/Installation <input type="checkbox"/>	Computer Programming <input type="checkbox"/>
GCE over 40 'O' & 'A' level subjects <input type="checkbox"/>	

Name: _____

Address: _____

P. Code _____



International Correspondence Schools, Dept. EGS86, 312/314 High St., Sutton, Surrey SM1 1PR. Tel: 01-643 9568 or 041-221 2926 (both 24 hours).

P. V. TUBES

104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.
Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

HOW TO ORDER
ADD 87p per order P+P
(U.K.). Heavier parcels e.g.
cable, service aids, degaus.
coils please allow £1.50 P+P
(U.K.). Export orders charged
at cost. First Class Mail is used
whenever possible. Add 15%
VAT to total except where it
states zero rate.

Goods are despatched on the day we receive your
order. If for any reason we are out of stock we will try
to inform you as quickly as possible. We try our best
to give a speedy, fair and efficient service. V.A.T.
invoice on request. Give us a ring - we'll give you
service. Please ask if what you need is not listed - we
will try to help. Prices are subject to change without
notice. In some cases we may have to supply an
equivalent.

SEMICONDUCTORS

AC107	35	BC550	10
AC126	34	BC557	10
AC127	34	BC558	9
AC128	34	BC635	19
AC128K	40	BC637	23
AC141	62	BC639	30
AC141K	39	BC640	32
AC176	35	BCY72	13
AC176K	35	BD115	45
AC186	41	BD116A	90
AC187	38	BD124P	84
AC187K	46	BD131	50
AC188	35	BD132	49
AC188K	46	BD133	60
AD142	92	BD135	38
AD143=OC28	82	BD136	38
AD161	54	BD137	38
AD162	54	BD138	35
AD161/62 MP	1.15	BD139	35
AF106	49	BD140	44
AF114	89	BD144	1.70
AF118	1.20	BD150	60
AF121	75	BD159	65
AF124	48	BD160	1.60
AF125	53	BD166	52
AF126	53	BD179	70
AF127	53	BD182	1.20
AF139	63	BD183	1.18
AF178	1.54	BD201	85
AF239	60	BD202	91
AF279	1.56	BD203	80
AL102	4.90	BD204	99
AU106	7.50	BD222	46
AU110	3.01	BD223	56
AU113	5.20	BD225	47
BC107	20	BD232	82
BC108	20	BD233	60
BC109	20	BD234	63
BC114	17	BD235	60
BC115	12	BD236	65
BC116A	35	BD237	57
BC117	30	BD238	65
BC118	24	BD243	85
BC119	36	BD244	85
BC139	32	BD410	79
BC140	32	BD434	74
BC141	30	BD437	86
BC142	30	BD436	94
BC143	31	BD507	69
BC147	13	BD508	80
BC148	9	BD509	86
BC149	12	BD510	86
BC157	16	BD278A	81
BC158	16	BD517	60
BC159	15	BD519	1.08
BC160	52	BD520	75
BC161	32	BD535	82
BC170B	15	BD536	91
BC171	15	BD696A	1.49
BC172	15	BD697	1.24
BC173	16	BD698=702	1.50
BC174	10	BD701	1.63
BC177	27	BD707	95
BC178	26	BDX32	2.10
BC182L	15	BF115	38
BC183L	15	BF117	36
BC184L	15	BF125	26
BC186	35	BF127	47
BC187	25	BF154	15
BC204	10	BF158	18
BC208	13	BF160	27
BC209	10	BF167	24
BC212	15	BF173	36
BC212L	15	BF177	52
BC213	15	BF178	46
BC214	15	BF179	42
BC237	14	BF180	3.07
BC236	14	BF181	3.07
BC251A	18	BF182	3.6
BC252	12	BF183	2.9
BC261	33	BF184	4.2
BC262	30	BF185	3.6
BC300	50	BF194/394	1.6
BC301	53	BF195	1.6
BC303	33	BF196	1.6
BC307	20	BF197	1.6
BC308	25	BF198	1.6
BC323	22	BF200	3.5
BC327	18	BF224	40
BC337	18	BF225	20
BC338	18	BF241	38
BC461	42	BF256	60
BC527	35	BF257	34
BC547	13	BF258	34
BC548	13	BF259	34
BCX32 = BC637	39	BF262	84
BC549	10	BF263	81

BF271	24	R2008B	1.90
BF273	24	R2010B	1.92
BF274	24	R2265	1.50
BF336	40	R2322	84
BF337	41	R2323	67
BF338	41	R2461	1.50
BF355	56	R2540	3.20
BF362	68	RC4558	2.20
BF363	72	RCA16334	1.90
BF371	30	RCA16029	1.18
BF392	35	RCA16039	1.18
BF422	34	RCA16041	96
BF423	46	RCA16040	94
BF435 = BF491	35	RCA16334	90
BF457	35	RCA16041	86
BF458	43	RCA16334	90
BF459	58	RCA16335	90
BF460 = BF462	86	RCA16957	2.88
BF469	63	TIC45	90
BF470	66	TIC46	60
BF471	16	TIC47	72
BF472	54	TIC48	65
BF473	54	TIC49	48
BF474	54	TIP29C	43
BF475	54	TIP30A	47
BF476	54	TIP30C	43
BF477	54	TIP31C	55
BF478	54	TIP32C	42
BF479	54	TIP33B	75
BF480	54	TIP34B	1.06
BF481	54	TIP41C	46
BF482	54	TIP42C	50
BF483	54	TIP47	93
BF484	54	TIP120	65
BF485	54	TIP161	2.15
BF486	54	TIP295S	90
BF487	54	TIP305S	63
BF488	54	TIS91	32
BF489	54	TU106/02	1.80
BF490	54	2N696	21
BF491	54	2N918	82
BF492	54	2N2904	51
BF493	54	2N2905	28
BF494	54	2N3054	60
BF495	54	2N3055	60
BF496	54	2N3056	79
BF497	54	2N3057	66
BF498	54	2N3058	66
BF499	54	2N3059	66
BF600	54	2N3160	66

INTEGRATED CIRCUITS

AN2140	3.91	SN76131N	2.00
AN240	3.84	SN76226DN	2.72
AN318	6.37	SN76227N	1.18
AN262	4.10	SN76533N	1.70
AN301	5.15	SN76033N	2.49
AN715Q	3.97	SN76544N	2.35
AN6340	2.80	SN76650N	1.24
AN6341N	8.97	SN76660N	8.0
AN6344	7.85	SN76666N	1.52
BA521	2.80	SN76530A	1.47
BA536	3.00	STK015	7.36
CA555	46	STK032 =	7.36
CA556	84	STK078	13.25
CA741	25	STK433	5.65
CA748	45	STK435	9.06
CA1532	4.20	STK436	6.50
CA3065	1.80	STK437	7.85
HA1151	3.99	STK439	8.40
HA1342	2.49	STK459	9.50
HA1306N	2.80	STK441	11.57
HA1366WR	2.80	STK461 = 465	12.60
HA1392	3.95	STK463	14.30
HA11219	4.21	STR441	6.50
HA11244	4.04	STR451	6.50
LA3350	1.59	STR6020	6.50
LA4031P	3.21	SW153	3.90
LA4032P	3.15	TA7050P	95
LA4102	3.37	TA7051P	95
LA4112	3.25	TA7063P	2.20
LA4400	3.46	TA7074P	3.46
LA4422	3.28	TA7108P	3.43
LA4440	4.07	TA7120P	2.43
LC7130	5.93	TA7129AP	3.76
LC7120	5.87	TA7130P	1.93
LC7137	5.50	TA7146P	5.67
LM1011	3.25	TA7193P	4.57
LM1340T	75	TA7171P	8.90
LM8361 =	8.90	TA7172P	8.90
MM5387ANN	3.69	TA7173P	8.90
MB3712	2.60	TA7176P	2.30
MC1907	1.99	TA7202P	4.27
MC1310P	1.84	TA7204P	3.77
MC1327	1.70	TA7205AP	3.72
MC1351P	2.93	TA7208P	3.40
MC1349	1.99	TA7210P	6.60
MC1350	1.50	TA7222	2.42
MC1352	1.75	TA7223P	3.94
MC1358P	3.00	TA7227P	5.78
MC1495L	6.00	TA7228P	5.98
MC14011BCP	66	TA7310P	2.78
MC14049UB	4.35	TA7609P	4.35
MC7742			

P. V. TUBES

104 ABBEY STREET, (0254) 36521
ACCRINGTON, LANCS BB5 1EE. 32611

SONY PARTS

SEMICONDUCTORS	
Diode CV12E	GEN 2.34
Diode GH3F	KV-GEN 1.42
Diode IS1555	GEN 25
Diode UO5G	KV1810UB 96
Diode V11N	KV1810UB 96
Diode 10E2	GEN 25
Thyristor SG-264A	KV-GEN 4.08
Thyristor SG629	KV1810UB 6.42
Thyristor SG-6533	KV-GEN = SG613 13.20
BX342	SLC7UB 4.08
CX104A	KV1810UB 5.28
CX136A	VTR-GEN 7.74
CX143A	SLC5/7UB 7.20
CX186	SLC5UB 5.28
M51231P	KV2200UB 2.34
STK2129	STRYX50L 13.20
TCP4621AF6	SLC6UB 13.87
TDA2578A	KV2752UB 3.24

Please ask for any part not listed.

UPC 1394C	KV2060/62U 2.34
UPD 546C107	SLC7UB 16.98
UPD 547C049	SLC7UB 8.94
TL494CN	SLC7UB 5.28
2SA 771	TAF5A 2.34
2SA 835	GEN 1.42
2SA 1027R	ICF-C820L 25
2SA 1175	SLC7UB 89
2SB 733	KV2204UB 96
2SB 740C	TCK88B 96
2SB 856	GEN 1.42

2SC 403C	GEN 25
2SC 867A	GEN 2.34
2SC 1034	GEN 5.28
2SC 1061=	GEN 2.34
2SC1986	GEN 2.94
2SC 1114	GEN 5.28
2SC 1124	GEN 96
2SC 1316	GEN 3.18
2SC 1362-7	GEN 25
2SC 1364	GEN 25

2SC 1413A	KV-GEN 7.38
2SC 1475	KV1810UB 25
2SC 1982	GEN 1.42
2SC 2009	GEN 25
2SC 2278	GEN 96
2SC 2335 Kit	SLC7 7.38
2SC 2369	SLC5/7UB 3.18
2SC 2551	KV-GEN 98
2SC 2785	AG-7UB 2.08
2SC 3153	KV2060UB 4.08
2SD 257	ST5150 2.34
2SD 725	KV2204/2704 8.94
2SD 773	BM715T 25
2SD 774	SL/HMK 96
2SD 870	KV2704E 6.42
2SD 1164	SLC6UB 96
2SD 1497-02	KV2252/2752 4.08
2SD 1497-06	KV2252/2752 4.08

SUNDRIES

UHF Tuner BT-871	KV1810UB 37.20
Booster Antenna	SLC7UB 31.38
RF Modulator	SLC6UB 60.38

SONY REMOTE CONTROLS

SLC5UB	19.80
SLC6UB	17.40
SLC7UB	42.00

VIDEO/AUDIO HEADS

Ace Assembly	SLC7UB 24.10
Ace Assembly	SLC6UB 47.22

Video Head DRS-21R	SLC9UB 43.20
Video Head DSR-35A	SLC20/30/40UB 41.34
Video Head DSR-36R	SLC5/6/7UB 42.00
Video Head DSR-43A	SL8000UB 46.74
Head Record-Play-back	PP128-3602C/GEN 13.87
Head Record-Play-back	181-3602D/TC/HMK3000 4.12

SPECIFIC COMPONENTS

Philips G8 knobs smrig	50
90° transducer	2.60
Thom 1591 speakers sm	6.20
lg	6.20
Thom 1500 controls	each 59
390K frame 470K line	2.95
Focus control Thom/GEC	8.40
Thom 9000 focus unit	4.75
Thom 8500 focus unit	10.20
Thom TX10 focus cont.	1.97
Decca bridge trans.	

MECH. REPLACEMENT PARTS

Drum Assembly Main	SLC7UB 192.52
Idler Kit/Rewind Kit	SLC7/C5UB 5.95
Idler Kit/Rewind Kit	SLC6UB 3.18
Forward Assembly	SLC9UB 8.94
Gear Kit	SLC9UB 8.94
Guide Pin Kit	SLF1/C9UB 5.28
Pinch Roller	TC-GEN 96
Pinch Roller	TC2045D 1.42
Pinch Roller	HMK44/44B 96
Pinch Roller	TCK55 96
Cassette Holder	TCX44 1.42
Assembly	WM2 96
Lever Forward	WM2 96
FWheel Assembly	WM2 3.18
Limiter Assembly	SLC7UB 2.34
Idler Assembly	SLC7UB/C5/3000 96
Brake Assembly	SLC7UB 1.42
Pulley Loading	SLC6UB 96
Assembly	HMP70 3.18
Thrust Bearing	WM2 25
Assembly	WM2 25
Screw Cassette Lid	WM2 96
Coil Spring	SLC7UB 96
Battery Lid	SLT6ME 96
Lid Timer	SLT6ME 96
Threading Gear	CS C7 Capstan Motor 34.00
C7 Drive Motor	C7 Drive Motor 32.95
C9 Gear Kit	C9 Gear Kit 8.94

BELTS

Belt	WMP2 96
Rubber Belt	TC-GEN 96
Take Up Belt	TC-GEN 96
Drive Belt	TC-GEN 96
Midway Pull Belt	TC-GEN 96
Capstan Belt	TC92 96
Capstan Belt	TC135/136SD 96
Flat New Belt	TC186SD 96
Capstan Belt	TC-GEN 96
Capstan Belt	HST300 96
Take Up Belt	HMK3000UK 96
Belt Capstan	HMK3000UK etc 96
Fast Forward-Rewind	VO2850P 1.82
Belt	VO2850P 1.02
Motor Belt	VO2850P 1.62
Capstan Belt	VP2000 4.22
Forward Belt	SLC7UB/SLC5UB 25
Capstan Belt	SL8000UB 96
Extension Belt	SL8000UB 2.34
Drum Belt	SL8000UB 1.52
Fast Forward Idler Belt	SLC7UB 96
Threading Belt	SLC7UB 25
Capstan Belt	SLC7UB/CS 96
Eject Belt	SLC7UB 25
Counter Belt	SLC7UB 25
Fast Forward Belt	SL77ME 96
Forward Belt	SL8000UB 96
Fast Forward Belt	SLC6UB 96
Counter Belt	SLC6UB 96
Threading Belt	SLC6UB 96
Relay Belt	SLC6UB 96
Capstan Belt	SLC6UB 96
Belt	PV-5520 etc 3.18

SWITCHES

Switch, Filter	KV2022UB 96
Switch, P.B. Channel	1820/2 & 1340 18.85
Switch, Push Power	KV-GEN 1.20
Switch, Push	SL8000UB 96
Switch, Push Button	Power 3.68
Switch, Power	KV14/2060UB 4.38
Switch, Slide Record	KV2022UB 96
Switch, Slide Record-Playback	SL8000UB 1.42
Switch, Push	KV1612UB 4.08
Switch, Power	KV-GEN 5.50
Button, Stop/Eject	WM4 96
Knob, Control	SLC7UB 96

MANUALS (Zero VAT)

Instruction Manual	SLC9UB 2.00
Instruction Manual	SLC6UB Mk 2 2.00
Instruction Manual	SLC7UB 2.00
Instruction Manual	SLC5UB 2.00
Instruction Manual	SL6UB 2.00
Instruction Manual	KV2212UB/E2 2.00
Instruction Manual	KV2705UB 2.00
Service Manual	HMK3000 8.25
Service Manual	KV1810UB Mk 1 8.25
Service Manual	KV1400UB 8.25
Service Manual	SLC7UB 8.25
Service Manual	SLC5UB 8.25
Service Manual	SLC6UB 8.25
Service Manual	SLC9UB 8.25
Service Manual	SLC6UB Mk 2 8.25

IF Gain module	9.00
C.D.A. Panel	20.00
G8 rear conv. panel	23.00
Decca 30 width cont.	50
Decca 2M2 HT cont.	25
Pye 731 HF choke	6.50
Delay lines DL20, DL60, DL50, DL700	2.20
CRT tube base	1.40
EHT final anode cap.	53
6.3V CRT boost trans.	5.80
Focus rod	1.25
Focus holder	2.20
AFC unit G8	8.82
Decca Speaker 8R	3.75
G11 47K pot plus switch	85
15R fused res. G9	61
G11 line in coil	3.80
G11 pot G2 R.G.B.	6.75
G11 line scan panel	54.00
G11 power panel	41.06
G11 trimbase panel	37.50
G11 bridge trans.	2.35
G11 EW correc. coil	1.95
G11 final anode lead	3.20
G11 focus unit	6.80
G11 38R 3W resistor	98
G11 RGB 10G diodes	69

THORN/FERGUSON SEMI-CONDUCTORS

Diode GL4850	TX10 74
Thyristor TIC45X	TX9 1.18
Diode 19022W	TX9 43
(Thyristor T9053V)	TX9 = T9054V 1.10
(Thyristor T9054V)	TX9 6.81
AN630	3V22 23.22
HA11741	TX90 23.22
M293	TX90 3.80
M50790SP	3V35 6.98
M54544L	3V32 3.80
MC13002	38030 4.98
MC14493	TX9/TX10 2.74
MN1219	3V36 11.43
TDA1236	TX10 3.44
TDA352	TX10 6.00
TDA4500	TX90 5.84
SL490	TX9/TX10/TX100 1.89
DT1144WF	3V35 3.20
ICE9000	TX9 6.9
TIP112H	TX9 3.48
TS051V	TX9 1.36
T6069V	TX9 3.48
T6071	TX100 1.46
T9063V	TX9 3.64
T9064V	TX90 1.14
UP0553C 164	3V29 20.76
UP07519G 031 036	3V36 17.13
UP07538C 020	3V38 11.06
10 Volt T05	3V29 8.74

MANUALS Please check for availability

Service Manual	TCE1690/1691 5.60
Service Manual	TCE1790 1.14
Service Manual	TCE9600 10.05
Service Manual	TCE9800 7.54
Service Manual	TX9 29.04
Service Manual	TX10 40.00
Service Manual	TX90 11.30
Service Manual	TX100 17.50
Service Manual	3V00 Stocks in soon 26.24
Service Manual	3V16 1.28
Supplement to 3V00	3V22 30.62
Stocks in soon	3V23 28.42
Service Manual	3V24 29.00
Service Manual	3V29 3.28
Instruction Manual	3V00 17.50
Service Manual	3V29 3.28
Service Manual	3V30 14.91
Instruction Manual	TX9 2.65
Service Manual	3V31 25.84
Instruction Manual	3V35 1.63
Service Manual	3V35/3V36 27.20
Supplement to 3V35	3V38 1.24
Supplement to 3V35/3V38	3V39 90
3V42	23.94
3V43	30.72

V.C.R. BELTS

Counter Belt 1	3292/3V00/3V16/3V22 60
Counter Belt 2	3292/3V00/3V16/3V22 60
Reel Drive Belt	3292/3V00/3V16/3V22 1.00
Relay Belt	3V00 2.79
Capstan Belt	3292/3V00/3V01/3V16/3V22 3.28
Unloading Belt	3292/3V00/3V16/3V22 60
Drum Motor Belt	3292/3V00/3V16/3V22 2.79
Cassette Drive Belt	3V23 60
Capstan Belt	3V29/3V30 1.62
Loading Belt	3V23 60
Loading Belt	3V29/3V30 60
Loading Belt	3V35/3V36/3V38 60
Tape Spool Drive Belt	3V35/3V36/3V38 60
Take Up Clutch Belt	3V29/3V30/3V35/3V36/3V38 60
Capstan Belt	3V35/3V36/3V38 1.21

VIDEO HEADS

Upper Drum Assmb	3292/3V00 35.94
Upper Drum Assmb	3V22 35.94
Upper Drum Assmb	2200/3660/3V16/3V23/3V24/3V31/3V35/3V36/3V38/3V39 35.94
Upper Drum Assmb	3V29/3V30 35.74

VIDEO LAMPS

Tuning Indicator	TX9 62
Cassette Lamp	3292/3V00 3.66
Cassette Lamp	3V16 1.53
Cassette Lamp	3V16 60
Cassette Lamp	3V23 1.95
Holder	3V29/3V30/3V31/3V32 60
Cassette Lamp	3V29/3V30 1.41
Cassette Lamp	3V31/3V32 1.60

PHILIPS KT3/K30 PARTS

KT3 positor	1.80
Mains electrolytic 225/25 380V	3.00
Selector unit Mod. 933	16.10
On/off switch Mod. 933	3.84
Tripler	12.80
Luminance chroma panel	31.09
2003 UF module	18.63
U321 IF module	16.60
R.G.B. panel	12.87
Sound panel	12.50
Power panel	21.48
Mains input panel	17.96
Line sync panel	26.49
Mark II chroma panel	19.80
Sound module	10.20
LOPT	10.06
Focus unit	3.68
Philips K35 Remote Teletext	26.21
TXT Slimline	26.21
Philips CTX EHT Lead	27.36

V.C.R. MOTORS

Capstan Motor	3292/3V00/3V01/3V16 51.45
Drum Motor	3292/3V00/3V01/3V16/3V22 43.49
SMP Reel Motor	3V23 32.79
Cassette Housing	3V23 10.32
Motor Assembly	3V23 52.81
Capstan Motor	3V23/3V24/3V29/3V30 8.56
Capstan Motor	3V29/3V30 27.32
Reel Motor	3V29/3V30 32.79
Lower Drum Motor	3V29/3V30 78.72
Assembly	3V35/3V36/3V38 6.92
Cassette Motor	3V35/3V36/3V38 5.95
Mode Control Motor	3V35/3V36/3V38 23.90

REMOTE HANOSETS

T723 Non Text	3767/3788 38.60
T725 Non Text	20A2/2282/3781/37041/37081/37101/3714/37351/37361/37371 19.40
T731 Text and Sibre	20A4/2284/37063/37093/37463/37493 20.01
T736 Text	20A3/2203/3795/3796/37003/37103/37353/37363/37373/37953/37963 31.60

SWITCHES

On/Off Switch	TX9 2.98
On/Off Switch	TX10 2.74
Focus Unit	TX10 10.20
8 Way Tuner Unit (Not Drawer)	37141 12.88
8 Way Tuner Unit (Not Drawer)	37360 13.50
8 Way Tuner Unit (Not Drawer)	37340/37370 20.44
Volume Control	38030 1.74
6 Button Switch Assmb	3722/4722/6722/8000 20.70

TRANSFORMERS & INDUCTORS

Line Output Transformer	TCE9000 25.53
FHT Transformer	TX10 33.80
Line Output Transformer	TX10 15.00
Line Output Transformer	TX9 23.85
Line Output Transformer	38030 6.18
RFI Choke	TX9 3.45
DC Input Choke	TX9 15.36
Mains Transformer	TX90 15.03
Linear Line Coil	TX9 1.77
RFI Input Choke	TX9 60

MECHANICAL SPARES - V.C.R. REPLACEMENT

Take Up Rubber Tyre	3292/3V00 60
Rewind Tyre	3292/3V00 60
Timing Gear Assembly	3V00 3.97
Audio Control Head	3292/3V00/3V01/3V16/3V22 42.38
Sub Assembly	3292/3V00/3V16 1.63
Fast Forward Idler	3292/3V00/3V16 1.60
Fast Forward Tyre	3V00/3V16 60
Pinch Roller	3292/3V00/3V01/3V16/3V22/3V23 7.30
Stop Solenoid	3V16 10.42
Pause Solenoid	3V16 16.60
Take Up Idler Assmb	3V00 up to Serial No. 19006 7.54
Take Up Idler Ass	

P. V. TUBES

104 ABBEY STREET, ACCRINGTON

TEL: 0254
36521/32611

SUNDRY EQUIPMENT	
Test Lead Set	4.20
Degaussing Coil Stick	19.00
Signal Ejector	4.00
Elect. Circuit Tester	1.50
5A Choc Bloc (12)	40
Fuse Wire 5A, 15A, 30A	05
4-way 13A Mains Conn.	5.00
Safe Block (mains)	8.50
13A Plug Top (box 10)	4.80
Probes (x10)	10.90
Probes (x1)	10.90
Micro Pliers	4.20
Micro Cutters	5.00
Philips Switchable Probes (x1, 2x10)	13.25
Factory recon. Avo meters	119.00
Avo Battery	2.95
Vero Board	2.59
LG Solder Sucker	6.20
Solder 500g	7.00
D.I.Y. Solder	45
Solder Sucker Antistatic	5.40
Nozzles	81
Trim Tools	
Metal End	30
Solda Mop Stnd.	74
Sidcutters sm.	1.20
Long Nose Pliers	1.20
Surge Protector Plug	12.50
Quick Set Adhesive	75
Sm. Neon Screwdriver	40
Lg. Neon Screwdriver	65
I.C. Inserters	1.18
Automatic Wire Strippers	6.95
Scart Plugs	2.95
Scart Leads	3.50
TAB1 Car Battery Leads/port. TV Thom 1690/91	4.47
TA51 Car Battery Leads/port. TV Thom 1613/1615	3.66
Car Battery Leads/port. TV Philips	3.95
Universal Car Accessory Cable	1.99
Dynascan 467 Rejuv.	399
Dynascan 470 Testers	299
B+K tube bases Dynascan	
No. 1	9.09
No. 3	9.50
No. 5	9.09
No. 6	11.08
No. 7	9.09
No. 8	10.08
No. 9	9.09
No. 13	11.11
C15 computer cass.	30
C20 computer cass.	33
5 1/4" floppy disc s/s s/d	1.61
2M Fly Lead	70
4M Fly Lead	1.20
10M Fly Lead	1.90
Figure 8 Mains Lead	62
Computer to TV	97
7 pin din to 5 pin din	98
5 pin din to 5 pin din	98
Fluorescent Starter 4-80W)	15p
Tinned Copper Wire	
14SWG 100 Amp	1.86
17SWG 60 Amp	1.86
19SWG 45 Amp	1.86
20SWG	2.75
22SWG 25 Amp	1.86
Insulated Copper Wire (0.4mm dia.)	9.11
Battery Press Studs Min. Std.	11

LOCKING CABLE TIES	
Up to 25mm diameter,	100 at 54p
Up to 55mm,	100 at £1.41

SOCKETS ELECTRICAL BA	
320A Single Gang	1.30
320B Single Switched	1.95
320C Two Gang	2.52
320D Two Switched	3.93

SWITCHES	
320E One Gang/One Way	80
320F One Gang/Two Way	1.05
320G Two Gang/Two Way	1.78

CABLES 100m	
F031 2 Core Round .75mm ²	15.47
F032 3 Core Round .5mm ²	15.75
F035 3 Core Round 1.25mm ²	28.21
F041 Speaker 7/0 2mm	3.90
Coaxial 75R	13.50

FILAMENT LAMPS	
HES ROUND BULBS 15p	
L23m x 0.11mm	
6.3V 0.3A	
12V 2.2W	
LILLIPUT (L.E.S.) BULBS 12p	
L20m x 0.5mm	
6V 0.025A	
12-14V 0.1A	
CAPLESS LAMPS 28p	
L11mm x 0.4m	
6V 0.04A	
12V 0.04A	
TUBULAR LAMPS CAPPED 31p	
L31mm x 0.6.3mm	
6.3V 0.15A	
6.3V 0.25A	
6.3V 0.3A	
8V 0.15A	
8V 0.25A	
8V 0.3A	
12V 0.15A	
12V 0.25A	
12V 0.2A	

WIRE ENDED LAMPS	
WIRE ENDED LAMPS 25p	
D3 2mm	
6V 0.04A	
8V 0.04A	
12V 0.04A	
14V 0.025A	
14V 0.04A	
D4 2mm	
4.5V 0.06A	
6V 0.06A	
6.3V 0.025A	
6.3V 0.08A	
8V 0.04A	
8V 0.06A	
8V 0.08A	
12V 0.04A	
12V 0.06A	
14V 0.06A	
14V 0.08A	

TUBULAR LAMPS (Wire ended) 31p	
L22m x 0.4.25m	
3V 0.06A	
6V 0.05A	
8V 0.05A	
9V 0.045A	
12V 0.05A	
14V 0.05A	

PLUGS AND SOCKETS	
5 pin DIN plugs 180°	20
5 pin DIN chassis sockets 180°	28
5 pin DIN line sockets 180°	28
5 pin DIN plugs 360°	28
5 pin DIN chassis sockets 360°	28
5 pin DIN line sockets 360°	28
6 pin DIN plugs	28
6 pin DIN chassis sockets	36
6 pin DIN line sockets	28
7 pin DIN plugs	35
7 pin DIN chassis sockets	36
7 pin DIN line sockets	30
8 pin DIN plugs	56
8 pin DIN chassis sockets	54
8 pin DIN line sockets	55
Phono plugs	12
Phono chassis sockets	10
Phono line sockets	20
2.5mm Jack plugs	11
2.5mm Chassis sockets	14
2.5mm Line sockets	17
3.5mm Jack plugs	15
3.5mm Chassis sockets	24
3.5mm Line sockets	18
3.5mm Stereo jack plugs	35
3.5mm Stereo chassis sockets	18
3.5mm Stereo line sockets	28
6.3mm Stereo jack plugs	36
6.3mm Stereo jack line sockets	25
Standard mono jack plugs	20
Loud speaker plugs 2 pin	10
I.D.C. plugs 36 conn.	5.90
I.D.C. sockets 36 conn.	6.90
BNC plugs	1.15
Coax plugs	Each 1.80
Pack of ten	1.80
Line connectors	16
Double ended female sockets	1.20
Car aerial plugs	1.30
PL259 with reducer	1.80
Reducers for the PL259	16
FM plugs	25
Crocodile Clips	25
In Line Socket (Metal)	25
Banana Plug	60
Banana Socket	60

We have a fully equipped computer store - Come and visit us -

VIDEO PINCH ROLLERS	
PANASONIC NV7000	4.35
PANASONIC NV8300-333-370-777	4.35
SANYO VTC9300-VBS7000	4.35
SONY C7-J7-SL77	4.35
JVC TCE 3V00-01-06-16-23-24	
JVC HR2200-3320-3330	
3660-1100-7700	4.35
AKAI VS9700	4.35
HITACHI VT5000	4.35
SHARP VC6300-6500	4.35

VIDEO BELT KITS	
VEKIT 1 AKAI VS9300-VS9500 VS9800	
JVC HR3330/HR3320/HR3330/HR3360	
TCE 8903.3V00.3V16.3V22	3.50
VEKIT 2 PANASONIC NV7000B/NV7200B	3.00
VEKIT 3 SONY SLC5E-SLC5SA-SLC5CH-SLC5E1-SLC7E	
SLC7UB-SLC7EC-SLC7F-SLC7:	
VEKIT 4 SONY SLC5-SLC7-SLT9MER: SL8000AS:SL8000E: SL8000SA: SL8000UB:SL8000AH: SL8500: SL8600:SL8600A: SL3000UB	3.75
VEKIT 5 SONY NV3000B	4.50
VEKIT 6 PANASONIC 9300P	4.00
VEKIT 7 PANASONIC NV2000B	4.25
VEKIT 8 PANASONIC NV8608:NV8610B: V011	3.75
VEKIT 10 TOSHIBA V8600	4.25
VEKIT 11 SHARP VC7300	3.00
VEKIT 12 SHARP VC6300/VC6600	3.50
VEKIT 13 SANYO VTC5300	4.00
VEKIT 14 SANYO VTC5300	1.95
VEKIT 15 JVC HR7650	2.50
VEKIT 19 HITACHI VT8000	2.50
VEKIT 20 HITACHI VT11/33	1.12
VEKIT 21 HITACHI 9500	1.12

VIDEO IDLER TYRES	
SONY 23.7 17.4 4.9	50p
SONY 24.2 18 5.1	50p
HITACHI 31.8 25 4.9	52p
HITACHI 39.5 30 4.2	52p
PANASONIC 37 27 3.9	52p
PANASONIC 34.5 27 3.1	50p
AKAI 26 20 3.9	50p
JVC 32.8 3.4 3.9	56p
JVC 23.9 4.8 4	56p

REPAIR KITS	
Remote control handsets for Philips sets KT/3 K30 chassis inc. foil unit button matrix and instructions.	
Philips part numbers:	
Foil 212 275 82 or 212 275 83	
212 275 82 or 432 370 37 or 432 370 38.	
Button matrices: 432 370 37 or 432 370 38.	
No. 1 without Teletext,	
No. 2 with Teletext	£4.50

REMOTE CONTROL HAND UNITS	
Some are original some are compatible types.	
DECCA 100/101 US Non T. Text	US8513 23.80
GRUNDIG TELEPILOT 12 IR	RTP20 13.87
GRUNDIG TELEPILOT 8 IR	RTP05 25.10
GRUNDIG TELEPILOT 160 IR	RTP06 25.10
GRUNDIG TELEPILOT 300 IR	RTP07 18.87
PHILIPS G11 US Non Text	US8253 22.00
PHILIPS G11 8 way IR Text	IR8435 23.80
PHILIPS G11 US 31 Button	69117187 27.00
PHILIPS G11 US 2 function	US8518 21.00
PHILIPS KT3/30 IR Text 1234	IR1234 19.87
PHILIPS KT3/30 IR Non Text 1201	IR1201 19.87
THORN TX10/JVC IR Text	TP8431R 22.00
Remote Control Tester	29.94

DATA BOOKS (Zero VAT)	
Pair of A-2/2N2S TV180	8.50
LIN IC Books (data only not Equiv.) LINI	5.95
IC equivalent booklet £3.25 and transistor equivalent booklet £3.25	
TDV1 Trans. Data Dictionary	7.50

TURNTABLE DRIVE BELTS ALL £1.20	
TB42 Most Thornes Models	25
TB23 Most Philips Models	25
TB50 Most Garrard Models	25
TB70 Most Hitachi Models	60
TB60 Some Sanyo Models	60
TB01 Most Panasonic, Sony, Pioneer, Technics and Sansui.	25
TB03 Most BSR	25

SUNDRY VIDEO ACCESS.	
VHS Drum Motor	25.50
VHS Capstan Motor	25.50
Sanyo 5000 Reel Motor	12.95
VHS Idler	5.95
Video Lamps	1.41
3V23 Lamps with Plug	1.95
Video Care Kit	3.50
Universal Copying Kit	5.50
Video Head Cleaner	9.00
Sharp Reel Motor	15.60
Reel Idler (Sharp)	2.48
381/383/386/9100/9300/9500 Sanyo Reel Drive Pulley	6.95
Hitachi Idlers	3.50

VIDEO HEADS	
3HSS UHS	30.00
4HS VHS	31.00
PS3B Beta/Sony	35.00
Philips V2000	64.00
Philips 1700	64.00
Sanyo 9300/9455/9500	53.00
Sanyo 5000/5300/5400	53.00
Toshiba V5470A BDP	52.50
Toshiba 9600 Upper Ass.	10.00
Toshiba 9600	50.00
Sharp 2300	58.00
Sharp 6300	58.00
Sharp 7300/7700/7750	58.00
Sharp 8300	58.00
Sharp 3300/9700	56.00
Hitachi H1V1	35.62
Hitachi VT33E/GEC 4004	35.62
Hitachi VT11/GEC 4100	35.62
Beta eccentricity gauge	55.00

VIDEO TAPE	
SKC E180	2.90
L750	3.20
Scotch E30	3.66
E60	4.00
E120	3.24
E180	3.86
Beta L750	5.22
VCC 240 White	6.20
360 Stocks	6.33
480 Last	7.23
LVC 1700) Philips 1200	17.50

NEW LABGEAR	
* CM7271-MHA 15db	8.66
* CM7274 4 Way Dist.	21.45
* CM7082 UHF VHF DA	65.69
* CM7080/10 UHF NHA	15.71

SERVICE AIDS	
SERVISOL Freeze-It	1.20
SUPER SERVISOL	1.04
SERVISOL Foam Cleanser	1.02
SERVISOL Plastics Seal	1.14
SERVISOL Silicone Grease	1.30
SERVISOL Tubes Silicone Grease	1.66
SERVISOL Aero Kiene	94
SERVISOL Aero Duster	1.28
SERVISOL Excel Polish	96
SERVISOL Video Head Cleanser	90
Super 40	3.66
Fire Extinguisher 640G	1.08
Heat Sink Compound 25G	1.10
Silicone Rubber Tube 110G	2.98
Solda Mop standard reel	77

EVER READY BATTERIES	
R20S	39
R6B	15
R14S	33
R03B	18
PP3B	54
PP3S	74
PP6	1.15
PP7	1.15
PP9	1.17
1289	63

RECHARGEABLES Ever Ready	
RX6 (HP7)	1.31
RX14 (HP11)	2.31
RX20 (HP2)	2.61
RX22 (PP3)	4.89
Universal Charger	7.50

WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER AERIAL EQUIPMENT	
Outdoor Splitter	5.50
Plastic Tape	50
F.M. Plugs	25
Set Top Aerial	2.30
Loop Aerial	1.00
Attenuator 6dB, 12dB, 18dB	1.80
27MHz Filter 50dB	2.10
Cable Clips 7mm	per 100 1.18
Single Outlets	80
Surface Splitter	1.70
A Splitter	70
100M Coax	15.00
Coax Plugs	per 10 1.80
1" U Bolts	3.30
J Bolts	25

ANTIFERRECE	
SB11 Splitter	2.37
COB11 Outlet	.96
CS1000 Combiner/Splitter	6.15
PU1240 Power Unit	11.65
UP1300 MHA	9.09
XS2U Xraset	14.56
4 way VHF/UHF Amp	40.71
6 way VHF/UHF Amp	50.68
XG8 High Gain Aerial A-B-CO-WB	17.10

LABGEAR	
CM7261 Power Unit 12V	11.80
CM7262 Reg. Power Unit 12V	12.86
CM7065 VHF/UHF MHA W/B 12V	15.05
CM7066	14.04
CM7067 UHF 12V MHA (Specify A-B or C/D)	11.25
CM7068 UHF 12V MHA High Gain (Specify A-B or C/D)	16.74
CM7253 Behind Set UHF Amp. (Mains)	13.66
CM7243 Second Set Amp. UHF	12.72
CM7093 Behind Set UHF Amp. 3 Sets	16.03
CM7063 Dist. Amp. VHF/UHF 17db/output 12V	23.27
CM7108 VHF/UHF 8+1 Dist. Amp. 43.26	
CM9700 27mhz CB Suppress.	4.45
CM6011 Outdoor Splitter (2 way W/B)	7.83
CM9003 Flush Single Outlet	1.95
CM9010 Flush Twin Outlet	2.04
CM9034 UHF Group Filters with DC Through Pass (state A/B/C/D)	8.07
CM9033 6 Way Passive Splitter	9.72
CM7042 TV Games Combin.	3.09
CM9009 Flush TV/FM Outlet	3.20
CM7091 Col. Bar Gen.	133.98
CM9006 VHF/UHF Diplexer	3.78
Televeta up converta CM7122	36.20
Televeta down converta CM7057	41.01
7064 DA UHF VHF 28dB	30.06
7094 DA 4 way	19.50

ANTEX SOLDERING EQUIPMENT	
C15W Iron 240V	6.20
C240 Element	2.75
Bits 102	1.10
106	1.10
820	1.10
821	1.10
CS17W Iron 240V	6.40
CS240 Element	2.75
Bits 1100	1.10

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US

G.G.L. COMPONENTS

108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY
PHONE (0228) 20358/39693

BUY WITH

E.H.T. TRAYS

DECCA 80	7.20
DECCA 100	7.35
ITT CVC 20/30	6.85
PHILIPS G8-550	7.90
PHILIPS KT3	7.95
RBMT20/T2A	7.35
THORN 8500/8800	7.60
THORN 9000	8.70
Universal	5.95

INTEGRATED CIRCUITS	TYPE	PRICE (£)
AN214	STK0039	6.45
AN301	STK0040	5.95
AN303	STK0050	7.50
AN305	STK077	7.25
AN7110	STK078	7.45
AN7114E	STK082	9.75
AN7115	STK2129	8.50
AN7116	STK415	9.66
AN7145	STK430	7.75
BA312	STK432	5.95
BA511A	STK435	6.50
BA532	STK437	7.25
BA536	STK439	7.55
HA1166	STK441	8.50
HA1322	STK459	7.35
HA1338	STK461	9.95
HA1339	STK465	9.95
HA1342A	TA7193P	4.30
HA1366 WWR	TA7204P	1.90
HA1374	TA7205AP	1.40
HA1377	TA7208P	1.95
HA1388	TA7222AP	1.85
HA1397	TA7223P	2.85
LA1201	TA7227P	2.95
LA1230	TA7310	1.55
LA1365	TA7313	1.45
LA3350	TA7510	4.3
LA4101	TBA120AS	95
LA4102	TBA120SB	90
LA4400	TBA120T	1.25
LA4430	TBA120U	1.00
LA4440	TBA520	1.30
LA4445	TBA530Q	1.00
LA4460	TBA540	1.37
LA4461	TBA550	2.45
LA4462	TBA560	1.60
MB3712	TBA720A	2.65
MB3713	TBA750	2.45
ML2318	TBA800	.80
ML232B	TBA810	1.35
SA11250	TBA820	1.40
SA11251	TBA890	2.95
SAA5010	TBA920	1.50
SAA5012	TBA950	2.65
SAF1032P	TCA270	1.55
SAF1033P	TCA940	1.55
SAS560S	TDA2030	1.95
SAS570S	TDA2190M	6.95
SAS580S	TDA2576A	3.95
SAS590S	TDA2577	4.85
SL1430	TDA365IAQ	3.75
SL1432	TDA3652	4.35

TYPE	PRICE (£)
TDA440	3.25
TDA1006A	2.95
TDA1035T	2.75
TDA1037	1.95
TDA1044	3.10
TDA1170	1.80
TDA1270	2.20
TDA1470	3.65
TDA2002	1.85
TDA2003	2.33
TDA2004	3.15
TDA2006	2.25
TDA2020	2.95
TDA2522	1.80
TDA2523	2.25
TDA2530	2.10
TDA2532	2.20
TDA2540	1.95
TDA2560	1.80
TDA2578A	3.25
TDA2581	2.15
TDA2582	2.20
TDA2591	2.30
TDA2593	2.30
TDA2594	2.95
TDA2600	6.35
TDA2611A	1.50
TDA2640	2.40
TDA2650	5.10
TDA3561A	5.35
TDA3562A	5.50
TDA4500	5.85
TDA4600	2.85
TDA4600-16PIN	3.95
TDA9503	2.35
UPC555C	.70
UPC566C	2.10
UPC585C	1.40
UPC1031H	2.95
UPC1032H	.95
UPC1156H	2.45
UPC1181H	2.20
UPC1182H	2.20
UPC1185H	3.30
UPC1230H	3.95
UPC1238H	2.35
UPC1350C	4.50
UPC1353C	2.60
UPC1365C	5.05
UPC1394C	2.95
UPC2002H	1.85
7805	0.65
7812	0.65

TRAN-SISTORS	TYPE	PRICE
BC107	BD701	.85
BC108	BD707	1.05
BC109	BF337	.28
BC141	BF338	.30
BC142	BF458	.30
BC143	BF459	.36
BC147	BF757	.75
BC148	BFR90	1.60
BC157	BR100	.18
BC158	BR101	.32
BC159	BR103	.55
BC237	BR303	2.95
BC327	BT106	1.15
BC328	BT116	1.30
BC337	BT151/	1.10
BC338	800R	1.10
BC547	BU126	1.78
BC548	BU205	1.42
BC557	BU208A	1.45
BC558	BU208D	1.85
BC637	BU326A	1.48
BC638	BU407	1.12
BC639	BU407D	1.45
BD124M	BU500	1.95
BD131	BU508A	1.95
BD132	BU526	2.00
BD222	BU807	1.30
BD225	BU826A	3.20
BD235	R2010B	1.45
BD236	R2540	2.35
BD237	TIP31C	.46
BD238	TIP32C	.47
BD410	TIP33	.80
BD437	TIP34	.95
BD438	TIP41C	.48
BD439	TIP42C	.48
BD677	TIP47	.75
	TIP2955	70
	TIP3055	70

TYPE	PRICE
2N3055	.50
2N3773	3.45
1580H	2.25
1585R	2.25
2SA 771	2.35
2SA 835	1.55
2SB 618	2.45
2SC 867A	3.25
2SC 1034	4.85
2SC 1061	1.15
2SC 1114	4.75
2SC 1124	.97
2SC 1316	3.20
2SC 1413A	3.95
2SC 1739	2.45
2SC 1942	2.95
2SC 1962	1.65
2SC 1969	1.95
2SC 2078	1.55
2SC 2335 (Kit)	7.55
2SC 2369	3.25
2SC 257	2.45
2SD 588A	1.97
2SD 725	7.95
2SD 870	5.95

THORN/SONY

LARGE RANGE OF SPARES FOR ABOVE MAKES OF TV/VIDEOS INCLUDING INSTRUCTION AND SERVICE MANUALS. PHONE OR WRITE FOR NEW LISTS. WE CAN ALSO SOURCE & SUPPLY OVER THREE THOUSAND I/Cs & SEMI CONDUCTORS.

SONY SPARES

C5/C7 Rewind Kit... 4.65
C5/C7 Belt Kit... 3.50
C6 Rewind Kit... 4.35
C7 Pinch Roller... 4.85
SG 613/6533... 8.95
CX 143A... 6.95
TDA 3652... 4.35

Large range of Sony spares available

VALVES

PCF802... 1.09
PCL82... 1.07
PCL85... 1.93
PCL86... 1.07
PL504... 1.59
PL508... 2.99
PL509/519... 5.99
PY500A... 2.25

LINE O/P TR.

DECCA 80... 7.95
DECCA 100... 8.50
ITT CVC 20... 8.85
ITT CVC 25/30/32... 8.95
ITT CVC 45... 8.45
PHILIPS G8... 8.75
PHILIPS G11... 13.50
PHILIPS KT3... 9.95
PHILIPS K30... 16.50
RBM T20A... 10.35
THORN 1615... 12.35
THORN 1690/1... 9.85

TV ELECTROLYTICS

DECCA 30(400/400)350V... 3.99
DECCA 80-80/100(400)350V... 3.99
(800)250V... 2.65
PHILIPS G8(600)300V... 3.99
PHILIPS G9(2200)63V... 1.45
PHILIPS G11(470)250V... 2.20
RBM A823(2500/2500)30V... 1.65
RBM T20A(220)400V... 2.35
THORN 1690/1(4700)25V... .94
THORN 3500(1000)70V... .99
THORN9000(400)400V... 3.10

PUSH BUTTONS/NEW TUNERS

DECCA/ITT 6 way... 8.50
PHILIPS G8 S/L... 14.90
PHILIPS G8 S/O... 14.75
PYE-G11 P/B... 8.50
HITACHI 4 way... 8.95
ITT CVC5 7 Button... 10.40
ITT CVC8/9... 12.80
1043/05... 8.95
U321... 8.75
U322... 7.40

Available also a range of 2SA/B/C/D Transistors. Phone or write for lists.

ORDERING

Please Add 50p For P/P U.K.
Add 15% VAT To This Total.
Export Orders - Cost.
DELIVERY BY RETURN ON ALL STOCK ITEMS.

P. V. TUBES

104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.
Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

WE CAN NOW SUPPLY ON AN EXCHANGE "HEAD FOR HEAD" BASIS

ONLY £22 + VAT inc P&P

Newlife VIDEO HEADS

THORN EMI VIDEO HEAD UPPER DRUM ASSEMBLIES				
ORDER FROM 3 VHS TYPES				
	(L)	or (J)	or (M)	
JVC MODELS	HR 3660 HRD 110 HR 7650 HRD 120 HR 7700	HR 7200 HR 7300 HR 7350	HR 3320 HR 3300 HR 3330 HR 4100	
AKAI MODELS	VS 9700 VP 77 VS 9800		VS 9300	
FERGUSON MODELS	3V16 3V31 3V23 3V35 3V24 3V36 3V38 3V39 3V49	3V29 3V30	3V01 3V00 3V22 3292	
BAIRD MODELS	8904 8943 8924 8944 8941	8930 8940	8900 8928 8902 8922	
DECCA MODELS	8400 8500	8300		
TATUNG MODELS	8400	8300		
I.T.T MODELS	VR3605 VR3905	VR3913		

SEND YOUR OLD HEAD PACKED UP CAREFULLY AND WE WILL SEND AN EXCHANGE ONE BY RETURN POST

P.V. NAMES TO TRUST

New Life Upper Drum Assemblies have been thoroughly life tested and carry a 12 month guarantee covering normal domestic use.

Universal Semiconductor Devices Ltd.

17 GRANVILLE COURT, GRANVILLE ROAD, HORNSEY, LONDON N4 4EP, ENGLAND.
TEL 01-348 9420/9425 * TLX. 25157 usdco g

WE OFFER ONE OF THE LARGEST RANGES OF SEMICONDUCTORS AT HIGHLY ECONOMICAL PRICES. THE FOLLOWING SEMICONDUCTOR TYPES ARE AVAILABLE FROM STOCK. IF WE DON'T STOCK WHAT YOU NEED THEN WE CAN GET IT FAST FROM OUR FACILITIES IN WEST GERMANY AND USA UPON REQUEST.

TRANSISTORS - BIPOLARS - GERMANIUM AND SILICON
SMALL SIGNAL POWER
DARLINGTONS - ALL SHAPES AND SIZES
VHF/UHF DEVICES - ALL SHAPES AND SIZES

FETS - POWER MOSFETS
UNIUNCTIONS

DIODES - GERMANIUM AND SILICON
RECTIFIERS AND BRIDGES
OPTO-ELECTRONIC DEVICES
LEDS OF ALL SHAPES AND SIZES

THYRISTORS AND TRIACS - ALL SHAPES SIZES RATINGS

INTEGRATED CIRCUITS:
CONSUMER - DIGITAL/ANALOGUE
MICROPROCESSORS AND PERIPHERALS
IC SOCKETS

MAIL ORDER CUSTOMERS: PLEASE SEND FOR OUR COMPREHENSIVE PRICE LIST, ENCLOSING £1.00 IN STAMPS, CHEQUE OR POSTAL ORDER.

CATALOGUE SENT FREE OF CHARGE, WHEN REQUESTED ON OFFICIAL LETTERHEAD (WITHOUT REFUND), TO OEM'S, SCHOOLS, COLLEGES, UNIVERSITIES, GOVERNMENT INSTITUTIONS, COMPUTER FIRMS, ELECTRONIC REPAIR FIRMS AND DISTRIBUTORS.

SPECIAL DISCOUNTS AND PAYMENT TERMS ARE AVAILABLE TO ABOVE INSTITUTIONS.

PLEASE ENQUIRE FOR QUANTITY DISCOUNTS.
WE WELCOME TELEPHONE AND TELEX ENQUIRIES!

JAPANESE COMPONENTS

VAST RANGE HELD OF DISCRETES & CONSUMER IC'S

HUSSAIN CENTRAL TV LTD

SALE SALE SALE OF THE CENTURY

BEST QUALITY AT THE LOWEST PRICES IN BRITAIN TODAY

G11 · 660	£25	ITT CVC 20/30	£15
PYE G11	£30	DECCA 80/100	£15
G11 REMOTE (with hand set)	£45	ITT REMOTE (with hand set)	£30
G11 TEXT (with hand set)	£55	TX TEXT (with hand set)	£55
G11 ELECTRONIC TUNER	£30	THORN 9000 REMOTE	£15
THORN 9600	£25	THORN 9200	£27
THORN 8800	£10	THORN 9800	£15
PYE 222	£10	G8 22"	£10
GEC SOLID STATE	£10	GEC STARLINE	£15

**MANY MORE LATE MODEL TVs IN STOCK INC.
REMOTE, TEXT, STEREO TEXT AND 14", 16" PORTABLES**

All TVs have excellent cabinets

VHS: Working. Bring your own tape and try them yourself at **£65**

Untested Electronic VHS £90

Working Electronic VHS £135 Ferguson 3V29, Hitachi 8000, J.V.C. 7200

ALSO IN STOCK

PANASONIC 7200, 7000, 2000, 2010, 366, NV777

HITACHI VT14, VT11, 9700, 9500, 8700, 8500, 8300

FERGUSON 3V31, 3V30, 3V23

ELECTRONIC Beta Full working £60

Untested Beta from £35

PLUS MANY MORE LATE MODEL VIDEOS IN STOCK

Prices are subject to 15% VAT

*Deliveries arranged on quantity or call at our branches
for fast and friendly service from the professionals*

BIRMINGHAM
48-52 PERSHORE ST.
021-622 1023
021-622 1517

PRESTON
UNIT 439
OAKSHOTT PLACE
WALTON SUMMIT IND. EST.
M6 JUNCTION 29.
0772 312101


LONDON
CEDAR HOUSE
NOBEL RD.
ELEY ESTATE
EDMONTON N18 3BH.
01-807 4090
01-884 1314

CHEPSTOW
UNIT 4
BULWARK IND. EST.
GWENT.
0291 271000

LINEOUT TRANSFORMERS		VALVES		REMOTE CONTROL UNITS		PUSH BUTTON UNITS		MIXED DIELECTRIC CAPACITORS		SOUND CONTROLS		PRESETS	
3600 DECCA 100	7.95	4666 ELC 104306 EXCH TUNER	6.00	4000 DECCA 100 NONTXRC RCU	21.50	11.00 2870 4 WAY DECCA ETC	0.25	4272 0.022 1KV X5	1.95	4883 10K LIN STD TV	0.55	4877 4K7 LOG STD TV	0.55
3601 DECCA 110	9.00	4667 ELC 104306 NEW TUNER	12.50	4010 DECCA 100 (TEST+PREST) RCU	9.50	11.00 2871 6 WAY DECCA ETC	0.25	4273 0.033 1KV X5	1.40	4884 150K LIN STD TV	0.55	4878 4K7 LOG STD TV	0.55
3604 DECCA 1730/1830	9.00	4972 ELC 2003 EXCH TUNER	12.50	4314 DECCA 100 (TEST+PREST) RCU	9.50	11.00 2872 8 WAY DECCA ETC	0.25	4274 0.047 600V X5	1.40	4885 150K LIN STD TV	0.55	4879 4K7 LOG STD TV	0.55
3599 DECCA 80	7.50	5534 GEC 2100 TYPE REPAIR CHGE	10.25	4315 DECCA 800 SERIES RCU	11.45	11.00 2873 10 WAY DECCA ETC	0.25	4275 0.047 1KV X5	1.20	4886 150K LIN STD TV	0.55	4880 22K LIN STD TV	0.55
3727 DECCA MS1700-2420	10.13	5535 PHILIPS GX EXCHANGE TUNER	7.25	4316 DECCA 800 SERIES RCU	11.45	11.00 2874 12 WAY DECCA ETC	0.25	4276 0.1 600V X5	1.20	4887 22K LOG STD TV	0.55	4881 22K LOG STD TV	0.55
3729 FIDELITY TV1721/VR120	5.50	4673 RRI RANGER/2 EXCH TUNER	9.75	4317 DECCA 800 SERIES RCU	11.45	11.00 2875 14 WAY DECCA ETC	0.25	4277 0.1 1KV X5	2.00	4888 22K LOG STD TV	0.55	4882 22K LOG STD TV	0.55
5328 FIDELITY ZX3000 ZZ	14.50	4680 RRI 720 NEW TUNER	12.40	4318 DECCA 800 SERIES RCU	11.45	11.00 2876 16 WAY DECCA ETC	0.25	4278 0.1 2KV X5	0.75	4889 22K LOG STD TV	0.55	4883 22K LOG STD TV	0.55
5308 FIDELITY ZX2000/3000	14.50	4678 RRI EXCH NEW TUNER	6.50	4319 DECCA 800 SERIES RCU	11.45	11.00 2877 18 WAY DECCA ETC	0.25	4279 0.2 2KV X5	1.40	4890 22K LOG STD TV	0.55	4884 150K LIN STD TV	0.55
3732 GEC 2100/2440	5.50	4681 U321 EXCH NEW	6.25	4320 DECCA 800 SERIES RCU	11.45	11.00 2878 20 WAY DECCA ETC	0.25	4280 0.2 600V X5	1.40	4891 22K LOG STD TV	0.55	4885 150K LIN STD TV	0.55
3731 GEC 2100	3.50	4670 U322 EXCHANGE TUNER	6.50	4321 DECCA 800 SERIES RCU	11.45	11.00 2879 22 WAY DECCA ETC	0.25	4281 0.2 1KV X5	1.20	4892 22K LOG STD TV	0.55	4886 150K LIN STD TV	0.55
3734 GEC 3133	3.50	4669 U323 NEW TUNER	7.95	4322 DECCA 800 SERIES RCU	11.45	11.00 2880 24 WAY DECCA ETC	0.25	4282 0.4 1KV X5	1.00	4893 22K LOG STD TV	0.55	4887 4K7 LOG STD TV	0.55
3733 GEC M1201/M1501H	13.25	4673 U324 EXCHANGE TUNER	7.25	4323 DECCA 800 SERIES RCU	11.45	11.00 2881 26 WAY DECCA ETC	0.25	4283 4700P 1.5KV X5	1.80	4894 150K LIN STD TV	0.55	4888 22K LOG STD TV	0.55
3614 GRUNDIG 5010/6100/ETC	12.95			4324 GEC 2114 VOL+SWITCH CONT	7.25	11.00 2882 28 WAY DECCA ETC	0.25	4271 0.01 1KV X5	1.20	4895 150K LIN STD TV	0.55	4889 22K LOG STD TV	0.55
3755 INDEBIT 24E/G	12.95			4656 GEC 22K MULTI TURN POT	4.65	11.00 2883 30 WAY DECCA ETC	0.25	4272 0.022 1KV X5	1.95	4896 150K LIN STD TV	0.55	4890 22K LOG STD TV	0.55
3617 IIT CV30	11.25					11.00 2884 32 WAY DECCA ETC	0.25	4273 0.033 1KV X5	1.40	4897 150K LIN STD TV	0.55	4891 22K LOG STD TV	0.55
3618 IIT CV45	9.75					11.00 2885 34 WAY DECCA ETC	0.25	4274 0.047 600V X5	1.40	4898 150K LIN STD TV	0.55	4892 22K LOG STD TV	0.55
3615 IIT CVCS-8	10.25					11.00 2886 36 WAY DECCA ETC	0.25	4275 0.047 1KV X5	1.20	4899 150K LIN STD TV	0.55	4893 22K LOG STD TV	0.55
3620 KORTING A21100 90° HYBRID	14.95					11.00 2887 38 WAY DECCA ETC	0.25	4276 0.1 600V X5	1.20	4900 150K LIN STD TV	0.55	4894 150K LIN STD TV	0.55
4508 PHILIPS E2 CHASS	10.00					11.00 2888 40 WAY DECCA ETC	0.25	4277 0.1 1KV X5	2.00	4901 150K LIN STD TV	0.55	4895 150K LIN STD TV	0.55
2862 PHILIPS G9	10.35					11.00 2889 42 WAY DECCA ETC	0.25	4278 0.1 2KV X5	0.75	4902 150K LIN STD TV	0.55	4896 150K LIN STD TV	0.55
5305 PVE 691 W/REO	5.00					11.00 2890 44 WAY DECCA ETC	0.25	4279 0.2 2KV X5	1.40	4903 150K LIN STD TV	0.55	4897 4K7 LOG STD TV	0.55
3628 PVE 725 90°	5.00					11.00 2891 46 WAY DECCA ETC	0.25	4280 0.2 600V X5	1.40	4904 150K LIN STD TV	0.55	4898 22K LOG STD TV	0.55
3629 PVE 731 110°	8.95					11.00 2892 48 WAY DECCA ETC	0.25	4281 0.2 1KV X5	1.20	4905 150K LIN STD TV	0.55	4899 22K LOG STD TV	0.55
3632 RANK A823	5.50					11.00 2893 50 WAY DECCA ETC	0.25	4282 0.4 1KV X5	1.00	4906 150K LIN STD TV	0.55	4900 22K LOG STD TV	0.55
3634 RANK T16A	3.50					11.00 2894 52 WAY DECCA ETC	0.25	4283 4700P 1.5KV X5	1.80	4907 150K LIN STD TV	0.55	4901 22K LOG STD TV	0.55
3636 RANK T20A	12.95					11.00 2895 54 WAY DECCA ETC	0.25	4271 0.01 1KV X5	1.20	4908 150K LIN STD TV	0.55	4902 22K LOG STD TV	0.55
3726 RANK T26A	12.95					11.00 2896 56 WAY DECCA ETC	0.25	4272 0.022 1KV X5	1.95	4909 150K LIN STD TV	0.55	4903 22K LOG STD TV	0.55
3637 RANK T179	11.25					11.00 2897 58 WAY DECCA ETC	0.25	4273 0.033 1KV X5	1.40	4910 150K LIN STD TV	0.55	4904 150K LIN STD TV	0.55
3639 RANK Z718 2Z	21.75					11.00 2898 60 WAY DECCA ETC	0.25	4274 0.047 600V X5	1.40	4911 150K LIN STD TV	0.55	4905 150K LIN STD TV	0.55
3770 REDIFUSION MK1 CHAS	9.38					11.00 2899 62 WAY DECCA ETC	0.25	4275 0.047 1KV X5	1.20	4912 150K LIN STD TV	0.55	4906 150K LIN STD TV	0.55
3771 REDIFUSION MK3 CHAS	14.95					11.00 2900 64 WAY DECCA ETC	0.25	4276 0.1 600V X5	1.20	4913 150K LIN STD TV	0.55	4907 4K7 LOG STD TV	0.55
3775 SANYO CT75101	16.50					11.00 2901 66 WAY DECCA ETC	0.25	4277 0.1 1KV X5	2.00	4914 150K LIN STD TV	0.55	4908 22K LOG STD TV	0.55
3643 THORN 1400 SERIES	5.95					11.00 2902 68 WAY DECCA ETC	0.25	4278 0.1 2KV X5	0.75	4915 150K LIN STD TV	0.55	4909 22K LOG STD TV	0.55
3644 THORN 1500 20"	5.95					11.00 2903 70 WAY DECCA ETC	0.25	4279 0.2 2KV X5	1.40	4916 150K LIN STD TV	0.55	4910 22K LOG STD TV	0.55
3645 THORN 1500 24"	5.95					11.00 2904 72 WAY DECCA ETC	0.25	4280 0.2 600V X5	1.40	4917 150K LIN STD TV	0.55	4911 22K LOG STD TV	0.55
3646 THORN 1500 SERIES	10.85					11.00 2905 74 WAY DECCA ETC	0.25	4281 0.2 1KV X5	1.20	4918 150K LIN STD TV	0.55	4912 22K LOG STD TV	0.55
3647 THORN 1615 SERIES	10.85					11.00 2906 76 WAY DECCA ETC	0.25	4282 0.4 1KV X5	1.00	4919 150K LIN STD TV	0.55	4913 22K LOG STD TV	0.55
3649 THORN 1650/91 SERIES	10.85					11.00 2907 78 WAY DECCA ETC	0.25	4283 4700P 1.5KV X5	1.80	4920 150K LIN STD TV	0.55	4914 150K LIN STD TV	0.55
3713 THORN 1780	8.95					11.00 2908 80 WAY DECCA ETC	0.25	4271 0.01 1KV X5	1.20	4921 150K LIN STD TV	0.55	4915 22K LOG STD TV	0.55
3714 THORN 3787	15.23					11.00 2909 82 WAY DECCA ETC	0.25	4272 0.022 1KV X5	1.95	4922 150K LIN STD TV	0.55	4916 150K LIN STD TV	0.55
3652 THORN 3K 3KS EHT TX	8.95					11.00 2910 84 WAY DECCA ETC	0.25	4273 0.033 1KV X5	1.40	4923 150K LIN STD TV	0.55	4917 4K7 LOG STD TV	0.55
3651 THORN 3K 3KS	8.95					11.00 2911 86 WAY DECCA ETC	0.25	4274 0.047 600V X5	1.40	4924 150K LIN STD TV	0.55	4918 22K LOG STD TV	0.55
6172 THORN 3K 3KS	7.95					11.00 2912 88 WAY DECCA ETC	0.25	4275 0.047 1KV X5	1.20	4925 150K LIN STD TV	0.55	4919 22K LOG STD TV	0.55
2868 PHILIPS KT3	10.95					11.00 2913 90 WAY DECCA ETC	0.25	4276 0.1 600V X5	1.20	4926 150K LIN STD TV	0.55	4920 22K LOG STD TV	0.55
						11.00 2914 92 WAY DECCA ETC	0.25	4277 0.1 1KV X5	2.00	4927 150K LIN STD TV	0.55	4921 22K LOG STD TV	0.55
						11.00 2915 94 WAY DECCA ETC	0.25	4278 0.1 2KV X5	0.75	4928 150K LIN STD TV	0.55	4922 22K LOG STD TV	0.55
						11.00 2916 96 WAY DECCA ETC	0.25	4279 0.2 2KV X5	1.40	4929 150K LIN STD TV	0.55	4923 22K LOG STD TV	0.55
						11.00 2917 98 WAY DECCA ETC	0.25	4280 0.2 600V X5	1.40	4930 150K LIN STD TV	0.55	4924 150K LIN STD TV	0.55
						11.00 2918 100 WAY DECCA ETC	0.25	4281 0.2 1KV X5	1.20	4931 150K LIN STD TV	0.55	4925 150K LIN STD TV	0.55
						11.00 2919 102 WAY DECCA ETC	0.25	4282 0.4 1KV X5	1.00	4932 150K LIN STD TV	0.55	4926 150K LIN STD TV	0.55
						11.00 2920 104 WAY DECCA ETC	0.25	4283 4700P 1.5KV X5	1.80	4933 150K LIN STD TV	0.55	4927 4K7 LOG STD TV	0.55
						11.00 2921 106 WAY DECCA ETC	0.25	4271 0.01 1KV X5	1.20	4934 150K LIN STD TV	0.55	4928 22K LOG STD TV	0.55
						11.00 2922 108 WAY DECCA ETC	0.25	4272 0.022 1KV X5	1.95	4935 150K LIN STD TV	0.55	4929 22K LOG STD TV	0.55
						11.00 2923 110 WAY DECCA ETC	0.25	4273 0.033 1KV X5	1.40	4936 150K LIN STD TV	0.55	4930 22K LOG STD TV	0.55
						11.00 2924 112 WAY DECCA ETC	0.25	4274 0.047 600V X5	1.40	4937 150K LIN STD TV	0.55	4931 22K LOG STD TV	0.55
						11.00 2925 114 WAY DECCA ETC	0.25	4275 0.047 1KV X5	1.20	4938 150K LIN STD TV	0.55	4932 22K LOG STD TV	0.55
						11.00 2926 116 WAY DECCA ETC	0.25	4276 0.1 600V X5	1.20	4939 150K LIN STD TV	0.55	4933 22K LOG STD TV	0.55
						11.00 2927 118 WAY DECCA ETC	0.25	4277 0.1 1KV X5	2.00	4940 150K LIN STD TV	0.55	4934 150K LIN STD TV	0.55
						11.00 2928 120 WAY DECCA ETC	0.25	4278 0.1 2KV X5	0.75	4941 150K LIN STD TV	0.55	4935 150K LIN STD TV	0.55
						11.00 2929 122 WAY DECCA ETC	0.25	4279 0.2 2KV X5	1.40	4942 150K LIN STD TV	0.55	4936 150K LIN STD TV	0.55
						11.00 2930 124 WAY DECCA ETC	0.25	4280 0.2 600V X5	1.40	4943 150K LIN STD TV	0.55	4937 4K7 LOG STD TV	0.55
						11.00 2931 126 WAY DECCA ETC	0.25	4281 0.2 1KV X5	1.20	4944 150K LIN STD TV	0.55	4938 22K LOG STD TV	0.55
						11.00 2932 128 WAY DECCA ETC	0.25	4282 0.4 1KV X5	1.00	4945 150K LIN STD TV	0.55	4939 22K LOG STD TV	0.55
						11.00 2933 130 WAY DECCA ETC	0.25	4283 4700P 1.5KV X5	1.80	4946 150K LIN STD TV	0.55	4940 22K LOG STD TV	0.55
						11.00 2934 132 WAY DECCA ETC	0.25	4271 0.01 1KV X5	1.20	4947 150K LIN STD TV	0.55	4941 150K LIN STD TV	0.55
						11.00 2935 134 WAY DECCA ETC	0.25	4272 0.022 1KV X5	1.95	4948 150K LIN STD TV	0.55	4942 150K LIN STD TV	0.55
						11.00 2936 136 WAY DECCA ETC	0.25	4273 0.033 1KV X5	1.40	4949 150K LIN STD TV	0.55	4943 150K LIN STD TV	0.55
						11.00 2937 138 WAY DECCA ETC	0.25	4274 0.047 600V X5	1.40	4950 150K LIN STD TV	0.55	4944 150K LIN STD TV	0.55
						11.00 2938 140 WAY DECCA ETC	0.25	4275 0.047 1KV X5	1.20	4951 150K LIN STD TV	0.55	4945 150K LIN STD TV	0.55
						11.00 2939 142 WAY DECCA ETC	0.25	4276 0.1 600V X5	1.20	4952 150K LIN STD TV	0.55	4946 150K LIN STD TV	0.55
						11.00 2940 144 WAY DECCA ETC	0.25	4277 0.1 1KV X5	2.00	4953 150K LIN STD TV	0.55	4947 4K7 LOG STD TV	0.55
						11.00 2941 146 WAY DECCA ETC	0.25	4278 0.1 2KV X5	0.75	4954 150K LIN STD TV	0.55	4948 22K LOG STD TV	0.55
						11.00 2942 148 WAY DECCA ETC							

How to teach your old remote new tricks

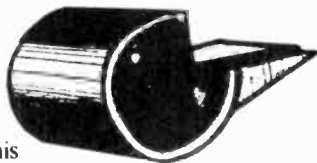The man who invented the Apple Computer has just discovered a way to make your TV and VCR remote controllers work better than ever.



He's Steve Wozniak and, at his new company, CL9, he needed to create a portable test device to improve those sluggish remote controllers. This test device became the world's first power booster.

With this brand new power booster, you should be able to operate your remote controller the way Steve could in his laboratory: From as far away as 40 and 50 feet. You'll no longer have to aim the controller carefully. The remote will now be able to bounce signals around obstacles. And very often it will work when aimed in the opposite direction.



This great power enhancer is called the **TYRON**. It works with almost all infrared remote controllers. It attaches without any tools to your present controller. And it even includes the great Duracell Alkaline 9-volt battery.

You can retail it now, for only **£19.95 inc. VAT.**

Generous terms for trade stockists.

Distribution in Europe by:

Advanced International Marketing (U.K.) Ltd.
74a Heath Road, Twickenham, TW1 4BW.
Tel: 01-891 3644. Telex: 946461



SWITCH ON TO PROFIT!

3,000 TV'S IN STOCK
MOST MAKES

Quality range of working TV's including Remotes and Teletext with Handsets. Mechanical & Electronic Videos

TELETEXT from £50
VIDEOS from £45

SUPERB RANGE OF WORKING VIDEOS

TRADE ONLY

NEW AND REGRADED TOP NAMES LOWEST PRICES

WITH MAKERS WARRANTY

Auto Washing Machines from £95
Washer Dryers from £120
Cookers from £160
Refrigeration from £90
Good Range of Built-In Appliances.



Incorporating MONITEC

NEW 16,000 sq. ft WAREHOUSE

UNIT 22, GREEN ST INDUSTRIAL ESTATE
GREEN ST, KIDDERMINSTER DY10 1HN
Telephone (0562) 741666 or 755526

City

FIRST IN TUBE REBUILDING TECHNOLOGY 30AX, 30AX, 30AX

LOOK! AT NO EXTRA COST, FIDDLE FREE 30AX REBUILDS.

WHY STRUGGLE WITH EXTERNAL MAGNETS TO OBTAIN CONVERGENCE AND PURITY. FIT OUR DIRECT REPLACEMENT.

QUALITY REBUILDS

SPECIAL OFFERS!
ON INLINE



Get on the hot-line today!

LOOK! NO EXT. POLE PIECES
30AX PRE CONVERGED

061
681 2959

most types of Inline Re-builds or new ex-stock
PRICES SUBJECT TO GLASS EXCHANGE

Delta Rebuilds

Up to 19" £28
Up to 22" £30
Up to 26" £34
110° up to 22" £34
110° up to 26" £38
Low focus +£2
A47 342 New £28
17FHP New £30
470EHB New £30
Delta only. Less 5% 5+

Inline Rebuilds

Up to 22" ... From £40
Up to 26" ... From £45
A56-540x £56
A66-540x £58
Bonded Coil +£5

ALL SIZES OF NEW AND REBUILT MONO TUBES AT COMPETITIVE PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

Please enquire types not listed

370 HFB-A37-590 £45	AXT 56-001 £62
370 HUB £45	660 AB £65
AXT 37-001 £45	A67-701 £65
420 CSB £45	670 CZB £65
420 EDB-A42-590 £45	A66-540 with coil £85
420 EZB £45	420FSB £55
420 ERB £45	
470 KUB £50	
510 UFB/A51-590 £55	
510 VSB £60	
AXT 51-001 £60	
560 DYB-560 DTB £62	
560 EGB £62	
560 CGB £62	
560 DMB £62	

MIN. CARRIAGE £5
10+ CARRIAGE PAID
TERMS
Cash with order
ALL PRICES
EXCLUSIVE OF VAT

QUANTITY DISCOUNT AVAILABLE
Ask for details

★ ASK FOR DETAILS. OUR TECHNICAL DEPT. WILL ADVISE YOU ON PROBLEMS YOU MAY ENCOUNTER ON FITTING INLINE TUBES


DELIVERY: Ex stock items immediate dispatch on receipt of order. Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST



CHROMOVAC LTD., PUMP STREET,
HOLLINWOOD, OLDHAM OL9 7LR

Ask for Mr Butterworth ON: 061-681 2959

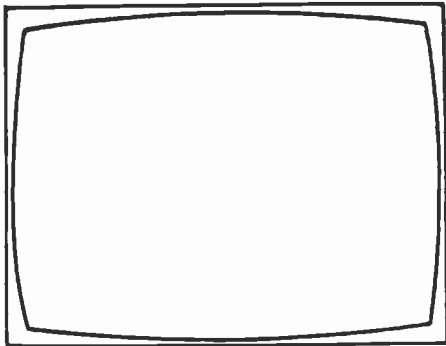

TELEVISION

Broadcasting Options

At the time of writing this, official publication of the report from the Peacock committee, set up by the previous Home Secretary to consider the future financing of broadcasting in the UK, is still a couple of days off. Not very helpful timing for us! There has nevertheless been a lot more leaking of the committee's conclusions. The report has been under consideration by a Cabinet subcommittee and it appears that disagreement amongst ministers has been the basis of the considerable press coverage that has appeared recently.

It seems that the report could instigate quite a lively public debate. In fact this could possibly be its main aim – to stir up discussion and see what comes of this, whether or not specific recommendations made in the report are adopted. Strong words have already appeared in the press. According to the *Financial Times*, the present Home Secretary feels that “the committee did not appear to have understood the nature of public service broadcasting, had gone beyond its brief and had produced a mixture of incompatible proposals that would offer very little obvious benefit to the public”. He has been asked to prepare a more diplomatic statement for the House of Commons.

What lies behind this dissension? As far as TV broadcasting is concerned the Peacock committee's views seem to envisage a three-phase development during the period up to the end of the century. In the first phase the BBC would be left to continue as at present, with its income tied to changes in the cost of living. ITV franchises would be put up for auction when they lapse. The second phase would see a strong move towards subscription services, with scrambled transmissions. It's emphasized that changes during this phase would depend on technological developments. Phase three would see a move towards consumer purchase of the individual programmes he wishes to view, a computerised credit card system being used for this purpose. While the Peacock committee makes definite recommendations for phase one it seems that its proposals for phases two and three are to be taken more as “possibilities which the government might care to consider”.

Going beyond its brief? Well, the committee was originally set up, in early 1985, to consider the future financing of the BBC. It seems to have come to the conclusion along the line that it should broaden its terms to take an overall look at all forms of broadcasting. This is no bad thing in itself. There was a strong feeling when the committee was set up that its main purpose would be to commercialise the BBC. In the event it decided to take a much broader view – and to recommend shelving the idea of advertising on BBC during phase one.

Phases two and three would depend on the technology available. Scrambling and signal decoding are nothing new, but the idea of computerised programme selection is. Whether this would have to rely on cable distribution or whether enabling signals could be transmitted to a receiver/decoder in the set is not clear. It looks as if we shall have to wait to see what's technically feasible.

The Peacock committee included members with strong “free-market” views, i.e. that things – in this case programmes – should be paid for separately by the consumer. There's been a move in this direction in many fields, for example the provision of pensions and health care and the privatisation of services such as the supply of water and gas. The question here is whether broadcasting is in some fundamental way different. Some members of the committee seem to have felt that the public should purchase programmes in the same way that it buys newspapers, books, cassettes and so on. There is certainly some logic in this, but while a wide range of newspapers, cassettes, etc. can be made available to the public with broadcasting we come up against the limited number of channels available. Given this limitation, the emphasis has to be on “public service” – making the best use of the available broadcasting time to provide the public with a balanced supply of programmes giving reasonable choice.

This of course is a difficult problem that can lead to some unpleasant conclusions. What is balanced programming and who is to decide? The reason that the BBC lost its original monopoly was to some extent public feeling that the BBC took an unduly paternalistic view of what the public should be offered. Competition altered that. But would marketing of individual programmes change things for the better? Suck it and see seems to be the only possible answer, but the problem with this is that you jeopardise existing arrangements that by and large work perfectly well.

This brings us to the problem of whether the public is being well served. AGB Cable and Viewdata recently carried out, on behalf of Tyne Tees Television's Nightline programme, some research on public opinion in this field. It found that 45 per cent of all adults polled felt that the quality of TV had declined over the past five years – the percentage rose to 48 per cent of adults aged 35 and over. When asked whether television overall provides the programme mix viewers want 48 per cent answered no while 44 per cent answered yes. Amongst those aged under 35 59 per cent considered the mix to be wrong. The results were admittedly based on only a small sample – 555 adults – though the sample was weighted by age, sex and housing tenure to correspond with general UK census data. The findings should nevertheless leave broadcasters with an uneasy feeling.

Whether radical changes in the way that TV programmes are disseminated would end up by giving the public a better service is impossible to know. The safe policy seems to be to make the best of the institutions we already have, adapting them as the technology advances. One thing's for sure; the debate will go on!

EDITOR

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 617.

ADVERTISEMENT MANAGER

David W.B. Tilleard
01-261 6671

SECRETARY

Janet Reeve
01-261 6671

CLASSIFIED ADVERTISEMENTS

Pat Bunce
01-261 5942

ADVERTISEMENT COPY AND MAKE-UP

Ron Scorey
01-261 6035

TV BRANDS

Many thanks to readers who provided spares/data information on Tensai and Winthronics sets – see note in Teletopics (page 642). Can anyone help with information on Intel colour receivers? These sets seem to have been distributed mainly in N. Ireland.

COVER PHOTO

Not much explanation required this month – tuning in to satellite TV! See article on page 636.

Letters

TEST CARDS PLEASE

After reading the comments from Keith Lane (June) I wholeheartedly agree about the absence of test cards on our television network. Test Card F is the ideal test pattern for setting up a television receiver, not only for the more technically minded but for general purposes, i.e. line and field linearity, height, width etc. Also, I think most engineers will agree that the colours in the centre circle have become so well known that most of us can set the grey-scale, colour etc by eye with very good results – provided that tube emission is all right.

For early birds Test Card F is transmitted on BBC-2 between 8.30 and 9 a.m. I've recorded an HG three-hour VHS tape in half-hour sessions, putting on my own sound. It produces very good results despite two and a half years' use eight hours a day in the workshop. But of course it's not as good as an off-air Test Card F. So how about it BBC and ITV: let's have Test Card F on one channel where it can do us engineers proud. After all, we do have the best television service in the world, so let's keep our receivers giving optimum performance.

*P.G.A. Crockett (thirty years' service),
D. Clarke – Radio and Television,
Hemel Hempstead, Herts.*

TIFAX TELETEXT DECODERS

In view of recent letters in *Television* concerning the Tifax teletext decoder the following information may be helpful to your readers. The first joint BBC/IBA/BREMA teletext specification was issued in October 1974. Minor changes were added in January 1976. Certain control codes however were left undefined until September 1976, when the final teletext specification as used by broadcasters today was published.

The Texas Tifax XM11 decoder was the first to use custom LSI chips and was introduced before the final specification. It therefore lacks the features which at that time were undefined (double height, separated graphics, graphics hold, background colour) although a later version (XM11/DH) did offer double height.

There's another problem with the XM11 however, and this could be causing some of the effects described by your readers. It concerns row address decoding and arose following a refinement in the teletext specification introduced between 1974 and 1976. The manufacturer was aware of this and the XM11 was soon replaced by the XM12 mentioned by Mr. Sears. However only prototype quantities of this decoder were made before Texas withdrew from the market.

Each teletext TV line contains a 5-bit row address which can be of any value from zero to 31. Zero to 23 directly correspond with the 24 rows of text display. The range 24-31 was reserved for other uses, many of which have now been defined. Receivers offering additional features (e.g. page linking) provided by these should be available later this year.

Both 1976 specifications stated that decoders should ignore row addresses 24-31, but when confronted by one of these an XM11 ignores both that line and the following data line containing data intended for display. The effect is to miss out a row of text and either leave it blank or

continue to display text left behind from another page. The chances are that this will be filled in next time round in the transmission sequence, providing it's not part of a rotating page set.

Since February 1982 the BBC has been transmitting occasional row numbers above 23 to assist with the development of the next generation of decoders. In September 1985 one teletext line per field blanking interval on BBC-2 was dedicated to Datacast, an experimental data service which also uses these row addresses. The remaining teletext lines (four initially, now five) carry the normal BBC-2 Cefax service. Unfortunately this has highlighted the row decoding fault, causing the effect described by Mr. Cummins, i.e. every fifth line of any BBC-2 Cefax is missed by the XM11.

The fact that these decoders are obsolete and that the problem is caused by them not precisely meeting the agreed specification is of no consolation to viewers still using them, especially as they gave satisfactory service initially. In view of this the BBC ran an experiment to try to establish how many XM11s are still in use. In late 1985 a message normally visible only with XM11 decoders was transmitted on the index page, asking viewers to call a telephone number. The response to this was so small that we came to the conclusion very few XM11s could still be in use. Those that are probably tend to be owned by television enthusiasts.

*M.J. Winston, Senior Planning Engineer,
Planning and Installation Department, Television,
British Broadcasting Corporation.*

Editorial note: Mr. G. Beard, who started this correspondence off, comments as follows: The index page referred to in Mr. Winston's letter could have been page 100 or the alphabetical index page, which in either case would be missed by numerous viewers as the XM11 doesn't initialise on page 100 and most viewers go straight to pages of their choice. Readers using XM11 decoders might like to notify the magazine: if the number of letters received is sufficient details could be forwarded to the BBC.

AMSTRAD CTV1400

Further to the note on the Amstrad CTV1400 (TV Fault Finding, June) the following may be of interest to readers. An apparently dead set with an audible whistle coming from the chopper transformer should direct attention to the soldered joints around the line driver transformer. Even when they appear to be good this has been the cause of the problem on a number of these sets.

*D.G. Hopwood,
Worsley, Manchester.*

VHF/UHF SOUND RECEIVER

I've received several letters from readers asking about my v.h.f./u.h.f. sound receiver (May issue). The 40673 dual-gate MOSFET mixer transistor, about which some readers enquired, is available from Maplin Electronics and East Cornwall Components. Cirkit have a similar device which is somewhat cheaper, type 3SK81.

For L3 a Mapiin former type 722/8 (order no. LB21X) can be used with screening can type 15 (LB39N) and cores type 4 (LB41U). Ten turns instead of 13 will probably give the correct tuning range but I'd suggest using two 22pF film dielectric trimmers instead of the 10pF mica capacitors. An alternative circuit using prewound coils

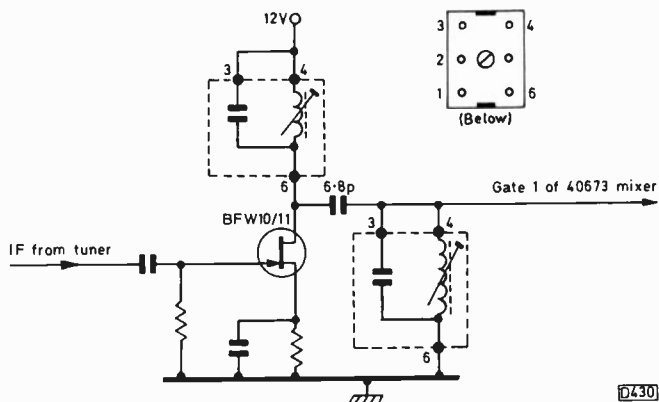


Fig. 1: Alternative circuit using prewound coils.

type TKXCA34732CON (Cirkit type 35-47320) is shown in Fig. 1. I've not tried this in the original receiver though it works in an alternative set-up I've built.

Paul Barton,
Harrogate, Yorks.

SOUTH AFRICAN VIEW

I am with your correspondent Keith Lane (June) on the matter of the failure of the BBC to broadcast test cards, having been one of these engineers who lobbied the BBC many years ago to change the early test card when its frequency charts were becoming outdated by the arrival of the 625-line services. Here in South Africa the SABC broadcasts a test pattern on TV2 during all non-programme hours: on TV3 there are teletext samples for 45 minutes in the hour and a test card during the other fifteen minutes. There are sometimes colour bars before each programme start.

The new M Net commercial, privately-owned service has started test transmissions here on channel 39, much to the annoyance of many viewers who are losing their reception of Bop TV on ch. 37 due to interference – at the moment there's a market for notch filters to help. The SABC have always been against us whites receiving Bop TV and have made it difficult for us here in the Reef area to get more than a few microvolts – to this end they erected large side screens to prevent overspill into the suburbs of Johannesburg. The M Net system is owned by a consortium of local newspapers and will be a rental service – about R200 for a decoder plus approximately R30 per month to receive the station. About five hours of transmissions a day are planned and up-to-date movies are expected. The present service is TV1 alternately English/Afrikaans, TV2/3 vernacular – English mainly but some Afrikaans each night from 9:30 p.m. to midnight or thereabouts.

To return to the subject of test cards, if the SABC can do it with such a small population surely the BBC/IBA could manage some transmissions?

Leonard E. King,
Kempton Park, Transvaal, RSA.

FUSE PROBLEM

Here's a fault that had me running around in circles on a Grundig set fitted with the GSC100 chassis. The symptoms were lack of height with non-linearity at the top of the picture. My reaction was that the supply to the TDA1170 field timebase chip was low, and sure enough a check on the +D line revealed that it was at 15V instead

of 18V. The supply is derived from the line output transformer but a thorough check on the rectifier and filter components failed to reveal anything amiss while the pulse input was correct. Changing the TDA1170 had no effect.

In desperation I changed the fuse in this supply, Si627 (1A anti-surge) – with immediate success. A check on its resistance produced a reading of 1Ω compared to 0.2/0.3Ω for a good fuse. Placed as it is between the cathode of the rectifier and the reservoir capacitor C628 this small resistance had a devastating effect on the +D supply. Maybe I was slow in diagnosing this fault but one does get used to thinking of an operational fuse as a short-circuit, which an anti-surge type certainly isn't.

L.P. Watkinson, Telesonic Services,
Holsworthy, Devon.

GRUNDIG CUC SERIES

I was interested in the article on the Grundig CUC series chassis (July). Here are a couple of faults I've come across on a number of occasions on these sets: (1) Distorted sound with the CUC220 and CUC720 – when the station is detuned the sound will come in perfectly but the picture will be distorted. The cause is the TDA120T intercarrier sound chip in the tuner/i.f. module. (2) Excessive width with the CUC720 chassis, the width control having no effect and the voltages around the BC875 diode modulator driver transistor T576 being low. The cause is modulator diode D572 (SKE4G2/06) being short-circuit.

George Farrueia,
M'xlokk, Malta.

NORDMENDE F10/F11 CHASSIS

A printing error occurred in my article on the NordMende F10/F11 chassis (June). In the caption to Fig. 3 it mentioned that RF12 is 3.3Ω in the F11 chassis whereas it's normally 2.7MΩ or on occasion 3MΩ. Since compiling the list of common faults one more has appeared in recent months – set dead due to failure of the mains fuse FP01 caused by the degaussing thermistor going short-circuit. This would appear to be due to a faulty batch of thermistors that fail after a few months' service.

Christopher Holland,
Dundalk, Co. Louth.

Editorial note: The error was our fault – we meant RF21 which is in series with the field scan coils. Our apologies.

COSSOR CDU150 OSCILLOSCOPE

Readers may be interested in the following modifications to the Cossor CDU150 oscilloscope. These twin-channel oscilloscopes have been sold on the surplus market for about £170. They are all solid-state and feature delayed timebases, a quoted bandwidth to 35MHz with observable signals at over 100MHz, and many features. They are also small and light despite the six inch screen. The rugged, military style construction should protect them against rough handling in the workshop or in the field.

My scope failed due to a flashover between the p.d.a. multiplier and the e.h.t. and blanking board. Remove the rear cover to locate these. I fitted an aluminium guard between them to prevent a recurrence.

I noticed that the c.r.t.'s heater glowed brightly at switch on before reaching an even temperature. Fearing that this could eventually lead to filament failure and

costly c.r.t. replacement I have installed a slow-start circuit for the heater to eliminate the fault. It's built on an aluminium panel fixed to the tube base – the whole circuit floats at about the tube base potential. Fig. 2 shows the circuit. Power is obtained by using a bridge rectifier to rectify the heater voltage. At switch on the 3-3Ω resistor R3 is in series with the tube's heater. The 470μF electrolytic C2 charges slowly via R1, eventually switching on Tr1 to operate the relay and short out R3. Tr1 can be a BC384L or similar npn transistor. R3 needs to be a wirewound type. The relay is an STC type 4184GC.

This arrangement could be used for any c.r.t. heater or lamp that might be damaged by a switch on surge. Once the relay has closed the tube will receive the same heater current as in an unmodified unit. The only change will be the additional power dissipation in the 170Ω relay coil. With a 6-3V heater this will be under 0.5W, even allowing for rectification and smoothing.

This has little to do with oscilloscopes, but I've found a

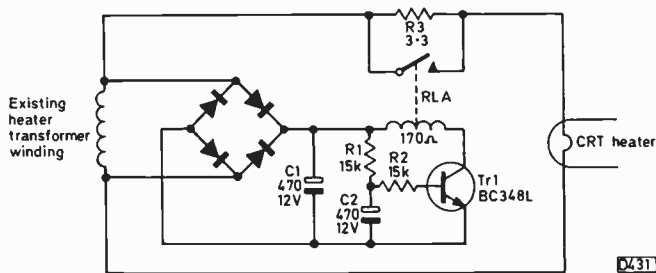


Fig. 2: Slow-start c.r.t. heater circuit.

good way of stopping cables pulling out of 13A plugtops. With appliances such as garden tools the cable often slips out of the plug leaving only the insulated wires. To prevent this happening, put a blob of thermosetting glue on the cable inside the plug, past the clamp.

John de Rivaz, B.Sc (Eng.),
Porthtowan, Cornwall.

Single-channel Indoor Aerial

Ivor Nathan

A distant signal can often be received in only a quite closely-defined position: moving the receiving aerial by a few feet in either the vertical or horizontal plane may cause complete loss of signal. At my location in Southgate, North London even reception of the four local channels can be a problem because of the hilly nature of the surrounding district. I've nevertheless found it possible to receive alternative signals by using a separate indoor aerial and aerial amplifier.

I started experimenting using a commercial indoor log-periodic aerial and amplifier. This established that reception of TVS (Television South) on ch. 42 was feasible, providing a choice of extra programmes when they differed from the London ITV ones. The aerial was placed in various positions about the room. For a noise-free signal the best position was found to be three and a half feet above the floor, surprisingly not very near to a south-facing window – and with nothing of the correct height to rest the aerial upon. This prompted me to build the aerial and its floor-stand described in the present article: see Fig. 1, right.

The base of the stand can be made of plastic or wood: it needs to be heavy to ensure stability. The aerial itself consists of a half-wave dipole, reflector and director – all made of heavy-gauge wire – on a boom, and an extra horizontal reflector made of domestic aluminium foil sheet. The height of the stand and the mounting position for the aerial depend on the locally available signal(s): trial and error with an existing indoor aerial is the only way to check on this, with an aerial amplifier if need be. The aerial element dimensions shown in Fig. 1 are calculated for ch. 42: if you wish to receive a different channel optimum results will be achieved only by recalculating the dimensions for the appropriate half-wave dipole and its associated elements and their spacings.

The dipole is assembled on a four-screw plastic terminal block: the connections to the low-loss coaxial feeder can be made as shown. Tape the feeder to the stand – the feeder should be long enough to enable the assembly to be placed anywhere in the room. The director and reflector are similarly assembled on four-screw plastic

blocks. The extra reflector, which is mounted on an arm below the main array, provides a surprising degree of extra gain. It consists of a rectangular sheet of aluminium foil pasted on a piece of stout card.

It's best for the floor-stand support components to be of square or rectangular section rather than circular so that they can easily be joined together and so that the plastic terminal blocks and the foil reflector can readily be fitted to the supporting arms.

If an aerial amplifier is already in use it's a simple matter to change aerials at the amplifier input when using the newly constructed aerial instead of the existing local-channel installation. Regardless of whether an aerial amplifier is in use some readers may prefer to add a changeover switching system.

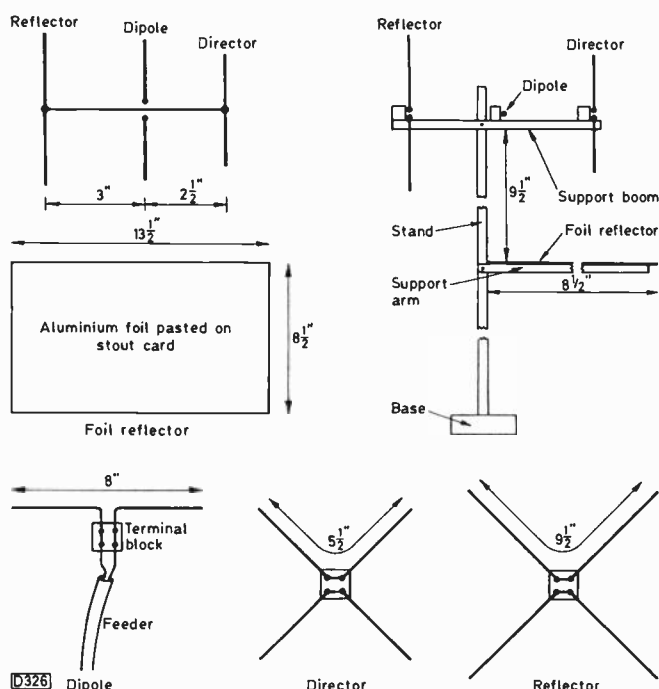


Fig. 1: Details of the aerial.

POST A PART ELECTRONICS

6 CHAPMAN COURT, CHARFLEETS ROAD,
CANVEY ISLAND, ESSEX SS8 0PQ.

Telephone 0268 690868
Telex 99305



TRADE COUNTER OPEN

ORDERS DESPATCHED SAME DAY
ADD 75p P&P, THEN 15% VAT.
ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thom 10C 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 70C	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
Pye 725 Complete Tube Base Panel	1.25
TX9 Complete Tube Base Panel	2.75
TX10 Complete Tube Base Panel	3.75
TX90 Complete Tube Base Panel	4.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket IIT CVC32	45p
Tube Base Socket Thom 3000/8000 etc	50p
IC Inserter 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lopt	90p
Anode Cap	47p
Sanyo Anode Cap Assy + Lead. 127CD-CT-16	65p
Degauss VDR E299D/HP230 3000/8000	25p
Degauss Thermister C8 ROH (TX90)	1.20
Control Knob Thom TX90	4 for 1.80
On/Off Knob Thom TX90	65p
Push Button Assy Thom TX90	9.80
Tube Neck Correction Assy. 20AX AT1081	5.00
EHT Cable	Metre 25p
BF259 with Heatsink	14p
TIP110 with Heatsink	1.40
L129/130/131 Coil	10p
6MHz Ceramic Filter	25p
DL700 (Philips) Chroma Delay Line	1.00
DL500 Chroma Delay Line	1.00
TS006A Lum Delay Line	1.00
8K59K Lum Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100R	15p
Thom 2000 Focus Pot	1.00
Thom 9000 Focus Pot	3.75
Thom 9600 Focus Pot	2.00
Thom 8K5 Focus Pot	2.40
Thom 4000 Focus Pot	2.75
Thom TX10 Focus Pot (New Type)	9.00

SERVICE AIDS

Ambersil MS4 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	8oz 1.89
Ambersil Ambertron	16oz 2.25
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Ambersilens Foaming Cleaner	13oz 1.26
Ambersil Circuit Lacquer	14oz 2.15

THICK FILM RESISTOR UNITS

3500 Thom (5 Pin Connection) video	1.70
4000 Thom (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

FUSES

20mm		1/4"	
50MA	10 for 70p	250MA	10 for 65p
250MA	10 for 50p	750MA	10 for 65p
315MA	10 for 50p	7A	10 for 50p
500MA	10 for 50p	10A	10 for 50p
2.5A	10 for 100p	20A	10 for 50p
315A	10 for 1.00	50A	10 for 50p

Thom Mains TX 3000/3500	7.50
Thom Mains TX 8000/8700	10.00
Thom Mains TX 3000 (T701)	10.00
Thom Mains TX 3600 (T512)	10.00
Thom S.O.P.T. 8000/8500	3.50
Thom Scan TX 3000/3500	6.00
Thom EHT TX 3000/3500	6.00
Thom LOPT 9000	10.00
Thom LOPT 9600	12.00
Thom LOPT 1590/91	7.25
Thom LOPT 1690/91	7.25
Thom LOPT 8000	9.80
Thom LOPT 8500	9.80
Thom LOPT TX9	9.85
Thom LOPT TX10	19.00
Thom LOPT TX90	13.75
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT G9	8.80
Philips LOPT G11	13.75
GE LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	6.75
Philips LOPT G8	7.80
Sanyo LOPT (CW21) 4-2751-44700	9.60
IIT LOPT CVC5-9	9.60
IIT LOPT CVC30	8.75
IIT LOPT CVC45	9.75
Baird 8750	10.25
Baird 8752	10.25
Thom Line Drive TX TX9 (T2)	3.00
Thom Line Drive TX 8K etc. (T402)	1.85
Thom Line Drive TX 9K (T705)	2.00
Thom Switch Mode TX 9K6 (T511)	3.75
Thom Input Choke TX9 (L64)	4.00
Thom Choke TX90 (L120)	2.95

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	1.00
20 Mixed VDR & Thermistors	1.00
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC174B	23	BCX33	22
AC131	40	BC177	24	BCX34	21
AC138	40	BC182LB	12	BD115	49
AC141K	39	BC183L	12	BD131	46
AC142K	38	BC184L	13	BD132	46
AC153	39	BC187	24	BD133	59
AC176	33	BC204	15	BD139	36
AC176K	38	BC208	9	BD140	38
AC128K	33	BC212L	9	BD144	1.70
AC188	38	BC213L	12	BD150	50
AD142	1.18	BC237	12	BD163	98
AD143	1.08	BC238B	8	BD201	74
AD149	98	BC238L	8	BD203	78
AD161	32	BC250A	15	BD204	99
AD162	1.05	BC252A	20	BD225	50
AD263	42	BC254	28	BD226	52
AF127	45	BC294	37	BD232	50
AF139	38	BC301	32	BD233	60
AF239	41	BC303	31	BD234	60
BC107	15	BC307	10	BD237	95
BC108	15	BC308	8	BD238	65
BC109	15	BC309	14	BD241	59
BC115	16	BC327	18	BD244	85
BC117	21	BC328	18	BD248A	81
BC125	26	BC337	17	BD386	68
BC126	23	BC338	17	BD433	71
BC139	27	BC347	8	BD437	83
BC141	34	BC394	8	BD592	1.20
BC142	30	BC454	8	BD595	1.20
BC143	31	BC455	8	BD599	1.20
BC147	12	BC456	10	BD679	1.42
BC148	12	BC460	40	BD701	1.04
BC149	12	BC463	22	BD702	1.12
BC153	16	BC466	8	BD707	95
BC1540R	16	BC474	12	BD708	95
BC154YL	16	BC489	12	BD839	1.30
BC157	12	BC549	8	BDX10	93
BC158	12	BC557	10	BDY20	1.08
BC159	15	BC568	10	BDY82	99
BC171	9	BC569	8	BF137	20
BC172	9	BC595	8	BF153	20

INTEGRATED CIRCUITS

BRC1330	1.40	SN76013ND	1.00
BRC3064	1.00	SN76023N	1.00
BRC/M/200	1.00	SN76033N	1.00
BRC/M/300	1.00	SN76115	1.50
CA3060	1.58	SN76131N	1.00
LM1303P	1.48	SN76226N	1.25
ML2118B	2.20	SN76227N	1.00
ML237B	2.00	SN76530P	1.30
ML239B	2.86	SN76622N	1.00
MC1327AP	1.25	SN76660N	80p
MC1358P	1.30	SN76666N	75p
MC1455P	18p	SN76744	1.92
MC14516BCP	60p	SY153A	2.50
SA41025	7.20	TAT117P	1.00
SA41124	4.50	TAT109AP	2.80
SA45010	6.00	TAA611	1.40
SL432A	1.80	TBA120B	1.20
SL1430	2.50	TBA120C	1.20
SL1432	2.50	TBA120CQ	70p
SN15846N	6.00	TBA120S	70p
SN74123N	65p	TBA120U	1.00
SN74154N	1.40	TBA395	1.00
SN76001N	1.40	TBA480Q	1.40
SN76110N	1.14	TBA510	1.90

Thom 8/8K5 ex equip panels untested	2.88	PSU	3.75
FTB	3.75	LTB	3.75
Decoder	4.00	Video	2.50
Thom 9K ex equip panels untested	12.00	IF	1.75
PSU	5.00	Conv. 3K	3.00
Decoder	5.00	Conv. 3K5	3.75
Thom 9K6 ex equip panel untested	5.75	Autovox Decoder FG01 boxed	5.00

UHF TV Aerial for portable	50p
Indoor Aerial With Reflector	2.50
To Help Combat Ghosting Problems	38p
Line Connectors	1.00

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
20 Mixed Valve Bases	1.00

BF154	25	BFH52	31	NKT1276	20
BF167	22	BF167	28	NKT453	1.65
BF173	29	BF173	29	DT112	1.92
BF179	32	BF179	25	DT121	2.08
BF180	49	BF180	33	BF180	1.74
BF184	46	BF184	30	BF184	2.08
BF185	59	BF185	30	BF185	1.40
BF194	36	BF194	16	BF194	40
BF195	38	BF195	16	BF195	1.30
BF196	1.70	BF196	16	BF196	80
BF197	50	BF197	15	BF197	50
BF198	98	BF198	19	BRC116	1.50
BF199	74	BF199	15	BRC1693	1.43
BF223	18	BU105	18	BU105	1.25
BF224	19	BU126	1.10	RCA16640	1.40
BF228	48	BU207	1.05	RCA16739	1.13
BF240	52	BU208	1.15	RCA16800	1.42
BF241	50	BU208A	1.15	RCA16802	1.38
BF255	60	BU264	1.30	RCA16815	1.20
BF256LB	38	BU407	1.70	SP3385	2.65
BF265	20	BU408	2.76	SI299	2.25
BF266	28	BU500	2.30	S28000	1.25
BF267	28	BU526	2.46	T6050V	1.30
BF271	25	BU806	1.80	T6052V	1.30
BF274	81	BF274	11	BU807	2.94
BF337	29	C1129	9	T9010V	1.45
BF338	71	BF338	34	CT172B	9
BF355	40	ES386	54	T9054V	1.00
BF362	50	E9003	28	T9039V	1.10
BF391	21	E9005	25	TIC45X	50
BF422	16	ME0404	10	TIC46	48
BF434	47	ME0412	10	TIC106C	40
BF423	53	ME6002	10	TIP23	42
BF450	43	MJ2501	2.36	TIP30	42
BF453	53	MJ3001	2.21	TIP31	35
BF458	37	MJE340	50	TIP32	43
BF459	40	MJE520	50	TIP33	61
BF461	59	MJE2955	1.40	TIP41	42
BF462	35	MJE3055	1.50	TIP42	45
BF465	15	NKT241W	8	TIP110	61
BF469	16	NKT241G	8	TIS91	25
BF475	62	NKT241Y	8	ZTX550	30

Pye 78+161	50p	EHT TRAYS	
Pye 147+260	50p	Thom 3000	5.50
Thom 56+1K+47+12	1.24	Thom 8000	4.50
Thom 50+40+1K5	60p	Thom 8500	6.00
Thom 128+16+1K7+	7.00	Thom 9000	7.90
116+462+125	50p	Thom 9600	6.00
Thom 120+72+300	50p	Thom 900/950	1.50
RBM 250+14+58	63p	Thom 1500 3 stick	2.40
(TV161)	63p	Pye 713 4 lead	5.83
Pye 3R5+15+45 (T13)	90p	Pye 713 5 lead	5.97
Philips 2R2+682	90p	Pye 725	6.35
Philips 47R	52p	Decca Bradford	5.00
Thom 6+1+100	92p	Baird 8750	7.10
Thom Cut-Out	1.45	Korting A29100	7.10
Thom 3000 Metal	1.45	Philips G8 (520)	6.50
Thom 8/8500 Plastic	1.45	Philips G8 (550)	6.50
Universal	5.00		

MULTISECTION CAPACITORS

220+47	350V	65p	200+200+100	350V	55p
200+150+50	350V	60p	200+200+75+25	350V	60p
200+200+100	325V	54p	50+50+8	300V	55p
32+32+16	275V	52p	100+50+100	350V	55p
200+200+100+32	350V	70p	100+150+50	350V	55p
100+50+150	350V	58p	2500+2500 (Thom 8K)	63V	1.05
400+400	200V	72p	150+150+100	300V	1.80
32+32+16	350V	52p	200+47	250V	65p
200+32+300+100	350V	70p	500+500	175V	50p
225+25	350V	70p	Thom TX9		1.00
200+200+100	350V	70p	175+100+100	350V	1.00
200+100+100+50	325V	65p	Thom 3K5		2.25
350V	60p		400 400V Thom 9K		2.50
			470 250V Weidel Type		1.71

LOOK AHEAD!

WITH MONOLITH MAGNETIC TAPE HEADS

DOES YOUR VCR GIVE WASHED OUT NOISY PICTURES - ITS PROBABLY IN NEED OF A NEW HEAD - FAST FROM OUR EX-STOCK DELIVERIES. SAVE ££'s ON REPAIR CHARGES.

Our replacement video heads fit most models of VHS or Betamax VCR's. Following our replacement guide and with a practical ability, you can do the whole job in your own home with our head replacement kit.

**VIDEO HEADS
AT LOW LOW
PRICES!**

VIDEO HEAD REPLACEMENT KIT



VMC-02 KIT ONLY £19.95 inc. VAT. + £2.50 p&p
(Kit does not include video head)

TELEPHONE US NOW FOR INFORMATION OF THE REPLACEMENT HEAD FOR YOUR VIDEO RECORDER.

CATALOGUE: For our full Catalogue of Replacement Video and Audio Cassette/Reel to Reel Heads, Motors, Mechanisms, etc. Please forward 50p p&p.

THE MONOLITH ELECTRONICS CO. LTD.
5-7 Church Street, Crewkerne, Somerset TA18 7HR, England.
Telephone: Crewkerne (0460) 74321 Telex: 46306 MONLTH G

SADELTA FIELD STRENGTH METER MODEL TC-402

THE SADELTA FIELD STRENGTH METER TC-402 has been designed to measure the signal levels delivered by the antenna to a TV or FM receiver. In order to test the performance of the antenna and evaluate the best conditions during installation etc. To facilitate measurements, the tuning frequency readout is shown on a digital display.



FEATURES

- Covering FM and all TV bands (UHF/VHF) including CATV freq.
- Digital tuning display (3 digits) for direct frequency readout.
- Accurate 10 turn tuning potentiometer.
- Built-in loudspeaker enables monitoring of sound in AM/FM.
- Meter measurement in voltage and dB from 20uV (26dB/uV).
- Continuity tester 0-500 Ohms.
- Fully portable (battery).
- Sturdy carry case.

PRICE £249 + £37.35 VAT

U.K. POST PAID. export enquiries welcome. Visa/Access or cheque with order, payable to B.K. Electronics. Official orders welcome from Govt. Depts., Colleges, P.L.C.s etc. Large S.A.E. for technical leaflets of complete range delivery normally within 7 days.


B. K. ELECTRONICS Dept. 'T',

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,
ESSEX. SS2 6TR TEL: 0702-527572

DISPLAY ELECTRONICS LTD.

- ★ Do you use cathode ray tubes?
- ★ Can't find a replacement or shocked by the cost?
- ★ It may well be that a rebuilt tube will solve your problem.

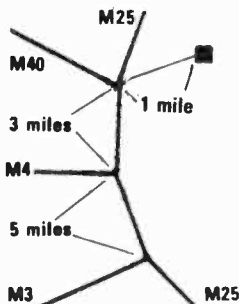Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.



WE ARE LOCATED IN UXBRIDGE

At probably the most accessible part of S.E. England. The nearest junction of the M25 is only about 1 mile away and we are less than 10 minutes from the interchanges on the M25/M3, M25/M4, M25/M40.

Why not telephone Terry Smith on Uxbridge (0895) 55800, to discuss your requirements?

DISPLAY ELECTRONICS LTD.

UNIT 4, SWAN WHARF,
WATERLOO ROAD,
UXBRIDGE, MIDDLESEX.

THE FULL THORN RANGE now available from SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
Southall, Middlesex
01 574 4631 EXT 28

9K-9K6-TX9-TX10 TEXT &
FULL REMOTE ALSO VIDEOS
V.H.S. & BETA. LOTS OF
WORKERS FOR BUSY DEALERS

TUNERS + TUNERS

- ★ If you repair sets regularly - phone us today and we will dispatch immediately - no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TAE PART
(U.K. ONLY)

32 Temple Street,
Wolverhampton WV2 4LJ.
Phone: (0902) 29022.

Thanks Denis

Les Lawry-Johns

Some months back (January) I mentioned a Network colour portable – Model NW1414, fitted with the Grundig GSC100 chassis. The original fault was that the fusible resistor R607 in the start-up circuit would go open-circuit for no apparent reason. Resoldering it restored normal operation, and despite my suspicions nothing showed up during a prolonged soak test. Network's service manager Denis Mott subsequently got in touch and provided some tips. He drew my attention to his article in the September 1984 issue of *Television* and said that the set would come back to me. Well it did, after some months though.

This time I followed Denis's suggestions and also checked a number of other things. No fault could be found. I eventually resoldered R607 and everything was lovely for a day and a half. Then it pinged again and we started replacing components en bloc. The result of this was that the set refused to come on at all when R607 was resoldered. My language was deplorable and Zeb went away and hung his head. Spock jumped up on to the highest shelf in the shop. Honey Bunch was out so she didn't have to hear it. Suddenly I stopped swearing. This is what we'd wanted in the first place, a fault that was there all the time. Unless I'd put it there when replacing various resistors and transistors. Supposing one had been defective? But I'd tested them all before fitting, as I always do. So I put this thought out of my mind and started a general check.

The line output thyristor, which had checked all right during previous tests, was now open-circuit between its gate and cathode. It should record about 30Ω one way and about 200Ω the other, with no reading between the anode and the other two electrodes when disconnected. Now it showed no reading at all. It was speedily replaced: the set worked for the rest of the day and the week that followed.

The Blind Comes Up

A chap staggered in carrying a 26in. Ferguson set fitted with the TX10 chassis. He explained that after about an hour's use a blind came up from the bottom, leaving just a few inches of picture at the top with the rest of the screen blacked out. I'd never heard of this one before.

I let the set run for some time, not really expecting anything to happen as the shop is a lot cooler than the customer's home. Then I removed the back cover and brought the hairdryer into action. I directed hot air at the field output transistors and the surrounding components. When I lingered on the TDA1044 chip the bottom of the screen blacked out and the blind rose until only the top few inches of picture remained. I grabbed the freezer but with the heat off the blind came down again and a normal picture was displayed. Again I heated the chip and again the blind rose, only this time I was ready with the freezer and the blind came down as soon as the chip was cooled. I didn't have a TDA1044 in stock so I looked under it to see what the ventilation was like. As there wasn't any near the chip I drilled a hole to let in some air. I explained to the chap what I'd done and mentioned that the TDA1044

would be here when the blind came up again – if it does come up again.

The Bush BC6004

Shortly after our second encounter with the Network set a Bush BC6004 colour portable came in. Another German chassis, this time manufactured by Saba. The customer's complaint was that it would be fine for an hour then shut off! It's the set with the small enclosed unit at the top right containing the line output transistor (BU208), line driver transformer etc. I changed the BU208 and the set worked fine for the best part of an hour. Then it shut down again.

I tapped the BU208 with the handle of a screwdriver, more out of frustration than anything else. The set then started up and shut down after an hour. This time I moved the line output stage housing cautiously and the set started up again. So I took the housing out of its socket, having removed the two screws, and carefully resoldered all the input joints – though none looked suspicious. I then touched up any other joints that looked the slightest bit shaky and refitted the unit. It played away for the rest of the day and as far as I know it's still playing away quite happily. I wish I was.

GEC C1404H Series

These 14 and 16in. portables are made by ITT in W. Germany, using the CVC1110/CVC1112 series chassis. They suffer from a common fault: a bright white screen, suggesting that the tube's cathodes have lost their bias. The RGB output transistors with their 12kΩ collector load resistors are mounted on the tube base panel. No voltage will be found on these resistors. The source of the 150V supply is the line output transformer: the series-connected rectifier diodes D504 and D505 are on the right side of the main panel. There's a small surge-limiter resistor in the feed from the transformer, R514 (1.5Ω). It looks very small and is intended to be, acting as it does as a fuse. It doesn't burn out for nothing. The cause could be leakage in the diodes or in the associated 10μF reservoir capacitor C506 or the 1μF smoothing capacitor C1002 on the tube base panel. Occasionally one of the three RGB output transistors may be at fault, but this doesn't happen very often. Then of course it may be the tube . . .

This and That

The editor must be taken to task for a couple of mistakes that got into my column in the June issue. First about my overcoat. I said it cost 37/6d made to measure, also that this works at one pound eighty seven and a half pence. In print it said one pound thirty seven and a half pence. I also said that we filled up with petrol on the A2 just a little way from home. This came out as the A3, which is a long way from home. Oh well, I suppose we can't all be perfect . . .

It amazes me what Honey Bunch gets given to her. Boxes of chocolates by the dozen (we don't eat chocolates but Zeb does, so does her aunt). Last Sunday lunchtime we were in Dave's for a drink and H.B. happened to mention that she hadn't had duck's eggs for years. Next day one was brought in. I haven't had (given to me) a bottle of whisky since Christmas, and I'm not likely to till next Christmas. It won't be long now however. This year has simply rocketed by.

Satellite TVRO Installation

Part 1

Harold Peters

It's one thing to get a dish up and working outside your own premises with all your colleagues to help, quite another to install a satellite TV receiving system on the patio of one of your best customers. At that time you're on your own and possibly beginning to wish you'd given more attention to all those *Television* articles that didn't seem relevant at the time. So if your company has recently decided to expand into satellite TV here's a recap of the things you ought to know and a bit of background information to tie it all together. Some specialist firms are now offering equipment at below the £1,000 mark: we'll assume that one such outfit has arrived and that you've been selected to get it going. Fig. 1 shows a typical satellite TV receiving system block diagram.

Commissioning the Receiver

Commissioning the receiver will be the part most familiar to you, so we'll tackle this first. Hopefully the manufacturer will have air tested it and left it tuned to a known channel – usually Music Box. If so you leave the tuning severely alone: your first problem has been overcome before you start!

Table 1 gives a list of the satellite TV stations currently available in the UK. Receivers generally have a baseband video output of 1V at 75Ω, with a separate audio output at around the 300mV level. A modulator is usually included to give a standard u.h.f. TV signal at around

channel 36. Where this is missing but needed a VCR's auxiliary input does equally well.

An integral part of the receiver is the low-noise amplifier and down-converter mounted on the dish. This assembly is often referred to as a low-noise block (LNB). An 18V d.c. supply goes from the main receiver to the LNB via the same coaxial feeder that the i.f. signal from the converter comes down to the receiver. It's a good policy therefore not to disconnect the LNB with the receiver powered up.

A rough and ready test can be applied before aligning the dish. With the receiver on but the LNB disconnected you should see about the same order of noise (snow) as on a domestic set. Connect the LNB and the snow should increase perceptibly. Point the LNB at a warm patch of sunlit ground and there should be more snow still. An AVO 8 on the low-ohms range connected across a cold LNB input should give a typical diode reading: low one way, high the other.

The Dish

Assembly of the dish from its flatpack is simply a matter of following the leaflet enclosed. Make sure that the dish doesn't get distorted: store it flat, not on edge.

There are two kinds of mount: "Az-El" (azimuth/elevation) with simple vertical and horizontal adjustment of the dish, and "polar" which permits the dish to be tracked across the sky, following the Clarke Orbit, and stopped at any satellite of your choice. Both types should be bolted to a firm base. The connections to the LNB and the LNB/feedhorn junction should be sealed over with waterproof material.

With the dish roughly in position, take care when working at the focus: you may need sunglasses to counter the glare concentrated by the dish – and watch out for passing jets that may cross the beam (dishes concentrate sound as well as s.h.f.!).

Siting the Dish

The whole dish must have a clear sight of the satellite you want. Eutelsat 1 (originally known as ECS-1 and officially designated Eutelstat I-F1) is at 13°E of south while Intelsat VA F11 is at 27.5°W of south. Their elevations are roughly 29° and 24° respectively above the horizon. As a rough guide, the sun should fall on the chosen spot between 11 a.m. and 3 p.m. in November and February. For more precise surveying you can make up a


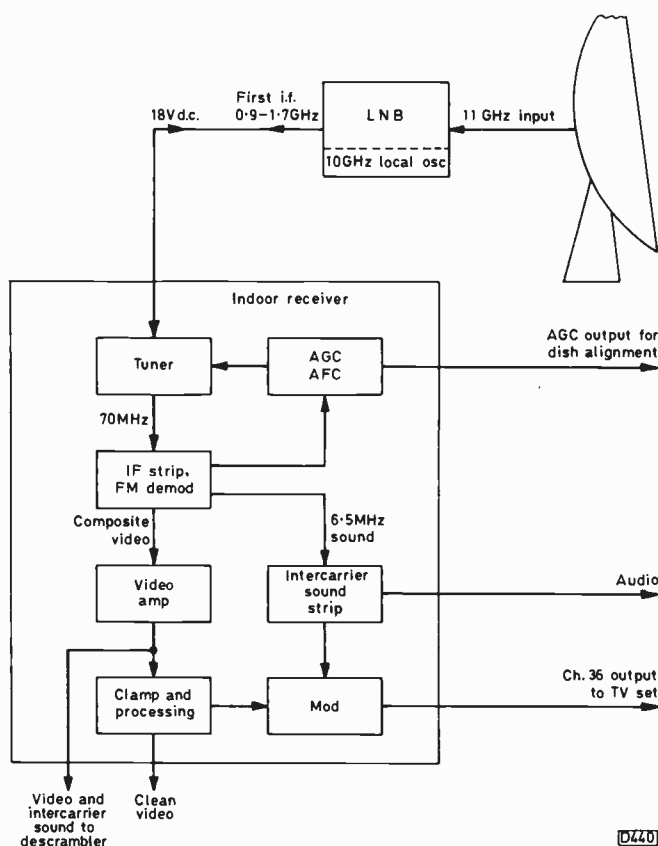


Fig. 1: Block diagram of a typical TVRO installation.

Fig. 2: A simple theodolite for site surveys. There's little point in making it taller than the dish bottom. Put the pipe at the satellite's elevation and set the azimuth with a compass. Look up the pipe and hope to see just the sky.

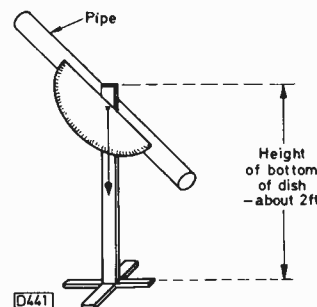

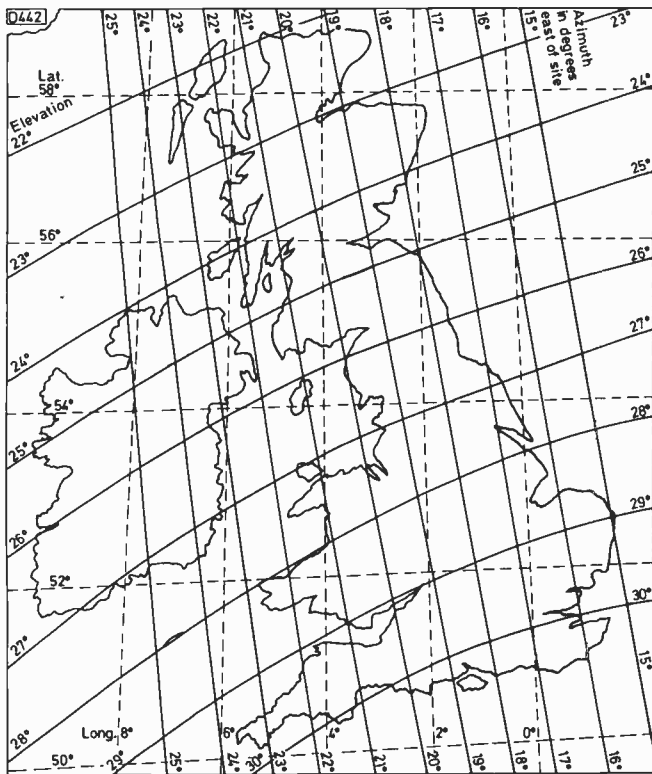


Fig. 3: Eutelsat 1 finder. Pinpoint your site on the map and interpolate dish elevation from the sloping horizontal lines and the azimuth east from your site from the vertical lines.

simple theodolite as shown in Fig. 2. You'll be surprised how few domestic sites are suitable for mounting a 1.8m dish.

Finding due south is important, especially with a polar mount. You can use a compass, allowing for magnetic variation. True south is 7° to the right of magnetic south. The trouble with compasses is that unless they are used well away from the gear they always point to the dish or the van. The Pole Star is an accurate north, if you keep late hours, but there's nothing like the sun if it's available at the time.

Table 1: Station finding guide by frequency.

Frequency (GHz)	Station/polarisation	Satellite
10-986	Teleclub/V	Eutelsat 1
11-005	RAI/H	Eutelsat 1
11-015	Premiere/Childrens/H	Intelsat VA F11
11-135	Screen Sport/H	Intelsat VA F11
11-138	Filmnet/V	Eutelsat 1
11-155	CNN/V	Intelsat VA F11
11-170	Europa/H	Eutelsat 1
11-471	TV5/H	Eutelsat 1
11-507	Sat-1/V	Eutelsat 1
11-650	Sky/H	Eutelsat 1
11-674	Music Box/V	Eutelsat 1
11-676	NRK/H	Eutelsat 2

Table 2: Solar transit times.

Times (GMT – add one hour for BST) when the Sun is due south.

Aberdeen	12-08	Douglas	12-18	Manchester	12-08
Belfast	12-24	Dublin	12-25	Newcastle	12-06
Birmingham	12-08	Glasgow	12-16	Norwich	11-54
Bristol	12-10	Leeds	12-05	Plymouth	12-16
Edinburgh	12-12	London	12-00	Swansea	12-16

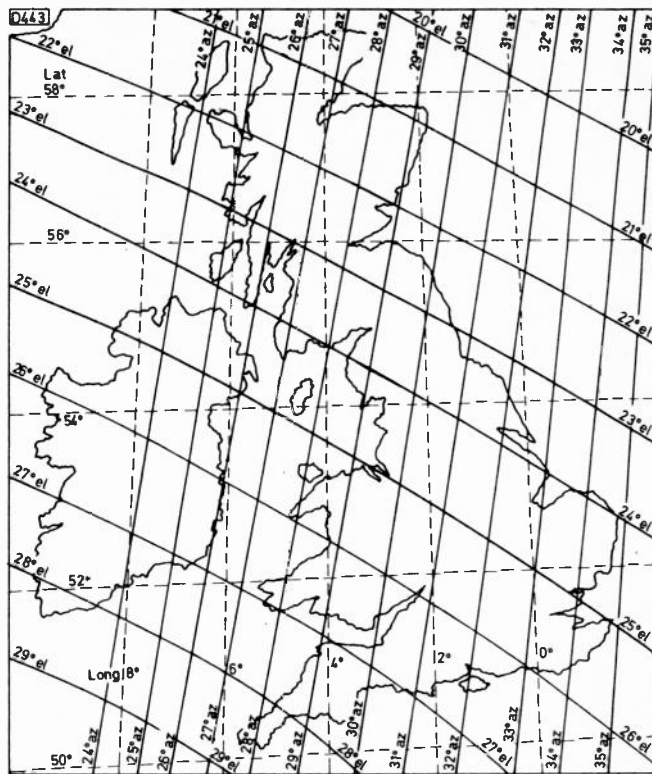


Fig. 4: Intelsat VA F11 finder. Pinpoint your site on the map and interpolate dish elevation from the sloping horizontal lines and the azimuth west from your site from the vertical lines.

Allow four minutes of time for every degree you are off the meridian. The sun is due south at 12 noon GMT (1 p.m. BST) at Greenwich, Cleethorpes and Newhaven but at Ipswich you plot at 11:56 a.m., at Portsmouth and Nottingham 12:04 p.m., at Birmingham and Manchester 12:08 p.m. and at Liverpool and Carlisle 12:12 p.m. Table 2 shows some more times. As a double check use an Ordnance Survey map: the popular series shows magnetic and grid variations at the edge of the sheet.

The hinge where the dish swivels on the mount should be pointed due south. This need be only approximately so with an Az-El mount. With the dish in position and everything connected up, point the dish at the required satellite, using the maps (Figs. 3 and 4) and a simple inclinometer (see Fig. 5) to get the elevation as nearly correct as you can. Set the azimuth with respect to south.

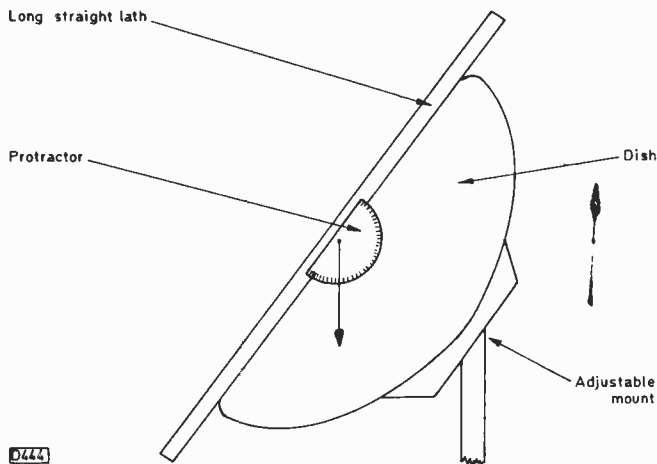


Fig. 5: A primitive inclinometer using a long straight lath and a protractor. Accurate enough at 4GHz and for dishes up to 1.8m at 11GHz.

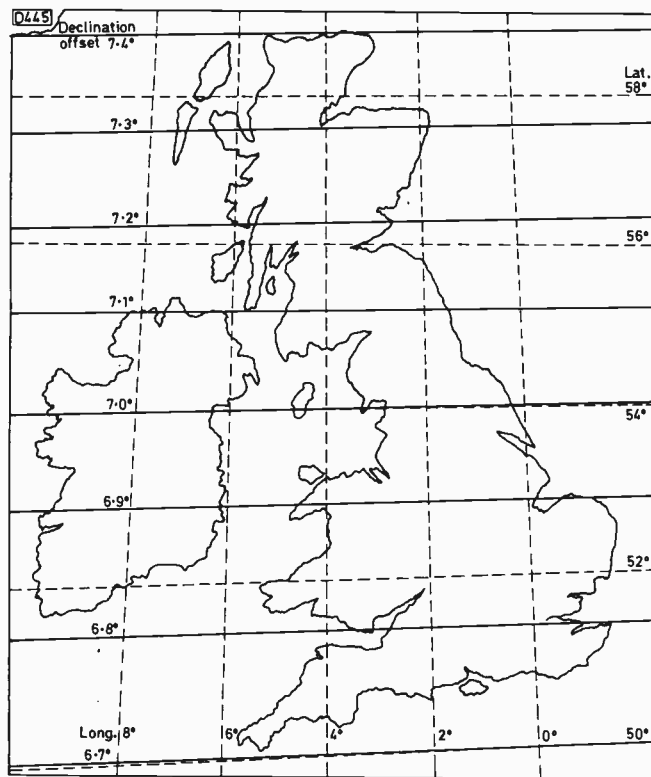


Fig. 6: Declination offset for polar mounts. Pinpoint your site on the map and read off to the nearest declination offset line.

You'll notice that the azimuth angle is always greater than the difference between the site longitude and the satellite longitude. For example Eutelsat 1 is at 13°E of south, Ipswich at 1°E of south, a difference of 12°. The azimuth setting however is 15°E of south. Why? Well the stated longitude of a satellite is that seen by an observer at the North Pole. The farther south you go the wider the azimuth angle becomes, until you reach the equator when you have only elevation to worry about.

Tuning in

Having done all the above according to the book, why do we still get nothing? With a 1.8m dish you have to be within 1.5° to get the slightest hint of a signal. Your LNB might be on the wrong polarity or the set not tuned to a station. Call your supplier if the latter is suspected – all those the writer has dealt with have been most helpful and can give you a dial setting to correspond with the wanted signal. Many leave them tuned to the station on which the set was air tested. If the polarity is in doubt turn the LNB to 45° when it should resolve a readable signal from transponders with either type of polarisation. Music Box and Sky share the same nominal band but their carriers are sufficiently offset to come in on quite different settings with the average receiver.

You will need to monitor the results at the dish. A battery operated monochrome set adapted to take a video feed is ideal. If the satellite receiver is provided with an a.g.c. port, take a meter out as well, with a long lead. If you're going to do a lot of installations a spectrum analyser is a worthwhile investment. It will do the whole job, better than a TV set. The writer has used the low-priced AVCOM PSA 35 (imported from the USA) to good effect.

Loosen the mount adjustments so that the dish can be

rocked about 10° in both planes, then methodically scan the patch of sky thus covered. Don't go too fast, and be prepared to freeze at the first sniff of signal. Remember that the signals are f.m. and once captured will hold over a small amount of detuning.

From now on everything is a matter of squeezing the lemon to get the last picowatt of signal into the system. Optimise the azimuth, elevation, polarisation and receiver tuning, then go over the lot again until no improvement can be obtained. Bear in mind that you need to allow for some 2dB loss in heavy rain or snow.

If, having got a strong signal, you find that the picture jitters badly you've chosen the wrong video output port on the set. There are often two: one with the sound and the dispersal signal removed and another with both left in for feeding to a descrambler or whatever – that's the one you've got.

Don't be surprised to find that the polarisation of the LNB – this is best adjusted for minimum cross-polarisation of the unwanted signal – is not exactly horizontal or vertical. Unless the satellite is due south you'll be looking at it somewhat obliquely.

If you cannot make sense of Music Box you've either got Sky which is scrambled, or Norway on the wrong satellite (Eutelsat I-F2) with MAC-C encoding. If the picture looks o.k. but the sound is in German you're on the right satellite but the wrong channel – watching Music Box on Sat-1, one channel down.

Keep monitoring the signal as you tighten the adjusters on the mount. You can easily lose the picture altogether as you wrap up the job.

Polar Mounts

In the three decades during which this writer has contributed to *Television* he's always left the awkward bits till last. This is no exception.

The current trend is to use polar mounts. These permit the dish to be swung round either by hand or a motor to follow the Clarke Orbit, stopping at any satellite at will. If this could only be done by a single simple adjustment to the azimuth it would be a piece of cake, but unless you are either at the North Pole or the Equator (strictly speaking the Clarke Orbit isn't visible from the Pole) the orbit, as seen from the ground, is not a simple radius but an oblate ellipse. To correct the dish tracking truly, so that it follows the orbit exactly right down to the horizon, would require a complex tracking mechanism of the kind found on an observatory telescope. In practice however it's sufficient to offset the dish so that it leans a few degrees forward on its mount when facing due south.

For most of central England this declination is 7°. It varies by only the odd degree over the whole range of latitudes we occupy (see Fig. 6). If you swing a polar mount you will see that the effect of this offset is less as you get to the horizon, compensating for the extra distance between you and any satellites at the two ends in comparison with a satellite at the meridian a mere 22,300 miles away. All this is difficult to check because there are few satellites that can be received well enough at the horizon. Provided the dish tracks well enough over the centre of the range it will suffice for your purposes.

You must first ensure that the hinge of the dish is pointing exactly due south. Don't bolt it down yet as you may have miscalculated. Start with the average offset (or use the table provided with the dish) and capture Eutelsat I-F1 as previously described. Then swing round to Intelsat

VA F11 and note how much elevation (upwards) or declination (downwards) you need to capture the signal. So that you can get back to them, mark your settings at every turn on the adjusters using a Magic Marker. The best two channels to use for alignment are RAI on Eutelsat I-F1 – this is at the other end to Sky, with the same polarisation – and Children's Channel (shared in the evenings with Premier/MirrorVision) which has the same polarisation but is on Intelsat VA F11.

Since RAI is at 11.005GHz and Children's Channel at 11.015GHz virtually no retuning will be needed. Thus whatever errors there are will be due to incorrect setting of the polar mount. If for optimum resolution of Children's Channel you have to point the dish upwards it means that your hinge is too much to the east of south. If you have to point the dish downwards it's a little to the west. Adjust it and try again.

Once signals from these two satellites are coming in at equal strength check the polar tracking of the dish by picking up Eutelsat I-F2 at 10°E. This has NRK (Norway) with MAC-C encoding on virtually the same channel as Sky on Eutelsat I-F1. You should also now be able to pick up Intelsat V F2 at 1°W, where you can usually tune in two scrambled channels. This will enable a precise check on the declination adjustment to be made. If elevation

adjustment is needed to optimise reception from this satellite do it with the declination screw, noting how much change is required, then set the declination to half the error, making up the rest with the elevation screw.

It's quite likely that the tracking may still be out towards the horizon, but there's little to see down there at present. The next launches of any interest, Eutelsat I-F4 at 7°E and the French/German DBS satellites at 11°W, are well within the arc of the adjustment achieved. A new head end will be needed for the DBS satellites since their channels start above the high end of the ones at present in use.

Note that for best results as you swing between Eutelsat I-F1 and Intelsat VA F11 the polarisation of the LNB should be optimised to reduce interference from signals with the other polarisation.

All that now remains is for you to tighten up all your adjustments and grease well around their threads.

Next Month

Having got you started, the next part in this series will recap on the basics of satellite TV reception and look at some of the equipment available. The final part will deal with the theory in more detail and discuss future trends.

VCR Clinic

No Playback: JVC HR2650

Two general rules of thumb apply to VCRs that return to the stop mode a few seconds after play has been selected. First, if the tape loads to the heads, or even partially to the heads, and the machine then cuts out, the fast forward and rewind modes appearing to function correctly, suspect missing drum pick-up head pulses. If however the VCR plays for a few seconds before cutting out, while fast forward and rewind also trip out soon after selection, the problem is that the machine thinks the tape spools aren't rotating due to the absence of reel pulses or take-up pulses depending on the model in question. In this case there's usually no counter movement during the brief time that the tape is moving, since these pulses are used to drive the counter. This would apply to electronic counters and not the earlier mechanical counters, though it should be mentioned in passing that in the early JVC piano-key machines there are no take-up pulses when the counter belt is displaced.

And so to the machine under consideration. The HR2650 is a small portable VCR with stereo sound capability. It runs off a rechargeable 12V battery and has an accompanying tuner/charger unit. The fault with this one was no play, though an apparently good picture did appear for a few seconds. Fast forward and rewind were equally brief and what caught my eye was that the tape running indicator LED was illuminated all the time. All this pointed to an absence of take-up reel pulses, so the outside covers were removed and sure enough the pulses at pin 1 of connector 3 on the front control panel were found to be very weak, less than one tenth the amplitude the diagram said they should be. This voltage swing would be insufficient to activate the operational amplifier in IC6 and thus give an output to the tape running indicator, the counter and the mechacon panel. The problem was due to the reel sensor itself. Before condemning it we removed it

*Reports from Christopher Holland,
Philip Blundell, Eng. Tech., Mick Dutton
and Jeff Herbert, G4JJH*

and checked that there was no dirt affecting its optocoupler, something we've encountered previously with other machines. C.H.

Samsung V1510T

A number of these Korean made VCRs have passed through our workshops recently. Amongst the run of the mill problems of head cleaning and extracting foreign objects from the mechanism, something that seems to go with front-loading machines, we've on several occasions had no playback colour. The usual cause seems to be poor quality 4.43MHz crystals that either won't oscillate or can't be adjusted properly. If both crystal oscillator circuits work correctly however try a recording. If this shows that the drum servo is out of lock in the record mode the fault is due to the colour a.f.c. circuit which also provides sync pulses for the drum servo. Check for a bad joint at plug 11-16. C.H.

JVC HR7650/Ferguson 3V31

The machine JVC brought out to replace the HR7700 proved to be much more reliable. A problem I've encountered on several occasions however has been absence of any reel motor drive. A check on the mechacon panel will reveal that transistors Q18 and Q19 have blown apart physically. Further checks with an ohmmeter will show that Q10 and Q11 have also failed and will lead you to the ultimate cause of the mayhem – Q15 which will be found to be short-circuit. Don't use the nearest European style transistors as equivalents – this will only end in tears, not to mention small puffs of smoke as the replacements expire shortly afterwards.

Another problem I had with one of these machines was a complaint about intermittent failure to eject a cassette.

We could never produce the fault in the workshop and every time suggested that the owner bring along a tape that wouldn't eject. He replied that it happened only with library tapes and that this couldn't be the problem as no one else complained. Eventually the machine came in with the owner clutching a cassette. One attempt at ejecting the tape showed the cause of the problem: the library proprietor was sticking code numbers on dymo tape on the body of his cassettes in such a way that they caught on the left-hand side of the cassette housing during an attempt at ejecting them. Naturally only this model was affected. The customer was quite happy with the solution we offered: pull off the dymo tape each time and stick it back afterwards. **C.H.**

Philips VR6460 and Clones

These machines use special Torx screws to hold the motors but the manual doesn't say which size of screwdriver is needed – and there are 25 to choose from! Many thanks to my SEME rep. Dale for telling me that it's Torx size T10. This size doesn't fit the rotating guides however – does anyone know which size does? I've had a few cases of Finlux and Marantz VCRs with too little take-up torque – this causes tape spillage on forward search. Replacing the reel motor usually cures this. **P.B.**

Mitsubishi HS700B

Any intermittent sound or erase problems with this machine should be cured by removing plugs AF and DF and soldering the wires directly to the audio panel and the full erase head. **P.B.**

Hitachi VT11/GEC V4100

Over a period of several weeks I struggled with one of these machines that had a very intermittent capstan speed fault. What would happen is this: the machine would play a three-hour tape all the way through without a fault, but if it was rewound and played a second time the capstan would be "held back" and rotate very slowly – even though its voltage was sufficient. Changing the capstan motor had no effect, but changing the clutch assembly seems to have cured the fault. I hope . . . **P.B.**

Sharp VC9700

Timer display faults are quite common with this machine. The two usual ones are as follows: either no or intermittent display due to C5005 or the timer microcomputer chip I5002, or the display goes dim after an hour due to PR6601 on the audio board. **P.B.**

Blaupunkt VCR

This machine (a Panasonic NV333 in disguise) came in because the tape was playing too fast – it looked more like search speed than play speed. The output voltage from the servo was correct and an FG pulse was being fed back from the motor. We concluded that the capstan motor was faulty: a replacement plus setting up restored normal operation. **M.D.**

Hitachi VT7000

This portable had been dropped on to its base with the multi-plug that connects it to the timer/power supply unit

plugged in. The result was a cracked PCB around the connection socket. There's a lot of very fine print in this area and much careful work was required. We eventually got the machine to work but there was no colour. This was traced to a crack in the chroma panel under a plastic fixing lug. **M.D.**

Ferguson 3V31

This machine wouldn't load a tape and the drum motor was running all the time. Although the loading arms were fully retracted it seemed the machine thought that loading was at least partly completed. An investigation of the lower mechanism revealed that the after-loading switch had jammed. Freeing this restored normal operation. **M.D.**

Ferguson 3V35

The complaint was that noise bands moved up the picture at regular intervals on playback. We found that a recording made on the faulty machine had the same noise bars (tracking errors) when played back on another machine. On both machines the sound was perfect, with no wow or flutter. The capstan servo was ruled out therefore and investigations were made in the drum servo circuit. While playing the standard test tape the usual "clover leaf" strobe effect on the head drum screws could be clearly seen to rotate at regular intervals that coincided with the noise bar travelling up the screen. Since the drum servo obviously wasn't locking the drum discriminator adjustment R463 was checked as detailed in the manual. The slightest turn resulted in the picture breaking up into lines (the servo going way off speed) then returning slowly to a locked picture. It was impossible to adjust for 4.6V at TP423 with a digital voltmeter as the voltage was varying all the time.

Scope checks on the drum FG signal were normal but the output from the frequency-voltage converter in IC404 was incorrect – pulsating d.c. at pin 15 with a superimposed sawtooth, where the stable drum speed correction voltage should be. Replacing IC404 made no difference but when the feedback resistor R466 (270kΩ) was checked it turned out to be open-circuit. Replacing R466 corrected IC404's output waveform and after R463 was adjusted a perfectly locked picture with no noise bands was obtained.

I had the same machine in a month before with a similar complaint, but at that time it could be locked by adjusting R463. I suspect that R466 goes high in value before going open-circuit and would recommend checking it whenever the drum servo requires adjustment. **J.H.**

Hitachi VT63/GEC V4005

The drum and capstan motors both stopped just after the tape had loaded: the spool rotation sensor then returned the machine to the stop mode. When rewind or fast forward were pressed the brakes released but there was no spool rotation. This turned out to be due to loss of the 12V supply from the STK5451 regulator i.c. During motor start-up 16V is applied to the motor drive chip IC603. Once the motors are running the microcomputer i.c. switches on the regulator to provide the 12V output. The 16V line is used in the search mode to supply the extra load with the increased motor speeds. This provided the

clue. Fitting a new regulator chip (IC151) cured the trouble – the internal 12V regulator produced no output.

We've found that the capstan bearing is very often noisy on these machines, causing groaning and vibration. This can be difficult to diagnose as it's often intermittent and stops when the machine is put on end to remove the

bottom cover. Hitachi technical recommend that the capstan flywheel is removed and the chromed shaft checked for scoring. Renew if marked, then lubricate with Castrol MS3 grease. We now do this as a matter of course when these machines come into the workshop. To date lubrication has provided a cure in every case. **J.H.**

Simple RGB Interface Circuit

Brian Webb

Having recently bought a computer with RGB output, and realising the advantages of using this mode of direct c.r.t. drive to eliminate the cross-colour and bandwidth limitations that are inherent in the PAL system, I decided to convert a ten-year old GEC colour set to RGB input as cheaply and as simply as possible while still maintaining safety.

The first requirement (a must) was to provide mains isolation for the chassis. A suitably VA rated 1:1 ratio transformer is used for this purpose, with the set's chassis earthed via the earth pin of the mains plug. Such a transformer can be expensive: I have it in a separate box so that it can be readily used for other purposes, e.g. servicing, making the purchase more economic.

Circuit Description

The circuit I decided upon (see Fig. 1) was kept as simple as possible while maintaining an upper working frequency of around 10MHz. The 74LS240 TTL chip was chosen for its high speed and cheapness. It's an eight-stage inverting buffer with separate enabling for the two groups (A and B) of four buffer/inverters. The RGB inputs are applied to three of the A group buffer/inverters with enabling from the sync input, ensuring good blanking. The sync input goes to one of the B group buffers. Another can be used depending on the requirement for positive- or negative-going sync pulses in the timebase department. The output from a TTL circuit at 5V peak-to-peak may be too large for some timebase arrangements. Fig. 2 shows a simple emitter-follower to enable the pulses to be potted down. It may also be necessary to use this circuit where there's a long run to the timebases – a suitable screened cable may also be required.

The GEC solid-state C2110 series chassis, like many of its contemporaries produced during the early 70s, uses a TBA920 sync separator/line generator chip. This will work directly from a TTL buffer, positive-going sync pulses being required.

Should connecting the sync input to the timebase section of the set be rather impractical an alternative option that could be adopted is to use an off-air signal, feeding the demodulated video to the sync separator in the usual manner. The sync signal available at the RGB socket should still be used for blanking.

The digital RGB signals are fed to the emitters of the three BF259 RGB output transistors via 2.2kΩ presets. These are used in conjunction with the set's first anode controls to set up the black level.

Construction

Spread the circuit out as much as possible, bearing in mind that the output transistor collector load resistors

dissipate a certain amount of heat – a heatsink should be provided for the transistors themselves. Also remember that since the upper working limit of the circuitry is hopefully around 10MHz suitable separation should be used – especially if construction is on Vero board.

I disconnected the i.f., sound, colour decoder and video drive sections of the set. This has the advantage of minimising the power across the isolating transformer.

The older type of delta-gun tube can give a good account of itself at up to 10MHz. The convergence has to be looked at carefully, especially with a computer display.

Remember good common chassis connections throughout.

I hope the circuit presented here will give you ideas for cheap ways to improve your computer displays. Have fun with it!

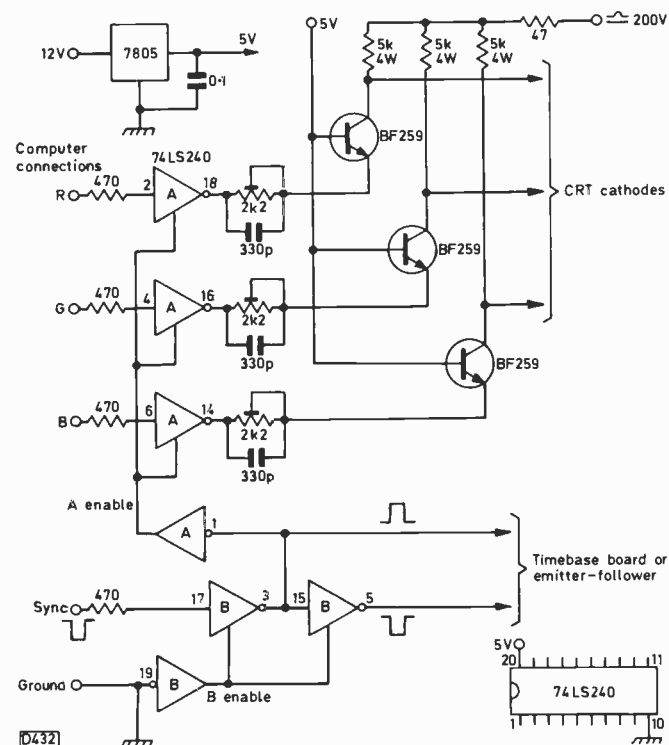


Fig. 1: RGB/sync interface circuit.

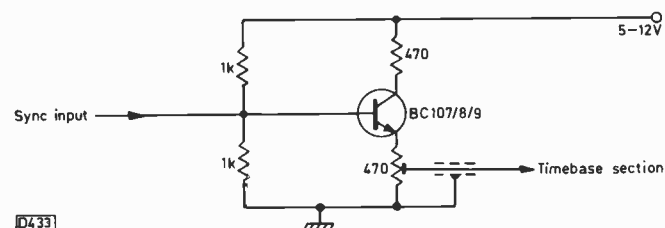


Fig. 2: Emitter-follower stage for sync pulse interfacing.

Teletopics

TVRO RECEIVER IN KIT FORM

Here's something of a breakthrough in the cost of satellite TV reception. Comex Systems Ltd. (Comet House, Unit 4, Bath Lane, Leicester LE3 5BF, telephone 053 325 084), the small order trade and retail distributors for Astec TVRO modules, TV and computer products, have introduced a TVRO receiver in kit form. The kit comprises a motherboard and components for mounting the r.f. and i.f. modules, the video, control and i.f. circuits, plus two Astec modules, a tunable converter covering 950-1,450MHz and an i.f. processor with wideband f.m. quadrature detector. The board is silkscreen printed and is simple to construct. Detailed paperwork covers the many possible options for the board's use - the kit has been designed for versatility. Comex is also able to supply much of the other equipment required for a satellite TV receiving installation - dishes, wideband preamplifiers, F type plugs (at least one is required for the board), scalar horns and Mitsubishi heterodyne converters. Price details are as follows:

TVRO receiver motherboard and component kit	£35.00
Motherboard only	£11.75
Astec AT1020 tuner module	£35.10
Astec AT3010 i.f./demodulator module	£54.65
F type plug for AT1020	£00.50
Mitsubishi 10GHz heterodyne receiver	£47.00
Scalar horn for above	£42.00
60-1,700MHz wideband, low-noise preamplifier kit	£35.00

F-to-BNC adaptors are available at £1.70 each. The prices include VAT. For orders below £100 add £1.50 post and packing, for orders above £100 add £2.50. Comex plans to introduce shortly a tuning display for the TVRO receiver, a tunable sound i.f. giving the kit stereo sound, a keyer unit and a portable power supply with 13.8V input and 18V output. A 1.6m spun aluminium dish with polar and horn mounts is available at £365. Comex can also supply ATV transmission equipment for the 23cm band.

IBA TO REPLACE TRANSMITTERS

The IBA has started a u.h.f. TV transmitter replacement programme that will involve expenditure of around £40 million - some of the existing transmitters are now over twenty years old. A £7.5 million contract with Marconi Communication Systems has been signed covering the first phase of the programme. This provides for replacement of the original fourteen high-power transmitters. Associated engineering work will bring the total cost to £11.5 million. The programme envisages transmitter replacement at a rate of six a year starting in 1988.

EUROPE ADOPTS MAC

European trade ministers, meeting in Luxembourg, have decided to adopt the MAC-packet system as the standard for satellite TV transmissions to Europe. The advantage over the Japanese high-definition system that has been advocated as a worldwide DBS standard is that MAC signals can be decoded and displayed on a standard TV receiver. The system allows for a wider aspect ratio with higher definition to be added, again compatible with

existing European TV standards. The agreement lasts until the end of 1991 and allows each Community country to choose the system best suited to its needs, provided it conforms to the basic MAC specification - whilst C-MAC is favoured by the UK, a variant known as D2-MAC is favoured by France and W. Germany. A chip to make these two systems compatible is being developed. The whole DBS program has unfortunately been put back by the recent Shuttle and Ariane failures.

The board of Eutelsat has received a report on the potential for a European DBS system called Eurosat. What further action to take on this project will be decided at the board's next meeting in September.

NEW SALORA/LUXOR TVRO EQUIPMENT

New satellite TV receiving equipment is to be introduced by Salora and Luxor at Cable 86 (July 8-10th), the satellite and cable TV show. Salora's new receiver, Model SRV1150, features remote control. The ACU1160 actuator control unit is also new and the equipment available includes an aerial actuator with polar mount and a polariser with 1.2m dish. A similar range is available under the Luxor brand name.

MICROELECTRONICS SERVICING SEMINAR

The Institution of Electronic and Radio Engineers (IERE) and the Society of Electronic and Radio Technicians (SERT) are to run a one-day seminar, entitled Microelectronics Repair and Maintenance, at the Royal Institution of Great Britain, 21 Albermarle Street, London W1 on September 9th. Application forms can be obtained from the IERE Conference Dept., 99 Gower Street, London WC1 (01-388 3071). Registration fees, inclusive of attendance, documentation, coffee, lunch and tea, are: £45 plus VAT, members rate £35 plus VAT (members of the IERE, IEE, SERT or IEEIE), or £16 plus VAT for student and retired members.

TENSAI AND WINTRONICS SPARES

Our thanks to readers who have come up with sources of spares for Tensai and Wintronics TV sets. Spares and data for Tensai sets are available from the UK agents John Walker Ltd., First Floor Suite, 55 North Street, Thame, Oxfordshire OX9 3BN (telephone 084 421 6929). For Wintronics spares and data contact Laltex and Co., Ltd., 1 Canal Street, Manchester (061-832 6132).

ZANUSSI CHANGE

Seleco UK, 43 West Street, Reading have taken over from IAZ International (UK) Ltd. the UK distribution of Zanussi TV receivers. A new range of models is being introduced.

GOOD BUSINESS IN CASSETTES

The British Videogram Association reports record first quarter sales of prerecorded video cassettes by its members. Approaching a million cassettes worth over £24 million were distributed, an increase of 32 per cent compared to the same period in 1985.

A report entitled *Home Video Recorder Populations and Cassette Usage*, distributed in the UK by Benn Electronics Publications Ltd. (Chiltern House, 146 Midland Road, Luton, Beds LU2 0BL) for US consultants Magnetic Media Information Services Inc., predicts a fourfold increase in worldwide sales of video cassettes by 1989 (compared to 1984). It expects sales to reach 2.5 billion units in 1989, including both prerecorded and blank

tapes. The report expects 140 million VCRs to be in use worldwide by 1989. A fall in Japanese VCR production of 10 per cent in 1986 (the first ever) is predicted, with further falls of 13 per cent and 15.5 per cent in 1987 and 1988 respectively. This is likely to depend very largely on currency movements. The report is available from Benn at US\$995 per copy.


Market research consultants Mackintosh International (Mackintosh House, Napier Road, Luton, Beds LU1 1RG) have also published an optimistic report which predicts an "explosion" in the market for consumer tapes and discs over the next ten years. The 500-page report, entitled *Discs and Tapes - the next ten years*, expects the world market for consumer discs and tapes to reach a value of \$30 billion by 1995.

NEW GENERATION INDOOR TV AERIAL

Antiference have introduced an interesting new indoor aerial which has taken two years to develop at a cost of a quarter of a million pounds. Its performance is certainly impressive, with a forward gain of 6-8dBd across the entire u.h.f. bandwidth and good directivity. While the design is basically a log-periodic one the elements are formed on two aluminium sheets giving a large surface area. The Silver Sensor incorporates electrical isolation to BS5373 and is expected to retail at around £10. For further details apply to Antiference Ltd., Bicester Road, Aylesbury, Bucks.

TELELIFT's UK LAUNCH

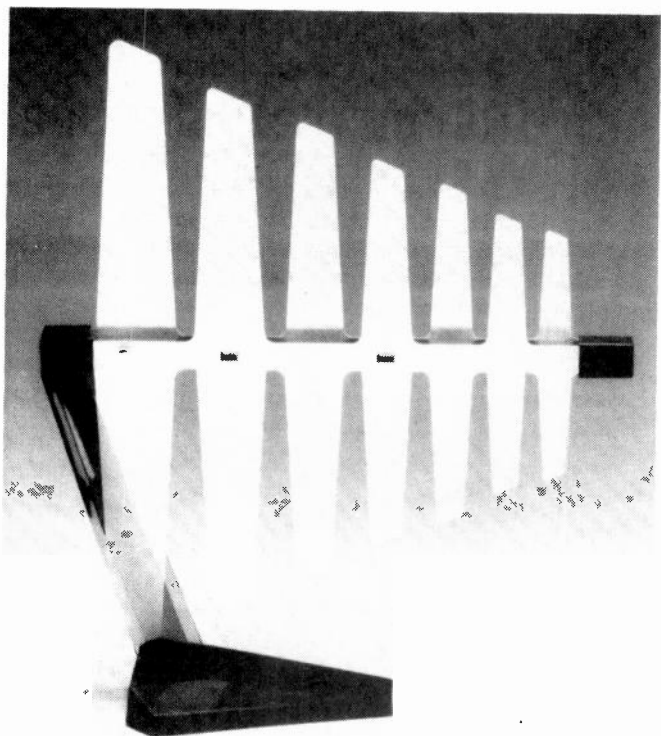One of the dangers - a very real one - to which those in the TV trade are exposed is injury caused by lifting and manipulating heavy TV sets. It will be avoided by the use of a new trolley which has been designed to enable one person to transport safely heavy TV receivers and other domestic appliances. The Telelift trolley comes to the UK after three years of extensive field trials both here and



The Antiference Silver Sensor log-periodic set-top aerial, shown here with the boom position for reception of vertically polarised transmissions.

abroad. To date it has moved over half a million sets without injury to users. The trolley incorporates a number of well thought out features. It enables a bulky console set to be rotated to allow passage through narrow doorways, has a built-in suspension system to protect delicate mechanisms, provides lifting into and out of vehicles and incorporates a unique, patented stair climbing system. The Telelift is available from Courier Handtrucks Pty, Ltd., 59 Earls Court Road, London W8 6EE (01-937 1996) at £139 plus VAT and transport.

According to the National Institute for Safety and Health, Washington DC, USA serious and permanent spinal injury is likely if an attempt is made to lift a TV set or appliance weighing more than 44lb from ground level to workbench height, regardless of body size. Use of the Telelift trolley, which is solidly made and should give many years trouble-free service, is recommended.

NEW COLOUR PATTERN GENERATOR

A versatile, mains-operated colour pattern generator, designed and manufactured in the UK, has been introduced by Black Star Ltd., 4 Stephenson Road, St. Ives, Huntingdon, Cambs PE17 4WJ (048 062 440). The Orion pattern generator has been developed for those engaged in servicing, manufacture or design of TV sets, VCRs and monitors. Features include separate r.f. and composite video outputs with level control, tunable r.f. carrier, internal or external sound modulation, switchable sound carriers (5.5, 6 and 6.5MHz) and positive or negative vision modulation. A front panel source of field and line sync pulses is provided for scope triggering. The generator covers the v.h.f. and u.h.f. channels and is compatible with the PAL systems B, D, G, H, I and K. The full range of colour and monochrome test patterns includes colour bars, grey scale, focus, raster purity, dots, gratings and vertical/horizontal lines. There are also rear panel R, G, B and sync outputs with switchable signal levels and sync conditioning to ensure compatibility with the majority of video and computer monitors. We expect to publish a review of this generator in the next few months.

VCR SPARES DISCONTINUED

Ferguson have announced that from August 1st spares will no longer be supplied for the following VCRs, tuners and cameras: Models 3292, 3V00, 3V01, 3V03, 3V04, 3V06 and 3V17. In addition cabinet and presentation parts will from the same date no longer be available for Models 3V20, 3V23, 3V24, 3V25, 3V26 and 3V28.

REMOTE CONTROL BOOSTER

A booster unit for use with infra-red remote control transmitters has been released by Advanced International Marketing (UK) Ltd., 74a Heath Road, Twickenham TW1 4BW (01-891 3644). The Tyron "power enhancer" is said to increase the range of an IR transmitter to 40-50ft and make careful aiming unnecessary. It simply clips on and operates from a 9V battery.

MITSUBISHI DEVELOPMENTS

Mitsubishi has announced in Japan the development of a 40in. colour tube along with a monitor/receiver to drive it. It's intended initially for business use and is to be shown at the Chicago Summer Consumer Electronics Show. Also announced are a 200in. projector system with a newly developed optical arrangement and the Mark II version of the Diamond Vision colour display system. The latter has a display size of 4.8 x 3.6m and weighs three tons.

Modern Receiver Circuitry

Part 5: Timebase Synchronisation

J. LeJeune

Faithful reproduction of a television picture depends not only on adequate video bandwidth, accurate colour decoding and luminance-chrominance registration but also on precise synchronisation of the line and field scanning in the camera and the receiver. The use of integrated circuits has led many service engineers to take synchronisation for granted, but a knowledge of the basic circuits and principles is always an advantage.

One requirement for precise synchronisation is that the received sync pulses are free from impulsive electrical interference and noise generated in the receiver's tuner and i.f. strip. With simple, direct sync the effect of noise is ragged verticals and occasional loss of field sync. An important step in improving the line synchronisation is to use an indirect system to control the line oscillator – the flywheel line sync system, in which the timing of the received line sync pulses and the line flyback pulses is compared by a phase detector which produces an error voltage to pull the oscillator back into lock. With this arrangement the oscillator is controlled by a voltage that's proportional to the phase difference between the incoming sync pulses and its own operation. The speed of the correction can be slowed down by including a time-constant in the phase detector's filter circuit: the effect of this is to give correction of longer-term drift while making the system immune to short-term disturbances such as interference and internally generated noise.

Simple Transistor Sync Separator Stage

Before any synchronising arrangement can work it requires a clean sync pulse which has been separated from the composite video signal. A simple transistor sync separator stage is shown in Fig. 1(a). The demodulated composite video signal, with positive-going sync pulses, is fed via C1 to the base of the transistor. The important thing is that the output should consist of sync pulses only, i.e. with no picture information. C1, R1, R2 in the base circuit provide the conditions required for this. R1 and R2 apply a small bias voltage to Tr1's base – too small to bias Tr1 as a normal class A amplifier. Tr1 conducts when a positive-going sync pulse appears at its base. The combination of the small bias provided by R1, R2 and the positive-going sync pulse drives Tr1 into saturation. As a result, the tip of the sync pulse is clipped, thus removing noise – see Fig. 1(b). When Tr1 saturates the coupling capacitor C1 will be charged by Tr1's base current, acquiring a negative charge on its right-hand plate. This holds the transistor cut off during the picture part of the line scan. During this period C1 discharges via R1. The time-constant is such that Tr1 will saturate rapidly as soon as the next sync pulse arrives. The value of R1 is thus important – it's a common cause of sync problems in some chassis.

Flywheel Line Sync

The sync separator stage itself cannot provide sufficient immunity against interference – which with negative-going vision modulation is of the same polarity as the sync

pulses. Thus for good line locking the flywheel sync system already touched upon must be used.

Fig. 2 shows a typical discrete component flywheel line sync phase detector circuit. The inputs consist of negative-going line sync pulses which are coupled to the cathodes of diodes D1 and D2 by C1 and a flyback pulse from the line output transformer. The flyback pulse is integrated by R4 and C4 to produce a sawtooth waveform that's coupled to the detector circuit by C2. Capacitive coupling removes any d.c. component, ensuring that the waveform at the junction of D1, R1 swings positively and negatively about zero volts. D1 and D2 conduct when a negative-going sync pulse arrives. If the sawtooth voltage is at zero at this time synchronisation is correct and the circuit produces zero output. If the sawtooth is positive with respect to zero volts when the sync pulse arrives the circuit will be unbalanced: D1 will conduct more than D2 and C1 will acquire a positive charge. This is filtered and used to adjust the phasing of the line oscillator. Conversely if the sawtooth is negative with respect to zero when the sync pulse arrives D2 will conduct more than D1 and C1 will acquire a negative charge. C2 fulfils two functions in this circuit configuration: it acts as coupling capacitor for the sawtooth and as the reservoir capacitor for the output – the charge established on C1 when D1/2 conduct is transferred to C2 during the picture period. R3/C3 provide filtering and R5/C5 add a time-constant to the filtering action to damp the effect of short-term disturbances.

The Modern Approach

The circuit just described is rather crude in comparison with the arrangements used in modern sync processing/timebase generator chips. It nevertheless forms the basis of flywheel line sync action. A typical modern sync processing chip may provide line and field drive signals, AV switching, between-channel sound muting and a sandcastle pulse that's used for flyback blanking and burst gating.

A block diagram of a typical sync processor i.c., the TDA2578A, is shown in Fig. 3. Composite video is fed in at pin 5 where it goes to the sync separator. The slicing level is determined by the components connected to pins 6


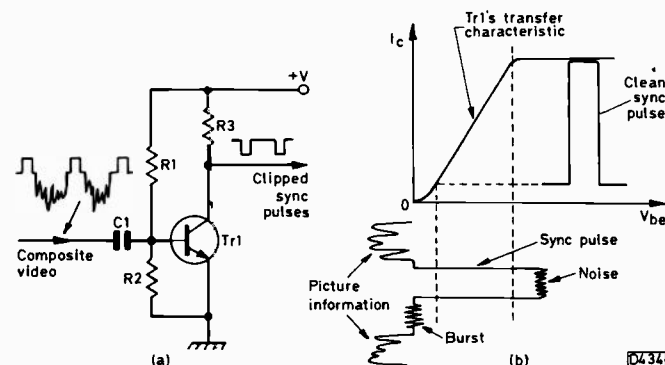


Fig. 1: Simple sync separator circuit using a transistor (a), operating conditions (b).

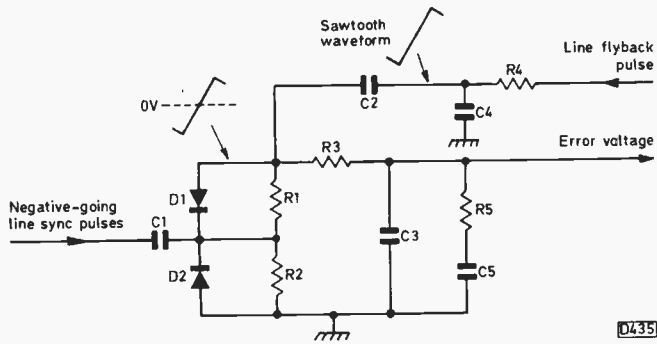

D435

Fig. 2: Typical discrete component flywheel line sync circuit. Note the RC time-constant network in the filter.

and 7: this level is maintained over a wide range of video input signal levels. The output from the sync separator goes to a pair of phase detectors, 1 fast and 2 slow, to a coincidence detector, and to the field sync pulse integrating stage. It also goes to a burst timing circuit which produces a pulse to coincide with the colour burst: this pulse forms part of the sandcastle pulse output at pin 17.


Phase detectors 1 and 2 have different response times and are used to lock the line oscillator to the incoming line sync pulses. The gating circuit determines which phase detector is used. For good noise immunity with off-air reception the phase detector with the slow response time is used. With an off-tape signal a faster response time is required: the AV switching thus brings phase detector 1 into operation. The fast-acting phase control loop is also used to restore sync rapidly after momentary loss of signal due to a change of channel and when the set is first switched on.

In the absence of a video signal the coincidence detector brings the muting circuit into operation. The voltage at pin 13 will then be at about zero and can be used to give inter-station sound muting.

Although the line oscillator has been locked a further problem has to be overcome before a completely stable picture can be guaranteed. With a power transistor such as the type used in the line output stage there's a time delay between the removal of the base drive and the cessation of collector current. This delay lengthens as the demand made on the line output stage increases. Nearly all line output stages are called upon to generate flyback e.h.t., and the beam current requirements will vary rapidly from one moment to the next. The timing of the line drive switch-on is not too critical since there's some overlap in the operation of the line output transistor and the efficiency diode. The timing of the line drive switch-off, i.e. the start of the flyback, is critical however since it governs the position of the picture within the raster. A second control loop is used to offset the effect of delays in the line output device. Phase detector 3 compares the output from the line oscillator with the line flyback pulses. Its output adjusts the timing of the trailing edge of the line drive pulse via a pulse width modulator circuit. The central position of the picture is thus maintained. A d.c. voltage can be applied to pin 14 for horizontal shift purposes.

The field sync pulse integrating capacitor is connected to pin 4. The field oscillator stage is simply a discharge circuit for the field ramp capacitor connected to pin 3: the capacitor is charged from a relatively high voltage via a high value resistor. The sawtooth produced in this way is scan-corrected before passing to the linearity correction section where feedback from the field scan circuit is applied. The voltage at pin 2 is also monitored for tube protection purposes: if the voltage at pin 2 is less than 2.5V or more than 5V the screen blanking circuit produces 2.5V at pin 17 to give a blank screen.

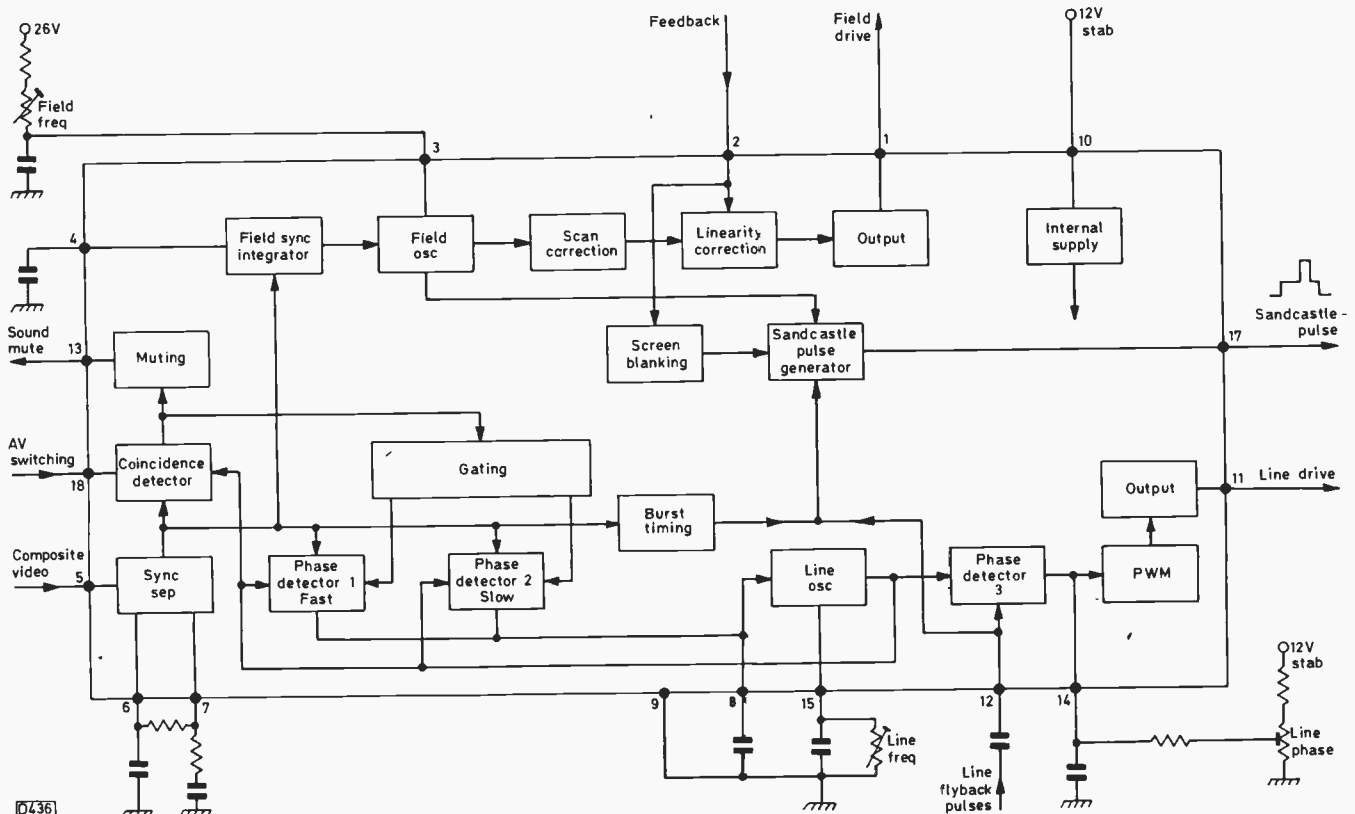The sandcastle pulse generator produces a composite blanking and burst gating pulse at pin 17. The output here is at three levels: 2.5V gives field flyback blanking and



D436

Fig. 3: Block diagram of a modern sync/timebase generator chip, the TDA2578A.

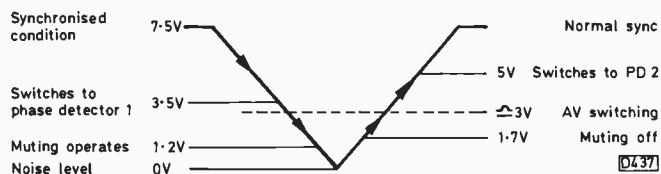


Fig. 4: Voltage conditions at pin 18 of the TDA2578A for flywheel sync phase detector switching and sound muting.

4.5V line flyback blanking. The 10V burst gating pulse sits on top of the line flyback blanking pulse.

Fig. 4 shows the voltage levels at pin 18 under various conditions. With the set receiving a TV transmission the synchronised condition will be marked by the presence of

7.5V, phase detector 2 will operate and the muting circuit will be inoperative. When the receiver is detuned the voltage at pin 18 will fall: phase detector 1 is switched in at 3.5V and muting operates at 1.2V. With no signal the voltage is approximately zero, rising again as another signal is tuned in. Muting ceases at 1.7V and return to control by phase detector 2 occurs at 5V. Application of an external AV voltage of approximately 3V for VCR or disc playback purposes should produce control by phase detector 1 without muting: the AV voltage should obviously be stable – to prevent unwanted switching to control by phase detector 2 or muting.

This then is the contemporary way of generating and synchronising the set's scanning signals.

TV Fault Finding

Reports from Steve Leatherbarrow, Philip Blundell, Eng. Tech., Hugh MacMullen, Keith Hamer, Garry Smith and J. K. Potts

Ferguson TX9 Chassis

Intermittent colour can be a problem and this case was no exception. A fellow engineer had attacked the set with freezer and a hairdryer: after demonstrating his ability to produce colour at will he replaced the crystal. The set then worked all right in the shop for a couple of days after which the colour went off. With the set back on the bench we found that heating the TDA3560 decoder chip brought back the colour. Unfortunately heating the replacement chip had the same effect.

Careful examination of a test pattern revealed what looked like a slight hum bar. Like a man possessed I stabbed the meter on the 115V rail. Bingo! – a good 6V low. Resetting the h.t. voltage removed the hum from the picture and put an end to the thermal sensitivity of the decoder circuitry.

This time the set gave four days' service before the colour went off again. I'll save you from reading through the rest of the torture. Suffice it to say that if similar problems come your way it pays to replace the chroma delay line before going any further. It seems that everyone was aware of this except me.

S.L.

ITT CVC32 Chassis

This set had the rather daunting symptoms of no bottom scan accompanied by distorted sound. The remote control unit worked outside the set but not when in the "parked" position. What field scan there was in the top half of the screen was non-linear and "synchy". We eventually discovered that the 35V supply reservoir capacitor C64 (2,200 μ F) was responsible for all the symptoms, the only clue being that the 35V rail was 3V low.

While on this chassis, the symptom of low h.t. when cold (or sometimes when warm just to add to the fun), often intermittent and looking like a fault in the chopper control module, is often due to the h.t. smoothing capacitor C52 (47 μ F). This capacitor can also produce the fault permanently of course.

S.L.

Grundig CUC41 Chassis

There was low output from the power supply and a loud whistling. The latter is symptomatic of a loaded h.t. rail. A check around the line output transformer revealed an 0.33 Ω safety resistor that was burning. This provides a

feed to the deflection module which, in an attempt to isolate the fault, was removed. The output from the power supply then returned to normal so attention was turned to the deflection module. The rectifier that produces the 25V supply for the TDA2655 field output chip lives on this module – D2751. When it goes short-circuit, as in this case, it loads down the line output transformer. A BY298 seemed to be a suitable replacement.

S.L.

Tandberg CTV2 Chassis

The problem with this set was intermittent contrast variations – the fault was tappable (dry-joints are common in this otherwise excellent chassis). After carrying out some resoldering however the fault was still present. The board was particularly sensitive around the 12V regulator transistor's heatsink and a meter check revealed that the rail would rise to 14.5V. The transistor itself was responsible.

S.L.

ITT 80-90° Chassis

If you're faced with one of these sets that suffers from tuning drift a good place to start looking is in the line output stage! If the 90V supply reservoir capacitor C514 (10 μ F) has dried up the supply will be low, affecting the regulation of the tuning voltage stabiliser.

P.B.

Decca 80 Chassis

This set had suffered from poor field lock for several years. When the set came to us however the report was "dead". The usual faulty tripler had killed the line output transformer and BU208. There was also the common burning of the now famous orange wiring and connectors. After all this had been sorted out the set worked perfectly but with very poor field lock. A hole had been cut in the back for the customer to adjust the field hold control (a very unwise action) – the customer had mentioned that the trouble had been present from new.

The sync output from the TBA920 sync/line generator chip goes to the TDA1170 field timebase chip via an active field sync pulse integrator stage comprising Tr301 and associated components. A check here revealed that

Tr301 had no collector volts and about 2V at its base. In other words either the transistor was hard on or its load resistor R328 was open-circuit. Both the resistor and the transistor were o.k. however. We then found that the field sync pulse at the base of Tr301 was almost non-existent. The next step was to discover why Tr301 had a positive voltage at its base. Every resistor and capacitor in the base circuit was removed, also the transistor itself. We were alarmed to find that there was still a positive voltage at the base print – and the reading was now 100V. This voltage disappeared when the print was cut away 1/8in. back from the base hole. There was no sign of any burning, even when the panel was examined with a magnifying glass, but drilling a few small holes between the base print and the nearby red first anode print cured the fault. I can only assume that the panel had been defective from the start. Incidentally there was no discolouration around the first anode controls and their series resistors – a common problem with these sets. **H.MacM.**

Philips G11 Chassis

A G11 with persistent h.t. fuse blowing caused us quite a problem because the BU208A line output transistor was always o.k. The usual h.t. reservoir electrolytic on the power panel and other components here had been changed and a new BU208A tried just in case. Normal operation might last for days or in some cases weeks and there were never any faulty components to blow the fuse. Once again two pairs of specs and a magnifying glass came to the rescue. There was a microscopic pip on the BU208A's cooling plate. When this was compressed via the insulating pad the result was occasional earthing of the BU208A's collector – with no damage to the transistor itself. **H.MacM.**

Field Judder – sort of

I hesitate to include this item in a fault-finding section – but it shows that you sometimes have to study the owner as well. His complaint was of field judder, but only at certain times of viewing – his set was a brand new Philips receiver but could have been one of any type. We gave it a thorough soak test in the workshop and checked all relevant components but couldn't find anything amiss. After its return the customer made the same complaint – I might add that his previous set, which he'd traded in, had been an old 22in. GEC model with a very dim tube. When conversing with the owner I noticed that he chewed all the time. When he stopped chewing the field stopped bouncing! If you try chewing a tough boiled sweet while looking at the screen you'll find that the crack does cause a definite bounce. **H.MacM.**

Ferguson TX9 Teletext Chassis

The complaint was simple – no sound. Without further ado the sound channel chip's feed resistor R156 was checked for being open-circuit, which it wasn't. The loudspeaker and associated connections proved to be innocent but a check at pin 6 (volume control) of the i.c. produced a very low reading. Operation of the volume control had no effect whatsoever so our efforts were directed to the PC1515 remote control processing board. To prove that the sound chip was o.k. the lead between panel PC1515 and the d.c. volume control input pin on the main panel (pin 5 of PL8) was disconnected. This

restored the sound at full blast. On checking around the volume control output transistor (TR106) on panel PC1515 we found that its emitter voltage was absent. This was due to a dry-joint at one end of D123 (AA143). A dab of solder soon put matters right and the musical delights of boring Ceefax blared out once more. **K.H.-G.S.**

Philips CTX-S Chassis

The symptom was a dead set and our first reaction was to check the 4.7Ω surge limiter resistor which commonly goes open-circuit. It was o.k. this time and there was voltage at the collector of the BUX84 chopper transistor. But not at its base and emitter. The BF422 driver transistor had the same voltages at its collector and base due to a collector-base short-circuit. **K.H.-G.S.**

Panasonic TC2031

A quickie on these sets. If you get called out because the remote-control unit is stuck inside turn the set upside down to release it. Then tighten the screw holding the remote control casing together. The screw works loose due to vibration: it then catches in the housing mechanism. **K.H.-G.S.**

GEC C2110 Series

An elderly GEC Model C2121 came our way recently. The customer insisted that the picture flashed up green intermittently and that water had entered the set from a burst pipe. We couldn't find any sign of water damage and as usual the fault refused to appear during our call (we did notice a dry-joint on the RGB output panel, but this was purely coincidental). Our attention was also drawn to the fact that the local "poke-and-hope" brigade had tried to trace the fault without success – a quick check revealed that the fuseholder had been linked with wire and a 3Ω fusible resistor mounted between dropper sections had been shorted out. These matters were attended to and the video drive presets were then cleaned – these are a common cause of colour flashing in this chassis.

The repair bounced and when we got the set back to the workshop we were able to analyse the fault more carefully. The picture's green content was indeed increasing, especially from cold. The voltage at pin 13 (green output) of the TBA530Q i.c. was erratic, and further discrepancies were encountered when we traced back to the preceding TBA990Q demodulator chip. We swapped over the drive connections between these two i.c.s and the picture then began flashing in blue. The demodulated colour-difference outputs from the TBA990Q are passed to the TBA530Q via simple RC filter networks: C313 (27pF) in the G – Y filter was the offending item – it read leaky on the AVO. **K.H.-G.S.**

Some Quickies

Sharp C2072: For lack of height check C511 (22μF) in the field output stage – it tends to dry out. For no sound check whether R319 (270Ω, 0.5W) is open-circuit.

Sharp C2095: Set dead – check whether the 130V, 1W zener diode ZD702 in the line oscillator supply is short-circuit.

Saba T51S20: A two-inch high unmodulated raster was traced to RL27 (4.7Ω, 1/8W) being open circuit. Don't be misled by no sound on this set due to interstation muting. **J.K.P.**

The Development of Colour Tubes

Part 3

Eugene Trundle

The basic job of the yoke is to deflect the electron beams so that they scan out a raster on the screen. In very small colour tubes the deflection angle may be as small as 50° . The most common deflection angle is 90° ; 100° is widely used in the USA and 110° is popular for minimum cabinet depth, particularly in Europe. The widest deflection angle tubes in regular production are some Trinitron types that have a deflection angle of 114° . These deflection angles refer to the angle through which the beam is deflected in scanning the tube's diagonal. For a 90° tube the horizontal scan angle is 78° , the vertical scan angle 60° .

As we've seen, the key to the self-converging picture tube lies in the distribution of the magnetic field produced by the yoke. The principle was understood and proved as long ago as 1954, when Haantjes and Lubben filed a patent in the USA describing an in-line gun array operated in conjunction with an astigmatic deflection field.

The Precision Static Toroid

Some of the earliest in-line gun tubes used toroidally wound deflection yokes. The precision static toroid (PST) was shown in Fig. 12. It depends for its precision on the exact positioning of every single turn of copper wire in moulded slots at each end of the core. By this means the flux field shown in Fig. 11 is created with sufficient accuracy to need only a trimming adjustment at the factory – the flare end of the yoke is panned and tilted for optimum screen-edge convergence before being wedged and sealed to the glass with hot-melt adhesive.

The PST gives the best possible precision and repeatability in yoke manufacture but does have some drawbacks. Its deflection sensitivity is low, due to the relatively small number of turns that can be wound; it has a powerful stray field and strong coupling between the line and field coils; it runs very warm, due to low efficiency and resulting I^2R losses; it allows the designer almost no freedom in terms of impedance optimisation and restricts the setmaker to low-voltage, high-current output stages; and inherent in it is an effect called coma, i.e. the rasters produced by the outer beams are larger than the raster produced by the centre beam. To correct for coma, early PIL type tubes were fitted with internal magnetic field shapers that were incorporated in the guns – shunts and enhancers for the outer and centre beams respectively. Unfortunately these tended to have a deflection defocusing effect on the outer beams.

Semi-toroidal and Saddle Yokes

The traditional saddle-wound yoke is much more efficient and adaptable. More copper can be got into it and its greater length means that the electron beams stay under its influence longer, giving high deflection sensitivity. The problem is to achieve sufficient precision in the winding of a layered coil to provide the astigmatic fields required for self-convergence. Semi-toroidal yokes made an appearance initially. These have a layered toroidal winding for field deflection and a carefully wound pair of saddle coils

for line deflection. The semi-toroidal yoke halved the power required for vertical deflection and improved the efficiency of the horizontal deflection by 25 per cent.

In their 20AX design Philips/Mullard introduced saddle/saddle yokes. These were refined and improved for the 30AX series. Modern in-line gun tubes use semi-toroidal and saddle/saddle yokes in a variety of designs.

Producing an Astigmatic Field

How is the astigmatic field produced? Fig. 26 shows the basic form of a symmetrical pair of single-turn deflection coils. The angle subtended by each is α . The critical angle for α is 120° : this will generate a homogeneous magnetic field in the gap between the coils. If the angle α is made less than 120° the magnetic field produced will be barrel-shaped: the wide spacing of the coil edges – see A in Fig. 27(a) – permits some of the flux to “escape” at the edges of the field gap, as shown. This is what's required for the field deflection coils. If on the other hand the angle subtended by the coil halves is greater than 120° the distance between the coil edges is small – B in Fig. 27(b) – and the result is a concentration of flux in this region. Here the diametric centre line is subject to the least flux density and the result is a pincushion-shaped field, as required for line deflection in a self-converging tube.

Astigmatism and coma both depend on the magnetic flux distribution. Whereas the main influence on astigmatism is the field distribution at the front (screen side) of the yoke, coma depends on the field distribution throughout the length of the yoke. Here lies the key to generating a coma-free astigmatic field. In the yoke design evolved for 20AX and 30AX tubes the field shape developed by each pair of deflection coils has both forms of astigmatism – see Fig. 28. To achieve this result the line coils are wound with an angle of 90° at the electron gun end

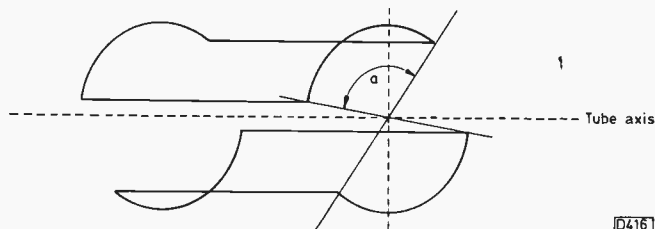


Fig. 26: Elementary scan-coil configuration.

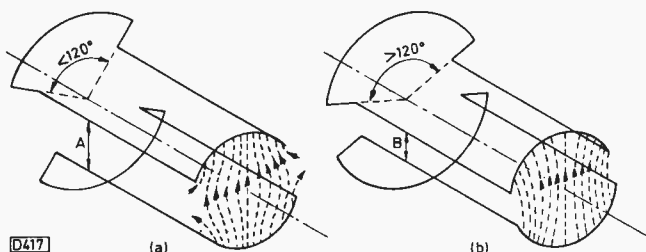


Fig. 27: Winding arrangements for generating astigmatic deflection fields.

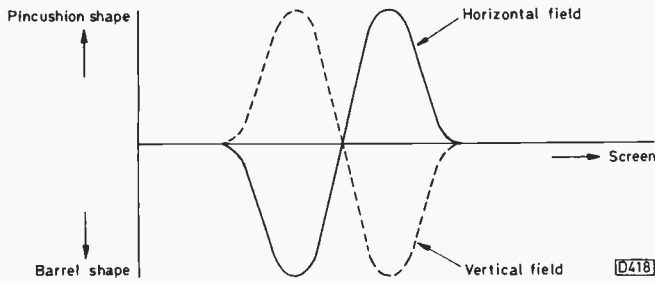


Fig. 28: Field shape engineering for minimum coma. The beam deflection characteristic depends mainly on the curves at the right.

increasing to 150° at the screen end. Conversely the field coils have an angle of 150° at the rear end narrowing to 90° at the flare end. This winding arrangement imparts the necessary astigmatism to the deflection field without introducing the coma effect.

The required winding precision is achieved by the so-called "pin-shooting" technique. Each winding is divided into many sections, the starting point and direction of each being defined by a separate index pin. Cumulative errors are thus avoided.

Four-pole Convergence Coil

Not all in-line gun tubes are fully self-converging. In some consumer tube designs provision is made for dynamic line convergence by means of a four-pole coil – see Fig. 29. This has the effect of pulling the outer beams into registration with the central one and operates at both line and field frequency, as the waveforms show. Parabolic waveforms adjustable for tilt are fed to the coil which becomes the main source of convergence correction. In such tubes the deflection fields are wholly or nearly homogeneous for minimum aberration – Trinitron fine-pitch monitor tubes are an example.

Pincushion Distortion

The flatness of the screen's curvature relative to the image field gives rise to pincushion distortion. It's worse with 110° tubes than with 90° types and is more pronounced with FST screens than with the older, more radiused types. How much correction is called for in the scan drive circuits, in the form of amplitude modulation of the deflection current, depends very much on yoke design. The astigmatic fields required for self-convergence compensate for much of the NS pincushion effect while increasing the amount of EW pincushion distortion.

Various means of countering pincushion distortion can be built into the yoke: cutting and shaping the ferrite cup core; fitting permanent magnets; adding field sharpeners on or within the yoke; and varying the density of winding across the coil's span are examples. By these means pincushion-distortion free tubes have been produced – mainly with 90° deflection. Wider deflection angle tubes require some EW correction, typically a modulation depth of 6-10 per cent of the line scan current for a 110° tube.

Shadowmasks

The four current shadowmask configurations are shown in Fig. 30. Delta-gun arrangements are now used only in special purpose tubes where very high resolution is required. Sophisticated dynamic convergence circuitry is

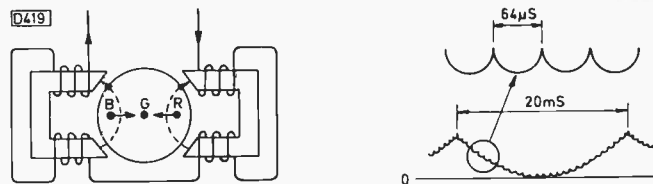


Fig. 29: Four-pole correction field generated by electromagnets. In some tube/yoke designs the outer faces of the ferrite U cores are capped by rotary permanent magnets for static convergence adjustment.

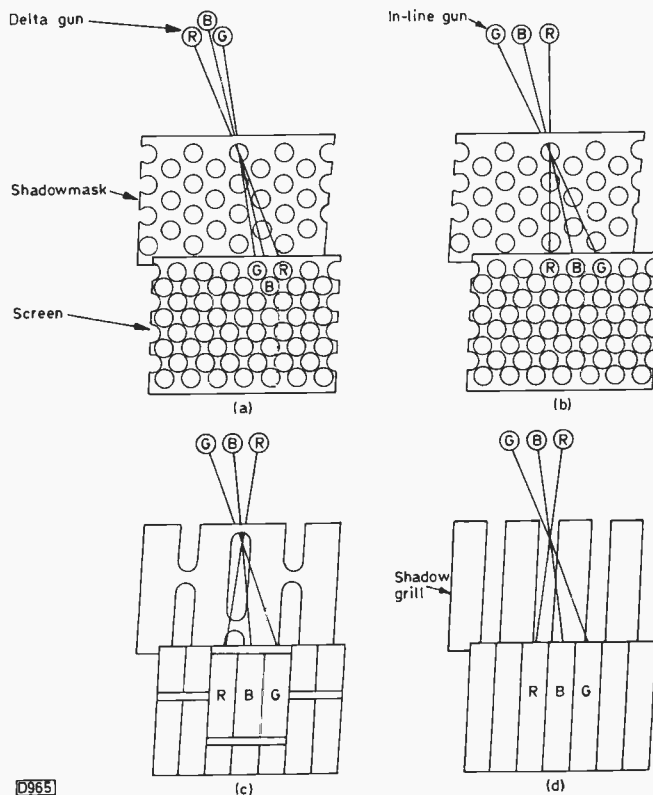


Fig. 30: Basic gun/mask/screen arrangements. (a) Delta-gun configuration. (b) In-line gun with dot screen. (c) Slotted shadowmask. (d) Trinitron system.

required in this case. The phosphor dot screen/in-line gun arrangement is used for medium and high resolution applications. The slotted mask is used in most domestic and monitor tubes and the Trinitron system in Sony TV sets and monitors.

Whatever form it takes, the task of the shadowmask is not to "guide" the electron beams to the correct phosphor dots/strips but rather to provide a solid barrier to prevent the beam from any gun striking any but the appropriate phosphor. The apertures in the mask are not straight sided but chamfered in a special way to prevent electrons bouncing off the side walls and scattering on to surrounding phosphor material – see Fig. 31. Each mask is chemically etched from both sides to achieve this precise aperture profile.

The mask material is low-carbon steel which is washed and dried before being coated on both sides with photoresist material. The sheet is then clamped between two photographic glass plates and the image of the required shadowmask pattern is then fixed on both sides by pulsed xenon lamps. The resist areas exposed in this way are insoluble: a wash removes the unexposed areas to leave dots, slots or stripes, as the case may be, of bare steel for the acid etchant. These are smaller at the back

(gun side) than at the front of the mask to give the profile shown in Fig. 31(b). Thus exact alignment of the two photographic glass plates is crucial. It's held to better than 2.5 microns by accurate alignment of registration marks on the plates.

A development in the mask pattern for in-line gun slotted screens is the contoured-line type in which the vertical phosphor lines are bowed to match the profile of the screen edges – see Fig. 32. The effect is pleasing to the eye whether the set is on or off. The biggest problem here is in the mathematics involved in computing and plotting the geometry of the master photographic plates used for mask etching. The bow at the sides must be gradually and evenly reduced until the lines become straight at the screen centre line. The etching pattern must also take into account the fact that the mask is domed, not necessarily to the same profile as the screen. Once the required pattern has been obtained however the contoured-line mask is easier to etch and the phosphor-fixing (lighthouse) process is also simpler.

Phosphor Fixing

For slot-mask tubes the ultra-violet lamp used for phosphor fixing is not a point source, as for phosphor-dot and Trinitron screens, but a vertical line source. This prevents the slot-bridges in the mask casting shadows on the phosphor and permits the formation of continuous lines of phosphor.

Phosphor fixing is not quite as simple as the usual description suggests. The problem (see Fig. 33) is that the apparent deflection centre varies with the deflection angle. A correction lens must therefore be interposed between the light source and the mask/screen ensemble. The beam landing accuracy at the corners of the screen depends very much on the design of this lens. For high-resolution tube manufacture Hitachi use a segmented correction lens that gives a closer simulation of the deflected beam paths.

Pitch Grading

To ensure correct purity at the screen edges and corners a reduced beam landing tolerance can be provided by decreasing the size of the mask apertures here. The presence and degree of this "pitch-grading" varies with different makes and types of tube. In current FS tubes a grading factor of 20 per cent is applied at the screen edges. The consequent 20 per cent loss of brightness goes virtually unnoticed by the human eye, largely because of the very gradual transition.

Mask Dissipation

The main problem with shadowmasks relates to heating effects. Depending on the tube design, around 80 per cent of the beam energy is intercepted by the mask. Since the total of the three beam currents with a bright scene and a large-screen tube can exceed 1.2mA at 25kV, mask dissipation can reach 24W. The average dissipation is way below this – say 5-10W for normal pictures and control settings – but the steel of which the mask is made expands as it gets hotter, and particularly where the beam current is strong in a small area (a stationary highlight on the screen) local overheating can occur. The mask then bulges to upset the colour registration at this point – in practice white usually gets a red tint.

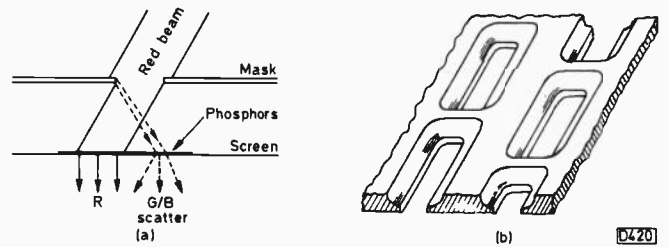


Fig. 31: Shadowmask hole contouring. To prevent the impurity and loss of definition caused by beam scattering – see (a) – the apertures in all types of mask are chamfered. A typical pattern for a slot mask is shown at (b), viewed from the screen side.

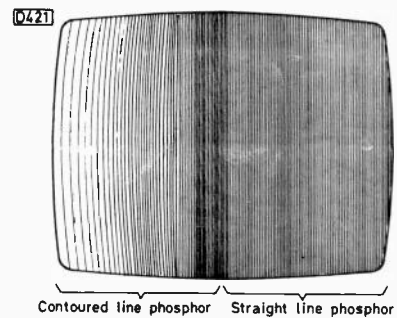


Fig. 32: Phosphor line patterns, new and old. Note the ugly foreshortening of the stripes at the right: contoured line phosphors were introduced in the late seventies.

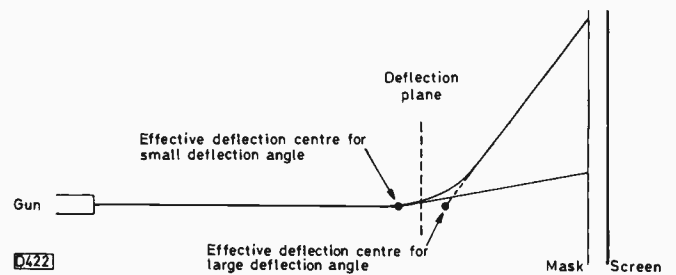


Fig. 33: The deflection centre appears to move forwards as the scan angle increases – the effect is due to the varying curvature of the beam paths.

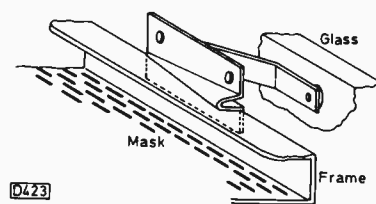


Fig. 34: Heat compensating suspension system for a shadowmask: bimetal mounting strips are used.

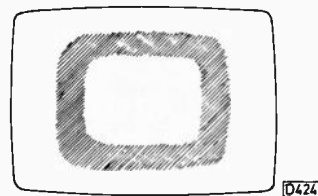


Fig. 35: The areas at risk of being impure during the initial warm up of a conventional shadowmask.



Fig. 36: Conventional shadowmask arrangement (a). Mask expansion has a greater effect on beam landing with this than with the Super Arch Mask shown in (b).

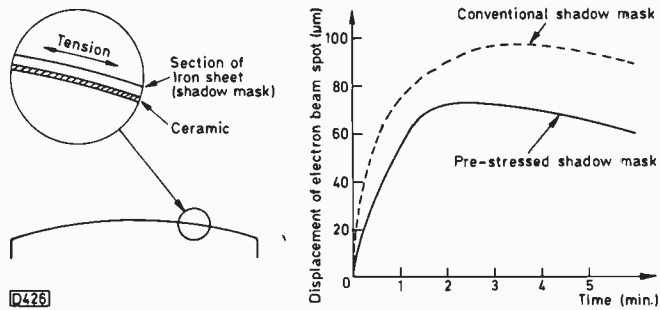


Fig. 37: Applying a ceramic coating to reduce hot bulge.

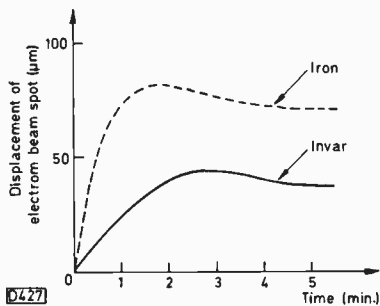


Fig. 38: Invar as an alternative mask material is less affected by high power dissipation.

Heat conductivity away from a hot spot is more difficult with a grille type mask (Trinitron), where in large-screen sizes three horizontal microfine tiebars are welded across the screen to stiffen the fine vertical grille strips. Local conductivity is better with other types of mask due to their continuous nature, though a concentrated stationary highlight can cause impurity with early types of tube, especially when the purity is not set up at centre tolerance or when the beam limiter is not doing its job properly.

Design Aims

Designers of shadowmasks have the triple aims of making the mask more "transparent" to the electron beams, minimising the heat developed in the mask and minimising the effects of their inevitable expansion when they do heat up. Some types of delta-gun tubes have masks with hexagonal rather than the circular holes. This gives a small gain in transparency. Even so delta-gun mask transparency never exceeded more than about 17 per cent at the centre and 12 per cent at the corners. This compares with about 21/16 per cent for Trinitron tubes and 19/14 per cent for slot-mask tubes. "Hi-Bri" slot masks just exceed 20 per cent transparency.

Mounting the Mask

The mask would buckle as expansion occurs if it was rigidly mounted, completely upsetting the purity. To prevent this the frame on which the mask is mounted is fitted with bimetal temperature compensating elements on spring arms (see Fig. 34) to permit the whole mask assembly to move along the tube axis (towards the phosphor screen) as it heats up. There are usually four such mounting points that clip on to tapered studs heat-sealed into the panel side walls.

The bimetal mount system doesn't work until the mask and its heavy and thermally inert frame have reached thermal equilibrium. This leads to a risk of purity errors in the first five or ten minutes of operation. The regions

most at risk are not at the screen centre, where mask doming has little effect on beam landing, nor at the extreme edges, where the heatsinking effect of the frame prevents rapid rise of temperature. It's the midway areas that suffer (see Fig. 35), and various remedies have been devised by tubemakers.

Super Arch Mask

An early one was RCA's Super Arch Mask, in which a very pronounced curvature is given to the cold mask. As a result, short-term, localised and warm-up expansion effects have much less effect on beam landing. This type of mask has greater slot spacing at the sides, which helps with beam-landing tolerances here but does slightly reduce the brightness at the extreme edges of the picture. Fig. 36 shows the Super Arch principle.

Surface Treatment

Some alternative approaches to the problem involve surface treatment of the mask. A simple and widespread technique is to blacken the mask. Many tubes have the back of the phosphor screen (after aluminising) painted black as well to act as a heatsink of sorts – the large glass screen has the makings of an excellent heat radiator. A further step is to coat the surface of the mask with a low thermal expansion ceramic material then fire it on the steel surface at high temperature in an oven. This leaves considerable residual tension in the mask material when cool – to be relieved in operation as the coated mask warms up. The presence of the ceramic coating reduces the mask temperature for a given dissipation while mask expansion is minimised by the relief of internal tension. The principle is not unlike that of continuous welded railway track. It gives a reduction of about 20 per cent in beam landing error (see Fig. 37).

Invar Mask

For fine-pitch tubes Toshiba use an alternative metal (Invar) for the mask – its coefficient of expansion is much lower than that of steel (see Fig. 38). Invar is more expensive than steel and more difficult to handle, hence its restriction to expensive fine-pitch tubes.

45AX Mounting System

A better way to avoid localised and transient overheating of the mask is to do away with the heavy metal frame and bimetal spring support system with their thermal inertia and long thermal paths. Philips/Mullard have adopted a completely new approach to mask suspension in their 45AX tube system. Here the mask is attached to a light diaphragm which defines the picture borders and is suspended at each corner by a swing link that pivots on a stud fused into the glass. As the mask warms up its expansion forces the suspension links to rotate about their mounting studs, moving the enlarged mask forward towards the screen to maintain correct beam landing. This system reaches thermal equilibrium within fifteen minutes of switch on and is unaffected by ambient temperature. The closer control and more precise placement of the mask allow a larger beam landing reserve.

Coming Next Month

Next month we will continue with screen phosphors.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

15/80H	3.30	2SA940	1.01	2SC535	0.79	AF180	0.55	BA656	8.99	BC560C	0.14	BDX63A	1.96	BFY52	0.27	BYX71-350	0.72
15/85R	3.30	2SA940-2	2.14	2SC536	0.51	AF181	0.53	BA7100	10.85	BC635	0.36	BDY20	1.21	BFY79	0.49	BYX94	1.14
16039	0.79	2SA950	0.72	2SC537	0.44	AF186	0.53	BA841A	16.72	BC636	0.42	BDY81	1.18	BFY90	0.61	BYX96	1.20
16181	1.04	2SA950	1.26	2SC605L	1.16	AF239	0.43	BA843	3.96	BC637	0.24	BF115	0.40	BLY49	0.22	BZ293C30	1.86
16182	1.04	2SA966-Y	1.16	2SC620	1.46	AF279	0.88	BA854	5.76	BC639	0.20	BF117	0.66	BR00	0.20	BZ288 RANGE	0.10
16334	0.94	2SA999	1.36	2SC643A	1.54	AL113	1.36	BAV18	0.21	BC640	0.24	BF118	0.67	BR01	0.75	BZ261 RANGE	0.18
16335	0.94	2SB774	1.15	2SC668	1.67	AN115	1.36	BAV19	0.21	BC679	0.39	BF121	0.25	BR03	0.75	BZ279 RANGE	0.10
16446	0.98	2SB185	1.13	2SC681	1.40	AN155	1.89	BAV20	0.31	BC680	0.31	BF123	0.13	BR03	1.26	C106D	0.46
16600	1.38	2SB375	3.87	2SC682	1.89	AN206	2.58	BAV21	0.34	BCX34	0.40	BF127	0.13	BRC116	0.67	C106M	0.76
16802	1.27	2SB400	0.40	2SC684	1.65	AN208	3.55	BAW62	0.19	BCY70	0.30	BF137	0.29	BRC300	2.01	C1129	2.08
17052	1.51	2SB405	1.03	2SC693	0.63	AN210	2.28	BAX12	0.44	BCY71	0.21	BF153	0.58	BRC5296	0.77	CA3046	0.56
17053	5.61	2SB407	3.24	2SC710	0.69	AN211	3.25	BAX13	0.11	BCY72	0.20	BF154	0.26	BRC6109	0.83	CA3089	0.83
17074	9.30	2SB449B	6.93	2SC711A	0.50	AN2140	2.75	BAX16	0.11	BD115	0.46	BF157	0.33	BRC82	1.08	CA3090AO	3.25
17089	5.35	2SB511	2.50	2SC717	1.28	AN231	14.65	BC107	0.13	BD116	0.11	BF158	0.18	BRC83	2.19	CA3094	2.20
17127	3.51	2SB544	1.39	2SC734	1.43	AN234	5.92	BC107A	0.11	BD131	1.31	BF159	0.18	BRC84	2.08	CA3131EM	3.12
17376	1.58	2SB546	3.75	2SC761-Y	0.95	AN236	3.78	BC107B	0.18	BD124P+KIT	0.69	BF160	0.69	BRC83	0.63	CBF16848N-071	1.58
17523	1.32	2SB556	2.80	2SC783	3.98	AN239	6.95	BC108	0.15	BD132	0.42	BF167	0.38	BRX44	0.50	CD4001	0.36
17524	1.06	2SB618A	2.22	2SC790Y	1.64	AN240P	1.52	BC108B	0.15	BD133	0.42	BF173	0.35	BRX49	0.69	CD4002	0.27
1N4001	0.06	2SB631	3.25	2SC828	0.28	AN241	1.71	BC109	0.12	BD136	0.36	BF178	0.40	BRY39	0.69	CD4008	1.35
1N4002	0.06	2SB643	0.54	2SC867A	3.05	AN245	4.49	BC109B	0.15	BD138	0.26	BF179	0.36	BSS38	0.87	CD4008	0.29
1N4003	0.06	2SB669	3.67	2SC876	0.96	AN253	2.97	BC109C	0.12	BD139	0.36	BF180	0.36	BSTC0246	5.25	CD4011	0.24
1N4004	0.06	2SB681	3.96	2SC930	0.54	AN260	3.85	BC113	0.14	BD137	0.36	BF181	0.36	BSTC0233	7.25	CD4013	0.29
1N4005	0.06	2SB695	1.98	2SC935	0.13	AN262	1.98	BC119	0.36	BD138	0.46	BF182	0.32	BSTC0143	3.07	CD4016	0.46
1N4006	0.08	2SB75	1.04	2SC936	8.66	AN272	7.92	BC126	0.20	BD139	0.34	BF183	0.34	BST01043	2.85	CD4017	0.82
1N4007	0.07	2SB774	0.65	2SC940	6.66	AN281	6.65	BC132	0.14	BD140	0.37	BF183	0.39	BSV57B	3.49	CD4020	1.23
1N4448	0.04	2SB819	0.89	2SD1128	2.90	AN295	5.52	BC135	0.14	BD144	1.70	BF184	0.43	BSW68	0.60	CD4021	0.39
1N4448	0.05	2SC1034	6.75	2SD1138	0.99	AN301	5.55	BC137	0.18	BD140	1.25	BF185	0.39	BSX19	0.34	CD4023	0.28
1N5401	0.14	2SC1050	5.06	2SD1273	1.25	AN302	3.99	BC138	0.34	BD157	0.67	BF194	0.14	BSX20	0.34	CD4025	0.64
1N5402	0.15	2SC1096	1.16	2SD1453	1.25	AN303	4.39	BC139	0.28	BD160	1.60	BF195	0.14	BSY52	0.50	CD4028	0.84
1N5403	0.16	2SC1104	3.98	2SD152K	2.64	AN305	9.47	BC140	0.45	BD163	0.71	BF196	0.17	BSY79	0.51	CD4040B	1.06
1N5404	0.15	2SC1106	4.54	2SD198	3.87	AN315	2.46	BC141	0.34	BD165	0.62	BF197	0.16	BT100A	0.61	CD4047	0.85
1N5408	0.35	2SC1114	6.75	2SD234	0.49	AN316	5.53	BC142	0.34	BD166	0.42	BF198	0.17	BT106	1.55	CD4049	0.46
1N914	0.04	2SC1116	4.95	2SD235	0.60	AN318	6.27	BC143	0.33	BD168	0.73	BF199	0.17	BT108	1.45	CD4052	0.75
IR3403	5.00	2SC1124	1.26	2SD24	2.29	AN320	5.47	BC147	0.00	BD175	0.60	BF200	0.37	BT119	1.76	CD4066	0.39
IS1555	0.20	2SC1129	0.34	2SD257	2.94	AN321	2.25	BC148A	0.10	BD179	0.49	BF218	0.36	BT120	2.17	CD4069	0.28
IS44	0.10	2SC1131	0.50	2SD292	2.59	AN322	5.85	BC148B	0.13	BD181	0.99	BF224	0.17	BT121	2.48	CD4070	0.66
IS5012A	0.81	2SC1158	3.33	2SD313	2.59	AN331	4.59	BC148C	0.11	BD182	0.99	BF227	0.65	BT123	1.98	CD4081	1.35
IS921	0.10	2SC1162	1.05	2SD325D	1.95	AN337	5.37	BC149	0.11	BD183	0.99	BF240	0.17	TA970	3.06	CD4093	1.12
2N1303	0.38	2SC1172	2.22	2SD348	16.13	AN340P	1.17	BC149B	0.13	BD184	1.21	BF241	0.17	BT151-800R	1.15	CD4951	0.70
2N2219A	0.40	2SC1195	3.26	2SD350	5.20	AN355	5.98	BC153	0.14	BD187	0.53	BF245	0.50	BT160A	4.82	CD4528	2.04
2N2222	0.38	2SC1212A	1.97	2SD350A	2.80	AN362	1.75	BC154	0.14	BD189	0.69	BF245A	2.49	BT18124	2.49	CD4556	3.47
2N2646	0.80	2SC1213	0.89	2SD353	7.50	AN370	3.95	BC159	0.36	BD190	0.69	BF245B	0.49	BU106	2.48	CR02AM-8	1.55
2N2904	0.36	2SC1226	1.46	2SD389	2.41	AN5010	5.70	BC160	0.40	BD201	0.53	BF246A	2.52	BU108	1.50	CV12E	3.07
2N2905	0.43	2SC1293	0.90	2SD401	2.55	AN5111	2.92	BC161	0.28	BD202	0.60	BF255	0.20	BU109	2.25	CX0950	3.14
2N2906	0.38	2SC1306	1.98	2SD414	1.98	AN5120N	4.50	BC168	0.36	BD203	0.50	BF256	0.28	BU110	5.69	CX104	9.64
2N2926	0.15	2SC1316	4.10	2SD471	2.13	AN5132	4.39	BC169C	0.16	BD204	0.59	BF256L	0.42	BU111Y	4.16	CX108	10.50
2N3053	0.27	2SC1317	0.87	2SD560	2.95	AN5250	2.89	BC170	0.16	BD207	1.79	BF256L	0.42	BU125	2.48	CX109	7.86
2N3054	0.99	2SC1364	0.49	2SD588A	1.39	AN5435	3.08	BC171	0.11	BD208	1.23	BF257	0.34	BU126	1.55	CX130	8.76
2N3055	0.61	2SC1383	1.20	2SD600	3.25	AN5610	7.43	BC172	0.13	BD222	0.49	BF258	0.36	BU137	9.25	CX134	11.04
2N3442	1.56	2SC1391	2.45	2SD601R	1.05	AN5612	3.81	BC172B	0.27	BD225	0.49	BF259	0.34	BU205	1.08	CX139	11.83
2N3702	0.14	2SC1398	0.94	2SD613	0.63	AN5613	3.80	BC173	0.17	BD228	0.63	BF262	0.57	BU206	1.27	CX151	4.84
2N3703	0.14	2SC1413A	3.05	2SD621	12.85	AN5630	3.35	BC174B	0.27	BD229	1.05	BF263	0.57	BU207	1.65	CX158	4.10
2N3705	0.16	2SC1446	1.25	2SD636	0.56	AN5701N	1.66	BC177	0.20	BD232	0.67	BF271	0.34	BU208	1.12	CX158	4.10
2N3706	0.14	2SC1447	2.07	2SD639-R	0.85	AN6250	2.95	BC178	0.26	BD234	0.42	BF273	0.20	BU208/02	1.97	CX177	5.26
2N3707	0.16	2SC1475	0.37	2SD655	0.98	AN6300	7.00	BC179	0.26	BD237	0.47	BF274	0.20	BU208A	1.12	CX187	5.26
2N3711	0.11	2SC1505	1.00	2SD657	2.85	AN6310	8.74	BC182	0.09	BD238	0.39	BF324	0.23	BU208D	1.95	CX185	12.95
2N3717	2.04	2SC1514	1.41	2SD661A	0.80	AN6320N	4.28	BC182L	0.10	BD239	0.45	BF336	0.33	BU209	1.33	CX188A	6.85
2N3772	1.71	2SC1573Q	1.25	2SD731	2.45	AN6340	6.46	BC182LB	0.14	BD240	0.37	BF337	0.40	BU226	2.95	DEC1	2.20
2N3773	2.29	2SC1578	8.74	2SD773	0.33	AN6341	6.40	BC183L	0.11	BD241	0.39	BF338	0.44	BU326	2.00	DEC2	2.20
2N3819	0.42	2SC1583	1.17	2SD811	5.54	AN6342	1.61	BC183LB	0.26	BD242	0.37	BF355	0.49	BU326A	2.00	DS3486N	4.33
2N3823	1.17	2SC1617	3.89	2SD823	1.98	AN6363	16.00	BC184	0.13	BD243A	0.39	BF362	0.66	BU326S	2.20	DS3487N	4.33
2N3904	0.62	2SC675	1.41	2SD837	1.20	AN6371	9.24	BC184L	0.14	BD243C	0.79	BF363	0.60	BU406	1.49	E1222	0.40
2N3908	0.62	2SC1678	1.98	2SD841	3.65	AN6387	7.95	BC184LB	0.26	BD244	0.51	BF371	0.50	BU406D	1.79	E5024	0.28
2N4101	1.33	2SC1741	1.25	2SD856	2.25	AN6531	1.95	BC186	0.27	BD244C	0.79	BF391	0.25	BU407	0.82	E5386	0.25
2N4240	3.30	2SC1810	1.70	2SD857Q	1.84	AN6551	1.35	BC187	0.28	BD245C	0.99	BF417	0.84	BU407D	1.09	E9003	0.45
2N4444	1.73	2SC1815	0.66	2SD882	1.50	AN6552	0.68	BC204	0.16	BD246C	0.89	BF418	1.87	BU412	9.15	E9005	4.50
2N5293	0.50	2SC1826	0.65	2SD894	1.50	AN6610	2.40	BC207	0.14	BD253	0.67	BF422	0.29	BU426A	1.67	ESM310BP	0.15
2N5294	0.50	2SC1829	2.22	2SD898	5.45	AN6677	6.60	BC212	0.11	BD278A	0.80	BF423	0.52	BU500	1.89	FN0500	5.78
2N5296	0.49	2SC1875	5.19	ZSK105H	2.15	AN7111	1.45	BC212B	0.26	BD317	2.60	BF450	0.35	BU508A	1.95	GC374	1.65
2N5297	0.50	2SC1881K	2.98	ZSK152	2.95	AN7114E	5.94	BC213L	0.10	BD318	2.85	BF451	0.29	BU536	5.80	GD243	4.95
2N5298	0.61	2SC1893	3.02														

TEL 0902 712083 TELEX 338490

HA1374	4.80	LR3419	9.37	NE665N	1.33	SKE4F2/08	1.24	STK3042	11.05	TA7312P	2.45	TD62106P	2.50	TD43560	5.25	TUA2000	8.98
HA1377	3.96	LR3471	9.37	NE6458N	3.35	SKE4F2/06	0.85	STK3044	5.75	TA7313AP	1.50	TD62104P	2.50	TD43571Q	2.97	TV106	1.76
HA1389R	2.05	LU1141	7.27	NP1106	5.61	SKE4F2/10	1.24	STK4019	4.50	TA7314	5.94	TD62706P	4.50	TD43576	7.09	TY6010B	2.97
HA1389	2.39	LU2012	5.95	OA202	0.11	SKE4G2/02	0.90	STK4300	11.75	TA7323P	3.15	TD41001B	2.31	TD43580	5.79	U05G	1.14
HA1392	3.90	LU2011	4.95	OA47	0.14	SKE5F3/10	1.96	STK4330	5.45	TA7325P	1.15	TD41003A	2.25	TD43591	6.45	ULN2204	11.45
HA1394	3.95	LU03112	12.37	OA91	0.09	SKS1/10	2.15	STK4332	8.25	TA7329P	1.35	TD41005A	2.22	TD43650	7.50	UPA35C	4.94
HA1397	3.76	M193	12.75	OA95	0.09	SL1310	3.14	STK4335	5.94	TA7340P	5.06	TD41006A	4.11	TD43652	5.44	UPC1003	4.95
HA1398	3.98	M21C	1.00	OC28	2.95	SL1430T	3.21	STK4352	12.25	TA7607AP	13.90	TD41010AF	2.25	TD43651AQ	2.96	UPC1009C	6.32
HA1406	2.07	M23C	0.83	OC29	2.15	SL414	2.09	STK4336	7.80	TA7611AP	4.80	TD41011	1.95	TD43651A	2.65	UPC1025H	2.90
HA1452	1.63	M293	9.15	OC36	1.28	SL432A	3.48	STK4337	3.85	TA7616P	5.25	TD41011A	5.25	TD43650B	4.98	UPC1028H	2.00
HBF4030AF	2.48	M293	9.15	OC44	0.35	SL439	2.44	STK4372	8.31	TA7622AP	8.94	TD41028	2.45	TD44050B	2.77	UPC1020H	2.77
HD14538	2.07	M51102L	6.35	OC45	0.18	SL471	4.78	STK4379	11.28	TA7628P	5.62	TD41034B	2.42	TD44280	7.20	UPC1032H	0.62
HD38702-A2	7.45	M5115P	5.24	OC72	0.44	SL480	3.14	STK441	10.29	TA7629P	7.50	TD41035S	2.95	TD44290	4.47	UPC1042C	8.95
HD38750A53	8.71	M51203L	3.15	OC75	0.44	SL490	2.37	STK443	14.83	TA7630P	2.98	TD41035T	2.55	TD44400	2.27	UPC1156H	2.96
HD38750A-7	7.25	M51231P	3.04	ON236	1.06	SL901B	8.32	STK457	9.68	TA7640AP	1.19	TD41037	1.98	TD44420	5.01	UPC1158H	5.94
HD38800A50	14.09	M5134-9341	4.13	ON782	1.96	SL918A	9.07	STK460	14.83	TA7672P	1.75	TD41037D	2.65	TD44422	2.02	UPC1161C	4.50
HD44801A05	18.25	M51353P	5.25	OT121	1.45	SN16861A00	4.35	STK461	11.53	TA7676P	2.81	TD41044	2.62	TD44427S	9.00	UPC1182H	1.82
HFH4001BP	0.67	M51381P	4.95	PT6042	2.45	SN16862AN	2.98	STK463	11.77	TA7726P	10.25	TD41047	4.10	TD44431	2.27	UPC1186H	1.05
HISH1010	8.59	M51393AP	7.80	PT8504	4.96	SN16966N	10.25	STK466	11.53	TA7726P	11.53	TD41047A	0.80	TD44440	2.87	UPC1187H	1.25
HISH1004	6.00	M51394P	11.97	R1038	2.19	SN29717N	7.19	STK4633	6.95	TA7726P	16.32	TD41059B	4.10	TD44442	4.85	UPC1185H	2.94
HISH1002	9.50	M5142P	5.49	R1039	2.19	SN29716N	3.66	STK501	16.92	TA7726P	6.35	TD41054M	1.21	TD44450	2.60	UPC1188	6.95
HM6231	9.81	M5144P	4.25	R2008B	1.36	SN29715N	6.04	STK502	5.74	TA7726P	9.48	TD41060	1.60	TD44600	2.84	UPC1213C	0.99
HM6232	8.89	M51513L	2.55	R2009	1.93	SN29722	11.95	STK5314	9.78	TA7726P	2.65	TD41082	3.25	TD44610	2.90	UPC1212C	1.72
HM6251	5.70	M51515BL	3.23	R2010B	1.33	SN29723AN	7.65	STK5730	3.95	TA7726P	2.52	TD41105	2.25	TD44620	4.78	UPC1225H	3.25
HM7103	2.46	M51517L	3.71	R2029	1.33	SN29764AN	1.38	STK7216	12.67	TA7726P	12.67	TD41190	2.11	TD44500	4.78	UPC1230H	7.24
HM9032	3.22	M5192	2.20	R2030	1.33	SN29767	4.98	STK772	6.95	TA7726P	6.95	TD41190G	3.96	TD44500	2.60	UPC1238H	2.98
HM9012	3.22	M5194AP	5.74	R2257	3.71	SN297708A	4.24	STR1096	11.75	TA7726P	4.87	TD41200	1.50	TD44570S	2.25	UPC1263	3.45
HM9015	3.24	M5231L	1.95	R2265	1.49	SN297728B	4.91	STR4090	7.85	TA7726P	2.83	TD41225	3.88	TD448190	3.47	UPC1277H	5.85
HT4207	17.16	M53274P	1.36	R2305	1.18	SN297711B	4.93	STR440	7.85	TA7726P	2.83	TD41226	3.00	TD44903	3.15	UPC1278H	4.85
HT4208	18.25	M54532P	2.15	R2322	0.59	SN29791	1.57	STR441	6.50	TA7726P	2.52	TD41270	3.76	TD44903G	5.92	UPC1351C	1.81
IN5401	0.11	M54544L	4.75	R2323	0.76	SN29798N	1.66	STR451	4.95	TA7726P	1.06	TD41327A	1.30	TD449513	2.44	UPC1350C	1.10
IR2403	4.25	M58478P	6.75	R2354A	2.01	SN270	0.44	STR453	8.16	TA7726P	1.16	TD41412	1.05	TDB1033	6.68	UPC1353	7.85
IR2C05	4.25	M58485P	10.74	R2354B	2.01	SN7400N	0.34	STR454	7.50	TD4120A5	1.24	TD41420	1.55	TD41420	1.61	UPC1355C	2.13
IR3P06	2.25	MA06	1.07	R2443	0.88	SN7401N	0.36	STR6020	8.31	TBA1205B	1.05	TD41420	1.05	TE626	1.49	UPC1363	4.20
IR3P08	4.95	MA8001	0.82	R2461	1.50	SN7402N	0.65	TB029V	5.75	TBA1201T	2.50	TD41470	3.16	TEA1002	3.47	UPC1362	7.75
IR94558	6.25	MA8003	1.16	R2540	2.31	SN7404N	0.24	TB035V	0.67	TBA1207A	1.05	TD41470P	7.45	TEA1009	1.85	UPC1365C	6.98
IS751	2.85	MB3705	1.98	R2540X	3.30	SN7408N	0.27	TB036	2.11	TBA120A	2.03	TD41506	7.45	TEA1014	3.15	UPC1366	7.25
ITT425	0.18	MB3712	1.65	R2615	0.67	SN7410N	0.27	TB037	0.97	TBA1201T	1.62	TD41510	5.90	TEA1020SP	8.21	UPC1360C	4.51
I20003GE	5.37	MB3713	1.89	RCA16029	2.01	SN74121	1.60	TB044	0.97	TBA144G	1.50	TD41512	2.98	TIC106C	0.61	UPC1378H	4.25
I20020GE	5.93	MB3730	3.25	RCA16600	1.38	SN7413N	0.37	TB045	1.45	TBA1441	1.75	TD41515	16.15	TIC106M	0.77	UPC141C	3.75
K1749P	3.46	MC13002	3.55	RCA16802	1.08	SN74141N	2.65	TB049	1.45	TBA240A	3.98	TD41559	3.60	TIC116Y100	2.07	UPC1458	8.66
KA2101	2.92	MC1310P	2.25	RCA17074	6.60	SN74151AN	1.51	TB052V	0.87	TBA250A	0.87	TD41670	4.48	TIC44	0.72	UPC151C	2.95
KC581C	6.32	MC1327P	1.33	RCA17376	1.58	SN74154N	1.27	TB058	0.59	TBA395Q	1.10	TD41770	6.85	TIC45	0.77	UPC2002	1.48
KC582C	3.97	MC1330P	1.69	RCA17524	0.83	SN74190	2.00	TB059	0.65	TBA395Q	0.80	TD41905	1.76	TIC47	0.35	UPC30C	2.51
KC583C	5.54	MC1350P	1.61	RCA17523	0.83	SN7420N	0.34	TB063	1.25	TBA395Q	2.39	TD41908	2.76	TIP120	1.06	UPC324C	4.70
L200CV	1.69	MC1351P	3.96	RCA2060	2.00	SN7430	0.49	TB065V	2.38	TBA400	2.45	TD41940	1.95	TIP110	0.53	UPC32C	4.94
LA1201	1.02	MC1352P	2.50	RGPO1-15	0.70	SN7440N	0.27	TB011V	0.49	TBA449P	2.45	TD41950	1.30	TIP112E	0.85	UPC339C	4.90
LA1210	1.56	MC1357P	1.15	RG1P10	0.50	SN7472	1.54	TB013V	2.96	TBA4800P	6.58	TD42005	5.08	TIP112	0.88	UPC41C	2.10
LA1230	2.87	MC1358P	2.15	RG3P0M	0.59	SN7474N	0.44	TB014V	7.60	TBA500P	6.58	TD42006	1.55	TIP117	0.95	UPC4558C	4.15
LA1320	2.87	MC14001	0.40	RT402	1.58	SN7480AN	0.93	TB016	1.02	TBA510	1.98	TD42004	2.27	TIP121	0.87	UPC474	5.11
LA1352	1.75	MC14013	2.41	RT905A	2.38	SN74LS26N	0.53	TB019V	1.58	TBA520Q	1.68	TD42002	0.90	TIP126	0.73	UPC554C	1.85
LA1367N	11.07	MC14493P	3.44	S1299	5.74	SN76001N	1.65	TB034V	1.38	TBA520Q	1.30	TD42003	1.75	TIP132	1.40	UPC566H	2.95
LA1373	7.25	MC14494P	2.15	S175	31.48	SN76013ND	2.48	TB035V	1.39	TBA530	1.30	TD42010	1.85	TIP137	1.50	UPC574	3.25
LA1364	3.02	MC14497	3.65	S2062D	2.07	SN76023N	5.15	TB035V	1.15	TBA540	1.15	TD42020	2.77	TIP29	0.66	UPC575C2	2.40
LA1365J	3.44	MC14510BAL	3.75	S2800D	5.54	SN76023ND	3.96	TB035V	7.45	TBA540C	1.15	TD42030	1.99	TIP2955	0.95	UPC576H	2.58
LA1385	1.94	MC14511BPC	1.10	S2802	3.47	SN76033N	4.15	TB035V	0.79	TBA560C	1.40	TD42140	1.59	TIP29A	0.46	UPC577H	1.25
LA1387	6.00	MC14528BPC	2.70	S2818	4.05	SN76110N	0.90	TB062V	0.40	TBA560C	1.60	TD42150	6.20	TIP29B	0.63	UPC578C	7.35
LA3155	1.25	MC1712	3.88	S3702S	6.15	SN76115AN	1.61	TB064	4.35	TBA570C	1.60	TD42151	1.93	TIP29C	0.40	UPC580C	4.13
LA3301	1.65	MC192	13.50	S40W	10.89	SN76131	1.92	TB6002	1.51	TBA570C	1.71	TD42160	4.01	TIP29D	0.75	UPC587C2	1.34
LA3350	1.43	MC7724CP	3.49	S6808B	8.80	SN76227N	1.33	TB7027	1.70	TBA611A12	4.13	TD42161	1.85	TIP30E5	0.75	UPC592H	2.15
LA3361	1.23	MC7818C	2.18	SAR063	5.17	SN76226D	1.98	TB7050	4.84	TBA611E72	3.03	TD42170	2.98	TIP30A	0.41	UPC595	2.95
LA3365	3.98	MCR1007	1.65	SA1006	4.75	SN76228N	3.27	TB7051	1.74	TBA651	2.55	TD42190	4.95	TIP30C	0.16	UPC596	1.98
LA3390	4.25	MCR106-5/6	0.65	SA1020	1.76	SN76242	8.95	TA7054	2.55	TBA651	2.60	TD42270	4.65	TIP31A	0.34	UPD1514C	8.95
LA4030P	4.20	MCR2207	2.28	SA1025	4.40	SN76243	5.23	TA7060AP	1.27	TBA670	1.85	TD42510	7.85	TIP31B	0.38	UPD2819C	4.98
LA4031P	3.20	ME0402	0.17	SA1024	2.81	SN76396	2.90	TA7061AP	0.71	TBA700	1.55	TD42520	2.37	TIP31C	0.50	UPD4013B	4.90
LA4032P	2.35	ME0404/2	0.47	SA1075	6.25	SN76533N	2.47	TA7069	1.83	TBA720	3.55	TD42522	3.46	TIP32A	0.63	UPD4066H	4.95
LA4100	1.25	ME0411	0.28	SA1121	5.14	SN76532N	2.95	TA7070P	1.83	TBA750Q	2.90	TD42524	4.50	TIP32B	0.59	UPD553-164	19.25
LA4101	1.30	ME6002															

The Operation of Electric Motors

Part 1

Mike Phelan

Most of the components we have to replace from time to time in consumer electronics equipment are relatively inexpensive – capacitors, resistors and the like. There are also more costly items such as cathode-ray tubes, wound components, etc. These are not normally scrapped without at least trying to do something with them. With VCRs, another group of expensive bits and pieces has joined the ranks. Of these the two that carry the highest prices are the video head assembly and the various motors. Sadly both have a limited life, due to mechanical wear.

Video head drums can now be refurbished by specialist companies. But to the best of our knowledge no equivalent facility is available for the motor, despite the fact that one of these can easily cost more than a video head assembly for the same machine.

This series of articles will attempt to redress the balance, by outlining the theory of electric motor operation and providing a few practical hints on how a motor can possibly be retrieved from the scrap bin and put to further service. We hasten to add that such a motor could be less reliable than a new one and that it's often not practical to attempt repair. But if we stuck to the principle of fitting new replacements every time we had to deal with a failure there would be no need for such things as tube boosters – maybe not even of switch cleaner! In addition one is quite often stuck for a part that's not immediately available: attempting a repair in these circumstances is quite justified.

The electric motor comes in many shapes, sizes and types. They can be broadly divided into two groups: the a.c. induction type and the universal commutator type that will run from an a.c. or a d.c. supply. We'll deal with the theory of each separately, though if you go back to first principles they are fundamentally the same. Indeed

it's debatable to which group the direct-drive brushless motors we now have in VCRs belong. Table 1 shows a sort of motor family tree: we've left out types that are not relevant to the sort of equipment with which we are concerned – you won't find a three h.p. three-phase motor in a VCR (despite the propensity of some users to try to squeeze various large objects into the cassette slots of their machines . . .).


Basic Theory

To return to the theory (sorry!), the basis of all electric motors is that a conductor carrying a current will try to move when positioned in a magnetic field. Its direction of movement depends on the directions of the flow of current and the magnetic field. Fleming's left-hand rule (see Fig. 1) gives the relationship between these three characteristics. If the left hand is held with the thumb, the first finger and the second finger at right angles to each other, then with the first finger (F) pointing in the direction of the magnetic field and the second finger (C) pointing in the direction of current flow the thumb (M) will point in the direction of motion of the conductor. In practice it's probably not necessary to know this. Suffice it to say that any conductor carrying a current will tend to move at right-angles to a magnetic field. As far as an electric motor is concerned the magnetic field may be provided by a permanent or an electromagnet and the current may be supplied to or induced in the conductor.

The AC Induction Motor

We'll discuss the a.c. induction motor first. As its name suggests, its operation depends on inducing a current into something. This type of motor was used in some first-

Table 1: Types of electric motor.

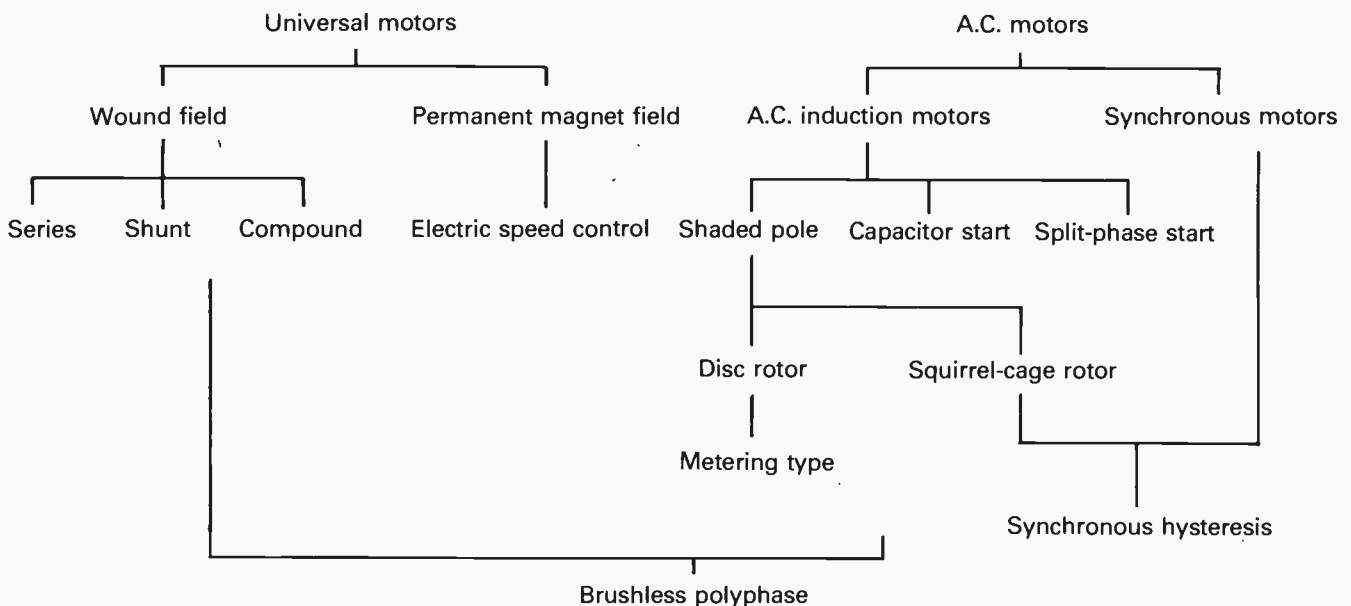

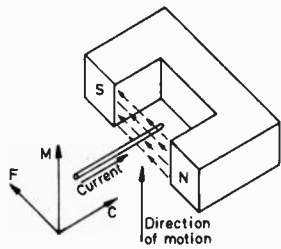


Fig. 1 (left): Fleming's left-hand rule.

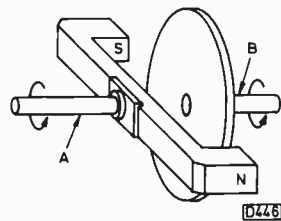


Fig. 2 (right): Elements of a simple induction motor.


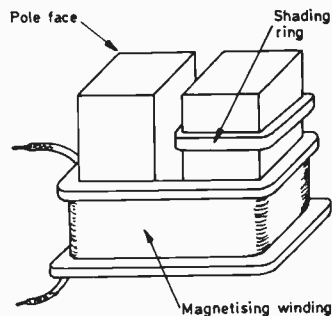


Fig. 3 (left): The shaded-pole arrangement.

Fig. 4 (right): The squirrel-cage rotor.

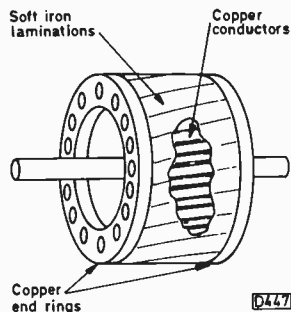

generation VCRs. It was also used with the motor-driven turret tuners employed in some television sets made in the sixties. Consider the arrangement shown in Fig. 2, consisting of a horseshoe magnet embracing a disc of conductive material, e.g. aluminium. If we rotate shaft A which carries the magnet shaft B will attempt to follow it but will never reach the same speed. This effect is due to induction: rotating the magnet around the disc will induce a current in the disc – this is in effect a dynamo. What we have here is the converse effect of the reaction between a magnet and a current carrying conductor – we'll refer to this as repulsion henceforth. The current induced in the disc by the rotating magnet repels the disc which thus tries to follow the magnet. It can never reach the same speed since if there was no relative movement between the two there would be no induced current in the disc.

If a mechanical load is applied to shaft B the disc will slow down. But the relative motion between the disc and the magnet, and therefore the induced current, will increase, thus giving more torque to drive the load. It can be seen that if we replace the mechanically driven magnet with a rotating electromagnetic field we shall have a motor of sorts. If you think that the device with the disc is useless, consider the situation when the disc's shaft is spring loaded and the disc carries a pointer. This will indicate the speed of shaft A and is the principle used for speedometers and revolution counters.

Producing a Rotating Field

We now have the makings of an electric motor but require a method of producing a rotating field. If instead of shaft A and its associated magnet in Fig. 2 we have a stationary electromagnet that's energised by a source of alternating current the direction of the magnetic field will reverse itself at twice the frequency of the a.c. This is not quite a rotating field but if shaft B, carrying the disc, is spun in either direction it will continue to rotate in that direction. The reason for this is that although a pulsating field cannot get the disc to rotate in either direction from

rest the repulsion principle will provide sufficient impulse to maintain rotation if the disc is already rotating. This will become clearer when we come to consider synchronous motors.

All we now require to produce a motor to run on a.c. is some means of providing a rotating field to start the motor. If this rotating field is maintained for running the motor the result will be a smoother delivery of torque. One way of providing a rotating field, used in many small motors, is the "shaded pole" arrangement. The polepiece (see Fig. 3) is split into two lobes: around one of them there's a copper ring that acts as a shorted turn. The effect of this is that the flux in this half of the pole is delayed in its growth and decay as the current reverses. The moving field thus produced across the polepiece provides sufficient torque to overcome the initial inertia of the disc.

Rotors

At this point we should mention that a disc is not the usual form of rotor, as this part of an a.c. motor is called (the stationary part is called the stator). The type of rotor normally employed is the "squirrel cage" type – I decline to offer a reason for this odd term. The squirrel cage rotor (see Fig. 4) consists of a laminated soft iron cylinder, slotted or punched to carry typically about twenty axial copper rods, and two copper end rings into which the rods are soldered or riveted. Aluminium is sometimes used for the rods. The laminations, and thus the rods, are usually given a slight helical twist to provide smoother running. As you can see the rods form conductors which are connected in parallel by the end rings. A laminated core instead of an air core is used for greater magnetic efficiency: lamination is necessary to prevent currents being induced in the iron – its resistance would give rise to heating as a result of such "eddy currents".

This type of motor was used in the Philips N1500 VCR and in many autochanger mechanisms. It gives a fairly constant speed which is always just below the field's speed of rotation. The latter, for a two-pole motor run off a 50Hz mains supply, is 3,000 r.p.m. So the motor will run at something like 2,850 r.p.m. Incidentally this is the highest speed that can be achieved from an induction motor running off a domestic 50Hz mains supply – you cannot have fewer than two poles. A four-pole motor runs at approximately 1,425 r.p.m. – most audio motors were of this sort. The shaded-pole motor performs reasonably well with very light loads but always runs hot, due to the loss introduced by the shorted turns.

The disc rotor was actually used in some early gramophones, with a copper rotor some ten inches in diameter driving the 78 r.p.m. turntable directly. It also drove a governor of the brake variety – a hangover from the earlier spring-driven motors – as a result of which the motor ran at less than its free-running speed. This made the speed independent of the load.

The induction-disc motor is far from dead. Almost all of us use at least one. The humble electricity meter consists of an induction-disc motor loaded with a permanent magnet brake, with a winding in series with the house supply as well as one across it. This means that the speed depends on the energy supplied by both windings – in fact the product of current and voltage, i.e. watts. As the disc rotates in time it measures watts multiplied by time – kilowatt-hours.

Our saga will continue next month with more types of a.c. induction motor.

Servicing Sinclair Microcomputers

Part 4

Ken Taylor

Last month we dealt with the main parts of the Spectrum, including the CPU, ROM, ULA and 16K RAM. Fig. 1 showed the main computing circuitry (issue 3 version) while Fig. 4 showed the voltage stabiliser and generator circuits. Fig. 5 this month completes the Spectrum circuit: it covers the tape recorder input and output and sound sections, and the video circuits. You'll find several references to Figs. 1-4 in this month's article: these refer to last month's diagrams.

The 32K Extension RAM


Before looking at these new areas of the circuit there are a few points that remain to be dealt with concerning last month's circuitry. The first of these is the extension memory. This section, using IC15-IC26, extends the RAM memory from the initial 16K to 48K. It was originally an optional extra, with sockets provided to enable these i.c.s to be fitted later. So you sometimes find that these i.c.s can be easily removed for checking or for eliminating a possible source of trouble. The extension

memory chips are IC15-IC22 and may be Texas TMS4532 or OKI MSM3732 chips – the memory chips must all be of the same type. These are both 64K DRAMs with only 32K of serviceable area. This area is sometimes in the address range zero to 32K and sometimes in the range 32K to 64K. This is why there's a link panel on the printed board (between the MIC socket and the edge connector – see Fig. 2 last month). The connections required for the various memory permutations are as follows:

Memory chip	Links required
Texas TMS4532-3	T1 and 3
Texas TMS4532-4	T1 and 4
OKI MSM3732-H	OKI and H
OKI MSM3732-L	OKI and L

The pin connections for these chips are shown in Fig. 6. Pin 9, which is normally the A7 address connection, is here referred to as AR – high/low memory address select: it's connected to either 5V or 0V depending on whether the useful memory area is high or low.

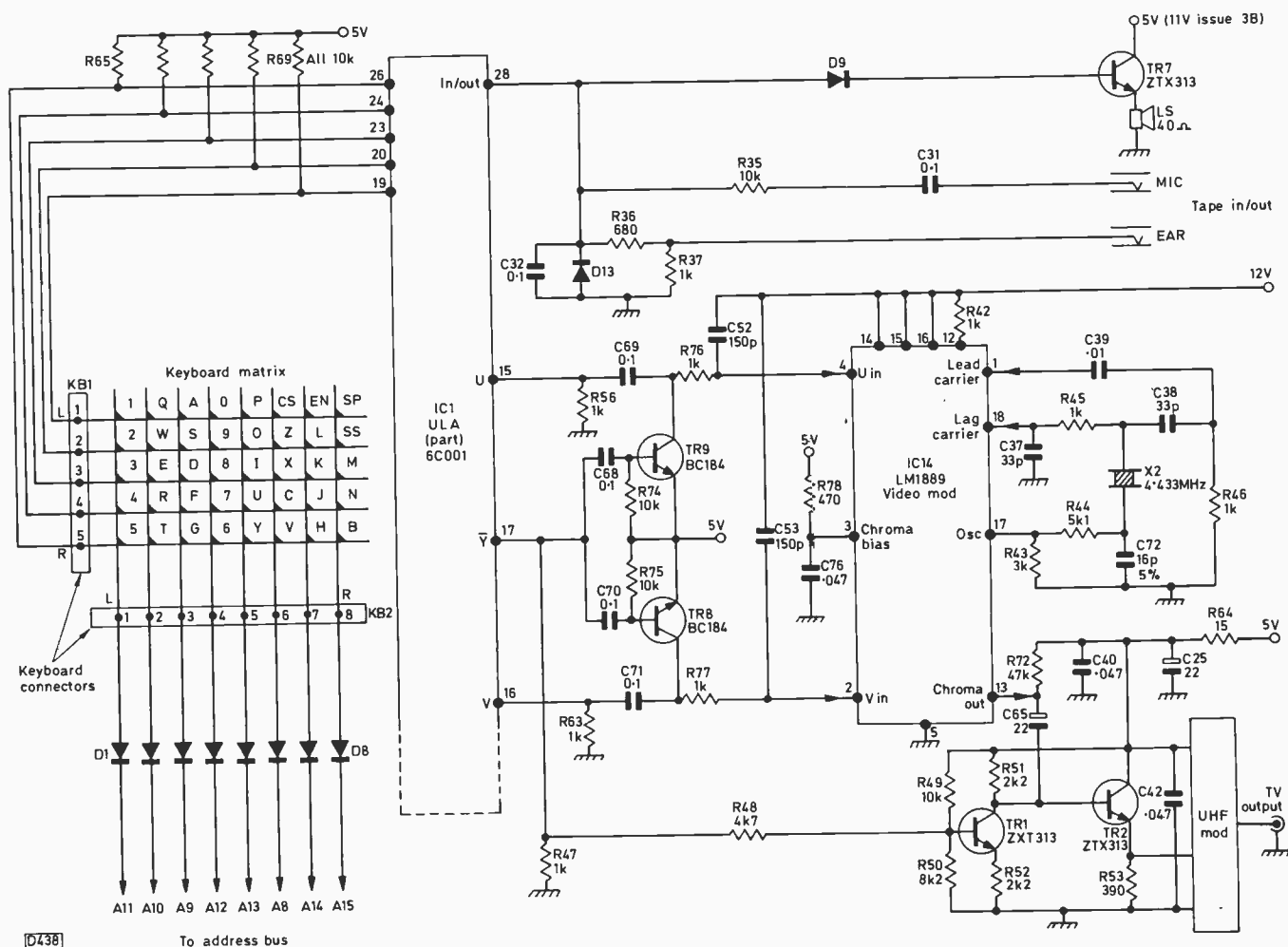The other chips associated with the extension memory



D438

To address bus

Fig. 5: Final part of the Spectrum issue 3 circuit diagram, showing the keyboard matrix, the tape input and output and the video and TV output circuitry. Note that C65 is 0.1 μ F in some issues of the Spectrum, also that to simplify the circuit many of the supply line decoupling capacitors have been omitted, also the edge connector connections (see Table 3). R47, R56 and R63 were 220 Ω in early versions: C72 is present in issue 3B versions. Some pin numbers were missed off IC3/4 last month: R23 goes to pin 12, R22 to pin 4, R21 to pin 7, R20 to pin 9, R19 to pin 12, R18 to pin 4 and R17 to pin 7.

are the address decoders (IC23 and IC24) and the row/column multiplexers (IC25 and IC26). The decoders activate the memory only when the A15 address line is high, thus setting the address range from 32768 (decimal) upwards.

While we're discussing addresses it's worth noting the memory map for the Spectrum. The 16K ROM starts at address zero and is followed at 16K (16384 decimal) by the 16K RAM (the 4116 chips). This continues to address 32767 and is followed by the 32K extension memory which carries on to the final address of 64K (65535). The model description - 16K or 48K Spectrum - indicates the size of the RAM. The 48K model often has a label on the underside.

RAM Checks

When you've finished a repair, especially when it has involved removing the extension memory, it's good practice to check that the entire memory is operational. This is a simple matter since one of the tasks in the initiation program is to determine the maximum usable memory available. This data is needed by the computer and is therefore stored in one of the system variables. Access is by entering the following line:

PRINT PEEK 23732 + 256 * PEEK 23733 (Enter)

Note that print and peek are words on the keys. The printout should be 65535, or 32767 if it's a 16K model. Any shortfall indicates that there's a memory fault that will have to be traced. If it's simply a defective memory chip diagnosis should be possible using the computer, because each i.c. is responsible for the same binary data bit at each of its addresses. If we can find the faulty bit in the data word and we know which i.c. handles which bit we shall be home and dry.

The above check will have told us that the faulty address is the one beyond the printout address number. We now need to find out which bit at this address is wrong. To do this we put 85 at this address, using the command poke. If you remember your binary you will know that 85 is 01010101. We next read what is in the address, using peek, and see if there's an error. If there is we can tell which i.c. is responsible because we know which data line goes to which i.c. (see Fig. 1). We also know that D0 is the least significant digit - the one at the right-hand end - and D7 the most significant digit, the first figure on the left.

So there we are. Except that an error may not show if the faulty cell registers the same digit we've put into it. In this case try again, this time putting in 170 which swaps the bits to 10101010. This must reveal the culprit.

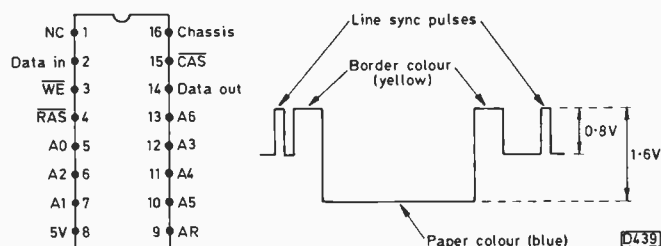


Fig. 6 (left): Pin connections for the 32K extension memory chips. Pin 3 is write enable, pin 4 row address strobe, pin 9 high/low address select, pin 15, column address strobe.

Fig. 7 (right): The TV line waveform at pin 18 of the edge connector when the computer is displaying a yellow border, blue paper and no characters.

TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

BAIRD: 8290, 8752, 8773	12.00	ITT: VC200 to VC402	9.20
RANK BUSH MURPHY		CVC1, CVC2 (FORGESTONE)	11.50
A774 with stick rectifier	9.78	CVC5, CVC7, CVC8, CVC9, CVC20	10.35
A816, T16, T18, Z712, Z715	10.35	CVC25, CVC30, CVC32, CVC45	9.20
T20, T22, T26, Z179, A823	11.50	CVC800, 1100, 1150, CVC40	P.O.A.
Z718 Basic unit	13.50	CVC1200, 1204, 1210, 1215, 2600	P.O.A.
DECCA: 1210, 1211, 1511	11.50	PYE: 169, 173, 569, 368	9.20
1700, 2001, 2020, 2401, 2404	9.20	CT200, CT200/1, CT213	10.35
CS1730, 1733, 1830, 1835	9.20	725-731, 735, 737, 741	9.78
30, 70, 80, 90, 100, 120, 130	9.20	PHILIPS: 170, 210, 300	9.20
FERGUSON, THORN: 1590, 1591	9.20	320 series	9.78
1690, 1691, built in rect.	9.78	TX, T8, TX2, TX3 mono	P.O.A.
1600, 1615, 1700, 1790	P.O.A.	G8 and G9 Series	£9.20
3000, 3500, 8000, 8500, 8800	P.O.A.	KT2, KT3, series	9.20
9000, 9200, 9300 series	12.00	CTX G11, K30, split diode	P.O.A.
9500, 9600, 9650 series	10.99	BINATONE: 9909, 9860, 9488	P.O.A.
9800, TX9, TX10 series	P.O.A.	DORIC Mk3, Mk1	11.50
MOVIESTAR 3781, 3787	12.00	SONY KV 1400, 1612, 2000	P.O.A.
TX10 focus unit	10.25	GRUNDIG: most models in stock	P.O.A.
FIDELITY: FTV12 mono	10.35	NORDMENDE: 8290, Z206, Z306	P.O.A.
ZX2000 ZX3000	P.O.A.	SANYO: 5101, 5103, 7118	P.O.A.
G.E.C. 2047 to 3135 mono	9.20	SHARP: C1851H, C2051H	P.O.A.
1201H, 1501H, 2114, 3133, 3135	9.20	TOSHIBA: C800, C800B	P.O.A.
DUAL & SINGLE hybrid col.	10.00	TANDBURG: 190, CTV2, CTV3	P.O.A.
SINGLE STD solid state	12.00	TELEFUNKEN: most models in stock	P.O.A.
SINGLE STD split diode	P.O.A.	HITACHI: 1471, CPB260, 2501	P.O.A.
INDESIT: 24EGB, 12LGB, 12SGB	10.35	SIEMANS: FF series	P.O.A.
WINDINGS		Tidman Mail Order Ltd.,	
TYNE: main winding	6.80	236 Sandycombe Road,	
RBM: T20, T22, T26, Z179	6.33	Richmond, Surrey.	
WALTHAM: W125 eht winding	2.37	Approx. 1 mile from Kew Bridge.	
WALTHAM: W190, W191 eht coil	6.00	Phone: 01-948 3702	
KORTING: hybrid winding	6.90	Mon-Fri 9 am to 12.30 pm &	
THORN: 8000, 8500, 8800 eht	6.70	1.30-4.30 pm	
		Sat 10 am to 12 noon.	

Table 1: RAM check procedure.

The following routine will isolate a fault at one address of the RAM:

- Enter the following:
PRINT PEEK 23732 + 256 * PEEK 23733
- If the result is other than 65535 or 32767 (16K version) there's a fault.
- Add one to the faulty result. Let's say it was 54321. Enter:
POKE 54322,85 (Enter)
then:
PRINT PEEK 54322 (Enter)
Use your result + 1 in place of the example quoted above.
- If the answer returned is 85, repeat step (3) using 170 instead of 85.
- One of the answers should differ from the 85 or 170 entered. Provided there is only one faulty i.c. at the address, Table 2 will indicate which one it is. Find the line with the wrong data bit then refer to IC6-13 if the address is below 32768 or IC15-22 if the address is above 32768.
- Repeat step (1) after the repair to ensure that there isn't another fault.

Table 2: Identifying the faulty chip.

Wrong answer obtained from procedure given in Table 1	Wrong data bit	Defective chip	
		16K	32K
84 or 171	0	IC6	IC15
87 or 168	1	IC7	IC16
81 or 174	2	IC8	IC17
93 or 162	3	IC9	IC18
69 or 186	4	IC10	IC19
117 or 138	5	IC11	IC20
21 or 234	6	IC12	IC21
213 or 42	7	IC13	IC22

If you don't want to exercise your binary skills, Table 1 lists the check procedure and Table 2 the faulty i.c. against the number read out. Remember that the system works only for a single fault at an address, though it's unlikely that there will be more than one when all the rest of the memory is operational. But there may be a fault at a higher address, so repeat the procedure until the correct final address has been obtained.

ROM Check

The program given below will enable you to verify that the ROM is satisfactory:

```

10 LET 1=0
20 FOR n=28003 TO 28033
30 READ a
40 LET 1=1+a
50 POKE n,a
60 NEXT n
70 DATA 17,0,64,62,0,33,0,0,1,0,0,134,48,2,3,63,35,
    29,32,247,21,32,244,50,96,109,237,67,97,109,201
80 IF 1=2033 THEN GO TO 110
90 PRINT "Error in Data"
100 STOP
110 RANDOMIZE USR 28003
120 PRINT PEEK 28000 + 256 * PEEK 28001 + 65536 *
    PEEK 28002
180 STOP

```

This will work with either make of ROM and should return the number 1926175. If "Error in Data" appears you've entered a wrong number in line 70. Incidentally if you remember that the ZX81 ROM check took over a minute to run you may be surprised at the speed of this one. Although the ROM is twice the size the check uses machine code, giving an almost instantaneous result. This is a measure of the difference between BASIC and machine code: when you consider that apart from all the addressing procedures etc. over 16000 additions have been made in the time you can see the potential speed of the CPU.

A connection link similar to that for the RAM is provided for the ROM. It provides for fitting a chip of either NEC or Hitachi manufacture. The link is no longer used since current ROMs work with either set of connections.

The Keyboard

Like the ZX81, the Spectrum's keyboard is of membrane construction wired in matrix form with decoding by the CPU. The keyboard (see Fig. 5) is scanned by sequentially putting a low on each of the address lines A8 to A15 and monitoring the data lines D0 to D4. If a key is pressed the appropriate pin of the ULA chip is pulled low: this is transmitted to the relevant data line via an inverter in the ULA.

Fault diagnosis is straightforward – the usual faults are in the tails that connect the membrane to the sockets. A fault here affects either a row or column of keys. It's a simple task, with the aid of the diagram, to determine which tail is at fault. If the whole keyboard is dead a quick check is to make connections across from one socket to the other in place of the keyboard. This can also be done quite safely when the keyboard is removed for servicing the computer. No damage will be done even if more than one socket contact is shorted.

The Spectrum Plus keyboard has an extra complication. In order to simulate the pressing of two keys by operation of one of its special keys it has a double-layer membrane. The connections between these are made by clamping the tails together, print side to print side, using a plastic clamp. This is not entirely satisfactory and can lead to some unexpected characters appearing. Replacing the Spectrum Plus keyboard is much simpler than with the earlier model however since it's assembled with screws instead of double-sided adhesive tape.

Keyboards are relatively cheap and as they often take a lot of punishment it's expedient to replace any that give trouble.

Tape and Sound Circuits

The tape recorder input and output and the speaker are always operated independently so only one pin of the ULA is used for all three. This combined circuit also provides a sound output from the speaker when the recorder is loading. There are few components in this area and it should be a simple matter to check that the circuit is working correctly. As a guide, a 5V peak-to-peak signal at the EAR socket should give a 2V p-p signal at the ULA. With almost all such tests however the best guide is to compare the suspect signal with that in a good machine. In this particular case, if the signal is o.k. but there's no

Table 3: Connections to edge connector pins.

Pin	Component side (top)	Underside
1	A15	(1) A14 (1)
2	A13	(1) A12 (1)
3	D7	(1) 5V
4	NC	9-11V
5	Slot	Slot
6	D0	(1) Chassis
7	D1	(1) Chassis
8	D2	(1) Clock. ULA pin 32
9	D6	(1) A0 (1)
10	D5	(1) A1 (1)
11	D3	(1) A2 (1)
12	D4	(1) A3 (1)
13	INT. CPU pin 16	IORQULA. ULA pin 33
14	NMI. CPU pin 17	Chassis
15	HALT. CPU pin 18	U.H.F. modulator input
16	MREQ. CPU pin 19	Y. ULA pin 17
17	IORQ. CPU pin 20	V. ULA pin 16
18	RD. CPU pin 21	U. ULA pin 15
19	WR. CPU pin 22	BUSRQ. CPU pin 25 (2)
20	-5V	RESET. CPU pin 26
21	WAIT. CPU pin 24	(2) A7 (1)
22	12V	A6 (1)
23	-12V	(3) A5 (1)
24	MI. CPU pin 27	(2) A4 (1)
25	RFSH. CPU pin 28	(2) ROMCS. ULA pin 34 (4)
26	A8	(1) BUSAK. ULA pin 23 (2)
27	A10	(1) A9 (1)
28	NC	A11 (1)

Notes: (1) These pins connect directly to the CPU address or data lines.

(2) Some CPU control lines are used in the Spectrum, some are not. The latter connect only between the CPU and the edge connector and are not shown on our circuit diagrams.

(3) Sinclair refer to this as -12V. It actually connects to TR4's load coil (see Fig. 4). TR4's collector waveform superimposed on a d.c. voltage is present at this pin.

(4) This pin does not connect directly with pin 34 of the ULA: it goes to the ROM side of R33, at its junction with the ROM link (see Fig. 1).

loading the ULA must be at fault. From bitter experience I'd recommend that you make this test before quoting for the job: the ULA is the most expensive item in the computer, costing over eight pounds at present, so it's not the sort of pricing detail to overlook.

The tape output at the MIC socket should be sufficient to produce a clean recording on a standard mono tape recorder. As this level is rather low the easiest check is to save a simple one or two line program then check that it loads.

Colour and Video Circuits

The colour and video section is where you come into your own. At least you can work on signals you recognise, even though they are being assembled into a composite video signal rather than being decoded from it.

The initial organisation of the display is carried out by the ULA, which every fiftieth of a second reads the display file – the memory area that holds the display details – and produces U, V and inverted-Y output signals. The U and V signals are fed to pins 4 and 2 respectively of the LM1889 video modulator chip IC14 which produces a standard PAL chroma output signal at pin 13. The chip incorporates a 4.43MHz oscillator which, in conjunction with the external crystal network, produces phase-shifted subcarriers at pins 1 and 18. The inverted-Y output from the ULA is inverted by TR1 and added to the chroma signal at the base of TR2. The resultant composite video output is then fed to a standard Astec u.h.f. modulator which produces an output on channel 35.

If the sound output works all right but there's a problem with the display you'll need to check the circuit with a scope. One of the best points for making checks, if you have a suitable socket, is at the edge connector (see Table 3). Pin 15 on the underside of the connector is the u.h.f. modulator's video input, pin 16 carries the inverted-Y signal from pin 17 of the ULA while pins 17 and 18 carry the ULA's V and U outputs. With the computer initiated, i.e. switched on, and no key pressed pins 17 and 18 will carry only the sync pulses. These are positive-going and of 0.8V p-p amplitude. If a colour border, or paper, is displayed blocks appear between these sync pulses. Fig. 7 shows a typical waveform but you must appreciate that the amplitude and polarity of the signal, i.e. whether it's above or below the sync base line, changes with the colour.

With a full-screen display the inverted-luminance signal at pin 16 is a normal looking TV line signal of 2.5V p-p with no colour burst. The colour burst is very pronounced at pin 15, which carries the u.h.f. modulator's input signal. The overall signal here is only 1V p-p however.

The Edge Connector

Having just referred to the edge connector, this seems a good point at which to provide the details of this output port. It's a double-sided 28-pin board-edge connector – sockets to mate with it are readily available. Every useful line in the computer is brought out to a pin and the connector provides a ready means of linking the computer to the outside world. Rather too ready at times since, as I've said before, my belief is that most of the damage to these machines occurs when devices are fitted or removed without first switching off.

Next month we'll review some of the differences between earlier and later versions of the Spectrum.

next month in

TELEVISION

● SERVICING THE FIDELITY ZX3000 CHASSIS

These sets like to go dead, blowing the chopper transistor and fuse. After careful tests the service engineer fits replacements and the set may work well for five to thirty minutes, after which there's a bang and the same fault is present. Using a variac at this stage is no help . . . If a certain procedure is followed however servicing becomes straightforward and the sets go on to give reliable service. Also the service engineer is relieved of considerable stress! David Botto explains how to go about it.

● COLOUR TUBE DEVELOPMENTS

This time we reach the screen: types of phosphor, methods of improving the contrast ratio, stripe pitch and faceplate glass characteristics. Also flashover and X-ray protection.

● THE SAA5000 REMOTE CONTROL SYSTEM

The final instalment in J. LeJeune's modern receiver circuitry series deals with remote control, specifically the Mullard SAA5000 system with infra-red transmission link.

● QL TEST PATTERN PROGRAM

A comprehensive test pattern program for the Sinclair QL computer, which is capable of producing a high-quality display. Devised by John de Rivaz, B.Sc. (Eng.).

● SERVICING THE TOSHIBA V5470

John Coombes provides a detailed guide to common faults on this Betamax VCR – symptoms and what to check. The same chassis was used in the Bush Model BV6900.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....
(Name of Newsagent)

Please reserve/deliver the September issue of TELEVISION (£1.20), on sale August 20th, and continue every month until further notice.

NAME

ADDRESS

Saturday Plight Fever

Chris Avis

Why does it all happen on Saturdays? From Monday to Friday business is just hectic: on Saturday the temperature rises to a fever pitch that no self-respecting fusible resistor would tolerate. Witness a few events during a typical Saturday in the life of yours truly. . .

8:30 a.m. Open shop-cum-workshop, then open bleary eyes and see Friday's leftover Ferguson 3765B (TX10, early version) on the bench. Complaint intermittent tripping. Find h.t. rail correct at 150V. Original focus unit replaced with improved version a few months before. Try further replacement anyway, just in case. Leave set on test.

9:00 a.m. Reconditioned Philips 550 (G8 chassis) running on display appears to have slight lack of height. About to remove back and adjust when first customer arrives with Rank T20 chassis (fortunately in cabinet).

"It's been going off for several weeks, but we could always get it back with a thump. Now it's gone right off."

Resist temptation to say it's probably concussed, agreeing instead with owner's request to collect set after lunch in time for wrestling – or boxing? TX10 trips again, but no tube flashover. T20 reveals an assortment of classic faults, including a short-circuit BU208A line output transistor and burnt pin 1 of connector 5Z1 on the line output panel. The BU208A's 1Ω base resistor (5R8) has been replaced with a 2-2Ω resistor and the 910Ω resistor (4R16) in the 12V regulator circuit with two paralleled 470Ω 1W resistors in series with one 680Ω 2W resistor! 5R8 replaced with a 1Ω, 4W resistor and 4R16 with a 1kΩ, 1W resistor mounted half an inch off the board. New BU208A fitted, set switched on and adjusted. Good picture, left on test.

10:00 a.m. TX10 back on bench. Decide to disconnect e.h.t. and focus leads from tube and try again.

10:15 a.m. Philips 550 definitely losing height – and width too. Must investigate before potential buyer appears but diverted by arrival of Prinz T125 monochrome portable and Amstrad CTV1400 colour portable, closely followed by respective owners. Prinz "comes on then blacks out", Amstrad "makes loud buzzing noise but there's no sound or picture". Both owners happy to collect on Monday – considerate, my customers.

Tackle Prinz first and discover sound o.k. but dark, fluctuating picture with low e.h.t., then no picture. Start signing "Some day my Prinz will come on", beat time on chassis with screwdriver and picture appears. Remember common fault associated with TO3 cased line output transistors and tighten this one's mounting nuts and bolts: e.h.t. now normal with good picture.

11:00 a.m. Amstrad CTV1400 sounds like wasp sprayed with freezer. H.T. rail at zero. Switch off, extract nearly twenty sewing pins from surface of main PCB and switch on – wasp still shivering. For two pins feel like giving up, but lengthy search reveals just those very items still clinging to the line linearity coil's magnet and shorting across to the collector of the line output transistor. No damage caused, thanks to power supply protection circuitry. (Female owner later confessed to keeping needle-work box on top of set – makes a change from flower

vases.)

12:00 a.m. TX10 hasn't tripped for two hours. Reconnect e.h.t. lead only and try again. Philips 550 now no picture or sound with the h.t. down to 100V on the BA13 power supply panel. Parallel 100kΩ resistors R1386/1373 in the charging/phase shift network look immaculate but one is open-circuit. Replacement restores status quo (and picture).

12:30 p.m. Early lunch break, necessitated by diabetes and early breakfast.

12:45 p.m. Investigate previously reconditioned Thorn 1590 12in. monochrome portable that had misbehaved recently when demonstrated to an interested customer. The picture rolled erratically, though the set had appeared to be o.k. on test earlier. Sync crushing in the i.f. stages suspected, perhaps due to an a.g.c. fault? The voltage readings around the first two i.f. amplifier transistors VT2/3 were o.k. but closer inspection revealed that they had both been replaced at some time with BF194s. The correct BF196 is appropriate for forward a.g.c., the BF194 isn't, hence ineffective a.g.c., excessive i.f. amplification and crushed sync pulses. Fitting the correct transistors cured the trouble. The set was put back on the shelf to await further interest.

1:45 p.m. Still no hiccups from the TX10: reconnect focus lead and switch on again – set trips once then runs normally. Watch closely for ages (at least two minutes) but no repeats. Interrupt vigil to serve customer with Shure N70B stylus at £6.24 including VAT (Valuable Avis Time). "I've tried everywhere but nobody has them. One place said they could order it for £15 then tried to sell me a new cartridge." No wonder I'm still struggling. TX10 takes another trip. Remove focus connector cover on tube base but no clue at spark gap. Could it be? . . . Order new base from HRS and hope.

2:30 p.m. Mr. Karate calls and collects his satisfactorily performing T20. Says he can manage to load set into car boot unaided but tries to take shop door frame with him as he passes through.

Door remains intact enough to admit gentleman with Sony TV121 12in. monochrome portable. "The picture is very bright with poor contrast and won't keep still, then it almost disappears. Someone has looked at it and says the high gain control may be faulty but it would have to be looked at by a Sony approved dealer." Doubt whether Sony would approve of several Ghastly Catastrophic Semiconductor conversions I've successfully done to KV1810s, KV2000s etc. thanks to helpful *Television* articles but promise to search diligently for "high gain control". Fortunately this proves unnecessary as the picture is large enough for a 20in. tube and the l.t. rail is 15V instead of 11.6V due to a faulty error detector/driver transistor (O602, type 2SC1209) in the series regulator circuit. Fit BC338 and find set none the worse for overdose of electronic adrenalin but put it on soak test to convalesce.

3:30 p.m. Mr. Karate returns with T20 and red face. "It's just the same as when I brought it in to you and paid good money for you to fix it." Well he didn't quite put it that way but that's what it amounted to. Set immediately checked on bench. Trips when switched on. Find plug 5Z2 on line output panel half off and EW modulator driver transistors 4VT17/18 damaged. Customer had put set into car boot on its back, which had pushed against 5Z2's plastic locating peg. Transistors replaced, 5Z2 refitted (peg length cut by 50 per cent) and set placed face down on back seat of car, all "under guarantee". We live

and learn – though live and earn would be better.
4:00 p.m. Just the set to end the week comes in – a Sony KV1810 Mk. I with no sound or picture. Set plugged in with sinking heart and preparation for last rites when gloom is pierced by noise on sound and raster on screen, though attempts to tune in signals are thwarted by wildly erratic tuning voltage variations. Voltage at tuning supply stabilising zener diode D209 o.k. so channel selector unit replaced with one from scrapped set. No difference. These sets have a tuning meter to show the approximate channel positions. It's driven by a transistor (Q215, type

2SA678) whose base is connected to the selected tuning voltage. Fitting a BC213L in this position restored stable tuning and good performance to this ten year old Senior Sony, but how long before Guesswhats Commit Suicide?

So another week drew to a close as a weak and drawn engineer locked up and tilled up. Good, there's enough to see us through Sunday and some left over for the VAT return and the mortgage and the rates and the Inland Revenue and. . . Oh well, at least the replacement TX10 tube base eventually cured the tripping. Makes it all worthwhile, doesn't it?

Resistor Troubles

Gordon Haigh

A good number of TV faults are due to resistor troubles of one sort or another. Here's a collection of resistor faults worth noting.

Thorn TX9 chassis: In the event of a poor, dark degraded picture with perhaps only the highlights present check the value of R233 (390k Ω , changed in late production sets to 300k Ω) which is in series with the first anode preset control. For reduced height or almost complete field collapse check R268 (1.5M Ω) and R269 (1.8M Ω) which are in series with the height control – in the early version of the chassis (main panel PC1001) a single 3.3M Ω resistor is fitted in this position (R268). If R223 (panels PC1001 and PC1040) is burning or distressed it's certain that the line driver transistor VT67/TR67 is faulty, also the 15V zener diode W87/D87: the replacement resistor should be a 470 Ω type.

Thorn 3500 chassis: If the 10 Ω wirewound resistor R751 on the convergence panel fails plenty of smoking, burning and damaged components will need replacing.

Fidelity CTV14R/CTV14S (ZX2000 chassis): If R826 (39 Ω , 1W) goes high in value the chopper transistor TR13 will soon fail.

Grundig 2210/2222/2252R/5012/6022: The trouble with one of these sets was no +B supply (14V) for the line generator/driver circuits. This supply is derived from a mains transformer which also supplies the c.r.t.'s heaters. The mishap here was that the fine primary wires were too close to R615 (4W) and R643 (7W): having got toasted and brittle they'd finally gone open-circuit.

A point to note with any Grundig set using a cluster of vertical wirewounds and with an unstabilised h.t. supply is that the h.t. can be alarmingly high, say over 300V when it should be around 280V, if surge limiter/dropper resistors have been replaced with types of the wrong value. I had a case where over-generous resoldering had unwittingly shorted one out.

Autovox 2284GB/2684GB etc.: Failure of the resistors in the focus control network is a common problem and getting replacements is often difficult. The focus VDR (type E298ZZ/103) from a GEC, Decca or ITT hybrid colour chassis can be used instead with a series resistor – see Fig. 1.

JVC 7440GB: The problem with one of these sets, which had been fitted with a newly regunned tube, was alarming picture size expansion accompanied by clicking noises. I turned the h.t. down from 120V to the correct 110V but there was no change. All roads led to the tripler but the

circuit I had showed this as a "black box" – no internal details were given. Experiments with universal types were not successful – the original is a special (it's a special price too at nearly £60). Feeling lumbered with the set and having a bit of spare time I decided to attempt an economy repair. After painstakingly removing the soft rubbery filler from the original tripler I found that all the original components could be recovered and that the design was conventional though with three additional 47M Ω resistors to provide a feed for the focus control (see Fig. 2). Using a universal tripler as a replacement, with the three recovered 47M Ω resistors, a stable, well focused picture was obtained though there are annoying brightness changes with camera switches (any ideas?). A complete waste of time? Not quite: I found out how the tripler had failed – the series resistor R had burnt out.

Harnesses and leads: I've been caught out on occasion through not tying up harnesses. I always now watch that the wires near the dropper in the G8's power supply don't touch the dropper – amongst other things the field output transistors don't then need to be changed. When the chassis is hinged up in solid-state Decca sets I always watch the RGB leads.

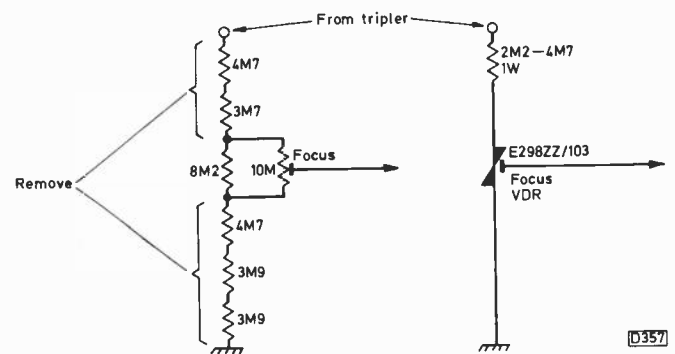


Fig. 1: Autovox focus circuit conversion – original circuit shown on the left. Bolt the focus v.d.r. to the right-hand heatsink on the Autovox chassis, high up, using a plastic nut and bolt.

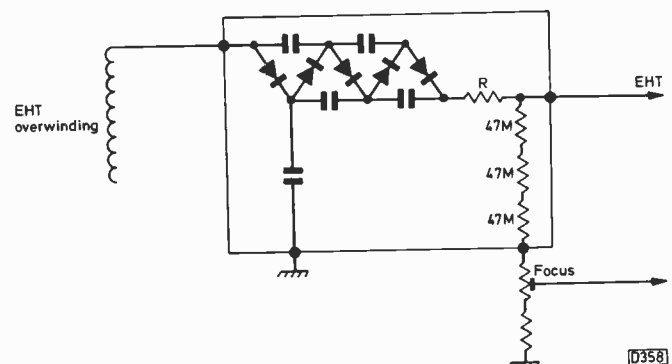


Fig. 2: JVC 7440GB tripler circuit.

Long-distance Television

Roger Bunney

Long-distance television reception conditions improved greatly during May. Many long, intense Sporadic E openings produced reception from most parts of Europe while several signals were received from Arabic sources. Here's a general log of SpE reception in the UK:

- 7/5/86 ORF (Austria) ch. E2A; TSS (USSR) R1, 2; TVR (Rumania) R2; ARD (West Germany) E2; RAI (Italy) IA; +PTT (Switzerland) E2; TVE (Spain) E2, 3.
- 8/5/86 CST (Czechoslovakia) R1, 2.
- 9/5/86 SR (Sweden) E2, 3, 4; CST R2; RTP (Portugal) E3; TVE E2, 3.
- 10/5/86 RAI IA; TVE E2, 3, 4; TSS R1.
- 11/5/86 TVE E2, 3, 4; RAI IA; ORF E2a; CST R1; TVP (Poland) R1; MTV (Hungary) R1.
- 12/5/86 TVE E2.
- 13/5/86 +PTT E2.
- 14/5/86 TSS R1; MTV R1.
- 15/5/86 TSS R1, 2, 3; CST R1; MTV R1; TVP R1, 2; JRT (Yugoslavia) E3; RAI IA, IB.
- 16/5/86 TSS R1, 2, 3, 4; YLE (Finland) E3, 4; SR E2, 3, 4; NRK (Norway) E2, 3, 4; TVP R1, 2; DR (Denmark) E3, 4; ARD E4; DFF (GDR-East Germany) E4; MTV R1; RAI IA; TVE E2, 3, 4; TVE-2 E2; RUV (Iceland) E3, 4.
- 17/5/86 NRK E2, 3, 4; SR E2, 3, 4; MTV R1; TSS R1, 2, 3, 4; TVP R1, 2; YLE E3, 4; +PTT E4; RUV E3, 4.
- 18/5/86 TSS R1; RUV E4; NRK E2, 4; RAI IA.
- 20/5/86 RAI IA.
- 21/5/86 CST R1, 2; MTV R1, 2; TSS R1, 3; TVR R2; JRT E3, 4; RAI IA, IB; ORF E2a.
- 22/5/86 RTP E3; TVE E2, 3, 4; TVE-2 E2.
- 26/5/86 TVE E3, 4; RTP E3; RAI IA, IB; JRT E3, 4; MTV R1, 2; TVR R1; ARD E2; RTS (Albania) IC.
- 27/5/86 RUV E4; NRK E2, 3; SR E2, 3; TVE E2, 3, 4.
- 28/5/86 TVE E2, 3, 4; RAI IA, IB; ARD E2, 3, 4; +PTT E2, 3; ORF E4; JRT E4.
- 29/5/86 NRK E2, 3, 4; SR E2.
- 30/5/86 TSS R1, 2, 3, 4; TVP R1, 2; YLE E3; RUV E3, 4; CST R1, 2; ORF E2a; ARD E2; MTV R1; RTS IC; RTP E3; TVE E2, 3, 4; +PTT E2; JRT E3, 4.
- 31/5/86 TSS R1, 2; RAI IA; NRK E2, 3, 4; SR E3; TVE E2, 3, 4; ARD E3; TVP R1, 2; RTM (Morocco) E4.
- 1/6/86 RUV E3, 4; NRK E2, 3; TVE E2, 3, 4; RAI IA.

- 2/6/86 SR E2; TSS R1, 2; TVP R1.
- 3/6/86 DFF E4; TSS R1, 2; RAI IA; TVP R2, 3.
- 4/6/86 TSS R1; RAI IA, IB; +PTT E2.

An extremely busy month then, with several points of interest. On the 15th and 16th the SpE m.u.f. reached the 2m (144MHz) amateur band – at 1900GMT on the 15th and for the whole morning from 0915 GMT on the 16th, the latter giving reception from Sweden, the USSR, etc.

At 1100GMT on the 16th Cyril Willis (Norfolk) noted a ch. E4 programme that went to Arabic credit titles at 1119. The same programme was visible on ch. E3 but much weaker. Any ideas? At 1358GMT on the 26th Cyril received a ch. E3 signal with poor picture quality and, in poor English, the following words: "Good evening. The Royal Garden Company will now play . . .". The signal was from the SSE. Thoughts are maybe NTA Nigeria, though the "good evening" would perhaps be too early! Again, any ideas?




At 1403GMT on the 30th Cyril received RUV ch. E4, a very strong signal that was followed by and changed with a much weaker, fluttery and rolling signal. The latter could have been a 525-line signal on ch. A2. Later that day Tony Privett logged Arabic singing/chanting along with TVE on ch. E3 at 1647GMT. The following day Tony hit the jackpot with RTM (Morocco) ch. E4 at 1599-1620GMT, showing an Arabic film. The signal was from the south west.

I had myself noted Arabic singing at 1356GMT on the 30th: the signal was at 52.8MHz, probably an obscure harmonic. On the same day here NCT or another Italian (ch. IA) private station was noted with a most unusual test card, vaguely resembling the FUBK pattern but with a prominent series of black/white squares across the top and a moving (right to left) caption at the lower centre.

Other reception notes are few. A small aurora was noted in Scotland on May 6th. There was a tropospheric lift over the 24-25th, giving DXers in the central and southern UK high-level signals from W. Germany and the Benelux countries in Band III and at u.h.f. Dave Shirley and Tim Anderson (Hastings) have both received French TV5 signals from Paris ch. E30 and Maubeuge ch. E32. Thanks to the following for reception reports to supplement my own log: Derek Juniper (Angus), Roger Pates (Nottingham), Reg Roper (Torpoint), Bill Cotteril (Tipton), Iain Menzies (Aberdeen), Tony Privett (Basingstoke), Simon Hamer (Powys), Cyril Willis (Norfolk), and Dave Shirley and Tim Anderson at Hastings.

News Items

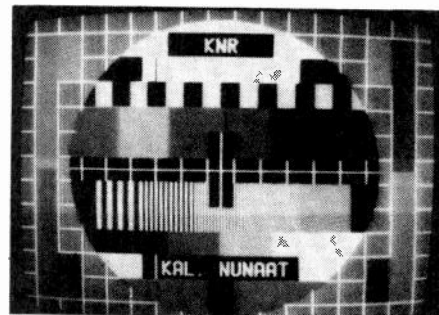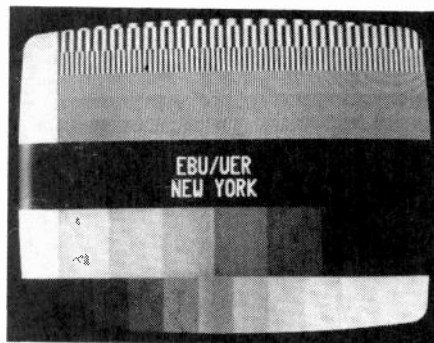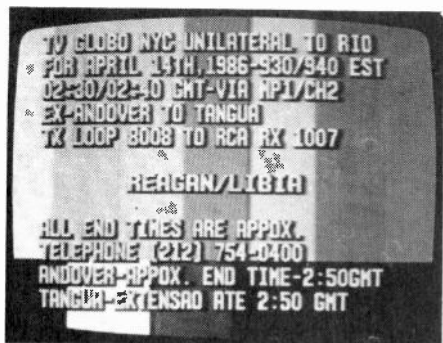France: The TV5 and TV6 networks are being distributed



Left: Newsfeed via Satcom F1 transponder 5 during the Libyan crisis, showing the signal routing. Centre: Newsfeed from New York to A2 France. Both photos from Frank Lumen in Denver. Right: The PM5544 test pattern put out by Kalaallit Nunaata Radioa, Nuuk, Greenland. Six ch. E10 transmitters operate in the south west of the country with powers around 1.5W.

throughout mainland France by the Telecom satellite, in scrambled form to prevent unauthorised viewing. Close examination of off-air signals along the south coast of the UK should reveal telltale random black ends to the scanning lines to confirm scrambling.

Denmark: The new TV2 network should commence operations in 1988, with twelve main regional transmitters and eventually fill-in relays where necessary. The service will be independent of Danmarks Radio (DR) and will be commercially financed. A 100W ch. E9 relay is at present operating near the main ch. E7 Sonderjylland transmitter.

Stereo sound: The Italian RAI-3 network (u.h.f.) is at present experimenting with stereophonic sound, using the two-carrier system. There are some two hours of stereo transmissions a week. In the USA NBC is gradually converting its entire system to stereo: over twenty hours of stereo broadcasts a week are at present being transmitted from fifty main stations covering 47 per cent of mainland USA, with satellite signal distribution.

Satellite news: The 4GHz Intelstat bird at 31°W has ceased operations. Libya (transponder 17) and Argentina (transponder 24) have moved to the Intelstat satellite at 27.5°W. NTA (Lagos) is on transponder 19 with "appalling quality" – the sound is likened to speech down a cardboard tube! The USSR has been testing a new satellite, with three TV channels at 32dBW level, at 11°W. TSS-1 remains on the 3-675GHz satellite at 14°W. Thanks to Nick Harrold for this information on 4GHz transmissions.

An unusual Ku band aerial was shown by the US firm Focus Technology at a recent exhibition. It's a flat, frequency-selective device made from a two-inch thick sheet of aluminium on which concentric parabolas are machined. The feedhorn is mounted at the focal point of the centre parabola.

On a personal note, I was surprised to see lightning flashes displayed on the picture while watching the CNN Europe 11GHz feed via a 2m dish during a heavy thunderstorm! Then down came the summer rain, the picture became noisy and virtually disappeared with loss of syncs. The picture gradually returned to the noise-free condition as the torrent subsided.

Multi-standard TV Receivers

The use of multi-standard TV sets with automatic

Table 1: S channel allocations.

Ch.	Bandwidth (MHz)	Ch.	Bandwidth (MHz)	Ch.	Bandwidth (MHz)
S2	111-118	S14	251-258	S26	342-350
S3	118-125	S15	258-265	S27	350-358
S4	125-132	S16	265-272	S28	358-366
S5	132-139	S17	272-279	S29	366-374
S6	139-146	S18	279-286	S30	374-382
S7	146-153	S19	286-293	S31	382-390
S8	153-160	S20	293-300	S32	390-398
S9	160-167	S21	302-310	S33	398-406
S10	167-174	S22	310-318	S34	406-414
S11	230-237	S23	318-326	S35	414-422
S12	237-244	S24	326-334	S36	422-430
S13	244-251	S25	334-342	S37	430-438

Belgian variations: S1-S10 referred to as M1-M10, S11-S19 as U1-U9, S20-S37 not used. Belgian channel S1 is 69-76MHz, S2 76-83MHz, S3 83-90MHz.



CATALOGUE ONLY 65p

EQUIPMENT & PROFESSIONAL ADVICE

Aerial Techniques offer a unique blend of the best equipment and impartial professional advice for Television/FM DXing or simply better domestic reception.

LABGEAR UPCONVERTERS ideal for TV-DXing, used but guaranteed in good working order, mains powered, limited stock **£17.95**

FERNSEH-ANTENNA DR1712 Combined Band 1/3 wideband aerial for TV-DXing, covers 47-68MHz and 175-230MHz; 2 elements (Band 1); 9 elements Band 3 gold anodised, requires single download **£48.70**

SPECIAL OFFER! - ANTIFERRECE XG14 Multi-element 17dB (peak) High Gain Wideband UHF aerial, covering channels 21-68 **£39.95**

LABGEAR CM7271 UHF Wideband Masthead Pre-amplifier, 15dB Gain; very low noise figure of only 1.6dB. High signal handling 200mV **£16.20**

LABGEAR CM7261 Matching Power Supply for above pre-amp **£13.50**

SPECIAL OFFER! - THOMSON TS 2503PI 10" screen Colour Television/Monitor, Multi-standard PAL/SECAM for Systems B/G/L, I and D/K with switching between PAL/NTSC/SECAM - the NTSC option is useful for watching AFN-TV in suitable locations. The set's coverage includes the S channels used for cable distribution. Because losses are greater at u.h.f. than v.h.f. in a cable system there's a tendency for cable operators to convert to v.h.f. Table 1 lists S channel allocations. Delivery 7-10 days. **£296.90**

'NEW' BEST OF CO-TV book by John Wood **£3.50**

Whether your need is for local or fringe reception, alternative channels, TV/FM DXing, or for a distribution system, Aerial Techniques is the 'one stop' address for all equipment.

All prices inclusive of VAT and Carriage. Delivery 7-10 days. ACCESS & VISA Mail and Telephone orders welcome.



AERIAL TECHNIQUES (T)

11, Kent Road, Parkstone,
Poole, Dorset, BH12 2EH. Tel: 0202 738232.



switching between standards is increasing. Luxor, Salora and Grundig all produce such sets. Our Brussels correspondent recently bought a Grundig P40/242/90 which can tune over 48-340MHz plus u.h.f., has 99 channel memory selection and a wide range of fine tuning. It covers systems B/G, L, I and D/K with switching between PAL/NTSC/SECAM – the NTSC option is useful for watching AFN-TV in suitable locations. The set's coverage includes the S channels used for cable distribution. Because losses are greater at u.h.f. than v.h.f. in a cable system there's a tendency for cable operators to convert to v.h.f. Table 1 lists S channel allocations.

Narrow-band IF Amplifier

The use of a narrow i.f. bandpass response for weak signal reception or for improved selectivity during an intense SpE opening gives greatly improved results. Most established DXers use a degree of switched selectivity. Originally use of a 405/625-line dual-standard receiver would do the trick, the 405-line section providing the narrow vision i.f. bandwidth required. Subsequently use has been made of surplus Philips G8 chassis vision selectivity modules and designs have appeared in this magazine (see the February 1982 issue). More recently HS Publications of Derby have introduced a commercial unit, type D100, that consists of an integrated tuner/i.f. strip with switched selectivity. Narrowing the i.f. bandwidth will reveal signals that are completely lost with a standard, wide i.f. bandwidth.

Paul Barton recently sent us a relatively simple circuit (see Fig. 1) that will provide a 2MHz bandwidth when correctly aligned. The components required are readily

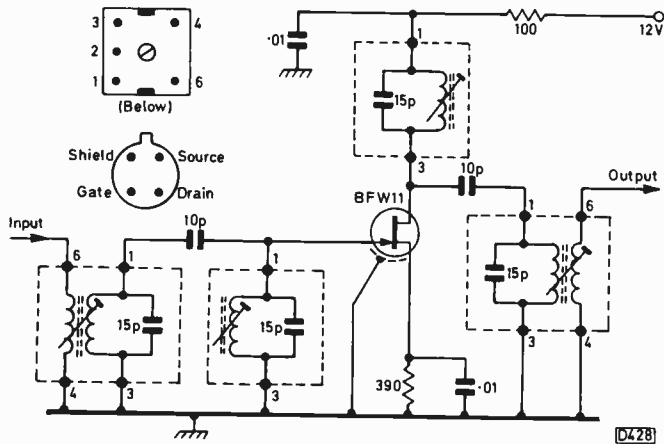


Fig. 1: Narrow-band i.f. amplifier circuit suggested by Paul Barton. All coils Toko type KANK3335R - available from Cirkit, order no. 35-33350.

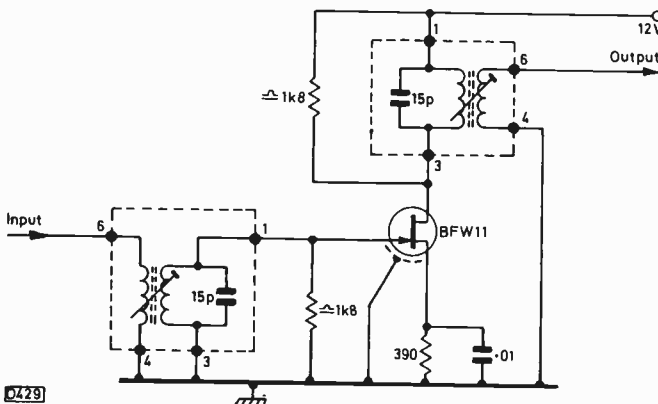


Fig. 2: Wideband version of the circuit.

available - mainly four Toko coils that can be obtained ex-stock from Cirkit. A pair of tuned circuits apply the input to the gate of a BFW11 f.e.t.: the output is taken from a second pair of tuned circuits of the same type. Construction is simple but lead lengths should be kept short. Alignment is also simple. Connect the circuit immediately after the tuner's i.f. output, tune in a weak but steady signal, then peak the four coils for minimum noise on the screen - start from the output.

It would in practice be better to build two such stages with one operated in the standard wideband mode. Fig. 2 shows a wideband circuit: damping resistors of about 1.8kΩ are required. Connect the two stages in parallel with switch selection at the input and output for wide/narrow bandpass operation. Our thanks to Paul for providing details of these circuits.

European Test Pattern Book

An excellent publication has recently been published in W. Germany, "TV-Bildkatalog", a collection of test cards/patterns etc. at present in use by various broadcasters in the European area. The 176-page book is in A5 size format and is bound with a thick gloss card cover: the reproduction is clear and sharp - noise is present on some of the pictures since they are off-air photos taken under DX conditions. The book covers Europe, the Mediterranean including Cyprus/Turkey and, to the east, the USSR. Unfortunately it doesn't cover the Middle East and North Africa. In addition to the photos there's a two-language (German and English) text describing the broadcasting

activities in each country. This highly recommended book is available from Aerial Techniques (T), 11 Kent Road, Parkstone, Poole, Dorset BH12 2EH at £5.95 including post and packing.

Cordless Phones

The DTI plans to introduce new legislation that will make it illegal to import, sell, manufacture or own non-approved cordless phones. This would make the at present commonly used 49 and 70MHz systems illegal. A New Malden company is now marketing an upmarket radiophone system operating in these bands. It's known as the Shuttle Ace System and has a basic range of 12km. Improved base aerials increase the range to 20km while a linear amplifier gives 100km.

Publications

Dave Shirley and Tim Anderson are distributing a DX-TV newsletter called *Screen Europe*. It aims to provide news and information on basic DX-TV techniques for all those interested in alternative TV reception. The first newsletter contains quite a lot of information on the French TV5 and TV6 networks, with valuable updated transmitter listings, and a page of test cards. For further information, a sample copy and details of "club subscription" write to Dave Shirley at 93 Alfred Road, Hastings, E. Sussex TN35 5HZ enclosing three 12p stamps and a foolscap s.a.e.

The German monthly magazine *Tele-Audiovision* has expanded from being a TV/FM DXing publication to a high-quality magazine covering TV/FM and in particular satellite reception. The latest issue runs to some 50 A4 pages. It contains much material for the satellite enthusiast and is perhaps the only European magazine that provides regularly updated technical details on this subject. Recommended, albeit in German. A single copy costs DM8 in Europe, annual subscription DM90. Write to *Tele-Audiovision*, Postfach 801965, D-8000 Munchen 80, W. Germany (telephone 089 448 03 28 from the UK). The first large edition (May/June 1986) is no. 36: it includes reviews of satellite downlinks and receivers, information on developments and general news on TV, radio and cable activity.

A Tribute

A correspondent well known in the DX-TV field passed away very suddenly on May 22nd. Reg Roper of Torpoint, Cornwall was in his 78th year and had been TV-DXing for over two decades. He was a true enthusiast who made most of the equipment he used, from aerials to amplifiers and receivers. Some years back he wrote for this magazine an article giving constructional details of a short backfire u.h.f. array - an aerial of this type subsequently became available commercially for a while.

Reg's finest hour came with reception of 860MHz signals from the ATS-6 satellite, broadcasting to India at 35°E, in 1976 using entirely home-constructed equipment. Reg introduced many enthusiasts in the Plymouth area to DX-TV, and on the night before his death had been planning a portable DX-TV expedition with several friends. He was also an active CB enthusiast and had experimented considerably with "hidden" aerials for 27MHz. He wrote to us only a few days before his death, giving details of SpE reception during early May - active to the end. Our sympathy goes to his immediate family in their sad loss. We will miss you Reg, rest in peace. Roger B.

If you've Got it, Flaunt It!

With Teleafit, one man can transport heavy TVs and appliances alone and in complete safety.

Whilst Teleafit has just become available in the UK, it has been extensively field-tested both here and abroad - in fact to date, hundreds of Teleafits have lifted and shifted in excess of half a million TVs without injury to the set or the operator.

Teleafit was specifically designed for TVs, but it has proved equally successful for a wide range of heavy appliances.

For further information please contact Malcolm Richardson, SEME Limited, Unit 2E Saxby Road Industrial Estate, Melton Mowbray, Leicestershire LE13 1BS. Telephone (0664) 65392.



Satellite TV

Stockists of 4, 11 & 12GHz Equipment. Distributors for:



DH Satellite TV



DX ANTENNA

Specialists in supplying to Dealers

Harrison Electronics

22 MILTON ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 7JX. ENGLAND
TELEPHONE: (0702) 332338 TELEX: 995801 GLOTLX-G REF: H25

BILLINGTON VALVES

23 Irwin Dr., Horsham, W. Sussex RH12 1NL

Mail Order Only - Callers by Appt. only

NEW BOXED VALVES - 90 DAY GUARANTEE

DY87	45p	KT66 USA	1000p	PCL85	55p	PL519	440p
DY802	43p	KT66 GEC	1400p	PCL86	54p	PL802	600p
ECC81	115p	KT88 USA	1100p	PCL805	55p	PL802T	390p
ECC82	40p	PCF802	55p	PL504	90p	PY88	45p
ECC83	55p	PCL82	60p	PL508	165p	PY81/800	65p
EL34	250p	PCL84	45p	PL509	480p	PY801	65p
						PY500A	150p

E.H.T. MULTIPLIER. Good quality universal triplers £4.40 + VAT + post. Suitable for most sets - B+O, Decca, GEC, Grundig, IIT, Philips, Pye, Rank & continental sets.

BU208A TRANSISTOR. Good quality 75p ea + VAT + post.

C.R.T. 12" A38/170W Hitachi with scan coils £10 + VAT post paid - Ideal for a monitor.
15" A38/170W Hitachi £8 + VAT post paid.

Please add 50p post/pkg per order and VAT @ 15%. Please allow up to 8 days for delivery. Massive stocks of all the above types! Every popular type stocked and we specialise in unusual types. SAE quotation on any type not listed. SAE catalogue. Govt + export orders welcome. Discounts given for v. large quantities.

WE WILL BUY VALVES + TRANSISTORS! Including complete shop clearance etc. We urgently require a qty of valves types PX4 + PX25 (or equivalents PP3/250, PP5/400, DA30) Ex-equipment would be acceptable. Please state price required, if possible.

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY A816 solid state mono 9.00 CROWN 14CX25 15.00	PHILIPS 170 series dual std mono 8.00 210 300 series mono 8.00 G8 & G9 series colour 8.00
DECCA MS1700 2001 2020 2401 mono 7.00 MS2404 2420 2424 mono 7.00 CS1730 1733 colour 9.00 CS1830 1835 colour 9.00 '30' series Bradford colour 9.00 80 series colour 8.00 100 series colour 8.00	PYE 368, 169, 569, 769 mono 8.00 725-741 colour 8.00 REDIFFUSION Doric Mk.3 10.00
FERGUSON HMV MARCONI 1600 8.00	WINDINGS Autovox 2282 2693 8.00
G.E.C. 2047 to 2105 7.00 2000 to 2064 dual std mono 7.00	RANK BUSH MURPHY A640, A793, A774 overwind 6.00 T20a T22, T26 Pri & Sec 6.00 Z718 primary state 18" or 22" 6.00 Z718 EHT overwind 8.00 SONY 1320UB overwind 15.00
Indesit 20EGB 24EGB mono 8.00	SOVEREIGN FARA 14" colour overwind £15.00
KB - ITT VC200 VC205 VC207 mono 8.00 CVC5 CVC7 CVC8 CVC9 col. 9.00 CVC20 series colour 8.00 CVC30 CVC32 series colour 8.00 CVC45 8.00 FT100 FT110 state p/n. 10.00 TXV80 10.00	ULTRA THORN 1690-1691 EHT overwind 7.00 Waltham 190 EHT overwind 6.00 1590 EHT overwind 6.00

**PRICES INCLUDE
P.P. & 15% VAT**

All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm
Delivery by return.

**PAPWORTH
TRANSFORMERS**

80 Merton High Street,
London SW19 1BE

REWIND SERVICE
S.A.E. all enquiries
Barclaycard and
Access welcome



24 hour answering service

For orders placed at the post office
Trans cash
506 4856

01-540 3955

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.50 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

MITSUBISHI CT202B

The picture is good apart from the presence of Hanover bars. An attempt to adjust the decoder has produced only a marginal improvement. Any hints on likely component failure would be welcome.

Associated with the chroma delay line are a potentiometer marked "level adjust" or "amplitude adjust" and a miniature coil which is directly connected to the pins of the delay line. Clean the potentiometer thoroughly with switch cleaner/lubricant, scrubbing the slider to and fro to clean the track, then carefully adjust the potentiometer and coil to remove the Hanover bar effect. If the bars cannot be eliminated it's likely that the delay line itself is faulty.

TOSHIBA V31B

Peak white parts of the display have a sideways wobble to the right, especially captions and teletext (Ceefax in vision etc.). There's also spaghetti though this is not as noticeable as the wobble which is sometimes severe, making the picture unwatchable. The f.m. deviation and sync tip frequency controls have been set up correctly. Turning down the deviation reduces the wobble but gives a duller picture. One or two voltages around IC201 (TA7693P) are slightly out. Could this be the cause of the trouble?

While IC201 could be faulty it's unlikely – we would expect greater voltage changes if it was defective. From our experience of this machine we feel that the problem lies in the head itself. Before condemning the disc, try thoroughly cleaning it. We've found that rotating the head tips against a stiff card, e.g. a visiting card, held against the cylinder sometimes does the trick.

GRUNDIG 6010

This set suffers from an intermittently over bright raster with flyback lines and foldover. I've replaced the components in the line scan thyristor's gate circuit – they showed signs of previous damage – and have also gone over the joints in the line timebase area. The first anode presets and their feed resistor R546 have been replaced – they had also suffered some damage – but the problem persists.

The field foldover is an important clue, suggesting that the supply to the field timebase is falling when the fault is present. Assuming that pin E of the line output transformer is firmly earthed, this may well be due to a heavy load on the e.h.t. supply and the line output stage during the fault condition. Check the c.r.t. base voltages when the fault is present. If the grid voltages rise, suspect control Ab which sets the bias applied to the colour-

difference output transistors, and the colour-difference panel. If the cathode voltages vary, check the continuity of the 279V supply to pin 13 of the luminance panel then suspect the BF459G output transistor and IC365 (TBA970) in that order. If the first anode voltages rise, check R545 on the "earthy" side of the presets.

ITT CVC1112 CHASSIS

At switch on there's no sound or colour. The brightness and contrast appear to be normal but the customer contrast control has no effect. No commands from the remote control handset alter the settings. The standby LED is lit all the time and after several minutes the set goes off. Operating the on/off switch restores the initial conditions, the fault sequence being repeated.

A very common cause of these symptoms is failure of the 18V regulator IC1401. If replacing this three-legged chip doesn't cure the problems the SAA1251 remote control receiver chip is suspect.

HITACHI VT8300

The machine unlaces about five-six seconds after selecting the play mode. All the motors turn but the pinch roller doesn't engage. The solenoid has been replaced with no effect.

It seems that loading is not being completed. The most likely cause of this is a stretched loading belt, in which case replacement will cure the problem. If not, check at pin 29 of IC901. This should change state at the end of the loading sequence. If it doesn't, check the loading switches under the loading motor and replace or adjust as necessary. If you still have problems there's a mechanical fault as the pinch roller is mechanically engaged by the loading motor, the solenoids being merely for the operation of the various brakes. Try loading the machine by hand, turning the loading motor with the machine unplugged: examine the mechanical operation carefully.

DECCA 80 CHASSIS

The original fault was low, distorted audio. I've changed the i.c.s that handle the sound signal and have checked thoroughly for dry-joints. There don't seem to be any obviously leaky capacitors. The sound is now good, after adjusting the appropriate coils, but is still of low amplitude.

First ensure that the shunt regulator controlling the supply to the audio amplifier chip is working correctly: there should be 25V at pin 1 of the TBA800 audio chip – this voltage should vary little with load. If necessary disconnect PIC4 on the i.f. panel. If this increases the volume pin 5 of the TBA120S intercarrier sound chip is being incorrectly biased. If there's no change check the speaker coupling capacitors C146/7 (both 220 μ F) before suspecting the speaker itself.

RANK T16A CHASSIS

The problem with this monochrome portable is excessive height. Extensive checks in the field timebase have failed to reveal anything at fault.

Excessive height usually suggests lack of negative feedback. We suggest you check R43 (1 Ω), C34 (47 μ F), R41 (33 Ω) and R39 (220 Ω). Leakage in D5 (1N4148) could also increase the scan amplitude by supplementing the height control network.

TEST CASE

284

Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

The Philips K30 chassis was designed for use with the 30AX tube and produces a good picture. It's difficult for us to assess its reliability since we've never sold any of these sets (we're not Philips agents). The odd one or two that come our way will have moved into this area with their owners or been sold by other dealers in the district. Unfamiliarity is no excuse however for the ninth-rate diagnostic procedure to be described. . . .

The owner staggered into our service department carrying the set in his arms. Between panting and puffing he managed to get out that the problem was no colour. The set went on to the bench in due course: it produced a very good black-and-white picture without a trace of colour. Just as the man said. With the set tuned to the workshop colour-bar generator's output a subcarrier dot pattern was seen, indicating that the chroma signal was being correctly received. An oscilloscope check at the chroma channel input coil L3195 then proved that adequate chroma signal was being applied to the TDA2560Q luminance/chroma chip IC3192 – the set had the earlier two-chip decoder.

The next check carried out with the scope probe was for the presence of the reference signal at crystal X3233. The signal was present but the scope wouldn't lock to it in the usual way. The excitement died down when it was realised that the crystal is an 8.86MHz one, as is usual with more recent sets.

To override the colour-killer on this decoder panel you earth pin 16 of the TDA2523/4Q reference signal generator/demodulator/matrix chip IC3223. This was done but it had no effect on the monochrome picture. Back to the scope. A check at pins 5 and 6 of IC3223, where the output signals from the delay line circuit should be present, revealed that the colour signals were not reaching this point. They weren't present at the input to the delay line or at the output pins of the TDA2560Q i.c. either. There was a perfectly good burst signal however, and this disappeared into noise when the colour-bar generator was switched off. Well!

The presence of the burst signal in the delay line circuit, followed by a long gap where the colour-bar chroma signal should have been, convinced our man (who shall remain nameless) that something very strange was happening in the TDA2560Q i.c. He scoped pin 5 of the decoder panel and after some deliberation pronounced that the sandcastle pulse was present and correct with respect to amplitude and shape. He then confirmed that it was reaching pin 3 of the TDA2560Q unscathed. A

further check at pins 1 and 2 of the i.c. (balanced chroma input) confirmed that the complete chrominance signal was present here. It seemed safe to assume that the TDA2560Q chip was faulty, so a new one was ordered from our friendly supplier. While he awaited its arrival however our man was beset by doubts as to whether the replacement would cure the fault.

And it didn't! Of course not! The new chip produced exactly the same results, with the same burst only output at pin 6. The problem was really down to lack of knowledge on the part of the man with his oscilloscope. He would have done better in fact with a test meter! A read of the circuit description might also have helped, but wouldn't have been essential.

What did our man miss? Why was the burst signal coming through the delay line without the chroma signal? One voltmeter reading would have revealed the root of the problem, as we'll see next month.

ANSWER TO TEST CASE 283 – page 596 last month –

Last month we followed the progress of an Hitachi Model CBP220 (NP8CQ chassis) through field and workshop diagnosis of two faults. The first was simply solved on site but the second, intermittent problem was something of a puzzler. In spite of reasonably correct cathode and first anode voltages the raster would sometimes, especially from cold, be of vastly increased brightness with flyback lines. The tube itself could have been responsible, but this seemed unlikely in the circumstances (fault clearing as tube heated).

The only logical conclusion in view of the symptoms and test results was that the common grid pin was "floating", and so it proved to be. The tube's grid pin was firmly in contact with its base socket: the problem lay on the c.r.t. base panel. On this panel the printed lands for the electrode connections have a narrow neck connected to a printed earthing ring: during manufacture the neck is broken by a machined slot to provide a spark gap. In the case of the earthed control grid land print the copper neck is made wide to give continuity around the ends of the short slot – the print pattern can just be discerned at about seven o'clock on the base panel in the photo on the front cover of the June 1985 issue. In our set a hairline crack had spread sideways from each end of the machined slot . . .

QUERY COUPON

Available until 20th August 1986.
One coupon, plus a £1.50 (inc. VAT)
cheque or postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 666.

TELEVISION AUGUST 1986

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by the The Riverside Press Ltd., Thanet Way Whitstable, Kent. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £14, overseas (surface mail) £17 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

SPECIAL OFFER THIS MONTH

**PHILIPS YEARS AHEAD
THE CREDIT CARD CALCULATOR
SOLAR POWERED £6.00**

NEW PHILIPS SBC 1833 Solar & Battery Powered Calculator £10.00

NEW PANELS

G8 100K Pots on Panel & Lead for 6 Push Button Unit	£2.00
K30 Mains Switch remote	£1.00
K35 Mains Switch remote	75p
K35 Aerial Socket and Plug in Lead to Tuner	£1.50
KT3-K30 Slider Pots 4.7k/47k	20p each
LARGE Focus Pots. Fis Pye, GEC, ITT, Decca	50p
G8 Power Supply Panel	£4.00
THORN 4000 LOPT Panel	£15.00
THORN 9000 Line Panel	£12.00
THORN 8000-8500-8800 Decoder	£10.00
GLASS BEADS Diodes 20k/1.2A	25 for £1.00
G11 IF Panel	£9.00
THORN 9600 Line Panel	£12.00
G11 Decoder Panel	£8.00
POWER SUPPLY 731	£6.00
G11 611 Condenser 470/250V ITT	£1.50
G9 Power Panel	£3.50
G8 Line Panel	£12.00
G8 6 Push Button	£9.00
KT4-KT3-K30 Handset Replacement	£8.00
HT520 METER 20,000 Fuse Diode Protector Logic Test Facility	£15.90
9000 SERIES Decoder 01 929 014 080 Thorn	£5.00
THORN TX remot panel. SI. C. ML923-SL490-MC14528B-MC14493P-SL470 & Main Trans	£5.00
20AX GEC LOPT Panel with Split Diode	£4.00
LOPT Split Diode 2432871	£7.00
RANK T20 Focus Pot	£1.00
RANK 718 Focus Pot	75p
THORN 9000 LOPT Panel	£12.00
26" LOPT Split Diode 2432301	£8.00
16" LOPT Split Diode 2433481	£6.00
Ex Panel Split Diodes 2432871/2432981	£5
HITACHI Mains Switch	50p
HITACHI AE Socket	30p
1 CONDENSER Axial Leads 450 A/C 1200 D/C	15p
MAINS TRANSFORMER 240v in/20w/8v	£1.00
GREEN FLAT, NEC, LED's	3p each 100 for £2
12+12V 2.8VA Print 1"x1"	75p
8+8V 1 Amp Print	75p
HITACHI 6 x 4 - 80 Speaker	50p
ET596 UHF V/CAP Tuner, small	£2.50
FIDELITY Panels with LC	£1.00
FIDELITY LOPT Split Diode AT2076/80	£3.00
FIDELITY FBS 1245AE LOPT Mono	£1.00
FIDELITY Split Diode FCC2015BE	£5.00
HI-FI MICROPHONE N8501 Philip	£8.00
G8 TUNER V/CAP on Panel	£3.50
G8 SPEAKER	75p
4000 TRIPLES	£3.50
9,000 SPEAKER	£1.00
5 AMP METERS, AC, DC	£2.00
THORN 9000 Sound OP Panel	£30p
ONE LC K35 Decoder	£7.00
THICK FILM, Hitachi RB-32 4A	£2.00
K30 IF/K35 IF	£1.00
THICK FILM, Hitachi Frame	£5.00
THORN Lopt 8500-8800	£4.00
TX9 THORN Tuner Panel with ICS Pots	£3.00
80 ft THORN Speaker	15p
Split Diode 2433752	£6.00
BY223 Replacement	30p
THORN CHASSIS 1600-1700 Series Mono	£10.00
THORN 1600 Rec & Anode Cap	50p
KT3-K30 Slider Pots 4.7k/47k	£1.00 for 10
ET-614 UHF V/CAP Tuner	£2.00
6 x 2 1/4 SPEAKER 5W Hitachi 80	50p
K35 20 Turn Pots	6p each
HITACHI & GEC 20k Pots	20 for £1.00
KT3 K30 Speaker	30p
K35 Sound O/P Panel Plug in	£1.00
K35 12 way Push Button Unit	£1.50
K35 L.O.P.E. Split Diode	£6.00
RANK T20 Front Panel	£6.00
G8 6 Button Unit, New Type	£9.00
6 off LED DISPLAYS, Mixed	£1.00
HAND SET TESTER, Infra Red	£8.00
PHILIPS SBC 471 2 Way Stereo Headphone with Volume Controls	£17.00
AERIAL SPLITTER with filter	£1.00
DYNAMIC STEREO HEADPHONE EM 6146	£10.00
PHILIPS UNI DIRECTIONAL Dynamic Microphone	£10.00
20 TURN POTS with Band Switch	10p
PUSH BUTTON Mains Switch with Screw Holes Fixing	4 for £1
PYE 713 Line Trans	£4.50
PYE 731 Line Trans	£1.50
8000 DIODES at 1 amps. Glass Beads	6p each, 20 for £1.00
PYE 6 Touch Button Unit for G11 with IC and Cable Forms	£10.00
KT3 Line Output Transformer	£5.00

SENDZ COMPONENTS

63 BISHOPSTEIGNTON,
SHOEBURYNESSE, ESSEX SS3 8AF.
SAME DAY SERVICE

All items subject to availability. No Accounts. No Credit Cards. Postal Order/
Cheque with order. Add 15% VAT, then £1 Postage. Add Postage for Overseas.
Callers: To shop at

212 LONDON ROAD, SOUTHEND. Tel. 0702-332992

Open 9-1/2.30-6. GVMT + school orders accepted on official headings. Add 10% handling charge.

VIDEO HEADS

AKAI VS9800, VS9500, VS9700, VS9800	£34.90
FERGUSON 3V00, 3V16, 3V22, 3V23, 3V24, 3V29, 3V30, 3V31, 3V35, 3V36	£34.90
HITACHI VT4000, VT4200, VT5000, VT5500, VT6500, VT6800, VT8040, VT8300, VT8500, VT8700, VT9300, VT9500, VT9700, VT11	£35.95
JVC HR3300, HR3320, HR3330, HR3660, HR4100, HR7200, HR7600, HR7650, HR7700	£34.90
SHARP VC381, VC383, VC385, VC386, VC2300, VC3300, VC6000, VC6300, VC7300, VC7700, VC8300, VC9300, VC9500, VC9700	£45.95
SANYO VTC5000, VTC5350, VTC5400, VTC5500, VTC9100, VTC9300, VTC9350, VTC9500	£45.95
SONY SL8000, SL8080, SL8500, SL8600, SL8650, SL8700, SL8750, SL8760, SL8770, SL9990, V9500, V9550, V9600, V9650, V9700, V9750, V9800, V9850, V9900, V9950	£38.50
NATIONAL PAN. NV333, NV2000, NV3000, NV7000, NV7200, NV7800, NV8050, NV8400, NV8600, NV8610, NV8620	£45.95

PINCH ROLLERS

Awa, NEC, Sony, Toshiba, etc.	£4.95	National Panasonic	£4.95
Akai, JVC, Mitsubishi, Nordmende, Saba, Telefunken, Thom, etc.	£4.95	Sanyo, Fisher, Tensai, etc.	£4.95
Akai VS9700	£4.95	Sharp	£4.95

MOTORS, CLUTCH ASSEMBLY, IDLERS, ETC.

JVC & FERGUSON CAPSTAN MOTOR, PU45979	£26.50	SHARP CAPSTAN MOTOR, VC8300	£32.89
JVC & FERGUSON DRUM MOTOR, PU46414M	£26.50	SANYO REEL DRIVE PULLY	£8.50
JVC & FERGUSON CLUTCH ASS. 01K01003368	£5.95	SANYO REEL MOTOR 5000	£13.50
JVC & FERGUSON CLUTCH ASS. 01K01018729	£6.50	SHARP REEL IDLER, VC381, 9300, ETC.	£3.90
SONY REWIND KIT, CS,C6,C7	£4.85	HITACHI FFREWIDLER, VT8000	£4.75
SHARP CAPSTAN MOTOR, VC7300, VC7700, VC7750	£19.45	HITACHI PLAY IDLER, VT9300	£6.50

VIDEO BELT KITS

AKAI VS2EG, VS5EG, VS9300, VS9500, VS9700, VS9800	£2.95
FERGUSON 3292, 3V10, 3V11, 3V16, 3V22, 3V23, 3V24, 3V29, 3V30, 3V31, 3V32, 3V35, 3V36	£2.95
FISHER VBS7000, VBS7500, VBS7600, VBS9000, VBS9900	£2.95
HITACHI VT3000, VT5000, VT8000, VT9500, VT33	£2.95
JVC HR3300, HR3330, HR3660, HR3660, HR4100, HR7200, HR7650, HR7700	£2.95
NATIONAL PANASONIC NV330, NV333, NV2000, NV3000, NV7000, NV7200, NV8600, NV8610	£2.95
SANYO VTC5000, VTC5350, VTC5400, VTC5500, VTC9300	£2.95
SHARP VC381, VC383, VC385, VC386, VC6000, VC6500, VC6600, VC7300, VC7700, VC7750, VC8300, VC9300, VC9500, VC9700	£2.95
SONY SL3000, SL8000, SL8080, SL8500, SL8600, SL8650, SL8700, SL8750, SL8760, SL8770, SL8780, SL8790, SL8800, SL8810, SL8820, SL8830, SL8840, SL8850, SL8860, SL8870, SL8880, SL8890, SL8900, SL8910, SL8920, SL8930, SL8940, SL8950, SL8960, SL8970, SL8980, SL8990, V9500, V9550, V9600, V9650, V9700, V9750, V9800, V9850, V9900, V9950	£2.95
TOSHIBA VS475, VS480, VS600	£2.95

RECTIFIER TUBES	PYE	ELECTROLYTICS	SEMICONDUCTORS	ICs (Cont.)
THORN 691/693	713/715/4LEAD £6.50	PHILIPS GR600/300 £2.25	BC640 £0.19	TB8810 £0.99
1400 35T £4.00	713/715/5LEAD £6.50	G9600/300 £2.44	BC131 £0.19	TB8810 £1.25
1500 35T £5.35	A823 £8.50	G11470/250 £2.25	BD132 £0.35	TB8820M £0.85
1500 55T £5.35	T20/T20A £7.50	TIP31A £0.29	BD139 £0.30	TD81 70 £1.56
3000 £8.00	UNIVERSAL £7.95	TIP32A £0.29	BD140 £0.30	TD8200 £1.25
8000 £6.00	PHILIPS G8 £7.95	TIP31C £0.35	BD202 £0.49	TD8203M £1.60
8500 £8.00	G9 £9.25	TIP41A £0.39	BD202 £0.49	TD8203M £1.65
9000 £8.95	G11 £13.95	TIP41C £0.45	BD202 £0.49	TD8203M £1.65
DECCA 1730 £4.95	RANK A840 £11.50	TIP295 £0.60	BU126 £1.10	UPC1181 £1.25
1830 £4.95	A774 £12.95	TIP295 £0.60	BU126 £1.10	UPC1182 £1.25
2030 £7.50	A823 £11.95	BC147 £0.10	BU208 £1.45	UPC1156 £1.76
2230 £7.50	T20 £12.50	BC148 £0.10	BU208 £1.45	UPC1156 £1.76
2630 £7.50	PYE 697 PC £13.50	BC149 £0.10	BU208 £1.45	UPC1200H £3.25
30 £7.50	UNIVERSAL £7.95	BC152 £0.10	BU208 £1.45	UPC1200H £3.25
ITT CV1-9 £8.50	THORN 8000 £18.95	BC158 £0.10	BU208 £1.45	UPC1200H £3.25
DVC20/25/30 £8.25	8000A £18.95	BC158A £0.10	BU208 £1.45	UPC1200H £3.25
DVC45 £8.65	8500/8800 £15.95	BC171A £0.10	BU208 £1.45	UPC1200H £3.25
PHILIPS G8 520/530 £6.95	9000 £20.45	BC237B £0.10	BU208 £1.45	UPC1200H £3.25
G8 550 £6.95	9600 £13.45	BC327 £0.10	BU208 £1.45	UPC1200H £3.25
G9 £7.50	9800 £30.65	BC327 £0.10	BU208 £1.45	UPC1200H £3.25
KT3 £7.50	763 £19.95	BC327 £0.10	BU208 £1.45	UPC1200H £3.25

UNIVERSAL ELECTRONIC DISTRIBUTORS

40 SILVER ARCADE, LEICESTER LE1 5FB. TEL: 0533 29438

MINIMUM ORDER £5.00 PLEASE. AND WELCOME. PLEASE ADD £1.00 P&P AND 15% VAT TO THE TOTAL. ALLOW MORE POSTAGE ON HEAVY ITEMS. PLEASE ALLOW UP TO 7 DAYS FOR DELIVERY.

GETTEL

SUMMER CLEARANCE SPECIALS

VHS VIDEO FROM £40 IN TENS
THORN · PHILIPS · DECCA · PYE · ITT
SONY · SANYO · ETC. ETC.
SONY C7 OFF PILE ONLY £35
SANYO 5000 WORKING £75
FOR THE BEST PRICES IN TOWN
RING 0708 861404
2 BREACH ROAD, WEST THURROCK
ESSEX RM16 1NR

HITACHI VHS COLOUR CAMERAS

**Mains Only Tested/
Working**

VHS VIDEOS

FERGUSON

**3V00, 3V22, 3V23, 3V16, 3V29,
3V30, 3V31, 3V32, 3V35**

**NATIONAL PANASONIC
NV8600, 8610, 2000, 7000,
370, 333, 2010**

SHARP

620, 630, 640, 2300 H T/P

BETAMAX

SANYO VTC 9300, 5000, 5300

**SONY C5, C6, C7, C9
and SL F1UB T/P**

Also Bush, Toshiba, Hitachi and Blau Punkt

PLUS

**17" 18" 20" 22" 26" Hybrid/
Solid State CTVs**

Remote Control & Teletext

Discount for Quantities

Complete loads delivered from pick up point

**JOHN CARTER
(Electrical) LTD
FURNACE ROAD,
GALLOWES INN,
ILKESTON**

Phone: 0602 303124

CINEMA VISION PROJECTION UNITS

★ ★ ★ ★

**Philips, Grundig,
Toshiba, National
Panasonic and ITT. 40",
45" and 78" screens.
Floor and suspended
models. New boxed and
used. Quantity of test
equipment.**

**Oscilloscopes, cross
hatch – pattern – colour
match – colour bar –
and signal generators.
Avo and Taylor test
meters. Televerters slot
meters.**

RADIO TELEPHONE SYSTEMS

★ ★ ★ ★

**John Carter (Electrical) Ltd.,
Furnace Road,
Gallows Inn,
Ilkeston,
Derbyshire.
Phone 0602 303124**

MANTEL

No 1 for Quality TVs & Videos 100s of V.H.S. Videos in stock

Large Quantities of Late Model Thorn TVs. All with first class cabinets.

TELE-TEXT/ULTRASONIC/INFRARED/REMOTES

All at UNBEATABLE PRICES for QUANTITY & QUALITY

Also Philips G11/Pye G11/Basic/Remote/TELE-TEXT

Some examples of QUALITY working TVs

THORN 8800 ★★★★★★★★★★★★★★★★★★ £25
 THORN 8800 (remote) ★★★★★★★★★★★★★★★★★★ £30
 THORN 9000 ★★★★★★★★★★★★★★★★★★ £30
 THORN 9000 (remote) ★★★★★★★★★★★★★★★★★★ £35
 THORN 9600 ★★★★★★★★★★★★★★★★★★ £40
 THORN 9600 (full feature remote) ★★★★★★★★★★★★★★★★★★ £45

THORN 9600 TELETEXT ★★★★★★★★★★★★★★★★★★ from £75
 (VARIOUS MODELS)
 THORN 9900 ★★★★★★★★★★★★★★★★★★ £50
 THORN 9900 f/remote ★★★★★★★★★★★★★★★★★★ £60
 PHILIPS G11 ★★★★★★★★★★★★★★★★★★ £55

(prices quoted are based on quantity)

NO DEALER TOO LARGE OR SMALL. SINGLES SOLD

Brand New Remote Control Hand Sets Available for the majority of British & European TV sets.

1000s of UNTESTED Colour TVs

I.E. DECCA 30s, GEC 2110, GRUNDIG, TANBERGS, G8s 520s-550s, Thorn 3500/8000/8500, TT, PYE, ETC.

(Many of these untested TVs just switch on)

ALL AT LOW LOW PRICES

VAN LOADS DELIVERED DIRECT FROM SOURCE RING FOR QUOTE

New TV Trolley Stands

£4.95 Also Video Stands

POA

Colour TV panels & tubes available

All prices subject to V.A.T.

CALLERS WELCOME


Export Orders Welcome for those Countries using the P.A.L. System

**419 BARLOW MOOR ROAD,
 CHORLTON, MANCHESTER M21 2ER.**

TEL: 061-861 8501

SADELTA TV COLOUR PATTERN GENERATOR MODEL PAL MC 11B UK

THE SADELTA TV HAND HELD COLOUR PATTERN GENERATOR is intended for use in production, installation and service of both colour and monochrome TV sets. In order to control and adjust the various parameters of the colour TV, eight switchable patterns are provided. The technician has ready access to laboratory workshop and field use as the generator has been designed using the latest micro technology to achieve a truly pocket size instrument.

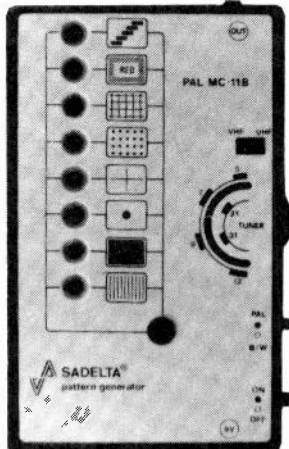

FEATURES

- PAL System I
- Eight switchable patterns:— colour bar, grey scale, red, crosshatch, dots, centre cross, centre dot, white and vertical lines.
- Sound output.
- Band IV (21-34)
- Band III (5-12)
- Output 10mV into 75 Ohms.
- Internal rechargeable Ni-Cd battery.
- Supplied with soft carry case and 9 volt power supply/charger.
- Pocket size 131 x 81 x 23mm.
- Weight only 250 gms.

PRICE £124.95 + £18.74 VAT

Also available to special order SECAM, Video Composite, and R.G.B. versions. Details available upon request.

U.K. POST PAID, export enquiries welcome. Visa/Access or cheque with order, payable to B.K. Electronics. Official orders welcome from Govt. Depts., Colleges, P.L.C.s etc. Large S.A.E. for technical leaflets of complete range delivery normally within 7 days.

B. K. ELECTRONICS Dept. 'T',
 UNIT 5, COMET WAY, SOUTHEND-ON-SEA,
 ESSEX. SS2 6TR TEL: 0702-527572

OSCILLOSCOPES

COSSOR CDU150. Dual Trace 35MHz Solid State. Portable 8x10cm display. With Manual £200
 TELEQUIPMENT D61 Dual Trace 10MHz With Manual £150
 ADVANCE OS250TV. Dual Trace 10MHz With Manual £160
 S.E. LABS SM111. Dual Trace 18MHz Solid State. Portable AC or External DC operation 8x10cm display. With Manual £150
 TELEQUIPMENT D43. Dual Trace 15MHz. With Manual £100
 TELEQUIPMENT SS4A. Single Trace 10MHz. Solid State. With Manual £110
 TELEQUIPMENT S43 Single Trace 25MHz With Manual £75

PHILIPS DIGITAL MULTIMETERS

4 digit, auto ranging. Complete with batteries and leads (p&p £5)
 TYPE PM2517X (LCD) £75

MULTIMETERS

AVO 9 Mk4 (Identical to AVO 8 Mk4 but scaled differently) Complete with Batteries & Leads. £55
 AVO 8 Mk2 Complete with Batteries & Leads £45
 Above Items in GOOD WORKING ORDER - appearance not A1 hence the price.
 AVO TEST SET No 1 (Military version of AVO 8) Complete with batteries, leads & Carrying Case £65
 AVO Model 7x. Complete with batteries, leads & carrying case £40
 AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads £18
 AVO 72 - Similar to above but no AC current range. With batteries & leads £10

AVO TRANSISTOR TESTER TT169

Handled. GO/NO GO for In-situ Testing. Complete with batteries, leads & instructions. (p&p £3) NOW ONLY £12

PROFESSIONAL 9" GREEN SCREEN MONITORS made by KGM for REUTERS Gives quality 80 column x 24 line display. Composite video in. Cased. Good condition ONLY £32 each
 DISK DRIVE PSU.240V 1N; SV 1.6A & 12V 1.5A out. Size: W125mm, H75mm, D180mm. Cased. Un-used. Only £10.00 each (P&P £2)
 Qwerty keyboard (as in Lynx Micro). Push to make. Cased £5 each (P&P £2)
 Various 5 1/4" Floppy Disk Drives and Stepping Motors Available.

LARGE COLOURMATCH PATTERN GENERATOR

Type CM6038-DB Crosshatch/Grey Scale/Blank Raster. Mains or Battery. ONLY £12 each (P&P £2)
 ADVANCE AM/FM SIGNAL GENERATOR Type SG63A 7.5-230MHz £75
 ADVANCE AM SIGNAL GENERATOR SG62B. 150 KHz-220MHz £45
 ADVANCE AM SIGNAL GENERATOR Type 62. 150KHz-220MHz £30
 METRIX WOBBLATOR Type 210. 5-220MHz £20
 PHILIPS WOBBLATOR 6M28775 5-220MHz & 440-880MHz £100
 LARGEAR COLOUR BAR GENERATOR CM6037 (P&P £4) £60
 VIDEO CIRCUITS V31A CRT ANALYSER/BOOSTER (Scratched Case) £50
 WAYNE KERR COMPONENT BRIDGE B521 (CT375) 100uH-500KHz; 1pF-5F; 1 milliohm-1000Mohm £35
 RACAL 32MHz UNIVERSAL COUNTER TIMER Type 836 with Manual £50
 MARCONI TF2604 (Later version of TF 1041 VTVM) 20Hz-1500MHz; AC/DC/Ohms AC 300mV-300V FSD £60
 MARCONI VALVE VOLTMETER TF2600 10Hz-10MHz; 1mV-300V FSD £40
 PHILIPS COLOURBAR GENERATOR type 5501 (P&P £5) £100
 PHILIPS COLOURBAR GENERATOR type 5508. Video out. Many Functions £125
 TES FIELD STRENGTH METER type HC661 in Carrying Case (P&P £5) £80

ISOLATING TRANSFORMER

240V In - 240V Out 500VA £15 each P&P £5
 240V In - 240V Out 200VA £8 each P&P £3

NEW EQUIPMENT

HAMEG OSCILLOSCOPE 605. Dual Trace 60MHz. Delay Sweep. Component Tester £515
 HAMEG OSCILLOSCOPE 203.5. Dual Trace 20MHz. Component Tester £270
 All Other Models Available.

BLACK STAR FREQUENCY COUNTERS P&P £9
 Meteor 100 - 100MHz £99
 Meteor 600 - 600MHz £126
 Meteor 1000 - 1GHz £175
 BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 £110

HUNG CHANG DMM 6010. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. P&P £4 £33.50

OSCILLOSCOPES PROBES. Switched x1; x10. P&P £2 £11

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £12. VAT to be added to Total of Goods & Carriage.

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL
 Telephone: 0734 68041



Callers welcome 9 am-5.30 pm Mon.-Fri. (until 8 pm Thurs.)



AA117	9p	BC337	6p	BF184	20p	BFY57	25p	TIP32A	24p	2N.1131	28p	BY296	20p	7818	35p	PCL805	55p	LA-4461	180p	TBA560	100p	74LS22	17p
AA119	9p	BC338	6p	BF185	20p	BFY64	25p	TIP32C	28p	2N.1132	28p	BY298	20p	7824	35p	PFL200	85p	LA-5112	120p	TBA750	100p	74LS24	38p
AA193	28p	BC339	6p	BF194	5p	BFY69	25p	TIP32D	50p	2N.1513	24p	BY299	20p	7835	35p	PL519	80p	LM301	20p	TBA800	35p	74LS26	38p
AC107	28p	BC340	6p	BF195	5p	BLY48	85p	TIP34	80p	2N.1111	24p	BY476	90p	7912	40p	PL82	45p	LM311	35p	TBA810S	60p	74LS27	17p
AC126	17p	BC341	6p	BF196	5p	BLY49	85p	TIP41A	22p	2N.2102	60p	BYX10	15p	7915	40p	PL83	32p	LM324	35p	TBA820	75p	74LS28	17p
AC127	15p	BC342	6p	BF197	7p	BR100	14p	TIP41C	25p	2N.2160	300p	BYX55/350	30p	7916	40p	PL84	50p	LM325	45p	TBA920	100p	74LS30	17p
AC128	15p	BC343	6p	BF198	7p	BR101	14p	TIP41E	22p	2N.2218A	24p	BYX55/300	30p	7917	40p	PL85	45p	LM326	45p	TBA930	100p	74LS31	17p
AC129	15p	BC344	6p	BF199	7p	BR103	17p	TIP42C	25p	2N.2219	24p	BYX70/300	32p	7918	40p	PL86	45p	LM327	45p	TBA940	100p	74LS32	17p
AC141K	30p	BC345	6p	BF200	15p	BSX20	15p	TIP47	40p	2N.2221	23p	BYX70/300	29p	7919	40p	PL87	45p	LM328	45p	TBA950	100p	74LS33	17p
AC142K	30p	BC346	6p	BF201	15p	BSX22	18p	TIP48	40p	2N.2222	23p	BYX70/500	32p	7919.5	40p	PL88	45p	LM329	45p	TBA960	100p	74LS34	17p
AC153K	15p	BC347	6p	BF202	15p	BSX24	18p	TIP49	40p	2N.2223	23p	BYX70/500	32p	7920	40p	PL89	45p	LM330	45p	TBA970	100p	74LS35	17p
AC176	18p	BC348	6p	BF203	15p	BSX26	18p	TIP51	120p	2N.2484	20p	BYX71/600	80p	7921	40p	PL90	45p	LM331	45p	TBA980	100p	74LS36	17p
AC176K	20p	BC349	6p	BF204	15p	BSX28	18p	TIP52	120p	2N.2646	40p	OA47	6p	7921.5	40p	PL91	45p	LM332	45p	TBA990	100p	74LS37	17p
AC187	15p	BC350	6p	BF205	15p	BSX29	18p	TIP53	120p	2N.2904	20p	OA90	6p	7912.4	40p	PL92	45p	LM333	45p	TBA995	100p	74LS38	17p
AC188	17p	BC351	6p	BF206	15p	BSX30	18p	TIP54	120p	2N.2906	20p	OA91	6p	7913.5	40p	PL93	45p	LM334	45p	TBA998	100p	74LS39	17p
AC188K	23p	BC352	6p	BF207	15p	BSX31	18p	TIP55	120p	2N.2908	20p	OA92	6p	7914	40p	PL94	45p	LM335	45p	TBA999	100p	74LS40	17p
AC189	17p	BC353	6p	BF208	15p	BSX32	18p	TIP56	120p	2N.2910	20p	OA93	6p	7915	40p	PL95	45p	LM336	45p	TBA999.5	100p	74LS41	17p
AC189K	23p	BC354	6p	BF209	15p	BSX33	18p	TIP57	120p	2N.2912	20p	OA94	6p	7916	40p	PL96	45p	LM337	45p	TBA999.5	100p	74LS42	17p
AC191	48p	BC355	6p	BF210	15p	BSX34	18p	TIP58	120p	2N.2914	20p	OA95	6p	7917	40p	PL97	45p	LM338	45p	TBA999.5	100p	74LS43	17p
AC192	48p	BC356	6p	BF211	15p	BSX35	18p	TIP59	120p	2N.2916	20p	OA96	6p	7918	40p	PL98	45p	LM339	45p	TBA999.5	100p	74LS44	17p
AD149	45p	BC357	6p	BF212	15p	BSX36	18p	TIP60	120p	2N.2918	20p	OA97	6p	7919	40p	PL99	45p	LM340	45p	TBA999.5	100p	74LS45	17p
AD162	22p	BC358	6p	BF213	15p	BSX37	18p	TIP61	120p	2N.2920	20p	OA98	6p	7920	40p	PL100	45p	LM341	45p	TBA999.5	100p	74LS46	17p
AF124	25p	BC359	6p	BF214	15p	BSX38	18p	TIP62	120p	2N.2922	20p	OA99	6p	7921	40p	PL101	45p	LM342	45p	TBA999.5	100p	74LS47	17p
AF125	25p	BC360	6p	BF215	15p	BSX39	18p	TIP63	120p	2N.2924	20p	OA100	6p	7922	40p	PL102	45p	LM343	45p	TBA999.5	100p	74LS48	17p
AF126	25p	BC361	6p	BF216	15p	BSX40	18p	TIP64	120p	2N.2926	20p	OA101	6p	7923	40p	PL103	45p	LM344	45p	TBA999.5	100p	74LS49	17p
AF127	25p	BC362	6p	BF217	15p	BSX41	18p	TIP65	120p	2N.2928	20p	OA102	6p	7924	40p	PL104	45p	LM345	45p	TBA999.5	100p	74LS50	17p
AF128	25p	BC363	6p	BF218	15p	BSX42	18p	TIP66	120p	2N.2930	20p	OA103	6p	7925	40p	PL105	45p	LM346	45p	TBA999.5	100p	74LS51	17p
AF129	25p	BC364	6p	BF219	15p	BSX43	18p	TIP67	120p	2N.2932	20p	OA104	6p	7926	40p	PL106	45p	LM347	45p	TBA999.5	100p	74LS52	17p
AF130	25p	BC365	6p	BF220	15p	BSX44	18p	TIP68	120p	2N.2934	20p	OA105	6p	7927	40p	PL107	45p	LM348	45p	TBA999.5	100p	74LS53	17p
AF131	25p	BC366	6p	BF221	15p	BSX45	18p	TIP69	120p	2N.2936	20p	OA106	6p	7928	40p	PL108	45p	LM349	45p	TBA999.5	100p	74LS54	17p
AF132	25p	BC367	6p	BF222	15p	BSX46	18p	TIP70	120p	2N.2938	20p	OA107	6p	7929	40p	PL109	45p	LM350	45p	TBA999.5	100p	74LS55	17p
AF133	25p	BC368	6p	BF223	15p	BSX47	18p	TIP71	120p	2N.2940	20p	OA108	6p	7930	40p	PL110	45p	LM351	45p	TBA999.5	100p	74LS56	17p
AF134	25p	BC369	6p	BF224	15p	BSX48	18p	TIP72	120p	2N.2942	20p	OA109	6p	7931	40p	PL111	45p	LM352	45p	TBA999.5	100p	74LS57	17p
AF135	25p	BC370	6p	BF225	15p	BSX49	18p	TIP73	120p	2N.2944	20p	OA110	6p	7932	40p	PL112	45p	LM353	45p	TBA999.5	100p	74LS58	17p
AF136	25p	BC371	6p	BF226	15p	BSX50	18p	TIP74	120p	2N.2946	20p	OA111	6p	7933	40p	PL113	45p	LM354	45p	TBA999.5	100p	74LS59	17p
AF137	25p	BC372	6p	BF227	15p	BSX51	18p	TIP75	120p	2N.2948	20p	OA112	6p	7934	40p	PL114	45p	LM355	45p	TBA999.5	100p	74LS60	17p
AF138	25p	BC373	6p	BF228	15p	BSX52	18p	TIP76	120p	2N.2950	20p	OA113	6p	7935	40p	PL115	45p	LM356	45p	TBA999.5	100p	74LS61	17p
AF139	25p	BC374	6p	BF229	15p	BSX53	18p	TIP77	120p	2N.2952	20p	OA114	6p	7936	40p	PL116	45p	LM357	45p	TBA999.5	100p	74LS62	17p
AF140	25p	BC375	6p	BF230	15p	BSX54	18p	TIP78	120p	2N.2954	20p	OA115	6p	7937	40p	PL117	45p	LM358	45p	TBA999.5	100p	74LS63	17p
AF141	25p	BC376	6p	BF231	15p	BSX55	18p	TIP79	120p	2N.2956	20p	OA116	6p	7938	40p	PL118	45p	LM359	45p	TBA999.5	100p	74LS64	17p
AF142	25p	BC377	6p	BF232	15p	BSX56	18p	TIP80	120p	2N.2958	20p	OA117	6p	7939	40p	PL119	45p	LM360	45p	TBA999.5	100p	74LS65	17p
AF143	25p	BC378	6p	BF233	15p	BSX57	18p	TIP81	120p	2N.2960	20p	OA118	6p	7940	40p	PL120	45p	LM361	45p	TBA999.5	100p	74LS66	17p
AF144	25p	BC379	6p	BF234	15p	BSX58	18p	TIP82	120p	2N.2962	20p	OA119	6p	7941	40p	PL121	45p	LM362	45p	TBA999.5	100p	74LS67	17p
AF145	25p	BC380	6p	BF235	15p	BSX59	18p	TIP83	120p	2N.2964	20p	OA120	6p	7942	40p	PL122	45p	LM363	45p	TBA999.5	100p	74LS68	17p
AF146	25p	BC381	6p	BF236	15p	BSX60	18p	TIP84	120p	2N.2966	20p	OA121	6p	7943	40p	PL123	45p	LM364	45p	TBA999.5	100p	74LS69	17p
AF147	25p	BC382	6p	BF237	15p	BSX61	18p	TIP85	120p	2N.2968	20p	OA122	6p	7944	40p	PL124	45p	LM365	45p	TBA999.5	100p	74LS70	17p
AF148	25p	BC383	6p	BF238	15p	BSX62	18p	TIP86	120p	2N.2970	20p	OA123	6p	7945	40p	PL125	45p	LM366	45p	TBA999.5	100p	74LS71	17p
AF149	25p	BC384	6p	BF239	15p	BSX63	18p	TIP87	120p	2N.2972	20p	OA124	6p	7946	40p	PL126	45p	LM367	45p	TBA999.5	100p	74LS72	17p
AF150	25p	BC385	6p	BF240	15p	BSX64	18p	TIP88	120p	2N.2974	20p	OA125	6p	7947	40p	PL127	45p	LM368	45p	TBA999.5	100p	74LS73	17p
AF151	25p	BC386	6p	BF241	15p	BSX65	18p	TIP89	120p	2N.2976	20p	OA126	6p	7948	40p	PL128	45p	LM369	45p	TBA999.5	100p	74LS74	17p
AF152	25p	BC387	6p	BF242	15p	BSX66	18p	TIP90	120p	2N.2978	20p	OA127	6p	7949	40p	PL129	45p	LM370	45p	TBA999.5	100p	74LS75	17p
AF153	25p	BC388	6p	BF243	15p	BSX67	18p	TIP91	120p	2N.2980	20p	OA128	6p	7950	40p	PL130	45p	LM371	45p	TBA999.5	100p	74LS76	17p
AF154	25p	BC389	6p	BF244	15p	BSX68	18p	TIP92	120p	2N.2982	20p	OA129	6p	7951	40p	PL131	45p	LM372	45p	TBA999.5	100p	74LS77	17p
AF155	25p	BC390	6p	BF245	15p	BSX69	18p	TIP93	120p	2N.2984	20p	OA130	6p	7952	40p	PL132	45p	LM373	45p	TBA999.5	100p	74LS78	17p
AF156	25p	BC391	6p	BF246	15p	BSX70	18p	TIP94	120p	2N.2986	20p	OA131	6p	7953	40p	PL133	45p	LM374	45p	TBA999.5	100p	74LS79	17p
AF157	25p	BC392	6p	BF247	15p	BSX71	18p	TIP95	120p	2N.2988	20p	OA132	6p	7954	40p	PL134	45p	LM375	45p	TBA999.5	100p	74LS80	17p
AF158	25p	BC393	6p	BF248	15p	BSX72	18p	TIP96	120p	2N.2990	20p	OA133	6p	7955	40p	PL135	45p	LM376	45p	TBA999.5	100p	74LS81	17p</

**BRITAIN'S
LARGEST SUPPLIERS**

OF

**Ex RENTAL
TV & VIDEOS**

OVER 1500 ARRIVING WEEKLY

*Makes inc. PHILIPS, GEC,
HITACHI, ITT, BUSH,
PANASONIC, SONY, DECCA,
FERGUSON, GRUNDIG etc.*

COLOUR TV from £5
VIDEO RECORDERS from £40

**CALL & SEE OUR SELECTION
DELIVERY ARRANGED FOR
BULK PURCHASES
LOAD DIRECT FROM SOURCE
AT VERY KEEN PRICES**

FRANK FORD
(TV TRADE DISPOSALS)
SCHOOL LANE
GUIDE
BLACKBURN, LANCs
TEL: 0254 64489

WD-TV

THE T.V. WAREHOUSE,
WATLING STREET (A5)
HOCKLIFFE, LEIGHTON BUZZARD,
BEDFORDSHIRE
(M1 Jnct. 12 - 3 miles)
TEL: 0525 210686

100's of CLEAN WORKING COLOUR TVs

HYBRID FROM £10 WORKING
PHILIPS G11 £50
G11 TELETEXT £100 WITH HANDSETS
9000 £35
9000 REMOTE £40 WITH HANDSET
SOLID STATE 18" £30
COLOUR PORTABLES FROM £50

VHS VIDEOS

ALL WORKING AND CLEAN

FERGUSON FROM £85
HITACHI + NATIONAL PANASONIC
FROM £150
DUAL SPEED INFRA-RED REMOTE,
DOLBY STEREO £200
VARIOUS BETAMAX FROM £50
★ SPARES ★ LEADS ★ PANELS ★
★ REMOTE UNITS ★ TUBES ★
★ USED VALVES ★
ALL AT LOW LOW PRICES
CALL OR PHONE ★ TNT DELIVERY AVAILABLE
POSTAL DESPATCH ★ ACCESS OR VISA
OPEN MONDAY-SATURDAY 9am-5.30pm

HOCKLEY DISCOUNT TELEVISIONS

We give "The Best Deals"
that's why we have the
cleanest reputation in the
trade!!!

Prices start Working sets
From **£6.00** From **£12.00**

OR

Lorry loads delivered
from SOURCE

We have huge stocks of
TV's + V.H.S. Videos
to offer, including:-

Philips G8's, G11's Thorn 8000, TX9,
Pye Solid State 9000, 9600, TX10,
Pye Chelsea Latest Hitachi
G.E.C. Solid State I.T.T. CVC30, CVC45,
Rediffusion Mkl, MkIII Bush T20, T22

ALSO

VIDEO + T.V. STANDS AVAILABLE!

**DON'T HESITATE TO CONTACT US
BECAUSE YOU WILL NEVER LOOSE!!**

MIDLANDS BRANCH:-
Hockley Discount Televisions,
94 Soho Hill, Hockley, Birmingham B19 1AE.
021-551-2233 - Ask for Jazz



NORTH-EAST BRANCH:-
Northern TV Distributors, Unit 2, Pert Court,
11th Ave, Team Valley,
Gateshead, Tyne & Wear.
091-487-5389 - Ask for Joe



BOLTEN LTD.

45/46 London House,
271, King Street, London W6 9LZ.
Tel: 01-748 4137 (2 lines)
Telex: 262421 BOLTEN G

Video Heads

Sony C5/C7/T7	£31.95
Ferguson/JVC (Universal)	£30.95
National Panasonic (Universal)	£30.95
National Panasonic (370/380)	£33.95
Hitachi	£33.95
Sanyo	£44.95
Fisher VHS Genuine	£51.95
Akai (most Models)	£30.95
Sharp	£44.95

Heads suitable for many other Brands also available.
Please call for full list.

Belt Kits (Most Models)	£3.99
Remote Controls for T.V.	
Grundig/Philips	£16.95
Video Cable Kit (any model to any model)	£7.50
Pinch Wheels (Various Models)	£5.95

Please add 15% VAT plus £1.00 p&p per order.

Delivery within 7-14 days
subject to availability



CRICKLEWOOD ELECTRONICS LTD



It's no secret...

that there is a *real difference* at *Cricklewood Electronics*.
That's why you should never be without the *FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE* for sheer variety, *competitive prices* and *service* from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your *FREE* copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LIMITED

40 Cricklewood Broadway, London NW2 3ET

Tel: 01-450 0995/01-452 0161
Telex: 91 4977



TV

UPDATING COURSES

HIGH PERCENTAGE OF PRACTICAL WORK INTENDED FOR QUALIFIED SERVICE ENGINEERS.

VCR SERVICING

(3 WEEKS FULL TIME)

NEXT COURSE STARTS ON OCTOBER 6th - TUITION FEE £575

MICROCOMPUTER SERVICING

(ONE WEEK FULL TIME)

NEXT COURSE STARTS ON OCT. 27th - TUITION FEE £230

(MSC grants available on JTS/ATS training schemes, subject to approval. If you are unemployed, or are currently employed and require retraining, or updating, you or your employer may be eligible for financial assistance under one of the above schemes.)

Further details from:

LONDON ELECTRONICS COLLEGE (VC Dept.)

20 Penywern Road, Earls Court, London SW5 9SU

Tel: 01-373 8721

AN1270	£1.75	CX136	£5.50	HA11768	£4.50	M51521AL	£1.75	TA7130P	£1.00	UPC1028H	£0.90	2SA899	£0.75	2SC1505	£0.70
AN203	£2.20	CX143A	£7.50	HA11788	£4.50	M54543L	£2.75	TA7136P	£1.00	UPC1031H	£1.00	2SA940	£0.80	2SC1546	£0.30
AN210	£1.75	CX157	£3.95	HA11816NT	£6.50	M54548L	£6.75	TA7137P	£1.00	UPC1032H	£1.50	2SA952	£0.35	2SC1664	£2.50
AN211A	£2.25	CX158	£3.50	HA11828NT	£3.50	MB3705	£1.60	TA7138P	£1.50	UPC1035C	£1.20	2SA1015	£0.30	2SC1682	£0.30
AN214Q	£1.80	CX160	£2.50	HA12035	£3.50	MB3712	£1.50	TA7145P	£1.80	UPC1037H	£0.75	2SA1102	£1.90	2SC1741	£0.30
AN217B	£2.20	CX161A	£2.50	HA12413	£2.50	MB3712	£1.50	TA7150P	£1.80	UPC1043C	£1.20	2SA1103	£1.90	2SC1815	£0.25
AN228W	£2.75	CX162	£3.40	HA13402	£3.50	MB3730	£2.50	TA7166P	£1.56	UPC1158H	£0.60	2SA1104	£1.90	2SC1826	£0.60
AN236	£2.50	CX170	£6.50	HA13403	£3.50	MB3731	£2.60	TA7193P	£3.50	UPC1161C	£0.75	2SA1105	£2.25	2SC1849	£0.30
AN239Q	£3.80	CX181	£8.50	HA13430A	£3.50	MB8719	£3.50	TA7200	£2.00	UPC1163H	£0.60	2SA1106	£2.50	2SC1945	£3.50
AN240P	£1.50	HA1124A	£2.75	LA1111P	£3.95	PLLO1A	£2.30	TA7201	£2.00	UPC1167C	£0.70	2SA1198	£0.35	2SC1946A	£3.50
AN241P	£1.50	HA1125	£1.50	LA1222	£0.80	FLLO3A	£4.95	TA7202P	£2.00	UPC1168C	£0.90	2SB22	£0.40	2SC1957	£0.80
AN247P	£2.50	HA1137	£1.75	LA1230	£1.50	SI-1125H	£7.50	TA7203P	£1.80	UPC1170H	£1.50	2SB54	£0.70	2SC1969	£1.30
AN259	£2.75	HA1149	£1.40	LA1240	£1.75	STK011	£3.75	TA7204P	£1.10	UPC1171C	£1.20	2SB75	£0.60	2SC2021	£1.30
AN262	£1.50	HA1151	£2.50	LA1320	£1.50	STK013	£6.25	TA7205AP	£1.60	UPC1179C	£1.50	2SB341V	£2.60	2SC2026	£0.65
AN271A	£2.50	HA1156	£1.10	LA1365	£1.20	STK014	£6.25	TA7207P	£1.50	UPC1177H	£1.20	2SB405	£0.80	2SC2028	£0.75
AN274	£2.50	HA1166	£1.60	LA1368	£2.20	STK015	£3.00	TA7208P	£1.50	UPC1178C	£1.00	2SB426	£2.60	2SC2075	£0.25
AN295	£3.25	HA1196	£3.75	LA1460	£1.95	STK016	£4.75	TA7209P	£2.00	UPC1180C	£1.40	2SB471	£0.50	2SC2078	£0.75
AN303	£2.50	HA1196	£3.75	LA2200	£1.75	STK019	£7.50	TA7210P	£1.50	UPC1181H	£1.00	2SB492	£0.75	2SC2091	£0.60
AN313U	£2.75	HA1197	£1.50	LA3101	£0.95	STK020	£4.50	TA7211P	£2.50	UPC1182H	£1.00	2SB5090	£1.70	2SC2092	£0.95
AN315	£2.00	HA1199	£1.40	LA3155	£0.95	STK022	£3.25	TA7215P	£2.80	UPC1183H	£1.20	2SB534	£0.60	2SC2098	£0.95
AN316	£3.50	HA1306W	£1.60	LA3160	£0.90	STK025	£6.75	TA7217AP	£1.20	UPC1185H	£2.20	2SB536	£0.60	2SC2166	£0.95
AN318	£4.75	HA1319	£2.00	LA3201	£0.95	STK041	£6.50	TA7220P	£1.75	UPC1186	£0.80	2SB546	£1.50	2SC2238	£0.65
AN331	£2.75	HA1339A	£1.60	LA3300	£1.40	STK077	£3.95	TA7222AP	£1.25	UPC1187V	£1.30	2SB561	£1.50	2SC2375	£0.70
AN360	£1.20	HA1366W	£1.50	LA3301	£1.20	STK078	£3.50	TA7223P	£1.95	UPC1190C	£0.95	2SB568	£0.30	2SC2385	£1.50
AN362L	£1.30	HA1366WR	£1.50	LA3350	£1.20	STK080	£7.20	TA7224P	£1.25	UPC1191V	£0.75	2SB755	£2.50	2SC2386	£4.25
AN366P	£1.50	HA1367	£3.25	LA3361	£1.20	STK082	£7.75	TA7225P	£2.50	UPC1198H	£0.70	2SB755	£2.50	2SC2386	£4.25
AN370P	£1.75	HA1368	£1.60	LA4030P	£2.00	STK086	£3.25	TA7226P	£2.20	UPC1200V	£1.00	2SB772Q	£0.90	2SC2570	£1.90
AN374	£4.75	HA1368R	£1.65	LA4031P	£1.40	STK430	£4.75	TA7227P	£1.50	UPC1208C	£0.80	2SC717	£0.30	2SC2577	£2.20
AN5722	£1.50	HA1370	£2.75	LA4032P	£1.40	STK433	£4.50	TA7229P	£1.30	UPC1211V	£1.25	2SC720	£0.90	2SC2578	£2.20
AN5730	£1.85	HA1374	£2.50	LA4051P	£1.40	STK435	£5.00	TA7230P	£1.75	UPC1215V	£1.95	2SC737	£0.30	2SC2579	£2.20
AN5732	£1.85	HA1377A	£2.20	LA4100	£1.00	STK436	£5.00	TA7232P	£2.75	UPC1216V	£1.60	2SC737	£0.30	2SC2580	£2.20
AN5753	£1.95	HA1388	£2.35	LA4101	£1.00	STK437	£6.30	TA7310P	£1.40	UPC1217G	£1.90	2SC748	£0.30	2SC2582	£2.20
AN5750	£2.30	HA1389	£1.75	LA4102	£1.20	STK439	£3.50	TA7312P	£1.30	UPC1218H	£1.40	2SC748	£0.30	2SC2582	£2.20
AN5344	£4.75	HA1389R	£1.40	LA4110	£1.10	STK441	£6.00	TA7313AP	£1.75	UPC1222C	£0.90	2SC748	£0.30	2SC2582	£2.20
AN7105	£2.20	HA1392	£2.30	LA4112	£1.30	STK443	£6.95	TA7315AP	£1.30	UPC1223C	£1.75	2SC748	£0.30	2SC2582	£2.20
AN7110	£1.40	HA1394	£2.75	LA4120	£2.50	STK467	£5.50	TA7325P	£0.85	UPC1225H	£1.60	2SC748	£0.30	2SC2582	£2.20
AN7114E	£1.60	HA1397	£2.50	LA4125	£2.00	STK469	£5.75	TA7328P	£1.80	UPC1226C	£1.25	2SC748	£0.30	2SC2582	£2.20
AN7115E	£1.60	HA1398	£2.40	LA4140	£2.70	STK460	£7.50	TA7607AP	£2.75	UPC1227V	£0.95	2SC748	£0.30	2SC2582	£2.20
AN7120	£1.40	HA1457W	£0.90	LA4182	£2.00	STK461	£6.50	TA7608P	£2.50	UPC1230H	£2.50	2SC748	£0.30	2SC2582	£2.20
AN7130	£1.50	HA1215A	£4.25	LA4192	£1.95	STK463	£7.40	TA7609P	£2.30	UPC1238V	£0.85	2SC748	£0.30	2SC2582	£2.20
AN7145M	£1.80	HA1221	£2.30	LA4200	£1.50	STK465	£8.50	TA7611	£1.75	UPC1245V	£1.50	2SC748	£0.30	2SC2582	£2.20
AN7145M	£1.85	HA1223W	£3.80	LA4220	£1.20	STK0025	£4.95	TA7658P	£2.75	UPC1277H	£2.00	2SC748	£0.30	2SC2582	£2.20
AN7154	£1.75	HA1225	£1.95	LA4230	£1.75	STK0029	£4.25	UH0001	£4.80	UPC1278H	£2.50	2SC748	£0.30	2SC2582	£2.20
AN7156N	£2.40	HA1235	£2.00	LA4400	£1.90	STK0039	£4.35	UH0004	£4.80	UPC1350C	£1.20	2SC717	£0.30	2SC2582	£2.20
AN7158N	£3.25	HA1423	£4.75	LA4420	£1.40	STK0040	£3.50	UPC16C	£1.30	UPC1353C	£1.75	2SC717	£0.30	2SC2582	£2.20
AN7158	£2.25	HA1170	£4.50	LA4422	£1.20	STK0049	£3.75	UPC20C	£2.20	UPC1356C	£1.50	2SC732	£0.30	2SC2582	£2.20
AN7310	£2.25	HA11702	£4.90	LA4430	£1.30	STK0059	£6.00	UPC30C	£1.80	UPC1358H	£1.60	2SC733	£0.30	2SC2582	£2.20
AN7311	£1.00	HA11703	£4.50	LA4440	£2.20	STK0080	£6.50	UPC41C	£2.20	UPC1360C	£1.60	2SC792	£2.85	2SC2582	£2.20
BA301	£0.75	HA11704	£4.75	LA4460	£1.75	STK2028	£6.50	UPC55C	£1.25	UPC1363C	£1.95	2SC799	£1.75	2SC2582	£2.20
BA311	£0.95	HA11705	£6.50	LA4461	£1.75	STK2029	£3.75	UPC55S	£0.60	UPC1365C	£3.00	2SC828	£0.20	2SC2582	£2.20
BA313	£1.75	HA11706	£4.75	LA4500	£2.50	STK2230	£6.00	UPC561C	£2.00	UPC1366C	£1.50	2SC848	£1.50	2SC2582	£2.20
BA318	£1.75	HA11710	£4.50	LA4505	£2.50	STK2240	£3.75	UPC566H	£0.60	UPC1367C	£2.00	2SC867	£0.25	2SC2582	£2.20
BA402	£0.75	HA11711	£3.50	LA6588	£0.90	STK3042	£6.50	UPC571	£1.95	UPC1368H	£1.75	2SC900	£0.35	2SC2582	£2.20
BA511A	£1.80	HA11713	£6.00	LA7800	£1.95	STK5211	£6.75	UPC573C	£2.20	UPC1370C	£1.95	2SC9290	£0.35	2SC2582	£2.20
BA514	£1.75	HA11714	£5.75	LA7806	£2.50	STK5421	£6.50	UPC574J	£0.35	UPC1373H	£1.95	2SC930	£0.30	2SC2582	£2.20
BA521	£1.75	HA11715	£6.25	LA7810	£3.50	STK5451	£6.75	UPC575J	£1.00	UPC1378H	£1.75	2SC945	£0.35	2SC2582	£2.20
BA527	£1.50	HA11716	£6.25	LA7813	£3.50	STK720	£6.00	UPC578H	£1.30	UPC1382C	£0.75	2SC1034	£0.75	2SC2582	£2.20
BA532	£1.50	HA11717	£6.25	LA7816	£3.75	STK730	£6.00	UPC577	£0.75	UPC1384C	£2.50	2SC1061	£0.95	2SC2582	£2.20
BA536	£2.25	HA11718	£4.75	LA7816	£3.75	STK730	£6.00	UPC580	£2.70	UPC1458C	£0.90	2SC1096	£0.60	2SC2582	£2.20
BA612	£1.80	HA11724	£18.25	LA7817	£2.75	TA7051P	£0.80	UPC585C	£0.95	UPC277	£4.50	2SC1114	£3.50	2SC2582	£2.20
BA1310	£1.75	HA11725	£16.00	M5106P	£2.25	TA7054	£1.70	UPC592	£0.95	2SA103	£0.60	2SC1115	£3.75	2SC2582	£2.20
BA1320	£1.25	HA11726	£15.00	M5115P	£3.50	TA7063	£0.80	UPC595C	£1.70	2SA330	£0.60	2SC1162C	£0.80	2SC2582	£2.20
BA1330	£1.75	HA11727	£9.50	M5134P	£2.75	TA7066	£1.50	UPC596	£0.50	2SA495	£0.35	2SC1170B	£0.75	2SC2582	£2.20
BA5304	£2.20	HA11736	£16.00	M5135P	£3.50	TA7070P	£1.40	UPC1001H	£1.75	2SA539	£0.30	2SC1172	£2.75	2SC2582	£2.20
CX0642	£3.50	HA11745	£9.00	M5155	£1.50	TA7073	£2.25	UPC1009C	£1.20	2SA562	£0.30	2SC1317	£2.95	2SC2582	£2.20
CX0658	£2.50	HA11747	£9.50	M51513L	£1.50	TA7074P	£1.95	UPC1017G	£1.30	2SA634	£0.60	2SC1316	£2.95	2SC2582	£2.20
CX0758	£2.20	HA11747ANT	£9.50	M51514AL	£1.75	TA7104P	£1.35	UPC1018C	£0.95	2SA643	£0.65	2SC1342	£0.75	2SC2582	£2.20
CX095C	£2.80	HA11749	£4.50	M51515BL	£2.50	TA7106	£1.75	UPC1020	£1.75	2SA673					

SIGHT & SOUND

185 UTTOXETER ROAD, LONGTON, STOKE-ON-TRENT

STOKE-ON-TRENT 0782 335262

PHILIPS G8	£5	ITT	£18	GEC	£12	NAT./PAN. 333	£150
THORN 9000	£12	G11's	£20	COLOUR PORTABLES	£45	KT3	£50
THORN 9600	£20	G11 TEXT	£45	BLACK/WHITE	£3	TX9	£60
THORN 8+8	£11	PYE 222	£8	NAT./PAN. VIDEO's 2010	£135	TX10	£70
HITACHI's	£15	BUSH	£4	NAT./PAN. VIDEO's 366	£140	GRUNDIG	£30
DECCA 100's	£15	BUSH T20	£20	NAT./PAN. 7200	£145	NAT./PAN.	£40

SATISFACTION GUARANTEED

FRIENDLY SERVICE - NO GIMMICKS

PERSONAL ATTENTION - ASK FOR JOHN SAHOTA

D.I.Y. TV TUBE POLISHING

with our DIY Polishing Kit

The Kit includes everything you need to polish approx. 25* tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

Kit Price £49 inc P&P and VAT. Available from Luton only.

*Depends on depth and area to be polished.

TV TUBES FREE DELIVERY*

5% DISCOUNT ON TUBES COLLECTED FROM LUTON

Quality, High Temperature Reprocessing

TUBE SIZE	DELTA i.e. A51-110X A56-120X A66-120X A67-120X	DELTA SPECIALS i.e. A47-342X 470CTB22 510GLB22 A56-410X A66-410X A67-150X A67-200X	IN LINE & P.M. i.e. 470ESB22 470ERB22 A51-161X A51-570X 510QKB22 560AKB22 A56-510X A66-510X	HITACHI IN LINE etc. AXT37-001 AXT51-001 AXT56-001 510VAB22 510VLB22 510VSB22 A51-421X A51-426X A51-580X A51-590X A51-610X A51-701X	HITACHI IN LINE etc. A56-540X A56-615X A56-711X 560BYB22 560DZB22 560EGB22 560FGB22 560GAB22 A66-540X A67-711X	SONY TRINITRON 330AB22 400EFB22 470BEF22 470DLB22 470FWB22 520KB22 520NB22 520SB22 570EB22 570HB22 680DB22 680EB22
UP TO 20"	£30	£32	£40	£44	£44	£58
UP TO 22"	£34	£36	£42	£46	£46	£64
UP TO 26"	£36	£38	£44	£48	£48	£70

Tube types not listed, please enquire.

All tubes sold with 1 or 2 year guarantee, with optional extension by extra 2 years. Prices shown are for 12 months guarantee. All tubes exchange glass required.

Your good, working tubes with scratches or small chips, can be POLISHED with our purpose built polishing equipment. From £7 per tube.

Delivery charge on colour tubes: Within 40 miles of Luton.

1 or 2 tubes £6. 3 or more tubes FREE DELIVERY*

Nationwide delivery available, charges on application.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

WELL VIEW

114-134 Midland Rd,
Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-1pm. Tel. 0582-410787.

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

H. K. Television, London, E.2. Tel. 01-729 1133.

West One Distributors Ltd., Gt. Missenden, Buckinghamshire.

Tel. 024 06 3609

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933 314901

Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562.

Phone between 12-2p.m., & 6-9 p.m.

WANTED A56/A66-510X/540X, Hitachi and Sony, old glass for cash

TVS TRADE SERVICES BROMSGROVE

Large selection of quality clean TV & Video always in stock, including:

BUSH T20/24 DECCA 80/100

GEC STARLINE

HITACHI ITT (full remote)

PHILIPS G8

PHILIPS GII PHILIPS KT3

THORN 9600 including TELETEXT

THORN 8800 THORN 9000

(remote) (remote)

THORN TX

VHS VIDEO from £85 (working)

We specialise in working sets, fully serviced and ready to deliver to your customer's home. Spares back up service available to customers. You've seen the junk, so why not now come and pay us a visit - we think you will be pleasantly surprised by our prices and the quality of our equipment. Delivery service available.

STOP PRESS

Electronic Video including Ferguson 3V29/30, Amstrad 7000, Sharp 9300, now in stock at unbeatable prices. We also specialise in direct loads delivered to your door direct from source.

For further details phone:

COLIN BROOMFIELD,

UNIT 7, STATION STREET,

BROMSGROVE, WORCS.

(0527) 37037/71186



APOLLO LANCASHIRE

MAIL ORDER GB 3-4 DAYS PHONE FOR COST SONY TYPES

LOCAL DELIVERY - 2 YR GUARANTEE - PILL GLASS BOUGHT

PORTABLES. 37-590, AXT 37001, 370HUB, NEW £65 INC. DELIVERY

A47 342/343X - 470 BCB22/CTB22/BGB22/DHB22

470-ESB22/EFB22/ERB22/FTB22

A51-220X/192X

A51-161X/162/163/168

510-JKB22/JEB22/JDB22/ALB22/GLB22

510-VLB22(E55) DTB22/001/RFB22/RCB22/SFB22

A51-590 New

A51-570X/580/001/210/241

A56-120X/123/140/410

560-DZB22(E56)/HB22/AKB22/TB22/AWB22

560-ETB22/DTB22/CSB22/DMB22/DNB22

A56-611X/615X

A66-120X/A67-120X/140/150/200/410

20AX - A56-500X/510X - A66-500X/510X

30AX - A56-540X - A66-540X

PLEASE PHONE BEFORE CALLING
LOCAL DELIVERY FROM ACCRINGTON, LANCs.

Phone enquiries and letters to:

**Apollo, The Potters Wheel,
Mullion Cove, Mullion, Nr. Helston, TR12 7ET.
0326 240781**

LONDON'S LARGEST
TELEVISION WHOLESALE...
with over 4½ thousand sq. feet

"TELEMANN"



8-10 RHODA STREET (off Bethnal Green Road)
LONDON E2. FREE CAR PARK

SPECIAL OFFER!!

- Parcel of 25 Monos £1.00 each
- Parcel of 10 Philips 22" G8 550 £15.00 each
- Parcel of 10 Decca Bradfords (6 buttons) £12.00 each
- Parcel of 10 Japs Colour £20.00 each

LORRY LOADS DELIVERED DIRECT FROM SUPPLIERS
NO CHARGE FOR DELIVERY IN THE LONDON AREA!

01-739 2707 → 2 LINES ← 01-739 3123

FREE CAR PARK + NO YELLOW LINES OUTSIDE!

SUMMER SAVERS!

LONDON WAREHOUSE ONLY

5000 VCR'S MUST GO!

**VCR MECHANICALS
IN 25 LOTS**

THORN 8.8 AND 26" AND 9.6
PHONE FOR OUR SPECIAL PRICES

£60

EACH

ALL COMPLETE — MANY WORKING

VISIT THE LARGEST EX RENTAL WAREHOUSE
IN THE UK!! 10,000 sq ft of VCR'S & CTV'S AT
UNREPEATABLE SUMMER PRICES

OPEN 6 DAYS WEEKLY AND SUNDAY BY APPOINTMENT AT

ALL WAREHOUSES

SLIGHTLY SUBSTANDARD **VCR'S**

(Some Trims and Flaps Missing etc)

IN LOTS OF 25

£40
EACH

BRADFORD
TRITEL TV
1043 Leeds
Road
Thornbury
Roundabout
BRADFORD

LEEDS
TRITEL
DISCOUNT
STORES
Long Row
Horsforth
LEEDS

SCOTLAND
TRITEL TV
Unit 4
Peacock Cross
Industrial Estate
Burnbank Road
HAMILTON

Tel: 0274 665670 Tel: 0532 590252 Tel: 0698 282141

**UNIT E1,
WATERLOO
ROAD,
STAPLES CORNER,
LONDON NW2**

**Tel: 01 208 2063
OR 01 208 2042**



Kent Ledgerwood Wholesale Ltd.

CREWE WHOLESale TV

77 COLERIDGE WAY, CREWE

Tel: 0270 582924

G11s working **£50**

GEC from **£11**

Delivered in Bulk

BUSH T20 T22 and 24s

ITT CVC 20 Upwards

Series 3 DORIC

working from **£40**

Remote + Text Available

Large range of

THORN from 8800 upwards.

Price and availability on request

**CASH ONLY UNLESS BY
PRIOR ARRANGEMENT**

ALL PRICES + 15% VAT

★★ CHANGE OF ADDRESS ★★

ALL ORDERS SHOULD NOW BE SENT TO OUR NEW ADDRESS SHOWN BELOW

TOP 50 VIDEO SPARES

CASSETTE LAMP (FERG/JVC)	£1.80	PINCH ROLLER (SANYO)	£7.95
CASSETTE LAMP (PANASONIC)	£1.80	PINCH ROLLER (SONY C5/C7)	£5.95
CASSETTE LAMP (SHARP, 9300 ETC)	£2.15	VIDEO HEAD DRUM (FERG)	£37.50
BELT KIT SONY (STATE MODEL)	£6.50	VIDEO HEAD DRUM (PANASONIC)	£39.50
BELT KIT FERGUSON (STATE MODEL)	£6.50	VIDEO HEAD DRUM (PAN NV366)	£56.95
BELT KIT SHARP (STATE MODEL)	£6.50	VIDEO HEAD DRUM (HITACHI)	£39.95
BELT KIT PANASONIC (STATE MODEL)	£6.50	VIDEO HEAD DISC (SONY C5/C6/C7)	£39.50
BELT KIT SANYO (9300, 5300, 5400)	£6.50	VIDEO HEAD DISC (SONY SL8000)	£44.50
BELT KIT SONY (5000)	£1.99	VIDEO HEAD DISC (SANYO)	£49.90
BELT KIT HITACHI (STATE MODEL)	£6.50	VIDEO HEAD (SHARP 7300, 7700)	£51.58
REWIND KIT SONY C5/C7	£6.95	VIDEO HEAD (SHARP 9300, 381 ETC)	£49.90
REWIND KIT SONY C6	£6.95	VIDEO HEAD (TOSHIBA 9600)	£49.95
REEL IDLER (SHARP, 9300, 381, ETC)	£3.90	VIDEO HEAD (TOSHIBA 8600)	£54.60
FF/REW IDLER (HITACHI VT-11, ETC)	£6.50	REEL DRIVE PULLEY (SANYO 5000)	£8.88
FF/REW IDLER (HITACHI VT8000)	£4.72	REEL MOTOR (SANYO 5000 ETC)	£14.20
FF/REW IDLER (HITACHI VT9300)	£4.75	REEL MOTOR (SHARP 9300, 381, ETC)	£15.30
REEL IDLER (FERG, 3V29/30)	£3.45	CAPSTAN MOTOR (SONY C5/C7)	£39.85
PLAY IDLER (HITACHI 9300)	£6.50	A.C.E. HEAD (SONY C5/C7)	£26.45
FF/REW IDLER (NAT/PAN NV370)	£4.50	CAPSTAN MOTOR FERG/JVC 3V22 ETC	£36.45
REEL IDLER (NAT/PAN) STATE MODEL	£3.45	DRUM MOTOR FERG/JVC 3V22 ETC)	£36.60
PLAY IDLER (NAT/PAN) STATE MODEL	£4.72	TAKE-UP CLUTCH (FERG/JVC)	£6.95
PLAY CLUTCH (PAN NV7000)	£5.50	CLUTCH ASSY (FERG 3V29/30)	£4.50
PINCH ROLLER (FERG)	£5.95	AUDIO RELAY (SONY C5/C7)	£3.95
PINCH ROLLER (SHARP)	£7.90	HEAD CLEAMING STICKS	£0.50
PINCH ROLLER (PANASONIC)	£5.95	HEAD CLEAMING FLUID	£1.50

MOST SPARES AVAILABLE FOR HITACHI, PANASONIC, SONY, SANYO, SHARP ETC.
RING FOR AVAILABILITY.

TELEVIDEO SERVICES

NOTTINGHAM (0602) 226070

145 STATION RD, BEESTON, NOTTINGHAM.

Please add 50p post & packing and then add 15% VAT to the total.

ALL STOCK ITEMS ARE DESPATCHED BY RETURN OF POST

Send 17p stamp for full list

SETS & COMPONENTS

NEW AND SECONDHAND COLOUR TV SPARES. Panels & Tubes most makes also panel repair service. Tel. Southport (0704) 7411 anytime (24hr).

CASH PAID Now for your surplus TV spares, transistors, I.C.'s etc. Tel. MR. FORSHAW, (0902) 29022.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

HITACHI, MITSUBISHI, Panasonic, Sony, Toshiba, JVC, Sharp, fully refurbished. PEARSON TELEVISION 0484 863489. Delivery arranged.

PHILIPS G11 AND BUSH T20 regular supplies. For prices phone 01-845 2036.

GENUINE GRUNDIG SPARES. Fast helpful service. Sensible prices. TELEQUIPMENT PHILIPS Oscilloscopes. Test equipment, manuals. OCHRE MILL TECHNICAL. Stone 0785 814643.

REDIFFUSION SPARES AND PANELS for Mk3 and Mk4 etc, mostly new and refurbished. Approx. 25 large cartons. £1,500. TELESCENE, Nottingham 0602 291665.

WIZARD DISTRIBUTORS MANCHESTER TV & VIDEO SPARES

We stock spares for THORN, PHILIPS, PYE, RANK, GEC, SHARP, SONY, DECCA + ITT.

FIDELITY SPARES MAIN DISTRIBUTOR.

Did you know we also stock

FUSES	I.Cs
TUBES	TOOLS
AERIALS	VIDEO LEADS
AEROSOLS	AUDIO LEADS
RESISTORS	SEMICONDUCTORS
CAPACITORS	SERVICE MANUALS
VALVES	TEST EQUIPMENT
HANDSETS	TV/VIDEO TROLLEYS

AND MUCH MORE

Counter open Monday-Friday 9am-4.45pm

TRADE ONLY

EMPRESS STREET WORKS,
EMPRESS STREET,
MANCHESTER M16 9EN.

Tel: 061-872 5438; 061-848 0060.

PRECISION VISION LTD.

For:

- ★ LATE MODEL USED COLOUR TVs
- ★ REFURBISHED TO HIGH STANDARDS
- ★ BECOME ONE OF OUR REGULAR HIGHLY SATISFIED CUSTOMERS
- ★ EARLY COLOUR TVs FROM £5

Unit 10, Chiltern Business Centre,
Garsington Road, Cowley, Oxford
(next to B.L. Works).
Phone 0865 711966

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.78 per single column centimetre (minimum 2.5 cms). Classified advertisements 40p per word (minimum 12

PRICE BUSTERS IN BIRMINGHAM FOR

TESTED AND UNTESTED TV'S AND VIDEO'S

ALSO AVAILABLE DIRECT LORRY LOAD

RING - 021-772 2733

WILTSGROVE LIMITED

(Next Door to UNCLE'S DISCOUNT STORE)

128-130 Ladypool Road,
Sparkbrook, Birmingham B12 8JA.

CASH ONLY

"STOP PRESS"

NOW IN STOCK ELECTRONIC VIDEO'S AT UNBEATABLE PRICES

IF YOU OR YOUR COMPANY ARE INVOLVED IN
VIDEO SERVICING

READ THIS

VCR PROTECTIVE COVERS

PERSONALISED WITH YOUR TRADE NAME

- ★ Fits all modern VCR's - excluding portables
- ★ Made from sturdy quilted material
- ★ Gives all-round protection against damage/scratching during transit - no dangling mains flexes
- ★ Allows discreet removal to and fro - your customer will greatly appreciate this
- ★ Creates good caring company image

Price (including P & P)

£6.50 each

Pack of 5 - £30

Pack of 10 - £55

DON'T DELAY

- ORDER TODAY!

You'll wonder what you

did without them!

Just print out your trading name and enclose with your order and cheque/P.O. to:

N.F.P.C., 3 Fenham Hall Drive, Newcastle upon Tyne NE4 9UT

Tel: (0632) 272464

Please allow 21 days for delivery

EAST ANGLIA SUPPLIES (BARRY T.V. SERVICES)

WE SPECIALISE IN LATE MODEL TELEVISIONS AND V.H.S. VIDEOS.

T.V.'s

G11's, KT3, K30, K35, CTX.

Other makes available.

VIDEOS

Ferg 3V29, 3V30, 3V35, 3V36.

Nat Pan 2000, 2010, 333.

Hitachi 8000.

Mitsubishi - various models.

All items fully serviced and ready for sale or rent in excellent condition. Free delivery for sensible size orders (petrol only charged).

Phone today for prices and availability to:
CAMBRIDGE 69215

B.G. COMPONENTS

T.V. & VIDEO SPARES

We supply spares for most makes including Sony and Fidelity all at competitive prices.

We also stock a comprehensive range of rebuilt C.R.T.'s including Hitachi and Sony.

Open Monday-Saturday.

Hill Street, Oldham OL4 2AG.
061-624 1753.

PHILIPS VIDEO SPARES

Model VR 2324. Brand new unused includes power supply tuner, timer clock, R.F. panels, cabinet, electronics only, no mechanism £35 inc VAT and postage.

EFJAY PRODUCTS

13 Placehouse Lane, Old Coulsdon, Surrey
Phone: Downland (07375) 55287 anytime

SERVICE PAGES

words), box number 70p extra. All prices plus 15% VAT. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank PLC". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 204B (H.H.), IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5942).

COME OVER TO DATEL LTD. FOR GREAT DEALS ON SUPER SETS

- ★ 96 CHASSIS IN 5's £25.00 ★
- ★ 9,000 CHASSIS IN 10's £17.00 ★
- ★ VHS VIDEO'S FROM £50.00 ★

All Thorn range in stock from 8.8 to TX 10 Stereo
Large stocks of working TV's and Video's.

Phone or call in today. You won't be disappointed.

Delivery to you can also be arranged.

Also complete postal service for all Thorn range of panels and spares. All panels and spares for mech. videos.

DATEL LTD.

0245 469779

2 Oyster Place, Montrose Rd., Dukes Park Ind. Est., Chelmsford, Essex

FYLDE T.V. AND VIDEO DISTRIBUTORS

Unit 7, Arkwright Court.

Blackpool/Fylde Industrial Estate
Very End of M55 left at roundabout.

UNLIMITED SELECTION OF

THORN	8800	PHILIPS	G11
	8800 R/C		G11 R/C
	9000		G11 TTX
	9000 R/C	GEC	S/S
	9600 R/C	JVC	20"
	9600 TTX	MONO's	20" + 24"

AND MANY MORE

TRADE WORKERS TO ORDER

PHONE BLACKPOOL

(0253) 64413

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Cross-hatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White, Mains Powered. **£75.90**

OUTPUTS PROVIDED

UHF OUTPUT
VIDEO OUTPUT
SOUND OUTPUT
LINE PULSE
FIELD PULSE



Same as above plus RGB output **£81.50**
Line Output Transformer Tester **£11.50**
B/W Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale UHF output **£18.50**
Same as above but with Video Output **£20.50**
Capacitance Meter measures 10pF to 1µF complete with moving coil meter **£14.75**

CRT TESTER/REJUVENATOR SEND S.A.E.

S.A.E. for details. Prices include VAT.
Postage on Colour Bars £1.75, others 75 pence.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,
Wolverhampton WV1 3DW.
Tel: (0902) 871563

VIDEO & HI-FI ELECTRONICS

379 EDGWARE ROAD
LONDON W2
TEL 01-258 0328

ALL VHS PARTS AVAILABLE. EXAMPLES:

VIDEO HEADS

JVC, Ferguson, Akai, Saba, Telefunken **£35.00**
Sony (Betamax) **£45.00**
National Panasonic **£45.00**
All Hitachi heads from **£42.00**

INTEGRATED CIRCUITS

UPC 1365C **£6.30**
UPD 553C **£10.20**
UPD 552C **£9.56**
HA 11711 **£10.50**

All makes of idlers, pressure rollers, clutch assembly and motors in stock.

Many other parts available. Send SAE for list.

ALL PRICES INCLUSIVE OF VAT
ADD £2.00 FOR P&P

TRADE TV's & VIDEO'S

Ex-Rental & Repossessed

Video's from £20.00

TV's Colour £5.00

TV's B/W £1.00

Working TV's Colour from £10.00

Spares, Panels from 50p

Tel. Bradford 480281/733373

TELEFIX

1 Ellingthorpe St, Wakefield Rd.,
Bradford 4

TUBES

NEW OR REGUNS

ONE YEAR GUARANTEE

14" FROM £45 370 - KRB - LHB - HGB - HFB - HUB - BRB - EGB - EFB - MEB - GUB - AXT 37 - 001 - AXM 37 - 001 - 37 - 565 - 570 - 552 - 554 - 590 - A34 EAC 00X.
Broken Tube We Can Help.

16" 420 EDB - EFB - CZB, 42 - 001, 42 - 556.

20" 51 - 161 £40, 51 - 500 - 554 - 570 - 575 - 580 - 590 - 510 - 001 AXT - 510 JKB - VB - UFB - RJB - UDB - HWB - 510 ABUB from: £45.

22" 56 - 500 £45, 56 - 540 - 610 - 611 - 615 - 700 - 712 - 560 EGB - DAB - DMB - BYB - EGB - TB - GAB - AXB - ETB - HB - DYB - ATB - BMB - HW 56 - 001 AXT. FROM £45.

26" 66 - 500 - 510 - 540 - 611 - 615 FROM £55.

HITACHI 510 HWB - VLB - VSB - 560 DZB - HWB - 490 DKB22 FROM £34.

SONY £65 Cash & Carry only.

DELTA £29.00 Reguns. One year guarantee
£14.50 Slightly used, 6 month guarantee.

A56-120 A56-140 A51-110 A49-191 A47-342 or 343
A44-270-1 A66-120 A66-140 (410) A67-120
(All 26" add £5)

PROFESSIONAL STICK
DE-GAUSSING COILS
£21.00 (1 YEAR GUARANTEE)

Philips G11 AND DECCA 100

Panels from £10.00. Breaking for spares. Push button units. Tube bases. All good working order.

RADIO and TELEVISION SERVICING BOOKS
(MacDonalds) New 74/75, 75/76, 76/77, 77/78, 78/79, 79/80, 80/81, 82/83, 83/84, 84/85, 85/86. See our special offer advert under Books.

FREE DELIVERY

Except Tubes £5 each. All prices are inclusive

U-VIEW

29, Warmsworth Road, Doncaster,
Yorkshire DN4 0RP. Tel: 0302 855017.
Callers ring first, open every day including Sunday
1/2 a mile from A1

BESCO LTD T/A NORTH WEST ELECTRONICS NEW STOCKS ARRIVING DAILY

**NEW TRADE SHOWROOM NOW
OPEN. WORKING TVS AND VIDEOS
ON SHOW.**

**H.P. REPOS AND EX. RENTALS
COLOUR TV'S AND VIDEOS**

Refurbished TV's

BUSH T20/T26 £45
G11 £50
PYE KT3 £65

Others done
to order.

**DISCOUNT
FOR
QUANTITY**

Annual Clearance Rock Bottom Prices

PYE G11 EXC CAB.	£40	PYE KT3	£50
BUSH T20/26 CH	£35	GEC 2213	£30
HITACHI 191 ...	£20	THORN 3000	£7
FERGUSON TX		GRUNDIG G415/ 4206	

(NOT D.E.R. Etc.) £65
GEC 2010 £20
PYE 222 £20
PHILIPS 550 £15
BUSH 718 £20
BUSH 2 CHIP £8
GRUNDIG 5010 £10

Best Stock in
Country
over 2000 in stock
(90% of our TV's
Switch on)
Special Price
Quoted
For Bulk Purchases
From Source.

Video


SHARPS 7300,
8300, 9300
HITACHI,
VT11,
FERGUSON
3V29
(Not Ex D.E.R.
etc.)
SANYO,
SONY,
BETA

**LAUREL STREET, LEEDS ROAD,
BRADFORD, W. YORKSHIRE BD3 9TP.**

5 MINS FROM MOTORWAY

100's PX
**HOOVER JUNIOR
VACS**
All models in stock

**Tel (0274)
660995**

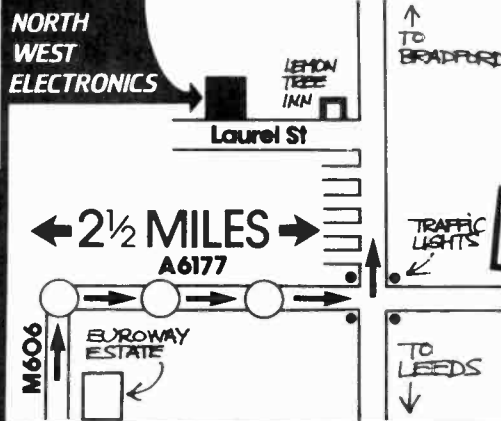

**P.X. WASHERS
COOKERS
ETC**

CASH ONLY

**OPEN 6 DAYS
SAT 9-5.30**

'BOBS'

TELEVISION WAREHOUSE

A NEW CONCEPT IN EX-RENTAL T.V. & VIDEO

**BOB IS BACK AND OPENS HIS NEW WAREHOUSE
IN ESSEX ON JULY 1ST**

NO FREE HOLIDAYS OR WINE. JUST THE USUAL GOOD HONEST T.V. & VIDEO AT GOOD HONEST PRICES. WORKING T.V. AND VIDEO ENGINEERED TO THE HIGHEST SPECIFICATION READY FOR YOUR SHOWROOM. NON-WORKING GUARANTEED COMPLETE AND UNCANNIBALISED.


COMPLETE LOADS DIRECT FROM SOURCE. NEW GRADE "B" T.V. & VIDEO AT LOW PRICES. DELIVERY SERVICE AVAILABLE.

PHONE BOB BEAN ON:

0268 728966

AND DISCUSS YOUR REQUIREMENTS — ALL MAKES AND MODELS AVAILABLE —

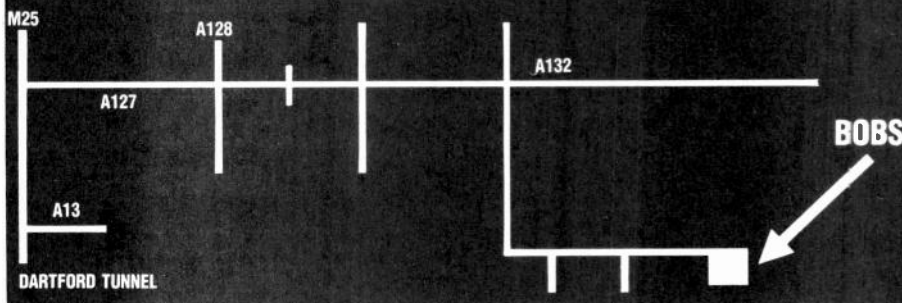BOBS T.V. WAREHOUSE, 1 Swinbourne Ct, Burnt Mills, Basildon, Essex



INDEPENDENT TELEVISION AND VIDEO COMPANY

LARGE STOCKS TO CLEAR
EVERY WEEK

COMPETITIVE PRICES

EXAMPLES:

B&W 20"-24" From £1.00

COLOUR:

Bush 1-2 I.C. £4.00
Philips 520-550, 26" £6.00
Thorn 3500 £6.00
GEC-Decca-ITT £6.00

Philips 550 22" £10.00
Pye 18"-20"-22" £10.00
GEC 20"-22" 26" £12.00
Thorn 8800-9000-9800 £15.00

Many Other Modern Sets
and VHS Videos

PHILIPS G11 - ITT - Bush T20-T22-
T26, Hitachi, Nat. Pan. - Sony
Off Pile from £40

Phone Steve: Nottingham
(0602) 864627

Unit 3

Meadow Trading Estate,
Meadow Lane,
Nottingham NG2 3HQ.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of

Television for

insertions. I enclose Cheque/P.O. for £
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

NAME

ADDRESS

Send to: Classified Advertisement Dept.

TELEVISION

Classified Advertisement Dept., Room 2612,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-251 5942.

Rate: 40p per word, minimum 12 words.
Box No. 70p extra + 15% VAT.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS. 8/86

WORKING CTVs THE BEST & CHEAPEST IN LANCASHIRE SPECIAL OFFER

Working Decca Bradford Including
Black Fronts
18" 20" 22" 26" ONLY £20.00 each in 6
units

Working GEC Plastic & Wooden. All models
20" 22" 26" ONLY £22.00 each in 6 units

Working Bush 20" 22" 26"
ONLY £15.00 each

Philips G8 (520) 22" & 26"
ONLY £20.00 each

Plus many more makes & sizes in stock,
inc. Tanburg, Nordmende, Thorn.

1st COME 1st SERVED

ALL SETS TESTED & WORKING

CALL

JOHN POWNEY

TRADE TV SALES & SERVICE

Unit 31 Progress Industrial Estate,
Kirkham, nr Preston

(0772) 683392

UNTESTED PANELS FOR ALL MAKES OF TV
£1.25 per panel plus post & packing

G.11s Pye & Philips	£20
ITT Remote with handset	£35
G.11 Text	£55
KT3's	£55

ALSO ON STOCK

THORN, DECCA, BDFD, 80-88-100, PYE CHELSEA 222, TTT CVC 20, 23, 30, 32 Remote, PANASONIC, HITACHI, TANDBERG, GRUNDIG, GEC 2002, 2242, 2642, 2202, and many others, changing daily.

VIDEO AS AVAILABLE. FROM **£20.**

VHS HITACHI, 9500, 9300, VT9, 8500, 8300, 8000, PANASONIC, 366, 7200, TRIUMPH 9500, JVC, FERGUSON.

BETAMAX SONY C5-C6, C7, SANYO, 5000, TOSHIBA.

2000 SYSTEM PHILIPS 2020, 2021, 2022, GRUNDIG 244.

STANDS, SLOT METERS, PANELS, SETS FOR SPARES, CLEARANCE COLOURS CHEAP. PRICES BASED ON QUANTITY. ALL PLUS VAT.

GENERAL FACTORS
UNION STREET,
DONCASTER, SOUTH YORKS.
0302-49583

CASH NO CHEQUES.
ONLY 2½ MILES FROM
(A1M) FOR M18-M1.
10 am to 5 pm Daily

BOURNEMOUTH

**LARGE STOCKS OF NICE
CLEAN WORKING SETS,
MOST MAKES AND SIZES.**

FAIR PRICES – TRADE ONLY

**WAREHOUSE OPEN:
Mon-Fri 9-1, 2-5**

**HILLIER'S, UNIT 2A,
11-15 FRANCIS AVENUE,
WALLISDOWN. TEL: 0202 581932**

PLEASE
MENTION
TELEVISION
WHEN
REPLYING
TO
ADVERTISEMENTS

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS
£4.95 inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

HALTON TV TRADE DISPOSAL

THE WHOLESALE YOU WON'T FIND COMPETING WITH YOU ON THE HIGH STREET.

TVs & Videos off the pile
Philips, GEC, Doric, Decca, etc.

Remember we have NO retail outlet
St Michaels Industrial Estate, Unit 1,
Block B, Widnes. Tel: 051-423 1577.

NORMAN ENTERPRISES LTD

Weston-Super-Mare, Avon.
Tel: 518335

Colour TVs fully engineered
with a special care on tubes

Hitachi 217 Remote Control	£85
Thorne 9000 Remote Control	£42.50
Pye G11	£47.50
Rank T20	£42.50
Pye Chelsea 6 Button	£27.50
Pye 725	£37.50
Pye 721	£27.50
Thorne 9600	£45
Thorne 9200	£42.50
Bush T20 Remote Control	£49.50
Bush T24	£55.50

ITT 20 INLINE TUBE
£45.00 + VAT.

All above prices include hand sets if available. Ready for sale.

Phone now, limited number each month. All the above off the pile, less a 3rd

EUROLEC U.K.

VCR CASSETTES

BASF LVC £8.00, LVC 150 £6.50, LVC 120 £5.00, PHILIPS LVC 90 £4.00, LVC 60 £3.00 (Some have outer wrappings removed but are all new).

Above prices include V.A.T. & P&P. NTSC-PAL-NTSC transfers, VHS, BETA, +UMATIC £15 first hour, thereafter £10 per hour (Tapes included in price). Optical transfer 8mm standard & super 8 transfer to VHS 50p per minute, tape & postage extra. We specialise in the sale & purchase of NTSC equipment. We also buy and sell Sony edit equipment & recorder/players.

Mail Order address:

35 Sandy Lane, South Wallington, Surrey.
Telephone 01-669 2611

EXPRESS PANELS

A highly skilled staff using specialized service jigs and some of the most up to date techniques and test equipment available means we can save you time, money and headache.

EXAMPLES FROM OUR RANGE (exch. basis)	
Bush T20/22/26 power supply	Sony 1820/2000/2204 power supply
£14.75	£16.75
G11 power supply	GEC 20AX/30AX power supply
£14.60	£14.75

All prices subject to VAT, P&P FREE (if orders over £10.00). Panels also available for outright sale, discount for quantities (any mix) all panels guaranteed 3 months, are chemically cleaned and print re lacquered, and have no damaged print etc, so they not only work they look good too. Send S.A.E. for NEW CATALOGUE or ring with your requirements.

TRADE SERVICE AVAILABLE for VCR's.

Callers by appointment only. Telephone orders accepted using Access & Visa.

021-359 3753

**ARGO SERVICES (B.HAM) 53,
Lawley St, B.Ham B4 7XH**



STARLITE ELECTRONICS

WILLOWS FARM,
A13 RAINHAM, ESSEX.
Rainham 23225 also
Hornchurch 50238.

EX RENTAL TVs
UNTESTED FROM £15.00
WORKING TVs £20.00
RE-GUNNING TUBES

2 year guarantee
Most types available
including Sony



WANTED

WANTED FOR CASH. Ex rental colour televisions and videos. Large or small quantities. Will collect. Tel. 0272 211179.

WANTED VIDEOS, Portables, colour TV etc. Any quantity. Immediate collection, cash paid. Tel. Stoke on Trent 416401.

WANTED. First and second edition servicing with the oscilloscope by G. J. King. (Good price paid). Launceston 0566-4517. 6pm-10pm.

WANTED. Cossor 2100 Oscilloscope manual-circuit. Telephone Belfast 623456.

CASH PAID now for your surplus TV spares, transistors, I.C.'s etc. Tel. MR. FORSHAW, 0902 29022.

CASH PAID for service manuals VCR, CTV, or V/ Camera 1971 onwards. Must be complete and originals in new or good-used condition (no photocopies). Tel. 0202 892279.

WANTED

**Ex RENTAL COLOUR
TVs IN BULK
QUICK COLLECTION**
Phone 0742 312832
(Sheffield)
IN STRICTEST CONFIDENCE

REPAIR SERVICE

INSTRUMENT REPAIRS, Oscilloscopes, generators, multimeters & more. Phone VIKING ELECTRONICS 0394 450006.

PRINTED PANEL REPAIR SERVICE

for example: G11 - T20 - AX PSU - **£15.00**
G11 - T20 - AX - LTB - **£16.00**
Most makes and models covered.
RING 0934 418545
for price list or quotation

MISCELLANEOUS

GET SHARP PARTS FAST

TELEPHONE
0734 - 876444
TELEX 848953



SHARP

Main U.K. Spare Parts Distributor

Audio-TV-Video ★ Microwave ★ Photo-copier ★ Typewriter

All U.K. model spares available. Same day despatch of orders received before 1pm.
Microwave, photocopier and typewriter spares to authorised service dealers/centres only.

WILLOW VALE ELECTRONICS LTD.,
11 Arkwright Road, Reading, Berks.

MAIL ORDER MANUALS

BURROWS SERVICE
33 HANCOCK ROAD,
LONDON SE19 3JN.

£1 LISTS (Refundable on orders)

The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes

- Part 1.**
The Colour Signal
Part 2.
The Receiver Decoder
Part 3.
Receiver Installation



VHS★★★V2000★★★
BETAMAX★★★UMATIC



For full details telephone
0253 725499 (Day)
0253 712769 (Night)

Or send for precis details
FLINTDOWN CHANNEL 5
339 CLIFTON DRIVE SOUTH,
LYTHAM ST ANNES FY8 1LP
(enclosing this advert)

NAME
ADDRESS
TEL:

To advertise in
TELEVISION
ring
01-261 5942

SOLE SUPPLIERS TV/VIDEO Repair manuals/circuits, 1000s s/manuals supplied by return. S/sheets £2.50 except CTV/m.centres/stereos £3.50. LSAE with every order/query please brings free price list/magazine inc sheet - or phone 0698 884585 (883334 outside business hours) TIST, 76 Church Street, Larkhall, Lanarkshire.

NOW TOTAL SPARES SUPPORT FOR



FROM



ALL from STOCK (Subject to availability from Fidelity)

Trade Prices subject to official order - all others supplied at retail

**CABINETS ★ KNOBS ★ TUNERS ★ CONTROLS ★ CRT'S ★ TRANSFORMERS
SEMI'S ★ I.C.'S ★ CAPACITORS ★ REMOTES ★ TRIMS ★ END USER PARTS**

Tel:
0734
876444

Willow Vale Electronics Ltd

11 Arkwright Road, Reading, Berkshire RG2 0LU

Tel:
0734
876444

GENUINE FIDELITY PARTS AT STANDARD FIDELITY TRADE PRICES

SERVICE SHEETS

TECHNICAL INFO SERVICES (T) - 76 Church St., Larkhall, Lanarkshire ML9 1HE.

World's Sole Publishers of Comprehensive TV/Video Repair Manuals & Largest Known Stockists of Service Manuals and Service Sheets for all kinds of equipment both British and Foreign from 1935 to latest issues.

Big Catalogues of thousands of Service Sheets & Manuals + Chassis Guide + £4 Vouchers - saves time and expense £3.

Any published single service sheet for £2.50 + Isae except ctv/mus-c/combis from £3.50 + Isae.
A selection from our stocks of thousands of Service Manuals ready for despatch by return post.
Any Sony: Hitachi ctv from £8.50. Thom 3000/3500 £9.50. Thom 8000/8004/8500/8600 £9.50. Philips G8 complete £9.50. Decca 30/31 £8.50. Ferguson/JVC 1st video £19.50 or 3V00 types basic manual £19.50. Any Finlandia: Tyne CTV £9.50 each. Rank A823 complete £9.50.

COMPREHENSIVE PRACTICAL TV REPAIR MANUAL £9.50 PRACTICAL RADIO SERVICING & REPAIR COURSE £9.50
THE 11 TUNBRIDGE REPAIR MANUALS ONLY £38 THE 5 McCOURT REPAIR MANUALS ONLY £55
ANY SET OF 5 INDIVIDUAL VIDEO REPAIR MANUALS FOR £12.50 OR ALL 3 SETS (15 MANUALS) FOR £36.

UNIQUE COLLECTIONS OF CIRCUITS, LAYOUTS, ETC. . . . FANTASTIC VALUE

British ctv from hybrids to modern (3 binders) £58 Videos, all types (3 binders) £58 . . . any 1 for £20
Mono TV (2) £38 Foreign ctv (2) £38 Domestic Eqpt (2) £38 Portable British ctv (1) £20.

COMPLETE REPAIR SYSTEMS . . . huge savings from published prices

British ctv 3 binders of Circuits plus 6 Repair Manuals plus ref books, etc. for only £140
Foreign ctv 2 binders of Circuits plus 4 Repair Manuals, etc. for only £65
Videos 3 binders plus 15 individual Repair Manuals cover all the commonest models for only £85
Complete Integrated T.V. Repair System only £250 or in 12 sections at £25 per section.
Contents: 8 binders of circuits/16 Repair Manuals/dozens of other manuals . . . Any new publications from us within 1 year of ordering 1st section will be added at no extra charge.

NEW - PRACTICAL TRANSISTOR - **NEW** - VIDEO REPAIR SYSTEM 3 £28 - **NEW**
From beginners/students elementary theory to more advanced. Huge section British/Foreign equivalents/alternatives/other data. £5.80 Post Free. Binder of Circuits alone £29 5 Repair Manuals £12.50
3V31/32 Sharp 2300 to 9700 Philips Laser Disc Pan 7000/7200/7800.

Repair data/Circuits/Service data almost any individual mono tv £12.50 basic ctv £16.00 video £25.00
Repair data/Circuits almost any individual mono tv £10.50 ctv £12.00 video £10.50

LSAE BRINGS ANY REQUESTED QUOTATION - FULLER DETAILS - FREE MAGAZINE - PRICE LISTS ETC.
PHONE 0698 884585 Mon-Fri before 5pm or 0698 883334 any other time - FOR FAST QUOTES

BOOKS AND PUBLICATIONS

THE DOMESTIC VIDEO RECORDER SERVICING BOOK

THE ENGINEERS BIBLE

WITH CHAPTERS ON HI FI, DIGITAL SERVOs, LUMINANCE AND CHROMINANCE SIGNAL CIRCUITS, FAULT GUIDES AND CONNECTION DATA.

A MUST FOR ALL VIDEO REPAIRERS AND STUDENTS. THE COMPLETE REFERENCE TO VIDEO RECORDER CIRCUITS

ORDER YOUR COPY NOW

FOR ONLY £16.95 inc. P&P
FROM NEWARK VIDEO CENTRE

(0636) 71475

OR DIRECT FROM:

GROVE FARM, LONG LANE, BARBY IN THE WILLOWS, NEWARK, NOTTS.

CHEQUES AND PO'S PAYABLE TO D. BEECHING.

SPECIAL OFFER

MACDONALDS RADIO & TV SERVICING BOOKS, NEW 74-75, 75-76, 76-77, 77-78, 78-79, 79-80, 80-81, 82-83, 83-84, 85-86.

Macdonalds Price £5-85 £24.30 delivered
OUR PRICE AVAILABLE £22.50 delivered
Two or more 10th AUG £21.00 each
Full set of 10 £199.00

Prices include delivery

U-VIEW, 29 Warmsworth Road,
Doncaster, Yorkshire DN4 0RP.
Tel. 0302-855017. Callers ring first

SERVICE MANUALS, SERVICE SHEETS

For Television, Radio and V.C.R. Prices from £2.00

Send large s.a.e. for free catalogue with your enquiries. Mail Order only.

TECHNICAL DEPARTMENT, YOLANCEN LIMITED,
1 Buckingham Street, York YO1 1DW.

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 505885.

METERS

AVON METERS

We buy and sell and repair TV coinmeter.
Reasonable prices, one year guarantee.

327 Church Road,
St George, Bristol.
0272 559761

METERS. Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) LTD. (0202) 683498.

TELEVISION METERS. All types required for cash. We collect. P & J WALES, Tel. (0803) 25832.

AERIALS

SATELLITE TV RECEPTION EQUIPMENT



Dishes 0.9 to 2.8m, complete systems 10.9-12.7GHz, 4GHz LNB's, demodulators, and all those accessories.

Manufacturers and Distributors of high quality satellite TVRO equipment.

DX
ANTENNA

KESH ELECTRICS LTD.

Main St., Kesh, Co. Fermanagh, N.I.
Phone: KESH (03656) 31449

SERVICE DATA-UK VCR & CTV

Circuits only or complete with layouts setting-up instruction etc.

CTV from £2.25 VCR from £4.75

SAE bring lists

DATA-GO, 112 Aameysford Road,
Ferndown, Dorset BH22 9QE.

FOR INFORMATION ON
CLASSIFIED ADVERTISING
PLEASE RING PAT BUNCE

01-261 5942

SATELLITE TELEVISION


Buy direct from the manufacturers, low cost, full band satellite TV systems. Full band system £650 + VAT and Carriage

Write or telephone for details or call in at our factory showroom

NETWORK SATELLITE SYSTEMS LTD.
Unit 7-8, Newburnbridge Ind. Estate,
Hartlepool, Cleveland
Tel. 0429 274239 or 869366

AERIALS (cont.)

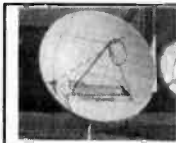MULTI-OUTLET/MULTI-CHANNEL Installations. Large or small distribution systems. Equipment and/or consultancy by post or on site. Catalogue (full of trade know-how and trade equipment) £1 (refundable). **WRIGHTS AERIALS**, 43 Greaves Sike Lane, Micklebning, Rotherham. (0709) 813419.



Euro-Sat
Parabolic Dish Antennas
(Parent company est. in
TV communications since 1969)
SATELLITE TVRO ANTENNAS
TOP QUALITY SOLID
GLASSFIBRE DISH ANTENNAS

TRADE PRICES	
1M. DIA 11-12.4 GHZ BAND	£77.00
1.2M. DIA 11-12.4 GHZ BAND	£93.00
1.6M. DIA 11-12.4 GHZ BAND	£117.00
1.8M. DIA (PETAL) 11-12.4 GHZ BAND	£157.00
2M. DIA. 11-12.4 GHZ BAND	£215.10
2.3M. DIA. (PETAL) 11-12.4 GHZ BAND	£248.10
3M. DIA 11-12.4 GHZ BAND	£737.00

Euro-Sat
107 Cross Street, Sale, Cheshire, England.
Tel. 061-437 2631 061-881 4249

SITUATIONS VACANT

T. V. VIDEO ENGINEER wanted to share small business in Herefordshire. Full or part-time use of premises. Very low overheads. Box No. 221.

FOR SALE

2 SETS OF FULLY RECONDITIONED tube re-gunning plants for sale. Training provided. From only £3,995. Tel. 0582-410787.

PHILLIPS V2000 TAPES. V2000 heads & spares, various service manuals. PM2517 digital meter. Telephone 0743632 406.

LEADER C.R.T. TESTER, REJUVENATOR Model LCT 910A £168. Telephone 051-648 1627 evenings.

DEVONICS

Quality Tube Rebuilders

2 YEAR WARRANTY

Inline Tubes	
Up to 19"	£43
20" to 22"	£45
26"	£46
Bonded Coil	+ £5
30 AX (-540x)	+ £7

Delta tubes from £30
All plus carriage and VAT

We currently seek sound inline glass for narrow neck (29mm) and 30AX types especially 560 AWB/BJB/BYB/CSB and 510 CJB.

**2A BARTON HILL ROAD,
TORQUAY TQ2 8JH.
0803 33035**



Sabaco For a great deal!

TRY US YOU'LL LIKE US
TOP QUALITY TV'S & VIDEO'S AT
ROCK BOTTOM PRICES

VAN LOAD DIRECT FROM SOURCES
ALL SETS & VIDEO'S OFF THE PILE
(Mostly switch-ons)

**Largest selection of 4000/8800/9000/9200/
9600/Ferg TX9/TX10 Stereo Teletext
Colour Portables**

Mainly teletext and remote with handset.

**Also Pye KT30/G11/T20/T26/Hitachi/
Philips 550/Grundig & many more.**

BRAND NEW SETS AT LOW PRICES

VHS VIDEO'S

**Good Working Order from 3V22, 3V23,
3V29 Portable Video's etc.**



**Also a selection of brand new video &
£180 video tapes**

OPENING HOURS:

MONDAY TO SATURDAY 9am to 5.30pm
SUNDAY 10am to 4 pm

CASH ONLY All goods subject to VAT & availability
**PHONE NOW FOR UP TO DATE COMPUTERISED PRICES
AND DELIVERY DAYS, BE HERE WHEN LORRY ARRIVES
FOR FIRST CHOICE — PHONE US NOW ON:**

(0602) 397555

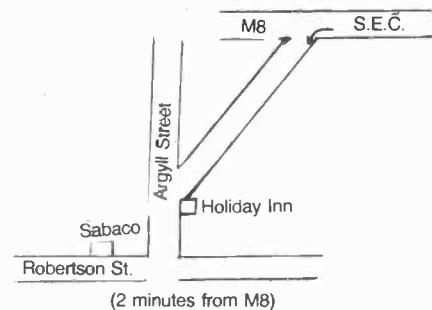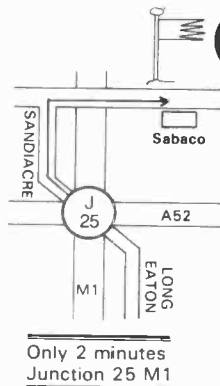

Head Office:
Sabaco
Saba House,
46A Derby Road,
Sandiacre, Nottingham
(0602) 397555

Sabaco
75 Robertson Street,
Glasgow
(041) 221-2146

THE WORLD OF ... **"TELEPANELS"**

52 Mount Pleasant Road, Chigwell, Essex, 1G7 5ER. Tel: 01-729 0506.

GRAND OPENING OFFER
SUPER WORKING PANELS FOR THE PHILIPS G11



**WORKING
 PANELS
 GALORE!**

P+P 1 PANEL £1.75. 2 PANELS OR MORE £3.50
 N.B. All panels despatched by recorded delivery
 to avoid loss.

	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	8.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731			10.00		18.00	10.00	7.00	8.00		4.50
BUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BUSH T/20	7.50	6.50	14.00		19.00	19.00	5.00	14.00		
PHILIPS G11	14.50 WITH COMBINED SOUND MODULE		12.00		19.00	19.00	5.00	11.50		
DECCA 80	12.00	POA	14.00		12.00	10.00		14.00		POA

POST OFF YOUR CHEQUE NOW! AND YOUR PANELS SENT BY RETURN OF POST!!!

SPRING SPECIALS

10 BUSH 2 CHIP	£50
10 BUSH T20	£250
10 REDIFFUSION MARK 3	£250
10 REDIFFUSION MARK 1	
REVAMP	£120
10 THORN 8000 17"	£150

**LARGE QUANTITIES
 OF BETA VIDEOS
 RING FOR SPECIAL PRICES**

ALL + VAT

TELETRADERS

Forde Road, Brunel Industrial Estate,
 Newton Abbot, Devon
 Telephone: (0626) 60154
THE NO. 1 WHOLESALE IN THE SOUTH

SPECIAL ANNOUNCEMENT

From:

NORGROVE TV TRADE SERVICES
 Water Street, Birmingham B4 6BJ.

Hundreds of TVs and Videos arriving weekly.
 Available for sale to the trade.

Most makes in stock including the full
 Thorn range, RBM, Philips, Pye, ITT,
 Hitachi, Sony, Panasonic, Sharp, Sanyo,
 Decca and many others.

Spares available. Deliveries arranged.
 Export enquiries welcome.

OPEN SUNDAYS BY APPOINTMENT.

For quotation. Please ring:

021 236 9616

N.G.T. COLOUR TUBES

First Independent Rebuilder with
B.S.I. CERTIFICATION

DELTA - IN-LINE - PIL - BONDED YOKE
 including
 AXT Series, DZB series 20AX - 30AX
 A56 610/67 610 series, A51 570/580/590X
 A51 161X, Sony types etc.

- ★ Rebanded with new adhesives
- ★ Excellent high voltage clean-up
- ★ Accurate alignment of Gun and Yoke
 for optimum convergence

N.G.T. ELECTRONICS LTD.,
 120 SELHURST ROAD, LONDON SE25
 Phone: 01-771 3535.

25 years experience in television tube rebuilding.

CentreVision

TEL: 0222-44754

SLOPER ROAD, LECKWITH, CARDIFF CF1 8AB
 OPPOSITE CITY FOOTBALL GROUND, 5 MINS FROM M4

FERGUSON VHS VIDEO £65

MANY ELECTRONIC VIDEOS IN STOCK

MANY TOP QUALITY REMOTE CONTROL WORKING TVs

PHONE FOR LATEST PRICES

PRICES SUBJECT TO VAT

OPENING HOURS:

MONDAY - FRIDAY 9.00 - 5.30; SATURDAY 9.00 - 1.00

INDEX TO ADVERTISERS

Advanced International Marketing (U.K.) Ltd.	627
Aerial Techniques	663
Apollo	676
Argo Services (B'ham)	682
Avon Meters	684
Barry TV Services	678
Besco Ltd. (T/A North West Electronics)	680
B.G. Components	678
B.K. Electronics	619, 634, 670
Billington Valves	665
Bobs T.V. Warehouse	681
Bolten Ltd.	674
Burrows Service	683
Carter, John (Electrical) Ltd.	669
Celltel	668
Centrevision	686
Chromavac Ltd.	627
Chromavision	672
CMJ Products	679
Crewe Wholesale TV	677
Cricklewood Electronics Ltd.	674
Data - Go	684
Datel Ltd.	679
Devonics	685
Display Electronics Ltd.	634
East Cornwall Components	628
Economic Devices	652, 653
Ejlay Products	678
Electric City	627
Eurolec (UK)	682
Euro-Sat	685
Flintdown Channel 5	683
Ford, Frank	673
Fylde T.V. and Video Dist.	679
Garton, D. & G.	683
General Factors	682
G.G.L. Components	624
Grandata Ltd.	672
Halton TV Trade Disposals	682
Harrison Electronics	665
Hillier's	682
Hockley Discount Televisions	674
Hussain Central T.V. Ltd.	625
ICS	619
Independent Television and Video Co.	681
Junction 11 T.V. Trade Disposals Ltd.	671
Kent Ledgerwood Wholesale Ltd.	677
Kesh Electronics	684
LRC (Spares) Ltd.	671
London Electronics College	675
Manor Supplies	618
Mantel	670
Monolith Electronics Co. Ltd., The	634
N.F.P.C.	678
Network Satellite Systems Ltd.	684
Newark Video Centre	684
N.G.T. Electronics	686
Norgrove TV Trade Services	686
Norman Enterprises	682
Padworth Transformers	665
Post A Part Electronics	633
Powell, T.	675
Powney, John	681
Precision Vision Ltd.	678
P.V. Tubes	620, 621, 622, 623, 624
Quick Save T.V. Spares	626
Repossessed T.V. Centres Ltd.	687
Sabaco	685
SEME Ltd. (Telelift)	665
Sendz Components	668, 688, Cover III, Cover IV
S & G Trade and Retail	683
Sight and Sound	676
Southpark Distributors	634
Starlite Electronics	683
Stewart of Reading	670
Technical Information Services	684
Telefix	679
Telemann	676
Telepanels	686
Tele-part	619, 634, 687
Teletraders	686
Televideo Services	677
Television	678
Tidman Mail Order Ltd.	657
TVS Trade Services	676
T.V. Trade Sales	687
Universal Electronic Distributors	668
Universal Semiconductor Devices Ltd.	624
U-View Tubes	679, 684
Video Hi Fi Electronics	679
WD-TV	673
Well View	676
Willow Vale Electronics Ltd.	683
Wiltsgrove Limited	678
Wing Electronics	682
Wizard Distribution	678
Yolancen Ltd.	684

REPOSSESSED T.V. CENTRES LTD.

061-273-2854


YOUR CHOICE

MINT WORKING SETS. These arrive at our premises in A1 working order, cabinets are superb. **£45 to £70**

GUARANTEED UNTESTED SETS. These are just as they arrive, in good condition with plenty of plug in workers. We do not sort them as we have our separate source of working sets. **£10 to £35**

VHS Videos in stock.

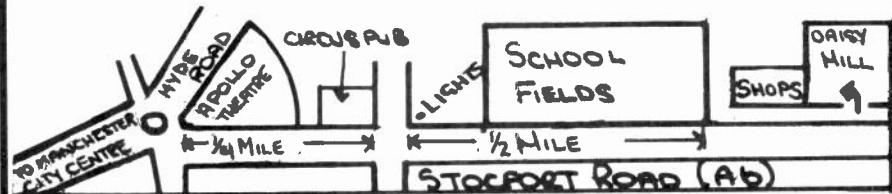*Well stored in large centrally heated premises. Ample viewing space and stored only four high!
Come and have a look round.*



**TRADE WAREHOUSE,
DAISY WORKS,
345 STOCKPORT ROAD,
LONGSIGHT,
MANCHESTER M13 0LF**

**ALSO AT
335-341 STOCKPORT ROAD
(NEXT DOOR)**

IRISH T.V. DEALERS

(PLEASE NOTICE)

LARGE SELECTION OF RECONDITIONED PRECISION-IN-LINE UHF-VHF COLOUR TVs, SOME WITH RE-GUN TUBES FITTED, "CABINETS RESTORED TO A1 CONDITION". PRICES START @ **£60.00** VAT INCLUDED. ALSO 20" & 22" RE-GUN TUBES IN STOCK, QUANTITY DISCOUNT, DELIVERY ARRANGED. VIDEO HEADS ALSO IN STOCK.

(EXPORT SPECIALISTS)

T.V. TRADE SALES	ALSO	T.V.T.S.
E.D.I. HOUSE		CLOVER PLACE
KYLEMORE PK. WEST		COLLEGE ST.
DUBLIN 10.		KILLARNEY.
Tel: 0001-264139 (Local calls 01-)		Tel: 064-33655

**EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●**

IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf", e.g. LOPTZ - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST — RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (WTON)

**32 TEMPLE STREET,
WOLVERHAMPTON (0902) 29022**

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Thorn Spares New 9000 Decoder £8.50 9000 Frame panel £8 9000 Cyclops panel £1.50 8000/8500 timebase panel £8 8800 convergence panel £6 8500 convergence panel £6 4000 Power supply £3 1600 Mains lead, switch 3500 6 push button + cable form £1.50 17605 VNPB TO66 8mV6A 9000 Sound output panel £1 3500 Focus unit £1.50 3500 Mains Trans £4 3500 cut outs 10 for £4 3500 IF panel £2 3500 Frame panel £3 3500 Line panel £3 3500 A1 Diode £2 Export 3500 IF panel £2 IC board with set of SN74LS £4 2000 Tube base £1 3500 A1 pots £5 Beam limiter panel £1.50 3500 Power panel with Y969 £1 3 Way regulated adaptor 240V 6V/ £1 7.5V/300mA £3.50 Rank/Toshiba preh unit 0354 £9.50 2 banks of 3 PB unit. Pyc 731 £2 4 Push button unit preh £1.00 6 Push button VHF/UHF for v/cap. GEC-Decca type £7.00 7 Push button for CVC5 ITT £8.00 G8 Push Button Unit £10.00 KT3 12 Push button unit £2.00 KT3 (Export) 12 F.B.U. £2 6 Push button Unit Thom £1.00 6 Push button Unit fits GEC & Decca etc. £6.00 Hearing aid unit £3.00 Rank Z718 4 P/B Unit MECH £4 7 Button Unit GEC with Lamps £7 Bush TS15A 6 bu ton unit with Pos & mains lead. 6 bust buttons. Bush26.00 697 Push Button Unit £6.00		K35 Decoder £8 K35 Sound OP £4 K35 Split Diode 3122-138-35930 £10.00 Fidelity Tube Base with transistor & focus pot £1.50 Bush Tube Base on panel £1.00 Line Transformers Hitachi Split Diode and GEC 1981 to 1984 £13 2 J/Pots 3.500 1 off each type £3.00 G8 Trans. Philips £7.00 G11 Split Diode £12.00 CVC820 Split Diode ITT £10.00 Thom B/W AD5308F + Stik + Lead £1.50 1690 Thom EHT over-wind with diode lead & anode cap £2.50 GEC 2040 £3.00 GEC 2110 £7.00 Mullard AT 2036 £1.50 Pyc 169 Line Trans £3.00 Rank mono T704A £3.50 Split Diode Trans £7.00 GEC 20 A.X.P. Rank Z522 £7.00 Rank L.O.P.T. Z970 £3 CVC 5-8-9 £3.00 CVC20 ITT £3.50 AT2080V5 £5.00 CVC30 ITT £5.00 CVC32 Line Tran £6.00 CVC800 Line Trans £6.00 CVC80 Slip/Diode £12.00 CVC 45 £3.00 GEC Portable G10T2041 £3.00 GEC Portable G10T2046 £3.00 EHT Split Diode Leads ITT £1.00 3500 L.O.P.T. & HT Trans each £2 LOPT Rank Z763 £5 K35 Split Diode 3122/1335930 £7		Triplers KT3-30 BG 20043 £6.00 ITT CVC 5-8-9 £3.50 Rank T25LE Tripler £2.00 Rank IITPC Ar823 £3.50 TU 25 30K Rank £3.00 11 TEZ Rank £3.00 G9 Philips £4.00 GEC 2110 £4.00 3500 Thom £3.00 900 Thom £6 9500 Thom £4.50 2040 GEC £3.50 GEC TVM25 Tripler £2.00 Universal Tripler £5.00 TVK 769 £3.00 G8 £4.00 GEC 825 ITT CVC 20.25/30/32 £3.50 Decca 80 100 £4.50 Grundig TVK 52 £2.50 IITBQ Pyc 731 £3.00 IITHY £4.00 D212 Pyc 18" colour portable £4.00 LP 119363 £4.00 BG 10041 £3.25 ERO Tripler print type with foas £5 PO7 BG2087 £5 T/text ultrasonic rec'r panel £14.00 Video cassette lamps on lead. 12-14V. 50p or 3 for £1.00 200 for £25.00 GEC 8 touch unit assy complete with all I.C.'s + pots £4.00 G11 E.W. Transformer 50p G11 E.W. coils £1.00 G11 Transient Suppressors 245V 10 for £1.00 G11 Scan Coils £5.00 G11 100K tuner pots 12 for £1 KT3 IF panel £6.00 KT3 line OSC transformer £1 KT3/K30 infra-red receiver head £1 K30 drawer unit with IC's (home) £10 K30 drawer unit with IC's (export) £10 KT3 AE Sockets 50p KT3 receiver panel £8 KT3 line driver transformer 50p Pyc, K30, GEC, etc. Pre-mains stand-by switch £1 Decca 80/100 IF panel £5 NPN PNP 80V 6 Amp TO66 O.P. Trans. pair 25p 5 button touch tuner BBC12 ITV12 £7.00 Control panel 5 sliders + mains lead £1.50 G11 8 touch button unit replaces old P.B.U. £24 Tube base + base unit for 820 Euro chassis £4.00 GEC Line O/P Trans. & Rec Stick for Portable £3.00 CVC 2025/30/35/40 decoder panel £10 CVC 2025/30/35/40 decoder panel (untested) £5 CVC 4045 IF panel £5 40K Transducer 50p PHILIPS NE511N £1.20 LM337M Reg. 30p 20 GEC Black Spark Gaps £1.00 G11 Line Driver Transformer 35p KT3 Front Panel Control Assy. £2.50 BTW 30/50 50p		Rank T20 Z136 Panel £6 NEW Pack THORN 17 off Manual £5.00 NEW 1617 THORN Chassis with ICs & AU113 £5.00 30V Power Supply 500M/A 4x2 1/4 £2.50 Pyc 731 Power Panel £13 6 Diode Universal Triplers £4.00 NEW Pyc 725 Line O/P panel with L.O.P.T. & Tripler £10.00 NEW GEC 20AX Power Supply Switch Mode £12.00 Complete new GEC portable chassis M1201H/M1501H with P.B.U./v/cap/LOPTI £10 Field + Jangle panel for GEC 3133/3135 £1.50 GEC 2110 line panel with transformer £7.00 GEC 2110 tuner unit + IF Panel £12.00 Pyc/Chelsea Line op panel £12.00 Pyc 205 Tuner £3.00 Pyc 205 Line op panel £7.50 Pyc 713 IF panel and tuner £7.00 Pyc 713 Chroma £10.00 Pyc/Chelsea Timebase panel with LOPTI £10.00 Pyc 731 Frame Panel £5.00 Pyc 731 Convergence Panel £10.00 Pyc 731 Chroma £10.00 Pyc 731 IF panel + tuner £18.00 Pyc CDA/205 panel £6.00 GEC portable chassis + LOPTI 2114 New £4.00 Thorn 1617/1713 chassis £9.75 G9 Power Panel £6.00 Mono RANK Chassis 127A NEW £10.00 NEW G9 Frame Panel £10.00 NEW G11 IF Panel £7.00 G8 Tuner Unit + Panel £4.00 G8 Power Supply £5.00 G8 6 Sloping PBU £8.00 G8 IF & Chroma £6.00 G8 Chroma £3.00 1/250AC 20p 1/100 20p 1/800 x 10 30p 4.7M/100 10p 470/100 20p 2000/100 5p 4700/100 75p 47/160 25p 300 300/300V 80p 800/160 50p 1/250 Pulse 5p 2.2 250v 10p 3n3250 A.C. 10p 33250V 25p 39250V 25p 4n7250 tested 5KV 15p 22/250 15p 47/250 10p 100/250 10p G11 470/250V £1.75 GEC600/250 60p 700/250 £1 300 + 300 MFD 350v £1.00 800/250 40p 32/300 20p 6 button switch portable £1.00 GEC V/cap VHF/UHF tuner and IF+ sound O/P PC 706B3 (Export) £12.00 GEC Line O/P PC 659B3 £6.00 2110 GEC Power Panel £8.00 GEC Power Supply (Export) £10.00 G11 dynamic correction panel £6 CVC 20 Front panel with sliders + mains input panel £4 CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £9.00 CVC9 slider pots panel 50p CVC 5 Mains on/off + 5 pots £2 Universal Focus. Fits Pyc, Thom and Decca Units. £1.00 T147 Rank tube base on panel £1.00 Z718 Focus Unit £1.50 T20 Focus Unit £1.00 Large Type 75p Decca Small 75p KT3 Focus Unit 75p KT3 Focus Pot 75p K30 Tube base on panel £1.00 TX10 Focus Units £7.00 CVC 32 Focus Unit 75p Fidelity Focus Unit 14R-14S 30p 3500 Thom Focus Unit £1.00 ITT Small for use with Split £1.00 Z718 Bush Focus £2.00 Diode 50p TV11 50p Remo TV12SP 50p 1600 Thom EHT Rec and Lead 50p TV13 50p TV14 50p TV18 60p TV20 £1.00 TV45 50p Thorn 14/1500 rec stick 5p		Tube Thermpath 167 £1.00 Rank Secam Decoder Panel UHF & VIF T115A £13.00 Multi-Caps 220 MFD Sprague 385V 50p 4,700/75 6 amp Rip £2.00 350V 300M + 300M £1.00 400V 400M 60p 350V 400M 60p Thom 3500 £1.00 175/100/100/350v £1.00 KT3/200/25/25/385v £1.00 300 + 300 + 150 + 100 + 50MFD 350V £2 47/220/350v £2.00 150/150/100/100/100/320v £6.00 2500/2500/63v 50p 150/200/200/300v 70p 400/400/200v £1.70 300/100/100/16/275v £1.50 100/200/325v 40p 150/150/100/375v £1.50 200/200/75/25M 325V £1 300/300/100/32/32/300v 2.00 1500/2000/30v 50p Jelly pot Thom 00D4A/13 £3 150/150/100/100/320v £2.00 100V350 + 300/200/100/16/275v £2.00 225 + 25/380 GEC 70p 200/100/100/350v £1.50 500/500/25v 50p 150/150/100/300v 75p 200/150/150/300v 1.00 ITT 8 and 6 Push Button £1.00 Pyc 725 LOPTs £6.00 Pyc 731 LOPTs £6.00 Thorn 8500-8800 LOPTs £5.00 Cmd 800 Chassis, No tuner £20.00 TAG 226/600 50p BD 650 50p UPC 574 30p BSS 38 30p G11 1 I.C. Receiver Panel £1.50 3 I.C. Power Supply G11 Full Remote Receiver Panel £3 Teletext Receiver Model T1 Fits on top of TV with handset. £95 FET Power VN88AF 50p PHILIPS SBC 469 Stereo Microphone £23.00 Meters Hills 520 £17.00 Meters Hills 420 £14.00 Infra-red Tester Handset £12.00 Infra Red Hanset Tester Works at 24 feet - Sound repeater. Works off 9 volt battery Fits in top pocket. £8.00 Repaired Handsets Philips K4-K35, RC5350, RC5300, RC5370, RC5375, repaired same day £10.00 RC4001 Full Remote KT3 K30 Teletext Handsets exchanged £9.00 GEC Full Remote Infra-red, 1983 models £15.00 Timers, 60 mins, small £1.00 G11 Touch Unit Full Remote £13 G11 Ultrasonic Teletext Handset £24.00 8 C.H. Ultrasonic GEC Full Remote C2014H/C2219H £15.00 New Replacement for G11 Ultrasonic Full Remote £12.00 Thorn 4000 insert with 7 buttons £5.00 Decca RC 11 £14.00 Decca RC 12 £14.00 G11 Infra-red full teletext £24.00 Dynatron-Full remote CTV 62, 63, 64 £19.90 Hitachi infra red handset £18 Philips full remote KT3, 16C928/20C934, 7228/7324; K12 26C 797/1ST 66K 1826 £12.00 G11, Full remote top button assy. £12.00 G11, Full remote repair service (exchange unit) £12.00 Philips infra red full remote 9 channel for 60 CP2605 £6.00 Philips infra red full remote 12 channel for 60 CP2605 £12.00 K35 KT3/K30 T/Text £15.00 KT3/K30 Full remote £15.00 KT3 Power supply £4.00 Hitachi 8 button unit with resistor unit. Last year mod. £7.00 GEC infra-red 2236-2025 £4.00 GEC push pad hand set button blobs 10p each Pyc & Philips handset KT3-K30 chassis. No RC5150-RC5176-RC5171-RC5177. Special Price £13.00 ITT Hand Set with TV-Teletext-VCR £12.00 RC4001 KT3 and Teletext £14.00 We have all parts for Philips Handsets	
Speakers 6x4 G11 25 ohm £1.00 5x2x2/2 3 ohm £1.00 5x3 30 ohm 70p 5x3 50 ohm 50p 5x3 35 ohm 70p 6x4 15 ohm £1.00 7x3 70 ohm £1.00 8x5 8 ohm 15 watt £2 8x5 8 ohm £1 5x3 8 ohm 70p 7x3 16 ohm £1.00 5" dia 16 ohm £1.00 5" dia 8 ohm £1.50 6 1/2" dia 4 ohm £1.50 6 1/2" dia 3 ohm £1.50 2 3/4" dia 8 ohm 75p 3" dia 8 ohm 75p 4 1/2" dia 15 ohm £1.00 KT3 speaker K30 75p 3" dia 15 ohm 60p 1690 5x3 12 ohm £1 K45 Philip 15 ohm 75p K30 15 watt £1		Diodes OF-550 10p OF-513 correction 10p OF-557 50p BY 126 10p BY 127 10p BY 133 10p BY 134 10p BY 164 50p BY 176 25p BY 179 40p BY 184 25p BY 187 10p BY 190 40p BY 196 30p BY 198 10p BY 204/4 8p BY 206 8p BY 208/800 8p BY 210/400 5p BY 210/800 10p BY 223 60p BY 224/600: 4.8A/600v bridge 60p BY 226 15p BY 227 15p BY 228 10p BY 229/400 10p BY 237 10p BY 254 10p BY 255 30p BY 298 10p BY 299 10p BY 406 8p BY 527 20p BY 407A 10p BY 527 10p BY 602 10p E 247 10p GP20G 50p XK 3102 5p BYV 28/200 20p 800v/2.75 amps 10p		DISPLAYS 4040 Clock £1.00 7seg Red LED 50p 2 digit LED 8.8 50p 2 digit LED ÷1.8 with panel + MC14511 £1.00 4700/63 £1.50 250/64 10p CVC 20-25-30 Mains Switches Infra Red and Ultrasonic G11 Teletext Decoder Panel £30 RANK & ITT Mains Remote On-Off Switch (720R) £1.50 RANK & ITT Mains Remote Switch 2865 ohm £1.50 RANK & ITT Remote Switch 2800 ohm £1.50 G11 Mains Switch 4 amp Mains Switch 4 amp 25p KT3 Mainswitch 30p THORN Rotary Mains Switch 30p G8 Mains Switch 75p Thyristor 600/4 amp C106/2 24p G11 Preh Red LED P/Button for C.H. Change 24p RANK TOSHIBA Transducers TPC-2011 50p Mains Switch ITT Long Type Print 75p Mains Switch Philip Long Type TAG 75p Mains Switch GEC Long Type TAG 75p Thorn 12 or 24 volt battery converter for portable colour T/V £6.00		KT3-K30 E.W. 10p correction 10p OF-557 50p DIODES BY 126 10p BY 127 10p BY 133 10p BY 134 10p BY 164 50p BY 176 25p BY 179 40p BY 184 25p BY 187 10p BY 190 40p BY 196 30p BY 198 10p BY 204/4 8p BY 206 8p BY 208/800 8p BY 210/400 5p BY 210/800 10p BY 223 60p BY 224/600: 4.8A/600v bridge 60p BY 226 15p BY 227 15p BY 228 10p BY 229/400 10p BY 237 10p BY 254 10p BY 255 30p BY 298 10p BY 299 10p BY 406 8p BY 527 20p BY 407A 10p BY 527 10p BY 602 10p E 247 10p GP20G 50p XK 3102 5p BYV 28/200 20p 800v/2.75 amps 10p International Rectifier EHT Diodes G770/144 6KV 3 for 8p 6A/600V Stud Diodes 20p 6A/1000V Stud Diodes 20p			

SENDZ COMPONENTS

63 Bishopsteignton,
Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE

All items subject to availability.
No Accounts - No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then £1 Postage
Add Postage for overseas

Callers: To shop at 212 London Rd.,
Southend. Tel. 0702-332992

Open 9-1/2.30-6. GVMT + school orders accepted on official
headings add 10% handling charge.

Tuner Units	
G8 6 Button Unit	£9
V/Cap Rank UHF Z776T/Unit	£6
V/Cap Rank VHF Z773T/Unit	£5
NEW G8 Tuner V/Cap	£3.50
T20 6 Push Button Unit	£7
ELC2000 on Panel	£2.50
GEC 6 Push Button Unit	£6
ITT 6 Push Button Unit	£6
DECCA 6 Push Button Unit	£6
GEC or Hitachi 6 push button unit 2110 Conversion	£8
GEC 2110 V/Cap	£5
ELC1043 (Ex Panel)	£3.75
ELC1042	NEW £5.50
ELC2000	NEW £4.00
ELC2004	NEW £8.00
ELC2006	NEW £6.00
GEC Tuner V/Cap Hitachi After 1979 ETS48, ETS47, ETS46, ETS41B	£8.00
ASTEC UM1183	£10.00
V314 (VHF)	£5.00
V317 (VHF)	£5
V334 (VHF)	£5
U321	£6
U341 UHF	£7.00
U342 (UHF)	£5
U411 UHF	£7.00
U.V. 411 Tuner	£10.00
U.V. 415	£7.00
U.V. 417	£7.00
Small V/Cap Mitsumi	£4.00
UHF	£4.00
VHF	£3.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
NSF-UHF/VHF Vancap (old type)	£8.00
Mosfit UHF/VHF (new type)	£8.00
UE2-B31 Fidelity V/Cap T/Unit	£6.00
UHF-VHF V/Caps on panel	£3.00
Thorn Tuner PANEL with 6x100K pots + cursors NO TUNER	£1.00
HITACHI 20 Turn Pot	£4.00
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR Video MTS 900	£2.50
Mullard Video Modulator. Application, video tape recorders, TV cameras, video games, closed circuit TV, C.C.I.R. system. Data supplied.	£10.00
V.T.100 Sound Tuner Kit, TV. Viosound. The latest design in low noise fitted with DNR, RF output and audio	£30.00
Sylvania UHF F4720B	£6.00
Sylvania VHF 900	£6.00
Small Tuner DX 175-220MHz	£4.00

Auto Changeover	£5.00
9000 Thorn Tuner on Panel	£7.00
THORN 1400 4P.B. Mech. Tuner	£5.00
THORN 1500 4P.B. Mech. Tuner	£5.00
THORN 1590 4P.B. Mech. Tuner	£5.00
THORN 3500 4P.B. Mech. Tuner	£5.00
THORN 8000 4P.B. Mech. Tuner	£5.00
THORN 8500 Mech. Tuner All new & boxed.	£4.00 each
Delay Lines DL20A 80p	DL60 £1.00
CR (Old Type)	£1
DL600	£1.00
DL700	£1.00
UDL11	£3.00
KT 3 Lumineux	75p
Lumiance Delay Line (CVC 45)	25p
10x500mA	80p
10x1 amp	80p
Co-Ax Joint	15p
15-A Belling Lee Plug	12p
Co-Ax Splitter	£1.00
UHF Modulator CCR	£3.00
Infra Red Emitting Diode	20p
NE286H Small Neon Lamps GEC & Philips	5p
Mullard 5 Watt Amps. LP1162 New	75p
T.V. Tubes 12" 1110" 31/510 with coils Post £2.50	£5
4.5" tube NEC 120ANB4	£8
12" A31300 Hitachi	£10
15" A38170W Hitachi	£8
18" Hitachi P1L tube with scan coils 470 KCB2-TC03	£25
10" Black and white tube scan coils & line trans	£6.00
Integrated Circuits AC76003	£1.50
AM251-S23PC	10p
BAV40	40p

BT18124	£1.00
BT18224	£1.00
BUP22A	£1.00
CA270AE	50p
CA270CW	50p
CA270CE	50p
CA270W	50p
CA920AE	£1.00
CA1310	50p
CA3046	50p
CA3065Q	50p
CA3094AE	50p
CA3121	50p
CA3146	£1.00
CA3189	40p
CBF16848	40p
CD4510	30p
DM7122	50p
HA1196	40p
HA1370	£2.00
HA11223	40p
HEF4001	10p
HEF4011 AF	10p
HEF4053B	30p
HEF4061	30p
HEF4528	20p
HD3890C	£3.00
K731D 1001012	£1.00
LA3220	50p
LM101IN	£1.00
LM8361	£3.00
M913	£2.00
M1024-SAA	£2.00
M1025-SAA	£2.00
MC476p	£1.00
MC1307	75p
MC1312	£2.00
MC1349	75p
MC1352	50p
MC1358	50p
MC14002	15p
MC14013	25p
MC14016	60p
MC14066	30p
MC14514	80p
MC1748	50p
MEM4956	£1.00
ML2310	£2.00
ET16016	£2.00
ML232	£2.00
ML236E	£1.00
ML237B	£1.00
ML238B	£4.00
ML239	£2.00
ML926	£1.00
MMS587	£1.00
MMS587	£1.00
MMS611	£1.00
MMS840	£3.00
KSS Philips Receiver IC	£3.00
MS84014	£3.00
MMS290N-4	75p
MMS3108N	£4
MR1366	20p
NG4100	£1.00
NE555P	60p
NE555	60p
UPT1031H	£2.00
UPT1353C	£1.00
UPT1363C	£2.75
UPT1366C	£1.00
UPT1514C	£3.00
SAA611	£1.00
SAA661	£1.75
SAA1020	£4.00
SAA1021	£4.00
SAA1024	£2.50
SAA1025	£2.50
SAA1027	£3.00
SAA1074	£3.00
SAA1075	£3.00
SAA1124	£3.00
SAA1174	£3.00
SAA1176	£3.00
SAA1250	£3.00
SAA1251	£4.00
SAA1272	£3.00
SAA1276	£3.00
SAA3027A	£4.00
SAA5010A	£1.50
SAB3013	£2.00
SAB3210	£2.00
SAB4209	£2.00
TBO1124	£1.00
SAA5000A	£1.50
SAA5010	£2.20
SAA5012A	£5.00
SAA5020	£3.50
SAA5030	£5.00
SAA5040	£3.50
SAA5040A	£3.00

SAA5043	£4.00
SAA5050	£3.50
SAF1032p	£2.50
SAF1039	£2.00
SAS550	£2.00
SAS560T	£1.00
SAS570T	£1.00
SAS660	£1.00
SAS670	£1.00
SAS850	75p
SAS550	75p
SAS5210	£2.50
SL437E	£4.00
SL901B	£4.50
SL918	£4.50
TA7122	£1.15
TAA320A	50p
TAA470	£1.50
TAA570	75p
TAA611B	£1.00
TAA621	£2.00
TAA661	£1.00
TAA661	£1.50
TAA705Q	£1.00
TA7117	£1.00
TA7120P	50p
TA7315AP	50p
TA7607AP	40p
TA7609P	50p
TBA120A	40p
TBA120AS	40p
TBA120B	40p
TBA120SB	40p
TBA120T	50p
TBA120SQ	£1.00
TBA120V	75p
TBA120C	40p
TBA1441	£1.00
TBA231	75p
TBA395Q	50p
TBA396	75p
TBA440P	£1.00
TBA1440C	£1.00
TBA480Q	£1.00
TBA1512	£2.00
LM8361	£3.00
TBA540	£2.00
TBA550Q	£1.75
TBA560CQ	£1.00
TBA570	£1.50
TBA625	50p
TBA651	£2.00
TBA651	£2.00
TBA673	£1.00
TBA720A	£1.50
TBA750Q	£1.50
TBA780	£1.50
TBA800	£1.50
TBA810AP	60p
TBA810S	60p
TBA820	60p
TBA890	60p
TBA920	£1.50
TDA120Q	£1.50
TBA950	£2.50
TBA990Q	£1.00
TMS100NL	£2.00
TMS1943 N2L (clockchip)	£1.00
TMS2570	£2.00
TMS9901	£1.00
TMS270RJG45	45p
TMS27161L	£1.00
TMS3529	£1.00
TMS3720ANS	£3.00
TK16014	£1.00
TX-012	£1.00
TMS9902	£1.20
ULN2216	75p
UPC366H	£1.00
NE555P	£1.00
UPT1031H	£2.00
UPT1353C	£1.00
UPT1363C	£2.75
UPT1366C	£1.00
UPT1514C	£3.00
SAA611	£1.00
SAA661	£1.75
UPD8049HC	£2
SN29848	£1.00
SN29770BN	£1.00
SN29771BN	£1.00
SN29772BN	£1.00
SN7402N	£1
SN7472N	£1
SN74107	£1.00
SN74167	70p
SN7472N	20p
SN75108AN	£1.00
SN7601	£1.00
SN7603	£1.00
SN7608	£1.00
SN7603N	£1.50
SN76110N	£1.00
SN76115AN	50p
SN76131	50p
SN76141N	£1.00
SN76226	£1.00
SN76227N	£1.00
SN7628N	£1.00
RGP30G	40p
MPS43A	25p
MJ13005	25p
MJE517	25p
MJE340	25p
SONY IC 109	£3.00

SN76550	30p
SN76552	30p
SN76570	£1.00
SN76620	50p
SN76650	50p
SN76660N	40p
SN76620AN	50p
SN76666	£1.00
SN76705N	£2
SN76707N	75p
SN76708AN	75p
SN76720	£2.00
SN76709N	£2.00
UA783P3C	40p
BT100A/02	40p
BT138/10A	70p
BT146	30p
TBA540Q	£1.50
TCA270	£1.00
TCA270Q	£1.00
TCA660	£1.00
TCA270S	£1.00
TCA270SQ	£1.00
TCA740	£1.00
TCA800	£1.00
TCA830	£1.00
TCEP100	£2.25
TCE120CC	£1.00
TDA440Q	£1.00
TDA1003A	£1.00
TDA1010	£1.00
TDA1012	£1.00
TDA1060A	£1.50
TDA10337	£1.50
TDA1035B	£1.50
TDA1072	£1
TDA1151	30p
TDA1170	£1.00
TDA1190	£1.00
TDA1200	75p
TDA1270	£1.50
TDA1327A	£1.00
TDA1365	£2.00
TDA1512	£3.00
TDA2002	£1.00
TDA2003	£1.50
TDA2004	£2.00
TDA2010	£1.00
TDA2020	£1.00
TDA2030	£2.00
TDA2140	£3.50
TDA2160	£3.00
TDA2320	50p
TDA2525	£1.00
TDA2545A	£1.00
TDA2600	£5.20
TDA2640	£2.00
TDA2650	£1.00
TDA2530	£1.00
TDA2532	£1.00
TDA2540	80p
TDA2541	£1.00
TDA2560	75p
TDA2571AQ	£1.00
TDA2575A	£1.00
TDA2577	£2.00
TDA2579	£2.00
TDA2581	£2.00
TDA2590	£1.00
TDA2591	£1.00
TDA2593	£1.00
TDA2560	50p
TDA2611A	£1.00
TDA2611AQ	£1.00
TDA2615A	£1.00
TDA2632	£2.50
TDA2633	£4.00
TDA2640	£2.00
TDA2680	£1.00
TDA2690	£1.00
TDA3190	£1.00
TDA3560	£4.00
TDA3571Q	£1.50
TDA3590	£3.00
TDA3591	£1.00
TDA3650	£3.50
TDA3651AQ	£3.50
TDA3654Q	£2.00
TDA3710	£3.50
TDA9403	£3.00
TEA1039	£2.00
UPT1353C	£3.00
UPT1363C	£1.50
TDA3300B	£6.00
SN7415 125AN	30p
SN7415 248	30p
SIL4516	50p
SN16862AN	£1.00
SN16862AN	£1.00
SN16964AN	50p
SN29764AN	£1.00
SN76226	40p
SN76227N	40p
SN7628N	40p
RGP30G	40p
MPS43A	25p
MJ13005	25p
MJE517	25p
MJE340	25p
SONY IC 109	£3.00

MJE660	25p
MJE661	25p
MJE3055	£1.00
MJE2801	30p
MJE2955	50p
MJE13005	50p
Sanikron Diode	30p
Philips Cartridges GP412	£6.00
GP412/11	£6.00
GP406	£6.00
Transistors A1222	15p
A1223	15p
AC106	15p
AC121	15p
AC124	15p
AC128	15p
AC137	15p
AC151	15p
AC138	15p
AC152	15p
AC153K	15p
AC142K	15p
AC146	15p
AC176	15p
AC176K	15p
AC178K	15p
AC179	15p
AC186	15p
AC187K	15p
AC188	15p
AC188K	15p
AC188	25p
ACY21	25p
AD143	50p
AD149	50p
AD161/162	pair
AF17A	25p
AF139	25p
AF181	£1.00
AF239	25p
AF367	25p
AL102	£1.75
AU110	£1.50
BC161	30p
BD507	50p
BD509	30p
BD510	30p
BD519	30p
BD534	30p
BD535	30p
BD544D	30p
BD562	30p
BD610	40p
BD646	40p
BD676A	30p
BD678	50p
BD681	25p
BD807	50p
BD826	50p
BD848	30p
BDK75	30p
BDX32	£1.25