

Lyubshin

THREE FOUR PORTABLE

Practical Wireless

9^D
EVERY
MONTH


Vol. 23. No. 492.



Editor: F. J. CAMM



JULY, 1947

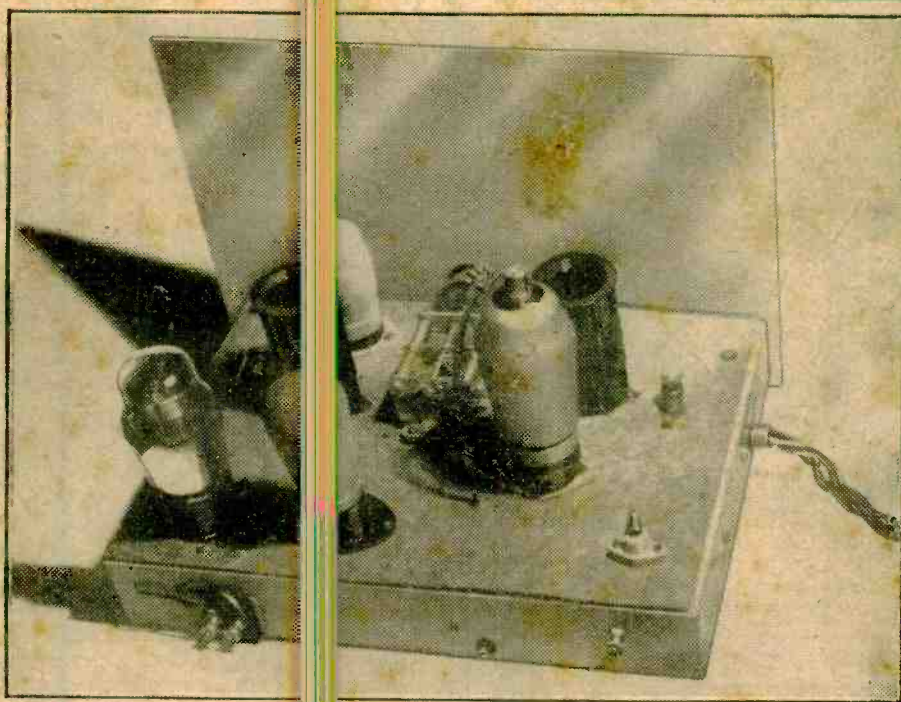

Short-Wave Four—See Page 268

PRINCIPAL CONTENTS

Simple Signal Tracing
Electronic Musical Instrument
Triode Vectors
On the Amateur Bands



Battery Fidelity Circuits
A Quality S.W. Superhet Unit
Transmitting Topics
Trade News

uent, re-
nt, re sol
u or as pa

"LET ME BE YOUR FATHER"

Thus is expressed the friendly, *personal* bond existing between the Bennett College and each student. It is this close individual tuition which leads to quick success. We teach nearly all the Trades and Professions by post in all parts of the world. The most progressive and most successful Correspondence College in the world. If you know what you want to study, write for prospectus. If you are undecided, write for our fatherly advice. It is free.



Distance makes no difference.

EARNING POWER IS A SOUND INVESTMENT

DO ANY OF THESE SUBJECTS INTEREST YOU ?

| | |
|--------------------------------------------------------|-----------------------------------------------------|
| Accountancy Exams. | Mining, Electrical Engineering |
| Advertising and Sales Management | Motor Engineering |
| Agriculture | Municipal and County Engineers |
| A.M.I. Fire E. Exams. | Naval Architecture |
| Applied Mechanics | Novel Writing |
| Auctioneers and Estate Agents | Plastics |
| Aviation (Engineering) | Play Writing |
| (Wireless) | Plumbing |
| Banking | Police, Special Course |
| Blue Prints | Preceptors, College of Press Tool Work |
| Boilers | Production Engineering |
| Book-keeping, Accountancy and Modern Business Methods. | Pumps and Pumping Machinery |
| B.Sc. (Eng.) | Quantity Surveying - Inst. of Quantity |
| Building, Architecture and Clerk of Works | Surveyors' Exams. |
| Builders' Quantities | Radio Service Engineering |
| Cambridge Senior School Certificate | Radio Short Wave |
| Carpentry and Joinery | Road Making and Maintenance |
| Chemistry | Salesmanship, I.S.M.A. |
| Civil Engineering | Sanitation |
| Civil Service | School Attendance Officer |
| All Commercial Subjects | Secretarial Exams. |
| Commercial Art | Sheet Metal Work |
| Common Prelim. E.I.E.B. | Shipbuilding |
| Concrete and Structural Engineering | Shorthand (Pitman's) |
| Draughtsmanship. All Branches | Short-story Writing |
| Engineering. All branches, subjects and examinations | Social Welfare |
| General Education | Speaking in Public |
| G.P.O. Eng. Dept. | Structural Engineering |
| Heating and Ventilating | Surveying |
| Institute of Housing | Teachers of Handicrafts |
| Journalism | Telecommunications (City and Guilds) |
| Languages | Television |
| Mathematics | Transport Inst. Exams, Viewers, Gaugers, Inspectors |
| Matriculation | Weights and Measures Inspector |
| Metallurgy | Welding |
| Mining. All subjects | Wireless, Telegraphy and Telephony |
| | Works Managers |

If you do not see your own requirements above, write to us, on any subject. Full particulars free.

COUPON-CUT THIS OUT



To DEPT. 104, THE BENNETT COLLEGE, LTD., SHEFFIELD.

Please send me (free of charge)

Particulars of (Cross out line
Your private advice which does
about not apply.)

PLEASE WRITE IN BLOCK LETTERS

Name

Address

THIS IS
THE B.B.C HOME
SERVICE...



SATURDAY NIGHT
Theatre Presents.

YOU WILL BE
SITTING IN THE STALLS
IF YOU'RE
USING...

Exide

L.T. ACCUMULATORS

AND

Drydex

H.T. BATTERIES

EDX 6C

The perfect pair for
battery Radio sets

THE CHLORIDE ELECTRICAL STORAGE CO. LTD.
CLIFTON JUNCTION, NR. MANCHESTER

Practical Wireless

15th YEAR
OF ISSUE

EVERY MONTH

VOL. XXIII. No. 492.

JULY, 1947.

and PRACTICAL TELEVISION

Editor F. J. CAMM

COMMENTS OF THE MONTH

BY THE EDITOR

The Fiftieth Milestone

IN April of this year was celebrated the 50th anniversary of the first demonstration of wireless telegraphy by Marconi; for it was in 1901 that Marconi first succeeded in sending signals across the Atlantic from Poldhu in Cornwall to Newfoundland.

Marconi, of course, was a true amateur in that he had few, if any, scientific qualifications. He experimented along the lines laid down by many previous scientific experimenters.

We are surprised that in the celebrations to commemorate the great work of Marconi so many famous names were forgotten. Sir Ambrose Fleming, Edison, de Forest, Sir J. J. Thompson, who discovered the electron, and many others were deserving at least of mention. Some did not even gain a passing reference.

It is true that the real starting point of much of the great achievements in radio science dates from the experiments of Marconi, whose feat was startlingly successful and confounded the critics. It was 20 years later that the existence of the Heavy-side Layer was proved.

It was Sir William Proce who provided Marconi with the necessary facilities and encouragement, and they remained collaborators for many years. In the early days when radio waves were produced by sparks, it was these two collaborators who set themselves the task of finding some other and more satisfactory means, although it was some years before electrons and thermionic valves provided the solution. It was not until the end of the first World War that a revolution in radio took place largely as the result of the experiments and developments which had taken place during that war.

Radio workers then considered that long waves were better than short waves for communicating with the Antipodes. It was largely due to the work of the Marconi engineers that the possibilities of the short waves were examined. They found that although almost useless for short distance work, they could be received thousands of miles away at great strength, and it is only now after 20 years of further experiment that we are really beginning to understand what happens to short radio waves

when they span the great distances between the component parts of our Commonwealth.

A great more, however, has to be done, for television is the inevitable next step, and to-day it is not much more advanced than was radio telephony at the end of the 1914-1918 war. It is true that its problems are perhaps greater notwithstanding the advance of our knowledge of electronics, but certainly the financial difficulties are not so great since we now have a Broadcasting Corporation drawing millions a year from the British public which it can devote to scientific advancement of electronics of which television forms but a small part.

The recording of programmes remains the great problem, but it is not insoluble. Someone may shortly discover the means, notwithstanding the great technical difficulties involved and the wide band of frequencies encompassed, of recording the programmes so that they can be repeated without requiring the presence of the artistes.

A great deal more is known to-day of the science of transmission, so television does at least start off on a firmer foundation than did radio in the days of Whittle, and 2LO. The sightless broadcast must eventually become as obsolete as the silent films.

Then there is the problem of colour television already well on the way to solution. It merely needs practical development. It is worthy of note that a system of television existed 20 years before the close of the last century and it was produced by Nipkow, a Russian, whose experiments were continued, not very successfully, by Baird.

Our Query Service

ONCE again may we remind our readers that our Technical Query Service is suspended and that a notice will appear in this journal when it is re-introduced. This does not apply, of course, to normal queries aroused by articles appearing in these pages.

We also regret that, owing to the absence of technical data relating to the very many items of ex-Service equipment which are now on the market, we are unable to answer queries concerning the modification, use or servicing of such apparatus.

Editorial and Advertisement Offices:
"Practical Wireless," George Newnes, Ltd.,
Tower House, Southampton Street, Strand,
W.C.2. Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for transmission by
Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and in articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

ROUND THE WORLD OF WIRELESS

International Telecommunications Conferences

THE United Kingdom Government has accepted an invitation from the United States Government to send delegations to attend the following international conferences to be held at Atlantic City during the coming summer :

- (1) An International Radiocommunication Conference, which opened on May 15th, for the purpose of revising the International Radiocommunication Regulations, last revised in 1938, including the allocation of the radio frequency spectrum between the various types of wireless service.
- (2) An International High-frequency Broadcasting Conference, to be held immediately following the International Radiocommunication Conference, for the purpose of securing a better regulation of long-distance broadcasting services.
- (3) A Plenipotentiary Conference of the International Telecommunication Union, which will begin on July 1st, for the purpose of drawing up a new International Telecommunication Convention to replace that signed at Madrid in 1932, and framing statutes under which the International Telecommunication Union will enter into relations with the United Nations Organisation.

R.S.G.B. Visits Eddystone's

DURING the morning of Sunday, April 20th, the president, council and regional representatives of the R.S.G.B. inspected the works of Messrs. Stratton & Co., Ltd.

They were then taken on a conducted tour round the various sections of the factory and were greatly interested in the many mechanical and electrical processes involved in the production of modern high quality radio equipment and components.

Following the tour of inspection, they saw a new item, the model "640" amateur communications receiver, an all-British product incorporating the latest methods of manufacture. This receiver has been designed as the result of close collaboration between a number of leading amateurs of wide practical experience.

Then came the presentation to the society (by Mr. Malcolm Laughton, a director of the company) of an Eddystone "640" receiver, for use at the new Headquarters station GB1RS. In preliminary speeches, Mr. A. C. Edwards (G6XJ), commercial manager of Stratton & Co., Ltd., said that many amateurs were on the staff of the company, which devoted much of its business to the needs of the amateur.

Broadcast Receiving Licences

THE following statement shows the approximate number of licences issued during the year ended March 31st, 1947.


| Region | Number |
|----------------------------|------------|
| London Postal | 2,016,000 |
| Home Counties | 1,431,000 |
| Midland | 1,531,000 |
| North Eastern | 1,652,000 |
| North Western | 1,426,000 |
| South Western | 921,000 |
| Welsh and Border | 615,000 |
| <hr/> | |
| Total England and Wales .. | 9,592,000 |
| Scotland | 1,033,000 |
| Northern Ireland | 155,000 |
| <hr/> | |
| Grand total | 10,780,000 |

During March there were 166 prosecutions for operating wireless receiving apparatus without the requisite P.O. licence.

1947 Radio Convention at Bournemouth

A RADIO CONVENTION, organised by the British Institution of Radio Engineers, was held at the Tollard Royal Hotel, Bournemouth, from May 19th to May 23rd, 1947. This was the first post-war event of its kind to be held by the Institution and was an extremely successful function.

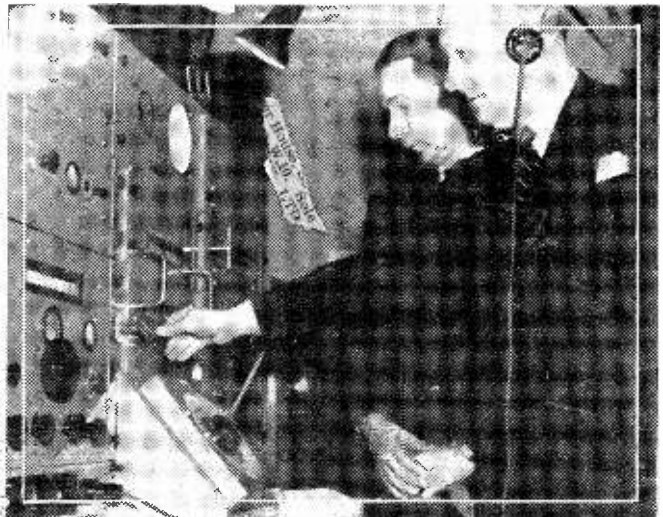The programme included lectures by authors of high repute in the scientific and engineering fields



Sir George H. Nelson recently opened an exhibition in London to commemorate the 50th anniversary of the Marconi Company. In the illustration above, Sir George, on the right, is seen with the Marchesi Giulio Marconi inspecting one of the exhibits.

of the British radio industry, as well as by French authors of equally high standing. The lectures covered a variety of subjects ranging from radio navigational problems to television and other aerials, valves, instruments, wave-guide multi-channel communications and transmitters.



Mr. Laughton presenting the new Eddystone "640" to Mr. Lewer, president of the R.S.G.B.

Another lecture of particular interest will be that on the ever controversial subject "High Fidelity Recording and Reproduction." This also will be accompanied by a series of demonstrations of modern technique developments.

Radiolympia Press Officer

THE Radio Industry Council have secured the services of Mr. Andrew Reid as Press agent.

Mr. Reid was Press Officer of the British Industries Fair for six years and of numerous other trade and public exhibitions before the war, as well as acting all the year round for various national industries. He served in the R.E. (Signals) in France in 1918 and in the Royal Signals from 1940 to 1945. From 1943 he held a General Staff appointment at the War Office.

Until immediately before the exhibition, Mr. Reid will work from his own offices at 11, Garrick Street, W.C.2 (Telephone: Temple Bar 4844), and he will welcome early information from exhibitors about their exhibits.

R.S.G.B. Delegates for Atlantic City

THE President (Mr. S. K. Lewer, B.Sc.) and General Secretary (Mr. John Clarricoats) of the Incorporated Radio Society of Great Britain are attending the World Telecommunications Conference in Atlantic City as representatives of the International Amateur Radio Union.

Their chief duty will be to endeavour to secure for the benefit of all amateurs additional frequencies and other privileges to as great an extent as circum-

stances will permit without endangering present frequencies and regulations.

Mr. George W. Bailey (President of I.A.R.U.) will be chairman of the delegation, and Mr. Kenneth B. Warner (Secretary of the I.A.R.U.) will act as his alternate.

The R.S.G.B. has proposed to the G.P.O. that the following bands of frequency be assigned to British Isles amateurs:

1,715-2,000 kc/s, 3,500-3,800 kc/s, 7,000-7,300 kc/s, 14,000-14,400 kc/s, 21,000-21,500 kc/s, 28,000-30,000 kc/s. Either 50-54 Mc/s or 58.5-60 Mc/s or 66-67.5 Mc/s. 166-170 Mc/s. 220-225 Mc/s, 400-430 Mc/s, 1,200-1,300 Mc/s, 2,300-2,450 Mc/s, 5,600-6,000 Mc/s, 10,000-10,500 Mc/s and 20,500-22,000 Mc/s.

With the exception of the frequencies 1,715-2,000 kc/s and 7,200-7,300 kc/s all allocations to be exclusively for amateurs.

Field-Marshal Montgomery Praises Army Set

IN a message to the Radiocommunication Convention recently, Field-Marshal Lord Montgomery gave high praise to the Army No. 10 Wireless Set, which provided eight telephone channels safe from interruption by the enemy. Lord Montgomery said (*inter alia*): "I have no hesitation in saying that I consider the No. 10 Set to be a very marked and rapid advance in wireless technique. No other army, allied or hostile, possessed equipment equally effective in its role.

"I had considerable personal experience of this Set during the campaign in N.W. Europe, most noticeably perhaps at the



A new radio which incorporates an alarm device and switches itself on at a desired programme. Seen at the B.I.F. and known as the Goblin.

crossing of the Rhine and during the final pursuit through Germany. By using a chain of No. 10 Set stations I was enabled to maintain my Tactical Headquarters as far forward as I did and still have direct contact with London."

The 100,000 ohm potentiometer must be insulated from the chassis and panel unless it is of a type with a neutral spindle. The screen of the R.F. valve will otherwise be shorted to earth.

A small insulated tag is used to support the .02mfd. condenser and 2,000 and 60,000 ohm resistors connected in the detector anode circuit. A second tag can support the long lead from the transformer. All the battery leads are taken to a terminal block secured to the side of the chassis, not shown in Fig. 3. (The cover illustration shows this.)

The insulator marked "X" supports a plate forming a capacity to the chassis, so that the R.F. stage may be trimmed. This will be explained later.

Next month we will deal with the AC/DC version of this receiver. and give operating notes.

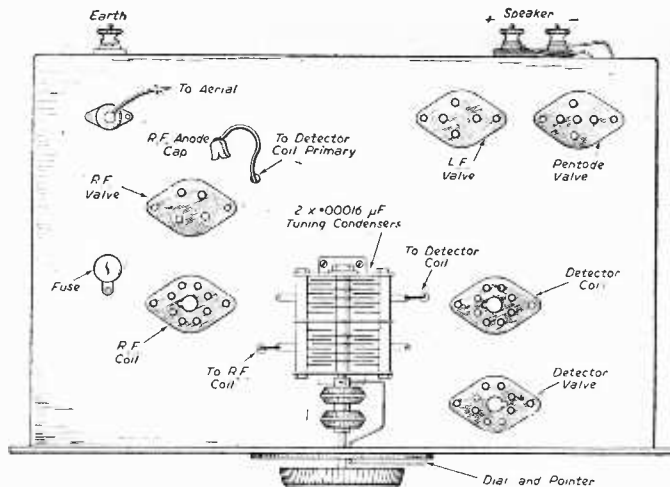


Fig. 2.—Chassis layout details.

New AC/DC Valves

A NEW range of Mullard A.C./D.C. valves to be released later in the year will be fitted with the spigotless version of the B.V.A. Standard Base. The introduction of alternative versions of the standard base is the result of varying manufacturing processes and technique, but the primary objective of interchangeability is nevertheless achieved. One standard socket (which must, of course, be designed to accommodate a spigot in any event to ensure interchangeability) will be used for both versions of the B8A base.


All-glass Valves

The new valves are a logical development of the Mullard all-glass valves (typified by the EF50, which was used in vast quantities during the war for a wide variety of applications). In these valves a flat glass disc, into which are fused rigid metal rods serving both as contact pins and electrode supports, replaces the glass pinch and plastic base. There are no separate leading-in wires with their numerous welded and soldered connections, the length of the lead-in is comparatively short, and the whole assembly is compact and rigid.

Insulation between pins is, of course, much higher than in valves of the "pinch" construction, and as the connections between electrodes and pins are very short, internal capacitances and inductances are greatly reduced. The result is a substantially improved performance at radio frequencies and particularly on short and very short waves.

While retaining all these advantages, the new valves are greatly reduced in size, thus satisfying the demand at home and abroad for small, inexpensive receivers. The new valves are only 22 mm. in diameter, and their length ranges from 66 mm. to 84 mm., according to type. They are fitted with the Standard B8A spigotless base and are used with the one type of socket which is suitable for both B8A versions.

Eight pins are employed and are spaced uniformly around a pitch circle of 11.5 mm. diameter. On account of this uniform spacing of the pins, a locating device is necessary. This takes the form of a small boss on the metal rim of the valve, which fits a corresponding groove in the socket. This is spring loaded and when the valve is pressed home it is effectively secured and cannot work loose or fall out in transit.

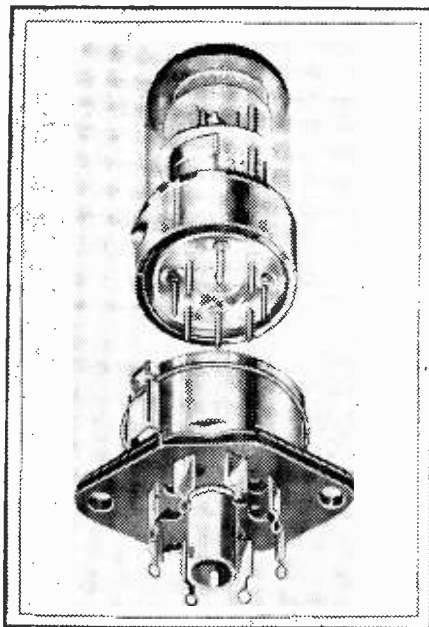

One of the new valves with a typical socket. The peripheral locating boss may be seen on the left of the base.

Simple Signal Tracing

Using Simple Equipment for Servicing Receivers.

By E. N. BRADLEY

WHILST signal tracing is becoming a popular method of fault finding in the servicing of radio receivers, the ready-made equipment used for signal tracing is so expensive to buy commercially, and is advertised in so many ways, that the ordinary radio experimenter is often confused as to the methods commonly used and may think that signal tracing gear is beyond his means. It is the purpose of this article, however, to show that signal tracing can be carried out with a minimum of gear, and, moreover, can be of as great value in the home workshop as it has proved to be in the service laboratory.

As might be expected, signal tracing is performed by tracing a signal through the set under test, the quality and amplification of the signal being observed aurally either in headphones or a loud-speaker, or by an indication given by a measuring



Fig. 1.—Details of the simple signal-tracing prod.

instrument or visual device such as a Magic Eye. The first necessity, of course, is to supply a signal to the set in question in order that it may be traced, so that in some cases commercial tracing equipment contains a signal generator, but a separate generator may be used quite apart from the tracer. A cheaper and quite suitable signal is, however, provided by the B.B.C.—at least for signal tracing in an ordinary receiver! An ordinary radio signal may be applied to the receiver under test, and this signal, first as an R.F. modulated carrier, then as a modulated I.F. carrier, and finally as an audio output, may be inspected in the various stages as satisfactorily as may a signal from a signal generator. It should be said, however, that an efficient aerial should be used, and the strongest local station tuned.

Immediately we see that an all-purpose signal tracer must contain a detector, in order that R.F. and I.F. carriers can pass on their modulated signal to the headphones or other indicator. After detection, too, the signal should be amplified.

The Simplest Method

Before dealing with all-purpose tracers, however, the simplest tracer of any may be mentioned—the

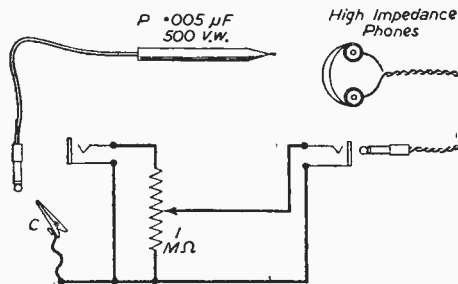


Fig. 2.—A simple audio-frequency tracer.

headphone set. Where a faulty amplifier or gramophone-player is under test, one giving perhaps a distorted output or no output at all, a pair of headphones connected across each stage in turn—not forgetting the pick-up itself—will show at which point in the circuit the distortion is introduced or the signal lost. Having found this, work can be concentrated on this one stage and the fault found with no waste of time and effort.

Headphones cannot be connected directly across a valve circuit without an isolating condenser, however, to block the flow of DC through their coils, and at the same time a test prod is needed in order that connections to various points can be made rapidly. Accordingly, the isolating condenser—a necessity with any type of tracer—and the contact point are combined in the test prod shown in Fig. 1. Even with a small tracer, where the amplification is limited, it pays to screen the whole of the circuit, whilst in a more comprehensive tracer heavy screening is an absolute essential to prevent feedback over the tracer itself, and screening of the prod must be most carefully arranged. The body of the prod may be formed of a bakelite test prod, with the isolating condenser fitted into the tube, the lead from the condenser to the main tracer being well screened and preferably of coaxial cable. The prod lead must be as short as is conveniently possible, for the prod and lead together will present an added capacitance to any tuned circuit and thus change the tuning to some degree, an unfortunate but unavoidable state of affairs. By keeping the lead short and the prod capacitance small, however, the effect on a tuned circuit is minimised.

The capacity of the condenser built into the prod depends on the type of tracing to be performed, but whatever condenser is used the screening of the lead to the prod must be carried on to include also the condenser, a small piece of copper gauze wrapped round the condenser and connected to the lead screen giving excellent protection. A small condenser must be chosen to fit into the prod, of course, and even so it may be necessary to enlarge the central bore, but this is a simple matter.

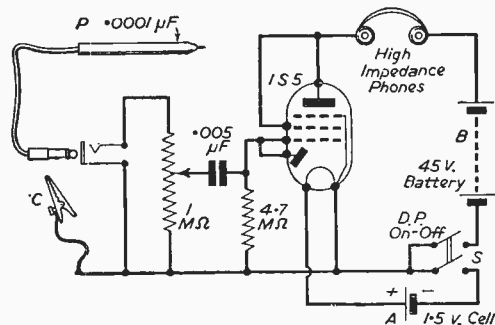


Fig. 3.—This is the circuit of a simple battery-operated tracer for R.F. and A.F.

The prod tip should also be no longer than necessary to give positive contact.

An A.F. Tracer

The prod for the simple tracer shown in Fig. 2 contains a capacitance of 0.005 mfd., since this tracer is designed to deal only with the audio frequencies. It is, indeed, no more than a pair of

being very small and thus fitting into a little space, but three or four grid-bias batteries connected in series to give 27 or 36 volts can be used just as effectively, and will provide a rather cheaper and more easily replaced source of current. The single cell may be of the ordinary small torch type, with connecting leads soldered on to the central brass cap of the positive electrode and the main zinc body

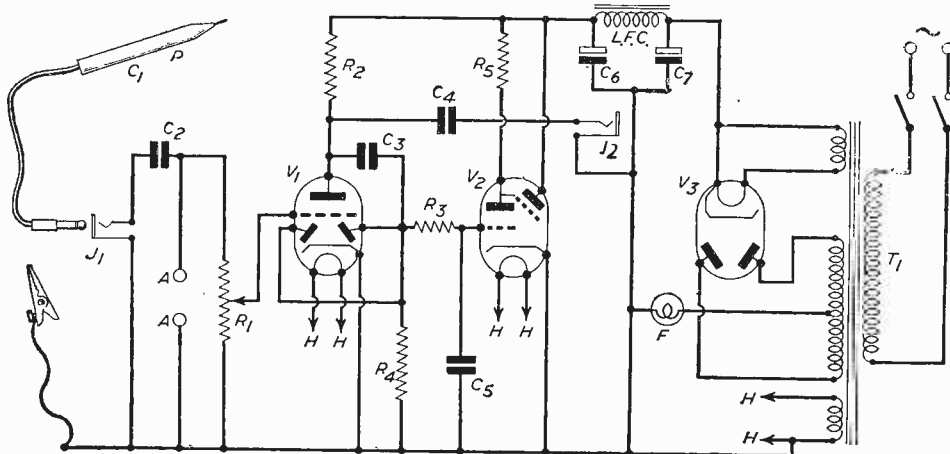


Fig. 4.—Circuit of a multi-purpose, mains-operated signal tracer.

headphones coupled to the isolating condenser via a volume control. The jacks shown in the diagram are by no means essential, but jack connection is a useful asset with most forms of tracer.

One side of the volume control, via the prod, is connected to the "live" side of the audio stage under test—a valve anode, a grid socket or pin, or a transformer terminal, etc.—whilst the circuit is completed through the clip C, which is connected to the chassis and thus gives an earth connection.

For dealing with R.F. and I.F. signals, however, a valve circuit is necessary, and a small tracer designed and used by the author is shown in Fig. 3. In this circuit one of the useful and efficient 1.4-volt filament valves is used, the 1S5, a type which combines a diode detector with an output pentode. Since less than 1 mA. is drawn from the H.T. battery and only 50 mA.s from the single cell which supplies the filament, the whole circuit with its batteries can be contained in a small metal case.

The prod is fitted with a 0.0001 mfd. condenser, and the volume control is isolated from the valve by a further 0.005 mfd. condenser, but even so the tracer can be used on either audio- or high-frequency signals with adequate signal transference in either case. When the prod is applied to a circuit carrying audio-frequency signals the diode has little effect on the working of the tracer, but when the prod is applied to an R.F. or I.F. circuit the signal is demodulated as in an ordinary diode detector, the audio signal voltages are set up across the high resistance to which both grid and diode are coupled, and thus are amplified and passed on to the headphones.

Power Supplies

A layer built type of H.T. battery is sufficient to provide the tiny H.T. current drain, such a battery

of the cell, the soldering operation being carried out as swiftly as possible to prevent heating of the cell's internal elements.

The tracer of Fig. 3 is used in the same manner as that of the previous circuit, the prod being tapped on to the "live" side of the gear under test with the clip C running to the chassis.

Although this type of tracer is capable of excellent work it cannot give an indication when connected to a circuit carrying unmodulated R.F.—for example, it would be difficult to ascertain with such a simple tracer whether or not the oscillator of a super-heterodyne receiver were working. To show the presence of an unmodulated carrier, the best indicating device is almost certainly the "Magic Eye" preceded by a detecting and amplifying stage or stages, and such a tracer is shown in Fig. 4.

Using a "Magic Eye"

In this circuit modulated R.F. is dealt with by the triode section of V1, which is connected as a grid detector, and since the bias applied to the valve is entirely dependent on the magnitude of the applied signal this detector can also be connected, without any change of circuit, to weak or strong straight audio signals. Whether modulated R.F., I.F. or straight audio is applied to the test prod, therefore, the final result is an audio signal in the headphones together with a fluttering of the shadow in the "Magic Eye." The signal is passed on to the diodes of the double-diode-triode and in consequence a direct current flows through R4, creating a voltage drop dependent on the momentary amplitude of the current and thus on the signal amplitude, so that a fluctuating bias is supplied to the control grid of the "Magic Eye."

The "Eye" therefore, may be used to give a comparison of signal strengths, but its main use is in the detection of unmodulated R.F. Such a signal will give no indication in the headphones, but when the prod is connected to the anode of an oscillating circuit, such as an oscillator in a super-heterodyne, the "Eye" will close either partially or completely, giving evidence of a carrier wave which cannot be traced by the use of aural indicators.

The circuit of Fig. 4 may be built using either 4- or 6-volt valves. The latter type will allow the first stage to give rather greater amplification, but there is little to choose in ultimate efficiencies.

COMPONENTS LIST FOR A MULTI-PURPOSE SIGNAL TRACER. Fig. 4.

- C1 (prod)—0.0001 mfd., mica.
 - C2—50 mmfd., silver-mica.
 - C3—0.0003 mfd., mica.
 - C4—0.1 mfd., non-inductive, 500 volt working.
 - C5—0.05 mfd., non-inductive, 350 volt working.
 - C6—16 mfd., electrolytic, 350 volt working.
 - C7—8 mfd., electrolytic, 500 volt working.
 - R1—1 megohm volume control.
 - R2 (for 4-volt operation)—51,000 ohms, 1 watt.
(For 6-volt operation)—220,000 ohms, $\frac{1}{2}$ watt.
 - R3—2.2 megohms, $\frac{1}{2}$ watt.
 - R4—470,000 ohms, $\frac{1}{2}$ watt.
 - R5—1 megohm, $\frac{1}{2}$ watt.
 - L.F.C.—20 henrys, 50 mA.
 - J1—Prod input jack.
 - J2—Headphone jack.
 - F—60 mA. fuse bulb with holder.
 - T1—200-250 volt primary.
250-0-250 v. 50 mA.
4 volt. 2A. 4 volt. 2A.
or 5 volt. 2A. 6 volt 1A.
- For 4-volt operation
- V1—ACHLDD.
 - V2—ME41.
 - V3—UU6.
- 1 British 7-pin chassis mounting valveholder.
 - 2 Mazda Octal chassis mounting valveholder.
- For 6-volt operation.
- V1—6SQ7.
 - V2—Y63.
 - V3—5Y3.
- 3 International Octal chassis mounting valveholders.
- Chassis, screening case, coaxial cable for prod, etc.
Input sockets, A—A.

For greater convenience in the testing of micro-phones and pick-ups, this tracer may have an alternative input point, A.A. Equipment connected here feeds directly into the triode.

Using the Tracer

To use a signal tracer to find faults in a receiver, first ascertain that the faulty set may be switched on with safety. If the power pack is in good order, the set is then put into operation and is tuned either to the strongest local station or to the output from a signal generator. Whether the loudspeaker of the receiver gives signals or not depends on the fault—the set may be right out of commission or may be giving distorted results, or intermittent changes in output amplitude, etc. Whatever the fault, commence signal tracing from the aerial input socket back towards the loudspeaker—that is, in the reverse direction to the generally accepted method of receiver inspection by other test means.

If the signal is strong, connecting the tracer to the aerial may bring in the station, together with other strong signals, but the signal should be heard in the tracer phones when the prod is applied to the first grid of the set—that is, when the prod and clip C are directly across the first tuned circuit. It may be necessary to "rock" the receiver tuning condenser to correct for the extra capacitance introduced by the tracer, but for the simple tracers described here the input signal must be strong for a good result to be obtained with the tracer connected across the first tuned circuit. Placing the prod on the anode of the frequency changer should certainly bring in the signal, however; if not, check the oscillator for correct working, shown by the "Magic Eye" tracer with ease and certainty. Continue to trace through the stages of the receiver, from grids to anodes. If no output from the set is obtained, the stage will rapidly be found where the signal disappears; if intermittent fluctuations or distortion are present these too will rapidly be traced to their sources. A full exposition of the theory and practice of signal tracing would require far more room than can be given to the subject in these pages, but with the circuits and hints given the experimenter will at least be able to build and operate a simple tracer, for, after all, a little practice is worth a great deal of theory.

Film Producer Uses Frequency Modulation

DURING the last couple of years a new battle has been developing in radio circles in the United States, and it is dividing the "hams" and the listening enthusiasts into two camps.

It is the battle of "A.M." v "F.M." It centres around the question whether future broadcasting shall be carried on by the old and trusty method of "amplitude modulation" or whether it shall be replaced by the comparatively new-fangled "frequency modulation."

The trouble is that the whole principle of technique is different, and the adoption of FM in place of AM involves tremendous expense at the transmitting end—practically new stations—and new type receivers at the listening end.

Latest application is in the use of the method of

film-production. FM two-way radio communication was utilised for the first time in photographing a train wreck sequence in David O. Selznick's "Duel in the Sun," at Sonora, California.

The film includes a scene in which a railway train is deliberately wrecked on a mountainside, and this called for close co-operation between various points on particularly difficult terrain. Any interference with communication at a crucial moment could have been both dangerous and expensive.

Application was made to the Federal Communications Commission in Washington, and two experimental licences were issued with the call signs KBPI and KBPK for FM operation on 33.54 Mc/s (8.94 metres). The radio side of the operation was supervised by William V. Stancil, a well-known U.S. radio and electronics engineer.

A Quality S.W. Superhet Unit

Variable Selectivity, R.F. and I.F. Regeneration, Cathode Follower Detector Circuit, and an Original A.V.C. System.
By C. SUMMERFORD

THE "straight" short-wave receiver has, since the start of broadcasting below 100 metres, been deservedly popular, especially with the beginner, on account of its simplicity of construction; and doubtless there are few experienced amateurs who at some time have not built one or more of these receivers.

One of the strongest arguments in favour of the "straight" receiver in the past has been that of low noise level or to put it another way, high signal-to-noise ratio.

This is very true, but (and it is a big but) it falls down badly on the question of selectivity because no matter whether the receiver has one, two, three, or more R.F. stages it will still compare unfavourably with a simple superhet in this respect. As to the signal-to-noise ratio of the superhet being inferior to the "straight" receiver, with modern valves and a properly designed circuit this argument no longer holds.

Most modern short-wave superhets have a single R.F. amplifying stage preceding the frequency changer, and as this does not usually give a high enough signal-to-noise ratio, an add-on unit containing at least two more R.F. stages is generally used. The writer does not favour this method because no matter how good a valve may be, it is bound to introduce a certain amount of noise which may quite possibly be out of proportion to the amount of gain obtained at, say, 10 metres.

Thus it will be seen that if two or more R.F. stages are used, the signal-to-noise ratio will be improved but will still be below that obtainable from a "straight" receiver.

This does not, of course, apply if one of the stages has regeneration. In any case, if regeneration is used before the frequency changer the extra valves are, in the writer's opinion, quite unnecessary.

Owing to the fact that the reception of short-wave stations is rather an erratic business, many constructors do not consider it worth while to build receivers for quality reproduction. But surely, no matter how distorted the signal is at the aerial terminal, it is very poor practice to allow it to be further distorted in its passage through the receiver. Besides there are times when scores of stations can be received at really high quality.

Very well then, our desired receiver is beginning to evolve. The points we have made so far are that we need a high signal-to-noise ratio without the need for an additional R.F. unit, and the ability to reproduce at high quality when required.

Two other items needing special attention are variable selectivity and automatic volume control; and these will be dealt with later.

The Circuit

Fig. 1 is the circuit diagram of a superhet unit covering all of the above requirements which has been designed specially for use with "The 10-watt Quality Amplifier" recently described. It is claimed that this has a signal-to-noise ratio at least as good as the T.R.F. receiver. Of the several frequency changers tried in this circuit, the 6K8 proved to be by far the most efficient, and besides being quiet in operation, it is practically non-microphonic. A most important point this last, especially when using the high selectivity position.

Standard "Eddystone" or similar type four-pin coils are used both for the input and oscillator circuits of this valve.

Tuning is carried out by a 150 mmfd. two-gang variable condenser, and in order to reduce the number of controls, mechanical bandspread has been decided upon in preference to the electrical kind.

LIST OF COMPONENTS

L1. See text.
L2, 3, 4, 5. Standard Eddystone four-pin coils.
Ch. 1. Any good quality short-wave choke.
Ch. 2. Wearite P A.F. coil.
I.F. 1. Bulgin C51.
I.F. 2 and 3. Bulgin C50.
C1, 2, 4, 5, 6, 8, 9, 11, 12, 13. .01 mfd. 350 volt mica.
C3. .00005 mica.
C7, C13. .001 mfd. mica.
C10. .05 mfd. tubular.
C14. .1 mfd. tubular.
C15, 16. .0003 mfd. mica.
C17. .0001 mfd. mica.
R1, R13. 1,000 ohms $\frac{1}{2}$ watt.
R2, 5, 8, 10. 5,000 ohms $\frac{1}{2}$ watt.
R3. .25 megohm $\frac{1}{2}$ watt.
R4. 40,000 ohms 1 watt.
R6. 30,000 ohms 1 watt.
R7. 350 ohms $\frac{1}{2}$ watt.
R9. 100,000 ohms $\frac{1}{2}$ watt.
R11. 90,000 ohms 1 watt.

R12. 325 ohms $\frac{1}{2}$ watt.
R14. 500 ohms $\frac{1}{2}$ watt.
R15. 10,000 ohms $\frac{1}{2}$ watt.
R16. 50,000 ohms $\frac{1}{2}$ watt.
R17. .5 megohm $\frac{1}{2}$ watt.
VR1. 10,000 ohms carbon type vol. control.
VR2. 10,000 ohms wire wound vol. control.
Sw. 1. Single pole three-way switch.
Sw. 2. Single pole toggle switch.
VC1, VC3, VC7. 150 mmfd.
VC2. 25 mmfd.
VC4. 25 mmfd., trimmer type.
VC5. 40 mmfd.
VC6. 250 mmfd.
TC1. 20 mmfd., trimmer type.

VALVES

V1. 6CS.
V2. 6K8.
V3. EF39.
V4. 6CS.
V5. 6H6.

VC4 is the oscillator trimmer condenser and is a preset of 25 mmfd., while VC2 is the first detector trimmer, and this takes the form of a 25 mmfd. variable which is panel controlled by a slow-motion drive having a reduction ratio of 9 : 1.

Preceding the 6K8 is a 6C5, which serves the dual purpose of reactor and A.V.C. controlled valve.

Several ways of applying regeneration to the input circuit of the 6K8 were tried before the use of a separate valve was decided upon; and even then capacity control was out of the question on account of the rather large tuning shift that takes place with this form of regeneration at the higher frequencies.

The cathode-controlled system shown in the diagram is quiet in operation, comes up to the oscillation point smoothly, and does not shift the tuning to any appreciable extent.

An inductance (Ch.1) inserted in the cathode return circuit of V1 is shunted by a variable resistance (VR1), a variation of which alters the input resistance of V1. As VR1 is increased, a point is reached, eventually, at which oscillation takes place. This is when the input resistance changes from positive to negative.

Ch.1 can be any good short-wave choke (the writer uses one of the Eddystone skeleton type), and VR1 is a carbon type potentiometer used as a variable resistance. In order that regeneration shall be smooth throughout the range to be covered, a small postage-stamp type trimmer (TC1) is included as shown, to reinforce the grid/cathode capacity of the valve. This will probably have to be slackened off until it is almost completely open, as a capacity of about 5 mmfd. is all that is usually required.

The grid-leak of the 6C5 has its earthy end taken to the A.V.C. line, and a switch (Sw.2) is wired in at the junction of this and the A.V.C. filter so that the A.V.C. may be switched in or out as required.

A minimum bias of about 7 volts is given to the 6C5 by R1, and this is by-passed in the usual way by C2.

Eliminating Deadspots

As there is no R.F. stage to act as buffer between aerial and frequency changer, we must find some other way to eliminate deadspots. This takes the form of a switched, tuned inductance (L1, Sw.1, VC7) inserted between the aerial and primary winding of the input circuit.

L1 consists of 50 turns of 22-gauge D.S.C. wire wound on a 1½ in. former, adjacent turns spaced by the thickness of the wire and tapped at six and 20 turns. The tuning condenser capacity is not critical and can be anything from 100 mmfds. upwards.

Due to the fact that the efficiency of the R.F. circuits is of very great importance in a good short-wave receiver, we have dealt with this at some length; however, we will now turn our attention to the remainder of the circuit.

Although it is becoming increasingly fashionable to have an intermediate frequency of 1,600 kc/s. such a high I.F. makes tracking of the input and oscillator tuning rather more difficult, especially so in a circuit such as this one when we have "sharp" tuning at the first detector. Furthermore, good selectivity is much more difficult to obtain.

An I.F. of 465 kc/s has therefore been chosen for this receiver. This makes tracking much easier

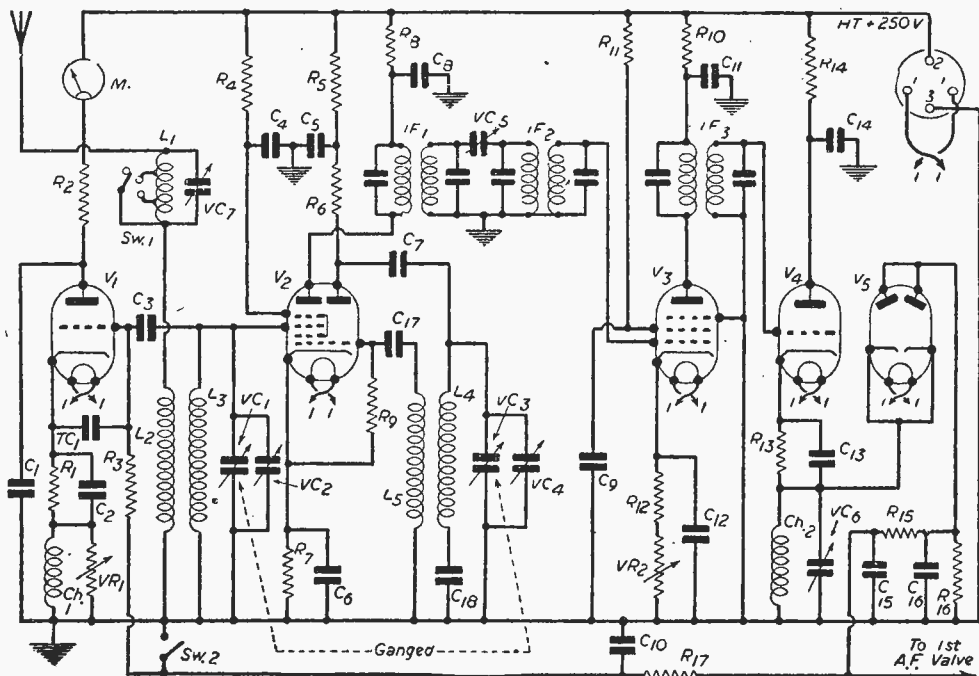


Fig. 1.—Theoretical circuit of the Superhet Unit. The 4-pin plug on the right is for connection to an amplifier—preferably the 10-watt Quality Unit described in these pages recently.

and gives us good selectivity. In order that selectivity may be variable, two I.F. transformers are used between the frequency changer and intermediate frequency amplifier, and these are connected back to back, coupling between them being by a 40 mmfd. variable condenser. A further I.F. transformer couples the EF39 to the 6C5 cathode follower.

All transformers are of the air-cored type made by Bulgin; I.F.1 is Cat. No. C51 and I.F.s 2 and 3 Cat. No. C50.

Some increase in gain could be obtained by using iron-cored I.F. transformers. There is a possibility that the receiver would be more stable. In series with the cathode resistor of the EF39 is a variable resistance of 10,000 ohms which is used as an I.F. gain control.

D.C. Load

One of the biggest problems with the ordinary diode detector is the difficulty of obtaining a reasonable ratio of A.C. load impedance to D.C. load resistance.

With most receivers the D.C. load resistance is kept fairly high and the ratio rarely exceeds 0.7, a figure which means that distortion is bound to be present on deep modulation.

By dropping the D.C. load resistance to 100,000 ohms or less, the handling capabilities are greatly increased. But if this is done the input impedance of the detector drops to rather less than 50,000 ohms and heavily damps the input circuit with consequent reduction of both sensitivity and selectivity. The undistorted output of the I.F. amplifier valve is also reduced.

All of these disadvantages may be overcome by feeding the diode from a cathode follower as shown in the diagram.

The output impedance of this valve measured at Ch. 2 is somewhere around 500 ohms, a value that is so small, relative to the probable detector input impedance, that the latter becomes more or less unimportant.

We can now make the detector load resistance 50,000 ohms without impairing selectivity, and if a value of .5 megohm is chosen for both the A.V.C. filter resistor and the grid-leak of the first A.F. valve, the A.C. to D.C. ratio rises to slightly more than 0.9. The cathode impedance Ch. 2 has an inductance of about 1,000 μ H and a Wearite type P A.F. coil is quite suitable in this position. If this is shunted, as shown, by a variable condenser (and this should have a maximum capacity of not more than 200 mmfds.) regeneration is obtainable at I.F.

A.V.C. Arrangement

Really good A.V.C. is usually rather difficult to obtain in a receiver of this nature, but in this circuit a somewhat original kind is used which has proved most effective.

Control of the frequency changer and I.F. amplifier was tried at first both by the delayed and non-delayed method, but was discarded for the following reasons: Tuning shift with variation in signal strength, poor control, cross modulation caused by overloading of the frequency changer on strong signals.

Finally, it was decided to apply simple A.V.C. to the grid of the R.F. reactor valve only.

In case there are any readers who think that control of one valve cannot possibly be effective, I would hasten to point out that with this receiver R3 signals produce practically the same aural output as those of a strength of R8, and even R9 plus signals are "held down" to reasonable strength.

The system is very simple really, and all that happens is that the A.V.C. takes the input circuit either up to, or away from, oscillation point as it follows signal variations. Naturally, the more critical the setting of VR1 the more effective will be the A.V.C. By installing a panel-mounted milliammeter between R2 and maximum H.T. we have a combined tuning indicator and "S" meter.

As the circuit stands, excellent regeneration is obtainable from 9 to 80 metres, but if it is desired to extend the range to take in the 160-metre band, a further variable resistance of 50,000 ohms must be wired in series with VR1 and the latter may then be used as a vernier control.

Unmodulated C.W. "fans" doubtless think that, due to the fact that no B.F.O. valve is used, their "pet" signals are not receivable with this unit. However, by fitting a slow-motion control to VC6 we can make V4 gently oscillate and give us a modulated signal of a pitch dependent on the setting of this control.

We now have a simply constructed receiver having the following refinements: A tuned aerial system, variable selectivity, R.F. and I.F. regeneration, efficient A.V.C., B.F.O. without an extra valve, and almost distortionless detection.

Adjustment follows normal superhet practice and calls for little comment; and although a modulated test oscillator is very helpful, especially for aligning the I.F.s, it is not absolutely essential. The oscillator trimming condenser (mounted on VC3) should be set "half in" and the small discrepancies in the ganging can then be "taken up" by panel operated VC2.

Operation

To operate the receiver it is recommended that with VC5 and VR2 at maximum and VC6 and VR1 at minimum settings, the required band should first be located and the ganged condenser tuned to the high frequency end, after which the wave-trap circuit (L1, VC7, Sw.1) should be adjusted for maximum gain.

Tune to a clear space between stations at the H.F. end, increase VR and at the same time slowly swing VC2 until there is almost oscillation, re-tune to bring in the first station in the band and adjust VC2 until a minimum reading is reached on the tuning indicator. Ganging will now "hold" over the entire band.

The settings of VC5, VC6 and VR2 are adjusted to suit the prevailing reception conditions.

Incidentally, the milliammeter tuning indicator can be used for accurately adjusting the I.F.s in the same way as described for the R.F. circuits, i.e., by adjusting for minimum reading.

The DX capabilities of this receiver have been thoroughly tested and in this respect can be said to be really exceptional.

Selectivity is completely adequate, and quality of the production, when using the least selective position and given decent conditions, is excellent.



ON YOUR WAVELENGTH

By THERMION

H. G. Wells and Radio activity

ONE of Mr. H. G. Wells's forecasts has not only been fulfilled, but it is particularly appropriate to the year of his death. I knew him intimately, and the last occasion on which he made a public appearance was at the Roadfarers' Luncheon at which he made a typically Wellsian and witty speech. The forecast to which I refer appeared in his book, first published in 1913, entitled "The World Set Free," and in it he foretold that in 1933 artificial radioactivity would for the first time be produced. It was in 1933 to the very year that Irene Curie and her husband, Professor Joliot, made their joint discovery. Production of radioactive substances was, of course, largely a wartime development of research on the atom. It is because greatly increased supplies of these substances will shortly be available, and because of the danger which attaches to any form of intense radioactivity that the Government is now seeking power to control their distribution. Their main use is, of course, in medicine and research, and it was these two uses which stimulated H. G. Wells's imagination in the latter years of his life.

It is not generally known that H. G. Wells was really a man of science as well as a writer of scientific fiction. As a lad, when he lived in Windsor, and became a draper's assistant to Rogers and Denyer in the High Street, he was extremely interested in the discoveries of Hertz and others who paved the way for the Marconi experiments, leading up to that epoch-making day in 1901 when Marconi transmitted from Poldhu in Cornwall to Newfoundland the first radio signal consisting of three dots. Much has been done since those days. He was greatly interested in radio and a keen listener as well as a critic. As far as I can recollect he did not appear before the microphone. He had not a microphone voice; it was high pitched, although I preferred it to some of the cacophonous voices we hear over the microphone to-day, and particularly in the Brains Trust.

Chatting to him one day in his flat, he told me of the enormous amount of trouble he took to get his scientific facts right. On the question of radio he consulted scientific experts who read through his manuscripts to make quite sure that the fiction did not transcend the bounds of feasibility. I hope these facts emerge when his biographer produces the life story of the greatest writer of our time.

Cheaper Television Coming

ONE of the interesting exhibits at the British Industries Fair were the high-quality, yet cheap, plastic lenses which can be made at a fraction of the cost of glass ones. It is claimed that they are specially suitable for television, and should materially assist in bringing television

within the means of all—that is to say, when the country is linked by chains of television transmitters, and the troubles with the coaxial cables have been overcome. These lenses are of the new plastic, and one firm demonstrated their use in television projection. This system, which was originally designed by Schmidt, consists of a large-aperture concave mirror which projects light from a cathode-ray tube. An aspheric corrector plate is employed to correct spherical aberration. The type demonstrated takes a 3½ in. projection cathode-ray tube, and gives a magnification of 7½ times. I have always thought that the large cathode-ray tube was but a passing phase in television development, and that the real answer is the use of a small tube and a system of optical projections. There is no danger of an implosion as there is with a large tube.

The Radio Scientists

SIR EDWARD APPLETON was in witty vein when he replied to the toast of the Radio Scientists at the dinner to commemorate the fiftieth anniversary of the first demonstration of wireless telegraphy. He said that many thought that the gift of wireless was specially vouchsafed to mankind for the primary benefit of the British Empire! In return for such a benefaction it can in justice be said that this country has played a great part in its amazing development. I do not, however, support Sir Edward when he says that the starting-point of this achievement was the work of Marconi. Marconi was a link only, and I object to the tendency of some people to give Marconi proprietorial rights in radio. But for the work of previous experimenters Marconi could not have conducted his own tests. Too little is heard of the work of Sir Ambrose Fleming, who invented the thermionic valve, Dr. Lee De Forest and Edison, who discovered the Edison Effect.

How "Song Hits" Are Made

Tom Trombone, leader of dance band,
Sat down and wrote a letter
To song publishers. Said No, thanks,
For I can do much better.
I'm out to make the most I can,
So kindly get this right,
Unless you care to raise your fee
My boys won't plug your tripe.
But raise your price and we'll respond,
Your song we'll take in hand,
And soon its tune most popular
Will be in all the land,
We'll plug it morning, noon and night,
And listeners educate
To think it really is supreme,
As we so boldly state. . . .
The firm agreed to Tom's demand,
A larger fee was paid,
The song, in spite of tortured ears,
Quite popular (?) was made.
And this is how this game is played,
In spite of B.B.C.,
But then, of course, "None are so blind
As those who will not see."—"TORCH."

Electronic Musical Instruments-1

Practical Experiments in This Interesting Field of Development

By F. C. BLAKE

QUITE a large number of readers have shown considerable interest in recent articles on the electronic organ. In the Novachord the fundamental principle of operation is a master oscillator for each note of the highest octave, followed by a number of frequency dividers for succeeding lower octaves.

This instrument has a special feature which places it in a group separate from the normal electronic organ. This feature is the great

dentally whilst experimenting in the laboratory. An ordinary choke or even an L.F. transformer may be used, the inductance, however, should not be too high.

The frequency is adjusted by the size of the condensers, one of which may be preset, or the grid leak may be a variable. The value of the cathode resistor is best found by experiment; it should be just high enough to stabilise oscillation. Too low a value causes a badly distorted waveform, and frequency drift.

We now come to the dividers. Instead of using valves, which, apart from their cost, would need filament supplies, I intend to show how one may use the common or garden neon lamp. These lamps may be obtained from The General Electric Company, of Kingsway, London, and it is very important to note that they must be ordered *without* the usual series resistance. The lamps are described as .5 watt indicator lamps with S.B.C. contacts.

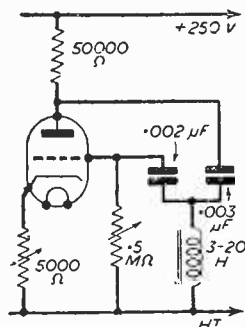


Fig. 1.—Basic form of valve oscillator.

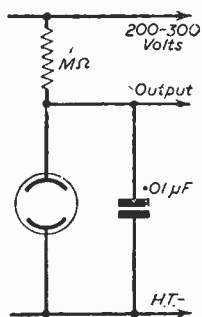


Fig. 2.—Neon relaxation oscillator.

flexibility of control of the sound "envelope," by which means, coupled with tonal variations, effects similar to plucked strings, bowed strings, bell-like chimes, and normal organ sounds may be produced.

To the would-be constructor of an electronic musical instrument I would like to point out that there are several avenues of exploration which are specially suitable for experiments. In this article are described details for the construction of an experimental instrument, utilising the frequency divider system somewhat similar to that used in the Novachord and Solovox. These instruments are manufactured by the makers of the Hammond organ.

The Basic Circuit

Twelve valve oscillators are required operating at the highest octave frequencies, one of which is shown in basic form in Fig. 1.

As far as I know this is a new form of oscillator, which I discovered acci-

Neons as Oscillators

Probably readers are aware of the fact that neon lamps can be used as relaxation oscillators and sawtooth waveform generators, as shown in Fig. 2.

If a synchronising signal is impressed on the D.C. potential, it is possible to lock the oscillator either to that signal or to a submultiple of it. By taking the output from what I shall term the cathode electrode, only the resultant "divided" frequency is obtained.

Fig. 3 shows circuit of master oscillator and neon dividers for three octaves. The dividers are locked by adjusting the voltage to each neon by means of a potentiometer. The adjustment is fairly critical

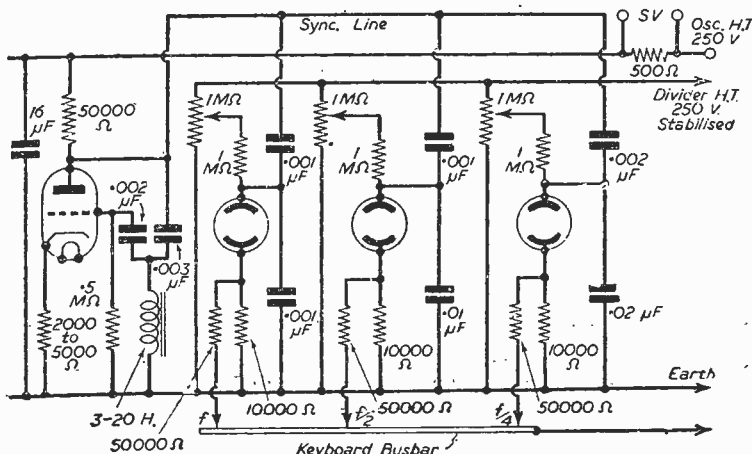


Fig. 3.—Master oscillator and neon dividers for three octaves.

especially when dividing the frequency more than twice. If a large compass instrument is to be built it will be necessary to use 12 amplifier valves boosting the neon outputs, and then, by feeding this series of amplified signals to further dividers, obtaining further tones of f8 and f16.

The locking potentiometers should be set in the

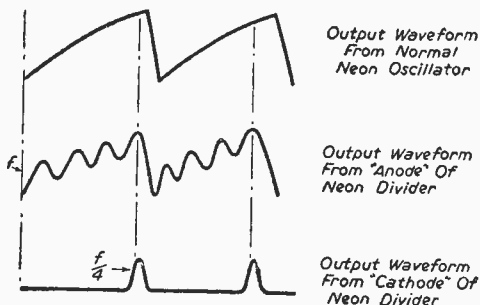


Fig. 4.—Waveforms of neon oscillator and dividers.

centre position of two unstable positions which is found by rocking the control slightly to left and right. Incidentally, I have succeeded in dividing down to $\frac{f}{24}$ that is, when using, say, a 1,000 cycle signal, obtaining an output frequency of 42 cycles approximately. Fig. 4 shows waveforms of neon oscillator and dividers as shown on an oscilloscope.

So that the output from dividers and master oscillators shall be approximately the same in voltage and harmonic content, it is best to use a neon working at the fundamental frequency, and extract the output from the "cathode," rather than tap the output direct from the master oscillator.

The H.T. supplies to the master oscillators and dividers should be separate, and it is advisable to stabilise the voltage by means of stabilising neons.

It is not necessary to use S.B.C. lampholders for the neons, the simplest method of fixing is to wrap insulating tape round the brass cap to bring its diameter a little larger than the bulb, and fix to chassis or metal coated baseboard by means of a saddle clip. The neons should be screened from any extraneous light, as this would impair the stability, as light falling on the electrodes alters the striking potential.

The Keyboard

The outputs from the dividers are selected by the keyboard, which can be made as described in the April issue, from an old piano or harmonium. One pair of contacts are needed per note, one of which forms the busbar shown in the diagrams.

The contacts, if possible, should make with a wiping action, otherwise trouble may be experienced after a time due to faulty contacts.

If the output from the neons were fed directly

into an amplifier, the resultant reedy tones would quickly become monotonous, so that some form of tonal correction is needed. The method usually used in an instrument of this type is shown in Fig. 5 and consists of a series of tuned circuits in series which can be switched in and out or modified at will by means of controls or stop switches.

Should a vibrato stop be required to enhance the tones still further, it can be provided by arranging a simple switching device which makes and breaks S.V. Fig. 3. This causes the master oscillator line voltage to fluctuate, which causes a slight variation in frequency.

A small electric motor operating a cam switch at a speed from 5-10 c/s. is needed, and this can also provide a tremolo stop by arranging another similar cam to switch S.T. Fig. 5. Where component values are not given it should be understood that these are best found by experiment, as they will depend on the inductances used.

With the vibrato stop the periodic frequency variation is transmitted to the dividers, but care should be taken not to have too "heavy" a vibrato, otherwise the dividers would not cope with it.

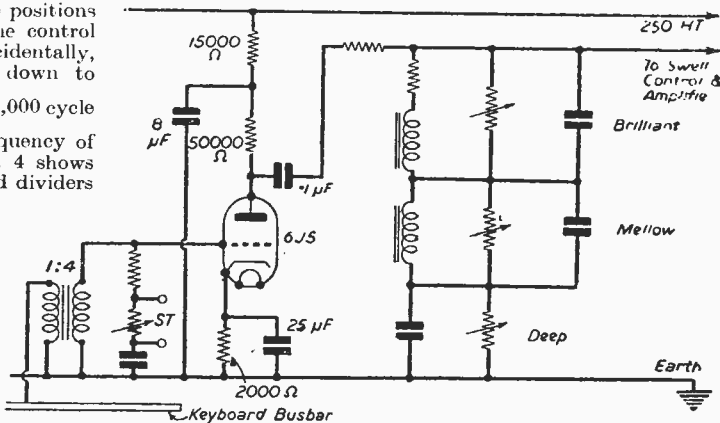


Fig. 5.—Tone correctors in an oscillator stage.

The output from the tone corrector stage is taken via a volume control or swell to the main amplifier. This can be anything from a domestic radio set to a high-power P.A. amplifier.

Another method of generating tones electronically will be described in the next issue.

NOW AVAILABLE

METRIC & DECIMAL TABLES

By F. J. CANN

3/6, or 4/- by post from

GEORGE NEWNES LTD., Tower House, Southampton Street, Strand, London, W.C.2

Notes from the Trade

Philco's New Car Receiver

PHILCO announce a new car radio for 1947, known as Model K.526.

Tested on a number of leading makes of post-war cars, this new Philco has met with all-round approval. Although suppression equipment, consisting of one distributor head suppressor and a condenser on the coil, has been fitted, reports from British motor-car manufacturers give evidence that the suppression equipment could be dispensed with.

The set is priced at £21, plus £4 18s. 3d. purchase tax.

Types: Model K.526T requires a 12-volt battery; Model K.526S requires a 6-volt battery.

W/B Speakers

W/B Stentorian cabinet loudspeakers, in senior and junior models, are now available.

The Senior Model has:

Cabinet: Width, 14½ in. Height, 12 9/16 in. Depth, 7 in.

Speaker: 9 in. diameter. Diecast chassis. Handling capacity, 7 watts.

Magnet: Flux density, 12,000 lines/sq. cm. Total flux, 47,400 lines.

Price: Type SC (with universal transformer), £5 15s. 6d. Type SX (less universal transformer), £5 2s. 6d.


The Junior Model has:

Cabinet: Width, 13½ in. Height, 11½ in. Depth, 6½ in.

Speaker: 8 in. diameter. Diecast chassis. Handling capacity, 6 watts.

Magnet: Flux density, 10,000 lines/sq. cm. Total flux, 39,500 lines.

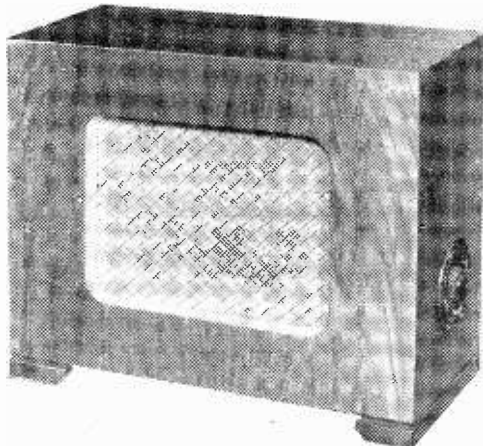
Price: Type JC (with universal transformer), £5. Type JX (less universal transformer), £4 10s. 6d.



This illustration shows the neat appearance of the new W/B cabinet speakers.

Thrush C.R. Bridge

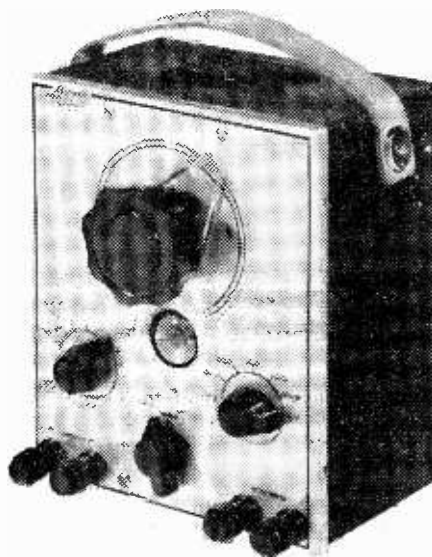UTILISING a standard Wheatstone bridge circuit, this Tester enables condensers and resistances to be measured with an accuracy over the major portion of the scale to within two per cent. The instrument is for A.C. mains operation and utilises a two-section neon indicator so that, in addition to normal readings of capacity and resist-



The Thrush C.R. Bridge. The case is of steel—black crackle finished, the panel is of silvered aluminium, and the leather handle is detachable.

ance, it is also possible to provide a Leakage indicator for capacities rated for operation at 150 volts D.C. and over. Separate terminals are provided for capacity and resistance, and a matching position is provided on the range selector switch so that it is possible to provide an external standard in place of the built-in unit. Then, by placing a standard at one pair of terminals various similar components (including inductances) may be placed at the other pair and values balanced. Ranges are as follows: Capacity 5-5,000 pF; .0005-.5μF and .05-50μF. Resistances, 5-5,000Ω; 500Ω-.5MΩ and 50kΩ-50MΩ. Power Factors up to 60 per cent. may be obtained on a separate control, and this component incorporates the on/off switch for the instrument. The main dial is calibrated from .05 to 50, and our only criticism is that as this follows a log law the higher ranges are rather cramped, but readings are sufficiently accurate for all normal purposes and come within the usual makers' tolerances. The case is finished in black crackle steel and the panel is silvered. The total weight is only 4½ lbs. and the overall size 8 in. by 6½ in. by 4 in. The price is 13½ guineas, and the makers Thrush Radio and Electrical Industries, 1, St. Thomas's Square, E.9.

RADIO IN EVERY ROOM


with these
**NEW & BETTER
EXTENSION SPEAKERS**

Are you enjoying the pleasure and convenience of having your radio instantly available in any room. These moderately priced Stentorian extension speakers, with their handsome acoustically designed wooden cabinets, give such superb quality of reproduction that you will be amazed at the difference a Stentorian makes to your receiver. Ask your dealer for a demonstration.



SENIOR MODEL
Type SC with Universal Transformer £5.15.6
SX minus £5.2.6
Walnut Veneered Wooden Cabinet. P.M. Unit
9in. diameter. Handling capacity 7 watts.
MAGNET Flux density 12,000 lines/sq.cm.

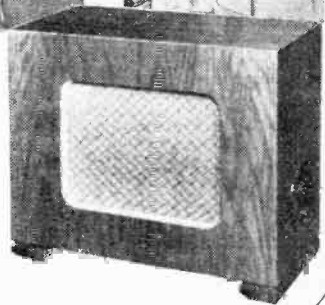JUNIOR MODEL
Type JC with Universal Transformer £5.0.0
JX minus £4.10.6
Walnut Veneered Wooden Cabinet. P.M. Unit
8in. diameter. Handling capacity 6 watts.
MAGNET Flux density 10,000 lines/sq. cm.



Stentorian

THE FINEST EXTRA SPEAKER FOR ANY SET

WHITELEY ELECTRICAL RADIO CO. LTD., MANSFIELD, NOTTS.



*Products of
Quality & Reliability*

**MAINS TRANSFORMERS
A. F. TRANSFORMERS
SMOOTHING CHOKES
THERMAL
DELAY SWITCHES
POWER RESISTANCES**

Made by

OLIVER PELL CONTROL LTD

Telephone - WOOLWICH 1422
CAMBRIDGE ROW - WOOLWICH S E 18

Manufacturers
SPECIFY IT BECAUSE IT IS
THE FINEST CORED SOLDER
IN THE WORLD

**MULTICORE
SOLDER**

FOR RADIO ELECTRICAL MOTOR
AND ALL HOUSEHOLD PURPOSES

CONTAINS 3 CORES
OF FLUX

NO EXTRA
FLUX REQUIRED

You
WILL PREFER TO USE
IT BECAUSE IT MAKES
PRECISION SOLDERING
SO SIMPLE

SPECIAL
HANDY CARTON

6^D
ENOUGH FOR
200 AVERAGE
JOINTS

MULTICORE SOLDERS LTD., MBLIER HOUSE, ALBEMARLE STREET, LONDON, W.1

CLYDESDALE

The Radioman's Shop

for Ex-Government Surplus Bargains in New and slightly used Radio Equipments

Call, Phone or Write for Our New Illustrated List (in preparation) Now
BRAND NEW EX-AMERICAN AIRCRAFT RADIO RECEIVER ONLY each. 42/6

Receiving and Carriage 7/6 extra.
 No. CWS43AA4 24 v. Input. I.F.F. Receiver Transmitter. Frequency 158 to 186 mcs. 10 Valves supplied. 2 off 793 (TX). 2 off 646 metal. 6 off 6SH7 metal. Pioneer Dynamotor, using Carbon Pile Voltage Regulator. Input 18 v. H.T. output 450 v. also operates switched tuning. Plus a host of V.H.F. components, relays, condensers, resistors, 1 to 150 w., etc. Also No. C'ZRR3AAX 12 v. Input, same as above. Dynamotor. Input 9 v. Available at same price, both finished black crackle. Size 12 1/2 in. x 12 in. x 8 in. approximately.

EX-R.A.F. R.1124A POWER UNIT OUR PRICE 12/11 ONLY each.

Carriage and Packing 5/- extra.
 Type 320. 24 volts input. Permanent Magnet type Motor Generator, with smoothing equipment and stabilised H.T. voltage. V.S. 110 Neon Stabiliser. Output H.T. 200 volts 50 m.a. L.T. 15 volts 1.8 amps. 5,000 r.p.m. Housed in Metal Case. 13 1/2 in. x 7 1/2 in. x 5 1/2 in. Weight 17 lbs. Slightly used, good condition.

WE ARE YOUR "EDDYSTONE" AGENTS

Full range of Short Wave Components always in Stock. **2/9**
 Eddystone S.W. Manual No. 5, with supplementary data. post free.

CIRCUITS AVAILABLE

M.C.R.1.—Midget Receiver Circuit, diagram with circuits of suitable A.C./D.C. Mains Units and other useful data. 2/9 per set, post free.
 R1116'A—Receiver Circuit, 5 diagrams with parts list. Price 2/3 per set, post free.


T1154—Transmitter Circuit diagrams for Models A to M, with parts list and other useful data. Price 2/3 per set, post free.

R1155—Receiver Circuit diagram with parts list. Price 1/3 each, post free.

R1155—A.C. Mains Power Unit, circuit and parts list. Price 6d. each, post free.

Always at your service

CLYDESDALE SUPPLY CO., LTD.
 2, Bridge Street, Glasgow, C.5 'Phone South 2706/9
 Visit our Branches in SCOTLAND, ENGLAND and NORTHERN IRELAND.



CELESTION
 Queen of Loudspeakers

CELESTION LTD.,
 KINGSTON-ON-THAMES,
 SURREY

C.4.



FOR THE RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I.C.S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept 94, International Buildings, Kingsway, London, W.C.2.


Please explain fully about your instruction in the subject marked X.

- Complete Radio Engineering
- Radio Service Engineers
- Radio Service and Sales
- Elementary Radio
- British Institute of Radio Engineers
- P.M.G. Certificate for Wireless Operators
- City and Guilds Telecommunications
- Wireless Operator, R.A.F.
- Wireless Mechanic, R.A.F.

If you wish to pass a Radio examination, indicate it below.
 Write to the I.C.S. Advisory Dept., stating your requirements. It places you under no obligation.

Name..... Age.....
 (USE BLOCK LETTERS)

Address




WIRELESS INSTRUMENTS

(LEEDS LTD.)

AMAZING OFFER OF—
Ex-U.S. NAVY 6 VALVE AIRCRAFT RECEIVERS

AT A FRACTION OF ORIGINAL COST

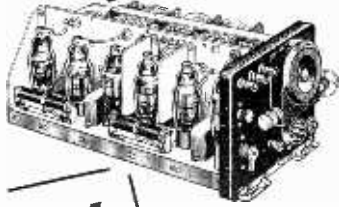

Suitable for breaking down or rebuilding—24 volt operation. These sets are less coil packs. Power unit is not incorporated

EACH SET CONTAINS:—

6 valves (3 type 78, 2 type 77, 1 type 3823). 1.4 gang condenser with trimmers, micro vernier tuning dial. 28 Resistances. 26 Condensers, etc. Brand new, unused and in manufacturers' original cartons.

55/-
 CARRIAGE PAID

54-56, THE HEADROW LEEDS, 1
 Tel. 22262

Transmitting Topics

Details of Some Useful but Seldom-used Apparatus for the Amateur.

By W. J. DELANEY (G2FMY)

MANY newcomers to the transmitting field have made certain that they are well equipped with suitable test gear, by which they mean circuit testers, resistance and capacity bridges, wavemeters and so on. But the majority, as judged from correspondence and visits to many new stations, have overlooked quite a number of incidental items which, whilst not regarded by even some "old hands" as necessary, are, nevertheless, invaluable if real experimental work is to be carried out. Chief among these items is the field strength meter. The intelligent use of this piece of

would allow access to their gardens for the short time such measurements are necessary, although those who are fortunate enough to be situated in an open country district could take far more readings with less trouble. Such a set of measurements, plotted around the transmitting site, will provide a polar diagram and enable one to see very quickly just what is going on, and what any suggested changes may do, without having to make a long-distance contact. A contact of this kind at a later stage will, of course, enable results to be checked and confirmed.

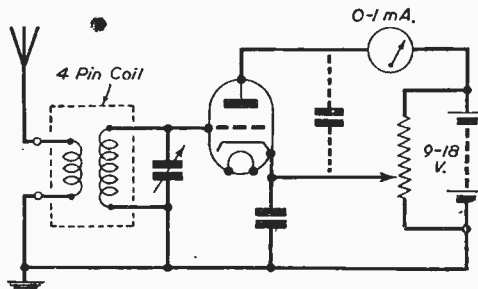


Fig. 1.—Circuit for a simple field strength meter.

apparatus may save evenings of wasted time trying to contact some part of the world which is not covered by the particular aerial in use. Also, if a change has been made in an aerial system, many amateurs simply rely upon reports of their signal strength from different parts in order to get an idea as to the effects of the change. It may take a week or more to collect sufficient data this way to ascertain what the changes have done, whereas all the necessary information (or, at least, the major part of it) may have been ascertained in one evening with a field strength meter.

Field Strength Meter

The meter is nothing more than a simple valve-voltmeter, consisting of a tuned circuit, valve, sensitive low-reading milliammeter and power supplies (preferably batteries). A single 9 or 18 volt G.B. battery will provide sufficient energy with many types of valve. For best results this equipment should all be housed in a metal box with a short metal rod or length of wire projecting from the lid. This is joined to the tuned circuit, and the biasing supply adjusted to bring the meter reading to zero. Most reliable results are obtained if a length of wire is anchored to the "earth line" of the circuit and to the screening box, and this is provided with a spike which may be dug into the earth so effectively screening the entire assembly. This may be taken to a number of points situated at various bearings around the transmitting site and the readings on the meter noted when the transmitter is keyed. No doubt friendly neighbours

Surge Impedance Meter

If the transmitter has to be so situated that long feeder lines have to be employed, it may be desirable to carry out tests so that really accurate line matching may take place. This type of measurement has to be made, of course, at radio frequency, so that all that is required is a source of R.F. (at the frequency which will be used), a measuring device such as a valve-voltmeter or equivalent, and a reliable resistance of the variable type capable of covering the required resistance value. As one generally assumes a maximum of about 600 ohms for most amateur feeders, a good resistance with a maximum value of 750 will be suitable and is readily obtained. In place of a valve-voltmeter it is possible to employ an ordinary

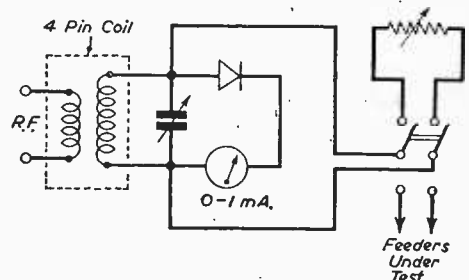


Fig. 2.—A simple impedance meter, suitable for testing feeder lines.

H.F. metal rectifier and a milliammeter and, to avoid differences and difficulties due to the loading of the device, a loose-coupled input circuit should be used. The source of R.F. can very conveniently be the transmitter itself, coupling the input by the standard link circuit to either the C.O. or buffer stage. A standard double-pole change-over switch on the output side will enable the feeder lines to be substituted by the resistance, and it will be obvious that the method of using this piece of equipment is merely to place the feeders in circuit, energise the meter, note the reading, and substitute the variable resistance. Adjust this to obtain the original meter reading, and the resistance then in circuit is obviously the same as that of the feeders of lines

previously tested. If the resistance is not calibrated, its value may be ascertained by means of a standard resistance meter, but it is obviously desirable that the resistance should be provided with an accurately calibrated scale. It should hardly be necessary to point out to amateur transmitters that the resistance must be non-inductive and also capable of dissipating the wattage fed from the transmitter if this is used as the R.F. source.

Modulation Measurements

Many amateurs licensed since the war are now changing over from C.W. to 'phone, and there is wide scope here for pieces of apparatus which will ensure that the transmitted signal will reach a high standard. So far as the modulation circuits are concerned, there is not a very wide range of choice, and the majority of amateurs prefer a good standard amplifier with a hefty push-pull output stage. This can be operated at either Class A or Class AB, although as experience is gained Class C may be preferred. Remember that overloading can be quite a nuisance with a Class A amplifier whilst the same amount of overloading may not prove so troublesome with the other arrangements. As a start, a simple milliammeter in the H.T. lead to the output valve will give a guide as to the loading of the stage. With Class A the needle should remain practically stationary, although slight *upward* kicks can be tolerated. With the other forms of amplification the meter indications are not reliable.

The method of modulation will govern the question as to what type of measurement may next be taken. As there are some rather serious differences, and as changes may be required from time to time, there is little doubt that a really reliable monitor is one of the most satisfactory instruments, although if really serious work is to be carried out a good oscilloscope will be worth its weight in gold. A very

satisfactory monitor is the receiver used at the station, provided that it has a reliable R.F. stage and thus removes risk of detector overload. If a change-over switch is used at the aerial, so that when on transmit the receiver has only a very short lead up to the switch, and the R.F. gain is turned

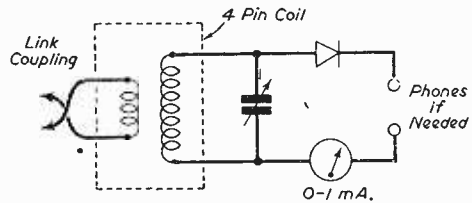


Fig. 3.—A very simple, but effective, monitor circuit.

well back, this will give quite a good indication as to the transmitted quality.

To test the depth of modulation a good valve voltmeter must be used, and the carrier current measured. A steady modulation is then provided, either by a steady whistle into the mike, or by a prolonged "Haaaalo" and the rise in the meter reading noted. The voltmeter must, of course, be inductively coupled to the aerial tank coil or otherwise provided with an induced aerial current, and the coupling so adjusted that overloading or false readings due to too strong an input are avoided.

To avoid over-modulation a simple tuned circuit may be coupled to the transmitter and a diode or metal rectifier connected across the tuned circuit, with a milliammeter in series. This may then be adjusted so that no reading is shown on the meter with normal or full modulation. Over-modulation will result in an upward flick of the meter needle. Such a piece of equipment may also be used to provide audible checks by inserting 'phones in series with the meter.

Secret Receivers in Occupied Territory

DURING the German occupation the Dutch were strictly forbidden to listen to foreign broadcasts, but as long as they were left in possession of their wireless sets, few obeyed the orders. When, however, in 1943, the German authorities enforced their commands by confiscating wireless sets on a large scale, there arose a need everywhere for pocket-size receivers, which could either be hidden away in a small corner or camouflaged in an article of daily use. It was, of course, primarily the task of the Philips concern in Eindhoven to satisfy this demand, and though a normal and organised production was out of the question, personal initiative was not lacking. Soon a lively activity sprang up in small workshops and private rooms and the amateur set-making of earlier days underwent a temporary but intensive revival.

Battery and mains supplies were used for these receivers—mains power being obtained in some cases from cycle lighting dynamos through special transformers.

Official production figures are lacking and no one knows exactly what was achieved, but it is estimated that several thousands and perhaps tens of thousands of these pocket-size receivers were produced in Eindhoven.

Circuit Designs

Preferably "button" or "acorn" valves were used to keep the set as small as possible, and talcum powder tins, books, bed-lamp holders and chocolate boxes were but a few of the devices used to conceal these minute radio sets. The so-called "reflex" circuit was very popular owing to the high sensitivity to be obtained from it with only two of these miniature valves. In this circuit the first serves both as high-frequency and low-frequency amplifier, while the second is used as grid detector with feedback; the low-frequency signal from the anode of this last valve is impressed on the grid of the first valve. In this circuiting system the H.F. and L.F. parts must be carefully separated by filters to avoid self-oscillation.

Another popular circuit combined grid detection and L.F. amplification in a single valve thus making possible a receiver of truly minute proportions. This was the circuit used for the "talcum powder" set.


The connecting flex camouflaged by knitted covering was used as a grille on the mother's dressing gown. The earphone covered in similar fashion was hung in the cot as a baby's rattle. (*Philips Technical Review.*)

Practical Hints

Dial Bulb Fixing


RECENTLY experiencing some difficulty in replacing a dial bulb in an awkward portion of a mains receiver, I used the simple holder as shown below.

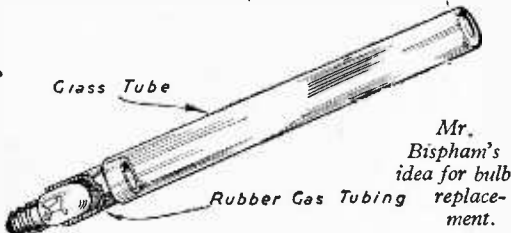A glass tube, such as those in which malt extract tablets are sold, was fitted with one inch of flexible rubber gas tubing. The tubing was a tight fit in the tube, and was secured with a touch of suitable adhesive. The method of using this device is obvious.—H. BISPHAM (Rossendall, Lanes).



Disc Cutter

THE shaft of this drill is cut from a suitable $\frac{3}{8}$ in. steel bolt filed square at the top end to fit into the chuck of a carpenter's brace. The last $\frac{1}{4}$ in. of the threaded end is filed or turned down to about $\frac{1}{4}$ in. diameter to form a shoulder that will bear on the sheet metal that is being cut. The actual cutter is made out of a right-angled hexagonal key, such as is used for undoing secret head screws or bolts, ground to a sharp chisel edge as shown. The bolt is drilled with a small hole just large enough to take the spanner.

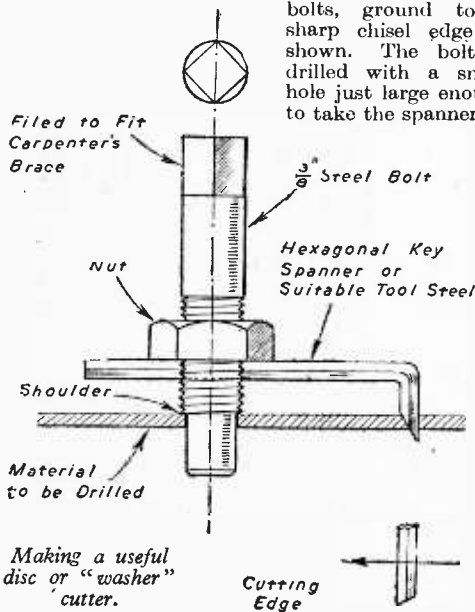

THAT DODGE OF YOURS!

Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay half-a-guinea for every hint published on this page. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Practical Hints."

SPECIAL NOTICE


All hints must be accompanied by the coupon cut from page iii of cover.

To use the cutter mark out the hole to be cut and drill $\frac{1}{16}$ in. hole in the centre. Insert the end of the bolt, adjust the cutting blade to the correct diameter and tighten the hexagonal nut to clamp the blade in position. The hole can now easily be cut by rotating the cutter with a brace.

These cutters are ideal for making valve-holder mounts in metal chassis.—H. W. CUFF (Bournemouth).

A Simple Screening-can Locking Device

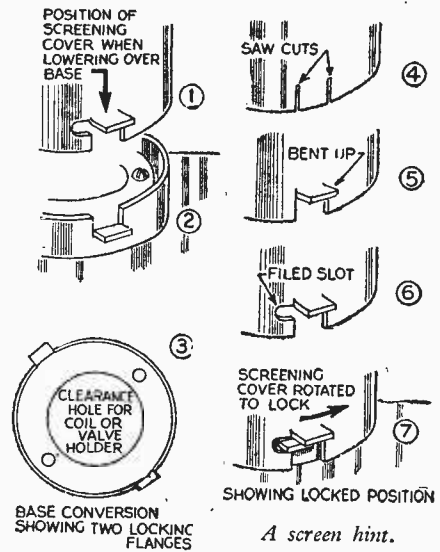NOWADAYS most components are adjusted and matched by the manufacturers and are supplied complete with the necessary screening



plates or covers often being made into one complete unit. However, the old type of screening-can with its separate base will often come in useful to the experimenter for odd coils, etc. These cans, however, are often fixed to their bases with small set screws, and this presents a snag where quick experimental changing of the component is required.

The idea illustrated allows of such quick changing whilst still retaining good fixture of screening cover to its base.

Briefly, both the base and cover are arranged with small projecting lugs, bent downwards and upwards respectively, whilst those in the cover are provided with short slots to one side. When the cover is placed over the base so that the sets of lugs in each coincide and the cover is rotated slightly, the lugs in the base project into the slots of the cover, thus effectively locking cover to base.—R. L. GRAPER (Chelmsford).

THE wiring diagrams were given in the last issue, from which it will be noted that several of the leads or connections were shown outside the chassis. This was merely to show the wiring as clearly as possible in this rather condensed view. These connections will, of course, be included inside the chassis and will in all cases be much shorter. The four leads going to the transformer unit are, of course, external flex leads from the short connection panel.

The two fixed condensers C10 and C11 shown full at the side, are shown dotted in the positions they occupy in the chassis. This is again for illustrative purposes in order to show the wiring to the valve holders. Similarly, the small high-frequency choke HFC2 (which is a small unshielded one, measuring lin. diameter \times $\frac{1}{4}$ in. thick) actually lies flat just above the valve holder for V2, and not end on, as shown. This reaction choke might be home made, if any difficulty is experienced in purchasing one small enough for this position. As a basis to work on, a former might be made from four thin insulating material discs of lin. diameter, with three inner spacing discs of $\frac{1}{4}$ in. diameter by $\frac{1}{4}$ in. thick. A small set screw, and nut, passed through the centres of the discs, would complete the former. The three slots could then be almost filled with 38 or 40 s.w.g. enamelled wire. Soldering tags, for the start and end of the winding, should, of course, be securely fitted to

The Three-fo

Further Details of a Self-contained Attache-ca

the former, so that the choke may be soldered firmly in position. By the way, a low value resistance might be used in place of this H.F. choke, one of about 10,000 ohms being suggested. The condenser C13 coupling V2 to V3, should still remain connected to the top end of this resistance, as when the choke is used.

When commencing the wiring, owing to the somewhat restricted space available, a definite procedure is advised. It is a good plan first to fit the main earth, or chassis wire, which is along the rear, and extends down each end, and the extremities soldered to tags bolted to the chassis. The filament wiring should then be attended to, and this can be conveniently tucked close against the chassis, if good insulating sleeving is used. Then attend to the other valve holder connections, those to the switch, and phone jack. Also, do not forget the connections to the ganged tuning condenser, through the $\frac{3}{4}$ in. clearance holes in the chassis. All wiring may be done with about 22/24 s.w.g. tinned copper wire, and good quality slip-on sleeving. The main wire from the frame aerial tag



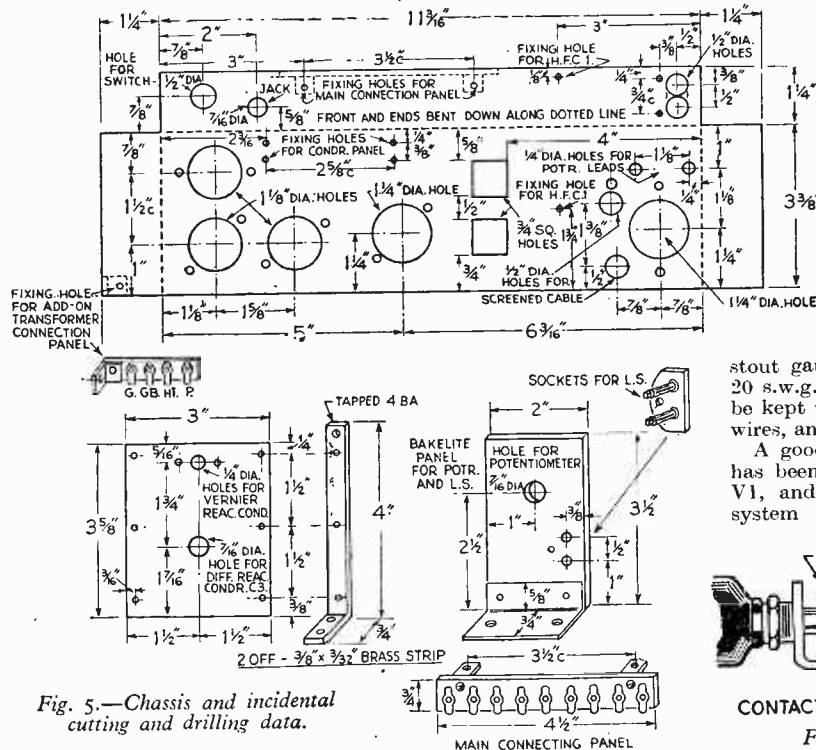


Fig. 5.—Chassis and incidental cutting and drilling data.

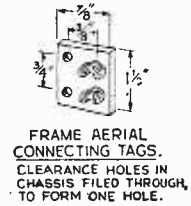

to the grid of V1 and shown in Fig. 3 as a black and white hatched one, should be quite stout gauge, about 18 s.w.g. or 20 s.w.g. This wire should also be kept well spaced from other wires, and components.

A good high-frequency choke has been used in the anode of V1, and a good one in this system of coupling the R.F.

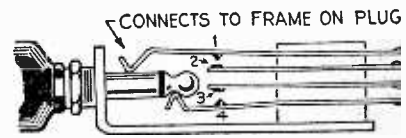

CONTACTS 1-2 AND 3-4 MADE 101
Fig. 4.—Details of wiring for

Portable

Receiver Described by R. L. G.

valve to the detector, is most essential. The component used is a Bulgin all-wave choke, type H.F.15, and although an all-wave choke is not essential, its dimensions of 1½ in. diameter by 2½ in. long overall will be found to fit nicely into the space available, and the business-like stand-off soldering tags are very convenient. The baseboard fixing disc supplied with this component was not used, the choke being securely strapped to the chassis by means of a band of stoutish gauge aluminium, and two very small nuts and bolts. All the resistances used are half watt types, and

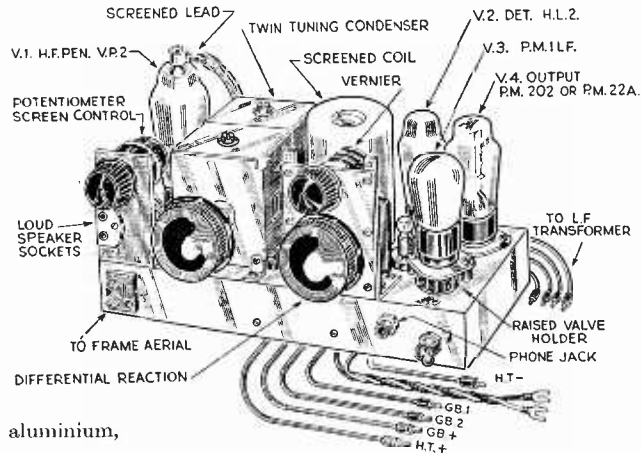


Fig. 8.—The completed receiver with details of leads, controls, valves, etc.

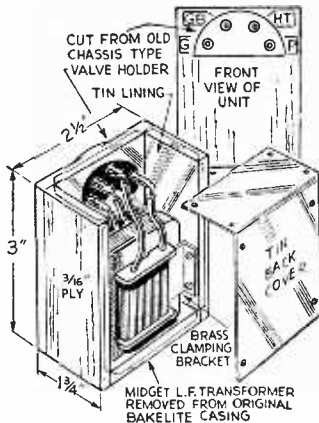


Fig. 6.—Details of the screened transformer unit.

of the loudspeaker sockets is taken along the rear of the chassis, and adjacent to the main earthed or chassis wire. The casing of this screened cable can be conveniently soldered to this wire, and if not of solderable metal, several turns of tinned copper wire may be twisted round it at intermediate positions and the ends soldered to the earth wire.

The decoupling condensers C5, C7 and C9 are all positioned just above the screened cable, and these condensers, as well as C10 and C11, should preferably be of a good paper type. The screened cable, from the anode of V1, to H.F. choke 1, should be of ample diameter to give good clearance from the inside lead, the latter being of moderate gauge. The screened cable used by the author is about ½ in. diameter. Co-axial cable, would, of course, be ideal for such a position, but might be found a little difficult to bend for so short a distance. The screen covering of this cable should also be suitably earthed to chassis.

The Switch

The on-off switch operates parallel with the chassis, but this should not be found an inconvenience. The switch used is a mains, double-pole change-over type having six terminals or soldering tags. Only one side is used, however, the two central tags being connected together and go to L.T.— and one side of the fuse-holder. The top outside tag goes to chassis whilst the bottom outside tag goes to R3. As previously mentioned this is to disconnect the resistance network of V1. A normal three-point on-off switch could be used if desired.

The phone jack can be seen to the right of the switch, and that used by the author is an old component, of French manufacture, but no doubt a more modern type will be found to substitute, but see that the jack used “breaks” a pair of contacts on the insertion of the phone plug, in order to switch out the filament of V4. As, in the model shown, the outer contact strip is connected via the plug to the framework of the jack only when this plug is inserted, the chassis connection shown

these will be found quite satisfactory and space saving.

It will be found that the audio end of the receiver is quite compact, and for this reason the valve holder for V3 has been raised above the top of the chassis by two ¾ in.-long collars. This allows condensers C10 and C11 to fit comfortably clear of the wiring beneath. C10, which is the 1mf. decoupling condenser, might, of course, be mounted above the chassis, but fitting it elsewhere below chassis is not advised, as the right-hand side of the under-chassis

should be as clear as possible to give spacing to leads and components carrying R.F. currents. R8, by the way, is a grid-stopper resistance to prevent these R.F. currents straying into the audio section.

It will be seen from Fig. 3 that the screened lead from the anode socket of V4 to one

- SECTION TO CHASSIS
- TO NEG. FILAMENT LEG OF OUTPUT VALVE
- UNUSED
- C.11 AND C.12
- REMOVAL OF PHONE PLUG
- the phone jack.

from this contact strip is still necessary, so that the filament of V4 goes to chassis when 1 and 2 come together on withdrawal of the phone plug.

The main connecting panel is located just to the right of the switch and jack, and is bolted to the front face of the chassis just below the level of the top edge. When the wiring of the set has been completed, the necessary short lengths of flex, suitably labelled, are soldered direct to their appropriate tags. A separate projected view of this tagboard is given in Fig. 3, showing these external connecting wires. No flex leads are specified for the eighth and ninth tags, as the former is a spare one, and the latter acts merely as an anchoring tag for R3, and its connecting wire to the three-point switch.

The small connecting panel for the transformer unit is located at the rear of the chassis being secured to the side of the chassis by a simple stout brass bracket and small nut and bolt. This panel is adjacent to the unit when the set is in its case, and the flex connections are thus very short. A short length of flex should be taken from the chassis and soldered to the tin cover of the unit when the portable is finally assembled.

Differential Reaction Condenser

There are three connections to this. One set of fixed plates go to reaction winding pin 4, and to H.F.C2. The other set of fixed plates go to the end of the reaction winding only, pin 3, whilst the moving plates are earthed to chassis. The moving plates of the vernier condenser are also earthed, whilst its fixed plates go to differential reaction condenser tag connected to pin 3. Should an anticlockwise motion of dial be experienced for an increase in reaction, then the connections to the two sets of fixed plates should be reversed. This would then apply to the vernier condenser also. This vernier condenser is a small capacity trimmer type in the region of .00005 mfd. A small one-plate condenser of the solid dielectric type could be used, but a check of centres should be made to see if this will fit.

Screen Control to V1

As previously mentioned, this is obtained by a potentiometer of 20,000 ohms, R2. The moving arm goes to screen and C5. The top end goes to H.T.+ via a 20,000 ohm fixed resistance, and the lower end to a 30,000 ohm fixed resistance, R3. This latter resistance is connected to the three-point switch as previously stressed, and will prevent the small drain on H.T. that would otherwise occur. Should readers have objection to this slight extra consumption, for this method consumes a slight current when in operation, a plain series resistance might be tried, or a plain tapping to H.T. if this is available. The spare tag on the connecting panel might then be used for this extra lead. The potentiometer could then be used for variable- μ grid bias.

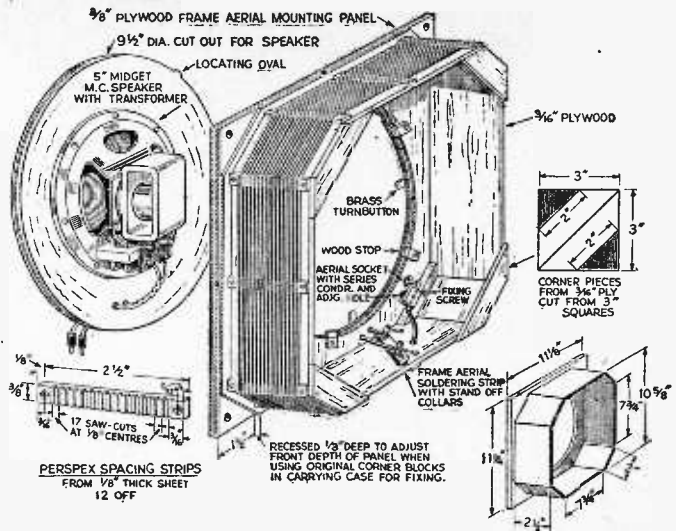


Fig. 7.—Details of the speaker and frame aerial mounting.

As with the reaction control, the correct outer connections should be ascertained for clockwise motion of control, before wiring, otherwise reversal of these connections may be necessary.

The connections to the fixed plates of the ganged tuning condenser are taken to the bottom tags, and adequate clearance holes each measuring $\frac{3}{4}$ in. square have been cut in the chassis for these connections. The moving plates go to chassis, and a short length of wire may go through one of the $\frac{3}{4}$ in. holes to the spindle soldering tag.

A five-pin valve holder has been used for the output valve, and the centre connection is taken to H.T.+ . This, of course, only comes into use when using a five-pin output pentode, so need not be omitted or removed when using a four-pin power output valve.

Transformer Unit

For this unit, a simple three-sided box can be made from plywood, and lined with tin for screening purposes. A portion from an old discarded chassis-type valve holder, or a complete four-pin type, can be used for a connecting panel, or just small terminals fitted if preferred. The tin lining inside the front should, however, be well clear of these sockets or terminals. The small "Pip" transformer used was removed from its original bakelite casing and a piece of sheet brass passed through between the laminations and spool, to form a fixing bracket, this being screwed to the side of the box. The original short connections to the windings are soldered to the four sockets, and the front clearly inscribed with the correct connections. Finally, a simple tin cover can be made and screwed to the box with $\frac{1}{4}$ in. countersunk brass screws. The unit is seen in Fig. 6.

Frame Aerial and Loudspeaker Panel

Full details of the frame aerial and its former are given in Fig. 7, together with the loudspeaker panel, which fits in the centre of it. Fuller details will be given next month.

On the Amateur Bands

A Monthly Report of Results and Conditions Experienced
on the Short Waves.
By "KAYAK"

More 50 Mc DX

ALL existing records for DX on this frequency have been broken. The first two-way contact between North and South America has occurred, and reception of signals from Holland have been reported in South Africa.

The North-South America contact was made by W4IUI, of West Palm Beach, Florida, and OA4AE, in Lima, Peru, a distance of over 3,000 miles. W4GJO, of Orlando, Florida, also worked OA4AE shortly after. W4IUI becomes eligible for the Milwaukee Radio Amateurs' Club 50 Mc/s cup offered to the first amateur making two-way contact with another continent from the United States mainland. On the day following these contacts, reception of automatic transmissions from PAUX in Holland was reported by South African stations ZS1P, ZS1T, ZS1AX and ZS1DJ, over a 6,000 mile path, the greatest distance at which V.H.F. signals have ever been heard. DX conditions on this frequency are likely to hold for a few more weeks, especially over north-south paths.

28 Mc/s Band

Conditions on this band have remained good apart from odd days, when fade-outs occurred caused by sun-spot activity. D. L. McLean, Somerset, reports over 100 good DX 'phones heard. His list includes the following: Chilean CE8AB, CE8AG; CX2CO, Uruguay; EL2A, Liberia; HZ1AB, Saudi Arabia; J9ANA, Okinawa; PZ1A, Surinam; XZ2DN, Rangoon; and five "Marine Mobile" stations. He says that South American stations have been heard up to 23.30 G.M.T., a most unusual happening. Mr. McLean mentions much QRM caused by the R.A.F. radar station on 29.7 Mc/s, which spreads all over the band. Other reports of interference from this station come from North America, South Africa, and Okinawa. Remarks overheard from amateurs in these countries indicate that the QRM is severe enough to interfere with DX working. The source of the QRM is less than 50 miles from Mr. McLean's QTH, and as the noise is mostly R9 we understand how difficult he must find conditions.

Dennis Tylor is active on this frequency and informs us of ZC6FP, near Jaffa; J9ANA, Okinawa; Australian VK5NR (a very consistent signal); VP6YB, Barbados; XU6GRL, who is W6GRL, operating from Nanking; and CR4AA, in the Cape Verde Islands.

A station mentioned in many reports is OIX7, an experimental broadcasting station belonging to the Finnish Broadcasting Company.

D. L. McLean says the station is mostly operated by pre-war OH2NM, with occasional assistance from pre-war OH6NS. OIX7 is making many contacts with amateur stations.


14 Mc/s Band

This band continues just as interesting, with many unusual DX stations reported. On "key" we came across VS6DY, who was working from the s.s. *Anglo African*. Input was given as 10 watts and the transmitting antenna was said to be 25ft. above sea level. No QTH was given apart from address for cards, so we presume the station was operating from Hong Kong, otherwise why the "VS6" prefix? LB90 provided us with a puzzle until he gave information that he was working a portable station in Trondheim, Norway: so that any "LB" calls heard can be taken as portable working from Norway. Other CW stations of interest: O12KAA, Helsinki, Finland, who is running 700 watts; VS6AA, Hong Kong; VQ8AD, Mauritius; VS7EV, Trincomalee, Ceylon; VP4TX, Trinidad; CT2XA, Azores; VP2AD, Leeward and Windward Islands; OA4U, station of the Magnetic Observatory at Huanacayo, Peru; HC1OE, Ecuador; KH6JW, Hawaiian Islands; EA7AV, Madrid; and ZD1KR, Sierra Leone. Two of unknown origin were CZ70 and SS2MB. Any suggestions?

Best R/T stations logged by us were XZ2BA, near Rangoon; KAIAN, Philippine Island; ZB1AF, Malta; CE3BM, Santiago; Cuban C07CX; Y16AB, Iraq; XACP, Sardinia; and XU6GRL, Nanking.

'Phones reported by BSWL 804 include CT2AB, Azores; EA9AI, Spanish Morocco; VK4NK,

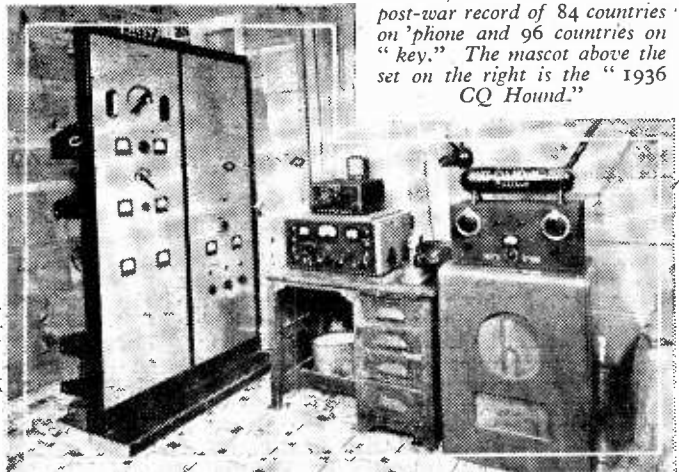A fine American amateur station, W8TT at California. With a rotary beam aerial on 14 and 28 Mc/s this station has a post-war record of 84 countries on 'phone and 96 countries on "key." The mascot above the set on the right is the "1936 CQ Hound."



Port Moresby, New Guinea; WNNI, Colorado; KH6GF, Hawaii; VQ6LW, British Somaliland; LI2BO, near Tobruk; and HI2L, Dominican Republic. Receiver used by BSWL 804 is a Sky Champion S20, with one-valve regenerative pre-selector.

John Brookes, North London, sends along the following 'phones: J9AGP, Okinawa; OQ5AV, Belgian Congo; VE8MQ, Bafin Island; and VP9D, Bermuda. On CW he lists CR7AD, Mozambique; EPIAA, Iran; NY4CM (QTH?); ZP8AC, Paraguay; and LI2BO, El Adem. "Locals" listed RAEM, Moscow. This station is very active on the 14 Mc/s band and the "commercial" call-sign has often puzzled us. However, Mr. Brookes gives the explanation. The call RAEM was originally assigned to the 1938 Russian Polar Expedition. Upon return to the U.S.S.R. the chief operator of the station was granted permission to adopt the call-sign for his own use on the amateur bands.

'Phones listed by Dennis Tyler include FF8FP, French West Africa; LI3BO, El Adem; CP1AP, Bolivia; W4BOW/Iwo Jima; ZP6AC, Paraguay; and CR4AA, Cape Verde. C.W. stations heard include PK6AX, Celebes; I6USA, Asnara; VQ5JTW, Uganda; CR9AN, Macao; LZ1XX, Sofia; YO5WZ, N. Roumania; and PI1L, The Hague.

7 Mc/s Band

DX pickings on this frequency come to those who have the patience to wade through the European QRM. CW stations heard by us around midnight include Cuban CM8GA, CM2CZ and CO6AV; HK4AF, Colombia; CX1DB, Uruguay; XE1GA, Mexico City; and KP4EN, San Juan, Porto Rico. This latter station was as loud as any European! KP4EN uses 1 kw., with a vertical antenna. North American signals are at their best around breakfast time. For signals from Australasia try around 1900 G.M.T. DX stations known to be active on the 7 Mc/s band are ST2AM, Sudan; TF3A, Iceland; KH6AL, Hawaii; ZL4GA, Dunedin; and VU2QY.

Kon-Tiki Expedition

This expedition is scheduled to leave on a 4,000 mile trip by raft across the Pacific Ocean. It is leaving from Ilo, Peru, and will make for the Polynesia group. A 15-watt transmitter is being taken and contacts with amateurs will be made on the 14 and 28 Mc/s bands using call-sign LI2B.

Shorts

New Zealand 'phones are limited on 14 Mc/s to the 14,200-14,300 portion of the band. . . . According to OI2KAF, heard on 14 Mc/s, Finnish amateurs are not yet licensed. OI2KAF is attached to an expedition and is the only officially licensed station in that country. . . . "XA" stations in Greece have now been issued with "SV" call-signs. SV1AH in Athens is the station formerly operated by XAAP, who has now returned to the U.S.A. . . . The Ronne Antarctic Expedition is now established at its base station at Stonington Island, Marguerite Bay, Antarctica. Call-sign is AYZH and known frequencies used for amateur contacts are 12,480 and 8,330 kc/s. . . . The Canadian Broadcasting Corporation recently radiated a coast-to-coast broadcast featuring amateur radio. Principal speaker was Alex Reid, VE2BE, Canadian

General Manager of the A.R.R.L. . . . VR6AY, Pitcairn Island, may soon be active again. Reports say that Andrew Young and a New Zealand amateur are busy rebuilding the station ready for amateur activities. . . . At the coming world-telecommunications conference, now being held at Atlantic City, American delegates propose a new amateur band covering the frequency band 2,100-21,500 kc/s. . . . There are now 75,000 licensed amateurs in the United States.

Current DX QTH List

| | |
|-----------|----------------------------------------------------------------------------------------------------|
| OI2KAA | Box 250, Helsinki, Finland. |
| OE9AA | R. Richards, A.P.O. S/565, Klagenfurt, Austria, C.M.F. |
| HZ4DO | P.O. Box 112B, Mekka, Arabia. |
| VP4TX | 52 Mucurapo Road, Port of Spain, Trinidad. |
| CT2XA | A.P.O. 406, c/o Postmaster, New York. |
| VS6DY | Radio Operator, S.S. Anglo African, c/o Sir Wm. Reardon Smith, 70, Bute Street, Cardiff. |
| KP4DO | Collego of Engineering, Mayaguez, Puerto Rico. |
| LI2JC | R.A.F., El Adem, Near Tobruk, Libya. |
| I6USA | U.S. Army Radio Station, Eritrea. |
| HZ1AB | Dharan, Saudi Arabia. J. P. Anderson, A.P.O. 788, c/o Postmaster, New York. |
| NY4AB | U.S. Navy Base, Guantanamo Bay, Cuba. |
| SV1AH | Trans-World Airlines, Hasani Airfield, Athens. |
| VO6K | U.S. Govt. Coastguard Radio Station, Battle Harbour, Labrador. Navy 228, c/o Fleet P.O., New York. |
| VS9AA | c/o 12, Elder Grove, South Shields, Co. Durham, England. |
| W2MMO/MM | Matthew Krim, Box 49, 25 South Street, N.Y.C.4, New York. |
| W3KCG/VP2 | Bruce Williams, 155 A.A.C.S. Det., Antigua, A.P.O. 855, c/o Postmaster, Miami, Florida. |
| ZB1AD | c/o A.P.O., Malta. |
| VQ3EDD | Box 166, Dar-es-Salaam, Tanganyika. |
| XE1AC | P.O. Box 9581, Mexico City. |

Broadcasting Stations of the World

A MOST valuable booklet is published by Iliffe & Sons, Ltd., which lists long, medium and short-wave broadcasting stations in geographical and wavelength tables. The book is based on information available at November 30th last, and in addition to giving the station names, frequencies, wavelengths and power, a space is provided in which dial readings may be entered. The four sections of the book, which measures 5½ in. by 4¼ in. are: Long- and Medium-wave European Stations, with Frequencies, Wavelengths and Powers; Geographical List of Long- and Medium-wave European Stations with Frequencies; Short-wave Stations of the World, with Frequencies, Wavelengths, Powers and Call-signs; and Geographical List of Short-wave Stations with Frequencies. The price is 1s. net.

Triode Vectors—3

Concluding Details on the Subject Discussed During the Past Months.

By "DYNATRON"

Combined Effect of Grid and Anode

FIG. 5(b) is the circuit under consideration at the moment.

When E_g rises in a positive sense I_a increases in step, a voltage drop V volts will occur across R , whilst the valve anode-to-cathode volts will fall by the same amount, i.e., max. (or R.M.S.) voltage change across the valve = $V_o = -V$.


Hitherto we have used the symbol v_a in a loose, undefined manner. We simply called it the "voltage across the valve." More precisely, v_a denotes the voltage change (increase or decrease) across the valve at any instant in a cycle—small letters are used to represent instantaneous values, whilst capitals such as V , V_o denote R.M.S. values, or maximum values V , V_o .

Now, a fundamental point in valve theory is the fact that, if a change E_g volts occurs at the grid, the resulting change, I_a , of anode current will be the same as if the anode potential were changed by μE_g volts—where μ = the valve amplification factor. Stated simply, the grid is μ times as effective as the anode in controlling electron flow.

Stated the other way about, a change V_a in the anode potential will produce a current change equivalent to a change of V_a/μ volts at the grid. If E_g (an applied signal E.M.F.) is varying in a positive sense, then V_a in Fig. 5(b) will be decreasing, or varying in a negative sense. Hence, the resulting current change will be that due to an effective electric field at the cathode due to a potential of:

$$(E_g - V_a/\mu) \text{ volts.}$$

Fig. 5.—Without an anode load (a), the volts on the anode will be constant, and I_a and E_g will be in phase. Also, with load as in (b), there will be no phase-shift between anode current and grid potential—the load resistance R simply determines the maximum value of I_a , i.e., the magnitude of I_a

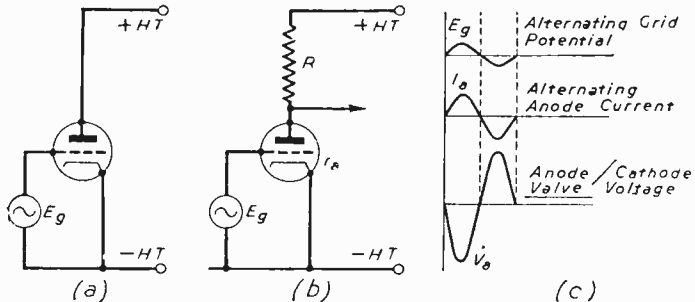

If we bear in mind that E_g and V_a must be given appropriate signs, this basic equation may be written in the form:

$$I_a = E_g + V_a/\mu,$$

where I_a denotes the anode current change.

In Fig. 5(b), V_a will reach a maximum (in a negative sense) at the instant when E_g is a maximum in a positive sense. In other words, V_a will be at its lowest value when E_g is at a maximum in a positive sense. Yet E_g will here determine the maximum value of the anode current, i.e., though the magnitude of this maximum will depend on E_g and V_a —and therefore upon the anode load—

maximum I_a will occur at the same instant as E_g ; E_g and I_a will remain exactly in phase.

When the load is a pure resistance, as shown, maximum electric field drawing electrons to the anode will occur at the same instant as E_g is a maximum—even though V_a has some larger value at some other instant. Remember that V_a denotes the value of an alternating potential at a given instant; across the valve, it will reach a maximum positive value at the instant when E_g makes the grid of greatest negative potential, since I_a , and the voltage drop $I_a R$ in the load, will be a minimum at this point.

The normal relations are illustrated by a set of sine curves in Fig. 5(c).

Value of V_a/μ

It might be thought that the effect of the anode potential change will in any case be negligible compared with the effect of E_g , because, for one thing, the grid is much nearer to the cathode, and moreover is " μ times" as effective as the anode in controlling electrons.

But don't forget that V_a may be nearly μ times as great as E_g , owing to the stage amplification. In fact, a few figures will quickly show that the effect of V_a , at the grid (or near the cathode), can be of about the same order of magnitude as E_g itself, since in an amplifying stage V_a/μ will be nearly equal to E_g .

Thus, suppose $\mu = 10$, whilst at a given instant $E_g = 1.0$ volt. Then suppose the anode load is such that the stage amplification is about $0.8\mu = 8$ (a load resistance of four times the valve r_a). When E_g varies by 1.0 v., a potential change of

$8 \times 1.0 = 8$ v. will occur at the anode. If E_g is increasing in a positive sense, V_a represents a fall in the valve voltage of -8 v., i.e., $+8$ v. more across the resistance load.

What will be the effect of this -8 v. in terms of the total electric field produced near the cathode?

The answer is $v_a/\mu = -8/10 = -0.8$ v. The grid potential has increased by 1.0 v. in a positive sense, but, simultaneously, the electric force exercised by the anode in the vicinity of the cathode has decreased by -0.8 v. The resultant effect of both changes will be equivalent to 1.0 v. $- 0.8$ v. = 0.2 v.

So, the total effective potential causing the anode current to increase is only 0.2 v. We could consider as "effective" the whole of the 1.0 v. applied to the grid and say the *dynamic mutual conductance* of the valve, with a resistance of 4ra in series, is only 0.2 mA/V—assuming it was 1 mA/V.

Both statements come to the same thing. But from our present point of view main interest resides in the fact that when the combined effect of grid and anode potentials is taken into account 1.0 v. at the grid is really equivalent to only 0.2 v. Evidently, the effect of V_a/μ is very considerable.

Even so, *maximum* electric field near the cathode will occur at the instant E_g is at peak value. Thus if $E_g=2$ v. peak, $V_a=8 \times 2=16$ v., and $V_a/\mu=16/10=0.4$ v. This will be the greatest possible value under the given conditions, hence I_a reaches maximum at the same instant as E_g —there is no question of a phase difference.

Reactive Load


But E_g and I_a will also get out of phase if the load has *reactance*. This is because V_a will not be out of phase with I_a (and E_g) by some angle other than 180 deg. For example, if after allowing for the shunting effect of ra the phase-shift between I_a and the load voltage v is 45 deg., then the anode-to-cathode voltage V_a will be out of phase with E_g by an angle of (180 deg.+45 deg.)=225 deg., assuming inductive reactance. Therefore, V_a will be at its minimum not when E_g is at its peak, but 45 deg. later.

Matters are becoming slightly difficult to try to

visualise. In Fig. 6 is shown the R.M.S. grid potential as a vector E_g (or it might represent the peak value). Then, let V_a/μ be represented by the vector OM, at some angle to E_g greater than 180 deg. The resultant potential drawing electrons across to the anode will be OP E_g .

Note that OP really denotes the resultant electric

Fig. 6.—With reactive (e.g., inductive) load, the resultant voltage OP drawing electrons to the anode will be de-phased on E_g , and I_a will be in phase with OP—or phase-shifted upon E_g .

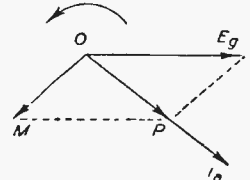

field at the cathode due to both potential changes (anode and grid). The important thing to observe is that the alternating anode current I_a will be in phase with OP, not with E_g . In this case, the electric force at the cathode will reach its maximum after E_g has passed its positive peak, since OP is lagging behind E_g .

The whole vector diagram must be imagined rotating in an anti-clockwise direction about the point O. First, E_g reaches a perpendicular (maximum) position, then, a little later, OP. I_a will reach its peak at the same time as OP, and is therefore lagging on E_g .

I will summarise this part with the aid of values in a later article. Bear in mind that, throughout, we have been considering triodes. As explained earlier, the effect of V_a is negligible in a pentode, compared with E_g .

Quality Battery Circuits

Details of Two or Three Receiver Circuits for High Quality
Reproduction with Battery Supplies. By R. V. LUMBARD

IT will be realised that the battery receiver is seldom considered by the radio-constructor in search of realistic reproduction. Mains receivers usually take precedence where a high standard of musical fidelity is required. However, the possibilities of a fidelity battery receiver are by no means limited. Improved frequency response and freedom from harmonic distortion can readily compensate for the absence of "shake the room" output which typifies many powerful mains receivers.

The circuits given are chosen as a basis for experiments in fidelity battery receivers. Emphasis has been placed upon quality of reproduction; and not on the sensitivity of the circuits to stations beyond the "local" B.B.C. transmitters.

Fig. 1 is the diagram of a two-valve fidelity head-phone receiver. Both valves are of the 2-volt rating, although there is no reason why 1.4 volt valves should not be used. In the latter instance component values may require alteration. V1 should preferably be an H.F. pentode of low impedance. V2 is a normal double-diode-triode. For simplicity only coils of the medium waveband are used. Tuned H.F. anode replaces the usual

H.F. transformer coupling between stages. Tuning is by a straight 2-gang .0005 mfd. condenser. If preferred, switches and pre-set condensers tuned to the local stations may be used.

The 'phone transformer is a standard, not midget, inter-valve transformer with a ratio of 1:3-1:5. Contrary to general procedure, it is connected as a step-down unit. The normal secondary winding is used as primary in this instance, and conducts the 1-1.5 mA. anode current of the D.D.T. Anode current is limited by the application of 1.5 volts negative bias on the valve's grid. Regarding 'phones, those of between 2,000 and 4,000 ohms are quite satisfactory. Low resistance 'phones can be used where a suitable transformer is available.

For Loudspeaker Working

Fig. 2 incorporates a tetrode or pentode output stage for loudspeaker reception. Parts for the H.F. and diode stages remain identical to those used in Fig. 1. A feedback voltage from the output transformer secondary is, however, applied to the "earth" end of the D.D.T. grid resistance. Resistance-capacity coupling precedes the final

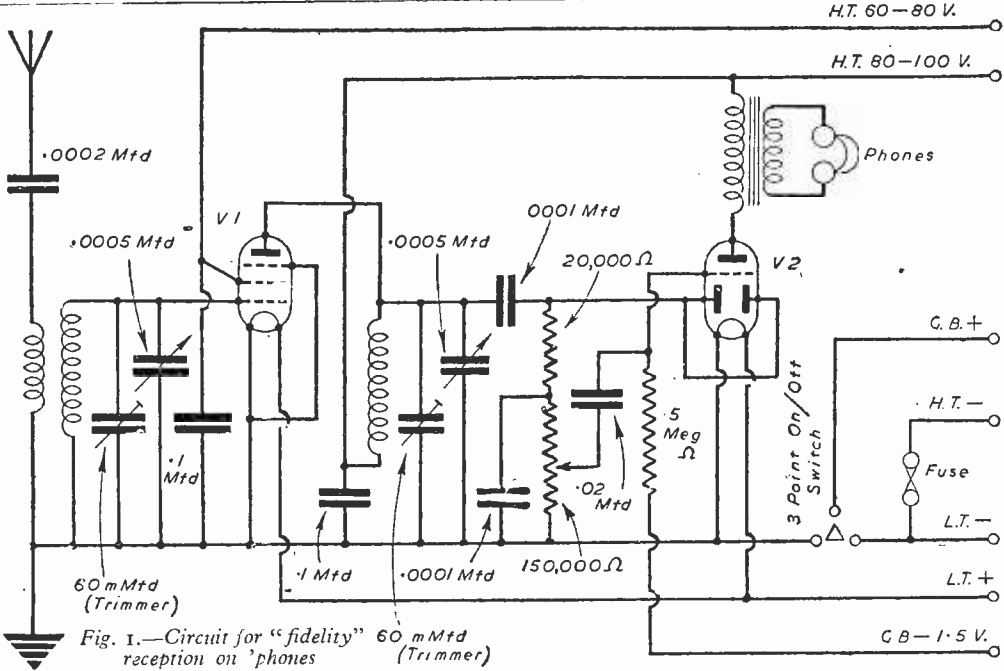


Fig. 1.—Circuit for "fidelity" reception on "phones"

stage. Bias for the output valve will usually be in the region of 2.5-4.5 volts, depending upon the type of valve employed and the H.T. voltage available.

The load impedance of the output valve determines the ratio of output transformer required. For matching purposes, if the ratio is unknown:

Screen H.F.

H.T. 60-80 V.

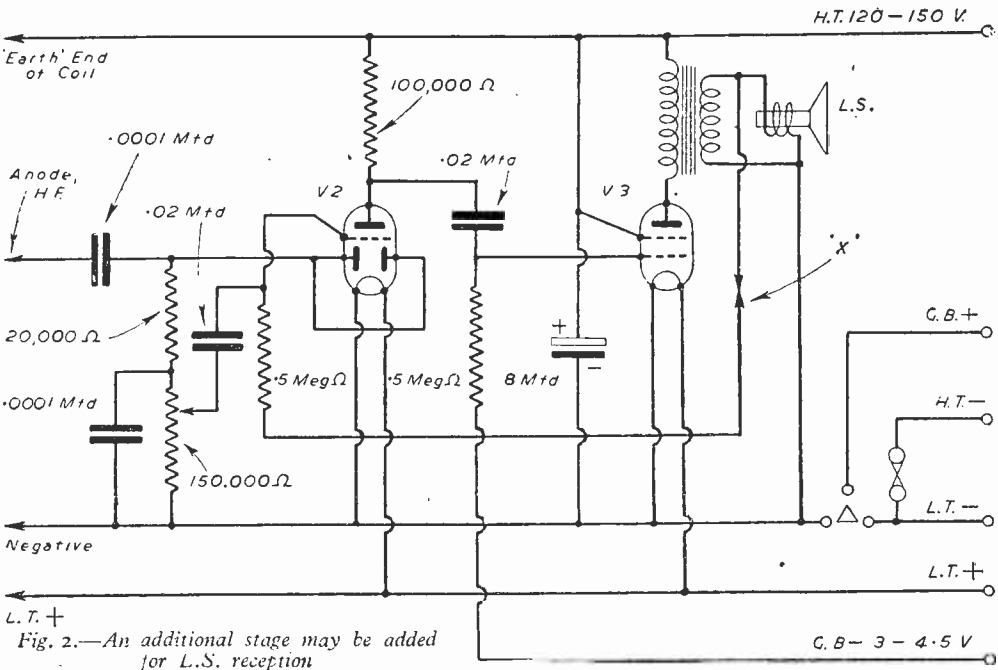


Fig. 2.—An additional stage may be added for L.S. reception

Underneath the Dipole

Television Pick-ups and Reflections. By "THE SCANNER"

WHILST most readers of this journal are interested in radio as a hobby, a good many of them combine this interest with an active part in the radio industry. Not all of them pay much attention to the financial columns of the newspapers, where the City Editors currently report "Gramophones and radios dull, and Old Consols 1½ lower," a comment which has no connection whatsoever with the top-cut tone control on their wireless receivers. Nevertheless, the technical progress of the British radio industry is closely related to such reports, and the healthier the radio companies' balance sheets are, the more likely it is that the boards of directors will authorise the allocation of more money for research, to the ultimate benefit of us all.

Radio Exports

An encouraging feature of the more recent annual reports of various radio manufacturing companies has been the reference in all of them to the increasing volume of exports. These exports in some instances reach the amazing proportion of more than half of the value of the output of wireless parts, sets and accessories, and, in particular, of complete radio stations and transmitters. In the face of intensive competition from the big American radio companies, our own representatives in many lands have secured contracts of great value. I do not think that any criticism can be directed at the "foreign policy" of our big radio companies, whose foreign salesmen are usually first-class engineers, linguists, diplomats, hosts, spell-binders and high-pressure commercial travellers all rolled into one! Men with strong personalities, plus all these qualities, have been doing this kind of job for years, and are quite unlike the timorous, ill-informed foreign representatives of certain other British industries. Technical excellence is a most important selling point, of course, but it is the "personal" touch which counts in the long run. Some years ago there was intensive competition for large radio transmitting stations in a Balkan country, and the specification and prices of British and American tenders were practically the same. But the scales were turned in favour of the British offer, due to an amazing impromptu music-hall turn given by the British salesman at a party at a cabaret when several members of the Cabinet of that country were present. This salesman, who was also a brilliant engineer, gave satirical imitations, in the course of a song, of the prominent members of the opposition party, much to the delight of the Prime Minister and his friends. After this, the contract was secured without further difficulty!

The Permanent "Nine Days' Wonder"

These exports are, however, largely to "soft currency" countries: getting our radio products into America or other dollar areas is quite a different matter. The power of the big American radio companies and corporations is enormous and covers a wide field of activity. The recording machines

of R.C.A. and Western Electric are, for instance, products of their subsidiaries, and the huge royalties remitted annually to America by British film companies for the use of American apparatus and patents must offset a large proportion of the value of our exports. Somebody must have been very much asleep about twenty years ago, when one leading British radio company was actually restrained legally from proceeding with the development of its film recording apparatus through the manoeuvres of a big American radio and gramophone company. At that time, I suppose that the British company directors had less foresight, and dismissed the development of the talking picture as a mere nine days' wonder. That decision has cost this country millions. It is a lesson that must be taken to heart when similar decisions have to be made in respect of television. In this field we are ahead of America. Perhaps we might export a few dozen of our latest types of cathode-ray tubes in exchange for dried eggs, nylons or—hush!—American film recording apparatus.

Man-made Static

Encouraged by good results obtained under favourable conditions in their localities, viewers have increased in number at the extreme range of the Alexandra Palace transmission—and even at points normally regarded as being beyond the range. Good results on individual receivers installed at such places as Chichester, Harwich, Bournemouth, Broadstairs, Malvern and Babbacombe have led optimists to try their luck at such distances. Radio dealers are helpful in this matter, and are usually prepared to allow a would-be purchaser to have a try-out free of charge, except, perhaps, for a nominal one to cover the erection of a dipole aerial. Results are dependent largely upon the immediate surroundings, and especially upon the extent of interference by man-made static from cars, diathermy and other electric appliances. There are other man-made interferences which could be reduced: harmonics of 20-metre transmissions from Service and amateur stations, which cause an unpleasant noise just between the sound and vision frequencies. Owing to the flatness of tuning in the average television receiver, this type of interference is sometimes the worst of the lot. The only remedy is to orientate the aerial system until the reflector comes between the dipole and the offending station, even if it means the sacrifice of a little signal strength on the A.P. signal. There are also various commercial short-wave aerials of extreme directional type. I have seen a dipole with three reflectors which has reduced interference successfully, and some keen amateurs have erected weird and wonderful aerial arrays which include a couple of "directors" in front of the dipole, in addition to a reflector behind. Aerial systems of this kind are easier to talk about than to install and maintain. They cover a big area and require a lot of guy and supporting wires and poles. They are also vulnerable to high winds, storm and tempest. On the whole,

the simple dipole and reflector takes a lot of beating, and I have myself seen excellent pictures thus received as far away as Babbacombe.

Television Relays

There are a number of towns at the extreme range which are unfortunately placed so far as screening is concerned. Brighton, for instance, is screened by the adjacent South Downs, which effectively cut off the possibility of direct television pick-up in the low-lying parts of the town. Hundreds of potential viewers are lost because of the very low field-strength in such situations. On the hill overlooking Brighton, the results are good. Here is a case where the problem would be solved by making use of the relay system. The television signals would be picked up by a "central" receiver, installed in a high and favourable position. Using Post Office lines, the signal would be sent to subscribers, who would feed the signal through to amplifiers, loudspeakers and cathode-ray tubes. But even in Brighton itself, good reception has been obtained in some parts of the town—usually with the aid of a very high aerial.

Television results are indeed capricious at such distances, and it is always worth "trying your

luck" if you are able to persuade a dealer to make a temporary installation.

Television and "Prefabs"

I am interested to note that the broadcast receiving aerial is considered to be an integral part of some of the new prefab bungalows, and is sometimes attached decoratively as part of the design. The aerials usually take the form of a vertical tube, a type of aerial which is becoming increasingly popular for general use. How much pleasanter these are than the unsightly, badly erected aerials one sees in many suburban back gardens. It wouldn't be very much more expensive for the prefab manufacturers to go one step further and incorporate a dipole aerial into the design. The cost would be increased by a very small amount only, and the tenant could use it for his ordinary radio receiver until he decides to purchase a television set. Of course, the "badge" of the dipole might lead the Post Office official "snoopers" to think that a £2 subscription is due. But think of the satisfaction to be derived from the act of pointing out the mistake, and frustrating just one of the army of form-filling officials with which we are now inflicted!

A Simple Lightning Arrester

THIS quickly made lightning arrester was improvised from an old broken-down mains switch. The switch mechanism was first entirely dismantled and the parts discarded, except for the two connecting sockets with their fixing nuts and washers. The two mouldings were both thoroughly cleaned inside.

Next, two similar plates were cut from stout gauge sheet brass to fit exactly each side of the recess in the porcelain moulding. On the inner faces of each plate were cut a number of teeth. The plates were cut of such a width as to allow the teeth in each just to clear each other when the plates were assembled in the recess. This clearance between teeth was made to measure approximately 1/32in. Two lengths of single rubber-covered flex were then passed from the base of the moulding through the original fixing holes, and their bared ends secured to the plates by means of the original wire connecting sockets.


The switch cover was then refixed by means of the original set screws, sealing compound from an old H.T. battery being used to seal up the opening formerly occupied by the switch toggle.

Further, the meeting edges of the two halves of the moulding and the set screw holes were treated with sealing compound, spread on by means of a heated knife, to make the assembly quite waterproof.

The completed arrester was then connected directly between aerial and earth by means of the two lengths of flex. The arrester will offer an easy path (across the small air gap between the teeth) to any sudden lightning discharge striking the aerial, whilst the capacity is so minute as not to interfere with the reception. If a lightning-change-over switch is already fixed, outside or inside the house, this need not be dismantled, and

may be used in conjunction with the arrester described. The arrester itself works automatically, needs no switching and will need no further attention once fitted.

The most important point, of course, is the construction of the brass plates. They should seat themselves exactly in the recess and no lateral movement should be possible, even without their respective connection sockets tightened up. A few minutes careful filing and shaping will achieve this exact fitting, and it should never be possible for the teeth in the two plates to touch. A thin sheet of mica could, of course, be inserted between the two sets of teeth to make doubly certain.

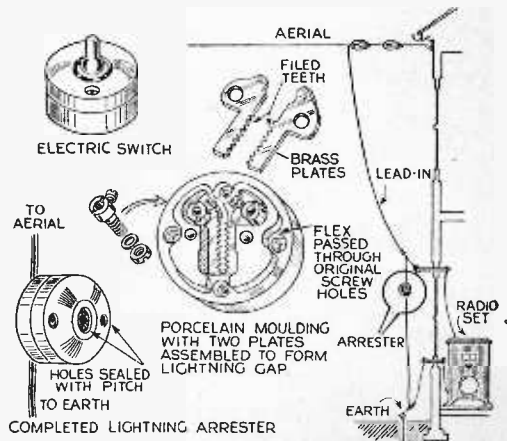

Constructional details of the lightning arrester described above

Pitman **RADIO** Books

CATHODE RAY TUBE HANDBOOK

By S. K. Lewer, B.Sc. Second edition. 6s. net.
 "An excellent survey of the basic principles of the tube leading to the complete oscillograph, with a surprising amount of interesting allied information."—ELECTRONIC ENGINEERING.

RADIO RECEIVER SERVICING & MAINTENANCE

By E. J. G. Lewis. A practical manual specially written to give the radio dealer and the service engineer up-to-date and reliable assistance in the technical details of their work. A handy fault finding summary is a feature of the book. Third edition. 8s. 6d. net.

RADIO SIMPLIFIED

By John Claricoats. Specially prepared for those requiring a sound basic knowledge of the subject in the shortest possible time. Explanations are simple and lucid and there are many diagrams to illustrate the text. Second edition. 4s. 6d. net.

Parker Street, **PITMAN** Kingsway, W.C.2

CLIX

Radio and Television Components
are used by all the leading set manufacturers

★


Points of Low Contact Resistance in Circuit Design of Miniature Receivers

B7G

Miniature

Laminated Valveholder

for use with IT4, IR5, etc.

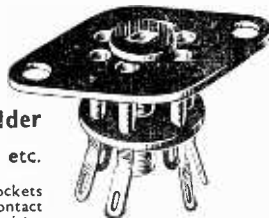

Designed with 7 special sockets giving extremely low contact resistance and ensuring positive location of pins. Tags and centre screen pre-tinned. Fixing centres .875, Hole Dia. .100.

PLATE DIMENSIONS: Major axis 1.093, Minor axis .680. For mounting either above or below chassis.

BRITISH MECHANICAL PRODUCTIONS LTD.

21 BRUTON STREET, LONDON. W.1 Telephone: MAYfair 5543
Foremost in Valveholder design

EX AIR MINISTRY

Components



Thermo coupled RF ammeters, .5 amp., 2in. dial, by leading maker. 15/-



Moving coil meter, 30m.a. scale; movement 5m.a. shunted, 2in. dial, by leading makers. 15/-



3-gang condenser, 50 mmfds. per section extension shaft and knob. 7/6

2-gang ditto. 5/6




Relay D.P.C.O. with activating coil. 2/6



Short wave tuning condenser, 250 mmfds, midget type, with epicyclic reduction drive, bakelite control knob and degree dial. 5/-

Post Orders add 9d.
Write for list of other bargains.

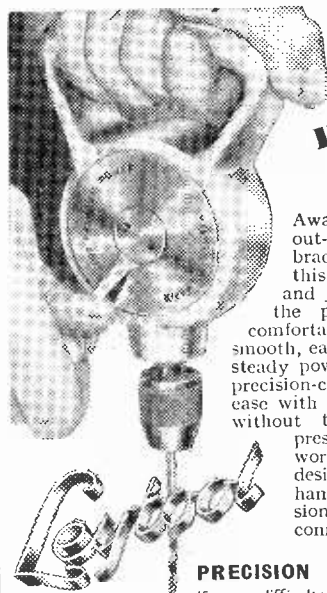THE STAMFORD RADIO CO.
199, STAMFORD STREET,
ASHTON-UNDER-LYNE, LANCS.
Telephone: ASHton 1964.




A PLEASURE TO USE

Away with your old, out-of-date hand drill brace! Get your hand on this new "Leytool" drill and feel the difference in the perfect balance, the comfortable hand grip and the smooth, easy action. Note the steady power produced by the precision-cut gears, and the ease with which it does its job without the need for body pressure. Here is a noteworthy improvement in design on all previous hand drills... a precision-made tool without compare.

PRECISION HAND DRILL

If any difficulty in obtaining locally, send your order direct, or write for fully descriptive leaflet. 24/-

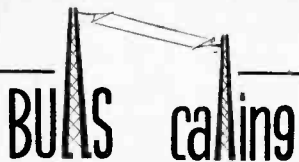LEYTONSTONE JIG & TOOL CO., LTD.
LEYTOOL WORKS, HIGH ROAD, LEYTON, LONDON, E.10.



YOU, advising to write to **J. BULL & SONS (P.V.)**, 246, High Street, Harlesden, N.W.10 or call at the above address. Bus 18b, Troleys 662, 664. Tube or L.M.S.: Willesden Junction.

Phone: ELGAR 4448-74 (extension 5). Wire: BULLRAD HARLES LONDON.

CABLE: BULLRAD LONDON for RADIO VALVES: British and American, from 5/10. All at official List Prices, not increased since 1946.

HUMAM. D6, 5B, 250A, 6B6, 6C8, 6X6, 6K7, 6SJ7, 6SN7, 6T7, 6V6, 7B5, 7B7, 7B8, 7C6, 7D5, 7Y4, 8D2, 9D2, 10D1, 11D3, 11D5, 12SR7, 25Z4, 1D5, 15D2.

COSSOR. 4TPB, 4TSP, 135FA, 41MP, 41MPT, 41MRC, 4200P, 42-OT-DD, 42P7B, 203THA, 210DG, 210LF, 220OT, 220P, 220PA, 807, DDLA, MP/PEN, MS/PEN, MS/PEN B, MVS/PEN, MVS/PEN B, OM4, OM6, OM9, PT10, 2P, 13VFA, 41MSP, 41SPT, 42P7B, 202VFB, 210DDT, 215SG, 220HPT.

HIVAC. XD1, XH, XL, XP, XSC.

MARCONI—B30, CRT-EB102/B, 7D1, D42, D62, DA30, DL63, DL74M, DN41, GTC, G50, H30, H63, HA2, HD24, HL2, KT2, KT4, KT4A, KT83, KT86, KT74, KTW61, KTW83, KTZ41, KTZ63, KTZ73M, L63, LP2, MH41, ML4, MS4B, MSP4, N14, P2, PT25H, PX25, QP21, 523, U1P, U17, U18, 2U, U50, U52, U74, V1PAC, VM43, W21, W42, XH1, X61M, X65, X71M, Y83, Z14, DG2, DS, HL2K, LTB, LSSB, MKT4, U23, X31, X41c, Z22, 301, 302, 303, 304.

MAZDA. AC2PenDD, AC5Pen, AC5PenDD, AC6Pen, ACHL, AC3, AC1, AC4, AC7H, H1V1, ACVPP2, P1, DD207, DD620, HL2D1, HL2D3, HL2D4, HL41, HL41DD, HL42DD, HL13DD, HLDD1320, P41, Pen25, Pen45DD, Pen46, Pen383, Pen45DD, PenD4020, QP25, QP230, SG215, SP22, SP41, SP2220, TH41, TH233, TH2321, TP22, TP25, TP26, TP2620, U6, U7, U7B, V914, VP23, VP41, VP133, VP1322, DCF, DC5G, DD41, DD101, H210, Pen383, UZ5, 300, HU14APD, 2D41, 2D13C, GY2, GY5, 6D8, 6J7, 6L6, 6Q7, 6R7, 16V4, A21, A31, CCH35, CY1, DF51, DL35, D026, D030, DW2, EA50, EB34, EBC3, EBC33, EC52, ECC31, ECH35, EP6, EF39, F60, FF54, EL2, EL3, EL32, EL33, EL38, FM34, RM35, RW45, HL30, H1W, H13, KB32, KF35, KK32, KL35, Pen4VA, Pen42M, PenA4, PM2, PM2H, PM4DX, PM12B, Pn202, QP22B, SP4, SP4B, SP13, 76D, TDD2A, TDD13C, TH4E, TH12C, TH30C, TH4, U32, U33, V7, V7A, V74B, V74C, VP13A, DF33, DW4350, EBC32, EF22, EL35, EL50, HVR2, HVR2A, PM2LD, PM5B, PM22A, PM22D, SP13c, UY31.

PHILLIPS. Cl, C1C, 328, 329, 340, 357, 452, 1012, 1038, 1120, 1551, 1729, 1738, 1821, 1904, 1912, 1914, 1920, 1928, 2030.

TUNGSRAM. 5Z4, 6B8, 6J5, 6V6, 6X5, 25Y5, 807, APP4c, AAP4C, DD13, DD818, ECH2, EF12, EH2, EL5, EL11, EM4, E24, HL33, HP13, IP1018, HP1118, HP2018, HP2118, H141, H151, MH1108, MH1105, LD210, LL25, MH19, PP6E, SP2B5, SP4B, SP4S, SS210, VP4S.

AMERICAN. OZ4, 1A4, 1A5, 1B4, 1C5, 1D7, 1E5, 1E7, 1F4, 1F5, 1F6, 1F7, 1G6, 1H4, 1H5, 1H6, 1L6, 1L6G, 1L75, 1N5, 1S4, 1S5, 1T4, 1T5, 2A6, 2A7, 2B6, 2B7, 5U4, 5V4, 5Y3, 5Z3, 5Z4, 6A4, 6A6, 6A6E5, 6A6E, 6AG6, 6B7, 6B8, 6C5, 6C6, 6D5, 6D6, 6D8, 6E6, 6F5, 6F6, 6F7, 6G6, 6H6, 6J5, 6J7, 6J8, 6K5, 6K6, 6K7, 6K8, 12K7, 6L5, 6L6, 6L7, 6N7, 6P7, 6Q7, 6S47, 6S7, 6S77, 6S77, 6SN7, 6T7, 6V6, 6X5, 6Y5, 7A6, 7A7, 7B5, 7B6, 7B7, 7B8, 7C5, 7C6, 7H7, 7S7, 7Y4, 10, 12A, 12A5, 12A6, 12B7, 12J5, 12K8, 12K7, 12S47, 12F5, 12SRT, 12Z5, 13A7, 15, 17, 18, 20, 23, 25, Y5, 25Z4, 31, 32, 33, 34, 35Z5, 37, 38, 39, 48, 49, 50, 53, 55, 57, 59, 71A, 77, 79, 80, 81, 82, 83, 89, 807, 954, 955, 956, 117Z6, 1299A, 9001, 9002, 9003, 9004, 9005. Further types just in: LL4, 6A3, 6AG5, 6AG7, 6AK5, 6B4, 6C8, 6E7, 6F8, 6SK7, 6SL7, 7C7, 12SJ7, 12SK7, 12SN7, 12SQ7, 2Z55, 26, 29, 78, 18, 37, 39, 44, 41, 42, 43, 76, 84, and 101 more types. Order C.O.D. STOP PRESS—BULLS BIRMALIZING 12A7 and 25A7, particulars 5d.

PRATTS RADIO

1070 Harrow Road,
LONDON, N.W.10
(Nr. SCRUBS LANE)

Phone: LAD 1734.
SPEAKERS.—P.M. L/Tr. 21in. 25/-; 31in. 29/-; 5in. 18/-; 61in. 21/-; 8in. 21/6; 10in. 38/6.

TRANSFORMERS.—350-0-350v. or 275-0-275v. 4v. or 6v. 63v. C.T. 29/6; speaker transfrs., midget universal 5/-; multi-ratio, 5 watt, 7/6; 30 watt, 22/6; I.F. transformers, Weymouth midget, 18/6; standard, 15/- pair (465 k.c.s.).

VARIABLE CONDENSERS.—2 gang .0005 with trimmers 12/6; less trimmers, 11/6; Dielectric, .0005 and .0003 mid. 4/6 each; preset, .0005, 2/3 each; .0001, 1/3 each; 50 pf. 9d. each.

COILS.—Midget 300 ohm, 4/9; standard 60 m. 20 by 300 ohm, 6/3; 20 by 450 ohm, 25/0 m. 24/6; 150 m. 21/-; 90 m. 9/6. **MAINS DROPPERS.**—3 amp. 800 ohm, 5/-; 2 amp. 1,000 ohm, 4/9 (inc. feet and sliders); linecord, 3 amp. 60 ohm, per ft., 3-way 8d. ft., 2-way, 7d. ft.

CONDENSERS.—Most types in stock. **COILS.**—Weymouth coil packs, 38c.; L.M. and S. wave coils, aerial and osc., 465 k/c.s., 11/6 set; L. and M. wave coils with reaction, 9/- pair, dual range coil with reaction, 4/6 each; Variable P coils, 3/- each.

MISCELLANEOUS.—Midget L.F. transfrs. 3-1, 5/6; 5-1, 5/9; volume controls, less sw., 3/6; with sw., 6/6; valveholders, paxolin, 7/4; amphenol, 9d.; knobs 1in. to 2in., 6d. to 10d. each. Plus, solder, dials, slow motion drives, T.C. wire, vibrator, everything for the radio amateur. Overseas orders invited.

VALVES.—6K7, 6J7, 1C5G, 1H5G, 1N5G, 6A, 6C8, 6D6, 12SK7, 6R7, 77, OZ4, 6J7C/T, 5Z4C, 6Y3C, 5U4C, 6B8G, 12SR7, 35Z4, 6H6, 6L6G, 6V6G, 6F6G, 6K6G/T.M., 12J5G/T, 6X5G, 6F5G/T, EF39, EL33, FL32, TP22, 7P, VP13C, MS4B, AZ31, U403, Pen45DD, 3914, etc. S.A.E. for list or advice. Orders over 30/- post free C.O.D. or C.W.O. Buses 662, 664, 18B pass door.

NEW UNUSED GOODS 10Y.

GALPINS

ELECTRICAL STORES
408, HIGH STREET, LEWISHAM,
LONDON, S.E.13.
Telephone: Lee Green 0309. Near Lewisham Hospital.

TERMS: CASH WITH ORDER. NO C.O.D.

EX-R.A.F. CRYSTAL MONITORS TYPE 2. 3-valve Battery working, complete and ready for use less valves and xtals, operational frequency depends on xtal frequency, condition as new. Price 19/6 each, plus 1/6 carriage. Complete in carrying case, size 8 1/2 in. x 6 in. x 6 in.

EX-R.A.F. MICROPHONE TESTERS. These consist of a Ferranti 2 1/2 in. m/coil 0 to 1 m. meter with Westinghouse Rectifier incorporated, calibrated at present 0 to 10 volts, microphone transformer, jacks, etc., all contained in polished steel case, size 6 1/2 in. x 5 1/2 in. Condition as new. Price 37/6 each.

EX-G.P.O. (AMERICAN) VIBRATOR PACKS. Type M222, 4 volts D.C. input, output 100/120 volts A.C. 20/30 ma. New and unused, 27/6 each, carriage 2/6.

METERS. All first grade moving coil instruments, new, boxed, ex-Govt., 0 to 40 volts, with series resistance removed. 5 ma. 15/- each, 0 to 10 amp. 15/-, 0 to 1 ma. 21/-, All 2in. scale and by well-known makers.

VOLTAGE CHANGER TRANSFORMERS. Ex-Govt., auto wound. Tapped 0, 10, 20, 25, 90, 130, 150, 190, 210, 230 volts, 1,000 watts, all tapping at 1,000 watts. New and unused 25/10/- each, carriage 5/-.

EX-NAVAL CATHODE RAY RECTIFIER UNITS. New and unused, sold for components which consist of:—2 x 5 mf. 2,500 v., 1 x 1 5,000 v., 6 x 2 mf. 800 v., 2 x 8 mf. 800 v., approx. 15 volume controls, various values, approx. 100 small condensers and resistances, smoothing choke and 9 v. holders, including 3 EF50 and 1 tube base. All components wired and with the addition of mains transformer would make a good oscilloscope. Price 55/-, carriage paid.

EX-R.A.F. AERIAL COUPLING UNITS, absorption type. Range from 1.2 to 5.3 mcycles, 10/- each, post 1/-.

ELECTRIC LIGHT CHECK METERS, for 200/250 volt 50 cyc. 1 phase, ideal for subletting, etc., guaranteed electrically 2 1/2 amp. load 12/6, 5 amp. 12/6, 15 amp. 20/-, 20 amp. 25/-, 30 amp. 30/-, 40 amp. 35/-, 50 amp. 45/-, 100 amp. 50/- each, plus 1/6 carriage extra.

EX-R.A.F. I.F.F. UNIT (Model) 3002 complete with 10 valves types 3X70E, 1E5F0, 4VR65, 2XYT61A, and rotary converter 12 volts input 450 volts 40 ma. output. These units are as new. Price complete, 23/10/- carriage paid. Ditto Model 3009, 24 volt input, 23/- carriage paid.

EX-R.A.F. R.F. UNITS TYPE 110A. New and unused, consisting of 5 valves, including grounded grid 750 mcly. tube, small 12 volt motor and numerous other components, would make very useful cracker. 55/- each, 5/- carriage.

EX-R.A.F. RADAR IMPULSE TRANSFORMERS (new, boxed). We have no actual data on these, but believe them to have an output of 15,000 volts at 3 kV, for a micro second. A bargain for the experimenter at 10/6 each, P.F.

L.T. RECTIFIERS (new), 6 volts, 1 1/2 amp. 7/6 each, 12 v. 1 1/2 amp. 10/6 each, 9d. post. Instrument Rectifiers, S.H., 10 to 20 ma. types, 4/6 each.

VOLTAGE CHANGER TRANSFORMERS, auto wound, fully guaranteed, immediate delivery, all tapped 0, 110, 200, 220, 240 volts, 250 watts, 45/-; 350 watts, 55/-; 500 watts, 70/-; 1,000 watts, 25/15/-; 2,000 watts, 28/15/-.

YOU can become a first-class RADIO ENGINEER

We are specialists in Home-Study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

T. & C. RADIO COLLEGE

NORTH ROAD, PARKSTONE, DORSET.

(Post in unscaled envelope 1d. postage.)
Please send me free details of your Home-Study Mathematics and Radio Courses.
NAME
ADDRESS
P. 81

News from the Clubs

WREKIN AND Y.M.C.A. AMATEUR RADIO SOCIETY
Hon. Sec. : T. L. Stevens, Sunny Cottage, Donnington Wood, Wellington, Shropshire.

THE above society held a further meeting at their H.Q., Y.M.C.A., Wellington, on Thursday, February 27th, when it was decided to amend the name of the society to read as above. The society now has a private room with workshop facilities; each member will be issued with a key giving him access to the room at any time.

Morse code instructions are now under way.

Sub-groups, such as transmitter, receiver, aerials, V.H.P., etc., are being formed.

Negotiations with the G.P.O. for transmitting facilities are now in progress.

Members will now meet on Monday, Thursday and Friday evenings each week, Friday being the evening for the business meeting.

NUNEATON AMATEUR RADIO SOCIETY

Hon. Sec. : B.R.S. 13,684, A. R. Stringer, 6, School Hill, Chapel End, Nuneaton.

A CLUB is now being organised and will be run on similar lines to other clubs around the district. Anyone who is interested in radio communication and short wave enthusiasts are invited to write for full particulars to the secretary.

WIGAN AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec. : H. King, 2, Derby Street, Spring View, Wigan.

THE club is still more active with the granting of its call, viz., G3BPK. The TX has been completed and aerial masts are under construction. The station is licensed for 'phone and C.W. on all bands, but will operate temporarily on 40, 20 and 10. At a later date operation on 80 and 160 is anticipated, and all members are looking forward with enthusiasm to future contests.

CHEADLE (STAFFS) AND DISTRICT AMATEUR RADIO SOCIETY

WITHIN three months this club has made enormous strides. Classes have already started in the following subjects:

Morse, Elementary Theory, Receiver Theory and Design, Transmitter Theory and Design, Aerials, and Workshop Practice and Measurements.

All tutors are qualified wireless officers, and the club now has 13 licences to its credit. This constitutes a record, as the population-ratio of licences in this country is about one in 30,000; Cheadle has one to every 680 people and more coming up.

THE STOURBRIDGE AND DISTRICT RADIO SOCIETY

Hon. Sec. : D. Rock, Flat 1, Block 1, Worcester Road, Summerfield, nr. Kidderminster.

AT the general meeting of the above-named society, held on April 1st, 1947, there was a very good attendance to hear a most interesting lecture, together with demonstration. This was conducted by Mr. C. Young (G2AK), of Birmingham, who erected a portable radio transmitter and receiver working on 5 metres. During the description and explanation of this equipment he demonstrated its operational capabilities by contacting the vice-president, Mr. H. Littley (G2NV), of Stourton, who spoke to the society from his home.

The lecture was in non-technical language, and the members were entertained to the full.

ST. PANCRAS RADIO SOCIETY

Hon. Sec. : H. Brown, 84, Blenheim Gardens, Willesden Green, N.W.2.

ALTHOUGH weather and power cuts have taken a toll of attendance during the past few months, these have now returned to normal and the club is looking forward to a very active period next session.

On Saturday, June 28th, it is hoped to participate in an "Open Day" Exhibition of the Kentish Town Men's Institute where they have their headquarters. It is hoped to demonstrate the activities of the club, and also to let the public see a "ham" at work in his shack. All friends are welcome as are all those interested in wireless.

THE WEST BROMWICH AND DISTRICT RADIO SOCIETY

Hon. Sec. : R. G. Cousens, 38, Collins Road, Wednesbury, Staffs.

THE club now has over 30 members on its books, and meetings continue to be held weekly at the "Gough Arms" Hotel, Jowetts Lane, West Bromwich, at 7.30 p.m.

The subjects of recent talks were:

"5-metre receivers—straight and superhet," by G8NC.

"Simple Transmitters," by G2BJY.

"Measuring Instruments," by Mr. L. Harrison.

"Radio Interference—Its Causes and Cures," by a G.P.O. engineer.

A film show is being arranged for the near future, the previous one being very popular.

Members are taking it in turn to construct the club field day transmitter, for which a transmitting licence has already been granted by the G.P.O.

RADIO SOCIETY OF GREAT BRITAIN (BRIGHTON AND HOVE GROUP)

Town Representative : Lt.-Com. J. R. D. Sainsbury, 80, Lansdowne Place, Hove.

THERE has been a good deal of activity in the area recently—meetings take place on alternate Mondays at the Golden Cross P.H., Western Road, Brighton, commencing at 7.30 p.m. It is known that there is still a small number of members living in the area whose names and addresses are not known to the T.R. Circular letters giving local news and details of meetings are sent out periodically and it is therefore requested that any member who has not so far received such a circular communicate with the T.R. or with any member of the local committee.

At a recent meeting, Mr. Crabtree demonstrated the modern method of lining up a superhet., using a P.M. oscillator and a 'scope. On another occasion, Mr. Geof. Johnson gave an interesting talk on power supplies and mentioned a number of modifications to improve stability. He also gave a useful cascade doubler circuit not generally known.

A radio quiz, organised by Mr. Epton, was the main subject of another meeting. This was a great success and members voted in favour of another at an early date. 3APO excelled in answering questions on international prefixes, many of which fooled other competitors.

So far as future activities are concerned it is not possible to make any announcement. Negotiations are in hand to arrange for demonstrations by manufacturers and talks by well-known people. Something of interest will be laid on for each meeting and members notified in due course.

G5ZQ, having had a long battle with the local Council, has at last obtained permission to erect masts at his QTH. By the time this is in print they should be up and a 150 watt P.A. should be in use.

PROPOSED CHELMSFORD AND DISTRICT CHAPTER, INTERNATIONAL SHORT WAVE LEAGUE

MR. W. C. MILLS, ISWL/G26r, of 3, Elm Cottages, Broomfield, Chelmsford, is anxious to form a club in Chelmsford under the above name. The I.S.W.L. will give the club full support. Will all hams and S.W.L.s interested contact Mr. Mills at above address?

Programme Pointers

Further Comments on a Concert Programme Plebiscite.

By MAURICE REEVE

GREAT minds sometimes think alike. Just about the time that my last article appeared, I attended a concert at the Albert Hall. What did I find inside the programme? Why, nothing less than a slip of paper on which I was invited to record my ideal concert programme. There were spaces marked a, b, c and d. . . . The concert was the popular orchestral type plus pianoforte concerto, and the question was being asked by the agent.

Now, my idea of a plebiscite would be something much more exhaustive and, consequently, in the long run, much more selective and valuable a guide to programme building than this. I do not set out just to ascertain what sort of entertainment people want on a Sunday afternoon—the particular concert in question was of the Sabbatarian postprandial variety only. I want to know what different types of people want on different days and at different times of the day; also in different halls—or listening in, and even at different prices, or no price at all!

Supposing, for example, the concert agent referred to above collected a thousand plebiscite slips and, after careful analysis, found that that afternoon's particular audience preferred the following programme—or type of programme:

- (a) Overture, "Le Carnaval Romain" (Berlioz)
- (b) Pianoforte Concerto in B flat minor (Tschaikowsky)
- (c) Suite, "Casse Noisette" (Tschaikowsky)
- (d) Symphony No. 5 in C minor (Beethoven)

and decides to give "the public" what it asks for. A very varied and long concert-going experience tells me that if he mounted that programme at any time or in any place he would get some of the shocks of his life.

Every type of concert produces its own reactions, born very largely of its own traditions and historical associations. If these reactions, or aesthetic demands, are not met, or, what is even worse, if they are outraged in any way, the results are plain to see in diminished and disgruntled audiences. To take an extreme, hypothetical, case. Kodaly's brilliant suite "Hary Janos" as played at the Promenade Concerts, with the zylphonist wearing Hungarian national costume and receiving his own personal ovation, would be hugely frowned upon at one of the classic symphony concerts. Although the work is in the repertory of most orchestras, the zylphonist would be denied his personal glory and would appear as an ordinary member of the orchestra. Conversely, what we pay several shillings to hear at a symphony concert in January may be less acceptable for two shillings standing in the promenade in August.

All this would have to be carefully sorted out. We must be most wary against giving people what they don't want just because we have carelessly offered it to them at the wrong time. The resulting empty seats may only be caused by this and not because they were given something which they didn't want "no how nowhere."

How Many Concerts

How many types of concerts are there? I am, of course, dealing with symphony concerts and not with specialist recitals for solo instruments. Well, the three which obviously draw the largest audiences—whose wishes should first of all be consulted—are, of course, the B.B.C. studio concerts, the Promenade Concerts and the B.B.C. Symphony Concerts, both in the provinces and London. In addition, but the most important from the commercial and "musical well being" point of view, are the series of winter symphony concerts, usually about eight to 10 in number, and dependent almost entirely on box office support. It is these concerts which are now beginning to suffer from the decline in the wartime boom, and whose audiences are rightly tired of the fare they have had dished up to them for so long. I feel that if there is anything we can do to help maintain the patronage they enjoyed during the war years and immediately after we should do it, and if they are losing that patronage through faulty programme building then the obstacle should not be too big to overcome. It is only one of the difficulties. I know. A glutted market is a bigger one.

The Promenade Concert programmes may, with some truth, be said not to be in need of interference. The public support they enjoy could be cited as proof. But doesn't that also serve as a cry to the organisers of the less prosperous series? We can almost hear the plea, "Give us the programmes we want and we, too, will buy the seats." It is in the attempt to provide *not* "the public" but the *different* concert-going publics that I submit the following questions.

When do you like attending a symphony concert best—time, day, season? This is very important and will give the clue to many of the items voted for).

Your favourite symphonic writer? Your favourite concerto writer? Do you like the one-composer programme? Do you prefer the austere classical composer such as Bach, Beethoven, Brahms? Do you prefer the more flamboyant type like Tschaikowsky or Dvorak? Do you prefer symphony concerts with or without a concerto? About how many symphony concerts do you attend in a year? How many do you listen-in to in a year? Which forms do you prefer, symphonies, concertos, overtures, suites, operatic scenes and excerpts?

These are the questions which my plebiscite would set out and seek answers to. Naturally, the whole thing would appear more cut and dried, and business like, than it does here. But I do think that, were this properly organised and responded to, a major problem might be solved. And the B.B.C. seems obviously the most suitable authority to suggest it to.

If the Tschaikowsky and Rachmaninow war horses were voted out of programmes as a result, then pianists would have to stifle their annoyance and *amour propre* and get down to it and learn something new for a change.



THIS MONTH'S
SPECIAL OFFERS

with Webb's Unconditional
GUARANTEE of satisfaction

EDDYSTONE
Non-Standard Microdensers.

5 mfd. 3,000 v. spacing. Useful for U.H.F. tuning and neutralising ... 1/6
100 p.f. normal spacing. Brass finish, for short wave tuning, etc. 3/6

ERIE CERAMICON tubular ceramic condensers for H.F. work. 12, 75, 85 and 100 p.f. All ... 1/-

HEADPHONES. Webb's Light-weight by Browns, 2,000 ohms... £1 5 0
Brown's type "K" Moving Coil Phones for high fidelity reproduction ... £5 5 0
Matching Transformer for "K" phones, 7,000 to 90 ohms ... 7/-

Special Offer
B.T.H. HEADPHONES
4,000 ohms. Complete with cord and plated headband. Per pair ... 9/-

BOOKS. Two useful and informative technical publications.
"Wireless Servicing Manual" (Cocking) 360 pp. ... 10/6
"Television Receiving Equipment" (Cocking) 380 pp. ... 12/6

"AMATEUR RADIO PRODUCTS."

Four Band Coil Unit, assembled on sub-chassis with 4 coils, trimmers and wave-change switch. Complete with circuit details for assembly into an efficient two-valve "straight" receiver. Wave range 9.7 to 208 metres. Price of Coil Unit... £1 10 0

WEARITE "P" COILS now available in entire range. All 3/- each

DENCO. We are recognised stockists of the Denco range of H.F. components (DENCO "MAXI Q" plug-in octal iron-cored inductances now available.)

WEBB'S RADIO,
14, SOHO ST., OXFORD ST.,
LONDON, W.1.
Note our SHOP HOURS : 9 a.m. to 5.30 p.m.
Sats., 9 a.m. to 1 p.m.
Telephone : GERrard 2089

COULPHONE RADIO

Prop. C. COULBORN : G3AJM
"THE RETURN OF POST MAIL ORDER SERVICE"
Note New Address :
58, Derby Street, Ormskirk, Lancs.

Phone ORMSKIRK 496.
New Goods Only—C.O.D. or cash with order. All orders over 5/- post free. A few of our lines are listed below, send 2/d. stamp for latest 24-page catalogue.
Valves.—All B.V.A. and Tungstram, including American.
Eddystone short wave gear. S.W. Manual. 2/6.
Mains Transformers. — Interleaved and Impregnated. For 200 250v. mains, 300v. 60 mA. 4v. or 6v. L.T.S. 23/6 ; 350v. 100 mA. 4v. or 6v. L.T.S. 28/6 ; 450v. 200 mA. with three L.T.S. 4v. or 6v. 45/-.
Smoothing Chokes.—40 mA. 5/- ; 60 mA. 6/- ; 90 mA. 7/- ; 100 mA. 12/6 ; 200 mA. 21/6.
Speaker. Transformers. — Midget Power Pen. 40 mA. 5/6. Std. size Push-Pull Universal, 60 mA. 6/6 ; Heavy Duty. P.-P., 22/6. Extra H.D. 100 mA. 37/6.
Mains Dropper Resistors, with feet and two sliders. 2 amp. 4/3 ; .3 amp. 4/6. Resistors 1w. 6d. ; 1w. 9d.
Loud Speakers P.M. 2 1/2in. 25/- ; 3 1/2in. 28/6 ; 5in. 20/6 ; 8in. 23/6 ; 10in. 35/-.
With Trans. 8in. 29/6 ; 10in. 42/6.
Weymouth Tuning Coil Pack.—Completely wired. Short, Medium and Long Wave Superhet type for 465 kc.s. 1.P., 36/6. Midget I.F.T.s. 18/9.
Line Cord, 60/70 ohms per foot. .3 amp. Note price per yard. 2-way, 2/2. 3-way, 2/6. 14.36 flex 6d. ; 23.36 flex 7d.
Tuning Condensers.—Midget 2-gang .0005 with 2-speed drive 16/6. L.Dr. 11/6.
Aluminium Chassis 3in. deep, 10in. x 8in., 9/6 ; 12in. x 8in., 9/6 ; 14in. x 8in. and 16in. x 8in., 10/6 ; 20in. x 8in., 12/6.
EXCLUSIVELY MAIL ORDER.

BULGIN


A Name famous in Radio



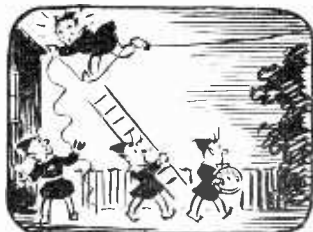A. F. BULGIN & CO., LTD.
Bye Pass Road, Barking, Essex
Tel: RIPPleway 3474 (5 lines).

POST-WAR TELEVISION

The advance in Radio Technique will offer unlimited opportunities of high pay and secure posts for those Radio Engineers who have had the foresight to become technically qualified. How you can do this quickly and easily in your spare time is fully explained in our unique handbook. Full details are given of A.M.I.E.E., A.M.Brit.R.F.E. (City & Guilds) Exams, and particulars of up-to-date courses in Wireless Engineering, Radio Servicing, Short Waves, Television, Mathematics, etc., etc.
We guarantee "NO PASS—NO FEE." Prepare for to-morrow's opportunities and post-war competition by sending for this very informative 112-page guide NOW—FREE and without obligation. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 242), 17, Stratford Place, London, W.1.



The "Fluxite Quins" at Work
"I'll soon fix the aerial tight,"
Said Oh, "with a spot of FLUXITE."
"Ah, the ladder!" cried EE,
"I'll borrow it, see,
Or we'll never get finished to-night!"

See that FLUXITE is always by you—in the house—garage — workshop — wherever speedy soldering is needed. Used for over 30 years in government works and by the leading engineers and manufacturers. Of all ironmongers—in tins, 10d., 1/6 and 3/-.

To CYCLISTS: Your wheels will NOT keep round and true unless the spokes are tied with fine wire at the crossings and SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT.

The FLUXITE GUN puts FLUXITE where you want it by a simple pressure. Price 1/6, or filled, 2/6.



ALL MECHANICS WILL HAVE

FLUXITE
IT SIMPLIFIES ALL SOLDERING

Write for Book on the ART OF "SOFT" SOLDERING and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE, also on "WIPED JOINTS." Price 1d. EACH.
FLUXITE LTD. (DEPT. W.P.),
BERMONDSEY ST., S.E.1.

LONDON CENTRAL RADIO STORES

"WESTECTORS." Type W.X.6. New. 1/6 each.

TUNING CONDENSERS. Single .0005. Best quality, air spaced, 1in. spindle. New. 3/6 each.

CONDENSERS. Split Stator, 2-gang. 10/6.

TAXLEY TYPE SWITCHES. 2-pole. 6-way. 2/6.

VIBRATORS. 12 volt, 4 pin. New, with holder, 0/6 each.

WIRE WOUND POTS. Resistance 400 ohms and 25,000 ohms. 1/9 each.

We have a stock of **R.A.F. VALVES**, every one guaranteed. EF50, BL63, X85, MHLD6, SP41, EBC33, KT602, 8D2, EB34. All at 5/6 each. For 6 at 4/6 each. Ask our price for three, six and twelve dozen lots.

ELECTRO MAGNETIC COUNTERS. 500 ohms coil. Counting up to 9,999. Operating from .25v. to 50v D.C. Many industrial and domestic applications. (S.H. and G.P.O., all perfect.) Postage 0d. 5/6.

PRESS BUTTON UNITS. 4- or 5-way, with Buttons, 4/6; 7- or 9-way, with Buttons, 5/6.

SELF-ENERGISING TABLE MICROPHONES AND HEADSETS. The microphone is mounted on a fully adjustable stand with on-off switch. No batteries or current required to operate. Unused in cartons, complete. 1 set 25/-, 2 sets 45/-.

PLUGS AND JACKS. These ex-Govt. Jacks have powerful phosphor-bronze springs, ensuring a perfect contact. Overall length 3in. (including 1in. threaded shank). Supplied with nut for panel mounting. Price complete with best quality plug, 2/6. Postage 0d.

EX-GOVT. HIGH SPEED RELAYS. 6/6. For details see March issue.

SLIDING RESISTANCES, heavy duty type resistance, 14 ohms, 5 amps. Size 13in. long. 13/6.

BARGAIN OFFER in Brand-new Permanent Magnet Loudspeakers. 5in. diam. cone, less transformer, 2-3 ohms, 19/6. 8in. diam. cone, less transformer, 2-3 ohms, £12/6. Goodman's 12in. P.M., 15 ohms, voice coil, less transformer, £8/15/0. Carriage and packing 5/- extra. Single co-axial cable, plastic covered, ideal for television feeder, 80 ohms. 1/- yard. Heavy duty ex-Admiralty projection type P.M. Loudspeaker units, handles 10-12 watts. Voice coil, 15 ohms. New condition £3/17/6.

EX-GOVT. OSCILLATOR UNITS, TYPE 217. These units contain very useful components, including 2 EF50 Valves, 3 P.O. type relays, numerous resistors and condensers, potentiometers, etc. £112/6.

MOVING COIL INSERTS, used in headphones or for mike, V/coil, 30 ohms. 5/- each.

EX-R.A.F. 1155 RECEIVER. Range 7.5 megs to 1,500 kcs. 10 valves, magic eye etc. Every set aerial tested. Need only power pack for immediate use. £17/10/0. Carriage and packing 7/6 extra. No C.O.D. FEW ONLY.

EX-U.S. ARMY ULTRA LIGHT-WEIGHT HEADSETS. Deaf aid type earpieces, 7/8in. diam., with soft rubber ear fittings. 100 ohms. Brand new and packed. 27/6.

CO-AXIAL CABLE. Heavy duty. Plastic covered, suitable for U.H.F. work, television etc. Impedance 80 ohms. 1/- yd.

TELEPHONE LINE OR UNISELECTOR SWITCHES. 25 contacts, 4- and 6-bank operate on 25-50 volts. 4-bank, 28/6 each. 6-bank, 30/- each.

WAVELENGTH SWITCH ASSEMBLY: New 10-bank, 4-way. Spindle length 4in. Brand-new. 5/6 each.

SMALL BRUSH TYPE ELECTRIC MOTORS. 24 volt size. 2in. diam. overall length 5in., spindle dia. 3in. 19/6.


SUPER QUALITY HEAVY DUTY TWIN SLIDING RESISTANCES. 5.4 ohm at 20 amp. 47/6. 12 ohm at 10 amp. 39/6. 70 ohm at 5 amp. 35/2.

23, LISLE ST., LONDON
W.C.2

GERrard 2969

SAIS

WORTHY PRAISE FOR A WORTHY PRODUCT

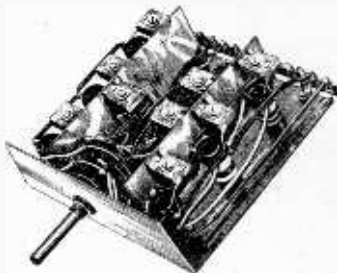

The "blowing of one's own trumpet" is often desirable, but since the introduction of our Model 40 Coil Pack, our customers have been lavish in their praise. One writes: ". . . the 40 Coil Pack is extremely efficient. It saves time in receiver construction . . . performance is excellent."

MODEL 40 COIL PACK

A Superhet Coil Pack with H.F. stage. Uses 9 iron-cored coils in 16-50, 200-550 and 800-2000 metres circuit for 465 kcs. I.F. Aligned and gain tested and complete with circuit diagram. With this coil pack, the amateur without signal generator can construct first class all-wave set. Circuit only, 21/6. 40 Coil Pack, price £3/10/0.

SEND FOR THIS

A comprehensive list is available giving details of other A.I.S. products including the now-famous 30 Coil Pack Series, High "Q" I.F. Transformers, Tuning Heart, High "Q" Iron-cored Coils, A.I.S. Receiver Circuits and so on.

Send 1d. stamp, for this. Mark envelope "P7", for immediate attention.

ALIGNED INSTRUMENTS
SERVICES, 1, COLWORTH
ROAD, LEYTONSTONE, E.11

SAIS

ELECTRADIX Stocktaking BARGAINS!

We offer below some special stock-taking bargains at greatly reduced prices.

HEADPHONES. Ex-G.P.O. single L.R. Receiver type, 5.G.B., with headband and cord, lightweight with bakelite case and cap, 5/- each, or 50/- per doz.

BATTERY superseder. H.T. D.C./D.C. for radio receivers, 6 volt input, 110v. 15 m.a. output, 12 volts input, 230v. 30 m.a. output, ball bearings reduced to 55/-.

D.C. FANS. 110-volt Oscillator type, on table stand with 12in. blade, 35/-, carriage and packing at cost.

TELEPHONES. G.P.O. wall type Telephone constructor's parts with wiring diagram, comprising cabinet with magnetic bell, magneto hand generator, bracket mike, transformer and condenser, switch hook and contacts, single receiver, old price 30/- each, or 50/- pair. Special offer for this month, 35/- per pair.

BUZZERS. The Tiny Townsend high note WIM Buzzer, the smallest Buzzer made; in all good condition, 5/- each.

MICROPHONES. Hand mikes in moulded bakelite case, latest model G.P.O. inset, 4/6. Tannoy hand mike, multi-cell carbon type, metal case with neat switch in handle for sports meetings and announcers, reduced to 12/6; special transformer, 8/6. G.P.O. microphone insets, 2/6.

SEND-RECEIVE Hand-com. All-metal field type, the famous No. 16 Govt. pattern as used in field telephones, mike and earpiece with damaged finger switch, reduced to 5/- each, no cord supplied. 4-way ex-G.P.O. Cord, 5ft. long, 2/6.

TRANSFORMERS. Surplus; double wound 230 volt 50 cy. input, 4 volt centre tapped 7½ amp., 2,000 volt test; sound construction, 17/6 each.

EX-G.P.O. Armoured Microphone insets, 3/6. High ratio Transformer, 4/6. **Telephones,** ex-G.P.O. Candlestick table telephones, fitted latest pattern carbon microphone inset with receiver and cord, 15/-; Moulded bakelite hand combination telephones with pressal switch in handle and cord, 15/-.

DYNAMOS. Special offer 30 volt 5 amp. D.C. enclosed type dynamo, shunt wound, ball bearings, 1,000 r.p.m., £5. Control box with cut-out and regulator, 20/-, 12 volt, 10 amp. Dynamos, £4 10s. 6 volt 10 amp., £4.

MOTORS. Small Sewing Machine motors, 1/20th h.p., high speed, square construction, 230 volt A.C./D.C., with flange, pulley and belt, 90/-; 1/50th h.p., as above without flange, 70/-.

G.P.O. CONNECTION STRIPS. Soldering Tags, Telephone type, moulded base, 60-way, 3/6. G.P.O. 4-way telephone plug only, 2/-; 10-way connection strips, 6in. x 1in., solid brass connectors and terminals 2/- each.

MAGNETS. D.C. Electric magnets, weight 10 oz., lift on 2 volts, 1½ lb., 4 volts 3 lb., 6 volts 4 lb., new surplus, 7/6 each. Permanent powerful flat bar magnets, 2in. x 1in. x 3/16in., drilled 2 holes each end, for any pole pieces, 2/- pair. Send for special Magnet Leaflet "P.W."

ELECTRADIX RADIO

214, Queenstown Road, London, S.W.
Telephone: MACaulay 2159

Impressions on the Wax

Review of the Latest Gramophone Records

AN interesting set of records this month are those by Jean Pougnet (violin), with the Royal Philharmonic Orchestra conducted by Sir Thomas Beecham, Bart. There are three records in the set, five sides of which are devoted to Delius's Concerto for Violin and Orchestra, whilst the sixth side is a recording by the orchestra only of Prelude to "Irmelin," also by Delius.

Although French by birth, Jean Pougnet has received all his training in England from a professor who has taught several other distinguished violinists, and until recently was leader of the London Philharmonic Orchestra. He possesses twin violins, each worth something in the region of £400. He likes to know that, if anything should happen to one of these instruments, he can rely upon having another closely similar in tone and "feel." The numbers of the records are *H.M.V. DB6369-71*.

The recent death of Manuel de Falla robbed music of a highly original composer, whose genius is especially evident in his ballets and the opera "La Vida Breve." This work won a prize offered for the best national opera when the composer was approaching thirty years old, though, ironically enough, it had to wait eight years for its first performance. The "Danse Espagnole" savours much of Spanish folk music, of which Falla was a keen student. The strong rhythms of the Iberian peasantry, constantly appearing in his stage and other works, give his music a vigour and crispness which comes over very well in an arrangement for violin. Kreisler's translation of the "Danse Espagnole" is cunningly laid out for the instrument, and Ginette Neveu's playing of it on *H.M.V. DA1865* is superb. The reverse of the record is occupied by "Hora Staccato," a piece by Dinicu, a Roumanian composer not often heard of outside this favourite of solo violinists.

Recording of "Euryanthe"

THE libretto to "Euryanthe" has proved such a handicap to representations of the complete opera that much fine music has remained tucked away on the shelves. The overture, however, has stayed in the concert repertory. It may be said to consist of two vigorous, stirring dramatic sections separated by the weird tomb motif. Most of Weber's overtures are of the type which contain some of the themes of the ensuing opera, and "Euryanthe" is no exception. John Barbirolli is meticulously careful to bring out the details in the scores he conducts, especially in regard to the strings. He began his musical career as a cellist, and the string section of the orchestra commands his closest attention. This recording of "Euryanthe," on *H.M.V. C3560*, is magnificently vigorous, clear-cut and dramatic: the ensemble of the Hallé Orchestra will be a delight to all lovers of fine orchestral playing.

When Tchaikovsky turned his attention to the string quartet, the sense of melody that makes his orchestral work so delightful served him in good stead. He made of the slow movement of the Quartet in D, Op. 11, a piece so characteristic of his

most melodious style that it has stepped outside the quartet as a whole and is often played independently. Andre Kostelanetz and the Robin Dell Orchestra of Philadelphia should be given a hearing in their attractive new recording of the masterpiece on *Columbia DX1354*. Coupled with it is a well-known number from Tchaikovsky's suite, "The Months"—a delightful Barcarolle.

Vocal Recordings

GWEN CATLEY is one of our most brilliant native sopranos. This month she has chosen an aria which makes heavy demands on the capabilities of any singer. The "Bell Song" from "Lakme" exacts great accuracy of intonation and phrasing, notably in the dazzling bravura passages. Here, Miss Catley gives a really outstanding performance which would convince anyone at one hearing of her very great talent. No wonder she is called the "English Lily Pons." The number of the record is *H.M.V. B9541*.

Both "Lohengrin" and "Tannhauser" are comparatively early works in the Wagner catalogue, and to many listeners the earlier Wagner is more attractive than the Ring dramas and "Parsifal." Joan Hammond's choice this month brings two of the most famous arias from the operas concerned. *H.M.V. C3562* is a distinguished record for the operatic collection.

It has been the fashion to laugh at many of the songs which held the audiences in Victorian drawing-rooms spellbound, but considered dispassionately these pieces reveal admirable craftsmanship and grateful writing for the voice. "The Holy City" is one of these, and as Gladys Ripley sings it one can feel the reasons for its enormous popularity with our grandparents. During the war years Miss Ripley has steadily risen into the front rank of British singers. Handel's "Largo" is on the reverse of this record—*H.M.V. C3549*.

Variety

SWING enthusiasts will be interested in the news that Columbia have started a new swing music series with world-famous artists. It is intended each month to feature the top swing-bands of the U.S.A. in up-to-date recordings, and so build up a valuable series. Among the stars introduced this month is Gene Krupa and his Orchestra, with a recording of "That Drummer's Band" and "Leave Us Leap," on *Columbia DB2290*.

The rhythm-style section of Parlophone is notable this month for the introduction of Artie Shaw and his New Recording Band. America's popular swing maestro now has two orchestras—one for swing and the other with augmented strings. "Let's Walk" and "The Glider," on *Parlophone R3027*, are by his swing combination, with Shaw himself on the clarinet.

Recordings by popular crooners this month include "September Song" and "Souvenirs," by Frank Sinatra, on *Columbia DB2286*; "The Thrill Is Gone" and "Dixie" by Dinah Shore, on *Columbia DB2284*.

COVENTRY RADIO

COMPONENT SPECIALISTS SINCE 1925.

SPECIAL OFFER!

High Grade Microammeters, centre zero 20-0-20 μ A, 3 1/2" straight line scale, edgewise meter. A valuable asset for laboratory or workshop use. £3-5-0 post paid.

COVENTRY RADIO,
DUNSTABLE ROAD, LUTON, BEDS.

BARGAINS IN EX-GOVERNMENT SURPLUS DISPOSAL COMPONENTS

MOVING COIL METERS. 0-50 microamps. Round, flush mounting, 3 1/4 in. dia. Resistance 1,200 ohm. 60/-, 0-500 microamps. 2 1/4 in. dia. flush mounting, Ferranti, 34/6. 0-1 ma. 3 1/4 in. dia. flush mounting, 45/-, 0-30 ma. 2 1/4 in. dia. 2.5 ohm resistance, flush mounting, 26/3. 0-50 v. 2 1/4 in. dia. flush mounting, resistance 11,900 ohms, 18/9. 0-10 amp. 2 1/4 in. square, black scale with white pointer and calibration Sungamo-Weston, 14/-, 0-20 amp. 2 1/4 in. dia. .075 v., with external shunt, 18/9.

SPECIAL OFFER. Everett-Edgcombe moving coil meters. 6 in. scale, calibrated 0-180 v., full scale deflection 0-1 ma. in black bakelite case, size 7 in. x 7 in. x 2 1/4 in. This meter has a magnificent movement and is worth double the price. Provides an ideal base for a multi-range meter 1,000 ohm per volt. Price £6.

SMOOTHING CONDENSERS. Paper: 4 mfd. 500 v. working, 4 1/4 mfd. 1,000 v. working, 11/3. Oil immersed: 2 mfd. 600 v. Aerovox, 1/8; 2 mfd. 1,000 v. Aerovox, 2/6, with ceramic insulators; 4 mfd. 1,000 v. Aerovox, 7/11; 4 mfd. 1,500 v. T.C.C., 12/6; 6 mfd. 1,000 v., 8/8.

METAL BOXES. Steel, size 6 in. x 6 in. x 6 in., lift-up lid, undrilled, 2/6. Short Wave Chokes, 5-180 meters, 1/-, Paxolin Coilformers, 4 in. x 3 1/4 in. plain, 6/-; 6 in. x 2 1/4 in. threaded, 8/-, Ceramic Coilformers 5 1/4 in. x 2 1/4 in. threaded, wound with 32 turns 16 S.W.G. silvered copper wire, tapped every 8 turns, with mounting base, 3/9. Please send your orders and enquiries for our immediate attention. We despatch goods wherever possible the day we receive your order. These are securely packed or C.O.D., whichever best suits you. When sending C.W.O. please include sufficient for packing and postage.

VALLANCE'S

144, Briggate, Leeds, 1 (Phone 24928 and 24929). Branches for callers only at 53, High Street, Scunthorpe, Lincs., and 16, Leaning Street, Mansfield, Notts. Staff Call Signs: G2HHV, G9SX, G3ABD, G3AHV, G3BDD.

MIDLAND INSTRUMENT CO.

All-dry Batteries, 90-v. H.T., 1 1/2-v. L.T., 5/-, post 8d. Sealed cartons of 8, 30/- post free. Vibrator packs, 6-v. to 90-v. 20-mA., 20/-, Motors fitted centrifugal pumps, 24-v., 35/-. Thermostatic switches, 2/6. Indicator lamps, red, 3 different. D.C. Rotary converters, 24-v. 9-amp. 21-c. to 230-v. 435-amp. 50-c.y. A.C., £5. Motor generators, 12-v. to 500-v. 50-mA., 20/-. A.C. relays, 40-ohm. d.p.c.o., 2/6. H.16 rectifiers, 9d. Telephones, combined mike and phone, perfect communication without batteries, 10-yds. connecting wire, 12/6 set. Also instrument wires, microphones, amplifiers, meters, motors, and hundreds of other interesting radio and electronic items, lists 2d. with s.a.e. Orders over 30/- post paid.

Moorpool Circle, Birmingham, 17
Tel. HARborne 1303.

HENRY'S

5, Harrow Rd., Edgware Rd., W.2.

Large Stocks of Guaranteed Components
ANOTHER "MIDGET" BARGAIN!

A.F. UNIT. Comp. 3 IT4 Valves, in bases. Wearite "Hyperloy" Mike Trans., Midget Potentiometer, 10 Condensers, 8 Resistors, Mounted on Paxolin Panel, 6 in. x 6 in. New and unused. 35/- ONLY!


CATHODE RAY INDICATOR. Comp. 3 1/4 in. Mullard ECR 35. Electrostatic Tube, 2 EF50 Valves, 2 EB34 Valves, high voltage Condensers and Resistors. Complete in metal case. Ideal for conversion to oscilloscope. £4 10s. 0. each. Limited quantity only.

"REGAL" TUNING HEART. 4 Wave-band Coil Pack, complete with 2-gang Con. Dial with epicyclic tuning, for 465 kc/s. Med., long, and two short waves. Gram. switch position. With circuit, 79/6.

CASH WITH ORDER, OR C.O.D. (OVER £1)
Our New Price List is Now Ready
Phone: PADdington 1008/9

RADIO

CRYSTAL PICK-UP

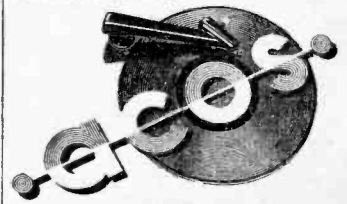

WITH *Unbreakable* CRYSTAL

The ACOS G.P.10 combines purity of reproduction with extreme reliability. A unique flexible assembly renders the crystal virtually unbreakable, while a needle-pressure adjustment is incorporated in the base. Resonance-free response from 50-8,000 cps. Output 1.5 v. at 1,000 cps. Needle pressure 1 1/2 ozs. (adjustable). Vibration-free arm movement. Screened lead. Price in Great Britain 44/- (including P.T.).

Flexible coupling A protects crystal B against breakage. (Brit. Pat. 579,524. Pats. pending abroad). Licensed by British Crystal Co. Ltd.



Obtainable only from Radio Dealers

COSMOCORD LTD
ENFIELD: MIDDLESEX

CALLING AMATEURS
with BUCCLEUCH
PRECISION BUILT
EQUIPMENT



STEEL CHASSIS SMOOTH BLACK
17 1/2" x 10 1/2" x 2 1/2" 9/9. 17" x 10" x 2"
8/9

PANELS-CRACKLE (same cost.)
19" x 24" - 4/-, 19" x 7" - 8/9
19" x 8" - 7/9, 19" x 10 1/2" - 8/9

ANGLE BRACKETS 12 1/2" long, pair 7/6.
(All in Bright Aluminium.)

COMPLETE RACK ASSEMBLY (Rigid 4-Pillar) 63" - £3/5s.
CHASSIS, etc. TO ORDER at 1d. sq. Inch.
(Include sides when costing)

BUCCLEUCH RADIO MANUFACTURERS
1 & 2 Melville Terrace, Edinburgh, 9
Grams: "Therm" Edinburgh.
Factory: Wheatfield St., Edinburgh.

A FREE BOOK

for all interested in



MORSE CODE TRAINING.

There are Candler Morse Code Courses for Beginners and Operators.

Send for this Free "BOOK OFFACTS" It gives full details concerning all Courses.

THE CANDLER SYSTEM CO. (S.L.O.)
121, Kingsway, London, W.C.2.
Candler System Co., Denver, Colorado, U.S.A.

SPARKS' DATA SHEETS

announce

THE EMPIRE ALL-WAVE TWO

No. 1.0/15. All-dry 2-Valver covering S.W. Bands, Medium and Long waves. Powerful Phone Sigs. on 9v. H.T. or Speaker results on higher voltage. Simple Coils. No Complicated Switching. Complete Data Sheet, giving Full-size Drilling Assembly, Wiring and Coil Plans, plus detailed descriptive matter, 2/6 plus Stamp.

SEND STAMP FOR FULL LIST OF 33 DESIGNS

Components for my designs available.

L. ORMOND SPARKS (P.)
9, Phoebeth Road, Brockley, S.E.4
*Phone: Lee Green 0220.

SOUTHERN RADIO'S LATEST

ex Government Purchases

BRAND NEW MOTOR GENERATORS

Input 11-12 volts, output, 480 volts, 40 mA. 17/6 each. TYPE F, input, 28 volts, output, 1,200 volts, 72 mA. 25/- each.

Carriage and Packing, 2/6 extra on either type.

Ex Government Morse Tappers, 1/6 each, 15/- dozen. Buzzers, 1/6 each, 15/- dozen, all brand new.

Portable TRANSMITTERS TYPE T1333. Brand New. Complete with Hand Driven Generator, etc., in original cases. 55/- carriage and packing 5/6.

SOUTHERN RADIO SUPPLY Co.,
46, LISLE ST., LONDON, W.C.
Gerrard 6653

Open to Discussion

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

Contacts Wanted

SIR,—I have recently completed the five-valve short-wave superhet as described in PRACTICAL WIRELESS (April, 1946, issue), and have had splendid results, although I had to add a 5:1 ratio transformer in the output stage to obtain the volume I required. Antenna in use is a 40ft. "end-on" single wire.

If any reader has made this set, I would like to hear from him with regard to type of aerial and valves in use, etc. All letters will be answered.—T. S. LEWIS (19, Cambria Avenue, Ellesmere, Shropshire).

Service Engineers

SIR,—Referring to all the writers in these columns on the above subject. I beg to summarise and to point out to all of them the following points:

1. Good radio-servicing *cannot* be carried out without *all* the best of test-gear, which must be accurate, and I would venture to say that both many of the *shops* and *private* individuals do not possess these.
2. There is only one way to do a job, and that is "As new"—be a credit to your profession.
3. *Practical* and *theoretical* training is essential, and it is my opinion that one is *dangerous* without the other.
4. A word about charges. A person who has had a radio repaired is not in the position to say that charges are excessive, because he *does not know* what is entailed in the repair of his set; therefore, to the serviceman—charge what the job is worth, taking into consideration the technical difficulties surmounted and the time involved, plus components. After all, no man in his right mind will work all the time for nothing.
5. It is my opinion that all servicemen should be prepared to study hard and be in possession of a complete set of good test gear or *get out* of the game.—W. F. PULFREY (Chatham).

[This correspondence is now closed.—ED.]

Correspondent Wanted

SIR,—I want one or two boys to correspond with me, and perhaps be able to exchange ideas, etc. I'm also an amateur radio operator.—MURRAY SCHAW, R.M.D., Waipawa, H. Bry, New Zealand, Nth Island.

R.A.F Tx TR/9

SIR,—I would like to correspond with any keen radio amateur conversant with, or in possession of, an ex-R.A.F. transmitter type T/R9.

One of these sets is in my possession, and I desire to acquire as much knowledge as possible

relating to the conversion of this set for amateur use.

As it seems impossible to obtain a circuit diagram of this transmitter I should be very grateful if this could have your attention, as I am sure there must be other amateurs as keen as myself who will welcome an exchange of ideas.—J. SAINTHORSE (81, Saltwell Place, Gateshead 8, Co. Durham).

Re Ex-Service Equipment R1155A

SIR,—I would like to answer a few points raised by your correspondent, A. W. Mann (Middlesbrough).

I have had one of these Rx's since September, 1946. I think the results on S.W. stations are very good, and are every bit as good as heard on some types of American commercial communications receivers. My main interests are in the amateurs; nearly all these are received on the L.S.

Here are some amateurs received to date: CE3CK, CN8AB, CO7PX, CO8MB, CX2AX, CX2CO, 9 D2s, 3 E1s, 5 D4s, 4 Fz, 171 Gs (mostly heard on 3.5 Mc/s), GC4LI, 4 G1s, 9 G3s, 11 GWs, 3 HBs, 4 Is, 4 LAs, LUBEQ, LU4HI, LU6AJ, ON4HC, 20 OZs, OX4MJ, 30 PAQs, 2 SMs, SV1AH, T120A, TR1P, UA1AB, 4 VEs, VO11 (3.8 Mc/s), VP9F, 120 Ws, 16 XAs, YR5V, YV3AL, ZB1AB.

I have also heard these S.W. broadcast stations on various bands: CNR, TAP, VLA4, VLBC, VLC4, PRL7, FSI, CKNC, CKLO, CHOL, WNRI, SBP, WNRA, HER3, CSW6, Andorra, VONH (5.97 Mc/s), SDB2, KOFA, WWV, OTC5, WOOW, WCBN, WNRJ, OTC2, Moscow on all bands.

Tuning is very easy, even on S.W., the S.M. dial being excellent. The noise-level can be very high when receiving weak stations and it is better to use 'phones then.

There is a certain amount of second-channel interference on 14 Mc/s, but this can be cured by using an external pre-selector. The Rx also makes an ideal one for general use, as the medium- and long-wave bands are included in most models. The Rx also works very well with a 40-metre converter and Rx tuned to about 3 Mc/s.

All stations listed were 'phone—no C.W.—as I cannot read morse yet.—W. A. TAYLOR (Newhaven).

Reports Wanted

SIR,—I would be pleased if you would publish my call, and I would also appreciate reports on my transmissions on 40-metre band.—A. C. APPLEBY (GBKK, Newcastle-on-Tyne, PSE QSL via RSGB).

S.130 Stabiliser

SIR,—I would very much like, through your columns, to contact some reader situated similarly to myself (e.g., age about 18 years, fair

knowledge radio, *hoping* to enter university next October).

May I take this opportunity of saying how interesting and helpful I find your technical and constructional articles. Finally, you recently described a piece of apparatus containing the Cosor S130 neon stabiliser. If anyone could tell me where these fabulous objects may be obtained, I should be grateful.—J. WILLIS (16, Queen's Road, Alton, Hants).

German Valve Details

SIR.—The following information may assist Mr. G. Somerville (May-June issue) who requires information on a valve RV12P2000. This valve is a German Army valve, and the code used by the German Army is explained below:

The first letter "R" stands for Röhre (valve).

The second letter gives the type of valve:

V = Verstärker (amplifier).

G = Gleichrichter (rectifier).

L = Leistung (power).

The first set of figures gives filament voltage.

The third letter:

P = Pentode.

T = Triode.

D = Diode.

The last set of figures:

For "V" valve = Amplification factor.

For "G" valve = D.C. output current (mA.).

For "L" valve = Power output (watts).

i.e., an RV12P2000 valve is an H.F. pentode with 12.6 volt filament. Actually this valve was very extensively used by all the German services, including Air Force and Navy, and was used for H.F. amplifier, I.F. amplifier, A.F. amplifier, and even as an output valve.

Heater current: 75 mA.

Anode volts: 220 volts.

Screen volts: 140 volts.

Impedance: 1.5 MΩ.

μ: 2,000.

Grid volts are determined by duty to which valve is put. For H.F. circuits: 2 volts.

The connections are as shown in the accompanying diagram.—A. J. THOMPSON (N.17).

[We wish to take this opportunity of thanking the many hundreds of readers who so kindly submitted data, interesting details and even actual samples of this particular valve. The information has been passed on to Mr. Somerville.—ED.]

Peculiar Faults

SIR.—Reference your issue for May-June "Open to Discussion," Richard G. Guy's letter and your reply.

I have met this peculiarity on many occasions and it has, as you say, always been in the output transformer, and anyone who is well acquainted

with the Marconi CR100 or Naval Type B.28 receiver will have experienced the same "freak."

In these sets, the transformer is mounted on the receiver chassis, and in the earlier models quite good reproduction could be obtained without 'phones or speaker if the L.F. gain was high enough. The only other noise I have met is from the output valve itself, and I believe it would be due to the rattling of the electrodes.—L. W. DODD, G3BIZ (Co. Durham).

Correspondent Wanted

SIR.—I have just been released from the Forces and I am taking radio as my hobby.

I am desirous of corresponding with other readers and enthusiasts in all parts of the globe. I shall be pleased if you will kindly assist me.

I am keenly interested in short-wave receivers, and transmitters, and I should like to exchange ideas, mutual aids, or to be helped by more advanced amateurs and keen experimenters in this field.

I trust you will assist me, and I promise that letters from SWLs will be answered where possible by air mail.—M. I. DADA (24, Voley Pougnet Street, Port Louis, Mauritius).

Spirituality or Spiritualism?

SIR.—With reference to "Thermion's" remarks in "On Your Wavelength" recently, may I say that I think the word "spirituality" is the one applicable to Christianity, as differing from spiritualism. I am sure "Thermion," as he says himself, or Mr. J. N. Maskelyne, formerly of Maskelyne's Hall of Mystery, could stage a séance.

The writer in the *Psychic News* seems to me to imply that we can act as a sort of "superhet" as regards the inner ultra-violet world, which we can call the "realm of the spirit," and that there are some particularly sensitive individuals better able to do so than others. I do not refer to the insane, D.T.s, or opium smokers, sufferers from liver disorders or indigestion.—M. K. HUGGARD (Co. Dublin).

"The Vector Problem"

SIR.—I have checked the point raised by A. O. Griffiths in your May-June issue, and find that Figs. 1 and 2 on page 157 are correct as they stand. The arrow above each diagram indicates that the vectors are moving in the standard anti-clockwise convention, so Eg is going negative. I suspect that Mr. Griffiths has unwittingly introduced a 180 deg. error in the course of his experiment to demonstrate his "provable fact." In any case, he cannot agree with Fig. 1 and not Fig. 2.—R. S. HATCH (Chorley).

WIRELESS TRANSMISSION

6/-, or 6/6 by post from

GEORGE NEWNES, LTD., Tower House,
Southampton Street, London, W.C.2

CLASSIFIED ADVERTISEMENTS

RATES: 3/- per line of part thereof, advance words to line. Box No. 60 extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

MORSE & S.W. EQUIPMENT

THE SHORT WAVE LISTENERS ANNUAL. 1947 Edition, is now on sale. Over 80 pages essential data for DXers. 2/6 from local booksellers, or 2/9 direct from "Short Wave News," 57, Malda Vale, London, W.9.

LITERATURE, ETC.—CQ SWLs make sure UR reports bring QSLs. Detailed radio station report cards (QSL sheet) in two colours. 50 for 4/6; 100 for 7/6.—B. G. U. Manufacturing Co., 24, Burns Street, Nottingham.

RADIO SOCIETY OF GREAT BRITAIN offers the following publications of interest to all transmitting amateurs and short-wave experimenters—

R.S.G.B. BULLETIN, the Society's journal, 1/6 monthly.

AMATEUR RADIO HANDBOOK (300 pages), 10,000 copies sold, paper cover 4/6, cloth 7/-.
RADIO HANDBOOK SUPPLEMENT (140 pages), 110,000 copies sold, paper cover 2/9, cloth 5/6.

THE TRANSMITTING LICENCE (32 pages), for the newcomer to Amateur Radio, 1/-.
SERVICE VALVE EQUIVALENTS (28 pages), gives Commercial Equivalents of numerous Service valves, including CV types, 1/-.

All prices include postage and packing. Watch for further publications in the R.S.G.B. "Amateur Radio" series. 28-30, Little Russell Street, London, W.C.1.

SILVER PLATING SETS for Plating Tuning Cond. Wire, Coil-holders, small parts. Send 3d. stamp for folder to: Argenta (C), 40, Harrogate Road, London, E.9.

"H.A.C." Short-wave Receivers, famous for over 15 years. Complete kits now available. All components, accessories, with full instructions. One-valve model 20/-, two-valve model 43/-. Easily assembled in one hour. Send S.A.E. for free catalogue.—"H.A.C." Products (S.W.), 66, New Bond Street, London, W.1.

RECEIVERS & COMPONENTS

OSMOR A.C./D.C. 3-wave 5v. superhet receivers, excellent reproduction and sensitivity, attractive cabinet, early delivery, shipping wave-band if required. Write for literature. Trade inquiries invited.—Morgan, Osborne and Co., Ltd., Southview Road, Warringham, Surev.

KITS of Radio Receivers from £7.80, 4 and 5 valve. All new materials. Table Models. Semi-Midget. Our latest Kit—Wylwyn Star 1947—has connections for Gramophone Pick-up and extensions to Loudspeaker. A.V.C. 6 hours average time for constructing. Full details and diagrams with each Kit, C.W.O. or C.O.D.—Esherwoods, Reme House, 81, Plungington Road, Preston, Lancs. Tel.: 3348. Estd. 1936.

THE NAME TO NOTE for all kinds of radio and electrical metalwork to specification, modern rustproofing, all shapes and sizes undertaken, and for tropical use. Components and sub-assemblies executed to meet receiving and material standards. Consultation, advice without obligation: Write Dept. 03, Sea Rescue Equipment, Ltd., Chiltern Works, Clarendon Road, Watford, Herts.

THE LAST WORD IN RADIO KITS! Really detailed Instructional Manuscript how to build best type of A.C. D.C. 4-valve receiver, 2/6. Absolutely complete Kit, including valves and super cabinet, £8, car. paid. Also 5-valve 3-wave Superhet Assembly, consisting of all main components, factory mounted on chassis, including very attractive dial, iron-cored coils and iron-cored I.F.S. Builds a first-class receiver for the discriminating listener. Price £6, carriage paid, with blueprints. A.C. only versions of above also now available. Send postage for specifications and Bargain List.—Northern Radio Services, 66, Parkhill Road, London, N.W.3. Gulriver 1453.

FRED'S RADIO CABIN

WEYMOUTH ALL-WAVE COIL PACKS. 465 kc/s I.C., I.F. Coils, 15/- pair.

465 kc/s I.F. coils, with ceramic trimmers, 12/6 pair.

T.R.C. COILS, with reaction winding, 8/6 pair. M.W.L.W. A.W. superhet coils, 9/6 pair. All coils with circuits. Adjustable iron-cored D.R. coils, M.W.L.W., 9/6 pair.

2-gang, .0005 mfd., W.T., 12/6.
P.V.C. 100K-UP WIRE, 18ft., 18 S.W.G., various colours, 1/- coil.

1in. dia. brass couplers, 9d.
41v. Bell Batts., 1/3. Multi-core Solder, 6s.

PORTRIMSTER MULTI-RATIO I.F. TRANS., 8/6. 2-socket terminal strips, 3s.

P.V.C. 100K-UP WIRE, 18ft., 18 S.W.G., M.W., L.W., TRF Dial Scales, 1/9. Dial Bulb-holders, 6d.

TRF MIDGET SET CABINETS, 12/6. .0005 dielectric tuning conds., midget type, 9/6.

MINIS TRANS., 350-0-350, 80 m.a., 4v. 4 a. and 4v. 2 a. or 6.3v. 3 a. and 5v. 2 a., 32/6.

CLEARANCE LINES
.000365 MFD. CONDS., with 1in. coupler, ceramic insulation, 4/6 each.

Col. Calif. Cap. 3in., 1 1/2in., 3d.
EX-R.A.F. VR91 (EP50), 12/6; VR55 (EB33), 7/6.

400 OHMS W.W. POT METERS, 2/6; 25,000 ohms, W.V. Pot Meters, 4/6.

SMALL SUPERHET CHASSIS, strong 21/6. Octal size (best), 2 I.F. Cut-outs, 10 1/2in. x 2 1/2in. x 4 1/2in., 4/6.

2 MEG. V.C.W.S., 4/6.
6J5 S.H. O.K., 5/-; Z14, 11/-; 2BD7, 5/-;

6SL7, 12/10. Hunts. 60+50 P.F., 1/-.
0-1 M.A. METRO V.M.A., 2 1/2in. scale, 32/6; 0-30 m.a., 2 1/2in. M.C., 2/1.

ELECTROLYTICS, 20 mfd., 150 V.W., 2/6.
20 S.W.G. COPPER WIRE, 25ft., 6d.;

PAN COIL FORMERS, 1in. x 2in., 2d.; 1in. x 1 1/2in., 4d.

5 VOLT CIRCULAR MESH FUSE BULBS, 6d. each. Large quantity for sale; special for gross.

OAK VIBRATORS, 6v. 6-pin, 6/6.
SYDLOK 15 AMP. FUSES, panel type, 2/6 each.

STATOR MIDGET POT. slot adjust type, 25,000 ohms, 6d.
JACK PLUGS, 9d. each.

E.L.A.C. 5in. T. M. Loud Speakers with transformer, 32/6 each.

12 volt 1 amp. I.F. rectifiers 8/6 each.
SPECIAL NOTICE

Open daily, 9 a.m.-6 p.m., including lunchtime; 1 p.m. Thursdays. Many other bargains in surplus R.A.F. and Army gear for callers.

FRED'S RADIO CABIN, 75, Newington Butts, Elephant and Castle, London, S.E.11 (one minute from Tube). Telephone: **RODNEY 2180.**

O. GREENLICK, LTD.

COILS—M. wave, 5 type, t.r.f., pr. 5/-; m. wave, Aer and Osc., pr. 5/-; m.l. wave, t.r.f. with reaction, pr. 7/6; iron cored, m.l. wave, t.r.f., 10/6; s.m.l. wave, superhet coils, pr. 10/6; midget i.f. trans., 465 kc/s iron cored, 18/9; standard i.f. trans., 465 kc/s, 15/-; standard i.f. trans., 2 Mc/s each, 4/6; Weymouth all-wave coil packs, 36/6. All coils supplied with circuit.

A.V.O. Capacity test bridge, 200 240 A.C., 2/1.

VARIABLE CONDENSERS—2-gang, .0005 mfd., 12/6; Tiny Tim ditto, ultra midget, 17/6; 2-gang, .0001 mfd., short wave, 7/6; 2-gang, split stator, .00017 mfd., 6/-.

TRANSFORMERS—Speaker trans. ultra midget, 5/-; standard, tapped, 5/6; Push-pull driver, 3/1; split secondaries, 12/6; Varley, 2.5:1, 20/-; p.p. output, 2-5L6, 6/600 A to A load, 7/5 and 15 ohms, 2/1; Pentant, p.p. output, 2:1, 15/-; Varley class B, 1.5:1 and 2:1, 15/-.

CABINETS—Midget cabinets, finished cream and green, internal dim. 13in. by 7in. by 6in., 35/-.

LINE CORD—Heavy quality, 3-wav., 3 amp., 3/- yd.; 2-wav., 3 amp., 2/- yd. (60 ohms per ft.).

SCREENED CABLE—Single core, pr. yd., 9d.; twin circular, outer rubber covered, pr. yd., 2/-.

ELECTRIC SOLDER IRONS—The best "Stanelco" long bit, 75 watts. List, 22/6; offered while available, 19/6.

CHASSIS—For 4-valve fully drilled, 1 1/2in. by 4 1/2in. by 2 1/2in.; for 5-valve superhet, fully drilled, 1 1/2in. by 5 1/2in. by 2 1/2in., 7/6.

DIALS—S.m.l. wave, in colours, 4 by 3 1/2 at 2/-, 5 by 5 1/2 at 2/6; m.l. wave, 6 by 5 at 1/6. Comprehensive lists monthly. 2/d. stamp enquiries. Postage all orders.

4, Avenue Hill, Bancroft Road, Cambridge Heath Road, London, E.11. Phone: STEPNEY Green 1334.

LOUD SPEAKER Repairs. New cone fitted, transformers, clock coils, chokes and mics, rewound. Prices quoted: E. Mason, 3, Balham Grove, S.W.12. Balham 6000.

REPAIRS to loud-speakers—Cones, coils fitted, fields altered, rewound. Output transformers, clock coils. No mains trans. accepted. Prices quoted. Satisfaction guaranteed.—L.S. Repair Service, 49, Trinity Rd., Upper Tooting, S.W.17, Closed Saturdays. Phone: Balham 2358.

COPPER Wires, enamelled 1 1/2, 2oz. lbs., 18. 2oz. 1 1/2; 22, 24g., 1 1/2; 26, 28g., 2; 30, 29g., 2 1/2; 34, 36g., 2 1/2; 38, 40g., 2 1/2; 42g., 3/6. Cotton-covered same prices. Silk-covered, 1 lb. 5/6; 18g., 1 lb. 7/-; 20g., 1 lb. 4/-; 22g., 1 lb. 2/6; 2 oz. reels, 2/6. 38g., 1 1/2; 38, 30g., 1 1/2; 32, 34g., 2/-; 35, 38g., 2 1/2; 40, 42g., 2 1/2; 41, 45g., 1 oz. 2/-.

Tinned copper, all gauges, 18-42g., available.

Laminated Bakelite Panels, 1in. thick, 6in. x 4in., 1/6; 6in. x 6in., 2/-; 8in. x 6in., 2/6; 10in. x 6in., 3/-; 10in. x 8in., 4/6; 12in. x 6in., 4/6; 12in. x 12in., thick same sizes, 1/-; 14, 18, 22, 2, 6, 3/-.

Polished Ebonite panels, 3/6in. thick, same sizes as above, 2/-; 3-, 3.9, 5-, 6/6, 7/6 respectively; ditto, 1in. thick 2.9, 4-, 5-, 6.9, 8.9, 10- respectively.

B.A. Screws, gross useful sizes, 2/6; ditto, nuts, 2/6 gr.; assorted gross screws and nuts, 2/6; brass washers, 1/6 gr.; fibre washers, 1/6 gr.; assorted soldering tags, 2/- gr.; assorted small eyelets and rivets, 1/3 gr.

New ex-G.P.O. hand telephone with microphone, switch, and leads, 12/6; used ex-R.A.F. low resistance earphone with switch, 2/-.

Tinned copper connecting wire, 20ft., 6d.; ditto, rubber covered, 10ft., 6/6. Finest quality stranded and single push-back wire, 12yds, 2/3; resin-cored solder, 1lb, 1/-.

New "Lucerne" Permanent Crystal Detector, 2/-; semi-permanent detector, 2/6.

"Lucerne" crystal coil with wiring instructions, 3/6; glass tube crystal detectors, complete, 2/6. Reconditioned headphones, 4,000 ohms, complete, 12/6.

All postage extra. Trade supplied.—Post Radio Supplies, 33, Bourne Gardens, London, E.4.

CONDENSERS—3 mfd., 500v., 3/6; 16 mfd., 5/-; .0005 two-gang, 10/-; 5in. Energised Speakers, 3/0; Lincrod 3A 3-core, 6/6; foot; sleeving, 1 1/4 yard, 1/-.

S.P. Transformers, 7/6; Volume Controls, 1/9. Large stock Valves, 1d. stamp for full list.—Nuttall, 9, Gorse Road, Blackpool.

PARTS of new and second-hand radio parts, 10/-; 2nd-hand second-hand 6in. energised speaker, choke and trans., 42/-; Dunstond, 39, Quemerford, Calne, Wilts.

SOUTHERN RADIOS WIRELESS BARGAINS

LATEST RADIO PUBLICATIONS: Radio Valve Manual—Equivalent and alternative American and British types, with all data, 3/6. Radio Circuits—Fully illustrated, 2/6. Ultra Short Wave Handbook, 2/6. Radio Fully descriptive circuits, 2/-.

Radio Coil and Transformer Manual, 2/-, Short Wave Handbook, 2/-, Manual of Direct Disc Recording, 2/-, Test Gear Construction Manual, 1/6. Radio Pocket Book—Formulas, tables, colour code, etc., 1/-.

Ten Hours for Radio Constructors 1/-, Bulbin Radio Service Manual, 2/6. Radio Constructor's Manual, 3/-, Radio Resistor Chart—Colour codes at a flick 1/-, Radio Reference Handbook—Cloth bound, all comprehensive and up to date, covering all branches of radio, 12/6.

American Service Manuals, Sparton-Emerson, Crosley-Belmont (Parts I and II), Stewart-Warner-Fada, 12/6 per volume. Aerial Handbook, 2/6. Ultra Short Wave Handbook, 2/6. Radio Hints, 2/6. Television Manuals, 3/6. Postage extra on all publications.

VALLEY type Rotary Switches, 2-way, 5/-, Resistances, assorted values, 2 watt to 1 watt, 20/- per doz., 10/- per doz. Crystal Detectors, 2/6 each. Aluminium Panels, 16-gauge, 18in. x 7in., 3/6. Cutler Harmer Rheostats, 30 ohms and 10 ohms, 4/6.

Ex-Government Morse Keys, brand new, 1/6 each (15/- per dozen). Ex-Government Buzzers, brand new, 1/6 each (15/- per dozen). Westcoasters, type WXG and W12, 1/- each (10/- per dozen).

LUBRA Adjustable Hole Cutters, for use on metal, wood, plastics, etc., 5/- each, 6/6 post.

Portable Transmitters Type T1333, Brand New, Complete with Hand Driven Generator, etc., in original cases, 55/-, carriage and packing, 5/6.

All goods advertised are postage extra. **406, LISIE STREET, LONDON, W.C. 2.**

7errard 9653.

TRANSMITTING VALVES. Have available the following types: RK29, RK60, RK66, 6A7/1852, 643, 965, 641, 832, 803, 872, 837, 813, 805, 955, 954, 6A87/1853, 814, 836, 250T, 100T, 811, 9003, 9302, 829, 838, 860, 956, 800, 830, 815, 150T, 23A, 832A, 50Y0C7, 6L6M, 3ST, 4E7, 12Z4, T230, 965, RK29, 1625, 807. All new and unused, guaranteed. Send S.A.E. for price list.

RADIOGRAPHIC LTD., 66, Osborne Street, Glasgow, C.I.

TELEVISION line and frame transformers—Valves—Ex. R.A.P. Hvac. Midgets, etc. I.F. transformers, pick-ups, mics, speakers, condensers, resistors, etc. S.A.E. for lists and terms.—Bobs Radio Supplies, 163, Osborne Rd., Romford, Essex.

RADIO BARGAINS.—Assorted conds. from 0.001 to 0.5 mfd., mostly metal cased, 5/6 doz. Metal cased tubular conds., 0.001, 1,000v. wkg., 4/6 doz.; 0.01, 1,000v. wkg., 5/3 doz.; 0.25, 350v. wkg., 5/6 doz.; 0.5, 350v. wkg., 5/6 doz. Assorted resistors: 1 watt assorted, 2/9 doz. Speakers, 8in. P.M., 2/6. Push-back wire, 1/6 doz. yards. Carbon microphones, hand type, with on-off switch and hex. 7/6. Postage extra. No C.O.D. after 30.—Kemp, BCM KRAE, London, W.C.1.

PERSEFX sheet, 5.32in., reduced from 1d. per sq. inch to 7d. Cut to any size. Discounts for quantity, post free over 15/—Inquiries, orders to: Midland Hamcar Co., 3, Shrubbery Street, Kidderminster.

PERSEFX sheet, clear and coloured, all sizes. Cement and polish etc. Packets from Plastikits, 15, Foster Street, Brompton, Yorks.

RADIOELECTRON, 22, FRANCES ST., SCUNTHORPE, Lincs.

Coast-to-Coast Radio Spares Service. Regular Stock Lines. New Goods Only. **RESISTORS.**—All Values. Carbon 1 watt, 1/4, 1/2 and 5/4. Wire Wound, 1 watt, 1/4, 1/2 and 5/4. 1 watt, 1/2 and 5/4. Mains Droppers, 2 adj. Taps. Feet 2 amp, 1,000 Ω , 4/3. 3 amp, 800 Ω , 4/6.

CONDENSERS.—Tubular 350-500 v. wkg. up to 0.05 mfd., 8d. to 1 mfd., 10d. to 25 mfd., 1/3 to 5 mfd., 1/4 mfd., 2/4. Electrolytic, 500 v. 4 mfd. 3/8, 8 mfd. 3/2, 8-8 mfd., 6/5; 450 v. 8-16 mfd., 8/8, 25 mfd., 25 v. 1/10, 50 mfd., 50 v. 2/10. Mica up to 0.05, 1 - to 0.1 mfd., 1/3. Tuning, 2 rang., 0.005 mfd., 1/11, with Trimmers, 12/6.

TUNING COILS.—M. and L. wave. With diagram, 9/3 pair.

VOLUME CONTROLS.—All values, long spindles, 3/4 to 6/6 with S.A. wire wound. Less S.W. 2 k., 5 k., 10 k., 30 k., 3/6.

TRANSFORMERS.—Intervalve, direct feed. Ratio 3-1 and 5-1. 7/6. Parl. Feed, 4-1. 6/- Class B Driver, 7/6. Output Pentode, 5/6. Universal, 6/6. Power Pen. PP, and Class B 7/6.

M. A. LOUD SPEAKERS, 5in. 20/-, 8in. 24/-.

BATTERY H.T. ELIMINATORS.—Input 200-250 v. A.C. Output 60-75 and 120 v. at 20 m.a. With 1/2 brick charger. Complete in metal case with connecting wires, wandle pins and spades, all ready for connecting up and switching on, 6/3 each.

TOGGLE SWITCHES, single hole fixing. S.P. on-off, 2/6. S.F.P. D.T., 3/-; D.P. on-off, 3/6; D.P. D.T., 4/-.

Every type of radio spare stocked; please state your requirements enclosing S.A.E. Terms—cash with order, post free over 10/- or C.O.D. extra.

1,000KC Oscillator Units in metal screening boxes. Complete with standard 1,000 Kc bar in holder. Only require valve insertions and connecting wires. 100 tubes, 100 valves and 100 volts H.T. for perfect 1,000 Kc signal generator. Price, 17/6 complete (excluding valve). Special Offer, 6/5 valves, sealed cartons, 4/6 each.—Wolsby, 1, Colnar Drive, Sheffield.

TRIMMER Tool Kits (new) given in exchange for old Service Sheets.—Bulls (P.W.), 246, High St., Harlesden, N.W.10.

AN EXCEPTIONAL COIL. The new Summersby S.A.2 is a midget in size only, Litz wire wound on a distrene former, adjustable iron dust core; the performance of this medium wave coil at 1,500 Kc. with 70 Pf. has a Q of 90, and at 600 Kc. with 490 Pf. has a Q of 170. Price, 3/3 each; immediate delivery. We believe that we are the first manufacturers to offer post-war to the trade and public a tuning coil that does not need a variable condenser—the Summersby Permeability Tuning Coil will be on sale in August. Be up to date. Use Summersby Wireless Ltd., Summersby, Ltd., 106, Heath Street, Hampstead, London, N.W.3.

SERVICEMEN!—Experimenters! Nu-plans, in addition to their Television Test Pattern Generator, announce the Nu-plans Signal Tracer and Fault Finder. Hear the trouble!—See the trouble! Easily, inexpensively built from Nu-plans Data sheets. Makes copying a pleasure. —2/6 from E. N. Bradley, Nu-plans "Whinnie Knowe," Escalls Cliff, Sennen, Cornwall.

KEEP a permanent record of your own circuits! Complete blueprint with component values, etc. inserted. Drawn from four data sheets. 5/- Makes copies 1/3 each to B.C.M./Manufacturers, London, W.C.1.

PRICE INCREASES. 40 h. 20 m.a. and 10 h. 40 m.a. chokes now 5/-. Knobs: 1in. now 7d.; 1in. now 7d.; 1 1/2in. now 8d.; 2in. now 10d. 2 ratio 30 m.a. output transformers now 5/8. P.V.C. battery leads 5-way now 7/-; 7-way now 3/6. Additional lines. Belling-Lee terminals, R type. 9d.; L type. 1/6. Push-pull on-off switches, 3/6. Re-action condensers, 0.003 or 0.005, 4/6 each. Browns Type F headph. condenser, 4 ratio output transformer, giving 60-1, 90-1 or 120-1 max. current 40 m.a., 7/6. We have good stocks of Rothermel Sapphire needles, straight or trailer type, at 12/6 each. Wearite "P" coils at 3/- each. Colvern potentiometers from 5/6. Centralab volume controls with switch, 6/-; less switch, 4/3. Varley thermal delay switches at 10/-, 32 mfd. 330 v. wkg. electrolytic condensers, can type, one hole fixing, 8/4. Postage extra conds., 100ms., 100ms., 499, Chiswick High Road, London, W.4. Phone: Chiswick 4530.

R.A.F. RADIO (Receiver RI125).—Two-valve preset U.S.W. 8D2 valves in case 10in.x6in.x3in., 17/6. A.C. electric pumps, 12 or 24 vts. D.C., takes 3 amps. from 12v. battery. Ideal for forced flow, clean well water, petrol, paraffin, etc.; brand new in maker's cartons, 50/-. Panel Controls in case 7in.x8in.x1 1/2in., with slide-in chassis containing 5 x 3 mfd., 1,500 v. rotary condenser, 4-section mains switch, in separate case, 5 amp. 4-way fuse unit and spare fuses, selenium rect., QMB switch, green panel light. A.C. vtc. regulator, W.W. res. and potentiometer, 15/-. Choke units in ventilated case 8in.x8in.x8in., slight alteration to wiring converts to trans., giving 12 v. 3 amp. from 230 v. 12/6. Power unit 626 new in cartons, 6 mains valves, A.C. motor switch unit, condenser block, 800 v., relay, H.F. choke, 48 res. and cond., 4-way 7 pin H.F. sockets, 12 v. 12 v. 2 transformers, etc. chassis 18in.x15in.x2 1/2in., 55/-. Rotary Transformers, 12 v. D.C., 275 v. 110 m.a., 500 v. 50 m.a. in case with smoothing switch, panel light, etc., 30/0 or less cash with only the rotary transformer, 20/-. Ditto, 24 v., 230 v. 50 m.a., 12 v. 1 1/2 amp. in case with all smoothing, voltage regulator valve, relay and fuses, etc., 21/-. Moving-Coil Meters of all types from 12/6. S.A.E. for list. Louvred Amplifier Cases, 12in.x14in.x3in., H. English, The Mailings, Rayleigh Road, Hutton, Essex.

TELERADIO have 50 only, 5v. all wave midget pocket superhets, size 7 1/2 x 3 1/2 x 2 1/2. These are offered complete with universal power pack or battery together with lightweight headphones and all leads and plugs. Sensitivity is very high, and American reception can be guaranteed. Illustrated leaflet is available, but as supplies are very limited, early ordering is advisable. In sealed carton at 10 sns. post paid. Deposit will secure.

KITS. 5-5v. All Wave Superhet for A.C. 12 gns. 4.5 watt A.C./D.C. amplifier. 24 1/2s. 6d. 4v. All dry superhet, 25 1/2s. A.C./D.C. TRP, 27 sns. 3v. Battery TRF, 24 1/2s.

All above include valves, but spkr. extra. **REPLACEMENT UNITS** (factory assembled). 5v. model 50a R/G chassis. 15/- plus P.T. 5d. 3v. model 50c high sensitivity amplifier for A.C./D.C. suits for electric guitar, etc., 6/6 5s. B.S.R. 10 watt gram amplifier with record player, 638 2s. 10/-

Comprehensive blueprint service is available to amateurs, and illustrated catalogue will gladly be forwarded on receipt of stamp. Components. Headsets (low impedance) can be used on ext. spkr. skts., 12/6 pair. High sensitivity coil packs for all purposes from 30/-. Iron-cored High C/P trans., 15/6 or Amphenol valveholders, 9d. each, 7/6 doz. Mains trans., semi-shrouded, 1st quality 350v. H.T., 5 and 6v. L.T. 80 ma., 25/-.

The **Tele-radio Co., 157 Fove Street, Edmonstone, N.18.** and 155, High Street, Ilfracombe, Tel. Tot 3386 and Ilfracombe 587.

CHARLES BRITAIN RADIO LTD. If you wish to read this, SELENIUM METAL RECTIFIERS, miniature type, Hi6 Sen-Ter-Cel, replaces any half-wave rectifier, 5/- each. Larger type, H25, 7/6 each. **SMOOTHING CHOKES.** Heavy duty, 360 ohms, 7/6 each. **MODULATION CHOKES.** First class, impregnated, 8/6 each. **TRANSCEIVERS.** Brand new WALKIE TALKIE, with valves, 'phones and mike, etc., only 24/5. Carriage paid. **TRANSCEIVERS.** Ex-army No. 22 sets, in good condition, 2-3 mcs., 21/10/- carriage paid. U.H.F. receivers RI147B contain the following new valves and are mainly new, 2, EF36, 1, EBC33, 2, EF50, EC32, 1, EF51 in strong packing case, 39/6 carriage paid. **INDICATOR UNITS** in metal case, 6in. E.S. tube, time base and amplifiers with 7 valves. Make your own scope, 26 each. (Sellers only this item). These represent a small part of our constantly-growing stocks, and we have all our previously-advertised and standard radio lines in stock; 2/d. stamp for list "W."

Charles Britain (Radio) Ltd., Radio House, 2, Wilson Street, E.C.2 Tel.: BIS 2966

SITUATIONS VACANT

"ENGINEERING OPPORTUNITIES." Have you had your copy of this free guide to A.M.I.Mech.E., A.M.I.E.E., and all branches of Engineering, Building and Plastics? Become technically trained on "NO PASS—NO FEE" terms for higher pay and security for the future. Write B.I.E.T. (Dept. 242B), 17, Stratford Place, London, W.1.

MINISTRY OF CIVIL AVIATION
Appointment of Radio Mechanics,
Grade II

Applications are invited for appointment as Radio Mechanics at Civil Aviation Radio Stations in the United Kingdom. Candidates must possess a knowledge of the fundamental principles of radio and radar with a general knowledge of one or more of the following radio aids for navigation: Direction Finding, Loran, Gee, Radar Beacons, A.C.R. or G.C.A. They should also have had practical experience in the use of tools, filing, drilling, hard and soft soldering, cabling and wiring and be experienced in the use of electrical and radio measuring instruments, including cathode-ray oscilloscopes. The possession of City and Guilds Certificates in Radio Communication and Technical Electricity will be an advantage. The pay will be 185/- per week inclusive, rising by annual increments of 3/- a week to a maximum of 190/- a week. Applications, which must be in writing, stating date of birth, full details of qualifications and experience and enclosing reference C.A. Est RM, should be addressed to the Establishment Division, Ministry of Civil Aviation, 10, Fleet Street, London, E.C.4.

TUITION

THE Institute of Practical Radio Engineers have available Home Study Courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.P.R.E. Service entry and progressive exams; additional fees for reference material moderate. The Syllabus of Instructional Text may be obtained, post free, from the Secretary, 20, Fairfield Road, Crouch End, N.8.

RADAR, WIRELESS, TELEVISION, etc. Be prepared for tremendous post-war developments. Students of all grades trained for appointments in all branches of radio. Boarders accepted. Low fees, 2d. stamp for prospectus.—Wireless College, Colwyn Bay.

THE British National Radio School offers you a Career. Write to-day for free booklet describing our wide range of training courses in Radio, Radar, Telecommunications Principles, Mathematics, Physics, and Mechanics. Correspondence and Day classes for the New Series of C. & G. Examinations. We specialise in turning Operators into "Engineers" and for this purpose our "Four Year Plan" (leading to A.M.I.E.E. and A.M.Brit.I.R.E., with 3 C. & G. Certificates as interim rewards) is unsurpassed. OUR Guaranteed No strings attached Studies Director, B.Sc., A.M.I.E.E., M.Brit.I.R.E., 66, Adiscombe Road, Croydon, Surrey.

Practical Wireless BLUEPRINT SERVICE

SPECIAL NOTICE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears; thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.C.

| PRACTICAL WIRELESS | | No. of Blueprint. | F. J. Cannon's A.C. Superhet 4 | PW56* |
|---------------------------------------------------------------------|--|-------------------|----------------------------------------------------------|--------|
| CRYSTAL SETS | | | F. J. Cannon's Universal 24 Superhet 4 | PW60 |
| Blueprints, 6d. each. | | | "Qualitone" Universal Four | PW73* |
| 1927 Crystal Receiver | | PW71* | | |
| The "Junior" Crystal Set | | PW94* | | |
| STRAIGHT SETS. Battery Operated. | | | SHORT-WAVE SETS. Battery Operated | |
| One-Valve: Blueprints, 1s. each. | | | One-Valve: Blueprint, 1s. | PW85* |
| All-Wave Cupren (Oxotone) | | PW31A* | Simple S.W. One-valver | PW85* |
| Beginners One-valver | | PW85* | Two-valve: Blueprints, 1s. each. | |
| The "Pyramid" One-valver (HF Pen) | | PW93* | Midjet Short-wave Two (D, Pen) | PW38A* |
| Two-valve: Blueprint, 1s. | | | The "Fleet" Short-wave Two (D HF Pen, Pen) | PW81* |
| The Signet Two (D & LF) | | PW76* | Three-valve: Blueprints, 1s. each. | |
| Three-valve: Blueprints, 1s. each. | | | Experimenter's Short-wave Three (SG, D, Pen) | PW30A* |
| Sedotone Battery Three (D, 2 LF Trans) | | PW10 | The Prefect 3 (D, 2 LF RC and Trans) | PW63* |
| Sunmit Three (HF Pen, D, Pen) | | PW37* | The Band-spread S.W. Three (HF Pen, D, Pen, Pen) | PW65* |
| Hill-Mark Cadet (D, LF, Pen (113)) | | PW48* | PORTABLES | |
| F. J. Cannon's Silver Soxavver (HF Pen, D, Pen, Pen) All-Wave Three | | PW93* | Three-valve: Blueprints, 1s. each. | |
| Cassio Midjet Three (D, 2 LF Trans) | | PW51* | F. J. Cannon's ELP Three-valve Portable (HF Pen, D, Pen) | PW85* |
| 1930 Sonotone Three-Four (HF Pen, HF Pen, Westcoter, Pen) | | PW53* | Parvo Flywheel Midjet Portable (SG, D, Pen) | PW77* |
| Battery All-Wave Three (113, LF RC) | | PW55* | Four-valve: Blueprint, 1s. | |
| The Monitor (HF Pen, D, Pen) | | PW61* | "Imp" Portable 4 (D, LF, LF Pen) | PW86* |
| The Tutor Three (HF Pen, D, Pen) | | PW62 | MISCELLANEOUS | |
| The Centaur Three (SG, D, LF) | | PW64* | Blueprint, 1s. | PW48A* |
| The "Clit" All-Wave Three (D, 2 LF RC & Trans) | | PW72* | S.W. Converter-Adapter (1 valve) | PW48A* |
| The "Rapid" Straight 3 (D, 2 LF RC & Trans) | | PW82* | AMATEUR WIRELESS AND WIRELESS | |
| F. J. Cannon's Oracle All-Wave Three (HF, Det, Pen) | | PW78* | CRYSTAL SETS | |
| 1938 "Tribune" All-Wave Three (HF, Pen, D, Pen) | | PW84* | Blueprints, 6d. each. | |
| F. J. Cannon's "Sprite" Three (HF Pen, D, Pen) | | PW87* | Four-station Crystal Set | AW427* |
| The "Hurricane" All-Wave Three (SG, D, Pen, Pen) | | PW89* | Lugene Tuning Coil for A.W.427, 6d. | AW444 |
| F. J. Cannon's "Pistol" 441111 Three (HF Pen, D, Pen, Pen) | | PW92* | 1934 Crystal Set | AW450* |
| Four-valve: Blueprints, 1s. each. | | | 150-mile Crystal Set | AW450* |
| Beta Universal Four (SG, D, LF, C, B) | | PW17* | STRAIGHT SETS. Battery Operated. | |
| Nucleo Class B Four (SG, D, LF, LF, LF) | | PW34B* | One-valve: Blueprint, 1s. | AW387* |
| Fury Four Super (SG, SG, D, Pen) | | PW34C* | B.C. Special One-valver | AW387* |
| Battery Hill-Mark 4 (HF, Pen, D, Push 4, B) | | PW46* | Two-valve: Blueprints, 1s. each. | |
| "Active" All-Wave 4 (HF Pen, D, Pen) LF, C, B | | PW83* | Melody Ranger Two (D, Trans) | AW388* |
| The "Standard" Four (HF Pen, HF Pen, D, Pen RC) | | PW90* | Full-volume Two (SG, det, Pen) | AW392* |
| | | | A modern Two-valver | WM409* |
| Mains Operated | | | Three-valve: Blueprints, 1s. each. | |
| Two-valve: Blueprints, 1s. each. | | | E5 5s. S.G. 3 (SG, D, Trans) | AW412* |
| A.C. Twin (D, LF, Pen) | | PW18* | Lugene Rander (SG, D, Trans) | AW422* |
| Sedotone A.C. Radiogram Two (D, Pen) | | PW19* | E5 5s. Three De Luxe Version (SG, D, Trans) | AW435* |
| Three-valve: Blueprints, 1s. each. | | | Transportable Three (SG, D, Pen) | WM427* |
| Double-Double-Tone Three (HF Pen, DDT, Pen) | | | Simple-Tune Three (SG, D, Pen) | WM327* |
| D.C. Ace (SG, D, Pen) | | PW23* | Economy Pentode Three (SG, D, Pen) | WM337 |
| A.C. Three (SG, D, Pen) | | PW25* | "W.M." 1924 Standard Three (SG, D, Pen) | WM351* |
| A.C. Leader (HF Pen, D, Pen) | | PW29* | E3.5s. Three (SG, D, Trans) | WM354 |
| D.C. Trouser (HF Pen, D, Pen) | | PW35* | 1935 6s. Battery Three (SG, D, Pen) | WM371 |
| Ubique (HF Pen, D, Pen, Pen) | | PW35B* | D, Pen | WM387 |
| F. J. Cannon's A.C. All-Wave Silver Solvent Three (HF Pen, D, Pen) | | PW36A* | PTP Three (Pen, D, Pen) | WM389* |
| "All-Wave" A.C. Three (D, 2 LF RC) | | PW36* | Certainly Three (SG, D, Pen) | WM393 |
| A.C. 1916 Standard (HF Pen, HF Pen, Westcoter, Pen) | | PW36* | Minute Three (SG, D, Trans) | WM396* |
| Mains Record All-Wave 3 (HF Pen, D, Pen) | | PW36* | All-wave Winning Three (SG, D, Pen) | WM400 |
| Four-valve: Blueprints, 1s. each. | | | Four-valve: Blueprints, 1s. 6d. each. | |
| A.C. Fury Four (SG, SG, D, Pen) | | PW34D | 6s. Four (SG, D, RC, Trans) | AW370 |
| A.C. Fury Four Super (SG, SG, D, Pen) | | PW34E | Self-contained Four (SG, D, LF, LF, B) | WM331 |
| A.C. Half-Mark (HF Pen, D, Push Full) | | PW45* | Lugene Straight Four (SG, D, LF, Trans) | WM350 |
| Universal Half-Mark (HF Pen, D, Push-Full) | | PW47* | E5 5s. Battery Four (HF, D, 2LF) | WM381* |
| | | | The H.K. Four (SG, SG, D, Pen) | WM384 |
| SUPERHETS | | | The Auto-Straight Four (HF, Pen, HF, Pen, DDT, Pen) | WM404* |
| Battery Sets: Blueprints, 1s. each. | | | Five-valve: Blueprints, 1s. 6d. each. | |
| Superhet (Three-valve) | | PW40* | Superquality Five (2 HF, D, RC, Trans) | WM320 |
| F. J. Cannon's Superhet | | PW32* | Class B Quadrupole (2 SG, D, LF, Class B) | WM344 |
| Mains Sets: Blueprints, 1s. each. | | | New Class B Five (2 SG, D, LF, Class B) | WM340 |
| A.C. 6s Superhet (Three-valve) | | PW43* | Mains Operated | |
| D.C. 6s Superhet (Three-valve) | | PW42* | Two-valve: Blueprints, 1s. each. | |
| | | | Consoloelec Two (D, Pen) A.C. | AW403* |
| | | | Economy A.C. Two (D, Trans) A.C. | WM286 |
| | | | Three-valve: Blueprints, 1s. each. | |
| | | | Home Lovers' New All-Electric Three (SG, D, Trans, A.C.) | AW383* |
| | | | Mantovan A.C. Three (HF, Pen, D, Pen) | WM374* |
| | | | E15 15s. 1936 A.C. Radiogram (HF, D, Pen) | WM401* |
| | | | Four-valve: Blueprints, 1s. 6d. each. | |
| | | | Al-Metal Four (2 SG, D, Pen) | WM329 |
| | | | Harris' Ambilee Radiogram (HF, Pen, D, LF, D) | WM386* |

| SUPERHETS | | Blueprints, 1s. 6d. each. | WM395* |
|----------------------------------------|--|---------------------------|--------|
| Vanity Four | | .. | WM397 |
| The Request All-Waver | | .. | WM397 |
| Main Sets: Blueprints, 1s. each. | | | |
| Heptode Super Three A.C. | | .. | WM359* |
| PORTABLES | | | |
| Four-valve: Blueprints, 1s. 6d. each. | | | |
| Hollyday Portable (SG, D, LF, Class B) | | .. | AW396* |
| Family Portable (HF, D, RC, Trans) | | .. | AW447* |
| Tycon Portable (SG, D, 2 Trans.) | | .. | WM367* |

| SHORT-WAVE SETS. Battery Operated | | Blueprints, 1s. each. | AW425* |
|------------------------------------------------------|--|-----------------------|--------|
| One-Valve: Blueprint for America | | .. | AW425* |
| Rona Short-Waver | | .. | AW452* |
| Two-valve: Blueprints, 1s. each. | | | |
| Ultra-short Battery Two (SG, det Pen) | | .. | WM402* |
| Home-made Coil Two (D, Pen) | | .. | AW440 |
| Three-valve: Blueprints, 1s. each. | | | |
| Experimenter's 5-metric Set (D, Trans, Super-regen) | | .. | AW448 |
| The Carrier Short-waver (SG, D, Pen) | | .. | WM399* |
| Four-valve: Blueprints, 1s. 6d. each. | | | |
| A.W. Short-wave World-Header (HF, Pen, D, RC, Trans) | | .. | AW456* |
| Standard Four-valver Short-waver (SG, D, LF, D) | | .. | WM385* |
| Superhet: Blueprint, 1s. 6d. | | | |
| Simplified Short-wave Super | | .. | WM397* |

| Mains Operated | | Blueprints, 1s. each. | AW458* |
|---------------------------------------------------------|--|-----------------------|--------|
| Two-valve: Blueprints, 1s. each. | | | |
| Two-valve Mains Short-waver (D, Pen, A.C.) | | .. | AW458* |
| Three-valve: Blueprints, 1s. each. | | | |
| Embrator (SG, D, Pen) A.C. | | .. | WM352* |
| Four-valve: Blueprints, 1s. 6d. | | | |
| Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) | | .. | WM391* |

| MISCELLANEOUS | | Blueprints, 1s. each. | AW459* |
|-----------------------------------------------|--|-----------------------|--------|
| S.W. 1-valve Converter (Price Ltd) | | .. | AW459* |
| Enthusiast's Power Amplifier (10 Watts) (1/6) | | .. | WM387* |
| Listener's 3-watt A.C. Amplifier (1/6) | | .. | WM392* |
| Radio Unit (2s.) for WM392 (1/6) | | .. | WM398* |
| Harris' Electrogram Battery and pHifer (1/5) | | .. | WM399* |
| De Luxe Converter A.C. Electrogram (1/5) | | .. | WM403* |
| New Style Short-wave Adapter (1/5) | | .. | WM388 |
| Short-wave Adapter (1/5) | | .. | AW455* |
| B.J. D.L.C. Short-wave Converter (1/5) | | .. | WM405* |
| Wilson Tone Master (1/5) | | .. | WM406 |
| The W.M. A.C. Short-wave Converter (1/5) | | .. | WM408* |

HINTS COUPON

This coupon is available until July 7th, 1947, and must accompany all Practical Hints.

PRACTICAL WIRELESS, July, 1947

All applications respecting Advertising in this Publication should be addressed to the ADVERTISEMENT DIRECTOR, GEORGE NEWNES, LTD., Tower House, Southampton Street, Strand, London, W.C.2. Telephone: Temple Bar 4383.

CONDITIONS OF SALE AND SUPPLY: This periodical is sold subject to the following conditions, namely, that it shall not, without the written consent of the publishers first given, be lent, re-sold, hired out or otherwise disposed of by way of Trade except at the full retail price of 9d., and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorized cover by way of Trade; or affixed to or as part of any publication or advertising, literary or pictorial matter, whatsoever.

'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Registered Trade Mark.

The UNIVERSAL AVOMINOR

Electrical Measuring Instrument



A small but highly accurate instrument for measuring A.C. and D.C. voltage, D.C. current, and also resistance. It provides 22 ranges of readings on a 3-inch scale, the required range being selected by plugging the leads supplied into appropriately marked sockets. An accurate moving-coil movement is employed, and the total resistance of the meter is 200,000 ohms.

The instrument is self-contained for resistance measurements up to 20,000 ohms, and, by using an external source of voltage, the resistance ranges can be extended up to 10 megohms. The ohms compensator for incorrect voltage works on all ranges. The instrument is suitable for use as an output meter when the A.C. voltage ranges are being used.

Supplied complete with leads, testing prods, crocodile clips, and instruction booklet.

D.C. Voltage

0-75 millivolts
0-5 volts
0-25 "
0-100 "
0-250 "
0-500 "

A.C. Voltage

0-5 volts
0-25 "
0-100 "
0-250 "
0-500 "

D.C. Current

0-2.5 milliamps
0-5 "
0-25 "
0-100 "
0-500 "

Resistance

0-20,000 ohms
0-100,000 "
0-500,000 "
0-2 megohms
0-5 "
0-10 "

Size: 4 1/2" x 3 1/2" x 1 1/2"

Nett Weight: 18 ozs.

Sole Proprietors and Manufacturers —

AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
Winder House, Douglas Street, London, S.W.1

Phone: VICTORIA 3404-9

AMBITIOUS ENGINEERS

HAVE YOU HAD YOUR COPY OF "ENGINEERING OPPORTUNITIES"?

Whatever your age or experience—whether you are one of the "old school" or a newcomer to Engineering anxious to hold your position under post-war conditions—you must read this highly informative guide to the best paid Engineering posts.

The Handbook contains among other intensely interesting matter, particulars of B.Sc., A.M.I.C.E., A.M.I.Mech.E., A.M.I.E.E., A.M.I.A.E., A.M.I.P.E., A.M.Brit.I.R.E., CITY & GUILDS, CIVIL SERVICE, and other important Engineering Examinations, outlines courses in all branches of CIVIL, MECHANICAL, ELECTRICAL, AUTOMOBILE, RADIO, TELEVISION, AERONAUTICAL and PRODUCTION ENGINEERING, DRAUGHTSMANSHIP, GOVERNMENT EMPLOYMENT, BUILDING and PLASTICS (the great peacetime careers), MATRICULATION, etc., and explains the unique advantages of our Employment Department.

WE DEFINITELY GUARANTEE 'NO PASS—NO FEE'

If you are earning less than £10 a week you cannot afford to miss reading "ENGINEERING OPPORTUNITIES": it tells you everything you want to know to make your future secure and describes many chances you are now missing. In your own interest we advise you to write for your copy of this enlightening guide to well-paid posts NOW—FREE and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

409, SHAKESPEARE HOUSE, 17, 18 & 19, STRATFORD PLACE, LONDON, W.1.

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by W. SPEAIGHT & SONS, LTD., Exmoor Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTCH (A/sia), LTD. South Africa: CENTRAL NEWS AGENCY, LTD. Subscription rates including postage: Inland 10s. 6d. per annum; Abroad 10s. per annum. Registered at the General Post Office for the Canadian Magazine Post.