

PRACTICAL WIRELESS




FEBRUARY 1966

2¢

**FREE
INSIDE**

Double Sided
BLUEPRINT
TO BUILD A
**PROGRESSIVE
SHORT WAVE
RECEIVER**

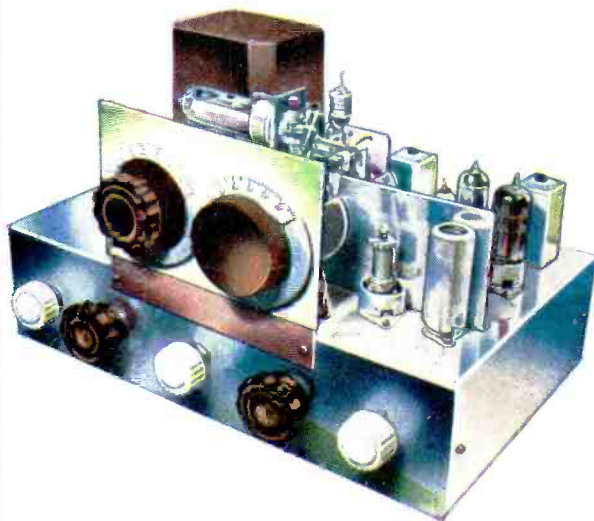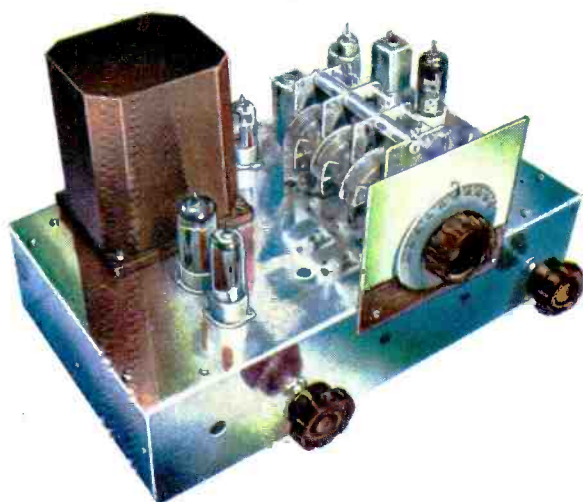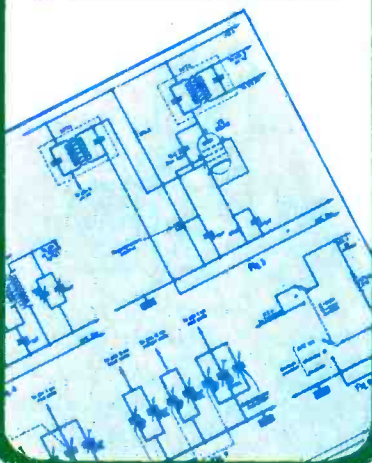- ★ BASIC 5V SUPERHET PLUS
- ★ R.F. STAGE
- ★ I.F. REGENERATION
- ★ BANDSPREAD
- ★ TUNING INDICATOR





SOLDERING INSTRUMENTS AND EQUIPMENT



DESIGNED FOR THE AMATEUR'S RADIO STATION

ILLUSTRATED
List No. 70 $\frac{1}{8}$ " BIT
IN
PROTECTIVE
SHIELD
List No. 68

for catalogue apply direct to:—
Sales and Service Dept.

**ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD, LONDON, S.W.4**

Telephones MACaulay 4272 & 3101 Telegrams SOLJOINT LONDON SW4

NOMBREX INSTRUMENTATION TRANSISTORISED AUDIO GENERATOR Model 63 £17.1.9

- ★ Laboratory Specification 10 C/s to 100 Kc/s.
- ★ Direct Calibration. ★ Sine and square output



Also available:

- ★ INDUCTANCE BRIDGE 66 ... £18. 6.9
- ★ POWER SUPPLY UNIT 61 ... £6.14.6
- ★ C.R. BRIDGE 62 ... £8.11.9
- ★ R.F. SIGNAL GENERATOR 27 ... £9.16.9

All prices include Battery, Post and Packing.

Prompt delivery

S.A.E. for Technical
Leaflets

Trade and Export
enquiries invited

NOMBREX LTD.

Phone: 3515

Estuary House, Camperdown Ter., Exmouth, Devon



**For quick, easy
faultless
soldering**

Ersin Multicore 5-core solder is easy to use and economical. It contains 5 cores of non-corrosive flux, cleaning instantly heavily oxidised surfaces. No extra flux is required. Ersin Multicore Savbit Alloy considerably reduces the wear of copper soldering iron bits.



HANDY SOLDER DISPENSER

12 ft. of 18 s.w.g. SAVBIT alloy in a continuous coil, used direct from free-standing dispenser.
2/6 each



LOW TEMPERATURE SOLDER

Size 9 pack contains 24 ft. of 60/40 high tin quality 22 s.w.g.
2/6 each
Size 10 pack 212 ft.
15/- each.



SAVBIT SIZE 1 CARTON

Contains approx. 30 ft. of 18 s.w.g. SAVBIT alloy. Also available in 14 and 16 s.w.g.
5/- each



BIB WIRE STRIPPER AND CUTTER

Strips insulation, cuts wire cleanly. Adjusts to any size.
4/- each

Available from all Electrical and Hardware shops.

If unobtainable write to:

MULTICORE SOLDERS LTD.

Multicore Works, Hemel Hempstead, Herts. Hemel Hempstead 3636 M.4/B

VALUE IN VALVES

Satisfaction of Money Back Guarantee on goods if returned unused within 14 days. ALL VALVES ARE NEW UNLESS OTHERWISE INFORMED. FREE TRANSIT INSURANCE. POSTAGE 1 valve 6d. 2-11 1/-. Free over 12.

024	4/6	6K25GT	8/3	1457	14/0	6E041	6/3	E224	5/9	R19	9/6
147GT	9/6	6K25	8/6	1465	7/9	6E031	5/9	E231	5/1	JF41	2/3
1053T	7/6	6L1	9/7	2013	5/6	6E-0	7/6	Z51	6/7	6P61	2/1
1135T	8/9	6V6G	7/6	2024	9/4	6E149	7/6	33	8/7	1441	6/9
1N63T	6/9	6L6G	6/6	2021	16/7	6E121	1/6	6232	7/6	1DD4	7/7
184	7/6	6L15	7/9	13P1	3/7	6E1	15/6	1V1R2	5/7	014	7/6
2D21	5/6	6B19	12/6	2023	11/7	6E32	3/7	KT33C	3/7	015	7/6
3A4	4/7	6L20	7/7	50P4	1/7	6E32	3/7	KT39	14/7	023	6/9
3A5	6/7	6E25	6/6	25AG6	8/7	6E034	8/7	KT44	6/7	024	12/6
3D6	4/7	6P28	9/6	35L6GT	7/6	6E04	6/5	KT45	8/6	025	8/3
3Q4	5/7	6Q7C	7/7	6E031	7/7	6E031	4/9	KT61	8/6	026	7/7
594G	8/7	6Q7GT	8/7	3CF3	6/7	6E032	4/7	KT73	5/9	035	12/6
5U4G	4/7	6SA7	5/7	30FL1	9/7	6E034	5/6	KT93	12/7	050	14/6
5Y3GT	9/6	6S67	4/7	30LL5	8/7	6E034	7/6	KT94	6/7	067	12/6
5Y3GT	4/7	6S7	5/7	30P4	9/7	6E035	6/7	KT33	17/6	091	9/7
5Z4	9/7	6S17GT	5/6	30P12	11/7	6E035	9/6	KT61	5/9	0281	8/6
5Z4G	7/7	6S20GT	4/6	30P11	9/3	6E030	6/7	KT63	5/9	0282	15/7
5Z4GT	9/6	6S2GT	5/7	30P5	5/8	6E031	8/3	KT23	7/7	0301	12/6
630L2	9/7	6U1GT	8/7	35L6GT	3/7	6E041	11/6	KT14	10/6	031	12/6
6A5G	7/9	6V6G	4/7	30P4	9/7	6E035	7/6	33	10/6	031	19/7
6A7G	7/6	6V6GT	6/7	35Z4GT	5/6	6E042	8/6	73	13/7	043C30	7/7
6AK5	4/3	6X4	4/4	6L6GT	5/5	6E031	7/7	NT05	1/7	04F42	19
6AQ7	5/7	6X5G	5/7	80	5/7	6E0193	6/3	PC36	10/7	0J41	6/6
6AT6	5/7	6X5GT	6/7	135BT	15/6	ECL89	6/6	PC37	7/6	0C41	7/6
6AV6	6/7	6Y7	6/7	18E1TA	19/6	ECL89	8/6	PC38	6/6	0C81	6/6
6BA6	5/6	705	7/3	807E	4/9	6E036	10/3	PC08	11/9	0F89	7/6
6BE6	5/6	70C	7/3	513	4/9	6E036	3/6	PC09	8/6	0C81	9/6
6B6G6	15/7	7H7	5/7	506A	12/6	F39	4/6	PC039	13/6	0E59	7/6
6BH6	5/7	7S7	5/7	984	3/6	F39	11/6	PC08	9/6	0C80	8/6
6B8	5/6	7S7	4/6	93	2/5	FL41	3/7	PC32	6/7	0C81	9/3
6BR7	8/6	10C1	9/7	956	2/7	FL54	3/3	PC34	12/7	0C142	7/3
6BW6	6/9	10C2	14/6	9001	2/7	FL40	3/6	PC36	7/6	0C131	7/9
6BW7	5/7	10P1	4/9	9002	2/7	FL45	6/7	PL32	7/5	0L82	8/7
6C4	2/6	10P14	6/16	6003	5/6	FL35	7/6	PL33	9/7	0L33	10/6
6E1	5/6	10P17	8/6	6P24	2/6	FL31	6/6	PL34	7/7	044	6/6
6C9	5/6	10D114	9/6	6Z21	6/7	FL31	6/7	PL35	10/7	0F42	4/9
6C9	11/7	12A4H7	7/7	80	4/6	FL32	3/7	PL36	10/6	0U30	6/3
6C0D6	17/7	12A4H8	9/7	6L31	19/7	FL133	9/6	PE25	8/9	0F85	7/6
6D6	3/7	12A4T6	6/6	6L33	9/7	FL134	9/6	PE45	8/6	0F89	5/9
6E1	4/9	12A4T7	8/6	6L31	7/6	FL32	8/6	PE46	4/6	0L1	7/6
6F6G	3/6	12A4U6	9/7	6AF91	4/6	FL33	6/6	PL13	8/6	0L44	14/7
6F13	4/3	12A4U7	4/6	6AF90	7/3	FL34	11/6	PL38	9/6	0L46	8/3
6F14	9/6	12A4V6	6/3	6D91	6/7	FL35	6/7	PL28	17/6	0L84	7/7
6F15	9/6	12A4X7	6/7	6D92	7/3	FL33	12/6	PL51	7/9	0R1C	7/6
6F23	6/6	12B4B6	7/7	6D96	8/7	FL41	8/7	PL52	6/6	0M30	8/6
6F53	3/7	12B4E6	6/6	6K91	5/6	FL42	7/9	PL13	6/6	0U6	8/9
6J5GT	4/3	12B4H7	8/9	6K92	7/7	FL44	6/6	PL34	7/6	0U6	11/7
6J6	2/6	12E1	17/6	6K96	7/4	FL44	6/6	PL31	8/7	0Y21	9/6
6J7G	4/9	12J7GT	8/7	6L82	5/7	FL50	7/9	PS32	10/7	0Y41	6/7
6J7GT	7/6	12J7GT	8/6	6L84	6/6	FL31	6/6	PS39	6/6	0Y41	6/7
6K5GT	6/7	12K3	9/9	6L86	7/3	FL24	8/9	PS1	5/9	0Y85	5/7
6K7	5/9	12K3GT	9/6	6EABC80	6/6	FL35	8/6	PS2	5/9	0V105	5/7
6K7G	1/7	12Q7GT	5/7	6EAF42	3/8	EY51	3/6	Y38	9/7	0V150	7/9
6K7GT	4/6	12S47	6/3	6E041	5/7	EY38	7/3	Y38	8/6	X66	7/9
6K8	9/6	12S47	2/9	6E041	2/9	EY38	8/6	Y38	8/6	Y38	6/6
6K8G	5/7	12S47	7/6	6EBC33	4/9	EY49	6/6	Y23	9/6	Z66	8/6

GUARANTEED 3 MONTHS BY RETURN OF POST

Tubes

MOST MULLARD	12in.
MAZDA, COSSOR	14in.
EMITRON, EMISCOPE, BRITE	15-17in.
PERANITYPES	19in.
PROCESSED IN OUK OWN FACTORY	21in.
	23in.

SATISFACTION GUARANTEED

HIGHEST QUALITY—COMPARE OUR PRICES

GUARANTEE		NEW TYPES
6 months	12 months	MW31/74
£2. 0. 0	£3. 0. 0	£3.15. 0
£2.10. 0	£3.10. 0	MW 38/24
£3. 5. 0	£4. 5. 0	£4.15. 0
£3. 5. 0	£4. 5. 0	CRM 172
£3.15. 0	£5.15. 0	MW 43/64
		£6.0. 0

Autochangers, etc.

LATEST GARRARD
All Factory Fresh. All with cartridge.
SRP10 Mono (Single) Player, £4.19.0.
SP25 Semi-Transcription (Single), £11.19.0.
AUTOSLIM (Standard Auto), £5.19.0.
AT6 Auto (Limited Number), £8.19.0.
AT5 Slimline—similar to AT6, £7.15.0.
Model 1,000—Compact low-priced record changer, automatically playing up to 10 records, £6.19.0.
Model 2,000—Automatic record changer with large turntable, playing up to 5 records, £7.19.0.
Model 3,000 Designed for use with high-compliance cartridges; low mass arm gives exceptionally low record wear, £10.19.0.
AT60 Automatic or manual operation has precision arm, bias compensator and heavy turntable, £11.19.0.
AT70 For the critical user—offers automatic playing with push-button platform, and many other features, £19.19.0.
LAB80—An outstanding automatic transcription turntable for professional reproduction, £22.19.0.
301—Transcription Heavy Table, £22.
401—Transcription turntable with heavy 12in. turntable, machine-cut tone arm, neon lamp and speed control, £29.19.0.
Model 50—Automatic record changer with large turntable, weight-counterbalanced arm and plug-in pick-up head, £9.19.0.
H.S.R.
KUT7—Single Deck Complete, £45.0.
UA14 or U25—Auto Changer, £5.15.0.

DULCI (VHF) FM. TUNERS MODEL PMT5. Self powered 200-250 vae. High sensitivity and automatic gain control for long distance reception. Size 11 1/2 x 8 1/2 x 3 1/2 in. Weight 7 1/2 lbs. In case finished satin chrome & black. Due to fortunate purchase we can offer limited number of these Hi-Fidelity instruments at special prices normally £21.15.5 at

ROPHONE ORDERS
Your C.O.D. order for any items exceeding £1 can be telephoned to BRIGHTON 650722 at any time day and night for seven days a week.

TEST EQUIPMENT. ITI-1 Transistorised Signal Injector, complete with Transistor Oscillator with Indicator Lamp, Detachable Test 35/- Probe and instructions.

IDEAL FOR ANY RECORDER. PRICES SLASHED. GUARANTEED. APPLICABLE TO ALL THE WORLD FAMOUS MAKE BY EXHAUSTIVE PURCHASE.

★ TAPE ★
We offer you fully tensilised polyester/nylon and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control—manufacture. Not substandard in any way. Try one for yourself. They are truly worth a few more coppers than acetate, substandard, jointed or cheap imitations. Try one and prove it for yourself!

Standard Play	Double Play
3" 150ft. 2/3	3" 300ft. 4/7
4" 300ft. 4/8	4" 600ft. 8/5
5" 600ft. 7/6	5" 1200ft. 15/5
6" 900ft. 10/6	6" 1800ft. 19/7
7" 1200ft. 13/6	7" 2400ft. 27/7
Long Play	Triple Play
3" 225ft. 2/9	4" 900ft. 13/4
4" 450ft. 4/6	5" 1800ft. 22/5
5" 900ft. 10/6	6" 2400ft. 34/7
6" 1200ft. 13/7	7" 3600ft. 44/7
7" 1800ft. 18/8	8" 4800ft. 8/7

Postage 1/- or Post Free less 5% on three reels. Quantity and Trade enquiries invited.

HITACHI PORTABLE TAPE RECORDER
Fabulous quality and reproduction of music. 6 transistor, 1 1/2in. and 3 1/2in. speeds. Output 500mw into high quality 8-ohm speaker. Automatic control knob. Fast forward and rewind. Battery level and record level meter. Fast load. Precision capstan drive with dynamic capstan motor recording. Radio recording leads. Outside speaker facilities. The most outstanding portable in the country. Size 8 1/2 x 3 1/2 x 6 1/2 in. Genuine normal price of 35 guineas. Unrepeatable. 12 months guarantee. All spares available. With 19Gns. tape, tape reel, mike, etc.

HITACHI AM/FM Radios
Wonderfully styled, guaranteed top make, 10-transistor with full long and medium waves. Size 9 1/2 x 6 1/2 x 12 1/2 in. Magnificent reproduction. A pleasure to look at. "An aristocrat in its class." 12 months guarantee against faulty manufacture. Genuine retail price £26.7s. 17Gns. Unrepeatable.

PRICES SLASHED

L227 TAPE RECORDERS. Famous make, latest Silver/Grey finish, 4-inputs 2-speed 3 1/2 x 7 1/2in. Complete with microphone, footage counter, volume level indicator, tone control, spare spool. This machine takes 7in. spools and is a full size Recorder, not a toy! Price normally **£17.10.0** £30.9.0. 5/- p.p.

HITACHI 4 TRACK MODEL TRA-505. This superior 48 guinea recording machine is on very special limited offer. Two channel recording. Plays stereo tapes, 1 1/2in. and 3 1/2in. speed. One track can be listened to on an earphone whilst recording on the second track, and thereafter both tracks played simultaneously through the loudspeaker. Ideal for languages, singing to music etc. Excellent reproduction through Hi-Flex. Elliptical speaker. A.C. erase. Dimensions 11 1/2 x 5 1/2 x 7 1/2 in. 1 lb. Dynamic mike. Sound level meter. Footage indicator. **Two 29Gns.**

TRANS/CEIVER TYPE RT68. The very latest Silver/Black finish. They gave a fantastic performance with reliability, long telescopic aerial, crystal controlled. Radio licence required to transmit. They compare with much dearer mod- **£8.19.6** etc. 2/6 p.p.

25 WATT GUITAR SPEAKERS. Very heavy coated 12in. cast chassis. There is nothing to touch it for power handling and quality at this price. Plus 6/- p.p. **£4.19.0**

CONNECTING WIRE

P.V.C. Bright Colours. Five 4/- 25ft. coils only.

MAINS TRANSFORMERS

Excellent Quality Guaranteed Upright mounting 250-0-250v. 60mA, £37. 3A (80mA 12/6). Ditto semi-shrouded. **9/6**

SPECIAL C.R.T. OFFER

Due to huge Bulk Special Purchase we are offering CRM141 and MW 36/24 Tubes at the unrepeatable price of 39/-. P.P. 12/6. The above are guaranteed for 6 months.

BULK BARGAINS ★

12 POTS. Popular values. 5K to 2 Meg. Unused, mixed present, long sp. switch, etc. **4/6**
CONDENSERS. 25 mixed electrolytics, various popular sizes. List value 5s. Our price **10/-**

100 RESISTORS 6/6
Excellent. Sizes 1-3 watt.
100 CONDENSERS 9/6
Miniature Ceramic and Silver Mike Condensers, 3pF to 5.000pF. LIST VALUE OVER 5s.
25 TAG STRIPS 4/-
2, 4, 6, 8-way etc. Unused.
100 HI STABS 9/6
1 1/2 to 5 1/2 100 Ω to 5 M Ω.

TRANSISTORS

GUARANTEED TOP QUALITY (Blue transistor, Red Spot standard L.F.s or now only White Spot R.F.s.....) **1/6**
Mullard Matched Output **12/6**
Kits OC31D and 2-0C31 **12/6**
3 transistors.
AF114 8/- OC44 5/6
AF115 7/6 OC45 5/6
AF116 7/6 OC72 5/6
AF117 7/6 OC91 5/6
AF127 9/6 OCSD1 5/6
OC26 12/6 OC82 8/6
OC38 14/- OC170 8/6
OC171 8/6

GERMANIUM DIODES

General Purpose miniature detector A.C.C. etc. **8d.**
30/60 series **1/-**
Gold Bonded highest quality individually tested. **1/-**
9/6 doz.

SILICON RECTIFIERS

Guaranteed performance. Top Makes. Tested 250v. working. 100mA (3 for 9/6) **3/9** (20mA) **7/6** (3 for 18/8)

LOUDSPEAKERS. 3 Ω Top Makes 6 1/2in. **7/6** 5in. **8/6** 7 x 4in. **8/6**

TECHNICAL TRADING CO.

Post: 25lbs. 2/-, 4lbs., 2/6, 7lbs., 3/6, 15lbs., 4/-, etc. (C.O.D. extra). ALL VALVES LESS 5% AND POST FREE IN DOZENS. Retail only, Hi-Fi Demonstrations, 72 East Street, Southampton, Tel. 20224. 350/353 Fratton Road, Portsmouth, Tel. 20224. ALL MAIL ORDERS AND REPLIES AT TECHNICAL TRADING CO., 11-12 NORTH ROAD, BRIGHTON




Heathkit models offer outstanding performance plus highest quality - at lowest cost

Anyone can build a Heathkit model. The easy-to-follow instruction manual issued with each kit-set show you how. You will be proud of the professional appearance and performance of your finished model.

A KIT FOR EVERY INTEREST . . . FOR HOME, WORKSHOP, SERVICE & TEST DEPT.

TEST INSTRUMENTS

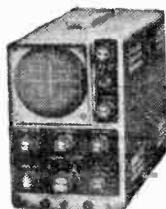

OS-2

NEW! 3" PORTABLE 'SCOPE, OS-2
With improved performance and modern styling. "Y" bandwidth 2 c/s-3 mc/s. Automatic Lock-in sync. Mumetal C.R.T. shield. P.C. Board. Size 5" x 7" x 12" deep. Weight 9½ lb.
£30.8.0 Assembled

£22.18.0 Kit

5in. OSCILLOSCOPE Model 10-12U.
Laboratory quality at utility oscilloscope price. Wide band amplifiers essential for T.V. servicing, F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges.
£45.15.0 Assembled

£35.17.6 Kit

DE-LUXE TRANSISTOR TESTER, IM-30U
Provides complete d.c. analysis of PNP, NPN transistors and diodes.

£35.10.0 Assembled

£24.18.0 Kit

REGULATED POWER SUPPLY Model IP-20U. Transistorised, 0.5-50 v. D.C. Up to 1.5 amps. Compact: 9½ x 6½ x 11 in.
£47.8.0 Assembled

£35.8.0 Kit

VALVE VOLTMETER, Model V-7A. The world's best selling VTVM. Measures up to 1,500 volts (d.c. and r.m.s.) and 4,000 pk. to pk. Res. 0.1 Ω 1,000 MΩ. Centre zero dB scale, d.c. input resistance 11MΩ. 4½in. meter. Complete with test prods, leads and standardising battery.

£19.18.6 Assembled

£13.18.6 Kit




V-7A

DE-LUXE 6in. VALVE VOLTMETER, Model IM-13U. Similar spec. to model V-7A but with improved accuracy. Larger meter. Unique gimbal mount.

£26.18.0 Assembled

£18.18.0 Kit

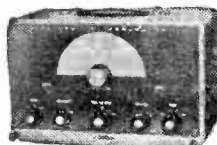

IG-82U

NEW! SINE/SQ GENERATOR, Model IG-82U. Freq. range: 20 c/s - 1 Mc/s in 5 bands. Simultaneous sine and square wave outputs.

£36.10.0 Assembled

£24.10.0 Kit

HARMONIC DISTORTION METER, Model IM-12U. Fre. cov.: 20-20,000 c/s.

£34.0.0 Assembled

£24.15.0 Kit

TV ALIGNMENT GENERATOR, Model HFV-1. Covers 3½ to 220 Mc/s fundamentals.

£47.10.0 Assembled

£37.18.0 Kit

RF SIGNAL GENERATOR, Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s harmonics. Up to 100 mV output on all bands.

£19.18.0 Assembled

£13.8.0 Kit

MULTIMETER, Model MM-1U. Ranges: 0-1.5 v. to 1,500 v. a.c. and d.c.; 150µA to 15A d.c.; 0-2Ω to 20MΩ. 4½in. 50µA meter.

£18.11.6 Assembled


£12.18.0 Kit

A wide range of other test instruments available including: R/C Bridge C-3U £10.10.0, AF V/Voltmeter AV-3U £16.10.0 Wattmeters AW-1U, £17.5.0. Capacitance meter CM-1U £15.15.0. Power supplies, Decade boxes etc.

AMATEUR EQUIPMENT

AMATEUR TRANSMITTER, Model DX-100U. Covers all amateur bands 160-10M. 150 w. d.c. input, self contained with power supply. Modulator, VFO
Assembled £104.15.0

£79.10.0 Kit

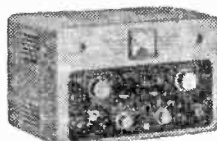

DX-40U

AMATEUR TRANSMITTER, Model DX-40U. Covers 80-10 m. Power inputs 75 w. C.W., 60 w. peak C.C. phone. Output 40 w. to aerial. Prov. for VFO

£33.19.0 Kit

Assembled £45.8.0

AMATEUR BANDS RECEIVER, RA-1

Outstanding performance at low cost. Covers the amateur bands from 160-10 metres. Half lattice filter. Signal strength meter.
£52.10.0 Assembled

£39.6.6 Kit



Other kits in the amateur range include: SSB Adaptor SB-10U £39.5.0. Variable freq. Oscillator VF-1U £10.17.6. Balun Coil Unit B-1U £4.15.6. Grid-Dip Meter GD-1U £10.19.6. Q Multiplier QPM-1 £8.10.0. Reflected Power Meter HM-1U £8.5.0. Receiver, RG-1 £39.16.0.

HI-FI SPEAKER SYSTEMS

BERKELEY Slim-line LOUDSPEAKER SYSTEM


★ Now from Heathkit, a loudspeaker kit with a fully finished walnut cabinet. ★ A 2 speaker system. ★ Modern, slim-line styling. ★ 30 c/s to 17 kc/s. ★ Only 7½" thick. ★ Use it horizontally or vertically. ★ Stand it on the floor or in your bookshelf.

Kit £18.10.0. Assembled £23.0.0.

COTSWOLD STANDARD MODEL
Acoustically designed enclosure "in the white" 26 x 23 x 15½in. 12in. bass speaker, elliptical middle speaker, 2in. pressure unit. Covers 30-20,000 c/s.

Complete kit with all controls.

£25.12.0 Kit

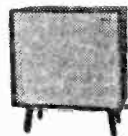

MFS SYSTEM

A minimum floor space model for the smaller room. 26in. high x 16½in. x 14in. deep. Similar performance to standard model.

£25.12.0 Kit

SSU-1 SYSTEM

A practical solution to the problem of a moderately priced speaker suitable for Stereo Mono amplifiers where the equipment has to be compact. Two speakers, balance control, ducted port reflex cabinet.

Incl. P.T. £11.17.6 Kit

(less legs)

Set of 4 legs (7" or 15") 14/6 extra.



DAYSTROM LTD

Dept. PW2 GLOUCESTER, ENGLAND


MODELS FOR HOME. TEST AND WORKSHOP.
BRITISH HEATHKIT MODELS USE BRITISH COMPONENTS



HI-FI AMPLIFIERS

DE-LUXE ALL TRANSISTOR STEREO AMPLIFIER AA-22U.

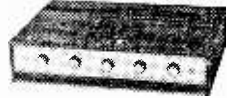At last, a British transistor amplifier with high power (20 + 20W) at a reasonable cost, capable of delivering full power at all frequencies in the audio band. Handsome fully finished walnut veneered cabinet available. Professional slim-line styling. Send for full specification. Kit (less cabinet) £39.10.0 Cabinet £25.0. Accessories for panel mounting £1.18.0.



6W DE-LUXE STEREO AMPLIFIER. Model S-33H. An inexpensive stereo amplifier with high sensitivity. Suitable for use with Decca Deram cartridge. £15.17.6 Kit

TAPE RECORD/REPLAY AMPLIFIER KITS. Will operate with most tape decks. Send for details.

TA-1M (Mono), £19.18.0 Kit. **TA-IS (Stereo),** £25.10.0 Kit. **STEREO CONTROL UNIT.** Model USC-1. Ideal for use with MA-12 amplifiers. Kit £19.10.0. Assembled £26.10.0.

6W STEREO AMPLIFIER Model S-33. 3 w/ch.. Inputs for radio, tape and gram. Stereo/Mono ganged controls. Sensitivity 200mV. £18.18.0 Assembled £13.7.6 Kit



S-33

TRANSISTOR MIXER, Model TM-1. A must for the Tape enthusiast. £11.16.6 Kit

5W HI-FI MONO AMPLIFIER. Model MA-5. A low priced amplifier based on the S-33. Printed circuit construction makes it easy to build. £10.19.6 Kit

HI-FI MONO POWER AMPLIFIER. Model MA-12. Ideal for use with Models USC-1 and UMC-1, 0.1 THD at 10W. Wide frequency range. £11.18.0 Kit

18W STEREO AMPLIFIER. Model S-99. Ganged controls. Stereo/Mono gram. radio and tape record inputs. P/B selection. £38.9.6 Assembled £28.9.6 Kit




S-99

A range of R/players, T/Decks available.
Send for full spec. of any model


TRANSISTOR RECEIVERS

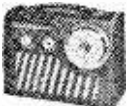"OXFORD" LUXURY TRANSISTOR DUAL WAVEBAND RECEIVER. The ideal domestic or personal portable receiver. 10 Semi-conductors. Solid leather case. Send for full details. £14.18.0 Kit Incl. P.T.



6 TRANSISTOR PORTABLE. Model UXR-1. Preamplified I.F. transformers. Printed circuit, 7in. x 4in. high flux speaker. Real hide case. Very easy to build. Incl. P.T. £12.11.0 Kit

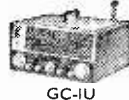
"MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U. Excellent portable or general purpose receiver for "amateur" or short wave listening. See full spec. leaflets. Assembled £45.17.6 £37.17.6 Kit



GC-1U

PA/GUITAR AMPLIFIERS

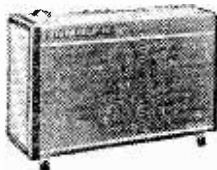Model PA-1 (similar to PA-2 illustration) 50 watt output. Two 12" L.S. Variable tremolo, 4 inputs. Assembled £54.15.0 Kit £74 legs or castors available (extras). **Model PA-2** (illustrated). **Starmaker 33.** All transistor 20 watt output, two 12" L.S. Variable tremolo, 4 inputs. Compact size. Assembled £59.10.0 £44.19.0 Kit



PA-2

Legs or castors available (extras). 50 watt Power Amp. MA-50 Assembled £27.18.0 £19.18.0 Kit

HI-FI TUNERS

Model FM-4U. Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s. I.F. (£2.15.0 incl. P.T.), I.F. Amp. (FMA-4U) complete with cabinet and valves (£13.13.0). Total £16.8.0 Kit



FM-4U

Assembly can be arranged. **AM/FM TUNER.** Covers FM 88-108 Mc/s. A.M. 16-50, 200-550, 900-2,000 m. Tuning heart (£4.13.6 incl. P.T.), and I.F. Amp. (£22.11.6). Total £27.5.0 Kit Send for leaflets. Assembly can be arranged.

EQUIPMENT CABINETS



A large range, in kit form or assembled and finished, available to meet most needs. Illustrated details on request. Prices from £8.8.0 to £46.4.0

SPEAKERS FOR YOUR OWN ENCLOSURE

12" Heavy-duty Bass (Fane 122/12) £7.7.0.
2" Tweeter (Fane 301) £3.1.6.
(both as used in the Cotswold systems).
12" Bass speaker (Audiom-51) £9.12.5.
8" Goodman's General Purpose GB £1.8.6.
Two Speakers + Cross-over System SCM-1.
(As used in model SSU-1) with details for enclosure £5.5.0.

ELECTRONIC WORKSHOP KIT. Model EW-1. An outstanding experimental kit for children. £7.13.6 incl. P.T.

A WIDE RANGE OF BOOKS ON ELECTRONICS AND RADIO. PLEASE SEND FOR LISTS OR PRICES.

American Heath Catalogue, price lists in £ s. d. and details of direct delivery scheme sent for 1/- p. paid.

Many other models for HOME, OFFICE or WORKSHOP send for **FREE BRITISH CATALOGUE** Instrument Brochure or Amateur Radio Brochure

To DAYSTROM LTD. Dept. P.W.-2, GLOUCESTER, ENG.

Please send me FREE BRITISH CATALOGUE (Yes/No)

Full details of model(s) _____

NAME _____

ADDRESS _____

BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090

NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK, ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE, PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE.

0A3	5/8	68X6	4/3	7B7	9/6	25Z5	7/3	AC/PEN	E834	1/4	E185	7/8	L7329	6/8	RG1/240A	U301	11/-	GD14	10/-		
0B2	6/1	6C4	2/8	7C3	8/1	25Z6GT	8/1	(C) 17/6	E841	4/8	E186	7/8	MH24	7/6	U329	9/-	GET108	7/6	GET108	7/6	
0Z4GT	4/2	6C5	4/1	7C6	6/9	28D7	6/9	AC/PEN	E891	2/3	E191	2/6	MHLD612	6/8	RK34	6/8	U339	9/8	GET104	3/6	
LA3	2/6	6C6	3/-	7C7	5/7	30C1	6/1	(7) 17/-	E8C3	2/6	E195	5/-	ML6	6/9	B130	22/6	U403	9/8	GET106	7/6	
LA5	12/6	6C8	3/-	7D3	15/-	30C15	10/0	AC/80	E8C30	6/-	E1360	27/-	M84B	20/5	8P4B	19/8	U404	6/1	GET111	2/6	
LA7GT	7/6	6C10	5/-	7P7	9/7	30C17	11/6	AC/80	E8C41	6/-	E1820	16/8	MU12144/6	8P4F	11/8	U409	15/-	GET113	6/8		
IC1	4/-	6C12	5/8	7H7	5/9	30F5	5/8	AC/TH110	E8C90	3/6	EL180	13/6	MX40	8/9	8P4Z	12/6	VMF40	14/8	GET114	6/8	
IC2	8/-	6C6DG	13/-	7R7	12/6	30FL1	9/3	AC/TP	E8C19	5/6	EM4	17/8	N9	10/8	8P61	2/-	VMS4B	12/-	GET175	3/6	
IC3	6/6	6C07	6/8	7Y7	5/7	30L1	5/6	AC/VP1	E8F90	5/6	EM34	11/8	N78	26/-	8U25	27/2	VP2	3/6	GET174	6/8	
IC5	5/4	6C8	6/8	7Y4	5/7	30L15	10/0	AC/VP2	E8F93	7/8	EM35	12/-	N108	26/2	T41	9/-	VP2B	9/8	GET113	6/8	
IC6	10/6	6C9W4	24/-	8D3	2/6	30L17	11/6	ATP4	E8F77	18/6	EM77	18/6	P23	25/-	TD2	14/8	VP4	14/8	GET114	6/8	
LD6	6/6	6D1	1/6	8B9W6	9/6	30P1	12/-	AZ1	E8L21	10/8	EM50	5/3	P4	3/6	TD4	7/6	VP4A	14/8	GET115	6/8	
LD9	6/6	6D3	9/6	9D2	3/6	30P12	7/6	AZ31	E8C52	4/3	EM61	7/-	P61	2/6	TE4B	10/8	VP4B	12/-	GET116	6/8	
LD11	6/6	6D5	3/1	9D7	7/6	30P16	5/8	AZ41	E8C13	12/6	EM84	8/-	PAC80	6/9	TE21C	10/8	VP3C	7/6	GET117	6/8	
LD15	6/6	6D9	9/6	10D1	7/8	30P19	13/8	B30	4/9	FC34	6/-	EM85	8/9	PBC9	9/9	TE30C	14/8	VP3B	2/6	GET118	6/8
LD16	6/6	6D9	9/6	10D1	7/8	30P14	9/6	B349	10/8	FC70	9/8	EM87	7/6	PC8	8/8	TE41	15/8	VP4	14/8	GET119	6/8
LD17	6/6	6D9	9/6	10D1	7/8	30P13	14/8	B719	5/9	EC90	2/3	EN31	10/-	PC95	8/9	TE23	3/6	VP3	3/6	GET120	6/8
LD18	6/6	6D9	9/6	10D1	7/8	30P14	11/3	BL63	10/8	EC91	4/-	EN91	5/6	PC97	6/8	TE33	3/6	VP7	21/-	GET121	6/8
LD19	6/6	6D9	9/6	10D1	7/8	30P15	9/6	CL	12/6	EC92	6/8	EY51	5/6	PC84	5/6	TE25	5/-	VP105	5/6	GET122	6/8
LD20	6/6	6D9	9/6	10D1	7/8	30P16	9/6	CEK506	6/8	EC93	7/3	EY81	7/3	PC95	8/9	TE26	7/6	VP150	4/8	GET123	6/8
LD21	6/6	6D9	9/6	10D1	7/8	30L17	11/6	CF498	6/8	EC94	12/6	EY82	6/8	PC98	9/11	TE68	11/6	VP160	4/8	GET124	6/8
LD22	6/6	6D9	9/6	10D1	7/8	30L18	11/6	CL33	11/6	EC95	29/1	EY84	9/6	PC99	9/11	TE69	11/6	VP170	4/8	GET125	6/8
LD23	6/6	6D9	9/6	10D1	7/8	30L19	11/6	CW6	2/6	EC96	24/7	EY86	5/6	PC189	10/-	TE70	11/6	VP180	4/8	GET126	6/8
LD24	6/6	6D9	9/6	10D1	7/8	30L20	11/6	CV63	10/8	EC97	4/8	EY88	9/8	PCF80	6/8	TE71	11/6	VP190	4/8	GET127	6/8
LD25	6/6	6D9	9/6	10D1	7/8	30L21	11/6	CV71	12/6	EC98	7/6	EY91	3/6	PCF82	6/8	TE72	11/6	VP200	4/8	GET128	6/8
LD26	6/6	6D9	9/6	10D1	7/8	30L22	11/6	CV72	12/6	EC99	7/6	EY93	3/6	PCF84	6/8	TE73	11/6	VP210	4/8	GET129	6/8
LD27	6/6	6D9	9/6	10D1	7/8	30L23	11/6	CV73	12/6	EC00	7/6	EY94	3/6	PCF86	6/8	TE74	11/6	VP220	4/8	GET130	6/8
LD28	6/6	6D9	9/6	10D1	7/8	30L24	11/6	CV74	12/6	EC01	7/6	EY95	3/6	PCF88	6/8	TE75	11/6	VP230	4/8	GET131	6/8
LD29	6/6	6D9	9/6	10D1	7/8	30L25	11/6	CV75	12/6	EC02	7/6	EY96	3/6	PCF90	6/8	TE76	11/6	VP240	4/8	GET132	6/8
LD30	6/6	6D9	9/6	10D1	7/8	30L26	11/6	CV76	12/6	EC03	7/6	EY97	3/6	PCF92	6/8	TE77	11/6	VP250	4/8	GET133	6/8
LD31	6/6	6D9	9/6	10D1	7/8	30L27	11/6	CV77	12/6	EC04	7/6	EY98	3/6	PCF94	6/8	TE78	11/6	VP260	4/8	GET134	6/8
LD32	6/6	6D9	9/6	10D1	7/8	30L28	11/6	CV78	12/6	EC05	7/6	EY99	3/6	PCF96	6/8	TE79	11/6	VP270	4/8	GET135	6/8
LD33	6/6	6D9	9/6	10D1	7/8	30L29	11/6	CV79	12/6	EC06	7/6	EY00	3/6	PCF98	6/8	TE80	11/6	VP280	4/8	GET136	6/8
LD34	6/6	6D9	9/6	10D1	7/8	30L30	11/6	CV80	12/6	EC07	7/6	EY01	3/6	PCF00	6/8	TE81	11/6	VP290	4/8	GET137	6/8
LD35	6/6	6D9	9/6	10D1	7/8	30L31	11/6	CV81	12/6	EC08	7/6	EY02	3/6	PCF02	6/8	TE82	11/6	VP300	4/8	GET138	6/8
LD36	6/6	6D9	9/6	10D1	7/8	30L32	11/6	CV82	12/6	EC09	7/6	EY03	3/6	PCF04	6/8	TE83	11/6	VP310	4/8	GET139	6/8
LD37	6/6	6D9	9/6	10D1	7/8	30L33	11/6	CV83	12/6	EC10	7/6	EY04	3/6	PCF06	6/8	TE84	11/6	VP320	4/8	GET140	6/8
LD38	6/6	6D9	9/6	10D1	7/8	30L34	11/6	CV84	12/6	EC11	7/6	EY05	3/6	PCF08	6/8	TE85	11/6	VP330	4/8	GET141	6/8
LD39	6/6	6D9	9/6	10D1	7/8	30L35	11/6	CV85	12/6	EC12	7/6	EY06	3/6	PCF10	6/8	TE86	11/6	VP340	4/8	GET142	6/8
LD40	6/6	6D9	9/6	10D1	7/8	30L36	11/6	CV86	12/6	EC13	7/6	EY07	3/6	PCF12	6/8	TE87	11/6	VP350	4/8	GET143	6/8
LD41	6/6	6D9	9/6	10D1	7/8	30L37	11/6	CV87	12/6	EC14	7/6	EY08	3/6	PCF14	6/8	TE88	11/6	VP360	4/8	GET144	6/8
LD42	6/6	6D9	9/6	10D1	7/8	30L38	11/6	CV88	12/6	EC15	7/6	EY09	3/6	PCF16	6/8	TE89	11/6	VP370	4/8	GET145	6/8
LD43	6/6	6D9	9/6	10D1	7/8	30L39	11/6	CV89	12/6	EC16	7/6	EY10	3/6	PCF18	6/8	TE90	11/6	VP380	4/8	GET146	6/8
LD44	6/6	6D9	9/6	10D1	7/8	30L40	11/6	CV90	12/6	EC17	7/6	EY11	3/6	PCF20	6/8	TE91	11/6	VP390	4/8	GET147	6/8
LD45	6/6	6D9	9/6	10D1	7/8	30L41	11/6	CV91	12/6	EC18	7/6	EY12	3/6	PCF22	6/8	TE92	11/6	VP400	4/8	GET148	6/8
LD46	6/6	6D9	9/6	10D1	7/8	30L42	11/6	CV92	12/6	EC19	7/6	EY13	3/6	PCF24	6/8	TE93	11/6	VP410	4/8	GET149	6/8
LD47	6/6	6D9	9/6	10D1	7/8	30L43	11/6	CV93	12/6	EC20	7/6	EY14	3/6	PCF26	6/8	TE94	11/6	VP420	4/8	GET150	6/8
LD48	6/6	6D9	9/6	10D1	7/8	30L44	11/6	CV94	12/6	EC21	7/6	EY15	3/6	PCF28	6/8	TE95	11/6	VP430	4/8	GET151	6/8
LD49	6/6	6D9	9/6	10D1	7/8	30L45	11/6	CV95	12/6	EC22	7/6	EY16	3/6	PCF30	6/8	TE96	11/6	VP440	4/8	GET152	6/8
LD50	6/6	6D9	9/6	10D1	7/8	30L46	11/6	CV96	12/6	EC23	7/6	EY17	3/6	PCF32	6/8	TE97	11/6	VP450	4/8	GET153	6/8
LD51	6/6	6D9	9/6	10D1	7/8	30L47	11/6	CV97	12/6	EC24	7/6	EY18	3/6	PCF34	6/8	TE98	11/6	VP460	4/8	GET154	6/8
LD52	6/6	6D9	9/6	10D1	7/8	30L48	11/6	CV98	12/6	EC25	7/6	EY19	3/6	PCF36	6/8	TE99	11/6	VP470	4/8	GET155	6/8
LD53	6/6	6D9	9/6	10D1	7/8	30L49	11/6	CV99	12/6	EC26	7/6	EY20	3/6	PCF38	6/8	TE00	11/6	VP480	4/8	GET156	6/8
LD54	6/6	6D9	9/6	10D1	7/8	30L50	11/6	CV00	12/6	EC27	7/6	EY21	3/6	PCF40	6/8	TE01	11/6	VP490	4/8	GET157	6/8
LD55	6/6	6D9	9/6	10D1	7/8	30L51	11/6	CV01	12/6	EC28	7/6	EY22	3/6	PCF42	6/8	TE02	11/6	VP500	4/8	GET158	6/8
LD56	6/6	6D9	9/6	10D1	7/8	30L52	11/6	CV02	12/6	EC29	7/6	EY23	3/6	PCF44	6/8	TE03	11/6	VP510	4/8	GET159	6/8
LD57	6/6	6D9	9/6	10D1	7/8	30L53	11/6	CV03	12/6	EC30	7/6	EY24	3/6	PCF46	6/8	TE04	11/6	VP520	4/8	GET160	6/8
LD58	6/6	6D9	9/6	10D1	7/8	30L54	11/6	CV04	12/6	EC31	7/6	EY25	3/6	PCF48	6/8	TE05	11/6	VP530	4/8	GET161	6/8
LD59	6/6	6D9	9/6	10D1	7/8	30L55	11/6	CV05	12/6	EC32	7/6	EY26	3/6	PCF50	6/8	TE06	11/6	VP540	4/8	GET162	6/8
LD60	6/6	6D9	9/6	10D1	7/8	30L56	11/6	CV06	12/6	EC33	7/6	EY27	3/6	PCF52	6/8	TE07	11/6	VP550	4/8	GET163	6/8
LD61	6/6	6D9	9/6	10D1	7/8	30L57	11/6	CV07	12/6	EC34	7/6	EY28	3/6	PCF54	6/8	TE08	11/6	VP560	4/8	GET164	6/8
LD62	6/6	6D9	9/6	10D1	7/8	30L58	11/6	CV08	12/6	EC35	7/6	EY29	3/6	PCF56	6/8	TE09	11/6	VP570	4/8	GET165	6/8
LD63	6/6	6D9	9/6	10D1	7/8	30L59	11/6	CV09	12/6	EC36	7/6	EY30	3/6	PCF58	6/8	TE10	11/6	VP580	4/8	GET166	6/8
LD64	6/6	6D9	9/6	10D1	7/8	30L60	11/6	CV10	12/6	EC37	7/6	EY31	3/6	PCF60	6/8	TE11					



MAIL ORDERS TO: 54 WELLINGTON STREET, LEEDS 1

Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

PERSONAL SHOPPERS WELCOME AT ANY BRANCHES BELOW. OPEN ALL DAY SATURDAY.

BRADFORD 10 North Parade Tel. 25349 (Half-day Wed).

BRISTOL 14 Lower Castle Street (Half-day Wednesday) Tel: 22904.

BIRMINGHAM 30/31 G. Western Arcade, opp. Snow Hill Station. CENTral 1279. No half-day

DERBY 26 Osmaston Rd., The Spot (Half-day Wed.) Tel: 41361

DARLINGTON 13 Post House Wynd (Half-day Wednesday) Tel: 68043

EDINBURGH 133 Leith Street, (Half-day Wed.)

GLASGOW 326 Argyle Street, Tel: City 4158 (No half-day).

HULL 51 Savile Street (Half-day Thursday) Tel: 20505

LEICESTER 32 High Street (Half-day Thurs.) Tel: 56420

LEEDS 5-7 County (Mecca) Arcade (No half-day) Tel: 28252

LIVERPOOL 73 Dale St. (No half-day) Tel: CENTral 3573

LONDON 238 Edgware Road W2 (Half-day Thursday) Tel: PADdington 1629

MANCHESTER 60A-60B Oldham St. Tel: CENTral 2778 (No half-day) New large store.

MIDDLESBROUGH (Half-day Wednesday) 106 Newport Road. Tel: 47096

SHEFFIELD 13 Exchange Street Castle Market Bldgs. (Half-day Thursday) Tel: 20716

VACANCIES FOR STAFF

AT VARIOUS BRANCHES SHOP EXPERIENCE UNNECESSARY Write to: Wellington St. Leeds 1

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-250v, 50 c/s, Screened. MIDGET CLAMPED TYPE 24 x 2 1/2 in. 250v. 60mA, 6.3v. 2a ... 13/9 250-0-250v. 60mA, 6.3v. 2a ... 14/9

TOP SHROUDED DROP THROUGH 250-0-250v. 70mA, 6.3v. 2a, 0-5-6.3v. 2a 17/9 350-0-350v. 80mA, 6.3v. 2a, 0-5-6.3v. 2a 21/9 250-0-250v. 100mA, 6.3v. 2a, 6.3v. 1a ... 21/9 250-0-250v. 100mA, 6.3v. 3.5a, C.T. ... 11/9 250-0-250v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a 28/9 300-0-300v. 130mA, 6.3v. 4a, 6.3v. 1a, for Mullard 510 Amplifier ... 35/9 300-0-300v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a 28/9 350-0-350v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a 28/9 350-0-350v. 150mA, 6.3v. 4a, 0-5-6.3v. 3a 37/9

FULLY SHROUDED UPRIGHT 250-0-250v. 60mA, 6.3v. 2a, 0-5-6.3v. 2a Midget type 2 1/2 x 3 in. ... 18/9 250-0-250v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a 29/9 300-0-300v. 100mA, 6.3v. 4a, 5v. 3a ... 29/9 300-0-300v. 130mA, 6.3v. 4a, C.T. 6.3v. 1a, for Mullard Amplifier ... 36/9 350-0-350v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a 28/9 350-0-350v. 150mA, 6.3v. 4a, 0-5-6.3v. 3a 38/9 425-0-425v. 200mA, 6.3v. 4a, D.T. 5v. 3a 57/9 425-0-425v. 200mA, 6.3v. 4a, D.T. 5v. 3a 57/9 450-0-450v. 250mA, 6.3v. 4a, C.T. 5v. 3a 59/9

TWEETERS R.A. 3 ohm 25/9 15 ohm 25/9

FANE HEAVY DUTY HI FI SPEAKERS 12" 70 watt. Type 1:2/10. Post 5/6. Only 5 Gns.

R.S.C. POWER PACK 39/9

Metal case only 8 x 5 1/2 x 2 1/2 in. For 200-250v. A.C. mains. Output at 4 pin plug and socket 250v. 60mA fully smoothed at 6.3v. 2a.

ARMSTRONG, TRUVOX, LEAK, QUAD, ROGERS, LINEAR, W.B., FANE, WHARFEDALE, GOODMAN, GARRARD, GOLDRING, GRAMPIAN, LUSTRAPHONE, SHURE, RESLO, TANDBERG, FERROGRAPH Products stocked. Usual credit terms available.

FLAMENT TRANSFORMERS

200-250v. 50 c/s primaries 6.3v. 5a, 5/9; 6.3v. 2a, 7/8; 12v. 1a, 7/11; 6.3v. 3a, 8/11; 6.3v. 6a, 17/8; 12v. 1.5a, twice, 17/6.

OUTPUT TRANSFORMERS Standard Pentode 5,000 Ω to 3 Ω Standard Pentode 7,000 Ω to 3 Ω Push-Pull 8 watts, EL84, or 6V6 to 9 Ω or matched to 15 Ω ... 9/9 Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5-8 to 15 Ω ... 19/9 Following types for 3 and 6V6 or 15 Ω speakers Push-Pull 10-12 watts, 6V6 or EL84 ... 18/9 Push-Pull 15-18 watts, 6L6, 6K6 ... 22/9 Push-Pull Mullard 510 Ultra Linear ... 29/9 Push-Pull 20 watts, sectionally wound 6L6, KT66, EL34 etc. ... 49/9

SMOOTHING CHOKES

60mA, 10H 400 Ω 4/11. 100mA, 10H, 220 Ω 8/9 80mA, 10H 350 Ω 5/9. 150mA, 10H, 250 Ω 11/9

CHARLIER TRANSFORMERS

All with 200-230-250 v. 50 c/s Primaries: 0-9-15v. 1a, 12/5; 0-9-15v. 2a, 14/9; 0-9-15v. 3a, 18/9; 0-9-15v. 5a, 19/9; 0-9-15v. 6a, 23/9; 0-9-15v. 8a, 28/9.

AUTO (Step up/Step down) TRANS.

0-110/120-230/250v. 50-80 watts, 13/9; 150 watts, 27/9; 250 watts, 49/9; 500 watts, 99/9.

MIKE PULSERS

120:1 1/9.

AUDIOTRINE HF100D 10in. 15 WATT HI-FI LOUVERS

AKERS Heavy cast construction. Dual cone Rubber surround. Smooth frequency response. 20-15000 c.p.s. Speechcoil 3 or 15ohm.

£5.15.0

R.S.C. GRAM AMPLIFIER KIT, 3 watts output.

Negative feedback Controls: Vol. T.C. and 5 switch. Mains operation 200-250v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr. 3/9.

SCOOP PURCHASE OF HIGH QUALITY RECORD CHANGERS

Brand new Garrard 3000 LM. Very latest model. Normal Retail price approx. £12.15.0. Heavy turntable and light Carr. 5/6 weight pick-up arm. High fidelity Stereo/Mono cartridge. Fully guaranteed.

11 GNS.

R.S.C. 4/5 WATT A5 HIGH GAIN AMPLIFIER




A highly-sensitive 4-valve quality amplifier for the home small club, etc. Only 50 millivolts input required for full output, is suitable for use with the best High-fidelity Pick-up heads and all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls provided giving full long-playing record equalisation. Hum level negligible being 71dB down 15dB of Negative Feedback used. A.T. of 200v. 25mA and I.H.F. of 6.3v. 1.5a, available for supply of Radio Feeder Unit or Tape-Deck pre-amplifier. For A.C. mains 200-230-250v. 50 c/s. Output for 2-3 ohms speaker Chassis is not alive. Kit is complete in every detail with fully punched Gold Hammer finished chassis, point-to-point wiring diagrams and in-struct. Manual. Exceptionally ready for use 25/- extra, plus 2/6 carr., deposit 22/6 and 5 monthly payments of 22/6 (total £8.15.0) for assembled unit.

R.S.C. SUPER 15 HI-FI AMPLIFIER R.S.C. SUPER 30 STEREO AMPLIFIER

FULLY TRANSISTORISED 200-250v. A.C. Mains Operation. OUTPUT 10 WATTS R.M.S. into 15 ohms. OUTPUT 15 WATTS R.M.S. into 3-ohms. Maximum Instantaneous Peak Power Output 28 watts. PRINTED CIRCUIT CONSTRUCTION. LATEST MULLARD TRANSISTORS AD149, AD149, OC127Z, OC81Z, OC44, OC44, OC91Z, OC44, AC107. 5 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES. SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV. FREQUENCY RESPONSE: 20-20,000 c.p.s. TREBLE CONTROL: +15dB to -15dB at 10 Kc/s. BASS CONTROL: +12dB to -15dB at 50 c/s. HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.35%. HUM LEVEL:-75dB. NEGATIVE FEEDBACK: 52dB.

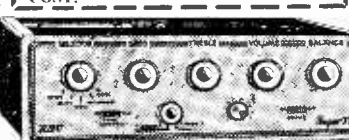WE PROUDLY INTRODUCE TWO COMPLETELY NEW UNITS WITH TECHNICAL SPECIFICATIONS COMPARING MORE THAN FAVOURABLY WITH SIMILAR AMPLIFIERS OFFERED AT 2-3 TIMES THE COST.



A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuits. Close tolerance Ganged Pots. Matched Components. CROSS-TALK:-52dB at 1,000 c.p.s. CONTROLS: 5 position Input Selector. Bass Control, Treble Control, Volume Control Balance Control, Stereo/Mono Switch, Tape Monitor Switch. INPUT SOCKETS (Matched Pairs) (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone. Operation of Input Selector Switch assures appropriate equalisation. Rigid 18 s.w.g. Chassis. Size approx. 12" Wide, 3" High, and 8" Deep. Attractive Facia Plate and Matching Knobs, Nona Panel Indicator. Above facilities, etc., except for Ganging and Balance Control, apply also to Super 15.

IMPORTANT NOTE. Rated output figures are given in R.M.S. and not speech and music or I.H.F.M., otherwise we could obviously quote much higher outputs.

Complete Kit of parts with full constructional details and point to point wiring diagrams. If preferred printed circuit ca. be supplied with parts soldered in and tested for 21/- extra. Attractive Walnut or Teak finished cover 6 Gns. Or Deposit 19/- and 9 monthly payments 13/2. Total £6.17.6. Or unit factory built and tested, complete with Cover and with our usual 12 months guarantee. Or Deposit £3.2.0 and 9 monthly payments 43/3. Total £22.11.3. A.L.I. COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING BRITISH MANUFACTURERS. Send S.A.E. for leaflet.

9 1/2 Carr. 10/- GNS. 19 1/2 Carr. 12/6 GNS. 2 Carr. 12/6 GNS.

THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MIC. CURRENTLY AVAILABLE REGARDLESS OF THE COST. SUPERIOR SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts, point to point wiring diagrams and detailed instructions 18 GNS. If required printed circuits can be supplied with appropriate components assembled, soldered and tested for 2 Gns. extra. Terms: Deposit 6 Gns. & 9 mthly payments 36/6 Total £22.14.6. Attractive Walnut or Teak finished cover 6 Gns. or Deposit 19/- & 9 mthly payments 13/2 Total £6.17.6. Or unit completely assembled ready for use fitted cover as above or 29 GNS. Deposit £4.12.0 & 12 mthly p'ments 48/6 Total £33.8.0 GNS.

R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER


PROVIDING 10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL

SUITABLE for "MIKE", GRAM., RADIO OR TAPE. INTENDED FOR THE HOME OR STUDIO BUT SUITABLE FOR LARGE HALLS OR CLUBS

- ★ Four-position tone compensation and Input Selector switch.
- ★ Will amplify direct from Tape Heads.
- ★ Stereo/Mono switch so that peak monaural output of 28 watts can be obtained.
- ★ Separate Bass "Lift" and "Cut" and treble "Lift" and "Cut" controls.
- ★ Neon panel indicator.
- ★ Handsome Perspex Frontplate.

Based on a Mullard design and employing valves ECC83, ECC83. ECL86. ECL86. ECL86. ECL86, EZ81. Send S.A.E. for leaflet.

Output transformers are high-quality sectionally wound to required specification. Output matchings for 3 and 15 ohm speakers on each channel. Carr. 12/6. Complete set of parts with point-to-point wiring diagrams and instructions, or Factory assembled, tested and supplied with our usual 12 months guarantee for **13 Gns.** or DEPOSIT 5/7- and 9 monthly payments of 89/10 (total £20.15.6). **18 Gns.** A protective wooden cabinet covered in 3 pleasing shades of leathercloth and fitted carrying handles and feet can be supplied for 59/6 extra. Carr. 5/6. Terms DEPOSIT 6/6 and nine monthly payments 6/6 (Total 67/6).

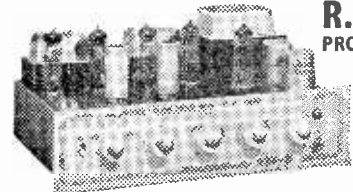


FREQUENCY RESPONSE ± 2 dB. 30-20,000 c.p.s.
HUM LEVEL 65dB down.
SENSITIVITY: 3 millivolts maximum.
HARMONIC DISTORTION (each channel) 0.2%.

AUDIOTRINE HI-FI TAPE RECORDER KIT 25 1/2 Carr. 18/6 Gns.

REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR. Incorporating the latest Magnavox Tape Deck. The Audiotrine High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet of latest styling and finished dark grey leathercloth. Size 14 1/2 x 17 x 8 1/2 in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £50-£60 class. S.A.E. for leaflets. TERMS: Deposit 4 gns. and 12 monthly payments of 42/- (Total 28 Gns.) 4 Track Model 3 Gns. extra.

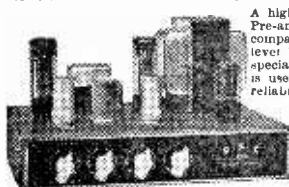R.S.C. A10 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER



A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 dB down. Frequency response ± 3 dB 30-20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used 6F86 6F6, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, BASS, LEAD OR RHYTHM GUITAR, STRING BASS, etc. For standard or long-playing records, OUTPUT SOCKET PROVIDES L.T. and H.T. for use with 807 output valves. Two separate inputs are provided. Six valves are used 6F86 6F6, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, BASS, LEAD OR RHYTHM GUITAR, STRING BASS, etc. For standard or long-playing records, OUTPUT SOCKET PROVIDES L.T. and H.T. for use with 807 output valves. Two separate inputs are provided. Six valves are used 6F86 6F6, ECC83, 807, 807, GZ34.

RADIO FEEDER UNIT. An extra input with associated volt. and H.T. for use with Gram and "Mike" can be mixed, 200-250v. 50 c/s. A.C. Mains output for 3 and 15 ohm speaker. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and 100 instructions. Supplied factory built with EL24 output valves and 12 months' guarantee, for 14 Gns. If required perforated cover with carrying handles can be supplied for 1 Gns. Send S.A.E. for leaflet also speaker. Terms: DEPOSIT 45/- and 6 monthly payments of 32/4 (Total: 16 Gns.) **11 Gns.**

INTEREST CHARGES REFUNDED


on H.P. and CREDIT SALE Accounts settled in 6 months.

LINEAR TAPE PRE-AMPLIFIER. Type LP/1. Switched Equalisation. Positions for Recording at 1in., 3in., 7in. per sec. and Playback, EM8 Recording Level Indicator. Designed primarily as the link between a Collaro Tape Deck and Hi-Fi amplifier, suitable almost any Tape Deck. S.A.E. for leaflet. **9 1/2 Gns.**

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram., as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, EZ81. High quality sectionally wound output transformer specially designed for Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response ± 3 dB 30-20,000 c/s. Six negative feedback loops. Hum level 65 dB down. ONLY 23 millivolts input required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for STANDARD or LONG PLAYING RECORDS. FOR MUSICAL INSTRUMENTS such as STRING BASS, LEAD or RHYTHM GUITARS, etc. OUTPUT SOCKET with plug provides 300v. 30mA. and 6.3v. 1.5A. for supply of a RADIO FEEDER UNIT. Size approx. 12 x 9 x 7 in. For A.C. mains 200-250v. 50 c.p.s. Output for 3 and 15 ohm speaker. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only **8 Gns.** Carr. 10/- (Or factory built 51/6 extra).

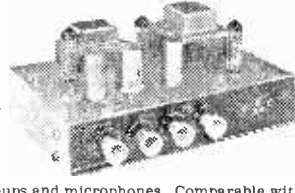

If required, louvered metal covers with 2 carrying handles can be supplied for 2/6. TERMS ON ASSEMBLED UNITS: DEPOSIT 33/3 and 9 monthly payments of 2/1 (Total £12.10.0). Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Mikes, etc.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER




A complete set of parts for the construction of a stereo-phonograph amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation for "lift" and "cut". Provision is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, EZ81. Outputs for 2-3 ohm speakers. Point-to-point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. **8 Gns.** Full constructional details and price list 2/6. Carr. 10/-

Or supplied factory assembled with 12 months' guarantee for £11.7.6. Carr. 10/- Terms: Deposit 2 gns. and 9 monthly payments of 24/2 (Total £12.19.6).

Always in Stock at keen prices SINGLE and AUTO RECORD PLAYING UNITS, PICK-UPS, CARTRIDGES, MICROPHONES, CABINETS VALVES and COMPONENTS TOO NUMEROUS TO LIST

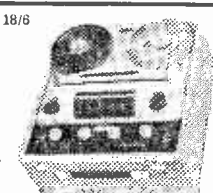ONLY 4 PAIRS OF SOLIDIFIED JOINTS PLUS MAINS



12in. 10 W. HIGH QUALITY LOUDSPEAKERS in walnut veneered cabinet. Gauss 12,000 lines. Spec. extra. 3 ohms or 15 ohms. Only **£4.19.6** Terms: Deposit 15/- and 6 monthly payments of 10/10 (Total £5.12.6). 12in. 20 Watt Hi-Fi Loudspeakers in Cabinets, 15 ohm. Size 18 x 19 x 10in. Finish as above. **£7.19.6** Terms: Deposit 24/6 and monthly payments of 17/- (Total £8.17.6). Carr. 3/6. 12in. 30 Watt Model, 15 ohms. **10 Gns.** Cabinet finish as above. Carr. 10/- or Deposit 32/- and 9 monthly payments, 25/-, Total £11.10.0.

W.R. "STENORIAN" HIGH FIDELITY P.M. SPEAKERS HP102, 10 watts rating. Where a really good quality speaker at a low price is required we highly recommend this unit with an amazing performance. Please state whether 3 or 15 ohms required. **£4.19.9**

R.S.C. JUNIOR BASS REFLEX CABINET. Designed for above speaker, but suitable for any good quality 8in. or 10in. speaker. Acoustically lined and ported. Polished Walnut veneer finish. Size 18 x 12 x 10in. Strongly made. Handsome app. **£4.7.6** carriage. Superb reproduction. Carr. 5/6.

R.S.C. STANDARD BASS REFLEX CABINET. For 12in. loudspeaker acoustically lined and ported. Size 20 x 14 x 13in. Beautifully finished. Recommended for use with Audiotrine Speaker System. Carr. 7/6. **£5.19.6**

AUDIOTRINE CORNER CONSOLE CABINETS Strongly made. Beautifully polished walnut veneered finish. Pleasant design. JUNIOR MODEL. For up to 8in. speaker. Approx. 20 x 11 x 4in. Carr. 5/6. **49/9**

STANDARD MODEL. To take up to 10in. speaker. Size 27 x 14 x 12in. Carr. 7/6. **5 Gns.** SENIOR MODEL. To take up to 12in. speaker and with Tweeter cut-out. Size approx. 30 x 30 x 15in. (Recommended for use with Audiotrine speaker system). Carr. 8/6. Terms available. **8 Gns.**


AUDIOTRINE HI-FI SPEAKER SYSTEMS Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating. **£4.19.9** 5/6

Or Senior 20 watt. £c.19.6. Carr. 7/6.



R.S.C. BASS-REGENT 50 WATT AMPLIFIER

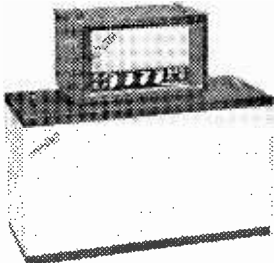AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT
For lead, rhythm, bass guitar and all other musical instruments
For vocalists, gram, radio, tape and general public address



- ★ UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 15in. 30 watt unit PLUS a FANE 12in. 20 watt unit with extended frequency response.
 - 4 Jack Socket Inputs and two independent Volume Controls (for simultaneous use of up to 4 pick-ups or 'mikes').
 - ★ Separate cabinets fully covered in contrasting tones of Rexine/Vynair with gold trimming for speakers and amplifiers.
 - ★ Separate Bass and Treble Controls giving 'Boost' and 'Cut'.
- Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at more than three times the cost.


49 Gns. Or deposit **£7.16.0** and 12 monthly payments of **48/-** (Total **£21 Gns.**)

TRANSISTORISED SOUND MIXER

Enables mixing of up to 4 standard jack inputs, i.e. mike, tape, gram, tuner, etc. into single output. Compact and completely self-contained. Uses standard 9 volt battery **49/9**

R.S.C. G15 15 WATT AMPLIFIERS for Lead or Rhythm Guitar, Mike, Gram or Radio

High-fidelity push-pull output. Separate bass and treble 'Cut' and 'Boost' controls. Twin separately controlled inputs so that two instruments or 'mike' and pick-ups can be used at the same time. Loudspeaker is a heavy duty flux 12in. 20 watt model with cast chassis. Cabinet is covered in contrasting shades of Rexine/Vynair. Size approx. 18 x 18 x 8in. **19 Gns.** Carr. 12/6. Only **12/9** or DEPOSIT **3 Gns.** and 12 monthly payments of **32/6** (Total **£22.13.0**). S.A.E. for leaflet.

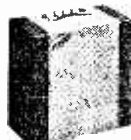

Full Range of FANE and GOODMANS Speakers in Stock and all types 'Mikes'. Credit terms if required.

R.S.C. B20 MULTI-PURPOSE AMP. especially suitable for Bass Guitar

A highly efficient unit incorporating massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give amp. 'Boost' and 'Cut'. Two jack socket inputs separately controlled. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 18in. Send S.A.E. **29 1/2 Gns.** Carr. 17/6. Or deposit **£4.14.0** and 12 monthly payments of **48/-** (Total **£21 Gns.**)

R.S.C. G5 AMPLIFIER

4 watt high quality output. Incorporating high flux 12in. 10 watt loudspeaker. Sensitivity 40 mV. High impedance jack input. Handsome cabinet (size 14 x 14 x 7in. approx.) finished in Rexine/Vynair. **£9.19.6** Or deposit **30/9** and 9 monthly payments of **22/3** (Total **11 Gns.**) Carr. 7/6

R.S.C. BATTERY CHARGING EQUIPMENT

Guaranteed 12 months



All for A.C. Mains 200-250v., 50cs
Assembled **4 amp 6/12v.** Fitted Ammeter meter and variable charge rate selector. Also selector for 6v. or 12v. charging. Louvred steel case with stoved grey hammer finish. Fused and ready for use with mains and output leads and clips. **59/9** Or deposit **12/-** and 6 monthly payments **12/-** Total **£3.12.0**. Carr. 1/6

BATTERY CHARGER KITS

Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses. Fuse-holders. Grommets, panels. Heavy Duty Clips, circuit. Carr. 3/6
6v. or 12v. 1 amp. **22/9**
As above with ammeter **28/9**
6v. or 12v. 2 amps. **25/9**
6v. or 12v. 2 amps. **25/9**
Inclusive of ammeter. **35/9**
6v. or 12v. 4 amp with Ammeter and variable charge rate selector. **52/6**
Less meter.

CHARGER AMMETERS

0-15a., 0-2a., 0-7a., 8/9 each.

R.S.C. 4 WATT GRAM AMPLIFIER KIT

Complete set of parts to build a good quality compact unit suitable for use with any record playing unit. Mains isolated chassis separate Bass and Treble controls. Output for 2-3 ohm speaker. For 200-250v. A.C. **59/9**

R.S.C. BABY ALARM or INTERCOMM KIT

Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250v. A.C. mains. Fully isolated. Controllable at both units. An intercomm. of this class would normally cost £20-£30. Only **58/6** carr. 5/- Ready for use. **6 Gns.**

R.S.C. BATTERY TO MAINS CONVERTER UNITS

BMI. An all-dry battery eliminator. Size 5 1/2 x 4 1/2in. approx. Completely replaces batteries supply 1.4v and 90v where A.C. mains 200-250v. 50 cfs is available. Suitable for all battery portable receivers requiring 1.4v. and 90v. Complete kit with diagram **39/9** or ready for use **46/9**

EX GOVT. SELENIUM RECTIFIERS 12v 15 AMP (BRIDGE) F.W. ONLY

19/9

INTEREST CHARGES REFUNDED ON H.P. ACCOUNTS SETTLED IN 6 MONTHS



Addresses Page 829

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address. Normally supplied for 15 ohm matching but can be supplied for 100v. line for 35/- extra.
Type C58. 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. 42 x 10 x 5in. **12 1/2 Gns.** Carr. Or deposit **10/-** and 9 monthly payments of **27/6** (Total **£14.9.0**)
Type C42. 40 watts. Fitted four 12in. 12,000 line 10 watt speakers. Overall size 56 x 14 x 9in. approx. **19 Gns.** Carr. 15/- Or deposit of **3 Gns.** and 9 monthly payments of **43/2** (Total **21 Gns.**)

30 WATT HI-FI AMPLIFIER FOR LEAD, RHYTHM BASS GUITAR and for VOCAL or INSTRUMENTAL GROUPS



A Four Input, two volume control Hi-Fi unit with separate Bass and Treble 'Cut' and 'Boost' controls. Designed for vocal or instrumental groups. For Bass, Lead or Rhythm Guitar. Mullard or Brimar latest type valves. Housed in strong Rexine covered cabinet with twin carrying handles. Attractive black and gold perspex fascia plate. For 200-250v. A.C. mains. Output for 3 or 15 ohm speakers. Carr. Send S.A.E. for leaflet. **17 Gns.** Or deposit **£3** and 9 monthly payments of **37/-** (Total **£19.13.0**)

HEAVY DUTY CHARGER KIT

6/12v. 6 amps., variable output Consisting of Mains Transformer 0-200-250v.; F.W. (Bridge) Selenium Rectifier; Ammeter, Variable Charge Rate Selector Panels, Plugs, Fuses, Fuseholder and circuit. Carr. 5/6 **59/9**

SELENIUM RECTIFIERS F.W. (BRIDGED)

6/12v. 1a. 3/11; 6/12v. 3a. 9/9; 6/12v. 6a. 15/3; 6/12v. 2a. 6/11; 6/12v. 4a. 12/3; 6/12v. 10a. 26/9; 6/12v. 15a. 35/9.

COMPLETE POWER PACK KIT

Consisting of Mains Trans., Metal Rectifier, Double electrolytic smoothing choke, chassis and circuit. For 200/250 v. A.C. mains. Output 250 v., 60 mA. 6.3 v., 2a. **19/11**

COMMUNICATION RECEIVERS RX 60 DE LUXE 4 BAND

220/240v. 50/60 C.P.S. A.C. mains operation. Frequencies covered 1600 Kc/s to 30 Mc/s continuous. Incorporates 5in. speaker. Slide rule tuning dial 'S' meter. Internal ferrite aerial 58in. 10 section for short waves. Fitted sockets for optional outdoor aerial. Headphones, external speaker socket. Other features are electrical bandspread tuning, Noise limiter, A.V.C., B.F.O., stand by switch. Size approx. 12 1/2 x 5 1/2 x 8 1/2in. Handsome crackle finished metal cabinet. Brand new with full instructions manual. Usual guarantee. Carr. 10/-. **19 Gns.** Or deposit **£5** and 9 monthly payments **37/8** (Total **£21.19.0**).

15in. 40 WATT EXTRA HEAVY DUTY LOUDSPEAKERS

Famous make. Normal price approx. £219. **11 Gns.** Very limited number to clear with full guarantee. Carr. 15/-

LINEAR TREMOLO PRE-AMP UNIT

Suitable for use with any of our Amplifiers. Controls are Speed (frequency of interruptions). Depth (for heavy or light effect). Volume and Switch. **4 Gns.**

FANNOY RE-ENTRANT LOUD-SPEAKERS

For outdoor or Factory use. 8 ohms, 8 watts. Plus 4/6 carriage **27/6**

HI-FI 12 WATT AMPLIFIERS

BRAND NEW Carr. 7/6 **£7.19.9**
EX-GUITAR AMPLIFIERS
Manufacturers discontinued. Model. Push-pull output. Latest high efficiency valves. Dual separately controlled inputs for 'Mike' and gram. Separate Bass and Treble Controls. High Sensitivity. Output for 3 or 15 ohms speaker. Guaranteed tested and in perfect working order.

JASON FMT1 V.H.F./F.M. Radio Tuner










design. Total cost of parts including valves, tuning **£6.19.6**

SUPERHET FEEDER UNIT

Design of a high quality Radio Tune; (specially suitable for use with our Amplifiers). Delayed A.V.C. Controls are Tuning, W.Ch. and Vol. Only 250v. 15mA H.T. and L.T. of 6.3v. lamp required from amplifier. Size approx. 6 x 6 x 7in. high. Simple alignment procedure. Point-to-point wiring diagrams, instructions and priced parts list with illustrations, 2/6. Total building costs **£5.5.0**. S.A.E. for leaflet.

TRANSISTOR SALE

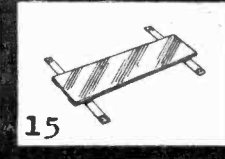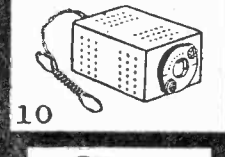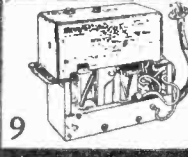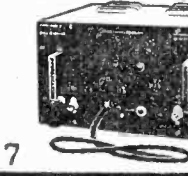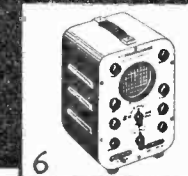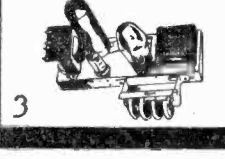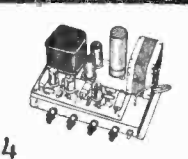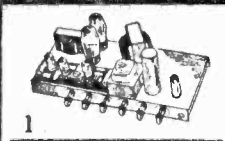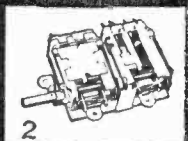Mullard OC71 2/11 OC45 3/11. OC44 C/11. OC72 2/11. OC81 2/11. OC171 8/9. AF117 6/9. Ediswan XA101 3/9. XA112 3/9. XC101A 3/9. Postage 6d. for up to 3 transistors.



1. **6 VALVE 15 WATT PUSH-PULL AMPLIFIER** 15 x 7 x 1 1/4 in. A.C. Mains 200-250 volts. 4 inputs with controls for same and bass and treble lift controls. Tapped for 3 and 15 ohm speakers. Extra H.T. and L.T. for F.M. Tuner supplies etc., built and tested. 7 gns. P. & P 15/6.
2. **CYLDON AM FM PERMEABILITY TUNERS FOR ALL TRANSISTOR OPERATION.** Size 2 1/2 x 2 1/2 in. approx. By famous manufacturer. A.M. I.F. 470 kc/s. F.M.-I.F. 10.7 Mc/s. A.M. coverage from 1620 Kc/s-325 Kc/s. F.M. coverage 108 Mc/s-88Mc/s. Circuit diagrams 2/6. FREE with Tuner, 1st 2nd and 3rd A.M. I.F.'s, 1st, 2nd, 3rd and 4th F.M. I.F.'s. V.H.F. Osc. choke. A.M. I.F. trap. All the above are the B.F. end of an A.M./F.M. receiver car radio etc. The above items £2.10.0.
3. **AMPLIFIER KIT, 3 to 4 watt Amplifier Kit.** Comprising chassis 8 1/2 x 2 1/2 x 1 in. Doubt's wound mains transformer output transformer volume and tone controls, resistors, condensers etc. Valves 6V8, ECC81 and metal rectifier. Circuit 1/6. free with kit. 29/6 plus 4/6 P.&P.
4. **8-WATT 5-VALVE PUSH-PULL AMPLIFIER & METAL RECTIFIER** Size: 9 x 6 x 1 1/2 in. A.C. Mains, 200-250v. 5 valves. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Output 8 watts at 5 per cent total distortion. Separate bass and treble lift control. Two inputs, with controls for gram. and mike. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested. 23.10.6. P. & P. 8/-.
5. **40W FLUORESCENT LIGHT KIT** incorporating GEC Choke size 8 1/2 x 1 1/2 x 1 1/4 in. 2 bi-pin holders, starter and starter holder, 11/8. P. & P. 4/6. Similar to above: **80W Fluorescent Light Kit** incorporating GEC choke size 11 1/2 x 1 1/2 in. 2 bi-pin holders, starter and starter holder, 17/6. P. & P. 5/6.
6. **OSCILLOSCOPE** for D.C. and A.C. APPLICATIONS. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Wave form available for external use; pulse output available for checking TV line O/P Transformers, etc. Provision for external—P and C.R.P. Brightness Modulation. A.C. mains 200-250v. £18.18.0. P. & P. 10/- **FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE.**
7. **FIXED FREQUENCY SIGNAL GENERATOR.** Crystal controls in metal case, size 10 x 6 x 8 in. Incorporating two FC13 valves, mains transformer, metal rectifier, choke inductor, lamp crystal and numerous components. Modulated and unmodulated output socket. Originally used for I.T.V. frequencies. Brand new. 39/6 plus 7/- P. & P. A.C. mains 200-250 volts. P.I.V., 760mA. Six for 7/6 post paid.
8. **POCKET MULTI-METER.** Size 3 1/2 x 2 1/4 x 1 1/4 in. Meter size 2 1/2 x 1 1/4 in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1,000. D.C. current 0-150mA. Resistance 0-100k Ohm. Complete with test prods, battery and full instructions. 42/6 P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering iron value 15/- to every purchaser of the Pocket Multi-Meter.
9. **CHANNEL TUNER I.F. 18-19 Mc/s.** Continuously tunable from 174-218 Mc/s. Valves required—PCF80 and PC84 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxis etc. Brand new by famous maker. 10/- P. & P. 3/-.
10. **POWER SUPPLY KIT** in metal case size 3 1/2 x 2 1/4 x 2 in. incorporating mains transformer, rectifier and condensers. 230/250 A.C. mains Output; 5v. 10mA. 10/6 plus 3/- P. & P.
11. **B.S.R. MONARCH UA16 WITH FULL FI HEAD,** 4-speed, plays 10 records, 12 in., 10 in., or 7 in. at 16, 33, 45 or 78 r.p.m. Internixizes 7 in., 10 in. and 12 in. records of the same speed. Has manual flip position; colour brown. Dimensions: 12 1/2 x 11 in. Space required above baseboard 4 1/2 in., below baseboard 2 1/4 in. Fitted with full FI turnover crystal head. 24.19.6. P. & P. 7/6.
12. **FIRST QUALITY PVC TAPE**

5 1/2 in. Std. 850ft. 9/-	5 in. L.P. 850ft. 10/6
7 in. Std. 1200ft. 11/6	3 in. T.P. 600ft. 10/6
3 in. L.P. 240ft. 4/-	5 in. T.P. 1800ft. 25/6
5 1/2 in. L.P. 1200ft. 11/6	3 1/2 in. T.P. 2400ft. 32/6
7 in. L.P. 1800ft. 15/6	7 in. T.P. 3600ft. 42/6


P. & P. on each 1/6. 4 or more Post Free.
13. **MAYFAIR 6-TRANSISTOR TAPE RECORDER** Captain-driven. battery operated, 7 1/2 and 3 1/2 l.p.s. Precision made. Push-button controls. High quality 2 1/2 in. speaker. Push-pull circuit. Output: 400 mw. Frequency response: 200-7,000 kc/s. Fast rewind. Up to 1 hour twin track playing time. Automatic erasing for re-recording. Dimensions: 8 in. x 11 in. x 3 in. Weighs only 7lbs. £11.11.0 plus 7/6 P. & P.
14. **BSR TAPE DECK** AC 200/250v, tape speed 3 1/2 twin track. 25.5.0 P. & P. 7/6.
15. **GEC FLAT HEATER ELEMENT 500 w.** Can be used for wash boilers, washing machines etc. Five or six elements can be used in parallel to give 2500/3000 watts. Size 8 1/2 x 1 1/2 copper enclosed. 2/6 each, P. & P. 1/- 4 or more Post Paid.

RADIO & TV COMPONENTS (ACTON) LTD.
 21b High Street, Acton, London, W.3.
 All enquiries Stamped Addressed Envelope.
 Goods not despatched outside U.K.
 Shop hours 9 a.m.—6 p.m. Early closing Wednesday



**COMBINED PORTABLE
and CAR RADIO**

The Radio with the STAR features

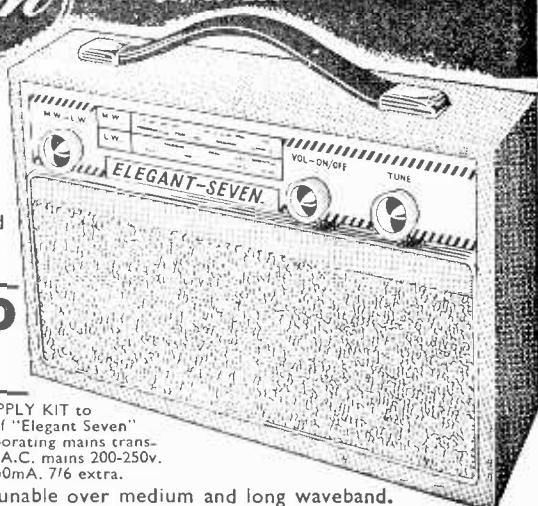

- ★ 4in. Speaker
- ★ 7-transistor superhet. Output 350mW.
- ★ Wooden cabinet, fitted handle with silver coloured fittings. Size 12½ x 8½ x 3½ in.
- ★ Horizontal tuning scale, size 1¼ x 2½ in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial
- ★ I.F. neutralisation on each stage 460 kc/s.
- ★ D.C. coupled output stage with separate A.C. negative feedback.
- ★ All components: ferrite rod and tuning assembly mounted on printed board.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.

ONLY £4.4.0

Plus 6/6 P. & P. Parts list & circuit diagram 2/6. FREE with parts.

POWER SUPPLY KIT to purchasers of "Elegant Seven" parts, incorporating mains transformer, etc. A.C. mains 200-250V. Output 9v. 50mA. 7/6 extra.

- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket. Full after-sale service.

All enquiries Stamped Addressed Envelope.

RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London W3

Open 9 a.m.—6 p.m. including Sats. Early closing Wed.

Goods not despatched outside U.K.

Terms C.W.O.

SURBITON PARK RADIO

MARTIN AUDIOKITS & RECORDAKITS

- F.M. TUNER UNITS Nos. 15, 16 and 17 (H.P. Price £12.17.6)
 Or Dep. 51/6 and 12 m. pymts. of 18/10 (H.P. Price £12.17.6)
TRANSISTORISED AMPLIFIER with 5 position input selector, pre-amp and controls, 10 watt amplifier and Power Pack For 3 Ohm Speaker. Cash £14.5.0
 Or Dep. 571- and 12 m. pymts. 20/10 (H.P. Price £15.7.0)
 For 15 Ohm Speaker. Cash £15.5.0
 Or Dep. 621- and 12 m. pymts. 22/6 (H.P. Price £16.12.0)
ALL above include Front Panels, Knobs and Instructions.
TWO TRACK RECORDAKIT AMP. (Valve) FOR STUDIO DECK, 6 valves, controls, self powered Cash £11.11.0
 Or Dep. 47/- and 8 m. pymts. 25/6 (H.P. Price £12.11.0)
COLLARON STUDIO DECK 3-speed latest Two Track Cash £10.19.6
 Or Dep. 44/- and 8 m. pymts. 24/6 (H.P. Price £12.0.0)
COMPLETE KIT with case, spkr., tape and mic. Cash £29.19.6
 Or Dep. 120/- and 12 m. pymts. 44/- (H.P. Price £32.8.0)
FOUR TRACK AMP. as above Cash £12.12.0
 Or Dep. 52/- and 6 m. pymts. 27/6 (H.P. Price £13.12.0)
FOUR TRACK COLLARON DECK Marriott "X" Series heads. Cash £13.19.6
 Or Dep. 56/- and 12 m. pymts. 20/6 (H.P. Price £13.2.0)
COMPLETE KIT with case, spkr., tape and mic. Four Track Cash £33.19.6
 Or Dep. 136/- and 12 m. pymts. 49/10 (H.P. Price £36.14.0)
TAPE PRE-AMP for Studio Deck, self powered. Two Track Cash £8.8.0
 Or Dep. 34/- and 6 m. pymts. 25/8 (H.P. Price £9.3.0)
 Four Track Cash £9.9.0
 Or Dep. 39/- and 6 m. pymts. 28/4 (H.P. Price £10.9.0)
We are leading stockists for all Martin Constructional Kits.

AMPLIFIERS-TUNERS Selection

- ARMSTRONG 221 10-10 watts Stereo, Mag PU and Filter** Cash £33.15.0
 Or Dep. 135/- and 8 m. pymts. 49/6 (H.P. Price £36.9.0)
ARMSTRONG 224 10-10 watts Stereo Amplifier Cash £27.10.0
 Or Dep. 110/- and 12 m. pymts. 40/4 (H.P. Price £29.14.0)
ARMSTRONG 224 F.M. Tuner Powered. Cash £22.10.0
 Or Dep. 90/- and 12 m. pymts. 33/- (H.P. Price £24.6.0)
ARMSTRONG 223 AM/FM TUNER Powered. Cash £28.15.0
 Or Dep. 115/- and 12 m. pymts. 42/2 (H.P. Price £31.1.0)

SURBITON PARK RADIO LTD.

- ARMSTRONG 127 MONO 5W** with AM/FM Cash £26.10.0
 Or Dep. 100/- and 12 m. pymts. 38/10 (H.P. Price £28.12.0)
ARMSTRONG 127 STEREO as above Stereo amp. Cash £37.10.0
 Or Dep. 150/- and 12 m. pymts. 55/- (H.P. Price £40.10.0)
ARMSTRONG 227 MONO 10W amp. with AM/FM Cash £30.15.0
 Or Dep. 147/- and 12 m. pymts. 53/10 (H.P. Price £33.13.0)
ARMSTRONG 227 STEREO as above with Stereo Amp. Cash £52.15.0
 Or Dep. 211/- and 12 m. pymts. 77/4 (H.P. Price £56.19.0)
ARMSTRONG 226 STEREO as above, but Mag. P.U. Filter. Cash £61.0.0
 Or Dep. 260/- and 12 m. pymts. 88/- (H.P. Price £65.16.0)
Teak Cases for all Armstrong Units. Cash £23.10.0
ROGERS CADET MK. 3 10-10 watt Stereo Amp, Mag. P.U. Cash £20.10.0
 Or Dep. 118/- and 12 m. pymts. 43/3 (H.P. Price £21.17.0)
CASE MODEL, ROGERS CADET MK. 3 £3.0.0 - extra
LEAK STEREO 20 TRANSISTOR AMPLIFIER. Cash £40.10.0
 Or Dep. 198/- and 12 m. pymts. 72/5 (H.P. Price £53.9.1)

LOUDSPEAKERS Selection

- FANE 123/10 Heavy Duty 12in.** 20 watt. Cash £5.5.0
WHARFEDALE SUPER 8/RS/DD Cash £7.0.0
WHARFEDALE SUPER 10/RS/DD Cash £13.4.0
 Or Dep. 47/6 and 8 m. pymts. 25/9 (H.P. Price £12.13.6)
GOODMAN'S MAXIAL Cash £17.10.6
 Or Dep. 70/6 and 12 m. pymts. 25/8 (H.P. Price £18.18.9)


MOTORS-PICK-UPS Selection

- GARRARD SRP10 Mono** Cash £5.10.0
GARRARD Model 1000 Mono Cash £15.10.0
GARRARD Model 2000 Mono Large Table Cash £25.10.0
 Or Dep. 34/- and 6 m. pymts. 26/- (H.P. Price £30.10.0)
GARRARD Model 3000 Stereo Lightweight arm Cash £11.11.0
 Or Dep. 47/- and 8 m. pymts. 25/6 (H.P. Price £12.11.0)
GARRARD S.P.25 Less cart. Single player. Cash £12.10.0
 Or Dep. 50/- and 6 m. pymts. 27/6 (H.P. Price £13.10.0)
GARRARD A70 8-S cart. Heavy table Cash £13.0.0
 Or Dep. 52/- and 12 m. pymts. 19/- (H.P. Price £14.0.0)
GARRARD LAB80 Push button oper. less cart. Cash £27.10.0
 Or Dep. 110/- and 12 m. pymts. 40/4 (H.P. Price £29.14.0)
GARRARD 401 Transcription Table. No arm Cash £32.10.0
 Or Dep. 130/- and 12 m. pymts. 47/8 (H.P. Price £35.2.0)
GOLDRING G66 Mono Single Player Cash £11.11.0
 Or Dep. 47/- and 8 m. pymts. 25/6 (H.P. Price £12.11.0)
GOLDRING G158 less cart. Heavy table, single play Cash £11.1.0
 Or Dep. 69/- and 12 m. pymts. 24/11 (H.P. Price £18.8.0)
GOLDRING G170 trans. Unit with arm, less cart. Cash £29.18.8
 Or Dep. 120/6 and 12 m. pymts. 43/9 (H.P. Price £32.5.8)
 Leaflets available upon receipt of 6d. stamp

48-50 Surbiton Road, Kingston-on-Thames, Surrey
 Phone KIN. 5549:: Hours 9 a.m. to 6 p.m. daily (1 p.m. Weds.)

STERN-CLYNE

HIGH FIDELITY EQUIPMENT

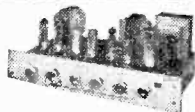

(1) **Mullard "10 Plus 10" Stereo Amplifier**
A High Fidelity design providing up to 10 watts (per channel).
KIT OF PARTS £20.0.0.
Built and tested £24.0.0 (C. & I. 7/6).
You can also see the Main Amplifier in operation with our Dual Channel Pre-amplifier.
KIT OF PARTS £27.0.0.
Built and tested £34.0.0 (C. & I. 10/6).



(2) **Mullard Dual Channel Pre-Amplifier**
A four-valve design for both Stereo-phonics and Monophonic operation.
KIT OF PARTS £12.10.0.
Built and tested £15.0.0 (C. & I. 5/4).



(3) **The "Twin Three" Stereo Amplifier**
Based on a recent design by Mullard Ltd. it is ideally suited for use in Portable Record Players.
Built and tested £9.0.0 (C. & I. 7/6).
To construct a Stereo Portable Record Player, we offer:
Assembled Amplifier with two 3 x 5in. Loudspeakers and Portable Case for £16.10.0 (C. & I. 10/4).

Fully descriptive leaflets available on any of the above items.

Instruction Books and Detailed Price Lists are supplied Free with Kits of Parts but may be purchased separately if required.

Items 1, 2 and 14, 3/- each;
6 and 13, 3/6 each; 7, 8, 9,
10, 2/- each; 11, 2/6 each;
12, 5/-. All Post Free.



(7) **MULLARD 2-VALVE PRE-AMPLIFIER**
Employing two EF86 valves and designed to operate with the Mullard MAIN AMPLIFIERS but also perfectly suitable for other makes. Now with new design front panel.
KIT OF PARTS £6.0.0.
Built and tested £9.10.0 (C. & I. 8/4).




(5) **Tudor AM/FM Tuner**
Self-powered VHF/FM long and medium waves. FM 87.5-108.5 Mc/s. A.M. MW 527-1,830 Kc/s. LW 145-270 Kcs. Multiplex output.
Built and tested 24 Gns. (P. & P. 7/6).



(6) **Mullard 3-Valve Pre-Amplifier Tone Control**
Designed mainly for the Stern Mullard range of Monophonic Power Amplifiers.
KIT OF PARTS £10.0.0.
Built and tested £13.13.0 (C. & I. 5/-).




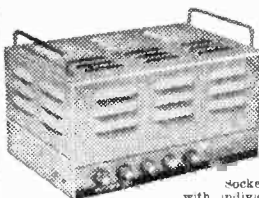(8) **Mullard "5-10" Main Amplifier**
For use with Mullard 2- or 3-valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained.
KIT OF PARTS £10.0.0.
Built and tested £13.10.0 (C. & I. 6/6).
Above incorporating Partridge Output Transformer £1.8.0 extra.




VERITONE 30 AMPLIFIER
A general purpose amplifier of outstanding quality ideally suitable for Dance Bands, Clubs, Hotels, Factories, Indoor and outdoor. Public address requiring a powerful robust portable Amplifier which will provide high quality reproduction, distortion free. The Amplifier has two standard Jack "socket" multi-high gain and low gain with individual volume controls and with the master volume control the inputs may be mixed and balanced as required. Housed in a really robust steel case finished in smooth grey harmonie finish with chrome handle and silver grey front panel with contrasting letters and knobs. Built in Pre-amplifier and Control Unit. 30 watt Undistorted Output. Switched Output for 3 or 15 ohm Loudspeakers. Fully assembled and tested. Carriage and insurance 10/-. Ventilated Cover with chrome handles as illustrated. 35/- extra.

Price 18 Gns.

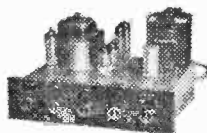

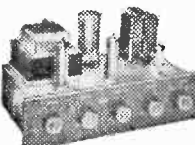(9) **Mullard "5-10RC"**
The popular "5-10" complete incorporating Passiv. Control Unit providing up to 10 watts high quality reproduction with an input of 600mV.
KIT OF PARTS £12.0.0.
Built and tested £16.0.0 (C. & I. 7/6).
With Partridge Output Transformer £1.8.0 extra.




(10) **Mullard "3-3RC"**
A high quality Amplifier developed from the very popular 3-watt Mullard "3-3" design.
KIT OF PARTS £8.8.0.
Built and tested £11.10.0 (C. & I. 8/6).



(11) **The "Mono-Gram"**
A small Amplifier of genuine high quality performance producing up to 3 watts undistorted output.
KIT OF PARTS £4.10.0.
Built and tested £6.0.0 (C. & I. 3/6).




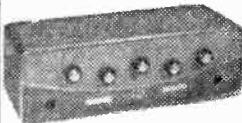(16) **JL10 Power Amplifier**
Incorporates the latest diode/pentode ECL86 valves in push-pull Partridge ultra linear output transformer. Partridge mains transformer and smoothing choke. 10 watts power output, surplus.
Built and tested £12.12.0 (C. & I. 7/6).



(17) **Double Feature Pre-Amplifier**
Inputs for microphone, crystal or magnetic pick-up, tuner unit, and 1 addition offers full facilities for tape recording and high fidelity replay. This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape deck.
Built and tested £13.15.0 (C. & I. 5/-).
Prices if both units purchased together:
Built and tested £26.3.0 (C. & I. 16/4).

VERITONE 30

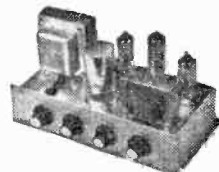

A small versatile 3-4 watts Gram Amplifier suitable for crystal Pick-up or Radio Tuner. Ideally suited for a small domestic installation. Output imp. 3 ohms, volume control, treble control, base control and middle control. Valve line-up: EL84, EF86, E280.

Chassis size 8 1/2 x 4 x 1 1/2in. Silver anodised finish. Attractive front panel silver grey finish with contrasting lettering and knobs. Size 8 1/2 x 2 1/2in. Fully assembled and tested 6 Gns. (C. & I. 5/-).



(12) **Stereo Tape Pre-Amplifier Model STP.1**
For use with current Truvox, Brantell or Collaro "Studio" 1 and 4-track Stereo Decks. Now with new design front panel.
KIT OF PARTS £22.0.0.
Built and tested £28.0.0 (C. & I. 8/6).



(13) **Mullard Type "C" Tape Pre-Amplifier**
Suitable for most 4-track Mono Tape Decks. Now with new design front panel.
KIT OF PARTS £14.0.0.
Built and tested £19.10.0 (C. & I. 7/6).



(14) **Mullard Type "A" Tape Pre-Amplifier Model HF/TR3**
Based on Mullard's type "A" design and suitable for most 4-track Mono Tape Decks. Now with new design front panel.
KIT OF PARTS £13.13.0.
Built and tested £19.0.0 (C. & I. 7/6).

Introducing the new veritone saturn transistorised FM Tuner



Veritone bring to you a new design in
F.M. Tuners unique in both circuitry and styling
—designed for the modern-minded enthusiast

THE VERITONE SATURN TRANSISTORISED F.M. TUNER

Specifications:

Transistors:—1 x AF125, 1 x AF121, 4 x AF116 . Diodes:—4 x OA79 . 1 Variable Capacity Diode . Solid State Full Wave Bridge Rectifier, 10AZ212 Zener Diode . 4 I.F. Stages . Switchable A.F.C. . Tuning Meter . Tuning Range 87.5-108.5 Mc/s . Stabilised Power Supply Din Outlet Socket . Fully Variable Audio Output Attenuator . Sensitivity 4 mV for 30 dB signal to noise ratio . Attractive Black and Silver Grey front panel with mirror strip top and bottom

Facility for Plug in Multiplex Stereo Adaptor (available at a later date)

PRICE 25 gns. (Inc. P.T.) TEAK CASE OPTIONAL EXTRA

Full technical information and details available on request

NOW ON DEMONSTRATION AT ALL BRANCHES

STERN-CLYNE

SEE FOLLOWING PAGE FOR ADDRESSES

STERN-CLYNE

ELECTRONIC CENTRES THROUGHOUT GREAT BRITAIN

TWO SPECIAL TAPE RECORDER BARGAINS



TR2 PORTABLE TAPE RECORDER. A truly first-class portable machine by famous manufacturer incorporating the renowned HBR single speed 2-track Tape Deck. 3 1/2 i.p.s. Tape Counter. Record Level Indicator. Volume and On/Off Tone Control. 3 watts output. Inputs for recording from Microphone and Radio. Tape Monitor Socket. Extension Loudspeaker Socket. Attractive two-tone grey/cream rexine covered Portable Cabinet. Supplied complete with Microphone, Reel of Tape and Spare Spool. Carriage and Insurance 15/- extra. Credit Terms Originally 28 Gns. £2,18.0 deposit and 1' monthly payments of £1,9.4 total credit price £20,10.0. **OUR PRICE 18 Gns.**

TR3 PORTABLE TAPE RECORDER. A high quality Portable Tape Recorder for the discerning enthusiast incorporating the latest BSR TD10 3-speed Tape Deck 11 3/3 and 7 1/2 i.p.s. 2-Track Record Interlock to prevent accidental erasure. Tape Counter. Record Level Indicator. 3-4 watt output. Volume and On/Off Tone Control. Inputs for recording from Microphone and Radio. Tape Monitor Socket. Extension Loudspeaker Socket. Attractive two-tone blue rexine covered Portable Cabinet with silver trimmings. Supplied complete with Microphone Lead for recording from Radio or Record Player. Full Reel of Tape and Spare Spool. Carriage and insurance 15/- extra. Credit Terms: Originally 28 Gns. £3,3.0 deposit and 12 monthly payments of £1,12.8. Total credit price £22,10.0. **OUR PRICE 20 Gns.**

FULLY AUTOMATIC TAPESPLICER

14/6. P. & P. 1/6.

PLASTIC TAPE SPOOLS

3in., 1/3; 4in., 2/-; 5in., 2/-; 6 1/2in., 2/3; 7in., 2/6.

PLASTIC SPOOL CONTAINERS. For spool sizes: 5in., 1/6; 3 1/2in., 2/-; 7in., 2/3. Any single item plus 3d. P. & P. Orders over £1 post free.

We carry fully comprehensive stocks of Tape Recorders, Decks and Accessories at all Branches or order with confidence by mail.

AMERICAN RECORDING TAPE

6in.	500ft. Std. Acetate	..	8/6
6in.	900ft. LP Acetate	..	10/-
6 1/2in.	1,200ft. LP Acetate	..	12/6
3 1/2in.	600ft. DP Polyester	..	11/6
5in.	1,200ft. Std Polyester	..	12/6
5in.	1,200ft. DP Polyester	..	15/-
7in.	1,500ft. LP Polyester	..	20/-
6 1/2in.	1,800ft. DP Polyester	..	22/6
7in.	2,400ft. DP Polyester	..	25/-
P. & P. 1/- per reel. 4 or more reels			
POST FREE.			

ETCH YOUR OWN PRINTED CIRCUITS

A complete kit of parts to make your own printed circuit board to your own specification, high quality materials used to ensure perfect results. Price complete with all necessary chemicals and copper clad laminated boards, 19/6. 2/3 packing and postage.



★ MEDIUM AND LONG WAVES. ★ 12 VOLT POSITIVE EARTH. ★ Push Button Wave Change. ★ SIZE 7 x 2 x 7in.

9 1/2 Gns.

P. & P. 5/-

Ready built complete with 7 x 4in. speaker fitted to baffle fixing brackets, all nuts and bolts and fitting instructions.

Optional Extras: Chromium plated weatherproof telescopic aerials. Type 1, 22in./50in., 19/6. Type 2, 12in./43in., 29/6. Type 3, fully retractable and locking 1in./50in. Depth below wing, 14in., 39/6. All plus P. & P. 2/6, if purchased separately.

LONDON

18 Tottenham Court Road, W.1. MUSEum 5929/0095. Half Day Saturday.
28 Tottenham Court Road, W.1. MUSEum 3461/2. Half Day Thursday.
308 Edgware Road, W.2. PADDington 6863. Half Day Thursday.
189 Fleet Street, E.C.4. FLEET Street 5813/5. Half Day Saturday.
162 Holloway Road, N.7. NORTH 7941. Half Day Thursday.
9 Cumberwell Church Street, S.E.6. RODney 2575. Half Day Thursday.
NOW ALSO OPEN AT:
220 Edgware Road W.2. PADDington 5607 (New-Max).

CROYDON

19 Suffolk House, George Street, MUNICIPAL 3250. Half Day Wednesday.

BRISTOL

26 Merchant Street, Bristol 1. BRISTOL 30061. Open 6 days a week.

ANOTHER NEW CENTRE

Now open at
EASTOWN HOUSE
LINCOLN ST.
NOTTINGHAM
Tel. 46889

LIVERPOOL

52 Lord Street. Royal 7400. Open 6 days a week

MANCHESTER

20/22 Withy Grove, Manchester 4. BLACKfriars 6379/5246
Open 6 days a week

SHEFFIELD

125 The Moor, Sheffield. Sheffield 29993. Half Day Thursday

MAIL ORDERS AND ENQUIRIES TO:

Dept. P.W. 3/5 Eden Grove, Holloway London, N.7
NO 8th 8161/6

DESPATCH-TODAY?-PHONE-R.C.S.!

DE-LUXE RECORD PLAYER KITS

Antiohance 2-tone Cabinets 17 x 15 x 8 1/2 in. High flux loudspeaker, 3 watt 16 ohm in. c.p.s. amplifier ready built. Quality output. Volume and Bass controls. All items fit together perfectly. Special instructions enable assembly in 30 minutes only 5 wires to join. 12 months guarantee.

AUTOCHANGE KITS. Absolutely complete.
E.S.R. Monarch £10.10 P.P. 7/6
Garrard "1000" £11.13.6 P.P. 7/6
Garrard AT70 £12.10.0 AT70 £14.5.0 P.P. 7/6
OR SEPARATELY
 Cabinet with board 14 x 13 in. £3.9.6 P.P. 5/6
 3 watt amplifier with speaker £3.12.6 P.P. 3/6
AUTOCHANGERS with LP778 xtal pick up
P.S.R. UA25 or UA14 Mono. £5.19.6 P.P. 3/6
Garrard "1000" Mono. £6.10.0 P.P. 3/6
Garrard AT70 £8.10.0 AT60 £10.10.0 P.P. 3/6
SINGLE PLAYERS with LP778 xtal pick up
E.S.R. Junior £2.7.6 E.S.R. GUT £4.17.6 P.P. 2/6
GARRARD TRANSITIONS EP26, £11. A70 £21. LAB80, £25; 401, £30. P.P. 5/6 each.



Q MAX CHASSIS CUTTER

Complete die punch Allen screw and key

1/4 in.	1/4 in.	1/8 in.	1/4 in.	22/6
1/2 in.	1/4 in.	1/8 in.	1/2 in.	34/3
1/2 in.	1/4 in.	1/8 in.	2 1/2 in.	37/9
1/2 in.	1/2 in.	2 in.	2 1/2 in.	44/3
1 in.	1 1/2 in.	2 1/2 in.	3 1/2 in.	44/3
1 in.	1 1/2 in.	2 1/2 in.	2 1/2 in. sq.	31/6

CRYSTAL MIKE INSERTS

1 1/2 in. dia. x 1 in., 6/6
 1 1/2 in. dia. x 1 in., 7/6
TAJAN M.C. Insert 1 1/2 in. dia. x 1 in. 8/6
TANNOY CARBON MIKE complete, 5/6

Coils Weatrite "P" 4 1/2-8smor "Q" from 4/6.

Reps. DRR2 L & M. with reaction, 4/6.
 Ferrite Aeriatric Valve, M. 3/6; M.L. 12/6.
 Ferrite Aericals, L & M. for transistor circuits. OSMOR. 10/-
WEYRAD, 12/6.
 Ferrite Rod 8 x 1/4 in., 6 x 1/4 in., 6 x 1/2 in., 3/- each.
H.F. Choke, 2/9.
Osamor OCT1, 6/9.
 Test Prods., 4/6 pp. Set Trim Tools, 3/-
Neon Mains Tester Screwdriver, 5/-
Multicope Solder, 6d. yd. Dispenser, 2/6.
VALVE HOLDERS, Int. Oct. 6d. Mazda Oct. 6d.
RTG BSA, B4G, B9A, 92d. RTG B9A Cans, 1/-
 Coroner I.O. RTG BGT B9A. 1/4. Valve plugs 3/3.

MOVING COIL MULTIMETER TK

2000 0-1000V, A.C./D.C. ohms. 0 to 1000. etc. 47/6.
MOVING COIL MULTIMETER E710K
 0-1000V A.C./D.C. ohms 0 to 3 meg. etc. 70/6.
MOVING COIL MULTIMETER E120K
 0-2300V, D.C. 0-1000V, A.C. 30,000 ohms per volt. J to 6 meg. 50 Microamps 99/6
MOVING COIL MULTIMETER EP200K
 0-1200 D.C. A.C. volts, 30,000 ohms/V. (D.C.)
 0-10 meg. 23 microamps. Full scale. Decibels
 0 to +2 dB.

L.F. TRANSFORMERS 7/6

465 K/S Six Turn Miniature Can, 3 x 1 in. dia. High Q and good band width. Data supplied.



1966 GRAM CHASSIS

Three Wavebands. Five Valves ECH91, Long. Med. Short. EF89, EB81, EL54, EZ80 12-months guarantee. A.C. 200/250V. Ferrite Aerial. 5 watts. 3 ohm. 13 1/2 x 7 in. high x 5 in. deep. Dial size 13 x 4 in. horizontal working. Aligned, calibrated. Chassis isolated from mains.

BRAND NEW £9.19/6 Carr. 5/6
 Matched speakers 10 x 6 in., 22/3; 3 x 6 in., 45/-

VHF-PM RADIOGRAM CHASSIS £10.10.0
 With Long and Med. Wavebands, 15 in. x 7 in. x 9 in.

NEW ELECTROLYTICS FAMOUS MAKES

TUBULAR	TUBULAR	CAN TYPES
1/350V 2/-	100/25V 2/-	8/800V 9/-
2/350V 2/8	250/25V 2/8	16/800V 12/-
5/350V 2/8	500/15V 2/6	16+16/500V 7/6
8/450V 2/8	2000/50V 11/8	32+32+32/350V6/6
16/450V 3/-	8+8/450V 3/6	32+32/450V 6/-
32/450V 3/6	8+16/450V 3/6	50/50350V 7/-
25/25V 1/8	16+16+16/4/3	64+120/350V 11/8
50/50V 2/-	32+32/350V 4/6	100+200/275V 12/-

PAPER TUBULARS

350V. 0.1 9d., 0.5 1/9; 1 mFd. 3/4; 1-2 mFd. 150V. 3/4-500V. 0.001 to 0.05 9d.; 0.1 1/-; 0.25 1/8; 0.5 2/6 1.000V. 0.001, 0.0022, 0.0033, 0.0047, 0.01, 0.022, 1/6; 0.047, 0.1, 2/-, 0.22, 0.47 3/-
 350V. 0.001, 0.002, 0.003, 0.004, 0.05, 0.1 1/8
 Sub-Mim. 0.001, 0.005, 0.01, 0.02, 0.04, 0.05, 0.1 1/8
 Sub-Mim. Electrolytic 1 2 4 5 8 16 25 30 50 100, 500. 1 000 mFd. 15V., 2/6. 1.000 mFd. 50V. 7/8

SILVER MICA (tolerance 1pP). 2.2 to 47pF. 1/8 ditto 1% 30 to 800 pF. 1/-; 1.000 to 2.000 pF. 1/8
CERAMIC 500 1pF to 0.01 mFd. 9d. each. **TWIN GANGS.** 0.1-200 pF. 176 pF. 30/6; "O" 365 pF. 2/6. AP15, 3/6. 2/6. 0.06. 11/8. Sub-Mim. 0.001. 3/6

TUNING AND REACTION. 100 pF. 300 pF. slow motion standard. 9/-; small 3-gang 500 pF. 9/9. **Single "O" 365 pF. 7/6 SHORT WAVE.** Single 10 pF 25 pF 50 pF. 75 pF. 100 pF. 150 pF. 5/6 each. Can be changed together. Contour 9d. each.

TRIMMERS ceramic 30. 50. 70 pF. 8d.; 100 pF. 150 pF. 1/3. 250 pF. 1/8; 500 pF. 750 pF. 1/8.

HEADPHONES. 2,000 ohms 12/6; 4,000 ohms 15/6
EL84 Transformer De Luxe. Push-Pull 30w. 90/-
EL84 (510) Ultra Linear Push-Pull. 10w. 49/6.
 10w. Multi-rano Push-Pull, 18/6. **EL84 (3-3) 25/-**
 Standard Pentode. 5/6. **EL180** o.p.t. 12w., 45/-

TRANSISTOR MAYNS

ELIMINATOR PPI-6V. PP9-9V. 29/6
DOUBLES 42/6. PPI + PPI PP9 + PP9, PPI1 (4+4) Size as batteries. Also min. 9v. 18/6.

WEYRAD P50 COILS

Ferrite aerial 12/6; Osc. P50 IAC. 5/6; 1st and 2nd I.F. P50/2CC. 5/7 each; 3rd I.F. P50/3CC. 6/-
Driver Trans-L.F.D.T4. 9/6.
 Printed Circuit 9/6; 35 ohm Speakers, 3in.; 17/6; 6x4in. 21/6; Book 2/-; 3 ohm OPT 10/6

NEW MULLARD TRANSISTORS

Holders 1/3; AC81 3/-; OC71 6/-; OC72 7/6; OC71 7/6; AF115 10/6; AF117 11/6; OC94 8/-; OC45 7/-; OC171 9/-; OC170 8/6; AF117 9/6; OC26 12/6; ORP12 12/6.
SILICON RECTIFIERS. OA210 500 mA. 200v., 5/6; BY100 550 mA. 400v., 10/-

MAINS TRANSFORMERS Postage 2/- each.

STANDARD 250-0-250, 80mA. 6.3v. 3.5a.	
tapped 4w. 4a. Rect. 100V. 50V.	
100V. 25V. 25V. 25V. 25V. 25V.	29/6
MINIATURE 200V. 200mA. 6.3V. 1a	10/6
MIDGET 220V. 45mA. 6.3V. 2a	15/6
SMALL 300-0-300 70mA. A. 6.3V. 4a	19/6
EAL. 250-0-250, 100mA. 5V. 2a. 6.3V. 1 1/2a	17/6
HEATER TRAP. 6.3V. 1a. 7/6; 4.3V. 4a. 10/6	
DATA, tapped 1.4, 2, 3, 4, 5 6.3V. 1a	8/6
GENERAL PURPOSE LOW VOLTAGE 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30V. 25/-	
1 amp. version. 14V. and 1.5 amp. up to 60 V. 29/6	
ALTO TRANSFORMERS. 250-110V. 40w. 18/6	
0-115, 200, 250, 240V. 150W. 25/-; 500W. 82/6	
MULLARD "510" Mains Transformer 33/6	
TRANSISTOR 9V. 50mA. 1 1/4 x 1 1/4 in. 7/6	

BEST BRITISH P.V.C. (Spare 2/6 ea.) RECORDING TAPES Spools

LP 5in. 900ft. 11/6 DP 5in. 1200ft. 18/6
 LP 5 1/2 in. 1200ft. 14/6 DP 5 1/2 in. 1800ft. 24/6
 LP 7in. 1800ft. 19/6 DP 7in. 2400ft. 29/6

Volume Controls 80 ohm COAX

Linear or Log Track. Semi-arc spaced 4in. and 5in. Midget 40 pfs. 17/6; 60 pfs. 25/-
 6d. yd. I.S. 2/- D.F. 4/6

Ideal 625 lines U.H.F. Low loss. 3dB. 1000-300 Mc/s. 1/6 yd.

TELESCOPIC CHROME SPRINGS.


12 to 33in., 6/8.
TELESCOPIC BANDAID 1/6
COAX PLUGS 1/2-LEAD SOCKETS. 2/-
PANEL SOCKETS. 1/6
OUTLET BOXES (Surface or flush). 4/- each.
BALANCED TWIN FEEDERS. 6d. yd. 80 to 500 ohm
TWIN SCREENED. 10 p per yard. 80 ohms only.

THE "INSTANT" BULK TAPPE ERASER AND RECORD HEAD DEMAGNETIZER

200/250V. A.C. 35/-
 RETURN OF POST DESPATCH
 P.P. Charge 1/6 Full list 1/-. C.O.D. 2/6 extra

BAKER LOUSPEAKERS

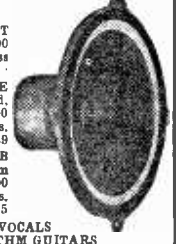HANDMADE BY CRAFTSMEN
 HIGH FIDELITY MODELS



12in., 15w. STALWART 3 or 15 ohm. 45-13,000 c.p.s., 12,000 lines. Bass res. 45 c.p.s. 25.5.
 12in., 15w., DELUXE Foam Cone Surround. 25-16,000 c.p.s., 14,000 lines. Bass res. 35 c.p.s. Remarkable value. 29

12in., 20w. SUPERR Aluminium Drive, Foam Cone Surround 20-17,000 c.p.s., Bass res. 22 c.p.s. Unbeatable value. £15

GROUP MODELS FOR VOCALS
BASS LEAD and RHYTHM GUITARS
 Frequency response 30-10,000 c.p.s.
 (Voice Coil 15 ohm Heavy Duty outputs.
 "GROUP 25" 12in. dia. 25w., 12,000 lines 5 c.p.s.
 "GROUP 35" 12in. dia. 35w., 14,000 lines 8 c.p.s.
 "GROUP 50" 15in. dia. 50w., 17,000 lines 18 c.p.s.

LOUSPEAKERS P.M. 3 OHM FAMOUS MAKES.
 24in. 3in. 4in. 5in. 7 1/2 in. 15/6 each; 8in. 17/6; 10in. 16/6; 10in. 30/-; 12in. 30/-; (15 ohms 25/-); 10 x 6in. 22in. 8 x 3in. 21/-; 9 x 6in. 21/-
 EM1 15 x 8in. ceramic, double cone, 3 or 15 oh. 45/-
WAVE-CHANGE SWITCHES. 2 p. 2-way or 4 p. 2-way; 3 p. 4-way or 1 p. 12-way; 4 p. 2-way or 2 p. 3-way; 6 change; 8 in. 4-way 2 water. 6/6.
WAVE-CHANGE "MAKITS" available 1 p. 12-way 2 p. 6-way; 3 p. 4-way 1 p. 8-way 6 p. 2-way. Kit Price 1 water 8/6; 2-water 12/6; 3 water 18/6. Extra wires 8/6 each, extra long shafts 2/6 extra.
TOGGLE SWITCHES 3/2- d.p. 3/6, d.p.d.t. 4/6

RADIO BOOKS (P.P. 9d.)

Valves, Diodes, Transistor equivalents. 10/6
 Transistor Amplifier. 10/6
 Shortwave Transistor Receivers. 5/6
Beginners' Modern Transistor Sets 7/6
 Sub-miniature Transistor Receivers 5/6
Boys' Book of Crystal Sets .. 2/6
"R.V.W." Radio Valve Data .. 7/6
High Fidelity Speaker Enclosure 5/6
TV Fault Finding .. 6/-
Multirad Amplifier Manual .. 8/6
Valve Guide, Books 1, 2, 3, 4 or 5 5/- each
Practical Radio Inside Out .. 4/6
Transistor Communication Sets .. 7/6
Transistor Controlled Models .. 8/-
International Radio Stations .. 2/6

JACK SOCKETS. Standard 2/6, closed circuit 4/6.

5-pin type 3-pin 1/2. Lead True 6/-
 Phone Plug 1/-
Socket 1/2- Banana Plug 1/6
JACK PLUGS. Screened 3/-. Grounding 3-pin 3/6
 2-pin 3/6; P73 3-pin 4/6; P194 6-pin 6/6; P106 12/6
RESISTORS. Preceding values, 10 ohms to 10 meg. 4 x w. 1 w. 20% 4d. 1 w. 3d., 2 w. 1/2-
HIGH STABILITY 1 w. 1 1/2-
All Values. 10 ohms to 10 meg. Ditto 5% 10 ohms to 22 ohms. 9d.
 5 watt } 0.5 to 82 ohm 3 W
 10 watt } WIRE-WOUND RESISTORS
 15 watt } 1/8 1/6
 1/2 ohm values, 0-500 ohms
 10 K 15 K 25 K 10 w.
MAINS DROPPERS Midget. With sliders 0.5a., 1 K, 0.25a. 1.2 K, 0.15a., 1.5 K, 0.1a. 2 K. 6/-
 each. Line cord 100 ohms ft. 3-way 1/6 ft.
 Wirewound Ext. Speaker Controls 10 1/2 2 1/2 25 6/6
WIRE-WOUND POTS 3 Watt. Miniature TV Type. All values 10 ohms to 25 K, 3/- each, 30 K, 4/-.
 Carbon 30K to 2 meg. 3/1-. All with knob.
WIRE-WOUND POTS 4 WATTS. Long 4in. 8-pin. Value 30 ohms to 50K, 6/6; 100 K, 7/6
SPARK FRET Texan various colours. 82in. wide iron 18/- ft.; 26in. wide from 5/- ft. Samples S.A.E.
EXPANDED METAL Gold or Silver 12 x 12in. 6/-
ARDENTE TRANSISTOR TRANSFORMERS
 D805 7.5 Ohm Push-Pull to 5 ohms output 11/-
 D304 1.5 Ohm Push-Pull Drive Output 11/-
 D305 11.5 Ohm Output 3 ohms. 11/6; D1001, 12/-;
 D239 4.5 ohm over 11/6; D240 8.5 Ohm Drive. 11/6
TRANSISTOR POTS 5 K Switched VC1545 5/3
SUB-MIN EARPIECE Kial or Magnetic 7/6
SUB-MIN JACK AND PLUG 25 or 3.5mm. 3/6 pp.

TV REMOTE CONTROL

For Philips 19G111A, 121A, 125A, 142A, 23TG111A, 113A, 121A, 123A, 124A, 125A, 777A, 778A


SNIPERSCOPE

Famous wartime "cat's eye" used for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it. It follows that as light from an ordinary lamp is rich in infra-red these cells will work burglar alarms, counting circuits, smoke detectors and the hundred and one other devices as will the simpler type of photo cell. Here then is a golden opportunity for some interesting experiments, price 5/- each. Post 2/-. Data will be supplied with cells if requested.



Speaker Bargain

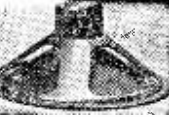12in. High-fidelity loudspeaker. High fidelity magnet type with either 3 ohm or 15 ohm speech coil. Will handle up to 10 watts. Brand new by famous maker. Price 29/6 + 3/6 post and insurance.



SPOT OR FOG LAMP

Made by Lucas. Flat or pencil beam, 36 watt. Suitable for car, boat, caravan, etc. Complete with 6 or 12v bulb, flex, cables and fixing bolt. Remarkable bargain. Price 12/6 + p. & p. 3/6



THERMOSTATS

Type 'A' 15 amp for controlling room heaters. Ring adjustable, firing cupboard. Has spindle for pointer knob quickly adjustable from 30°-80°F. 9/6 plus 1/- post. Suitable box for wall mounting, 5/-, P. & P. 1/-.
Type 'B' 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-650°F. Internal screw alters the

setting so this could be adjustable over 30° to 1,000°F. Suitable for controlling furnace, oven, kiln, immersion heater or to make flamestat or fire alarm. 8/6 plus 2/9 post and insurance
Type 'C' is a small porcelain thermostat as fitted to electric blankets, etc. 1/4 amp. setting adjustable by screw through side. 3/6, P. & P. 6d.

Type 'D' We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 amp. Has many uses, one of which would be to keep the loft pipes from freezing if a length of our blanket wire (16 yds. 10/-) is wound round the pipes. 7/6, P. & P. 1/1.

Type 'E' This is a standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature, 7/6, plus 1/- post.

9-Way push-button switch
Each way having two single pole change over and one shorting switch, good length push rods 30/- per doz. 3/6 each, post 2/9 doz.

Waterproof Heater Wire

16 yds. length 70 watts self regulating temperature control. 10/-, post free.

Three Unusual Items

OZONE OUTFIT—for removing smells and generally improving any oppressive atmosphere. Kit consists of Philips Ozone Lamp and mains unit only needs box. 19/6 plus 3/6 postage and insurance.


BLACK LIGHT UNIT. 40 watt intensity, comprises lamp, lamp holder and 40 watt choke. Only 19/6 plus 6/6 carr. & ins.

TIMER KIT. Special offer of all components except metal box to make mains operated interval timer for photography etc. 12/6 plus post 2/6.

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/8.

INFRA RED HEATER

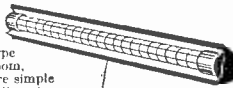Make up one of these latest type heaters, ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—use silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 75 watt element, as illustrated, 21/6 plus 3/6 post and insurance. Full switch 3/- extra.



SNIP FOR RECORD LOVERS

Acos GP83 Turnover Cartridge

for Stereo—LP—and 78 records fitted with two Styli—diamond for Stereo and LP—Sapphire for 78. This is mounted and is a standard replacement for most record players using (Garrard)—B.S.R.—Collaro, etc. The regular price of this cartridge is 55/-. We offer these new and perfect for 15/- (less than the price of one stylus) plus 2/- post and insurance.



GANGED POTS

Standard type and size with good length of spindle—If made by Morganite. List-price is 12/- each but if you act quickly you can have them at 12/- doz. (or 1/6 each if less than doz). Following values in stock all "jin"—5K+5K—10K+10K—100K+100K—500K+500K—1 meg + 1 meg all new and unused. Post 2/8 on 1st doz then 1/- per doz 6 doz or more post free.




YOUR LAST CHANCE FOR THIS



A complete kit of parts to build 6 transistor 2 wave superhet receiver at only 39/6. Post and Ins. 3/6.

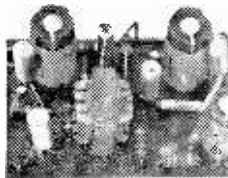"CORONET" Mk. IV
It fully covers the medium waveband and that part of the long waveband to bring in B.B.C. Light. The circuit includes a 2 1/2in. P.M. speaker. Overall sizes approximately 4 1/2 x 2 1/2 x 1 1/2in. Supplied complete with carrying case and instructions.



750 mW TRANSISTOR AMPLIFIER

4 transistors including two in push-pull input for crystal or magnetic microphone or pick-up—feed back loops—sensitivity 5 mV.

Price 19/6

Post and insurance 2/6, 36 ohm Speaker 12/6 extra.

THIS MONTH'S SNIP—


B.S.R. UA 16 RECORD PLAYER

WHICH IS THE BEST RECORD CHANGER TO BUY?



If you want a "pretty" unit which will give next to perfect results and years of trouble-free service, even though it may not always get the most careful treatment then the unit for you is the B.S.R. UA16. It operates records (mixed sizes if you like), is super slim and fitted with famous "Full-Fit" head for 33 or 78 records. You can have one of these brand new in perfect order, guaranteed and sent by insured transport for only £4.19.6 plus 7/6 carriage and insurance.

THE "MINY" TAPE RECORDER

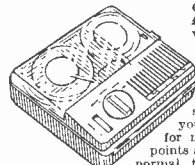

Of the many tape recorders to offer at £12 or less we have at last found one we can recommend. This instrument uses two motors, is completely portable and is beautifully styled and looks like a good tape recorder.

Among its many good features is a switch on the microphone to stop and start the tapes, a very useful feature for you when recording, and for your typist for note taking, stock taking, etc. Other points are twin track recording—40 mins. with normal tapes, standard batteries. Although originally sold at £16.18.0 we are able this month to offer for only £8.19.6 plus 5/- post and insurance. Brand new and complete with microphone, batteries, tape and spools, nothing else to buy. DON'T MISS THIS AMAZING OFFER.

BATTERY ELIMINATOR



With this you can operate your pocket radio from the mains. You can also recharge PZS batteries five or six times. Only 18/6 plus 3/- post and insurance. Will save its cost in no time.

TWO WAY RADIOS

Give communication over 2 mile. FULLY transistorised—crystal controlled built-in telescopic aerial—press button operation—PZS batteries—pair instruments complete and ready to use. £7.96, plus 5/- post and insurance. G.P.O. Licence required if used in this country.



FOUR-STATION INTER-COM



Will save time and improve efficiency.

Ideal in home—office—shop—surgery etc. Complete outfit comprises Master unit and three substations each of which can call the master and have full two-way working. No wiring problems as subs fitted with 60ft. twin flex and they plug into sockets. Also included is packet of staples—and battery. Nothing else to buy—£7.15.0 plus 4/6 post and insurance.

13 AMP SOCKET

Change all those old-fashioned ones to these modern fused types or install a new ring main. White sockets for surface mounting or for letting into wall or skirting—best make (G.C.C.). 5/6 with switch or 3/9 less switch. Six or more post free otherwise add 2/-.

HEAT & LIGHT UNIT

Gives 300 watts of heat with approx. 150 watts of light and simply fits in place of lamp. 29/6. Plus 3/6 carriage and insurance.



SEED AND PLANT RAISING



Soil heating wire and transformer. Suitable for standard size garden frame. 12/6 plus 2/6 post & ins.

TURRET TUNERS



By the famous Cydon or Brayhead firms complete with coils, but less coil cover valves and knobs—all 35 mcs—wonderful bargain at 6/6 each plus 2/9 post.

Sheet Paxolin

Ideal for transistor projects. Special offer 12 panels 5 x 8in. 5/-.




MAINS POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v—9 to 12 volts (for up to 500mA class B working). Takes the place of any of the following batteries: P1-P3-P4-P6-P7-P9 and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor, 5000 and 600 mfd condensers zener diode and instructions. Real snip at only 14/6 plus 3/- post.

ELECTRONICS (CROYDON) LTD

Callers: 266 LONDON ROAD, WEST CROYDON, SURREY
Post orders to: Dept. P.W., 4 Springfield Road, Eastbourne, Sussex

INCREASE YOUR KNOWLEDGE

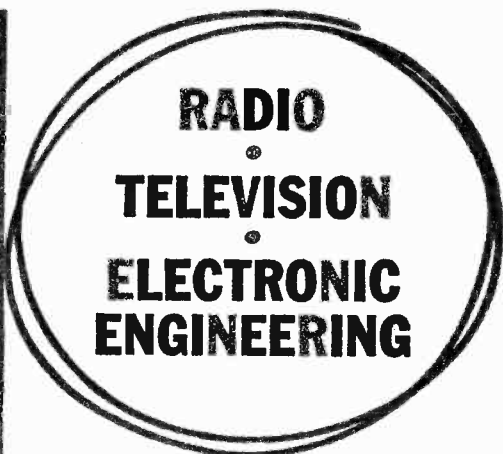

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

CHOOSE THE SIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING,
INDUSTRIAL TELEVISION, RADIO AND
TELEVISION SERVICING, ELECTRONICS,
COMPUTERS AND PROGRAMMING
ELECTRONIC TECHNICIANS, SERVOMECH-
ANISMS, TELEMETRY, COLOUR TV,
INSTRUMENTATION, AND PRINCIPLES OF
AUTOMATION.

ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers
C. & G. Telecommunication Techns' Cert.
C. & G. Supplementary Studies
R.T.E.B. Radio/TV Servicing Cert.
P.M.G. Certificate. Radio Amateurs' Exam.

LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of
Radio as you build **YOUR OWN** 5-valve superhet
Receiver and Transistor Portable, Signal Generator
and High Quality Multimeter. At the end of the course
you have invaluable practical equipment and a fund of
personal knowledge and skill. ICS Practical Radio
Courses open a new world to the keen amateur.

THERE IS AN ICS COURSE FOR YOU


Whether you need a basic grounding, tuition to com-
plete your technical qualifications, or further special-
ised knowledge, ICS can help you with a course
individually adapted to your requirements.

There is a place for you among the fully-trained men.
They are the highly paid men—the men of the
future. If you want to get to the top, or to succeed
in your own business, put your technical training in
our experienced hands.

ICS Courses are written in clear, simple and direct
language, fully illustrated and specially edited to
facilitate individual home study. You will learn in
the comfort of your own home—at your own speed.
The unique ICS teaching method embodies the
teacher in the text; it combines expert practical
experience with clearly explained theoretical training.
Let ICS help you to develop your ambitions
and ensure a successful future. Invest in your own
capabilities.

**FILL IN AND POST THIS COUPON
TODAY**

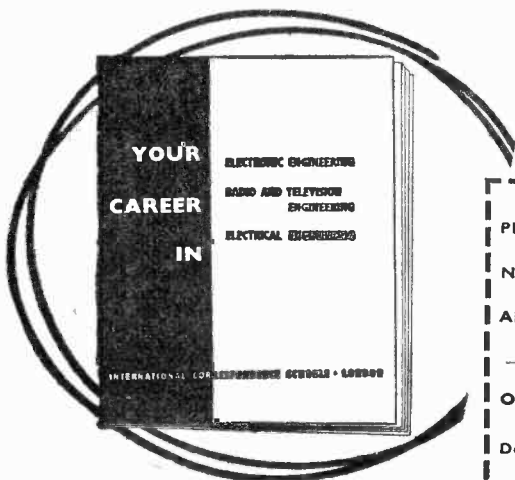You will receive the **FREE ICS Prospectus** listing the
examinations and ICS technical courses in radio, television
and electronics. **PLUS** details of over 150 specialised
subjects.



PLEASE SEND FREE BOOK ON _____

NAME _____

ADDRESS _____

OCCUPATION _____ AGE _____

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEXT HOUSE, PARKGATE RD, London SW11
2.66



Offer the Finest Value and HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days when the sum paid will be refunded less postage.

THE "SKYROVER" RANGE

GENERAL SPECIFICATION

7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 v. torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and Short Waveband 31-94 M and also 4 separate switched band-spread ranges, 13M, 16M, 19M and 25M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning head is completely factory assembled wired and tested. The remaining assembly can be completed in under three hours from our easy to follow stage by stage instructions.



NEW—The SKYROVER Mk 111


Now supplied with redesigned cabinet, edgewise controls, black and chrome plastic cabinet. Size 10 x 6 1/2 x 3 1/2 in. with carrying handle. **£8.19.6** Post 5/- Can now be built for **£7.19.6** Total I.I.P.—Price £10.0.3.

NEW—The SKYROVER DE LUXE

Tone Control Circuit is incorporated with separate Control. In a wood cabinet size 11 x 6 1/2 x 3 1/2 in. covered with a washable material with plastic trim and carrying handle. Car aerial socket fitted. Can now be built for **£10.19.6** I.I.P. Terms: 33/- dep. and 11 mths at 19/2. Total I.I.P.—P. £12.3.10

A simple additional circuit provides coverage of the 1100/1950M. band (including 1500 M. Light programme). All components and detailed construction data. **Only 10/- extra** Post Free This conversion is suitable for both models that have already been constructed.

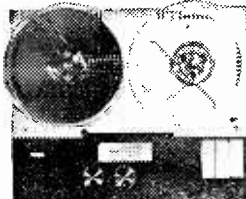Data for Receiver 2/6 extra Refunded if you purchase the parcel. Four U2 batteries. 3/4 extra. All components available separately.



The Very Latest MAGNAVOX-COLLARO 363 TAPE DECKS

3 speed model—11, 3 1/2, 7 1/2 i.p.s., available with either 1 track or 4 track heads. Features include: pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor; interlocking keys; size of top plate 13 1/2 x 11 x 5 1/2 in. deep below unit plate. For 200/350V. A.C. mains, 50 c.p.s. operation. New, unused and fully guaranteed.

LASKY'S PRICE with 1 track heads **£10.10.0** Carriage and packing 7/6 extra
LASKY'S PRICE with 4 track heads **£13.9.6**

SPECIAL for OVERSEAS CUSTOMERS—the new Magnavox-Collaro 363 Deck: for 110/125 v. 50 or 60 c.p.s. mains now available, prices as above. Post to any part of the World 33/-

Give a Lasky's Gift Voucher

The ideal gift for Birthdays and all those other special occasions. Any value in multiples of 10/6 (min.) upwards.

Special Inaugural Offer—Vouchers worth more than you pay! e.g. 1 Guinea Voucher for £1-10/6 Vouchers for 10/- etc.

You save money and give pleasure with a Lasky's Gift Voucher.

TRANSISTORS new and guaranteed

GET 81, GET 85, GET 86, 2/6; 873A, 874P, 8/8; OC45, OC71, OC81D, 4/6; OC44, OC70, OC76 - OC81 (match pair 10/6) 5/8; AF117, OC75, OC76 8/8; OC42, OC43, OC73, OC82D 7/8; OC201, OC204 15/-; OC205, OC206 19/6; OC28 24/8.

TRANSFILTERS BY BRUSH CRYSTAL CO.

TO-01B 465 kc/s. ± 2kc/s.
TO-01D 470 kc/s. ± 2kc/s.
TO-02B 465 kc/s. ± 1kc/s.
TO-02D 470 kc/s. ± 1kc/s.
TF-011B 465 kc/s. ± 2kc/s.
TF-01D 470 kc/s. ± 2kc/s.
7/6 EACH Post 6d.

B.S.R. AUTOCHANGERS—BRAND NEW AT LOWEST EVER PRICES

Brand new and fully guaranteed—complete with cartridge and stylus.

UA14 4 speed mains model £4.9.6
UA16 4 speed mains model £4.19.6
UA16 9v. battery model £5.19.6
UA20 4 speed mains model £5.19.6
Add 5/- carriage and packing on each.


INTERNATIONAL TAPE

3in. Message tape, 150ft. 3 6
3in. Message tape, 225ft. 7 11
3in. Message tape, 300ft. 7 6
3 1/2in. Triple play, 600ft., Mylar base 15 0
4in. Triple play 300ft. Mylar base 17 8
6in. Double play, 1,200ft., Mylar base 15 0
6in. Long play, 900ft., Acetate base 10 0
6in. Standard play, 600ft., PVC base 8 6
6in. Triple play, 1,800ft., Mylar base 35 0
6in. Double play, 1,800ft., Mylar base 22 6

Famous American Brand—Fully Guaranteed
5 1/2in. Long play, 1,200ft., Acetate base 12 6
5 1/2in. Standard play, 500ft., PVC base 11 6
5 1/2in. Long play, 1,200ft., Mylar base 15 0
6 1/2in. Triple play, 2,400ft., Mylar base 45 0
7in. Standard play, 1,200ft., Acetate base 10 0
7in. Standard play, 1,200ft., Mylar base 12 6
7in. Long play, 1,800ft., Mylar base 19 6
7in. Double play, 2,400ft., Mylar base 25 0
7in. Long play 1,800ft., Acetate base 15 0
7in. Triple play, 3,600ft., Mylar base 58 6
P. & P. 1/- extra per reel: 4 reels and over Post Free.

The "REALISTIC" Seven

★ 7-Transistor Superhet. ★ 350 milliwatt output into 4in. high flux speaker
★ All components mounted on a single printed circuit board. ★ Full medium and long wave cover. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in., Blue/ Grey or all Grey.
★ Socket for car aerial. ★ I.F. frequency 470 Kc/s.
★ Ferrite rod internal aerial. Operates from PPS or similar battery. ★ Full data supplied. All coils and I.F.'s etc. fully wound ready for immediate assembly. An outstanding receiver. **Can be built for £5.19.6** Post 4/6. P19 Batt. 3/6. Data and Instructions separately 2/6. Refunded if you purchase the parcel. All parts sold separately.

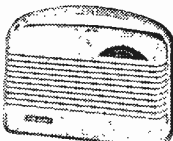

REALISTIC Seven DE LUXE

With the same specifications as standard model—PLUS a superior wood cabinet contemporary styling with full vision circular dial. **ONLY £1 EXTRA**

GOODMANS OF ENGLAND CROSSOVER UNITS

XO750 HALF SECTION CROSSOVER. For use with bass and treble speakers. 150 imp. to crossover at 750 c.p.s. Rated at 25 watts (British). In wood case 6 1/2 x 4 1/2 x 4 in. New and unused.

LASKY'S PRICE 29/-

Post 2/6.
STEREOPHONIC FILTER. This is a frequency divider/mixer for use with a Stereo amplifier. Its function is to combine the bass frequencies up to 300 c.p.s. into a single bass speaker for both channels and to divide the frequencies above 300 c.p.s. into two separate mid/top range speakers. It can also be used as a 300 c.p.s. crossover for a mono system. 150 imp. Rated at 25 watts (British). In wood case 10 x 4 1/2 x 3 in. New and unused.

LASKY'S PRICE 19/6

Post 2/6.

SINCLAIR MINIATURES

We stock the complete range of Sinclair Super-miniature Kits.
THE MICRO-6 pocket radio 59/6
THE SLIMLINE pocket radio 49/6
THE N-20 Amplifier £7.19.6
Ready built and tested £9.19.6
THE X-10 Amplifier £5.19.6
Ready Built, and Tested.
See our Practical Wireless November '65 advertisement for details.

U.H.F. TUNERS

Only a few available. Complete with PC86 and PC88 valves. We regret no circuit or data is available. Knobs included.

LASKY'S PRICE 69/6

Post 2/6.

GORLER UT 340 FM/VHF TUNING HEART

Permeability tunes—covering 87 to 108 Mc/s. For use with one ECC85 valve. In metal case. Size 3 x 2 1/2 x 1 1/2 in. Circuit supplied.

LASKY'S PRICE 19 11

ECC85 valve 9/- extra. Post 2/-

LASKY'S FOR D.I.Y. CONSTRUCTION BARGAINS

Service in Great Britain to both & HI-FI ENTHUSIASTS

TAPE RECORDERS · RECORD PLAYERS · AMPLIFIERS ETC.
COMPLETE MONO/STEREO SYSTEMS TO YOUR SPEC.



NEW COMMUNICATION RECEIVERS MODEL KT 320 KIT




Supplied in sub-assemblies for easy building. Covers range from 540 Kc/s to 30 Mc/s. Ham Band is provided with a scale for direct reading and can also be band spread 9 valves. Facilities: A.N.L., A.V.C. and M.V.C. Q-Multiplier; also serves as B.F.O. H.F. stage and two I.F. stages ensure high sensitivity and selectivity (all coils and I.F.s are supplied pre-aligned). 2 Aerial Sockets. Stand-by position for use with a transmitter 3 meter fitted. 200-250v. A.C. mains. Steel cabinet, grey crackle finish. Size 15 x 8 x 10in. Dial 12 x 4in. All parts new and fully guaranteed. Complete with full construction data and operating manual.

LASKY'S PRICE 25 GNS. POST FREE
Also available ready built and tested 29 gns.
H.P. Terms available.

MODEL HE30 Still a few available—
as advertised June '65
LASKY'S PRICE 33 GNS.
H.P. Terms available.

MODEL HE40

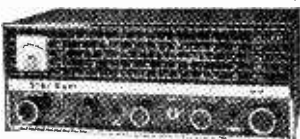

Covers medium wave band and 1.6-4.4 Mc/s, 4.5-11.0 Mc/s, 11.0-30.0 Mc/s. In separate switched band spread ranges. Controls include B.F.O. Sensitivity, A.N.L. Receiver—Stand-by Switch, Tone Switch, S-Meter. For 200-250v. A.C./D.C. Internal loop and telescopic antennae fitted. Valve line-up: 12BE6, 12BA6, 12AV6, 50C5, and metal rectifier. Size 13 1/2 x 9 1/2 x 9 1/2 in. Instruction manual included. No Kit available.

LASKY'S PRICE 19 GNS. POST 10/-
H.P. Terms £4.00. dep. and 11 months at £112.0
Total H.P.P. £21.12.0.

MODEL HE80 14-valve super sensitive communication receiver. Freq. range 540 Kc/s—30 Mc/s and 144-146 Mc/s. Dual conversion on 2 metres, with extra R.F. stage. Single R.F. stage, two I.F. stages on all other bands. B.F.O. and Q-multiplier circuits. Improved A.N.L. and voltage regulated powerpack. "S" meter band spread on amateur bands, large illuminated dial with logging scale. All controls fitted. Output for speaker and phones. Valve line-up: 4 x 6AQ5, 2 x 6BA7, 2 x 6BB6, 1 x 6BL8, 6AL5, 6AQ5, 6CA4, and OA2. Steel case 17 x 7 1/2 x 10in. For 200/250v. A.C. mains. Brand new with full instruction manual. No Kits available.

LASKY'S PRICE 59 GNS. POST FREE
H.P. Terms £12.19.0 dep. and 11 monthly payments of £4.15.0. Total H.P.P. £66.17.0.

SPECIAL ANNOUNCEMENT—Our Head Office and Mail Order Departments have now been transferred to our new building 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1

Telephones: STEpney Green 4821/2
All Mail Orders, correspondence, H.P. enquiries/accounts etc. should now be sent to the above address.
These premises have been especially designed for us to facilitate the handling of Mail Orders and continue our aim of rapid despatch coupled with good service, with which our name has been synonymous over the past 35 years

Ideal Seasonal Presents

TRANSISTOR POCKET RADIOS

All supplied complete with personal earpiece, battery and carrying case. Fully guaranteed—ready to use. POST FREE.

BOY'S 2 TRANSISTOR In attractive plastic case. Size only 4in. x 2 1/2in. x 1in. Fitted 2 1/2in. speaker. Socket for personal earpiece. Uses PP3 battery. Tunable over full medium waveband.

LASKY'S PRICE 35/-

BOY'S 4 TRANSISTOR MODEL **LASKY'S PRICE 45/-**

6 TRANSISTOR MODEL

Fully built in plastic case, 4in. x 2 1/2in. x 1in. with 2 1/2in. speaker. Uses single PP3 type battery. Tunable over full medium waveband.

LASKY'S PRICE 59/6

2 Waveband (Long and Medium) Model Size 5 x 3 1/2 x 1 1/2in. Cream/black plastic case. Incl. earpiece & carrying case. **LASKY'S PRICE 89/6**

THE "TRANSWAVE" DE LUXE TWO WAVEBAND RADIO

8 Boy's transistors give super sensitive reception over the full Med. and Long wavebands. Internal ferrite and detachable chrome telescopic aerials, 2 1/2" p.m. speaker. Smart black plastic cabinet with metal trim—size 6 1/2 x 3 1/2 x 1 1/2in. Uses 3 pen light batteries. Complete with leather case and shoulder strap, earpiece and batteries. Post 2/6

LASKY'S PRICE 99/6

3 WONDERFUL SETS FROM THE U.S.S.R.

THE "SELGA" 7 TRANSISTOR RADIO

High sensitivity circuit gives excellent reception over full Med. waveband and powerful volume. P.M. speaker. Uses PP3 type battery. Black and ivory plastic cabinet size 7 x 4 x 2in. Socket for external aerial. Complete with solid hide case and shoulder strap, earpiece and battery.

LASKY'S PRICE £5.9.6 Post 2/6



THE "SOKOL" 7 TRANSISTOR TWO BAND RADIO

Super quality receiver covering the full Med. and Long wavebands with exclusive rechargeable battery which can be recharged from any 110/250v. A.C. mains supply. Also operates on PP3 type dry battery. real leather case, rechargeable battery and charger, dry battery and earpiece.

LASKY'S PRICE £6.9.6 Post 2/6

THE "CONVAIR" 10 TRANSISTOR PORTABLE RECEIVER

Extremely well designed and made receiver covering the Long, Med. and Short wavebands. The Short waveband has switched band spread on 13m, 16m, 19m, 25m, 31m, 41m bands. Internal ferrite rod and telescopic aerials. Sockets for external aerial and earth and gram. pick-up. Strong cream and black plastic cabinet with carrying handle—size 10 x 7 1/2 x 3 1/2in. Uses six U2 type batteries (supplied).

LASKY'S PRICE £12.19.6 Post 5/-



SPECIAL OFFER: GARRARD AT5 AUTOCHANGERS

4 speed mains model—brand new and fully guaranteed
With mono crystal cartridge **LASKY'S PRICE £5.19.6** With stereo cartridge **£6.9.6** Post 5/-

207 EDGWARE RD, LONDON, W.2
33 TOTTENHAM CT. RD., LONDON, W.1

Tel: PAD 3271
Tel: MUS 2605

42 TOTTENHAM CT. RD., LONDON, W.1
152 3 FLEET STREET, LONDON, E.C.4

Tel: LAN 2573
Tel: FLE 2833

Both open all day Saturday. Early closing Thursday.

Both open all day Thursday. Early closing Saturday.

Mail Orders and correspondence to 3-15 Cavell St., Tower Hamlets, London, E.1. Tel: STE 4821/2

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

Brand new individually checked and guaranteed

VALVES

Table listing various vacuum tubes with their types and prices. Columns include tube types like AC/HL, AC/PC, AL60, etc., and prices in pence and shillings.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Tubes. All U.K. orders below £1. P. & P. 1/-; over £1. 2/-; over £3. P. & P. free

MARCONI COMMUNICATION RECEIVERS CR. 150. Frequency coverage 2-60 Mc/s in 5 bands. Two lfs 1st 1,600 kc/s, 2nd 463 kc/s. Image signal protecting over 40 dB up to 30 Mc/s and 20-40 dB from 30-60 Mc/s. Self-checking calibration (built-in calibrator). Stabilisation of supply and temperature compensation. Electrical and mechanical indicator Bandpass from 100 c/s to 10 kc/s bandspread. Metering and visual tuning in 5 stages. Acoustic filter associated with 100 c/s. Bandpass position for CW reception. Facilities for diversity reception. Excellent checked condition. £39. Mains P.S.U. by P.C. Radio £4.10.0 Carriage 30/- CR.150/2. Frequency coverage 1.5-22 Mc/s in 4 bands, all other features as in CR.150. Price £31. Carriage 30/-.

P.C. RADIO'S mains P.S.U. for above, 90/-.

H.R.O. SENIOR TABLE MODEL in excellent, fully checked and tested condition together with set of general coverage coils and mains P.S.U. £28. Carriage and Packing 30/-.

ORIGINAL MAINS POWER SUPPLY UNIT FOR H.R.O. RECEIVER, 260/115v. Brand New 65/-, P. & P. 5/-.

AR80D RECEIVERS. Fully reconditioned, £55, rebuilt models £85. Carriage paid U.K.

EVERSHED MEGGER CIRCUIT TESTER. 2 ranges 0 to 1,000Ω, 100Ω to 200,000Ω. With test leads, leather carrying case. Tested £4.19.6. P. & P. 3/6

PANEL METERS (round) table listing meter types and prices. Columns include meter types like 500mV, 500mV*, 500mA, etc., and prices.

MARCONI SIGNAL GENERATOR TYPE TF 801B/3/S. Frequency range 12-485 mc/s in five ranges. Directly calibrated frequency dial. Output waveform: CW sinewave A.M., pulse A.M. (from ext. source only). Internal modulation frequency 1,000 c/s. Output: A normal—continuously variable directly calibrated from 0.1V-0.5v. b. high up to 1v. modulated; or 2v unmodulated; or 50Ω impedance 50 ohms. Fine frequency tuning control, carrier on/off switch, built in crystal calibration for 2 mcs and 10 mcs. Stabilised voltage supply. In excellent "as new" condition, fully checked and guaranteed. £115. Carriage 30/-.

THERMAL PULSE MECHANICAL CIRCUIT BREAKER FOR A.C. & D.C. Current 1 amp. Protects against shorts (instantaneous cut-out at approximately 8 amps) and against overloads: 1-8 amp 30 seconds, 2-1 amp 15 seconds, 2.5 amp 8 seconds. Delayed cut-off may be adjusted to different currents and times. Separate pair of contacts to indicating device. Dimensions 3 1/4 x 1 1/2 x 1 1/2 in. Price £12/6. P. & P. 2/6.

SEMI-AUTOMATIC BATTERY CHARGER "Baby Estroon". Initial charging rate 3-5 amps DC automatically reducing to 1-5 or lower (depending on specific gravity of battery acid). As the battery receives the charge indication lights indicate visually the high current or when incorrectly connected. Meter incorporated. For 6 or 12v batteries. Mains voltage 200V/240v AC. Price £3. P. & P. 4/6.

VARIOMETER for No. 19 set, 1/6, P. & P. 3/6.

TELEPHONE HANSET. Standard G.P.O. type, new 12/-, P. & P. 2/-.

WIRELESS SET NO. 52 (CANADIAN). Complete station consisting of Transmitter, Receiver, supply unit for 12 v. All contained in special carrier. 1.75-16 mc/s in 3 bands. 813 as output valve. 45.75 v. phone and MCW. 70-100 watt CV. M.C.O. or crystal. Receiver includes crystal calibrator. Tx. can be exactly tuned to Rx. frequency. Noise limiter. Sidetone. Loudspeaker on receiver with on/off switch. All brand new with accessories. Export. Price on application.

P.C. RADIO LTD 170 GOLDHAWK ROAD, W.12. Shepherd's Bush 4946 Open 9-5.30 p.m. Thursday 9-1 p.m.

Circuits • Diagrams • Repair Data

Here's all you need for servicing

OVER

1,450 Models

(1962-1965)



There is no other publication like Newnes **RADIO & TV SERVICING** . . . the greatest time-saver and money-maker you can own! 3 volumes packed with circuits, data and hints for repairing over 1,450 models (1962-65). *TV, radio, tape recorders* . . . all the famous makes are here. Plus big section of latest Radio and TV developments. Examine it, **USE** it for a week **FREE!** Don't miss this opportunity—simply post coupon today. Absolutely no obligation.

All these makes

Ace, Aerodyne, Ajax, Alba, Argosy, Baird, Berec, Bush, Cossor, Dansette, Decca, Defiant, Doric, Dynatron, E.A.R., Ekco, Elizabethan, Elenco, E.M.I., Emerson, Eumig, Ever Ready, Fergusor, Ferranti, Fidelity, G.B.C., G.E.C., Grundig, H.M.V., Hitachi, Invicta, K-B, Magnavox, Marconiphone, Master-radio, McMichael, Motorola, Murphy, National, Newmatic, Pam, Perdio, Peto Scott, Philco, Philips, Playmate, Portadyne, Portogram, Pye, Radiomobile, Recording Devices, Rediffusion, Regentone, Retra, Revelation, R.G.D., Roberts' Radio, Sharp, Sinclair, Sobell, Sonolor, Sony, Sound, Standard, Stella, Stereosound, Stuzzi, Teletron, Thorn, Trans Arena, U.K.W., Ultra, Volmar, Waltham-Standard, Zenith.

3 VOLUMES
1,848 PAGES

OVER 2,000 CIRCUITS & DIAGRAMS

- TELEVISION • RADIO
- RADIOGRAMS
- TAPE RECORDERS
- RECORD REPRODUCERS



Examine it—use it **FREE FOR A WEEK**

ONE REPAIR JOB CAN REPAY ITS COST

Compiled by a team of research engineers this big 3-volume library gives you, instantly, the vital data and circuits you need. Cuts out guesswork and delays, steps up your earning power.

Nearly 60,000 Sets of previous editions sold! Are you missing extra income? Find out why this big servicing aid is in such demand—send for your Free Trial Set today.

To: George Newnes Ltd.,
15-17 Long Acre,
London, W.C.2

Full Name
(BLOCK LETTERS) (Mr., Mrs., Miss)

Address

Occupation

Signature

Please send **RADIO & TV SERVICING** (3 volumes) without obligation to buy. If you accept this application I will post 10/- deposit 8 days after receipt of books, then 20/- monthly for 8 months, paying £8. 10s. in all—or return the books. Cash in 8 days £8. 10s.

Free Trial applies G.B. For Ireland send cash price (refundable if title returned in 8 days).

43/1756

If under 21 your father must fill up coupon.

Tick ✓ where applicable

The address on left is—

My Property	<input type="checkbox"/>
Rented unfurnished	<input type="checkbox"/>
Parents' Home	<input type="checkbox"/>
Furnished Accom.	<input type="checkbox"/>
Temporary Address	<input type="checkbox"/>

Why NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...


BACKED BY OUR SUPER AFTER SALES SERVICE

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans available separately at prices stated. Overseas post 10/-.

FIRST FOR QUALITY, PERFORMANCE & PRICE!

NEW ROAMER SEVEN Mk IV

7 WAVEBAND PORTABLE OR CAR RADIO
★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS
FULLY TUNABLE ON ALL WAVEBANDS ● 9 stages—7 transistors and 2 diodes
 Amazing performance and specification. Covers Medium and Long Waves, Trawler Band and three Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned 7" x 4" speaker. Air spaced, gated tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S waves. Real leather look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PP7 batteries available anywhere.)
★ EXTRA BAND FOR EASIER TUNING Total cost of parts now only **£5.19.6** P. & P. 5/6
OF PIRATE STATIONS etc Parts Price List and easy build plans 3/- (FREE with kit)

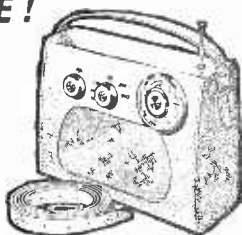

MELODY SIX

"... amazed at volume and performance... has really come up to my expectations."
 S.G. Stockton-on-Tees.


● 8 stages—6 transistors and 2 diodes



Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial. Push-pull output. Home and Light, 20R and

Wonderful reception of B.B.C. Home and Light, 20R and many Continental stations. Handsome leather-look pocket size case, only 6 1/2 x 3 1/4 x 1 1/2 in. approx. with gilt speaker grille and supplied with hand and shoulder straps.
 Parts Price List and easy build plans 2/- (FREE with kit)

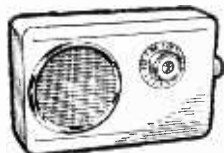Total cost of all parts now only **£3.9.6** P. & P. 3/6



with red speaker grille. (Uses 1289 battery available anywhere.) Total cost of all parts now only **42/6** P. & P. 3/6

New TRANSONA FIVE

"Home, Light, A.F.N., Lux. all at good volume."
 G.P. Durham.

● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2 1/2 in. speaker etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere.)

Parts Price List and easy build plans 2/- (FREE with kit)


TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Push-pull output, Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere.) Carrying strap 1/- extra.

Total cost of all parts now only **59/6** P. & P. 3/6

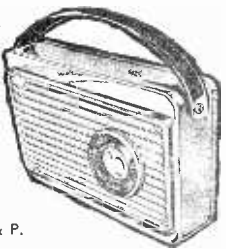Parts Price List and easy build plans 1/6 (FREE with kit)




POCKET FIVE

● 7 stages—5 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2 1/2 in. moving coil speaker, built into attractive black case with red speaker grille. Size 5 1/2 x 1 1/4 x 3 1/4 in. (Uses 1289 battery available anywhere).

Parts Price List and easy build plans 1/6 (FREE with kit)

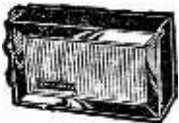Total cost of all parts now only **42/6** P. & P. 3/6



NEW ROAMER SIX

NOW WITH PHILCO MICRO-ALLOY R F TRANSISTORS

● 6 WAVEBAND !!

● 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long waves, Trawler band and two Short Waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 7 1/2 x 3 1/2 x 1 1/2 in. Carrying strap 1/6 extra.

★ EXTRA BAND FOR EASIER TUNING OF LUX, etc. Parts Price List and easy build plans 2/- (FREE with kit)

Total cost of all parts now only **£3.19.6** P. & P. 3/6



reception. Special circuit incorporating 2 R.F. Stages, push-pull output, 3in. speaker (will drive larger speaker). Size 7 1/2 x 5 1/2 x 1 1/2 in. (Uses 9v. battery, available anywhere.)

Total cost of all parts now only **£3.19.6** P. & P. 3/6

Parts Price List and easy build plans 2/- (FREE with kit)

SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful

RADIO EXCHANGE CO

61, HIGH STREET, BEDFORD

Telephone: Bedford 52367

Callers side entrance Barratts Shoe Shop open 9-5 p.m. Sats 10-12.30 p.m.

PRACTICAL WIRELESS

FEBRUARY 1966
VOL 41 NO 708

INCONSISTENCY

THE radiation of unlicensed radio signals is illegal. Yet how does the responsible body—the GPO—deal with offenders? It depends, it would seem, not so much on points of law but of expediency.

Unlicensed "hams" are quickly pounced upon, fined and their equipment confiscated, as can be seen from the names and addresses of those now sadder and wiser which appear in the RSGB Bulletin. And recently, the Postmaster General quickly clamped down on the use of radio microphones following a clamorous press campaign.

But what of the pop pirates? Despite an EBU agreement and despite assurances from the PMG shortly after taking office that "steps will be taken", all we have had so far is prevarication. Admittedly, a Government not wishing to jeopardise its popularity would have to think twice before taking steps against these stations. And in the meantime, they are allowed to go their merry way, untouched and—we cannot help thinking—with tacit approval.

On the other hand there are no political undercurrents associated with the sphere of piracy manifest in the 27 Mc/s walkie-talkie situation. The Board of Trade continues to license the import of these transceivers, radio dealers continue to sell them to all and sundry and the GPO (except for the recent spectacular swoop on the fisherman's radio net) appears to sit back and wait for individuals to start using them.

This is a ludicrous situation from any standpoint, yet it could be solved simply and quickly given a little energy. In the matter of unlicensed radio transmitting the GPO moves in wondrous and mysterious ways. Some consistency of purpose is very long overdue. *One practical idea is to make the production of a licence legally essential before anyone can purchase any transmitting equipment.*

CONTENTS

	Page
News and Comment	846, 876
Progressive Short Wave Receiver	848
Measurements with the GDO	852
Insensitivity in Transistors	855
Educational Quiz Machine	859
Practically Wireless	864
Walter "Metropolitan"	867
Modulated Light-Telephone Link	872
Modifying Mains Transformers	878
Mini-Modulator	881
Single Circuit Panels	885
On the Short Waves	890
Add-in Transistor Stage	894
Noise Abatement	897
Club Spot—University of Sheffield A.R.S.	905

All correspondence intended for the Editor should be addressed to The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes: Rand London. Subscription rates, including postage: 29s. per year to any part of the world. © George Newnes Ltd., 1965. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproduction or imitations of any of these are therefore expressly forbidden. **The MARCH ISSUE WILL BE PUBLISHED ON FEBRUARY 3rd.**

Ham or Sham?

THE editorial in the December issue of P.W. brought back many happy memories of the early 20's when I first became a "ham" and the proud possessor of the call-sign 2OY. Later, in 1924 when I was transferred to India, I was able to re-open my station there with the call-sign 2JL.

When 2OY first transmitted it was with largely home-built equipment; so also was 2JL. Government surplus became available and the station was improved with components from surplus sets.

In order to obtain my licence it was necessary to have five sponsors who stated in writing that they would be willing to exchange signals with me and to give full details of the equipment to be used. The P.O. official who called at my home to give the 12 w.p.m. morse test did so at about 20 w.p.m. and when I said, "Wasn't that a bit fast for 12 w.p.m.?", he said he thought he would see what I could do.

I was first licensed to transmit on 1000 metres and wavelengths up to 180 metres. Sometime later 1000 metres was cancelled and 440 metres substituted.

My transfer to India was made at fairly short notice so I wrote to the Posts and Telegraphs Dept., Delhi, and explained the position and said I proposed to bring my equipment with me in the hope that it would be admitted by Customs on arrival at Bombay and that I might be allowed a licence later. Imagine my pleasure and surprise to find a letter awaiting me on arrival saying the customs officials had been authorised to admit my equipment and my licence approved. Would I be so good as to remit the licence fee at my convenience.


But to come back to your point. I wonder if I would have made a bee-line for a store selling commercially made transmitters and receivers? I doubt it! The pleasures of surmounting the many obstacles would have been missed, including the numerous congratulations I received on the quality of the speech and music transmissions using an early model Ford ignition coil as the power supply.

E. J. Hobbs,

Sidcup,
Kent.

NEWS AND..

NEW PAM RADIO

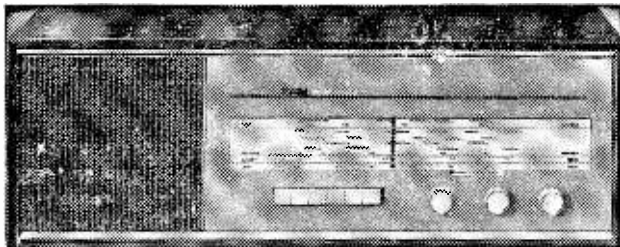

From Pam (Radio & Television) Ltd., comes the solid state mains radio, model 5230. Features include: ten transistors with complimentary push-pull output of over 2½W; four wavebands (v.h.f., long, medium and short); piano key controls (gram, tape, LW, MW, SW and f.m.) and an 8in. x 5in. 15Ω speaker. The slim-line cabinet is of selected Sapele veneer with scratch-resistant finish. Weight is 15lbs. and the price, 32 guineas.

SELLOTAPE INSULATING TAPE

Sellotape polythene insulating tape, which is invaluable for the serviceman, is available from most good hardware and electrical stores. The tape is available in six colours—red, blue, black, white, green and yellow. It is fully insulating and completely waterproof, and has a certain amount of elasticity which makes for neat and tidy repairs. A ¾in. x 15ft. roll retails at 1s. 9d.

HEATHKIT GUITAR/PUBLIC ADDRESS AMPLIFIER

From Daystrom Limited, Gloucester, comes the Heathkit PA-2 power amplifier.

It employs a fully transistorised circuit, capable of delivering 20W r.m.s. power (33W IHFM) when fully loaded, into the two 12in. heavy-duty loudspeakers.

Two channels are provided—one with a tremolo facility—and each channel has two inputs.

Sensitivity is sufficient for the vast majority of electric guitars and for most microphones. An input suitable for the more sensitive type of microphone is available on one channel.

The equipment, comprising a preamplifier with controls, a power amplifier and two 12in. loudspeakers, is housed in a sturdy, attractive cabinet. Legs or castors are available as optional extras.

SPECIFICATION. Power output: 20W r.m.s., 33W IHFM; output impedance, 8 ohms. Channel 1: sensitivity, input A, 20mV; input B, 5mV. Controls: continuously variable; volume, bass and treble. Channel 2: sensitivity, inputs A and B, 20mV; controls: continuously variable; volume, bass, treble, tremolo speed and tremolo depth (with tremolo On/Off switch). Transistor complement: 5—OC44, 2—2N2712, 1—2N408, 4—BC107, 2—2N2147, 2—2N2148. Diode complement: 8—silicon diodes, 2—1N2326. Speakers: two 12in. heavy duty, 15 ohms each, approx. 8 ohms in parallel. Hum and noise: channel 1:—50dB channel 2, —44dB; cabinet: wood, finish black/gold Vynair, gold trim. Power requirements: 100-250V a.c., 50/60c/s 32W. Dimensions: 19in. high x 30in. wide x 10in. deep. Net weight, 49lb; shipping weight, 60lb. Kit price, £44 19s 0d.

Optional extras: set of four legs, 17s 6d; set of four 1½in. diameter castors, 13s 0d.

.. COMMENT

"PRACTICAL WIRELESS" AND "PRACTICAL TELEVISION" FILM SHOW

The Film Show, which is held annually, is to be held, as before, at Caxton Hall, Caxton Street, Westminster, London, S.W.1. The date of the Show, which is arranged in collaboration with Mullard Limited, is Friday, February 4th, 1966, at 7.30 p.m. sharp. The films to be shown are "Electromagnetic Waves, Part II" and "Thin Film Microcircuits". The illustrated talk will be on "Transistor Topics". The talk will be given by Mr. Ian Nicholson of Mullard Limited, and in the chair will be Mr. W. N. Stevens, Editor of "Practical Wireless" and "Practical Television".

Refreshments will be provided during the interval.

Applications for free tickets should be made to FILM SHOW, "Practical Wireless", Tower House, Southampton Street, London, W.C.2 and NOT to Caxton Hall. A stamped addressed envelope must be enclosed.

NEW STC PUBLICATION

STC have just published Application Notes covering the use of their BCY42 transistors in: (1) A 10Mc/s wideband amplifier. (2) An audio amplifier delivering 1mW into a 600Ω load.

Circuit diagrams and components lists are given and both Application Notes are in publication MK/185X available from STC Components Marketing Division, Footscray, Sidcup, Kent.

"BIJOU" MAINS POWER PACK



The drawback of the pocket-type transistor radio is the strictly limited life of the small battery when the set is extensively used. The voltage quickly drops and the reception becomes distorted. With the "Bijou" 9V power unit the voltage remains constant all the time; the consumption being less than that of an electric clock.

This power unit is easy to use: the battery should be removed and the battery clip of the set connected to a similar clip which is on one of the leads coming from the power pack. The other lead from the unit goes to 250V a.c. mains.

A "Booster" strap is also supplied with the unit. This enables old batteries to be reactivated. The Booster strap is connected to the clip of the power pack, and the old battery plugged into the other side of the Booster strap. The makers state that to get best results from the Booster strap, it

should be plugged in soon after the set has been switched off.

The photograph shows the power unit complete with Booster strap. The price of the complete unit as shown, is 17s. 6d. plus p. and p., and it is obtainable from R.C.S. Products Ltd., 11 Oliver Road, London, E.17.

more News and Comment

Plastic Sheet Tagboards

In your November issue you published a letter from Mr. W. E. Thompson, in which he advised readers not to use any form of decorative plastic sheet, on the grounds that "As it is heat-resistant it has a thin metal foil sandwiched in it, and this foil can cause short-circuits."

I would like to make it clear to your readers that "Arborite" decorative laminate, although heat-resistant, has no metal foil sandwiched in it.

L. Allen,
Publicity Manager,

Arborite Ltd.,
Ealing,
London, W.2.

Guitar Preamp

I RECENTLY constructed the guitar preamp described by Mr. Kampel in the June issue of PRACTICAL WIRELESS and although I found this little unit excelled itself in normal domestic use, the large amount of subsequent amplification needed for high-power work exposed a very troublesome hiss, which did not appear to be caused by faulty components. After some research, I found it was necessary to make two modifications to the circuit to overcome the hiss. One was to fit a resistor directly across the input: the value of resistor being about the same as the impedance of the pickup. (This can be found approximately by doubling the d.c. resistance of the pickup.) The second adjustment was to connect a capacitor across the output to effect a form of treble cut. The value of this capacitor can be found by trial and error, however, a good starting point is about 0.01μF if the next stage is transistorised, and 0.001μF if it employs valves.

One feels, however, that these measures are rather unsatisfactory as some attenuation of the signal is bound to occur. It would perhaps be interesting to know whether other constructors who have built this preamp have managed to find any other more satisfactory ways of suppression.

Ian Gregorig.

Borehamwood,
Hertfordshire.


on page 876

The blueprint given away with this Issue provides all the circuits and wiring diagrams.

designed by

R. F. GRAHAM

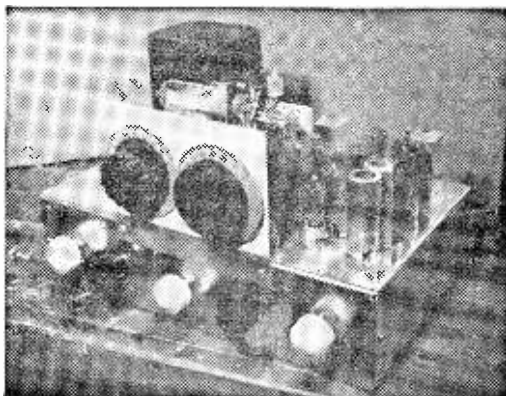- ★ 5V SUPERHET
- ★ R.F. STAGE
- ★ I.F. REGENERATION
- ★ BANDSPREAD
- ★ TUNING INDICATOR



PROGRESSIVE SHORT WAVE RECEIVER

THIS receiver can be constructed in a number of stages, beginning with the basic 4-valve (plus rectifier) superhet. It should thus be useful for anyone who is looking for a sensitive and selective receiver covering medium and short wave bands, but who hesitates to build a rather complicated set immediately.

Coverage is from 580 to 9.5 metres, or 515kc/s to 31.5 Mc/s, in four bands. Ready made miniature plug-in coils are employed, to avoid the complication of switching. Actual band coverage is approximately as follows: 515—1545kc/s (580—194m), 1.69—5.3Mc/s (180—57m), 5—15Mc/s (60—20m), 10.5—31.5Mc/s (28—9.5m).

Some of the additions which can be made to the original receiver, to increase its scope, include bandspreading, r.f. stage with r.f. gain control, regenerative i.f. amplifier, tuning indicator, and stand-by/a.v.c. switching. These extras are added after the original receiver is in working order, and a high standard of performance is obtained.

Basic Circuit

This is shown in Fig. 1 and the receiver is first made in this form. Very good results are obtained on all bands. The aerial plug in coils are blue, and the oscillator coils are red. Each oscillator coil has a different pin-P for the padder capacitor, so that the correct capacity is automatically in use when a coil is inserted. VC1 and VC2 are sections of the ganged tuning capacitor. VC3 is a fully variable aerial circuit trimmer, so there is no need for a separate pre-set trimmer for each band. TC1, in the oscillator circuit is the only pre-set capacitor, and there are no trimming difficulties, despite the full waveband coverage of the receiver.

The second valve is the usual intermediate frequency amplifier, followed by a double-diode triode for detection, a.v.c. bias, and audio amplifi-

cation. The a.v.c. bias also controls the tuning indicator, when fitted. The 6BW6 output stage delivers ample volume for all ordinary purposes. The 6X4 is a full-wave rectifier.

For general all-wave reception, the receiver can be kept in the form shown in the circuit. For greater range and more freedom from 2nd channel interference, the r.f. stage can be added. Bandspreading can be incorporated in the original circuit, or added with the r.f. stage. It is useful to simplify tuning on crowded s.w. bands. The tuning indicator can be added at any time and also acts as an aid to alignment or when netting the receiver on a transmitter frequency. The standby switch (which leaves heaters on) is useful when operating the receiver in conjunction with a transmitter. Adding i.f. regeneration offers a simple way of receiving c.w. and gives an improvement in selectivity for crowded amateur bands.

Chassis Drilling

The chassis is 7 x 12 x 3in. deep and the positions of most holes can be marked from the dimensions in Fig. 2. An adjustable cutter or valveholder punch is very handy for making the larger holes. It is best to do most of the drilling before mounting any parts.

The mains transformer actually fitted was surplus but there is plenty of space for any transformer of the rating listed. Drop-through transformers need an opening, which can be made by drilling holes, then cutting with a metal saw. Other transformers mount above the chassis with leads descending through small holes.

Each i.f. transformer needs four clearance holes for pins two holes for 6BA bolts and a central hole to permit adjustment of the lower core. The valveholders are placed as in Fig. 3 and a 6BA tag added under each nut.

The ganged capacitor has three sections to allow tuning of the r.f. stage later. An insulated lead is soldered to each tag and passes down through a $\frac{1}{4}$ in. hole. The dial plate is bolted to the front of the chassis and the ball drive is fixed to it. Trimmer TC1 is a 30pF air-spaced beehive soldered directly from VC2 to a tag bolted to the tuning capacitor frame.

The rotor tags of the ganged tuning capacitor are wired together and to 6BA tags under the heads of the fixing bolts. Other tags on the same bolts below the chassis provide earthing points for the oscillator coil padders and aerial coil holder.

Below Chassis

Components and wiring appear in Fig. 3. Leads to the coil holders, variable capacitors, padders and 12AH8 should be short and direct. Wires to VC1 and VC2 are clear of the chassis.

The 6.3V heater connections are against the chassis and away from other circuits. The mains transformer shown had a separate 6.3V winding for the rectifier heater but the 6X4 heater may be connected in parallel with other heaters if this winding is not available. To do this connect positive on C17 to pin 7 only and take pin 3 to chassis and pin 4 to the 6.3V line.

If the mains transformer has a 5V heater winding for a rectifier such as the 5V4, 5Y3 or 5Z4 it is quite in order to fit an octal holder for one of these and use it instead of the 6X4.

The two i.f. transformers have numbered pins which must be located as in Fig. 3. All points MC are tags bolted tightly to the chassis. A tag strip is used to anchor some of the components near the 6AT6. Leads to the volume control VR1 run against the chassis. Speaker connections can be made by fitting terminals (insulated from the chassis) or by employing a two-way socket strip. The aerial connector may be a coaxial socket, socket strip or terminal.

The mains lead should pass through a grommet and be well anchored. All the power-pack components are near the right runner (Fig. 3). Connections should be checked throughout before inserting the valves for a first test. A $2/3\Omega$ speaker in a cabinet or fixed to a baffle is necessary.

I.F. Circuits

These are aligned at about 465kc/s. This can be done by tuning in a weak station and rotating the cores with an insulated trimming tool for best volume. If the tuning indicator is fitted later this will prove to be an aid to exact alignment.

When adjusting the cores by ear it is necessary to remove the aerial or choose a weak signal so that the automatic volume control does not mask the effects of adjustments. No loss of efficiency arises if the transformers are aligned at some frequency which is not exactly 465kc/s.

If a signal generator is available its output can be used to check adjustment of the cores in the usual manner.

Aerial and Oscillator

Provided the aerial trimmer VC3 is not at the limit of its travel in either direction, aerial and oscillator circuits are sufficiently well aligned and good efficiency is obtained. But to avoid unnecessary adjustment of VC3 each band may be checked and the aerial or oscillator coil cores may be moved if needed.

First set the trimmer TC1 at about half capacity. The medium wave band is best checked first by inserting the appropriate blue and red coils. All coils have a pip which should lie between sockets 1 and 9 of the holders.

If a station around 1,400-1,500kc/s is tuned in, VC3 should peak reception quite sharply. Stations of lower frequency are then tuned in and the aerial coil core is rotated for best volume. This is continued up to about 600kc/s. If it proves necessary to close VC3 as frequency is reduced this shows that the aerial coil core is too far out. It should thus be screwed in. On the other hand, if VC3 has to be opened as frequency is reduced the core is too far in. When the cores are correctly positioned only occasional slight adjustment of VC3 is required throughout the waveband. *Exact* alignment throughout the band would mean that VC3 does not need adjusting at all and this is generally unobtainable. It is thus clear that having VC3 as a panel control allows maximum possible efficiency at all points of the scale and with any aerial.

Short wave ranges are treated in the same way as the medium wave band. If it is found that with the ganged tuning capacitor fully open VC3 has to be set to almost minimum capacity for best reception then TC1 should be screwed down slightly.

With the high frequency bands "images" will begin to become apparent. Such interference (also called "second channel") arises at twice the intermediate frequency from the required transmission, that is about 930kc/s from the wanted station. This is always so with a simple superhet on the high-frequency bands and it will be very much reduced when the tuned r.f. stage is added. Such interference will not be experienced on the lower frequencies.

Band coverage depends on the position of the coil cores, so can be modified if wanted until it approximately agrees with the ranges quoted. Some change in coverage will not influence actual results. When alignment with all coils is satisfactory, fix TC1 with sealing wax and place a 6BA locknut on each coil core stud. Dial readings can then be logged.

Tuning Indicator

The holder for the EM84 is bolted to a piece of scrap aluminium which can be attached to the front of the tuning capacitor. With the holder viewed from below connections are as in Fig. 9. It is most convenient to mount the 470k Ω resistor R1 directly on the holder. The 470k Ω resistor R2 is soldered to pin 4 of the first i.f. transformer. Four colour-coded flexible leads can then be taken

from the EM84 holder. They are twisted together and run through a hole in the chassis near the front of the tuning capacitor. The leads can then be taken to their appropriate points.

The indicator has a central shaded area which reduces its length when signal strength increases. So VC3 can be peaked at any frequency by rotating it to secure maximum length for the luminous areas or minimum shaded area.

The i.f.t. cores may be touched up by observing the indicator with a station tuned in. This allows much more accurate adjustment than possible by ear. Both cores of i.f.t.1 are tuned for minimum shadow. The top core of i.f.t.2 is similarly adjusted. However, the a.v.c. is not obtained from the secondary of i.f.t.2, so the lower core (diode winding) is adjusted for a small *fall* in the length of the luminous areas in the usual manner for this type of circuit.

The indicator allows netting of a transmitter with the receiver by tuning the transmitter v.f.o. and buffer stages for minimum shadow length.

I.F. Regeneration

This is easily provided by adding a 50k Ω potentiometer in the h.t. circuit to pin 6 of the 6BA6 as in Fig. 5. The potentiometer is mounted on the front runner with a control knob.

A piece of stiff wire about $\frac{3}{4}$ in. long is soldered

the transmission or c.w. morse will produce an audible beat. If this happens with the regeneration control only slightly above its zero position bend the wires forming capacitor C away from each other. Repeat if necessary until the heterodyne only appears when the 50k Ω potentiometer is well turned towards maximum (say half or three-quarters of its rotation).

If a weak station is tuned in, suffering from adjacent channel interference in a crowded band, it will be found that interference is reduced if regeneration in the i.f. amplifier is brought *nearly* to the oscillation point. For best results touch up i.f. alignment with the circuit in this state. Regeneration also increases the sensitivity to weak signals.

Standby and A.V.C.

An a.v.c. in/out switch is useful to render the i.f. stage independent of a.v.c. bias when operated in the regenerative state for c.w. or weak signals. Such a switch can merely short the a.v.c. line to chassis.

A standby switch which leaves the heaters running is also often convenient and especially when using the receiver with a transmitter. Both these functions can be arranged in a single two-pole, three-way switch wired as in Fig. 8. This switch is mounted on the front runner. It disconnects the h.t. circuit for "Standby", the 47k Ω resistors serving as a bleeder to discharge the smoothing capacitors.

R.F. Amplifier


The addition of the tuned r.f. stage increases range and selectivity and greatly reduces second channel interference on the h.f. bands. The lead from tag 2 of the 12AH8 is removed from tag 6 of the aerial coil. The extra coilholder and valveholder can then be added in the positions in Fig. 2.

Fig. 4 shows the circuit of the r.f. stage. The existing blue coils with VC1 are now used for the grid of the 6BA6. A.V.C. is taken from pin 4 of i.f.t.1 to the 1M Ω resistor. VC3 remains as the aerial trimmer connected as originally.

Tags of the yellow coilholder are wired as in Fig. 4 and the centre section of the ganged capacitor is used for tuning. To avoid any loss of efficiency or difficulty with ganging the yellow coils have their own 50pF trimmer mounted on the front runner and fitted with a knob.

The 6BA6 should have a screening can and a vertical aluminium screen runs between aerial and yellow coils from the ganged capacitor to the edge of the chassis. A 50k Ω potentiometer with knob acts as r.f. gain control.

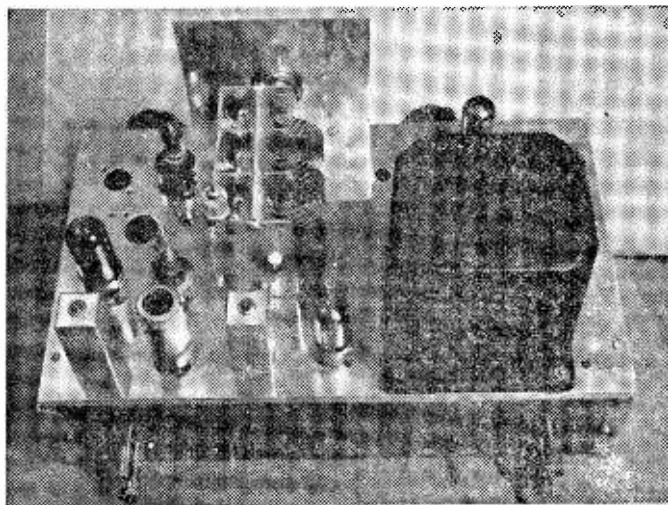The yellow coils are adjusted to gang with the blue aerial coils in the way already described.



Rear view of receiver built up to the basic 5-valve stage.

to tag 1 of the holder, standing vertically when the receiver is upside down. A similar wire is soldered to tag 5. These two wires form the small capacitor C (Fig. 5) and they are bent so that they are about $\frac{1}{4}$ in. apart.

A check should then be made by tuning in a weak transmission and advancing the regeneration control slowly from zero. When oscillation begins a heterodyne note will be heard on tuning through

Only occasional adjustment of the panel trimmers will be required to obtain maximum possible efficiency with weak transmissions.

With the r.f. stage added sensitivity is much higher and really long distance reception is possible. For many transmissions the r.f. gain can be set a little below maximum and left provided the a.v.c. is on. When the a.v.c. is off the 50k Ω potentiometer is rotated as necessary to adjust signal strength and avoid overloading.

It is convenient to place the new 50pF trimmer a little to the left of the ganged tuning capacitor when viewing the receiver from above and the front. The r.f. gain control can then be situated between the two 50pF trimmers.

Bandspreading

Bandspreading allows a narrow range of frequencies such as an amateur band to be tuned with a wide movement of the capacitor. Two methods have been tried. Both are successful, though they are rather different in character.

The simplest method is shown in Fig. 7 and has the bandspreading capacitor in parallel with the oscillator circuit only. The capacitor is 10pF or 15pF maximum value and has its own dial. If the two 50pF trimmers are peaked for best results, as shown by the tuning indicator with the bandspreading capacitor at half capacity, a narrow range of frequencies can be tuned effectively. If necessary the 50pF trimmers may be slightly readjusted so there is no loss of efficiency.

The method of bandspreading in Fig. 6 is easier to use as no readjustment of the trimmers is required. In terms of results or efficiency Fig. 7 is the same as Fig. 6. In Fig. 6 a three-gang bandspreading capacitor is used. It is possible to obtain miniature low-value capacitors or to gang individual capacitors with couplings but this is relatively expensive. After trying various arrange-

ments it was decided to use an ordinary three-gang capacitor from which most plates had been stripped.

The capacity required is about 25pF to 35pF per section. An equal number of plates must be removed from each section. The ganged capacitor used had fairly wide spacing and two rotor plates were left on each section the resultant capacity being nearly 25pF. An idea of the capacity to expect may be fairly easily obtained. To do this count the number of times the surface of a fixed plate is near the surface of a moving plate and divide the total capacity by this figure to get the capacity of a single fixed plate near a single moving plate; e.g., if the capacitor has 12 fixed plates and 11 moving plates there are 22 individual "capacitors", so the value of one with a 500pF gang is $500/22$ = about 23pF. If preferred alternative plates can be removed to obtain double spacing. This is more difficult and the capacity will have to be measured or found by trial.

The three-gang bandspreading capacitor is fixed near the main tuning capacitor and connected to it with short leads. It is most convenient to use a 0-100 or 0-180 dial on the main tuning control with a 6:1 or similar ball drive for bandspreading. With a 0-100 dial the amateur bands were located as follows:

Range 2. 1.9Mc/s, 70. 3.65Mc/s, 0.

Range 3. 7Mc/s, 71. 14Mc/s, 0.

Range 4. 14Mc/s, 60. 21Mc/s, 20. 28Mc/s, 0.

Range 1 is medium waves, and the 14Mc/s band may be tuned in on both Range 3 and Range 4. Exact readings will naturally depend on core and trimmer settings.

With the r.f. stage added, measurements were made of sensitivity and susceptibility to second channel interference on 21Mc/s. Sensitivity was slightly better than 2 μ V. The image ratio rejection was just over 18dB. Harmonic markers allowing exact calibration have been described in past issues.

PRACTICAL TELEVISION FEBRUARY

★ MEET THE SETMAKERS

The inside story of the men who design and produce domestic TVs.

★ OSCILLOSCOPE FROM TV CHASSIS

How to convert an old TV to a 'scope. Timebase covers 200 c/s—20 kc/s.

★ EFFECTS OF FAULTY CAPACITORS

First of a series on capacitors, resistors and chokes.

On Sale 20th January Price 2/-

SOMETHING FOR EVERYONE IN PRACTICAL ELECTRONICS

PORTABLE RATEMETER
COMPACT POWER UNIT
VIBRATO UNIT

plus


RADIO CONTROL OF MODELS

FEBRUARY ISSUE
On Sale January 13 Price 2/6

MEASUREMENTS WITH THE G.D.O.

.....
 a modified version of a
 previously described design
 and
 some notes for newcomers
 on the applications of the G.D.O.

K. L. SMITH, G3JIX

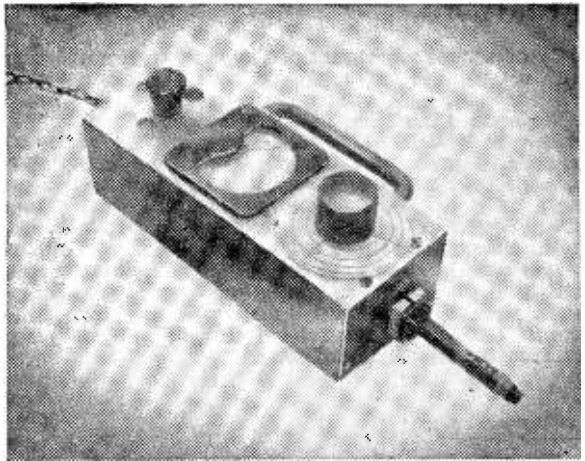

BEFORE discussing the main item of this article, modifications to the original GDO ("Grid Dip Oscillator", PRACTICAL WIRELESS, August, 1960, page 319) will be described showing how various difficulties of construction have been overcome. In this modified instrument the performance is slightly better. Many readers wrote saying that the coil pins were difficult to obtain and also that the split stator capacitor seemed to be a rare item. The following design is put forward to overcome these difficulties.

The oscillator circuit has been changed from the original Colpitts to a Hartley arrangement. This circuit requires a tap on the coils but only a single gang capacitor. The tap does not appear to add any difficulty because the new plug-in coil system makes available more pin connections. The circuit is shown in Fig. 1. The circuit action is similar to the earlier description except, of course, the feedback tap is into the inductance of the tuned circuit instead of into the capacitive arm.

A point which does require a little discussion is

the new method of controlling the amplitude of the signal" to the amplifier driving the meter. Instead of keeping the oscillator h.t. supply at the same value and tapping off the voltage from the grid leak by means of a variable control (VR1 in the original) the whole oscillator level is varied by altering the h.t. to it by the use of VR3. This enables the amplitude of the oscillations to be set to an optimum value on each range.

One reason why it was desirable to reduce the amplitude of the oscillations in this way, was that it was possible to light a loop lamp on some ranges—and this was considered to be more than adequate power in an instrument of this type (especially when checking aerials!).

CONSTRUCTION OF THE COILS

The coils are wound on the long (0.3in.) diameter formers usually found in the small square section cans on the chassis of television receivers. Old, obsolete sets are a very fruitful source of this type of component, although such coil formers

appear to be easily obtainable new at about 1s. each. The cores are not used but if experimental coils are wound then no reason exists why they should not be used to set on to a given frequency and then fixed, etc. The four small metal eyes in the base of the former through which the leads from the coil normally pass just about fit the corresponding four pins in an octal valve base. This therefore is a very convenient way of mounting a plug on the coil.

The remainder of the old valve base is sawn away carefully and filed up to make a neat job then fairly stout tinned copper wires are soldered into the coil former eyes and pulled through the four pins on the valve base. The wires are snipped off at the bottom of the valve base pins

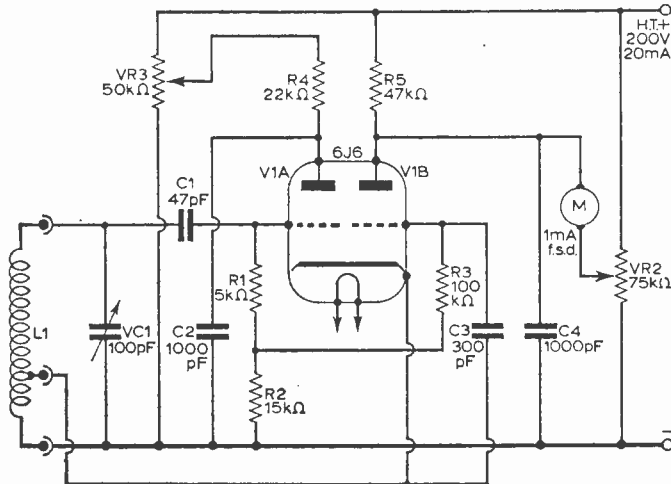


Fig. 1: Circuit of the redesigned G.D.O.

and neatly soldered into them (see Fig. 2 and Table 1). This method makes very good plug-in coils for all purposes, even when it is required to replace the can.

A standard octal socket is mounted on the "perspex" panel of the GDO in place of the original screw sockets. The appropriate tags of the socket are wired up to correspond with the coil connections. The actual pins used can be decided upon by the constructor but pin "6" is best avoided as it is missing more often than not as the writer found out! The ranges are calibrated using a receiver and/or other methods as described in the earlier article.

A good quality variable capacitor mounted in a box with a calibrated dial is a very useful piece of auxiliary gear to have in the radio workshop. It can be used to insert a known value of capacitance into r.f. circuits (using short leads, of course) and to measure the value of small

dial can be turned until the dip is again seen. Of course the setting of the GDO is not altered while the other adjustments are being made. It is seen that the reduction in capacity of the calibrated variable capacitor must be exactly the same as the added unknown value, which is now read off the dial.

Using a procedure similar to the above the variable capacitor can be calibrated. It is necessary, of course, to have a fixed capacitor of fairly accurately known capacitance (say 50' or 100pF $\pm 1\%$). The minimum capacitance point on the variable capacitor dial is assumed to be "zero", i.e. stray capacitance is assumed to be absent. With the dial at "zero" the known fixed capacitor is placed across the terminals and the GDO is tuned for a dip as described before. The fixed capacitor is now removed and the variable capacitor increased in capacity until the dip is obtained again. This point must be 50 or 100pF

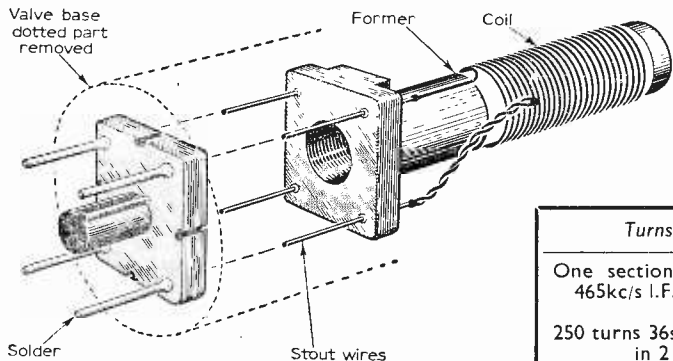


Fig. 2: Constructional details of the coils and winding information.

unknown capacitors. The photograph shows the general plan of such a component and the constructor could no doubt build up the device to his own requirements. No extensive description will be given here. Suffice it to say that a capacitor with semicircular plates—that is, one whose capacity varies regularly with rotation—is most convenient because it enables a linear scale to be used.

The matter of calibration is best carried out using a capacity bridge. Perhaps a local radio service station or the engineering department of a technical college will have such a bridge. Failing the availability of a bridge, the capacitor can be calibrated by using a technique very similar but used in reverse to the method of measuring the value of unknown capacitance described below.

Assume the capacitor is calibrated, and has an inductance placed across it thus forming a parallel tuned circuit. The value of the inductance does not matter as long as it resonates with the capacitor at a frequency convenient for one of the ranges of the GDO (around 1 to 2Mc/s is satisfactory). Place the variable capacitor dial at maximum capacity and couple the GDO to the inductance. Tune the GDO for a dip, keeping the coupling as loose as possible. If a small capacitor is now placed across the terminals the resonant frequency is altered and the calibrated capacitor

TABLE I

Turns	Range
One section of a 465kc/s I.F. winding	I.F. Band
250 turns 36s.w.g., in 2 layers	Medium waves
150 turns 36s.w.g., in 2 layers	1-4 to 2.7Mc/s
75 turns 36s.w.g. 25 turns 28s.w.g.	2.7 to 9Mc/s 8-5 to 30Mc/s
2 turns self-supporting $\frac{1}{2}$ in. diam	30 to 100Mc/s
$\frac{1}{2}$ turn loop, $\frac{1}{2}$ in. diam.	85 to 160Mc/s? (according to construction)

All tapped at half-way point

according to the fixed capacitor size. Leaving the dial at this position the fixed capacitor is added again and the GDO returned. The capacitor is removed, the variable again increased, giving another 50 or 100pF interval. This is repeated over the whole dial.

Naturally any errors introduced tend to add up using this method and a good plan would be to have another accurately known fixed capacitor whose value was different and to use this to check the appropriate points on the dial.

GENERAL USE OF GDOs

One finds two general methods employed to couple the GDO to external circuits. On the one hand, the magnetic field can be linked directly

with the circuit or via a loop system (see Figs. 3a and b). On the other, the coupling can be electric via capacity, stray or otherwise (Fig. 3c). In both cases overcoupling will detune the GDO and inaccurate readings obtained. Therefore whenever the instrument is used the final reading should be taken with the coupling loosened as much as possible consistent with seeing the dip. This requirement for small coupling means that the GDO should be removed as far as possible from the circuit being investigated.

If a number of tuned circuits are clustered together then the field of the GDO may link with more than one of them and a confusion of dips obtained. It is necessary to couple close to the required tuned circuit and gradually "follow the dip" as the GDO is removed. It should be moved to give minimum coupling with the other circuits. By the way, to tell whether the GDO is oscillating it is only necessary to take hold of the coil and at the same time notice the meter. Also if there is doubt concerning the dip this can be resolved by tuning the GDO over the range away from any resonant circuits, etc. If the tuned circuit being tested is inaccessible then the extension link can be used, but its own resonance dip should be determined before using it.

The above deals with the general use of the instrument to check resonances in receiver tuned

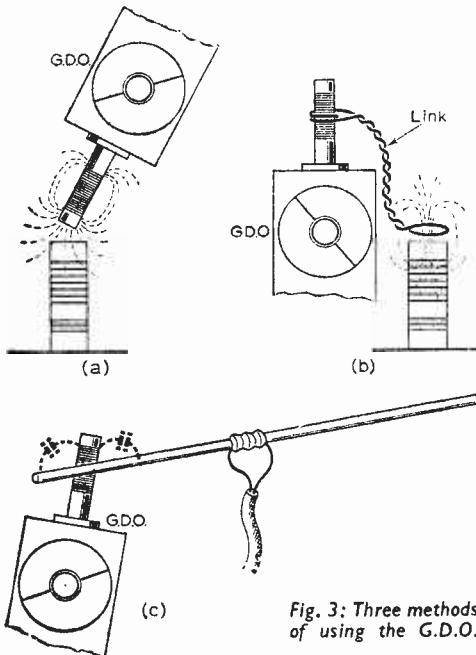


Fig. 3: Three methods of using the G.D.O.

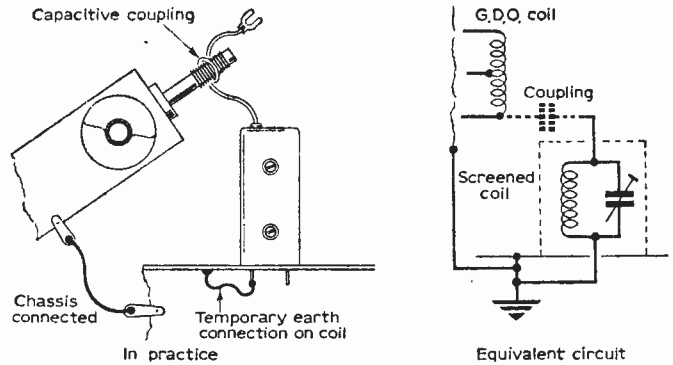


Fig. 4: Checking an i.f.t. using the G.D.O.

circuits transmitter tank circuits and especially when "pruning" v.h.f. tuned circuits in 2m converters or television tuners, etc.

The GDO can be used to check aerial resonances. If a voltage point is thought to exist at the point of testing then the "hot" end of the coil should be brought near for maximum electric coupling (Fig. 3c). If, on the other hand, a low-impedance point is expected the GDO coil should be placed to give magnetic coupling—a loop can be made in the wire and the GDO coupled to that. Checks on aerials should be made as quickly as possible with loose coupling to avoid the possibility of radiating strong interference.

Sometimes it is required to check an i.f. transformer or a coil inside a screening can. This precludes the direct coil-to-coil coupling normally used, but the writer successfully measured the resonant frequency of such a unit by using electric coupling into the "hot" side of the winding as shown in Fig. 4.

When checking aerials in position outside it is much more convenient to use a battery or some other portable supply to cut out the trailing power leads. The problem can be nicely overcome by using a transistor oscillator (M. R. Lord, "Transistorised Grid Dip Oscillator", PRACTICAL WIRELESS, March, 1962, page 1033). Although a transistor "dipper" (there is difficulty in justifying the word grid!) cannot be made to oscillate up to 2m and ITV frequencies (without expensive high-frequency transistors) the v.h.f. types such as the AF712 will oscillate up to 150Mc/s all right.

The GDO can be used as a signal generator. The tracking and trimming of a superhet can be roughly carried out before power is put on, using the GDO in the normal way, then if it is stood aside still oscillating it will produce a note for the final trim-up when the receiver power is switched on. Modulation has been applied in the ordinary way quite successfully, that is by applying the audio in series with the h.t.

Use As Absorption Wavemeter

With VR3 wiper placed at earth the oscillator stops as already noted. The instrument is now coupled near an energised tuned circuit such as a

—continued on page 875

Insensitivity in Transistors

diagnosis and cures

DIAGNOSING cases of low sensitivity or power is always more difficult than tracing causes of complete breakdown, particularly in transistor radios, where a succession of small defects instead of one clear-cut fault may be found and where even small voltage variations are indicative of possible trouble. However, in practice probably the first thing to do (after checking battery voltage on load) is to note if the insensitivity is confined to one band, if it increases towards one end and if it is also accompanied by any distortion.

If the alignment does not appear to have been tampered with, variation of gain with wavelength often indicates a faulty frequency changer or oscillator, while poor gain and distortion usually indicate incorrect emitter bias on an i.f. or audio transistor. However, before actually getting down to meter testing, check that there are no cracks in the ferrite rod aerial and that none of the aerial coils has become displaced.

The first meter tests undoubtedly should be to determine the voltage developed across the emitter resistor of each transistor, working back from the output stage. Any variation greater than 20%

by G. R. Wilding

from the maker's figures should give cause for suspicion and merit a careful check on the two other transistor voltages. Incorrect emitter voltage does not, of course, indicate a fault in the emitter wiring such as a leaky or s/c bypass capacitor as the wrong emitter p.d. could well be caused by incorrect base voltage produced in turn by changed value or dry-jointed bias resistors. However, wrong value emitter voltage always indicates that the stage is not working properly and so pinpoints the area for especial consideration.

Assuming that all voltages checked are within the limits, what then? Obviously all the transistors and current carrying resistors are normal, so the fault or faults lie in those components associated only with the signal, r.f. or a.f., and not with the d.c. supplies, which means in practice the coupling, decoupling and fixed trimmer capacitors, the i.f. and audio transformers.


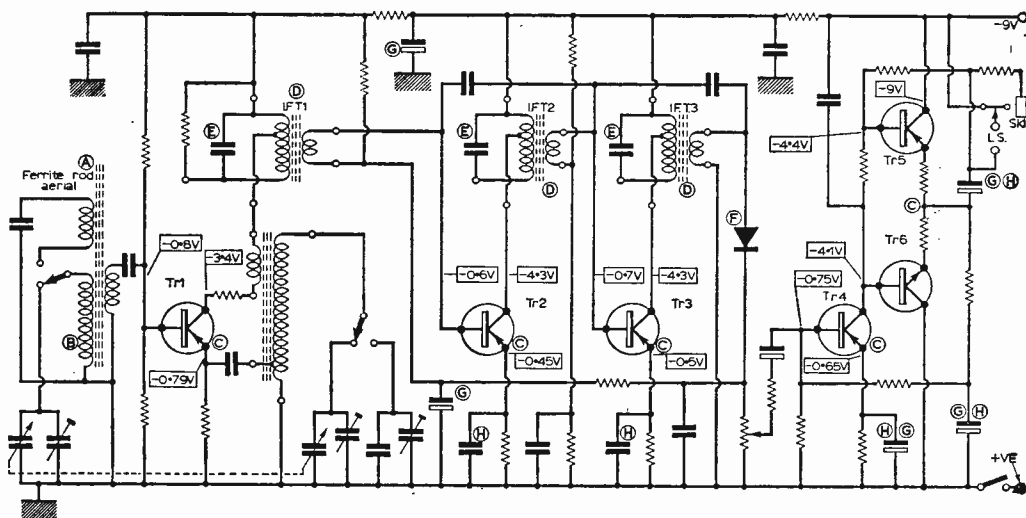


Fig. 1: Typical transistor portable (Ekco PT399), showing points to check when investigating lack of gain.

- A CRACKED FERRITE AERIAL ROD
- B DISPLACED AERIAL COILS
- C INCORRECT EMITTER VOLTAGES
- D O/C i.f. TRANSFORMER WINDINGS OR SHORT CIRCUITED TURNS ON TRANSFORMERS

- E REDUCED CAPACITY FIXED i.f. CAPACITORS
- F DEFECTIVE DIODE DETECTOR
- G REDUCED CAPACITY ELECTROLYTICS
- H O/C OR DRY JOINTED BYPASS CAPACITORS

Fig. 2: Inexpensive signal tracer with probe; a two-stage R-C coupled amplifier operating from miniature 4.5V battery and requiring the minimum of components. RV4 sets the operating level of Tr2 (3mA)—courtesy Mullard Ltd.

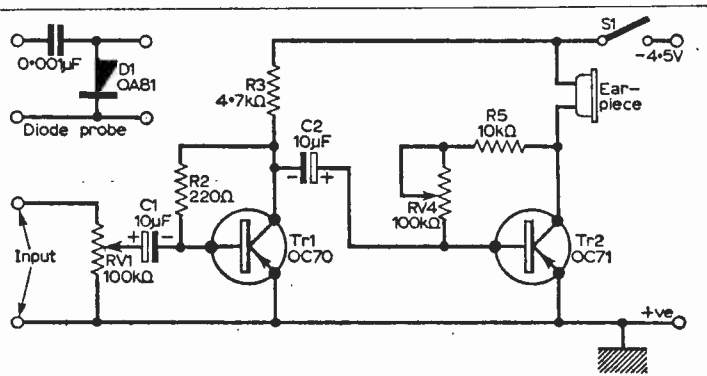

For instance the secondary of a transformer feeding both the base voltage and the signal to a transistor could have many shorted turns, thus greatly loading the stage and decreasing gain without producing any effect on the voltages of the transistor. Similarly the miniature high-value electrolytics, if of reduced or even negligible capacity, produce no noticeable effect on rated test point voltages unless, of course, they instigated self-oscillation or motor-boating.

A short-circuited or leaky capacitor, depending on its position in the circuit, would almost certainly influence some transistor voltage but in practice, due to the very low voltages employed, develop mainly a loss in capacity. The simplest way of checking this possibility is, of course, to add a known good equivalent across the suspect and note results, but where it is feasible that some deterioration may have occurred inside the capacity, due to the ingress of moisture or salt water, it may be advantageous to simply replace it as any slight leak present would still be in circuit when the replacement was added.

If after checking or replacing all relevant capacitors and finding gain still below normal it may well pay to check the d.c. resistances of the various transformer windings. Although this is a useful test it is by no means conclusive, since perfect transformer windings may have a d.c. resistance substantially different to that of the maker's figure, so that short-circuits involving only a few turns will not show up. However, the test does show up gross variations from normal and, of course, completely o/c windings.

Most i.f. transformers in transistor radios feed the following stage from a tapping on the secondary so that it is very possible for a complete break in the secondary winding not to show up on the transistor voltage tests, since the break may not be in the section carrying the d.c. base current.

Similarly if the primary is tapped a break could well develop in the section not carrying the collector current from the preceding transistor and here again would produce no voltage indication on that transistor.

It should be mentioned at this stage that breaks in such transformer windings very frequently develop if the set has been dropped and usually where the fine leading-out wire joins the exterior soldering tag. While therefore one cannot be

dogmatic about interpreting variations in measured to stipulated d.c. resistance when checking push-pull audio transformers, whatever their value, the main point is that both halves should be really close.


Capacitors often overlooked in practice are those fixed i.f. trimmers shunted across the primary and secondary transformer windings and usually mounted inside the i.f. can. Often about 250pF in value and with only a 2% tolerance any small reduction in their capacity drastically reduces gain by mistuning the stage to a higher i.f. frequency. When tracing insensitivity such capacitors would not be o/c but only partially deficient, so that a quick test is to add a small value picofarad capacitor across each suspect and note if gain increases. Values of 10 to 25pF should be ample to show up any loss of capacity without at the same time running into the danger of over-correcting by mistuning to a lower than specified i.f. If such action increases volume and the receiver is a normal peak-tuned model it can be taken as certain that the fixed trimmer under test is defective, always assuming, of course, that the i.f. slugs are still sealed. If the slugs have been readjusted this test would more likely indicate that a realignment was necessary.

Of course all such tests are static and very often the dynamic method of fault location, either by injecting a suitable r.f. or a.f. signal into each stage or by means of a signal tracer and probe determining just where the signal loses ground, is more to be preferred. Such a signal tracer, easily constructed and designed by Mullard Ltd., is shown in Fig. 2. Employing only five resistors, two capacitors, an earpiece and two transistors, types OC70 and OC71, this device can prove very helpful indeed when tracking faults in transistor sets.

To trace h.f. and i.f. signals the simple diode probe inset can be switched into the front end. When constructing the probe everything must be concentrated on keeping its self-capacity and hand-capacity to the absolute minimum so that it will have no appreciable effect when applied to the various tuned circuits.

Finally, don't overlook the possibility of the receiver's diode detector being faulty and, if complete realignment is called for, follow the maker's instructions. ■

CODAR — QUALITY

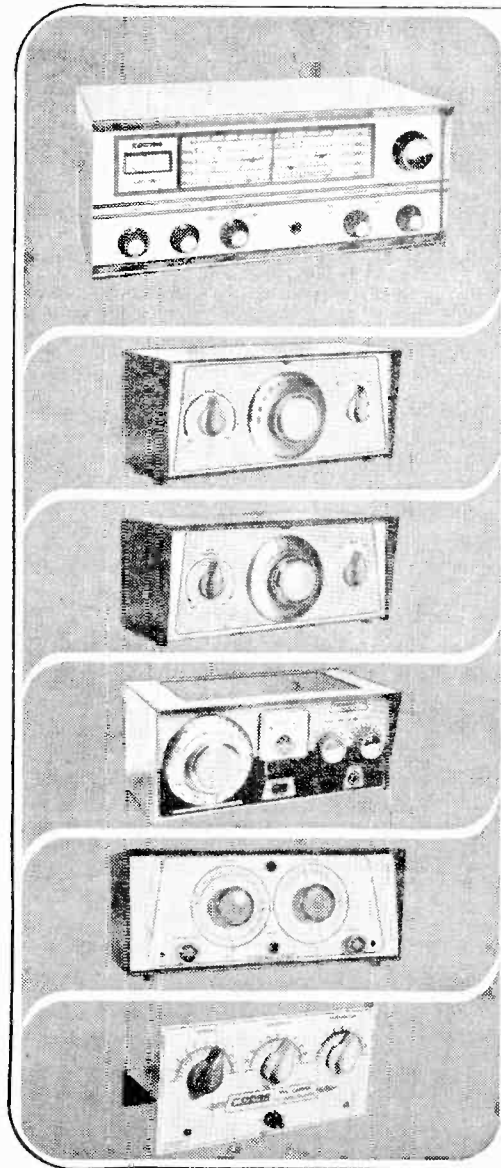

ANOTHER CODAR TRIUMPH!

THE NEW 1966 CR.70A COMMUNICATION RECEIVER

This completely new receiver sets a new high standard for performance and finish unequalled at the price, and is a worthy addition to the outstanding range of CODAR quality communication equipment. Frequency range: 561 Kc/s-30 Mc/s (510-10 metres) in four ranges: 560 Kc/s-1.5 Mc/s; 1.5 Mc/s-4.2 Mc/s; 4.2 Mc/s-11.5 Mc/s; 11.5 Mc/s-30 Mc/s. Slide rule scales for each band calibrated in frequencies plus an additional logging scale in degrees. Two speed vernier tuning control with reverse slow tune action. Unique aerial input stage exclusive to the CR.70A employing High Q Air-spaced (011A)-001L Inductor giving extremely high gain with low noise level. Panel aerial trimmer for peaking weak signals. Double tuned I.F. Iron cored transformers. 470 Kc/s with EF183 frame grid valve (or maximum gain and selectivity. 5 valves (including two twin triodes) giving 7 valve line-up. Separate B.F.O. stage for CW and SSB reception. Calibrated signal strength 'S' meter, illuminated. Automatic Volume control. Panel phone jack for "private" listening. 2-3 ohm output for external speaker. Superstyling, metal cabinet in the new Organazol Satin lustre finish. Size 13" x 5 1/2" x 7". For A.C. 200/250 v. Ready built. Not a Kit at the fantastic low price of £19.10.0. Carr. 7/6.

CODAR B.F. PRE-SELECTOR MODEL P.R.30. Considerably improves the performance of any superhet receiver over 1.5-30Mc/s. Uses EF183 Frame Grid Valve and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12mA H.T. 6.3 volts, 0.3 amp L.T. Size 8 1/2" x 5 1/2" x 4in. Ready built, complete with cables, plugs and instructions. £5.10.0. Carr. 3/6. **MODEL P.R.30X.** Self powered model for 200-250v. A.C. Also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £7.4.0. Carr. 3/6.

CODAR "Q" MULTIPLIER MODEL R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW, or SSB. B.F.O. Size 8 1/2" x 5 1/2" x 4in. Power requirements 180-250v. H.T. at 5mA 6.3v.0.3 amp L.T. Ready built complete with cables, plugs and instructions. £6.15.0. Carr. 3/6. **MODEL R.Q.10X.** Self powered version for 200-250v. A.C. and also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £8.8.0. Carriage 3/6.

CODAR A.T.5. 12 WATT 2 BAND TRANSMITTER. The newest most compact transmitter for fixed or mobile use on 160-80 metres. "The tiny TX with the BIG voice". Size only 8 1/2" x 5 x 4in. (Base area is less than two-thirds of this page!) High stability new type calibrated VFO. 1.6-2 Mc/s and 3.5-3.8 Mc/s (up to 1 Mc/s export). Air-spaced CODAR COIL Pi-net output. P.A. Plate current meter plus neon indicator. Plate Screen modulator. AM/CW switch and Panel key jack. Plug changeover for 6 or 12 volts heater supply. Ready built £18.10.0. Carr. 4/-. A.L.S. **POWER SUPPLY UNITS.** For 200/250v. A.C. and 12v. Sold state for Mobile use. Complete with all Transmitter/Receiver changeover switching available.

CODAR-KIT CR.45K MAINS I.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandspread. ★ 3 slow motion vernier dials. ★ Low loss polystyrene plug-in coils. Rotary aligned. ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2/3 ohm speaker. ★ Valve line-up: ECC81, EL84, EZ80. Size 12 x 5 1/2 x 7in. **CODAR-KIT CR.45K** complete with valves, 3 coils (10-28, 25-75, 60-175 metres) and 11 page instruction manual. £9.10.0. Carr. 5/6. Extra coils 4/9 each. Instruction manual only 2/- (credited on order). (Can also be supplied ready built—price on request).

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER. ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4-page instruction manual. PRICE 39/6. Carr. 3/-. Extra Coils 4/9 each. Instruction Manual only 2/- (credited on order). Electrical Bandspread available. Provision to add 2 transistor amplifier.


SEND 6d. IN STAMP FOR ILLUS. LEAFLETS OF THE CODAR RANGE • H.P. TERMS AVAILABLE • WORLD-WIDE MAIL ORDER SERVICE



CODAR RADIO COMPANY
 BANK HOUSE, SOUTHWICK SQUARE
 SOUTHWICK, SUSSEX. Tel. 3149
 G3JRE G3HGQ

Canada: Codar Radio of Canada, Tweed, Ontario.

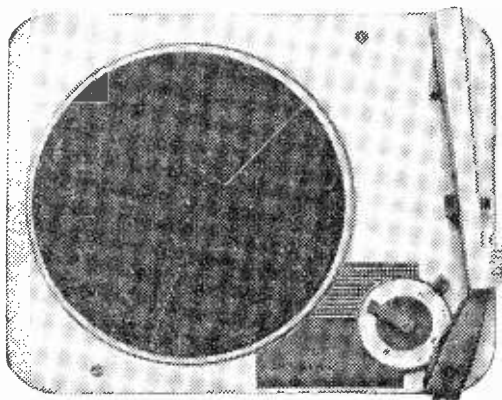An integrated hi-fi turntable unit from only 11 gns?



YES!

Only Goldring's 60 years of experience of making gramophone turntables and pick-ups could lead to a unit like this . . . the ideal integrated turntable, arm and pick-up for do-it-yourself hi-fi aspirants . . . at such a modest price. Just look at the features of this remarkable G.66 unit:

Silent, specially made Swiss mains motor. Pressed steel turntable on precision bearings evens out mains current fluctuations. Die-cast light alloy arm with full stylus pressure adjustment. Plug-in head shell, wired for mono and stereo, takes alternative pick-up cartridges. Eddy-current speed control (as fitted on some professional units) varies the four standard speeds by $\pm 10\%$. Pick-up raising/lowering device coupled to on/off switch and idler-wheel disengagement mechanism. Deck size $12\frac{1}{2}'' \times 10''$.

See the Goldring G.66 at your dealers—or write for descriptive leaflet.

THE GOLDRING G.66

G.66/MX.2 £9.18. 8 + £1.12.4 P.T. £11.11.0
G.66/CS.80 £10.10. 0 + £1.14.2 P.T. £12. 4.2
G.66/CS.90 £12.12.10 + £2. 1.2 P.T. £14.14.0



Goldring Manufacturing Co. (GB) Ltd.,
486-488 High Road, Leytonstone, London E.11
Telephone: Leytonstone 8343

Make Your Ability PAY

UNLIMITED OPPORTUNITIES exist today for "getting on" . . . but only for the fully trained man. Let ICS's tuition develop your talents and help you to success.

STUDY IS EASY with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. **MODERATE FEES INCLUDE ALL BOOKS.**

Take the right course now . . .

ADVERTISING & ART
Copywriting Cartooning
Layout and Typography
Commercial Illustrating
Oil and Water Colour
BUILDING & CIVIL ENG'NG
Architecture, Bricklaying
Building Construction
Builders' Draughtsmen
Builders' Quantities
Interior Decoration
Quantity Surveying
Heating & Ventilation
Carpentry & Joinery

COMMERCE
Book-keeping
Accountancy & Costing
Business Training
Office Training
Purchasing, Storekeeping
Secretariats
Shorthand & Typing
Computer Programming
Small Business Owners

DRAUGHTSMANSHIP
Architectural, Mechanical
Drawing Office Practice

ELECTRONICS
Computers
Electronic Techniques
Industrial Electronics

FARMING
Arable & Livestock
Pig & Poultry Keeping
Farm Management & Accounts

GENERAL EDUCATION
G.C.E. subject at Ordinary and
Advanced Level
Good English
Foreign Languages

HORTICULTURE
Home Gardening
Park Gardening
Market Gardening
MANAGEMENT
Business Management
Hotel Management
Industrial Management
Office Management
Personnel Management
Public Relations (P.R.)
Transport Management
Works Management
Work Study
Foremanship

MECHANICAL & MOTOR ENG'NG
Engineering Maths
Diesel Engines Welding
Industrial Instrumentation
Workshop Practice
Refrigeration
Motor Mechanics, etc.

POLICE
Entrance Examination
Police Promotion (Educ. Subj.)

PHOTOGRAPHY
Practical Photography

RADIO TV & ELECTRICAL
Servicing & Engineering
Radio Construction (with Kits)
P.M.T. Certificates
Telecommunications
Electricians'

Electrical Contractors'
SELLING
Company Reps.
Sales Management

Marketing
WRITING FOR PROFIT
Television Scriptwriting
Short-story Writing
Freelance Journalism

INTENSIVE COACHING for all principal examinations
—G.C.E., Secretaryship, Accountancy, Engineering,
Work Study, Management, Radio, Architecture and
Surveying. Special course for G.C.E. French Oral Test.

Member of the Association of British Correspondence Colleges

Start today the I.C.S. way!

INTERNATIONAL CORRESPONDENCE SCHOOLS
(Dept. 172)
Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on.....

Name.....


Address.....

Occupation.....

2.66

INTERNATIONAL CORRESPONDENCE SCHOOLS

? ?

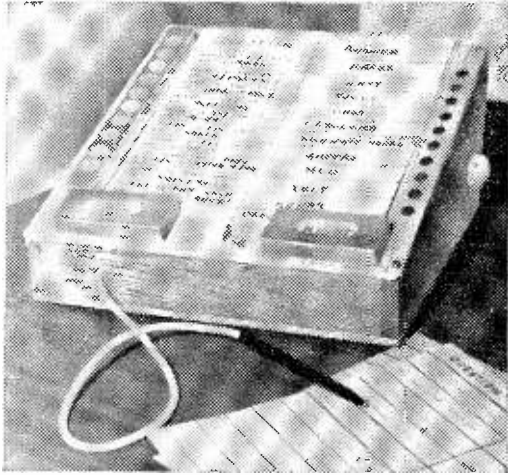

An Educational QUIZ MACHINE

||| A NOVEL PROJECT FOR
||| EXPERIMENTERS, CLUBS
||| AND SCHOOLS |||

by Michael J. Hughes M.A.

THERE has for some time now been a group of electrical educational toys on the market. One of these is that shown in Fig. 1. It consists of a card with a set of questions all of a similar nature on the left-hand side. For every question there is an answer on the right-hand side of the card but not necessarily in the correct place. Alongside each question and answer is a small electrical contact such as a piece of aluminium foil. These contacts are wired under the card so the contact representing a given question is connected to the one alongside the correct answer. The idea of the game is for the child to select a question in the left hand column and place a probe on the contact. The child then selects what it thinks is the correct answer and places a second probe on the answer contact. There will be a battery and a lamp or buzzer in series with the two probes and if the correct answer is chosen the circuit is completed, thus indicating on the lamp or buzzer.

Some time ago the writer had occasion to make one of the above devices and in doing so found out that some of its obvious faults were:

- (1) Difficulty in handling two probes.
- (2) Lack of facilities to change programmes.
- (3) The ease with which the correct answer can be found by a process of "trial and error", i.e. by sliding the answer probe down the answer contacts until the answer is indicated.
- (4) The fact that recognition is only made of a correct answer and no indication is made of errors.

It was with these points in mind that the following instrument was designed. On the face of it this instrument gives the same results but it is much more sophisticated in design and, apart from forming the basis of a useful teaching machine, involves some quite interesting relay circuitry.

The circuitry requires 12 relays which may be of any type provided they have four double-throw contacts, 10 diodes capable of passing the holding current of the relays and having a reverse breakdown voltage greater than the voltage required to power the relays. In the instrument to be described indications were made with 6.3V bulbs and 13 of these will be required, together with suitable holders. Apart from the above components, most of which may be obtained cheaply from ex-Government stores, all that is required is a plentiful supply of connecting wire and patience as a considerable amount of wiring is involved.

Relay Circuitry

As a number of readers may not be fully aware of the way relay circuits are drawn a brief description of the notation used will follow.

One of the beauties of relays in application but also one of their drawbacks when drawing circuit details is the fact that the contacts of a particular relay coil are electrically completely independent of the controlling circuit, i.e. there can be no leakage or breakthrough between the controlling circuit and the controlled circuit. In a simple circuit such as an electronic timer, which has

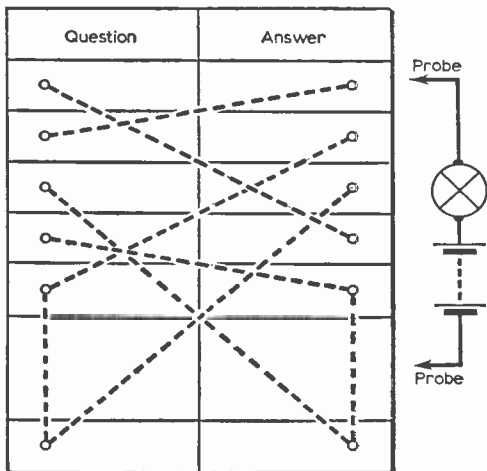


Fig. 1: Question and Answer board.

appeared many times in this magazine, the emphasis is in the control circuitry and the controlled half is usually left to the imagination of the reader. In the example quoted the controlled circuit may only be a simple make or break switch in series with an enlarging lamp. In a simple circuit it is easy to show the contacts in close proximity to the operating coil as shown in Fig. 2.

If, however, the same relay was to drive a more complex circuit, for example one which required four double-throw contacts, a total of 12 separate contacts would have to be drawn; this by itself might not seem a very great problem. However, if one continues this reasoning further to cover a circuit which includes a large number of relays and also a lot of the controlled circuitry the theoretical circuit would sooner or later start to resemble the Hampton Court maze.

To prevent this happening a standard form of circuit is drawn with the relay coil forming part of the control circuit and the contacts are drawn completely separate in their correct positions in the controlled circuit; it only remains to identify each set of contacts with their controlling relay coil. There are various ways of doing this and the notation in this article is to label the controlling relays RLA, RLB or RLC, etc. The contacts controlled by relay RLA are numbered A/1, A/2, A/3, etc. If the contacts are double throw they are designated A/1a, A/1b, A/2a, A/2b, etc. This type of notation coupled with the fact that normally closed contacts are shown completely black and normally open ones are left white (see Fig. 3) gives a much clearer representation of the circuit.

Operation of the Instrument

Before any attempt is made to describe the circuitry, it will be best to acquaint the reader with the external appearance of the instrument, and the way in which it would be used.

The front panel consists of a board, on which a set of questions and answers may be rested in accurate location with a series of 10 contacts down each side of the question sheet. Each question sheet is given a "programme number" which corresponds to a position on the programme

switch (this varies the order of the answers) which is on the side of the instrument.

To operate the instrument, the child selects himself a question from the left hand column. He does this by touching a probe on the respective contact. Immediately he does this, a lamp will light alongside that particular question. It is now impossible for the child to change the question asked without answering it, or resetting the instrument. If he tries to probe another question nothing will happen.

The child must next decide which answer he thinks is the correct one; he then touches the same probe on the contact next to that answer. If correct, a lamp will light up indicating "Right", but if the incorrect answer is chosen, a second light will indicate "Wrong". It is impossible for the child to have second thoughts and try a second answer until he has reset the instrument, and started again. This discourages the "Trial and Error" method as described for the simple toy. Most of the complexity of the circuit is due to the fact that the machine is both cheat proof, and fool proof to operate.

The Circuit

The diagram is shown in Fig. 4 There are several distinct sections to the circuit, these are:

- (1) The main control circuit.
- (2) The question illumination circuit.
- (3) The "Right" "Wrong" illumination circuit.
- (4) The "Reset" illumination circuit.

The method of indicating right or wrong is entirely up to the reader, it may be by illumination, as in the prototype, or by a bell and buzzer system. Likewise the reset warning light, which may be omitted altogether, if desired.

To ask a question, the probe is placed on one of the contacts connected to diodes D1—D10. The negative power line is coupled via the normally closed contacts A/4a to J/4a (which are all connected in series) to the probe. One end of each of the relay coils RLA—RLJ is connected to the positive line, therefore when the probe is placed on any of the question contacts, the respective diode is forward biased, and conducts, passing a current sufficient to energise that particular relay coil. As an example, assume the probe is placed on question contact 3, D3 conducts, and RLC is energised, the action due to the energising of RLC is to close the contacts C/1 which then applies the negative line immediately to the coil, when the probe is removed, the relay holds in. The relay is now "self-locked". C/3 closes lighting the lamp referring to that question. Simultaneously the change over contact C/4a is opened, thus breaking the negative supply to the probe, and C/4b is closed, which applies the positive line to the probe. C/2a, which keeps the potential at contact 3 in the answer column normally negative opens, and C/2b closes, connecting number 3 contact via contact W/2 to the energising coil RLR, which if operated in the process of answering will operate the "Right" lamp. It should be noticed at this stage that all the other answer contacts are connected via R/2 and RLW to the negative line.

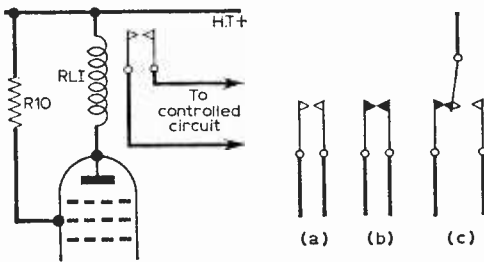


Fig. 2 (left): Part of electronic timer circuit.

Fig. 3 (right): (a) normally open contacts. (b) normally closed contacts. (c) changeover contacts.

If the probe, which is now negative is placed on the correct answer, RLR will be energised, closing R/1 which locks the relay in, it also opens R/2 which breaks the circuit to all the other possible answers, thus preventing a second choice without resetting. The right answer is displayed by contact R/3 closing, thus lighting the lamp. If the

wrong answer is chosen, i.e. any contact other than 3 is touched, current flows through R/2 and energises RLW which locks in with W/1, and kills the possibility of selecting the right answer by opening W/2, it also closes W/3 which illuminates "Wrong".

After an attempt to answer the question whether

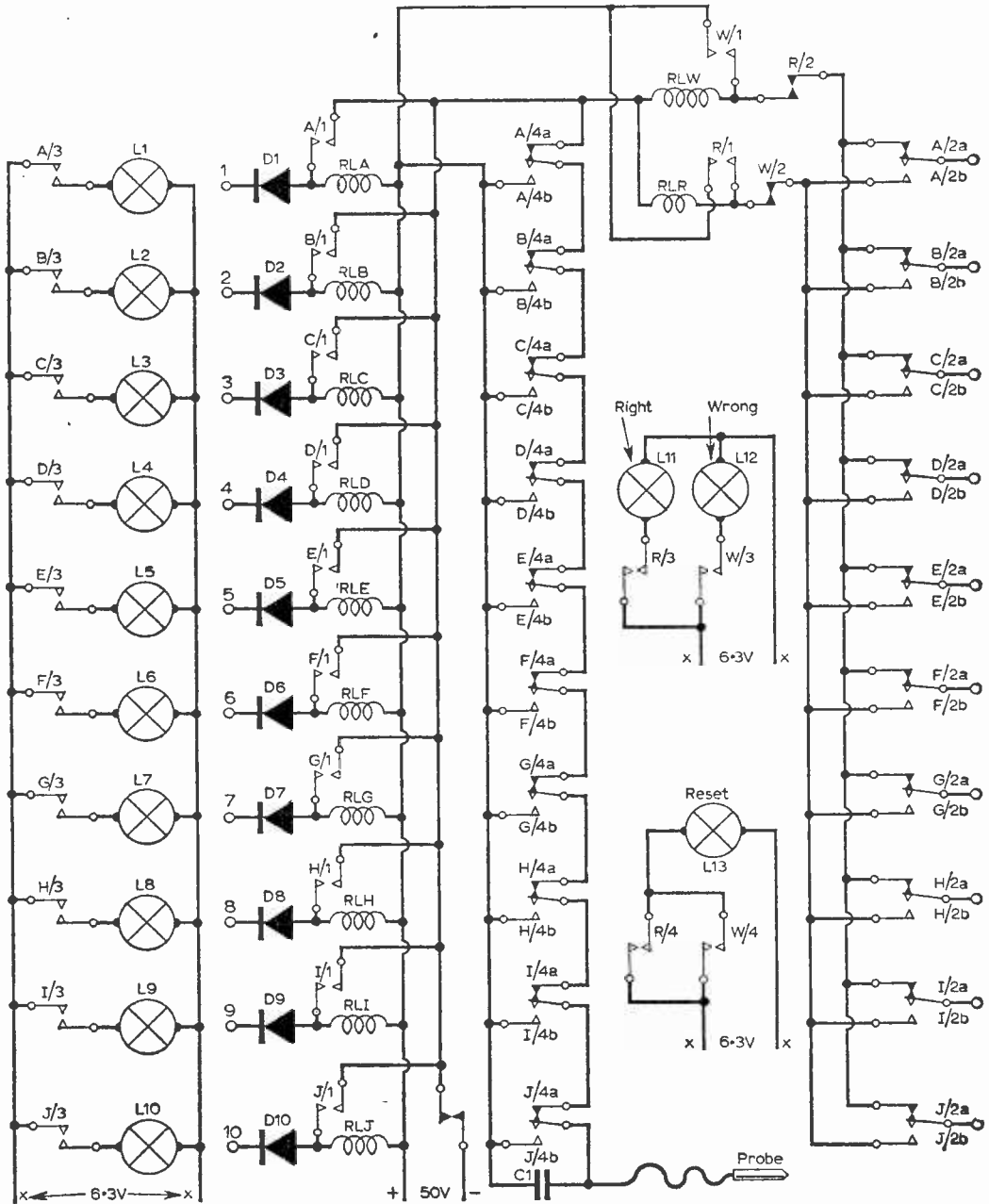


Fig. 4: Circuit diagram of the quiz machine.

right or wrong, the instrument must be reset. It was thought desirable to display a reminder of this, and this was readily done by using contacts R/4 and W/4. If either RLW, or RLR is operated, the reset lamp will light.

To reset the instrument, it is necessary merely to momentarily break the power supply to all the locked relays, this is most easily done by pressing the push button S1, situated in the main power line.

It should now be pointed out that if the probe is placed on any answer contact without asking a question, nothing will happen, as the probe which is initially negative is at a common potential with all the answer contacts. The polarity of the probe is changed only on asking a question. Likewise, when a question is asked, the probe is made positive, and if placed on any other question, will not operate any other relay because the diodes will be reverse biased.

Because of this change over of polarity of the probe, there is a danger that one of the relays may begin to oscillate at its natural mechanical frequency, in much the same way as a buzzer. It is therefore necessary to prevent this happening, and to do this, a capacitor of about $1\mu\text{F}$ must be wired between the probe, and one of the supply lines. This capacitor is shown as C1.

For the sake of simplicity in drawing, and explaining the various functions, the answer contacts have been shown in the same position as their respective questions. There is no reason why the positions should not be jumbled up in any random order. The writer gives a word of warning here, and recommends colour coded wiring for the answer contacts, as he himself forgot which contacts were connected to which relay. This was also complicated by the programme switch which is described later in this article. It is therefore necessary to use as clear a layout as

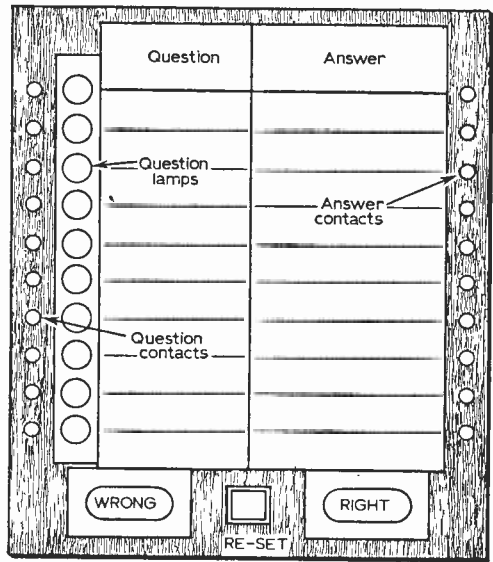


Fig. 6: Front panel layout.

possible, and use labels on the ends of the respective wires, so that there is no chance of an error when wiring up.

Constructional Details

Most of the intricate wiring is between the contacts of the relays and for this reason it is suggested that either a small chassis be made to hold the relays, or that some of the modern miniature plug-in-relay be used. The latter were used in the prototype, so it was possible to strap all the sockets together on two bars, thus forming a compact unit. Layout is not at all critical as all the circuits are low impedance operating on d.c., however it is suggested that a neat symmetrical system is used, as this will greatly simplify the wiring.

The two relay banks are screwed to the base-board, the programme switch is bolted to one of the sides, and the "Reset" button to the front.

The sloping front panel holds the two rows of contacts, and the indicator lamps. The wiring from these are terminated at two long tag strips which are connected in turn to the relay banks by bundles of colour coded flexible wire. The sloping panel is hinged to the main cabinet, and the bundles of coupling wires should be long enough to prevent any strain on the soldered connections when the panel is opened.

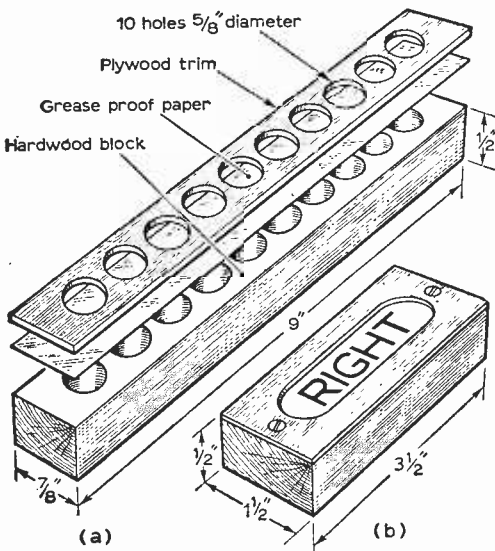


Fig. 5: Method of making the lamp covers.

COMPONENTS LIST

- 12 Relays and Sockets 4 contact with 50 volt coil. (Woden Transformer Co. Ltd., Moxley Road, Bilston, Staffs.)
- 1 Illuminated Key switch. (T.M.C., Martell Road, West Dulwich, London, S.E.21.)
- 10 Diodes Ferranti type 10AS (or similar).
- 1 Switch 4 bank 3-pole 3-way.
- 12 6.3V. bulbs. (M.E.S.)
- C1 $1\mu\text{F}$ 150V paper

Cabinet

The size of the cabinet depends largely on the type of relays used. In the author's case miniature relays were used, and this enabled quite a compact unit to be built, the overall dimensions being:

- Width 12in.
- Depth 12in.
- Height at front ... 2in.
- Height at rear ... 6in.

1/4in. soft wood was used for the sides, and 4 mm plywood for the sloping panel, and the base.

The front panel was drilled to accept the twelve lamps. For economy, the author dispensed with bulb holders by drilling holes which would hold the shanks of the bulbs tightly, and soldered connections directly to the bulbs from the underside of the panel.

Long brass plated drawing pins were found to be the most readily available items to make the contacts. They were fitted by drilling small holes with a fine drill in the respective places, and pressing the pins tightly home. The pins should be long enough to allow soldering to the shank on the reverse side of the panel.

A hole must be cut in the front of the panel to allow the reset button to protrude.

Covers for the lamps were made from hardwood. The cover for the question lights was made as a single unit 9in. long x 7/8in wide x 1/4in. deep. Ten holes 1/8in. diameter were drilled through this piece to coincide with the positions of the bulbs. A piece of greaseproof paper was stuck over the surface to cover all the holes and a trim of thin plywood, suitably drilled, was pinned over the top of this paper, see Fig. 5. This figure also shows the type of cover made for the "Right" "Wrong" lamps. The method of making these was identical to that already described, except that the words "Right" and "Wrong" were printed on the paper.

When the bulbs had been inserted, these covers were screwed to the panel and apart from making inexpensive covers, formed good registration jigs for holding the question sheets in position. Fig. 6 shows the layout of the completed front panel.

WIRING DETAILS NEXT MONTH

PRACTICAL WIRELESS BINDERS

The Practical Wireless Easi-binder is designed to hold normally 12 issues. Please state volume number required otherwise a blank cover will be sent.


A new version of the Easi-binder with a special pocket for storing blueprints and data sheets is now available. The price is 11/6d inclusive of postage.

Order your binder from: Binding Department, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

NEXT MONTH IN PRACTICAL WIRELESS

SIMPLE PROXIMITY ALARM

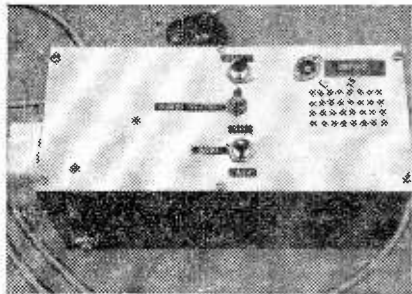Adaptable for a wide variety of uses, including burglar alarm, in houses, shops or larger buildings. Built-in protection prevents alarm sounding when occupier returns to premises. Full constructional details.



MOBILE TRANSMITTER

Entirely solid state amateur band transmitter, specially designed for mobile and/or portable work. High efficiency—low power drain. Complete with self-contained modulator to provide 10W. fully modulated on 160m. 'ham' band.

SWITCHED TUNED SUPERHET

Modern circuitry, using miniature range valves. Internal ferrite rod, excellent sensitivity. Station selection at touch of button avoids band-hunting. How-to-build details and wiring diagrams.

MARCH ISSUE

ON SALE FEBRUARY 3rd

ORDER YOUR COPY NOW!

PRACTICALLY WIRELESS

DESPITE the doom-laden warnings given out in the October 1965 contribution to this column "On Turning Pro", the feeling that the professional radio repairman is in a gilt-edged occupation appears to persist.

Not only do some readers request further advice on getting into the trade but others, grinning, no doubt, into their ink, relate how successful their step from amateur to professional turned out to be. Apart from the observation that some chaps would make a success whatever they turned their hands to and others as inevitable fail, there is little point in continuing my argument.

So Henry bows to the wind of opinion and devotes a few remarks to the practice behind the practice of radio repair.

Unless one begins as an apprentice and is inaugurated into the art of making the tea and sweeping the workshop floor, the usual point of entry is as a "field engineer". This is the rather high-flown term for the activity required by some firms, who require only valve and chassis changers, with a minimum of easily acquired knowledge and a penchant for working long hours.

The important word, though, was that little adjective, "field". In many cases, it is all too true. The poor chap has to trudge through the winter mud to some

isolated farmhouse to change a battery in a transistor radio or instal a TV in the byre to keep the cows happy.

No, I am serious. More than one milking shed in Henry's patch has soft music laid on. And humidity plays havoc with tapes and mechanisms.

Life in the built-up areas is by no means all beer and skittles. There being less distance between calls, the serviceman will be expected to rush around a lot more. He has traffic to contend with instead of livestock—and it's an arguable premise whether a sheep is more intractable than a bus driver, or a hen less predictable than a flustered L-driver.

In addition to an ability to tackle any kind of electronic repair, the serviceman has to deal with people. Or, more accurately, with customers.

The distinction becomes obvious when the smiling housewife who greeted you at the door turns into the snapping virago whose receiver you are attempting to remove for workshop repair.

It is all very fine fiddling about with the innards of some receiver, with PRACTICAL WIRELESS at your elbow; quite another matter to crouch behind an alien radiogram, wheedling toffee-papers from the mechanism while Mrs. Customer flips around you with a duster. Mr. Customer grumbles morosely about the impending bill. Customer Junior surveys each move with the cynicism of an embryo astronaut, and the dog searches for bones in your tool-box.

You may have taken note of a couple of graphic labels perpetrated by my friend Pax (Nov. '65). The radio repair trade does not—despite popular belief—treat sets with such cavalier abandon! Where one would hack away at a recalcitrant chassis in the seclusion of one's den, the method of treatment "in the field" depends on a bit of extra showmanship—dusters on the



Flips around with a duster


floor, tools laid out in neat rows, valves tapped only when the client looks the other way, etc.

All this assumes that you have got there! Very often, it takes as long to locate the address as to service the set.

A while ago there was a snide account in most newspapers of Mr. Henry Pounds's defiance of Havant Urban Council. He wanted to retain the name of his house, "Beechlands"; they insisted he post up the number—49. He did, on the *inside* of a doorpost where it could not be seen from the street. He was taken to court and fined £2. Mr. Pounds could afford to shrug it off. My paper described him as a "wealthy ship-breaker". Any field serviceman who has groped up drive-ways on a dark or foggy night and barked his shins on unnumbered gates can think of other things to call him.

These are only some of the factors to be considered on entering the trade. Joe, Messrs. Mullard have summed them up beautifully in an illustrated poster and booklet, whose theme is: "There's more to service than repairing the set".

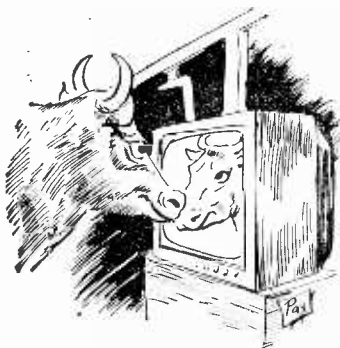I agree, wholeheartedly, and wish there were space to reproduce their humorous advice.



A TV in the byre

EXCLUSIVE TO PRACTICAL WIRELESS READERS

MORE TERRIFIC OFFERS FROM CONCORD!

TRANSISTOR
POCKET RADIOS




BULK PURCHASE ENABLES US TO MAKE THIS FANTASTIC OFFER—AND WITH MONEY BACK GUARANTEE

The 'SAN REMO'... so tuned that it brings the voices of star entertainers and vocalists dramatically to life—in your home, office, etc. Only 4 1/2 x 2 1/2 x 1 1/4. Fits easily into your pocket or handbag. Works for months of 1/2 battery. Should last a lifetime, anyone can assemble it in an hour or two with our easy plan. Miniature speaker, carrying case—everything only 28/6, 2/6 P. & P. (Parts can be bought separately.) Limited period—so rush your order before it's too late. DEMONSTRATIONS DAILY.

ONLY 28/6
NO MORE TO PAY

DON'T WALK—

JUST TALK!!

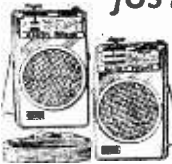

INTERCOM
OUTFIT &
BABY ALARM

LIMITED QUANTITY SAVE £3.13.1

ONLY 49/11 Robustly made, brand new current models. You get 2 separate, fully transistorised intercommunicating sets — each can speak or listen to the other — complete with 60 ft. connecting wire. Fixed in a flash. Ends baby-crying worries. Ideal for Workshop to House. Sickroom, hundreds of uses! Hangs on wall or stands up. Our absurd price 49/11, but only 2/6 extra. Post, etc. 3/7. Money refunded if not 6 gns. value!

MAKE 5 DIFFERENT
TRANSISTOR RADIOS

FOR
35/-



NO EXPERIENCE NECESSARY. No Soldering. Only 8 connections for first radio to work. Just look, you get A.B.C. Plans, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, Screws, etc. **YES — EVERYTHING!** Loud clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS GALORE.** Mr. R. O'P. of Londonbury, writes:— "I received your components and I must say that I am very satisfied with them I have already set up!... COMPLETE HOME/RADIO COURSE. Originally £6 SEND ONLY 35/- plus 3/6 post, etc.

IT HAD TO COME EVENTUALLY! THE "SKYSCRAPER" PERSONAL COMMUNICATIONS RECEIVER, Highly sensitive. World-wide short-wave reception including news in English and countless other broadcasts from RUSSIA AMERICA, etc., etc. Take it anywhere—it's featherweight 6in. x 3 1/2in. x 1 1/2in. Bandspread Tuning Vernier Dial Miniature Valve Circuits, Plug-in Coils, Own Rod Aerial, etc. 50% of production to be exported. Anyone can assemble it within 2 hours—only a few connections to make—experience unnecessary. Parts incl. Case. Personal phone. Easy-to-follow plan—48/6 plus 2/6 Post, etc.

TRANSISTOR RADIO KITS SOLD IN DEPARTMENT STORES AT £5.9.0.

OUR PRICE 37/6 P. & P. 3/6 Extra

Well-known brand Transistor Radio Kits—YOU SAVE £2.10.6. Covering all medium-long wave with parts including Mullard Semi Conductors, 48-page instruction manual, Entertaining and educational. No soldering, just plug in, making many different Radios in a few mins.

CAR CIGARETTE LIGHTER DISPENSER

High Class Stores sell at 2 gns. — save £2.4.6 Top quality chromium. Car cigarette — lighter — Dispenser. Fixed in a lift — Pressing Button delivers ready-fit Cigarette into your hand! Takes 10 cigarettes—King size or any size. As fitted to luxury cars. Safe, fool-proof. 4 1/2 x 4 x 1 1/2 in. Lifetime tested, ready to use. Refund if not worth 2 gns. 250 only. 18/6 plus 1/6 P. & P. (state 6 or 12).

FABULOUS ST. TROPEZ MK. 6 The Sensational Pocket Radio

This fantastic offer will amaze you—the beautifully compact ST. TROPEZ, measuring 4 1/2 x 3 x 1 1/4 in. receives perfectly in bedroom office or gardens—over all medium waves including Luxembourg (under 1d. per hour running cost. ANYONE can assemble it in one or two hours using our simple A.B.C. plan. 25/- (P. & P. 2/6 extra). Case extra. Parts can be bought separately.

Read what just a few of our satisfied customers say R.C. of Harringay writes Received with thanks Skyrama... Very pleased. Working well. B.M. of Harrigate writes... I would like to thank you... It was a real bargain. L.S. of London W.8 writes... given it a good try out and I am very pleased with the results. S.B. of Somerset writes... delighted with this radio... glad if you could send one more. T.F. of Stevenage writes... I would just like to say how pleased my son is with this radio.

10 TRANSISTOR PERFORMANCE HI-FI RADIO

ONLY 55/- POST 3/6

LIQUIDATION PURCHASE 500 ONLY Made to sell at 51 gns — Save £30.6. Latest camera style radio. Big-Set tone from tone-chamber moving coil speaker, new device plucks in Station after Station including Luxembourg, Caroline, etc. Fantastic coverage — 187-577 metres! Expensive looking finish, simulated leather, black and chromium. Size 4 1/2 x 2 1/2 x 1 1/2. 7 semi-conductors. 55/-+2/6 batt. +3/6 P. & P. Refund if not delighted.

NEW RADIO VOLKSRADIO ANYONE CAN BUILD IN 2-3 HOURS 19/6

EVEN THE OLDER CHILDREN BUILD THEM!... no soldering—only 16 connections! then hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4 1/2 x 2 1/2 x 1 1/2 in. Many Testimonials: M.H. of Bradford, writes: "I have just completed one of your sets successfully. It is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me. Your instructions and plan have obviously been very carefully thought out so that even the most dim can follow them... Direct from Manufacturer to You. Send 19/6 plus 2/6 pos., etc. PARTS AVAILABLE SEPARATELY

AMAZING CIGARETTE RADIO 18/6

Yes, a perfectly ordinary packet of cigarettes! — but watch your friends' astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 Cigarettes—yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our buying testimonial file. Mr. D. B. of Huddersfield, writes: "I have fitted the parts in and it is working wonderfully..." ALL PARTS including Semi-Conductors, A.B.C. Plans, etc. ONLY 18/6 plus 2/6 post etc. PARTS AVAILABLE SEPARATELY

WEYRAD

TRANSISTOR RECEIVER COILS


Special versions of the P50 Series are now available for the AF.117 or OC.170 Transistors. Details of the simple modifications to our standard receiver are given in the latest edition of the Constructors Booklet which is priced at 2/-.

The new components and their original equivalents are listed below:


			For OC45	For AF117	Price
Oscillator Coil	P50/1AC	P50/1AC	5/4
1st I.F. Transformer	P50/2CC	P51/1	5/7
2nd I.F. Transformer	P50/2CC	P51/2	5/7
3rd I.F. Transformer	P50/3CC	P50/3V	6/-
Rod Aerial	RA2W	12/6
Driver Transformer	LFD4/1	9/6
Output Transformer	OPT1	10/6
Printed Circuit	PCA1	9/6

WEYRAD (ELECTRONICS) LIMITED

School Street, WEYMOUTH, Dorset

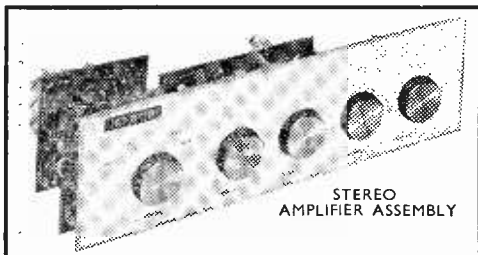

STEREO AMPLIFIER ASSEMBLY

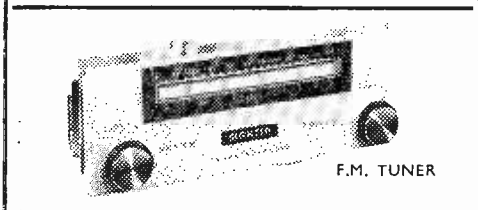

F.M. TUNER

- 5 stage input Selector £2.76
- Pre-amp. and vol. control £1.17.6
- Pre-amp. with tone controls £3.2.6
- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0

Send for leaflet describing entire range



Martin Audiokits and Recordkits are obtainable from good stockists everywhere. In cases of difficulty please write direct.

MARTIN ELECTRONICS LTD., 154/155 HIGH ST., BRENTFORD, M'SEX

Phone: ISLeworth 1161/2

KITS WITH A FUTURE

The Martin Audiokit assembly you own today can become part of an even better hi-fi system tomorrow. No other system allows you to enlarge your installation stage by stage in the way Audiokits do. They comprise a wide range of very well made prefabricated units in which the connections are standardised throughout. Each is rigorously tested to stated specification before despatch. NEW KITS FOR ADDING ON ARE IN COURSE OF PREPARATION NOW—so by starting with Martin today, you insure yourself for still better listening tomorrow.

Choose Martin for quality

- Build for 3 or 15 ohm system
- Start with Mono and add Stereo or start completely with Stereo
- Power packs available
- Professionally styled escutcheon plates
- Assembly is easy by following the well presented instructions

MARTIN ELECTRONICS LTD., 154-155 High Street
Brentford Middlesex

Full details of Martin Audiokits please

NAME

ADDRESS

(Block letters)

PW.2

The Walter "Metropolitan"

K. T. WILSON

MODIFICATIONS TO IMPROVE PERFORMANCE
OF THIS TRANSISTOR TAPE RECORDER

THE Walter "Metropolitan" Transistor Tape Recorder first appeared at the 1960 Radio Show, and was one of the first all-transistor tape recorders to offer all the facilities now accepted as standard on good quality machines. The tape speed was fixed at $3\frac{1}{2}$ in./sec and the maximum reel size was $5\frac{1}{2}$ in. Recording was twin-track, to CCIR characteristics, and both high and low level input sockets were provided. The amplifier could be used for monitoring during recordings, and could also be used separately, though with some inconvenience. Sockets were provided for external loudspeakers (muting the internal speaker) and for connecting to external amplifiers. Separate motors were used for record/playback and for wind/rewind.

Shortly after the introduction of the "Metropolitan", the Walter Company went into liquidation and the entire stock of the "Metropolitan" Tape Recorders was sold off at a very much reduced price. As some 6,000 machines were involved, many of these instruments must be in the hands of readers of this magazine, who will undoubtedly be interested in the modifications which can be carried out to improve the "Metropolitan".

The Motors

The Metropolitan, in its original form, is a mains/battery recorder using a 9V supply taken from 3 PP9 batteries or from a mains transformer and rectifier unit. The change from battery to mains or vice versa is by a switch which also blanks off the mains socket in the battery position.

The motors are small 9V d.c. units made by Greencoat Industries under the trade mark "Staar". The record/play motor is fitted with a governor which limits its speed to 3,000 r.p.m., and is also suppressed, although the suppression is not so effective at Television Band III frequencies. Ferrite beads (from Radiospares) fitted on the leads as close to the motor as possible will cut out this interference. The wind/rewind motor is not suppressed at all, and to avoid interference it is advisable to fit a $1\mu\text{F}$ 25V capacitor across the leads as close to the motor as possible. This capacitor is already fitted to the record-play motor.



The main trouble with this otherwise admirable system is that the governor contacts of the record/play motor wear and become pitted to such an extent that the action of the governor is completely upset and the result is severe speed fluctuations. In its early stages this can be con-

fused with wow caused by an eccentric capstan idler wheel. Since the motors cannot be replaced directly, they must either be repaired or the recorder modified to take a different type of motor. Small shaded-pole AC mains motors are cheap and easily obtained and it might be thought that one such could be fitted. It is certainly possible, but there are several great disadvantages. The facility of battery operation is lost, to start with. More serious is the point that the capstan flywheel is intended to smooth the impulses due to the cutting in and out of the governor, a process which is said to take place at a very high frequency, and is much too light to cope with the power pulses of a two-pole shaded-pole motor. The result is severe flutter, even 100 c/s hum.

The most serious disadvantage is the difficulty of fitting a shaded-pole motor, which is usually a large unit. Very few motors of adequate power will fit in the space vacated by the original motor, and since the drive is by a brass wheel against a rubber tyre on the rim of the flywheel, a change of motor position involves a change in the method of driving. It is just possible to fit a shaded-pole motor in the space between the speaker and the control stick and drive by elastic belt, using a V-cut pulley and having a suitable V cut in the capstan flywheel. The motor pulley should be twice the diameter of the existing brass wheel, since the motor speed is now 1,500 r.p.m. This method is open to the objection that the shaded-pole motor is now rather near to the early stages of the amplifier, and there is considerable hum pickup, which can be only partially reduced by magnetic screening.


Fitting New Motor

The best course, if the original motor is beyond repair is to fit a similar type of motor. The name and address of a supplier who can frequently be helpful in this respect is given at the end of the article. If the motor has not had too much use, or if the governor points can be rebuilt by electroplating with silver (not an expensive operation) then a long life can be ensured by modifying the governor to a transistorised system. The point of this method is that the transistor handles the motor current and the governor points handle only the transistor base current, which will be $1/\beta$ times the collector current. Since the β of suitable transistors is of the order of 70-100, the governor points will last indefinitely. The original and modified circuits are shown in Fig. 1.

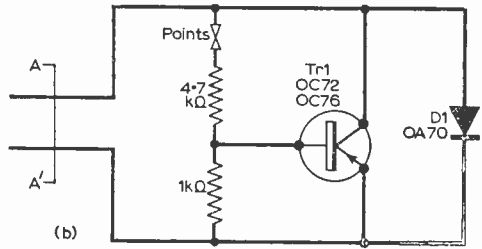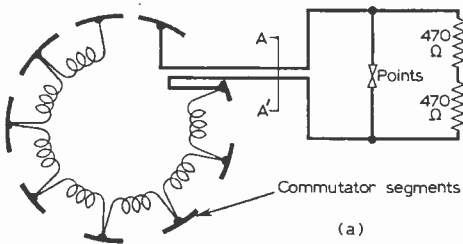

Since all the circuitry has to be fixed to the motor shaft and rotate at 3,000 r.p.m., small components and good fixing are essential. The motor is dismantled by removing the leads, taking great care not to lose the brushes (phosphor-bronze) which are attached to the terminal screws. The motor can then be slipped out of its foam-rubber casing and the remaining screws removed to allow the armature assembly to be removed. Connections to the governor leads should be made as far from the governor points as possible to avoid changing the speed by a mechanical loading on the governor. A useful tip is to secure every point of the circuitry with Durofix, which can readily be softened with acetone if replacements are required.

Fig. 1: (a) original motor circuit. (b) modified circuit. (c) alternative circuit.

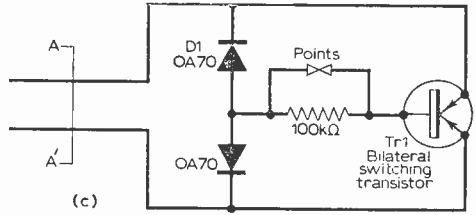

Amplifier Mods.

Having attended to the motor, the remaining modifications concern the amplifier. In the original circuit, the first three transistors are common to

both record and replay circuitry. The collectors are earthed, and bias is by a feedback resistor between collector and base in each case. The recording feed to the head is taken from the third transistor via a 1μF capacitor and a bias trap (a simple L-C trap). With this system, the recording level is very low, and leakage in the coupling

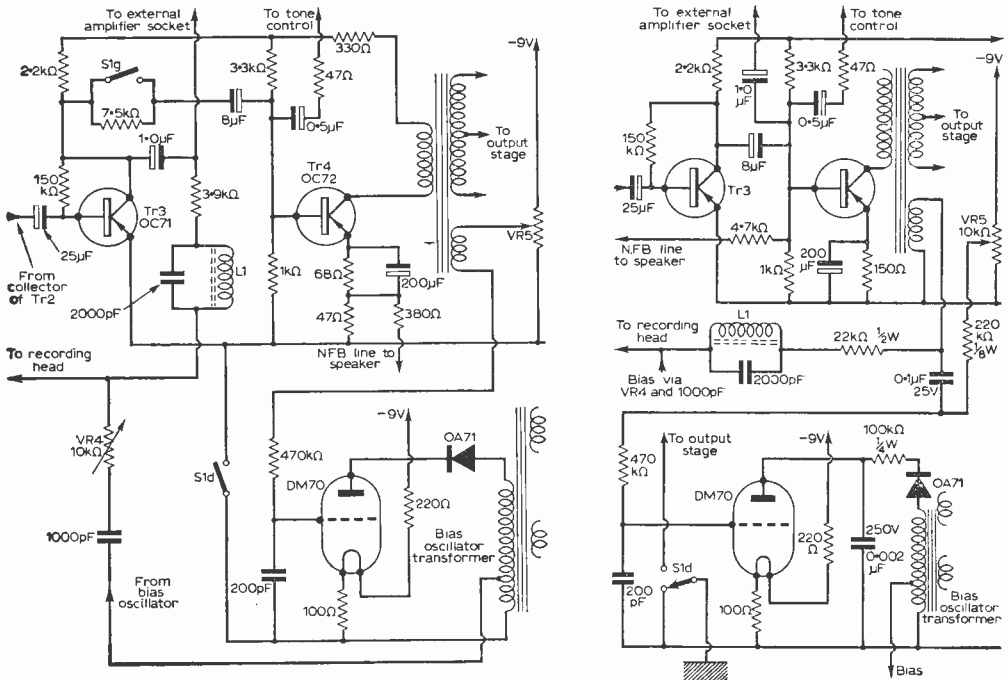


Fig. 2 (left): original stages before modification, and (right) after modification.

capacitor causes the head to become magnetised; this raises the noise level considerably. Very much better results can be obtained if the recording head is driven from the next stage, which in the unmodified recorder is the driver stage for the output transistors. Incidentally, the circuit of the original recorder, together with a practical layout diagram is obtainable, priced 7s. 6d., from J. E. Sexton Ltd., of 162 Grays Inn Road, London, W.C.1.

The modified stage is shown in Fig. 2 along with the modifications also needed to the recording level indicator. The driver transformer has an extra winding which on the original circuit is used to feed a.f. voltages to the grid of the DM70 recording level indicator. If this winding is used for feeding the recording head through a much higher series resistor, the high frequency response of the recorder will be considerably improved as the CCIR recording characteristic assumes that the head is fed from a resistance which is high compared to the head impedance at the highest frequency of interest. The recording level indicator can now be fed through a simple R-C coupled circuit as the grid impedance of the record level indicator is high.

Record Level Indicator

Some modifications can now be made to the record level indicator itself. In the original recorder, the level indicator is barely satisfactory; the indicator, which is of the "exclamation mark" type, appears closed all the time, and only a very slight overlap can be seen at the correct recording level. The reason for this is not hard to find on the original circuit; the anode of the indicator is supplied with 90 volts by rectifying the voltage present on an overwind of the bias oscillator coil. The reason for the erratic behaviour of the indicator is that the rectified 40 kc/s is not smoothed in any way. The addition of a 100kΩ resistor and 0.002μF capacitor completely cures this. During this modification, do not forget to remove the 7.5 kΩ resistor which in the original was used to cut down the drive to the output transistors during recording. This was originally necessary as the first three stages had to be run at full gain, and some attenuation was required to avoid overdriving the output transistors. The potentiometer which acts as a treble cut during replay also serves as a volume control during replay, but it acts by adding series resistance to the speaker and is therefore incapable of reducing the drive. When the 7.5kΩ is removed the wiring should also be removed from the associated switch section to be used later. Note that the potentiometer VR5 is used to set the initial position of the column of the record level indicator. This must be set so that 100% recording level corresponds to the column meeting the dot underneath.

Output Stage

The next modification concerns the output stage. In the original, the output stage is stated to be a Class B transformer coupled stage with 2.3W output. As the output transistors are OC26's or their Ediswan equivalents, using the chassis of the recorder as a heat sink, this output seems very

modest. In actual fact, the standing current in the output transistors is very high, corresponding more to class A operation, and causing restricted output, low volts on the mains unit (along with considerable hum) and very short battery life. Higher outputs can be obtained by reducing the base bias current in this stage, and the circuits of original and modified stages are shown in Fig. 3. It can be seen that the emitter circuitry has been altered to. During replay the 1.5Ω resistors are in series with the emitters to give a measure of feedback and to aid thermal stability. During record, the 10Ω resistors are also in series to reduce the dissipation in the output transistors since (as explained earlier) the drive is no longer attenuated during record. The portion of switch previously made redundant is now pressed into service along with the portion used to earth the bias oscillator circuit during recording. Note that in the original circuit, the feedback loop is disconnected during recording. This avoids feeding any harmonics produced by the output stage back into the recording head. For feeding external speakers, and where the highest output is required, the 10Ω resistor across the output transformer should be replaced by 33Ω.

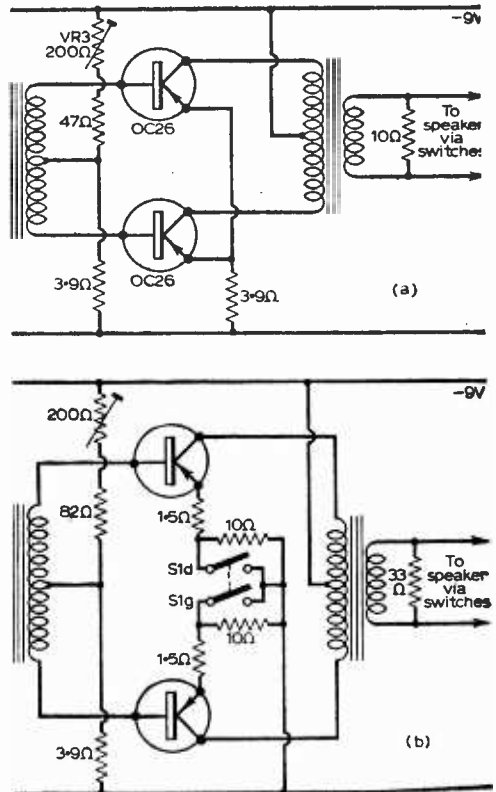


Fig. 3 (a) Unmodified circuit of output stage. (b) modified.

Other Modifications

Two other modifications are very much worth while. In the original, in order to use the amplifier separately it was necessary to switch to record, having removed the tape spools or set the "pause" control, so as not to record on a tape. It is often inconvenient to run the recording motor during periods of use as a straight amplifier, apart from considerations of wear and tear on a valuable motor, and furthermore, the treble boost is in circuit during this time, making the output unnecessarily shrill. It is a simple matter to add a switch to cut the recording motor and the treble boost when the amplifier is being used alone, and this simple modification adds considerably to the versatility of the machine.

The other useful modification concerns the erase arrangements. Permanent magnet erase is used on the "Metropolitan", but the system used, a Walter patent, is a great improvement on earlier systems. A short bar magnet is used and is swung into position by a pivoted arm when the joystick control is in the "record" position. It will be found, however, that recordings made using the original system are by no means consistent in background noise level; this is almost invariably due to the amount of slack in the mechanical coupling from the joystick to the magnet. Good, noise-free erase is obtainable at only one setting of the angle between the magnet and the tape; the angle is about 5°. The amount of slack in the mechanical coupling is usually enough to make it impossible to achieve this setting consistently. The erase magnet is mounted on a bell-crank, the other end of which engages in a forked lever. It is this joint of bell-crank and forked lever which is the main source of trouble, and two remedies are possible. The forks of the forked lever may be bent into each other so that they grip the end of the bell-crank more firmly in the "record" position. A better method is to put some rubber

tubing (of the type used for cycle valves) over the prongs of the fork and, if necessary, over the end of the bell-crank as well. The fit of the bell-crank on its pivot should be checked also, slackness here is more difficult to take up without making the whole assembly too stiff, in which case the arm carrying the magnet may not move into the tape at all, as it is connected to the bell-crank by a spring, this arrangement allows the erase head to be swung aside for superimposing recordings. By carefully filing the hollow spindle which passes through the bell-crank, the fit can be improved, but only a minute quantity of metal at a time should be removed, checking the fit each time. This concludes the description of the modifications, and we pass to a few notes on the practical aspect.

Practical Notes

First of all, the lid should be removed. For work on the motor and the erase head, the deck cover must also be removed. Remove tape reels, and pull off the small plastic cover which shields the heads. The flat-headed screw under this cover should now be removed together with the other two above the tape-spindles. The volume-control knob is removed, and the knobs on the joystick and the "Push-to-record" safety switch are unscrewed. The plastic deck-cover can now be lifted clear, although it may be rather stiff due to the retaining clip fitted at the centre of the loud-speaker side. For working on the motor, it is desirable also to remove the speaker, which involves unsoldering the leads and unscrewing the retaining Philips screws. If the external loud-speaker connection is now used, the recorder can be checked in this condition after modifications have been made. In this state, the adjustments to the erase magnet can be made. To reach the motor, rather more dismantling must be done. Remove the hairpin spring which holds the

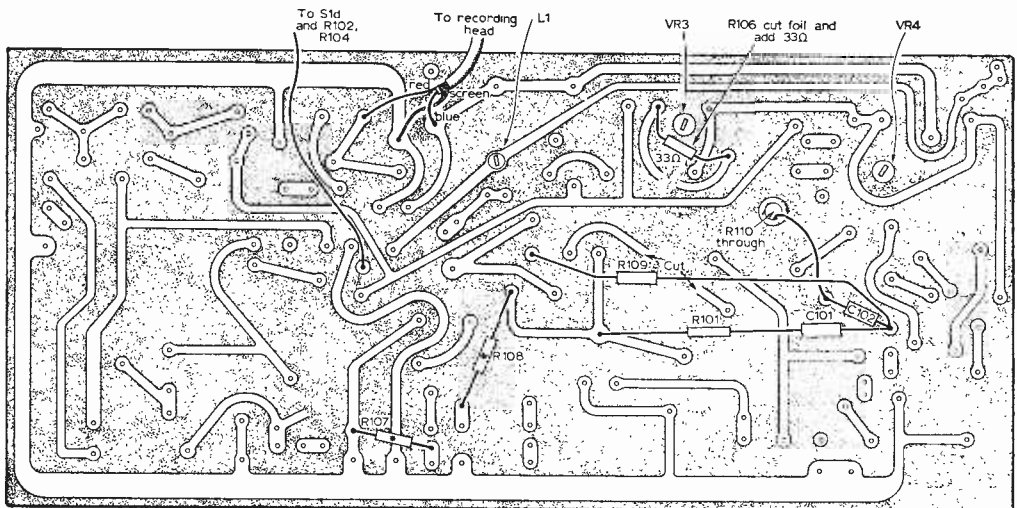


Fig. 4: Printed circuit board layout, including modifications.

SHORT WAVE RECEIVER

PRICE
5/-

NER HOUSE, SOUTHAMPTON STREET, LONDON W.C.2.

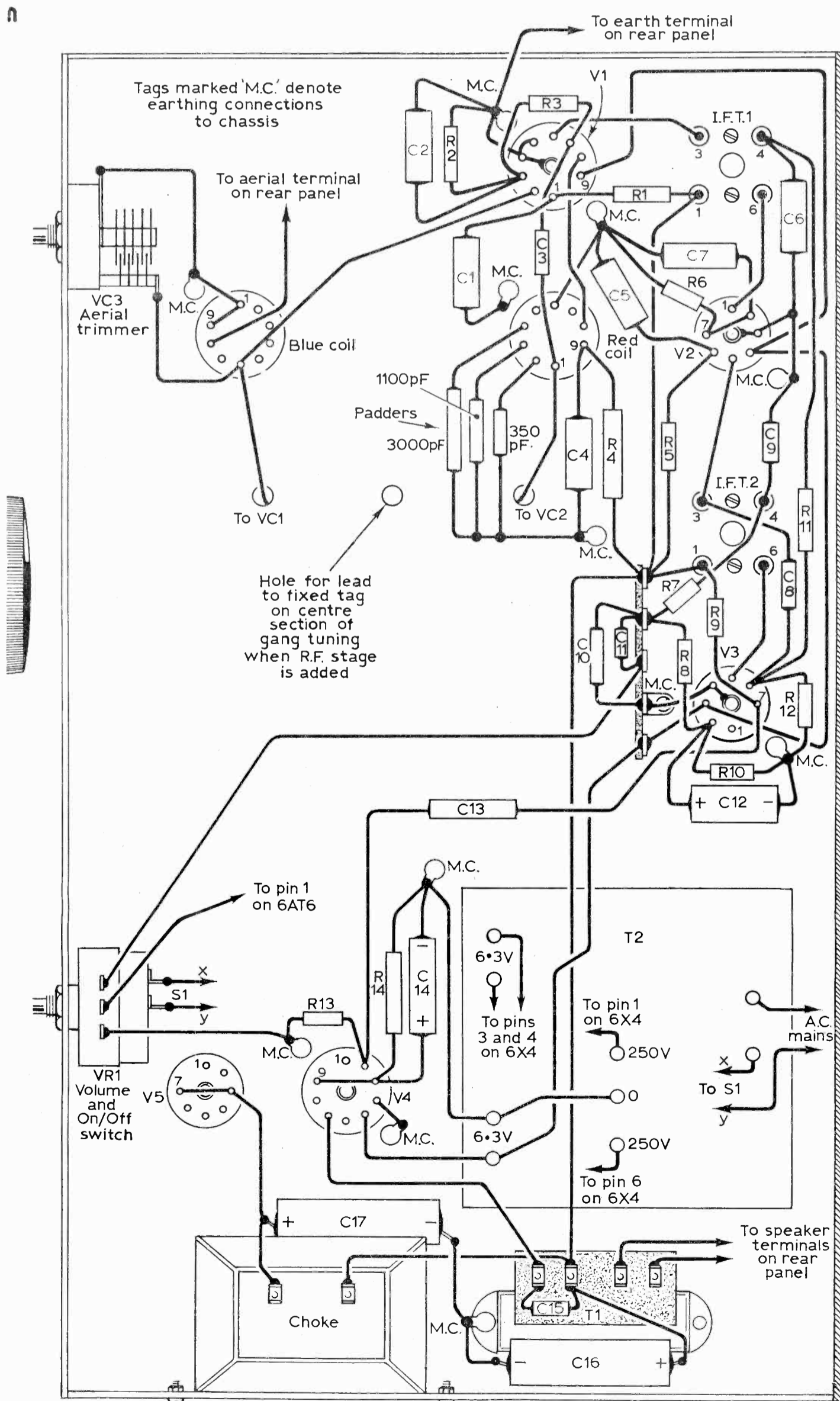
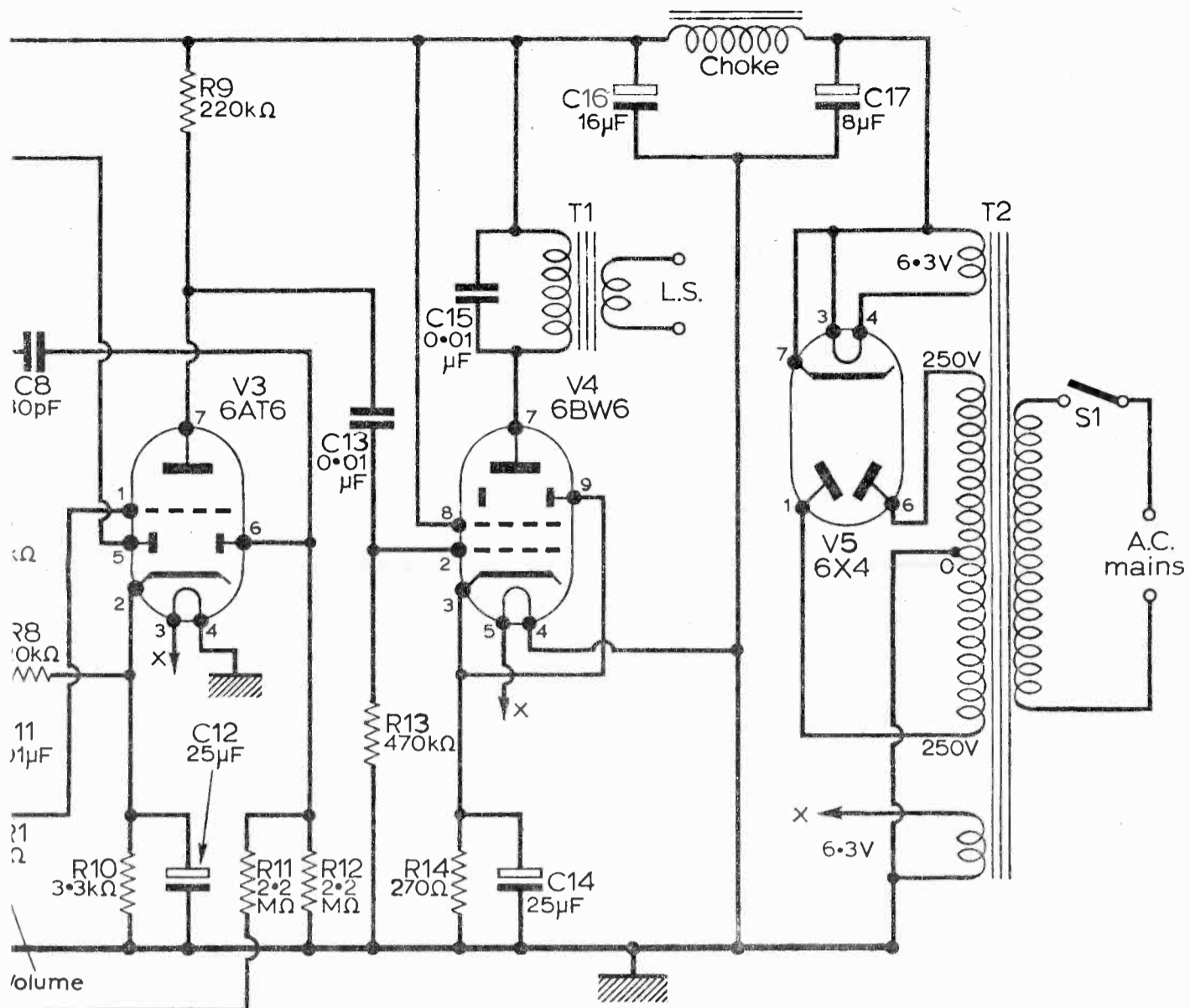


Fig.3. Under chassis wiring

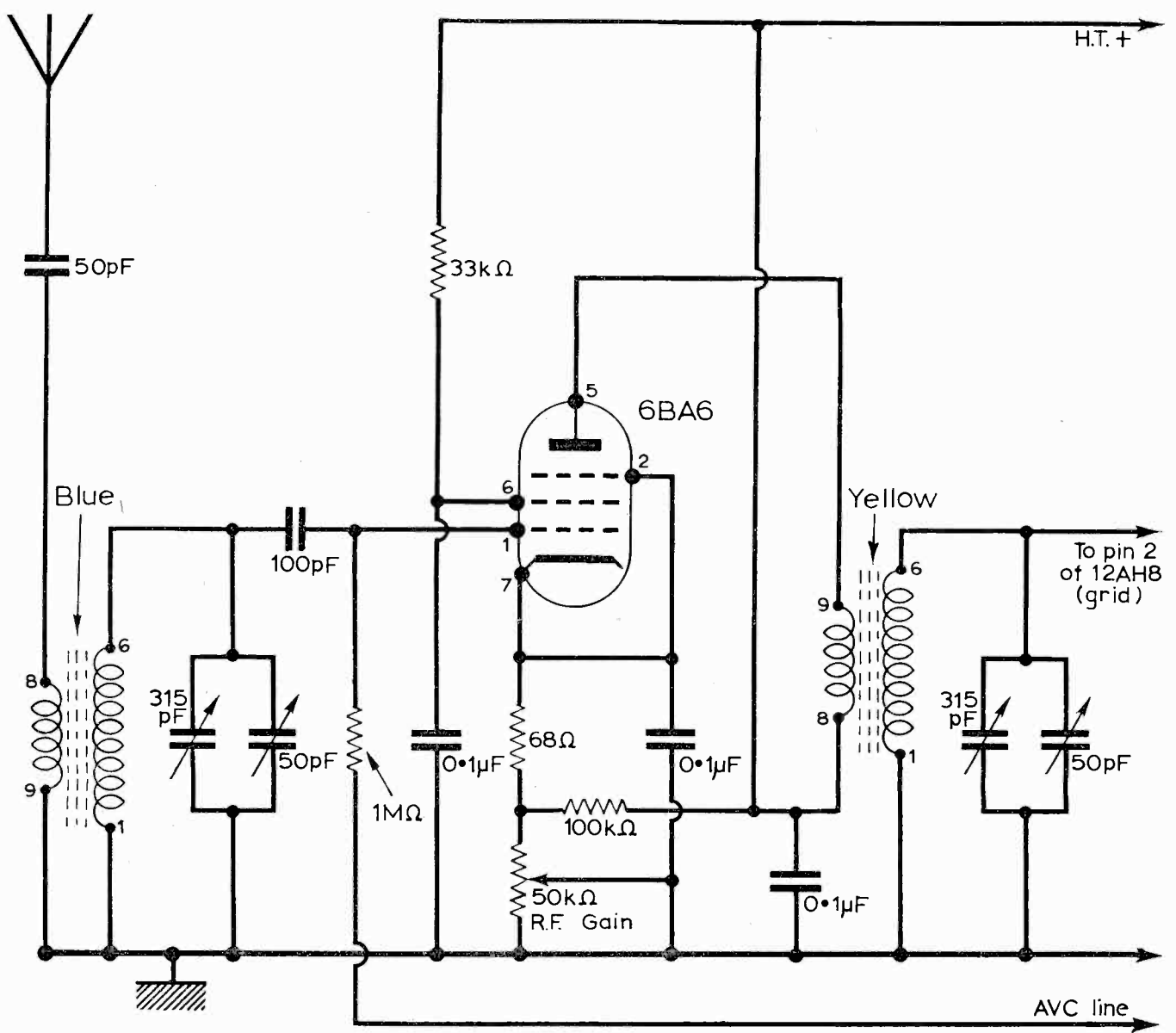


Fig. 4

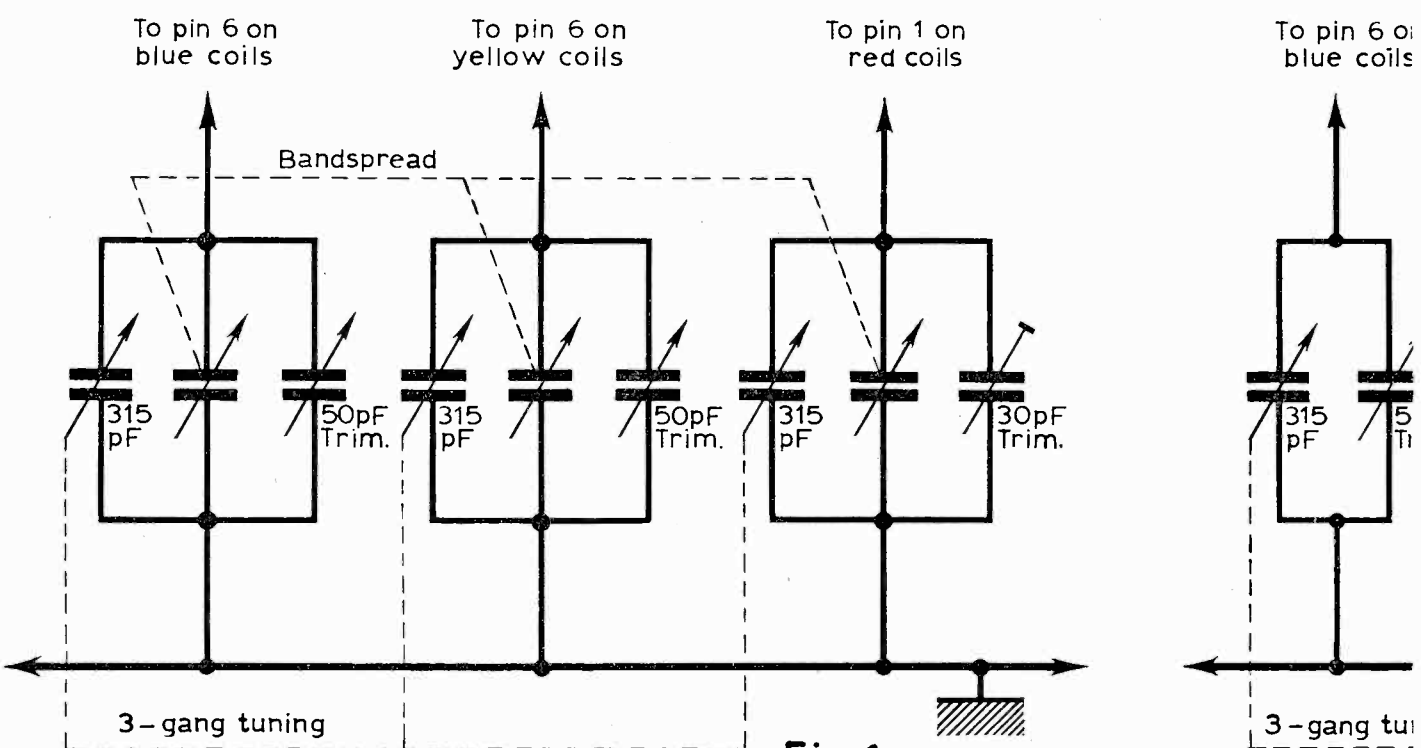


Fig. 6



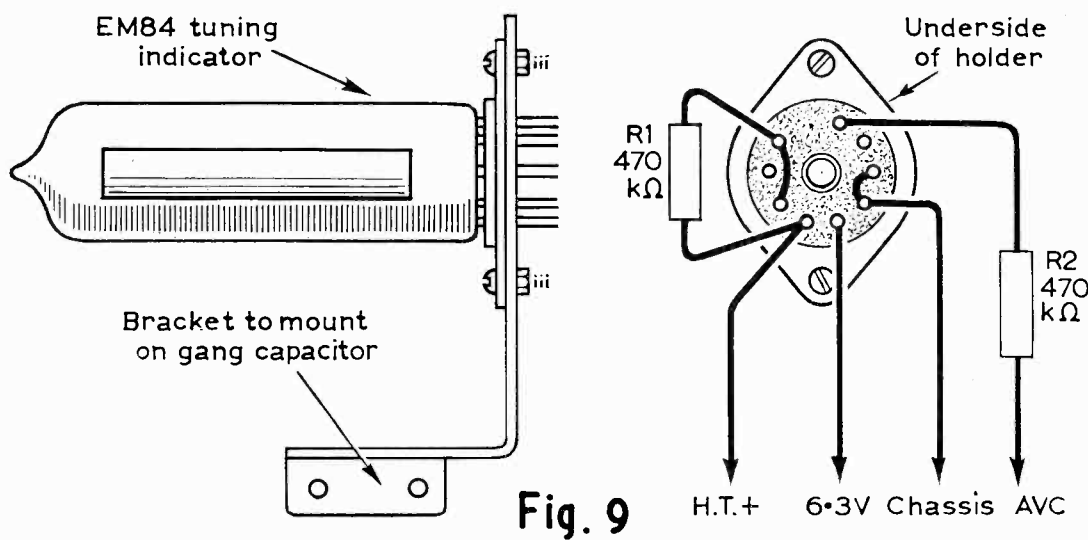


Fig. 9

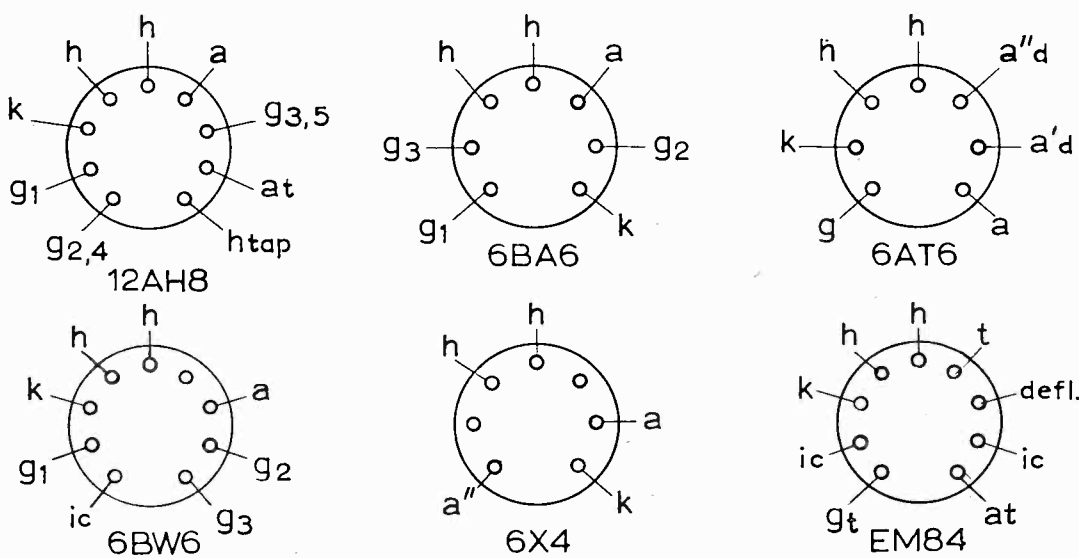

Valve base connections

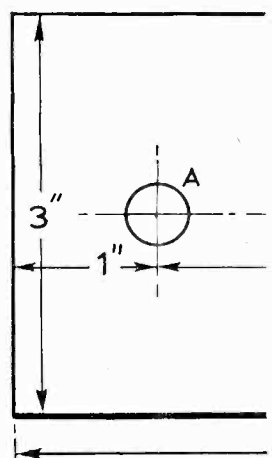

COMPONENTS

Capacitors:

- C1 0.1μF 350V
- C2 0.1μF 350V
- C3 100pF mica or ceramic
- C4 0.05μF 350V
- C5 0.1μF 350V
- C6 0.05μF 150V
- C7 0.1μF 350V
- C8 30pF mica or ceramic
- C9 200pF mica or ceramic
- C10 200pF mica or ceramic
- C11 0.01μF 350V
- C12 25μF 25V electrolytic
- C13 0.01μF mica or ceramic
- C14 25μF 25V electrolytic

Inductors:

- C15 0.01μF 350V
- C16 16μF 350V electrolytic
- C17 8μF 350V electrolytic

Valves:

- V1 12AH8
- V2 6BA6
- V3 6AT6
- V4 6BW6
- V5 6X4

Transformers:

- IFT1 IFT2 Denco IFT11 (465 kc/s). T1 5kΩ/3kΩ 60mA ratio 40:1. T2 6.3V 2.5A or 3A and 250/0/250V 70mA mains transformer.

Resistors:

- R1 33kΩ
- R2 220Ω
- R3 47kΩ
- R4 27kΩ 1W
- R5 38kΩ
- R6 68kΩ
- R7 22kΩ
- All 10% 1/4W carbon unless stated

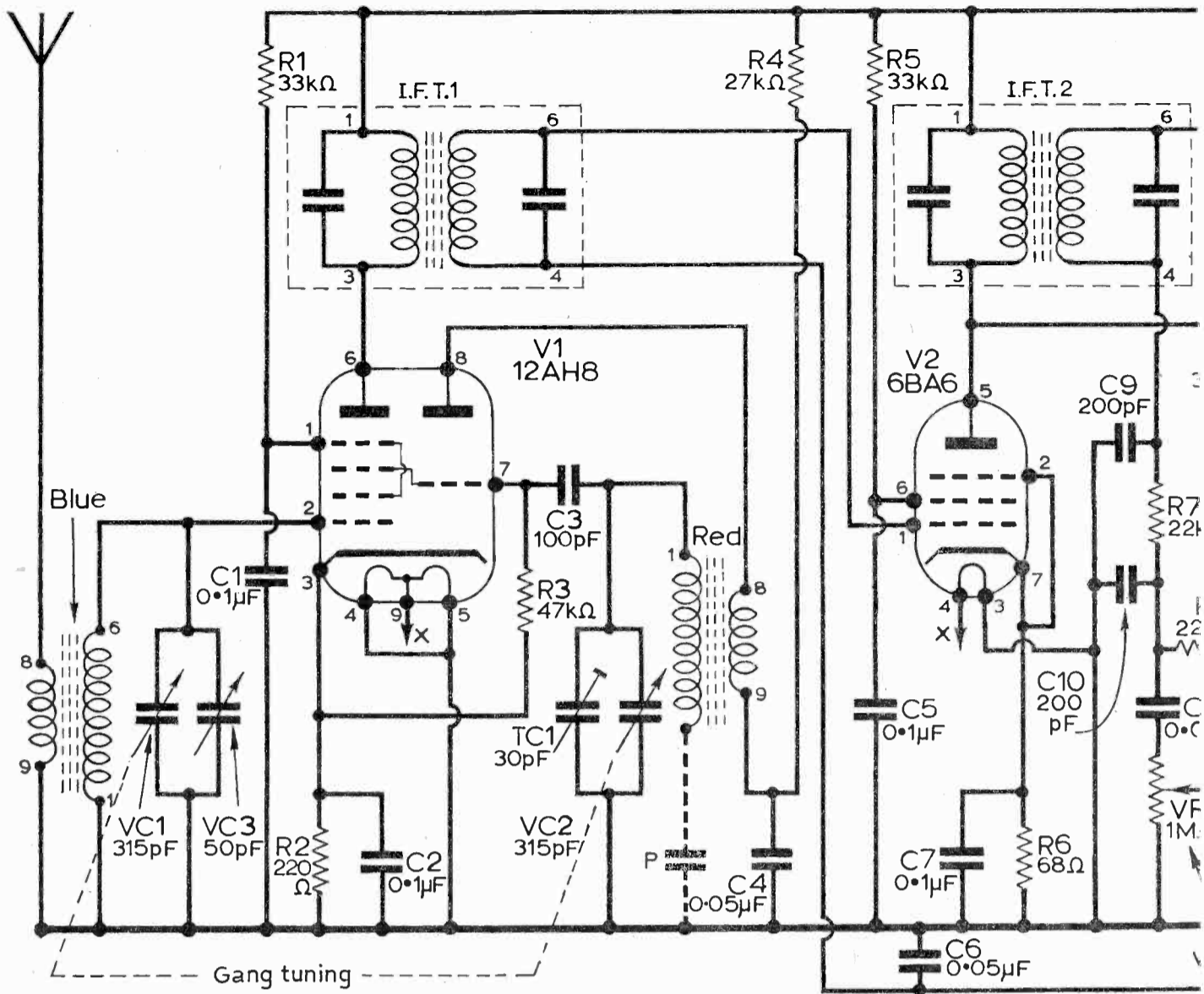


Fig.1. Complete circuit diagram

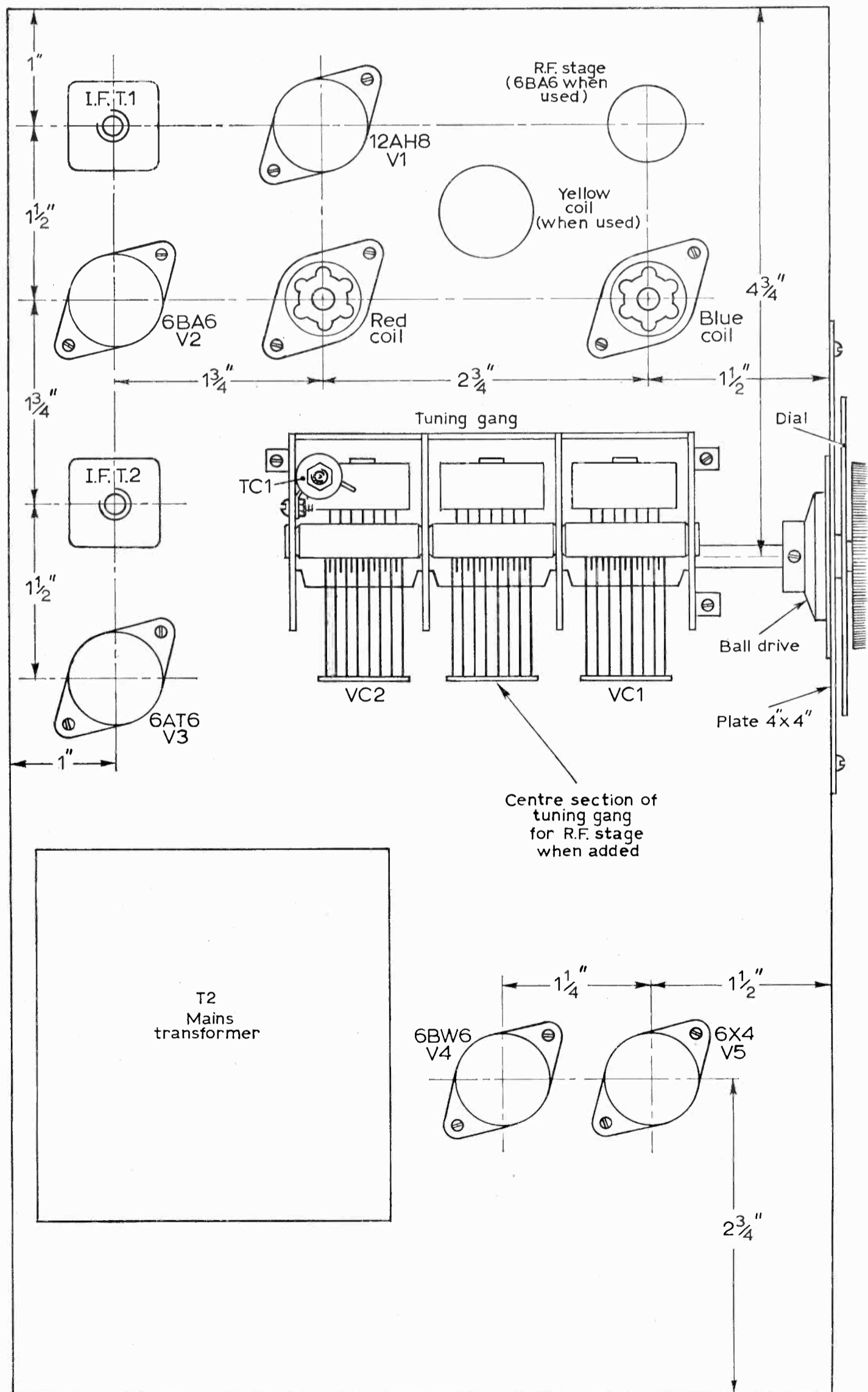


Fig.2. Top chassis layout

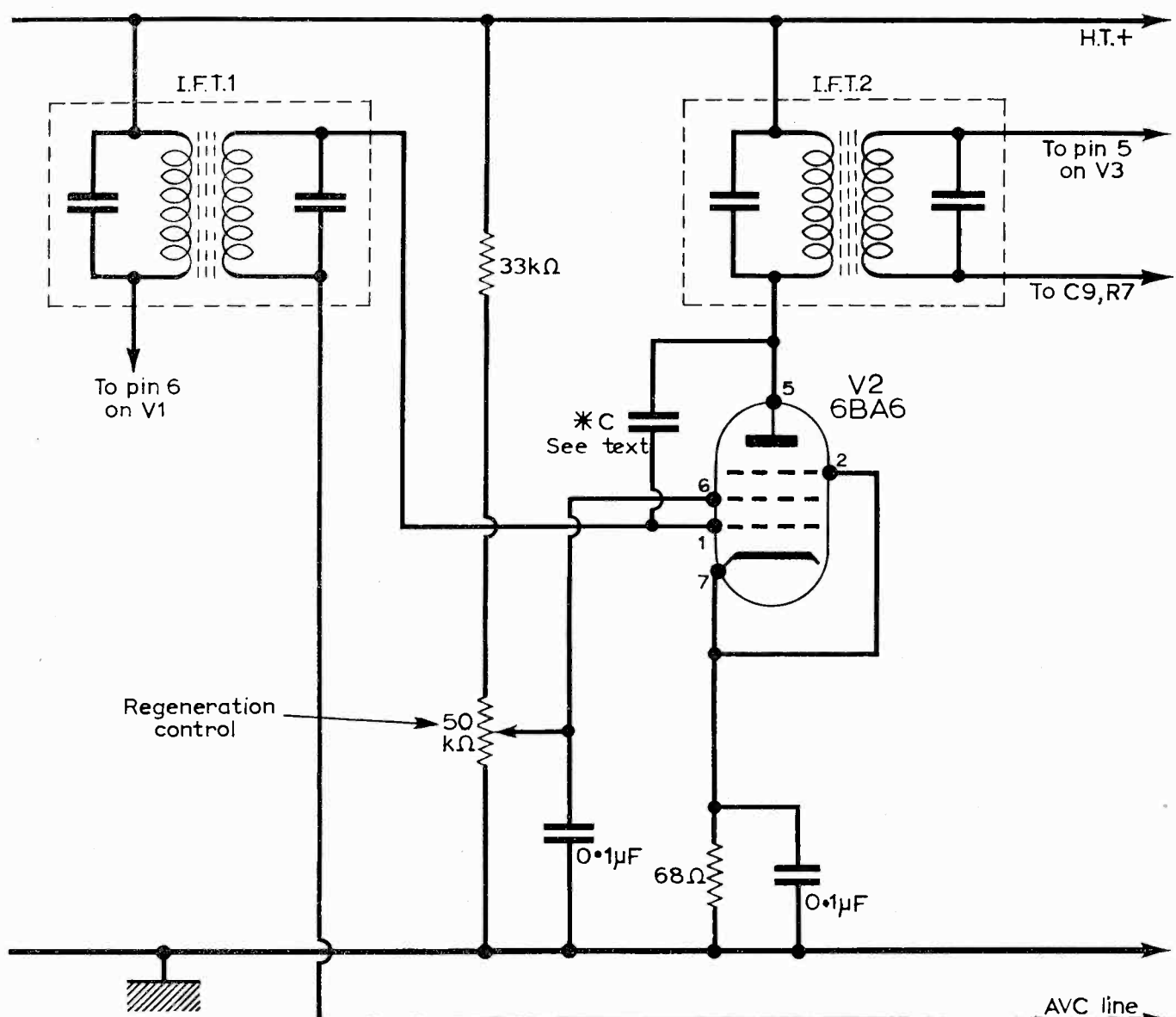


Fig. 5

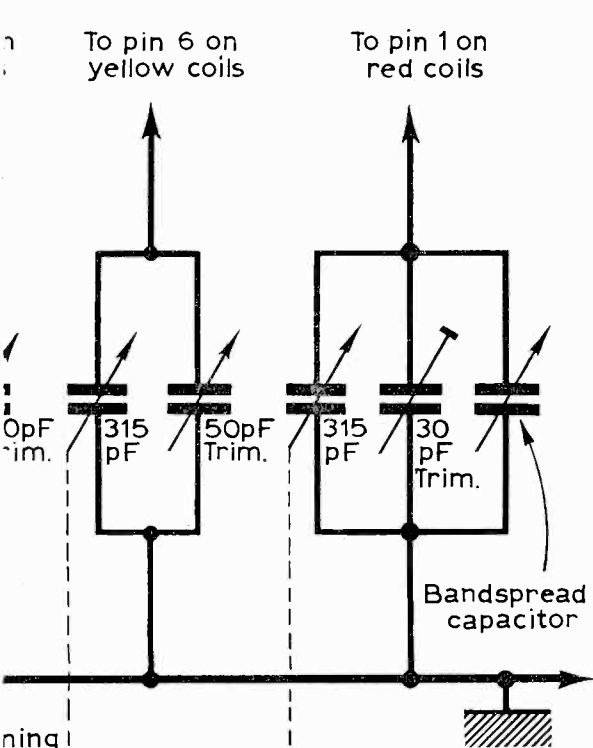


Fig. 7


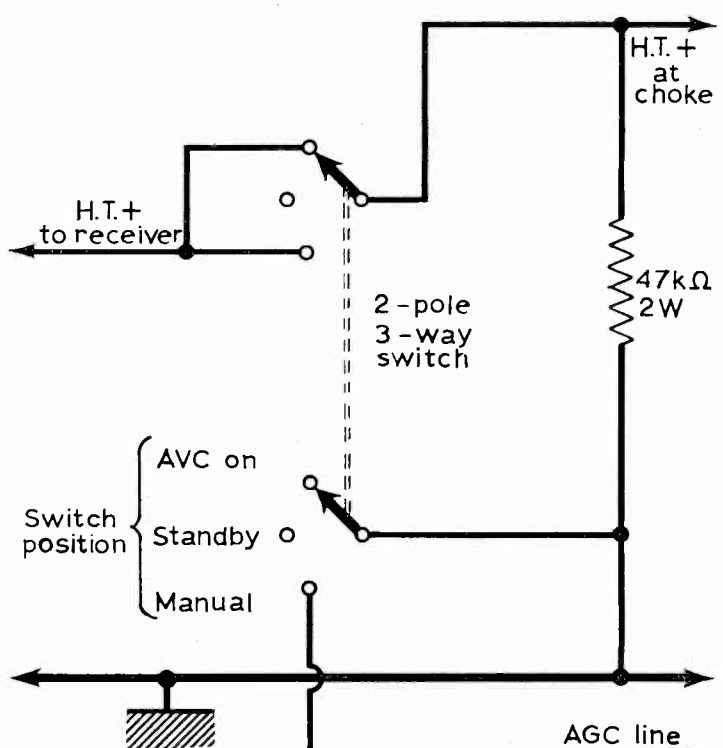


Fig. 8

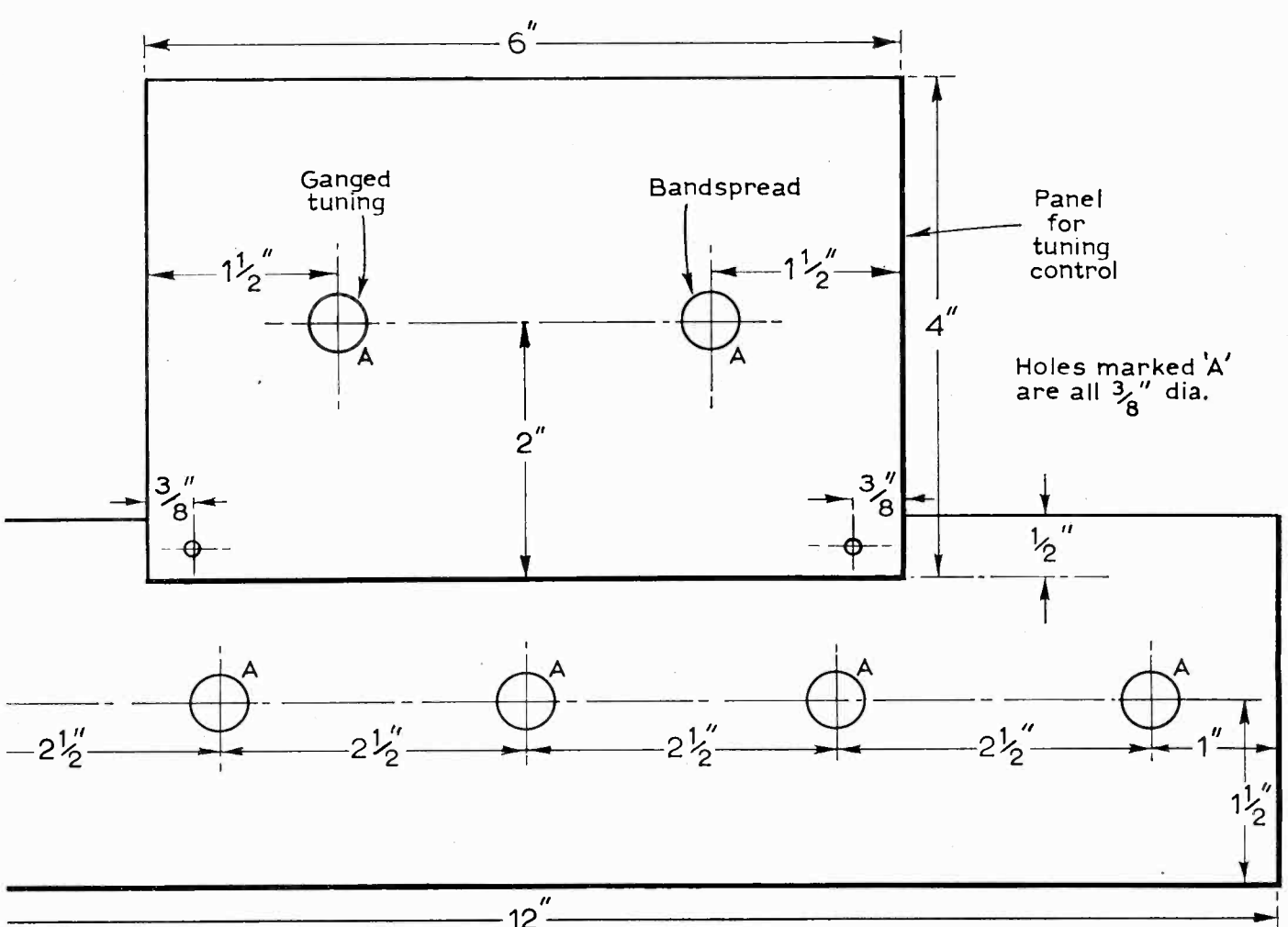

Front chassis and tuning panel

RESISTOR LIST

are plug-in coils, Blue (Aerial) and Yellow for r.f. stage

- 8 220kΩ
 - 9 220kΩ
 - 10 3.3kΩ
 - 11 2.2MΩ
 - 12 2.2MΩ
 - 13 470kΩ
 - 14 270Ω 1W
- unless otherwise

Miscellaneous:

Three B7G holders. Four B9A holders. VC1/VC2 3-gang 315pF capacitor. 6:1 ball drive. Bulgin scale and knob. Padders 350pF range 2, 1100pF range 3, 3000pF range 4. (Close tolerance silver mica).

VRI 1MΩ volume control with s.p. switch.

VC3 50pF air-spaced trimmer with knob. TC1 30pF beehive trimmer. Chassis 12 x 7 x 3 in. 60mA smoothing choke.

Additions:

Tuning Indicator, EM84. B9A holder. Two 470kΩ resistors.

Regeneration. 50kΩ potentiometer. Standby/AVC. 2-pole 3-way rotary switch. 47kΩ 2W resistor.

R.F. Amplifier. 6BA6. B7G holder. Yellow coils. 50pF trimmer with knob. 50kΩ potentiometer. Three 0.1μF 350V capacitors. 50pF and 100pF capacitors. 68Ω 33kΩ 100kΩ and 1MΩ resistors. B9A holder.

Bandspreading see text.

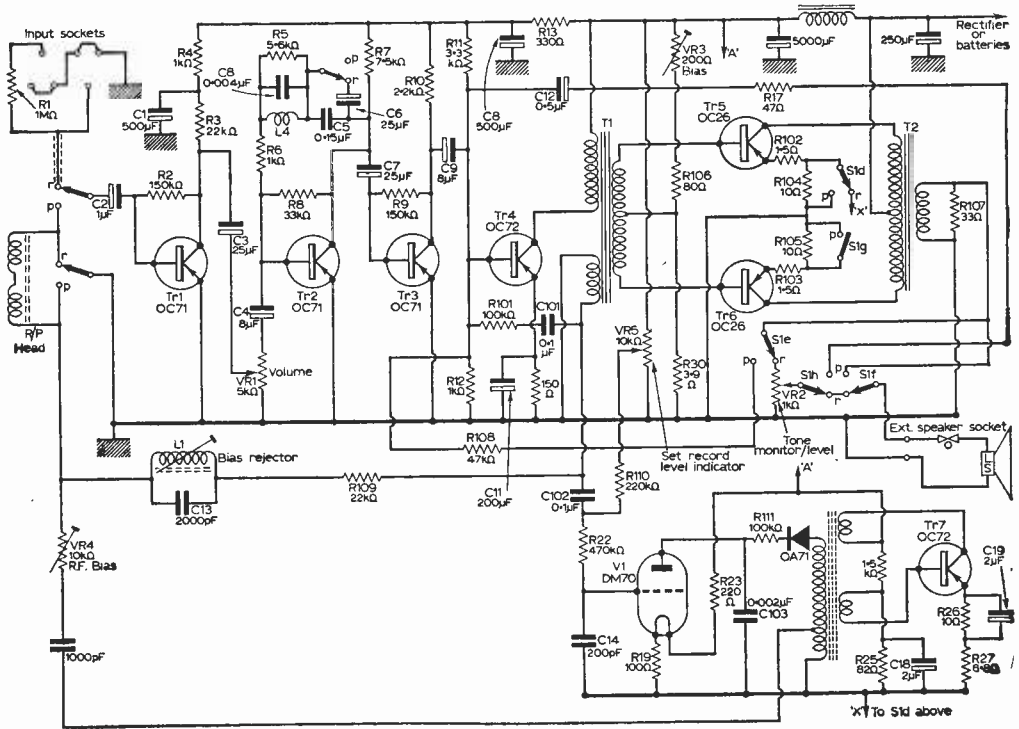


Fig. 5: Complete circuit diagram of the modified amplifier etc.

capstan idler wheel arm in position, and withdraw the split washer which holds the arm on to its pivot. Remove the arm and also the four Philips screws which hold on the sub-frame containing the motor, the recording head and the rewind idler-wheels. The erase head lever will have to be disengaged from its fork to do this. This procedure is not strictly necessary if the motor is being replaced by another identical part, but it makes work much easier.


Access to Amplifier

For the modifications to the amplifier, the back cover of the recorder must be removed. This is merely a matter of removing the four feet and lifting off the cover. The output transistors and the output transformer are at the input/output terminal side opposite the mains plug. With the exception of the power-pack and the running controls, all the rest of the components are on the printed circuit board. This board is removed by unscrewing the two retaining bolts at one end, lifting carefully with one finger holding the lever underneath which operates the record/play switch and, when the operating arm of the switch is clear, sliding the two pegs on the opposite end of the panel out of their grommets. It is important, incidentally, that these grommets should not be lost, as they act as insulators to prevent earth loops which would cause instability or excessive hum. The amplifier modifications can, however, be carried out without disturbing the board unduly, as the small parts required can be mounted

on the printed side of the board—i.e., facing upwards. Fig. 4 shows the locations of the extra components. Fig. 5 shows the circuit diagram of the completely modified amplifier.

It is advisable to set-up the values of bias and head drive on the make of tape which will be most used on the recorder. A make of tape which seems very tolerant of set-up conditions, and which works very well with the Metropolitan is the American "Lafayette" tape, which is marketed over here as "International" Tape at about 12/6 for a 1,200ft. 5½in. reel. Check that the head is perfectly clean, using nothing but a clean cloth to remove any oxide coating. First of all, set up the erase magnet position. Run a short length of tape through under recording conditions, but with no signal input and with the volume control turned down to prevent transistor noise being recorded. Note the position of this piece on the counter, replay at full volume and listen to the noise. Now make similar recordings on subsequent parts of the tape with the erase head slanted first one way then the other. The positions of the head can be charted by holding a straight-edge against the magnet and marking the line on the deck with a pencil. Now play back at full volume again and compare the three recordings for noise. If the initial recording was best, reset the magnet to this position. If one of the other positions was better, then another set of recordings must be made around that

—continued on page 906

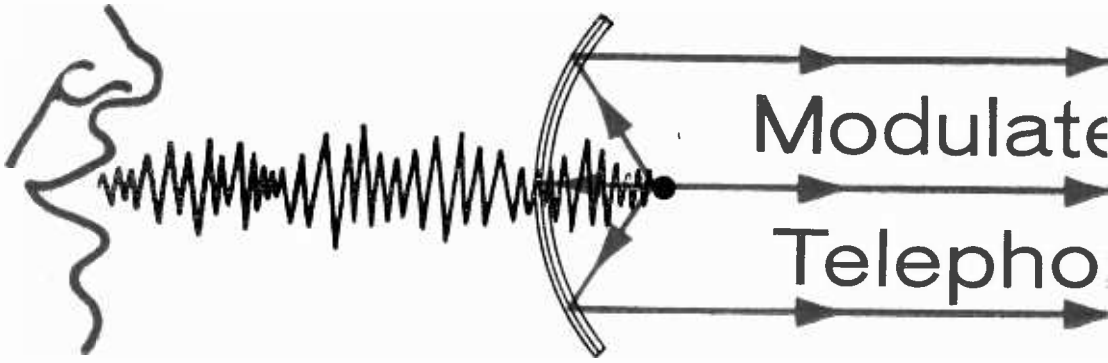

THIS article describes an interesting method of obtaining a short-distance, one-way telephone link between two points where the conventional wire connection is not possible. It is not the most efficient but it is straightforward and needs little extra equipment outside the assets of most readers.

The schematic diagram of Fig. 1 is an ideal way to use this apparatus. The a.c. source can be a microphone or a crystal set (in fact any means of producing a signal, even prerecorded music, although results will not be as good as speech). Amplifier 1 need only have an output of about 3W but amplifier 2 should have a larger gain and output capabilities of about 10W.

A two-way system can be constructed, duplicating each piece of apparatus. Or a switching device can be devised to enable one amplifier only to be used at each end.

The system was used successfully over a range of some 40yd; any smaller distances than this will produce good results. Greater distances will produce a weaker signal requiring greater amplification at the receiving end.

Basic Principles

If a source of modulated light is placed at the focal point of a spherical mirror then a roughly parallel beam of modulated light is produced. If in the same plane another similar mirror is placed with a photoelectric device for converting the

pulses of light received into similar pulses of electricity then a practical means of communication has been achieved.

Transmitter

This consists of a suitably chosen torch bulb connected across the secondary winding of an audio amplifier output transformer (Fig. 2a). It must be stressed that the right type of bulb is of the utmost importance. That is to say the resistance of the bulb should be in the same region as that of the loudspeaker removed from the amplifier; e.g. an output transformer needing a 15Ω speaker would require a 4½V bulb rated at 0.3A or a 9V bulb rated at 0.15A, etc.

It was found, however, that the temperature of the filament could not fluctuate fast enough to follow the complicated pattern of pulses fed into it from an a.c. source. This presented quite a problem until the idea of using a standing direct current was hit upon (Fig. 2b). This means that if pure a.c. is fed to a lamp the light output consists mostly of second harmonic distortion. This is because the filament heats up during each half-cycle. To avoid this frequency doubling it is essential to apply a d.c. bias equal to the peak a.c. input. Hence the use of s.d.c. In practice this was produced by placing a 3V battery in series with the output transformer and the bulb. The modulated light signal is then added to produce a small flicker of light on the basic s.d.c. Any large


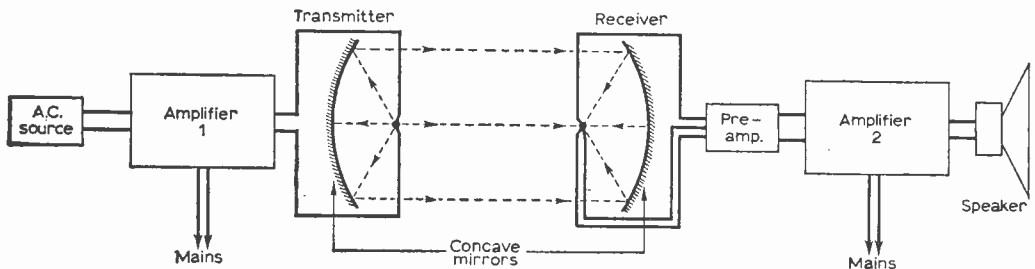


Fig. 1: Schematic diagram of the complete system.

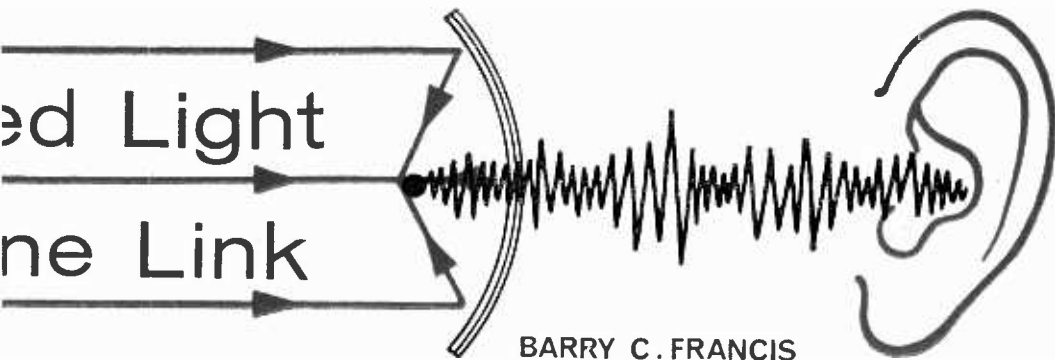

BARRY C. FRANCIS

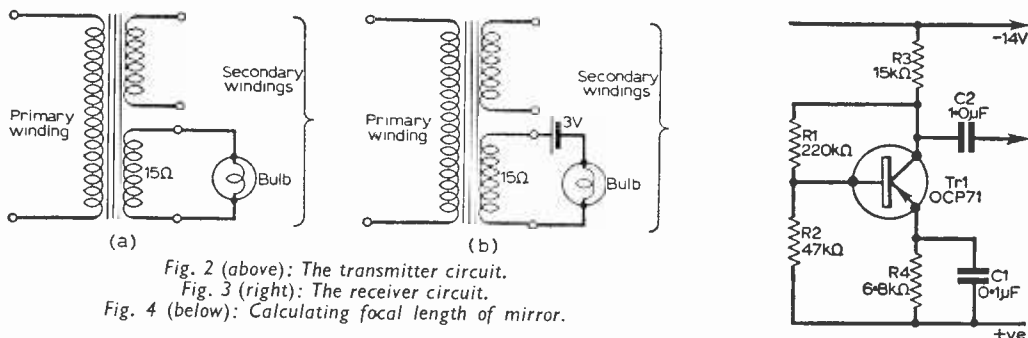


Fig. 2 (above): The transmitter circuit.

Fig. 3 (right): The receiver circuit.

Fig. 4 (below): Calculating focal length of mirror.

fluctuations were found to produce large amounts of distortion.

Receiver

The receiver consists of a Mullard phototransistor (OCP71) placed at the focal point of the second mirror. The associated light detector is merely for the conversion of the modulated light waves received into pulses of electricity ready for amplification.


The components were mounted on a six-way miniature group board which was housed in the vicinity of the mirror. It was found necessary to place R4 and C1 directly under the phototransistor.

Constructional Details

The unit to be described was designed for a specific purpose to fill certain requirements and, while it has fulfilled these, it may not meet the needs of every particular constructor. However, there are a few points that will apply to anyone making even a vaguely similar instrument and so for this reason alone the complete apparatus is described.

Mirrors

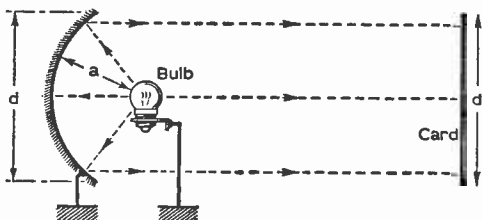The size of the mirrors used in each case will, of course, depend upon the distance over which



transmission is required. This is because the concave spherical mirrors used will give not a parallel beam of light but one that diverges. Therefore for the maximum amount of power to reach the receiver the transmitted beam should be as condensed as possible. The mirror that was found to be the most suitable for the transmitter had a diameter of 4in. The one used in the receiver had a diameter of 6in., and a focal length of 3in., the distance of transmission being 50yd.

The focal length of a concave mirror can be calculated roughly as follows (the focal length of each mirror is required for the positioning of phototransistor and transmitting bulb): Secure the mirror in the vertical position as shown in Fig. 4. Support the torch bulb so that its filament is directly in line with the centre of the mirror. This

continued over

can be done by obtaining a length of stiff wire and making a loop at one end to enable the bulb to be held by its base. The other end of this wire can be secured to a small block of wood to hold it vertical. Now place a white card with a circle the same size as the reflecting part of the mirror

traced on it facing this mirror (Fig. 4). Switch on and move the bulb along a line parallel to both mirror and card until a circle of light of diameter "d" appears on the card. The bulb is now at the focal point of the mirror and the distance "a" from its centre can be measured and recorded.


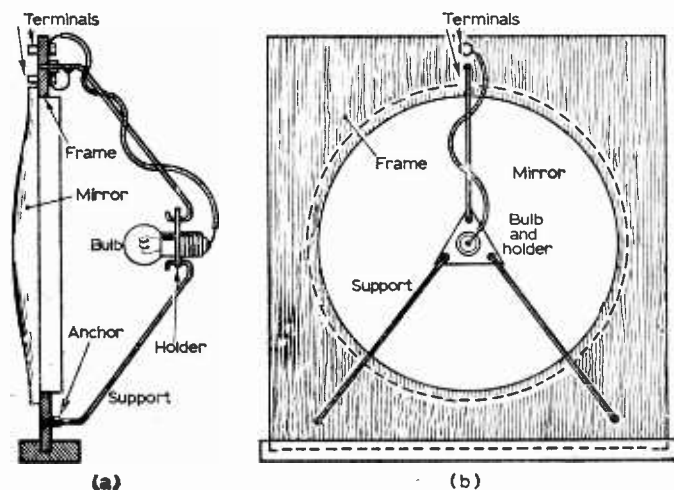
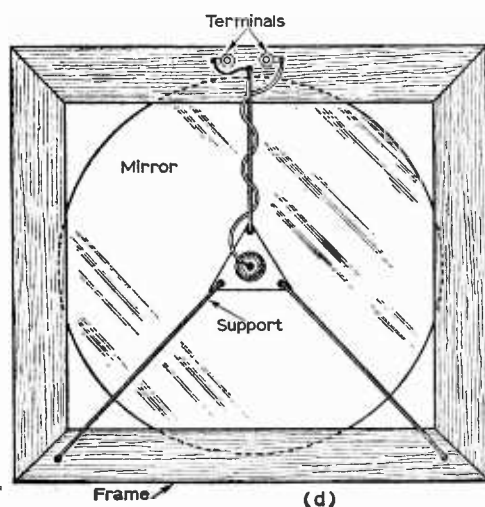


Fig. 5: Constructional details of the mirror unit.

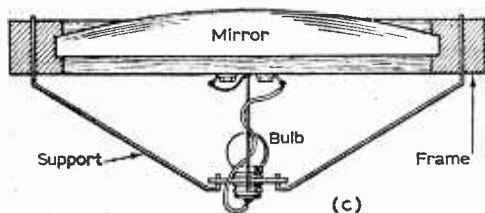

Transmitter

Fig. 5a shows a side elevation of the completed transmitter. The concave mirror was mounted on a piece of five-ply (Fig. 5b gives a front view of Fig. 5a). This mounting may prove difficult for any mirror without a backplate and so an alternative mounting position is shown in Figs. 5c, d.

The sides for this case were made from strips of balsa wood $1\frac{1}{4}$ in. square, glued together as shown. The actual bulb support was fashioned from an old piece of toothpaste tube that had been cleaned and battered into a triangle of side $9/10$ in. Three pieces of galvanised wire were constructed as supports and soldered to the triangular piece of metal, one at each corner, after a hole had been drilled to accommodate the bulb. The other ends of these pieces of wire were placed through holes in the mirror mounting. One of these supports formed the connection to the bulb case. The other connection (to the base of the bulb) was made by carefully heating the nipple and attaching to it a piece of wire. This wire was then twined around one of the supports and taken to the back of the mirror. The supporting wires were made about 10% longer than necessary (i.e. "a") so that final adjustment of the bulb could be obtained.

When this position was obtained the connecting leads to the centre of the bulb were strapped to the upper support. The supporting wires were then anchored by attaching insulating tape on their inside in the form of a role as illustrated in Fig. 5a.

Receiver

The support for the phototransistor (Figs. 6a, b) is slightly different from that of the transmitter. The actual frame supporting the phototransistor was made from one piece of galvanised wire stretched across the full length of the mirror and attached at either end to the mirror frame as illustrated in Fig. 6b. A third piece of wire was then attached to the centre of this and to the base of the frame. The centre attachment was then effected, using a strong solder joint. For this the wire must be clean.

The transistor holder consisted of two pieces of aluminium about the width of the transistor base

and measuring 1½ in. long. This piece of metal is shaped so as to hold the transistor in a clamp.

CAUTION: The metal must not be wrapped too firmly around the transistor base.

The transistor was soldered, using a heat shunt, and the connecting wires attached.

The horizontal position of the phototransistor can be altered by adjusting bolt A (Figs. 6a 7a) and its distance from the mirror can be altered by moving the supports in or out. The part of the transistor facing away from the mirror was hooded as shown in Fig. 7b to prevent interference from unwanted sources.

The most sensitive part of the transistor is near the top directly above the words OCP71, but it should be moved about until, after focusing the best results are obtained. The connecting wires can be wound around any support in the same manner used for the transmitter. The two components mentioned earlier should be strapped to the centre support directly under the transistor.


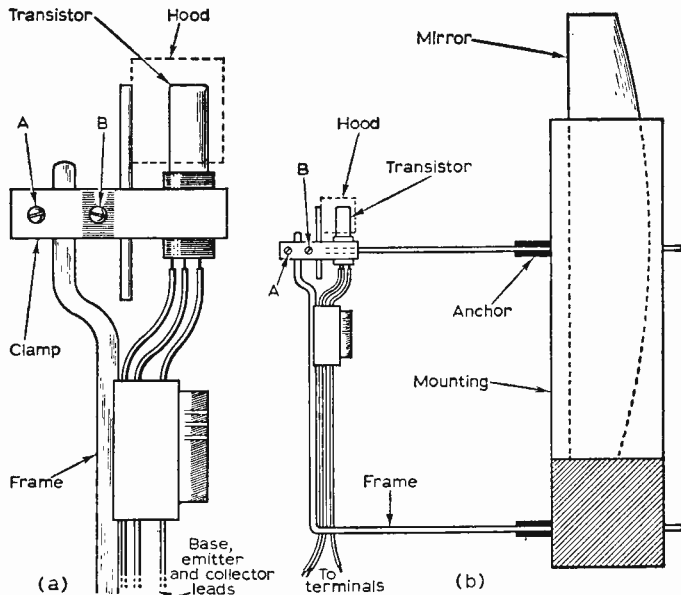


Fig. 6 (above) and Fig. 7 (below): Details of phototransistor support and transistor hood.

Lining Up

The process of lining up the transmitter and receiver is straightforward if carried out carefully. If the bulb used is rated at 4V 0.3A then an ordinary battery placed across it will give a bright enough beam to be seen. From the first mirror the spot of light produced by the second mirror can then be focused on the most sensitive part of the phototransistor. This lining up is best carried out under poor light conditions as the beam can be seen more easily. If the transmitter is for use out of doors then the best time would be around dusk.

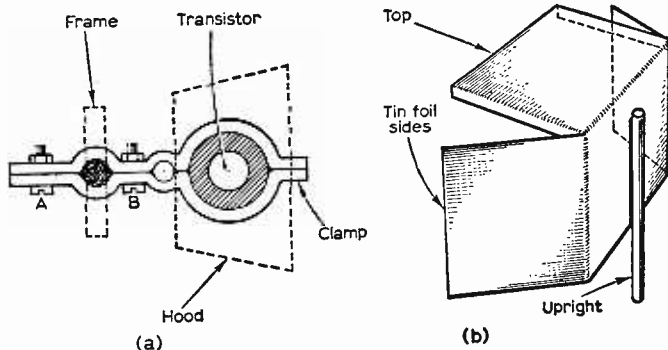

When the lining up has been completed the 4V battery can be disconnected and the circuit connected up.

MEASUREMENTS WITH GDO

—continued from page 854

local oscillator in a receiver or a stage in a transmitter. With an appropriate coil in position the dial is turned until a rise is obtained on the meter. This indicates the resonant point and the dial reads the frequency. If it is suspected that the local oscillator of a receiver is inactive then the GDO can be tuned to about the correct frequency (i.e. signal minus the i.f. frequency) and made to oscillate, then when it is coupled to the local oscillator circuit the receiver should start to

function, the GDO now supplying the local heterodyne signal.

These are a few of the uses of a GDO and if the constructor new to this type of instrument builds one, then a good idea is to set up odd tuned circuits, lengths of wire, etc., and practice using the instrument. After a short while the characteristics will be understood and it can be used on actual apparatus without much fear of false readings or whether in fact a resonance dip is being obtained. After some time it becomes possible to judge the "Q" of circuits by the sharpness of the dips.

Room for Everyone

FORTUNATELY there are always beginners in any hobby, but in an era of highly sophisticated and competitive telecommunications there is also clear need for those who wish to keep abreast with the times.

Those of us who have long since graduated from the bread-board and coffee-can stage cannot deny that the complexity of modern multi-band communications equipment, capable of reliable world coverage with minimum interference to other users, is beginning to place advanced design and self construction beyond the scope of most non-professional enthusiasts.

Constructor versus operator is a played out theme, damaging to the true image of the radio amateur. Given tolerance, there is still room for everyone in the game and it is perhaps sobering to reflect that the knowhow of getting a signal up and away counts for as much, if not more, than its mere generation.

Surely we are judged not by the equipment on our shack table but in what we say and how we behave whilst communicating.

T. S. Tatton, G2BSR.

Churchdown,
Gloucestershire.

P.W. Copies

I HAVE 36 copies of PRACTICAL WIRELESS complete (1962-3-4). If any of your readers are interested and wish to contact me, I will be willing to sell them at a reasonable price.

All enquiries must be accompanied by a stamped, addressed envelope.

G. N. Skinner.

29 Highbury Hill,
London, N.5.

Tapespondent Wanted


I WOULD to tapespond with anyone interested in Short Wave Listening and who is about 15 years old. My tape recorder is a Corsor 1602/04, 4-track, 3½ i.p.s. and can take up to a 7in. spool.

David Griffiths.

18 Northwood Gardens,
Clayhall,
Ilford,
Essex.

NEWS AND..

BAIRD STEREOGRAM MODEL 102

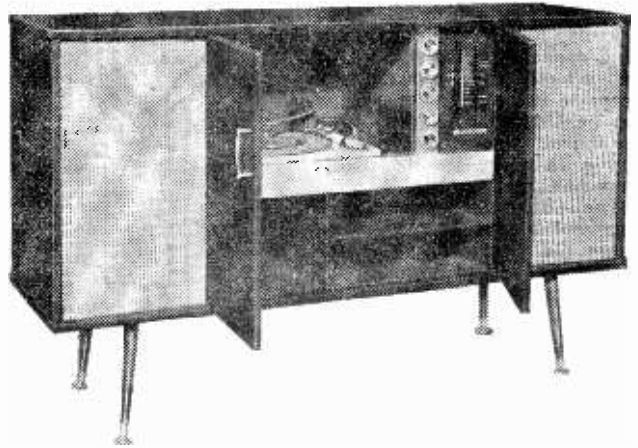

From Baird TV Distributors Ltd., Empire House, 414 High Road, Chiswick, London, W.4, comes the 102 stereogram.

On opening the doors, the auto player is illuminated. Up to ten mono or stereo records can be loaded on to the record changer, and there is ample room for record storage.

This fully-transistorised a.m./f.m. radio has twin transistorised amplifiers. Separate bass and treble controls are provided and there is push-button switching between wavelengths and 'gram.

The size is 50½ in. wide x 16 in. deep and 22½ in. high (excluding legs). The circuit contains 19 transistors and four diodes and sockets are provided for tape recording and external speakers. The price is 85 guineas.

AERIALS FOR THE MINISTRY

The Ministry of Aviation have recently awarded two important contracts with Modern Aerials Ltd., a Member of the Controls and Communications Group of Companies. One for over £100,000 for the supply of a large quantity of their 27ft Telescopic Aerial Masts, and one for £26,000 for a larger quantity of "walkie talkie" aerials.

RADIOTELEPHONE SYSTEM TO BEAT CRIME

A new police radiotelephone system, the first of its kind in the world operating on a secret channel in the u.h.f. band, was officially opened today by the Glasgow police in their Pollok sub-division.

The use of this new frequency band means that police messages can be passed in secrecy because information transmitted on u.h.f. cannot be picked up by unauthorised persons listening on domestic radio receivers.

By utilising ultra high frequencies it has been possible for the first time to ensure highly efficient two-way radiotelephone communication between the police station and foot patrol men throughout the Pollok sub-division. All wires and cumbersome aerials previously associated with walkie-talkie equipment have been eliminated.

The equipment used is designed and manufactured by Pye Telecommunications of Cambridge.

.. COMMENT

"PROTON-2" SPACE STATION LAUNCHED

A heavy scientific space station, Proton-2, has been launched in the Soviet Union.

In addition to scientific and measuring instruments, the space station carries a radio transmitter working on the frequency of 19.545 Mc/s. The information sent from the station shows that all scientific equipment on board is functioning normally. The telemetered information is then processed at the co-ordinating and computing centre.

STEREO MUSIC WHILE YOU DRIVE

A new car-stereo set, which plays continuous music from a wide range of pre-recorded tapes, is now on the market from Skytone Electronics Ltd., superseding the model introduced with great success some time ago.


Called the Craig Car-Stereo, it is fully transistorised, completely self-contained with two speakers, and fits compactly under the dashboard. Because it is independent of a car-radio, the stereophonic reproduction is of superb quality, with no crackling or fading at any speed or over any surface.

You slip the cassette—with vocal, instrumental or orchestral tape—into the set, and it starts playing immediately. There are two pre-set playback heads, operated by a flick of a switch to change tracks. Tape cassettes can be changed with one hand. The tapes are of 30 minutes and one hour's duration and repeat until switched off.

Retailing at 46 gns., with tapes at £2 (½ hour) and £3.9.6 (1 hour), the Craig Car-Stereo is marketed by Skytone through Hasmick Promotions Ltd., 13 Elvaston Place, London S.W.7.

SPECIFICATION—Tape speed: 3.75in. per second. Playback method: Quarter track in-line stereo playback 2 head system. Drive motor: 12V D.C. brush type with governor. Output power: 8W (4W per channel) at 4 ohms. Frequency response: 100-6,000 cps + 3dB. Speaker impedance: 4-6 ohms. Power requirement: 12V d.c. (10.7-14.5V) 1 amp maximum, negative ground. Controls: volume, balance and tone. Amplifier: 12 transistors. Dimensions: 3½in. (H), 9½in. (W), 9¼in. (D). Weight: 11 lb.

NEW ARCOLECTRIC SWITCHES

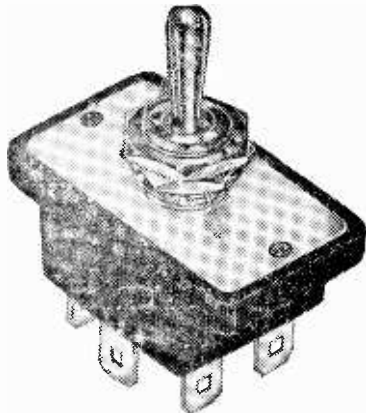

Recent additions to the Arcolectric range of switches are the "27" and "28" ranges of lever and semi-rotary switches. The "27" range switches are normally assembled with nickel plated brass lever and fixing neck. Alternatively, switches can be assembled with black nylon fixing neck and nylon lever to meet double insulation requirements.

The photograph shows Cat. No. C273, a double-pole double-throw three-position lever switch with centre OFF position.—Arcoelectric Switches Ltd., Central Avenue, West Molesey, Surrey.

Home-Built Equipment

BEFORE too much printer's ink is spilled on the subject of home-built equipment, perhaps I may be permitted to express a point of view, from the outside fraternity, so to speak?

Many letters printed in your columns emanate from "called signed enthusiasts" and the like—types who doubtless eat, drink and sleep radio! One wonders, sometimes, do they realise there are snags to home-building equipment.

I have been "doing it" and "making it" myself for as long as I can remember—woodwork, metalwork, pretty well anything that is going. Now, of latter years, influenced by P.W., P.E. and similar publications, I have built the "Citizen" transistor radio, a very good R-C bridge, several test meters and am now embarking on the Beginner's Short Wave Superhet.

For my part, building equipment can take months mainly due to the difficulty of obtaining components (without the expense of special journeys to suitable cities, of course). Given the tackle, I can build — so what about the chap who's not too good at it anyway. Don't be too hard on him with his factory-built set!

R. Brown,

Salisbury,
Wiltshire.

Any Offers?

I HAPPENED to read a copy of PRACTICAL WIRELESS, which is very interesting indeed! Although I would love to subscribe to P.W., it is rather difficult for us here to remit the subscription due to the recent foreign exchange restrictions.

I wonder whether any of your readers would be kind enough to offer a gift subscription which will be fully compensated by a similar gift subscription for any Indian publication of their choice. Alternatively, regular mailing of old copies of PRACTICAL WIRELESS would do.

B. G. Kamath.

7 Ramdevi Mansion,
10th Road, Khar,
Bombay-52, India.

Modifying Mains Transformers

B. C. MACDONALD

THE usual mains transformer has three output windings, and these are normally a high tension winding which gives say 350—0—350V, a valve heater winding giving 6.3V and a rectifier winding giving 5V. It is quite easy to alter either or both the 5V and 6.3V windings or to remove them both and put on a new winding. If the high tension winding is removed as well as the low voltage windings a new winding can be put on to give a variety of low voltage taps from 1V to 40V or more, in selected steps.

The work of rewinding is not tedious because the wire is thick and the turns comparatively few. A normal 6.3V winding only contains some 25 turns. Such a modified transformer is clearly useful and can be used as a filament transformer allowing high voltage valves to be run in parallel.

The first step in making the modification is to dismantle the transformer so that we can remove the coil. It will be found that the core laminations are held together by two screws, which also serve as fixing screws. If the nuts are unscrewed and the screws removed any screening cap that may be fitted can be pulled clear, if the transformer is not screened there will simply be two end rims to pull off. The core that remains is built up from a large number of thin iron stampings fitted, or laced together as shown in Fig. 1. These stampings must be prised apart to release the coil, use a small

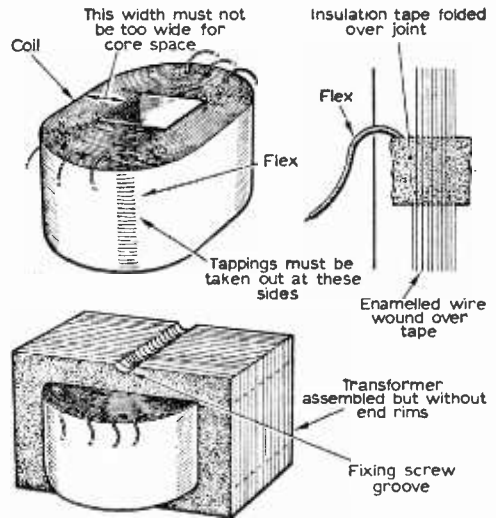


Fig. 2: Details of transformer construction.

pocket screwdriver and release the long strips first, then withdraw the stampings out of the coil. Be very careful not to damage the coil and note the order of assembly, since it may differ from that shown, and must afterwards be replaced in the same way.

The coil is usually wrapped in waxed paper and the outer covering of this should be torn away to reveal the top winding. This can then be removed to give access to the lower winding which, if desired can also be removed. Below this lies the high tension winding of a very large number of turns of very fine wire. This winding cannot be altered and unless it is intended to remove it, it should not be uncovered. If it is desired to remove the high tension winding, each layer should be cut through with a pair of nail scissors, great care being taken not to damage the mains winding which lies beneath. It is impracticable to try and unwind this winding, hence the reason for cutting through each layer.

This is how we dismantle the transformer, but it is essential before we remove the top windings that we should count the number of turns in them. This is best done by drawing the point of a pencil slowly across the wires and counting the "bumps". Make a note on paper of the result, 5V winding 19 turns or 6V winding 23 turns and so on.

Suppose we wish to add a 19V winding in place of the 6.3V winding. We know this latter winding contains 23 turns so we calculate thus:

$$23 \times \frac{19}{6.3} = 69.4$$

or nearly 69 and a half turns are required on the new winding, in fact the half turn can be disregarded. If we had wished to reduce the voltage of the new winding from 6.3V to 3V, the calculation would have been:

$$23 \times \frac{3}{6.3} = 11 \text{ turns.}$$

—continued on page 904


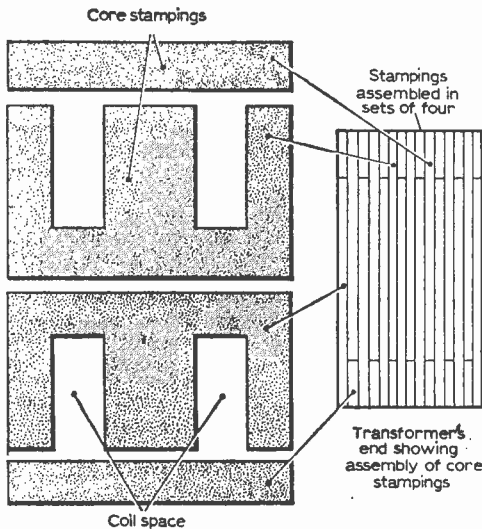


Fig. 1: Assembly of core stampings.

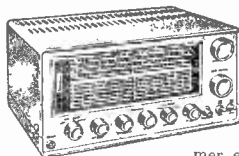

LAFAYETTE HA 63 COMMUNICATION RECEIVER


7 valves + Rectifier. 4 Bands 550 Kc/s-31 Mc/s. 'S' Meter-BFO-ANL-Bandspread Tuning. 200/250v. A.C. Brand New. 24 Gns. carr. paid.



NEW MODEL LAFAYETTE HA-230 AMATEUR COMMUNICATIONS RECEIVER

Supersedes model HE-30. 8 valves + rectifier. Continuous coverage on 4 bands. 550 Kc/s-30 Mc/s. Incorporates 1 RF and 2 IF stages. Q Multiplier, BFO, ANL, 'S' meter, electrical bandspread, Aerial trimmer. Supplied brand new and guaranteed. 33 Gns. SAE for full details.

Also available in Semi-Kit form 25 Gns

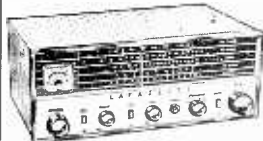

STAR SR 40 COMMUNICATION RECEIVER

4 Bands 550 Kc/s-30 Mc/s. 'S' Meter - BFO - ANL - Bandspread Tuning-Built in speaker, 200/250v. A.C. Brand New. 184 Gns. Carriage 10/-.

OS/8B/U OSCILLOSCOPES

High quality Portable American Oscilloscope. 3in. c.r.t. T/Y 3c/s-50 kc/s X Amp. 0-500 kc/s Y Amp. 0-2 Mc/s. Power requirements 105-125v. A.C. Supplied in "as new" condition, fully tested. £25. Carr. 10/-. Suitable 230/115v. Transformer. 15/6.



CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil panel meters available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows. Type MR38P 1 1/2 in. square fronts.

2mA	22/6
5mA	22/6
10mA	22/6
20mA	22/6
50mA	22/6
100mA	22/6
150mA	22/6
200mA	22/6
300mA	22/6
500mA	22/6
100µA	22/6
200µA	22/6
500µA	22/6
100-500µA ..	22/6
100-0-100µA	27/6
100-0-500µA	22/6
1mA	22/6

3V. DC	22/6
10V. DC	22/6
20V. DC	22/6
50V. DC	22/6
100V. DC	22/6
150V. DC	22/6
300V. DC	22/6
500V. DC	22/6
750V. DC	22/6
15V. AC	22/6
50V. AC	22/6
150V. AC	22/6
300V. AC	22/6
500V. AC	22/6
'S' Meter 1mA	29/6

POST EXTRA. Larger sizes available. ILLUMINATED "S" METER 1 1/2 in. square front. Cal. in S units, 6V. lamp. 29/6. P.P. 1/-. Ditto 2 1/2 in. square. 39/6. P.P. 1/-.

AVOMETER MODEL 7



First class condition, fully guaranteed. Complete with leather case and leads. 13 gns. P. & P. 5/-.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with bats, & wall bracket. 7 gns. part. P. & P. 5/-.

TWO-WAY RADIOS

Superb quality. Complete with all accessories and fully g't'd. 3 Transistor £7.19.6 pr. 4 Transistor 11 gns pr. 5 Transistor 19 gns pr. 10 Transistor 28 gns pr. Post extra. (S.A.E. for full details).

ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPES



Timebase 2 c/s-750 kc/s. Separate X1 and X2 amplifiers. Up to 5.5 Mc/s. calib at 100 kc/s. and 1 Mc/s. 110/230 v. A.C. Guaranteed perfect. £27.10.0. Barr. 20/-.

MINE DETECTOR No. 4A

Will detect all types of metals. Fully portable. Complete with instructions, 39/6 each. Carr. 10/- Battery 5/6 extra.

MAGNAVOX 363 TAPE DECKS

New 3 speed tape deck, supersedes old Collaro studio deck. 2 track. £10.10.0. 4 track. £13.10.0.

SILICON RECTIFIERS

200 P.I.V. .. .	20mA	2/6
1,000 P.I.V. ..	650mA	7/6
800 P.I.V. .. .	500mA	5/6
400 P.I.V. .. .	3 amp	7/6
400 P.I.V. .. .	500mA	3/6
150 P.I.V. .. .	165mA	1/-
70 P.I.V. .. .	1 amp	3/6
35 P.I.V. .. .	3 amp	5/6

Post extra.

AMERICAN TAPE

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities. 3in. 2551 L.P. 4/- 3in. 600ft. T.P. mylar 10/- 5in. 600ft. std. plastic 8/6 5in. 490ft. L.P. acetate 19/- 5in. 1200ft. D.P. mylar 15/- 5in. 1800ft. T.P. mylar 25/- 5in. 1200ft. L.P. acetate 12/6 5in. 1800ft. D.P. mylar 22/6 5in. 2400ft. T.P. mylar 45/- 7in. 1200ft. std. m.lar 12/6 7in. 1800ft. L.P. acetate 15/- 7in. 1800ft. L.P. mylar 50/- 7in. 2400ft. D.P. mylar 25/- 7in. 3600ft. T.P. mylar 58/6 Postage 2/- Over 43 post paid.

VOLTAGE STABILIZER TRANSFORMERS

Will stabilize your mains voltage. Ideal for TV receivers and industrial equipment. Input 80-120 v. and 160-240 v. Constant output 110 v. or 240 v. 250 watt's. Brand new guaranteed. £10.10.0 Carr. 7/6.

VARIABLE VOLTAGE TRANSFORMERS


Brand New Guaranteed. Fully Shrouded. Input 230v. 50/60 c/s. Output 0-260 v. 1 Amp £4.10.0 2.5 Amp £5.17.6 5 Amp £9. 0.0 8 Amp £13.10.0 10 Amp £17.19.0 12 Amp £19.15.0 20 Amp £32.10.0 2.5 Amp Portable Metal Case with Meter, Fuses, etc. £9.17.6.

NEW MODEL LAFAYETTE HA-55 AIRCRAFT RECEIVER

108-136 Mc/s. High selectivity and sensitivity. Incorporates 2 RF stages including 6CW4 Nuvistor. 8 tubes for 11 tube performance. Solid state power supply. Adjustable squelch control, slide rule dial, built in 4in. speaker and front panel phone jack. 220/240v. A.C. Supplied brand new and guaranteed. 19 Gns. Carr. 10/-.

TE-22 SINE SQUARE WAVE AUDIO GENERATORS

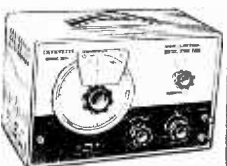Sine: 20 c.p.s. to 200 Kc/s on 4 bands. Square: 20 c.p.s. to 25 Kc/s. Output imp. 500Ω 60ms. 200 240 v. A.C. Brand new Guaranteed. £15. Carr. 7/6.




LAFAYETTE 46 RESISTANCE CAPACITY ANALYSER

2Pf. 2,000 mF/d. 2 ohms, 200 megohms. Also, checks impedance. Turns ratio. Insulation 200/250v. A.C. Brand New. £15. carr. 7/6.

LAFAYETTE NUVISTOR GRID DIP METER

Compact true one hand operation. Frequency range 1.7-180Mc/s. 230v. A.C. operation. Supplied complete with all coils and instructions. £12.10.0, carr. 5/-.

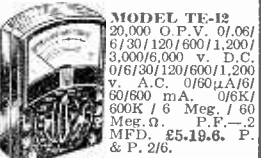

MODEL 500

30,000 o.p.v. 0/5f 112.5/1025/50/100 250/1500/1,000 v. DC 0/2.5/10/25/100/250/500/1,000 v. AC 0/50/1A/5f 50/500mA/12amp DC. 0/60K/6 Meg/60 Meg. Post £8.17.6. Paid, S.A.E. for full details.

TE-51 NEW 20,000Ω VOLT METER

0/16/80/120/1,200 v. AC. 0/3/30/60/300/600/3,000 v. DC. 0/60µA/12/300 mA DC. 0/60K/6 Meg. ohm. £45.0. Post & pack. 2/6.

OPEN 9 a.m. to 6 p.m. EVERY DAY MONDAY-SATURDAY Trade Supplied.

G.W. SMITH & CO (RADIO) LIMITED
 Phone: GERRARD 8204/9155
 Cables: SMITHEX LESQUARE
 3-34 LISLE STREET, LONDON, W.C.2

TRANSISTOR ELECTROLYTICS

COMPARE THESE PRICES!

32µF	1.5 volt	25µF	6 volt	4µF	15 volt
·25µF	3 volt	30µF	6 volt	5µF	15 volt
2µF	3 volt	50µF	6 volt	6µF	15 volt
3µF	3 volt	100µF	6 volt	8µF	15 volt
8µF	3 volt	2µF	9 volt	16µF	15 volt
10µF	3 volt	10µF	9 volt	32µF	15 volt
12µF	3 volt	20µF	9 volt	50µF	15 volt
20µF	3 volt	2µF	12 volt	64µF	15 volt
30µF	3 volt	3µF	12 volt	2.5µF	25 volt
40µF	3 volt	4µF	12 volt	16µF	25 volt
·25µF	6 volt	10µF	12 volt	32µF	25 volt
2µF	6 volt	20µF	12 volt	2µF	30 volt
3.2µF	6 volt	25µF	12 volt	16µF	30 volt
4µF	6 volt	30µF	12 volt	25µF	30 volt
8µF	6 volt	1µF	15 volt	1µF	50 volt
10µF	6 volt	2µF	15 volt	5µF	70 volt

All the above at 1/2 each.

320µF	2.5 volt	250µF	15 volt	150µF	25 volt
200µF	3 volt	500µF	15 volt	100µF	30 volt
250µF	6 volt	100µF	18 volt	200µF	30 volt
400µF	6 volt	64µF	25 volt	50µF	150 volt

All the above at 1/6 each.

1,000µF	6 volt	750µF	15 volt	1,000µF	25 volt
1,000µF	12 volt	1,000µF	15 volt	500µF	50 volt
4,000µF	12 volt	500µF	25 volt	1,000µF	50 volt

All the above at 2/- each.

200/100µF, 257V or 200/200µF, 275V 6/6 each

CONDENSERS

Silver Mica, 3-3pF to 6,800pF. Including High Voltage Disc Ceramics (normally 3/- each) 10/- per 100
Paper Condensers: ·0001µF, ·001µF, ·002µF, ·005µF, ·02µF and ·04µF, all at 7/6 per 100. £3 per 1,000; ·1µF, ·25µF, ·5µF, 10/- per 100.

RESISTORS

1/10th, 1/6th, 1/4th, watt 10/- per 100
Mixed wattages 1/2 watt to 3 watt. Close Tolerance. Assorted Values. Polythene wrapped on cards of 10. Give-away price, 50/- per 1,000, plus 5/- post and packing.

TRANSISTORS (At a price you can afford)
OC71 equivalent, 1/- each, 25 for £1, 100 for £3.
NKT124 or NKT125. Switching transistors, 2/- each, 6 for 10/-.
Large Car Radio type Output Transistors, OC25, OC35, NKT405, 10/- each.

Packet containing: three 2G417, two 2G371, one 2G381, one 2G339, one diode (for making superhet with complementary symmetry transformerless output stage) ... £1 complete
Diodes, 1/- each. Zener Diodes, ZE12, ZB4-3, 5/- each.
BY100 Mains Rectifiers for TV Sets. 7/6 each.

SIGNAL INJECTOR. R.F./I.F./A.F. Transistors, components and circuit to make. Only 10/- complete.

LOUDSPEAKERS. Brand New, 4 inch. Excellent reproduction. 10/- each.

Midget Earpieces, complete with plug and lead	5/- each
Magnetic Lapel Microphone with plug and lead	10/- each
Transistor Holders	1/- each
Miniature Soldering Irons, complete with Bit	30/- each
Set of 5 assorted Bits to suit any job	20/- set
Crystal Set kits	15/- each
POCKET-SIZE MULTIMETERS, AC/DC/Ohms	£3
Transistor Intercom. Units	55/- pair

FLUORESCENT FITTINGS: 5ft. with choke and starter, 39/6; 4ft. with choke and starter, 32/6. Carriage 10/- per fitting.

ACOS PICK-UP HEADS. COMPLETE WITH NEEDLES
This is the price you would expect to pay for the needles only!

Monaural	14/-
Stereo	21/-
Diamond Stereo	28/9

Will fit most record changers. Can be very profitable!


RELAYS

700 ohm or 2,500 ohm coil. Transparent dust cover. 2 pairs of change-over contacts. PLUG-IN TYPE. Base included in price. 25/- each.
For orders less than 10/- please add 6d. towards postage.

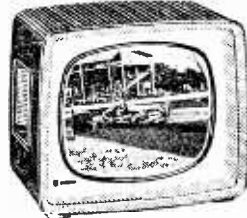G. F. MILWARD

17 PEEL CLOSE, DRAYTON BASSETT
Near TAMWORTH, STAFFORDSHIRE
Tamworth 2321 Post only

EX-RENTAL TELEVISIONS
14 in. £7.10.0
17 in. £11.10.0
12 months 3 star Guarantee
★Tube★Valves★Components
COLOURED FREE LIST
Channels for all areas
Demonstrations daily from Large Selection.



Personal collection or Insured
Carr. 14in. 20/-; 17in. 30/-

AERIALS. BBC/ITA combined Loft and room aerials—from 25/-
BBC/2UHF and colour aerials—from 28/8. SEND FOR FREE LIST

EX-MAINTENANCE TESTED TUBES
17in.—35/- Most makes and types available. 14in.—15/-
Guaranteed good picture Carriage 5/- extra.

ONE YEAR GUARANTEED TUBES

21 in.	99/6
17 in.	79/6
15, 14	59/6
12 in.	



100% REGUNNED
Add 10/- or old tube.
All 110°—99/6 plus
30/- refundable on
old tube. Carr. 10/6.
14in. Slimline 17 &
19 in. — overseas
postage 30/-

VALVES £1 per 100. Assorted TV and Radio. Surplus ex-rental dismantled receivers. Post 4/6. Send for list.

CONDENSERS 10/- per 100. New Assorted Electrolytics and P.P. 2/6.
RESISTORS 6/- per 100. New. Mostly High Stabs. Assorted. P.P. 2/-. Overseas 3/8.
SPEAKERS 7/9 6in., 8in., 7 x 4in., 8 x 3in. Ex-inf. Salvage. P.P. 2/3 Overseas 4/-

AERIAL BARGAINS

Latest 6 array combined all channels:
Loft 39/6; Outdoor 49/8. P.P. 4/6.
BBC/2/UHF 6 element pencil 29/8; 5 element add on extension 11/- P.P. 2/6.

DUKE & CO. (LONDON) LTD.
621/3 Romford Road, Manor Park, E.12
Liverpool St.—Manor Plk.—10 mins.
Phone: ILFord 600/11/2/3. Stamp for Free List

R S G B PUBLICATIONS For the RADIO ENTHUSIAST

AMATEUR RADIO CIRCUITS BOOK
A wide selection of circuits for use in transmitters, receivers and ancillary equipment. 96 pages. Price 7/6 (By post 8/6)

R S G B AMATEUR RADIO CALL BOOK, 1966 Edn.
The latest edition of this best-selling annual directory of Amateur Radio stations in the United Kingdom and the Republic of Ireland records more than 3,000 changes since the 1965 edition. 98 pages. Price 6/- (By post 6/6)

S.S.B. EQUIPMENT
A companion booklet to "Communications Receivers" describing the G2DAF Single Sideband Transmitter Mk. 2. 24 pages. Price 3/- (Post free)

COMMUNICATIONS RECEIVERS, SECOND EDITION
The G2DAF high performance receiver is described in detail. Contains information on the G2DAF H.F. Bands Converter and use of mechanical filters. 36 pages. Price 3/- (Post free)

TECHNICAL TOPICS FOR THE RADIO AMATEUR
Based on the long-running feature in the R S G B Bulletin. More than 230 line diagrams, 100 pages. Price 10/- (By post 10/8)

Further details of other R S G B publications, information about membership of the society, including a free copy of the monthly R S G B BULLETIN, and the book, itself may be obtained from the publishers:


RADIO SOCIETY OF GREAT BRITAIN
Dept. PW, 28 Little Russell Street, London, W.C.1.
HOLborn 7373, 2444.



Miniature Modulator

A SELF-CONTAINED
8.5 WATT UNIT

by A. Sydenham

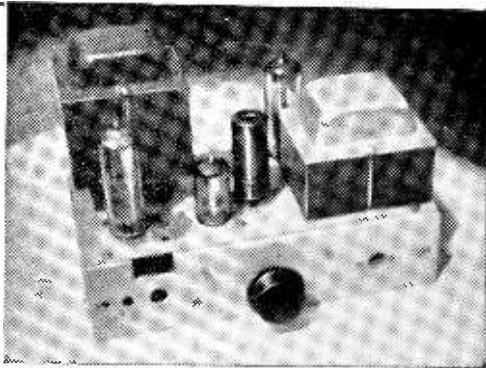

THE ELL80 is a quite remarkable device, and it is surprising that greater use has not been made of it, certainly amongst the ranks of home constructors. The valve is no larger physically than the well-known EL84 yet it does contain within one "bottle" two complete audio pentodes, each of which can deliver some 3W of audio power. The sections each have a mutual conductance of 6mA/volt and screen and anode current demands are typically 4.5 and 24mA when the source voltage is 250V d.c. The cathode is common to both sections and 6.3V a.c. at 0.55A is required for the heater.

The valve may be used in single-ended mode for stereophonic reproduction (3W per channel) or the sections may be operated monaurally in either the parallel or push/pull connection. In Amateur circles the push/pull configuration is likely to prove most useful for the 8.5W obtainable can be utilised to modulate a "Phone" transmitter. A transmitter in use a short time ago employed "controlled carrier" modulation on 'Phone. This was not entirely satisfactory and the circuitry was modified slightly so that external modulation could be applied; this proved completely satisfactory.

Circuitry

The circuit of the modulator constructed is shown in Fig. 2, injection being made at the cathode of the 6146 in the Tx. Running 50W good results have been achieved with excellent modula-

tion and plenty of gain in hand, the potentials applied to the 6146 screen and anode being 140 and 630V respectively. For cathode modulation it seems that some 5W is adequate compared to the 25-30W that would be needed for similar plate/screen modulation. The modulator could be used in plate/screen circuits of course but a lower r.f. capability would then be necessitated.

Conventional speech amplifier stages (V1/V2A) furnish the voltage necessary to enable V2A to do phase-splitter duty. Anti-phase voltages are developed across load resistors R8/9 to feed the output pair (ELL80). Thereafter transformer T1 combines the signals and output is available at the secondary winding.

For cathode modulation a step-down ratio of about 5:1 seems right when Ra-a is 11,000Ω. For best results T1 would be made a multi-ratio modulation transformer but in the test model an American type mains transformer was utilised in reverse. Voltage-wise the centre tap of T1 is fed with relatively unsmoothed h.t. this allowing the ELL80 anodes to receive the maximum available positive potential and at the same time permitting resistor R17 to be of low wattage rating. No hum exists and decoupling is adequate.


Note should be taken of the two "stopper" resistors R15/16 and these should not be omitted or troubles due to parasitic oscillations will result. These resistors should be soldered at one end direct to their respective grid pins. Other critical items

are resistors R8/9 and these should be bridge-matched to within 5% or better, their precise values being considered of secondary importance. Resistor R12 is merely a bias-fixing item.

Full wave rectification due to the EZ81 valve and its associated items is preferred since a short warming up period elapses at switch-on before the full h.t. is applied. Zero signal current drain is 65mA and although this rises on the application of signals no strain is likely to be felt, for the rectifier is capable of supplying up to 150mA at 350V from a r.m.s. supply of 350V per anode.

Constructional Notes

Plans showing the layout

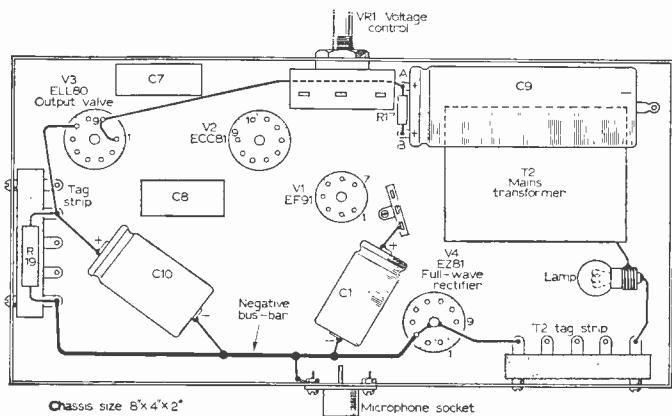

Chassis size 8"x4"x2"

Fig. 1: Location of major components—underchassis view.

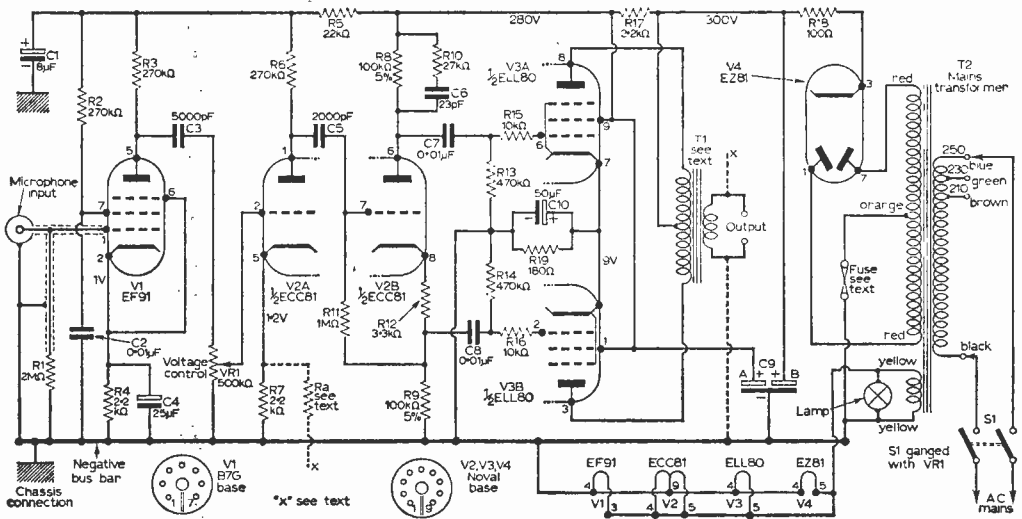


Fig. 2: Circuit diagram of the modulator.

adopted is shown in Fig. 1, this being the below-chassis diagram. The valveholders are preferably orientated as shown while, in the interest of hum elimination, the use of a negative bus-bar (to which all chassis returns are made) is recommended. The input lead to V1 must also be screened.

The chassis needs to be no larger than 8 x 4 x 2in., and three tag strips positioned as shown are adequate for lead and component anchorages. The fuse fitted to the centre tap of the mains transformer may consist of a small flashbulb and will rapidly burn out should a fault develop on the h.t. line in the form of a short-circuit. Mains fuses are hardly worth while when a fused plug is fitted.

Alternative Use

With a few small circuit changes the unit could be used to provide very pleasing results as an audio amplifier when used with a crystal pick-up, tape recorder, radio tuner, etc. Normally, V1 will not then be required, signals being fed to the top of VR1 via C3. Capacitors C3 and C5 should then however be increased in value to 0.1µF and 0.01µF respectively whilst a normal multi-ratio output transformer such as the Osmabet MRT/10 should be used for T1. The taps on the transformer should then be selected as recommended in the maker's leaflet to suit the particular speaker impedance in use, i.e. 3, 7.5 or 15Ω. Tone control stages may also be fitted and degeneration applied to the cathode of V2A to improve the response. If degenerative feedback is so incorporated from the secondary of the output transformer one side of this will have to be connected to the negative bus bar as is indicated by the broken lines in Fig. 1. The value required for Ra will have to be determined experimentally but may lie between 5 and 22kΩ. If the phasing is incorrect positive feedback will result and cause howling; this can be remedied by reversing the connections to the output transformer secondary.

COMPONENTS LIST

Resistors:

- | | | | |
|-----|-------------------------------|-----|----------|
| R1 | 2MΩ | R10 | 27kΩ |
| R2 | 270kΩ | R11 | 1MΩ |
| R3 | 270kΩ | R12 | 3.3kΩ |
| R4 | 2.2kΩ | R13 | 470kΩ |
| R5 | 22kΩ | R14 | 470kΩ |
| R6 | 270kΩ | R15 | 10kΩ |
| R7 | 2.2kΩ | R16 | 10kΩ |
| R8 | 100kΩ 5% | R17 | 2.2kΩ 1W |
| R9 | 100kΩ 5% | R18 | 100Ω 1W |
| VR1 | 500kΩ log pot with DP switch. | | |

Capacitors:

- C1 8µF 350V electrolytic
- C2 0.01µF
- C3 5000pF
- C4 25µF 6V electrolytic
- C5 2000pF
- C6 23pF
- C7 0.01µF
- C8 0.01µF
- C9 32+32µF 350V electrolytic
- C10 50µF 25V electrolytic

Valves:

- V1 EF91 (6AM6)
- V2 ECC81 (12AX7)
- V3 ELL80 (Mullard Ltd.)
- V4 EZ81

Transformers:

- T1 Modulation transformer
- T2 Mains transformer. Secondaries: 250-0-250V @ 100mA, 6.3V @ 3.5A. Drop through (R.S.C. Ltd.)

Miscellaneous:

- Chassis 8 x 4 x 2in. Valveholders—Noval (3), B7G (1), Coaxial socket, panel lamp, etc.

26¹/₂gn TAPE RECORDER for ONLY £19.10.

carr. 12/6
Bargain of the Year Offer
—cancelled Export Contract

Famous manufacturers brand new unused and factory tested 2 speed, 3 $\frac{1}{2}$ and 7 $\frac{1}{2}$ i.p.s. twin track tape recorder 3 Watt output. Tape position Rev.-counter, fast forward and rewind, take 7" reels, mike and gram input. Straight through amplifier facilities. Output sockets for ext. speaker, monitor or external amplifier. Super-imposed switching magic eye recording level and manual modulator. Volume and tone controls 7 $\frac{1}{2}$ 4 speaker. Attractively styled cabinet with detachable lid mike and reel storage facilities. A.C. 200/250 volts operation. Complete with crystal mike, tape spare reel and screen lead etc.



L.P. RECORDING TAPE BARGAIN

By leading British manufacturers—

PROFESSIONAL GRADE OFFER!

DOUBLE-SIDED

(each side coated) 5 $\frac{1}{2}$ " reels only
Special price offer 1,450 feet 20/-
(2 reels) post free

Ideal for the experimenter who wants to record both sides, and a good L.P. Tape for the enthusiast who wishes to record single side only.

Alumin. Chassis. 1 1/2" Plain/indrilled, double 4 side 22" deep, 8 $\frac{1}{2}$ " x 4 1/8"; 8" x 6", 5/9"; 10" x 7", 6/9"; 12" x 6", 7/6"; 12" x 8" 8/-, etc.
Alumin. Sheet. 1 1/2" 6" x 6", 1/-; 4" x 6", 1/6"; 6" x 12", 12/-; 12" x 12" 4/6, etc.

Jack Plugs. Standard 21" 1/2", Type 2/6. Serecord Ditto, 3/3. Miniature scr. 11", 2/3. Sub-min. 1/3. Soldering Irons. Mains 200/220V or 230/250V. Solon 25W Inst., 24/8. Spare Elements 5/6. Bits, 1/3. 65W, 29/6, etc.

SPECIAL OFFER 3" Message tape 150', 3/8; 3" L.P. 225', 4/9; 3" I.P., 300', 6/6. P. & P. per reel 6d.

TAPE REELS. Mofers, surplus 7", 2/3; 5", 2/-; 3", 1/3; spool containers, 3", 1/8; 5", 1/9; 5 $\frac{1}{2}$ ", 2/-; 7", 2/6.



MULLARD "3-3" & "5-10" HI-FI AMPLIFIERS

3 ohm & 15 ohm output
"3-3" Amp. 3 valve, 3 watt hi-fi quality at reasonable cost. Base Boost and treble controls quality sectional output transformer, 40 c/s-25 kc/s + 1 dB, 100mV for 3W, less than 1% distortion. Bronze escutcheon panel. Complete Kit only 7/- carr. 7/6. Wired and tested £8.10.0.

MULLARD "5-10" AMPLIFIER. 5 valves 10W 3 and 15 ohms output. Mullard's famous circuit with heavy duty ultra-linear quality output transformer £9.19.6 Carr. and Ins. 7/6.

Basic amplifier kit price **£9.19.6** Ready built 11/- gns.

CONTROL PANEL KIT. Bass, Treble and Volume controls with 4-position selector switch for radio tape and 11in. x 4in. escutcheon panel.

AMPLIFIER KIT AND CONTROL PANEL KIT, £11.19.6. Ditto, ready wired, £14.19.6.

2-VALVE PRE-AMP. UNIT. Based on Mullard's famous 2-valve (2xEF86) circuit with full equalisation, with volume, bass, treble and 6-position selector switch. Size 9 x 6 x 2 1/2in. Ready Built £7.19.6, Carriage 3/6.

6 VALVE AM-FM TUNER UNIT



A recommended Fidelity Unit for use with Mullard "3-3" or "5-10" Amplifiers. Now available as complete kit as illustrated, inc. power unit.

Ditto, but less power unit, £9.19.6 carriage 7/6. Circuit and construction details, 4/6, free with kit. **£10.19.6** Carriage 7/6.

Condensers—Silver Mica. All values 2pF to 1,000pF, 6d. each. Ditto Ceramic 9d. Tint. 45W T.A.C. etc. 6,000 mFD to 600 and 0.1/350V. 9d. 0.02-0.1, 500V., 1/-, 0.25 Hunt 1/6, 0.5 T.C.C. 1/9, etc. etc. Close Tol. S/Micas—10% 5pF-500 pF 8d. 600-5,000pF, 1/-, 1% 2pF-1,000pF, 9d. 100pF-500pF, 11d. 375pF, 5,000pF, 1/6. **Resistors**—Full Range 1 ohm-10 meg ohms 20% 1 and 1/2 W. 3d. 4W, 5d. (Midgest type modern rating) 1W, 5d., 2W, 6d. Hi-Stab. 3% 1W, 6d. (100 ohms-1 meg. Other values 9d. 1% 1W, 1/6, etc., etc.

JASON FM TUNER 6 UNITS. Designer-approved kit of parts. FMT1, 5 gns. 4 valves, 20/-; FMT2, £7.10.0. 5 valves 35/-; JTV MERCURY 10 gns. 3 valves, 22/6. JTV £13.19.6. 4 valves, 28/6. **NEW JASON FM HANDBOOK,** 2/6. 4s. hr. Alignment Service. 7/6. P. & P. 2/6.

TRIMMERS. Ceramic (Compression Type)—30pF, 50pF, 70pF, 9d.; 100pF/150pF, 1/3; 250pF, 1/6; 600pF, 1/9. **PHILLIPS.** Bee Hive Type (conc. air-spaced)—2.5pF, 1/-; 3-30pF, 1/-. **KNOBS**—Modern Continental types Brown or Ivory with Gold Centre; 1" dia., 9d. each; 1 1/2" 1/- each; Conc. knobs ivory with Gold Centre 1 1/2" dia. 2/9 per pair. Matching ditto 2/8 ea.

LARGE SELECTION AVAILABLE. METAL RECTIFIERS. STC Types—RMI, 4/9; RME, 5/8; RM2, 7/6; RMI, 16/-; RME, 21/-; RM4B, 17/6. **TUB-ELECTROLYTICS CAN** 25/25V 50/12V, 1/9; 8-8.450V, 4/6; 50/50V, 100/125V, 2/-; 32-32/275V, 4/6; 8/450V, 4/350V, 2/5; 50/250/250V, 8/6; 18-18/450V, 5/8; 60/250/275V, 12/6; 32-32/450V, 6/6; 100+200/275V, 12/6.

Volume Controls—5K-2 Meg. ohms. 3W. Spindles, Mergatite, Midgest Type 1 1/2in. diam. Guar. 1 year. LOG or LIN. ratio less Sw. 3/-; DP. Sw. 4/6. Twin Stereo less Sw 7/6. 100k to 2M ohms with DP sw. 9/6. **WAVECHARGE SWITCHES.** 1 p. 12-way 2p. 2-way, 2 p. 6-way. 3 p. 4-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6 ea.

EXPANDED ANODISED METAL. Attractive gilt finish 1in. x 2in. diamond mesh 4/6 sq. ft. Multiples of 6in. cut. Max. size 4ft. x 3ft. 47/6 plus carr. Do. finer pattern mesh 4/6 sq. ft. multiples of 12in., max. size 3 ft. x 2 ft., 27/6 sheet.

ENAMELLED COPPER WIRE—1lb. reels 14S-20S, 3/-; 22S-26S, 3/6; 36S-38S, 4/9; 39S-40S, 5/-, etc.

DE-LUXE RECORD PLAYER KIT



Incorporating 4 Sp. Garrard Auto-tune unit and Mullard latest 3 watt printed circuit amplifier (ECL 86 and EZ 80), vol., bass and treble controls, with 8" x 5" 10,000 line speaker. Contemporary styled 2-tone cabinet, charcoal-grey and off-white with matching blue-relief. Size 17 1/2" x 18" x 8". A stylish unit capable of quality reproduction. Circuit and const. details 2/6 (free with kit). **£13.19.6**

COMPLETE KIT £13.19.6
Carr. and Ins. 12/6 Ready wired 30/- extra Illuminated perspex control panel escutcheon, 7/6 extra. Four contemporary mounting legs 6in. 10/8; 9in. 11/8; 12in. 12/6 extra.

TRANSISTOR COMPONENTS

Midget I.F.'s—465 Kc/s 9/16in. diam. 1st, second or third, 5/6 Osc. Coil M. & L.W. 9/16 in. dia. 1/6. Midget Driver Trans. 9/1. M.F. 6/- Midget Output Trans. Push-Pull—3 ohms.....6/-

Elect. Condensers—Midget type 1 mFd.-50 mFd. ea. 1/9, 100 mFd. 2/-, 12V. Wkg.

Condensers 150 v. working: .01 mFd., .02 mFd., .03 mFd., .04mFd., 9d.; .05 mFd., 1 mFd., 1/-; .25 mFd., 1/3; .5 mFd., 1/6, etc. **Midget Tuning Condensers.** J.R. "OO" 208 pF and 176 pF, 8/6. ditto with trimmers, 9/6. J.B. 220 pF and 105 pF conc. slow motion 10/6. 265pF single 7/6. Sub. min. 1in. Dilemma 100 pF, 300pF, 500pF, 7/- each.

FERRITE AERIALS, M. & L.W. car aerial coil 9/3.

Midget Vol. Control with edge control knob—5 K/ohms, with switch 4/6; Ditto less switch 3/9

Speakers: P.M. 2in. Plessey 5 ohms 15/6; 2in. Continental 8 ohms, 13/6; 7 x 4in. Plessey 35 ohms, 23/6.

Ear Plug Phones—Min. Continental type 3ft. lead, jack plug and socket. High Imp., 8/-; Low Imp., 7/6.

Phone Plugs, 9d. Phone Sockets (open), 9d. Ditto (closed), 1/-; Twin Phone Sockets (open), 1/3.

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve line-up ECC85, ECH81, EF89 New 1965 Model now available

Three Waveband and Switched Gram. positions. Med. 200-550 m. Long 1,000-2,000 m. VHF/FM 88-95 Mc/s Phillips Continental Tuning Insert with permeability tuning on FM and combined AM/FM IF transformers. 400 Kc/s, and 107 Mc/s. Dust cover including all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2 x 6 1/2in. Height 7 1/2in. Edge illuminated glass dial 11 1/2in.

Vertical pointer. Horizontal station names. Gold on black background. A.C. 200/250v. operation. Magic-eye tuning. Circuit diagram now available. Aligned and tested ready for use £13.19.6. Carr. & Ins. 7/6. Comp. with Tape, O/P socket, ext. sp'kr and P/U sockets and indoor F.M. aerial and 4 knobs—w/valvt or ivory to choice. 3 Q P.M. Speaker only required. Recommended Quality Speakers 10" R.A. 27/6. 13 1/2" x 8" E.M.I. Fidelity, 37/6. 12" R.A. with conc. Tweeter, 42/6. Carr. 3/6.

BONDACOUST Speaker Cabinet Acoustic Wadding (1 in. thick approx.) 18 in. wide, any length cut. 2/3 per ft., 6/- per yard. **TINNED COPPER WIRE,** 16-22G. 4Y-1lb. **ERSIN MULTICORE SOLDER,** 60/40 4d. per yard. Cartons 6d., 1/-, 2/6 etc.

We manufacture all types Radio Mains Transf., Chokes, Quality O/P Trans., etc. Enquiries invited for Specials. Prototypes for small production runs. Quotations by return. Send for detailed bargain list, 3d. stamp.

RADIO COMPONENT SPECIALISTS

70 Brigstock Rd., Thornton Heath, Surrey. Hours: 9 a.m.-6 p.m., 1 p.m., Wed THO 2188. Terms C.W.O. or C.O.D. Post and Packing up to 4 lb. 1/-; 1 lb. 1/9; 3 lb. 3/-; 5 lb. 3/9; 8 lb. 4/6.



HERE'S VERSATILITY FOR YOU...

The **Brenell**


MONO/STEREO HI-FI TAPE LINK

Twin playback pre-amplifiers
Twin recording amplifiers
Variable bias
Push-pull bias/erase oscillator
D.C. heated valves
Rear sockets duplicated on front panel
Instant comparison of original and recorded signals
Frequency correction for 4 tape speeds
Dual concentric gain controls for recording amplifiers and playback pre-amplifiers
Twin recording level meters

PRICE including power unit £46. 0. 0.

Designed for use with 2/2 or 2/4 track heads

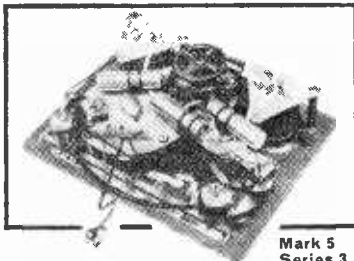Built to the same high standards as our tape recorders and decks this HI-FI TAPE LINK has been developed for use with your high fidelity equipment. It is capable of giving superb results when matched to one of our Mark 5 Series 3 decks fitted with the appropriate heads. Write for full details of this amplifier and deck and complete range of tape recorders.



Mark 5 Series 3 Deck

Brenell

BRENELL ENGINEERING CO. LTD.,
231/5 Liverpool Road, London, N.1.
Telephone: NORTH 8271 (5 lines)

GD378

EXPRESS ELECTRONICS

32 SOUTH END, CROYDON; SURREY

Telephone: Croydon 9186

FOR THE FOLLOWING BRAND NEW UNITS

AMPLIFIERS AND TUNERS

TRIPLETONE HI-FI MAJOR	12 watt	£15.18.6
TRIPLETONE CONVERTIBLE	5 watt	£6.19.6
TRIPLETONE GEMINI STEREO	5 watt	£15.15.0
TRIPLETONE FM TUNER	...	£15.14.6
LINEAR	3 watt	£6. 6.0
LINEAR DIATONIC	12 watt	£12.12.0
LINEAR CONCHORD	30 watt	£16.16.0
LEAK TL12	14 watt	£18.18.0
LEAK VARISLOPE PRE-AMP	...	£15.15.0
LEAK TL50	50 watt	£33.12.0
LEAK TROUGH LINE 3 FM TUNER	...	£31.14.6
QUAD	15 watt	£22. 1.0
QUAD STEREO/MONO PRE-AMP	...	£25. 0.0

LOUDSPEAKERS

GOODMANS AXIETTE 8in.	6 watt	£5. 5.0
GOODMANS AXIOM 10in.	10 watt	£6. 6.0
GOODMANS AXIOM 201	15 watt	£10.15.0

BAKERS 'SELHURST' 3 or 15 ohm

STALWART 12in.	15 watt	£5. 5.0
BASS GUITAR 12in. 'Group 25'	25 watt	£5. 5.0
BASS GUITAR 'Group 35'	35 watt	£8.18.0
BASS GUITAR 'Group 50'	50 watt	£18.18.0
STANDARD Heavy Duty 12in.	20 watt	£7. 7.0
BASS Heavy Duty 12in.	25 watt	£12.12.0
AUDITORIUM 15	35 watt	£18.18.0

RECORD PLAYERS

GARRARD MODEL 1000 4-speed MONO	...	£6.19.6
GARRARD MODEL 2000 MONO	...	£7.15.0
GARRARD MODEL 3000 STEREO	...	£10.10.0
GARRARD MODEL 401	...	£29.10.0
GARRARD MODEL LAB80	...	£24.10.0
GARRARD AT6 TRANSCRIPTION MONO	...	£9.17.6
GARRARD MODEL AT60	...	£11.15.0
GARRARD MODEL A70	...	£19.10.0
GARRARD SRP 10	...	£4.19.6

Delivered free U.K. S.A.E. enquiries.

Any holes in your knowledge of TRANSISTORS?

Whatever your interest in transistor circuitry, you will find the Mullard "Reference Manual of Transistor Circuits" and "Transistor Radios, Circuitry and Servicing Book", valuable sources of reference.

The former describes more than sixty circuits for both domestic and industrial applications.

The latter is an introduction to the subject and describes the basic properties of semiconductor, their function, elementary circuitry and servicing.

REFERENCE
MANUAL OF
TRANSISTOR
CIRCUITS
U.K. PRICE
12/6
Post extra 1/-

TRANSISTOR
RADIOS
Circuitry and
Servicing
U.K. PRICE
5/-
Post extra, 6d.



Get your copies from your radio dealer, or send remittance with order to:

MULLARD LTD - MULLARD HOUSE - TORRINGTON PLACE - LONDON WC1

SINGLE CIRCUIT PANELS

★ by W. Groome

designing
and making
economical
circuit panels
without acid

COMPARED with the slight cost of wire, single panels of printed circuit character seem to provide our conductors rather dearly and, with the acid-etch process, inconveniently. Recent bargain offers of copper-clad plastic suggest that the first objection may not always apply, in which case the very cheap alternative included in this article will cease to be of interest. On the other hand, the methods of forming circuits "dry" could be of lasting benefit. Our main concern, however, is design, for by whatever method a panel is made it presents very little scope for the correction of errors. It discourages the "lash-up" approach and imposes the discipline of thoughtful layout planning.

Basic Idea

As practical people we would rather begin with a basic idea than work entirely at random. I suggest, seriously, that the basis of a panel layout

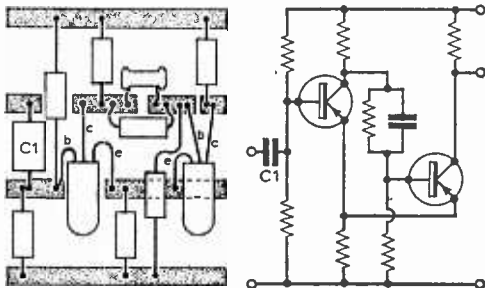


Fig. 1: Schmitt trigger circuit diagram and layout plan of circuit panel. Note similarities.

often exists ready made in the theoretical circuit diagram. The idea would have been ludicrous in the chassis and group board era but we are dealing with thin plastic panels and little wire-ended components that can be anchored almost anywhere we wish. Consider the circuit diagrams in this journal. Symbolically the components have been arranged or grouped according to function. Circuit sequence and signal paths have been clarified, power and earth lines clearly distinguished, all with an economy of line that aids scanning and with the minimum of crossings. The draughtsman's aim has been "readability" but the sorting out process has produced something close to a "map" of a circuit panel as we shall see.

Example

Compare, in Fig. 1, the diagram of a Schmitt trigger with the panel layout alongside and showing physical component shapes in place of symbols. The conductors (shaded) are facing us, while the components are to be taken as being on the other side with only their wire ends brought through holes for solder connection. One component (C1) has been reorientated, otherwise the two drawings are closely comparable. The layout is rather open for clarity and indeed I suggest that the first sketch for any circuit should be made without regard for ultimate compactness so that a good idea of arrangement and connection points can be formed. In the next sketch you can close the ranks while retaining the same general arrangement, shorten the conductors to suit and bring them to within, say, $\frac{1}{8}$ in. apart. Omit connections because they will be effectively the same as in the first sketch and will be difficult to show in the close drawing. Applied to Fig. 1 this compression would reduce the panel size from $1\frac{1}{2}$ in. x 2 in. to $1\frac{1}{4}$ in. x $1\frac{1}{8}$ in. Finally by setting the components perpendicular to the panel the conductors can be brought to $\frac{1}{4}$ in. apart and the panel size will become about $1\frac{1}{4}$ in. x 1 in. Such economy of area may not be essential physically but it helps to reduce the expenditure on copper-clad material.

Parallel Rows

A noticeable feature is the simple arrangement of the conductors in parallel rows achieved by using the circuit for guidance. It is, of course, only a two-transistor circuit but the observation is equally true of four-stage, six-transistor panels shown in the diagrams of Figs. 2 and 3. The simplicity is due largely to the geometrical fact that any point in an area can be reached by moving in two directions at right-angles. Generally but not as an unbreakable rule the components span the panel vertically (as viewed in the drawings), while the conductors advance the circuit horizontally. They are on opposite sides of the panel and can cross without touching. The amplifier panels described here comprise six rows, of which some have yet to be divided into separate conductors for the sake of further points to be mentioned later. The rows are: (1) Negative line, (2) collector networks and one push-pull phase,

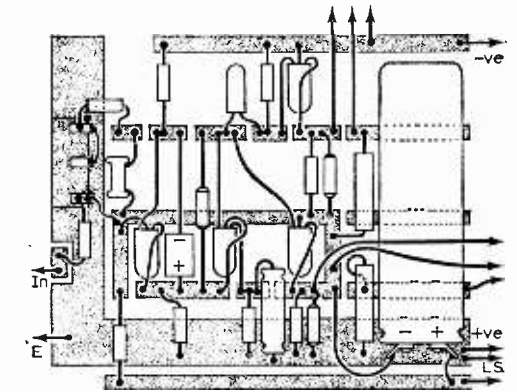
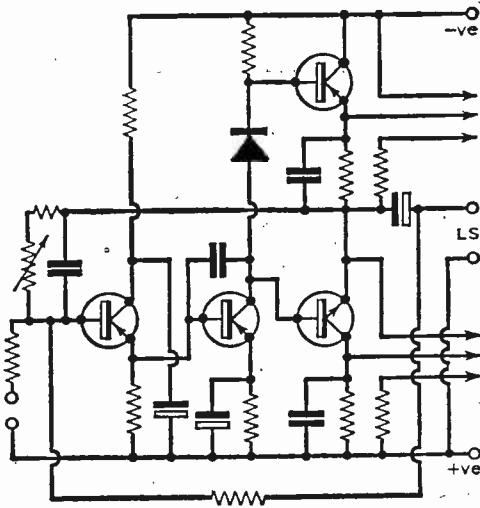


Fig. 2a (above): Circuit panel layout for the push pull amplifier of Fig. 2b (left) using the circuit diagram as a basis for the physical arrangement.

(3) mid-phase busbar, (4) emitter networks, (5) earth busbar and (6) feedback line. The practicality of the two-directional principle is demonstrated by the popularity in industry and elsewhere of ready-made striped panels in place of printed circuits.

Amplifier Circuit

The amplifier circuit of Fig. 2 includes all components except the output transistors, which are mounted separately on heat sinks and connected by wire as indicated. A larger panel is used, which has bare areas to accommodate the heat sinks—to be fitted on spacers, of course, to permit air circulation. Circuit and panel plan have

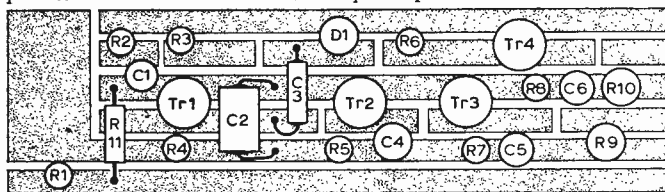


Fig. 3: Reduction of the panel area of the circuit panel of Fig. 2 effected by mounting the components vertically.

been brought together in Fig. 2 for ready comparison. The potentiometer should be fitted on a small bracket screwed above the broad earth area on the left, the feedback resistor has been moved to the left (without electrical change) to enable it to hop over the earth line, while the position of the output capacitor is dictated by its large size.

These variations are practical. In other respects the diagram and layout correspond. Here again we see the simple straight line conductor arrangement. The size of the circuit area, 4in. x 3½in., is reasonable compared with the heat sinks and the volume of most domestic cabinets, but many constructors will look askance at the large bare areas representing dearly bought copper that must

be thrown away with the acid. Economy, more than space considerations, can drive us to a more compact layout with a smaller proportion of waste foil. By upending the components and fitting the output capacitor elsewhere the circuit area can be reduced to 4in. (the length of the heat sinks) x 1½in. The component arrangement of this small panel is indicated in Fig. 3. Note the improved layout.

Width of Conductors

One more design aspect to be considered before turning to methods of making the circuit panels is the width of conductors. With the thinnest copper foil (0.0014in.) a line 0.015in. wide can carry 1A with only a few degrees' rise above ambient temperature and a ¼in. line 4A for 8° rise. On this basis we are not likely to produce by hand lines too narrow for the millimetre range. Narrow lines, more prone to failure than broad ones, are justified only in crowded areas. In any case they have to be broadened at connection points and, while the necessary rings, "cushions" or "blobs," have a nice space-age look, they are tedious to produce by any hand method. Most often the area demanded by the components is large enough to accommodate ¼in. lines to which connections can be soldered at any point. Use wider lines, of course, for really heavy currents and always make the earth lines as broad as space will permit.

Why use acid?

We turn to practical matters with a question. Why dabble with acid? Commercial panel material has a copper-to-plastic union capable of

LEARN ELECTRONICS —AS YOU BUILD

over 40 CIRCUITS EXPERIMENTS TEST GEAR



including . . .

● CATHODE RAY OSCILLOSCOPE

- Valve Experiments
- Transistor Experiments
- Electro-magnetic Experiments
- Basic Amplifier
- Basic Oscillator
- Basic Rectifier
- Signal Tracer
- Simple Counter
- Time Delay Circuits
- Square Wave Generator
- Morse Code Oscillator
- Simple Transmitter
- Electronic Switch
- Photo-electric Circuit
- Basic Computer Circuit
- Basic Radio Receiver
- A.C. Experiments
- D.C. Experiments

The full equipment supplied comprises; valves, transistors, photo-tube, modern type chassis board; printed circuit board; full range resistors, capacitors and inductors; transformers; potentiometers; switches; transistors; valves; all hardware, wiring and every detail required for all practical work plus CATHODE RAY OSCILLOSCOPE for demonstrating results of all experiments carried out. All practical work fully described in comprehensive PRACTICAL MANUALS. Tutor service and advice if needed.

This complete practical course will teach you all the basic principles of electronics by carrying out experiments and building operational apparatus. You will learn how to recognise and handle all types of modern components; their symbols and how to read a completed circuit or schematic diagram. The course then shows how all the basic electronic circuits are constructed and used, and HOW THEY ACTUALLY WORK BY USING THE OSCILLOSCOPE PROVIDED. An application is given in all the main fields of electronics, i.e. Radio; control circuits; computers and automation; photoelectrics; counters, etc., and rules and procedure for fault finding and servicing of all types of electronic equipment.

- NO PREVIOUS KNOWLEDGE NEEDED
- NO MATHS USED OR NEEDED
- REASONABLE FEE—NO EXTRAS REQUIRED
- SENT IN ATTRACTIVE BOX
- COMPLETE ADVICE SERVICE
- EVERYTHING REMAINS YOUR OWN PROPERTY

A completely NEW up-to-date home study experimental course by
BRITISH NATIONAL RADIO SCHOOL —
Britain's Leading Electronic Training Organisation.

POST NOW FOR FREE BROCHURE

To BRITISH NATIONAL RADIO SCHOOL, READING, BERKSHIRE. Please send free Brochure, without obligation, to

NAME


ADDRESS

Block Capitals Please

OR WRITE IF YOU PREFER NOT TO CUT COUPON PW 2.66



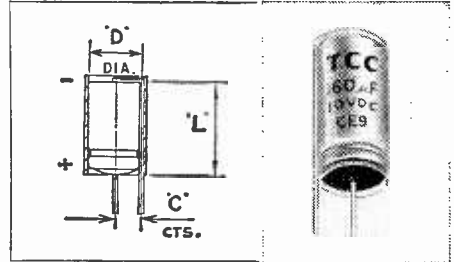Sub-miniature Electrolytics for Transistor Circuits



T.C.C. TYPE No.	Case Size in inches			Maximum D.C. Wkg. Voltages and Cap. (µF)					
	D	L	C	3V.	6V.	9V.	12V.	15V.	25V.
CE.2 'V' or 'H'	1/8	1/8	0.07	8	6	4	3	2	—
CE.3 "	7/16	7/16	0.1	25	20	15	10	6	4
CE.4 "	7/16	1/2	0.1	40	30	20	15	8	6
CE.5 "	1/2	7/16	0.14	50	40	25	20	10	8
CE.6 "	1/2	1/2	0.14	80	60	40	30	15	12
CE.7 "	7/16	1/2	0.18	100	75	50	40	20	15
	D	L	C	3V.	6V.	10V.	15V.	25V.	50V.
CE.8 "	1/2	3/4	0.14	100	80	60	40	25	8
CE.9 "	3/8	3/4	0.2	250	200	160	100	60	20

V=Vertical Mounting H=Horizontal Mounting

Operating Temperature Range. —20°C. to +60°C.

Connection wires are welded for low resistance contact, and solder-coated for ease of assembly, the standard length being 1 1/2" for the horizontal range, cropped to 3/8" long for the vertical range. The capacitors are in insulated seamless aluminium cases, and sealed with a synthetic rubber bung.

Cap. Tolerance. The standard tolerance of all capacitors is —20% + 100% of the rated capacitance.


Leakage Current. CE.2-7 may be determined from the following: 1 (µA) = 0.1 C.V. + 10 at applied working voltage and at 20°C. CE.8-9 may be determined from : .02 C.V. + 20 at applied working voltage and at 20°C.

THE TELEGRAPH CONDENSER CO. LTD.

Electronics Division • NORTH ACTON • LONDON • W.3 • Tel. ACOrn 0061 • Telex: 261383
also at CHESSINGT ON, SURREY and BATHGATE, SCOTLAND

GUITAR AMPLIFIERS with TREMOLO

12 months' guarantee (valves 3 months)

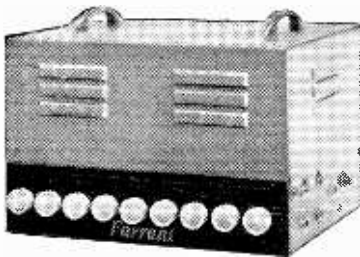

Five jack socket inputs with four separate mixing volume controls. High gain of 10 millivolts makes it suitable for all types of guitars and microphones. Separate Bass and Treble controls. Master gain control. Tremolo speed and depth controls. Remote tremolo switch socket. 7.5 and 15 ohms outputs. 30 and 50 watt valves

ECC83, ECC83, EL34, EL34, GZ34. 15 watt valves ECC83, ECC83, EL84, EL84, EZ81. Two extra valves ECC83 used in the tremolocircuit. Tremolo operates on one input only. Black and gold front panel (fitted tremolo type only at present) Chassis finished silver grey hammer. Cover with chrome handles 85/- extra.

PRICES

50 watt with tremolo	£21.78
50 watt less tremolo	£19.10.0
30 watt with tremolo	£18.17.8
30 watt less tremolo	£14.10.0
15 watt with tremolo	£13.17.8
15 watt less tremolo	£11.10.0

Add carriage 10/- any amplifier. Credit terms arranged. Descriptive leaflet free, stamp appreciated. Suitable speakers Bakers 12" Guitar L.S. 5 gns. Bakers 15" Group 50 L.S. 18 gns. Carriage free.

Cash with order only, regret no C.O.D. "No trade or Export"

STROUD AUDIO

CASHES GREEN ROAD, STROUD, GLOS. STROUD 783.

RETURN-OF-POST

ON CASH OR C.O.D. ORDERS

● GARRARD GRAMOPHONE EQUIPMENT

RECORD CHANGERS	Cash Price	Deposit	Credit Terms	
			Monthly Payments	Total Credit
Model 50 (GCS Mono PU)	£9.19.6	£1.19.6	12 of 15/5	£11.4.6
Model 1000 (GCS Mono PU)	£8. 9.6	£1.13.6	12 of 13/5	£9.14.6
Model 3000 (9TAHC Stereo/Mono PU)	£12.15.0	£2.12.0	12 of 19/-	£14. 0.0
AT90 (GCS Mono PU)	£12.19.6	£2.12.6	12 of 19/5	£14. 5.6
A70 (Deram PU)	£25.19.6	£5. 3.6	12 of 39/-	£28.11.6
LAB80 (Deram PU)	£31.19.6	£6.19.6	12 of 47/9	£35. 2.6
SINGLE RECORD PLAYERS				
SP25 (GCS Mono PU)	£12.15.0	£2.12.0	12 of 19/2	£14. 0.0
SP25 (Deram PU)	£16.10.0	£3. 6.0	12 of 24/5	£18. 3.0

IMPORTANT—When ordering units with the Decca Deram Pick-Up, please state whether Stereo or Mono required.

● GOODMAN'S LOUDSPEAKERS

Axion 201 12" 15 watts	Cash Price	Deposit	Credit Terms	
			Monthly Payments	Total Credit
..	£11. 8.9	£2. 5.9	12 of 17/4	£12.13.9
Axion 10, 10" 10 watts	£6.12.4	£1.12.4	6 of 20/-	£7.12.4
Axlette 8, 8" 6 watts	£5.10.11	£1. 7.11	6 of 17/2	£6.10.11

● MULLARD AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, 3-3, Two and Three Valve Pre-Amplifiers, Tape Pre-Amplifier, Stereo, Pre-Amplifier, Seven Watt and Three Valve Stereo Amplifiers all as described in the Mullard Manual for Audio Circuits. We can supply this publication for 9/6, post free.

● LATEST TEST METERS

All the latest models from current production. Illustrated list available.

AVO 8, Mk. 3	Cash Price	Deposit	Credit Terms	
			12 monthly payments	Total Credit
..	£25. 5.0	£5. 5.0	£1.17. 8	£27.15.0
AVO Multimeter Mk. 4	£9.10.0	£1.18.0	14. 9	£10.15.0
Taylor Model 98B	£24.10.0	£4.18.0	£1.18.10	£27. 0.0
Taylor Model 127A	£10.10.0	£2. 3.0	18. 0	£11.15.0
TMK Model 500	£8.19.6	£1.16.6	14. 0	£10. 4.6

All Cash and COD orders are dealt with on day of receipt. Credit orders are subject to only the minimum of delay.

WATTS RADIO (Mail Order) LTD

54 CHURCH STREET, WEYBRIDGE, SURREY
Telephone: Weybridge 47556

Please note: Postal business only from this address

withstanding considerable stress in tensile or shear but it is by no means proof against a deliberate peeling action that breaks the adhesive layer in an advancing narrow line. This, fortunately, is an abuse rarely met by panels in normal service but it is a weakness that we can turn to advantage.

The straight conductors that seem so suitable for many circuits are easy shapes to outline with a sharp knife and a straightedge, cutting the thin foil (which gives in easily) right through to the plastic base. Having isolated an unwanted area in this way you can ease an edge free with the point of the knife and peel the foil away, leaving the wanted conductor intact and neat on the panel. Keep the knife stoned to a keen edge. Score the outline lightly at first to make guide lines that will control the blade during subsequent heavier cuts. Try this method on a scrap piece and then ask yourself: Why dabble with acid?

Good Economy

The idea of making your own clad panel material is good economy but perhaps of greater interest is the fact that it leads to another simple way of forming shaped conductors. Laminates of the Formica type are suitable for the low voltages and impedances of transistor circuits. The small pieces we need are scrap offcut sizes to the ordinary user; they lie in abundance in many home workshops or can be bought at give-away prices. I have used the plain laminate sold cheaply as a balancer veneer, while at the other end of the quality range there are the paxolin types of sheet. For a few shillings the non-ferrous metal merchant or electrical trades stockist can supply enough 0.0014in. or 0.003in. copper foil to make a dozen or more radio panels.

The Adhesive

The main problem is the adhesive. The industrial hot-setting types are not available by retail and would be inconvenient to use if they were. Evaporation types are obviously unsuitable. Epoxy resin, excellent for steel and aluminium, has low-peel strength with copper unless a special primer is used. This leaves the impact types, of which I prefer "Fastbond 10" because it can be spread thinly and bonds copper to laminate with a tough neoprene rubber layer that withstands heat (the maker's claim) as well as the plastic.

Most laminates are lightly and evenly shotblast on the non-decorative side, to which our foil is to be attached. If you have a rough specimen it can be sanded smooth. Incidentally, a quick way of cutting this material is to score both sides and then break it.

The copper must be quite clean: I use hot water and a "Brillo" pad stolen from the kitchen. Apply glue to the panel and to the copper and avoid prolonging this to the point where it thickens and pulls. It is better to go back to a bare spot after the adhesive has dried. Allow ten minutes' drying for "Fastbond 10" and perhaps longer for other makes as instructed on the tin, then the two dry layers will bond instantly and permanently upon contact. Apply pressure for a minute or so to squeeze the glue layer to a thin and even line and

if you use the vice, as I do, remember to protect the copper from marking by covering it with another piece of plastic. Alternatively use a hard roller.

Bare Panel

This quick and easy method produces panels suitable for many circuits for only a few pence each. Returning to Fig. 2 and the waste when copper has to be removed to create large bare areas, the answer (you've guessed it!) is to begin with a bare panel and add only the wanted conductors, which can be first cut to shape with knife or scissors. This method was to make the larger panel for the output transistors and heat sinks. On the other hand, the close conductors of the smaller panels are easier to make by cutting and peeling and the waste is very small. In either case a row of short conductors is most easily produced by first forming a continuous line, and dividing this subsequently with about $\frac{1}{16}$ in. space between each.

Here I offer some astute manufacturer a suggestion without any hope of an early retirement on the royalties. Self-adhesive metal nameplates and instruction plates are already well established in industry and have a tenacity that withstands the shocks of transport and rough service. It should therefore be possible to produce self-adhesive copper strips or rolls of conductor width with a peel-away protective backing to enable circuit panels to be made quickly as required in experimental establishments, schools and amateur workshops. Is anyone listening?

Drilling, etc.

As with commercial panels the work of drilling, piercing, fitting and soldering should be contrived to aid the adhesive union rather than stress it. Drill from the copper side with a bit just large enough to make clearance for the component wires and to prevent the bit from wandering start the hole by indenting the copper with a fine awl.

Soldering has presented no problems. All the panels in the photograph have been tested by soldering a component in place before sending them for the editor's inspection. Draw the wire end through with just enough tension to hold the component against the panel on the other side while the solder end lies flat on the copper. This ensures that the component is supported by the panel without strain on the foil. Alternatively press the wire flat against both the plain and the conductor sides to form a clench that will support the component. Then solder it. Clean copper solders very readily and the spot joint can be made in a second with a hot small iron and good radio quality cored solder, and the heat is dissipated all over the conductor area before it has time to affect the adhesive or the plastic. This brief heating of spot areas is a technique that must be acquired in any case for soldering semiconductors and their associated components.

The panels were made with the thicker gauge of foil, 0.003in., and it will be appreciated that easier and neater work is possible with the thinner material, 0.0014in. ■

on the Short Waves

MONTHLY NEWS FOR DX LISTENERS

All times are in G.M.T.

All frequencies are in kc/s.

The Broadcast Bands by—John Guttridge

AFRICAN stations in the 41 and 31 m.b. are providing fair reception in the early evening at present for those with the patience to seek under the strong Europeans.

Switzerland: *S.B.C.* (3000 Berne 16) will transmit in English as follows until May: 1145—1315 9,665/11,865; 0115—0245 6,080/9,535/6,120; 0415—0545 6,120; 1330—1500 21,520/17,845/11,865/15,305; 1515—1645 9,665/9,655/11,865; 0830—1015 17,830/15,305/11,865/21,520; 0700—0830 9,670/11,865; 1515—1645 11,715. Unbeamed European service programmes on 6,165 and 9,535 now use 250kw transmitters.

International Committee of the Red Cross (7 Avenue de la Paix, 1211, Geneva 1) will have transmissions over the 7,210 transmitter of *S.B.C.* on the following dates in 1966: January 10, 12, 14, March 21, 23, 25, May 9, 11, 13, July 4, 6, 8, September 19, 21, 23 and November 21, 22, 23. Transmissions, lasting one hour, will be at 0600, 1130, 1500, 2100. Reception report forms are available. Regular listeners will be given a special diploma.

U.S.S.R.: *Radio Moscow* (Moscow) transmits to Europe in English until April 1966 at 0700—0730 on 9,740/9,480/7,280/7,240/5,980; 1200—1230 15,480/15,170/11,930/11,830/11,740; 1900—1930 7,330/7,280/6,150/6,050/5,980/1,320; 2000—2030 7,330/7,280/6,200/6,150/6,050/1,380, 2100—2200 7,330/7,280/7,260/6,060/6,050/1,490; 2200—22307, 7,330/7,280/6,050/5,960/1,490/1,380/1,320.

Congo (Rep.): *Radio Brazzaville* (B.P. 108, Brazzaville) transmits at 1400—1700 over 3,332/7,105/11,710/17,720/21,500 and 1730—2100 on 3,332/5,970/7,105/9,730/9,730/11,930/15,190. News in English at 1915.

Ghana: *Radio Ghana* (P.O. Box 1633, Accra) has new English schedule. 0330—0430 6,110; 2000—2100 11,800/9,700; 0430—0515 9,760/9,545; 0600—0645 9,760; 1500—1545 17,910/21,545/21,720; 0300—0345 6,130/6,070; 1330—1430 17,910; 1815—1900 15,285; 0530—0730 3,240; 1400—2015 6,130; 1945—2215 3,240; 0645—0730 and 2045—2215 to Europe on 9,545. Full QSL verification is given.

Portuguese Guinea: *Emissora Provincial da Guine* (Avenue da Republica, Bissau) can be heard signing on at 1800 on 5,041.

Afghanistan: *Radio Afghanistan* (Ansari Wat, Kabul) has stopped its external broadcasts in German. They will resume over two new 100kw TX in May 1966.

India: *All India Radio*, New Delhi, transmits in English to Europe from 1945—2045 over 11,630/7,235/9,515.

Israel: *Kol Israel* (Broadcasting House, Jerusalem) has a new English transmission from 0900—1000 on

Sundays over 11,910/9,009. The evening transmission is now from 2040—2100 on 9,725/9,009.

Macau: *Emisora Vila Verde* (Macau) has been reported audible at 2100 over 755 (medium wave)—a real DX feat this.

Turkey: *Radio Ankara* uses 15,160 for its 2200—2300 English transmission. This outlet is also used for the 1915—1930 French transmission. The home service appears to be relayed throughout the day on 9,515.

Canada: *C.B.C.* (P.O. Box 6000, Montreal) Caribbean transmissions (English 2300, Portuguese 2330 and Spanish 0000—0045) are now on 15,190/11,725/9,625. From January 2 15,190 will be replaced by 5,990. The 0230—0700 *Northern Canada Service* English service is on 5,970/9,625.

U.S.A.: *Radio New York Worldwide* (New York 19, N.Y.) has a slightly different frequency utilisation to that given last month. Details are 17,845 1200—1945; 17,730 1200—2145; 15,440 1400—2130; 15,385 1200—1445 (weekends only); 11,970 1900—2145; 11,905 2145—2400; 11,880 2000—2145; 9,740 2100—2400.

Netherlands Antilles: *Trans World Radio* (Bonaire) has German transmission until 1950 on 11,840 where there is English identification before close down.

Argentina: *R.A.E.* (Sarmiento 151, Buenos Aires) reported with English from 2300—2400 on 11,700 and in the 31 and 49m.b.

Bolivia: *Radio Aliplano* (Avenida Camacho de 1468, La Paz) has been heard with Latin American pop music until 0600 on the new frequency of 5,045.

Brazil: *Radio Brasil Central* (C.P.330, Goiania) can be heard from 1955—2045 on 11,815. *Radio Mayrink Veiga* (Rua Mayrink Veiga 15, Rio de Janeiro) may be occasionally heard on 9,575/11,775.

Chile: *Radio Nuevo Mundo* (Casilla 9255, Santiago) gives good reception at 0230 on 11,740. *Radio Sociedad Nacional de Minoria* (Casilla 2626, Santiago) can be heard with weak signal after 2130. Identification at 2200.

Peru: *Radio Universidad* (Casilla 23, Avequipa) is using the new frequency of 6,242.

Uruguay: *Radio Libertad Sport* (Difusoras del Uruguay S.A., Soriano 1287, Montevideo) can be heard over the El Espectador transmitter CXA19 on 11,835 at 1700.

Radio Oriental (Olimar 1364, Montevideo) can be heard at 2300 on 11,735. *Radio Sarandi* (Corporacion de Publicidad S.A., Enriqueta Compte y Rique 1282) has German test transmissions from 2030—2130 Tuesdays on 15,385. This channel can be also heard in Spanish from 2300—2400 sign off.

Czechoslovakia: *Radio Prague* (Prague 2) transmits to Europe in English from 1200—1230 in the 31, 25 and 19m.b.



These speakers from the Wharfedale Super Range are fitted with roll surrounds for low resonance and double diaphragm assemblies for extended H.F. response.

RANK WHARFEDALE LIMITED Idle, Bradford, Yorkshire
 Telephone Bradford 612552/3 Telegrams 'Wharfedel' Bradford

Super 8/RS/DD

Frequency range 40 c/s—20,000 c/s
 Impedance 10/15 ohms
 Power handling capacity 6 watts
 (12 watts peak) £7 0 0 (tax paid)

Super 10/RS/DD

Frequency range 30 c/s—20,000 c/s
 Impedance 10/15 ohms
 Power handling capacity 10 watts
 (20 watts peak) £11 13 4 (tax paid)

Super 12/RS/DD

Frequency range 25 c/s—20,000 c/s
 Impedance 12/15 ohms
 Power handling capacity 20 watts
 (40 watts peak) £17 10 0 (no tax)

POST THIS COUPON TODAY


For fully illustrated 8 page booklet on Wharfedale Speaker Units (Dept. PW.2)



NAME.....

ADDRESS.....

TOWN.....COUNTY.....

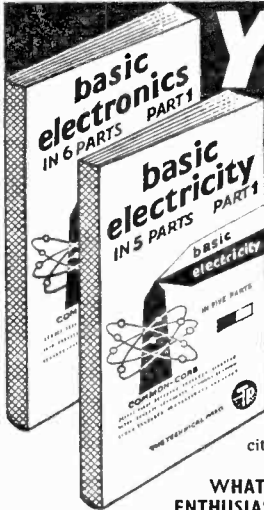

YOURS FREE FOR 7 DAYS

The New 'Picture-Book' way of learning
BASIC ELECTRICITY (5 vols.)
BASIC ELECTRONICS (6 vols.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

EVERY DAY WE RECEIVE LETTERS PRAISING THESE BOOKS, HERE ARE A FEW FROM THIS MONTH'S POSTBAG.

"... Sometime ago I was fortunate in ordering a set of **BASIC ELECTRONICS** and now that I have had time to read and digest their contents I should like to record the pleasure and gratification I derived from their simple and unique presentation of what has hitherto been regarded as a difficult subject to grasp..."
 J. P. Chester.

POST NOW FOR THIS OFFER!!

To Selray Book Co.
 60 Hayes Hill, Hayes, Bromley, Kent

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—5 parts), 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.
 Tick against set required (only one set allowed on free trial).

BASIC ELECTRICITY **BASIC ELECTRONICS**

Signature

(If under 21, signature of parent or guardian)

NAME
 BLOCK LETTERS BELOW
 FULL POSTAL ADDRESS

WIRECOMP ELECTRONICS

TRANSISTOR POCKET RADIOS

Ideal Gifts—all supplied complete with personal earpiece, battery and carrying case. Fully guaranteed. Post free.

BOY'S 2 TRANSISTOR MODEL (Illustrated)

In attractive plastic case. Size only 4 x 2½ x 1½ in. 2½ in. speaker. Uses PP3 battery. Tunable over full medium waveband. **45/-**

BOY'S 4 TRANSISTOR MODEL

45/-

6 TRANSISTOR MODELS

In plastic case 4 x 2½ x 1½ in. 2½ in. speaker. Uses PP3 type battery Tunable over full medium waveband. **59/6**

2 Waveband (Long and Medium) Model size 5 x 3½ x 1½ in. cream/black plastic case. **89/6**

FAMOUS MAKE TRANSISTOR RADIO THE "STELLA"

7 transistor portable radio. Lonz, Med. and Short wavebands. Fitted tone switch and sockets for personal earphone and external aerial; chrome telescopic aerial. Uses four 1.5 v. torch batteries. Plastic cabinet in beige and red. Size 4 x 7 x 1½ in. Excellent tone. 2½ in. p.m. speaker. Comp. with shoulder strap and external aerial. Full guarantee. Price **£9.19.6** P. & P. 5/-



WONDERFUL BARGAIN FROM RUSSIA THE "SOKOL"

7 transistor radio covering full Medium and Long wavebands with exclusive rechargeable battery which can be recharged from any 110/250 v. A.C. mains supply. Can also operate on PP3 type dry battery. High quality P.M. speaker. Ivory and black plastic case with metal trim—size 6 x 3½ x 1½ in. Sockets for external aerial and earpiece. Complete with real leather case, dry battery, rechargeable battery and charger, personal earpiece. **WIRECOMP'S PRICE £6.9.6** P. & P. 2/6

WIRECOMP'S BARGAIN STORE

48 Tottenham Court Road, London, W.1
Thousands of bargains: Transistor Radios—Record Players—Tape Recorders—Radiograms—Rock Bottom Prices

THE "REALISTIC" 7

Transistorised Portable Receiver made to the highest professional standard. Comprises 7 Mullard Trans. plus Crystal Diode. 350 milliwatt output to 4in. speaker.—I.F. frequency 470 Kc/s—fully tunable over medium and long wavebands. Two-tone plastic cabinet with handle—size 7 x 10 x 3½ in. fitted socket for car aerial. Complete with full instructions. **MAY BE BUILT £5.19.6** All parts sold separately for **£9.19.6** Battery 3/9 extra



P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.) Also De Luxe Model with superior PVC covered wood cabinet and full view tuning dial. **ONLY £1 EXTRA.** All parts sold separately. Battery 3/9 extra. P. & P. 4/6.

SINCLAIR SUPER MINIATURE POCKET RADIOS

THE MICRO-6. Pocket radio only 1½ x 1½ x 1½ in. Complete with earphone and detailed construction data. Can be built for only **59/6**

THE SLIMLINE. The new 2-transistor pocket radio size only 2½ x 1½ x 1½ in. Can be built for **49/6**

INTERNATIONAL BRAND TAPE—Fully Guaranteed

MYLAR BASE	15-	ACETATE BASE	
3½ in. Triple play, 600ft.	15/-	3½ in.—150ft.	3 6
4 in. Triple play, 800ft.	17/6	3 in.—22½ft.	4 11
5 in. Double play, 1,200ft.	15/-	3 in.—300ft.	7 6
5 in. Triple play, 1,800ft.	35/-	5 in. Long play, 900ft.	10 -
5½ in. Double play, 1,800ft.	22/6	5½ in. Long play, 1,200ft.	12 6
6½ in. Triple play, 2,400ft.	45/-	7 in. Stand play, 1,200ft.	10/-
7 in. Stand play, 1,200ft.	12/6	7 in. Long play, 1,800ft.	15 -
7 in. Long play, 1,800ft.	19/6	P.V.C. BASE	
7 in. Double play, 2,400ft.	25/-	5 in. Stand play, 600ft.	8 6
7 in. Triple play, 3,600ft.	58/6	5 in. Stand play, 840ft.	11 6
		P. & P. 1/- extra per reel, 4 reels and over Post Free	

323 EDGWARE RD., LONDON, W.2. AMBassador 7115

378 HARROW RD., LONDON, W.9. CUNningham 9530

All Branches open all day Saturday. Early closing Thursday

Mail Orders to the above address for prompt service

BARGAINS FROM BROADWAY ELECTRONICS

GARRARD Latest Model A.T.66. Mono or Stereo £12.0.0. Autoslilm £5.5.0. A.T.6 Stereo £6.15.0. Autoslilm pick-up arm fitted with Rockette Stereo 25/-; A.T.6 shells 5/-. OC8, OC2, cartridges with brackets 15/- ea.

The "BLAKE" 12in. Heavy Duty Cabinet. Size 24½ x 18 x 9½ in. The Baffle is ½ in thick. Covered in Rexine and Vynair 85/-. De Luxe model veneered with wood grain Formica and standing on smart 6in. legs 5/-. Please add 10/- for postage.

"HAYDON" Cabinet. 16½ x 15 x 7½ in. Fabric covered suitable 12in. speaker 45/-. Postage 7/6.

Vynair speaker cloth 50in. wide 14/- yard. Rexine leather cloth 50in. wide 10/6 yard. S.A.E. for samples.

The BM.3.CRYSTAL MIKE 30/-; table stand for same 9/6.

GUITAR PICK-UP complete with clip and screened lead. 12/6.

NEON PANEL LIGHTS. 240v A.C. Arcoelectric, 2/6 each.

BARGAINS IN TRANSISTORS
AC127 (NPN) 5/- each. AF114, AF115, AF116, AF117, AF118, AF119, OC169, OC170, OC171, OC172 4/6 each. OC81M, OC71 2/6 each. OC72, OC75, OC82 all at 3/- each, RF Packs two OC45, OC44 8/6; AF Packs two OC81, OC81D 6/-; AF Packs two GET119 (OC83 equiv.), GET118 Driver 5/6; OC28, OC29 7/6; ORP12 Light Cell 7/6; Diodes OA81 2/3; OA94 1/6.

TRANSISTOR ELECTROLYTICS: 1, 2, 4, 5, 8, 10, 16, 32, 50, 100 mfd. all at 15 volts, 1/3 each. 100 mfd. 6v, 9d. each special offer. 25 mfd. 50v, 50 mfd. 50v, 50 mfd. 100v, 250 mfd. 25v, 500 mfd. 25v, 100 mfd 50v, 1,000 mfd. 12v all at 3/- each.

FARPIECES with cord and 3.5 mm plugs, 8 ohm magnetic 3/-; 250 ohm 4/-; 180 ohm magnetic with clip 6/6; Crystal 4/-

BROADWAY ELECTRONICS

52 MITCHAM ROAD, TOOTING, S.W.17
Phone: BALham 3984
(four minutes from Tooting Broadway Underground Station)

YOUR CAREER in RADIO & ELECTRONICS?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.R.E. Exam.; the RADIO AMATEUR'S LICENCE; P.M.C. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television Transistors; Radar; Computers; Servomechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:

NAMEBlock

ADDRESSCaps

.....Please

2.66

BRITISH NATIONAL RADIO SCHOOL

Great Britain: *Manx Radio* (P.O. Box 20, Douglas, Isle of Man), the legal British commercial station gives good reception in London on 1,295 (medium wave) at 1215 when the B.B.C. European Service French transmission ends. Transmitter power is only 0.05kw.

A special vote of thanks this month to those who answered the appeal for information on South American stations. Reporters this month are Middlesbrough High School S.W. Club, T. E. J. Toth, P. J. Quinn, A. Newman, J. E. Snoad, H. P. Meed, J. M. Richardson and S. Ormerod.

The Amateur Bands—by David Gibson G3JDG

ALL sorts of stories coming in this month and one or two peculiar ones are confirmed by reports from so many different sources that they look like being true. To begin with, although it must be admitted that we are still very close to the worst 10 metre conditions (sunspot-wise), there are numerous reports of great activity on the band already. All three modes are in evidence as are VK stations—yes Australians romping in on a.m. phone.

Queries and stories from a number of sources about the mysterious voice on top band signing NS1 or NS1A. This character is apparently located on board one of the oil drilling rigs at work in the North Sea, hence the call NS1A. He has been heard giving out his week-end shopping list right in the middle of top band much to the indignation of licensed Amateurs in the vicinity. However the G's appear to be having the last laugh because as NS1A pauses in his weekly order—other voices take over for him and proceed to order quite a wide variety of objects.

Quite apart from NS1A, top band has its transatlantics in session at the moment offering a good chance to hear a bit of DX. Dates are January 16, February 6 and 20, all from 0500—0730 hrs., but any time after midnight is usually the beginnings of activity. Remember W's and VE's are on c.w. right down the bottom, 1800-1825kc/s. For the optimistic, the JA frequency is 1880kc/s.

The L.F. Bands

Some very good openings down near mains frequencies this past month. **R. Iball** (Worksop), SX28, PR30, 80ft. 1.wire logged W1BB/1 and WIHGT both on top band, whilst on 7/Mc/s his best were 4X4—FA, QT. **Steve Wilson** (Ossett), 19 set, 180ft.1.w. 1.8Mc/s—DL1, EI, GI, GW OK1, PA. On 3.5Mc/s, VE1—KGF, CN, AA, APO, AR, AFK, VE2AE, VE3-SS, HF, VO1-GW, DD, GC, JW, W1MKK, POY, EVT, AW (ARRL HQ) W2-JAE, AU, GO WA2-BMP, RIB, 2BFM, W3TAF, DKT, WA4FFW, WA5SOX/P/VO2, 9H1AB. **James Brown** (Cardiff), 19 set, dipole, shows what can be done with determination. So good was this log that I thought it was for 20 or 15, but NO! 80 metres—CN8AW, 11ZSQ, K8YWG, KX6VQ (Marshall Is.), MP4TBO, many VE's, VK2AVA, VP7NS, VS6AJ (Hong Kong), many W's, YV5BTQ (Venezuela), ZB2AO, 9M4LP. **Chris Peel** (Stoke-on-Trent), S750, 90ft. 1.w. 80 metres, MP4-TBO, BAA, VE, VO, VP9FK (Bermuda), W's, K's, W1/KP4, 4U1ITU, 5VJBTQ, 7X2AH, 7X2BA, 9M4LP (Singapore), all s.s.b. and between 2300-0200 hrs. 40 metres raised mainly EU's like CT1, DL, EA, II, LX, ON4 SM, UA1, YU, etc. **I. Black** (Gillingham), HE30, W6BCX,

Multee antenna for 3.5 and 7Mc/s. numbers are standard RST, F9RY/P/FC 59, HB3ITU 59, HV1CN 59, IØFGM 56, K2GL 53, VE-1AHP 56, 3KH 43, W-1IIM 57, 2ZPL 56, ØZPL 58, YU4FD 54, YV5BPJ 57, ZL5LM 32, 4U1ITU 59. On 40 many EU's plus OX3JV 58, SV1BH 57, VK2MO 45, YV-1II 56, 1PW 54, 3FQ 55, 5BPJ 58, 9AA 55, ZC4MO 55, ZL2BCG 56, 4X4FA 57, 7X2AH 53.

Late flash. Last night and early this morning, December 4/5, I listened with the **Verulam A.R.C.** and took part in the transatlantics on top band. The following stations were logged: VO1FB, DL1FF, OL1AEF, WIHCH, W2EQS, VE3DDR, VE2UQ, W8HG, K8CRJ, VO1HN, W1BU, OX1LM, OL1AEE, K1LMO, OK1AMK, WIHGT, OLSABW, VE3AGX. After a time it was decided to try our hand at working across the pond and the following were worked, your faithful scribe accounting for three scalps: W1BB/1 579, WIHCH 559, W2EQS 449, VE3DDR 569, VE2UQ 449, OL1AEF 559, VO1HN 569. The latter station also received us on sideband at 55, but we were not able to resolve VO1HN on a.m.

The H.F. Bands

Twenty metres, back to its seasonal "dying" at 20.00 hrs., seems to be providing quite a bit of activity during the hours it is open. Best listening times appear to be just after lunch. **H. P. Meed** (Poynton), HRO + pre-selector, 40ft. 1.w. SE/NW. IS1VAZ (Sardinia), KR6-D1, UL (Okinawa), KX6OR (Marshall Is.), OD5BZ (Beirut), UO5PK, VE3WQ, ZD8RD (Ascens.on Is.), ZL2JO (Wellington, N.Z.), ZL3DX, 5Z4-EC, IR, 5T5AO. **Stephen Beal** (Muswell Hill), uses a simple t.r.f. with an indoor antenna, some 60ft. of wire in fact. Homebrewed and working well as the following evidence suggests: EP2AX, FG7XL, FK8AC (New Caledonia), H18RSD, KL7EBC, KP4BKP, KR6UL, SU11M, TF2WG, VP9AK, VS9AE, WB6GCD, W7THX, 3A2BF, 7Q7PBD. All these on twenty, while on 15 Stephen's best were CN8BB, ZE2JJ, 5N2FEL and VK-2NN, 3ACD. **L. Dettman** (Hull), xtal controlled converter into a 19 set, 132ft. 1.w. 21Mc/s, CN8FT, EP3USA, K6BPE/MM, KP4AXC, KV4CX, OA8V, OHØNI, 9K2AD (Kuwait), 9G1FV, ZS1TV, ZS6AOU, ZE1AC, VS9AWR, VK5KM, PY1CK, OX3JV, 7Q7BN, 7X2BB, 5N3JRM. **I. Black** again reports 20 very lively with CR3GF, CR6DA, CR9A1 (Macao): CN8BB, JA3ARA, KZ5PW, OA4OA, PJ3CV, T12DA, VE3CVL/P/SU, W8CJY/P/KP4, 39 VK's (yes, thirty-nine), VK9-JO, X1, both on Cocos-Keeling, VP2SK, VP6KL, VP7CC, VU1BA.

—continued on page 894



Add-in Transistor Stage

EXTRA AUDIO GAIN FOR SMALL TRANSISTOR RECEIVERS

MANY popular transistor receivers have a combined audio amplifier and driver stage, followed by push-pull output. With this circuit, the driver immediately follows the diode detector, in superhets. An audio amplifier, placed between detector and driver, will then give a considerable increase in volume from weak transmissions.


The additional stage is normally not required in receivers which already have an audio amplifier before the driver, and instability would probably be caused by the addition. Nor is the extra stage

intended as a cure for low sensitivity and poor results caused by wrong alignment, or any other receiver fault. But when the receiver is in proper order, conversion from six transistors to seven, by including a low level a.f. stage can greatly improve results.

Fig. 1 shows a suitable circuit, needing few parts. R1 and C1 will be present, and point X will be connected to Y, Tr2 being the combined audio amplifier and driver. Point x is disconnected from y, so that Tr1, R2, R3 and C3 can be added. Base stabilisation is provided by R2 from the collector

of Tr1. C2 is optional, and can be included to reduce hiss and emphasise lower frequencies, often poorly reproduced in miniature receivers.

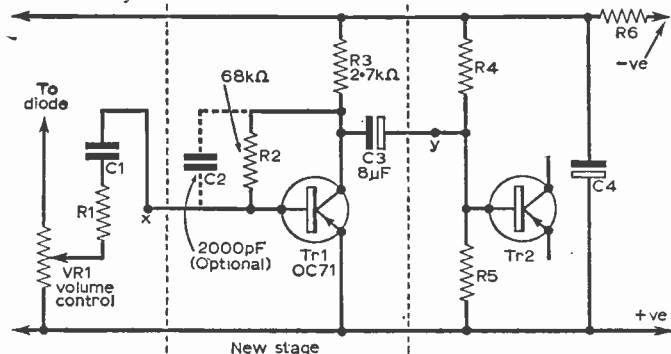In this circuit, the resistor values are generally not very critical. R2 may be 100kΩ. R3 can be 3.3kΩ or 3.9kΩ. Tr1 should be in good condition to avoid noise. The few items required can be assembled as a small packet, then inserted by soldering the appropriate leads to x, y, earth (positive) line, and negative. Leads from x and y, and also Tr1, should be short and direct.



Circuit diagram of the complete unit.

ON THE SHORT WAVES

—continued from page 893

XW8AX, ZL-1KG, 2UW, 3AB, 3MN, 4X4, 5T5, 5Z4, 6Y5, 7Q7, 7X2, 9G1, 9H1.

Ten Metres

Yes, its own heading. Many logs for this band, far too many to print, unfortunately. If ten sounds dead at your QTH—start checking the gear. The following log from Alex Thurlow (Croydon), SX101A, 3 ele. beam. Such a huge list that only the prefixes are mentioned, but all heard between 0900—1800 hrs. CR6-7, CX2-4, DL, EA, F, I1, LU2-3, 7, 1, 4, LA1, OH5, OZ1, PY1-2, SM, UT5, UL7, UY5, UB5, UA4, 6, 9, UQ2, UP2, ZC4, ZE2, ZS1, VK6QL (1024 hrs.), 7X2, 9J2, 4X4, 9H1, 7Q7, all on a.m. too. Stephen Beals's t.r.f. raked in CR6, DL, IØ, OH, OE, SM, UA, UB, UP, ZE, 5A3, 9H1.

Here and There

Sharp ears, keen s.w.l., rig in working order? If the answer's "Yes" then you are invited to

listen out for the following: VKØTO Macquarie Is. 20 c.w., FB8WW Crozet 15 and 20, WAØBDM/KG6 Mariana 20 s.s.b., JT1FM Mongolia 20, VR6TC Pitcairn Is. 20 c.w., YJ8BG 15 s.s.b. Notes for the diary, KG1 callsigns are now out and the sole prefix for Greenland will be OX. Watch for the call FR7ZI who hopes to do a jaunt around Comoros, Glorieuses, Juan de Nova and Europa, and Reunion Is. Dates in January for the contest minded include: 15-16th, Affiliated Societies Contest; 29-30th, CQ WW 160 metre DX Contest; 30th, First 144Mc/s Contest (c.w.).

PRICE CORRECTION

Will readers please note that the total H.P. price of the Imperial Hi-Fi Stereophonic Radiogram Chassis advertised by Lewis Radio, appearing in the issues dated November, December, 1965 and January, 1966, was shown as £44 4s. 6d., instead of £49 4s. 6d.

WHITELEY

SLIMLINE

LC.92

SPEAKER SYSTEM

● SLIM CABINET

only 6" deep. Height 29". Width 24"

● A 9", 15 OHMS DRIVE UNIT


with graded cone and extended treble response.

● ACOUSTIC LABYRINTH CABINET

gives balanced response throughout the audio spectrum.

● CLEAN DESIGN

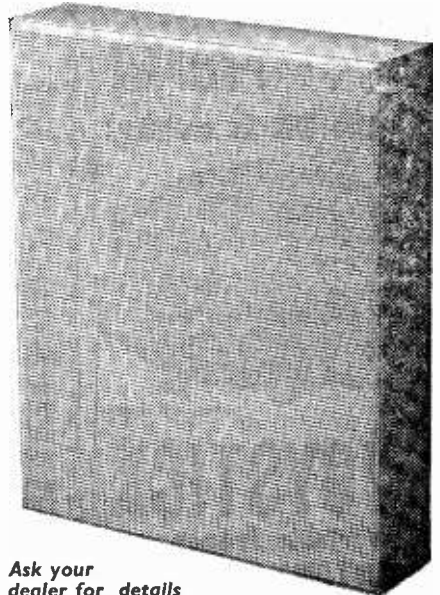Walnut cabinet with satin melemine finish.
Weight 25½ lbs.



Ask your dealer for details of the full range of Whiteley high fidelity cabinets, or write to:

WHITELEY ELECTRICAL RADIO CO. LTD., MANSFIELD, NOTTS.
Telephone: Mansfield 1762/5. London Office: 109 Kingsway, W.C.2

D. & B. TELEVISION (WIMBLEDON) LTD.

131 KINGSTON ROAD · SOUTH WIMBLEDON · LONDON S.W. 19

Telephone: CHerrywood 3955

ALL BRAND NEW VALVES GUARANTEED 3 MONTHS

Postage and Packing on Valves 6d. each.

AZ31	10/6	EF80	7/-	PCF80	8/4	UCH81	7/3	6F26	10/9
DAF91	7/10	EF85	7/-	PCF82	8/4	UCL82	8/8	6F26	9/8
DAF96	7/10	EF86	8/4	PCF86	10/6	UCL85	10/8	6L1	15/6
DF91	6/8	EF89	7/-	PCF801	10/-	UF41	7/6	6L18	12/6
DF92	6/8	EF91	11/-	PCF802	10/-	UF42	9/-	6/30L2	9/8
DF96	7/10	EF92	9/-	PCF806	10/-	UF80	7/6	10C2	12/-
DK91	7/10	EF183	8/8	PCL82	8/4	UF85	7/6	10F1	2/5
DK92	7/10	EL83	10/6	PCL83	9/8	UF89	7/-	10F9	8/-
DK96	7/10	EL84	8/8	PCL84	8/8	UL41	7/6	10F18	8/0
DL92	6/8	EL86	9/8	PCL85	8/8	UL46	10/6	10P13	12/6
DL94	6/8	EL41	5/-	PCL86	8/8	UL84	8/8	10P14	11/-
DL96	6/8	FL84	6/4	PL36	10/-	UY41	5/6	20F2	11/-
DY86	7/-	EM80	2/8	PL81	8/4	UY85	5/6	20L1	12/6
DY87	7/-	EM81	7/3	PL82	6/4	5Y3	5/5	20P1	13/-
EABC80	7/6	EM84	8/8	PL83	8/4	5Z4	7/6	20P3	12/-
EAF42	8/6	EM85	10/-	PL84	7/-	6V6	7/7	20P4	12/-
EB91	4/8	EY51	7/-	PL800	14/-	6X5	7/5	20P5	13/-
EBC38	11/2	FY86	7/-	PY33	9/6	R19	14/8	30C15	9/6
EBC41	7/2	EZ80	5/6	PY80	6/-	U25	10/3	30C17	11/6
EBC81	6/6	EZ41	5/6	PY81	7/-	U26	10/6	30C18	10/-
EBF80	7/-	EZ80	5/6	UY82	5/6	U191	8/9	30F6	10/-
EBF89	7/-	FZ81	5/6	PY83	9/6	U193	7/-	30FL1	15/3
ECC81	7/4	FZ86	5/-	PY88	7/-	U281	11/2	30L15	13/8
ECC82	7/4	GZ82	11/-	PY800	7/-	U281	13/9	30L17	11/6
ECC83	7/4	GZ84	11/-	PY801	7/-	U282	13/9	30P12	9/6
ECC84	7/8	HBC90	6/4	UABC80	7/-	U301	13/9	30P4	12/-
ECC85	7/4	PABC80	7/6	UBC41	7/-	U801	10/-	30P19	12/-
ECC86	9/6	PC86	8/10	UBC81	7/-	U99	8/6	30PL1	12/6
ECC85	13/-	PCS8	7/6	UBF80	7/-	6F1	9/6	30PL11	12/6
ECH42	8/6	PC97	8/10	UBF89	7/-	6F13	12/8	30PL13	12/6
ECH81	7/-	PCC84	7/4	UCC84	8/10	6F14	15/-	30PL14	11/8
ECL80	7/4	PCC85	7/4	UCC85	7/4	6F15	12/6	30FL14	10/6
ECL82	8/8	PCC88	12/3	UCF80	9/4	6P23	10/6	30FL12	10/6
ECL83	10/6	PCC89	10/6	UCH42	9/6	6P24	10/9	30FL18	10/6
ECL86	8/8	PCC189	10/6						

We are open 9 a.m. to 6 p.m. Monday, Tuesday, Thursday and Saturday 9 a.m. to 7 p.m. Friday. Closed all day Wednesday.

SERVICE SHEETS TELEVISION !! ALL MAKES AND MODELS 4/- P. & P. 4d.

SWLs · SWLs · SWLs · SWLs

Hark!
Hark!
-the DX is calling!



Special RX tuner
4 1/2" x 3 1/2" x 3 1/2"

JOYSTICK
Variable Frequency
ANTENNA SYSTEM

This revolutionary and pat. pend. aerial system possesses the unique property of an even response over all frequencies between 1.4-30 Mc/s.

Every JOYSTICK Aerial System is supplied complete with feeder and an aerial matching unit. Just connect your RX—it is ready to go and gives an unprecedented 'lift' to signal strengths especially for 'chiff' and 'cave' dwellers—EVEN FROM UNDERGROUND! Naturally the advantages of using the 'JOYSTICK' 'up-in-the-clear' are even greater!

4,000 Joystick aeriels all over the world have already shown that this is the first major break-through for 20 years in the field of aeriels. The performance for such a compact unit (7"6" assembly) is staggering. Even the sceptics have been convinced once they have understood the basic principles and have followed the simple 'tune-up' procedure given in the detailed instructions.

New Joystick Range

There is now a whole new range of Joystick Aerial Systems—made to match your QTH, your rig and your pocket! The SYSTEMS cover SWL, TX/RX, indoor and outdoors, mobile and even a new JOYMAST! Made only in the finest materials the SYSTEMS are reliable and permanent! Read all about them in our new brochures—

GUARANTEE: Partridge operate a rigid, 100% Money Back Guarantee if you're not completely satisfied!

Read testimonials from all over the world! "Four different receivers showed improved performance over a dipole" reports the U.S.A. C.Q. Magazine.

"Excellent results, Australia, Ceylon, South Africa at good strength although lately reception conditions have been poor." W. Cumming, Lossiemouth, Scotland.

READ ALL ABOUT IT! This ticket will bring you the new brochure by return of post!

PARTRIDGE ELECTRONICS LTD.

Caister House, Prospect Road,
Broadstairs, Kent. Tel: THANET 62335

NAME

ADDRESS

P.W.

TRANSISTOR POCKET BOOK

by
R. G. Hibberd

B.Sc., M.I.E.E., Sen.M.I.E.E.E.
Manager of the Research & Development Department of Texas Instruments Ltd.

25/- Postage 1/-
TECHNICAL TOPICS FOR THE RADIO AMATEUR, by J. Pat Hawker.

10/- Postage 1/-
AMATEUR RADIO CALL BOOK 1966, Edition. Compiled by R.S.G.B.

6/- Postage 8d.
TAPE RECORDER SERVICING MANUAL, by H. W. Heliery 63/-.

Postage 2/-
MUSICAL INSTRUMENTS AND AUDIO, by G. A. Briggs. 32/6.

Postage 1/-
THE RADIO AMATEUR'S V.H.F. MANUAL A.R.R.L. 18/-.

Postage 1/6.
GETTING STARTED WITH TRANSISTORS, by L. E. Garner, Jr. 28/-.

Postage 1/-
TELEVISION SERVICING HANDBOOK, by G. J. King. 35/-.

Postage 1/6.
REFERENCE MANUAL OF TRANSISTOR CIRCUITS, by Mullard.

12/6. Postage 1/-
COMPLETE CATALOGUE II-

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
British and American Technical Books

19-21 PRAED STREET LONDON, W.2

Phone: PADdington 4185
Open 6 days 9-6 p.m.

FAMOUS FOR THIRTY YEARS for
SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS



H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1966 RANGE

1-Valve model "CX", complete kit, Price 34/6
Customers say: 'Definitely the best one-valve S.W. kit available at any price.' This kit contains all genuine Short-Wave components—a drilled chassis, accessories and full instructions. Ready to assemble and of course, as all our products, fully guaranteed. **FULL RANGE** of other kits still available including the famous model K', price 77/-. Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to—

"H.A.C." SHORT-WAVE PRODUCTS
(Dept. P.W.), 44 Old Bond St., London W.1



EQUIPMENT CABINETS OF DISTINCTION



Imperial

- Illustrated in this advertisement are two fine cabinets from the Lewis Radio Range.
- These Cabinets are just two of a really extensive range.
- Each one carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Lowflex

FREE THE NEW LEWIS RADIO CATALOGUE

Designed to assist your choice of Cabinet.

The New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely FREE!

Please send your FREE 24 page cabinet catalogue.

NAME _____

ADDRESS _____

_____ (Dept. P.26)

Capitals please

LEWIS radio

100 Chase Side, Southgate, London P.26
Tel: Palmers Green 3733/9666

NOISE ABATEMENT

TRACING AND CURING NOISE FAULTS IN RECEIVERS

by K. Royal

PROBABLY one of the worst radio faults to diagnose and cure is that of noise. Noise in this context does not include those noises brought on by external interference but embraces all those noises which are created in the set itself by a host of fault possibilities.

Noise is made even more difficult to trace when it stops and starts at random intervals. This is often the case, and the fault tracing exercise is made really frustrating when it is found that the noise ceases temporarily for hours on end by the application of an instrument test prod or by operating the wavechange switch!

Often it happens that the set works for hours noise-free and then develops a bout of bad noise which more often than not stops before one has a chance to perform any detailed tests. Set noises range from distinct crackling to more subtle fizzing and frying effects emanating from the loudspeaker.

What can be done to trace this sort of noise and how do the professionals tackle the problem?

Do Not Disturb

The very first step is to locate the approximate whereabouts of the noise in the set with the very minimum of disturbance, for if the chassis is removed from the cabinet and the set generally subjected to vibration the noise may stop for many hours or even weeks.

The thing to do, then, is to get to know as much about the noise while it is actually present. Then, if the noise happens to stop one has at least made a good start on locating it next time it occurs.

Many crackling noises are caused by electrical interference picked up by the aerial, and to see whether the crackles, plops or fizzles are due to this cause the first thing to do is to remove the aerial from the set.

If the set is tuned to a station, removal of the aerial will, of course, stop the set from working or reduce its volume, but if the noise remains at its original intensity, one can be fairly safe in assuming that it is resulting from a set fault.

When the aerial is removed the noises may not disappear completely, neither may the programme signal, for modern sets are very sensitive and will often pick up signals—wanted and unwanted—without an aerial. Nevertheless, the point to note is whether the interference reduces in volume. If it does, the aerial is guiding the noise signals

into the set, so they must be radiated by something outside.

If the noises are developed by the set they normally continue at the same strength without the aerial connected.

Dealing With Portables

At this stage we must consider the portable or transistor set which employs a ferrite rod aerial or loop. This cannot be disconnected because it represents the aerial tuned circuit. What, then, can we do to prove whether or not the noises are coming in from outside?

We can often get a clue in this respect by tuning the set off a station and orientating it through 360° to see whether the noise intensity varies.

If it remains the same at all directions it is likely that the noise is occurring in the set itself, for if the intensity of the noise rises and falls as the set is rotated it means that the set is responding to an external signal.

In passing, it is interesting to note that a transistor portable can be employed to locate a noise source. A ferrite rod aerial is extremely sensitive to direction, especially from the aspect of **minimum** pick up. Maximum pick up occurs when the ferrite rod is in line with the signal field. The rod concentrates the signal field into the aerial windings, as shown at (a) in Fig. 1.

Pick up continues over a relatively wide arc, but when the field is at right-angles to the rod there is virtually zero signal induction and this happens only over a few degrees. Thus, by orientating a portable with a ferrite rod aerial for minimum signal or interference pick up, one can be sure that the signal or interference source lies somewhere on a line which is at right-angles to the ferrite rod, as shown at (b) in Fig. 1. This is the basis of radio direction-finding.

Another way to ensure that noise from a portable is occurring in the set is to screen it thoroughly by very fine wire netting or perforated zinc sheet. Before the screen is applied, the volume should be turned to maximum and the set adjusted to give maximum noise output. If the noise level remains the same with the set embraced by such a screen, something inside the set is undoubtedly responsible.

Once we have established that the set itself is responsible for the noise, the next move is to discover the approximate area within the set where the noise is being generated. Remember to do this with the minimum of disturbance to the set.

Three Main Sections

There are three main sections in a receiver. These are (i) the r.f. signal stages, including the i.f. amplifier and detector; (ii) the local oscillator; and (iii) the a.f. stages. The simple block diagram in Fig. 2 shows these. Without taking the set from its cabinet we can get a very good idea as to which of these three sections is responsible for the noise.

In all receivers the radio signal is changed to an audio-frequency signal at the detector, and the signal is then passed on to the a.f. stages via

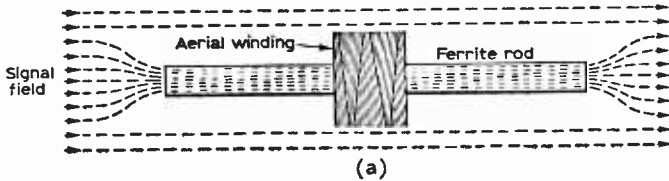


Fig. 1: The action of a ferrite rod aerial when at (a) it concentrates the signal field along its length to fully embrace the aerial winding (thus maximum pick-up occurs when the rod is in line with the field) and at (b) where there is virtually no pick-up with the rod at right-angles to signal field.

the volume control, as shown in Fig. 2. It follows, therefore, that if the noise continues with the volume control turned right down (so that the signal and oscillator stages are effectively isolated from the a.f. stages), then it must be generated somewhere in the a.f. stages.

Conversely, if the noise intensity rises and falls as the volume control is turned up and down and ceases when the control is turned right down, then the noise is undoubtedly being produced somewhere in the signal stages. At this time we have not isolated the oscillator.

Let us suppose that the noise intensity varies as the volume control is operated. We have now to find out whether or not it is coming from the local oscillator. This section of the receiver is often overlooked and yet it is a prolific noise source as it deals with relatively high amplitude r.f. signals which are likely to cause components to fail in such a way as to become noisy.

It may be wondered how on earth an oscillator can be tested for noise without dismantling the set or connecting instruments. Fortunately, there is a simple, though not very often used, method.

Oscillator Noise-test

An oscillator in a radio set is really a very small transmitter. It radiates radio signals to a small extent, although of course its purpose is to


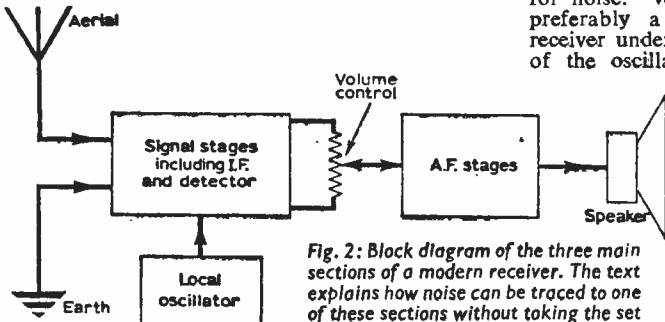


Fig. 2: Block diagram of the three main sections of a modern receiver. The text explains how noise can be traced to one of these sections without taking the set from the cabinet or connecting instruments.

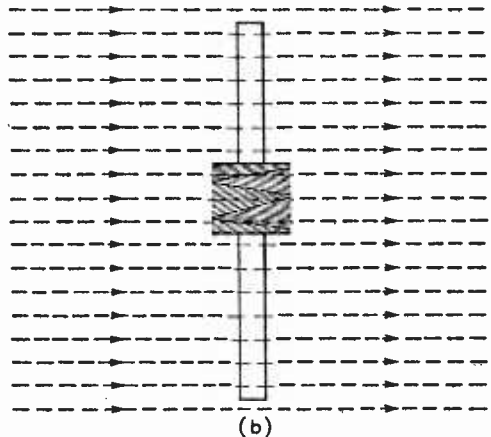

frequency. As ordinary broadcast a.m. sets nowadays have an i.f. of 470kc/s, this would put the local oscillator at 1.470Mc/s.

If there were a transistor capable of tuning to that frequency any modulation on the oscillator signal could, in fact, be heard.

Here, then, is how we can monitor the oscillator for noise. We simply set up a second receiver, preferably a transistor portable, close to the receiver under test and tune this to the frequency of the oscillator of the noisy set. As already described, the oscillator of a set tuned to 1Mc/s will push out a signal at about 1.470kc/s, and this is just a little above 200m on the m.w. band.

The thing to do is to adjust the tuning of the monitor receiver to a weak carrier or station around 200m and then tune the noisy set around 300m on the m.w. band until the oscillator is heard on the monitor set as a heterodyne whistle on the tuned station or carrier.

THE AUDIO FIDELITY STEREO-THIRTY

A High Fidelity All Transistor Stereo Amplifier providing 10 watts OUTPUT (per channel)

10 watts R.M.S. into 15 ohm load.
15 watts R.M.S. into 3.7 ohm load.

TOTAL HARMONIC DISTORTION

0.1% at 5 watts R.M.S. } into
0.3% at 10 watts } 15 ohm
R.M.S. 1,000 c.p.s. } load

DAMPING FACTOR 20

FREQUENCY RESPONSE

+11 dB 20-20,000 c.p.s.

HUM AND NOISE -80dB

CROSS TALK -42dB to -53dB.

MAINS INPUT SELECTION

100-110 120-200-210-220-240v. 50/60 c.p.s.

SEMI-CONDUCTORS (per channel)

AC107, OC44(3), OC81Z(2), OA5, OC127Z, AD149 (2).

BASS CONTROLS

+11 dB to -16 dB at 40 c.p.s.

TREBLE CONTROLS

+15 dB to -15 dB at 10 Kc/s.

EQUALISATION

Gram. to std. R.I.A.A. characteristic. Tape head to std. C.C.I.R. characteristic.

SIZE 12 1/2" x 4" x 8"


WEIGHT 12lb.

FILTER (Steep Cut)

7 Kc/s. 11 Kc/s. 15 Kc/s.

Incorporation of the very latest Mullard Transistors has made possible the really outstanding performance figures of this brilliant design. Compare them with other leading makes currently available.

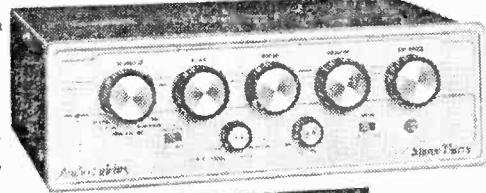NOTE: Rated output is in watts R.M.S. (continuous) which should not be confused with I.H.F.M. momentary pulses).



RETAIL PRICE 39⁹⁹

The Pre-amplifier is based on ideas incorporated in the Dinsdale MkII (W.W. Jan. 1965) IT ELIMINATES THE NECESSITY OF MATCHED INPUTS & COMPLICATED SWITCHING ARRANGEMENTS. IT ALSO PRODUCES CONDITIONS OF MINIMUM NOISE AT HIGHEST SENSITIVITIES.

R.M.S. on each channel

INPUT SENSITIVITIES

(for 10 watts R.M.S. into 15 ohms).

Pick-up Magnetic 3.5 m.v. 33 1/3 r.p.m. 7 m.v. 78 r.p.m.

Pick-up Crystal/Ceramic 400 m.v.

Microphone 5 m.v. Tape Head 2 m.v. Aux. (Radio Tuner, Tape Rec. Ceramic P.U. etc.) 100 m.v. (Above sensitivities will be doubled when output load is 3-4 ohms).

INPUT SELECTOR

33 1/3 r.p.m., 78 r.p.m. Aux. Mic. Tape Head.

INPUT SOCKETS

Magnetic P.U., Crystal/Ceramic Pick-up Aux. Tape Head Microphone.

Built to the highest standards employing latest materials and techniques.

DESIGNED FOR EASE OF FITTING IN CABINET OR FOR FREE-STANDING USE.

Tested for satisfactory operation in temperatures of up to 50°C. (120°F.)

EXPORT ENQUIRIES INVITED

Designed and developed by the Audio Fidelity Group of Companies.

Manufactured and Distributed by LINEAR PRODUCTS LTD. ELECTRON WORKS, ARMLEY, LEEDS.

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronic Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

SATISFACTION OR REFUND OF FEE.

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £30 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

(Dept. SE/21), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.,
- Electrical Eng.,
- Civil Engineering,
- Radio Engineering,
- Automobile Eng.,
- Aeronautical Eng.,
- Production Eng.,
- Buildng. Plastics,
- Draughtsmanship,
- Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I.Mech.E.
- A.M.I.C.E.
- A.M.I.Prod.E.
- A.M.I.M.I.
- A.I.O.B.
- B.Sc.
- A.M.I.E.R.E.
- City & Guilds
- Gen. Cert. of Education
- Etc., etc.

PRACTICAL EQUIPMENT

- Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics Etc., A.M.I.E.R.E., City & Guilds
- Radio Amateur's Exam R.T.E.B. Certificate P.M.G. Certificate
- Practical Radio
- Radio & Television Servicing
- Practical Electronics
- Electronics Engineering
- Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME

ADDRESS


.....

.....

SUBJECT OR EXAM THAT INTERESTS ME..... (SE/21)

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

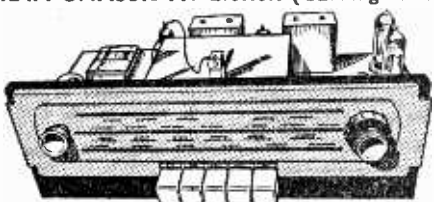BRAND NEW AM/FM (V.H.F.) RADIO GRAM CHASSIS AT £13.13.0 (Carriage Paid)



Chassis size 15 x 8½ x 5½ in. high. New manufacture. Dial 14½ x 4 in. in 2 colours, predominantly cream. 200-250v. A.C. only. Pick-up. Ext. Speaker. Ae., E. and Dipole Sockets. Five pushbuttons—OFF, L.W. M.W., P.M., and Gram. Aligned and tested. O.P. Transformer. Tone control. 1000-1900 Mc.; 200-550 Mc.; 88-95 Mc/s. Valves E280 rect.; ECH81, EF89, EA8C80, EL54, ECC85, 90-ohm speaker required. 9 x 6 in. ELLIPTICAL SPEAKER 20" to purchasers of this chassis. TERMS: (Chassis) £8.10.0 down and 5 monthly payments of £2.4.0. Cheap Room Dipole for V.H.F. 12/6. Feeder 6d. per yard. ALTERNATIVE DESIGN. Similar to above chassis. With addition of Shortwave 6-17 Mc/s. Price £15.15.0 (carr. paid). TERMS: £3.10.0 down and 5 monthly payments of £2.4.0. Total H.P. price £16.14.0. Circuit diagram 9/6. Carriage to N. Ireland 20/- extra.

2-VALVE GRAMPHONE AMPLIFIER Price 37/6 (P. & P. 2/6)

Overall size 4" wide x 5" high x 2½". Volume and tone controls. Mains lead. Screened lead input. With output transformer for 3-ohm. For series connections to Garrard and B.S.K. Autochangers and Players, having 90v. tapping. Valves UY85 and UCL82. Can also be supplied on fabric covered board with mains transformer and 6" x 4" speaker. Valves E280 and ECL82 at 55/-. (P. & P. 5/-). 3-valve Gram. Amp. Board 14" x 7½" (x 2½" overall). UY85. UCC85 and UL24 with speaker 7" x 4". Price 70/-. (P. & P. 6/-).


BATTERY ELIMINATOR

For 4 low consumption valves (96 range) 90v. 15mA and 1.4v. 125mA at 2/6. (4/- post), 200-250v. A.C. Also for 250 mA. 1.4v. and 90v. 15 mA at same price. Two units each 8½" x 5½" x 1½".

TAPE RECORDER AMPLIFIER


Fully built. Front panel 12½ x 3 in. Chassis size 10½ x 5 x 4 in. Valves EF86, ECC83 and 2EL84. Controls (1) Mic. Vol. (2) Tuner/P.U. Vol. (3) Play back or monitor, (4) Tone 2 lack sockets for Tuner/P.U. and Mic-switch for superimpose. Separate power pack containing trans. and rectifier. For Collaro studio deck only. Price £8.14.0 (6/- P. & P.).

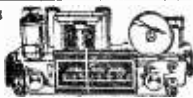SELF-POWERED V.H.F. TUNER CHASSIS
Covering 88-95 Mc/s. Dims. 8 x 6 x 6 in. high. Valves ECC85, EA8C80 and 3-EF89's with metal rectifier. Mains transformer. Fully wired and tested. ONLY £8.17.6 (carr. paid). Room dipole 11/6. Feeder 6d. per yard.



8 WATT PUSH-PULL O.P. AMPLIFIER £5.5.0 (6/- Carr.)

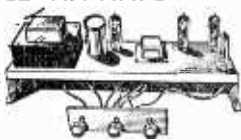200-240 A.C. mains. Bass, treble and vol. controls. EF80, ECC83 and 2-EL54. Chassis 10 x 2½ x 3½ in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as flying panel. With Cream/Black control panel whole length of front chassis.



4-SPEED AUTOCHANGERS

GARRARD AUTOSLIM	£5.10.0
GARRARD AUTOSLIM STEREO	£6.0.0
GARRARD A.T.6	£10.0.0
GARRARD A.T.6 STEREO	£10.10.0
GARRARD 3000	£8.18.0
GARRARD 3000 STEREO	£9.9.0

Carr. 5/- each

The
SUPER 6
LONG & MEDIUM WAVE
TRANSISTOR RADIO



A quality radio available as a kit or ready built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12. 12. 0 commercial model.

★ All new parts. ★ 6 transistors and diode. ★ 350mW output. ★ Superhet circuit. Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet. 11 x 7½ x 2½ in. ★ Vinyl covered in various colours. ★ 6 x 4 in. speaker giving good bass and treble response. ★ Full instruction booklet 2/-. Free with kit. ★ I.F. frequency 470 kc/s. ★ Lining up service if required. ★ All parts supplied separately. Write for list. S.A.E. please. ★ 9v. battery required. VT9 or P.P.3 (3/9 with kit). PLUS 5/- POST. COMPLETE KIT ONLY **£4.0.0** OR FULLY BUILT £6.17.6 Tax & Carr. Paid

V.H.F. Pre-amplifier with high signal-noise ratio and gain of at least 3:1 under average fringe area conditions. Metal container 3¼ x 3¼ x 1½ in. high with strap for eaves loft or skirting fixing. 9 volt battery operated, using transistor AF114. Covers all British and some Continental stations. 88 to 108 Mc/s. Order with coincidence of improved reception. Price 32/6 (3/- P. & P.)

TRANSISTORS

Packet of 3 coiled RF transistors (equivalent to OC44/5) 7/6 post paid. Set of 6 transistors and diode with circuit diagram. Neatly packed in foam-lined box; useful in presentation. 15/- post paid.

4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER HIGH IMPEDANCE



PRINTED CIRCUIT. 4 in. x 2½ in. x 1½ in. over transformers. Output for 3-ohm speaker. Suitable for microphone record player and stereo-com. 9 volt battery required. Frequency range 100 cps. to 25 Kcps. Push-pull output class B. Instruction sheet provided. Fully wired ready for use. Three types. 200mW 35/-; 500mW 41/-; 1.2W 57/6. (P. & P. 2/6 each).

AMERICAN BRAND RECORDING TAPES FULLY GUARANTEED AT RECORD LOW PRICES

MYLAR BASE			
7in. Stand. play. 1,200ft.	12/6		
7in. Long play 1,800ft.	18/6		
5in. Double play 1,200ft.	15/-		
5in. Double play 1,800ft.	22/6		
7in. Double play. 2,400ft.	25/6		
3in. Triple play 450ft. (Plain white boxes)	12/6		
3in. Triple play 800ft. (Plain white boxes)	14/-		
4in. Triple play 900ft. (Plain white boxes)	22/6		
5in. Triple play 1,800ft. (Plain white boxes)	42/6		
7in. Triple play. 3,600ft. (Unboxed)	76/-		
ACETATE BASE			
5in. Stand. play. 600ft.	8/-	MESSAGE TAPES	
7in. Stand. play 1,200ft.	11/-	3in. Stand. play. 150ft.	3/6
5in. Long play 900ft.	10/-	3in. Long play 225ft.	4/11
5in. Long play 1,800ft.	12/6	3in. Double play 300ft.	7/6
7in. Long play 1,800ft.	15/-		

Postage 1/- per reel (4 or more post. rec.)

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

2/2 mins. from Station and Buses. Aldershot 22246

CLOSED WEDNESDAY AFTERNOON

CATALOGUE 6d.

Regret overseas orders cannot be executed

AROUND THE WORLD
GO A.F.N. PATENTED
396
£2
POST FREE

Pat. App. For

On your OWN TRANSISTOR PORTABLE.
* No Plugs—No Connections! Just place Dewtron Wave Trap near radiol Boosts 'Pirate' and distant stations, reduces 'fading'.
* Extends Battery Life.
* Use in car or caravan Without Aerial!
British-made. Supplied with PP3 batt. (life several months) and instructions. Money refund guarantee.
D.E.W. LTD., Dept. P.W. Ringwood Road, FERNDOWN, Dorset.

TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR by Douglas, 18/- P. & P. 1/-
Amateur Radio Call Book, 1966, ed. by R.S.G.B. 6/- P. & P. 8d.
Pick Ups, the key to Hi-Fi by Walton. 10/- P. & P. 9d.
Transistor Substitution Handbook, American, Jap, etc. 12/6. P & P. 1/-
Elements of Transistor Pulse Circuits by Towers 35/-. P. & P. 1/3.
Solar Cell and Photo Cell Experimenters Guide by Hoberman. 24/- P. & P. 1/-
ABC's of Tape Recording by Crowhurst. 16/- P. & P. 1/-

Where possible 24 hours service guaranteed

UNIVERSAL BOOK CO.
12 LITTLE NEWPORT STREET, LONDON, W.C.2 (adjoining Lisle Street)

2 METRES 4

The thrills of VHF Amateur Radio! Complete Kit, 70-150 Mc/s, costs only 42/6 (by post. UK. 3/3 extra) also now available, new transistor Short-Wave kit model TR2 10-180 metres, ideal for beginners to Ham radio via simplified "Easy-Built" step-by-step instruction from 79/6. Write today enclosing a stamped addressed envelope for literature and full details. Overseas enthusiasts note we despatch to all parts of the world—local stamp OK for literature. "GLOBE-KING" (Regd.) precision standard products tried and trusted by Amateurs everywhere.

JOHNSONS (Radio)
St. Martins Gate, Worcester

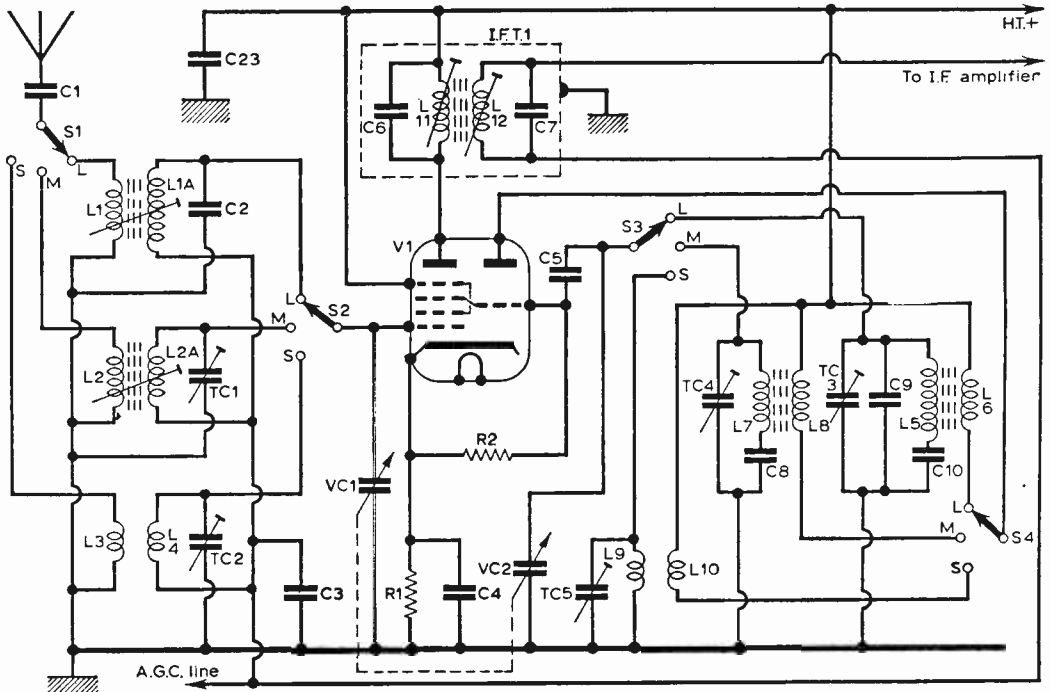


Fig. 3: The circuit of the frequency changer section of a receiver. The triode section of V1 is the local oscillator.

Once the appropriate tuning points of the two sets have been established the monitor set can be tuned near to its original setting to a clear place on the band and the noisy set retuned correspondingly until the oscillator signal coincides with the tuned frequency.

That the oscillator signal is being picked up will be revealed by the background on the monitor set going quiet, for there will be no whistle this time if there is no carrier for the oscillator signal to beat with.

Oscillator Coupling

Just how obvious it will be that the monitor set is, in fact, responding to the oscillator signal will depend upon how near the monitor set is placed to the noisy set. If the monitor set is a small transistor portable with a ferrite rod aerial it can be orientated so that the ferrite rod end is close to the oscillator side of the noisy set.

The closer the coupling, the better for this test. When the oscillator signal has been established on the monitor set, the tuning should be critically adjusted and the volume control turned up high.

An ear held close to the speaker of the monitor set will then detect any slight noise on the oscillator signal. If the oscillator is responsible for the noise, the oscillator signal as being monitored will carry a noise pattern similar to that produced by the faulty set.

Of course, at this time the volume control of

the noisy set will be turned right down to prevent the actual noise masking the possible noise on the oscillator signal. If there is no trace of noise on the monitored oscillator signal, yet the faulty set continues to produce a noise output, one can rest assured that the oscillator is not responsible.

Now, the simple tests that we have so far performed will tell whether the noise is external or in the set and they will also tell which of the three sections of the set (Fig. 2) is responsible for the noise. Once we have located the noisy section we are compelled to investigate further in greater detail.

Valve Noise

Before doing too much detailed work, however, it is as well to find out whether the valves themselves have some bearing on the noise. Valves can, indeed, be real noise producers after they have seen years of service.

At this stage in the exercise we should remove the back cover of the set without switching the set off if possible, for switching off and then on again may stop the noise for a while if it happens to be the intermittent variety.

With the back off, we should gently tap the valve (or valves) in the sections that we now know to be responsible. We should do that with the volume control at maximum and the set adjusted to give maximum noise output (i.e., we may have found that the noise is greatest on a particular waveband or at a certain tuning point).

If the noise ceases temporarily after a valve has been tapped loose electrodes are probably to blame. A replacement would almost certainly cure the trouble.

Old style valves with metallising on the outside sometimes lose electrical connection from their bases and they then become a potential noise source. This trouble can be remedied by winding several turns of 20 s.w.g. tinned copper wire between the top of the base and the metallised envelope, twisting the wire to lock it tightly in place and then covering the winding with several tight layers of insulating tape.

Another noise possibility around the valves is poor electrical connections between their pins and the sockets of the valve holders. This can be established by gently rocking the valves in their holders with the set switched on and the volume control turned up.

Crackling and frying noises will occur as a valve which is in poor connection is rocked. A cure may be effected either by cleaning the valve pins or closing the sockets for a tighter fit (or both). In bad cases a replacement valve holder may be necessary.

Bad Soldering

Noise in transistor models is rarely caused by noise in transistors. Nevertheless, a gentle tap on the side of those in a noisy section should prove this convincingly. Badly soldered connections on the transistor wires at the printed circuit are more likely.

Assuming that the valves are cleared of blame, it becomes necessary to delve into the noisy circuit section in greater detail. In the case of a noisy oscillator the components most likely responsible are those handling the oscillator signal. A simple frequency changer section is shown in Fig. 3.

Here the triode section of V1 is the local oscillator valve and vulnerable components are R3 and C5, particularly the latter. It pays to replace this straight off if oscillator noise is proved.

Some circuits have a resistor from the h.t. line to the top of the oscillator coils, the bottom of which go to the valve anode. This resistor is another noise source, as also is the associated capacitor.

If noise is troublesome only on one waveband, the corresponding oscillator coil is a very strong possibility. The insulation often weakens causing noise signals to be modulated on the oscillator signal. In this case a check should also be made of the capacitors associated with the noisy waveband. These would be T4 and C8 on the m.w. band and T3, C9 and C10 on the l.w. band of the circuit in Fig. 3.

Check Wave-change Switch

It should also be remembered that worn wave-change switch sections can also set up noise signals. However, this source is generally revealed by operating the wave-change switch or applying pressure to one side of the control knob when, if the switch is faulty, the noises will stop or start. Switch cleaner fluid injected on to the contacts

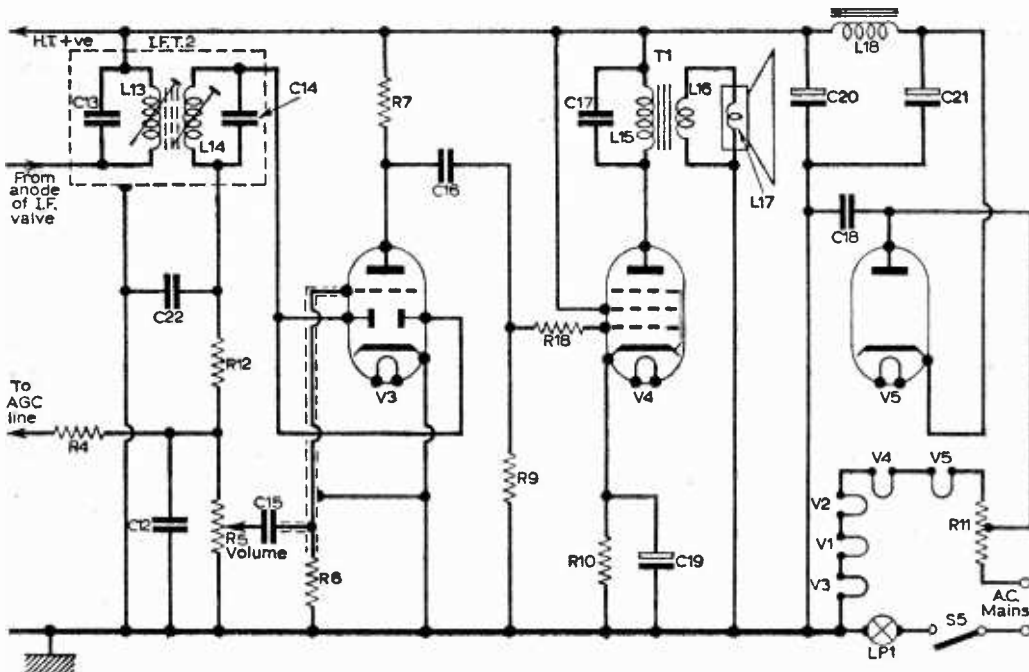


Fig. 4: Circuit of the a.f. sections of a receiver. Possible causes of noises originating here are examined in the text.

Kedoco ELECTRONICS

USERS ACCLAIM—KEDOCO PRODUCTS

MINICLASSIC SS3/9

69/- 3 watts output, 6 silicon planar epitaxial transistors, 2 diodes and one zener. All mounted on precision printed circuit board. Hi-Fi at its cheapest—16 c/s to 30 kc/s flat response. Many other uses. Requires 18v. power supply. Will operate directly from crystal pick-up. Used with tape Pre-amp it makes a complete Tape Amplifier. Also tone controlled Hi-Fi Pre-amp available at 39/-.

TAPE PRE-AMP

All silicon transistor. Zero hum. High gain fully compensated to give flat response output. Suitable for medium impedance heads such as Collaro, Truvox, B.S.R., etc.

29/6 COMPLETE

ALSO Tape Oscillator 49/6, and Record Amplifier at 35/-.

DO THIS SUM: SS3/9+Tape Pre-amp+Preamp+Tape Oscillator+Record Amplifier—Complete Hi-Fi System and wonderful value at only £11.2.0.

See "Practical Electronics" for other exciting **KEDOCO PRODUCTS** BEVERSTONE WORKS, TETBURY, Gloucester

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!


SETS 1R5, 1R5, 1T4, 3R4, 3V4, DAF91, DF91, DK91, DL92, DL94, Set of 4 for 15/-, DAF96, DF96, DK96, DL96, 4 for 24/6.

1A7GT	7/6	7B7	7/9	8SA2	3/9	8CC8	4/-	FW4	5/0	6/3	TH21C	9/6
1B3GT	7/9	7C5	7/9	8003	12/6	8CC84	6/3	8Z33	12/6	TH233	6/6	
1N3GT	7/9	7H7	5/9	AZ31	3/3	8CC85	5/6	GZ37	8/9	U23	8/6	
1L5	4/9	7H7	4/9	B36	4/6	8CCF80	7/6	KT61	6/9	U26	8/9	
1R4	4/9	7Y4	5/-	CL38	9/6	8CCF82	6/-	MU14	4/-	U47	8/6	
18A	3/9	9BW6	6/6	CY1	12/6	8CCF86	10/9	N18	5/6	U52	4/6	
1T4	1/9	10C2	11/6	DA32	7/3	8CC85	6/-	PC97	5/6	U54	8/9	
3A5	5/6	10F1	3/9	DAF91	3/9	8CC42	8/3	PC84	6/9	U78	3/6	
3Q4	3/6	10LD12	7/6	DAF96	6/-	8CC81	6/-	PCC89	9/6	U191	9/9	
384	4/9	12AT7	3/9	DCC90	6/9	8CC180	6/3	PC189	9/-	U301	10/9	
3V4	5/6	12AU6	4/9	DF33	7/9	8CC182	6/6	PCF80	6/6	U801	15/-	
5U4G	4/6	12AU7	4/9	DF91	1/9	8CC186	9/6	PCF82	6/-	UABC80	5/9	
6Y3GT	4/11	12AX7	4/9	DF96	6/-	8CC99	3/9	PCF84	8/-	UAF42	7/9	
8Z4G/GT	6/9	12K8GT	3/6	DH76	3/6	8CC41	6/9	PCF86	8/3	UBC41	6/6	
8J30L2	8/9	12K8GT	3/6	DH77	4/-	8CC80	4/9	PCF805	8/-	UBC81	6/3	
8AL5	2/-	12Q7GT	3/6	DH81	12/6	8CC85	5/-	PC182	6/3	UCF80	8/-	
8AM6	2/9	13B6GG	6/9	DK32	7/9	8CC86	6/9	PC183	8/3	UCF89	5/9	
8AT5	4/9	20L1	9/6	DK31	4/3	8CCF89	4/3	PCL84	8/3	UC884	8/-	
8AT6	4/-	20P8	10/9	DK92	8/-	8CCF91	2/9	PCL85	8/3	UC885	6/6	
8HA5	4/6	20P4	18/6	DK96	6/6	8CCF92	2/-	PC186	8/6	UCF80	8/3	
8BE6	4/6	20P5	11/6	DL33	6/9	8CCF97	7/6	PCN A4	6/6	UCB42	7/6	
8BH6	5/-	25L6GT	4/3	DL35	3/-	8CCF183	6/9	PEN383	9/6	UC181	6/6	
8B7G	5/6	25GT11	6/6	DL92	7/3	8CC99	6/6	PEN395	5/-	UC182	7/3	
8BW6	7/9	25Z4G	6/3	DL94	5/6	8CC138	11/6	PFL240	17/6	UC183	9/3	
6CH6	6/6	30C18	8/-	DL96	6/-	8CC141	7/3	PL36	8/9	UF41	6/9	
6FL3	3/6	30F5	8/6	DY86	6/9	8CC184	4/6	PL81	6/9	UF42	4/6	
6FL4	9/-	30FL1	9/6	DY87	6/9	8CC190	4/9	PL82	5/8	UF80	6/-	
6F23	9/-	30L15	10/3	EABC90	6/-	8CC183	5/-	PL83	6/-	UF99	5/9	
6K7G	1/8	30L17	12/-	EAF42	7/6	8CCM34	9/6	PL84	6/3	UL41	7/3	
6K8G	4/3	30P4	13/6	EB41	4/-	8CCM80	5/9	PL500	14/-	UL44	15/-	
6K8GT	7/6	30P12	7/6	EB91	2/-	8CCM81	7/3	PL801	7/6	UL46	8/6	
6P28	9/6	30P19	13/6	EBC33	6/-	8CCM84	5/9	PX25	7/9	UL84	5/9	
6P23	5/9	30P11	9/6	EBC41	6/6	8CCM87	6/6	PY32	8/9	UY41	4/9	
6SL7GT	4/9	30P113	10/9	EBF80	6/-	8CCY51	6/3	PY33	8/9	UY85	4/9	
6V6G	3/6	30PL14	11/-	EBF83	7/6	8CCY56	6/-	PY80	5/3	VP48	11/-	
6V6GT	5/6	35L6GT	6/3	EPB89	5/9	8CCZ40	6/3	PY81	5/3	W76	3/6	
8X4	3/6	35W4	4/6	8CC30	6/9	8CCZ41	6/6	PY82	5/-	W77	2/-	
6B35GT	6/3	35Z4GT	4/6	8CC31	3/9	8CCZ60	4/-	PY83	5/9	X79	24/6	
7B6	10/6	63KU	8/6	8CC82	4/9	8CCZ81	4/6	PY800	6/6	Z77	2/9	

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL LONDON N.16. STA 4587 & 85 TORQUAY GARDENS REDBRIDGE, ILFORD ESSEX. CRE 7441 Postage on 1 valve 9d. extra. On 2 valves or more postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

HIGH QUALITY

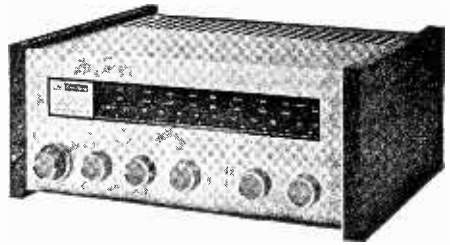

LOWER COST

Combine an Armstrong Tuner and Amplifier and you have all the advantages of separate units, plus compactness, easier installation, and equivalent performance at a lower price.

Stereo model 127, above, derived from the more expensive 127, has an identical AM-FM tuner section, with an amplifier section designed for those whose power requirements are more modest.

It has a more modest price too, as does the mono version model 127M.

Each Armstrong Tuner-Amplifier is ideal as the basis of a high fidelity system for radio and record reproduction, tape recording, and playback, and each unit may be built into your own cabinet or used in our optional case, of teak and vinyl hide, as shown.

For full details and technical specifications of all models plus list of over 300 stockists, post coupon or write mentioning 2PW66.

model 127 STEREO TUNER AMPLIFIER £37.10.0

model 127M MONO TUNER AMPLIFIER £26.10.0

optional case £3.10.0



ARMSTRONG AUDIO LTD-WARLTERS ROAD-N.7

Telephone: NORth 3213

Name _____
 Address _____

 2PW66

often assists in clearing noise troubles here.

Noises in the signal stages are often caused by a resistor in one of the electrode feed circuits arriving at the end of its useful life. If the noise is really bad (that is, loud) a rise and fall (flicker) in h.t. voltage at the valve electrode suffering from a worn feed resistor can often be detected on a voltmeter connected between the electrode of the valve concerned and chassis.

For example, if a screen feed resistor is causing the trouble, the pointer of the meter measuring the voltage may be seen flickering about its nominal voltage reading. This is an absolute indication that the feed circuit needs careful examination.

Note, however, that the flicker may be only slight but will be taking place to the pattern of the noise from the speaker.

Similarly, i.f. transformers or the capacitors across their winding, such as L11 and L12 and the capacitors C6 and C7 across them in Fig. 3, may be likewise afflicted. A flicker of voltage at the anode is generally more discernible than that at a screen grid where a feed resistor, as distinct from a winding on a transformer, is concerned.

A fixed tuning capacitor across an i.f. transformer winding can make a lot of noise without showing a flicker in voltage, however. If in doubt, it is best to try a replacement part. Note also that poor insulation in the winding of an i.f. transformer can cause quite a bit of noise without affecting the anode voltage.

A.F. Section Noise

Moving now to the a.f. section we find that potential noise sources are similar to those in the signal stages. Fig. 4 shows the a.f. stages of a typical radio set of the kind that the experimenter may be called upon to service.

Here the signal from the detector is fed across the volume control while the audio is tapped off from the slider to the grid of the triode in V3. The strapped diodes act as the detector and these work in conjunction with the secondary of the second i.f. transformer IFT2.

A noise source is the anode load resistor R7. C16 the coupler can also produce noise if leaky, but this generally adds distortion due to the control grid of the pentode V4 going a little positive

owing to the leak in the capacitor.

Noise is very bad if the primary of the speaker transformer OP1 (L15) goes intermittent of poor insulation. In most cases the cause can be proved by connecting a voltmeter between V4 anode and chassis and observing the flicker in reading in sympathy with the noise from the speaker.

Whether the noise originates from the triode a.f. amplifier or from the output stage can be proven by shorting the control grid of the output valve to chassis when the noise is occurring. If the noise ceases with the grid shorted it is developing in V3 stage, but if it continues the output stage of V4 is responsible.

The power supply section (V5 and associated circuits in Fig. 4) rarely goes noisy, but if it does it usually shows by a bad flicker of the voltage when measured on the h.t. line. The choke L18 in the circuit could go bad, but if this leaks to chassis, things could start getting hot and a fire-work display takes place inside the rectifier V5.

Printed-circuit Noise

Noise can be injected via the a.g.c. line, but this can be eliminated early in the noise tracing exercises simply by shorting it to chassis. Modern receivers are somewhat more noise prone than earlier models due to the new techniques in construction. Printed circuits can cause noise should the insulation between printed conductors go low due to excessive heat and/or dust accumulations.

Heat is sometimes transferred to the printed circuit board from a hot output valve, for example, via the special type of printed circuit valve holder.

The plastic board suffers from local scorching which with some base materials tends to reduce the insulation resistance. Under certain conditions a very high resistance path, of varying value, may develop between, say, the h.t. line and a control grid circuit and this sets up conditions for very elusive noise troubles.

Transistor circuits suffer less from the type of noises detailed in this article, but if they lack input signal in the early stages, due to misalignment, broken ferrite rod aerial and so forth, there can be trouble with a disconcerting hiss on a tuned station, especially if the station is not a very local one. ■

MODIFYING MAINS TRANSFORMERS

—continued from page 878

In general we have:

$$\frac{\text{No. of turns on existing winding}}{\text{existing winding}} \times \frac{(\text{Voltage of existing winding})}{(\text{Voltage of replacement winding})}$$

this holds if the new voltage is greater than the old. If the new voltage is less than the old, then we invert the term in brackets, placing the voltage of the replacement winding in top of the voltage of the existing winding.

Make sure that there is room for the winding you propose to use see Fig. 2, and that you take the wire ends and tappings out at a suitable point. Each layer of turns must be covered with stiff paper before the next layer is wound on. The

beginning and end of the coil should have a short length of plastic covered flex soldered to it and should then be anchored as shown in Fig. 2. In the case of tappings, when the required number of turns is reached scrape the enamel covering from the wire and solder on the length of plastic covered flex, then proceed with the winding after ensuring that the bare parts are insulated from the other wires with paper.

If you require the new windings to have the same wattage rating as the old you should use the same diameter wire. If you use a smaller diameter wire in order to gain more space the heat generation varies as the square of the diameter of the wire in order to gain more space the heat generation the wire it must carry only a quarter of the current carried by the thicker wire if the heat generation is to remain the same. ■



No. 4 **UNIVERSITY OF SHEFFIELD AMATEUR RADIO SOCIETY**

THE Society, which is affiliated to the R.S.G.B. was formed in November 1964. Since then the main activity has been to attempt to get the Society established, with some measure of success obtained.

Members are drawn from all sections of the University, academic and technical staff playing their part as well as the students. There are also a limited number of associate members who are not connected with the University in any other respect.

Members' interests range through the whole field of radio from amateur transmitting through short wave listening to high fidelity and tape recording. Attempts are made to cater for all these interests.

Lack of QTH

Activities have been limited during the life of the Society so far due to a lack of a permanent QTH. There have been offers but usually high authority has not been as co-operative as hoped.

There have been a few lectures arranged at fairly short notice but most activities have been undertaken by members acting as groups of individuals. However, as reported previously in P.W. the

Society arranged a December sitting of the R.A.E., at which six members passed.

Morse practices are held regularly, but so far only one member has taken the G.P.O. test—and failed.

Undoubtedly the most successful meeting to date was a demonstration of "High Quality Sound Reproduction" given by Messrs. W.B., makers of the Stentorian loudspeakers.


An attempt was made to participate in the Oscar III project, but this met with failure due to the hastily assembled equipment being inadequate. However, from the lessons learned from this attempt, it is hoped that future projects will be more successful.

10 Licensed Members

There are ten licensed amateurs in the Society,



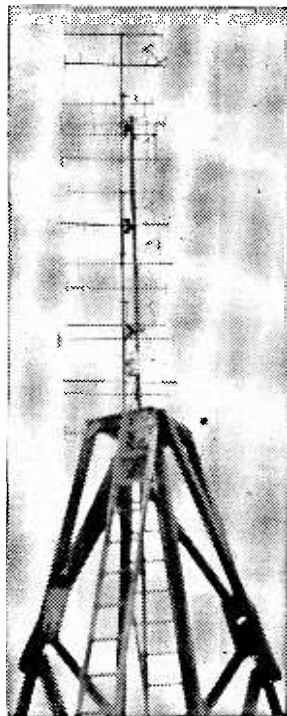Left: Members erecting the aerial array at the R.S.G.B. v.h.f. National Field Day.



Right: Photograph of the fully completed 128-element array on which five stations were worked.

and, not surprisingly, where technical qualifications prevail, sound "B" licences predominate. The following are the members' calls:—

G3MZY, G3RKL, G3TGN, G8AAC, G8AAZ (also G6RAX/T), G8ADZ, G8AET, G8AGH, G8AGN and G8AGQ.

Because of this predominance of "G8's" the emphasis is on v.h.f. and u.h.f. activities, and, in fact, it was two of these "G8's" who started off the Sheffield area v.h.f./u.h.f. activity nights on Wednesdays.

R.S.G.B. v.h.f. Field Day

The Society took part in the R.S.G.B. v.h.f. National Field Day on September 4th and 5th last year. Elaborate preparations were made for the 70cms band including a 10W transmitter and a 128 element array. Five stations were worked (one less than in May last year—when the aerial was a 12-element array).

However, h.f. activity is not ignored. G3TGN has his station in the Physics department, using a Heathkit DX-40U as his Tx and a CR-100 for his Rx. Unfortunately, access is limited so this cannot be used as a Club transmitter. Most QSO's are on 80m.

Several members are engaged on individual construction projects to promote group activities. The emphasis, at the moment, is on equipment for the "G8's" "Top Band". A 432Mc/s Tx using nine transistors has been built and operated. A valve

Tx with less than 1W to the final has been heard 30 miles away. A number of surplus klystron units became available in Sheffield recently and some members are preparing these for use on the 3400—3475Mc/s band. There is also some work going on with a 3cms transceiver.

Future Development

Being a recently formed Society, the emphasis is on future development rather than past glories. The acquisition of a QTH is the major objective, and many plans must be shelved until one is obtained. Once a QTH is obtained, priority will be given to setting up a station. For this, the Society hopes to use the call sign G3UOS when it becomes available.

The aim of the Society is to provide the enthusiast with help in obtaining his licence. It is possible for the beginner, joining at the start of the Society's year, to be on the air using his own call sign a few months later.

The Society maintains cordial relations with other Societies and Clubs in the area, and a number of joint meetings and visits have been arranged for this year.

To sum up, this is a new Society, it has little past history the emphasis must be on the future, and although ambitious projects are on the cards, we must first establish ourselves as a meeting point for people with an interest in, and a love for all aspects of Amateur Radio. ■

METROPOLITAN TAPE RECORDER

—continued from page 871

position. Clamp the magnet down firmly when the best position is found. This position will not necessarily be optimum for other brands of tape.

Next set the standing current on the output transistors. Remove the (black) supply lead from the output transformer and connect in a milliammeter or a multimeter reading on a 0-100mA scale. If the recorder is to be used mainly on batteries, the standing current with no signal in should be as low as the potentiometer VR3 allows, but for mains use a useful figure is 50mA.

Bias and drive must now be set. The bias potentiometer VR4 should initially be set at mid-range, as should also the drive indicator potentiometer VR5. Make a trial recording, preferably of the 400 cycle note which often accompanies TV test cards, or precedes radio broadcasts, or of a 400 c/s note from a signal generator. Noting the positions of the recordings on the counter, make several recordings at various positions of the drive potentiometer VR5 noting the "o'clock" position of the slot each time. Make sure that the volume control for each recording is set so that the indicator column just touches the dot. Determine the best recording from the point of view of distortion and volume and return the potentiometer to that setting. Now repeat this procedure with the bias potentiometer VR4 to find its optimum position.

Now check the setting of the bias rejector. Using a germanium diode in series with a 1mA meter at the "live" end of the head drive transfor-

mer, set the core of L1 for minimum reading. (Resistance in series with the meter may be needed if the setting is badly out.) Incidentally, an open circuit bias coil on this recorder causes heavy treble boosting and should be suspected if all recording sounds too shrill. If there is considerable noise on replay with no tape and the volume control full up, the first transistor is noisy, and should be replaced by a low-noise type such as the AC107. Frequently in these recorders, the second transistor is the culprit for noise; it pays in this case to put the first transistor in place of the second and use a low-noise type in the first position.

With the modifications described, the Metropolitan makes a transistorised tape recorder of outstanding versatility. The output is quite adequate for use in a small hall, and the separate amplifier facility is very useful, especially for public address work. Spares, however, are in short supply, and the following references may be useful.

All parts (Trade only—order through a dealer).

Tape Recorder Maintenance Ltd.
323 Kennington Road,
London, S.E.11.

Motors, Idlers, Pinch Wheels, Heads.

Manor Supplies,
64 Golder Manor Drive,
London, N.W.11.

Other Types of Motor.

H Franks,
58-60 New Oxford Street,
London, W.1. ■

YOU ARE ALWAYS AHEAD WITH A SINCLAIR DESIGN

The world's smallest radio

No transistor set has ever yet compared in its class with the Micro-6 for size, power, performance and design. Everything except the lightweight ear piece is contained within the smart minute white, gold and black case which weighs under one ounce complete. Quality of reproduction is so outstandingly good that you will derive enormous pleasure from this fantastic set. Order your Micro-6 now. See why it cannot be too highly recommended to build and to use. You can easily have it working in an evening!



- $1\frac{1}{5}'' \times 1\frac{3}{10}'' \times \frac{1}{2}''$
- PLAYS ANYWHERE
- COMPLETELY SELF-CONTAINED
- EASY TO BUILD




AMAZING CIRCUITRY

The six-stage circuit uses three special transistors to provide two stages of R.F. amplification with double diode detector and high gain 3-stage A.F. amplifier. A.G.C. counteracts fading from distant stations; bandspread brings in Luxembourg like a local station. Plugging in earpiece switches set ON. Tunes over medium waveband by vernier-type dial. Two self-contained batteries give about 70 hours working life.

Complete kit of parts inc. special earpiece and instructions

59/6

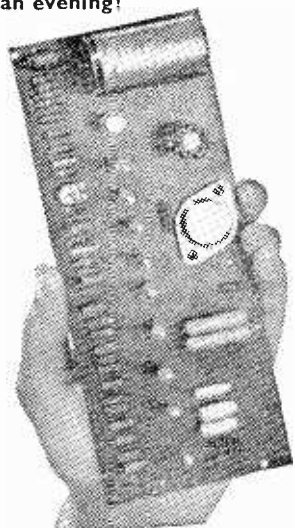MALLORY MERCURY CELL TYPE ZM.312 (2 required) each 1/11d.
Pack of six 10/6d.



Weights
 $4\frac{1}{2}$ oz.

MICRO FM and Z.12
See pages following

The world's most advanced audio amplifier

Size $8\frac{1}{4}'' \times 3\frac{1}{4}'' \times 1''$ Output 20 watts

The only audio amplifier in the world to use Pulse Width Modulation which, with circuitry developed specially by Sinclair gives power and quality years ahead of anything in its class. You can feed any signal source into the X-20—modern high quality pick-up, radio tuner, electric guitar, car radio, microphone, tape, etc. The X-20 manual shows a number of circuits by which inputs can be matched to the integrated pre-amplifier of the X-20 both in mono and stereo. When you have built this 12-transistor amplifier you use it in the same way as any other top quality hi-fi unit except that it is smaller, costs less and behaves perfectly.



- 20 WATTS R.M.S. OUTPUT INTO 7.5 ohms
- 20-20,000 cps ± 1 dB
- Constant square wave amplitude
- 95% conversion efficiency at output
- Input sensitivity—1mV into 5K ohms
- Power requirements—36V d.c. at 700mA

COMPLETE KIT OF PARTS COSTS

£7.19.6

Built and tested **£9.19.6**
Mains power **£4.19.6**
Unit

● FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS

SINCLAIR

SINCLAIR RADIONICS LTD., COMBERTON,
CAMBRIDGE Telephone: COMBERTON 682

A BRILLIANT NEW TUNER

The world's first pocket-size FM Tuner/Receiver



The SINCLAIR MICRO FM is a high quality FM tuner designed for use with hi-fi amplifier or tape recorder and independently as a self-contained pocket FM receiver for personal listening. Barely half the size of a packet of 20 cigarettes, the Micro FM is a fully-fledged 7 transistor 2 diode superhet circuit with unique and original design features to ensure fantastically good standards of performance. Pulse counting detection ensures better linearity than conventional detection methods, and therefore better audio quality. Powerful A.F.C. which locks on to the station tuned in, together with unusually good sensitivity make tuning easy and the set's own telescopic aerial suffices almost everywhere. In styling, this is the most elegant, most professional looking design in miniaturised equipment ever made available to constructors, and is one you will be very proud to possess. YET WITH ALL THESE WONDERFUL FEATURES, THE SINCLAIR MICRO F.M. COSTS POUNDS LESS AND MEANS THAT ANYONE CAN AFFORD AND ENJOY THE ADVANTAGES OF FM RADIO NOW.

SINCLAIR MICRO FM

7 TRANSISTOR SUPERHET FM TUNER/RECEIVER

- ★ SIZE 2½" x 1½" x ¾"
- ★ TUNES FROM 88-108 Mc/s.
- ★ A.F.C. FOR EASY TUNING
- ★ NO ALIGNMENT NEEDED

- ★ PULSE COUNTING DETECTION
- ★ EXCEPTIONALLY ELEGANT APPEARANCE

Use it as —

AN F.M. TUNER FOR YOUR TAPE RECORDER.



AS A SELF-CONTAINED POCKET F.M. RECEIVER.

(The only one in the World!)



BRIEF TECHNICAL DESCRIPTION

THE SINCLAIR MICRO FM is a seven transistor two diode FM superhet. The low I.F. dispenses with the need for alignment. A three stage I.F. amplifier limits the signal to produce a square-wave of constant voltage which is fed into the pulse counting discriminator. This converts the square wave formation into uniform pulses, the average output from which is directly proportional to the signal frequency, so that the original modulation is reproduced exactly. After equalisation, the signal is fed to the audio output socket for use as a tuner and also to the receiver's own audio amplifying stage for use as an independent self-contained receiver. A.F.C. "locks" on each station automatically. THE SINCLAIR MICRO FM is completely self-contained within a neat black plastic case faced by an elegantly designed front panel of brushed and polished aluminium with spun aluminium tuning dial to match. The tuning scale is marked in Mc/s. When built the Micro FM performs as well as any other good tuner.

THE COMPLETE KIT OF PARTS for building the SINCLAIR MICRO FM including extending aerial, 7 transistors, case, tuning dial, aluminium front panel, lightweight earpiece, plugs and sockets and instructions costs only

- ★ Operates from 9v. self-contained standard battery
- ★ Consumption 5mA
- ★ Audio response—10-20,000 ± 1dB
- ★ A GUARANTEED SINCLAIR DESIGN

£5.19.6

Full service facilities available to all Sinclair customers

SINCLAIR RADIONICS LTD.
COMBERTON, CAMBRIDGE


Telephone: COMBERTON 682

sinclair

A BRILLIANT NEW AMPLIFIER



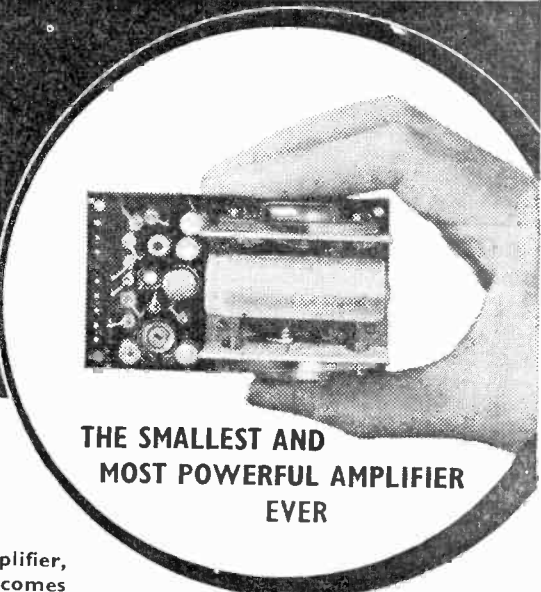**SINCLAIR
Z.12** COMBINED
AMPLIFIER
AND
PRE-AMP



THE SMALLEST AND
MOST POWERFUL AMPLIFIER
EVER

Fantastic power and quality

The Sinclair Z.12 is a universally flexible amplifier, exceptionally powerful, fantastically small. It comes to you ready built, and is very easy to instal and use. The Z.12 can be incorporated into any high quality hi-fi system. Its small size and high efficiency make it equally useful for a guitar, for car radio, P.A. system or any other application where high quality is the first requirement. The Z.12 incorporates its own pre-amplifier to which you add the tone and volume control system of your choice as shown in the Z.12 manual supplied with the amplifier. The size, the performance, and the price of the Sinclair Z.12 all favour the constructor who wants the best in modern transistor equipment; in fact, the Z.12 is unbeatable in every way and is today's finest buy in top grade high fidelity.

USE IT FOR
Hi-fi
Radio
Car Radio
Guitar, etc.

GUARANTEE
Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full and at once without question. Please quote PW.166 should you prefer to write your order instead of cutting out this coupon.

- TECHNICAL DETAILS**
High fidelity amplifier with pre-amp and ultra linear class B output. Eight special HF transistors are used in original circuitry to achieve laboratory standards of performance. Generous negative feedback ensures extra good quality.
- **FREQUENCY RESPONSE**—15 to 50,000 c/s ± 1dB
 - **OUTPUT**—12 watts RMS continuous sine wave (24 watts peak); 15 watts RMS music power (30 watts) peak
 - **OUTPUT IMPEDANCE**—suitable for 3 7.5 and 15 ohm speakers. Two 3 ohm speakers may be used in parallel if required.
 - **INPUT**—2mV into 2K ohms
 - **SIGNAL to NOISE RATIO**—better than 60dB
 - **QUIESCENT CURRENT CONSUMPTION**—10mA
 - **POWER REQUIREMENT**—6 to 20V
 - **IDEAL** for operating from a 9 or 12V battery.

- 3" × 1 3/4" × 3/4"
- Weighs 3 ozs.
- 12 watts R.M.S.

89%

Supplied ready built, tested and guaranteed, complete with Z.12 Manual.

SINCLAIR PX-1 Power Supply Unit £2.14.0

GUARANTEE ORDER FORM
To: SINCLAIR RADIONICS LTD.
COMBERTON, CAMBRIDGE

Please send me _____

for which I enclose Cash/Cheque/Money Order
value £. _____

NAME _____
ADDRESS _____

PW266

SEND COUPON WITHOUT DELAY →

TAPE RECORDERS, TAPES, ETC.

TAPE TO DISC — New High-level Cutters, 45 r.p.m., 2 1/4". S.A.E. leaflet. **DEROY**, 62 East Bank Lane, Lancaster.

SOUND RECORDINGS

A UNIQUE TAPE BUY! Top brand 7in., 2,400ft., 25/-; 5 1/2in., 1,200ft., 15/-; P. & P. 1 at 2/-, 2 at 2/9, 3-6 at 3/6. Bargains in all sizes. S.a.e. for list **E. C. KLINGSLEY & Co Ltd.**, 93 Tottenham Court Road, London, W.1. EUSTON 6500.

RECEIVERS & COMPONENTS

RESISTORS, LAB. MIXED: 4/- per 100, postage 6d., 500 or more post free. **C.W.O. Mail Order Only.** — 203 Long Lane, Finobley, N.1.

A.I. POST FREE BARGAINS

Stock clearance of reclaimed values

B36	2/-	PC182	4/-	UF42	1/9	10C1	7/-
EB41	1/9	PC183	3/3	UCH42	5/-	10C2	3/9
EB91	8d.	PEN46	1/9	UL46	5/8	10P13	3/9
EBF90	3/8	PL33	2/8	Z63	3/8	10P14	3/9
ECC82	2/8	PL23	2/-	Z66	3/8	20D1	1/9
ECF80	4/-	PL43	2/-	6F1	1/-	20P3	4/3
ECL80	1/8	PY31	1/8	6F13	2/9	20L1	3/9
EP42	2/9	PY32	2/9	6F14	2/9	20P1	2/6
EP80	8d.	PY80	1/8	6F15	2/9	20P3	3/-
EP85	4/8	PY81	2/9	6K26	3/8	30P1	3/9
EL42	4/8	PY82	1/8	6L1	3/9	30P5	3/6
KT30C	2/8	PZ30	1/9	6L18	3/9	30R1	3/8
KT36	3/8	T41	4/8	6L19	12/6	30P1	3/8
N7	1/6	U31	2/8	6LD20	4/3	30P12	3/9
N82	3/-	U31	3/9	6P25	2/9	185BT	7/6
N83	11/-	U32	3/9	6P28	4/8	KTW63	2/-
PC78	2/-	UB41	3/6	52018	9/9	KTZ63	3/6

EP80 4/- dom. ECL80 18/- dom. PCF80 18/- dom.
EB91 18/- dom. FY83 18/- dom. PL83 18/- dom.

A.I. RADIO COMPONENTS

14 The Borough, Canterbury, Kent

"HEATHKITs" can now be seen in London and purchased on easy terms. Free brochure. **DIREBOT TV REPLACEMENTS LTD.** Dept. FW/7, 124 Hamilton Road, West Norwood, S.E.27. **CIPAY Hill 6164.**




VALVE TESTER 1-177
Latest release of this wonderfully made American Valve Tester, using a well scaled meter Reading (Red) Replace (Green) Good, also 0-8000, 0-8000, 0-15000 microhms for the measurement of Mutual Conductance of Valves, Noise Test, Gas Test, a Top cap lead for the use of Testing Transmitter Valves with anode Top Caps, Test for Cathode Ray Indicator Valves LT Voltages 1.1, 1.5, 2, 2.5, 3, 4.3, 6.3, 7.5, 10, 12.6, 26, 35, 50, 75, 117, volts in small case 5 1/4" x 8 1/4" with carrying handle, Circuit, Instruction Book and Valve data. In very good order **41L10.0** post 7/6. This unit has a Supply Voltage of 110v. A.C. Therefore an Auto Transformer is Required. We can supply at 14/-.
JOHN'S RADIO
682 Co-op, Whitehall Road, Drighlington, Bradford

RATES: 7/3 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton Street, London W.C.2.

RECEIVERS & COMPONENTS


DIRECT TV REPLACEMENTS LTD., largest stockists of TV Components in the U.K. Line Output Transformers, Frame Output Transformer, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. for quotes. Day and Night Telephone **GIPSY Hill 6166**, 126 Hamilton Road, West Norwood, S.E.27.

TRANSMITTER RECEIVER

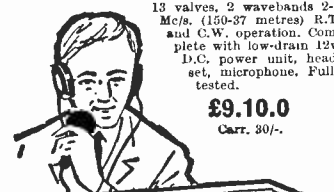

13 valves, 2 wavebands 2-8 Mc/s. (150-37 metres) R.T. and C.W. operation. Complete with low-current 12V D.C. power unit, headset, microphone. Fully tested.
£9.10.0
Carr. 30/-

MARCONI CANADIAN RECEIVER No. 52

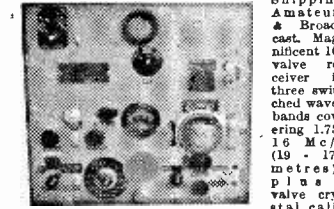

Shipping Amateur, & Broad-cast. Complete with 12V D.C. power unit, nineteen 10-valve receiver in three switched wavebands covering 1.75-16 Mc/s (19 - 170 metres), plus a 3 valve crystal calibrator employing dual crystal to provide marker check at 10-100-1000 kc/s. One RF and two IF stages. Other refinements: valve HT, and signal check meter. Internal 3in. speaker and two H/P Phone outputs with switched control. RF-AP Gain, Noise Limiter, Filter, BFO, Heterodyne pitch control. Wide and Narrow Bandwidth Man or AVC on CW & RT. Fast and slow tuning with lock. Additional OSC Tuning (plus & minus). Power requirements HT 160v, 60mA; LT 12v. 1 1/2 amps. SIZE 15 x 14 x 12in. Fully tested and working ONLY £9.10.8. Carr. 15/6 or complete with Power supply unit suitable for 115/230v. AC mains £12.10.8. Carr. 20/-

No. 52 GROUND-STATION comprising Receiver, Transmitter and 12v. D.C. Power Unit. £27.10.0. Carr. £2.10.0. (Mainland only).

TELESCOPIIC AERIAL MASTS. Tubular steel copperplated, spray finish, ring cam locking on each section provides for full or any height required. Suitable all fixings and base locations. Bottom section 1 1/2in. diameter, 20ft. (4 section) Closed 5ft. 9in. Weight 16lb. 55/- Carr. 5/- 34ft. (6 section) Closed 8ft 6in. Weight 20lb. 78/- Carr. 5/- Further height by adding 3-4ft. Whip sections 18/6 Carr. 4/- Special price for quantities.

ROTARY TRANSFORMER. 12v. D.C. Input, 250v. D.C. output at 125 mA. Size 3 1/2 x 6 1/2in. Brand new 17/6. P. & 5/-.

R.F. ANTENNA TUNER (A.T.U.) Calibrated scale, ideal 160/80/40 metres. Limited number only. Brand new with instructions, 17/6. P. & P. 7/6. Complete list of other bargains 1/- S.A.E. all enquiries.

A. J. THOMPSON (Dept P.W.)
"ELING LODGE"
ODDIOOTE, HITCHIN, HERTS.
Phone: ODDIOOTE 2948

RECEIVERS & COMPONENTS

(continued)

TV CHASSIS, 110 with v.h.f., store soldered. £5 including carriage. **NEW 19in.** TUBES with small spot burns £4 including carriage **C.W.O. TRURO VALVE SUPPLY LTD.**, Carclew St., Truro, Cornwall.

TRANSISTORS, UNMARKED, UNTESTED, 40 for 10/-, p. and p. 1/-, 4 packets post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc. (5,000 items), free. **K. R. WHISTON** (Dept. PRW), New Mills, Stockport.

SPEAKER REPAIRS, cones fitted. Satisfaction guaranteed. **L. S. RPAIRS**, Pluckley, Ashford, Kent.

R & R RADIO & TV SERVICE

Dept. P.W.
MARKET STREET, BACUP, LANCS.
Telephone 465

SALVAGE VALVES Tested before despatch

6F13	4/6	U329	5/-	PL38	6/-	20P4	6/6
6L18	4/6	10P14	5/-	PL32	3/6	30P16	5/6
EF80	1/6	20P5	6/8	U801	7/6	PC84	4/-
ECC82	3/-	30P	7/-	10P1	1/6	PY81	8/6
ECL80	3/6	6F15	5/-	20P3	5/3	U301	6/-
PL38	5/-	E301	1/-	30P11	5/3	10P13	6/6
PL38	6/-	EF85	5/-	PY32	6/-	20D1	2/-
PCF80	4/-	630L2	4/-	6U4GT	5/-	30P12	5/6
PL81	5/-	20P3	6/-	6P1	2/6	PY83	5/-
PZ30	5/-	30P11	4/-	ET86	4/-		

Speakers, 8x-7v. 6in. round 6 x 4in., 3/6; 8in. round, 6/-; post 3/-

Line Output Transformers available. State set model No.

Turret Tuners 8/-, post 2/-

Scan Coils, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

GIve - AWAY PRICES. Highest quality. Transistors: AP117, OC45, 3/6 each; OC71, OC72, OC81M, 3/- each. RTC/BY100 (500mA) Rectifiers, 5/- each. Earpieces (3.5mm Plugs), Low-Z. Magnetic, 3/6 each; Hi-Z. Crystal, 5/- each. Postage 6d. per item, 3 or more post free. AC05-40 Desk Microphones, 15/- each. AC05-45 Hand Microphones, 17/6 each; postage 1/- extra. Etch your own Printed Circuits, P-C Board, Kit of Chemicals and full instructions, 19/6, postage 2/- Laminated Copper Board (7in x 6in.) 3/- each, post free Full range of other components. Regret no lists, S.A.E. all enquiries. **C.W.O. only**—J. AND J. RADIO, 36 Bexley Terrace, Leeds 8.

6 TRANSISTOR PRINTED CIRCUIT RADIO



Components for the above as follows:—
6 transistor printed circuit 1/8, 2 1/2in. speaker 6/6, Ferrite block 1/-, Edge volume control D.P.S.K. 1/8, T.F. and Osc. coils set of 4/8 set. Slide switch D.P.D.T. 1/-. Ganged condenser 5/-, P.P output transformer 7/6, Driver transformer 7/6, Circuit 1/6.

All the above made specially and ready for assembly. Any item supplied separately. Add 1/6 P. & P. when order less than 10/-.
CLEVELAYS ELECTRICAL ENGINEERING Co.
Cleveland, Nr. Blackpool

V.H.F. Panoramic Adaptor ALA-2

This is a 30 Mc/s I/P Pan Adap that will display signals 5 Mc/s either side of 30 Mc/s. Uses 13 valves and C.R.T. 3 B.P.I. Power I/P is 115v 400 c/s if an external P.U. is to be used. The power requirements are +300 at 70ma - 1kV at 2ma and 6.3 twice. Controls focus, brill. X & Y shift, gain, centre freq. and width. These will work with any Rx or Converter with an I.F. freq. of 30 Mc/s. in good condition with circ. and mods. etc. Price £6.0.0 plus 7/6 carr.

Small Blower Motors

1/1P 115V 60 c/s, 22 watts, 3000 R.P.M. outlet 2 1/2" x 1 1/4", inlet 1 1/4" dia. Overall length 5 1/2". black crackle finish. Brand new and boxed. Price 25/- plus 3/- post. 230/110 Auto Trs. 9/6 post paid.

P.U. Type 311

1/P 200/250v 50 c/s O/Ps +300 at 250 ma. —130 at 40 ma and 12v D.C. smoothed at 4 amps. The O/Ps are all fused and can be switched remotely by means in the P.U. Complete in case with circ. in good condition. Price £5.10.0 plus £1 carr.

Meters 590 U.A.

Scaled 0 to 5 Marconi single hole fixing type, 2" O.S.D. 90 ohms into res. Price 15/- plus 1/6 post.

Monitor Unit AN/GRD

This comprises a Scope, Bearing Ind. and A.F. Monitor. The scope uses C.R.T. 2 BPI and valves 6A1UG x 2, 6AL5, 12AU7 x 2, 6AQ5 x 2, OA 4, 2D21, 12AX7, 5Y3 x 2, also 3" speaker, 3800" Bear. Ind. 4" dia. Controls, focus, brill., X & Y shift, Sync, Gain, X amp. Power I/P is 115v 50 c/s. 19" rack unit with outer cover in good condition with circ. diagram. Price £5.10.0 plus 12/6 carr.

Selenium Rectifiers

H.W. type I/P 300v, O/P 100 ma with mounting brackets. New and boxed. Price 2/6 plus 1/- post or 4 for 10/- post paid.

Chassis with cover

Size front 11 x 6 x 14" deep, with 4 Ind lamps 6v, 3 relays 24v 4P c/o 25 ohm pot etc. Aluminium construction finished in black crackle. Brand new. Price 22/6 plus 5/6 post.

Test Set type 5B

This is a battery operated, crystal controlled signal generator covering the band 100 to 125 Mc/s with modulation. There is also 1 Ma Meter 2 1/2" F.I. Rd, 3 gang 30 PF tuning cond. dial meter, var. cap., 2 section aerial, etc. Complete in case size 14" x 8" x 12" with front cover. Brand new and boxed. Price 35/- plus 10/- carr.

Ind. Unit CRT 100

This is a twin tube radar display unit with C.R.T.s CV2184 2 1/2", CV2286 3 1/2" and valves, EP91 x 6, EB91 x 5, 12AT7 x 6, CV261 x 2, 6CH6 12AU7, CV2179, 6F83. Meter edgewise reading type 0 to 3000 yds 1 Ma 2 1/2" linear scale, also 7 relays, 20 pots, 3" Magnifier on 2 1/2" C.R.T. large number of small parts. Complete with outer cover in good condition in transit case. Price £3.17.6 plus 12/6 carr.

Mains Transformers

Prta 230v 50 c/s Secs. 250.0-250 at 120 Ma, 6.3v at 3a and 6.3v at 1a twice. Price 25/- plus 5/- post. Prta 200/250v 50 c/s Secs. 425.0-425 at 150 Ma, 5v 3a, 6.3v C.T. 4a. Price 35/- plus 6/6 post. Prta 200/250v 50 c/s Secs. 500.0-500 at 120 Ma, 4v 3.6a, 4v 2.5a, 6.3v 300 ma. Price 17/6 plus 5/6 post. Smoothing choke 1 1/2" Henry, 150 Ma, will match above transformers. Price 10/6 plus 4/6 post. The above Trans and Choke are all brand new potted types made by Wooden & Partridge Trans.

B. SLATER

34 Lifford Street, Sheffield 9

RECEIVERS & COMPONENTS

(continued)

"EXPERIMENTAL" PRINTED CIRCUIT KIT

Contents

- (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2"
- (2) Resist. (3) Etchant, (4) Resist Solvent.
- (5) Cleanser/Degreaser.
- (6) 16-page illustrated booklet.

"PRINTED CIRCUITS FOR AMATEURS"

containing full etching instructions. Also free with every kit (7): Essential Design Data and Constructional Details of easy-to-build, transistorised 24 SUGGESTED PROJECTS which you can build on a P.C. chassis made from this kit using your own components. Circuit Diagrams, P.C. Chassis Plans, Assembly Drawings, Photographs. Many recently developed very efficient designs you probably haven't heard of yet, including... 4 Crystal Sets, Carrier Power Conversion Receiver, Matchbox Photocell Radio, Solar Battery L/S Radio, Pocket L/S Double Reflex, Triple Reflex with self-adjusting regeneration. Practical Bacteria-powered Radio. 3 micro-miniature radios just released. Postage-Stamp Radio 1.62" x .95" x .25". Wrist-Watch Radio 1.15" x .80" x .55". Ring Radio .70" x .70" x .55". 2 Intercoms. 4 Amplifiers, Photoelectric Alarms. Light-controlled Robot, Human Body Radiation Detector, "Perpetual Motion" Machine, Man/Woman Discriminator Transistor Tester and many more... (8) Attractive case 4 1/2" x 2 1/2" for a pocket Transistor Radio, Crystal Set etc. (9) Miniature Radio Dial MW/LW. (10) Miniature Radio Dial SW/MW/LW. Price 7/6 Post. and Packing 1/- Extra copper laminate available.

"YORK ELECTRICS"

181a, York Road, London, S.W.11

Send S.A.R. for full details



CANADIAN MARCONI 52 RECEIVERS as per previous adverts. £10.10.0. Carriage Paid Handbooks 5/-. Leaflet S.A.E. **LOUDSPEAKERS** 10in. 3 ohm in wood case. Case solld. 600 ohm Line Transformer. 25/- carriage paid. **TELEPHONE SETS** Headset with microphone, two sets make good telephone, no batteries needed. 10/- each or 17/6 pair, post paid. **RELAYS** 100 volts D.C. Coil, S/P 5 amp contacts, normally closed, 5/- post paid. **POCKET WATCHES** Ex-Government 15 Jewel, Swiss movements. 50/- plus Reg'd post 2/6. (Carriage charges apply to England and Wales only)

Telephone: Worthing 9097



FOR SALE

YUKAN SELF-SPRAY

YUKAN Aerosol spraykit contains 16 oz. fine quality durable easy instant spray. No toxic lacquer residue. Available in Grey, Blue, Gold, Bronze at 14/11 at our counter or 15/11, carr. paid, per push-button self-spray can. SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11. Please enclose cheque or P.O. for total amount to: (1) Price of 18 self-spray main colours and primer (Motor car quality) also available.

YUKAN Dept. P.W./1 307a Edgware Rd., London, W.2. (closed Thurs. afternoons, open all day Saturdays)



FOR SALE

(continued)

ARMATURE REWINDS. Hoover Junior Exchange Service. Models 375/139/1224 32/6 inc. post. Fields 45/-. Send for lists. JERVIS AND TONGE LTD., Ringwood Road, Birmingham, Chesterfield, Derbys, Tex, Oheast. 75267.

MORSE MADE!

The famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum.

One student, aged 20, took only 13 DAYS, and another, aged 71, took only 6 WEEKS to obtain a G.P.O. Pass Certificate. If you wish to read Morse easily and naturally please enclose 8d. in stamps or two international reply coupons for full explanatory booklet. To G&CHS, 46 GR EN LANE, FURLEY, SUPREY

FIVE-TON FACTORY CLEARANCE: Radio, TV Electrical Components in mixed parcels. Example: 22lb, mixed parcel £1, p.p. 7/6. Speakers, grilles, valves, bases, i.i.s. covers, condensers, etc. Hundred other items. S.A.E. list and postal orders to P. NEWTON, 16 Shaalocross Crescent, Hatfield, Herts.

SPECIAL OFFER

1 watt S.T.C. 300 mc/s M.P.N. Silicon Planer, 100% Transistors limited stocks. £1 for 6.

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16, GET20.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171.

5/- each. OC139, OC140, GET7, GET8, GET9, XCI41, BY100, OA211.

SUN SOLAR CELL KITS 24 page Booklet on Experiments inc. 4 Sun Solar Cells 11/- set.

G.P.O. DIAL TELEPHONES 20/- each. 35/- pair.

Send 6d. for full lists:— inc., S.C.R., Zeners.

CURSONS

78 BROAD STREET CANTERBURY, KENT

FOR SALE
(continued)
SPECIAL OFFER

GEVAERT TAPE. New, Boxed, 5 $\frac{1}{2}$ 600ft. with Stop and Leader Tapes, 9/- or 6 for 50/-.

GRUNDIG MA1 2 Transistor Pre-amps for Tape Monitoring or Microphone Boosters, 57/6.

LIST PRICE 4 GNS.

LEE ELECTRONICS
 400 Edgware Road, Paddington 5521
Send for Free Lists details of above

240 WATT ELECTRIC POWER ANYWHERE

ANYTIME from 12 VOLT CAR BATTERY
 with the **AMERICAN DYNAMOTOR UNIT**



Input 12v. Output 240/250/315 to 220 volts.
 Perfect for TELEVISION, POWER TOOLS and all universal AC/DC ELECTRICAL EQUIPMENT, gives wonderful results. Price only £11 + 20/- delivery.
 Send stamped envelope for full illustrated details.
 Dept. SCIENTIFIC PRODUCTS, CLEVELLYS, LANS.

HAMMERITE

HAMMER PATTERN BRUSH PAINT FOR PANELS AND BOXES

★ THE PATTERN IS IN THE TIN ★
 ALL YOU DO IS BRUSH IT ON!

9oz. tin 3/8 1 gallon 36/-
 1 pint 7/8 1 gallon 58/-
 1 pint 15/- (*sent by road)

Carriage: Orders up to 5/-, 9d.; up to 10/- 1/9; over 10/-, 2/9.

Colours: Blue, Silver or Metallic Black.
 Returns of post services, Mon. to Fri.
 From your component shop or direct from the manufacturer:

FINNIGAN SPECIALITY PAINTS (PW)
 Haking Square, Stockfield, Northumberland
 Phone: Stockfield 2280

SITUATIONS VACANT
SITUATIONS VACANT
(continued)

RADIO TECHNICIAN with a sound knowledge of at least three of the following types of equipment is required immediately for Meteorological Office Ocean Weather Ships' Single Side-Band Transmitter, Radar (Navigational), Radar Height Finding, Echo Sounders and Radio Receivers. Automatic D.F., V.H.F. and M.F. Low Voltage Servo Recorders, Digital Telemetering Equipment.

Salary scale £678—£1,104 per annum according to age, plus £120 per annum overtime allowance. Free food and accommodation provided on board ship. Applicants must be natural born British subjects. Full details from Shore Captain, Ocean Weather Ship Base, Great Harbour, Greenock. Telephone Greenock 24291.

RADIO AND TV Exam. and Courses by Britain's finest Home-study School. Coaching for Brit.I.R.E., City and Guilds Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from **BRITISH NATIONAL RADIO SCHOOL**, Russell Street, Reading.

A FULL-TIME TECHNICAL EXPERIENCED SALESMAN required for Retail Sales. Write, giving full details of age, previous experience and salary required, to the Manager, **HENRY'S RADIO LTD.**, 38 Edgware Road, London, W.2.

TV AND RADIO: A.M.I.E.R.E., City and Guilds, R.T.E.B. Cert., etc. on "Satisfaction or refund of fee" terms. Thousands of passes. For details of Exams and Home-training Courses (including practical apparatus) in all branches of Radio, TV and Electronics write for 156-page handbook—FREE. B.I.E.T. (Dept. 137K) 20 Wright's Lane, London, W.8.

SITUATIONS VACANT
(continued)

A.M.I.Mech.E., A.M.I.E.R.E., City and Guilds, G.C.E., etc. Become a Technician or Technologist for high pay and security. Thousands of passes. For details of Exams. and Courses in all branches of Engineering, Building, Electronics, etc. write for 156-page handbook—FREE. B.I.E.T. (Dept. 169K) London, W.8.

ELECTRONIC ENGINEERS required for maintenance and fault-finding on photo-typesetting equipment. Instruction courses can be arranged for suitable applicants. H.M. Forces experience of Radar or Pulse Circuitry would qualify for further training. Excellent pay and conditions of employment plus expanding opportunities in progressive printing group. Please write to Works Engineer, **SOUTHWARK OFFSET LIMITED**, 25 Lavington Street, London, S.E.1.

SERVICE SHEETS

SERVICE SHEETS for all makes of Radio and TV, 1925-1965. Prices from 1/- with free fault-finding guide. S.A.E. inquiries Catalogue of 6,000 models 1/6. Valves, modern and obsolete, Radio/TV Books. S.A.E. lists. **HAMILTON RADIO**, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio and Television 4/-, post paid. **VEST AND EMBRY**, 17 Halgarth St., Durham.

SERVICE SHEETS, Radio, TV, 5,000 models List 1/-, S.A.E. inquiries. **TEL RAY**, 11 Maudland Bank, Preston.

(Continued on next page)

ELECTRONIC TECHNICIANS

Vacancies exist for technicians in the electronic maintenance shop and test equipment laboratory at the Ballistic Missile Early Warning System establishment at Fylingdales in Yorkshire.

Applicants should have obtained considerable experience in the repair and maintenance of radar and wireless equipment. A special consideration will be given to applicants experienced in the repair and calibration of electronic test equipment.

Whilst academic qualifications are desirable,

military service training to RAF radar/wireless fitter standard is acceptable.

These are monthly staff appointments carrying attractive salaries. Rotating shift work is involved for which generous shift allowances and overtime are paid.

Fringe benefits include 3 weeks holiday, contributory Pension and free Life Assurance Schemes with assistance towards removal, relocation and initial subsistence expenses.

For further information please send brief details of your qualifications, experience and present salary to:



D. J. Symon, Personnel Department,
RCA GREAT BRITAIN LIMITED,
Fylingdales, Pickering, Yorkshire.

SERVICE SHEETS

(continued)

SERVICE SHEETS (75,000) 4/- each. Callers welcome. Always open. 5 South Street, Oakenshaw, Bradford.

SERVICE SHEETS

4/- ea., plus postage

We have the largest display of Service Sheets for all makes and types of Radios, Televisions, Tape Recorders, etc., in the country. Speedy service.

To obtain the Service Sheet you require please complete the attached coupon.

From:

Name:

Address:

To: **S.P. DISTRIBUTORS**

44 Old Bond St., London, W.1

Please supply Service Sheets for the following:

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

I also require list of Service Sheets at 1/6.

(please delete items not applicable) I enclose remittance of.....

MAIL ORDERS ONLY Feb. PW

BOOKS & PUBLICATIONS**SURPLUS HANDBOOKS**

19 set Instruction Handbook, 3/8, p/p 6d.
1155 Instruction Handbook, 3/8, p/p 6d.
H.R.O. Instruction Handbook, 3/8, p/p 6d.
38 set Instruction Handbook, 3/8, p/p 6d.
40 set walkie talkie Circuit & Notes 3/6, p/p 6d.
88 set walkie talkie Instruction Handbook, 4/8, p/p 6d.
Frequency Meter BC221 Instruction Handbook 3/8 p/p 6d.
Wavemeter Class D Handbook Mt. I, II and III, 3/8, p/p 6d.
18 set Circuit Details & Notes, 3/6, p/p 6d.
A.R. 98D Instruction Handbook, 15/-, p/p 1/8, R.107
Instruction Handbook, 4/8, p/p 6d.
R1118/A Circuit Diagram & Details, 1/8, p/p 6d.
R1224/A Circuit Diagram & Details, 1/8, p/p 6d.
R1355 Circuit Diagram & Details, 1/8, p/p 6d.
RF Unit/ 24 Circuit Diagram & Details, 1/8, p/p 6d.
RF Unit 25 Circuit Diagram & Details, 1/8, p/p 6d.
RF Unit 28 Circuit Diagram & Details, 1/8, p/p 6d.
Amplifier A1134 Circuit Diagram & Details, 1/8, p/p 6d.
Resistor Colour Code Indicators. Indicates the value of a resistor at a glance. Price 1/8 p/p 6d. All mail orders to: Instructional Handbook Supplies (PW) Talbot House, 28 Talbot Gardens Roundhay Leeds, 5

EDUCATIONAL

CITY AND GUILDS (Electrical, etc.) on "Satisfaction or refund of fee" terms. Thousands of passes. For details of modern courses in all branches of Electrical Engineering, Electronics, Radio, TV, Automation, etc., send for 56-page handbook—FREE B.I.E.T. (Dept. 168K), 29 Wright's Lane, London, W.8.

EDUCATIONAL

(continued)

RADIO OFFICERS' training courses. Write Principal, Newport and Monmouthshire College of Technology.

RADIO OFFICERS see the world. Seagoing and shore appointments. Our many recent successes provide additional trainee vacancies during 1966. Grants available. Day and boarding students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how **ICS** can help you in your career.

DEPTICS, 541 PARKGATE ROAD, LONDON, S.W. 11.

METAL WORK

METAL WORK: All types cabinets, chassis racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman St., Loughborough.

WANTED

WE BUY New Valves, Second-hand Cameras, Binoculars, Projectors, Amplifiers, Records, Car and Transistor Radios, Components, etc. Send s.a.e. to **EDDY'S (Nottm) LTD.**, 116 Alfreton Road, Nottingham.

WE BUY New Valves for cash, large or small quantities, old types or the latest. Send details. Quotations by return. **WALTON'S WIRELESS STORES**, 15 Church Street, Wolverhampton

WANTED VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

URGENTLY WANTED: New. Modern Valves, Transistors, Radios, Cameras, Tape Recorders and Tapes, Watches, Tools, any quantity. **S. N. WILLETTTS**, 16 New Street, West Bromwich, Staffs. Tel. 2392.

DAMAGED AVO METERS wanted. Models 7 and 8. Any condition. Any quantity. **HUGGETTS LTD.**, 2-4 Pawson's Road, West Croxford.

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. **R.H.S.**, Beverley House, Mannville Terrace, Bradford 7.

MISCELLANEOUS

Build Yourself a Record Player and save £22.5. Refined, one valve circuit yet simple to build. Backed by a comprehensive service and queries scheme, so even the complete beginner can tackle this job with confidence. Superb performance, Treble/Bass/Volume controls. Instructions and diagrams 5/6.

HARRIS

16, Melrose Avenue Portslade, Sx.

CONVERT ANY TV SET into an Oscilloscope. Diagrams and instructions 12/6. **REDMOND**, 42 Dean Close, Portslade, Sussex.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write **NOW** for free leaflet and further details to **C. & S.**, 20 Maude Street, Darlington, Durham. Send 3d. stamp

PADGETTS RADIO STORE

OLD TOWN HALL

LIVERSEDE, YORKS.

Telephone: Cleckheaton 2866

Special Offer. Brand New Boxed TV Tubes MW43/69, 65/-, MW36/24, 37/6, 90 Degree Tubes with slight glass fault 37/- each. Carriage on any tube in G.B. 10/- Fully Guaranteed for 12 months.
Reconditioned Tubes, Six months' guarantee. AW43/80, 30/-, MW43/80, 30/-, MW43/69, 30/-, CRM172, 30/-, CRM142, 17/-, 12 inch tubes, 10/-, 17 inch tubes perfect but without guarantee, 17/- each, Carriage on any tube in G.B. 10/-.
Scope tube removed from units, DG7-5, 2.5in., perfect condition, 30/-. Post 4/6.
New JAP earpieces complete with lead and plug, 3 or 5mm., 1/11 post paid or 20/- per dozen.
13 Amp Double Sockets. Brown surface type, 3/-, Post 1/6, 6 for 18/- post paid.
New Diodes, top grade, no duds, 3/- doz., post paid.
New 12in. Speakers with built-in tweeter, 3 or 15 ohms 28/6. Post paid.
Perfect Speakers ex. equipment, 8in. round, 6/-, Post 3/-, 7 x 4in., 5/-, Post 2/-, 6 x 4in., 3/-, Post 2/-, Six for 20/-, post paid, 6in. round, 3/-, Post 2/-, Phillips 5in. round, 5/-, Post 2/-.
Motors Single Phase 240v. quarter H.P., 26/-, 1400 Revs. Fully guaranteed, ex. washing machines, carriage 8/6.
13 Channel 17" Untested TV Sets, 50/-, 10/- carriage.
Rush 12in. TV 24 C 13 channel TV. Complete and tested with good tube, only wants clearing, 75/-, carriage 10/-, G.B.

VALVE LIST					
Ex equipment,	3 months' guarantee				
EL91	1/6	30P1	4/-	PCC84	4/-
EL90	2/8	40P1	3/8	PCL82	5/-
EL84	5/-	40U1	3/8	PCL85	5/-
ECC81	3/-	U281	5/-	PL36	5/-
ECC82	3/-	U282	5/-	12AT7	3/-
EY51	2/6	U329	5/-	6CH6	1/6
EY36	5/-	KT38	5/-	R18	3/6
EBF90	4/6	6V6GT	4/-	ARP12	1/6
EB91	9d.	6B3	1/6	50 for 51	
ECC83	4/-	6K25	5/-	807	5/-
EL38	5/-	6P25	3/6	EF50	1/-
EF81	9d.	6U4	5/-	Doz.	6/6
6F1	1/-	6Y33	6/-	EF80	1/6
6F14	5/-	6Y80	3/-	Doz.	10/-
6F15	5/-	6Y81	3/-	6K7	1/3
1002	5/-	PL38	8/6	Doz.	10/-
10F1	1/-	PL41	4/-	6V8	1/9
10P13	5/-	PL82	3/-	Doz.	18/-
10P14	5/-	PL83	3/-	6K8	1/9
20D1	2/-	6Y82	3/-	Doz.	18/-
20L1	5/-	PCF90	4/-	U25	5/-
20P3	4/-	RZ30	5/-		

All valves post paid

BARGAIN OFFER CORNER

MAINS TRANSFORMERS
Semi-shrouded drop thro' type. Pri. 200, 220, 240v. Sec. 260v. $\frac{1}{2}$ wave at 70mA and 6.5v. at 2 amp. c/t.
Stack size 3 x 2 1/2 x 1 1/2 in.

PRECISION 6-MINUTE DELAY ACTION SWITCH
Clockwork actuated. Made by Smiths. Separate switching actions at intervals up to 6 mins. Each switch action designed for current loading up to 15 amps. at 250 volts. Suitable for photographic timer sequence switching operations, etc. etc. Brand new and unused units offered at a fraction of their true value. **OUR PRICE ONLY 10/-** each. P. & F. 1/6. (3 or more post free). Special quotations for quantity.

HEAVY DUTY NON-INDUCTIVE D/P MICRO SWITCH
Conservatively rated 10 amps at 250v. Standard one-hole fixing. Body size 1 1/2 x 1 in. deep line terminals 3/- each. P. & F. 1/6 (6 or more post free).

NEON A.C. MAINS INDICATOR
For panel mounting, cut out size 1 1/2 x 1 1/2 in. deep line terminal. White case with warning ring brighter light. For mains 200/250v. 2/6 each P.P. 6d. (6 or more post free).

VYNAIR AND KEKINE SPEAKER AND CABINET FABRICS
Apprx. 54in. wide. Usually 85/- yard. **OUR PRICE 18/6** per yard length. P. & F. 2/6 (min. one yd.) S.A.E. by wave.

ACOS CRYSTAL MIKES
High Imp. For desk or hand use. High sensitivity 18/6. P. & F. 1/6.
TEL CRYSTAL STICK MIKE
Listed at 45/-, **OUR PRICE 18/6**. P. & F. 1/6.

E.C.O. SUPPLEMENTARY CONDENSERS
250v. A.C. .005 + .004 in. in tubular can $\frac{1}{2}$ in. long x $\frac{1}{4}$ in. dia. 2 for 3/-. post free.

TRANSISTOR DRIVER and O/P TRANSFORMERS
(Tapped 3 ohm and 15 ohm output). Plus 4 suitable Transformers giving approx. 1 watt output 25/-, P. & F. 2/6.
9-GANG .0005 TUNING CONDENSERS
2 1/2 in. h. x 2 1/2 in. d. x 1 1/2 in. w. with built-in trimmer, 4/6. P. & F. 2/6.

MATCHED PAIR OF 81 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS
Stack size 1 1/2 x 1 1/2 in. Output trans. tapped for 3 and 15 ohm output. 10/- pair. P. & F. 2/6.
BRAND NEW PLESSEY
12v. 4-pin non-synch. vibrator. Type 12.148D. ONLY 8/6. P. & F. 1/6 each.

TWIN TELESCOPE SERIAL
Comprising two 3-section heavily chromed rods. Closed 12in. each extending to 32in. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, coax lead and plug. Suitable for P.M. or TV. 12/6. P. & F. 2/6.
4-WAY NON-TANGLE TELEPHONE CABLE
Latest spring back coil type, extends 12in. to 5ft. Complete with rubber bushes. 4/6 each. P. & F. 1/6.

SPECIAL BRAND NEW TRANSISTOR BARGAINS

8GT-15 (Matched pair) 15/- V15/10p, 10/-; OCT1 5/-; OCT6 6/-; AP17 7/6.
Set of Mullard 6 transistors OC44, 2—OC45 OC81D matched pair OC81 25/-, OBP12 Cadmium Sulphide OC 10/6.

EDISWAG MAZDA

FXA101 6/6; XA103 6/6.
R.F. Pack: 1—PXA102 Mixer; 2—PXA101 I.F. Amp. (Equip. OC44 and OC45)10/6
R.F. 2 Pack: 2—PXA101 I.F. 1—PXA102 Mixer12/6
L.F. Pack: Consisting of FXB118 Driver Matched pair FX171 mounted complete with heat sinks (Equip. OC81D and OC81)12/6
ALL TRANSISTORS POST FREE.

SPECIAL PURCHASE!

FROM HI-FI MANUFACTURERS
7-10 watt OUTPUT TRANSFORMERS to match pair of EC186's in push-pull to 3 ohm output. ONLY 11/6. P. & F. 2/6.
7-10 watt ULTRA LINEAR OUTPUT TRANSFORMERS to match pair of EC187's in push-pull to 3 ohm output. ONLY 12/6. P. & F. 2/6.
SPECIAL MAINE TRANSFORMERS to match either of the above. Tapped primary. Secondary 250v. 50mA half wave and 6.3v. 2 amps. ONLY 12/6. P. & F. 2/6.

SPECIAL HARVERSON OFFER!!!

BRAND NEW HEAVY DUTY 12in. SPEAKERS
Response 45 c/o-12 Kc/s. 1 1/2 in. voice coil. Available in 3 or 15 ohms. Guaranteed full 15 watts British making. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE at 59/6. P. & F. 6/-. Also 25 watt Quiter Model available at 25.5.0. And 25 watt Quiter Model 28.5.0.

BRAND NEW 3 OHM SPEAKERS
8in., 12/6; 6in., 15/-; 8in., 21/-; 10in. 25/-; 12in., 27/6; (12in. 15 ohm 30/-) 10in. x 6in., 26/-; R.M.I. 12in. x 8in. with high flux ceramic magnet 42/-; 10in. 45/-, P. & F. 5in., 2/-; 6in. 2in., 2/6; 10 and 12 in. 3/6 per speaker.

4-SPEED PLAYER UNIT BARGAINS

All Brand New in Maker's Original Packaging SINGLE PLAYS
GARRARDSP25De Luxe.....£12.10.6, Carr. 5/6
B.S.R. GU7 with unit mounted pick-up arm. £4.18.8, Carr. 5/6
LATEST B.S.R. TU/12.....£3.8.6, Carr. 5/6
E.M.L. with unit mounted pickup arm. £4. 9.0, Carr. 5/6

AUTO CHANGERS

LATEST B.S.R. UA25 Super Slim mono. £2.2.6
B.S.R. UA15, £0.12.6; **B.S.R. UA16**, £2.19.6
LATEST GARRARD AT5.....£3.8.0
GARRARD AT6, £3.10.0 Carr. 6/6 on each.
All the above units are complete with 1/6 mono head and sapphire stylus or can be supplied with compatible stereo head for 12/6 extra.

FOR ONE MONTH ONLY!

Special offer of the famous COLLARO STUDIO 4-speed Semi Transcription Auto Changer Units. 200/250v. A.C. Really heavy duty motor and robust mechanism. Designed and built for long life. Stereo wired. Supplied complete with mono cartridge and stylus. Offered at Bargain Price of £5.12.6. Carr. 7/6. Stereo version £6.12.6. ALSO small number of GARRARD Autolinn Changers, with pic-in-head complete with Mono cartridge. To clear at £5.10.0 each or with Stereo cartridge 12/6 extra. Carr. 6/6.

NEW CARTRIDGE BARGAINS


RONETTE STEREO 105 CARTRIDGE (Stereo) L/P/78. Complete with two sapphires. Original list price 67/9. **OUR PRICE 24/-**. P. & F. 1/-.
ACOS 71-5 single sided crystal cartridge for Stereo and L.P. records. Complete with diamond stylus and universal mounting bracket. List price £2.6.4. Our price 18/6. P. & F. 1/6.
ACOS GP87-1 Mono complete. List price £11.0.0. Our price 18/6. P. & F. 1/6.

3-VALVE AUDIO AMPLIFIER MODEL HA34



Designed for Hi-Fi reproduction of records A.C. Mains operation. Really built on plated heavy gauge metal chassis size 7 1/2 in. w. x 4 1/2 in. d. x 4 1/2 in. h. Incorporates ECC83 EL84 EZ80 valves. Heavy duty double-wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line and cut with minimum insertion loss. Can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, £4.5.0 P. & F. etc. wired and tested for only 6/-.

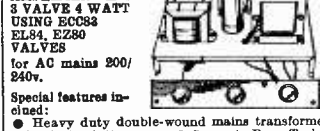
TYPE HSL 'FOUR' AMPLIFIER KIT 3 VALVE 4 WATT USING ECC83



EL84, EZ80 VALVES
for AC mains 200/240v.
Special features included:
● Heavy duty double-wound mains transformer with electrostatic screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. ● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar, microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● All this builds on to a chassis size only 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts solder etc. (No extras to buy).
PRICE: 79/6 P. & F.
Comprehensive circuit diagram, practical layout and parts list 2/6. (Free with Kit).
This kit although similar in appearance to HA34 it employs entirely different and advanced circuitry

STEREO AMPLIFIERS

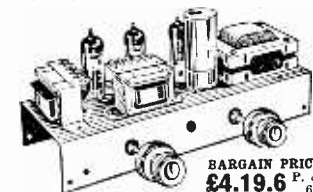Incorporating 2 EC186's and 1 EZ80 heavy duty double-wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



BARGAIN PRICE £4.19.6 P. & F. 6/6

SUPER DE LUXE version of above incorporating EC186 valves separate bass and treble controls and full negative feedback 8 gns. P. & F. 6/6.

QUALITY RECORD PLAYER AMPLIFIER

A top quality record player amplifier. Size 7 1/2 in. w. x 2 1/2 in. d. x 4 1/2 in. h. This amplifier (was used in a 28 cm. record player) employs heavy duty double-wound mains transformer. ECC83, EL84 EZ80 valves. Separate bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Ready built and tested.
PRICE 69/6 P. & F. 4/9.
ALSO AVAILABLE Mounted on board with output transformer and 6in. speaker ready to fit into cabinet below. **PRICE 89/6 P. & F. 5/9.**

QUALITY PORTABLE R PLAYER CABINET

Uncut motor board. Will take above amplifier and B.S.R. or GARRARD Autolinn or single Record Player Unit. Size 18 x 14 x 8 1/2 in.


PRICE £39.6. Carr. 7/6

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT



Type TA1
● Peak output in excess of 14 watts. ● All standard British components. ● Built on printed circuit panel size 6 x 3 in. ● Generous size Driver and Output Transformers. ● Output transformer tapped for 3 and 15 ohm speakers. ● Transistors (2ET14 or S1 Mullard OC81D and matched pair of OC81 type) ● 9 volt operation. ● Everything supplied, wire battery, clips, solder, etc. ● Comprehensive ease to follow instructions and circuit diagram, 1/6. (Free with Kit). All parts sold separately.
SPECIAL PRICE 45/- P. & F. 3/-.
Also ready built and tested 52/6. P. & F. 3/-.
A pair of TA1's are ideal for stereo.

10/14 WATT HI-FI AMPLIFIER KIT

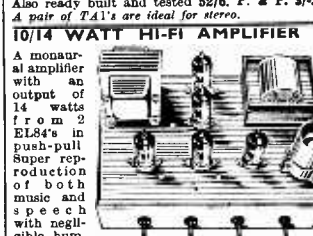

A monaural amplifier with an output of 14 watts from 2 EL84's in push-pull super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram. allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and independent volume controls and separate bass and treble controls are provided, giving good lift and cut. Valve line-up 2 EL84's, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 1/6. (Free with parts).
All parts sold separately. **£6.19.6** P. & F. 8/6
ONLY
Also available ready built and tested complete with standard input sockets. £8.15.0. P. & F. 8/6.
Carrying case for above 28/6. P. & F. 7/6

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19 CHERRYWOOD 3985


Open all day Saturday Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station (Please write clearly) PLEASE NOTE: P. & F. CHARGES QUOTED APPLY TO U.K. ONLY. P. & F. OVERSEAS ORDERS CHARGED EXTRA.

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SEE RIGHT HAND PAGE FOR MORE ITEMS

HARVERSON'S F.M. TUNER Mk. 1

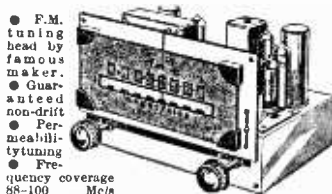

F.M. tuning head by famous maker.
 • Guaranteed non-drift
 • Permeability-tuning
 Frequency coverage 88-100 Mc/s
 • Balanced diode output. • Two I.F. stages and discriminator. • Attractive maroon and gold dial (7 x 3 in. glass). • Self-powered using a good quality mains transformer and valve rectifier.
 • Valves used: ECC85, two EF80's and E250 (rectifier). • Fully drilled chassis. • Size of completed tuner 8 x 6 x 4 1/2 in. All parts sold separately. Set of parts if purchased at one time £5.19.6. plus 8/6. • P. and Ins. Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye, front panel and brackets, £6.12.6. P. & P. 8/6.
 Mark III Version as Mark I but with output stage. (ECL82) and tone control £7.7.0. P. & P. 8/6.

SPECIAL PURCHASE! TURRET TUNERS
 By famous maker. Brand new and unused. Complete with PCC84 and PCF80 valves 34-38 Mc/s I.F. Biscuits for Channels 1 to 5 and 8 and 9. Circuit diagram supplied. ONLY 25/- each. P. & P. 3/9.

GÖRLER F.M. TUNER HEAD
 88-100 Mc/s 10.7 Mc/s L.F. 15/- plus 2/- P. & P. (ECC85 valve, 8/6 extra).

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. Printed circuit board (size 8 1/2 x 3 1/2 in.). • 5 pre-aligned I.F. transformers. • High-gain Ferrite Rod Aerial. • All First-grade transistors. • Car aerial winding. • Push-pull output. • All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time ONLY £4.5.0. P. & P. 2/6 (Circuit diagram 2/- free with set of parts).

35 OHM SPEAKERS
 Suitable for use with above. 2 in. Goodmans Ideal replacement for most pocket portables, 8/8; 3 1/2 in. 12/8; 7 x 4 in., £1/-; P. & P. 2/- per speaker.

Portable CABINET
 Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker, 25/-; P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET
 3 I.F. transformers one oscillator coil one driver transformer and wound Ferrite aerial (med. long and car aerial coupling), 32/6 complete post 2/- 6 transistor printed circuit board to match 8/6. Post 1/-. Circuit diagram 1/6 extra.

BARGAIN OF THE YEAR!

A wonderful opportunity for you to build a quality AM/FM TRANSISTOR RADIO TUNER UNIT

for 9v. operation. We offer the essential very high grade specially matched components comprising: FM Tuner Head pre-designed (88-100 Mc/s) complete with transistors. Two combined AM/FM I.F. Transformers, one discriminator transformer, one AM last I.F. transformer with diode detector. Most attractive coloured dial size 8 1/2 x 3 1/2 in. AM tuning chrome fittings. Speaker aperture 9 x 4 in. Overall chrome gang, hardware items for tuning mechanism. AM ferrite rod aerial (MW/LW) with coupling winding trimmer bank, tuning drum, pulleys, etc., and suggested circuit diagram giving coil connections etc.

OFFERED AT THE AMAZING PRICE OF 4 Gns. P. & P. 4/6
 Owing to the very high value offered and the limited number we regret that no correspondence can be entered into regarding this item.

QUALITY PORTABLE TAPE RECORDER CASE

Brand new and unused. Beautifully made and expensively finished in dark grey heavy grade rexine. 34th chrome metal grille front and chrome fittings. Speaker aperture 9 x 4 in. Overall size 15 1/2 x 15 1/2 x 7 1/2 in. Will take any standard tape deck or single record player. Limited number only. Worth at least £5. OUR PRICE 49/6. P. & P. 6/-

TAPE DECK
 B.S.R. MONARDECK. Single speed, 3 1/2 in. per sec. simple control uses 5 1/2 in. spools, £6.15.0, plus 7/6 carr. and ins. Tapes extra.

◀ Harverson Surplus Co. Ltd.

NEW VALVES!

Guaranteed Set Tested 24 HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET OF 4, 14/-	DAF96, DF96, DK96, DL96, SET OF 4, 23/6.
1R5 4/- EB91 1/9 PL36 8/6	1S5 3/3 EB41 6/3 PL81 6/8
1T4 1/9 EBF80 5/9 PL82 5/-	3S4 4/3 EBF89 5/9 PL83 5/11
3V4 5/- ECC81 3/3 PL84 6/-	6K8K 1/3 ECC81 4/6 PY32 8/8
6K8K 3/3 ECC83 4/6 PY33 8/6	6QT7 5/6 ECC85 5/3 PY80 4/9
6V6G 3/- ECR82 5/9 PY81 5/-	10C2 11/- ECH35 5/9 PY82 4/9
20L1 11/- ECH42 7/9 PY83 5/3	20P3 10/6 ECH81 4/6 PY800 5/11
20P4 13/- ECL80 5/11 U25 8/-	20P5 11/6 ECL82 6/6 U26 8/6
30PL1 9/3 ECL86 8/0 U191 9/6	30L15 8/9 EF39 3/3 U301 10/6
30PL13 10/- EF41 5/9 U801 14/9	35L6GT 5/6 EF80 4/6 UAB80 5/-
CL33 8/6 EF85 4/6 UAF42 6/11	DAC32 6/9 EF86 6/6 UBC41 6/-
DAF91 3/3 EF89 4/3 UBF80 5/6	DAF96 5/11 EF91 2/9 UB89 5/9
DF33 7/6 EL41 7/1 UCC84 7/1	DF91 1/9 EL84 4/6 UCC85 6/-
DF96 5/11 EY51 5/11 UCF80 8/3	DK32 7/- EY86 5/6 UCH42 7/-
DK91 4/- EZ40 5/6 UCH81 6/-	DK92 7/9 EZ80 3/9 UCL42 7/1
DK96 6/3 EZ81 4/3 UCL83 9/-	DL33 6/6 PCC84 5/6 UF41 6/6
DL35 4/9 PCC89 9/6 UF89 5/6	DL92 4/3 PCF80 6/3 UL41 4/9
DL94 5/- PCF82 5/9 UL84 5/9	DL96 5/11 PCF805 8/- UY41 3/11
DY88 6/3 PCL82 6/3 UY85 4/9	DY87 7/3 PCL83 8/6 W77 2/-
EABC80 5/6 PCL84 7/6 Z77 2/9	

Postage on 1 valve 9d. extra. On 2 valves or more postage 6d. per valve extra. All parcels insured against damage in transit 6d. extra.
 Office address, no callers.
GERALD BERNARD
 83 OSBALDESTON ROAD
 STOKE NEWINGTON
 LONDON N.16

4-STATION INTERCOM



£7/19/0
 solve your communication problems with this new 4-station Transistor Intercom system (1 Master and 3 Subs). In durable plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9v. battery. On/off switch. Volume control. Ideally suitable for Office. Factory Workshop, Warehouse, Hospital, Shop, etc. to keep instant inter-departmental contacts. Complete with long connecting wires and other accessories. Nothing else to buy. Post free.



Modernize your Office, Shop, Warehouse, Workshop, Surgery, Nursery and Home with this latest two-way Transistor Intercom, consisting of two units: Master and Sub. In strong plastic cabinets with chromium stands. Elegantly designed for use as two-way instant communication system—call/talk/listen—between two persons anywhere indoors or outdoors. Operates on one 9v. battery. Complete with 60ft. wire Battery 2/6. Ready to operate. P. & P. 2/6.

BATTERY ELIMINATOR & CHARGER, 27/6
 Use your Transistor Radio or Intercom from domestic A.C. mains and charge dry battery PPS 9v. to boost battery's life many times. Unbeatable value. Save you pounds on batteries. P. & P. 1/6. Out-let with Plug, Lead and Snap cord.
 Full price refunded if not satisfied in seven days.
WEST LONDON DIRECT SUPPLIES (PW/11)
 6 Chignell Place, West Ealing, London, W.18

A SUCCESSFUL CAREER IN ELECTRONICS, RADIO AND TV CAN NOW BE YOURS AT VERY LITTLE COST!

NEW. No. 500 RADIO AND TELEVISION COURSE 75/-

Here at last is your opportunity to own a most complete course at a very modest cost! This expanded course which now includes television as well as radio repair training could get you started on a whole new career!

The Radio Section of the course was ORIGINALLY DEVELOPED BY THE RADIO TECHNICAL INSTITUTE, while the Television Servicing Course has formed the basis of instruction provided by one of the world's largest television and electronic firms!

Compares lesson by lesson with some courses costing ten times as much! You save because you receive all the lessons at one time and are not required to purchase equipment you may not need.

The lessons are crystal clear, practical, easy to master and easy. Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical know-how of an expert!

The new 600 Radio & Television Course consists of 352 large quarto size pages of instruction, hundreds of illustrations. We positively guarantee that you will be delighted or your money refunded!

NEW. No. 600 RADIO-TELEVISION ELECTRONICS COURSE 85/-

This is really big value in home training. Similar in details to the above courses excepting that you get an extra 50 pages of instruction making a total of 408 quarto size pages. Hundreds of illustrations. Includes all the usual subjects plus Radio Transmitter Circuits, Electronic Test Equipment, Thyatron Tubes, Inter-Communicators, Sound Level Meters, Servicing Printed Circuits and many more similar items. This course could be your first step into the fascinating world of electronics!

No. 400. ELECTRONICS COURSE 45/-

A complete home-study course of 35 lessons. Consists of 216 large quarto size pages of instruction. Comes complete with instructor's notes and test questions. This is a modern course that teaches without resorting to comic strip methods... Thousands of readers of this magazine have taken this course and enjoyed every minute of it... Why not you? Clip this coupon for your free trial offer now!

UNCONDITIONALLY GUARANTEED TO GIVE COMPLETE SATISFACTION

Any course not satisfactory may be returned within 10 days post-paid for full refund or credit of the purchase price.

IF YOU SEND CASH WITH ORDER WE WILL INCLUDE A FREE BOOK worth 4/6 to 5/- if bought separately. By sending cash you reduce book-keeping and other costs which we pass back to you. But you must include cash at the time of order to get this special offer!

*** * * FREE TRIAL OFFER * * ***
PAY ONLY 5/- per week if you wish.


To: **SIM-TECH TECHNICAL BOOKS DEPT. G.3,** Gater's Mill, West End, Southampton, Hants.

Please send the courses I have circled.
 No. 500 _____ No. 600 _____ No. 400 _____
 If not delighted I may return any book post-paid without further obligation on my part. Otherwise I will pay cash price or 6/- weekly (10/- fortnightly) commencing not later than 10 days after delivery I am over 21 years of age. (If under 21 parents should place order).
 I enclose cash to the sum of £ _____
 I understand you will refund this money if I am not 100% satisfied and I return the book within 10 days.

Please send me the free book(s) I have ticked.
 Oscilloscope Book Electronic Gadgets Book
 Transistor Book Radio Instrument Book

Name _____
 Address _____

TEST METERS

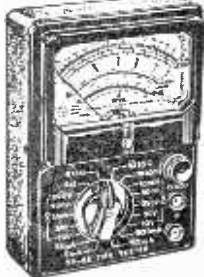

20,000 O.P.V. MODEL TP 58. Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Mega.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2in. x 5 1/2in. x 1 1/2in. £25.19.6.

2,000 O.P.V. MODEL TP 10. Reads A.C. and D.C. Volts up to 1,000 D.C. Current to 500mA; Resistance to 1 Meg.; Capacitance to 1µF; Decibels from -20 to +36; Output jack for Audio Measurements. Size 3 1/2 x 5 x 1 1/2in. £23.19.6.

30,000 OHMS PER VOLT MODEL 500. Reads voltages up to 1,000 D.C. at 30,000 ohms per volt and A.C. at 15,000 O.P.V.; D.C. current to 12 amps. Resistance to 60 Mega.; Decibels from -20 to +56; incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.F. output measurements. Size 3 1/2 x 6 1/2 x 2 1/2in. £25.19.6.

20,000 OHMS PER VOLT TESTMETER MODEL 700. Reads A.C. and D.C. voltages up to 5,000. Alternating and Direct Current up to 10 amps. Resistance up to 60 Mega.; Decibels from -10 to +42dB. Internal buzzer for audible warning of short circuits or continuity and fitted with automatic overload protection for movement. Meter size 4 1/2in. x 2 1/2in. overall dimension 7 1/2in. x 5 1/2in. x 3 1/2in. Has rigid handle which can be swivelled for use as a tilt support. ONLY £17.10.0.

TRANSISTORISED TEST EQUIPMENT. Fully guaranteed, brand new. By NOMBEX: 150 Kc/s.—350 Mc/s. Signal Generator, £910.0. Resistance-Capacitance Bridge, £85.0. 1-15 volts D.C. Power Supply, £6.10.0. Audio Generator 10/100,000 cps., £16.15.0. Inductance Bridge, £18.0.0.

VALVE VOLTMETER. D.C. Input Impedance 11 Megohms. 7 Voltage ranges. D.C. to 1,500 A.C. to 1,500 R.M.S., 4,200 Peak to Peak. Resistance 2 ohm to 1,000 Megohms. Centre zero setting for receiver alignment. Complete with A.C./D.C. probe and leads. Full illustrated details on request. ONLY £13.19.6 (Post 3/6).

FREQUENCY METERS TYPE LM. Frequency range 125-20,000 kc/s. in 2 bands. This is the United States Navy Model of the well-known BC221 Frequency Meter, but has many additional features which increase its usefulness. Voltage stabilisation circuits and Crystal control ensure extreme accuracy and in addition it is fitted with an Internal Modulation switch to allow use as a Signal Generator. Size only 8 1/2in. x 8in. x 8 1/2in. ONLY £15.


VARIABLE VOLTAGE TRANSFORMERS. Fully shrouded. Input 230 v A.C. 50/60 cycles. Output 0-280 v. 2.5 amps. type £5.17.6. 5 amps. type £9. 10 amps. type £16.10.0. 20 amps. type £22.10.0.

STANDARD TRANSFORMERS
Vacuum impregnated, interleaved E.S. screen, Universal mounting. Size 4in. x 3 1/2in. x 2 1/2in. ALL BRAND NEW 19/6 each. Post 2/6.
Type 1 250-0-250 v. 80 mA., 6.3 v. 3 a. tapped at 4 v. 4 a. 6.3 v. 1 a. tapped at 4 v. and 5v. 2 a.
Type 2. As above but 350-0-350 v. 80 mA.
Type 3. 30 v. 2 a. tapped at 12, 15, 20 and 24v. to give 3-4-5-6-8-9-10 v., etc.

HARRIS ELECTRONICS
(London) LTD.
138 GRAY'S INN ROAD
LONDON, W.C.1

Telephone: TERMINUS 7937
Please include carriage cost on ALL Mems.
Trading hours 9 a.m.—6 p.m., Monday—Friday.
Closed Saturday, We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.

BBC2 (625 LINE) TV AERIALS

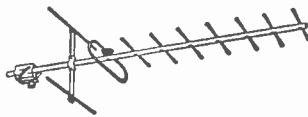

Mast Mounting Arrays. 9 element 45/-; wide spaced high gain, 11 element 55/-; 14 element 62/8. **Wall Mounting with Cranked Arm.** 9 element 60/-; wide spaced high gain, 11 element 67/8; 14 element 75/-; Chimney Arrays Complete, 9 element 72/-; wide spaced high gain, 11 element 80/-; 14 element 87/8. **Loft Arrays.** 7 element 32/8; wide spaced high gain, 11 element, with Tipping Arm, 62/8; 14 element 70/-; All high gain units have special Multi-rod Reflector. Low loss co-axial cable 1/8 per yard. UHF transistor pre-amps from 75/-.

BBC · ITV · F.M. AERIALS



B.B.C. (Band D). Telescope loft 21/-. External S/D 30/-. **I.T.V. (Band 3).** 3 Element loft array 25/- .5 element 35/-. Wall mounting, 3 element 35/- .5 element 45/-. **Combined B.B.C./I.T.V.** Loft 1+3. 41/3; 1+5 48/9; Wall mounting 1+3 56/3; 1+5. 63/9; Chimney 1+3. 63/8; 1+5. 71/3. **VHF transistor pre-amps from 75/-.** **F.M. (Band 2).** Loft S/D 12/8. "H". 30/-, 3 element, 52/8. External units available Co-ax. cable 6d. vd. Co-ax. plugs, 1/3. Outlet boxes 4/8. Diplexer Crossover Boxes, 12/8. C.W.O. or C.O.D. P. & P. 4/8. S.nd 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. P.W.)
27 Central Parade, New Addington
Surrey
LOD 2266

RESISTANCE SUBSTITUTION BOX. 15 ohms to 10 Meg in 24 steps. 28/- post 1/-.
CAPACITY SUBSTITUTION BOX. 100 pF to .22 µF in 9 steps. 19/8 post 1/-.
MULTIMETERS. EP10K 10K Ω/V. 67/8 post 2/-; EP30K 30K Ω/V. 105/8 post 2/9; EP50K 50K Ω/V. 145/- post 2/9; Leather cases, EP30K, 22/6; EP50K 30/- post 1/3.

NOUGHTS AND CROSSES MACHINE. Uses switches and lamps only, cannot be beaten. Circuit, wiring diagrams, instructions 3/6.
Precision Wirewound Resistors 1 Watt 1Ω to 5K 1% 3/- to 20K 4/3; 1% add 3d. Your value wound to order.
High Stability Resistors 1% 1W 2/- each. Full range 10Ω to 10 MΩ.

PLANET · INSTRUMENT CO.
25(W) DOMINION AVENUE
LEEDS 7

N.S. KITS

No Soldering — No Drilling

High performance Medium Wave Radio you can really build yourself. Unique kits that really work with add-on kits to increase power and range.

Kit No. NS.IVM, 47/6
Postage & Packing, 3/3

Full details sent on receipt of stamped addressed envelope.

Circuit diagrams and details send 2/6. (deductable on order).

G. A. TAYLOR LTD.
21 HYDE ROAD, DENTON
MANCHESTER

PRICE
SPECIAL RADIO
CHASSIS OFFERS



Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Complete with two 10" elliptical loudspeakers plus a mono/stereo 4-speed autochanger. Complete £29.19.6. Chassis only 19/6 gns. Special terms available of £4.10.0 deposit followed by 18 monthly payments of £1.13.0 (total H.P. of £34.4.0) + 15/- P. & P. Send £5.5.0 now.



The Imperial stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons. Long-Medium-Short and VHF bands. Complete with two 10" loudspeakers plus a mono-stereo 4 speed automatic record changer. Complete 39/6 gns. Chassis only 29/6 gns. Special terms available of £6.4.6 deposit followed by 24 monthly payments of £1.15.10 (total H.P. £49.4.6) + 17/6 P. & P. Send £7.2.0 now.



This fabulous 'Empress' Hi-Fi radiogram chassis is offered complete with 10" loudspeaker plus 4 speed autochanger. At only 23 gns. this is the bargain of the year. Chassis only 15/6 gns. Special terms available of £3.12.6 deposit followed by 18 monthly payments of £1.6.7 (total H.P. £27.11.0) + 15/- P. & P. Send £4.7.6 now.


All Lewis Radio equipment including valves are fully guaranteed for one year. Send your cheque or P.O. today while stocks last to Dept. P.26.

LEWIS radio
LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.14. Telephone: PAL 3733/9660

ARE YOU LOOKING for the UNUSUAL?


Because it may be standard catalogue stock to us. Here are a few examples—

THERMISTORS

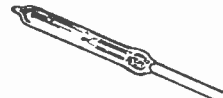

Type R.53	...	£1.10
Also stocked:		
A.15	12/6	A.55 12/6
A.26	12/6	R.24 £1.10
A.54	12/6	

HIGH VOLTAGE RECTIFIERS

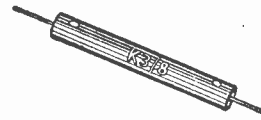

K3/40	...	9/-
Also stocked:		
K.3/15	...	6/-
K.3/50	...	12/4
K.3/100	...	£1.0.3
K.3/160	...	£1.5.6
S.T.C. FM Crystals	£3.15.0	

GANGED STEREO POTS



10K Log + 10K A/Log 10/-
 10K Log + 10K Log D.P. switch ... 12/3
 Also stocked:
 (Log or Linear) 10K, 50K, 100K, 250K, 1M, 2M 10/-

All the above and many thousands of other electronic items, both usual and unusual, may be found in our catalogue, price 7/6, plus 1/6 postage and packing. Each catalogue contains 5 coupons each worth 1/- if used as directed. Post the Coupon on the right with your cheque or P.O. for 9/-.

RESISTORS



1/0 1/2 watt
 Most values between 22 Ohms and 10 Meg.

VALVES

85A1	£2.11.6	TT21	£2.8.6	VR105/30	18/6
85A2	15/6	EN91	£1.6.0	VR150/30	18/6
Z803U	18/6	150B2	15/4	6141	£2.0.0
150C4	15/9	QVO6/20	£2.8.0	5763	£1.0.0
OA2	15/-			OB2	16/-

ALSO MATCHED PAIRS

OAZ222	...	£1.6.0
OAZ223	...	17/6
OAZ224	...	14/-

TRANSISTORS AND DIODES

AFI86	...	£1.7.6	GET115	...	9/6
AC107	...	14/6	GET116	...	17/-
BYZ13	...	11/6	OC76	...	7/-
ASY28	...	8/6	OC77	...	12/-
GEX66	...	15/-	OC83	...	6/-
GET103	...	7/-	OC84	...	8/-
GET106	...	17/-	SVC1	...	18/-
GET111	...	12/-			

Please write your name and address in block capitals

NAME _____

ADDRESS _____

HOME RADIO LTD., DEPT. P.W. 187 LONDON ROAD, MITCHAM

R.S.T. VALVE MAIL ORDER CO.

All valves brand new and boxed

Mon—Fri. 9 a.m. — 5.45 p.m.
 Wed. & Sat. 1 p.m.
 Open Daily to Callers
 Tel. MITcham 6202

211a STREATHAM ROAD, MITCHAM, SURREY

OA2	5/3	6BR7	10/8	6L1	9/8	10LD11	10/-	30C15	9/8	ATP1	1/9	EB91	3/-	EP98	10/-	N78	15/-	PY83	6/-	UCL33	8/9
OC3	5/-	6BR8	7/6	6L6G	7/6	10P13	12/6	30C17	12/6	ATP5	7/6	EB33	6/6	EF183	6/6	N108	15/-	PY800	5/6	UF41	7/-
LA7	7/9	6BR7	15/-	6L8	7/6	12A48	10/6	30F3	9/-	ATP7	4/6	EB44	6/6	EF184	6/6	NG1	8/-	PY801	6/3	UF89	6/6
ID3	6/-	6BW6	8/6	6Q70	5/6	12A76	4/6	30FL1	12/-	AU2	30/-	EB90	6/6	EL32	3/6	NG27	25/-	R2	4/-	UL41	6/6
IE5	7/6	6BW7	8/6	6Q70T	9/-	12AT7	3/3	30LL5	12/-	AU5	9/-	EBP80	5/-	EL33	17/6	OZ4	4/-	R19	7/-	UL84	5/6
1LD5	5/-	6C4	1/9	6SA7	7/6	12A16	2/9	30L17	12/6	AZ1	8/9	EBF83	7/6	EL34	9/6	PC88	8/-	RG5/500	UM80	7/-	
1N50T	8/-	6CG6	4/6	6S47	6/6	12A17	5/6	30P12	10/-	AZ31	7/9	EBF89	5/9	EL41	7/6	PC89	7/-	R130	59/-	UL6	13/6
1R5	5/-	6C6	3/9	6SG7	4/-	12A7X	4/6	30P19	14/-	CBL31	28/6	EBL1	17/6	EL42	7/6	PC97	9/6	R05	10/-	UL7	10/6
1S4	9/-	6CG8	6/-	6SH7	2/6	12BA6	6/6	30PL1	11/-	CK502	5/-	EBL21	10/6	EL84	4/6	PC084	5/6	SP4	9/-	UO9	8/-
1S5	3/3	6CD8G	22/6	6SJ7	5/-	12BE6	4/9	30PL13	12/6	CL33	12/6	EBL31	27/6	EL90	8/6	PC089	8/6	SP41	1/8	UY21	7/8
1T4	3/6	6CH6	6/-	6SK7G	4/6	12BH7	5/9	30PL14	12/6	CY31	12/6	EBL32	5/6	EM34	9/6	PCP80	6/6	ST25	19/6	UT6	4/9
3A4	2/6	6CW4	14/-	6SL7GT	4/6	12C8GT	7/6	36A5	17/-	DAC32	7/6	EBL33	5/6	EM81	7/6	PCF82	8/6	ST210	12/6	VCB7	27/6
3Q4	6/6	6D6	2/9	6SN7GT	4/-	12E1	19/3	35L6	5/9	DAF91	3/3	ECC83	4/6	EM80	6/6	PCF82	6/-	ST210	12/6	VCB7	27/6
3Q6	6/6	6E5	5/9	6SQ7	6/-	12J5GT	2/3	35W1	4/9	DAF96	6/-	ECC84	5/6	EM81	7/6	PCF84	8/6	T41	9/-	VCB217B	80/-
3S4	4/9	6F1	9/-	6U4GT	10/-	12J7GT	7/3	35Z3	10/-	DOC90	7/6	ECC85	5/9	EM84	6/6	PCP86	8/6	TH41	20/-	VCR817C	30/-
3V4	6/-	6F5G	5/-	6V5G	7/6	12K7GT	2/3	35Z4GT	3/9	DF33	3/6	EC088	8/9	ESU150	27/6	PCP802	9/9	U10	7/-	VMP40	30/-
3V4G	8/-	6F6G	4/6	6V6M	8/6	12K8GT	8/3	35Z5	5/6	DF70	5/-	ECP80	6/6	EY61	6/6	PCP805	10/9	U14	7/-	VP48	12/6
5U4G	4/-	6F8G	4/6	6V6GT	3/6	12Q7T1	3/-	37	5/6	DF91	2/6	ECP82	6/6	EY86	6/3	PCP805	10/9	U19	30/-	VR106/30	5/6
6Y3GT	8/-	6F11	12/6	6V6GT	7/6	12RA7	6/6	42	4/6	DF92	2/6	ECP81	19/-	EZ35	10/9	PCP806	12/6	U26	10/-	VR150/30	5/6
6Y3GT	8/-	6F12	5/-	6X34	4/9	12R6T	2/9	60B5	6/6	DF96	28/6	ECH33	13/-	EZ40	5/6	PCP808	12/6	U26	10/-	VR150/30	5/6
5Z4GT	6/6	6F14	12/6	6X3G	4/9	12RH7	2/9	60C5	6/3	DFH7	3/6	ECH42	8/6	EZ41	6/6	PCL32	6/6	U26	10/-	VT23	28/6
6/3012	10/-	6F23	9/6	6X5GT	7/6	12R7	3/9	60CDG24	6/6	DFH7	3/6	ECH81	5/6	EZ60	5/6	PCL33	5/6	U26	10/-	VT23	28/6
6A7	15/-	6G6	2/6	7B6	11/-	12K8K7	2/9	60L6GT	6/-	DK91	5/-	ECH83	6/6	EZ81	3/6	PCL44	7/6	U191	11/-	VT31	58/6
6AB6	12/6	6H6	1/3	7B7	12/-	12R8K7	5/6	75	5/-	DK92	7/6	ECH80	6/6	EZ30	8/6	PCL45	7/3	U251	11/6	YU11	6/6
6AC7	3/-	6J5M	6/6	7C5	10/-	12S1	20/-	78	4/6	DK96	6/6	ECH82	6/6	EZ32	9/6	PCL46	8/6	U301	12/6	YU20	9/6
6AK5	4/6	6J9G	2/6	7C6	6/-	19AQ3	7/6	80	5/-	DL70	7/6	ECL33	9/6	EZ34	9/6	PEN44	20/-	U301	12/6	YU20	9/6
6AL5	3/-	6J5GT	4/6	7D5	8/6	19Q1	10/-	85A2	8/6	DL92	4/9	ECL81	5/6	EZ60	5/6	PEN44	20/-	U301	12/6	YU20	9/6
6AM6	2/6	6J6	3/-	7H7	5/-	20E2	11/-	150B2	14/6	DL93	3/6	ECP80	20/-	KT61	17/6	PEN46	2/9	UAF42	7/6	X79	25/-
6AM6	2/6	6J7M	8/6	7R7	12/-	20L1	15/-	150C4	12/6	DL94	6/6	ECP86	3/6	KT66	12/6	PEN46	2/9	UAF42	7/6	X79	25/-
6AQ5	6/6	6J7G	4/3	7R7	18/6	20P4	14/-	801	5/-	DL95	6/6	ECP87A	9/6	KT81	10/6	PL36	9/6	UBCA1	6/6	XH1-5	5/6
6AS7	25/6	6J7GT	8/6	7Y4	8/-	22P5	12/-	807	7/9	DL96	6/6	ECP89	5/6	KT88	28/6	PL81	7/6	UBC81	7/6	XH1-5	5/6
6AT8	3/6	6K6GT	5/-	8B6G	8/-	23A8	14/6	813	80/-	DM70	5/-	EP11	6/6	KTW61	4/3	PL870	5/6	UBC90	5/6	XG1-5	10/-
6AU0	6/-	6K7M	5/-	10C1	12/6	25L6GT	4/6	866	10/-	DY86	7/6	EP50	2/6	KTZ41	8/6	PL83	6/6	UBC90	5/6	XG1-5	10/-
6B84	2/-	6K7G	1/3	10C2	12/6	25V5	4/6	954	4/-	DY87	7/6	EP80	4/6	ML4	17/6	PL84	6/6	UC084	8/6	XG1-5	10/-
6BA5	4/6	6K7GT	4/6	10P1	12/6	25Z4	6/3	1823	5/6	EY88C	14/-	EP85	4/6	ML6	12/6	PL500	14/6	UC085	6/6	XFP7	12/6
6BE6	4/9	6K8M	8/6	10P3	15/-	25Z5	7/-	402A	15/-	FAG0	2/-	EP86	6/6	MH14	12/6	PN4	13/6	UCP80	3/6	XFP1	5/6
6BH6	7/-	6KR4	3/-	10P9	9/6	27G3	10/6	5763	10/6	EABCS0	5/6	EP89	4/-	MU14	4/-	PN43	3/6	UCF42	7/6	CV1526	40/-
6R6	6/6	6K8GT	8/3	10F18	9/-	2817	5/6	7193	1/6	EAF42	7/6	EP91	2/9	NX40	12/6	PN51	6/6	UCB81	6/6	ACH13	6/6
6BQ7A	7/6	6K25	20/-	10L1	10/-	30C1	6/6	7475	2/6	EAP41	4/6	EP92	2/6	N37	10/6	PN52	5/6	UCL82	7/8	...	£3.0.0

SPECIAL 24 HOUR SERVICE
 OBSOLETE TYPES A SPECIALITY
 QUOTATIONS FOR ANY VALVE NOT LISTED
 Postage 6d. per Valve. C.W.O. No C.O.D.
 Send S.A.E. for list


Special 24 Hour
 Express Mail
 Order Service

SETS OF VALVES
 DAF91, DF91, DK91, DL92, DL94 ... Set of 4. 19/-
 DAF96, DF96, DK96, DL96 ... Set of 4. 25/-
 BRAND NEW TRANSISTORS
 OC35 9/6 OC72 6/- OC81D 4/-
 OC44 9/6 OC81 6/- OC82 6/-
 OC45 9/6 OC81m/pr 12/6 OC82D 6/-
 OCT1 4/6

Just published . . . a comprehensive guide for all interested in — or concerned with — transistors . . .

TRANSISTOR POCKET BOOK

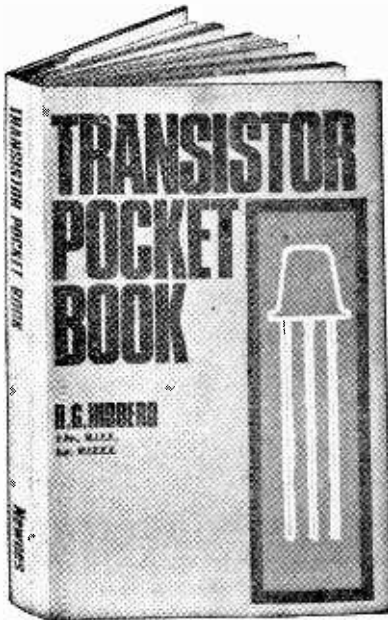by **R. G. Hibberd**
B.Sc., N.I.E.E., Sen.M.I.E.E.E.




This addition to Newnes' series of technical pocket books provides a comprehensive guide to the characteristics and use of the various types of transistor that have come into use in recent years. It is based on the junction transistor, fully taking into account the latest varieties including the epitaxial planar, field effect, metal-oxide silicon and thin film types.

Early chapters describe the principles of operation, transistor characteristics, equivalent circuits and parameters and establishing suitable d.c. operating conditions. A chapter is included on the manufacture of transistors, so that the effect of the basic methods of fabrication and types of junction on transistor characteristics is clearly understood. The operation and characteristics of associated semiconductor devices used in conjunction with transistors, such as the junction rectifier, silicon controlled rectifier, zener diode, tunnel diode, varactor diode and phototransistor are also described. Low level, high power and high frequency amplification; oscillator, switch and d.c. amplifier circuits; radio receivers and power supply arrangements are all covered in separate chapters, practical circuits complete with transistor types and component values being included for these various applications. The book also includes notes on handling and testing transistors, and a chapter on solid state circuit techniques.

Fully Covers

Historical Introduction; Basic Principles; Transistor Characteristics; Transistor Technology; Associated Semiconductor Devices; Transistor Equivalent Circuits and Parameters; D.C. Operating Conditions; Low Level Low Frequency Amplifiers; High Power Audio Amplifiers; High Frequency Amplifiers; Transistor Oscillators; Transistor Radio Receivers; The Transistor as a Switch; D.C. Amplifiers; Power Supplies; Use and Handling of Transistors; Solid Circuit Techniques; Recent Developments.

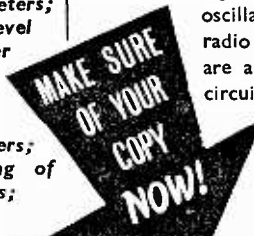

312 pages
220 illustrations
7 tables

only 25s. from
All BOOKSELLERS
or complete this coupon and post today

Published by
NEWNES

SEND NO MONEY NOW!

To **ODHAMS BOOKS DEPT. SF.330,**
Basted, Sevenoaks, Kent

Without obligation reserve me "TRANSISTOR
POCKET BOOK" and send special invoice with
100% Satisfaction or No Charge Guarantee.

BLOCK LETTERS BELOW


NAME

Full Postal Address.....

.....

ADAMIN Micro Soldering Instruments

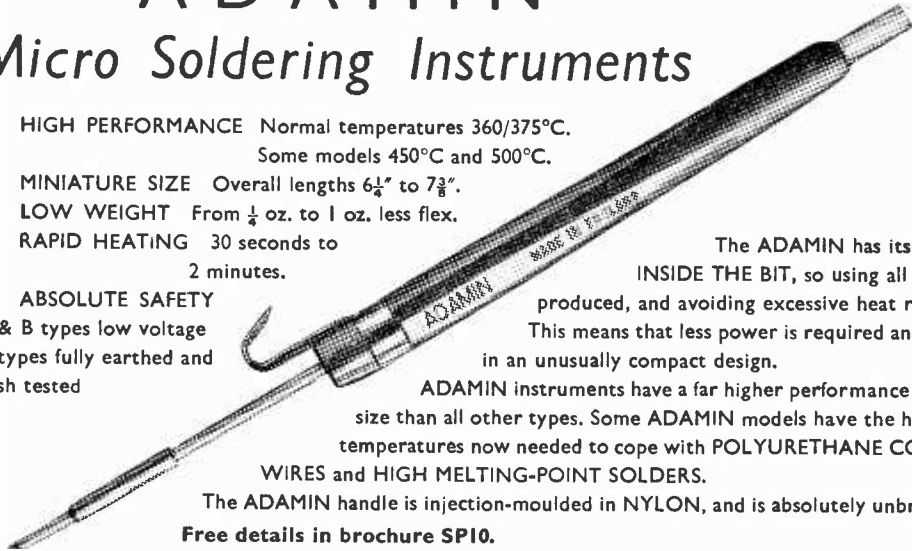- HIGH PERFORMANCE Normal temperatures 360/375°C. Some models 450°C and 500°C.
- MINIATURE SIZE Overall lengths 6¼" to 7⅜".
- LOW WEIGHT From ¼ oz. to 1 oz. less flex.
- RAPID HEATING 30 seconds to 2 minutes.
- ABSOLUTE SAFETY A & B types low voltage C types fully earthed and flash tested



The ADAMIN has its element INSIDE THE BIT, so using all the heat produced, and avoiding excessive heat radiation. This means that less power is required and results in an unusually compact design.

ADAMIN instruments have a far higher performance for their size than all other types. Some ADAMIN models have the higher bit temperatures now needed to cope with POLYURETHANE COVERED WIRES and HIGH MELTING-POINT SOLDERS.

The ADAMIN handle is injection-moulded in NYLON, and is absolutely unbreakable. Free details in brochure SP10.

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, Surrey.

Telephone: CROydon 8589

RADIO CLEARANCE LTD.

27 TOTTENHAM COURT ROAD, LONDON W.1. Telephone: MUSEum 9188
Bulk enquiries invited. The oldest component specialists in the trade. Est. 35 yrs.

LOUDSPEAKER BARGAINS STILL AVAILABLE

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at the LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOU-SPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY

Size in inches	Gauss in	Imped. ohms	Price	Size in inches	Gauss in	Imped. ohms	Price	Size in inches	Gauss in	Imped. ohms	Price
2	7000	80	8/-	3½	9500	3	10/6	4	9500	25	11/6
2½	7000	35	8/6	3½	7000	35	8/6	5	7000	3	8/6
2½	7000	50	8/6	3½	9500	50	10/6	5	7500	3	9/-
2½	7000	80	9/-	4	4000	35	11/-	5	9500	15	12/6
3	8500	3	10/-	4	7000	35	11/-	5	9500	15	12/6
3	7000	5	9/-	4	7500	5	9/6	5	8500	25	10/6
3	7000	35	9/-	4	9000	50	11/6	6½	7000	3	11/-
3	6500	50	9/6	4	9500	35	11/6				
3½	9000	15	10/-	4	9500	15	12/-				
3½	7000	3	9/6								
5 x 3	9000	35	12/-	7 x 3½	7000	3	9/6	8 x 2½	6000	3	8/6
5 x 3	7000	3	8/-	7 x 3½	9500	3	10/6	8 x 2½	7000	5	9/-
3 x 3	9000	3	8/6	7 x 3½	8500	3	11/6	8 x 2½	9500	3	10/-
6 x 4	9500	3	9/-	7 x 4	9500	3	11/-	8 x 2½	9500	3	10/-
6 x 4	8500	3	9/6	7 x 4	9500	30	12/6	10 x 6	11000	3	22/6
6 x 4	9500	3	10/-	7 x 4	10000	3	12/6	10 x 6	11000	5	22/6
6 x 4	9500	35	12/-	7 x 4	12000	3	12/6	10 x 6	11000	25	22/6

ALLOW 2/6 each Speaker for postage and packing and handling charge and please specify the exact requirements—the nearest available will be sent.

SELECTED BARGAINS

Beautifully geared AM/FM 2-gang Condensers 4/6c. AM/FM IFT'S 465 ko/s and 10.7 Mc/s 4/8 pair; Magnavox Crystal Tape Recorder Mikes, 12/6; 3 watt Stereo Amplifiers complete, ready to switch on. 79/6; Sentercell rectifiers R3/2D-D3-2-1-Y. 2/6 each. DIODES—OA79, OA90, CG46H, GD10. 2/- each. TRANSISTORS: OC45 4/6, PXA101, 3/9, AF115, 4/6. Sub min. Germanium diode 1/3. Mi diode 6/1, each. Silicon diodes, 400 p.v., 330mA, 2/6 each, please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogue—our stocks move too quickly! Kindly make provision for additional postage and package charge to avoid delay. Terms: Cash With Order or C.O.D. on Orders over 10/-.



The PUNCH you need!

HOLE PUNCHES

Instant Type	diameter
Instant Type	6/10 ea
Screw-up Type
1½" diameter Toggle switch	8/6 ..
"	8/6 ..
"	B7G	9/- ..
"	8BA, 89A	9/6 ..
"	10/2 ..
"	10/8 ..
"	11/8 ..
1½" diameter Int. Octal	13/4 ..
1½"	16/2 ..
1½"	18/10 ..
1½" ..	B9G	21/8 ..
1½"	24/4 ..
2½" ..	Meter	33/2 ..

Complete Set £9.3.6.

No extra charge for postage and packing in the U.K.

Now supplied by

TOMPKINS & LONGMAN LTD.

237 GIPSY ROAD

WEST NORWOOD, SE.27

Tel. Gipsy Hill 5000

Head Office and Warehouse:
44A WESTBOURNE GROVE
LONDON W2
Tel.: PARK 5641/2/3
Please write for full catalogue

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office
When sending cash with order, please include 2/6 in 4 for postage and handling
MINIMUM CHARGE 1/6. No C.O.D. orders accepted

Retail Shop:
85 TOTTENHAM COURT
LONDON W1
Tel.: LANGHAM 8403
Open all day Saturday

Table of electronic components with columns for part numbers (e.g., OAZ, OA3, OB2) and their specifications.

First Quality Fully Guaranteed



ELECTRONIC VALVES

Detailed table of electronic valves with columns for part numbers, descriptions, and specifications.

TRANSISTORS section listing various transistor models and their characteristics.

GERMANIUM DIODES section listing diode models and their specifications.

ZENER DIODES section listing zener diode models and their specifications.

SILICON BRIDGE CONDENSER POWER RECTIFIERS, 100 P.I.V.
1B20K10, 2 amps DC (100V) 25/-
1B40K10, 4 amps DC (100V) 35/-
1B80K10, 8 amps DC (100V) 55/-

PRACTICAL WIRELESS

blueprints

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-FEATURE BLUEPRINTS

The Strand Amplifier }	5/-
The PW Signal Generator }	
The Savoy VHF Tuner }	5/-
The Mayfair Pre-amplifier }	
The Berkeley Loudspeaker Enclosure }	5/-
The Luxembourg Tuner }	
The PW Troubadour }	7/6
The PW Everest Tuner }	
The PW Britannic Two }	6/-
The PW Mercury Six }	
Beginner's Short Wave Two }	5/-
S.W. Listener's Guide }	
Beginner's 10-watt Transmitter }	5/-
Transmitting and Aerial Data... .. }	
PW "Sixteen" Multirange Meter }	5/-
Test Meter Applications Chart }	
The Celeste 7-transistor Portable Radio }	5/-
The Spinette Record Player }	
Transistor Radio Mains Unit }	5/-
7 Mc/s Transceiver }	

SINGLE-FEATURE BLUEPRINTS

The Tutor }	3/-
The Citizen }	5/-
The PW Pocket Superhet }	5/-
The PW 35-watt Guitar Amplifier }	5/-
The Mini-amp }	5/-
The PT Multimeter }	5/-
The Autocrat Car Radio }	5/-
The Beginner's Short Wave Superhet }	5/-
The Empire 7 Three-band Receiver }	5/-
Electronic Hawaiian Guitar }	5/-

PLEASE NOTE that we can supply no blueprints other than those shown in the above list. Nor are we able to supply service sheets for commercial radio, TV or audio equipment.

QUERY SERVICE

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 3rd February, 1966 and must accompany all queries in accordance with the rules of our Query Service.




PRACTICAL WIRELESS, FEBRUARY, 1966

NEW 1966 CATALOGUE 150 PAGES

Fully detailed and illustrated components, equipment and Hi-Fi. All types and makes. 5000 Stock lines. The Finest Range available. A mine of information. Price 6/- post paid.

FREE with Catalogue, 6/- Discount vouchers gives 2/- in pound discount on purchases.

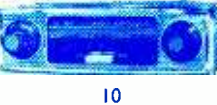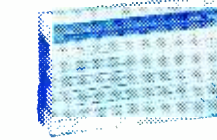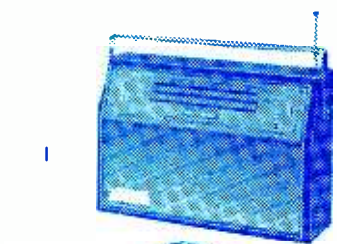CATALOGUE COSTS NOTHING AFTER USING VOUCHERS



HENRY'S RADIO LTD.
303 EDGWARE ROAD, LONDON W2
PADDDington 1008/9
Open Mon. to Sat. 9-6. Thurs. 1 p.m.
Open all day Saturday.

(1) **GLOBEMASTER MW/LW/SW PORTABLE**
Full 3-waveband tuning. Pushbutton wavechange. Superhet printed circuit. Black-chromed cabinet 11 x 7½ x 3½ in. (SVV 17-50 metres). Ear/Record sockets.
TOTAL COST £8.19.6 P.P. 2/6.
TO BUILD 3/6.

(6) **VHF FM TUNER**
87/105 Mc/s Transistor Superhet. Geared tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3½ x 2½ in.
TOTAL COST £6.19.6 P.P. 2/6.
(Cabinet Assembly 20/- extra)

10 AND 20 WATT TRANSISTOR MONO AND STEREO HI-FI UNITS

(2) **POWER AMPLIFIERS.** 10 watts RMS output. 100mV input. 30cs to 20kc/s ±1dB. 6 transistor. Push-pull. Panel size 4 x 2½ x 1 in. H/S 4 x 4 in. **TPA10** 3 3-5 ohm spkr. £5.10.0, p.p. 2/6
TPA10/15 12-16 ohm spkr. £5.19.6, p.p. 2/6
(Mains unit for 1 or 2 amplifiers, 5/9.6, p.p. 2/6)

(3) **PREAMPLIFIERS.** 8 input selector. Treble, bass, volume, filter controls. 1½mV to 300mV inputs. Battery operated or from Mains Unit. Output up to 150mV RMS.
MP2 Mono 9½ x 2½ x 2 in. £5.10.0, p.p. 2/6 (brown or gold front panel 8/6).
SP4 Mono/Stereo, 9 x 3½ x 1½ in. £10.19.6, p.p. 3/6 (front panel plate 12/6)

The Finest High Fidelity at Unbeatable Prices

● ALL UNITS BUILT AND TESTED

(4) **TRANSMITTER/RECEIVERS**
★ Up to ½-mile range £7.19.6, p.p. 2/6 per pair
★ Up to 5 mile range £22.10.0, p.p. 3/6 per pair.

HI-FI WE CAN NOW SUPPLY FROM STOCK ALL MAKES OF HIGH FIDELITY EQUIPMENT (Hi-Fi Room opening shortly)

(9) **MICROPHONES**
★ Professional 50K ohms Dm301 79/6
★ 50k Stick Dm107, Dynamic 69/6
★ 100c Xtal Stick with stand 32/6
★ BM3 Stick Mic. 37/6

(5) **BUILD A TAPE RECORDER**
Three speeds—3 watts. Complete kits with new "363" decks. Supplied as preassembled sections. Complete with portable cabinets and Speaker—excellent quality.
★ **TWO TRACK** ★ **FOUR TRACK**
£26 P.P. 8/6 **£30 P.P. 8/6**

(7) **5 WATT AMPLIFIER**
6-Transistor Push-pull, 3 ohms. 6mV into 1K. 12/18V supply. 2½ x 2 x 1½ in.
BUILT AND TESTED 79/6 P.P. (optional mains units 54/- p.p. 2/-)
New matching Preamplifier, 6 inputs, treble/bass selector/volume controls. 6-10mV o/put. 9-18V supply. 79/6, p.p. 2/-

(8) **REGENT-6 MW/LW POCKET RADIO**
6-transistor superhet. Geared tuning. Push-pull output. Moulded cabinet 5 x 3 x 1½ in. Phone socket.
TOTAL COST 85/- P.P. 2/6.
TO BUILD

MULTI-METERS
PT34 1kV 39/6 TP55 20kV £5.19.6
M1 2kV 49/6 EP30k 30kV £6.10.0
TP10 2kV 75/- EP50k 50kV £8.15.0
EPI0k 10kV 79/6 500 30kV £8.17.6
ITI-2 20kV 89/6 EPI00k 100kV £10.10.0
EP20k 10kV 99/6

FREE Lists on request.
★ 12 page. Transistor, SCR, diode, lightcell, quartz crystal, valve, heat sink, Zener catalogue and 4 page short catalogue of units.

(10) **ROADSTER MW/LW CAR RADIO**
Supplied as Preassembled Panels. Permeability tuned superhet. Push-button wave-changer. Push-pull output. Fits any car. 7 x 4 x 2 in. 12 volt (-) earth.
ASSEMBLY TOTAL COST £8.19.6 P.P. 3/6.
(Speaker/Baffle/Car Fixing Kit, 20/-)

SINCLAIR KITS
Micro FM (VHF) Kit ... £5.19.6
Micro 6 (MW) Kit ... £2.19.6
Slimline (MW) Kit ... £2.9.6
X10 Built } Mains unit ... £6.19.6
X10 Kit } 54/- ... £5.15.6
X20 Built } Mains unit ... £9.19.6
X20 Kit } 99/6 ... £7.19.6

● LET US QUOTE FOR PARTS FOR YOUR CIRCUIT. SEND LIST OF PARTS FOR QUICK REPLY. MOST PARTS IN STOCK FOR ALL PUBLISHED DESIGNS.

***PROVED AND TESTED DESIGNS— FULLY GUARANTEED**