

PRACTICAL WIRELESS

MAY
1971

20p (4'10)

NEW SERIES... **SERVICING** AN INTRODUCTION
TO FAULT-FINDING

'STATION FOCUS'
SIX
RECEIVER



ALSO:

10W AUDIO AMPLIFIER
HI-FI SIGNAL GENERATOR






ADCOLA Soldering Instruments add to your efficiency

ADCOLA 64 for Factory Bench Line Assembly





A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*. Standard temp. 360°C at 23 watts. Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

-  B'38 $\frac{1}{8}$ " — 3.2 mm CHISEL FACE
-  B 14 $\frac{3}{16}$ " — 2.4 mm CHISEL FACE
-  B 24 $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE
-  B 12 $\frac{3}{16}$ " — 4.75 mm EYELET BIT
-  B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

LONG LIFE

-  B 42 LL $\frac{1}{4}$ " — 4.75 mm CHISEL FACE
-  B 38 LL $\frac{1}{8}$ " — 3.2 mm CHISEL FACE
-  B 14 LL $\frac{3}{16}$ " — 2.4 mm CHISEL FACE
-  B 44 LL $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.




* Write for price list and catalogue

ADCOLA PRODUCTS LTD.,
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0201/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851



JACKSONS NEW AIRTUNE E


(C804E)

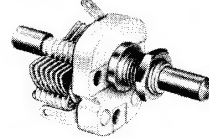

An old friend in a new guise
With spindle extended for ganging
No substitute when you need

VERSATILITY

Like this for instance:-

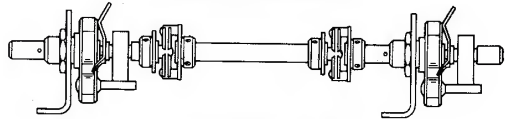

Front Area $\frac{1}{8}$ " \times $\frac{1}{4}$ "
Capacitance 25, 50, 100 or 150p
Low Minimum Capacitance

JACKSON BROS (LONDON) LTD.,
Kingsway, Waddon, Croydon CR9 4DG. Tel: (01)-688 2754/5
U.S. Office: M. Swedgal, 258 Broadway, New York, N.Y. 10007



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price **75p**



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price **75p**



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	15p*
Size 5 (illustrated)	Savbit	18	15p*
15	60/40	22	20p*

*Recommended Price



INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER, easily

adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price **50p**



From Electrical and Hardware shops. If unobtainable, write to:
Multicore Solders Ltd., Hemel Hempstead, Herts.

Selections from FELSTEAD ELECTRONICS' List

(Sent free for stamped addressed envelope to address below)

Transistors etc. AC126 124p. AF116 15p. A116 15p. AF117 20p. OA5 74p. OA10 74p. OA81 74p. OA85 74p. OC23 324p. OC25 30p. OC26 374p. OC28 424p. OC33 424p. OC44 14p. OC45 124p. OC71 124p. OC72 124p. OC75 124p. OC81 124p. OC81D 124p. OC82D 124p. OC170 20p. OC171 124p. Many more in list. S.D.R. BY100 800piv 14p. 6 amp series: BY213 300piv 20p. BY212 600piv 25p. BY211 900piv 30p. BY210 1200piv 35p. (Charges 64p. up to 11, plus for 12 and over). Sub-Min Transformers: OUTPUT (3 Ω for OC72, etc.) 14p. (up to 6 64p.). MULTIMETER. Our famous 2000 Ω per V £4-624 (15p.). Details and other in list. SOLDERING IRON. Slim, modern, British high-speed 52", all parts replaceable, highest quality, full guarantee: £10p. DIAMOND STYLII. Replacements for BSR TC8/LP, TC8/R, TC8/LP/STEREO; COLLARO 'O'; RONEITE BF 40LP; GARRARD GC2/LP and GC8/LP; ACOS GP65/67, all at 40p (6p). ACOS GP73, GP91; BSR ST4 (ST3, ST5), ST8 (ST9); SONOTONE 8TA, 9TA, 9TAHC; PHILIPS AG3306, 3060 (3063, 3066, 3301, 3302, 3304); Garrard (GK52) all at 75p. All are of the very highest quality. DOUBLE DIAMOND: ST4 (ST3, ST5), ST10 (ST9, ST8), 9TA, 9TAHC, 3306, GP91 (For GP92, GP93, GP94 cartridges); GP91SC for all GP91-SC Cartridges: All at £1-50 each (6p). PICK-UP CARTRIDGES All standard fittings and styli. MONO GP67/2 75p. STEREO-COMPATIBLE (MONO) GP31/SC (£1-05). STEREO GP93 £1-274. STEREO CERAMIC £1-924. SONOTONE STEREO 9TAHC (DIA) £2-374. GOLDRING G850 £4-874; G800 £8-50, G800E £13-50, G800 SUPER £19-50 (64p all types or Reg. Post 224p.). STYLII FOR ALL ABOVE TYPES, including GOLDRING available. RECORDING TAPE. Still the finest quality British Mylar available: Standard 5" 600 ft. 50p. 54" 900 ft. 50p. 7" 1200 ft. 56p. LONG PLAY 5" 900 ft. 50p. 54" 1200 ft. 56p. 7" 1800 ft. 90p. (74p on 5" and 54" 9p on 7"). MICROPHONES Crystal Mic 91, hand/desk 81p. MIC45 Curved metal handrip £1-00. CM21 Grey hand desk 524p. Stick '60' £1-024. CM70 "Planet" machined metal tapered stick type with neck cord, adaptor to fit floor stands £1-474 (all 9p) LAPEL (or hand) with clip 324p (6p). All are fitted with leads. Dynamic. Cream hand/cable MINY 74p (9p). M10K for desk, tapered stick type with swivel base and slide-out adaptor £1-974. MS11. Similar, but fixed on swivel swan neck to switch-fitted base £1-224 (Either 15p). Type 209 Cardioid ball, 50K/600 Ω, omni-dir., built-in vol. control, on/off switch, special lead, handle (as good as money can buy) £6-30. DM160. Non-Dir. Ball, 50K cable, adaptor £3-874 (274p either). MICROPHONE INSERTS. Dia. 1.75" OR 1.5" either size 274p. EARPIECES with lead & min. jack plug (2.5 or 3.5 mm., state which). Magnetic 9p. Crystal (3-5 only) 24p (Up to 3 for 60 on any). HEADPHONES De-luxe STEREO 8-16 Ohms, £2-474. Same, fitted vol. control each earpiece £4-20. Both have lead and stereo jack plug (174p). HIGH RES. 2000 ohm. Adjustable 924p. SPEAKERS. 12" ROUND fitted tweeter, 3 or 15 Ω (state which) £1-874 (274p) or for Stereo £4-25 pair, carr. paid, 24", 3 or 8 Ω (state which) 374p (6p). EMI 13" x 8", 3, 8 or 15 Ω (state which) £2-124 (25p) with single flared para. tweeter cone 8 or 15 Ω (state which) £2-274 (25p) with two tweeters and crossover network 8 or 15 Ω (state which) £3-75 (25p). VIBRATORS. Genuine Plessey 12V 4-pin non-synch. 121HD4, 24" ex. pins. 274p. Am. 12V 4-pin, non-synch. 7/16ths longer. 224p. 12V 7-pin Synch. (12SR) 624p (All types 64p per vibrator). CONNECTING WIRE. Packs of 5 coils asstd. cols. ea. coil 5yds. Solid core 14p (6p). Flexible 16p (74p). Super thin for transistor wiring 16p (6p). PICK-UP WIRE. Super thin twin flex, screened and shielded 6p yd. (6p up to 6yds.—over free). RETRACTABLE Flex. Leads. (Curlies) 6ft. phono plus ea. 224p. 12ft. 39p. 6ft. phono plus/phono socket other end 25p. 12ft. 424p. (6p per lead all types). BATTERY ELIMINATOR. 240V AC input 3, 6, 7 1/2 & 9V. DC output at 400 mA. Two switches, leads, pilot light and universal adaptor for all trans. appliances including all makes cassette tape recorders and players £3-15 (24p). SEND SAE for full free lists—Teletext and small 3W and 74W trans. amplifiers. Electrolytics, Vol. controls, all types of radio switches, car and portable expanding aerials, Meters, Test prods, all types of Brit. & Cont standard and min. plug and sockets, SDR's Thyristors, croc. clips (various terminals, etc. etc. and many "Special Offer" lines at lowest possible prices.

BRAND NEW

SGS/FAIRCHILD SILICON NPN TRANSISTORS.

BD 112 AUDIO	80 volts	20 watts	TO3 32p.	(10 for £2-50)
BD 116 AUDIO	80 "	20 "	TO3 45p.	(10 for £4-00)
CP400 REGULATOR	40 "	15 "	TO3 374p.	
CP401 REGULATOR	60 "	15 "	TO3 374p.	
CP402 REGULATOR	100 "	15 "	TO3 424p.	
CP404 AUDIO	80 "	15 "	TO3 374p.	
CP430/431 AUDIO	100 "	30 "	TO3 374p.	
CP433 AUDIO	120 "	40 "	TO3 424p.	
CP702 AUDIO	60 "	15 "	TO3 374p.	
CP704 RF or SERVO	80 "	30 "	TO3 474p.	
BLY68 AUDIO	100 "	25 "	TO3 50p.	
BLY72 HIGH POWER	80 "	100 "	75p	
CP703 HIGH CURRENT RELAY	60 volts	5 watts	224p.	
BFW76 MICROWAVE OSCILLATOR	4GHZ 30 volts	1 watt	£1-00	
2N3646 HIGH SPEED SWITCH	40 volt 1/2 amp	224p.		
2N4075 AUDIO	100 volts	30 watts	55p	
2N4076 AUDIO	100 "	30 "	45p	

VARIACAP UNDES
BBY10 6.8p. BBY11 10p. BBY12 12p. 25p each
INTEGRATED CIRCUITS. FLAT PACKS.
U6A 998979X. 4 CASCADE BINARY. 75p.
U3T 77119X. DUAL DIFFERENTIAL COMPARATOR 75p.
U3L 771239X DC AMP. up to 30 MHz. 75p.
U31.993151X. CLOCKED FLIP FLOP. 624p.
CHARGES: -64p up to 11, plus for 12 and over.

FELSTEAD ELECTRONICS (PW)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE
Cash for order only. No COD or Cash Service. Charges (Min. 16) in brackets after all items. Reprint Orders under 25p excluding postage, unacceptable. SAE please for enquiries or cannot be replied to. Changes apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).

NOW AVAILABLE LASKY'S AUDIO TRONICS CATALOGUE 1971

THERE'S MORE &
MORE & MORE
FOR EVERYONE!

The great new 1971 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 44 newspaper size pages—many in full colour—are packed with 1000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast. Electronics Hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories and introduces LASKY'S AUDIO TRONICS CREDIT CARD SCHEME offering holders one months interest free credit up to £50. Send your name and address 15p for post and inclusion on our regular mailing list.

LASKY'S LTD., (Dpt. P.W.)
3-15 CAVELL STREET
LONDON. E1 2BN



FANTASTIC BARGAIN OFFER! TRANSEUROPEAN

Transistorised Stereophonic High Fidelity
AM/FM Tuner Amplifier System.



This system includes this elegantly styled solid state Teak finished cabinet tuner/amplifier. Covering VHF/FM, Medium and long wavebands. The latest 4 Speed B.S.R. Mono/Stereo record changer with 2-10in. x 6in. matching elliptical speakers. A complete Hi-Fi Stereo Radiogram at less than half normal price.

Easily fitted no technical knowledge necessary.

SPECIAL OFFER

£44

P. & P. 88p

Credit Terms available. First monthly payment of £5-83 followed by 9 monthly payments of £4-95. Total Credit Sale Price £49-50. Send £5-83 today.

FABULOUS VALUE

Transistorised Stereo Hi-Fi Record Player. Build your own Hi-Fi Record Player with the Sorenson Transistorised amplifier which comes complete with 2-10in. x 6in. speakers and the latest 4 Speed BSR Speed Stereo/Mono Record Changer.

£30 P. & P. lowered by 9 monthly payments of £3-38. (Total 88p c/s price £33-08). Send £4-26 today.

EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED.

CALLERS WELCOME
PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Post coupon NOW for...
FREE leaflets

Name P.871
Address

LEWIS radio 100, Chase Side London N.14
Tel: 01-886 3733/9666

FIND BURIED TREASURE! TREASURE LOCATOR FULLY TRANSISTORIZED

NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorized metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits its inside—no connections needed.



ONLY
£2.37
(47/6)

FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC. ETC. Outdoors or indoors. Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderfully clear, easy to follow step-by-step, fully illustrated instructions—it really is easy as A.B.C. Fully transistorized—no valves, A.C. or D.C. power, PP3 battery. No soldering necessary. Size of detector head 13" x 10" x 2". Great demand expected at this remarkably low price—ORDER WHILE PRESENT STOCKS LAST. All parts including detector head case, nuts, screws, wire, simple instructions etc. etc. ONLY £2.37 (47/6) + 23p (4/6) p. & p. (Telescopic handle as illustrated £1.75 (35/-) extra). Parts available separately. Made up looks worth £15!

MAKE 5 PROJECTS INCLUDING 3 TRANSISTOR LOUDSPEAKER RADIO




TOTAL BUILDING PRICE
£1.97
(39/6)

Amazing Radio Construction set! Become a radio expert for £1.97 (39/6). A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated

Step-by-step Plans, all Transistors, loud speaker, personal phone, knobs, screws, etc., all you need. Presentation Box 37p (7/6) extra as illus. if required (extra parts available separately). Send only £1.97 (39/6) + 23p (4/6) p. & p

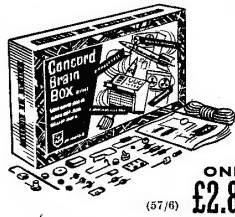"READ PEOPLE'S MINDS"—TEST THEIR NERVES —BEAT THEM AT CARDS—TEST THEIR MENTAL ABILITY, ETC. WITH THIS ASTONISHING ELECTRONIC BRAIN-BOX



ONLY
£2.87
(57/6)


If you've seen a giant computer on show at an electronics exhibition, you will have seen people of all ages queuing to pit their abilities against the giant electronic brain. There is a tremendous fascination that attracts ordinary people and professional engineers alike to electronic games of skill, chance and mystery. With this "Brain-box" you will be able to perform mind-boggling feats. THE MIND READING DEVICE will make people swear you have "telepathic" powers. THE AMAZING CARD TRICK UNIT completely mystifies and baffles from one to six people. You correctly "guess" the two cards each person has selected at random from a pack they themselves shuffled. THE ELECTRONICS NERVES TESTER

puts your friends to a very lively test. It gives out fail and finish signals (the winner is the person with lowest number of fail signals.) Can be adjusted from the weakest to strongest person. THE ELECTRONIC MAZE tests the mental ability of the player because it uses psychology with an electronic twist to it. You can change the maze pathways in seconds to prevent the maze becoming too stale after lots of use. Completely safe and foolproof. Size 18" x 12" x 6" (Max.). You can play all these games and more besides after building the "Brain box". WE GUARANTEE THAT ANYONE FROM NINE TO NINETY CAN EASILY ASSEMBLE ALL THESE PROJECTS IN UNDER ONE HOUR! You can't go wrong, no soldering, you get pictorial, easy as a.b.c. step-by-step stylis, signalling lights, wire, nuts, screws etc. etc. Uses standard battery. Presentation Box simple instructions. ONLY £2.87 (57/6) + 33p (6/6) p. & p. for all parts including chassis, switches 37p (7/6) extra as illus. if reqd. (PARTS AVAILABLE SEPARATELY) FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.

EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS

—JUST OUT V.H.F. AIRCRAFT BAND CONVERTER

ONLY
£2.37
(47/6)

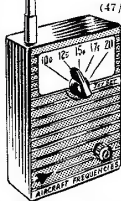


Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES, Eavesdrop on exciting conversation between pilots, ground approach, ground control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk-downs. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, KINGWY, PRESTWICK ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/2". All you do is extend rod aerial, place close to any ordinary medium-wave radio—(even tiny portables) NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN. SEND NOW. ONLY £2.37 (47/6) + 23p (4/6) p. & p. for all parts, including case, nuts, screws, wire, etc. etc. (parts available separately).

SHORTWAVE TRANSISTOR RADIO


Can be built in one evening

At last! After trying countless circuits searching for easy build, work first-time short wave. Giving advanced world-wide performance, we chose this "Sky Roma". Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and every one worked perfectly—no soldering necessary). 75 stations on rod aerial in 30 mins.—RUSTIA, Africa, USA, SWITZERLAND, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorised (no valves). Size only 8" x 4 1/2" x 1 1/2". As tremendous demand anticipated price held to only £2.25 (45/-) + 17p (3/6) p. & p. for all parts incl. Cabinet, screws, instr. etc. (Parts available separately).

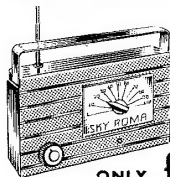

ONLY
£2.25
(45/-)

REAL WORKING ELECTRONIC ORGAN

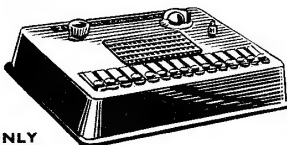

ONLY
£2.75
(55/-)

Anyone from nine years upwards can build it easily in one short evening following the fully illustrated, step-by-step, simply worded instructions. BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT at our low, low building price. ONLY £2.75 (55/-) + 23p (4/6) p. & p. for all parts, including case, loudspeaker transistors, condenser, resistors, knobs, transformer, volume control, wire, nuts, screws, simple (but full) instructions, etc. etc. Uses standard PP3 battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorized—no valves. Proper self-contained loudspeaker. Fifteen separate keys upon two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 18 1/2" x 10" x 2 1/2". You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. Take it anywhere—play it anywhere, NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER. No soldering necessary. It really is as simple as a.b.c. to make.

AMAZING TRANSISTORIZED CIGARETTE RADIO


Yes, a perfectly ordinary packet of cigarettes! But watch your friends astonishment on hearing its range of stations loud and clear. Holds 10 cigarettes yet conceals sensitive, fully transistorized circuit (including tiny battery). A young boy can assemble it in under 2 hours. No soldering. Only 16 connections to make. ALL PARTS including semiconductors. Simple as ABC Illustrated Plans, etc. ONLY £1.47 (29/6) + 13p (2/6) p. & p. Parts available separately.

TOTAL BUILDING PRICE
£1.47
(29/6)



UNIQUE RADIO FOR BEDROOM OR OFFICE

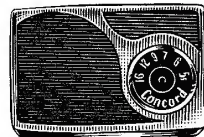No batteries, ONLY
no electricity, 97p
never wears out
(19/6)



Tune in your favourite programmes or the news, or sports in the Office or in your bedroom. Uses sensitive, germanium diode originally evolved from Wartime radar. Never bit a battery. Never use electricity. Never replace. Covers all medium waves. Clear beautiful tone. Size 4 1/2" x 2 1/2" x 1 1/2". In beautiful case. ONLY 7 CONNECTIONS AND IT'S WORKING. No soldering necessary. CAN BE BUILT ALMOST BLINDFOLDED IN UNDER 15 MINUTES! Ideal for absolute beginner from 8 years of age upwards. SPECIAL PRICE TO CLEAR STOCKS OF COMPONENTS, ONLY 97p (19/6) + 13p (2/6) p. & p. for all parts including beautiful case. Germanium semiconductor, tuning condenser, personal phone, wire, nuts, screws. SIMPLE AS A.B.C. INSTRUCTIONS. (Parts available separately).

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

CONCORD ELECTRONICS LTD (Dept. PW19)

8 Westbourne Grove, London W.2.
(Nr Bayswater & Queensway Tubes. 1 minute ABC Cinema)
Callers Welcome 9 a.m.-6 p.m. inc. Saturday

ARMSTRONG • TELETON • CONNOISSEUR • KOSS • APOLLO • SHURE • CELESTION

GARRARD

PRICES SLASHED! 55% BY UP TO 0%

GOLDRING

SME • LOWTHER • SINCLAIR • FERROGRAPH • STE-MA • THORENS • BRYAN • PHILIPS • KEF ETC

WHY PAY MORE? ALL GOODS ARE BRAND NEW & FULLY GUARANTEED FOR 12 MONTHS



SUPERB PLYNTHS AND COVERS as illustrated

Suitable for Garrard A760, SP25, 2000, 2500, 3000, 3500, 5100, 2025, 1025, SL65B and B.S.R. McDonald range. Superbly finished plynth, ready cut for use (fully assembled). Complete with tinted perspex cover. This unit is finished in Teak polish and will blend in any home. Please state deck when ordering.
PLUS
£3-50 50p P & P
SUPERIOR PLYNTHS AND COVERS for Garrard AP75, AP76, SL72B, SL75B and SL95B £4.95 +80p p & p (Recommended list price £10-90).

A COMPLETE STEREO SYSTEM FOR ONLY £37-80

+ £1-25 p. & p.

It's performance can be compared with equipment costing at least £130. **GUARANTEED 12 MONTHS** and 100% MADE IN ENGLAND. For full details and specifications, see March issue, Page 889.

VISIT OUR 3 STOREY WAREHOUSE PACKED WITH HI-FI & STEREO EQUIPMENT. 1000's OF ITEMS ALWAYS AVAILABLE TO SELECT FROM.

2 SHOWROOMS DEVOTED TO DEMONSTRATING SPECIALLY SELECTED SYSTEMS

TURNTABLES p.p. 60p

GARRARD 5100 with Cartridge	£7.97
GARRARD 2025 TC with Sonatone 9TAHC Diamond Cart	£8.50
GARRARD 3000 with Sonatone 9TAHC Diamond Cart	£9.50
GARRARD A70MKII	£10.97
GARRARD SP25 MK3	£10.97
GARRARD SL65B	£12.75
GARRARD AP76	£13.97
GARRARD SL72B	£25.00
GARRARD SL75B	£27.97
GARRARD 401	£27.50
GARRARD SL95B	£36.00
THORENS TD125	£61.00

PICK UP ARMS pp. 35p

SME 3009/S2	£25.50
SME 30012/S2	£27.50
GOLDRING Lenco L75	£9.99
GOLDRING Lenco L69	£6.75

STEREO AMPLIFIERS p.p. 50p

H.I. 6207 with Scratch Filter	£19.00
METRO SOUND 1720	£26.00
AMSTRAD 8000	£20.97
TELETON SAQ206	£18.97
SINCLAIR 3000	£34.00
SINCLAIR 2000	£23.30
SINCLAIR PRO 60/2 Z30/PZ5	£15.97
QUAD 303 & 33	£87.00
ARMSTRONG 521 (Teak case)	£43.50

SAN SUYI DUETTE now in stock special price on application.

TUNER AMPLIFIERS pp. 75p

TELETON MX990 WITH SPKS	£48.50
TELETON R8000 WITH SPKS	£47.50
TELETON CR10T WITH SPKS	£29.00
TELETON TFS50	£53.50
TELETON 7A71	£51.00
TELETON CR55	£90.00
TELETON 10A71	£105.00
TELETON 7A720	£78.00
PHILIPS RH781	£54.00
ARMSTRONG M8 Decoder	£7.00
ARMSTRONG 825	£74.00
ARMSTRONG 826	£82.50

TUNERS p.p. 50p

TELETON GT101	£32.97
TELETON RTQ204X	£38.97
SINCLAIR 2000	£19.00
SINCLAIR PRO 60	£20.50
ARMSTRONG 823 AM/FM	£42.00
ARMSTRONG 824	£32.00
ARMSTRONG M8 Decoder	£7.00

SAN SUYI DUETTE now in stock

PERSONAL CALLERS WELCOME. We are always available to advise on the best system to suit your need and pocket.

OUR OWN CAR PARK (at rear)
 You have no parking problems when you pay us a visit.

UNBEATABLE VALUE
 The largest and best quality range of stock at **LOWEST POSSIBLE PRICES** is usually available.

The prices shown are current at the time of going to press but are liable to alteration. They supercede any previous offer.

Send Postal Orders, Money Orders, Cheques, etc. to For information only send stamped addressed envelope

AUDIO SUPPLIES (PW5) 50 STAMFORD HILL LONDON, N.16 (The A.10)
 Open 9.30 a.m.-6 p.m. Monday to Saturdays. (Fridays to 8.30 p.m.) EASY TO FIND. Tel: 01-806 3611
 50 yards from (B.R.) Stoke Newington Station. 67, 149, 247, 76, 243 Buses pass our door.

Personal callers please note that cheques are only accepted if accompanied by a bank cheque card. (NOT BARCLAY CARDS)

CARTRIDGES (p. & p. 12½p.)

GOLDRING G850	£4-20
GOLDRING G800	£6-99
GOLDRING G800E	£11-00
GOLDRING G300 super E	£16-00
SONOTONE 9TAHC	£1-75
SHURE M3d	£4-95
SHURE M4497/c	£7-20
SHURE M55	£9-20
SHURE M75E/11	£15-00
SHURE M44E	£8-50

SCOOP BUY
SMC-101 MOVING MAGNET STEREO CARTRIDGE.
 PRICE: £3-25.

MC-1 HIGH FIDELITY STEREO MOVING MAGNET CARTRIDGE.
 PRICE: £6-00.
 For complete specification on the above see our March issue, Page 889.

SPECIAL OFFERS SPEAKERS

Wharfedale Example: wharfedale unit 3 speaker kit £10-00 — Denton — Triton — Melton — STE — MA
 Full range in stock at **UP TO 50% DISCOUNT** FOR PERSONAL CALLERS ONLY.

HEADPHONES
 For 1 month only we offer 25% OFF list price of all KOSS models.
 Example: PRO4A. List price £28-00.
OUR PRICE £21-00 plus 37p p. & p.

SAVE OVER 30% ON A COMPLETE SYSTEM

GARRARD SP 25 MK III	£16-45
PLYNTH AND COVER	£5-00
G800 CARTRIDGE	£13-00
HL AUDIO SA 707	£27-00
2 APOLLO 8 SPEAKERS	£27-50
	£89-95

OUR PRICE £56-94 + £2-50p. p. & p.

WHY PAY MORE—APOLLO 3-WAY SPEAKER SYSTEMS

The Systems are housed in handsome Slim-Line Cabinets of Modern Design, finished in Polished Teak with Padded Front Panel covered in I.C.I. Vynair Grille.

The **APOLLO 3-WAY SPEAKER SYSTEMS** are designed and built on the Infinite Baffle Principle and are completely Airtight and fully padded to damp out any Panel Resonance. Polished on all sides they can be used either vertically or horizontally and are ideal for Shelf or Wall Mounting.
 Below are just a few from the **APOLLO** comprehensive range starting with:

Crossover Network Specification: Impedance 4-8 ohms (15-16 ohms to order). Power Handling 10 watts RMS (20 watts peak). Frequency Range 50 Hz to 18,000 Hz. Size 21 x 111 x 91. Finish Polished Teak.
OUR PRICE £19.47 each (65p. p. & p.).

APOLLO-15 3-WAY SPEAKER SYSTEM
 Impedance 8 ohms. Power Handling 15 watts. RMS (30 watts peak). Frequency Range: 35 to 18,000 Hz. Colour: Teak. Size 21 x 15 x 7½ in.
PRICE £18-50 each (p. & p. £1-00).

APOLLO-8 3-WAY SPEAKER SYSTEM
 As above but 7 watts RMS (14 watts peak). F.R. 95 to 18,000 Hz. Size 20 x 12 x 8 in.
£10-12 each (50p p. & p.).

The **APOLLO-10 3-WAY SPEAKER SYSTEM** employs a specially designed 10in. Bass Unit which has a high efficiency Anisotropic Ferrite Magnet and two 4in. Treble Units and LC

APOLLO-66 3-WAY SPEAKER SYSTEM
 As above but 5 watts RMS (10 watts peak). F.R. 75 to 18,000 Hz. Size 14½ x 8 x 6 in.
PRICE £8.97 each (37½p p. & p.).



who wants a **£2,000+p.a.** opportunity in the dynamic new computer industry?

In only **4 weeks** you're in – and only the incredible **Eduputer** can make it possible.

Now for the first time anybody can train **outside** the computer industry for a lucrative career as a computer operator, **with actual experience on an Eduputer.**

Who created Eduputer? The internationally famous company Programming Science International. They developed it to the specific requirements of the massive New York city training board and its practical results have been one amazing success story.

We are proud to have been selected as the only commercial training organisation permitted to use the Eduputer in the U.K. **Thanks to Eduputer, nine out of every ten can learn to operate the most advanced computers in only four weeks. Unlike Computer Programming, no special educational qualifications and no maths required. Just you and the incredible Eduputer!**

Jobs galore! The moment you qualify, our exclusive computer appointments bureau introduces you to computer users everywhere with good jobs to offer (up to £40 a week full-time, £50 a week as a temporary). More than enough to go round, too—because 144,000 new operators will be needed over the next five years alone.

This is your big opportunity to get out of a rut and into the world's fastest-growing industry. And remember—LCOT is the only commercial computer school to have Eduputer. It means a lot to employers.

Telephone: (01) 734 2874 NOW!

Or post the coupon today for full details FREE and without obligation.

London Computer Operators Training Centre,
C16 Oxford House, 9/15 Oxford Street, London W.1.

Telephone: (01) 734 2874
127/131 The Piazza, Dept. C16, Piccadilly Plaza,
Manchester 1.

Telephone: (061) 236 2935.
Please send me your free illustrated brochure on exclusive Eduputer "hands on" training for computer operating.


Name _____

Address _____

Tel: _____

STEREO AMPLIFIER type HV—2 x 3 Watts

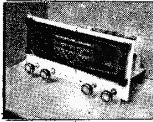Fully built. On off sep. vol. and tone each channel 1½ x 4½ x 5in. high. E230, EBC85, 2 x ECL86; for 3 ohm speakers, double wound main trans: fixing flanges and base plate, suitable for crystal cart. tuner etc. 200-250V. A.C.
Superior version — separate base, treble & vol. each channel with mono/stereo switch 75p extra. **£7.25** (Post 60p)



MONO GRAM CHASSIS 3 WATT

3 Wave band long-med-short. Gram., 200-250V A.C. Ferrite aerial. Chassis 13 x 7 x 5in. Dial 13 x 4in. Double wound mains transformer 5 valves. ECH81, EF89, EBC81, EL34, E230. Price **£10.72!**
50p p. & p.) Output trans. for 3-ohm speaker

½W MAINS GRAMOPHONE AMPLIFIER

E230, ECL82, O.P. Transformer (3 ohm). Vol./On-off and Tone Control. Double wound mains transformer. 2½ x 2½ x 2½in. separate but wired to chassis. 4 x 2½ x 4½in. over valves **£3.37!** including 5in. Speaker (**£2.75** less speaker). (Post 25p.) (Two less 10%.)

MAINS TRANSFORMERS (200-250V AC INPUT)

Postage in brackets. 6-3V at 2½A **37p** (20p).
Out 250V at 50mA and 6-3V at 1½A **50p** (22½p).
22V at 1A + 6-3V at 2A and 250V at 50mA **75p** (22½p).
250V at 40mA, 24V at 1A and 6-3V at 1½A **82½p** (22½p).
250V at 50mA, 22V at 1A and 6-3V at 1½A **87½p** (25p).
90V at 20mA and 1-4V at 250 mA **50p** (12½p).


Complete set of parts with wiring diagram for battery eliminator to give 90v. H.T. at 20-30mA. and 1-4v. at 125 or 250mA. (adjustable). With undrilled aluminium box approx. 6 x 3 x 3", trans., choke, two rectifiers, condensers and plugs and sockets. Price **£2.75** plus 20p p. & p.

25 Mixed Potentiometers, some pre-set, some stereo **£1** (Post 22½p).
100 Mixed Resistors ½W & ¼W **50p** (Post 10p).
100 Mixed Small Electronic & Paper Tubular Condensers **£1.50** (Post 12½p).
100 Mixed Ceramic Condensers 1PF to 0.1MF. **£1** (Post 12½p).
50 Mixed Wire Wound Resistors 3 to 6 watt. **22** (Post 22½p).

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

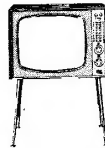(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240.
CLOSED WEDNESDAY. S.A.E. for enquiries please.



EX RENTAL TV's

19" — £29-95

23" — £39-95

All Channels 405/625
2 Years Guarantee.
Free List by return.

EX RENTAL 405 LINE TV's

17" and 19" £11-95, £15-95 Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1-95.

TEAK HI-FI STEREO CABINETS £14-95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1-00.

PRESS BUTTON SWITCHING UNITS. 4 Banks 17p. 6 Banks 27p
P. & P. 5p.

Transistor Radio Cases: 25p each. Size 9½" x 6½" x 3½". P. & P. 15p.
SPEAKERS 50p 25 Ω BRAND NEW. P. & P. 5p.

TRANSISTORS Post Free
AC 126 AF 179 OC 81
AC 128 OC 44 OC 81D
AF 114 OC 45
AF 117 OC 71 ALL AT 15p

POTENTIOMETERS 23p

Double & Switched	500 KΩ/500 KΩ	3½" shaft
Double & Switched	500 KΩ/100 KΩ	2" shaft
Double & Switched	1 MEG/100 KΩ	1½" shaft

Post. & Pack. 5p.—4 for 10p

KNOBBS 100,000 to clear (Brand New)


100 assorted Radio & T.V. knobs 50p. Postage 10p. (If you require sets 2 to 6 just ask)

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12

Phone 01-478 6001-2-3 Stamp for Free List

TV TUBES REBUILT GUARANTEED 2 YEARS

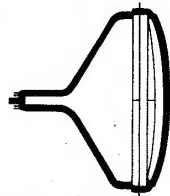

14"—£3-95, 17" & 19"—£5-95,
21" & 23"—£6-45.

Exchanged Bowls. Carr. 53p.

RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 2 sec to 100 milli sec/cm. Supplied complete with all accessories and instructions £87. Carr. paid.



MARCONI T/44/TF956 AF Absorption Wattmeter
1 μ watts to 2 watts.
£20. Carr. £1.

TE111. DECADE RESISTANCE ATTENUATOR

Variable range 0-11dB. Connections: Unbalanced T and Bridge T. Impedance 600 Ω range (0.1dB to 10) + (1dB to 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0.05dB. + Indication dB \times 0.1. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal external switch. Brand new. £27.50. P. & P. 25p.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000 Hz. Square 18-50,000 Hz

Output max. -10 dB (10 ohms) Operation in external batteries Attractive 2-tone case 7 1/2" x 5" x 2". Price £17.50. Carr. 17p.



TE-16A Transistorised Signal Generator 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800KHz modulation. 57 x 67 x 3 1/2 in. Complete with instructions and leads. £7.97. P. & P. 20p.




BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max +10 dB (10 Ω R ohms) Operation 230/240V. A.C. Size 215mm x 150mm x 120mm. Price £27.50. Carr. 25p.



TE-40 HIGH SENSITIVITY A.C. VOLTMETER

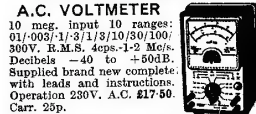10 meg. input 10 ranges: 0.1-0.05/1.5/1.5/1.5/1.5/1.5/300V. R.M.S. Acps.-1.5 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.50. Carr. 25p.



TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. £17.50. P. & P. 30p. Additional probes available: R.P. £2.12; B.V. £2.50.



MULTIMETERS for EVERY purpose!

TECH PT-34 1,000 O.P.V. 0.10/50/250/500/1,000V. A.C. and D.C. 0.1/100/500mA. D.C. 0.100K. £19.71. P. & P. 124p.



HONOR TE.10A 30k Ω /Volt 5/25/50/250/500/2,500 v. D.C. 10/50/100/500/1,000 v. A.C. 100mA/25mA/50mA/100mA D.C. 0.6K/8 meg. ohm. -20 to +22 dB. 10-0, 100 mid. 0.100-0.1 mid. £23.47. P. & P. 15p.



MODEL TE-200 20,000 O.P.V. Mirror scale, overload protection. 0.6/2.5/10/50/100/250/500/1,000V. A.C. 0.50 uA/250 mA. 0.6K/6 meg Ω . -20 to +62 db. £23.75. P. & P. 15p.



MODEL TE-300 30,000 O.P.V. Mirror scale, overload protection. 0.6/3/16/80/300/1,200V. D.C. 0.6/30/150/600/500/1,000V. A.C. 0.80uA/6mA/60mA/300mA/600mA. 0.8K/80K/800K/8 meg. ohm -20 to +65 db. £25.97. P. & P. 15p.



MODEL 500 30,000 O.P.V. with overload protection. mirror scale 0.6/2.5/10/25/100/250/500/1,000V. A.C. 0.50uA/5/50/500mA. 12 amp. D.C. 0.6K/6 Meg. 60 Meg Ω . £28.97. Post paid.



MODEL TE-80 20,000 O.P.V. 0.10/50/100/500/1,000V. A.C. 0.5/25/50/250/1,200 v. D.C. 0.6/30/150/600A. 0.6K/60K/600K/6meg. £24.87. P. & P. 15p.



MODEL TE-70 30,000 O.P.V. 0.3/15/60/300/600/1,200V. D.C. 0.6/30/150/600/1,200V. A.C. 0.30uA/3/30/300mA. 0.18K/160K/1.6M/16 Meg Ω . £25.50. P. & P. 15p.



MODEL TE-90 50,000 O.P.V. Mirror scale, overload protection. 0.3/12/60/300/600/1,200 v. D.C. 0.6/30/150/600A. D.C. 16K/160K/1.6/16 MEG Ω . -20 to +65 db. £7.50. P. & P. 15p.



TMK MODEL TW-50K 48 ranges, mirror scale, 50K/Volt. D.C. 5K / Volt A.C. D.C.: Volts 125, 25, 125, 2.5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50uA, 2.5, 5, 25, 50, 100, 250, 500mA. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω . Decibels: -20 to +81.5 db. £28.97. P. & P. 174p.



TMK MODEL TW-200E FEATURES RESETTABLE OVERLOAD BUTTON. Sensitivity: 20K Ω /Volt. D.C. 5K Ω /Volt. A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 0-2.5, 10, 50, 250, 1,000V. D.C. Currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K, 5 MEG Ω . Decibels: -20 to +65 db. £11.50. P. & P. 174p.



GIANT MULTIMETER. Mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0.2/5/10/25/100/500/1,000 v. A.C. 0.25/12.5/10/50/250/1,000/5,000 v. D.C. 0.60uA/10/100/500mA/10 amp. D.C. 0.2K/200K/2M/200M Ω . £15. P. & P. 25p.



MODEL AS-100D. 100K Ω /Volt. 5in. mirror scale. Built-in meter protection 0.8/12/60/120/300/600/1,200 v. D.C. 0.6/30/150/600/1,200 v. A.C. 0.18K/60/300/600A/12 Amp. 0.2K/200K/2M/200M Ω . -20 to +17 dB. £12.50. P. & P. 174p.



MODEL 5025 57 Ranges, Giant 5 1/2in. Meter, Polarity Reverse Switch. Sensitivity: 50K / Volt D.C. 5K / Volt A.C. D.C. 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 1K, 10K, 100K, 10 MEG Ω . Decibels: -20 to +85 db. £12.50. P. & P. 174p.



TMK LAB TESTER. 100,000 O.P.V. 6 1/2in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K Ω /Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000 V. A.C. Volt: 3, 10, 50, 20, 250, 500, 1,000V. D.C. Current: 10, 100uA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG. 100 MEG Ω . Decibels: -10 to 49 db. Plastic Case with Carrying Handle. Size 7 1/2in. x 6 1/2in. x 3 1/2in. £18.90. P. & P. 25p.




MODEL TE-12 20,000 O.P.V. 0.6/0.6/50/120/600/1,200/3,000/6,000V. D.C. 0.6/30/150/600/1,200V. A.C. 0.50uA/6/60/600mA. 0.6K/600K/6MEG/60 Meg. 0.50P/0.2mf. £25.97. P. & P. 174p.



SKYWOOD SW-500 50K Ω /Volt. Mirror scale. DC Volts 0.3/1.5/3/30/300/600. DC Current 20uA/60/600mA Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +57 db. £7.50. P. & P. 15p.



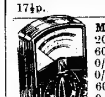FTC-401 TRANSISTOR TESTER
Full capabilities for measuring A, B and ICO. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. £28.97. P. & P. 15p.



270° WIDE ANGLE 1mA METERS
MW1-S 60mm square £2.97
MW1-B 80mm square £4.97
P. & P. extra



POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiring. Continuous rating. Wide range available ex-stock. Single hole fixing, 3/4in. dia. shafts. Bulk quantities available.



25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 721p. P. & P. 71p.
50 WATT. 10/25/30/100/250/500/1000/2500 or 5000 ohms, £1.06 P. & P. 71p.
100 WATT. 1.5/10/25/50/100/250/500/1000 or 2500 ohms, £1.37 P. & P. 71p.

230 VOLT A.C. 50 CYCLES

RELAYS Brand new 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40) Quantities available.




G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
3 Lisle Street, London, W.C.2 Tel: 01-437 8204
34 Lisle Street, London, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery

MODEL S-280 General Purpose Bench Mounting	MODEL S-280 B Panel Mounting	
	1 Amp	£5.50
2.5 Amp	2.5 Amp	£6.82
5 Amp	Please add postage	
8 Amp	INPUT 230 VOLTS, 50/60 CYCLES.	
10 Amp	OUTPUT VARIABLE 0-280 VOLTS.	
12 Amp	Special discounts for quantity	
20 Amp		

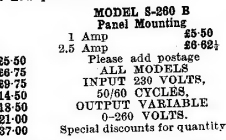

All Mail Orders to:
143 Church Street,
London, W.2
Tel: 01-262 6562
(Trade supplied)

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1
THE VALVE SPECIALISTS Telephone 01-722 9090

OA2	.30	8F13	.38	10P18	.38	30FL2	.75	DH76	.28	ECC8071.35	EL96	.35	N78	2.05	PL83	.38	UF41	.50	AC107	.15	BCZ11	.38	OA85	.09	
OB2	.30	8F18	.45	12A6	.68	30FL12	.80	DH77	.20	ECC80	.88	EM34	.90	N808	.98	PL84	.88	UF42	.60	AC113	.25	BD119	.45	OA260	.09
1A7GT	.37	8F23	.72	12A3X	.40	30FL14	.78	DK40	.55	ECP89	.88	EM39	.28	N849	1.63	PL92	.60	UF80	.60	AC120	.20	BF163	.20	OA292	.10
1BSGT	.35	8F24	.68	12A6D	.40	30L1	.38	DK92	.48	ECP86	.65	EM81	.42	P61	.60	PL500	.88	UF85	.34	AC128	.20	BF173	.38	OC28	.38
1M4	.18	8F25	.65	12A6E	.48	30L15	.54	DK96	.37	ECP8042.10	EM84	.34	PABC80	.35	PL504	.68	UF86	.63	AC130	.20	BF173	.38	OC28	.38	
1N5GT	.39	8F28	.70	12A7E	.28	30L17	.78	DL96	.37	ECH21	.63	EM87	.38	P68	.52	PL505	.44	UF89	.34	AC137	.25	BF180	.30	OC28	.38
1R5	.28	8H9GT	.15	12A7T	.19	30P-AMR	.98	DM70	.30	ECH33	.29	E761	.37	P688	.52	PL608	1.40	UL41	.59	AC141	.35	BF181	.40	OC28	.38
1S4	.24	8J5G	.19	12A7U	.24	30P12	.69	DM71	.38	ECH42	.64	E781	.35	P695	.53	PL509	1.44	UL84	.33	AC158	.38	BF185	.40	OC28	.38
1E58	.28	8J6	.18	12A7U	.28	30P19	.98	DW4	.48	ECH81	.29	Y83	.55	PC97	.40	PL802	.76	UM80	.38	AC176	.55	BFY60	.28	OC28	.25
1U4	.29	8J7G	.24	12A7V	.28	30P4	.60	350	.38	ECH82	.40	E784	.50	PC98	.48	PL804	.76	UM81	.38	AC177	.55	BFY61	.28	OC28	.25
1U5	.48	8J7GT	.38	12A7X	.28	30P11	.69	DW4	.48	ECH84	.38	E786/7	.33	PC99	.48	PL806	.76	UM82	.38	AC178	.55	BFY62	.28	OC28	.25
2D21	.35	8K7G	.10	12BA6	.30	30P12	.37	500	.38	ECL80	.35	EY88	.48	PC99	.48	PL808	.76	UM83	.38	AC179	.55	BFY63	.28	OC28	.25
3D6	.10	8K7GT	.28	12BE6	.30	30P13	.78	DY87/7	.29	ECL82	.33	EY91	.33	PC99	.48	PL810	.76	UM84	.38	AC180	.55	BFY64	.28	OC28	.25
3Q4	.38	8K8G	.20	12BH7	.40	30P14	.78	DY802	.48	ECL83	.52	EZ40	.40	PC99	.48	PL812	.76	UM85	.38	AC181	.55	BFY65	.28	OC28	.25
3Q6GT	.35	8L6GT	.30	12E11	.38	30P15	.88	E807	1.20	ECL84	.60	EZ41	.48	PC99	.48	PL814	.76	UM86	.38	AC182	.55	BFY66	.28	OC28	.25
3S4	.29	8L7GT	.63	12J7GT	.38	33L6GT	.44	E83F	1.20	ECL85	.55	EZ80	.33	PC99	.48	PL816	.76	UM87	.38	AC183	.55	BFY67	.28	OC28	.25
3V4	.32	8L18	.45	12K5	.50	33W4	.28	E88CC	.60	ECL86	.40	E281	.24	PC99	.48	PL818	.76	UM88	.38	AC184	.55	BFY68	.28	OC28	.25
3V4G	.38	8LD20	.48	12K7GT	.84	33Z4GT	.24	E180F	.95	E922	.63	E290	.22	PC99	.48	PL820	.76	UM89	.38	AC185	.55	BFY69	.28	OC28	.25
4Y6GT	.28	8N7GT	.40	12Q7GT	.38	33Z6GT	.30	E180CL13	E936	.33	FW4500.75	.33	PCL82	.37	R16	1.75	U404	.38	AC121	.30	GE119	.20	OC77	.27	
6Z4G	.35	8Q7	.45	12S47GT	.50L6GT	.45	E1148	.53	EF37A	.35	FW4500.75	.33	PCL83	.50	R17	.88	U801	.95	AC124	.25	GE123	.20	OC78	.15	
6/30L2	.58	8Q7G	.30	40	72	.33	EA50	.18	EF39	.40	GZ30	.35	PCL85/85	.85	SP42	.75	VP23	.40	AC129	.65	GE123.15	.08	OC78	.15	
6A8G	.38	8R7	.55	12S8C7	.35	85A2	.43	EA76	.88	EF40	.50	GZ32	.45	SP61	.48	VP41	.38	AT18	.68	GE127	.23	OC81	.13		
6A7G	.15	8R7G	.38	12S8G7	.38	85A2	.43	EA76	.88	EF40	.50	GZ32	.45	VP41	.38	AT18	.68	GE127	.23	OC81	.13				
6A05	.25	8S47GT	.35	12S7H	.15	5765	.50	EAC91	.38	EF42	.33	GZ24	.53	VP41	.38	AT18	.68	GE127	.23	OC81	.13				
6AK5	.25	8S47M	.35	12S7H	.23	AC2/PEN	.98	EF42	.33	EF42	.33	GZ24	.53	VP41	.38	AT18	.68	GE127	.23	OC81	.13				
6AL5	.12	8S7GT	.38	12S8K7	.24	AC2/PEN	.98	EF42	.33	EF42	.33	GZ24	.53	VP41	.38	AT18	.68	GE127	.23	OC81	.13				
6A05	.28	8S7GT	.38	12S7GT	.24	AC2/PEN	.98	EF42	.33	EF42	.33	GZ24	.53	VP41	.38	AT18	.68	GE127	.23	OC81	.13				
6A76	.20	8S17	.53	50	.50	DH	.98	EF41	.50	EF80	.38	HL23DD	.40	PEN4DD	UAB80.33	VU111	.44	B181	.50	M3	.15	OC82	.15		
6A7G	.36	8S17	.53	1A87	1.15	AC2/PEN	.98	EF41	.50	EF80	.38	HL23DD	.40	PEN4DD	UAB80.33	VU111	.44	B181	.50	M3	.15	OC82	.15		
6A76	.36	8S7GT	.38	12A6G	.24	AC2/PEN	.98	EF41	.50	EF80	.38	HL23DD	.40	PEN4DD	UAB80.33	VU111	.44	B181	.50	M3	.15	OC82	.15		
6B1G	.43	8V4G	.28	12A6G	.24	AC2/PEN	.98	EF41	.50	EF80	.38	HL23DD	.40	PEN4DD	UAB80.33	VU111	.44	B181	.50	M3	.15	OC82	.15		
6B4E	.28	8V6G	.18	12O1L	.98	AC/TH1	.50	EF80	.38	EF80	.38	HL23DD	.40	PEN4DD	UAB80.33	VU111	.44	B181	.50	M3	.15	OC82	.15		
6B6E	.24	8V6GT	.38	12O1P	.98	AC/TH1	.50	EF80	.38	EF80	.38	HL23DD	.40	PEN4DD	UAB80.33	VU111	.44	B181	.50	M3	.15	OC82	.15		
6B1G	.43	8V4G	.28	12A6G	.24	AC2/PEN	.98	EF41	.50	EF80	.38	HL23DD	.40	PEN4DD	UAB80.33	VU111	.44	B181	.50	M3	.15	OC82	.15		
6B3E	.43	8X4	.25	20P4	.98	ATP4	.12	E181	.20	EP98	.65	K744	1.00	PENDD	.98	UC84	.40	X61	.29	BC113	.25	OA47	.10	OC172	.35
6B7A	.38	7B6	.58	20P5	1.00	AZI	.40	EC86	.68	EP183	.30	K768	.83	4020	.38	UCF90	.42	X66	.60	BC116	.25	OA73	.15	OC201	.38
6B77	.78	7B7	.38	25A6G	.29	AZ21	.48	EC88	.90	EP184	.30	K788	1.70	PFL200	.59	UCF21	.60	28323	.60	BC118	.23	OA79	.09	OC202	.43
6B88	.63	7C9	.30	32L6G	.29	AZ41	.63	EC92	.35	EP90	.38	K791	.61	PL36	.48	UCH42	.63	AA119	.15	BCY10	.45	OA81	.09	OC203	.30
6B96	.72	7H7	.28	25Y5	.38	B36	.33	EC93	1.58	EL92	.18	K796.2	.63	P121	.48	UCH81	.32	AA120	.18	BCY12	.60	OA83	.08	OC204	.30
6B77	.67	7R7	.65	25Y6G	.43	CYIC	.55	EC94	.40	EL84	.53	K796.5	.50	PL51A	.83	UC82	.35	AA129	.15	BCY33	.20	OA90	.13	OC205	.43
6B96	.38	8D7	.72	32Z4G	.40	CY11	.68	EC95	.40	EL87	.87	MELD6	.57	PL52	.33	UC83	.35	AA130	.18	BCY38	.20	OA91	.09	OC212	.58
6C9	.73	1E11	1.35	20P3	.40	DA62	.95	EC98	.38	EL91	.29														
6C16E	1.15	10C2	.50	25Z9G	.43	DAF91	.22	EC98	.38	EL91	.29														
6C16E	.38	10P1	.75	30C1	.30	DAF96	.35	EC98	.38	EL91	.29														
6C15	.45	10P5	.55	30C1G	.25	DAF91	.22	EC98	.38	EL91	.29														
6C4V	.65	10F18	.55	30C17	.30	DF91	.14	EC98	.40	EL84	.24														
6F1	.68	10LD11	.53	30C18	.64	DF96	.35	EC98	.35	EL85	.40														
6F6	.62	10P13	.65	30F5	.80	DF97	.63	EC98	.38	EL86	.40														
6F6G	.28	10P14	1.10	30P11	.64	DH93	.60	EC98	.40	EL91	.29														

All valves are unused, boxed, and subject to the standard 90 day guarantee. Terms of business — Cash or cheque with order only. Postpacking 0.63 per item, subject to a minimum of 0.09. Orders under £5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 0.03 extra per order. Complete catalogue with conditions of sale price 0.07. We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.

4-STATION INTERCOM



Solve your communication problems with this 4-Station Intercom system (1 Master and 3 Subs), in deluxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. £6.40.

MAINS INTERCOM
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £12.95 P. & P. £10.50

INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery £0.12 P. & P. £0.25

TRANSISTOR TELEPHONE AMPLIFIER



Why not boost efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or conferences without holding the handset. A useful office aid. On/off switch. Volume Control. Battery £0.12 extra. P. & P. £0.20. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P.W.5)
168 KENSINGTON HIGH STREET, LONDON, W.8.

NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays. 7 element £2.25.
11 element £2.62. 14 element £3.00.
18 element £3.50. Wall mounting with Cranked Arm. 7 element £3.25. 11 element £3.75. 14 element £4.12. 18 element £4.50.
Chimney Mounted Arrays complete. 7 element £4.00. 11 element £4.37. 14 element £4.75. 18 element £5.25. Complete assembly instructions with every aerial. Low Loss Co-axial cable 8 1/2 yd. King Teboosters—Lab sear U.H.F. Boosters from £3.75.

BBC-ITV-FM AERIALS

B.B.C. (Band 1) Loft £1.25.
Wall S/D £1.62. 'H' array £3.00. ITV (Band 3) 5 element loft array £2.25. 7 element £2.75. Wall mounting 5 element £3.25. Combined BBC/ITV loft 1 + 5 £2.75. 1 + 7 £3.37. Wallmounting 1 + 5 £3.87. Chimney mounted 1 + 5 £4.50. Preamps from £3.75. Combined BBC/ITV/BBC 2 aerials 1 + 5 + 9 £4.00. 1 + 5 + 14 £4.84. 1 + 9 £4.00.

14 £5.00. Available loft only. FM radio loft S/B 97p. 'H' £1.92. 3 element array £2.87. Standard Co-axial cable 5 yd. Coax plus 8 1/2. Outlet boxes 30p. Diplexer crossover boxes 87p. D. & P. Aerials 40p. accessories 15p. C.W.O. or C.O.D. (Min C.O.D. charge 17p.) 5p for fully illustrated lists.

Callers welcomed—open all day Saturday.
K.V.A. ELECTRONICS (Dept. P.W.)
40-41 MONARCH PARADE,
LONDON ROAD, MITCHAM,
SURREY 01-648 4884

The Unique MULTI-MINI TWIN-VICE



An extra "Pair of hands" for those tricky jobs

ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING—ETC.


- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5.90 (24p P & P)
ALSO AVAILABLE
SINGLE VICE: £3.37 (20p P & P)
COVENTRY MOVEMENT CO LTD.
Dept. 101
BURNSALL ROAD, COVENTRY
CV5 6BU STD O203-74363



LIND-AIR AUDIO

C.1001 MULTI-TESTER

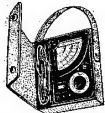


Overload protection. 20,000 opv. AC volts 10, 50, 250, 1,000V. DC volts 5-25, 125, 500, 2500V. D.C. Current 0-50 uA, 0-250 mA. Resistance: 0-60K 0-6 Meg ohm. Decibels -20 to +22dB.

Size of meter 4 1/2 x 3 1/2 in. Complete with case.

£4-25. P. & P. 17 1/2p

C.1050 MULTI-TESTER

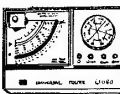

10,000 opv. RANGES: DC Voltage: 0-3-15-150-500-1200 Volt (10,000 ohms per Volt). AC Voltage: 0-6-30-300-1200 Volt (5,000 ohms per Volt). DC Current: 0-120 uA, 0-300 mA. Resistance: 0-50K, 0-5 Meg (R x 10)

Decibels: -20 to +17dB. (R x 1K)

£5-97 1/2. P. & P. 17 1/2p

C.1052 MULTI-TESTER



RANGES: AC Voltage: 6, 30, 150-500-1200 (15,000 ohm/V) DC Voltage: 0-6, 3, 15, 60, 300, 1200 (30,000 Ohm/V) DC Current: 0, 0.03, 3, 30, 300 mA Resistance: 0, 6k, 60k, 600k, 6 M ohms Decibels: -20 to +63dB.

£7-35. P. & P. 17 1/2p




SM-370 MULTI-TESTER
20,000 opv. RANGES: DC Voltage: 0-5-25-100-500-1000V (20,000 ohms/V) AC Voltage: 0-5-25-100-500-1000V (20,000 ohms/V).

DC Current: 0-50 uA, 0-250 mA Resistance: RX10, RX1K (3000 ohms and 30K ohms at centre scale). Decibels: -20dB to +16dB.

£3-55. P. & P. 17 1/2p

BATTERY ELIMINATOR

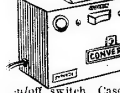

Enables transistor equipment to be operated from AC mains. 6/9/15v. output selector switch and instructions.


£2-97 1/2. P. & P. 17 1/2p

WELLER "EXPERT" SOLDERING GUN

Comfortable and easy to use. 240V. AC. Instant dual heat 100/140 watt with two position trigger control.

£3-37 1/2. P. & P. 27 1/2p

SINCLAIR PROJECT 60

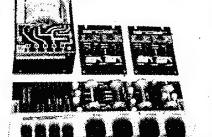

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly. Z50 24 watt Power Amplifier £4-47 1/2. (2 required).

Stereo Sixty Control/Pre-amplifier £9-97 1/2.

P.Z.5 Power Supply Unit £4-97 1/2.

SINCLAIR PROJECT 60 Package deal price £19-95. P. & P. 62 1/2p
Project 60 is supplied complete with instruction manual and templates for plinth mounting.

SINCLAIR IC-10 INTEGRATED CIRCUITS

10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years.

£2-97 1/2. P. & P. 7 1/2p

SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10
From A.C. mains 230/250V. Output 13v at 0.5 amp. 82p. P. & P. 12 1/2p

UNILEX AUDIO MODULES

Build a stereo amplifier for as little as £16-75. Send 5p for Mullard "Do It Yourself Stereo" booklet. All items in stock.

E.M.I. LOUSPEAKERS

MODEL 450
13 1/2" x 8" elliptical with twin tweeters. 8 ohm impedance. 10 watts. Brand New, guaranteed. Lind-Air Price £3-97 1/2. P. & P. 22 1/2p

MODEL 150
13 1/2" x 8" elliptical, 3 and 15 ohm impedance. 10 watts. Lind-Air Price £2-97 1/2. P. & P. 22 1/2p

CELESTION LOUSPEAKERS

7" x 4" elliptical. 8 ohms. New and guaranteed. £1-37 1/2. P. & P. 22 1/2p

CABINETS FOR ABOVE
Teak finish with cloth fronts. £2-47 1/2 each. P. & P. 22 1/2p


CARTRIDGE BARGAINS

- A.D.C. 220X £6.12 1/2
- A.D.C. 220XE £9.96 1/2
- A.D.C. 660XE £15.52 1/2
- A.D.C. 990XE £13.31
- Audio Technica AT66-7D £6.12 1/2
- Audio Technica AT66-6D £6.12 1/2
- Audio Technica AT66 £6.12 1/2
- Decca Deram Stereo £5.12
- Decca Deram Mono £3.15
- Goldring G800 £12.75
- Goldring 800H £10.50
- Goldring G800 E £18.50
- Goldring G800 Super E £28.00
- Goldring G850 £6.50
- Shure M3DM £7.41
- Shure M44 7 £10.15
- Shure M31 E £12.00
- Shure M55 E £12.50
- Shure M75 E £21.30
- Shure V15 II £20.75
- Sonotone 9TAHCD £2.75

Full range of diamond styls available for most current ceramic and crystal cartridges. All at £1-25 each. P. & P. 5p. Please state cartridge make and type number.

SANSUI SPECIAL PURCHASE

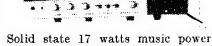SAVE OVER £14
FANTASTIC SANSUI 200 AM/FM MULTIPLEX STEREO TUNER AMPLIFIER



Solid state 17 watts music power. Fully tunable over Medium wave and VHF/FM Stereo. Inputs for gram and tape etc. Host of outstanding features—details on request. Rec. Retail Price £89.99. LIND-AIR PRICE £75-60. P. & P. 57p

DE-LUXE STEREO HEADPHONES



With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000 cps. With lead and stereo plug. £2-97 1/2. P. & P. 17 1/2p

STEREO HEADPHONE JUNCTION BOX

Enables Stereo headphones to be used with any amplifier. £1-47 1/2. P. & P. 12 1/2p

HI-FI CATALOGUE

100 pages fully illustrated with 8 page P.A. section. All leading makes and accessories plus details of Budget Stereo systems. 25p P. & P. 5p

GARRARD HI-FI TURNTABLES



- 2025 T/C with stereo cartridge £8.97 1/2
- 3000 with Sonotone
- 9TAH CD stereo cartridge £10.97 1/2
- SP25 Mk III £11.97
- SL65 B £15.97 1/2
- Base and cover for above £2.97 1/2
- AP76 £19.50
- SL72 B £24.97 1/2
- SL75 B £26.35
- SL95 B £39.45
- Base and cover for above £2.97 1/2
- 401 £28.50

P. & P. Decks 62p. Base & Cover 50p. Deck/Base/Cover 87p.

THIS MONTH'S SPECIAL OFFERS!

SP25 Mk III with base £12.97 1/2. P. & P. 75p

SP25 Mk III with Sonotone 9TAHCD cartridge and base £15.72 1/2. P. & P. 75p.

LA.20 STEREO SYSTEM


(SAVE £12)



Only takes a few minutes to set up the Lind-Air LA 20 Stereo Amplifier with the Garrard 2025 T/C Record Changer fitted stereo cartridge and a pair of Lind-Air General Purpose speakers and you have a superb stereo system at a money saving price. Total Rec. Price £53.47 1/2.

Price £41-47 1/2. C. & Ins. £1-75

S-DeC BREADBOARD

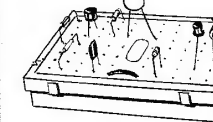

Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits.

£1-00. P. & P. 17 1/2p

4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. £3-95. P. & P. 22 1/2p

T-DeC KIT £2-50. P. & P. 17 1/2p

S-DeC STOR £2-50. P. & P. 22 1/2p

18/19, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1
Tel: 01-580 2225/7679
Open 9-6 Mon-Sat (Thurs until 7)

All Mail Orders and enquiries to Dept. FW5, Kirkham House, 54a Tottenham Court Road, London, W.1. Tel. 01-637 1601.

94-96, UPPER PARLIAMENT STREET, NOTTINGHAM
Tel: Nottingham 40403 (STD 0602)
Open 9-6 Mon-Sat (Weds until 7.30)

DISCOTHEQUE EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK.II AMPLIFIER PR. R.S.C. L19/25 35W L/S in cabinets Terms: Deposit £9 and 9 monthly payments of £5 (Total £54)	£35.50	PACKAGE PRICE £48 carr. £1
F.A.L. PHASE 50 MK.II AMPLIFIER PR. FANE POP 50 L/SPEAKERS Terms: Deposit £10.50 and 9 monthly payments of £5 (Total £55.50)	£35.50	PACKAGE PRICE £49.50 carr. £1
F.A.L. PHASE 100 AMPLIFIER PR. L125 50W L/S in cabinets Terms: Deposit £22 and 9 monthly payments of £11 (Total £121)	£69.85	PACKAGE PRICE £110 carr. £1.50
F.A.L. PHASE 100 AMPLIFIER 4 FANE POP 50 SPEAKERS Terms: Deposit £14 and 9 monthly payments of £10 (Total £124)	£69.85	PACKAGE PRICE £94 carr. £1.50

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 lines 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.75**

OR SENIOR 15 WATT INC. HF126
15,000 LINE SPEAKER carr. 35p **£6.75** Carr. 30p



AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. Please state choice. Exceptional performance at low cost.

HF801D 8" SW £2.71	HF100D 12" 15W £4.49
HF102D 10" 10W £3.40	HF126 12" 15W £5.25
HF120 12" 15W £3.99	HF126D 12" 15W £5.75

FANE 807 HIGH FIDELITY LOUSPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and lone throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Impedance 3 or £3.50 8-15 Ω. Gauss 10,000. Remarkable value.



HI-FI SPEAKER ENCLOSURES

Modern design. Teak veneer finish. Acoustically lined. All sizes approx. Carr. 25p. per enclosure

JB5 Size 16 x 11 x 9in. Pressurised. Gives **£4.75**

SE8 For optimum performance with any 5in. Hi-Fi 'speaker. Size 22 x 15 x 9in. Ported **£5.75**

SE10 For outstanding results SE12 For excellent performance with 12in. Hi-Fi 'speaker and Tweeter. Size 24x15x10in. Ptd. **£5.99** Size 25 x 16 x 10in. **£6.99**



RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amp. or Tape recorder.

RPIC Garrard 3000 4-Speed Auto-change Unit with Sonotone STA/HC Ceramic Stereo Cartridge. **£19.45** Carr. 50p.

RP23C Garrard SP25 Mk III fitted Goldring CS90 high compliance Ceramic Stereo/Mono cartridge with diamond stylus. **£26.09** Carr. 50p

RPC6 Garrard 8300 Auto Unit fitted Stereo Cartridge Plinth & Cover as RP20 **£15** carr. 50p.

Other types available with Magnetic cartridges and with alternative design plinths.

R.S.C. PLINTHS for Record Playing units, out for Garrard 1025, 2025, 3000, AT600, SP20 etc.

WITH TRANSPARENT PLYSTIC COVER **£3.15** **£6.30**

LEADING MAKES HI-FI EQUIPMENT AT CLEARANCE PRICES Available at branches only

R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BML An all-dry battery eliminator. Size 8 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50/cps is available. Complete kit with diagram £3 or assembled ready for use £3.50

R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER

200-250v. A.C. mains operated. Frequency Response 30-20,000 c.p.s. -20dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lit' and 'cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 4 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring. **£7.50** Carr. 40p

OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£9.45**

R.S.C. A11 HI-FI 12-14 WATT AMPLIFIER

PUSH-PULL OUTPUT. Two input sockets with sep. vol. controls for mixing. High sensitivity. 5 valves. Bass and treble controls. Response ± 3dB 30-20,000 c/s. Hum level -60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments etc. **£10.50**

Std. A.C. mains. For 3 & 15 ohm spkrs. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 60p S.A.E. for leaflet. Twin handled metal cover £1.75

Factory built **£14.75** or Dep. £3 and 9 mthly payments of £1.60 (Total £17.40)

R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS



All types 15 Ohms covered in Rexine Vynair
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C485 25-30 WATTS

Fitted four 8" high flux 8 watt speakers. Overall size approx 48 x 10 x 5 in. Carr. 75p
Terms: Dep £3 and 9 monthly payments £2 (Total £21)

TYPE C4100 100 WATTS inc. four 12" 50 watt speakers for conservative rating and pressurised. Terms: Dep. £7.50 and 9 mthly. pmts. £2.45 (Total £56.65). Carr. £1

TYPE C4125 50 WATTS

Fitted four 12" 11,000 line 15 watt speakers. Overall size approx 56 x 14 x 9 in. Carr. 75p
Terms: Dep. £4 and 9 monthly payments £3 (Total £31)

30 WATT HI-FI AMPLIFIER FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP

A 2 or 4 input, 2 vol. control Hi-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.C. facia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. **£19.95** Carr. 65p



HIGH QUALITY LOUSPEAKER UNITS

IN TEAK VENEERED CABINETS

L13 13" x 8" 10 Watt	£5.25 carr. 40p
10,000 lines 3 or 15 ohms. State impedance required.	
L12 12" 12 Watt	£9.50 carr. 45p
10,000 lines 15 ohms.	

L12/25 50 WATT
Two tone Rexine and vynair finish. Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. 75p **£29.50**

R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit optional horizontal or vertical mounting. **£60**

★ Two extra heavy duty 12in. Loudspeakers.
★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes".
Bass and Treble controls. Send S.A.E. for leaflet.
Credit Terms Deposit £16 and 9 monthly payments of £5.75 (Total £67.75)

FAL PHASE 50 MK.II AMPLIFIER 50W **£33.50** Carr. 65p
FAL PHASE 100 AMPLIFIER 100W **£61.95** Carr. 75p



FANE ULTRA HIGH POWER LOUSPEAKERS

All power ratings are R.M.S. continuous. 2 years' guarantee. High flux ceramic magnets. Heavy cast chassis. All carr. free.

'POP' 100 18" 100 Watt 14,000 gauss 8/15Ω £22.05	'POP' 60 15" 60 Watt 14,000 gauss 8/15Ω £12.90	'POP' 25/2 12" 50 Watt 13,000 gauss 15Ω £10.50
---	---	---

Dep. £6 and 9 monthly payments £2-10 (Total £24.90)
Dep. £3.30 and 9 monthly payments. £1.80 (Total £15).
FOR BASS GUITAR, ELECT. ORGAN, ETC.

FANE LOUSPEAKERS 'POP' 25/2 12in. 25 WATT Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). **£6.75** Carr. 50p
or Dep. £1 and 9 mthly payments 75p (Total £7.75).

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output. Hum level -70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, EF86, EC038, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. to be used for mixing purposes. 200-250 v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Complete Kit of parts with wiring diagram and instructions. Twin-handled perforated cover. **£15.75** or factory built with EL34 output valves and 12 months' guarantee for £19.75

TERMS: Deposit £4 and 9 monthly payments of £2-10 (Total £22.90). Send S.A.E. for leaflet.


RSC TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and interleaved where necessary

Primary 200-250v. 50c. Screened	FLAMEMENT OR TRANSFORMER POWER PACK Type 6.3v. 1.5a. 45p; 6.3v. 2a. 40p; 6.3v. 3a. 85p; 6.3v. 6a. £1.15; 12v. 1a. 50p; 12v. 3a. or 24v. 1.5a £1.20; 0.9-1.8v. 1.5a. 90p; 0.12-25-42v. 2a. £1.60
MIDGE CLAMPED TYPE 2 1/2 x 2 1/2 in. 90p	CLEARER TRANSFORMERS 0.9-10v. 1.5a. 95p; 2.5a. 95p; 5a. £1.10; 5a. £1.30; 6a. £1.40; 8a. £1.85
250-0-250v. 60mA, 6.3v. 2a. 90p	AUTO (Step Up/step DOWN) TRANSFORMERS 0-110/120v. 250-250-250v. 50-80 watts 95p; 150 watts, £1.70 250 watts £2.49; 500 watts £5.25.
250-0-250v. 60mA, 6.3v. 2a. 95p	OUTPUT TRANSFORMERS Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 45p
250-0-250v. 60mA, 6.3v. 2a., 0-5-6.3v. 2a. £1.25	Push-Pull 8 watts EL84 to 3 Ω or 15 Ω ... 75p
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 2a. £1.99	Push-Pull 10 watts 6V6, EL84 to 3, 5, 8 or 15 Ω ... £1.25
300-0-300v. 150mA, 6.3v. 4a., c.t., 5.5v. 1a. £2.49	Push-Pull Ultra Linear for Mullard 510, etc. £1.99
350-0-350v. 200mA, 6.3v. 4a., 6.3v. 3a., 5v. 3a. £4.89	Push-Pull 18 watts, sectionally wound 6L6, 6T66, etc. for 3 or 15 Ω ... £1.80
350-0-350v. 200mA, 6.3v. 4a., 0-5-6.3v. 2a. £1.69	Push-Pull 20 watt high quality sectionally wound 6L6, 6T66, 6L6, 6T66 etc. to 3 or 15 Ω £2.99
425-0-425v. 200mA, 6.3v. 4a., c.t., 5v. 2a. £4.49	SMOOTHING CHOKES 150mA, 7-10H. 250V. 50 Ω; 100mA, 10H, 20 Ω 55p; 80mA, 10H, 30 Ω 45p; 60mA, 10H, 40 Ω 50p.
425-0-425v. 200mA, 6.3v. 4a., 6.3v. 3a., 5v. 3a. £4.89	SELENIUM RECTIFIERS F. W. (Bridged) 6L6/12v. D.C. output Max. A.C. input 18v. 1a. 2p. 3p. 5p. 5a. 50p. 4a. 65p. 6a. 80p.
300-0-300v. 150mA, 6.3v. 2a., 0-5-6.3v. 2a. £1.20	
250-0-250v. 100mA, 6.3v. 3.5a. £1.40	
250-0-250v. 100mA, 6.3v. 2a., 6.3v. 1a. £1.45	
350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a. £1.50	
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 2a. £1.99	
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 2a. £1.99	
300-0-300v. 150mA, 6.3v. 4a., 0-5-6.3v. 1a. £2.35	
Suitable for Mullard 510 Amplifier ... £2.35	
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 2a. £1.99	
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.35	

Introducing R.S.C. MkIII SUPER 30 HI-FI STEREO AMPLIFIER

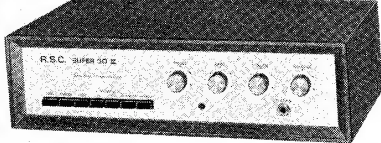A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE. REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.



- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONE CONNEX.
- ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE.
- ★ WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

Only high grade components by leading manufacturers.
COMPLETE KIT OF PARTS

Or **FACTORY BUILT** with 12 months guarantee
Dep. £5.75 and 9 monthly payments £3-50 (Total £37.25) **£33.75**

Or **FACTORY BUILT** in cabinet as illustrated
Dep. £8 and 9 monthly payments £3-88 (Total £40.74) **£36.75**

PRINTED CIRCUITRY. TWENTY SILICON TRANSISTORS.
FOUR DIODES. FOUR RECTIFIERS.
TECHNICAL DETAILS (Applying to each channel where appropriate)
CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off.
Bass, Treble and Balance. Plus Ceramic Mag P.U. Switch.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms.
10 watts R.M.S. (Continuous) into 15 ohms.

HUM & NOISE—75dB Min. Vol.—65dB Full Vol. **HARMONIC DISTORTION**
FREQUENCY RESPONSE—3dB Hz to 70KHz 0-1% at 1000 Hz 10 Watts


TREBLE CONTROL: +17dB to -12dB at 14KHz. **CROSS TALK**—58dB

BASS CONTROL: +17dB to -16dB at 40Hz

SENSITIVITIES: Disc Mag. 2.5mV. Radio 120mV. Tape 120mV.
REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

RSC HIGH FIDELITY STEREO 'PACKAGE' OFFERS

- ★ Four fully wired units ready to 'plug in.' in veneered housing
 - ★ **SUPER 30 AMPLIFIER** (15 + 15 watt) in veneered housing
 - ★ **GARRARD SP25 MKIII Turntable** on Plinth with cover
 - ★ **GOLDRING CS90 Ceramic Pick-up Cartridge** with diamond stylus
 - ★ **PAIR OF STANWAY II Speaker Units**
- Special Total Price Carr. £1.50 **£79-80**
- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
 - ★ **Golding GL69 II Transcription Turntable** on Plinth as illustrated
 - ★ **Golding Magnetic P.U. Cartridge.**
 - ★ **Pair of Stanway II speaker units**
- Special Total Price Carr. £1.50 **£96-75**

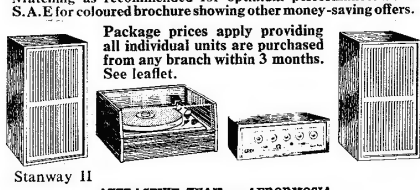

Matching as recommended for optimum performance. Send S.A.E. for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.

Attractive Teak or Afrormosia Veneered Cabinets and Plinths

- ★ **TA12 AMPLIFIER** 6.5+6.5 watt in veneered housing
 - ★ **GARRARD SP25 MK III Player** unit on Plinth
 - ★ **GOLDRING CS90 Ceramic P.U.** Cartridge with diamond stylus
 - ★ **PAIR OF DORCHESTER Loudspeaker Units**
- Special Total Price Carr. £1.25 **£58**
- Or Deposit £7.15 and 9 monthly payments £6-35 (Total £64.30). Trans. Plastic Cover £3-15 extra.
- Package as above but with Garrard 3000 Auto-changer and Sonotone 9TA Ceramic Cartridge in lieu of SP25 **£51-75** Carr. £1.25 and 9 monthly payments £5-70 (Total £57-30) Trans. Plastic cover £3-15 extra.

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM COMPLETE KIT £22

Moderate size only 25 x 14 x 10in. Response 30-20,000 c.p.s. Impedance 15 ohms

Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4.50 and 9 monthly payments £2-25 (Total £24.75).

DEMONSTRATIONS AT ALL BRANCHES

HIGH FIDELITY LOUSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled cosmetic damping. Ported where appropriate. Credit terms available.

DORCHESTER (Illustrated) Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 5in. Dual Cone speaker. Imp. 3 or 15 ohms. £9-45 Carr. 40p.


STANWAY II Size 20 x 10 1/2 x 9 1/2in. approx. Rating 10 watts. Inc. 13 x 5in. speaker with highly flexible cone surround, long throw voice coil and line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. See (package offers) for illustration **£17-85**

RSC G66 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Suitable for Crystal Pick-ups, etc., and for loudspeaker output impedances of 3 to 15 ohms. For standard 200—250v A.C. mains operation. Attractive silver finished metal fascia plate & matching control knobs.


COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£9-99**

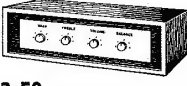Or **FACTORY BUILT IN TEAK VENEERED CABINET** as illustrated **£12-50** carr 40p, or dep £2 and 9 mthly pymts. £11.45 (Total £15-05)



R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER FULLY TRANSISTORISED. SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge, Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. — 3dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise — 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & Knobs. **COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS.** Factory built with 12 months guarantee **£19-50** or Deposit £3 and 9 mthly pymts £2-05 (Total £21.45). Or in Teak veneer housing **£15-50** Carr. 40p. **£23** Dep. £3 and 9 mthly payments £2.55 (Total £25.95). Send S.A.E. for leaflet

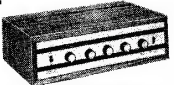

AUDIOTRINE A55 HIGH QUALITY STEREO SYSTEM 5 + 5 WATT OUTPUT

GARRARD S200 Changer with low mass pick-up arm and Stereo Cartridge.

CONTROLS: TREBLE, BASS, VOLUME, STEREO, BALANCE.

Operation on 200 - 250v. A.C. mains.

Output rating, I.H.F.M



PAIR OF LOUSPEAKER UNITS incorporating high flux 8 x 5ins. speaker. Size approx. 13 x 7 1/2 x 8 1/2 ins.

Price complete ONLY **£42** Carr. £1.25

Terms: Deposit £5.50 and 9 monthly payments £4.50 (Total £46.)

LOW DEPOSIT CREDIT TERMS

AVAILABLE ON PURCHASES OVER £8 (KITS OF PARTS EXCEPTED)

INTEREST CHARGES REFUNDED

ON CREDIT SALES SETTLED IN 3 MONTHS

A REALLY SURPRISING STANDARD OF QUALITY IS OBTAINABLE FROM THIS COMPACT LOW PRICE SYSTEM

PARTRIDGE "JOYSTICK" SHORT WAVE AERIALS AND TUNERS AT ALL BRANCHES (S.A.E. for full list)

- BRADFORD** 10 North Parade, (Half-day Wed.) Tel. 25349
- BLACKPOOL** (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM** 30/31 Gt. Western Arcade (Half-day Wed.) Tel. 021-236-1279
- DERBY** 26 Osmand Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. 556 5766
- GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL** 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Menconner Lane, Leeds 13. Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 25p extra under £2. 30p extra over £2 or as quoted. Trade supplied, S.A.E. please with enquiries. Branches open all day Sats. **MAIL ORDERS MUST NOT BE SENT TO SHOPS**

- 32 High Street (Half-day Thurs.) Tel. 56420 **LEICESTER**
- 5-7 County(Mecca) Arcade, Briggate (Half-day Wed.) Tel. 2825 **LEEDS**
- 73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 **LIVERPOOL**
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 **LONDON**
- 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 **MANCHESTER**
- 106 Newport Rd. (Half-day Wed.) Tel. 47096 **MIDDLESBROUGH**
- 41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**
- 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

R+TV

RADIO & TV COMPONENTS (Acton) Ltd.

21c HIGH STREET, ACTON, LONDON, W.3. 6NG
323 EDGWARE ROAD, LONDON, W.2.


ALL MAIL ORDERS TO OUR ACTON BRANCH

Terms C.W.O.

All enquires S.A.E.

Complete Stereo System £43

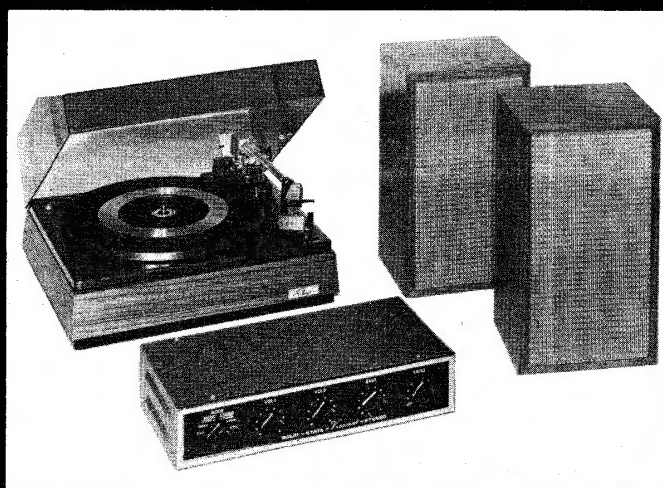WITH
VISCOUNT
F.E.T.
FIELD EFFECT TRANSISTORS
AMPLIFIER



This superb stereo system is a real price break through. It comprises the VISCOUNT F.E.T. Mk I amplifier on which full details are given below, the famous Garrard SP 25 Mk III (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers. Measuring 17½in x 10½in x 6½in, the Duo type 2 speakers are teak finished with matching Vynair grills. They incorporate a 3 ohm, 13in x 8in drive unit and Parasitic tweeter. Max. power handling 10 watts. Price £13.50 per pair plus p. & p. £1.50.

Complete stereo system £43 plus £2.50 p. & p. or with Mk II Amplifier and Magnetic Cartridge £48 & £2.50 p. & p.

The Viscount

F.E.T. Mk I £14.25 + 50p. p. & p.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

Specification—Output per channel 10 watts r.m.s. into 3 ohms Frequency bandwidth 20 Hz to 20 kHz + 1db at 1 watt. Total distortion at 1 kHz at 9 watts 0.5% Input sensitivities CER. P.U. 100mV into 3 meg ohms. Tuner 100mV into 100K ohms. Tape 100mV into 100K ohms. Overload Factor Better than 26db.

Signal to noise ratio—70db on all inputs (with vol. max). Controls—6 position selector switch (3 pos. stereo and 3 pos. mono). Separate volume controls for left and right channels. Bass ± 14db at 60 Hz. Treble (with D.P.S. on off) ± 12 db at 10 KHz. Tape recording output sockets on each channel. Size 12½in. 6in. 2½in. in simulated teak case. BUILT & TESTED.

MkII (MAG P.U.) £15.75 plus 50p. p. & p.

Specification same as Mk. 1, but with the following inputs. Mag. P.U. CER. P.U. Tuner. Spec. on Mag. P.U. 3mV at 1 kHz input impedance 47K. Fully equalised to within ±1db RIAA. Signal to noise ratio—65db (vol. max).

The £25 Stereo system


The Duetto is a good quality stereo amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

SPECIFICATION—

R.M.S. power output 3 watts per channel into 10 ohms speakers.

INPUT SENSITIVITY. Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.

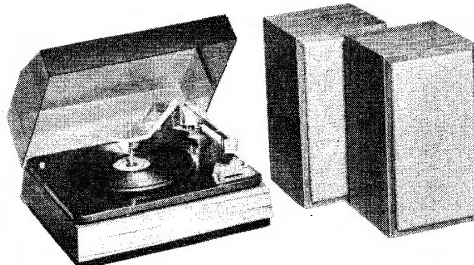CONTROLS: 4-position selector switch (2 pos. mono and 2 pos stereo) dual ganged volume control.




TONE CONTROL Treble lift and cut Separate on off switch. A preset balance control.

Duetto integrated transistor stereo Amp.	£9.50	50p
Garrard Changer from	£7.97	50p
Cover and teak finish plinth	£4.75	50p
Duo Type 1 speakers (see opp. page)	£4.20	50p
The above items purchased together	£25.00	£2.00

SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

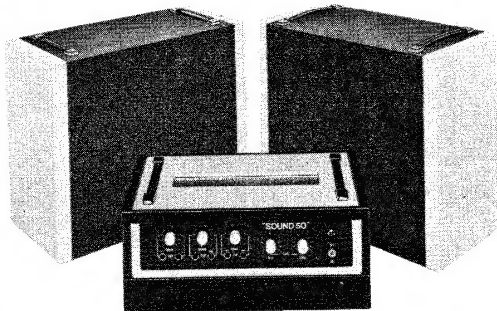

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.


Output Power: 45 watts R.M.S. (Sine wave drive). **Frequency response:** -3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. **Speaker Impedance:** 3, 8 or 15 ohms. **Bass Control Range:** ± 13dB at 60Hz. **Treble Control Range:** ± 12dB at 10 KHz. **Inputs:** 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power. **SPEAKERS!** Size 20" x 20" x 10" incorporating Baker's 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

COMPLETE SYSTEM £50 Plus £4 P. & P.
Sound 50 amp and 2 speakers

or available separately.

Amplifier **£28.50** plus £1.50 P. & P.

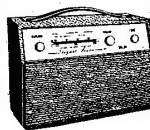Speakers **£12.50** each plus £1.75 P. & P.




The ELEGANT SEVEN Mk. III (350m W Output)

7 transistor fully-tunable M.W.—L.W. superb portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 47p extra.

Price £5.25 plus 50p. P. & P.

Circuit 13p **FREE WITH PARTS.**

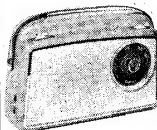


The DORSET (600m W Output)

Price £5.25 plus 50p P. & P.

Circuit 13p **FREE WITH PARTS**

7-transistor fully tunable M.W.—L.W. superb portable—with baby alarm facility. Set of parts. The latest modulsed and pre-alignment techniques makes this simple to build. Sizes : 12 x 8 x 3in.

MAINS POWER PACK KIT: 47p extra.

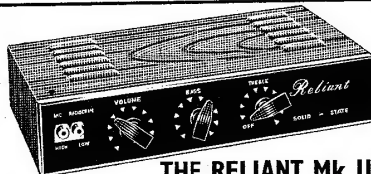

THE RELIANT Mk III SOLID-STATE GENERAL PURPOSE AMPLIFIER

in simulated teak case **£7.25** plus P. & P. 50p

SPECIFICATIONS

Output ± 10 watts. **Output impedance**—3 to 4 ohms. **Inputs** 1. -xtal mic 10mV Tone Controls—Treble control range ± 12dB at 10KHz. 2. -gram/radio 250mV. **Bass control range** ± 13dB at 100Hz. **Frequency Response**—(with tone controls central) Minus 3dB points at 20Hz and 40KHz. **Signal to Noise Ratio**—better than -60dB. **Transistors**—4 silicon Planar type and 3 Germanium type. **Mains input**—220/250V. A.C. **Size of chassis**—10in. x 4in. x 2in. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. **Built and tested.**

THE DUO SPEAKER SYSTEM

Similar in design to those on the previous page the 2-way speaker system is beautifully finished in polished teak veneer. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION:—

Impedance 8 or 10 ohms (please state requirement). It incorporates high flux 7in. x 3in. speaker and 2in. speaker. **Teak finish** 11in. x 6in. x 5in. **£4.20** each. 50p P. & P.

LIQUIDATED STOCK


DANSETTE TOURISTE MK3 CAR RADIO

ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts.

Originally sold completely built for £15.4.6 (£15.23) Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4in deep.

See top of previous page for address

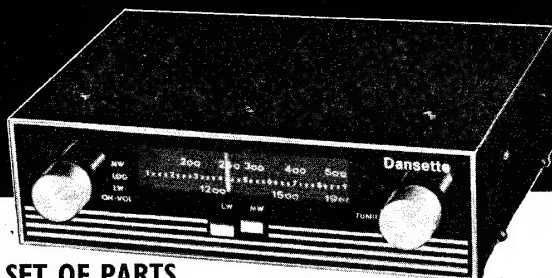

SET OF PARTS

£6.30

plus P. & P. 50p.

Circuit diagram 13p. Free with parts

Speaker, baffle and fixing kit


£1.25 extra plus 25p. p. & p.

Postage free when ordered with parts.

RADIO & TV COMPONENTS
R+TV
(ACTON) LIMITED

NEW FROM TRS

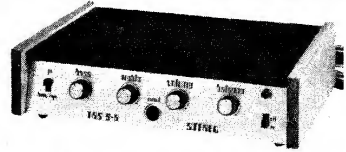This money saving **STEREO 8 + 8 AMPLIFIER**
in a new **PRE-ASSEMBLED MODULAR PRESENTATION**



A new conception in modular assembly which makes construction even easier than ever and results even better. Two pre-amp and two power amp modules, factory built, tested and guaranteed by a world famous maker come to you ready mounted with mains power unit on chassis forming part of the attractive TRS cabinet which simply need wiring for immediate use. A generous 8 watt RMS output per channel into 3-8 ohms is assured. Cabinet with aluminium front, charcoal grey top and wood sides measures 12in x 8 1/2in x 2 3/4in.

- Frequency resp.: 50Hz-16kHz \pm 3dB.
- Input: 110mV per P.U., radio 240mV.
- Output: 8W per channel. RMS into 3-8 Ω . Slightly less per 8-150 speakers.
- Record and playback facilities
- Bass/Treble/Volume/Balance
- Input/On-off controls.
- Extra easy to install.

Complete kit assembled ready to wire up with mains lead and instructions. **Unsurpassed value at only**

£17-50

Carriage and packing 38p in U.K.

COMPONENTS CORNER

VYNAIR speaker and cabinet covering by ICI. Sand 5p for samples—refundable on purchase. 12 1/2p per sq. ft. £1-38 per yd. 48in wide.

BONDACOUST speaker wadding 1in thick, 18in wide per yard 42 1/2p.

VEROBOARD in all latest sizes and forms. inc. 2 1/2in x 3 1/2in, 16p; 2 1/2in x 5in or 3 1/2in x 3 1/2in, 23p; 3 1/2in x 5in, 26p; 17in x 3 1/2in, 75p.

VOLUME CONTROLS. Long spindles all values 5Kohms to 2meg., log or lin., less switch 17 1/2p; with switch 25p.

Twin ganged stereo, 5K to 2meg. less switch, 48p; with switch 100K to 2meg. 52p.

STEREO BALANCE CONTROLS. Log/Anti-log 5K, 10K, 1/2, 1 or 2meg., 55p.

RESISTORS, CAPACITORS, WIRE, etc., etc.

MORE AMPLIFIERS FROM TRS MULLARD VALVES AMPLIFIERS

- 5-10 basic kit (mono) £10-99. Carr. 28p.
- 2 valve mono pre-amp basic kit for above £7-65. Carr. 28p.
- 10-10 stereo amplifier kit £18-99. Carr. 63p.

TRS 50 WATT VALVE AMPLIFIER

A ruggedly built unit in ventilated steel case with carrying handles: size 12in x 8in x 8in. Two input channels mixable (10mV and 150mV) bass and treble controls. EL 34's output (mono) in push-pull, with fixed bias. Excellent for P.A., musical group work, etc. Brand new and guaranteed £30. Carriage 75p.

FOR YOUR STEREO 8 + 8 OR OTHER HI-FI SYSTEMS

PLINTH AND MOTOR ASSEMBLY comprising modern style teak finished plinth cut to take famous Garrard AT6 auto/single playing unit wired for stereo, with hard smoke grey perspex lid. Plinth and AT6 less cartridge (Carr. and packing 53p). **£12.50**

SPECIAL CARTRIDGE OFFER TO PURCHASERS OF ABOVE ONLY

Acos stereo 6P93-1 (sapphire) £1-25.
Sonotone 9TA/HC (diamond) £2.
Various magnetic types from £3-50.

TRS SPEAKER BARGAIN

Ready now—Speaker and cabinet assembly comprising 8" unit (4 ohms) and easy to put together flat-pack cabinet, ported and lined, size 18in x 12in x 9in. £5-50 (carr. 40p).

TRS RADIO COMPONENT SPECIALISTS
70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY
Tel. 01-654 2188

Open all day
Sat., Wed.—1 p.m.

Almost next to
Thornton Heath Stn. (S.R.)

Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a

mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Education Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

Ring

01-637 2171

between 9 a.m. and 9 p.m. and ask for Mr Parsons

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.

Please give me further information.

Name _____

Address _____

Age _____

Phone _____

5D1

**CONTROL DATA
INSTITUTE**

**CONTROL DATA
LIMITED**

The Education Division of one of the world's largest Computer manufacturers.

Astrad ORION

THE WORLD'S SMALLEST TWO WAVEBAND, 6 TRANSISTOR RADIO

Music, news, sport, wherever you are. Fully built and tested, ready for immediate use. NO EXTRAS. This minute radio will play anywhere—anytime, beach, garden, park, home, office, school, etc. The super sensitive 6 transistor circuit is fully tuneable over both long and medium wavebands, with built-in ferrite rod aerial to provide excellent selection. The Orion operates from one tiny battery, either mercury or nickel cadmium, for long life and economical running cost. The output is via a crystal-type personal earphone, giving extreme clarity, which prevents disturbing other people when used in public parks, open spaces, etc. The small size of the Orion allows it to be carried easily in the pocket or handbag, and it is also supplied with an attractive presentation case. Complete with earpiece, battery and carrying case.



Specification: Waveband coverage. Medium 525kc/s to 1,605kc/s; Long 150kc/s to 300kc/s. Sensitivity: 35mV/m max. Selectivity (at -30kc/s detuning) -10dB. Power consumption: 4mA max. Power source: 1 x 1.4V Mercury battery. Mallory type RM625 or equivalent.

COMPLETE WITH EARPIECE ONLY RECHARGEABLE BATTERY POCKET CARRYING CASE **£1.48** Post 18p

*Spare battery 18p extra—post FREE with radio.

GARRARD SP25 MkIII

The SP 25 series record deck has proved to be one of the most popular of its type in the world. Styled in black and silver, this modern-acty priced three-speed unit complies with the Din 45-500 Hi-Fi performance standard. The tubular low resonance aluminium pick-up arm is counter-balanced by a resiliently mounted weight. Stylus force is adjusted by an optical-type knurled knob, finely calibrated from 0.5 grm. in steps of 1 grm. Bias compensation is set with a finger-tip adjustment, the scale being calibrated to correspond with the stylus force. The viscous damped cue control facilities raising and lowering the pick-up arm onto the track required without damage to either the record or stylus. The 10in. aluminium turntable is driven by the well-proven Garrard 4-pole high and low voltage induction motor. Actual size including max. rear and side overhang at pick-up arm 15 1/2in. wide x 12 1/2in. front to rear x 2 1/2in. above and 2 1/2in. below edge of unit plate.



With SONOTONE 9TA Cartridge **£13.95**

EXCLUSIVE TMI & TM5

MODEL TM-1 1000 ohms/v MINI-TESTER

The first of Lasky's new-look top value meters, the TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to $\pm 3\%$ of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case—with white and green metallic/green finishing. Ohms zero.

- DC/V: 0-10-50-250-1,000 at 1K/OPV.
- AC/V: 0-10-50-250-1,000 at 1K/OPV.
- DC CURRENT: 1mA, 100mA.
- Resistance: 0-150k Ω .
- Decibels: -10dB to +22dB.
- Complete with test leads, battery and instructions.



LASKY'S PRICE £1.95 Post 13p Size Only 3 1/2in. x 2 1/2in. x 1 1/2in.

MODEL TM-5 5,000 OHMS/V POCKET MULTIMETER

Another new look pocket multimeter from Lasky's providing top quality and value. The "slimline" impact resistant case—size: 4 1/2in. x 2 1/2in. x 1 1/2in. fitted with extra large 2 1/2in square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

- DC/V: 3-15-150-300-1,200 at 5K/OPV.
- AC/V: 6-30-300-600 at 2.5K/OPV.
- DC Current: 0-300 μ A, 0-300mA.
- Resistance: 0-10k Ω , 0-1M Ω .
- Decibels: -10dB to +16dB.
- Complete with test leads, battery and instructions.



LASKY'S PRICE £2.95 Post 13p

MP.60 McDONALD PROFESSIONAL SERIES FOUR SPEED SINGLE PLAY UNIT

High-precision low-mass fully counterbalanced pick-up arm, heavy balanced turntable, simply operated controls, viscous curing device, slide-in cartridge carrier, four pole motor.



LASKY'S PRICE £12.50 Post 35p

Complete with plinth and cover **LASKY'S PRICE £15.75** Post 40p

610 AUTOMATIC TURNTABLE

Same specifications as the MP60 but with synchronous four pole motor and full automatic change facilities.

LASKY'S PRICE £15.45 Post 35p WITH PLINTH AND COVER £18.75 Post 40p

510 AUTOMATIC TURNTABLE

Counterbalanced pick-up arm, pressed steel turntable, bias compensator, viscous curing and synchronous four pole motor.

LASKY'S PRICE £13.45 Post 35p WITH PLINTH AND COVER £16.95 Post 40p

310 AUTOMATIC TURNTABLE

Low-mass square section pick-up arm, cue and pause lever, visual stylus pressure indicator, slide-in cartridge carrier, four pole motor.

LASKY'S PRICE £9.95 Post 35p WITH PLINTH AND COVER £13.45 Post 40p

BSR McDONALD PACKAGES

PACKAGE No. 1

- BSR McDONALD 510 4 Speed Autochanger £17.00
- AUDIO DEVELOPMENT AD76K Magnetic Cartridge £ 4.50
- BSR Afrotramosia Plinth with black mounting board £ 5.00
- BSR Smoked Perspex Dust Cover £ 3.50

Recommended retail price £30.00

LASKY'S PRICE £26.00 Post 40p
ADD £5.50 if Microseiki M2100/E is preferred
ADD £6.50 if Shure M44/5 is preferred

PACKAGE No.2

- BSR McDONALD 310 4 Speed Autochanger £14.00
- AD76K Magnetic Cartridge £ 4.50
- BSR Afrotramosia Plinth with black mounting board £ 5.00
- BSR Smoked Perspex Dust Cover £ 3.50

Recommended retail price £27.00


LASKY'S PRICE £23.50 Post 40p
ADD 50p if BSR Ceramic Cartridge is preferred

NOW AVAILABLE EXCLUSIVE

LASKY-McDONALD plinth and cover **£4.75** Post 25p available separately at

SOUN SCAN WAFER TYPE ELECTRO DYNAMIC SPEAKER

This revolutionary idea in sound reproduction functions in a similar manner to the cone loudspeaker system. In place of the conventional paper cone is a flat, rigid plastic panel only a fraction of the depth of the equivalent cone structure. With a flat rectangular panel a larger piston area is also available thereby reducing the size compared with an equivalent cone loudspeaker. Power capacity: 20 watts (peak). Free. range, 40Hz-20,000 Hz. Input imp.: 8 ohms. Size: 1 1/2in x 1 1/4in x 1 1/2in. Weight: 9oz.

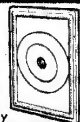

LASKY'S PRICE £5.75 each **£11** for two Post 20p each

Lasky's Radio Ltd

267 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271

33 TOTTENHAM CT. RD, LONDON, WIP 9RB. Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812

152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday


HIGH FIDELITY AUDIO CENTRE

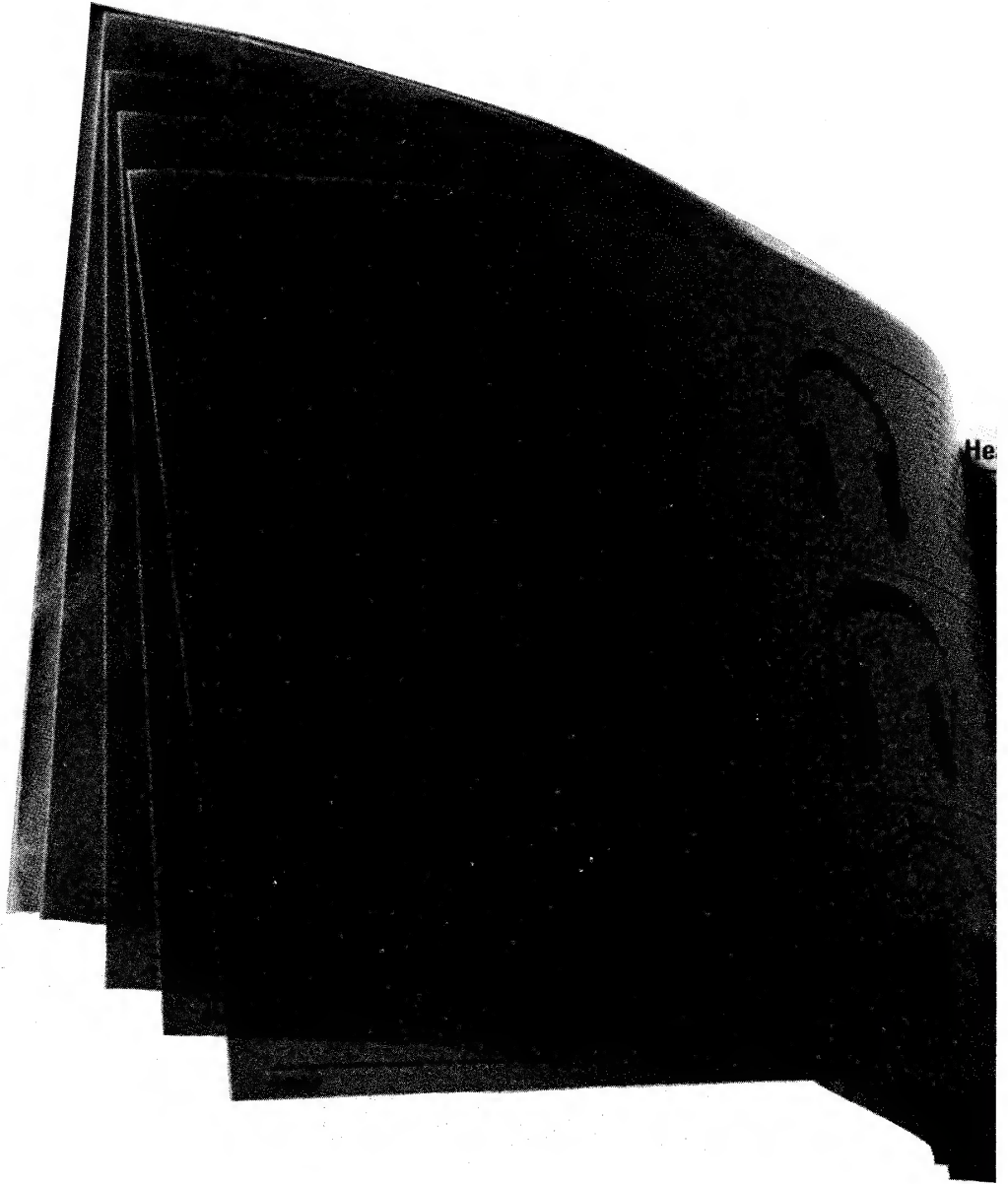42-45 TOTTENHAM CT. RD, LONDON, WIP 9RD. Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday



ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821



The Eagle Annual.

Sorry, no Dan Dare, Digby or P.C. 49. Because this is the new Eagle annual catalogue. And it's packed with interesting things. Like the new TSA 151 stereo amplifier: it uses a new block construction silicon output device for absolute reliability. It's got low noise silicon transistors throughout. Its output is 15 Watts per channel. That's 15 Watts RMS, not an exaggerated figure for maximum music power.

The price? A very reasonable £36. And for people who like to listen to stereo undisturbed, we've got the new SE 100 headphones.

Dual cone transducers are used throughout, and to keep the weight down, the independent volume controls are

mounted on a separate unit with a pocket clip. £16.00.

Every item in the annual has been specified or selected by Gerry Adler. Eagle is Gerry's baby, and he's very fussy about what goes out under the Eagle banner. He gets very twitchy at the thought of a duff diode. A bit like the Mekon in fact.

But he does it for a reason. He believes that if the first Eagle product you buy is O.K., you'll come back for more.

That's what's made Eagle a success.

Eagle International
we don't stand still.

Coptic Street, London WC1A 1NR
Tel: 01-636 0964

Headphones/Accessories



SE 28 Studio Stereo Headphones
This studio quality head-set offers a really extensive frequency response (20 to 20,000 Hz) by means of dome acoustic chambers and specially designed tweeters. Sensitive adjustable attenuators are also incorporated in each dome. Complete with stereo jack plug and cable - a first class instrument.
Frequency Range: 20-20,000 Hz Impedance: 8 Ohms per Channel. Weighting Impedance: 16 Ohms.




SE 80 Studio Stereo Headphones
Based on an entirely new open baffle concept the SE 80 Stereo Headphones have been developed to bring a new standard of comfort to professionals who have to wear a headset for very long sessions. Recording Engineers, Monitor Lists, Broadcasters, D.J.s, etc. Individual Slider Tone controls complete a list of features which include the use of fine leathers for padding.
Frequency Range: 20-20,000 Hz Impedance: 8 Ohms per Channel. Weighting Impedance: 16 Ohms per Channel.

TSA 309 Headphone and Boom Microphone
Designed in the language laboratory of the BBC for professional use, this microphone and boom microphone is designed to capture UK and foreign accents clearly, noise free. The microphone is mounted on a boom which can be positioned to suit the user's requirements.



SE 100 Professional Stereo Headphones
The SE 100 represents the ultimate development of classic design. Built in preference that see audible include force connected dual cone speakers and damped reflex baffles. To keep headset weight to an absolute minimum the independent volume controls are mounted in a separate unit. Leather padding, a 5 metre coiled lead and a moulded stereo jack plug finish a luxury specification.
Frequency Range: 20-20,000 Hz Impedance: 8 Ohms per Channel. Weighting Impedance: 16 Ohms.

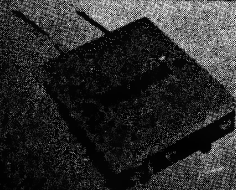

J.B.3 Stereo Headphone Junction Box
This simple, inexpensive unit is essential to stereo headphone users. It connects to amplifier and loudspeakers, phone attenuated stereo headphones, direct with a three-position switch to give headphones only, speakers only, or both together.
Weight: 100gms. Dimensions: 100mm x 50mm x 25mm. Price: £4.95.

Which ever way you choose

LEWIS AUDIO SYSTEMS

Fine equipment
competitively priced




**You are going to enjoy
better listening for
less cost and greater reliability**

(BUILT OR KIT)

MARTIN AUDIOKITS

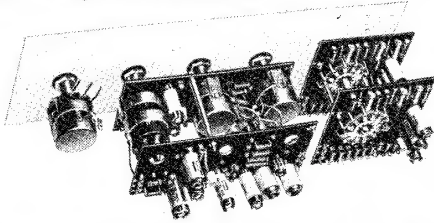For the do-it-yourself enthusiast, the return of a great range of hi-fi modules



ready to play

LEWIS AUDIO SYSTEMS comprise ready built equipment designed and built to advanced technical standards of efficiency and styling. Their prices make true hi-fi available to a wider public than ever. Based on the excellent **Lewis Audio SA. 55** stereo amplifier in which FETS are used in the pre-amp to ensure better quality throughout, the range offers choice of free-standing amplifier with separate playing unit in plinth with plastic hard top or the **Compact** assembly in which the amplifier is built into the base of the plinth and motor assembly. Separate matched speakers are available for either system. Illustrated above is the Lewis S.55 Mk. II Compact System.

LEWIS AUDIO SYSTEMS

SA.55 STEREO AMPLIFIER—6 watts RMS output per ch. into 15 ohm speakers
Controls— Input selector/Vol/Bass/Treble/Balance/ On-Off. Tape Record and replay facilities. DIN socket connections. Modern teak finished cabinet.
R.R.P. £18-90

SC.55 Mk. II 'Compact' with Garrard 2025TC and SA.55 amplifier built into plinth
R.R.P. £40-92

PLINTHS WITH HARD TOPS & FITTED GARRARD UNITS

Garrard 2025TC with Sonotone 9TA/HC
R.R.P. £16-50

Garrard 40B with Sonotone 9TA/HC
R.R.P. £20-16

Garrard SP.25 Mk. III less cartridge
R.R.P. £20-16

LOUDSPEAKERS

LS.16 "Major"—13" x 8" three way system in American Walnut finished cabinet. 8 ohms
R.R.P. £11-70

LS.17 6" three way system in teak or Am. walnut finish. 15 or 8 ohms
R.R.P. £10-80

LS.18 8" three way system in teak or Am. walnut finish 15 or 8 ohms.
R.R.P. £12-60

● TRADE ENQUIRIES WELCOME

Coupon brings information

LOUIS & LEWIS (ELECTRONICS) LTD

154-155, HIGH STREET, BRENTFORD, MIDDLESEX
Telephone 01-560 1161

for the constructor

MARTIN AUDIOKITS were first to make modular unit construction available to the hi-fi enthusiast keen to save by building his own assembly. **AUDIOKITS** were first to feature "add-on-ability" by which a simple system could be expanded to high performance stereo equipment by the addition of easily added on units. Many who built with **MARTIN AUDIOKITS** years ago continue to enjoy unsurpassed quality and reliability from them to this day. **NOW YOU CAN BUY AUDIOKITS AGAIN** to allow you to build a high fidelity system to your personal choice and which will satisfy completely on performance, simplicity of assembly, robustness and reliability. These units are beautifully engineered and solidly built for a lifetime of trouble-free service. You can start with mono and add on units to make stereo, or build with stereo throughout.

TYPICAL MARTIN ASSEMBLIES


1478E Five stage matched input selector unit; controls and pre-amp; power amp. (10 watts RMS into 15 ohms) power supply; front escutcheon plate (mono)
Total price £11-50

1478SE Similar to above but for stereo.
Total price £25-95

9748SE Stereo assembly for use with high grade ceramic and low power mag. pick-ups.
Total price £32-95

All units are obtainable separately.

State pick-up when ordering.

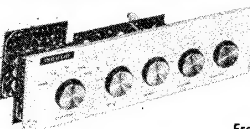

● EACH MARTIN AUDIOKIT MODULE IS COMPLETE IN ITSELF AND REQUIRES THE ADDITION OF NO FURTHER COMPONENTS TO IT.

● ALL UNITS INDIVIDUALLY TESTED AND CHECKED BEFORE LEAVING OUR FACTORY.

Front escutcheon panel of assembly 1478SE

TO LOUIS & LEWIS (ELECTRONICS) LTD. 154 HIGH ST. BRENTFORD, MIDD.

I am particularly interested in
Please send details, (post free) to:

MARTIN AUDIOKITS
LEWIS AUDIO SYSTEMS

NAME

ADDRESS

PW.2

PRACTICAL WIRELESS

VOL 47 NO 1

Issue 771

MAY 1971

TOPIC OF THE MONTH

★ components list!

THE ready supply of components is, of course, the life-line of the radio constructor, even if in these days they are sometimes crammed together to form integrated circuits or grouped and encapsulated as modules. But despite the existence of a vast multitude of components, we still hear of people unhappy about not getting what they want from their local suppliers or via mail order.

Undoubtedly, the supply position forms a different pattern these days; stocks of some items become exhausted quicker than they used to do; new versions appear as alternatives which are not always direct replacements. Years ago, a particular component would stay in a catalogue for a decade, but today's constructors cannot rely on an item staying in stock for even a year. Very often it is a case of 'take it or leave it—while it's there!'

Why, then, should this be so? Well, at the International London Electronic Component Show, opening at Olympia on May 18th, 358. British component manufacturers will be displaying their wares; these companies representing an industry with annual sales of more than £190 million. But despite this huge turnover, there is concern in the trade balance due to increasing imports of components. The exhibition will be a showplace for these competitors, from the USA, France, Russia, Israel, Hungary, India, Japan, Yugoslavia and other countries.

Components, then, are big business—big international business—and the competition is hot. To stay in the race demands investment, production and marketing of a very high level in the teeth of fiercely contesting rivals. Consider, then, this feverish background the next time you call in at your local dealer for a batch of 22k resistors, six 100 puffs and a couple of AF117's!

For the facts of economic life today mean that to many component makers the home constructor either does not exist or is very small fry indeed. In fact, if it were not for manufacturers' spin-offs and end-of-run oddments we would be in a very sad state. So next time you feel like complaining about components, be thankful that we are served as well as we are. Things could be far worse.

W. N. STEVENS—*Editor*

NEWS AND COMMENT

Leader	19
News . . . News . . . News . . .	20
Practically Wireless <i>by Henry</i>	31
MW Column <i>by Charles Molloy</i>	42
Electronotes <i>by S. Ginsberg</i>	42
On the Short Waves <i>by Malcolm Connah and David Gibson, G3JDG</i>	53
P.W. Filmshow	74

CONSTRUCTIONAL

Station Focus Six Receiver <i>by F. G. Rayer</i>	22
Take 20, Audio Amplifier <i>by Julian Anderson</i>	25
Ten Watt Amplifier <i>by Halvor Moorshead</i>	26
Crystal Companion <i>by Eric Dowdeswell</i>	45
Hi-Fi Signal Generator <i>by H. T. Kitchen</i>	48
Sound Effects Synthesiser, Part 3 <i>by F. C. Judd</i>	55
P.W. Workshop Oscilloscope, Part 2 <i>by A. Lester-Rands</i>	61

OTHER FEATURES

NEW SERIES—SERVICING

by H. W. Hellyer and G. J. King
Part 1 *by H. W. Hellyer* 32

I.C. of the Month (Precision
Voltage Detector—PA494)
by L. A. J. Ireland 73


Going Back *by Colin Riches and
Arthur Dow* 77

**JUNE ISSUE WILL BE PUBLISHED
ON MAY 7th**

©IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, ECA 4AD. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, ECA 4AD. Copies of some back numbers are available and orders should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, St. Queen Street, London WC2B 5DD.

NEWS... NEWS... NEWS...

Stereo from Teleton

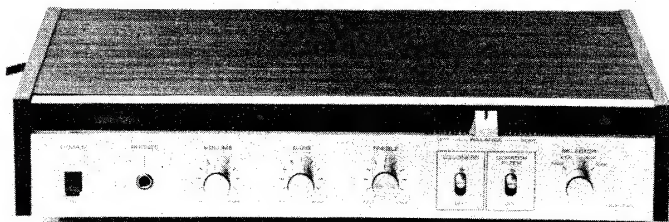

A new stereo amplifier with 26 semiconductors and 18 silicon transistors has been launched by Teleton Electro (UK) Ltd. The new amplifier, known as the SAQ 206, has an output power of 6 watts continuous at 1% distortion and a frequency response of 40-15,000Hz. It is equipped with inputs for magnetic and crystal

pick-up plus tape playback. Output from speakers and headphones is 8 Ω and the model is equipped with both scratch filter and loudness control. The amplifier has a brushed aluminium front and matt walnut cabinet. The SAQ 206 operates at 110/240 volts, 50Hz. Retail price of the SAQ 206 is £32.50.

The "S.S.S."



Briefly explained, this device consists of an electronic synthesiser which when placed between a mono programme source and a stereo amplifier will create a very realistic stereo effect from all forms of music. Whilst quality components are used throughout to give performance consistent with the most expensive high-fidelity equipment, the recommended retail price is just £10.

The most obvious uses to which the simulator might be put are: between tuner and stereo amplifier for the effect of stereo radio from mono transmissions; between a mono/stereo pickup and stereo amplifier to give simulated stereo with mono records; and between tape recorder and stereo amplifier to give the effect of stereo replay with tapes recorded on a mono machine.

Whilst normal retailer outlets, will be used, in order to enable the customer to more easily obtain this product during the early stages of production the company's fullest attentions will be concentrated upon mail order sales (p&p 20p). Their broadsheet on this product is available on receipt of a stamped addressed envelope. *Kampel Electronics Ltd., 99 Old Christchurch Road, Bournemouth BH1 1EP (Tel. Bournemouth 28998).*

Diary Dates

- Apr 19-22.** Physics Exhibition, Alexandra Palace, London.
- Apr 20-21.** Electromation Exhibition, Royal Station Hotel, Newcastle.
- Apr 20-23.** Technicom '71 — Conference and Exhibition, Hotel Technical Communication for Industry and the Professions, Hotel Metropole, Brighton.
- Apr 22-23.** Electromation Exhibition, Grand Hotel, West Hartlepool.
- Apr 23.** Colloquium on Railway Automation (IEE), Savoy Place, London.

Eton Computer

Boys at Eton College, the famous English public school, are learning the language and concepts of computers with the assistance of a Marconi-Elliott machine. A "903" computer is now in operation at the school and pupils are using it to learn what computers are, what they do, and how one makes them do it. By operating the 903 themselves, the boys are picking up the 'jargon' of the computer world, gaining knowledge of order and instruction codes and probing the intricacies of program writing.

The 903 is also being used more directly as a functional 'tool' by senior boys and members of the Eton staff to help them in the work that they are carrying out. For example, a teacher of Astronomy is using the processor to perform many of his more complex calculations.

Cassette Cleaner



The Bib Division of *Multicore Solders Limited, Hemel Hempstead, Hertfordshire*, announce the introduction of their new Cassette Tape Head Cleaning Tape, suitable for all compact cassette type recorders and car playing units.

The unit comprises a cassette tape container in which high quality cleaning tape has been incorporated to clean tape heads, capstan and pinch wheel. It is very simple to use, in the same manner as a tape cassette it is placed in the machine and operated in the play-back position. The whole operation takes only about a minute. A plastic container is provided in which to keep the cleaning tape cassette. This accessory retails at 10s. 7d./53p including p.t. and is available from leading Hi-Fi shops.

NEWS... NEWS... NEWS...

Mr. Fillmore



After a brief illness Mr. Leonard Walter Fillmore, Managing Director of Jackson Brothers (London) Limited died on the morning of Saturday, January 30th, aged 67. With his father and brother he founded Jackson Brothers in the early twenties and pioneered the development of Variable Capacitors and associated Drive Mechanisms. His inventive genius led to many patents in Components for communications equipments over a span of nearly 50 years.

During the war years he was very active on Ministry Standardisation Panels. From then right up to the time of his death he worked on Panel 'F', the Variable Capacitor Standardisation Panel of R.E.C.M.F. He was Chairman of Panel 'F' from September 1951 to January 1965. On relinquishing the Chairmanship he continued as Vice Chairman. Thus for nearly 30 years he devoted considerable time and energy to the Establishments of Standards both National and International for Variable Capacitors. His earlier work on the production of R.I.C. and R.C.S. Specifications has had great influence on the evolution of current International Specifications (I.E.C.).

In recent years he was deeply involved in the preparation of detailed Common Standards under the present Burghard System. His death is not only a great personal loss to his many friends but also to the entire Electronic Industry.

Group One

About a year ago, Home Radio (Components) Ltd., formed a buying group with about 15 other dealers in the London area, which they provisionally called "Group One". Its primary object was to buy components at the best prices in reasonable quantities. There are several secondary aims such as exchange of surplus stock and information.

In a letter to PRACTICAL WIRELESS, Mr. A. Sproston, a Director of Home Radio, says, "To some extent this has been forced on us because we wished to buy certain items that wholesalers do not wish to handle and the manufacturers will only sell in quantities that are beyond the pocket of one dealer to buy. But I would like to stress the fact that this is not aimed at distributors or wholesalers (I for one have always believed that they do a useful job and earn their money) in fact any small wholesaler or manufacturer would be welcome to join. I feel sure that you will agree this is a desirable scheme as ultimately it means we can offer readers a greater range of goods at the lowest prices. Initially we are going to limit it to about 20 dealers (not on account of any closed shop principle, but because we thought — quite wrongly — that we could not handle the administration of a larger number). Now we would like to offer membership to any Bona Fide trader in the U.K. and I would be very grateful if you could make this generally known through your columns. At the moment there is no entrance fee or subscription, if anyone is interested please write to me. Home Radio (Components) Ltd., 234-240 London Road, Mitcham, Surrey, CR4 3HD.

U.K.-Finland

The United Kingdom — Finnish trade deficit of over £72m appears to be set for a £10m reduction as a result of the British Trade Drive in Finland. Britain is now the third in the list of suppliers to Finland.

Camera catch

A camera which not only photographs a traffic offence at the moment it happens, but also simultaneously records the time and the date on the same negative, may soon be used by police forces in the U.K.

It has been developed by a South African company and is already in use by the police in that country.

Known as the Traffacam, the camera can be powered by either the car battery or the built-in power pack of eight Mallory Manganese Alkaline Mn1500 penlight size batteries for fully automatic instant use.


Spanish appliances

Fabrelec, one of Spain's biggest manufacturers of electrical appliances, and Westinghouse Electric Corporation, have signed patent licences, technical assistance agreements and trademark agreements for the manufacture of electrical appliances.

Powerful

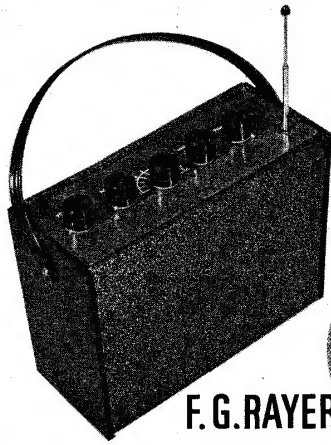The new range of seven zinc carbon batteries now being marketed by Mallory Batteries for general electrical and radio appliances. These are in addition to the mercury and alkaline batteries marketed under the company's Duracell brand name. Mallory Batteries Ltd., Gatwick Rd., Crawley, Sussex.





STATION FOCUS SIX

F. G. RAYER




WITH many transistor portables, tuning is somewhat sharp and possibly tricky, especially at the high-frequency end of the medium wave band. The receiver described here overcomes this by using "station focus"—a control which allows oscillator tuning to be shifted slightly, for easy and exact tuning of a signal.


The circuit is shown in Fig. 1, and a ferrite rod aerial is used for normal reception. This gives sufficient signal strength from most transmissions likely to be required. For weaker signals, or during those times of day when reception is less good, a telescopic aerial can be extended. This is coupled to the tuned winding of the ferrite rod, L1, by the small capacitor C1. VC3 is an aerial circuit trimmer, allowing L1 to be peaked for maximum possible efficiency on all frequencies, with the aerial closed or extended.

Normal medium wave coverage is about 550-1600kHz. In the interests of easy switching, full long wave frequency coverage is not provided. However, switch S1 places TC1 and C2 across L1, and S2 puts TC2 across the oscillator coil L3. This allows a narrow band around 200kHz to be tuned for BBC Radio 2 transmissions on this frequency.

Tr1 is an OC170, followed by two double-tuned i.f.t.'s with AF117 transistors, and this combination gives good sensitivity and selectivity. The OA81 diode D1 used with i.f.t.3 provides automatic gain control bias in the usual way, through R9, and VR1 is the audio volume control.

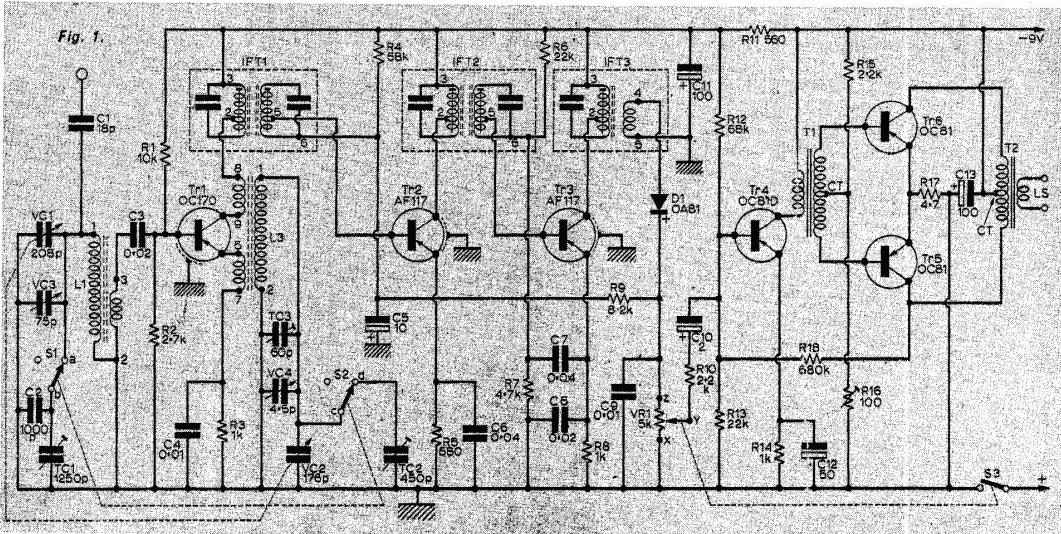The driver stage Tr4, OC81D, and output pair Tr5/6, 2 x OC81, are straightforward and give ample volume. R18 is for negative feedback over these stages, while R16 is adjustable, so that base operating conditions for Tr5/6 can be set for best results.



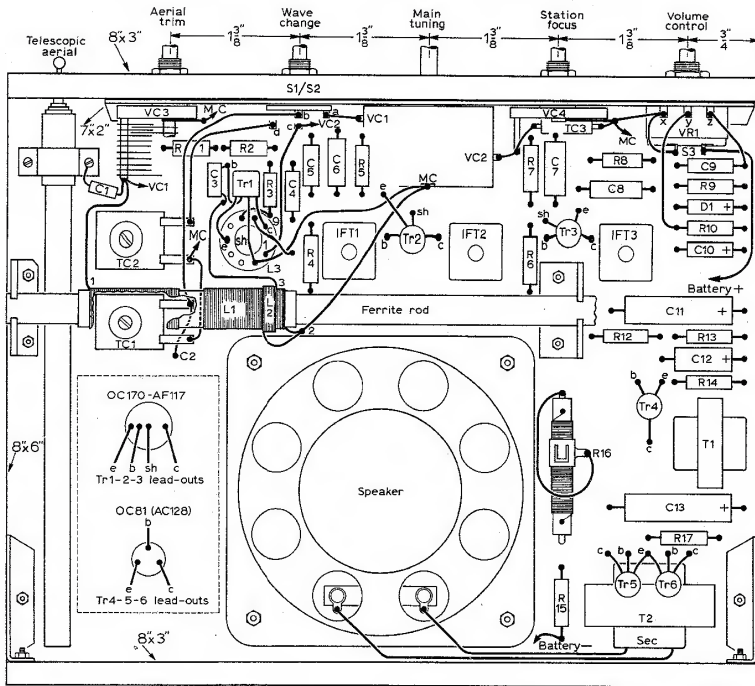

General Construction

The way in which the receiver is assembled is very convenient for wiring, testing and adjusting. The loudspeaker and all small components are on an 8 x 6in. perspex panel. A 7 x 2in. flanged aluminium plate ("universal chassis" ready-formed side) is bolted to the top of this panel, and carries the variable capacitors, switch and volume control. A three-ply panel 8 x 3in. is secured with the bush nuts of these items, and projects about $\frac{3}{8}$ in. over the wiring side of the 8 x 6in. panel. At the bottom of the 8 x 6in. panel, a further piece of three-ply also 8 x 3in. is fixed with brackets.

With this form of construction, the receiver will rest in any position, to insert and wire components and will stand vertically in a normal working position, without a cabinet. The bottom piece 8 x 3in. carries the battery. The controls are on the top, so the whole receiver can be lowered into the case which clears 8 x 6 $\frac{1}{2}$ x 3in. inside and has apertures opposite the speaker.

The 8 x 6in. panel is

$\frac{1}{8}$ in. perspex, so that all components and connections can be seen from either side. If this feature is not required, the receiver can be built on a paxolin panel.

Perspex is usually supplied covered on both sides with paper, which is left in place until cutting and drilling are finished. The panel is marked out to take components as in Fig. 2. A $\frac{1}{16}$ in. drill was used for the wire ends of resistors, etc., and $\frac{1}{8}$ in. for bolts which hold the speaker, brackets, etc.

Drilling positions for the i.f.t. pins can be found by pressing paper on pins, then locating the paper on the panel, and marking through with a sharply pointed tool. A central hole is necessary under i.f.t.1 and i.f.t.2, to take a trimming tool.

The speaker aperture is most readily cut with an adjustable washer or tank

cutter, but can be made with a fine toothed saw.

Check the holes against Fig. 3. Drilling is much easier before any components are mounted, but if any holes are missed, they can be drilled later. Drill the 7 x 2in. flanged plate and panel, so that they can be secured together with the two bolts

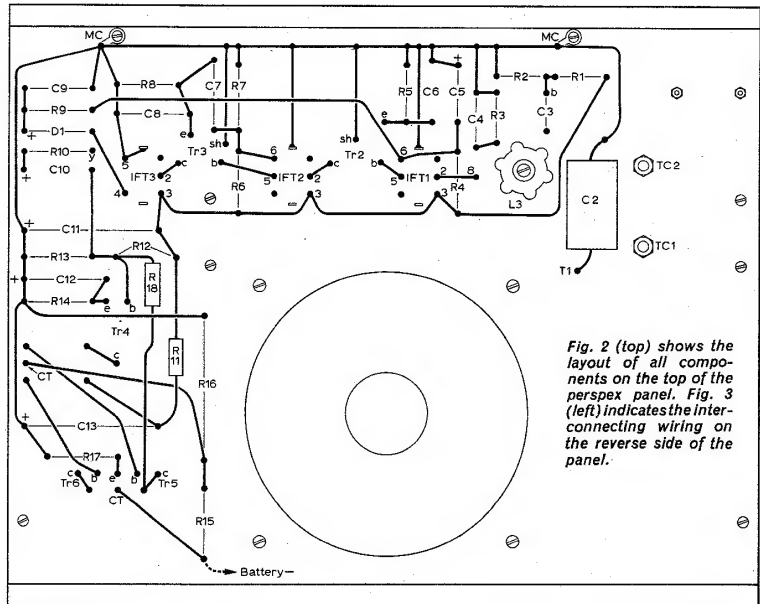


Fig. 2 (top) shows the layout of all components on the top of the perspex panel. Fig. 3 (left) indicates the inter-connecting wiring on the reverse side of the panel.

marked MC in Fig. 3. This plate is to the right in Fig. 2, to clear the extending aerial.


Fig. 2 also shows the spacing for the variable capacitors the holes for which are most readily made with a punch. VC1 is held with three bolts which run into tapped holes in the front plate. These bolts must be very short, or washers must be added, so that the ends do not foul the moving or fixed plates of the capacitor.

The ferrite rod and speaker are left off until last.

Wiring Tips

Place tags under the bolt heads and nuts of both bolts MC, Fig. 3. A 20 s.w.g. bare tinned copper wire is soldered from tag to tag, as shown, as a positive or "earth" return and VC1/2 is connected to this circuit through the metal plate. Connect VC3 and VC4 to the adjacent tags this side, Fig. 2, and also X on VR1, and S3.

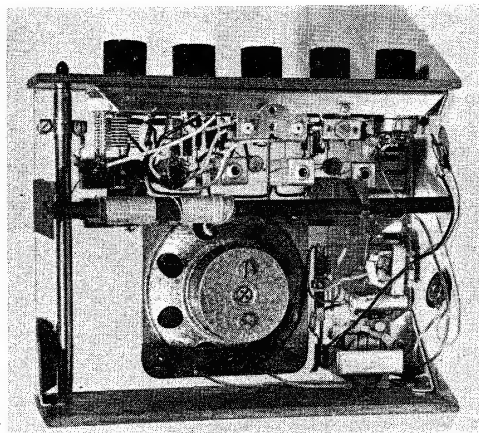All other wiring is carried out with 26 s.w.g. tinned copper wire, with 1mm. insulated sleeving. It is convenient to use red for all "earth" or positive circuits, black for negative circuits, and some other colour for other connections.



Compare this view of the completed receiver with Fig. 2.

I.F.T.'s 1 and 2 have slightly closer spacing between pins 1 and 2, and 5 and 6, as in Fig. 3 and must be inserted and wired this way. The cans of all i.f.t.'s are earthed.

As a check, each component can be marked with coloured pencil on the diagrams as it is inserted and each connection can be similarly marked, as it is made. If this is done systematically, it is unlikely that anything will be omitted.

Electrolytic capacitors must be inserted with the polarity as shown. Trimmers TC1 and TC2 are of a type which can be secured with nuts (Fig. 3). The small trimmer TC3 can be soldered across VC4, or supported on a small bracket from the flange.

The telescopic aerial is fixed so that it can be drawn up through a hole in the top panel. Wire VR1 to MC, C9 and R10 as shown, and run red flex from the switch on this control, S3, soldering on a positive battery clip. The battery negative lead comes from R15.

Connect a flexible lead from the slider of R16, to one end, as in Fig. 2.

Transistors

These are best added after the resistors and capacitors. Fig. 2 shows the four leads of Tr1, Tr2 and Tr3, which are for emitter, base, shield and collector.

Transistors Tr4, Tr5 and Tr6 have three leads, for emitter, base and collector, as shown in Fig. 2. If Tr4 is an OC81D and Tr5/6 are OC81's, with leads in line, then a red spot indicates the collector.

Shape the leads so that they are clear of each other, and will pass down through the correct holes. The transistors can be about 1/2 in. clear of the panel, but leads should not be unnecessarily long in the i.f. stages. They are then soldered as in Fig. 3, and snipped off.

Form the leads of Tr1 as in Fig. 2, and put sleeving on them before soldering. With Tr5 and Tr6, both emitter wires go through a single hole, to R17. Place D1 with its polarity as shown.

Heat shunts are not generally required if the connections are soldered rapidly with a properly heated iron. The iron is removed immediately the joint is made.

★ components list

Resistors:

R1 10kΩ	R7 4.7 kΩ	R13 22kΩ
R2 2.7kΩ	R8 1kΩ	R14 1kΩ
R3 1kΩ	R9 8.2kΩ	R15 2.2kΩ
R4 68kΩ	R10 2.2kΩ	R16 100Ω*
R5 680Ω	R11 560Ω	R17 4.7Ω
R6 22kΩ	R12 68kΩ	R18 680kΩ

All 1/4W 10% except R16 * Pre-set (Home Radio VR101) VR1/S3 5k Ω pot. (log) with switch.

Capacitors:

C1 18pF	C6 0.04μF	C11 100μF 12V
C2 1000pF 5M5%	C7 0.04μF	C12 50μF 6V
C3 0.02μF	C8 0.02μF	C13 100μF 12V
C4 0.01μF	C9 0.01μF	
C5 10μF 6V	C10 2μF 6V	

VC1/VC2	208 ± 176pF ganged (Jackson)	
VC3	75pF air-spaced variable, miniature.	
VC4	2 to 4.5 pF air-spaced variable, miniature.	
TC1	1250pF pre-set (Home Radio VC29SA)	
TC2	450pF pre-set (Home Radio VC29R)	
TC3	60pF pre-set	

Semi-conductors:

Tr1 OC170	Tr4 OC81D (or AC128)
Tr2 AF117	Tr5 OC81 (or AC128)
Tr3 AF117	Tr6 OC81 (or AC128)
	D1 OA81

Inductors:

L1/L2	Ferrite rod aerial (M.W. only) (Denco FRA1)	
IFT1	IFT18/465 (Denco)	IFT2 IFT18/465 (Denco)
	IFT3 IFT14/465 (Denco)	
L3	Range 2T Red (Denco)	

Miscellaneous:

Speaker, 3 1/2 in 3 Ω. T1, Driver transformer (Home Radio TR64). T2, Output transformer (Home Radio TR65A). S1/S2, 2 pole 2 way switch. Telescopic aerial with bracket. Universal chassis member 7 x 2 in. (Home Radio CU136). Knobs (5). Perspex (or paxolin) 8 x 6 x 1/8 in. Plywood 8 x 3 in. (2 off). "Radio Constructor" panel transfers.

TO BE CONTINUED

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.

IT is the aim of this page to give circuits and explain the operation of the simplest type of circuits and we are of course limited to £1.00 and twenty components and obviously this places certain restrictions on the quality of the finished articles. Nevertheless simplicity also leads to a lesser likelihood of mistakes and the circuits usually have a wide range of uses in many fields. This month's project fits into this category; it is an audio amplifier which may be used to boost the output of an earphone type radio, as a pickup amplifier or an intercom. It is extremely simple and, to my knowledge, has never been published before.

THE CIRCUIT

The secret of the simplicity of the circuit shown in Fig. 1 is the directly coupled Darlington Pair of transistors, Tr1 and Tr2. This configuration, which is also known as a super-alpha pair, acts rather like a single transistor with very high gain, the base being represented by the base of Tr1, the emitter by the emitter of Tr2 and the collector by the common collector connections. The gain of this combination is roughly equal to the products of the gains of the individual transistors. With the specified transistors the minimum gain should be no less than 8,000 using the green version of the 2N2926 (highest gain grouping) or a maximum of over 20,000!

With gains of this sort of order it's not surprising that few components are needed.

If one looks upon a transistor as a resistor whose value between the emitter and collector alters, depending on the base bias applied, it can quickly be seen how the circuit operates—and why the gain is so high. Regarding the operation in this way, Tr1 becomes a variable bias resistor for Tr2 so that the higher the input signal, the greater the bias.

The quiescent current through the transistor pair depends on the value of R1 and although the value shown—1.8M Ω —worked well with several transistors used for Tr1 and Tr2, the value does depend on the gain of the pair and may have to be selected from a range between 680k Ω and 3.9M Ω .

The quiescent current through Tr2 is fairly high—20mA or so—and it is for this reason that we are using a BFY51 rather than a transistor with a lower current handling capacity.

C1, VR1 and C2 simply act as d.c. blocking capacitors and as a volume control. The input impedance of this type of circuit is high and this allows for the use of low value blocking capacitors in conjunction with a high value volume control—here a 1M Ω type is used. It is not recommended to substitute an 8 Ω or a 3 Ω speaker directly into the collector circuit, though the use of a transformer with a ratio of about 5:1 would allow these to be used.

No. 25 AUDIO AMPLIFIER

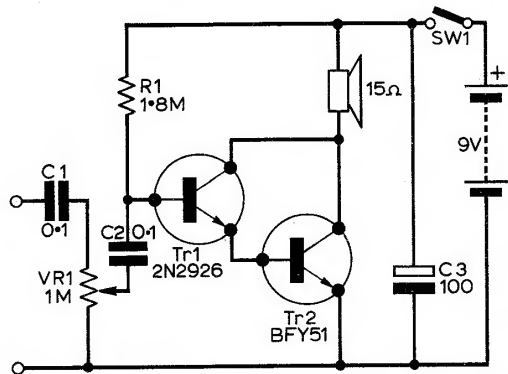


Fig. 1. The circuit of the "Take 20" Darlington pair audio amplifier

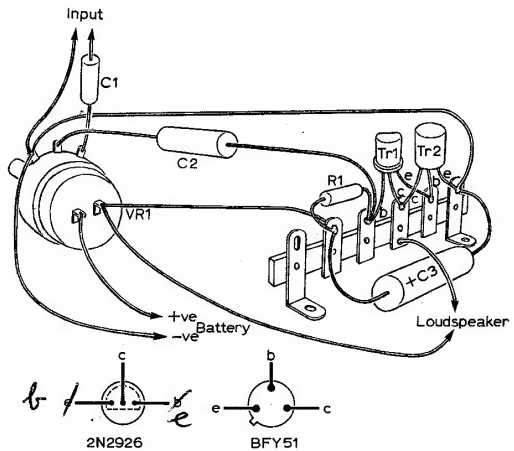


Fig. 2. A suggested layout for the amplifier using a small tag-strip; the transistor lead connections are shown below, viewed from the lead ends.

A suggested layout on a short tag-strip is shown in Fig. 2, though as the circuit is published as a general purpose type, it will normally be built as part of some other circuit.

A PP9 battery should be sufficient for this circuit; the smaller PP3 type will be unable to supply the necessary current as the power output of the amplifier will be about 200mW. This output level is quite adequate for most uses.

The final quality is surprisingly good and all-in-all the circuit will be found to be a very useful one. ■

10 WATT



AUDIO AMPLIFIER

HALVOR MOORSHEAD

IT is difficult to fit the amplifier described in this article into any normal category. By the DIN specification it is probably Hi-Fi but by current accepted standards of Hi-Fi it leaves a little to be desired.

The ten watt output is far higher than normal record player amplifiers, yet is well below the usual 25W which now seems to be the lowest power acceptable.

It is neither as cheap to build as the amplifiers featured in "Take 20" but neither does the cost approach that of commercial amplifiers. So this amplifier is in the "Mid-Fi" field. The quality is good—laboratory tests show a flat output from 40Hz to 20kHz with harmonic distortion below 1% at 1kHz at 5W output. This distortion level is high by prevalent standards but since the human ear cannot distinguish even 2% of harmonic distortion, it hardly matters.

The cost of the project is low. The amplifier by itself should be rather less than £5 and the cost of the separate power supply will probably add another £3—these prices do not, of course, include the loudspeakers.

The circuit and the construction details cover a mono version but naturally when doubled up, using dual pots for the volume and tone controls, and fitted with a balance control, it would be perfectly satisfactory for stereo.

Since the amplifier as described does have limitations in performance, it is not intended for use with expensive magnetic pickups and it is assumed that it will be used with ceramic or crystal types. If a magnetic pickup facility was to be incorporated, correction would also have to be applied.

No great originality is claimed for the circuit—it is largely based on Mullard designs though slight modifications have been incorporated. The output transistors are the common AD161-AD162 complementary pair and closely matched pairs of these are currently available for as little as 50p though they are more commonly sold for 80p.

The finished amplifier, in the monophonic version, is small, though not so small that construction is difficult and it was designed to this size so that it can fit into almost any record player cabinet. If the amplifier is to stand on its own a wooden surround

would improve appearances. The power supply is built separately and this can be mounted quite a distance from the amplifier—if fitted into a record player this can be fitted at the back.

Loudspeakers are not dealt with as this is a completely different field but the impedance can be anything between 5Ω and 15Ω. The amplifier has been tested running for several hours at full output on a 3Ω speaker system but this low impedance cannot be recommended in all cases, though no harm came to the prototype.

The hum and noise level are extremely low; at full output they were only just audible with an ear inside the speaker cone and at a foot away, non-existent.

One of the problems with home built amplifiers of this type is instability, the author has often come across this and knows of others who have experienced the same problems.

The design shown should be unconditionally stable and two features are incorporated in the circuit to increase stability, even though without them the stability was good; this means that anyone building the amplifier can be sure that these problems will not arise even if the layout chosen would tend to oscillation.

THE CIRCUIT

The complete circuit, apart from the power supply, is shown in Fig. 1 and this comprises three main sections: the preamp., the tone control and filter stage and the output amplifier.

It has already been mentioned that the amplifier is designed for use with ceramic or crystal pickups. Although these have got a very high output—at the very least 80mV and often ten times that level, the inherent impedance of these types is high and unless they are coupled to a high input impedance, the frequency response will suffer. Transistors in the common emitter mode have typical input impedances of about 20kΩ, far too low to mate the pickup to, so for this reason the inputs are connected directly to a 1MΩ resistor in series with the input and this, of course, determines that the input impedance is at

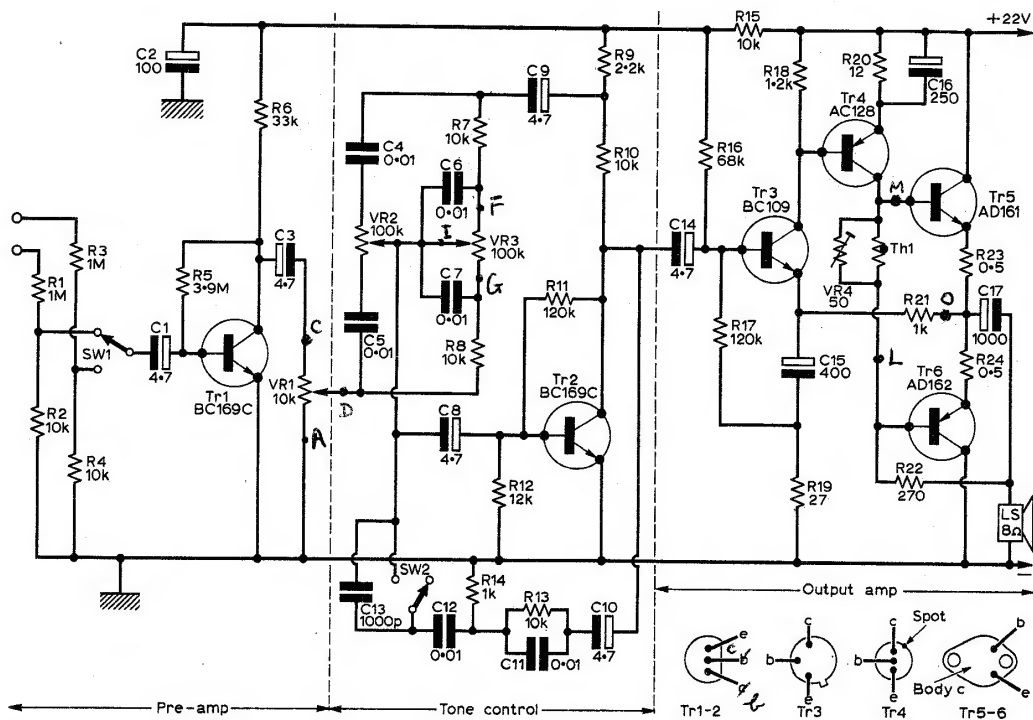


Fig. 1: The complete circuit of the 10W amplifier. A full description of the operation and function of the components is given in the text.

★ components list

Resistors			C5 0.01 μ F	C14 4.7 μ F 15V
R1 1M Ω —see text	R13 10k Ω	C6 0.01 μ F	C15 400 μ F 15V	
R2 10k Ω	R14 1k Ω	C7 0.01 μ F	C16 250 μ F 6V	
R3 1M Ω —see text	R15 10k Ω	C8 4.7 μ F 15V	C17 1000 μ F 25V	
R4 10k Ω	R16 68k Ω	C9 4.7 μ F 15V	C18 2500 μ F 50V	
R5 3.9M Ω	R17 120k Ω	Semiconductors		
R6 33k Ω	R18 1.2k Ω	Tr1 BC169C	Tr6 AD162	
R7 10k Ω	R19 27 Ω	Tr2 BC169C	TH1 VA1077 (32 Ω) (Electro-value)	
R8 10k Ω	R20 12 Ω	Tr3 BC109	BR1 Silicon Bridge Rectifier—see text	
R9 2.2k Ω	R21 1k Ω	Tr4 AC128		
R10 10k Ω	R22 270 Ω \pm W	Tr5 AD161		
R11 120k Ω	R23 0.47 Ω (or 0.5 Ω) 2W	Miscellaneous		
R12 12k Ω	R24 0.47 Ω (or 0.5 Ω) 2W	SW1, SW2 Miniature changeover slide switches		
All resistors \pm W, 5% except where stated		Transformer 250V pri., 17 or 18V secondary, 1.5A		
VR1 10k Ω log.	VR3 100k Ω lin.	Fuse With fuseholder, 1A		
VR2 100k Ω lin.	VR4 50 Ω skeleton preset.	Metal Chassis 7in x 4in x 1 $\frac{1}{2}$ in, H. L. Smith Ltd.		
Capacitors			Sockets Input, 3-pin DIN, Output, DIN L.S. Type	
C1 4.7 μ F 15V	C10 4.7 μ F 15V	Tagstrip 2-way		
C2 100 μ F 25V	C11 0.01 μ F	Veroboard 0.15in matrix, 4 $\frac{1}{2}$ in x 2 $\frac{1}{2}$ in		
C3 4.7 μ F 15V	C12 0.01 μ F	Heatsink Wrap around type for AC128		
C4 0.01 μ F	C13 1000pF			

least this high.

Two inputs are provided and as shown are for similar levels and impedances. One is provided for the pickup, the other for a radio tuner. Radio tuners have outputs which vary from about 50mV to 1V and R3 (if the tuner is to be connected to this section)

may well have to be varied from the given value to match the tuner used. The value shown is suitable for 500mV.

For a 1V output it should be 2M Ω while for 50mV it should be 100k Ω . Since the output impedance of tuners is rarely high it doesn't matter if the input

impedance is lower for this side. In any case the value should be chosen so that the levels at the input to Tr1 are similar for both tuner and pickup.

Therefore R1 and R2, R3 and R4 act as the input attenuators and matchers. The output for the attenuators go directly to the input select switch and the output from this goes to the base of Tr1 via the blocking capacitor C1.

The function of Tr1 is to raise the level of the signal to a suitable level to feed the tone control network and overcome the necessary attenuation brought about by the input resistors. Tr1 is a BC169C, a plastic version of the low noise BC109. R5 provides the base bias and is of this high value because of the high gain of the transistor.

The output of the preamplifier connects via the blocking capacitor C3 to the volume control, a 10kΩ log. potentiometer. If a stereo version is to be built the only additional component necessary would be a balance control which fits at this point in the circuit. This should be a 25kΩ linear pot., the outer tags connecting to the sliders of the two volume controls with its own slider going to chassis.

The output from the volume control goes to one side of the tone control network comprising VR2, VR3, C4 to C7 and R7 and R8. The other side of the tone control network is connected to a negative phase signal so that the output of the network can be varied from minimum bass and treble to maximums of the same signals.

The output of the network connects to the base of Tr2 which is biased by R11 and R12. The feedback to the tone control network is taken from the potential divider R9 and R10 which between them form the load for Tr2.

Another output from the collector of Tr2 is taken via blocking capacitor C10 to the "Hi-Cut" filter which is designed to couple back to the base as little of the frequencies below 7kHz as possible and as much of the higher frequencies as possible. As the filter is connected in the negative feedback mode

this has the effect of giving a very steep cut above 7kHz and acts very effectively as a scratch filter for poorly treated or old records.

In addition when used to amplify radio signals it will help to get rid of the higher frequency heterodynes present on many a.m. signals after dark.

A filter of this sort should not be confused with a tone control which is designed to gradually slope the high or low frequencies. The "Hi-Cut" filter is designed to have little effect below 7kHz and a lot above it.

The filter is switched in or out by SW2 but C13 is arranged to couple at all times. This is included so that even with the filter out there is a very steep cut at a much higher frequency—about 40kHz—and signals much above this are completely eliminated. Since this is well outside the audio range it in no way impairs the quality but it does serve two other functions.

The fantastic frequency response of the silicon transistors used in modern audio amplifiers leads to the amplification of any r.f. signals picked up in the wiring which tend to be detected at some point

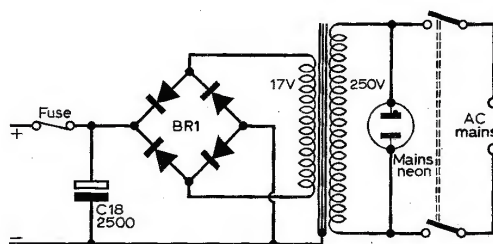


Fig. 2: The power supply circuit.

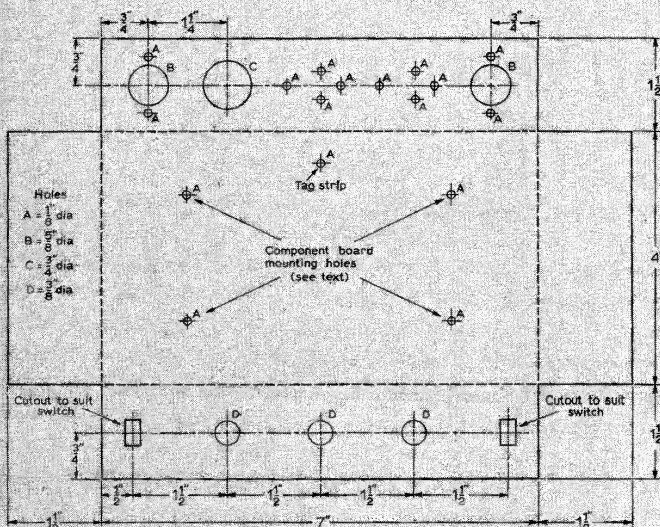


Fig. 3: The drilling of the chassis. A suitable inexpensive one, as used in the prototype is available from H. L. Smith Ltd., 287 Edgware Rd., London W.2.

in the circuit. The high input impedances included in the earlier stages do nothing to help this. The filter completely eliminates these problems.

For similar reasons it is quite common for instability to become a problem, output signals of a high level being capacitively coupled to the input circuitry. The filter greatly reduces the likelihood of this.

The output of the tone control couples to the output stage and is first amplified by Tr3 whose emitter is held at half the supply volts which appear at the junction of R23-R24 and is smoothed by C15. The inclusion of R19 incorporates a degree of negative feedback and thus improves the quality and stability of the output stage.


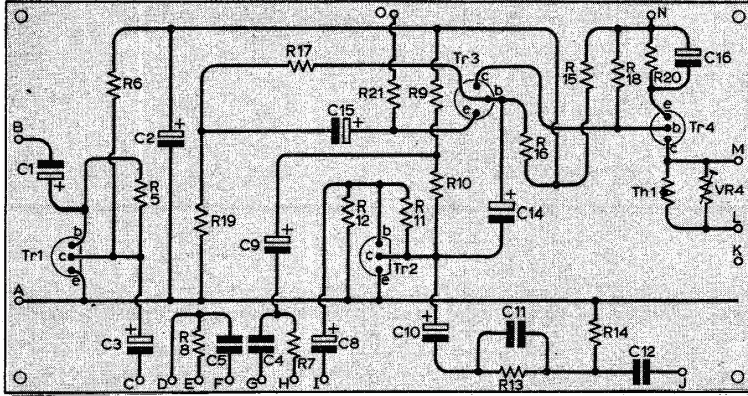
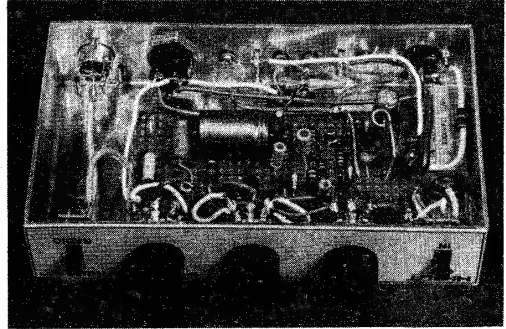


Fig. 4: The component layout on plain veroboard.

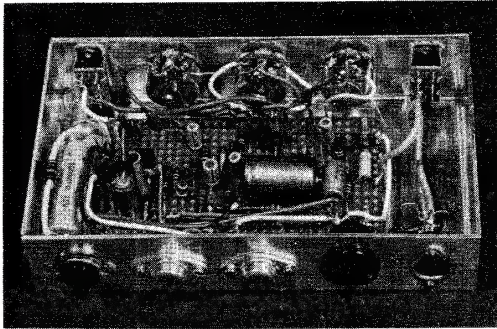

Two internal views of the 10W amplifier showing the general layout. Compare these with Figs. 4 and 5.

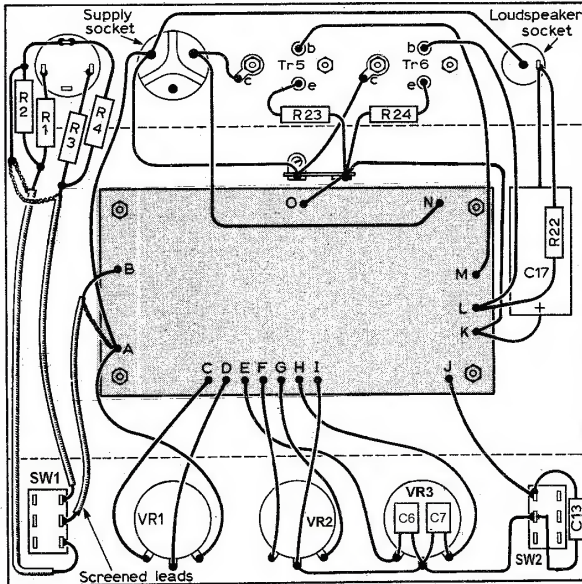


Fig. 5: The wiring between the component board and those components mounted directly on the chassis.

The output from Tr3 is directly coupled to the driver transistor Tr4, a p-n-p germanium type, which, because of the high currents it is passing must be protected from runaway by R20, decoupled by C16.

The output from Tr4 is coupled to the bases of the output pair Tr5 and Tr6, the slight bias necessary between them provided by the thermistor Th1 whose slope is made linear by paralleling it with a 50Ω preset whose setting also determines the quiescent

current in the output stage.

A degree of feedback is applied by connecting the load resistor of Tr4 (R22) through the loudspeaker.

The output of the complementary pair provides the low impedance output via C17 which has to be high in value to effectively couple the bass notes to the loudspeaker.

Amplifiers of this type require a low impedance power supply—batteries will be no good. The current drawn varies between a few milliamps and an amp. The transformer has a primary winding of 250V with a 17V, 1A secondary which connects to the Bridge Rectifier BR1. Various types are suitable and some inexpensive plastic encapsulated types such as the Mullard BY164 are highly suitable. However any type with a voltage and current rating of 30V, 1A should be satisfactory.

To keep the hum level down to an acceptable level, the reservoir capacitor has to be of a high value. Some protection to both the power supply and the amplifier is provided by the 1A fuse in the line.

Careful smoothing of the supply voltage is necessary in the earlier stages and this is catered for by C2; any value lower than this may lead to low frequency instability. If motor-boating does occur the value of C2 should be increased.

CONSTRUCTION

The amplifier is built inside a small aluminium chassis $7 \times 4 \times 1\frac{1}{2}$ in. with one long side holding the controls with the inputs, outputs and power transistors sited on the back. The drilling of the prototype chassis is shown in Fig. 3.

Small slide switches are used for SW1 and SW2 and rectangular holes have to be cut at each end of the control panel for these. Slide switches are designed to be bolted to the chassis but a much smarter and easier job is made by gluing these on using Araldite.

The holes for the power transistor leads and mounting screws are most easily made by using the mica washers, which should be provided with the transistors, as a template.

On the prototype the supply is arranged to plug in using a Bulgin connector, but of course a simple hole fitted with a rubber grommet would be just as good to feed the two wires to the power supply.

To make the wiring short, a small tag strip should be mounted near the output transistors to hold R23 and R24.

The majority of the components are mounted on a piece of plain Veroboard, 0.15 in matrix, sized $4\frac{3}{4} \times 2\frac{1}{2}$ in. The siting of the components on this is shown in Fig. 4. C15 is a bulky component and has to be sited as shown in order to fit in.

Tr4 will be warm in operation and it is important that a heatsink is fitted to avoid thermal runaway. The output transistors also need a heatsink and this is provided for by bolting these to the back. Even though the body of Tr6 is at chassis potential (the body being the collector) do not be tempted to leave off the mica insulating washer that is also needed for Tr5. Hum may be introduced due to earth loops if it is left off.

The output capacitor is connected directly between the output socket and a mounting pin fitted on the component board, so is R22.

The wiring between the board and the components mounted on the chassis is shown in Fig. 5.

No wiring is shown for the power supply as this will depend on the transformer and bridge rectifier used, but it is so simple that it can easily be worked out.

If a switch is needed for this it should be mounted on the power supply chassis.


Only one input socket is provided—a DIN 3-pin type and both inputs should be wired to it, the attenuator resistors are also mounted on it.

If the slide switches are glued to the chassis as suggested, a sheet of white card can be fitted over the front panel, as there will be no screws to stop it from laying flat, and a very acceptable face plate can be achieved as shown.

TESTING

Once the wiring is completed and thoroughly checked it is worthwhile measuring with an ohmmeter the resistance between the bases of the output transistors. The resistance should be low and the preset VR4 adjusted for minimum resistance. (This means that there should be a short between them.) Also check that the collector of Tr5 is insulated from the chassis. If all is well with these tests it is unlikely that harm will befall your newly completed project.

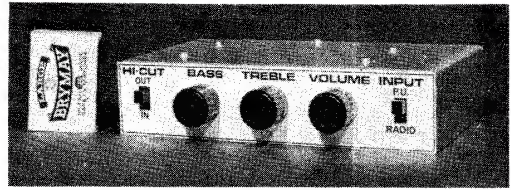If two PP9 batteries are available, these can be



The small size of the amplifier can be judged by the matchbox on the left yet the photographs on the previous page show that layout is not crowded.

used to supply 18V for initial testing. The noise level, even on full output, should be very low, but the dabbing of a finger on the input should produce a high hum level.

If all seems well a pickup can be connected. On full output there will be severe distortion due to the use of batteries but the use of these lessens the likelihood of destroying the transistors if there are any mistakes in wiring, etc.

With all these points checked, the power supply can be connected. There may still be distortion due to the setting of VR4 and this should then be backed off until the audible distortion just disappears while ensuring that Tr4, Tr5 and Tr6 do not get hot.

The effectiveness of the tone controls and the Hi-Cut filter should be considerable and the output be more than adequate. ■



INFORMATION WANTED

...details of the makers of the stereo amplifier marketed by Electronic Sales (Victoria) Ltd. I was led to understand that this was covered by maker's guarantee but have no idea who they were. The fault is that I switched on without speakers connected.—A. E. Webb, 25 Heather Road, Milton, Abingdon, Berkshire.

...any information on the FI-Cord 1A tape recorder. I wish to modify this machine to one with a more modern specification.—M. A. Amstell, 37 Basing Hill, Wembley Park, Middlesex.

...borrow manual of—or acquire constructional information on Heathkit battery portable UXR1—A. Pitt, Rendcomb College, Nr. Cirencester, Gloucestershire.

...any information, or the loan of a circuit for a Selmer Type 'C' Clarivoline with the transistor line-up 4 x 2SB176, 2SB175B and 2SB1738.—J. M. Newby, 27 St. Johns Road, Shildon, Co. Durham.

...any information on the Standard Radio 5AH transmitter. Also, where can I get a BA114 Mullard diode and has it an equivalent?—P. Gladwin, Westfield Farm, Towersey, Thame, Oxon. OX9 3QB.

...any information on modifications to, and the handbook and circuit diagram of the R 209 Mk. 2 receiver.—P. Reeves, 2 Hunts Mead, Billericay, Essex.

ISSUES WANTED

...Practical Wireless dated October 1967 containing the Music Box article. Ten shillings paid for same.—'The Occupier', 3 Lawrence Close, White City Estate, London, W.12.

...the March 1970 issue of Practical Television.—J. Barin, 7 Eastside Road, London, N.W.11 6AY.

...January to September 1968 copies of P.E.—M. Duxbury, 2 Jefferson Drive, Ulverston, Lancashire.

ISSUES FOR DISPOSAL

...copies of Practical Wireless for 1963/4/5/6. Anyone can have them FREE.—S. J. Wells, 34 Brockman Rise, Bromley, Kent.

...Practical Electronics from the start (November 1964) to December 1968. Practical Wireless from May, 1965 to April, 1966. All are complete and in binders. Any offers considered.—N. J. Moore, Flat 5, 7 Cortton Road, Ealing, London, W.5.

EQUIPMENT WANTED

...a dual i.f.t. numbered '18' for a Jason Argonaut f.m./a.m. tuner.—A. Kenway, 16 Hilliers Lane, Beddington, Surrey.

LITERATURE WANTED

...copy of Mullard Circuits for Audio Amplifiers, second edition (1962). The price at the time was 8s. 6d. Please state price and postage.—G. W. Saunders, 26 Rowan Crescent, Streatham, London, S.W.16.

practically wireless commentary by HENRY

No. 79

The
Tero-
Technologist

DESPITE the fact that there were only eight entries for last year's John Rouse Trophy (RSGB constructional entry for under-sixteens), and our disgruntled Editor found it necessary to bemoan (September 1970) that few radio amateurs now build their own main station gear, we feel encouraged by the response to Project Autumn 1970, to recommend those bright young sparks about to cast off the shackles of school to think about the radio servicing business.

Henry recently enjoyed a talk with a bunch of school-leavers. Many of them were captivated by the glittering world of electronics. Bemused by the button-pressing magic of *Dr. Who* and *Star-Trek*, bedazzled by the multi-million flash of instrumentation in the Space-age-for-real, they imagine that radio and television engineers in the entertainment industry must hold the key to perpetual interest.

Henry is amazed at the blurred occupational edges. These youngsters imagine that the lucrative and glamour-ridden world of the television 'star' is gained via the cabled chaos of the studio floor, or, at best, the hallowed hush of the control room.

Hush! Have you ever been in a control room when the producer is shouting at three camera-


men at once, when the *sotto voce* of the floor director's talkback is rattling the monitor loudspeakers, when the continuity girl has dissolved into tears over a lost page four and the musical arrangements depend on the cue-consciousness of a half-drunk tape recorder operator?

Very few performers come up from these ranks. To begin with, a few weeks behind the cameras, or abaft the mikes, soon disillusion any would-be entertainer. There's Harold Williamson, of course, but he is not exactly an entertainer. And there's 'Professor' Stanley Unwin, whose prowess should convince us that a spell in the camera crew would make anyone talk gobbledegook. One or two disc jockeys know a little of what goes on beneath the platter. But those who fancy *that* job may not have any notion of the sweat and toil that can go into sorting out, helping to edit and presenting 'a favourite *toon for Mrs. Pettifer of Lower Peckham Rye.*'

Sometimes, the yearning is genuine. The lure of electronics really fascinates youth. Some of the mystery has been peeled away by a keen science master, revealing even greater depths. Space-age phenomena make much that was wonderful seem mundane—when we hear a gravelly op-check from many thousands of miles away, we are now more likely to carp at its roughness than marvel we can get it at all!

But Miss Today and Master Tomorrow take miracles in their stride. Perhaps I should have told them about the openings in Tero-technology, a word the Min-Tech boys coined for Maintenance Engineers. These maligned gentlemen are fast becoming an élite. They work for large engineering companies, daily waving their magic wands over the fallible products of systems designers.

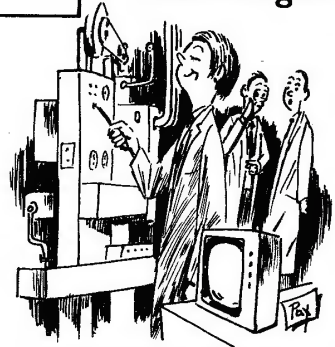They are expected to instal, commission and maintain any-



Leaving behind a trail of modified machinery.

thing from an air-drying purifier to a fully automated oilfield. Electronics is only part of the game to them—building blocks are what we should consider factory-sized projects.

I know one of these gents. He came out of redbrick with a poor degree, entered industry as an assistant to an assistant of an assistant designer. Moved from firm to firm, absorbing knowledge like a sponge and leaving behind a trail of modified machinery. He graduated to his present job simply because nobody else dared take it. And now he picks up all the bricks that scatter-brained designers have dropped besides acting as consultant for half-a-dozen international concerns.

From whence came his qualifications? Well, despite our modern technological age and the out-moded place for an amateur, I suggest he received his impetus and his capacity for a quirky open mind from his younger love of amateur radio, constructional hi-fi and continual dissatisfaction with marketed products. He is a gadget man' and proud of it, even if his present job of 'panel-changing' involves him in king-sized modules.

If anyone tells you, young shaver, that the day of the dabbler has gone, just point to the tero-technologist and be thankful.



The continuity girl dissolved into tears.

SERVICING



AN INTRODUCTION TO FAULT-FINDING

PART 1

H. W. HELLYER

THIS SERIES, WRITTEN BY H. W. HELLYER AND G. J. KING, BEGINS WITH A DISCUSSION OF THE BASIC COMPONENTS OF ANY PIECE OF ELECTRONIC EQUIPMENT, THE RESISTOR, CAPACITOR AND INDUCTOR, WITH SOME NOTES ON THE VALVE AND TRANSISTOR.

BEFORE we can repair a radio receiver, audio amplifier or any other piece of electronic equipment, we must understand something about the fundamental parts of the circuit. Any circuit can eventually be broken down into its component parts or combinations of parts, just as any whole circuit will separate, for convenience, into a number of 'building bricks', as we shall see when my colleague Gordon J. King takes over the next part of this series.

My job, this month, is to lay the ground, describe the 'bones' which form the skeleton circuits and give a few hints about their testing.

Description of components and their functions must needs be brief. We haven't the space for a detailed exposition or for more than a quick look at the three main classes of circuit bones—resistors, capacitors and inductors.

RESISTORS

Sub-dividing the first class, we have fixed, variable and non-linear resistors.

Fixed types may be of carbon, of composition, metal-oxide film on a glass rod or any of several proprietary substances. Values of these components will vary between a fraction of an ohm and several million.

Tolerances are important to the designer and to the engineer who follows in his footsteps by maintaining the equipment. For resistors the tolerances fall into groups, from 1% to as much as 20%. The current a resistor can safely carry is important also for this determines the choice of wattage of the component we may need, to replace a damaged one in a circuit.

The wattage (W) is equal to the product of the current (I) through the resistor (R) and the voltage developed across it (V). By Ohm's Law, $W=I^2R$ or V^2/R or $V \times I$.

Resistors of more than about 2 or 3 watts will usually be wirewound. These are generally bulkier and often consist of a ceramic tube with resistive wire wound on it anchored to stiff wire ends.

Non-inductive wirewound resistors are very necessary for some positions in the circuit and these are

made by winding the resistive element in such a way that the two legs of the 'coil' lie together and magnetic fields tend to cancel each other. Such bifilar winding, as it is called, will also be met with in coil construction, where it is used for the same purpose of cancellation of unwanted magnetic fields.

Practical points: composition resistors are easily damaged by heat. Discolouration of the coding or body paint is an indication that excess current has passed. Do not ignore the warning, look for the reason. Metal-oxide components (and some of the older composition types) had end caps clamped on, relying on physical pressure for their resistive contact.

A loose clamp, or a badly connected lead wire to a cap, is the possible cause of a 'high resistance' joint. As these types are often painted over, with the poor joint beneath the coating of paint, the end cap may not appear to be loose at all.

Colour coding has been standardised pretty well by now, although there are always awkward exceptions. Dirt, heat and age may discolour components and obscure or alter colours, so the rule should be: 'When in doubt—check.' A table of colour codes, including tolerances, etc., is given for resistors.


To some extent, the same code can be used for capacitors, as can the abbreviated method of indicating component values. Despite attempts at standardisation, values may be expressed in several different ways. A 4700 ohms resistor, for example, may be designated 4.7k, or 4k7, or given its full title.

Variable resistors come in a number of varieties, from the common, three-tag 'volume control' we know so well, to multi-section, tapped sliders, often ganged mechanically as well. Basically, the variable resistor can be sub-divided into carbon-track and wirewound types, and a further classification must specify whether the 'law' of the resistor is logarithmic or linear, i.e. log. or lin.

Linear types are self-evident; the resistance in circuit varies in proportion to the angular rotation of the spindle to which the wiper is attached (or the lengthwise travel of 'slider' types). Log. types have a track whose resistance increases logarithmically

as the spindle moves, so that for a great proportion of travel there is little change in resistance, then as the rotation continues, the resistance increases more and more rapidly, i.e., the scale of resistance is cramped toward the upper end. As this conforms more with the physical nature of hearing, such a control is more often used for a volume control, whereas lin. types will usually be found in tone and balance control circuits.

Practical points: noisy volume controls are a frequent complaint—not always justifiable. Very often, the real trouble lies in stages prior to the control, with the fault revealed as the control 'opens up'. An example here is a leaky coupling capacitor in a valved circuit, where the coupling is from the anode of the preceding stage to the 'top end' of the volume control, the potential across the capacitor being nearly that of the h.t. line. This causes a small current to flow through the variable resistor, with resultant noise.

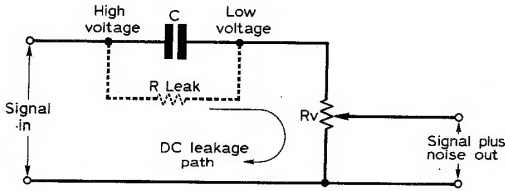


Reported "noisy" volume controls can be due to a leaky coupling capacitor.

Similar faults occur in transistorised equipment, where electrolytic capacitors are needed to maintain the time constants of the interstage circuits.

Noisy controls can be caused by poor connection between spindle and main body, or to wiper support. Where there is a divided section of the control casing, poor clamping or corrosion between surfaces can also be an unsuspected cause of noise, as can inefficient earthing.

A composition track volume control already damaged by current flow, caused by a leaking capacitor, may have a 'hot spot', a portion of the track pitted or burned. This will never succumb successfully to treatment. Replacement is the only cure. But carbon track variable resistors that have simply aged, which can be opened easily, could be treated by rubbing over the track with a soft lead pencil. If the damage is not too far gone, the crackle can sometimes be cured by injection of switch-cleaning fluid; several aerosol preparations are available.

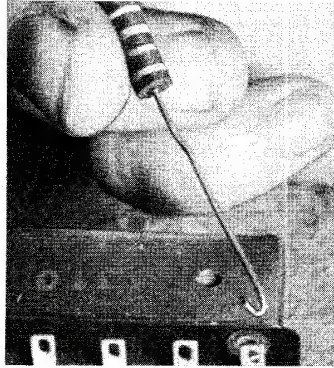

Even in black and white the colour bands on this 1-watt composition resistor are clearly seen.

Personally, I do not favour this method. It is, at best, a temporary solution. Replacement of the offending control is always best. But though the professional in me must advocate the fitting of new parts, the practical wireless hobbyist in me says 'what about cost and availability?' If you are prepared to spend infinite pains in rejuvenating an out-worn part, then good luck to you.

Small variable resistors, used as preset controls


COLOUR CODE FOR CAPACITORS AND RESISTORS

	First Figure 'A'	Sec'd. Figure 'B'	Multiplier 'C'		Tolerance 'D'		
			Resistors	Caps pF	Res	Ceramic Capacitors to 10pF	over 10pF
Black	—	0	1	1	—	2pF	±20%
Brown	1	1	10	10	±1%	0.1pF	±1%
Red	2	2	100	100	±2%	—	±2%
Orange	3	3	1,000	1,000	—	—	±2½%
Yellow	4	4	10,000	10,000	—	—	—
Green	5	5	100,000	—	—	0.5pF	±5%
Blue	6	6	1,000,000	—	—	—	—
Violet	7	7	10,000,000	—	—	—	—
Grey	8	8	100,000,000	0.01μF	—	0.25pF	—
White	9	9	1,000,000,000	0.1μF	—	1pF	±10%
No colour	—	—	—	—	±20%	—	—
Silver	—	—	—	—	±10%	—	—
Gold	—	—	—	—	±5%	—	—

A salmon-pink fifth ring or body colour denotes a Grade 1 high-stability composition resistor. There are variations in the code for capacitors other than ceramic tubular types.

The "preferred" series of values is as follows:—

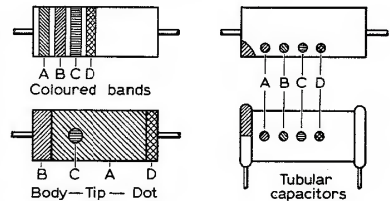1.0 1.2 1.5 1.8 2.2 2.7 3.3 3.9 4.7 5.6 6.8 8.2 and their decades.



Above, left, shows two ways of indicating the value of a fixed resistor; coloured bands and the body-tip-dot method. Above, right, shows how coloured dots are used for the same purpose with tubular ceramic capacitors. However capacitor coding has not followed the same standard pattern as resistor coding there being national and even manufacturers' variations. The code shown in the table is the common one. Manufacturers often use plain marking for the value, tolerance etc. on the body of a capacitor.

in many circuits, are vulnerable to damage by a heavy hand. The usual trouble is strain of the wiper portion from its open rivet attachment to the body of the control. These controls are not intended to carry much current. They will burn out easily and the burn is sometimes invisible—the usual place being adjacent to the end contact. If the control is used as a simple variable resistor and the track is damaged, a simple solution is to reverse the end connection, thus using the other terminal of the track. It is best, when connecting simple variable resistors into circuit, to bridge the slider to the 'common' end. Similar remarks apply to the potentiometer, or the larger variable control.

A final class, the dual concentric control, is being met very often in stereo equipment, needing another special point of attention to be noted. This is the possibility of noise due to imperfect contact between the sections of the control. Sliding metal surfaces tend to generate electrical as well as mechanical noise and this can sometimes be picked up and amplified. A cleaning and greasing regime for such controls will help—but really this is a design problem, and the root cause may be that the control is 'too early' in the circuit. I feel sure my colleague will have a few remarks to offer about such circuitry in a later part.


Non-linear resistors: Final mention has to be made of the special resistors increasingly being encountered: such things as temperature and voltage-dependent resistors, thermistors, varistors, etc. The thermistor at one time performed a voltage dropping function as part of the series chain in the heater line of an ac/dc receiver. As the component warmed, its resistance decreased and from a cold value of several thousand ohms reached an eventual value of one or two ohms (in some cases up to about

a ventilating flow of air, if the repairer or constructor has any choice in this matter. Care must be taken to dress wires away from the hot thermistor, and to keep other components out of its heat field.


Smaller temperature-dependent resistors will be found in power output stages, near or attached to the heat sinks of power transistors. Their purpose is to regulate the bias circuits so that an increase in heat causes a reduction in current. More will be said later about these protection devices.

Varistors are resistors which change their value according to the voltage across them. Again, they are met in many modern circuits where electronic control is needed, and some of the stabilising circuits in which they are employed will be dealt with in succeeding articles.

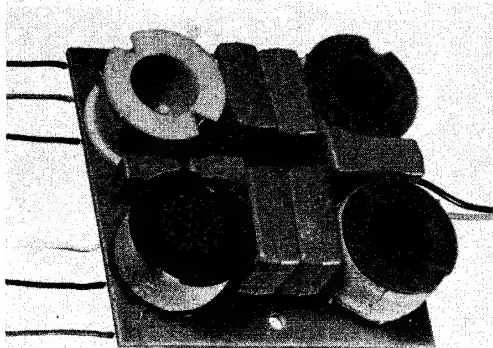Light-dependent resistors have a special function, their resistance decreasing as the light falling on their target area increases. There are a number of



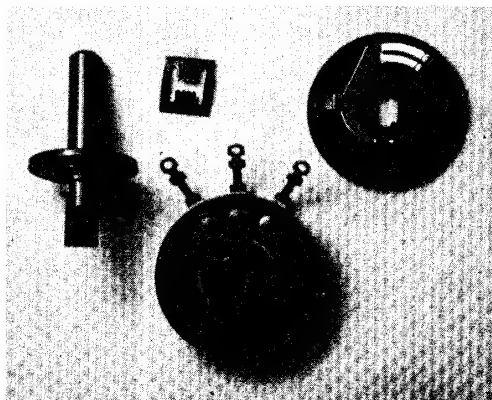Inductors and polyester capacitors in a speaker crossover network.



A dismantled potentiometer showing, top left, the spindle; top centre, the fixing spring; bottom centre, the carbon track with rivetted tags. At top right, the wiper with split spring for flexibility.

40 ohms) when at operating temperature. This regulated the current flow, preventing damage to cold valve heaters and obviating cathode stripping which can be caused by excessive emission. H.T. applied quickly, when semiconductor rectifiers are associated with valved circuits is a common cause of cathode stripping.

Practical points: such components must be allowed to dissipate their heat. They should be mounted in

special types with special applications and only a few of them will concern us here. A practical point arises from this: when these 'variable' or non-linear components are met, take great care that any replacement made shall be exact. There are seldom effective substitutes, and the designer may have chosen a particular component with parameters in mind which may not strike us immediately. The range of variation, the voltage rating and the current rating should be studied.

CAPACITORS


Capacitors sub-divide into three main groups: fixed, variable and electrolytic. Within these groups, there are many more divisions.

Fixed capacitors have various dielectrics and there are various methods of constructing and laying the foil or plates, giving all manner of special characteristics. It would be futile to attempt to explain these in detail, but a few salient points should be explained.

As with resistors, choice must be made according to capacitive value, tolerance, working voltage, peak voltage, temperature variation and in some special cases, frequency characteristics. For variable components, especially presets, the range of variation and its law must be taken into account.

Negative temperature coefficient components are widely used nowadays. There are many ways of

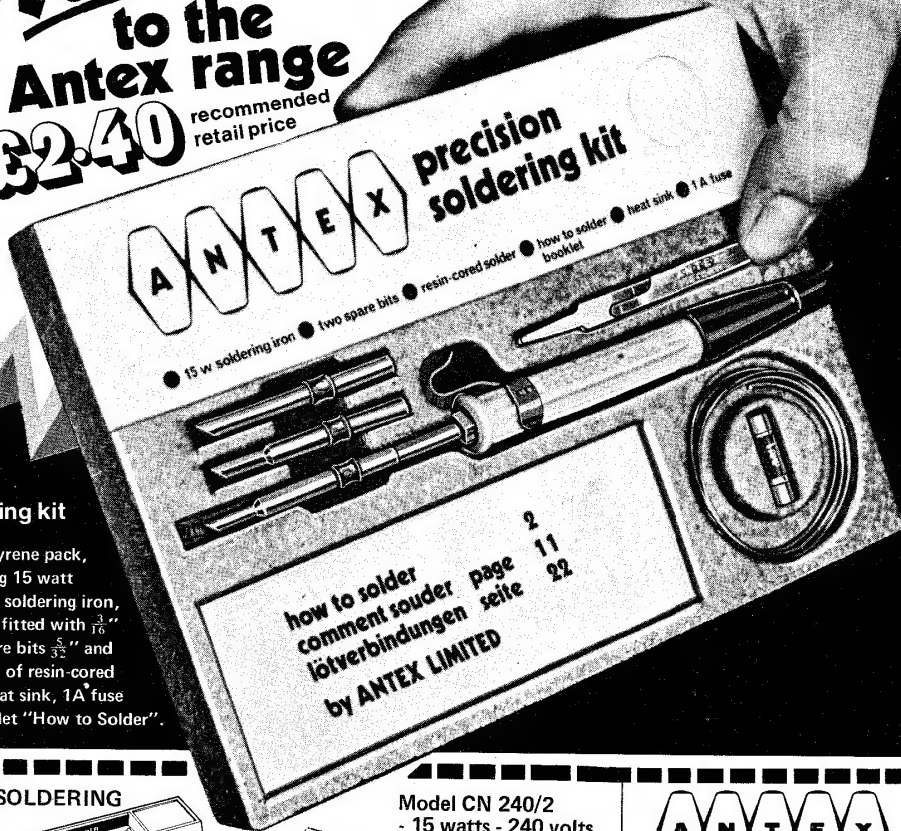
introducing the
New SK2 KIT
 to the
Antex range
 £2.40 recommended
 retail price



SK2 Soldering kit

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with $\frac{3}{16}$ " bit, 2 spare bits $\frac{5}{32}$ " and $\frac{3}{32}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".

SK1 SOLDERING KIT

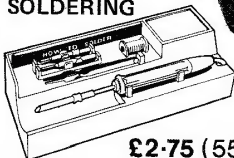

£2.75 (55/-)


In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted $\frac{3}{16}$ " bit. Spare bits $\frac{5}{32}$ " and $\frac{3}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder"

Model CN 240/2 - 15 watts - 240 volts



£1.70 (34/-)

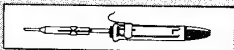Fitted with nickel plated $\frac{3}{32}$ " bit and packed in handy transparent box.



Model G - 18 watts. Fitted $\frac{3}{32}$ " bit. Spare bits $\frac{3}{8}$ ", $\frac{3}{16}$ " and $\frac{1}{4}$ " available. For 240 or 220 volts. £1.80 (36/-).



Model F - 40 watts. Fitted $\frac{5}{16}$ " bit. Spare bits $\frac{3}{32}$ ", $\frac{1}{8}$ " and $\frac{1}{4}$ " available. For 240, 220, 110, 20 volts. From £2.35 (47/-).

Model E - 20 watts. Fitted $\frac{1}{4}$ " bit. Spare bits $\frac{3}{32}$ ", $\frac{1}{8}$ " and $\frac{3}{16}$ " available. For 240, 220 or 110 volts. From £1.80 (36/-).

Model ES - 25 watts. Fitted $\frac{3}{8}$ " bit. Spare bits $\frac{3}{32}$ ", $\frac{1}{8}$ " and $\frac{1}{4}$ " available. For 240, 220 or 110 volts. From £1.80 (36/-).



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.
 Telephone: Plymouth 67377/8.
 Telex: 45296. Giro No. 2581000.

Please send me the Antex colour catalogue
 Please send me the following
 Quantity Model Bit Size Volts Price

.....

I enclose cheque/P.O./cash value

.....

NAME

ADDRESS

..... P.W.5

NEW VALVES

1A7	40	6B7	35	787	25	201	25	7C5	15	12SR7	35	37	40	DAC32	42	E8L21	60	EL34	53	N78	11	00	PL504	80	U404	40	
1CF31	50	6B8	45	6J7G	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45
1D5	40	6B7	45	6J7G	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45
1H5	40	6B7	45	6J7G	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45
1N6GT	48	6B7	45	6J7G	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45	7C6	45
1B5	35	6C4	35	6K8GT	50	10P3	90	10P3	90	10P3	90	10P3	90	10P3	90	10P3	90	10P3	90	10P3	90	10P3	90	10P3	90	10P3	90
1B4	27	6C6G	30	6K25	75	10F25	75	10F25	75	10F25	75	10F25	75	10F25	75	10F25	75	10F25	75	10F25	75	10F25	75	10F25	75	10F25	75
1B5	25	6C6	35	6L6G	45	10F18	45	10F18	45	10F18	45	10F18	45	10F18	45	10F18	45	10F18	45	10F18	45	10F18	45	10F18	45	10F18	45
1T4	25	6C6D6G	45	6L18	80	10LD11	80	10LD11	80	10LD11	80	10LD11	80	10LD11	80	10LD11	80	10LD11	80	10LD11	80	10LD11	80	10LD11	80	10LD11	80
3A4	35	6C1E	55	6Q7G	30	10P13	35	10P13	35	10P13	35	10P13	35	10P13	35	10P13	35	10P13	35	10P13	35	10P13	35	10P13	35	10P13	35
3Q4	40	6C4	35	6Q7GT	43	11E3	44	10C15	80	866A	75	DL66	12	25	ECL82	35	EZ41	48	PCF801	60	SP4	50	SP4	50	SP4	50	
3Q5	45	6D5	25	6S47M	30	12A7G	30	12A7G	30	12A7G	30	12A7G	30	12A7G	30	12A7G	30	12A7G	30	12A7G	30	12A7G	30	12A7G	30	12A7G	30
3B4	35	6E5	38	6S7C	70	12A7T	33	10C18	75	1895	75	DL92	35	ECL86	45	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45
3V4	45	6F1	70	6S7C	35	12A7G	30	10F6	35	4922AR	85	DL94	45	ECL800	45	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45
6R4GY	60	6F5G	60	6S7C	35	12A7G	30	10F6	35	4922AR	85	DL94	45	ECL800	45	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45
5U4G	38	6F6G	60	6S7C	35	12A7G	30	10F6	35	4922AR	85	DL94	45	ECL800	45	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45
5V4G	42	6F6G	35	6S7C7GT	60	12A7G	30	10F6	35	4922AR	85	DL94	45	ECL800	45	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45
5Y3GT	30	6F11	38	6S7C7GT	60	12A7G	30	10F6	35	4922AR	85	DL94	45	ECL800	45	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45
5Z4G	40	6F13	38	6S7C7GT	60	12A7G	30	10F6	35	4922AR	85	DL94	45	ECL800	45	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45
6J30L2	75	6F14	65	6S7C	40	12E1	11	35	30P4	12	ATP6	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	
6A7	75	6F23	50	6U4GT	60	12E1	11	35	30P4	12	ATP6	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	
6A8G	68	6F24	75	6U6G	40	12I7GT	35	30P12	80	AZT7	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45
6AK5	30	6F25	75	6V8M	30	12I7GT	35	30P12	80	AZT7	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45
6AM5	38	6F26	70	6V6G	80	12K3GT	50	30P12	80	AZT7	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45
6AM6	38	6F27	35	6V6GT	38	12K3GT	50	30P12	80	AZT7	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45
6AQ5	35	6G6	25	6X4	30	12K3GT	50	30P12	80	AZT7	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45
6AS7G	80	6H6	15	6X5G	35	12K3GT	50	30P12	80	AZT7	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45
6AT6	30	6J5M	50	6X5GT	35	12K3GT	50	30P12	80	AZT7	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45
6AU5	25	6J5M	50	6X5GT	35	12K3GT	50	30P12	80	AZT7	60	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45
6B4G	10	6J5G	20	7B6	70	12S7	30	35Z4GT	50	CY30	30	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45
6B8G	20	6J5GT	30	7B7	45	12S7	30	35Z4GT	50	CY31	48	E88CC	65	EZ81	28	PCF806	75	SP41	45	SP41	45	SP41	45	SP41	45	SP41	45


All prices in pounds and new pence

40	DAC32	42	E8L21	60	EL34	53	N78	11	00	PL504	80	U404	40			
40	DAF91	25	E8L31	11	38	EL38	11	25	N108	11	00	PL608	80	U801	11	18
40	DAF96	42	E8C90	38	EL41	55	OA2	38	PL609	11	45	U8C80	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL610	11	45	U8C81	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL611	11	45	U8C82	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL612	11	45	U8C83	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL613	11	45	U8C84	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL614	11	45	U8C85	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL615	11	45	U8C86	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL616	11	45	U8C87	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL617	11	45	U8C88	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL618	11	45	U8C89	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL619	11	45	U8C90	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL620	11	45	U8C91	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL621	11	45	U8C92	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL622	11	45	U8C93	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL623	11	45	U8C94	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL624	11	45	U8C95	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL625	11	45	U8C96	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL626	11	45	U8C97	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL627	11	45	U8C98	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL628	11	45	U8C99	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL629	11	45	U8C00	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL630	11	45	U8C01	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL631	11	45	U8C02	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL632	11	45	U8C03	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL633	11	45	U8C04	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL634	11	45	U8C05	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL635	11	45	U8C06	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL636	11	45	U8C07	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL637	11	45	U8C08	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL638	11	45	U8C09	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL639	11	45	U8C10	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL640	11	45	U8C11	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL641	11	45	U8C12	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL642	11	45	U8C13	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL643	11	45	U8C14	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL644	11	45	U8C15	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL645	11	45	U8C16	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL646	11	45	U8C17	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL647	11	45	U8C18	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL648	11	45	U8C19	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL649	11	45	U8C20	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL650	11	45	U8C21	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL651	11	45	U8C22	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL652	11	45	U8C23	35			
40	DAF99	40	E8C93	35	EL42	58	OC3	38	PL653							

stabilising tuned circuits but undoubtedly one of the easiest is to counter the drift due to warming up of the receiver by alteration to the tuning itself. This is done by the inclusion of a capacitor whose value decreases as the temperature increases. Important practical point here is, of course, to ensure that replacement shall always be with the same type.

Standard tubular capacitors are generally ceramic but there are variations such as the high voltage varicaps, made with barrier dielectric techniques, used widely with transistorised circuitry. These are junction-diodes chosen to take advantage of the capacitance effect: they will concern us later.

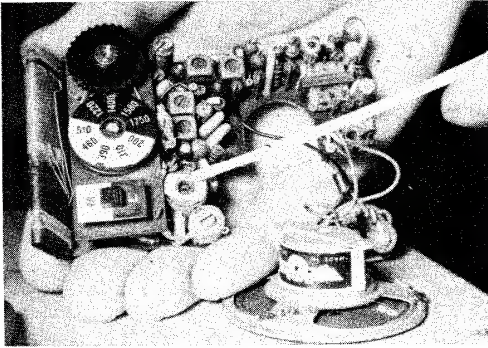Variable capacitors may be the simple compression types found atop the small sealed ganged tuning capacitors in modern transistorised radios, or larger, more precise versions with fine thread screws and several interleaved layers of dielectric. Beehive capacitors, with concentric barrels and a coarse thread, are often found in older sets.



A small pot-core inductor, used here as the tuned circuit of the frequency-changer stage.

Electrolytics have an additional factor in their leakage current. In power supply circuits, where electrolytics are used to filter alternating currents from a supply that should be essentially d.c., we often come across the device of an additional, smaller, decoupling component across the main decoupler. This is to bypass the higher frequency currents that may be present in the ripple current.

Ripple current, in power supply circuits, is an important factor. It bears a direct relationship to the direct current drawn by the equipment, the load. For full-wave rectification, ripple current is about $1\frac{1}{2}$ times the d.c., but a half wave circuit needs a reservoir capacitor in its filter circuit with a ripple current rating of three times the d.c.—a point to be watched when making replacements.

Excessive ripple current will cause overheating—application of “raw a.c.” across an electrolytic can cause a spectacular but dangerous explosion. A point to be watched is the relationship of frequency and capacity. If high frequency ripple is present, the impedance of the capacitor, which may have been sufficiently low at its filter frequencies, rises dramatically and the heating effect increases.

The inductive element of electrolytic capacitors may have to be taken into account. This also will be mentioned later, when we come to practical circuitry.


Polyester capacitors are being increasingly used in radio work because their method of construction decreases the inductive element. The tantalum capacitor, with some special virtues and few drawbacks except cost, has been used in many circuits, its advantage being a relatively large capacitance (albeit at low working voltage) for small physical size.

INDUCTORS

Inductors will be found in all sorts of applications, from the small ferrite beads with a single turn of wire around them to the multi-layer, tapped transformer of the modern stereo radio receiver. From the servicing point of view, inductance is either there or not—one seldom has to make up inductors, and we shall not waste space by talking about the factors determining inductance, permeability and so on. Instead, let's concentrate on the practical aspect of core variation, and the ways to overcome core breakage.

Iron dust cores are the usual way to change inductance of coils, these being threaded into the coil former. The individual particles of iron dust are insulated from each other, although closely packed, affording low loss and high permeability and so a miniaturisation of the whole inductor. But, for this reason, the cores themselves are more fragile.

It is not uncommon for wireless workshops to hold in stock large quantities of replacement iron dust cores. Instead of wasting time fiddling—often ineffectually—with painted, varnished, waxed or lacquered cores which crumble when torsional pressure is applied, the technique is to shatter the core, carefully remove the bits and clean the thread with a metal runner (of the same thread pitch), finally inserting a new core and aligning.

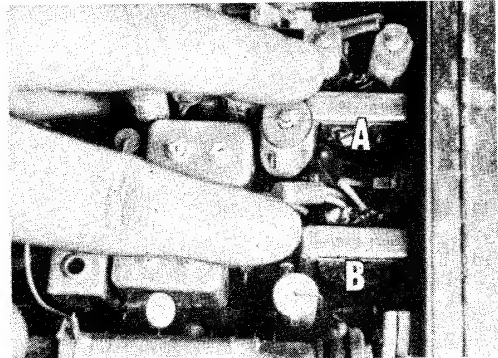

Interstage transformers A and B of a small transistor radio, with transistors between them wired directly into the circuit. Also to be seen are vertically mounted electrolytic capacitors and screened tuned circuits.

OTHER CIRCUIT ELEMENTS

A mention will have to be made of the alternative to the conventional inductor, the ceramic filter. The tuned circuit resonates at a frequency to which the crystal (usually a man-made crystal, a ceramic) is carefully cut and shaped. The actual arrangement is not straightforward as a simple crystal so used would have far too sharp a tuning response.

A pass-band of 180kHz is needed for the handling of the 15kHz audio signals at low distortion which we now require from our f.m. receivers. So two ceramic elements are used, with bandpass coupling. This gives the required bandwidth but retains the advantage of a sharp "skirt" at the extremes of the filter response curve.

Later we shall consider integrated circuits which are revolutionising receiver design in the same way as the innovation of transistors did some time ago. Also the use of various special semiconductors must be discussed. Field effect transistors (f.e.t.'s) have brought new opportunities to circuit designers, especially in the input circuits of v.h.f. receivers as well as to tape recording circuitry.

THERMIONIC VALVES

Valves are on the way out—thus runs the creed of some authorities. So they may well be, for there is little in the domestic field that is done by thermionic devices that can not be done as well or better by semiconductors. For a while, the barriers of high power meant that valves were still needed for certain applications. Now, with the improved silicon semiconductors available, even this barrier has broken down and the only remaining market for domestic valved circuitry appears to be in some television receivers, although a number of these are already fully transistorised.

But from the servicing aspect, valves are still very much with us. Not only do we need to know what they will do and how the circuits work but also what substitutes are available. Such information is not always convenient to come by—the best method of determining replacement suitability, of both valves and transistors, is a study of the relevant parameters.

Taking a simple case—nevertheless, not an uncommon case, for the triode amplifier stage is very often met with, especially in the low-signal sections of tape recorders—we have to consider first the

operating conditions, i.e., heater voltage and current, circuit suitability, etc., and after that we can look at the I_a/V_a curves, the I_a/V_g curves and the mutual conductance.


For any particular anode voltage there will be a curve which slopes up and then tails off when the anode current increases to and beyond a certain point, for a given grid voltage. There is a cut-off point where negative grid volts reduce anode current to zero and a saturation point where further positive grid volts cannot affect anode current. If we know the valve bias, cathode or grid, we can work out whether our alternative will do what we want.

If there is any further doubt, we can tackle the mutual conductance curves and the a.c. resistance. Amplification factor can be obtained from the results we already have, thus from the various factors already at our disposal we should be able to build up as good a picture about the valve we have as we are likely to need. Nine times out of ten we shall not need it: we shall be able to turn up our tables, select a replacement and go ahead. The tenth time could baffle us and this extra little bit of knowledge could save pounds.

SEMICONDUCTORS

Semiconductors can nowadays be divided into three sections: diodes, bipolar devices and others (which includes f.e.t.'s etc.). We are concerned with diodes very much indeed, as we shall see; there are plain rectifiers, diodes used as blocking devices, diodes used as circuit used lines and finally variable capacitance diodes which can play an important part in the tuning of circuits.

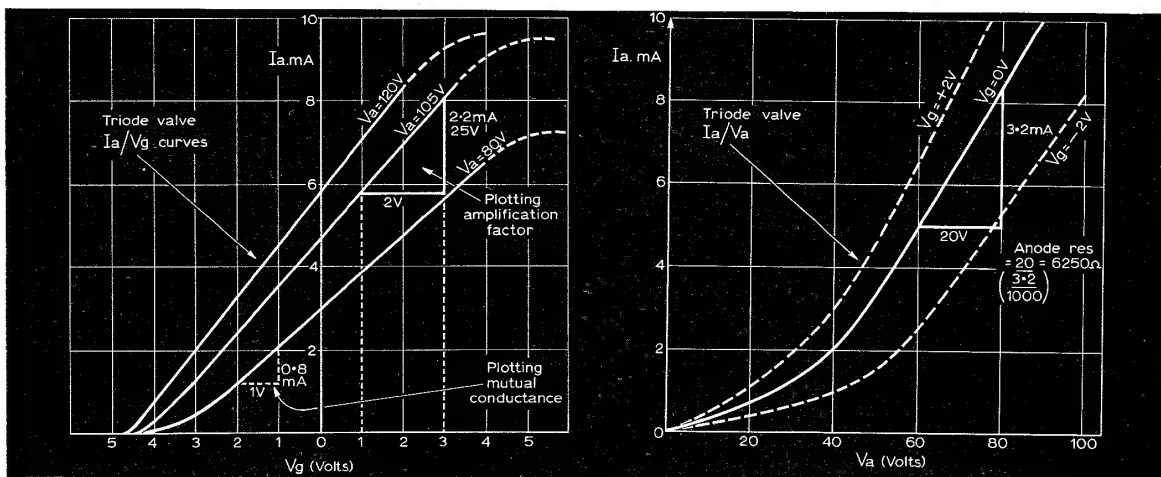The bipolar transistor (so called because it has two types of current carrier) has a few fundamental parameters that will enable us more easily to identify it and choose a possible substitute. Understanding of these parameters will also help us in the solution of some teasing circuit faults.




The I_a/V_g curves of valves tell us a lot about their characteristics. Three curves shown are plotted at different anode voltages. By comparing anode current change with grid voltage change causing it, we obtain the mutual conductance, g_m , in mA/volt. Comparing curves we get the amplification factor, μ .

Anode resistance of the valve is found from I_a/V_a curves. Given the anode load, the stage gain = $\mu \times \frac{R_a}{R_a + r_a}$

Where R_a = anode load, r_a = anode resistance and μ = amplification factor.

LOOK!

PRACTICAL!
VISUAL!
EXCITING!

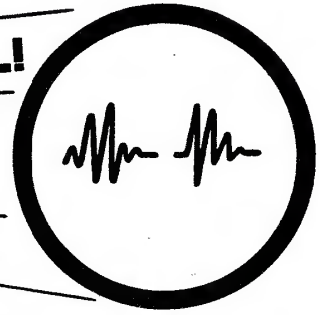

a new 4-way method of mastering
ELECTRONICS
by doing — and — seeing . . .

1 ▶ **OWN and HANDLE** a complete range of present-day **ELECTRONIC PARTS and COMPONENTS**

2 ▶ **BUILD and USE** a modern and professional **CATHODE RAY OSCILLOSCOPE**

3 ▶ **READ and DRAW and UNDERSTAND** **CIRCUIT DIAGRAMS**

4 ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW for **BROCHURE**
or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS
ADDRESS.....PLEASE

PW5

PHILIPS STEREO AND MONO AUTOCHANGER
£8.75


Precision hi-fi quality at bargain price.



Silver and grey deck enamelled finish. 10 in. dia. turntable. 4 speeds. 16, 33, 45, and 78 r.p.m. 10 1/2 in. discs which can be mixed. Fitted renowned Philips plug-in Xtal AG3906 with dual sapphire stylus for LP/EP/78. Sensitivity 100mv. Frequency response 30cp-16Kc/s. Lightweight stylus pressure 3-6 grammes. Board assembly required 14 x 12 in. Above 4in. Below 2 1/2 in. 18 month guarantee. (Also available with GP310 diamond stylus LP Stereo/EP and Sapphire 78 (21 extra)).

BSR 4-SPEED SUPERSLIM STEREO AND MONO CHANGER

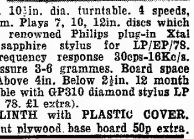Plays 12", 10" or 7" records. Auto or Manual. A high quality unit based by BSR reliability with 12 months' guarantee. Size 18 x 11 1/2 in. Above motor board 3 1/2 in. Below 2 1/4 in. AC 200/250v.



With STEREO and MONO XTAL £7 Post 25p

BSR Minichanger TMSO Stereo and Mono.
Plays 12", 10" or 7" records.
Size 12 x 8 1/2 in. AC 200/250v. **£8 Post 25p**

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond and Mono Sapphire. SP28 Mk II £15 Model 8000 Stereo and Mono Autochanger £14. Post 25p. Record 8000 Stereo and Mono Autochanger £14. Post 25p.

RECORD PLAYER PORTABLE CABINET £3.75
Space for amplifier and autochanger. Post 25p.

RC3 DE-LUXE 3 WATT AMPLIFIER. Ready made with 2-stage triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves ECL82, EZ80. **£4**

RS2 2 WATT AMPLIFIER with loudspeaker, tone and valves UCL82 and UVY5. Post 25p **£3**

R.C.S. TEAKWOOD BASE. Ready out for mounting (State player make and model) **£3.25**

R.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable tinted plastic, attractive appearance. **£3.25**

EMI PICK-UP ARM with mono Xtal and £1 25p

EMI JUNIOR 4 SPEED RECORD PLAYER £3 Post 25p
Mains operated motor, turntable and pick up 25p.

HI-FI RECORD CARTRIDGES. Diamond Stereo/Mono. STA 29 20p; GP94 22 75p; GP93 22 35p; Mono GP91 21 50p; GCS 11 25p; GP97 95p. ACOS L.P. only 50p.

All standard fixing complete with stylus.

WEYRAD P50—TRANSISTOR COILS

RAW Ferrite Aerial. 65p	Spare Cores 2 x 3p
Osc. P50/1AC 30p	Printed Trans. LFDT4 50p
I.F. P50/20C 470 kc/s 33p	Printed Circuit, P6A1 50p
3rd I.F. P50/30C 33p	10 B. Tuning Gang 50p
P51/1 or P51/2 33p	Weyrad Booklet 10p
P60/3V 33p	O.P.T. 10p

Mullard Ferrite Rod 8 x 1/2 in. 20p. 6 x 1/2 in. 25p.

VOLUME CONTROLS
Long spindles. Midget Size 5 K ohms to 2 Meg. LOG or LIN. 1/5 15p. D.P. 20p. STEREO 1/5 55p. D.P. 75p. Edge 6K S.P. Transistor 25p

WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 to 20 K. Carbon 30 K to 2 meg. **25p**

WIRE-WOUND 3-WATT STANDARD SIZE POTS. LONG SPINDLE 10 OHMS to 100 K. **40p**

VEROBOARD 0-15 MATRIX
24 x 5in. 19p. 24 x 3 1/2 in. 16p. 31 x 3 1/2 in. 19p. 31 x 5in. 26p. EDGE CONNECTORS 16 way 25p; 24 way 38p.

PINS 30 per packet 17p. FACE OUTLINES 35p.

S.R.P. Board 0-15 MATRIX 2 1/2 in. wide 3p per 1 in. 3 1/2 in. wide 4p per 1 in. 5 1/2 in. wide 5p per 1 in. (up to 17 1/2 in.). S.R.P. undrilled 1 in. Board 10 x 8 in. 15p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides. 6 x 4 in. 46p; 8 x 6 in. 50p; 10 x 7 in. 70p; 14 x 8 in. 90p; 16 x 8 in. 90p; 12 x 8 in. 30p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 8p; 8 x 6 in. 15p; 10 x 7 in. 17p; 12 x 8 in. 23p; 14 x 8 in. 27p; 12 x 12 in. 32p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p.
2 p. 2-way, or 2 p. 6-way or 3 p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p.
1 inch DIAMETER Waveshifter "MAKITS" 1 p. 19-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 60p, 2 water 90p. Extra waters up to six 90p.
TOGGLE SWITCHES, sp. 14p; dp. 18p; dp. dt. 23p.

ALL PURPOSE HEADPHONES
H.E. HEADPHONES 200 ohms Super Sensitive .. £1.75
LOW RESISTANCE HEADPHONES 3-5 ohms .. £2.00
DE LUXE STEREO HEADPHONES 8 ohms .. £3.25

"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER
£2.35



300/250 v. A.C. Leaflet S.A.E.

Minimum Post and Packing 15p RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME

RADIO COMPONENT SPECIALISTS
List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665

GENERAL PURPOSE TRANSISTOR PRE AMPLIFIER BRITISH MADE
for Mike Tape, P.U. Guitars etc.
Battery 9-12v or H.T. line 200-300v D.C. operation. Size 1 1/2 x 1 1/2 x 1". Response 25 c.p.s. to 25 Kc/s. 26db gain. For use with valve or transistor equipment.
Full instructions supplied. **90p** Post Brand new. Guaranteed. Details S.A.E.

NEW TUBULAR ELECTROLYTICS CAN TYPES

2/350V .. 14p	100/25V .. 10p	16-16/500V .. 55p
4/350V .. 14p	250/25V .. 14p	50-50/350V .. 25p
8/450V .. 14p	500/25V .. 20p	80-100/350V .. 55p
16/450V .. 14p	8-8/450V .. 15p	32-32/250V .. 15p
32/450V .. 20p	8-16/450V .. 20p	32-32/450V .. 35p
25/25V .. 10p	16-16/450V .. 25p	32-32-32/350V 45p
50/50V .. 10p	32-32/350V .. 25p	100-50-50/350V 48p

SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p; 500, 1000mF 13V 15p; 2000mF 50V 35p.

CERAMIC 1pF to 0.01 mF, 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-0.1 4p, 0-5 15p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 5p; 0.47 25p. 1.000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 5p; 0.047, 0.1, 14p. SILVER MICA. Close tolerance 1% 2.2-200pF 8p; 500-2 200pF 10p; 2.700-5 600pF 20p; 6.800pF-0.01, mfd 30p; each.

FTW GANG. 0-0.47 205pF 12p; 0.5p; 5p; Slow motion drive 365+365 with 25+25pF 55p; 600pF slow motion, standard 45p; small 8-gang 500pF £1.10. SHORT WAVE. Single 25pF 55p.

CHROME TELESCOPIC AERIAL, swivel base, 23in. 20p.

TUNING Solid dielectric, 100pF, 500pF, 85p each.

TRIMMERS Compression 3A, 700pF, 150pF, 150pF, 8p; 250pF, 18p; 600pF, 750pF, 1000pF 10p.

RECTIFIERS CONTACT COOLED wave 60mA 38p; 55mA 48p. SILICON 2Y211 30p; 2Y10 50p; 1000p, 1p.

Full wave Bridge Rectifiers 75mA 50p; 150mA 95p.

EX-GOVERNMENT RECEIPIERS 250v, 200mA, 30p.

NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p.

RESISTORS. Preferred values, 10 ohms to 10 meg. 1 w., 1 w., 20% 1p; 3 w. 5p.

HIGH STABILITY, 1 w. 2%, 10 ohms to 10 meg., 10p.


500-500 50p. 2 p. 4 p. 4 p. 10 ohms to 10 meg., 4p.

WIRE-WOUND RESISTORS 8 w., 10 watt, 15 watt, 10 ohms to 100K, 10p each; 2 1/2 watt, 1 ohm to 8 2 ohms 10p.

Q MAX CHASSIS CUTTER
Complete: a die, a punch, an Allen screw and key

1in. 85p	1 1/2in. 85p	1 1/2in. 85p	1 1/2in. 220	2 1/2in. 220
3in. 85p	1in. 95p	1 1/2in. 110	1 1/2in. 21 45	2 1/2in. 22 85
1in. 84p	1 1/2in. 85p	1 1/2in. 108	2in. £1.99	1in. sq. £1.33

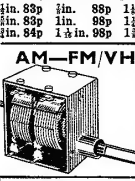AM-FM/VHF TUNING GANG
Super quality small size 1 1/2 x 1 1/2 in., plus slide 1 1/2 x 1 1/2 in. 55p + 25p. 250pF. British made. Geared slow motion drive 6:1. Plastic dust cover. 6BA tapped front. Vast. Custom aluminium frame **50p** Post Free



MAINS TRANSFORMERS

350-0-350 80 ma. 6.3 v. 2 amps, centre tapped .. £1.10	Post 25p each
250-0-250 80 ma. 6.3 v. 1 amp, i.a. or 5 v. 2 a. .. £2.00	
500-0-500 80 ma. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. .. £2.00	
350-0-350 80 ma. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. .. £2.00	
300-0-300 v. 120 ma., 6.3 v. 4 a. C.T. 6.3 v. 2 a. .. £2.50	
MINIATURE 200 v. 20 ma., 6.3 v. 1 a., 2 1/2 x 2 1/2 in. 75p	
MIDGET 220 v. 45 ma. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 90p	
HEATER TRANS. 6.3 v. 1 1/2 a. .. 70p	
Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1 1/2 amp. .. 80p	

GENERAL PURPOSE LOW VOLTAGE Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 12, 15, 18, 24 and 30 v. £2.00 1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, 25-00 2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. 25-00 AUTO TRANSFORMERS 0-115-230 v. Input/Output, 150w. £2.00; 500w. 45; 1000w. 11p.


CHARGER TRANSFORMERS. Input 200/250v. For 6 or 12v., 1 1/2 amp. £1.30; 2 amp. £1.50; 4 amp. £1.90.

FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12 v. outputs, 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.

E.M.I. 13 1/2 x 8in. LOUSPEAKERS
With flared tweeter cone and ceramic magnet. 10 watts. Bass res. 45-60 ohms. Flux 10,000 gauss.
State 8 or 9 or 15 ohm. Post 15p

Also with twin tweeters. With crossover, 10 watt. State 8 or 9 or 15 ohm. Post 15p

Recommended Teak Cabinet. Size 16 x 10 x 9 in. Post 25p **£5**




10W MINI-MODULE £3.25 LOUSPEAKER KIT
Triple speaker system combining on ready cut baffles. 1 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm.

TEAK VENEERED BOOKSHELF ENCLOSURE. 16 1/2 x 10 1/2 x 6 in. Modern Design, dark grey Tytan covered baffle **£5** Post 25p

★ RADIO BOOKS—LIST S.A.E. ★

ALL MODELS "BAKER SPEAKERS" IN STOCK
BAKER 12in. MAJOR £9




30-14,900 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. C.P.S. Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£11.50**

BAKER "BIG-SOUND" SPEAKERS

"Group 25" 12 inch £7	"Group 35" 12 inch £9	"Group 50" 15 inch £19
25 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front for 12in. round Loudspeaker .. £9. Post 25p
For 12 x 8 in. Loudspeaker .. £5. Post 25p
For 10 x 6 in. round Loudspeaker .. £4. Post 25p
LOUDSPEAKER CABINET WADDING 18in. wide, 15p. 1ft.

THIS ELAC CONE TWEETER IS THE VERY LATEST DESIGN AND GIVES A HIGHER STANDARD OF MORE EXPENSIVE UNITS.



The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth roll-off of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 2 in. deep. Rating 10 watts, 3 ohm or 15 ohm models. **£1.90** Post 10p

TWO-WAY XOVER NETWORK 3000 c/s.
With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 4 in. x 4 in. with control knob, tweeter and woofer leads and input terminals. Suitable for 3 to 8 ohm imp. **£1.90** Post 10p

Horn Tweeters 2-16Kc/s, 10W 8 ohm or 15 ohm £1.50.
De Luxe Horn Tweeters 3-18 Kc/s, 15W, 8 ohm £2.50
TWO-WAY 3000c/s CROSSOVERS for 8 or 15 ohm 85p.
SPECIAL OFFER: 80 ohm, 2 1/2 in. dia. 35 ohm, 3 in. dia. 25 ohm, 3 in. dia.; 6 x 4 in., 8 x 5 in. **90p EACH**
TYPE 3 ohm, 6 ohm, 8 ohm, 15 ohm, 2 1/2 in. dia. 5 x 3 in. 7 x 4 in. LOUSPEAKERS P.M. 3 OHMS. 9in. £1.10; 8 x 5in. £1.25; 8 x 2 1/2 in. 90p; 8in. £1.75; 10 x 6in. £1.90.

5in. WOOPER 8 watts max. 20-10,000 cps. 8 or 15 ohm £1.80.
ELAC 8 in. De Luxe Ceramic 8 ohm 15 ohm £2.50
RICHARD ALLAN TWIN CONE LOUSPEAKERS. 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 3 or 8 or 15 ohm models £1.95 each. Post 15p.

100 WATT ALL PURPOSE POWER AMPLIFIER
4 inputs speaker and music. Response 10-20,000 cps. Matches all loudspeakers. Weight only 12 lb. Size 8 in. Post AC 200/250v. Guaranteed. Details S.A.E. **£36** Free

ALL EAGLE PRODUCTS
SUPPLIED AT LOWEST PRICES
ILLUSTRATED EAGLE CATALOGUE 25p. Post Free.

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **£4**

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **£3**

BARGAIN FM TUNER 89-108 Mc/s. Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch **£10**

BARGAIN FM TUNER as above less cabinet **£7.50**


FM STEREO MULTIPLEX ADAPTOR. For above or general use. Ready made with 4 transistors, 8 diodes. **£5**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. **£3.50**

COAXIAL PLUG PEG. PANEL SOCKETS 6p. LINE 18p.
OUTLET BOXES, SURFACE OR FLUSH 25p.
BALANCED TWIN FEEDERS 5p. 50 ohms or 300 ohms.
JACK SOCKET 5id. open-circuit 14p, closed circuit 25p;
Chrome Lead Socket 45p. Phono Plug 5p. Phono Socket 5p.
JACK PLUGS 5id. Chrome 15p; 6mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 15p; 5-pin 15p. DIN PLUGS 3-pin 15p; 5-pin 25p.
VALVE HOLDERS, 8p; CERAMIC 8p; CANS 5p.

E.M.I. TAPE MOTORS
120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. Size 3 1/2 x 2 1/2 in. **£1.25**

BALFOUR GRAM MOTORS
120v. or 240v. AC. 1,200 r.p.m. 4 pole 60mA. Spindle 0.187 x 0.75in. Size 3 1/2 x 2 1/2 in. **85p**



The stated parameters will always depend on operating temperature, a typical mean figure being 25°C. If the operating conditions vary, it is important that the parameters be corrected accordingly, but this is not generally the province of the chap who is doing the repairs.

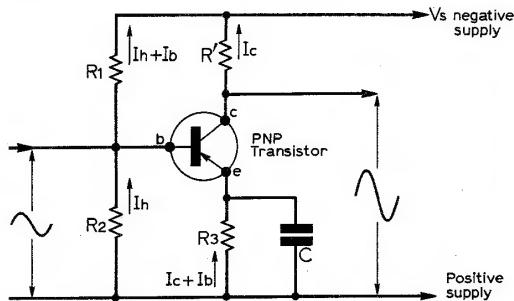


Fig. 1: Common-emitter PNP amplifier stage with arrows indicating "hole" conduction. Base voltage is stabilised by R1 and R2 with additional bias provided by R3.

It is to be assumed that the designer has done his homework. Table 1 gives the more important things we need to know about a transistor and a specimen set of figures for a general purpose n.p.n. silicon transistor has been quoted, to show the way these figures are expressed.

As an example of the use of these terms, Fig. 1 shows a p.n.p. transistor in common-emitter mode, as would be used for a simple amplifier. In this mode, we need to know the ratio of change of collector current for a change in base current, i.e., the current gain, β or $\alpha\alpha'$ (beta or alpha nought dash). The subscript nought means that the current gain applies to d.c., the dash indicates the signal input is applied to the base. A plain α (alpha), without the dash is the symbol for current transfer ratio, and we usually see this written in a statement showing increase, this $\Delta\alpha$ or $\delta\alpha$.

The relationship between alpha and alpha-dash is important, and the formula

$$\alpha' = \frac{\alpha}{(1-\alpha)}$$

will be encountered. In Fig. 1 we see the various currents and voltages outlined with the arrows denoting hole conduction.

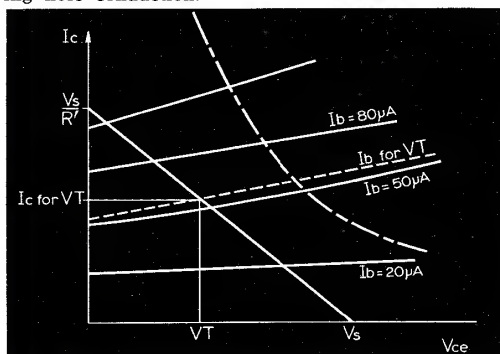


Fig. 2: A load-line drawn on the output characteristic curve of the transistor in Fig. 1. This depends on supply voltage Vs and value of R'. Chain-dotted line is power limitation and VT the working voltage.

TABLE 1

Ratings		
Max. Collector-Base Voltage	V_{CBO}	25V
Max. Collector-Emitter Voltage	V_{CEO}	25V
Max. Emitter-Base Voltage	V_{EBO}	5V
Max. Peak Collector Current	I_{CM}	500mA
Max. Dissipation (at $T_{amb} = 25^\circ C$)		300mW
Max. operating temp.		-55 to 125°C
Characteristics		
Max. Collector-Base Reverse Current	I_{CBO}	0.2µA
Max. Emitter-Base Reverse current	I_{EBO}	0.2µA
Max. Collector-Emitter sustaining voltage	$V_{CE(sus)}$	25V
Max. Collector-Emitter saturation voltage	$V_{CE(sat)}$	0.35V
Base-Emitter saturation voltage	$V_{BE(sat)}$	0.65-1.0V
DC current gain	h_{FE}	50-300
Min. Gain-Bandwidth Product	f_T	150
Max. output capacitance	C_{ob}	6pf
Typical Noise Figure	N	7dB

Characteristic curves. From what we already know, we can draw up a similar family of curves to those we used for valves. Fig. 2 shows just such a series of curves used to determine the static collector current for various output characteristic curves. Values in the simple diagram we saw before can be calculated from this load-line graph, thus:

At cut-off, $V_{ce} = \text{supply voltage}$.

At maximum current, all the voltage is dropped across R' and maximum current is V_{supply}/R' . If we choose a suitable voltage, call it VT for the collector, the base and collector currents can be determined from the load-line.

Volts drop across R' is $I_c \times R'$. Value of

$$R3 = V_s - [(I_c \times R') + VT.]$$

We get the static value of V_{be} from the input characteristic and know that the voltage drop across R2 = drop across R3 minus V_{be} .

$$\text{Then } V_{R2} = [R3 \times (I_c + I_b)] - V_{be}$$

If we now choose a suitable value of I_L we get the value of R2, thus:

$$\frac{[R3 \times (I_c + I_b)] - V_{be}}{I_L}$$

and the voltage across R1 is the difference between V_s and V_{R2} , or as calculated from the value of I_b (Ohms Law) taken from the load-line.

Dynamic considerations differ and the conditions for different kinds of transistor differ. These we shall tackle as they arise. The foregoing has been intended as an example—a way of laying the ground for Mr. King to launch into servicing techniques and circuitry without having to waste his time explaining every detail as he goes along.

END OF PART ONE


THE MW COLUMN

THE proposal to start local commercial radio on the medium waves has focused attention on two international common frequencies—1484kHz and 1594kHz. Many low power stations in Europe and parts of Africa occupy these channels, the only restriction being that there should not be interference between them. The BBC uses both frequencies for 2kW relays, so DXing on these channels will, in some parts of the country be limited to times when these locals are off the air. Manx Radio is on 1594kHz from sunset until 2015hrs while BBC3 broadcasts from Bournemouth and Dundee until 2230hrs. Look for CSB4 Emissoras Associadas de Lisboa; the US Air Force station in Athens; Marrakesh in Morocco and possibly Nova Lisboa in Angola; all on 1594kHz. The other channel—1484kHz—is more popular and is used by BBC4 in Kent, Lancashire and Norfolk; BBC2 in Scotland and BBC1 in Bournemouth. During the summer, the USAF base at Kenitra in Morocco has been heard on 1484 on several occasions while the USN 250-watter at Keflavik, Iceland, has also been logged. Radio Gibraltar is on this channel from 0655hrs to 2300hrs but has so far eluded the writer. Others to search for on 1484 are CSB90 in Funchal Maderia; Volos, a regional station in Greece; Riga in Latvia; Limassol in Cyprus; Ankara Turkey; Jeddah in Saudia Arabia.

A recent note by David Gibson referred lightheartedly to a DXer using the PW medium wave loop on the 10m amateur band. A MW loop will not, of course, function properly on 30MHz but it is quite easy to modify one to cover the Top Band. Remove one turn from the main winding; the range will now extend to 2MHz and the loop can be used for nulling-out Loran or other QRM. Useful results can be obtained in daylight with a modified MW loop to 3MHz but as frequency increases the directional properties gradually disappear.

As winter approaches in the southern hemisphere Latin Americans become prominent and can be heard in Europe from midnight until daybreak. Two high power stations in Buenos Aires Argentina are nearly always audible; LR1 1070kHz and LR3 950kHz. They are commercially owned and identify frequently between jingles. LR3 has the call Radio Belgrano and LR1 is Radio el Mundo. Others to look for include LR4 910kHz Radio Splendid Buenos Aires; LT2 1230kHz R. Splendid Rosario; LS6 1350kHz R. America Buenos Aires. From nearby Montevideo in Uruguay CX14 Radio Espectador is on 810kHz; CX28 R. Imparcial is on 1090kHz and CX16 850kHz has the unusual identification 'Radio Carve.' Venezuela is on a direct sea path across the Atlantic and can be logged on all parts of the band. Listen for YVLH 650kHz Radio Giradot in Maracay; YVKS 750kHz Radio Caracas; YVNM 1000kHz R. Mil in Moron; YVRS 1020kHz R. Margarita La Asuncion; YVQJ 1080kHz R. Barcelona; YVQT 1110kHz R. Carupano; YVOZ 1200kHz R. Tiempo Caracas; YVOH 1230kHz R. Valera.

CHARLES MOLLOY

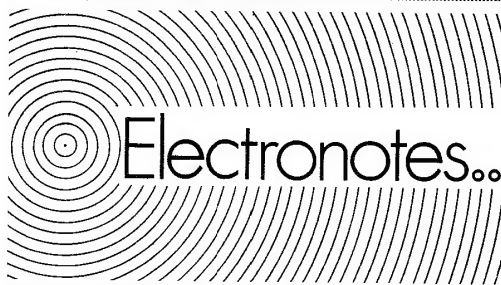

Electronotes..

S. GINSBERG

Solid-state devices are slowly but surely advancing in areas which were previously held by the valve. But there are some applications where transistors find it hard to compete. This is highlighted in places where high power coupled with high frequency are required. To produce kilowatts at microwave frequencies is still the prerogative of the valve.

An application which illustrates this is that of cooking. Microwave ovens are becoming a reality as various types of sustenance are bronzed to culinary perfection by very high frequency energy.

Strange things happen when one uses radar-type frequencies to cook. An egg, for example, can be "boiled" by placing it in the oven and setting the timer for some 25 seconds. Thirty-five seconds will supply the article hard-boiled. Funny thing is that at around the 45 second mark the egg goes off with a bang. This is because the microwave energy concentrates at the centre of the unfortunate egg.

Small tea cakes, made from a proprietary brand of cake mix, take barely 35 seconds to cook and it is amusing to watch a lifeless paper cup full of gooey cake mix suddenly spring into life and fill the container. The weekend joint is reckoned to take around the eight-minute mark. No washing up of pots if you put the food on a paper container.

Digital techniques are still gaining popularity in electronic circles. More and more voltmeters and multimeters are boasting a digital readout. But the readouts are now commonly becoming available by themselves and there is an increasing number of modules being launched. These usually take the form of a small oblong package which houses a number of readout devices and often all the necessary logic circuitry for driving the solid-state readouts themselves. The whole package is offered as a single unit which can be fitted on to a front panel. Thus instead of fitting a meter, it is now possible to fit a solid state direct digital readout device. One of the advantages of direct readout is that parallax is avoided—the difference in absolute reading which is dependant upon whether the eye is directly over the needle of a conventional meter or slightly to one side.

Perhaps the most advanced digital meter available is one which automatically checks its own accuracy against a standard cell between readings. The circuitry switches from the measurement at the probes to the standard cell and back again. It does this repetitively and any slight difference between the standard cell and what the meter should read is immediately corrected by a fast-acting feedback loop.

TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL


7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. 4 section 24" retractable chrome plated Telescopic aerial for Short Waves for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Total building costs £6.98 Post, packing and insurance 41p.
Overseas P. & P. 90p



roamer seven mk IV

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in. chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

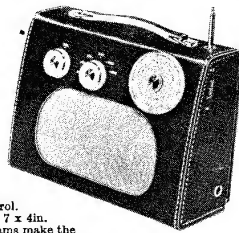


Total building costs £5.98 Post, packing and insurance 41p.
Overseas P. & P. 90p

NEW! trans eight

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER


Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 2 diodes. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra

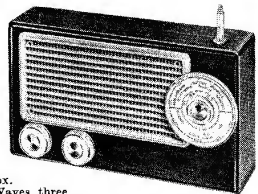

Total building costs £4.48 Post, packing and insurance 31p.
Overseas P. & P. 70p

pocket five MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

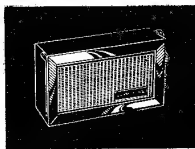
Attractive black and gold case. Size 5 1/2 x 1 1/4 x 3 1/2in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.



Total building costs £2.23 Overseas P. & P. 55p
Post, packing and insurance 21p.

transona five MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

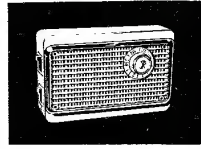Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra




Total building costs £2.38 Overseas P. & P. 55p
Post, packing and insurance 22p.

IMPROVED MODEL!

roamer six SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit, 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra

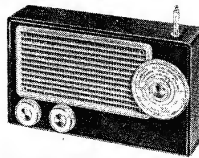

Total building costs £3.98 Overseas P. & P. 70p
Post, packing and insurance 26p.

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

- | | | | |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER EIGHT | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | ROAMER SIX | <input type="checkbox"/> |

Parts price list and plans for

Name

Address

PW.29

- * Callers side entrance Barratts Shoe Shop
- * Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

A COMPLETE STEREO SYSTEM

SAVE OVER £30



L & M stereo system comprises—Garrard SP25 Mk 3 record player with Goldring G800 Magnetic cartridge—complete with plinth and cover and ready wired.

Teleton SAQ 203 Amplifier and two full size 30" x 10" x 7 1/2" internationally acclaimed murette speakers. L & M Bargain Price **£70**

Teleton CRI0T AM/FM stereo tuner amplifier. Output 4W per Channel with pair of matching speakers.

£29.50

A complete stereo system comprising the above CRI0T tuner amplifier and pair of matching speakers with Garrard 2025 TC record player complete with plinth and cover. Ready wired. L & M Bargain Price **£43**

Hosiden DH 025 stereo headphones excellent value £2.40. Also available super quality stereo headset frequency response 20-20,000 CPS with adjustable volume controls. **£6.50**



L & M Sensational Bargain Garrard SP 25 MK 3 record player with Goldring G800 Magnetic cartridge. Complete with plinth and cover. Ready wired. **£22**

Teleton "8100" Hit Parade cassette tape recorder. Precision engineered with automatic level control battery operated normally £23.50. Our price **£19**

GARRARD TURNTABLES

Brand new and fully guaranteed

Plinths and covers. Fully assembled £3.75. Also available to be left in position when playing record	2025 TC 40 B SP 25 Mk 3 SL 65 B AP 76	£9.95 £10.95 £11.75 £14.95 £21.00
--	---------------------------------------	-----------------------------------

!! STARTLING REDUCTION !!

IC44 Magnetic cartridge rec. retail £7.50. Our price **£4**

Teleton GT101 AM/FM tuner audio output level 1 volt 100% modulated 17 transistor 17 diodes normally £45.50. Our price **£35**

Teleton TFS 50. Tuner/amplifier. 50 watts music power. 15 watts per channel RMS Normally £75.50. Our price **£55**

L & M SUPPLIES CREDIT FACILITY AVAILABLE

HAINAULT HOUSE, HAINAULT STREET, LONDON SE9
Tel. 01-850 0829 Callers Welcome. Own car park.

VALVES

SAME DAY SERVICE
NEW! TESTED! GUARANTEED

SETS IR5, 1S5, IT4, 3B4, 3V4, DAF91, DF91, DK91, DL82, DL84.
Set of 4 for £1.02. DAF96, DF96, DK96, DL86, 4 for £1.45.

1A7GT	-37	25U4GT	-87	DL82	-86	HL500	-82	PCL83	-80	UBC41	-82
1H9GT	-36	30C1	-80	DL84	-87	EM80	-81	PCL84	-87	UBF80	-84
1N9GT	-38	30C15	-83	DL96	-86	EM81	-81	PCL85	-45	UBF89	-93
1R5	-28	30C17	-80	DY86	-92	EM84	-83	PCL86	-41	UCR84	-85
1S5	-21	30C18	-87	DY87	-92	EM87	-87	PCL88	-72	UCR85	-88
IT4	-16	30E5	-76	EAB080	-82	EY71	-88	PCL900	-77	UCF90	-88
3B4	-28	30FL1	-63	EAF42	-50	EY86	-82	PEN44	-42	UCH42	-62
3V4	-37	30FL12	-72	EB91	-11	EZ40	-43	PEN30C	-70	UCH81	-82
3Y3GT	-30	30FL14	-72	EB033	-40	EZ41	-43	PFL300	-86	UCL82	-95
4Z4G	-37	30L1	-82	EB041	-82	EZ80	-82	PL87	-48	UCL83	-85
6/80L2	-58	30L15	-82	EB090	-82	EZ81	-84	PL81	-48	UF41	-62
6A1L5	-11	30L17	-73	EBF80	-83	GZ32	-43	PL81A	-61	UF89	-83
6AM6	-13	30L74	-65	EBF89	-81	GZ34	-48	PL82	-82	UL41	-60
6AQ5	-28	30P19	-77	EC81	-18	K741	-77	PL83	-85	UL44	£1.00
6AT6	-22	30P19	-65	ECC82	-82	K781	-48	PL84	-83	UL84	-85
6AU6	-22	30P11	-63	ECC83	-85	K790	-83	PL800	-85	UM80	-85
6BA6	-22	30P13	-83	ECC85	-82	LN319	-63	PL804	-67	UM84	-82
6BE6	-23	30P14	-70	ECC804	-60	LN329	-72	PL508	£1.17	UY41	-41
6BJ8	-42	30P15	-82	ECP80	-80	LN339	-63	PM84	-87	UY85	-88
6BW7	-40	35L6GT	-43	ECP82	-80	N78	-87	PX25	£1.17	VF4B	-77
6CD6G	£1.10	35W4	-84	ECH85	-80	PE1	-50	PY32	-86	W119	-85
6FL4	-45	8254GT	-25	ECH42	-83	PAB080	-85	PY33	-55	Z77	-82
6P23	-73	807	-45	EOH81	-82	PC86	-61	PY81	-82	Transistors	-82
6P25	-63	6063	-62	ECH83	-41	PC88	-61	PY82	-82	AC107	-17
6KXG	-12	AC1V2	-77	ECH84	-47	PC89	-67	PY83	-82	AC127	-18
6K8G	-17	AZ31	-47	ECL80	-35	PC97	-40	PY88	-84	AD140	-87
6SL7GT	-87	B349	-65	EOL82	-83	PC900	-87	PY800	-87	AF115	-80
6V6G	-17	3Z99	-62	ECH85	-40	PC854	-82	PY801	-87	AF116	-80
6V6GT	-32	CCH35	-87	EP39	-83	PC855	-80	R19	-82	AF117	-80
6X4	-23	CL33	-92	EF41	-58	PC838	-45	E20	-65	AF118	-80
6X6GT	-28	CY31	-83	EP80	-84	PC839	-47	U25	-88	AF125	-17
10P15	-25	DA022	-86	EP85	-81	PC819	-61	U36	-88	AF127	-17
10P18	-60	DAF91	-21	EP86	-81	PC805	-85	U47	-68	OC26	-85
12AH5	£2.95	DAF96	-36	EP89	-82	PCF80	-80	U49	-65	OC44	-12
12AT7	-18	DF33	-88	EP91	-13	PCF82	-82	U78	-84	OC45	-12
12AU6	-23	DF91	-18	EF183	-82	PCF86	-47	U91	-82	OC71	-12
12AU7	-23	DF96	-36	EF184	-82	PCF800	-87	U193	-42	OC72	-12
12AX7	-23	DH77	-22	EH90	-42	PCF801	-83	U251	-72	OC75	-12
18B6GG	-87	30E32	-87	EL33	-45	PCF802	-45	U301	-82	OC81	-12
20P2	-67	DK91	-83	EL84	-47	PCF805	-87	U329	-72	OC81D	-12
20P3	-85	DK92	-42	EL41	-55	PCF806	-80	U801	-88	OC82	-12
20P4	-92	DK96	-86	EL84	-84	PCF808	-72	UAB080	-82	OC82D	-12
25L8GT	-25	DL35	-25	EL90	-26	PCL82	-36	UAF42	-61	OC170	-82

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra.

AMAZING MINI-DRILL

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £4.50, p.p. 13p. De Luxe Professional Kit with 17 tools £7.00, p.p. 23p. Money ref. q'tee.

FOR PRECISION MODEL WORK

ONLY **£2** P.&P.10p

+ 6 TOOLS

MERLIN SUPPLY CO.


Dept. PW5D, Nailsea, Bristol BS19 2LP

When in LUTON, BEDS, you must visit the SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.
Closed all day Wednesday.

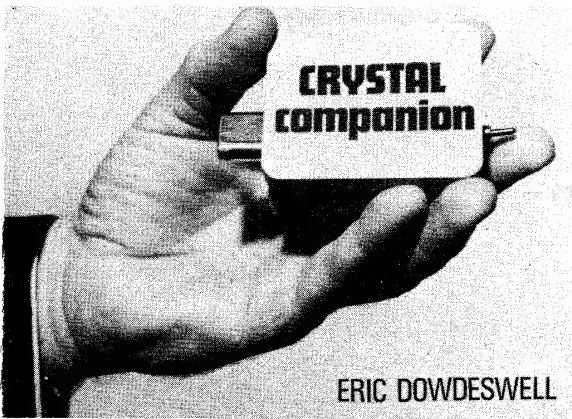SURPLECTRONICS
216 LEAGRAVE ROAD, LUTON, BEDS



ERIC DOWDESWELL

WITH the large numbers of crystals now available at low prices it is not unusual to go into a components shop and find a large box full of assorted crystals being continually churned over by eager hands in search of some peculiar frequency.


While the old 10X type of crystal can probably stand up to such rough usage the more delicate HC6U type is liable to succumb to such barbaric treatment.

The older "surplus" types can be over 25 years old and although well wrapped and apparently "as new" will often be found to have electrodes that have oxidised making the crystal useless. Having bought such a crystal and got it home it is a little annoying to discover that the wretched thing won't work!

This little crystal checker was designed to slip into the pocket so that it can be used to check almost any type of crystal before it is bought. It has worked with crystals from 100kHz to over 10MHz without any trouble.

Operation

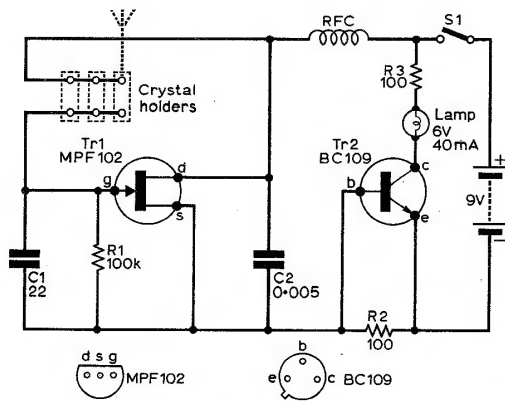The circuit is very simple but a little different from those usually found in this particular application



Transistor lead-out connections
Circuit diagram of the Companion.

insofar as the operation is "fail-safe". That is, the indicator lamp is on when the crystal is not oscillating thus providing a check on the working of the lamp. If the lamp came on only when the crystal was oscillating failure of the lamp to light could be due to either a faulty crystal or dud lamp.

The oscillator circuit itself uses an MPF102 f.e.t. transistor and just four other components plus three crystal holders. The lamp control circuit has a BC109 silicon transistor which acts as a switch for the lamp circuit.

In the non-oscillating state the MPF102 draws about 10mA current through resistor R2 which switches the BC109 "on" the lamp circuit being completed through the current limiting resistor R3 to the 9V supply. In this condition the lamp will light.

With a good crystal plugged in to one of the holders the MPF102 current drops to less than 1mA, depending on the activity of the crystal used, the BC109 is switched "off" and the lamp goes out.

Since the lamp draws around 30mA the unit should not be left switched on longer than is required to check a crystal in order to prevent the early demise of the PP3 battery.


Constructing the "Companion"


The checker can be built in any small box that will slip into the pocket and may be of metal or plastic or wood. The one used in the prototype is made up of a 3/4in. long section of plastic tube, rectangular in section, 2 5/8 x 2 1/8in. similar to that used in the construction of the popular Dewbox cabinets. Two Dewbox endcaps provide a handsome finish to the case.

Holes are drilled around the centre section to accommodate the three crystal holders to take 10X, HC6U and FT241/3 crystals so as to make the checker as versatile as possible. The holders are bolted on or fixed with Araldite. A 1/4in. diameter hole is drilled so that the indicator lamp is easily seen.

The simple wiring is mainly direct between components but a short busbar of thin tinned copper wire is run round one corner of the box to act as an "earth" return, one end of which is held under the locknut of the miniature on/off switch. Before doing this check that the dolly of the switch is isolated from the contacts.

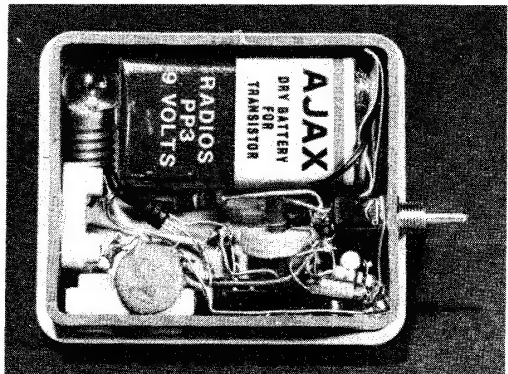After fitting the crystal holders, wire them in parallel, then fit one end cap and lay the PP3 battery



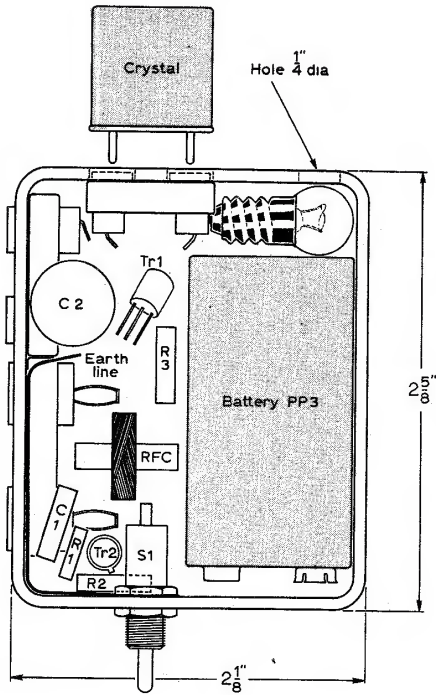


This actual size drawing of the Companion may be compared with the photograph on the previous page.

in position after which the remaining components can be soldered in place.

Because of the small size of this version of the checker a lamp holder was dispensed with and the connections soldered directly to the lamp. If a larger box is used a lampholder should be fitted.

The two transistors are wired into the circuit after everything else has been done. Especial care should be taken with the MPF102 transistor. Holding all three lead-out wires firmly in the jaws of a pair of longnosed pliers the wire ends should be tinned quickly and then soldered into the circuit without releasing the pliers. The BC109 is not so "touchy" but there is no harm in providing a heatsink when soldering it into place using the pliers as before.

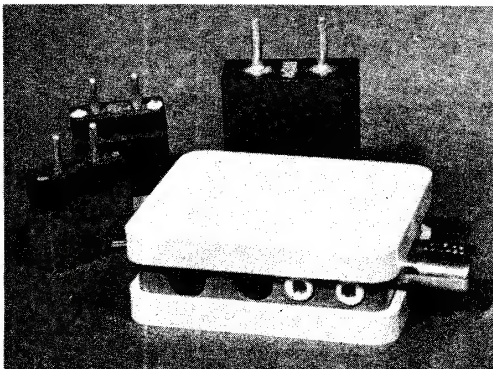

★ components list

Resistors:

R1 100kΩ 1/4W R2 100Ω 1/4W R3 100Ω 1/4W

Capacitors:

C1 22pF Polystyrene C2 0.005μF disc

Semiconductors:

Tr1 MPF102 Tr2 BC109

Miscellaneous:


Lamp 6V 40mA. Crystal holders (3) for HC6U, FT241/3 and 10X. S1, miniature on/off switch. Battery 9V PP3 and terminal clip. RFC, 2.5mH miniature. Dewbox 3/16 in. long with end caps or similar.

When the checker is completed the end caps can be pushed on leaving enough gap between them to accommodate an HC6U type crystal.

Checking Out

After double checking the wiring, paying particular attention to the transistor lead out connections, the unit can be switched on. Without a crystal plugged in the indicator lamp should light. Inserting a known good crystal should cause the lamp to go out.

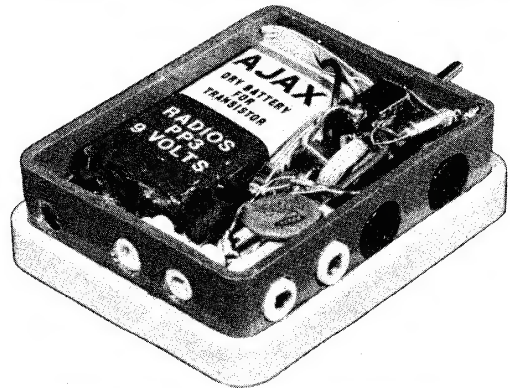The relative activity of a crystal may be estimated



This view clearly shows the hole for the indicator lamp.

by watching the lamp when the unit is switched on with a crystal in place. With an active crystal the lamp will go out immediately but if the crystal is reluctant to start the lamp will flash momentarily before going out. With a poor crystal the lamp may stay on but dimly.

With a really dud crystal the lamp will come on at full brilliance as if the crystal was not plugged in.

The "Companion" can be used on the workbench as a signal source for alignment purposes using crystals such as 470kHz or 1.6MHz for i.f. alignment or 100kHz or 1MHz for calibration work. A crystal on say 5MHz is very useful for calibration on the h.f. bands as well as for alignment.

If the checker is built into a plastic box there should be enough radiation for all the above purposes. If a metal box has been used it may be necessary to plug a short stiff piece of wire into any one of the unused crystal holder sockets to increase the radiation. A miniature telescopic aerial as supplied with some transistor radios is ideal for this purpose.



PRACTICAL WIRELESS

CROSSWORD COMPETITION No.2

THE 'CARLTON' RECEIVER

Many thousands of these tubular extension speakers are in use today—PW has rung the changes by putting a modern long and medium wave radio inside the speaker. Only the volume control and band switch show that the speaker is in reality a complete receiver. Circuitry comprises three silicon transistors and an inexpensive integrated circuit as an audio 'gain-block'. Full constructional information.

PLUS THE REGULAR "TAKE 20" AND "I.C. OF THE MONTH" SERIES AND OTHER CONSTRUCTIONAL ARTICLES AND FEATURES—ON SALE MAY 7th—PRICE 20p


ALL IN THE JUNE ISSUE, ON SALE MAY 7th

A 5-RANGE RF SIGNAL GENERATOR

This simple signal generator uses an FET in the oscillator which covers 150kHz to 30MHz. The audio modulation is separately available for testing of audio amplifiers and circuits. The only power requirement is a 9 volt battery contained within the unit.

SIMPLE IGNITION SYSTEM

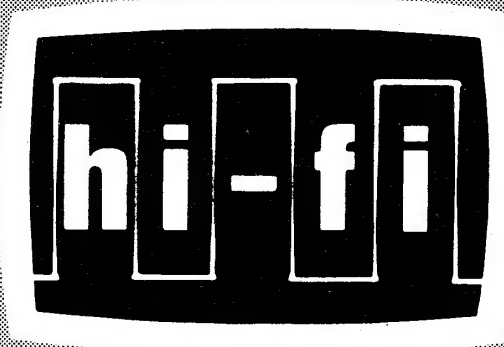You have seen advertisements for all kinds of gadgets that will reputedly save you many pounds a year in the running of your car. Here is one device, easily and quickly constructed, that will really carry out that promise. To try it is to keep it ... electronic timing for your car's ignition system. Circuits for positive or negative earth systems and all details in next month's issue of PW.



SIGNAL GENERATOR

THE audio frequency signal generator described here was designed and built to fill the need for a high quality, wide range instrument, capable of permitting accurate and reliable distortion, gain and frequency response measurements to be carried out on a wide range of audio equipment.

For an a.f. generator to be really useful, it must be accurate in respect of frequency and voltage output calibration, and it must maintain this degree of accuracy under widely varying conditions of use.

The initial calibration accuracy will depend on the frequency and voltage standards available at the time of calibration, plus the time and care taken over the calibration process. Also accuracy will be dependent upon the quality of the components used and, to a lesser extent, upon the workmanship involved. The basic design will, of course, also influence both factors.

On the present design, much thought has been expended, plus not a little experimental work, in producing a design that fulfils most adequately all the requirements of a very high quality instrument. Good quality components, used well within their ratings, ensure that initial calibration accuracy will be maintained almost indefinitely. The mechanical design also, has been aimed at producing a robust, easily assembled unit.

CIRCUIT

The generator is based, in common with virtually all available a.f. generators, upon the well known, and proven Wein Bridge. The three transistors Tr1, Tr2 and Tr3 form a high gain amplifier with d.c. coupling throughout, with the exceptions of the frequency determining capacitors. This has the twin advantages of being sparing of coupling capacitors, which lessens expense, and relieves the designer of solving unwanted phase shift problems.

The frequency of oscillation is dependent on the setting of VR1 and the capacitors selected by SW1. For oscillation to occur there must be adequate gain and there must be positive feedback, i.e. there must be a phase shift of 360° between the input and the output of the amplifier. For the Wein Bridge to oscillate, the gain requirement is very modest, being only 10db or three times. Since the gain of the


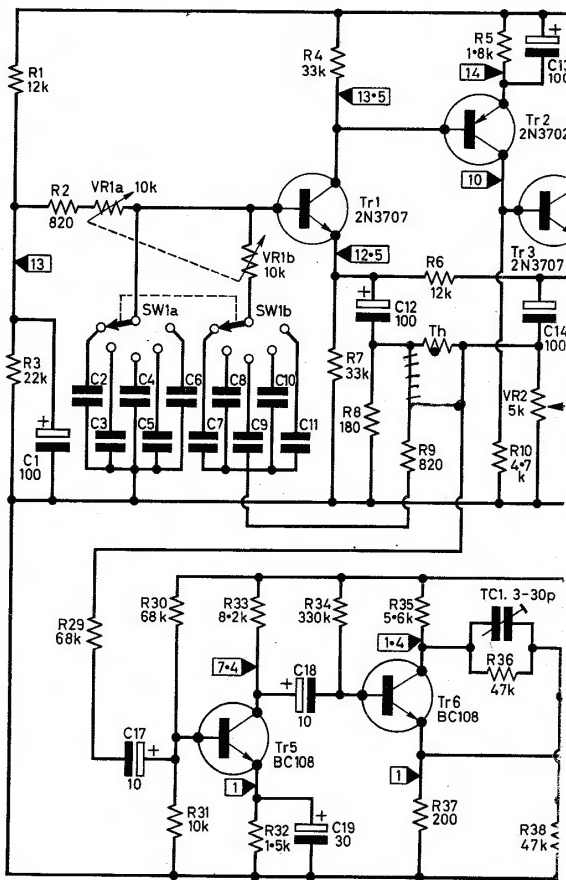
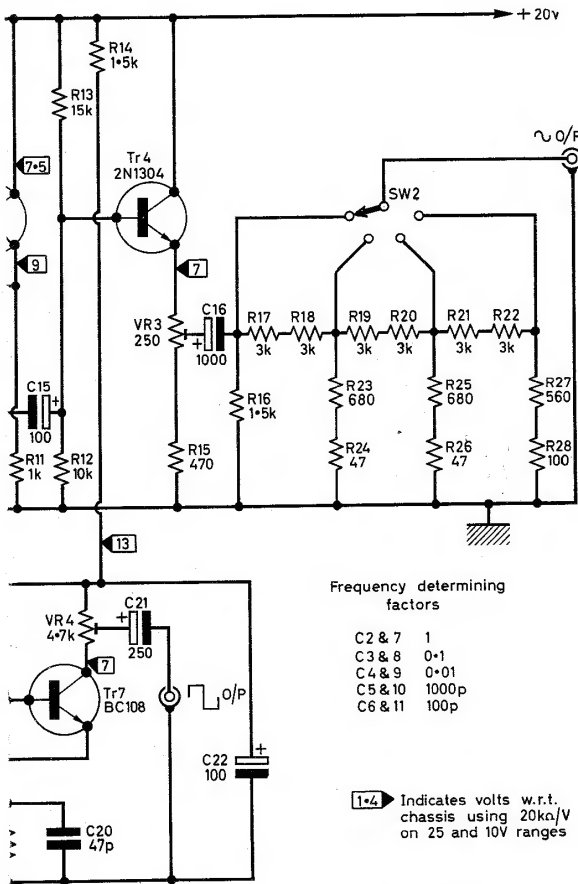


Fig. 1: The circuit of the Hi-Fi Signal Generator, an expl

TOR

H.T. KITCHEN

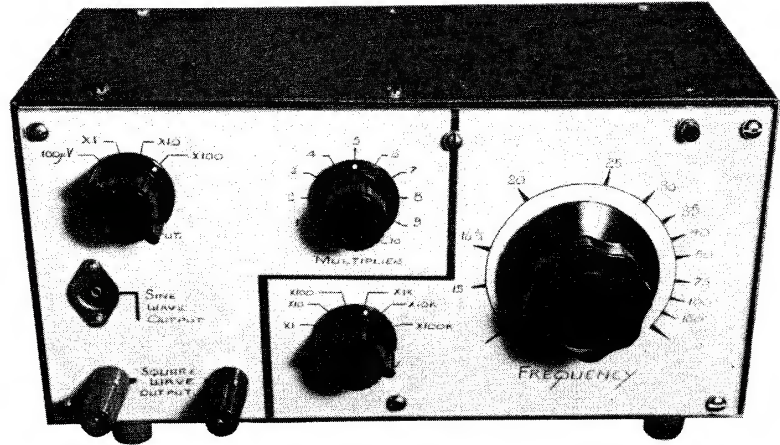

Frequency determining factors

- C2 & 7 1
- C3 & 8 0.1
- C4 & 9 0.01
- C5 & 10 1000p
- C6 & 11 100p

1.4 Indicates volts w.r.t. chassis using 20kV/4V on 25 and 10V ranges

operation of the operation of the various sections is given in the text.

★ components list

Resistors

- | | | |
|-----------|-----------|-----------|
| R1 12kΩ | R15 470Ω | R29 68kΩ |
| R2 820Ω | R16 1.5kΩ | R30 68kΩ |
| R3 22kΩ | R17 3kΩ | R31 10kΩ |
| R4 33kΩ | R18 3kΩ | R32 1.5kΩ |
| R5 1.8kΩ | R19 3kΩ | R33 8.2kΩ |
| R6 12kΩ | R20 3kΩ | R34 330kΩ |
| R7 33kΩ | R21 3kΩ | R35 5.6kΩ |
| R8 180Ω | R22 3kΩ | R36 47kΩ |
| R9 820Ω | R23 680Ω | R37 200Ω |
| R10 4.7kΩ | R24 47Ω | R38 47kΩ |
| R11 1kΩ | R25 680Ω | R39 4.7kΩ |
| R12 10kΩ | R26 47Ω | R40 2.2kΩ |
| R13 15kΩ | R27 560Ω | R41 1.5kΩ |
| R14 1.5kΩ | R28 100Ω | All 5% |
- VR1 10kΩ ± 10kΩ Lin. ganged
 VR2 5kΩ Lin. (can be 4.7kΩ)
 VR3 250Ω skeleton preset
 VR4 5kΩ skeleton preset (can be 4.7kΩ)

Capacitors

- | | | |
|---------------|----------------|----------------|
| C1 100μF 15V | C10 1000pF 1%† | C18 10μF 15V |
| C2 1μF 1%† | C11 100pF 1%† | C19 30μF 15V |
| C3 0.1μF 1%† | C12 100μF 15V | C20 47pF 1% |
| C4 0.01μF 1%† | C13 100μF 15V | C21 250μF 15V |
| C5 1000pF 1%† | C14 100μF 15V | C22 100μF 15V |
| C6 100pF 1%† | C15 100μF 15V | C23 1000μF 25V |
| C7 1μF 1%† | C16 1000μF 10V | C24 8μF 25V |
| C8 0.1μF 1%† | C17 10μF 15V | C25 100μF 50V |
| C9 0.01μF 1%† | | |
- TC1 3-30pF Beehive trimmer † see text

Semiconductors

- | | |
|------------|-------------------------------|
| Tr1 2N3707 | Tr8 BC108 |
| Tr2 2N3702 | Tr9 2N3053 |
| Tr3 2N3707 | ZD1 5.6V, 400mW Zener Diode |
| Tr4 2N1304 | TH S.T.C. R53 Thermistor |
| Tr5 BC108 | BR1 Bridge Rectifier, silicon |
| Tr6 BC108 | ○ BY164 or similar |
| Tr7 BC108 | |

Miscellaneous

- SW1 2-pole, 6-way (only 5 positions used)
 - SW2 2-pole, 4-way
 - SW3 Mains on-off
 - T1 Mains transformer, 240V pri., 12-0-12 sec (used as 0-24) 0.05mA, Home Radio Cat. No. TMM13.
- Aluminium and perspex for case; Indicator neon; knobs etc.

transistors used is considerably higher than this, no problem exists here. The phase shift requirements are also met, since the trio introduce a phase shift of 180° , and the frequency network introduces a further 180° . Since these phase shifts are effectively in series, the requisite 360° phase shift is produced.

Stability of the output voltage is important and to this end a thermistor is used. Since it has a negative temperature coefficient, it must be connected in the negative feedback mode. In Fig 1, it is in series with C12 and C14 and controls the a.c. negative feedback from Tr3 emitter to Tr1 emitter. The correct part of its coefficient slope is selected by the value of R8, under which conditions it will hold the output constant to better than $\pm 1\text{dB}$.

Although the a.c. gain is controlled by the negative feedback via the thermistor, the d.c. gain is still high. Although the silicon transistors chosen have very stable gain and leakage characteristics, the high overall gain does mean that any change in Tr1's characteristics, and to a lesser extent in Tr2's, will disturb the operating point of Tr3 to the detriment, if not complete failure, of the complete circuit. D.C. negative feedback via R6 provides a high degree of stability against any such changes.


In Fig. 1 five pairs of capacitors; C2-C6 and C7-C11, provide five frequency ranges, selected by SW1, with VR1 (a and b) providing continuous coverage with some slight overlap at either end. The degree of overlap is dependent on the values of R2 and R9, increasing them decreases the overlap, the converse also applying.

The output voltage from the oscillator is taken from the wiper of VR2, which acts as an infinitely variable control, in conjunction with the decade attenuator which follows later in the circuit. This feeds into an emitter follower, Tr4, which has a high input and low output impedance and effectively isolates the oscillator from any load which may be connected across its output. Tr4 is biased at 10mA emitter current by R12 and R13, permitting resistive loads as low as 150Ω to be connected across the output without altering the output voltage by any significant amount.

The coarse attenuator comprises SW2 and range resistors R16 to R28. It is a constant impedance type, with a characteristic impedance of 600Ω , and provides four decade voltage outputs of 1V, 100mV, 10mV and 1mV. This is somewhat more complex, and requires more resistors than the simple potential divider type of attenuator. It is preferred because of the near constant resistance it offers to the load on its four ranges. The resistance values as calculated are odd but the series connection of the range resistors enables preferred value resistors to be used with very little loss of accuracy. If an accurate a.c. millivoltmeter is available, the series connections enables individual resistors, i.e. R24, R26 or R28, to be changed to enable true decade switching to be achieved. The change in value should not be great; the next preferred value should prove satisfactory.

Although sine wave testing of audio equipment can reveal a great deal of information about it, it does not always tell the full story and needs to be complemented by another wave form.

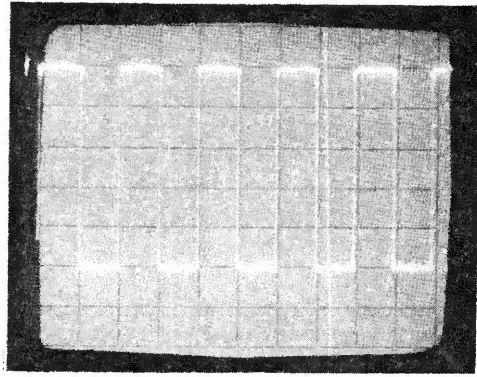The most commonly used such waveform is a square wave, and this is produced by the two transistors Tr6 and Tr7, with the assistance of Tr5. Tr5 is an overdriven amplifying stage, fed with the sine wave via R29 and C17. The output of Tr5 is



Actual photograph of the square wave at 1kHz.

partially squared and fed via C18 to Tr6, which in conjunction with Tr7, forms the well known Schmitt Trigger configuration. The component values were chosen for a very fast rise time. TC1 is a "speed up" capacitor, and is used in conjunction with R36, to form a time constant that exactly matches the parallel RC combination of the input impedance of Tr7 base. When these are equal, the coupling from Tr6 collector to Tr7 base is truly aperiodic, and extremely rapid rise times result.

The collector load of Tr7 is a preset resistor, VR4, so that the output of the square wave can be preset to any desired level, up to a maximum of approx 12V peak-to-peak. The coupling capacitor C21 must be as high in value as possible in order to maintain the tops of low frequency square waves as horizontal as possible.

POWER SUPPLIES

The question of power supplies will depend on the length of time the equipment is in use. For short, intermittent periods of use, batteries can be used. However, the current consumption of 25mA at 20v means four series connected 6V batteries of reasonably high capacity in conjunction with a 20V zener diode for stabilisation purposes. Four such batteries will be somewhat bulky, and the use of mains supplies is therefore an attraction. The circuit of the mains voltage power supply used on the prototype is shown in Fig. 2. The transformer used was rated at 50mA at 12.0-12V, used as 0-24. This is then rectified by the bridge BR1 to provide a voltage across the reservoir capacitor C25 of about 30V. This is then applied to the collector of the series regulator transistor Tr9, and to R41 which is the collector load of the error amplifier Tr8, the emitter voltage of which is held at a constant 5.6V by the zener diode ZD1. The current drawn by ZD1 is about 5mA.

COMPONENTS

For optimum performance and maximum long-term reliability, all the components used in the construction of the generator must be of good quality.

The semiconductors used were carefully selected, and should not be changed unless the individual knows what he is doing and why. Whilst comparable semiconductors do exist, their use has not been investigated, and no advice on this score is therefore offered.

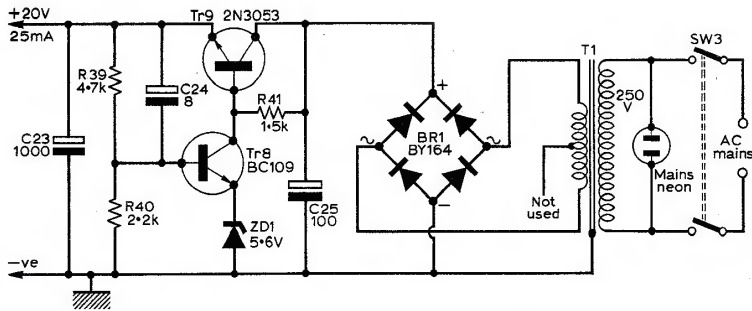


Fig. 2: The circuit of the stabilised power supply.

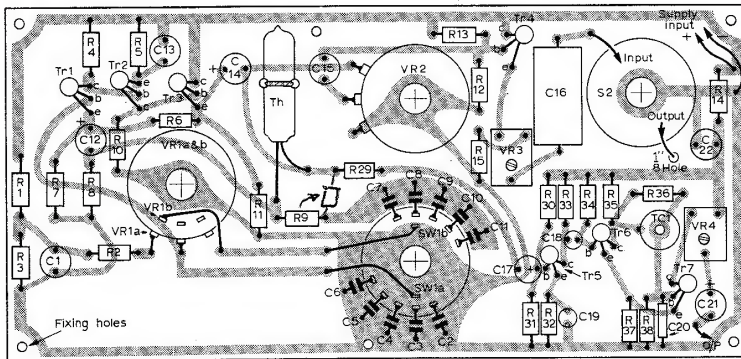


Fig. 3: The component layout and details of the printed circuit board.


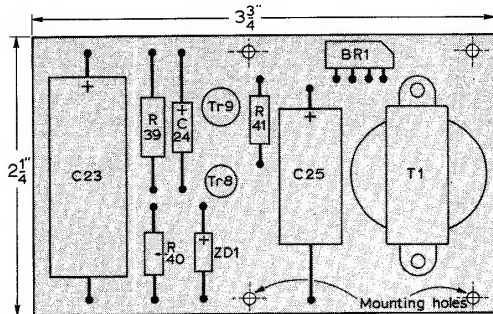


Fig. 4: The component layout of the power supply.

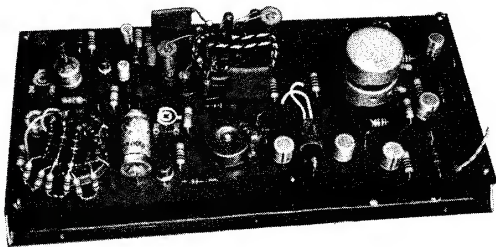

The neat construction using a printed circuit board can clearly be seen here.

With the availability, freely and cheaply, of high quality 5% carbon film resistors, there seems little point in using the inferior carbon composition types, unless these are to hand and cost is of paramount importance.

The majority of the electrolytic capacitors used are of the single ended, or P.C.B. type, as these assist in the conservation of space. The only radial ended electrolytics are those combining high capacity with a relatively high working voltage.

The capacitors used in the frequency determining network of the Wein Bridge should preferably be of 1% tolerance, as this means a single frequency scale can be used on the front panel. It must be admitted that 1% high value capacitors are somewhat expensive and wider tolerance capacitors can be used in the interests of economy. This then requires either the careful selection of capacitors, or the adoption of

a multiple frequency dial calibration if accuracy is not to be sacrificed to cost. Readers wishing to use 1% capacitors can purchase WIMA capacitors, as used on the prototype, from WAYCOM LTD., WORKINGHAM ROAD, BRACKNELL, BERKS.

CONSTRUCTION

For this type of circuit, a circuit board of some type is almost mandatory. The prototype was built on to an etched circuit board, measuring 9 1/4 in x 4 1/4 in, shown in Fig. 3. The fully completed board is supported behind the front panel, and parallel to it, by means of 1 in long insulated pillars drilled and tapped 4BA at either end. This allows 1/4 in 4BA bolts to be used for securing the circuit board, whilst the perspex and metal panel are secured by 1/2 in 4BA bolts.

The power supply is built upon a piece of plain Veroboard, 2 1/4 in x 3 3/4 in shown in Fig. 4 with the component siting.

The supply board is mounted on the rear of the cabinet. That on the prototype was backed by a piece of 1/8 in perspex to preclude any danger of short circuits between the component leads and the cabinet.

The front panel of the instrument was made of white card which is clamped to the front of the cabinet behind a protecting piece of 1/8 in perspex.

The cabinet for the prototype was made from 20s.w.g. aluminium to the sizes in Fig. 5. The easiest way of ensuring that the circuit board, cabinet front and perspex all line up accurately, essential if the control spindles are to pass without fouling through the front panels, is to make up the cabinet first. Then the circuit board and perspex are cut slightly smaller

so that they drop into the recess behind the front panel, formed by the top, bottom, and sides. The required holes are then scribed through, using the metal front panel as a template, and carefully drilled out. The holes for the controls in the circuit board will need to be of $\frac{3}{8}$ in diameter, the corresponding holes in the front panel can be $\frac{1}{4}$ in if accuracy in alignment is achieved. The holes for the output terminals will depend on the components actually used.

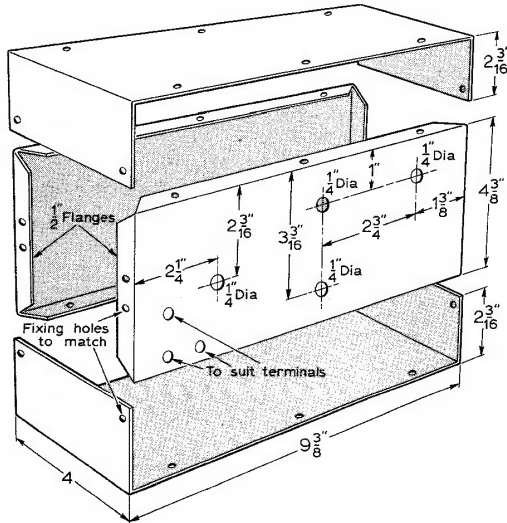



Fig. 5: The details of the case.

SETTING UP

After completing both circuit boards, they should be carefully inspected for soldering and for wiring errors. Then the power supply can be connected to the mains, its output disconnected from the generator board. The output should be monitored and either R39 or R40 altered if necessary to set the output voltage at 20V. The generator board can then be connected and further tests made. A meter capable of reading up to 25mA should be connected in series with one of the supply leads; a reading $\pm 10\%$ of this should be obtained. The meter can then be removed from circuit. Voltage tests using a 20K Ω /V meter should provide readings substantially in agreement with those given in Fig. 1.

In order to ensure that the generator is correctly 'calibrated' in respect of frequency and voltage, an accurate, wide range oscilloscope and a.c. millivoltmeter are required. Another a.f. generator of known accuracy is a useful aid, but is not indispensable. It is only really necessary if wide tolerance capacitors are used in the frequency network.

The oscilloscope and meter should be connected to the sine wave output, and a check made for oscillation throughout all ranges. The sine wave should "look good"; however a visual check for distortion does not reveal it unless it is really severe. Should this prove to be the case, transistor "spreads" may be responsible, in which a change in Tr1 bias effected by changing R1 or R3 may help. If it is due to a thermistor "spread," variation in R8 may help.

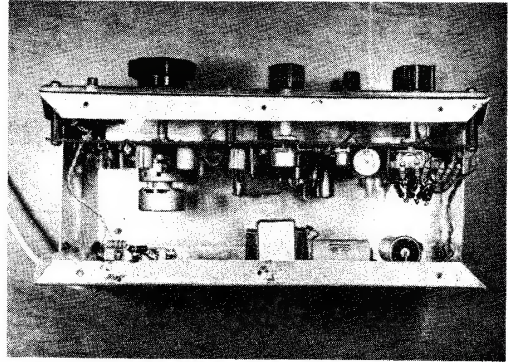

Components should not be varied unless really necessary, and even then variations should be in small steps.

If all seems well, attention can be turned to frequency calibration. Here two courses are possible. If 1% capacitors are used for C2-C6 and C7-C11, one frequency scale will suffice. If wide tolerance capacitors are used, a different scale for each range will be necessary, unless some accuracy can be sacrificed in the interest of simplification and one scale. Another a.f. generator will be necessary if different frequency scales are to be provided. The use of Lissajous figures for frequency calibration is well known and need not be repeated here.

Lissajous figures are used, using the mains as a frequency standard. VR1 is used on Range 1, and points plotted at 15Hz, 16.6Hz, 20Hz, 25Hz, 30Hz, 35Hz, 40Hz, 50Hz, 75Hz, 100Hz and 150Hz. Range 2 will be these frequencies $\times 10$, Range 3 will be $\times 100$ and so on.

The next step is to set the output voltage. VR2 should be at maximum, with SW2 on the 1V position. Using a frequency of 1kHz, VR3 is set to give a reading on the meter of precisely 1V. SW2 is then set at 100mV, and the output checked, similarly at 10mV and 1mV, if the meter will read as low as this R24, R26 and R28 can then be changed if necessary.

The frequency response can then be checked if required, and should be constant to ± 1 db from 15Hz to 150kHz, falling to -2.5 db at 1.5MHz.

For setting the Schmitt trigger, the ideal 'scope would be a d.c. coupled one, with the h.f. response extending to 10MHz or higher. On an a.c. coupled 'scope, considerable sloping of the tops of the low frequency square waves can be expected.

Similarly, unless the 'scope has a first class h.f. response, rounding off the shoulders of the leading edges of the square waves can be expected at high frequencies. The measured rise time of the prototype square wave at 1kHz was 250nS (nanoseconds).

The effect of TC1 is only apparent at the higher frequencies, where it should be adjusted so that the shoulders of the leading edges of the square waves have neither "overshoot" or "sag."

VR4 can be adjusted to provide a square wave output of up to 12V peak-to-peak. Designing an attenuator that does not degrade a fast square wave is not too easy and was not attempted.

The mark-space ratio should be one-to-one, and is dependent upon Tr5 providing a symmetrical output to the trigger. Any variation of this ratio from the required 1:1 can be corrected by variation in the value of R29. ■

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

DUE to the postal dispute no reports have reached me in time for inclusion in this issue. The following news items were obtained from Radio Sweden's DX programme: 'Sweden Calling DXers' and from my own log.

GERMANY. DRM23, *Radio Bremen* on 6190kHz has announced that it plans to increase its power from the present 10kW in the near future.

GUATEMALA. *Radio Cultural* has been reported at 1205 on 9505kHz with a strong signal.

NEW CALEDONIA. *Radio Noumea* is reported to be using the new frequency of 9510kHz. The times of the broadcasts are 0600-1100 and 2330-0200, the language used is French.

NORWAY. *Radio Norway* now broadcasts a DX programme called 'DX Radio Norway' on the first Sunday of every month. The first programme was scheduled to be broadcast on March 7th. The programmes are transmitted at 0800, 1000 and at two-hourly intervals throughout the day. Radio Norway has also reported that it hopes to have transmitters with power in the region of 500 to 1000kW in operation before the end of 1974.

PERU. *Radio Nacional*, Lima, Peru, has been heard broadcasting at 0300 on a frequency of 6082kHz. The programme consisted of Peruvian music.

Choosing a receiver

Since I started writing this column I have had many queries from readers, the most common being about the choice of equipment. In the following paragraphs I list the most important features for a DXer's receiver. Each DXer requires a slightly different receiver and the following is my own order of importance.

An adequate short-wave range. Before purchasing a receiver the listener should decide which bands he is interested in. Some listeners may require coverage of the 49m to 13m bands only, whereas others may have a special interest in the tropical bands (120 to 60 metres). Most listeners will probably settle for a general-coverage receiver (540kHz to 32MHz).

An external aerial connection. This is a very important point which can easily be overlooked. No short-wave receiver can give DX performance unless a good aerial is used.

Bandspread frequency control. With the present crowded state of the bands it is essential to have a receiver with this feature to enable adjacent stations to be separated. The receiver should also have a logging scale so that the setting can be noted and returned to at a later date.

Adequate selectivity. Selectivity is a measure of

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

the ability of the receiver to separate two adjacent stations. Some receivers have a variable selectivity control and this can be very useful.

Adequate sensitivity. Sensitivity is a measure of the receiver's ability to pick-up and amplify weak signals. A DXer's receiver must be sensitive as he is mainly interested in weak signals.

An aerial matching device. Sometimes called an antenna trimmer this very useful control allows the aerial to be correctly matched to the receiver. A very small mis-match can cause a serious loss of signal.

A crystal calibrator. This gives signals at intervals of 100kHz and is an invaluable aid to determining the exact frequency of any station.

A signal-strength indicator. Usually in the form of a magic-eye indicator or an S-meter. These indicators enable the relative strengths of incoming signals to be determined.

An r.f. gain control. Most receivers have an audio gain control only, the addition of a separate r.f. control can greatly assist in the reception of difficult signals.

An automatic gain control switch. All receivers incorporate some form of automatic gain control which adjusts the gain of the receiver to compensate for sudden fluctuations in the input signal. The a.g.c. switch enables the circuit to be disconnected, with the circuit out of action weak signals can be greatly amplified.

A noise limiter. Sensitive receivers are susceptible to noise interference. The noise limiter clips the tops of the noise signals and stops them from reaching the output of the receiver.

I hope that the above paragraphs have been of interest to those of you who are thinking of buying a receiver, I look forward to receiving reports from you in the near future.

All reports please to me at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex, by the 15th of the month.

1971 WORLD RADIO-TV HANDBOOK

Published by Billboard A.G. and available from
Fountain Press, 46 Chancery Lane, London, W.C.2.
372 pages, 9 × 6in. Price £2.30

FOR those not familiar with this publication it lists virtually every radio and television station in the world and provides all the information you are ever likely to need for DXing—in fact I don't know of a short wave listener who doesn't regard it as a sort of "bible".

Every year we look forward to the new edition and we have not been disappointed with this one. The introductory articles that used to take up the first part have been dropped and published separately for the first time under the title "How to Listen 1971".

We could hardly do without it at the P.W. offices and we are sure you will be in the same position if you are interested in any form of DXing.—H.W.M.

SHORT WAVES

EACH month, letters arrive which raise various queries. Some contain the usual questions which crop up again and again, others are peculiar to a person or piece of equipment. Over the years numerous questions have been answered but it seems obvious that more and more newcomers are reading this page and are, therefore, repeating the same questions which others before them raised. So for once, let's have a session of answers to some of the problems which have arrived over a period of months.

First query is usually a "By the way" enquiry and asks what gear does G3JDG use and on what bands can emission from your scribe be detected. Gear permits 120W of a.m./c.w. from 3.5MHz to 30MHz and 10W on topband. Main interests are the h.f. DX bands and an unashamed preference for c.w. Phone is used on topband and then, usually, mobile. The receiver is a valve type with r.f., mixer, two i.f., det. and one audio plus b.f.o. and Q-multiplier. An a.t.u. is always used since aerials are a source of much experimentation. Antenna for the past six months has been a solitary slither of wire some 60ft. long at about 18ft. Current move into a "new" house should see activity on 14MHz c.w. and on topband a.m. at first. A modified Pye reporter transceiver allows 18W on 70MHz.

Two questions which occur more often than any others. Where can I get a list of call signs and countries, and what is the "best" aerial to use? A country's list can be obtained from the R.S.G.B., 35 Doughty Street, London, WC1N 2AE, price is 6½p. Incidentally, those who are not members of the R.S.G.B. might like to send for a free specimen copy of the Society's monthly publication *Radio Communication*.

The short answer to the question, "What is the best aerial to use", is simply "There is no such animal". An aerial which is excellent for a particular band will not necessarily be any good on another frequency. Again, the particular physical location can affect the performance. Aerials are often largely a matter of suck it and see.

The only aerial which might be considered an "all frequency" affair (speaking now of 1.8 to 30MHz) is simply a length of wire as long as possible, as high as possible and as far from earthed objects as possible. The wire is then fed to the receiver via an a.t.u. (aerial tuner unit). This is, in fact, the system in use at G3JDG at the moment. It is essentially a compromise system and there are other set-ups which could quite easily out-perform it. Aerials, or antennas, are a subject in themselves and there are numerous textbooks which discuss the relative merits of each type to which interested readers are respectfully referred.

A common question from newcomers is simply where to start, what receiver, etc. If the receiver is to be home-built, then much will depend upon individual skills in construction. For the absolute beginner it might be easier to purchase a simple kit,

THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz • Times in GMT

the only real alternative being to buy a ready-made unit.

Headphones are a must and aerials have already been dealt with as has a country's list. Armed with these basic essentials one is all set to start the initiation of becoming a short wave listener (s.w.l.). Amateur bands to listen on (up to 30MHz) are: 1.8—2.0MHz; 3.5—4.0MHz; 7.0—7.1MHz; 14.0—14.35MHz; 21.0—21.45MHz; 28.0—29.7MHz.

A good wall map of the world is useful and a packet of coloured drawing pins will permit stations logged to be located on the map. Incidentally, this procedure, besides adding interest, will also provide a surprisingly good working knowledge of geography over a short period of time.


A point which often appears to baffle the beginner is the disappearance of signals from a particular band or bands. There are many causes of fluctuation in communications. For example, the height of the ionised layers above the earth which reflect the radio waves back has a marked effect. Again, the activity of the sun plays an important role as does the season or time of year. As an example, at the time of writing, the 14MHz or twenty metre band is mainly active from around 0700 to 2200hrs although some signals might be heard occasionally outside these times. The 21MHz band is mainly active between 0700 and 2000hrs while up on 28MHz the signals are in evidence between 0800 and 1800hrs.

Another favourite query is how to get a transmitting licence and what is involved. The licencing body in the U.K. is the Post Office. In order to obtain a licence the Post Office need to be satisfied of a persons technical competence to operate transmitting equipment.

There are two types of licence. For a full "A" licence, which permits the holder to transmit on all amateur bands from 1.8MHz upwards, it is necessary to pass a written technical examination. The other test is that the candidate is required to send and receive Morse at the rate of 12 words per minute. A pass in the technical paper is essential for either licence.

If the Morse test is not taken it is still possible to obtain a licence but in this case transmission is restricted to the amateur frequencies from 144MHz (two meters) and higher. Thus all the h.f. DX band would be "out of bounds" as regards transmission. This licence is called a "B" licence and holders are distinguishable by a call sign which begins "G8" followed by three letters. Some holders of full licences have a G8 call sign but these are followed by only two letters. Note that in Scotland call signs begin "GM" and in Wales with "GW". GI (Northern Ireland), GC (Channel Islands), GD (Isle of Man). Thus a G8 licence issued to a Scottish amateur would begin GM8, etc.

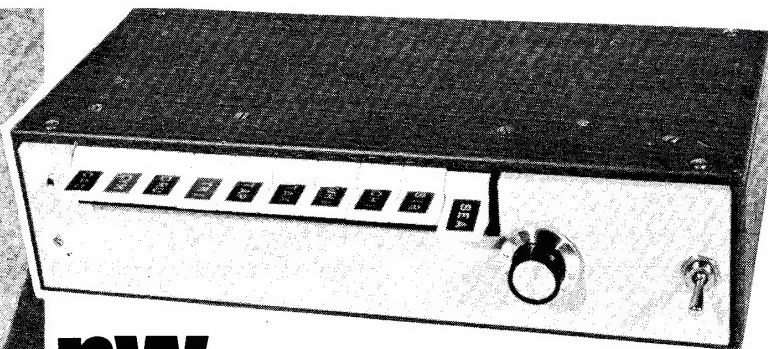Logs for the Amateur Bands must arrive before the 15th of each month. The address is:
14 Manland Avenue, Harpenden, Herts



pw sound effects SYNTHESIZER

PART 3

THREE more circuit boards and the power supply complete the electronic percussion and sound effects synthesiser for which general constructional details and the circuits etc. for castanets, cymbal, snare drum, triangle, woodblock, taxi horn, train whistle and bell chime were given in parts 1 and 2.

The remaining two generator circuits Nos. 9 and 10, are those for a ship's siren and the sound of the sea (surf). Details are also given in this part for the mixer amplifier and power supply etc. However, before going on to these circuits it would be as well to deal with the small modification that must be carried out on the organ key switch assembly.

There are 10 keys on this and when either one is pressed it will stay down until pressed again. This action is facilitated by small phosphor-bronze clips, one to each key and the function of each clip is to hold a small brass pin within the key guide frame. The operation of all the circuits 1 to 9 is that they must produce the sound when the key is pressed and instantly released, or pressed and held under pressure, i.e., the keys must behave like a piano key. All that is necessary is to remove the phosphor-bronze clips on keys 1 to 9 *only* and shake or pull out the small brass pins. When the keys are now pressed they will immediately return to normal when pressure is released. Key No. 10 which actuates the sea sound generator (circuit No. 10) must be left to work as intended i.e., when pressed down it must stay down until pressed again. This allows the sea sound to be run continuously without having to hold the key down.

The contact system on each key is simply a pair of single pole change-over switches and one or both can be used for the make and break of each keying circuit. The writer simply paralleled both sets of contacts but used them as a single make/break switch. This will be referred to again later.

Circuit for Ship's Siren—No. 9

This circuit is given in Fig. 22 and employs a phase shift oscillator (Tr1) operating at a frequency of about 120Hz and which can be adjusted by variation of R3. The output from Tr1 is attenuated by R8 and fed directly to Tr2 which is biased to cut-off by R16. The noise content for the sound is produced by the noise diode NDI, the output signal from this being slightly attenuated by R11. The sine-wave signal from Tr1 and the noise signal are combined in Tr2 which is keyed on by key No. 9. The output from Tr2 is attenuated to a level suitable for the mixer amplifier by R19/R20. The circuit board layout is given in Fig. 23. The circuit should require little or no adjustment except for pitch but the noise content of the sound, which should not be too predominant, can be regulated by variation of R11. Waveforms for this circuit are shown in Fig. 26 (Ship Siren circuit, A and B).

F.C. JUDD

Surf on the Beach—

No. 10

Surf rolling up on the beach and receding is a fairly slow movement and the sound itself, which is mainly random noise, rises and falls in amplitude at the same rate as the movement of the water. Here we need a slow but sinusoidal rate of change in signal level. The noise diode ND1 provides the white noise but to be effective a slight change of pitch in the noise is needed as well as the amplitude variation.

The noise signal is fed directly to Tr2 which is rendered almost non-conducting because of the large value resistor (1.5MΩ) between the base and positive rail. The base is however, directly coupled (via R7) to the collector of the slow running phase shift oscillator Tr1. As the potential at Tr1 collector rises and falls Tr2 will become fully conductive and/or quiescent at the same rate. The noise output signal from Tr2 will rise and fall accordingly. The phase-shift oscillator runs at approximately 1 complete cycle in 10 seconds. The change in pitch of the noise output is produced by feedback via C10. In operation, key No. 10 is pressed down and stays down (see above) so that the sound continues until the key is again pressed and released. The sound must not cut off completely as the amplitude falls but simply fall to a low level. Adjustment to the value of R10 (1.5MΩ) may therefore, be necessary, i.e., the value may have to be reduced to 1.2MΩ or increased to 1.8MΩ. The sound produced by the circuit is quite realistic but should not be too loud when used as a background effect for desert island type tunes. Note that the key for this circuit (No. 10) is wired so that the key contacts are "on" whilst the circuit is non-operational. When key No. 10 is closed as shown in the circuit, Tr2 is biased to cut off. The circuit board layout is shown in Fig. 25 and relevant waveforms in Fig. 26 (Surf on Beach Circuit A and B).

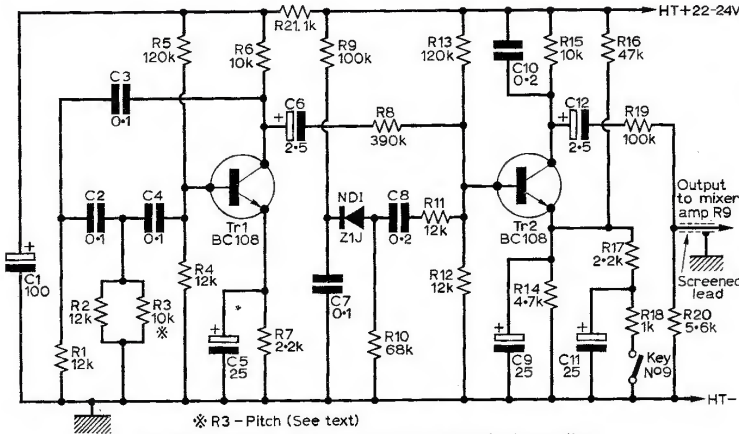


Fig. 22: The circuit of the ship's siren sound synthesiser section.

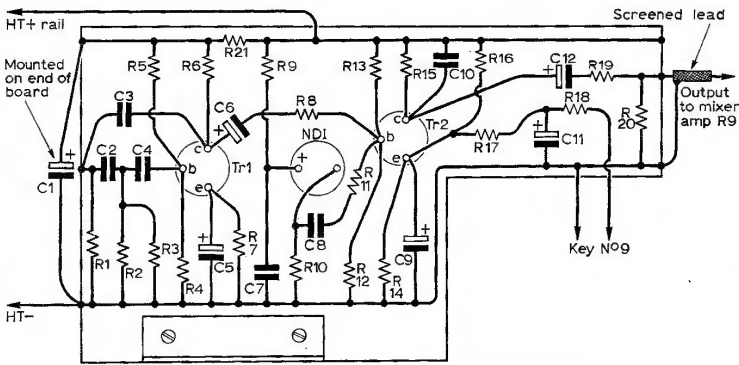


Fig. 23: The component layout for the ship's siren synthesiser.

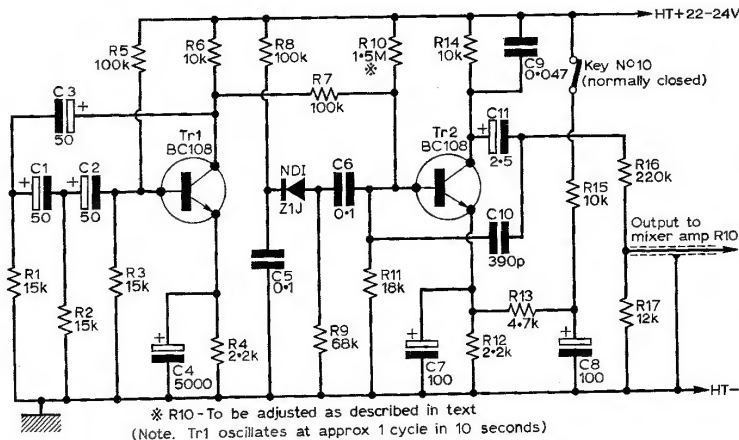


Fig. 24: The circuit for the 'surf on the beach' sound.

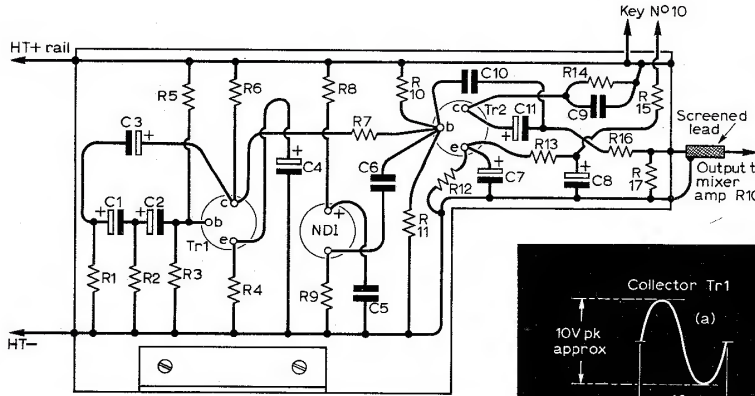


Fig. 25: The component layout for the surf sound synthesiser.

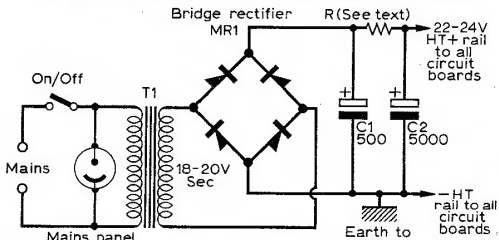


Fig. 27: The power supply circuit.

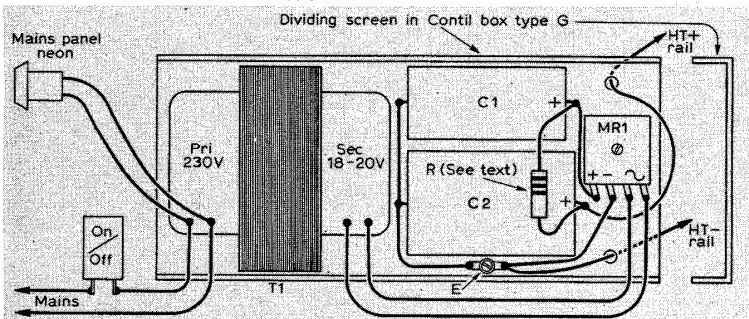


Fig. 28: The construction of the power supply section which is built on the dividing panel supplied with the case.

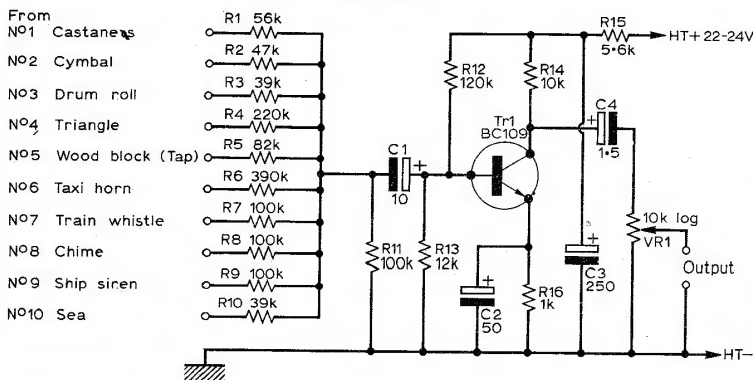


Fig. 29: The circuit of the mixer amplifier. The values of R1-R10 may have to be varied as mentioned in the text.

The Power Supply

The circuit for the power supply is given in Fig. 27. The supply on load, with all circuits connected but not keyed, should be not less than 22V and not greater than 24V. The smoothing resistor R, which should be

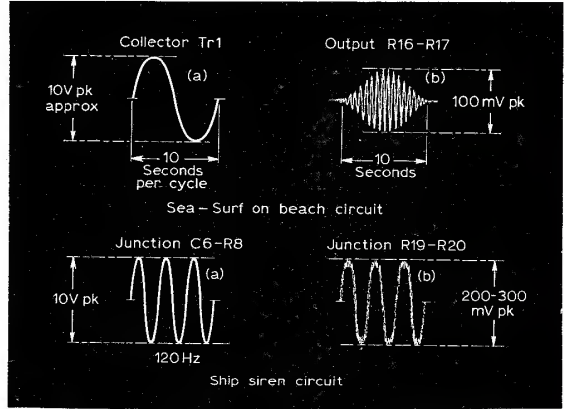


Fig. 26: The waveforms of the surf and ship's siren circuits.

about 1k Ω , may therefore require adjustment to value. The total current drawn by the generator circuits (not keyed) and the mixer amplifier should be approximately 20mA. The layout for the power supply as used on the dividing chassis of the Contil Mod 2 case employed for the prototype unit, is shown in Fig. 28.

Mixer Amplifier

This is a single stage signal amplifier with input attenuation to reduce the signals from each of the generator circuits to a level appropriate to each of the sounds. The input attenuation resistors R1 to R10 also serve to prevent impedance loading by each circuit and also signal overloading of the amplifier itself. The values chosen for R1 to R10 may require slight adjustment one way or the other in value so that the levels of the various sounds are relative for any setting of the volume control. The volume control has been provided simply to control the overall output from the unit.

★ components list — part three

Ship Siren Circuit No. 9

Transistors

Tr1, Tr2 BC108 Mullard

Noise Diode

ND1 Z1J (see part 1) Semitron

Resistors

R1 12k Ω	R8 390k Ω	R15 10k Ω
R2 12k Ω	R9 100k Ω	R16 47k Ω
R3 10k Ω	R10 68k Ω	R17 2.2k Ω
R4 12k Ω	R11 12k Ω	R18 1k Ω
R5 120k Ω	R12 12k Ω	R19 100k Ω
R6 10k Ω	R13 120k Ω	R20 5.6k Ω
R7 2.2k Ω	R14 4.7k Ω	R21 1k Ω

All ½W, 10% types

Capacitors

C1 100μF	C7 0.1μF
C2 0.1μF	C8 0.2μF
C3 0.1μF	C9 25μF
C4 0.1μF	C10 0.2μF
C5 25μF	C11 25μF
C6 2.5μF	C12 2.5μF

Sea (Surf on Beach) Circuit No. 10

Transistors

Tr1, Tr2 BC108 Mullard

Noise Diode

ND1 Z1J (see part 1) Semitron

Resistors

R1 15k Ω	R7 100k Ω	R13 4.7k Ω
R2 15k Ω	R8 100k Ω	R14 10k Ω
R3 15k Ω	R9 68k Ω	R15 10k Ω
R4 2.2k Ω	R10 1.5M Ω	R16 220k Ω
R5 100k Ω	R11 18k Ω	R17 12k Ω
R6 10k Ω	R12 2.2k Ω	

All ½W, 10% types.

Capacitors

C1 50μF	C6 0.1μF
C2 50μF	C7 100μF
C3 50μF	C8 100μF
C4 5000μF	C9 0.047μF
C5 0.1μF	C10 390pF

Mixer Amplifier

Transistors

Tr1, BC109 Mullard

Resistors

R1 56k Ω	R7 100k Ω	R13 12k Ω
R2 47k Ω	R8 100k Ω	R14 10k Ω
R3 39k Ω	R9 100k Ω	R15 5.6k Ω
R4 220k Ω	R10 39k Ω	R16 1k Ω
R5 82k Ω	R11 100k Ω	
R6 390k Ω	R12 120k Ω	

All ½W, 10% types

Capacitors

C1 10μF	C3 250μF
C2 50μF	C4 1.5μF

Power Supply

Transformer T1 Pri. 230V., Sec 18-20V (TS/18/2, Henry's Radio)

Resistor R 1 Watt (see text)

Capacitors C1 500μF 30v wkg.
C2 5000μF 25-30v wkg.

Rectifier MR1 Bridge type LT120 or LT119 (Henry's Radio)

Miscellaneous

Volume Control VR1 10k Ω log.
Jack or Phono type.
Mains on/off switch Toggle type
Panel Neon 230V mains type

The layout for the mixer-amplifier circuit is given in Fig. 30.

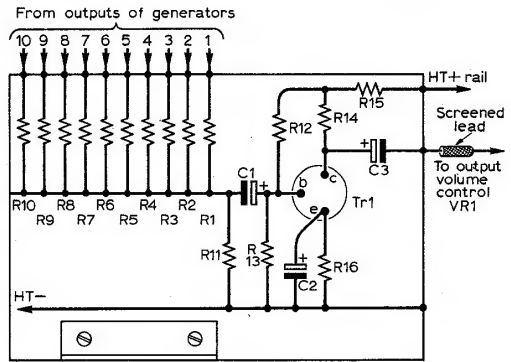


Fig. 30: The component layout of the mixer amplifier.

The Keying Contacts

The modification required to allow the keys to be pressed and instantly released, i.e., the removal of the phosphor bronze clips, was dealt with earlier. The switches attached to these keys are a pair for single pole changeover. Both sets can be used for keys 1 to 9 as shown in Fig. 31, i.e., both pairs are wired to provide a paralleled pair of on-off contacts. The same applies to key No. 10 (sea circuit) except that the rear pair as in Fig. 31b are used as the contacts are normally closed.

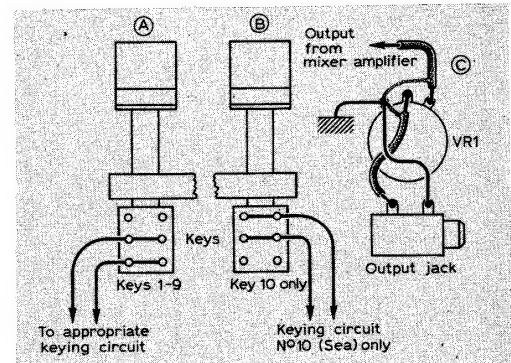


Fig. 31: The wiring of the keying contacts and the level control.

Final Assembly

If the specified case has been used, the final assembly should appear as shown in the photograph which shows the unit as seen from beneath, i.e., with the base panel removed. As explained in part 1 the circuit boards are assembled on what is really the top of the case so that when it is turned over the keys are all at the top as shown. Whatever type of case is used the assembly should follow this pattern, particularly if the unit is to be used with an electronic organ.

Operation

It was mentioned previously that each circuit

—continued on page 70

COMPLETE STEREO SYSTEM

FOR ONLY

£40.95
CARRIAGE £175



PREMIER STEREO SYSTEM "ONE" Consists of an all transistor stereo amplifier. Garrard 2025 T/C auto manual record player unit fitted stereo mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on off, stereo mono switch. Brushed aluminium front panel Black metal case with teakwood ends. Size 12" x 5 1/2" x 2 1/2" high (Amplifier available separately if required £14.95 Carr. 40p.) **NOW AVAILABLE - MATCHING FM TUNER £22.05**


PREMIER STEREO SYSTEM "TWO"
As system 'ONE' above but with Garrard SP25.
PREMIER PRICE £47 Carr. £1.75

MIDLAND AM/FM STEREO TUNER AMPLIFIERS

Two new all solid state receivers from Midland at economical prices. Beautifully styled in slimline cabinets.



MODEL 19-520

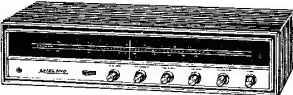

MODEL 19-542


	MODEL 19-520	MODEL 19-542
Specifications	19 transistors, 12 diodes, 2 varistors	22 transistors, 12 diodes
Tuning range	FM 88-108 MHz FM Stereo Multiplex AM 535-1605 kHz	FM 88-108 mHz FM Stereo Multiplex AM 535-1605 kHz
Aerial	Internal AM and external FM	Internal AM and external FM
Frequency response	50-17,000 Hz	35-20,000 Hz
Power output	2 1/2 watts rms per channel (8 watts music power)	4 watts rms per channel (18 watts music power)
Inputs	Magnetic/Ceramic phono and aux.	Magnetic/Ceramic phono and aux.
Speaker impedance	4-8 ohm	8 ohm
Controls	On/off, Volume, tone, balance, tuning, AFC, Stereo indicator	On/off, Volume, bass, treble, balance, tuning, AFC, Stereo indicator
Function selector	AM, FM, FM Stereo, Phono (Stereo indicator light)	AM, FM, FM Stereo, Ceramic, Magnetic, Aux.
Size	15" x 8 1/2" x 3 1/2"	16 1/2" x 9 1/2" x 3 1/2"
PRICE	£30.45 Carr. & Ins. 50p	£44 Carr. & Ins. 50p

PREMIER STEREO SYSTEM "SIX" SAVE OVER £16

Comprises Midland AM/FM Stereo Tuner Amplifier Model 19-542. Pair of loudspeaker systems as System "ONE" Garrard SP25 Mk. III fitted Goldring G850 Stereo Cartridges with teak plinth and cover. Total rec. list price over £81.


PREMIER PRICE £75 Carr. & Ins. £1.75

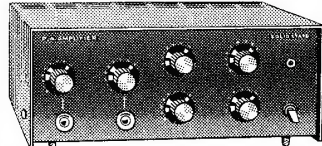50 WATT PUBLIC ADDRESS AMPLIFIER MODEL PA-5000



A top quality amplifier giving 50 watts rms power output (80W peak). Incorporates 8 transistors and 4 silicon diodes (silicon output transistors). Inputs for 2 microphones each with individual volume controls, plus phono/aux input. Master volume control and Bass and Treble Controls. Well presented front panel for ease of operation, on/off power flick switch and pilot light. Output impedance 4/8/16 ohms 3/16 and 2 sensitivity 2mV (50kΩ) Phono/Aux 300mV (100kΩ). Frequency response 50-20,000Hz. Fused output and thermal overload protection. A.C. Mains 220-250V, 50/60Hz Size 13 1/2" x 9 1/2" x 5 1/2".

PREMIER PRICE £39 P. & P. 50p

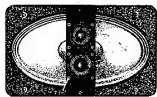

E.M.I. 13 x 8 in. HI-FI SPEAKERS
Fitted two 2 1/2in tweeters and crossover network. Impedance 8 or 16 ohm. Handling capacity 10W. Brand new.
£3.47 P. & P. 40p



HI-FI STEREO HEADPHONES
Designed to the highest possible standard. Fitted 2 1/2in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.
£2.47 P. & P. 25p.

STEREO STETHOSCOPE SET Low imp. £1.95 P. & P. 10p.
MONO STETHOSCOPE SET Low imp. 52p. P. & P. 10p.

PREMIER EXCLUSIVE! MIDLAND CASSETTE TAPE RECORDER 12-112



Solid state incorporating Automatic Level Control for trouble-free 2-track recording. Inputs for mike and aux. Earphone socket. Complete with batteries and earpiece. Size 10 1/2" x 5 1/2" x 2 1/2".
PREMIER PRICE £16.50 P. & P. 40p



POCKET SIZE MULTI-TESTER With wide angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C. 19 Ranges: 0.5-25-50-250-100-2000 volts DC. 0.1-10-50-100-500-1000 volts AC. 0.5-0.5A-2.5 mA-250 mA DC. 0-6000 ohms-6 megohms, 10μ μf-0.001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions. **£4.90 P. & P. 17p.**

SPECIAL OFFER!



GARRARD SP25 MK II SINGLE RECORD PLAYER FITTED GOLDRING G850 MAGNETIC STEREO CARTRIDGE COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER.

Total list price over £24.
PREMIER PRICE £18.90 P. & P. 50p.



"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped-attractively boxed.

LP3 3" 250' P.V.C.	25p	LP8 5 1/2" 1200' P.V.C.	68p
DT3 3 1/2" 600' POLYESTER	37p	DT6 5 1/2" 1800' POLYESTER	£1.12
SP3 5" 600' P.V.C.	42p	TF6 5 1/2" 2400' POLYESTER	£1.87
LP5 5" 900' P.V.C.	50p	SP7 7" 1200' P.V.C.	62p
DT5 5" 1200' POLYESTER	75p	LP7 7" 1800' P.V.C.	75p
		DT7 7" 2400' POLYESTER	£1.25
		TT7 7" 3600' POLYESTER	£2.50

TAPE SPOOLS 3" 10p, 5", 5 1/2", 7", 9", Post and Packing 3" 5p, 5", 5 1/2", 8p, 7" 10p. (3 reels and over Post Free).



TAPE CASSETTES	PRICE
C60 (60 min.)	37p £1.05
C90 (90 min.)	62p 3 for £1.80
C120 (120 min.)	87p 3 for £2.55

P. & P. 5p.

All cassettes can be supplied with library cases at 3p. extra each

PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

FULLY TESTED AND MARKED

AC107	15p	OC170	23p
AC126	13p	OC171	23p
AC127	17p	OC200	23p
AC128	13p	OC201	23p
AC176	15p	2G301	13p
AC177	15p	2G303	13p
AF239	87p	2N1302-3	40p
AF158	10p	2N1304-5	25p
AF159	87p	2N1306-7	30p
BC154	25p	2N1308-9	35p
BC171-BC107	13p	2N1389-FET	45p
BC172-BC108	13p	2N3844	25p
BF194	15p	POWER TRANSISTORS	
BF274	15p	OC20	50p
BFY60	20p	OC23	30p
BSY28	87p	OC25	40p
BSY26	13p	OC26	25p
BSY27	13p	OC28	40p
BSY28	13p	OC25	25p
BSY29	13p	OC36	37p
BSA95A	13p	AD149	30p
OC41	13p	AU Y10	£1.25
OC44	13p	2N3065	65p
OC45	13p	2S034	25p
OC71	13p	DIODES	
OC72	13p	AA Y42	10p
OC81	13p	OA81	25p
OC81D	13p	OA79	9p
OC139	13p	OA81	9p
OC140	17p	1N914	7p

FREE! Packs of your own choice up to the value of 50p with orders over £4.

RETURN OF THE UNBEATABLE P.I. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 50 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

P! PLEASE ASK FOR PAK P.I. ONLY 50p
10p P. & P. on this Pak

NEW UNMARKED UNTESTED PAKS

H10	25	Mixed volts 1½ watt Zeners Top Hat type.	50p
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-6 can.	50p
B66	150	High quality Germ. Diodes. Min. glass type.	50p
B83	200	Trans. Makers rejects. NPN/PNP. Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	50p
H15	30	Top Hat Silicon Rectifiers 750 mA. Mixed volts.	50p
B86	50	Sil. Diodes sub. min. 1N914 and 1N916 types.	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied.	50p
B88	50	Sil. Trans. NPN, PNP, equivalent to OC200/L, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes. Mixed voltages.	50p
H20	20	BY126/7 type Silicon Rectifiers 1 amp plastic. Up to 1,000 volts.	50p
H6	40	250mW. Zener Diodes DO-7 min. Glass Type. AV.40% Good.	50p

NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries .3 to .5 volt. .5 to 2 ma.	50p
H8	4	BY127 Silicon Recs. 1000 P.I.V. 1 amp. Plastic. Replaces the BY100	50p
B79	4	1N4007 Sil. Rec. Diodes. 1,000 P.I.V. 1 amp. Plastic.	50p
B81	10	Reed Switches, mixed types, large and small.	50p
B99	200	Mixed Capacitors, Post and packing 13p. Approx. Quantity counted by weight.	50p
H4	250	Mixed Resistors, Post and packing 10p. Approx. Quantity counted by weight.	50p
H7	40	Wirewound Resistors. Mixed Values. Postage 7p.	50p
H9	2	OCF71 Light Sensitive Photo Transistors.	50p
H12	20	NKT155/259 Germ diodes, brand new stock clearance.	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP silicon uncoated tolexan.	50p
H29	20	OA47 gold bonded diodes coded MCS2.	50p

COLOUR T.V. LINE OUTPUT TRANSFORMERS.

Designed to give 25KV when used with HL509 & FY500 valves. As removed from colour receivers at the factory.

ONLY £1 each. Post & Packing 25p

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART.


P.O. RELAYS 8 FOR

Various Contacts and Coil Resistances.
Post & Packaging 25p

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA POSTAGE.

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

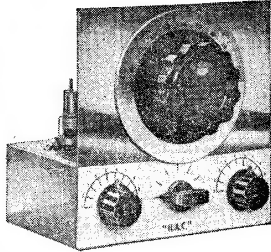

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER

Improved one-valve model "DX" mark 2. Complete kit—price £2.30 (post & packing 20p). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

Est. 1943 **JOHNSONS** Tel: 24864

New! **CV2**—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post paid, direct from makers. S.A.E. for literature.

JOHNSONS (RADIO)
St. Martin's Gate, Worcester
WR1 2DT

KEYNECTOR

The safe quick way to connect electrical equipment to the mains

£2.75 NET TRADE

Send for full details
EB INSTRUMENTS
49-53 PANCRAS ROAD, LONDON NW1
Tel: 01-837 7781

LOOK AT THESE PRICES

CARTRIDGES

Acos GP67-2, GP91-35C £1.12; Acos GP93-1 £1.34; Acos GP94-1 £1.62; Sonotone 9TAHC £1.97; All above in makers cartons; B8R 4XH £1.50.

FS 2500 STEREO AMPLIFIER

5 watts per channel; In attractive Cabinet, P.U. Radio & Tape input Tape output & Speaker outputs Dim. 12½" x 5½" x 3½". Our Price £18.97; SP25 Mk3 £12.87.

PLUGS & SOCKETS

Phono plugs, assorted colours 41p; 45p per doz; Coaxial plugs, aluminium 71p; Coaxial couplers 71p; 2 pin DIN plugs 15p; 3 pin DIN plugs 15p; 5 pin DIN plugs 17p; 2 pin, 3 pin & 5 pin DIN sockets 71p; Wandler plugs 21p; sockets 31p; Banana plugs 51p. Sockets 6p; 3.5mm J/Plugs 71p and 121p; Standard J/Plugs with solder terminals 10p; Chrome 15p; Side Entry J/Plugs black and chrome 24p; Insulated J/sockets—o/cct 16p, c/cct 17p.

ELECTROLYTIC CAPACITORS

4uF 150v 4p; 8uF 500v 15p; 8uF 12v 4p; 8uF + 8uF 450v 21p; 10uF 150v 4p; 12uF 25v 4p; 16uF 450v 14p; 16uF + 16uF 450v 23p; 30uF 10v 4p; 50uF 10v 4p; 100uF 9v 4p; 100uF 12v 4p; 150uF 12v 4p; 220uF 9v 5p; 1500uF 30v 19p; 10uF 15v 71p; 6000uF 25v 50p; 10,000uF 25v 75p; 20,000uF 30v 21.05.

MICROPHONES

Acos Mic 45 £1.12; Acos Mic 60 99p; Planet CM70 £1.50; Hand Mike 75p.


VALVES

FY81 36p; PCL82 39p; EF183 45p; EF184 45p.

PLEASE NOTE CHANGE OF ADDRESS

GEORGE FRANCIS (Dept PW),

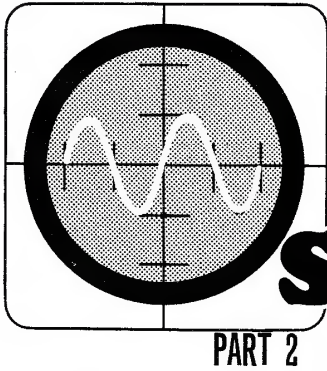12-14, Middle Gate, Newark, Notts.
Telephone: Newark 4733.



PW WORKSHOP scilloscope

THE circuit and other technical details of the P.W. oscilloscope were given in part 1. The prototype, as shown in the photographs, was constructed in a Mod-Contil case type Q which has overall dimensions of 13×9×7in. Any case of similar size could be used but the layout of the components should follow that given as closely as possible. Details for the front panel drilling are given in Fig. 2 and these apply of course to the panel of the Mod-Contil type Q case. The general assembly of the two end panels and the chassis and the positions of the c.r.t., the component tagboards and mains transformer are shown in Fig. 3. This layout is important even if a different case is used. The transformer T1 must be situated below and to the rear of the c.r.t. and as close to the end of the chassis as possible as shown in Fig. 4.

SUB-ASSEMBLIES

These include the main tagboard mounting screen, the panel for the c.r.t. base and the panels for the focus and brilliance controls and the X amplifier gain control. Details for the main tagboard mounting screen are given in Fig. 5 and on this are fitted the miniature tagboards as shown in Fig. 3 with insulating material beneath them to prevent short circuits. The panel and clamp material for the c.r.t. base are shown in Fig. 6 but note the slotted holes in the panel to allow the height of the c.r.t. to be adjusted relative to the front panel. The c.r.t. holder is not mounted on this panel but simply pushed on to the c.r.t. connecting pins.

Details for the focus (VR9) and brilliance (VR8) controls panel are given in Fig. 7b. The panel may be made from perspex or paxolin, 1/8in. thick. Both controls are at high potential with respect to chassis and for this reason must not only be mounted on a panel of insulating material but must also be coupled to the front panel control knobs via insulating spindle

couplers as shown in the photo. The remaining panel is that for the X amplifier gain control VR1 as shown in Fig. 7c and which is secured to the side of the chassis as in Fig. 7a. The spindle of this control must be cut very short (to about 1/8in.) and slotted as shown as adjustment is made, when required, by screw-driver. To facilitate this a hole is cut in the side panel exactly in line with the control i.e., on the right when facing the front panel.

The three small tagboards E, F and G are located


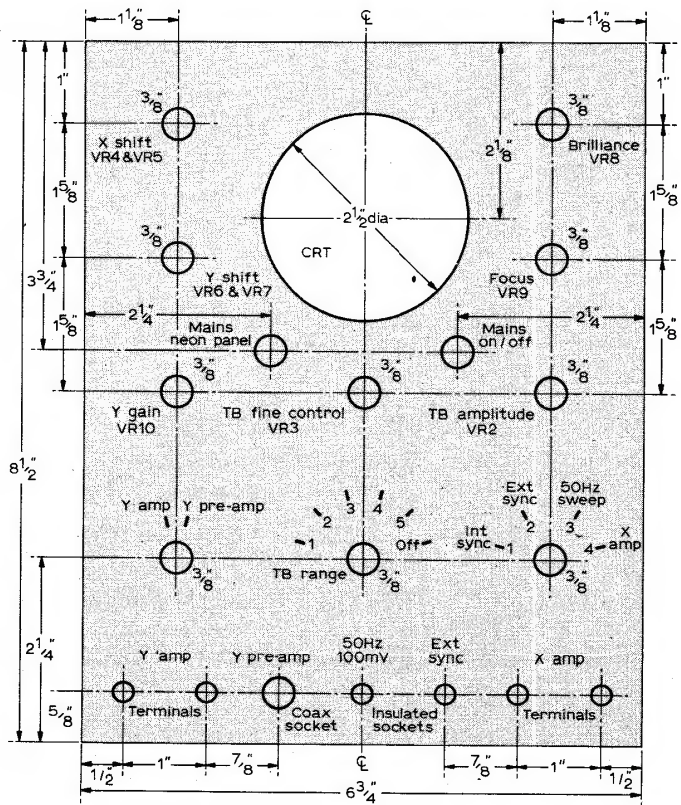


Fig. 2: The drilling of the front panel and location of the controls.

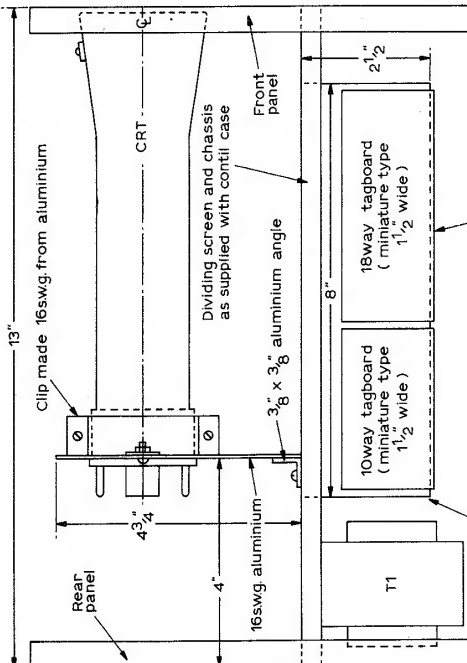

Centre dividing screen 16swg aluminium mounted on 3/8 x 3/8 aluminium angle

Tagboards each side of screen mounted with insulating material between tagboard and screen


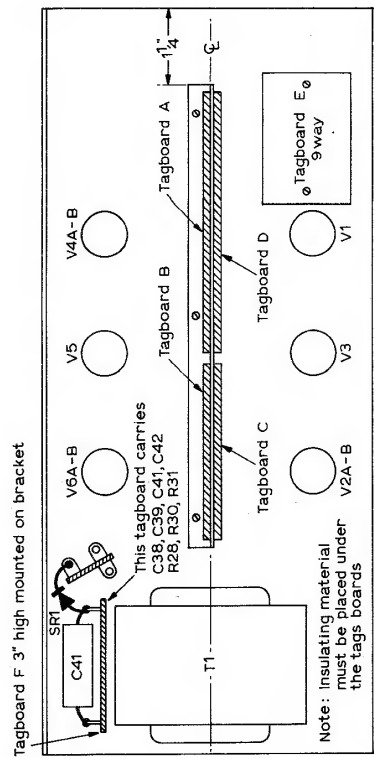
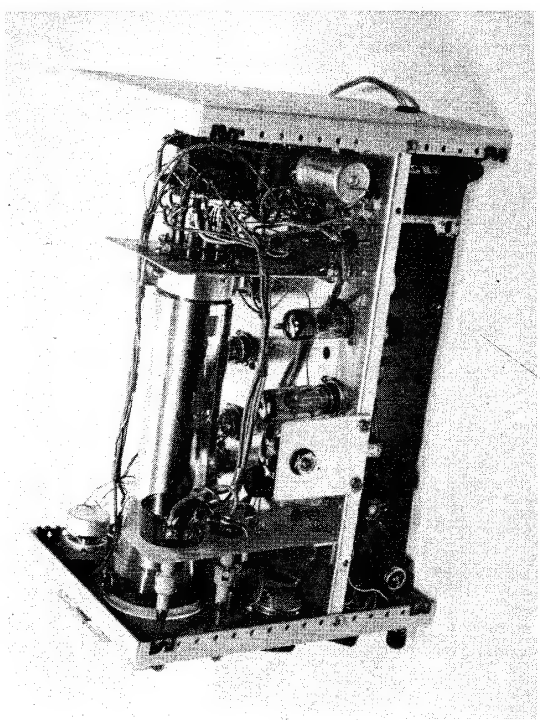


Fig. 3 (left): General assembly and layout using the specified case.

Fig. 4 (above): Location of the mains transformer, the centre screen and the tagboards.

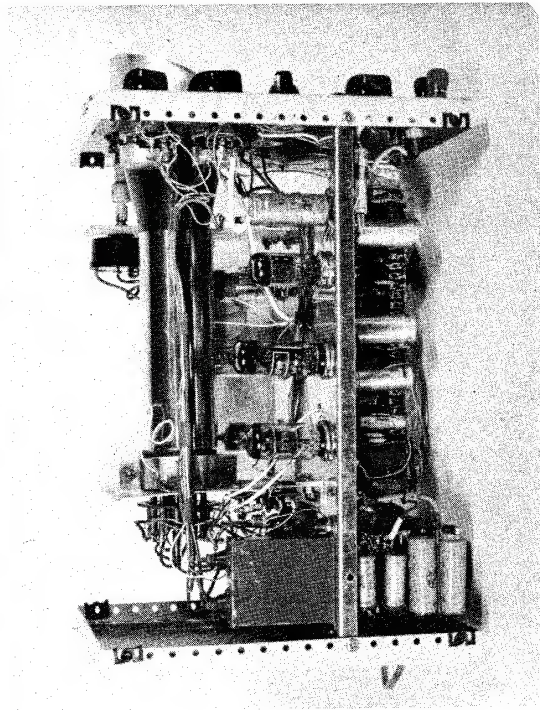General views of the P.W. Workshop Oscilloscope are shown below and these should be used in conjunction with the various drawings to site the main components.



HOW TO TELL A STEREO SYSTEM THAT LOOKS GOOD FROM A STEREO SYSTEM THAT SOUNDS GOOD--BEFORE YOU PART WITH YOUR MONEY.


There's only one way to buy stereo equipment. Listen to it. Lots of it. Until you find the sound you like for the money you've got.

Sound advice. But try acting on it in 99% of hi-fi dealers and you'll be asked to show the colour of your money. We at Roc think that's unfair. So we fitted out our store in the Edgware Road with a series of sound systems, so you can hear all the stereo you want until you find the equipment you like. With no hustling.

But if you're one of those poor unfortunates who cannot make it in person, we'll sell you a system by mail. We've got the best range in town from single speakers to complete stereo set-ups.

Here are just six of the systems we've got in stock.

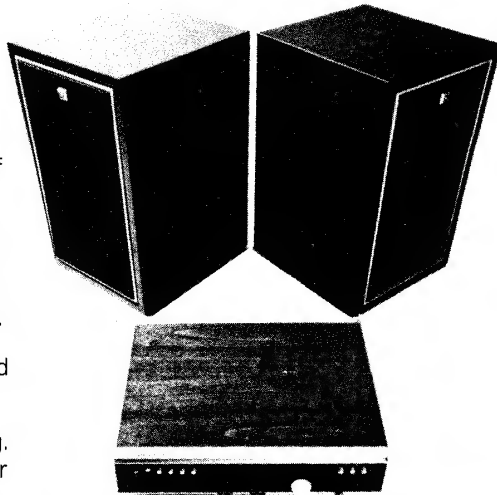Fill in the coupon and we'll have our systems brochure back to you by return.



Name _____

Address _____



ROC ELECTRONICS LIMITED
 193 EDGWARE ROAD LONDON W2 1ET
 TELEPHONE: 01-723 6211

	Amplifier Output per channel	Speaker Capacity	Turntable	Price
System I.	4 Watts	6 Watts	Garrard 2025TC	£39.90
System II.	8 Watts	10 Watts	As system I.	£49.90
System III.	15 Watts	As System II	IIIA Garrard 2025TC	£59.90
			IIIB Garrard SP.25 MK III	£69.90
System IV.	20 Watts	20 Watts	Garrard SP.25 MKIII	£79.90
System V	18 Watts	20 Watts	As System IV	£115.00
System VI.	30 Watts	30 Watts	Thorens TD150AB	£182.00

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- Radio Operator Certs
- General Certificate of Education, etc.

Now available Colour T.V. Servicing Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Stewarts Road, London, S.W.8.
Please send me the ICS prospectus—free and without obligation.
(state Subject or Exam).....

NAME (BLOCK CAPITALS PLEASE).....

ADDRESS.....

AGE.....OCCUPATION..... 5/71

INTERNATIONAL CORRESPONDENCE SCHOOLS

ELECTROVALUE

SEMI-CONDUCTOR BARGAINS

ALL BRAND NEW AND TO SPEC. NO 'SECONDS'

All power types supplied with free insulation sets.

40361	55p	AFI14	30p
40362	68p	AFI15	30p
2N696	20p	AFI17	28p
2N697	22p	AFI24	30p
2N706	12p	AFI27	28p
2N930	29p	AFI39	48p
2N1131	36p	AF239	49p
2N1132	40p	ASY26	27p
2N1302	19p	ASY28	27p
2N1303	19p	BC107	14p
2N1304	23p	BC108	12p
2N1305	23p	BC109	14p
2N1307	33p	BC125	33p
2N1308	36p	BC126	22p
2N1309	36p	BC147	15p
2N1613	23p	BC148	14p
2N1711	26p	BC149	15p
2N1993	34p	BC153	28p
2N2147	95p	BC154	28p
2N2218	34p	BC157	19p
2N2218A	43p	BC158	17p
2N2219	38p	BC159	18p
2N2219A	33p	BC167	17p
2N2270	62p	BC168	11p
2N2369A	19p	BC169	13p
2N2483	35p	BC177	17p
2N2484	42p	BC178	15p
2N2646	54p	BC179	17p
2N2904A	42p	BC182L	13p
2N2905	44p	BC183L	11p
2N2905A	47p	BC184L	13p
2N2924	20p	BC212L	25p
2N2925	22p	BC213L	25p
2N2926	11p	BC214L	25p
2N3053	27p	BCY70	19p
2N3055	75p	BCY71	33p
2N3702	13p	BCY72	15p
2N3703	13p	BF115	23p
2N3704	13p	BF167	27p
2N3705	13p	BF173	31p
2N3706	13p	BF194	17p
2N3707	13p	BF195	18p
2N3708	13p	BFX29	31p
2N3709	13p	BFX84	25p
2N3710	13p	BFX85	34p
2N3711	13p	BFX87	29p
2N3819	35p	BFX88	26p
2N3904	20p	BFY50	23p
2N3906	35p	BFY51	20p
2N4058	20p	BFY52	23p
2N4059	20p	BSX20	16p
2N4060	20p	C407	17p
2N4061	20p	MC140	25p
2N4062	20p	MP56531	35p
2N4124	18p	MP56534	30p
2N4126	27p	NKT211	25p
2N4284	15p	NKT212	25p
2N4286	15p	NKT214	23p
2N4289	15p	NKT274	18p
2N4291	15p	NKT403	65p
2N4292	15p	NKT405	79p
AC107	46p	OC71	29p
AC125	20p	OC81	25p
AC127	20p	OC81D	25p
AC128	20p	ZTX300	17p
AC153K	25p	ZTX301	12p
AC176	27p	ZTX302	16p
ACY20	20p	ZTX303	22p
ACY22	16p	ZTX304	27p
AD140	50p	ZTX500	18p
AD142	50p	ZTX501	21p
AD149	60p	ZTX502	25p
AD161	40p	ZTX503	22p
AD162	40p	ZTX504	52p

Appointed distributors and stockist for **SIEMENS (U.K.) LTD., NEWMARKET TRANSISTORS LTD., E. GRINSTEAD ELECTRONIC COMPONENTS LTD.**

COMPONENT DISCOUNTS. 10% on orders for components for £5 or more; 15% on orders for components £10 or more. (No discount on nett items.)
POSTAGE & PACKING. Free on orders over £2.00: Please add 10p if under: Overseas orders, carriage charged at cost.

ELECTROVALUE

Dept. PW.571, 28 ST. JUDES RD., ENGLEFIELD GREEN, EGHAM, SURREY. Phone Egham 5533 Telex 264475

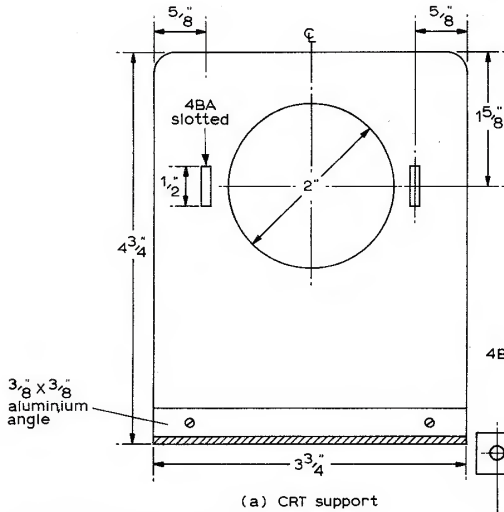


Fig. 6: The c.r.t. mounting panel and base clamp.

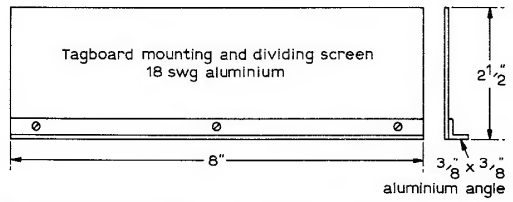


Fig. 5: The chassis dividing screen which is also used for mounting tagboards A, B, C and D.

as shown in Figs. 4 and 7 respectively. Tagboard F is mounted on a piece of 3/8 in. aluminium angle and located at the side of the mains transformer T1 (see Fig. 4). This tagboard carries the capacitors C38, C39, C41 and C42 which are fairly large so the board should be 2 in. wide and have at least 6 pairs of tags. Tagboards E and G are mounted on the chassis with spacers or insulating material underneath so that the tag eyelets do not touch the chassis. These boards may be miniature (1 1/2 in. wide), each with 10 pairs of tags. The location of the valveholders and other chassis mounted components such as C34, C35, C36 and C40, etc., are shown in Fig. 7.

CONSTRUCTION AND WIRING

These photos show the construction and layout as seen from both sides and above and below the chassis (see also photos in Part 1). The c.r.t. is mounted so that the final anode cap is uppermost as shown in Fig. 8. This will bring the 'key' on the c.r.t. base to the vertical position and ensure that the trace is horizontal when displayed. Fig. 8 also shows the c.r.t. connections. The lead to the final anode cap can be directly soldered to the projecting pin.

The layout for the Y amplifier, the timebase and the X amplifier tagboards is shown in Figs. 9 and 10 respectively. The tagboard pairs A and B, and C and D should each be regarded as one long

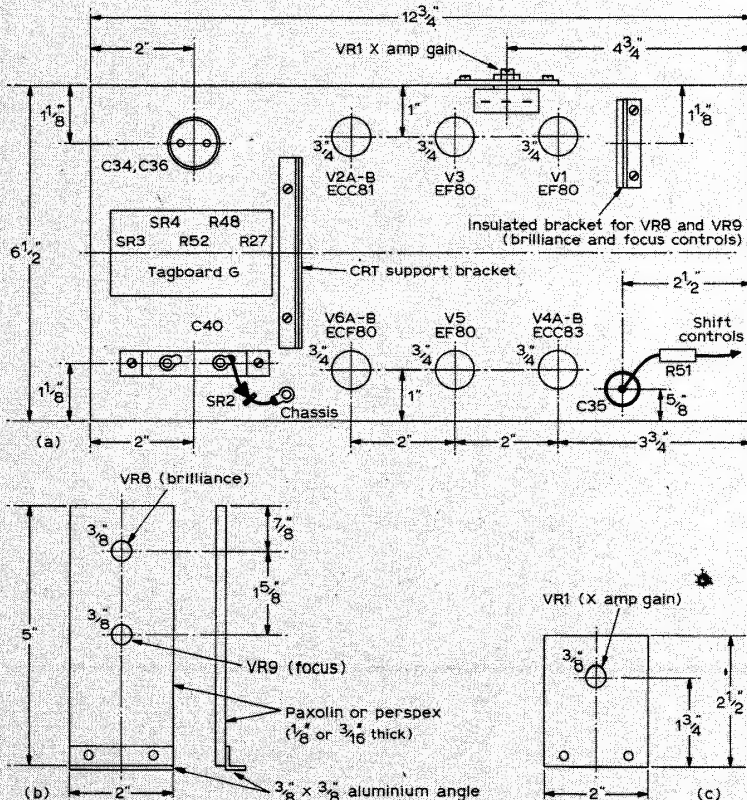


Fig. 7: Layout of the valve holders and other chassis mounted components and details for the brilliance and focus panel and the X amp gain control bracket.

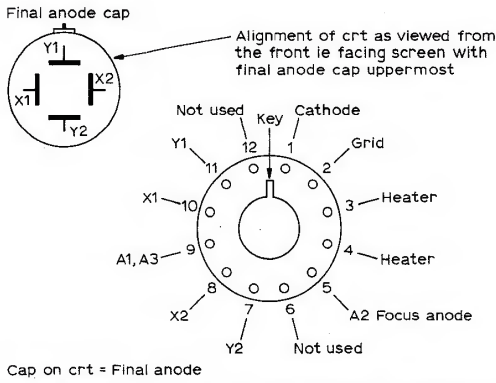


Fig. 8: C.R.T. base connections. Inset shows X and Y plate alignment in relationship to the final anode cap.

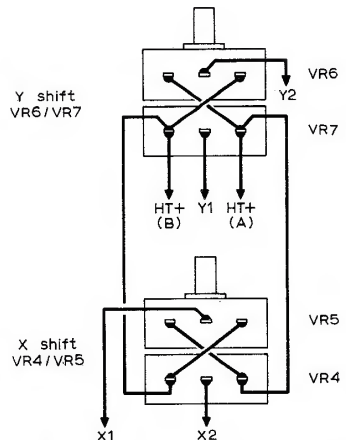


Fig. 11: Wiring of the X and Y shift controls.

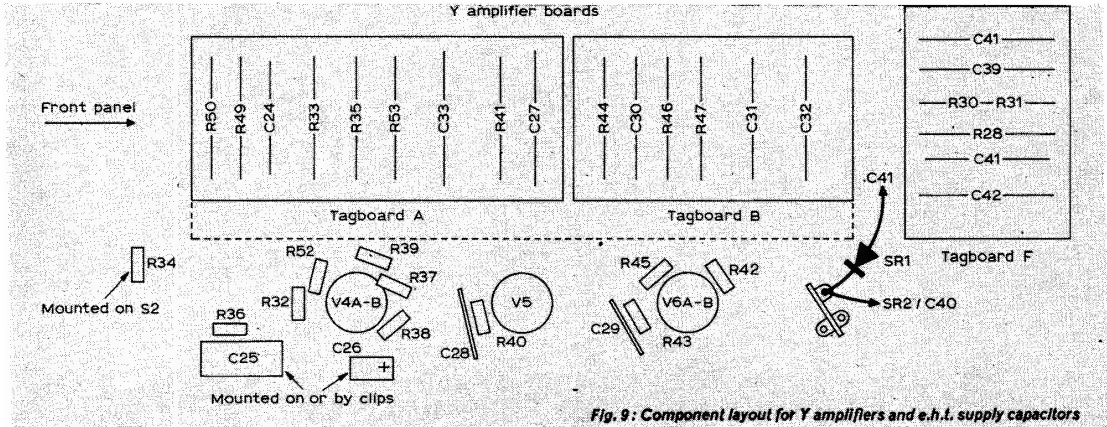


Fig. 9: Component layout for Y amplifiers and e.h.t. supply capacitors

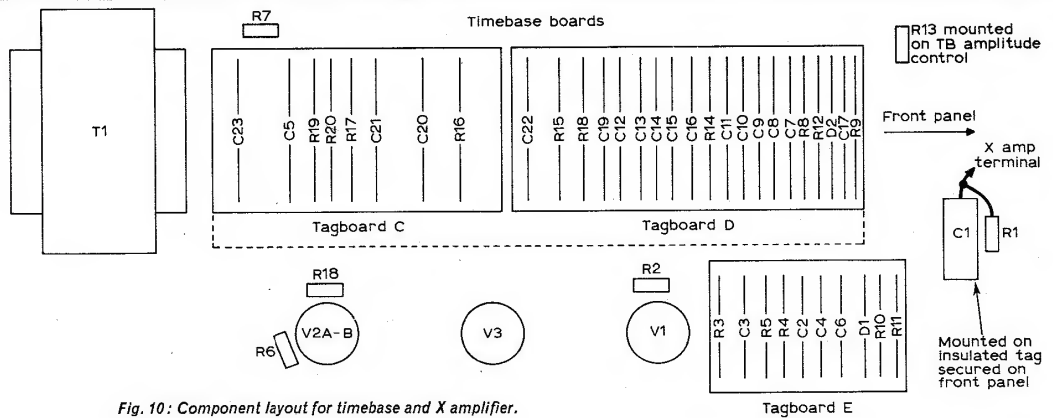


Fig. 10: Component layout for timebase and X amplifier.

board and the components spread out, each accordingly to the space required. For this reason some pairs of tags will not be used but there will be more than enough for all the components. Much the same applies to tagboards E and G. The wiring for the X and Y shift controls is given in Fig. 11. Clockwise

movement of the X shift control moves the c.r.t. trace upwards, and clockwise movement of the Y shift control moves the trace to the right and vice versa in both cases.

The only rule as far as wiring is concerned is to keep all wires short as possible and do not take wires

Build yourself a



great name HEATHKIT


You too can join the millions of satisfied Heathkit builders who have discovered the easy way to build better products than they could buy . . . have fun . . . and enjoy substantial savings in the process. Heathkit models are the beginner as well as the experienced man's first choice. Everything you need right down to the last nut and bolt is included in every kit. The wonderful step-by-step assembly manual is the last word in clarity. Want to know more . . . your first step is to send for the Free Heathkit catalogue and discover the unique satisfaction you can get from building the best.




SWL



HI-FI

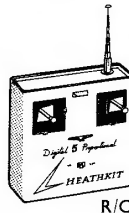

R/C

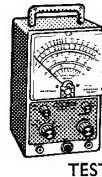

TEST



HOW TO BUY YOUR HEATHKIT

Orders for mail order dispatch from the factory may be placed at the London or Birmingham Heathkit Centres or by post to the Gloucester factory. Such orders are at 'direct-from-factory' prices which are lower than retail prices.

Goods may be purchased at the Heathkit Centres at retail prices.

Goods may be purchased at the Gloucester factory Showroom at 'direct-from-factory' prices.

London Heathkit Centre, 233 Tottenham Court Road.
Open Monday to Saturday 9 a.m. — 6 p.m. Phone 01-636 7349.

Birmingham Heathkit Centre, 17-18 St. Martin's House, Bull Ring.
Open Tuesday to Saturday 9 a.m. — 6 p.m. Phone 021-643 4386.

Gloucester factory Showroom, Bristol Road, Gloucester.
Open Monday to Saturday 9 a.m. — 5 p.m.

Please send me FREE Catalogue

NAME

ADDRESS

51/5/71



HEATH (GLOUCESTER) LTD.
GLOUCESTER GL2 6EE

PICKS UP AIRCRAFT TRANSMISSIONS (control to aircraft, etc.), SHIPS AT SEA, POP PIRATES, TAXIS, AMBULANCES, LOCAL RADIO STATIONS, CONTINENTAL STATIONS, ALL BBC, VHF & MANY, MANY MORE, including fascinating public service transmissions that we are not allowed to mention! A miracle of advanced technology! You get far, far more than an ordinary radio! An instrument that will bring a new dimension to your world of sound! Frequency range: MW 540-1600 KHz, FM 88-108 MHz, Air 108-136 MHz, Intermediate Frequency: MW 455 KHz, FM 10.7 MHz, Air 10.7 MHz. **18 SEMI-CONDUCTORS:** Transistors 11, Diodes 8 + Thermister! Automatic frequency control "locks-in", eliminating drift. Pinpoint station selection! Built-in adjustable 8-section 31" telescopic aerial. Lowest price ever! Tremendously strong leather-grained case with carry handle, 10 1/2" x 6 1/2" x 4" overall approx. Written guarantee. Only £11-97p., carr. etc., 38p.—with FREE pair of "aircraft spotter" high power "bino-scope" binoculars with built-in filters for viewing in strong sunlight & independent left & right eye focus. Send or call. *Compare it with sets costing £40 or more. Refund if not delighted. **BONUS OFFER:** Shoulder strap, earphone for personal listening & batteries, all for 25p extra, if required.

WHY PAY £40 OR MORE?
COMPLETE PORTABLE HIGH FIDELITY COMMUNICATIONS & RADIO RECEIVER
PLUS SPECIAL AIRCRAFT WAVEBAND!
OUR PRICE £11-97p. POST ETC. 38p.
FREE TO EVERY PURCHASER AIRCRAFT SPOTTER HIGH POWER "BINO-SCOPE" BINOCULARS

STOP PRESS!
You can still order "By Post" THIS WAY:—
 Whether you have a bank account or not—GO TO ANY BANK (Barclays if possible) obtain a **BANK GIRO FORM**—pay in the amount to cover your order (including carriage, etc.) write full name and address and details of your order on reverse side of Giro Form. Address your completed **GIRO PAYMENT/ORDER** to: **SHOPERTUNITIES LTD.** (WP/5) **G/O BARCLAYS BANK LTD.**, Code No. 20-13-91, **BRITISH MUSEUM BRANCH, LONDON, W.C.1** and hand to bank cashier. We'll arrange immediate despatch by carrier. This system of payment can always be used in the future (or for past ads.) if you wish.

SHOPERTUNITIES LTD. S/L Dept. WP/5, 164 UXBRIDGE ROAD, (facing Shepherd's Bush Green), LONDON, W12 8AQ (Thurs. 1, Fri. 7). Also 37 High Holborn, London, W.C.1 (Wed. 1, Thurs. 7). Both stores open from **MONDAY-SATURDAY 9-6.**

ONLY FROM US! FIRST SHIPMENT JUST ARRIVED!
BRAND NEW 1971 Model! RUSSIAN WORLD BEATER!
6 WAVEBAND 10 TRANSISTOR PORTABLE RADIO
WORLD WIDE RECEPTION £9-97p.
 THOUSANDS OF TRANSMISSIONS. AND STATIONS THE WORLD OVER!
NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!
THE LATEST 1971 MODEL. SUPERSEDING ALL PREVIOUS MODELS!—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO. DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"!! It's far better than any 6-wave radio even they have produced! Finest value we've ever offered! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of 234 radios! * Instant refund if you are astounded! Pure and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection. Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE! Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover world! Unique side control waveband. Unique aerial gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even ships at sea and messages from all over world—nothing is secret! The radio enthusiast has the world in his hand! Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume and Treble Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33 1/2" length. It's also a fabulous **CAR RADIO—any speed, requires no additional aerial. **UNIQUE** elegant black, white and Chrome finish case. **SIZE 10 1/2" x 8" x 3 1/2"** overall approx. Magnificently designed, made to give years of perfect service. **WITH WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST ETC. 43p.** Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.**

***COMPARE ITS PERFORMANCE WITH £34 RADIOS!**

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS** (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: **British National Radio School, Reading, Berks.**
 Please send **FREE BROCHURE** to

NAME Block
 ADDRESS Caps.
 Please
 5/71

BRITISH NATIONAL RADIO SCHOOL

M. & B. COMPONENTS (LEEDS) LTD.

(INCORPORATING M. & B. RADIO)
 38 BRIDGE END, LEEDS 1 Telephone 0532-35649

GEIGER COUNTERS
 Well-known contamination meter comprised of main unit fitted with meter marked in 'Milli Rontgens/Hour', probe, lead and carrying case. A very sensitive set which will give a good reading from most pocket watches. Very low battery consumption. Audio output available from socket on front panel. Supplied in new or as new condition.

Model 1. Supplied with internal vibrator power supply unit, enabling set to work from 4 pen cell batteries £4-47½ plus 37½p. p.p.
 Model 2. Requires 2 HT batteries (not included) £3-75 plus 37½p. p.p.

TRANSISTOR INVERTERS. Both models are brand new.
 Model 1. 12 vdc input 270 vdc at 150mA approx. output. £3-25 plus 20p p.p.
 Model 2. 12 vdc input 330 vdc at 330mA approx output. £5-75 plus 25p p.p.

VHF RECEIVER UNIT TYPE R1933A. 18 miniature valve vhf receiver ideal for 2 metres, 4 metres or aircraft band. Requires p.s.u. and oscillator. £2-25 plus 30p p.p.

ELECTRO MAGNETIC COUNTERS. 4 digit GPO type counters. Used but tested. Six for £1-30 plus 20p p.p.

DESK TELEPHONES. GPO type desk telephones complete with dials. Used but tested. Two for £1-62½ plus 37½p. p.p. Four for £3-00 plus 50p p.p.

MB2/20A 2 METER TRANCEIVER. Ideal for mobile, portable or fixed station use. Operating directly from a 12VDC supply. Fitted with a press to talk microphone. Crystal controlled tx using 4 valves in the RF stages giving 20WRF output. With a fully transistorized modulator giving high level amplitude modulation. Receiver uses 7 valves and 20 transistors in a double conversion superhet circuit with tune able front-end using a transistorized tuneable OSC. 12 vdc transistor inverter drawing 2/9 amps on RX 4. 15 amps on S/bye and 8 amps on transmit full power. Write for full details.

We also have in stock many other items of general interest. Please send s.a.e. for our latest lists.


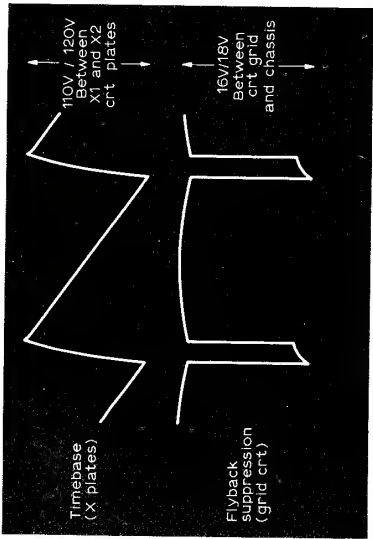


Fig. 12: Timebase and flyback suppression waveforms.

Fig. 13: The perspex graticule for the c.r.t. screen.

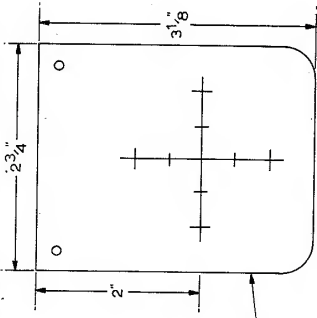

Material
1/8" thick perspex



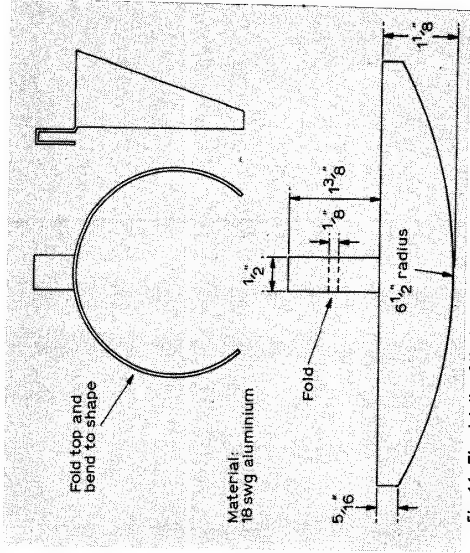


Fig. 14: The details of the hood for the c.r.t.

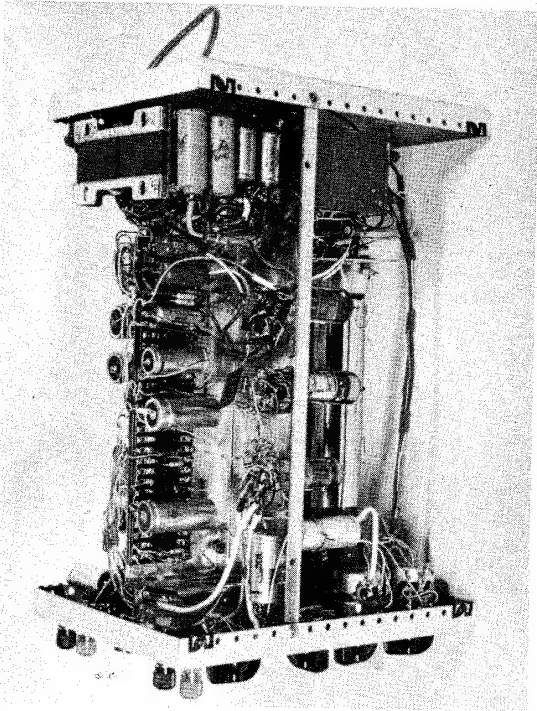

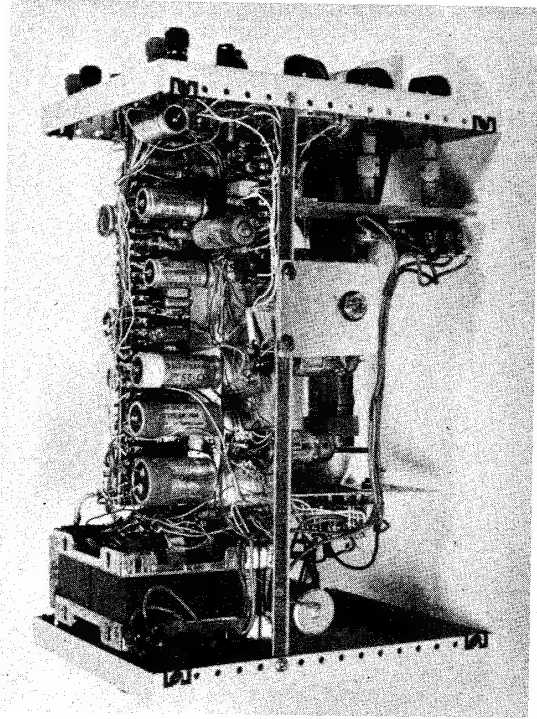Two views of the underside of the completed Oscilloscope are shown below.



associated with the timebase and its controls too close to the Y amplifier wiring, that is try to keep the timebase and Y amplifier wiring to the respective sides of the centre screen.

TESTING AND PERFORMANCE

It is most important that the various potentials as shown on the circuit are obtained but note that the voltmeter used must be at least 20,000 ohms per volt, otherwise the readings obtained will be inaccurate. The measured potentials should be within 3% of those listed. (Example—for a reading of 600V the measured potential should be not less than 580V and not more than 620V.)

If another oscilloscope is available the timebase waveforms and flyback suppression pulse can be checked quite easily and should appear as in Fig. 12. Failing this, set the timebase range switch to position 1 and the fine control to about midway travel. Set the timebase amplitude control to about one third travel and the X and Y shift controls to midway. Set the Y amplitude control to zero. Adjust brilliance and focus to obtain a bright but sharp trace which should be extended fully across the screen. Check that it remains fully extended on all timebase switch positions. Now turn the timebase switch to the 'off' position in which case only the c.r.t. spot should be displayed and this should be completely round and about 1mm. in diameter. Reduce brilliance a little for this test. Check that the spot can be centred on the c.r.t. screen by means of the X and Y shift controls the setting for these being almost exactly mid-range.

With either control it should be possible to move the spot up or down, or from left to right, completely off the screen. With the timebase range switch still at the 'off' position turn the sync switch (S1 AB) to position 3, 50Hz sweep. The trace displayed should be about 1.5cm. long.

The Y amplifiers can be checked next by first setting the timebase range to position 1 and the fine control to approximately half-way. Connect the 100mV 50Hz calibration signal to the 'live' Y amplifier terminal and make sure the Y amplifier switch is to 'Y amp' and not 'Y pre-amp'. With the Y gain control at almost maximum the 50Hz sine-wave displayed should be about 2cm. peak-to-peak and there should be at least 3 or 4 complete cycles. Now switch to 'Y pre-amp' and connect the 50Hz calibration signal to the co-axial Y input and set the Y gain to $\frac{1}{10}$ th of its travel. The 50Hz sine-wave displayed should again be about 2cm. peak-to-peak. Turn the Y gain a little higher so that the peaks of the test signal extend to the top and bottom of the screen. At this point the sine-wave should show no sign of clipping.

Further tests which include timebase synchronization, and the X amplifier gain etc., require the use of an audio signal generator. For the X amplifier test set the sync switch (S1 AB) to 'X amp' and turn the X amp pre-set gain control fully clockwise. Set the timebase range switch to 'off'. With a sine-wave signal of 1.5V r.m.s. to the X amp input the trace should deflect vertically to approximately 4cm. long.

Return the timebase range switch to position 2 or 3 and then set the sync switch to 'internal sync'. Inject a 1000Hz sine-wave of approximately 500mV to the 'Y amp' input and adjust the Y gain for a 4cm. display. Adjust the timebase fine control until the trace locks. Now run through the rest of the timebase

ranges using input signals of appropriate frequency to ensure that each range is functioning and that synchronization can be obtained on each.

The screen graticule on the prototype was made from $\frac{1}{8}$ in. thick perspex to the size shown in Fig. 13. The calibration marks were as shown, in centimetres and were produced by scoring the perspex on the side facing the c.r.t. screen. The scored lines and marks were filled with Chinagraph (soft wax pencil). The graticule can be fixed over the screen by two screws at the top which go into the front panel but with spacers on them to keep the graticule just off the tube face.

The c.r.t. hood can be made from 18s.w.g. aluminium as shown in Fig. 14. The tab at the top is folded as shown and this holds the hood on to the top of the graticule. The hood can be painted matt black inside if desired.


In the main circuit of the oscilloscope on page 1009 of the April issue the secondary of the mains transformer was marked 250-0-250V. This should have read 350-0-350V and is as the components list which gave it correctly.

P.W. SOUND EFFECTS SYNTHESISER

continued from page 58

could be tested separately with a 24V battery supply and the output coupled to an amplifier for aural checks. The output signal level from each generator is over 100mV. This is the best way of ensuring that each circuit is operating properly and producing the right sound and may well save time and trouble when the final assembly stage is reached.

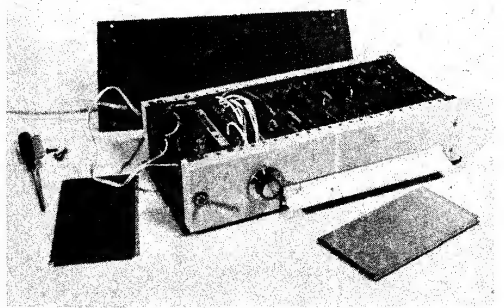The amplifier and loudspeaker used with the completed synthesiser should be capable of good quality reproduction and have a fairly wide frequency range. The power output will depend on how loud the sounds are to be produced but should be comparable with the power output of the organ. A minimum of 10W



The completed synthesiser with the bottom and side panels removed. The power supply can be seen on the left.

might be suitable for the majority of domestic electronic organs. It may be possible, of course, to couple the unit directly to the organ main amplifier but care should be taken with regard to required signal level and impedance matching.

A little gremlin seems to have been at work regarding the castanets circuit on page 914 of the March issue. C1 and C2 should be 0.2 μ F and not 0.02 μ F as given. In the text of the same section near the middle should read "The waveform from Tr1 and Tr2 is applied to the base circuit of Tr3 . . ." and not "emitter circuit."

BRAND NEW GUARANTEED

SEMICONDUCTORS & COMPONENTS

RETURN OF POST SERVICE

SOLE AGENTS FOR CONDUCTORS SYSTEMS DEVICES INC., (USA), IN U.K.

TRANSISTORS

2G301	20p	2N3403	22p	40309	32p	BC183	12p	B8X26	45p	NKT274	20p
2G302	20p	2N3404	32p	40310	45p	BC194	15p	B8X27	47p	NKT275	20p
2G303	20p	2N3405	45p	40311	35p	BC212L	12p	B8X28	32p	NKT281	27p
2G306	42p	2N3414	12p	40312	45p	BC230	27p	B8X30	82p	NKT401	87p
2G308	30p	2N3415	22p	40314	37p	BCY31	27p	B8X61	62p	NKT402	82p
2G309	30p	2N3416	37p	40320	47p	BCY32	37p	B8X76	32p	NKT403	75p
2G371	12p	2N3417	37p	40323	32p	BCY33	20p	B8X77	27p	NKT404	62p
2G374	20p	2N3750	21p	40324	47p	BCY34	22p	B8X78	27p	NKT405	75p
2G381	22p	2N3872	17p	40326	37p	BCY38	22p	BSY10	27p	NKT406	62p
2N404	22p	2N3605	27p	40329	30p	BCY39	52p	BSY11	27p	NKT451	62p
2N696	20p	2N3606	27p	40344	27p	BCY40	37p	BSY24	15p	NKT452	68p
2N697	35p	2N3607	22p	40347	57p	BCY42	15p	BSY25	15p	NKT453	47p
2N698	20p	2N3702	12p	40348	58p	BCY43	15p	BSY26	17p	NKT454	82p
2N706	12p	2N3703	12p	40360	42p	BCY54	32p	BSY27	17p	NKT613F	32p
2N706A	12p	2N3704	17p	40361	47p	BCY58	22p	BSY28	17p	NKT674F	30p
2N708	15p	2N3705	15p	40362	57p	BCY59	22p	BSY29	17p	NKT677F	30p
2N709	62p	2N3706	12p	40370	32p	BCY60	97p	BSY32	25p	NKT7713	20p
2N718	25p	2N3707	15p	40406	57p	BCY70	20p	BSY36	25p	NKT781	30p
2N726	30p	2N3708	08p	40407	40p	BCY71	42p	BSY37	35p	NKT1049	30p
2N727	30p	2N3709	10p	40408	52p	BCY72	17p	BSY38	22p	NKT1049S	30p
2N914	17p	2N3710	11p	40410	62p	BCZ10	27p	BSY39	22p		37p
2N916	17p	2N3711	12p	40410A	62p	BCZ11	27p	BSY40	22p	NKT10619	30p
2N918	30p	2N3715	22-25p	40408A	35p	BD116	11-12p	BSY51	32p		32p
2N920	22p	2N3716	22-30	40600	67p	BD121	65p	BSY92	32p	NKT20829	20p
2N930	27p	2N3791	22-75	AC 107	36p	BD123	82-85p	BSY53	37p		47p
2N1090	22p	2N3819	35p	AC126	30p	BD124	60p	BSY54	40p	NKT20839	30p
2N1091	22p	2N3823	37p	AC127	35p	BD131	87p	BSY56	30p		37p
2N1121	25p	2N3824	47p	AC128	20p	BD132	87p	BSY58	47p	NKT80111	37p
2N1132	25p	2N3854A	27p	AC154	22p	BDY10	11-87p	BSY79	45p		77p
2N1302	17p	2N3855	27p	AC176	25p	BDY11	11-62p	BSY82	52p	NKT80112	30p
2N1303	17p	2N3856	30p	AC177	25p	BDY12	11-62p	BSY86	52p		37p
2N1304	22p	2N3856	30p	AC188	37p	BDY15	11-75p	BSY95A	18p	NKT80113	18p
2N1305	22p	2N3856A	35p	AC177	27p	BDY19	11-97p	BSW41	42p		42p
2N1306	25p	2N3858	22p	AC178	25p	BDY20	11-12p	BSW70	27p	NKT80111	32p
2N1307	25p	2N3858A	30p	AC179	25p	BDY38	97p	C424	27p	NKT80212	30p
2N1308	30p	2N3859	27p	AC192	25p	BDY60	11-25	C424	27p	NKT80212	30p
2N1309	30p	2N3859A	32p	AC191	25p	BDY61	11-25	C425	55p		62p
2N1507	17p	2N3860	30p	AC222	30p	BDY92	11-00	C426	40p	NKT80213	30p
2N1613	20p	2N3866	21p	AC228	25p	BF115	25p	C428	37p		37p
2N1631	25p	2N3877	40p	ACY40	20p	BF117	47p	C744	30p	NKT80214	30p
2N1632	30p	2N3877A	40p	ACY41	25p	BF163	37p	D16P1	37p		32p
2N1637	30p	2N3904	37p	AD127	40p	BF167	45p	D16P2	37p	NKT80215	30p
2N1638	27p	2N3904A	40p	AD140	52p	BF173	33p	D16P3	37p		32p
2N1639	27p	2N3901	37p	AD149	57p	BF177	32p	D16P4	37p	NKT80216	30p
2N1711	25p	2N3903	35p	AD160	62p	BF178	52p	GET109	30p		62p
2N1859	32p	2N3904	37p	AD161	72p	BF181	20p	GET11	30p	OC20	30p
2N1893	37p	2N3905	37p	AD162	37p	BF180	35p	GET114	20p	OC22	50p
2N2147	82p	2N3906	37p	AF106	42p	BF181	32p	GET118	20p	OC23	50p
2N2148	57p	2N3908	17p	AF114	25p	BF184	35p	GET119	20p	OC24	50p
2N2159	57p	2N3908A	30p	AF115	30p	BF185	42p	GET120	20p	OC25	50p
2N2193	40p	2N4060	12p	AF116	25p	BF194	17p	GET873	12p	OC26	27p
2N2193A	42p	2N4061	12p	AF117	25p	BF195	20p	GET880	30p	OC28	28p
2N2194	30p	2N4062	12p	AF118	62p	BF196	42p	GET887	20p	OC29	62p
2N2217	27p	2N4063	12p	AF119	30p	BF197	20p	GET891	20p	OC30	62p
2N2219	32p	2N4285	17p	AF124	22p	BF198	42p	GET890	22p	OC36	62p
2N2219	32p	2N4286	17p	AF125	30p	BP200	52p	GET896	22p	OC41	22p
2N2220	32p	2N4287	17p	AF126	30p	BP201	52p	GET897	22p	OC42	22p
2N2221	32p	2N4288	17p	AF127	17p	BP225	20p	GET898	22p	OC44	20p
2N2222	30p	2N4289	17p	AF129	37p	BP227	22p	MJ400	11-07p	OC45	12p
2N2287	11-07p	2N4290	17p	AF178	47p	BP228	22p	MJ420	11-07p	OC46	12p
2N2297	30p	2N4292	12p	AF180	52p	BP229	22p	MJ421	11-12p	OC70	15p
2N2368	17p	2N4303	47p	AF181	42p	BPW11	47p	MJ430	11-02p	OC71	12p
2N2369	17p	2N5027	62p	AF229	42p	BPX13	22p	MJ480	97p	OC74	32p
2N2369A	17p	2N5028	62p	AF230	42p	BPX15	22p	MJ481	97p	OC75	32p
2N2410	42p	2N5029	47p	AF280	62p	BPX30	30p	MJ490	11-00	OC76	22p
2N2483	27p	2N5030	42p	AF211	32p	BPX42	37p	MJ491	11-37p	OC77	30p
2N2484	32p	2N5172	12p	AF212	35p	BPX44	37p	MJ1806	22-17p	OC81	30p
2N2489	22p	2N5174	62p	AFY27	37p	BPY28	37p	MJ240	11-02p	OC81D	22p
2N2540	22p	2N5175	52p	AFY28	27p	BPX84	25p	MJ520	87p	OC83	25p
2N2613	35p	2N5176	45p	AFY29	27p	BPX85	22p	MJ521	87p	OC84	25p
2N2614	30p	2N5224	45p	AFY36	27p	BPY26	25p	MJ522	87p	OC89	32p
2N2646	57p	2N5245	45p	AFY50	25p	BPX87	27p	MPF103	37p	OC140	32p
2N2696	32p	2N5246	42p	AFY51	32p	BPX88	25p	MPF104	37p	OC170	30p
2N2711	25p	2N5249	67p	AFY54	25p	BPX89	62p	MPF105	37p	OC171	30p
2N2712	25p	2N5265	82-85p	AFY86	32p	BPX93A	70p	MP8968	32p	OC200	37p
2N2713	27p	2N5268	22-75	AU103	11-50	BFY10	30p	NKT0013	47p	OC201	47p
2N2714	30p	2N5267	22-62p	AR221	42p	BFY11	42p	NKT124	42p	OC202	62p
2N2865	62p	2N5305	37p	AUY10	11-50	BFY17	22p	NKT125	27p	OC203	42p
2N2905	37p	2N5308	37p	BC109	12p	BFY20	11-62p	NKT138	27p	OC205	75p
2N2905A	45p	2N5309	62p	BC113	27p	BFY21	42p	NKT137	27p	OC271	42p
2N2906	25p	2N5310	42p	BC115	40p	BFY24	45p	NKT210	30p	ORP12	62p
2N2906A	27p	2N5324	27p	BC116A	37p	BFY25	25p	NKT211	30p	ORP61	50p
2N2907	30p	2N5325	27p	BC118	32p	BFY26	20p	NKT212	30p	P346A	22p
2N2923	15p	2N5326	32p	BC121	20p	BFY29	50p	NKT213	30p	T836A	62p
2N2924	15p	2N5326S	47p	BC122	20p	BFY30	50p	NKT214	22p	T843	40p
2N2925	15p	2N5326	32p	BC125	55p	BPY41	50p	NKT215	22p	T844	12p
2N2926	15p	2N5327	37p	BC126	55p	BPY43	62p	NKT216	37p	T845	12p
Green	14p	2N5457	37p	BC140	37p	BFY40	20p	NKT217	42p	T846	12p
Yellow	12p	2N5005	75p	BC147	17p	BFY51	30p	NKT219	20p	T847	12p
Orange	12p	2N5020	22-00	BC148	12p	BFY52	22p	NKT223	37p	T848	12p
2N3011	50p	2N5192	50p	BC149	15p	BFY53	17p	NKT224	25p	T849	12p
2N3014	32p	2N5193	25p	BC152	17p	BFY56A	57p	NKT225	22p	T850	17p
2N3053	25p	2N5194	25p	BC157	20p	BFY75	20p	NKT229	30p	T851	12p
2N3054	50p	2N5201	32p	BC158	17p	BFY76	42p	NKT237	35p	T852	12p
2N3055	30p	2N5202	30p	BC160	15p	BFY77	57p	NKT238	25p	T853	22p
2N3133	30p	2N5203	37p	BC160	62p	BFY90	67p	NKT240	27p	T856	22p
2N3134	30p	2N5204	40p	BC167	15p	BPW68	27p	NKT			

LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on thin chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.

ADASTRA DOUBLE



eminently suitable). Smart black escutcheon. £14.70. P. & P. 60np.

5 stereo solid state amplifier housed in handsome cabinet veneered in natural teak. Size $11\frac{1}{2} \times 6 \times 5\frac{1}{2}$ in. 10 Transistors—power output 3 watts peak per channel. 220-240v A.C. Output impedance 12 to 15 ohms (our Cowdrey speaker system eminently suitable). Smart black escutcheon. £14.70. P. & P. 60np.

ELF

An extension speaker of quality, $9 \times 5\frac{1}{2} \times 3\frac{1}{2}$ in. veneered in natural teak with smart gold and mottled Vynair front 3 ohm speaker. The baffle is half inch thick. A real bargain at £1.90. P. & P. 36np.



SPEAKER MATCHING TRANSFORMERS

3, 7, 15 ohms, 8 watt, 70np. P. & P. 17np.

VYNAIR

Widths from 40 to 54 in., 75np yd. off roll. P. & P. 10np, $\frac{1}{2}$ yard 40np. P. & P. 10np. Send 5np stamps for samples.

MONO

GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95np. T.T.C. Crystal High Gain, 75np. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7np.

CARTRIDGES

Stereo: Sonotone 9TAH/C Diamond £2.40. Ronette S105 Medium Output, £1.40. S106 High Output £1.40. Acos GP93 1 Sapphire, £1.90. GP94 1 Sapphire, £2. TA700 equivalent to B.S.R. SX1M, £1.75. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7np on each.




CAXTON COLUMN

This is a column cabinet $23\frac{3}{4} \times 5\frac{1}{2} \times 5\frac{1}{2}$ in. deep finished in black or woodgrain cloth with blue or grey Vynair front. Keyhole slot for wall mounting. Fitted with three speaker units. 9 ohms impedance. Handles 8 watts. Makes all the difference in quality and volume of tape recorders and record players. Real bargain at £2.95. P. & P. 57np each.


SPEAKERS

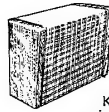E.M.I. $13\frac{1}{2} \times 8$ in, 3 ohm £2.50, 15 ohm. P. & P. 30np. E.M.I. 3in tweeter 95np. P. & P. 10np. E.M.I. $13\frac{1}{2} \times 8$ in. (15 ohm) Hi-Fi quality £6.25. P. & P. 30np. E.M.I. Crossover 85np. P. & P. 5np. Bakers 12in. 25 watt 8 and 15 ohms £7. P. & P. 30np. Eagle Crossover 90np. P. & P. 5np. Xtal lapel Mike, 40np. P. & P. 5np. Tel. P.U. 65np. P. & P. 5np.



IMP

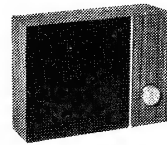Wedge shaped extension speaker $7\frac{1}{2} \times 6\frac{1}{2} \times 4$ in. (max.). Covered in walnut wood grain cloth with mottled Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only £1.25. P. & P. 36np each



THE FIESTA £2.95

P. & P. 36np. Brit. Isles. Fitted with 7 x 3 Speaker and Volume control. Teak veneered with Black Vynair.


TRANSISTOR SPEAKERS

$10'' \times 7\frac{1}{2}'' \times 3\frac{1}{2}''$ deep. 3 ohm ex TV Speaker. 3 in. 35 ohm. 50np. P. & P. 7np.

THE SHELLEY

Size $21 \times 11 \times 6\frac{1}{2}$ in.

An extremely elegant speaker system made of 12mm. chipboard covered with teak leathercloth with mottled Vynair front. This unique system uses three ex TV speakers. Carefully matched and tested. Will handle 10 watts and will match 8 ohms impedance. If preferred the speakers can be wired in series parallel to match 3 ohms impedance. A real bargain at £4.95 plus 70np P. & P. MATCHING TRANSFORMER for 15 ohms 80np post free.

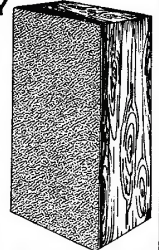

BROADWAY ELECTRONICS

(Nr. Tooting Broadway Underground Station)

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON S.W.17 01-672 3984

(Closed all day Wednesday)

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117)	33p
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	36p
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117)	36p
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	36p

Rod Aerial	RA2W	72p
Driver Transformer	LFDT4/1	58p
Output Transformer	OPT1	58p
Printed Circuit	PCA1	58p

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS


Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	39p
T41/2E	2nd I.F. Transformer	39p
T41/3T	3rd I.F. Transformer	57p
T41/3T	B.F.O. Coil	57p

Details of these and our other components are given in an illustrated folder which will be supplied on request with postage please.

WEYRAD (ELECTRONICS) LIMITED

SCHOOL STREET, WEYMOUTH, DORSET

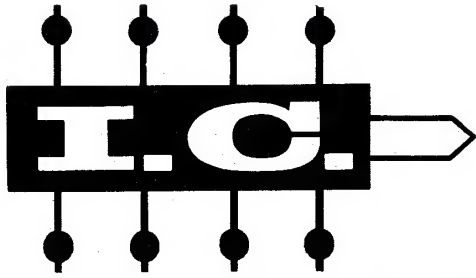

OF THE MONTH

L.A.J. IRELAND

Number 19

G.E. PA494 Precision Voltage Detector

BEFORE going on to consider the technical details of this month's circuit, it would be well to indicate some of the answers to the obvious question as to why the electronics enthusiast should be interested in a new high performance precision voltage detector such as the G.E. type PA 494. It was designed principally for applications requiring the logic function of a Schmitt trigger. In other words, the output of the i.c. would switch states very rapidly once the input threshold voltage had been exceeded. Applications for such a unit are obvious in circuits requiring pulse control, in that a trigger which has lost its shape can produce an accurate square wave output. In radio control of models for instance, this is a valuable feature permitting correction for signal degradation in propagation from the control transmitter to the model receiver. Of more general interest, however, are its uses in such systems as time delays, square wave generators, over-voltage and over-current protection systems, photo-electric controls, etc., some of these applications of the unit being considered in greater detail later on.

Operation


The PA494 itself comes as a four pin device mounted in a TO-5 package. The complete circuit diagram is shown in Fig. 1. Provided the input

voltage at pin 1 does not exceed the reference voltage set by the resistor pair R1, R2 then Tr2 and Tr4 will be biased on causing Tr7 to saturate and an output current of up to 250 mA may be drawn from pin 3. On the other hand once the reference voltage is exceeded at the input, Tr1 and Tr3 will conduct in addition to Tr5 resulting in positive feedback to the base of Tr2. This reduces the reference voltage and at the same time turns Tr2 off. Consequently the differential amplifier will have changed states and no output current will be available at pin 3 as Tr7 will have been biased off.

Due to the Darlington input configuration of the unit an exceptionally high input impedance is achieved with a mere 100 nanoamps needed to saturate Tr1. This makes the PA494 ideally suited for high impedance sources as a result of the low input current drawn. It combines many of the features of a f.e.t. in a bi-polar device; yet it does not suffer from failure due to static discharge as is sometimes the case with the f.e.t.

Practical Uses

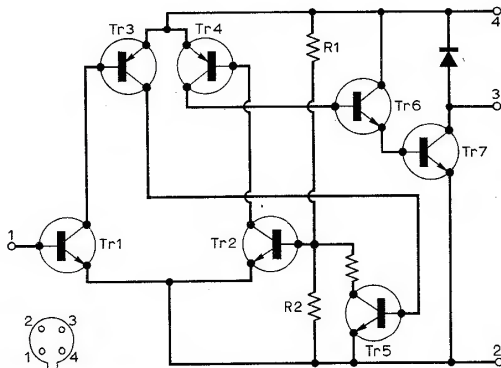Now let us consider some uses to which we can put the device. Fig. 2 shows a simple bridge configuration using a photoelectric cell or a thermistor



TO-5 package outline (Bottom view)

Fig. 1: Circuit of the PA494 with transistors circled for clarity.


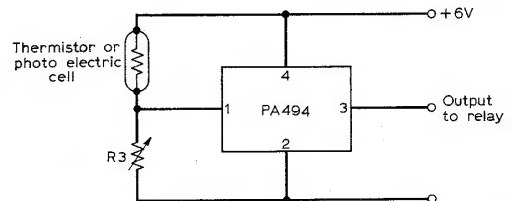


Fig. 2: (above) the PA494 in an alarm or warning system; and Fig. 3 (below), in a timing circuit.

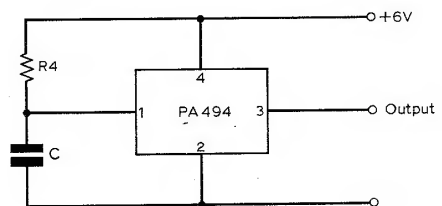

in one arm. The coil of a relay can act as the load for Tr7 thereby providing simple photoelectric control systems or on the other hand if preferred a discrete p.n.p. power transistor may be inserted for direct control of currents up to several amperes.

The PA494 also lends itself to very neat timing circuits of intervals of up to 1 minute, by a simple r.c. network. As can be seen from Fig. 3 a d.c. output is obtained when the threshold voltage is reached in contrast to the unijunction which generates a pulse.

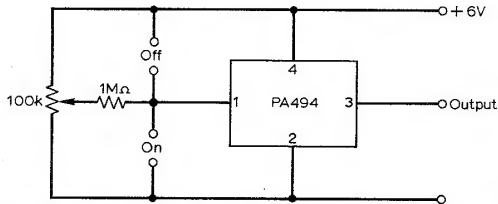


Fig. 4: Another application of the PA494. A switching or shaping circuit.

By biasing Tr1 midway between saturation and cut-off a number of interesting uses may be obtained. The same circuit as shown in Fig. 4 may be utilised as either an on-off touch switch, sine to square wave converter or pulse shaper.

No doubt further uses for the PA494 will spring to mind; a few designs have been given here in the hope that further innovations will be realised on the part of the individual constructor.

U.K. distributors for the PA494 are:— Jermyn Industries Ltd., Vestry Estate, Sevenoaks, Kent.

TELEVISION

USING THE 'SCOPE

The oscilloscope is an increasingly important servicing tool with the number of colour sets rapidly increasing and a whole range of video-cassette devices soon to appear on the market. Yet many enthusiasts and engineers are uncertain about its capabilities and use. Hence this new series by Keith Cummins—starting next month—to clear up exactly what can be done with the oscilloscope and how to do it.

DYNAMIC TV PICTURES

The video circuits in most sets are something of a compromise and do not do full justice to the contrast range of the transmitted picture. Norman McLeod presents a circuit for the experimenter to try which overcomes these defects and provides dynamic TV pictures.

LOGBOOK OF VAN 13

As you might suppose, Van 13 is on the colour run! Harold Peters in this feature provides details of common—and some not so common—faults found in colour receivers.

APRIL ISSUE-OUT NOW

P.W. DESIGNER'S TROPHY

Presented at Film Show

Although the postal strike prevented the despatch of the usual invitation cards, a reasonable number of readers turned out to see the filmshow at the Caxton Hall, Westminster, London, on 5th. March, run as usual by Practical Wireless and Television magazines in conjunction with Mullard Ltd.

The first part of the evening was devoted to the showing of two films, "Now and Then" featuring John Pertwee and "The Electrons Tale", a light-hearted look at the story of the electron.

Following the films, the Editor, Norman Stevens, presented the Practical Wireless "Designer's Trophy 1970" awarded for the most meritorious article submitted for the Project Autumn Competition. The reader was Caleb Bradley and his article "A High Impedance Voltmeter" was featured in the April issue of PW.

Following refreshments the rest of the evening was given over to a talk by Philip Hunt of Mullards. Entitled "I.C. Story-Continued" it was a continuation of the "Introduction to the I.C." lecture given at last year's Filmshow. This time the theme was the application and servicing problems of I.C.'s.

This year's show was the last to be run in conjunction with Mullard. The company have decided to make cuts in the film and lecture department but Mr. Stevens assured those present that every effort would be made to continue the Filmshows in the years to come.




Caleb Bradley receiving the P.W. Designer's Trophy from Norman Stevens.

Discosound

P. A. AND DISCOTHEQUE EQUIPMENT

— A COMPREHENSIVE RANGE COVERING EVERY REQUIREMENT

AMPLIFIERS, MIXERS, LIGHT CONTROL UNITS.

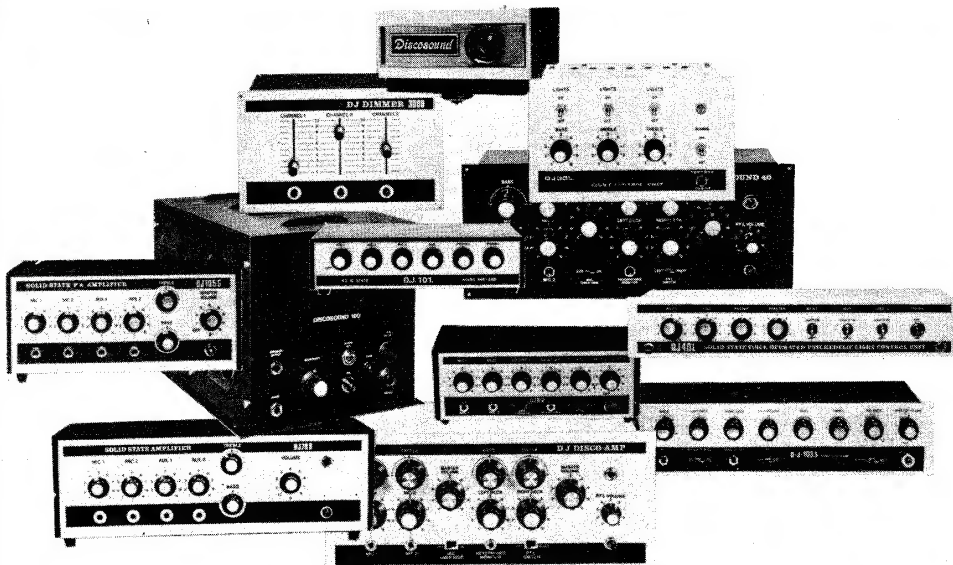

D.J. 102 Discotheque Mixer Pre-Amplifier

4 inputs each with its own volume control plus master volume control, PFL monitoring and mic override switches.

Size 10½" x 4" x 4".
Suggested Retail Price £25-00

D.J. 1055 P.A. Amplifier

4 channel mixing facilities each with separate inputs and volume controls. 90 watts r.m.s. power output A.C. Mains 200/250v A.C. Size 11½" x 5" x 6".

Size 10½" x 4" x 4".
Suggested Retail Price £41-00

D.J. 70S Integrated Mixer Amplifier

Power output 70 watts r.m.s. 4 channel mixer with separate inputs and volume controls, plus master volume and separate bass and treble controls.

Size 15½" x 5" x 6".
Suggested Retail Price £68-00

D.J. Disco-Amp

Designed specifically for use with discotheques. Power output 100 watts r.m.s. Two mike inputs and two gram inputs, with independent volume controls plus bass and treble controls. Incorporates many exclusive features.

Front panel size 18½" x 7".
Suggested Retail Price £85-00

D.J. 101 Mixer Pre-Amplifier

Six inputs allow full mixing facilities for all types of equipment. 9v battery operation. Size 10½" x 2½" x 4½".

Suggested Retail Price £14-00

Discosound 40 Discotheque Pre-Amplifier

Features independent inputs and volume controls for two microphones and two turntables plus separate bass, treble and master volume controls. Self powered and ideal for use with Discosound 100

Power Amplifier (is capable of running 10 of these power amplifiers—total 1000 watts)

Front panel size 18½" x 7".
Suggested Retail Price £40-00

Discosound 100 Power Amplifier

100 watts r.m.s. power amplifier (at 8 ohms) utilising all silicon transistors and features full automatic overload against short or open circuits. Frequency response 20-20,000 Hz ± 3db. Distortion less than 1% at 70 watts r.m.s. ± 1db.

Size 10½" x 8" x 7".
Suggested Retail Price £49-50

D.J. 1035 Stereo Pre-Amplifier

A high quality stereo discotheque pre-amp unit. Incorporating two microphone and two turntable inputs each with independent volume control, plus bass, treble, balance and master volume control. Offers full mixing and monitoring facilities.

Front panel size 10½" x 5½".
Suggested Retail Price £49-50

D.J. 30L Psychedelic Light Control Unit

3 channel light unit enabling bass, middle and treble frequencies from the amplifier to be operated individually. Handles 1000 watts per channel.

Front panel size 10" x 6".
Suggested Retail Price £37-50

D.J. 40L Sound Operated 3 Channel Light Unit

Features built-in microphone which eliminates the need for connections to any amplifier or sound source.

Handles 1000 watts per channel.
Suggested Retail Price £56-25

D.J. DIMMER 3000

3 channel light dimmer unit offered in two versions: Dimmer 3000—a straight three channel dimmer unit with mains input and three light outputs.

Dimmer 3000S—for use in conjunction with D.J. 30L Light Control unit only and has three mains inputs and three light outputs. Front Panel size 10" x 6".

Suggested Retail Price £38-50

Discosound Disco-Wheel

A projector designed to project a range of liquid wheels and colour change wheels for special lighting effects, adding colour and variety to any form of entertainment.

Size 7½" x 10½" x 5½".
Suggested Retail Price £30-00

A range of complete Discotheques with matching Speakers also available.

DISCOSOUND PRODUCTS ARE GUARANTEED FOR 12 MONTHS

For full details of the Discosound range of products call at or write to your nearest Discotheque Centre—Demonstrations given at any time.

DISCOSOUND

122 Balls Pond Road, London N.1. Tel: 01-254 5779

HENRY'S RADIO LTD.,

309 Edgware Road, London W.2. Tel: 01-723 6963

BI-PAK SEMICONDUCTORS

SILICON RECTIFIERS—TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	4p	5p	5p	7p	14p	21p	47p
100	4p	6p	5p	13p	18p	23p	75p
200	5p	9p	6p	14p	20p	24p	11
400	6p	13p	7p	20p	27p	37p	£1.25
600	7p	16p	10p	23p	34p	45p	£1.35
800	10p	17p	13p	25p	37p	55p	£2
1000	11p	25p	15p	30p	46p	65p	£2.50
1200	—	38p	—	38p	57p	75p	—

NEW LOW PRICED TESTED S.C.R.'s

PIV	1A	3A	7A	10A	16A	30A
50	23p	25p	47p	50p	58p	£1.15
100	25p	33p	55p	58p	68p	£1.40
200	35p	37p	57p	61p	75p	£1.60
400	43p	47p	75p	89p	£1.75	—
600	53p	57p	77p	97p	£1.25	—
800	63p	70p	90p	£1.20	£1.50	£4

2A POTTED BRIDGE RECTIFIERS. 200V. 50p

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 75p each.

DUAL-IN-LINE LOW PROFILE SOCKETS
14 AND 16 Lead Sockets for use with Dual-in-Line Integrated Circuits.

Order No.	Price	1-24	25-99	100 up
TS014 14 pin type	23p	37p	34p	—
TS016 16 pin type	23p	37p	34p	—

2N5060 NPN SIL. TRANS. SH. trans. suitable for P. B. Organ. Metal Diodes TEXAS. OUR PRICE 25p each

TRIACS.

2A	6A	10A
VBOM T05 T068 T048	100	50p 63p 21
200	70p	90p £1.35
400	90p	£1.20

VBOM—Blocking voltage in either direction.

SILICON DIAC
For use with Triacs

BR100	37p each
-------	----------

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed

Pak No.	EQVT.
T1	8 2G371A OC71
T2	8 2G374A OC72
T3	8 2G377A OC73
T4	8 2G381A OC81
T5	8 2G382T OC82
T6	8 2G344A OC44
T7	8 2G345A OC45
T8	8 2G375A OC75
T9	8 2G389A 2N1302
T10	8 2G417 AF17

All 50p each pack.

CADMIUM CELLS
ORP12 48p
ORP60, ORP61 40p each

PHOTO TRANS.
OC71 Type 48p

FREE
One 50p Pack of your own choice free with orders valued £4 or over.

SIL. G.P. DIODES
300mW 30 50p
40P.V. (Min.) 100 £1.50
Sub-Min. 50p
Full Tested 1000 29
Ideal for Organ Builders

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequaled Value and Quality
Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.

U1	120 Glass Sub-min. General Purpose Germanium Diodes	50p
U2	60 Mixed Germanium Transistors A/RF	50p
U3	75 Germanium Gold Bonded Diode sim. OA5, OA47	50p
U4	40 Germanium Transistors like OC81, AC128	50p
U5	60 300mA Sub-min. Sil. Diodes	50p
U6	30 Silicon Planar Transistors NPN sim. B5Y95A, 2N706	50p
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	50p
U8	50 Sil. Planar Diodes 250mA OA/300/592	50p
U9	20 Mixed Volts 1 watt Zener Diodes	50p
U11	30 PNP Silicon Planar Transistors T0-5 sim. 2N1132	50p
U13	30 PNP-NPN Sil. Transistors OC200 & 2N104	50p
U14	150 Mixed Silicon and Germanium Diodes	50p
U15	25 NPN Silicon Planar Transistors T0-5 sim. 2N897	50p
U16	10 3-amp Silicon Rectifiers Stud Type up to 1,000 PIV	50p
U17	30 Germanium PNP AF Transistors T0-5 like ACY17-22	50p
U18	8 6-amp Silicon Rectifiers BYZ13 Type up to 600 PIV	50p
U19	25 Silicon NPN Transistors like BC108	50p
U20	12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	50p
U21	30 AF Germanium alloy Transistors 2G360 Ser. & OC71	50p
U23	30 Mat's like MAT Series PNP Transistors	50p
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	50p
U25	25 300Mc/s PNP Silicon Transistors 2N708, B5Y27	50p
U26	30 Fast Switching Silicon Diodes like 1N914 Micro-min.	50p
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	£1
U29	10 1-amp SCR's T085 can up to 600 PIV CR81/25-600	£1
U31	20 Sil. Planar NPN trans. low noise Amp 2N8707	50p
U32	25 Zener diodes 400mW D07 case mixed Volts, 3-18	50p
U33	15 Plastic case 1 amp Silicon Rectifiers 1N4000 series	50p
U34	30 Sil. PNP alloy trans. T0-5 BCY26, 2B302/4	50p
U35	25 Sil. Planar trans. PNP T0-18 2N2906	50p
U36	25 Sil. Planar NPN trans. T0-5 BFY50/152	50p
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2B322	50p
U38	20 Fast Switching Sil. trans. NPN 400 Mc/s 2N3011	50p
U39	30 RF Germ. PNP trans. 2N1303/5 T0-5	50p
U40	10 Dual trans. 6 lead T0-5 2N2060	50p
U41	25 RF Germ. trans. T0-1 OC45 NKT72	50p
U42	10 VHF Germ. PNP trans. T0-1 NKT767 AF17	50p

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

UNFUNCTION
U746, Eart. 2N2648 Eqvt.
T1543, BEN3000 27p each
25-99 25p, 100 UP 20p

NPN SILICON PLANAR
BC107/8/9 10p each, 50-99 8p, 100 up 8p each, 1,000 off. 7p each. Fully tested and coded T0-18 case.

120VDC NIXIE DRIVER TRANSISTOR
Sim. B5X21 and C407, 2N1893 FULLY TESTED AND CODED ND150, 1-24 17p each, T0-5 NFN 25 up 15p each.

AD181 NPN AD182 PNP
OUR LOWEST PRICE OF 63p PER PAIR.

2N3055 115 WATT SIL. POWER. NPN.
OUR PRICE 63p EACH

PRINTED CIRCUITS EX-COMPUTER
Packed with semiconductor and components, 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 50p + 10p p. & p. 100 boards £3 + 80p p. & p.

FULL RANGE OF ZENER DIODES
VOLTAJE RANGE 2-33V. 400mW (D0-7 Case) 13p ea. 1-5W (Top-Hat) 17p ea. 10W (SO-10 8lead) 25p ea. All fully tested 5% tol. and marked. State voltage required.

BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.



BI-PAK Order No.

Order No.	Description	Price and Qty. Prices
BP00 7400N	Quad 2-Input NAND GATE	23p 20p 15p
BP01 7401N	Quad 2-Input NAND GATE—OPEN COLLECTOR	23p 20p 15p
BP04 7404N	HEX INVERTER	23p 20p 15p
BP10 7410N	Triple 3-Input NAND GATE	23p 20p 15p
BP20 7420N	Dual 4-Input NAND GATE	23p 20p 15p
BP30 7430N	Single 8-Input NAND GATE	23p 20p 15p
BP40 7440N	Dual 4-Input BUFFER GATE	23p 20p 15p
BP41 7441N	BCD to decimal decoder and N.I.T. Driver	87p 77p 67p
BP42 7442N	BCD to decimal decoder (TTL O/P)	87p 77p 67p
BP50 7450N	Dual 2-Input AND/OR/NOT GATE—expandable	23p 20p 15p
BP63 7453N	Single 8-Input AND/OR/NOT GATE—expandable	23p 20p 15p
BP60 7460N	Dual 4-Input—expandable	23p 20p 15p
BP70 7470N	Single JK Flip-Flop—edge triggered	35p 32p 28p
BP72 7472N	Single Master Slave JK Flip-Flop	35p 32p 28p
BP73 7473N	Dual Master Slave JK Flip-Flop	43p 40p 37p
BP74 7474N	Dual D Flip-Flop	43p 40p 37p
BP75 7475N	Quad Bistable Latch	47p 45p 43p
BP76 7476N	Dual Master Slave Flip-Flop with preset and clear	47p 45p 43p
BP83 7483N	Four Bit Binary Adder	87p 77p 67p
BP90 7490N	BCD Decade Counter	87p 77p 67p
BP92 7492N	Divide by 12 4 Bit binary counter	87p 77p 67p
BP93 7493N	Divide by 16 4 Bit binary counter	87p 77p 67p
BP94 7494N	Dual Entry 4 Bit Shift Register	87p 77p 67p
BP95 7495N	4 Bit Up-Down Shift Register	87p 77p 67p
BP96 7496N	5 Bit Shift Register	£1.10 £1.00 80p

Data is available for the above Series of I.C.'s in booklet form price 12p each.

GERM. POWER TRANS.

Type	Price each
OC29	50p
OC32	30p
OC23	33p
OC25	25p
OC26	25p
OC28	40p
OC29	40p
OC35	33p
OC39	40p
AD140	30p
AD142	40p
AD149	43p

D18D1 Silicon Unilateral switch 50p each.
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

EX-EQUIPMENT MULLARD
AF17 transistors. Large cut 4 lead type. Leads out short but still usable. real value at 15 for 50p.

SILICON HIGH VOLTAGE RECTIFIERS
10-Amp 3-K.V. (3000 P.I.V.) Stud Type with Flying Leads, 80p each.

TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	QTY.	PAK No.	QTY.
UI000 = 12 x 7400N	50p	UI073 = 8 x 7473N	50p
UI001 = 12 x 7401N	50p	UI074 = 8 x 7474N	50p
UI002 = 12 x 7402N	50p	UI075 = 8 x 7475N	50p
UI003 = 12 x 7403N	50p	UI076 = 8 x 7476N	50p
UI004 = 12 x 7404N	50p	UI079 = 5 x 7489N	50p
UI005 = 12 x 7405N	50p	UI082 = 5 x 7482N	50p
UI010 = 12 x 7410N	50p	UI083 = 5 x 7483N	50p
UI020 = 12 x 7420N	50p	UI086 = 5 x 7486N	50p
UI031 = 12 x 7431N	50p	UI090 = 5 x 7490N	50p
UI041 = 5 x 7441AN	50p	UI092 = 5 x 7492N	50p
UI042 = 5 x 7442N	50p	UI093 = 5 x 7493N	50p
UI050 = 12 x 7450N	50p	UI094 = 5 x 7494N	50p
UI060 = 12 x 7460N	50p	UI095 = 5 x 7495N	50p
UI070 = 8 x 7470N	50p	UI096 = 5 x 7496N	50p
UI072 = 8 x 7472N	50p	UI097 = 5 x 7497N	50p

UI098 = 25 x ASST' 74's £1.50

Packs cannot be split but 25 assorted pieces (our mix) is available as PAK UI0CX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

RTL FAIRCHILD (U.S.A.) I.C.'s

RTL Micrologic Circuits	Qty. prices each
Epoxy case T0-5 temp. range 15°C to 55°C	1-11 12-24 25-99 100+
µL 900 Buffer	40p 35p 33p 27p
µL 914 Dual two-input GATE	40p 35p 33p 27p
µL 925 J-K Flip-flop	53p 50p 47p 45p

Full data and circuits for I.C.'s in Booklet form price 7p each.

LINEAR I.C.'s



Type No.	Case	Leads	Description	Price
BP201C—SL201C	T0-5	8	G.P. Amp	85p 83p 45p
BP701C—SL701C	T0-5	8	OP Amp	35p 33p 45p
BP702C—SL702C	T0-5	8	OP Amp Direct O/P	63p 63p 45p
BP702—72702	D.I.L.	14	G.P. OP. Amp (Wide Band)	53p 45p 40p
BP709—72709	D.I.L.	14	High OP Amp	53p 45p 40p
BP709P—µA709C	T0-5	8	High Gain OP Amp	53p 45p 40p
BP741—72741	D.I.L.	14	High Gain OP. Amp (Protected)	75p 60p 50p
µA703C—µA703C	T0-5	6	R.F.—IF Amp	43p 35p 27p
TA4263	T0-72	4	A.F. Amp	70p 80p 55p
TA4263	T0-74	10	G.P. Amp	90p 75p 70p

ALL PRICES IN NEW PENCE.
Please send all orders direct to our warehouse and despatch department.

BI-PAK SEMICONDUCTORS

P.O. BOX 6, WARE, HERTS.
Postage and packing add 7p. Overseas add extra for Airmail. Minimum order 50p. Cash with order please. G.H.O. No. 388-7006

GOING BACK...

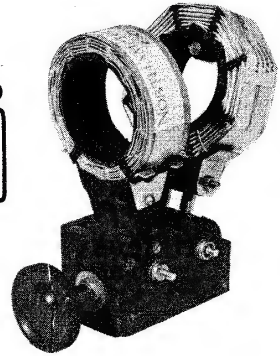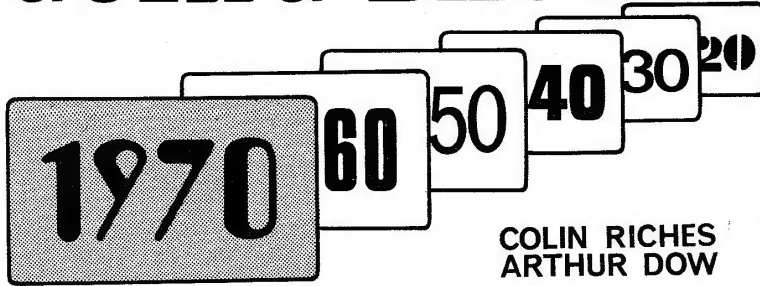

COLIN RICHES
ARTHUR DOW

ONE reads nowadays of the extremely high power stations that are being used on the very low frequencies for maintaining communication with nuclear submarines even when they are submerged. Megawatts on frequencies at the top end of the audio range are not unusual.

It was a similar combination of power and long wavelengths that opened up radio communication in the first decade of this century, but it would be invidious to compare the efficiency of those old transmitters and their aerial systems with those in use today.

We recently came across an article, written in 1912, that endeavoured to correlate power, distance and wavelength. At that time it was known that

signals was thought to be due to their "absorption" in the upper layers of the atmosphere but assuming no absorption at all the signals over the night path were still stronger than the calculated values.

Apparent changes in the degree of absorption between summer and winter had also been noted and it was thought that the conductivity of the upper atmosphere was increased by the action of the sun's rays.

Table 1 shows the calculated relationship between the aerial current at the transmitter and two ranges, 'working range' and 'extreme distance of audibility'. The first range produced 40μA in the 'receiver resistance' of 25 ohms and the second range 10μA, corresponding to 1000μV and 250μV.

These ranges were between two ships each having aerials at 130 feet so presumably the transmitter aerial current was measured in what was the base

TABLE 1

Aerial Current	Working Distance		Extreme Distance	
	Day	Night (zero absorption)	Day	Night (zero absorption)
amps.	miles	miles	miles	miles
1	75	90	200	360
2	135	180	300	720
3	180	270	375	1,080
5	235	450	475	1,800
7	280	630	550	2,520
10	345	900	630	3,600
15	420	1,350	725	5,400
20	475	1,800	790	7,200
25	525	2,250	840	9,000
30	565	2,700	900	10,800
40	630	3,600	970	14,400
50	685	4,500	1,025	18,000
60	725	5,400	1,150	21,600

received signal strengths in the daytime were roughly inversely proportional to distance but the rule only seemed to work up to about 150 to 200 miles after which signal strength dropped off quite rapidly. This was reception by ground wave, as we know it today.

Attempts to formulate some kind of law for signals travelling over a night path came to grief as it was observed that such signals were very irregular in strength and generally stronger than the signals received over the day path. The attenuation of

of a top loaded vertical over an almost perfect ground plane. The wavelength in use for these experiments was 1000 metres (300kHz).

However our mathematician seems to have gone astray by overlooking the impracticability of a 21000-mile night path; perhaps he was already thinking of going into orbit!

At this time, 1912, no one doubted the great advantages of long waves for communicating with distant stations and Table 2 was published to prove the point. This was based on two stations with aerials 450 high and again the distance quoted is working range.

It seems strange, in this scientific age, that brute

TABLE 2

Nautical Miles	λ=	λ=	λ=	λ=
	1,000 m.	2,500 m.	3,750 m.	6,000 m.
	amps.	amps.	amps.	amps.
1,000	15	13.5	15	17
1,250	38	27	27	30
1,500	91	49	44	46
1,750	200	95	77	74
2,000	490	155	122	105
2,250	—	245	314	160
2,500	—	470	414	235
2,750	—	—	500	335
3,000	—	—	775	500

force and long waves are still needed to establish solid communication at a distance regardless of conditions. One would think that an entirely new method of communication would have been dreamed up by now.

Ship Shack 1912

It is somewhat difficult for us, even the old-timers, to realise that in 1912 only the largest passenger ships were fitted with wireless telegraphy apparatus of a sort, that smaller ships, particularly cargo ships, were virtually lost to the rest of the world for weeks or even months on end once they had left our shores.

They did of course make visual signals to other ships and to coast stations en route so that owners had some idea of what was going on. Nevertheless ships, passengers and crews were lost at sea in circumstances where a brief radio call, had it been possible, would have brought other ships hurrying to their aid.



A typical ship's wireless cabin of 1912 fitted with the Marconi "1/2kW cargo set". The cabinet contains the vertical rotary converter with the disc discharger on top.


A dock labour dispute in 1911 did a lot to accelerate the equipping of the smaller ships with wireless telegraphy especially as owners realised that this would enable them to re-direct ships at a moment's notice which was particularly important with perishable cargoes. It was left to the Marconi company to produce a wireless installation that was small enough and cheap enough to be suitable for the smaller ships.

Called the "1/2kW cargo set" it could transmit spark signals between 200 and 600 metres wavelength and receive signals between 200 and 1600 metres. The ship's d.c. mains supply energised a rotary converter which gave a 1/2kW of a.c. at "a spark frequency of 300 per second." A disc discharger on top of the converter was adjustable so that the discharge took place at the peak voltage output of the converter.

Tapped inductors were wound with copper strip

on ebonite formers and these in conjunction with capacitors made from glass and zinc plates formed the "oscillation transformer".

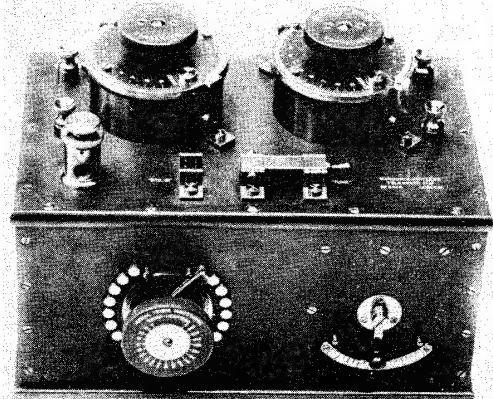It is interesting to note that the receiver, a "magnetic detector", was permanently connected to the aerial but was shorted out by an auxiliary pair of contacts on the key, "thus enabling the receiving operator to 'break-in' on the transmission in the event of erroneous reception and thus avoid waste of time". Even today very few amateur c.w. stations



A close-up of the "magnetic detector" receiver that can also be seen in the general view of the equipment

have proper "break-in" facilities, although they may have a fast changeover system, but that is not the same thing at all. Those that have true break-in do not use it to its best advantage but it must be admitted that the licence regulations governing the use of call signs does nothing to encourage the use of break-in!

MAXWELL



TRANSISTORS
NEW LIST—NEW PRICES
SEND FOR FREE COPY TODAY
BRAND FULLY
NEW GUARANTEED

2N404	22p	RAY81	7p	BFY68	17p
2N406	17p	RAY38	17p	BFY64	42p
2N407	17p	BFY10	15p	BSX20	12p
2N408	17p	BFY10	15p	BSX21	17p
2N409	17p	BFY10	15p	BSX22	15p
2N410	17p	BFY10	15p	BSX23	15p
2N411	17p	BFY10	15p	BSX24	15p
2N486	17p	BFY10	15p	BSX99	15p
2N487	17p	BFY10	15p	BSX00	15p
2N488	17p	BFY10	15p	BSX01	15p
2N489	17p	BFY10	15p	BSX02	15p
2N490	17p	BFY10	15p	BSX03	15p
2N491	17p	BFY10	15p	BSX04	15p
2N492	17p	BFY10	15p	BSX05	15p
2N493	17p	BFY10	15p	BSX06	15p
2N494	17p	BFY10	15p	BSX07	15p
2N495	17p	BFY10	15p	BSX08	15p
2N496	17p	BFY10	15p	BSX09	15p
2N497	17p	BFY10	15p	BSX10	15p
2N498	17p	BFY10	15p	BSX11	15p
2N499	17p	BFY10	15p	BSX12	15p
2N586	17p	BFY10	15p	BSX99	15p
2N587	17p	BFY10	15p	BSX00	15p
2N588	17p	BFY10	15p	BSX01	15p
2N589	17p	BFY10	15p	BSX02	15p
2N590	17p	BFY10	15p	BSX03	15p
2N591	17p	BFY10	15p	BSX04	15p
2N592	17p	BFY10	15p	BSX05	15p
2N593	17p	BFY10	15p	BSX06	15p
2N594	17p	BFY10	15p	BSX07	15p
2N595	17p	BFY10	15p	BSX08	15p
2N596	17p	BFY10	15p	BSX09	15p
2N597	17p	BFY10	15p	BSX10	15p
2N598	17p	BFY10	15p	BSX11	15p
2N599	17p	BFY10	15p	BSX12	15p
2N600	17p	BFY10	15p	BSX13	15p

HENRY'S LOW COST **INTEGRATED CIRCUITS**

WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF BRAND NEW CERAMIC FULL SPECIFICATION LOW COST TTL 7400 RANGE OF INTEGRATED CIRCUITS

Part Number	Description	Price 1-49	Price 50-99	Price 100+	Price 500+
7400	Quad 2-Input NAND Gate	25p	20p	18p	15p
7401	Quad 2-Input NAND Gate Open Collector	25p	20p	18p	15p
7402	Quad 2-Input Positive Nor Gate	25p	20p	18p	15p
7404	Hex Inverter	25p	20p	18p	15p
7405	Hex Inverter with Open Collector	25p	20p	18p	15p
7410	Triple 3-Input NAND Gate	25p	20p	18p	15p
7430	Single 8-Input NAND Gate	25p	20p	18p	15p
7440	Dual 4-Input Buffer Gate	25p	20p	18p	15p
7441	BCD to Decimal Decoder and NIX Driver	£1.00	80p	80p	75p
7442	BCD to Decimal Decoder (TTL)	£1.00	80p	80p	75p
7443	5 Bit Shift Register—Expandable	25p	20p	18p	15p
7453	Single 8-Input and/or Not Gate—Expandable	25p	20p	18p	15p
7460	Dual 4-Input—Expandable	25p	20p	18p	15p
7470	Single JK Flip Flop—Edge Triggered	40p	35p	30p	25p
7472	Single Master Slave JK Flip Flop	40p			

Sinclair Project 60



the world's most advanced high fidelity modules

Sinclair Project 60 presents high fidelity in such a way that it meets every requirement of performance, design, quality and value and now that the remarkable phase lock loop stereo FM tuner is available, it becomes the most versatile of high fidelity systems. With Project 60, it is possible to start with a

modest mono record reproducer and expand it to a sophisticated stereophonic radio and record reproducing system of fantastically good quality to hold its own with any other equipment, no matter how expensive. Project 60 is a unique high fidelity module system where compactness and ease of assembly are combined with

circuitry that is far in advance of any other manufacturer in the world. Thus it is extraordinarily easy to assemble any combination of modules using nothing more complicated than the simplest of tools, and you certainly do not have to be experienced to build with complete confidence. The 48 page manual free with Project 60 equipment makes everything easy and you can house your assembly in an existing cabinet, motor plinth, free standing cabinet or virtually any arrangement you wish. Once you have completed your assembly you will have superlatively good equipment to give you years of service and enjoyment. You will have obtained superb value for money because Project 60 is the best selling modular system in Europe and can therefore be produced at extremely competitive prices and with excellent quality control.


Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire PE17 4HJ.
Tel: St. Ives (048 06) 4311

sinclair

System	The Units to use	together with	Cost of Units
A Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	£4.48
B Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
C 20+20W. R.M.S. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., most dynamic speakers, F.M. tuner etc.	£23.90
D 20+20W. R.M.S. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
E 40+40W. R.M.S. deluxe stereo amplifier	2 x Z.50s, Stereo 60 PZ.8, mains trsfrmr	As for D	£34.88
F Outdoor P.A. system	Z.50	Mic., up to 4 P.A. speakers controls, etc.	£5.48
G Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43
H High pass and low pass filters	A.F.U.	C, D or E	£5.98
J Radio	Stereo F. M. Tuner	C, D or E	£25.00

Sinclair Project 60

Z.30 & Z.50 power amplifiers

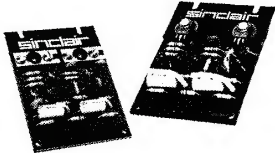

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z50 units are interchangeable with Z30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms, using 50 volts.

Frequency response: 30 to 300 000 Hz \pm 1dB.

Distortion: 0.02% into 8 ohms.

Signal to noise ratio: better than 70dB unweighted.

Input sensitivity: 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size: $2\frac{1}{2} \times 2\frac{1}{2} \times \frac{1}{2}$ in.

Z.30

Built, tested and guaranteed with circuits and instructions manual


£4.48

Z.50

Built, tested and guaranteed with circuits and instructions manual.

£5.48

Power Supply Units

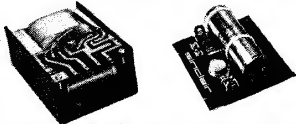

Designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

PZ-5 30 volts un-stabilised £4.98

PZ-6 35 volts stabilised £7.98

PZ-8 45 volts stabilised

(less mains transformer) **£7.98**

PZ-8 mains transformer £5.98

Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

Stereo 60 pre-amp/control unit



Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS

Input sensitivities: Radio—up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve \pm 1dB: 20 to 25,000 Hz.

Ceramic p.u.—up to 3mV; Aux—up to 3mV.

Output: 250mV

Signal-to-noise ratio: better than 70dB.

Channel matching: within 1dB.

Tone controls: TREBLE \pm 15 to $-$ 15dB at 10KHz; BASS \pm 15 to $-$ 15dB at 100Hz.

Front panel: brushed aluminium with black knobs and controls.

Size: $8\frac{1}{2} \times 1\frac{1}{2} \times 4$ ins.

Built, tested and guaranteed.

£9.98

Active Filter Unit



For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system.

Two stages of filtering are incorporated—rumble (high pass) and scratch (low pass). Supply voltage $-$ 15 to 35V. Current $-$ 3mA. H.F. cut-off ($-$ 3dB) variable from 28k Hz to 5k Hz. L.F. cut-off ($-$ 3dB) variable from 25 Hz to 100Hz. Distortion at 1kHz (35V. supply) 0.02% at rated output.

Built, tested and guaranteed

£5.98

Stereo FM Tuner



first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time, the principle has been applied to an FM tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Sensitivity is such that good reception becomes possible in difficult areas. Foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

SPECIFICATIONS:

Number of transistors: 16 plus 20 in I.C.

Tuning range: 87.5 to 108 MHz

Capture ratio: 1.5dB

Sensitivity: 2 μ V for 30dB quieting; 7 μ V for full limiting.

Squelch level: 20 μ V.

A.F.C. range: \pm 200 KHz

Signal to noise ratio: $>$ 65dB

Audio frequency response: 10Hz—15KHz \pm (\pm 1dB)

Total harmonic distortion: 0.15% for 30% modulation

Stereo decoder operating level: 2 μ V

Pilot tone suppression: 30dB

Cross talk: 40dB

I.F. frequency: 10.7 MHz


Output voltage: 2 x 150mV R.M.S.

Aerial impedance: 75 Ohms

Indicators: Mains on; Stereo on; tuning indicator

Operating voltage: 25-30 VDC

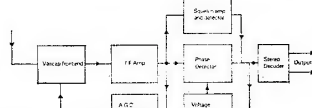Size: 3.6 x 1.6 x 8.15 inches; 91.5 x 40 x 207 mm



Price: **£25** built and tested. Post free

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send _____

for which I enclose cash/cheque/money order.

Name _____

Address _____

Sinclair IC10/Q16/Micromatic

IC10



The world's most advanced high fidelity amplifier

This is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself is a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, having 5 watts RMS output (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, and is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is more rugged and has considerable performance advantages, including complete freedom from thermal runaway and a very low level of distortion. The IC10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. It may also be used in other applications including car radios, electronic organs, servo amplifiers (it is dc coupled throughout) etc.

Circuit Description


The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. There is generous negative feedback round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory. Each IC10 is sold with a comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include oscillators, etc. The pre-amp section can be used as an RF or IF amplifier without any additional transistors.

Specifications:

Output: 10 watts peak, 5 watts RMS continuous.
Frequency response: 5Hz to 100kHz $1 \pm$ dB.
Total harmonic distortion: Less than 1% at full output.
Load impedance: 3 to 15 ohms.
Power gain: 110 dB (100,000,000,000 times) total.
Supply voltage: 8 to 18 volts. (A Sinclair power unit, PZ.7 is available for mains operation).
Size: 1 x 0.4 x 0.2 in. plus heat sink and tags.
Sensitivity: 5 mV.
Input impedance: Adjustable externally up to 2.5 Mohms.

Price (with manual): **£2.98** post free.

Q16

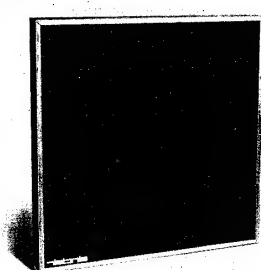

High fidelity loudspeaker


The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

Specifications:

Construction: Special sealed seamless sound or pressure chamber with internal baffle.
Loading: up to 14 watts TMS.
Input impedance: 8 ohms.
Frequency response: From 60 to 16,000 Hz, confirmed by independently plotted B and K curve.
Driver unit: Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and a special cone suspension for excellent transient response.
Size and styling: 9½ in square on face x 4½ in. deep with neat pedestal base. Black all-over cellular foam front with natural solid teak surround.
Price **£8.98.**

Micromatic

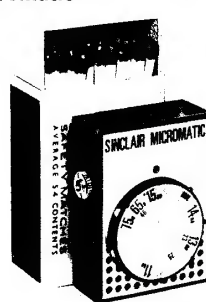

Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute and attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

Specifications:

Size: 36 x 33 x 13 mm (1¼ x 1⅓ x ½ in.)
Weight: including batteries, 28.4 gm (1 oz.).
Case: Black plastic with anodised aluminium front panel and spun aluminium dial.
Tuning: medium wave band with bandspread at higher frequencies, (550 to 1,600 Hz).
Earpiece: Magnetic type.
On/off switching: By inserting, and withdrawing earpiece plug.
Kit in pack with earpiece, case, instructions and solder **£2.48.**
Ready built, tested and guaranteed, with earpiece **£2.98**
Two Mallory Mercury batteries type RM675 required. From radio shops, chemists, etc.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

for which I enclose cash/cheque/money order.

PW571

Sinclair Radionics Ltd., London Road, .
 St. Ives, Huntingdonshire PE17 4HJ.
 Tel: St. Ives (048 06) 4311

sinclair



G.E.C. INDUCTION MOTOR

Very powerful 1/40th h.p. 725 R.P.M. For normal 230/240V 50 c/s mains. Switch start £2.50 including switch plus post & ins. 621p.



HORSTMANN "TIME AND SET" SWITCH
(A 15 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1.50, p. & ins. 23p.

SPARTAN Portable RADIO

Long and medium wave, 7 transistor, size 6in. X 4in. X 1 1/2in. with larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carry sling, earplug and case £3.75 plus 25p post and ins.



12 VOLT BATTERY CHARGER

Made in Japan, this is very small and neat. Regular use will keep your car battery in good trip throughout the winter. Silly price £1.25 plus 25p postage and insurance.

QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12v. car model also available £1.



PLINTH AND COVER

Suitable for most auto changers, teak base with tinted perspex cover £4.25 plus 50p postage.



THYRISTOR LIGHT DIMMERS

Will dim incandescent lighting up to 600 watts from full brilliance to out. Assemble and wired ready to install £3.



AUTO ELECTRIC CAR AERIAL

With dash board control switch—fully extendable to 40" or fully retracted. Suitable for 12V positive or Neg. earth supplied complete with fitting instructions and ready wired dash board switch £3.95 plus 25p. p. & p.



COMPUTER TAPE

2,400 ft. of the best magnetic tape money can buy. Made by E.M.I., 1/2in. wide almost unbreakable and on a 10 1/2in metal computer spool. Users have claimed successful results with video as well as sound recordings £1 plus 33p post. Cassette to hold spool 50p extra.




1 HOUR MINUTE TIMER

Made by famous Smiths company, these have a large clear dial, size 4 1/2 X 3 1/2, which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch £1.15.



THE FULL-FI STEREO SIX

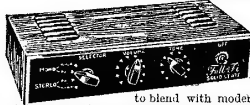

The amplifier sensation of the year. You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled in simulated teak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. UNREPEATABLE PRICE is £9 plus 38p post and insurance.

STANDARD WAFER SWITCHES

Standard Size 1 1/2 wafer—silver-plated 5 amp contact, standard 1/2" spindle 2", long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole ..	33p	33p	33p	33p	33p	33p	33p	33p	33p
2 poles ..	33p	33p	33p	33p	33p	33p	33p	33p	33p
3 poles ..	33p	33p	33p	33p	55p	55p	55p	75p	75p
4 poles ..	33p	33p	33p	55p	55p	55p	55p	95p	95p
5 poles ..	33p	33p	55p	55p	75p	75p	75p	115p	115p
6 poles ..	33p	55p	55p	55p	75p	75p	75p	135p	135p
7 poles ..	55p	55p	55p	75p	95p	95p	95p	155p	155p
8 poles ..	55p	55p	55p	75p	95p	95p	95p	175p	175p
9 poles ..	55p	55p	75p	75p	115p	115p	115p	195p	195p
10 poles ..	55p	55p	75p	95p	115p	115p	115p	215p	215p
11 poles ..	55p	75p	75p	95p	135p	135p	135p	235p	235p
12 poles ..	55p	75p	75p	95p	135p	135p	135p	255p	255p

Where postage is not stated then orders over £5 are post free. Below £5 add 90p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

MULTI-SPEED MOTOR

Replacement in many well known food mixers. Six speeds are available. 500, 850 and 1100 r.p.m. from either or both of the nylon sockets (Where the beaters of the food mixers normally go) and 8,000, 12,000 and 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. Very powerful and useful motor size approx. 2in. diameter, 5in. long. Price 90p plus 23p, p. & ins. 12 or more post free.



MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 X 2 X 2in. £1 each.



DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fixing. To drive models, oven, blower heater, etc. 50p each, plus 15p post and insurance, 6 or more post free.



0.005mFd TUNING CONDENSER


Proved design, ideal for straight or reflex circuits 13p each, £1.20 doz.



ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CRO-2TH
Also 102/3 Tamworth Road, Croydon

It costs ONLY 63p post paid

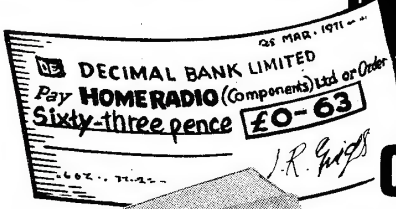

for today's MOST USEFUL COMPONENTS CATALOGUE

Many radio and electronic enthusiasts say that our catalogue is "priceless"! Be that as it may, we charge you only 63 pence. What is more the catalogue contains 6 vouchers, each worth 5 pence when used as indicated. And for good measure, we throw in a useful Bookmark giving electronic abbreviations and a 30-page Price Supplement. *Why are you waiting?* By the way, if it suits you to call at our shop you save yourself another 20 pence—the post and packing costs.

POST THIS GUPON

with your cheque or P.O. for 63p



Please write Name and Address in block capitals.

Name

Address



HOME RADIO (Components) LTD.
Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD

The price of 63p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only **£2**, less than the value of the clock alone—post and insurance 14p.




20 AMP ELECTRICAL PROGRAMMER

Learn in your sleep: Have Radio playing and kettle-boiling as you awake—switch-on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smiths Instrument Company. This is essentially a 230/240 volt mains operated Clock and a 20 amp Switch, the switch-off time of which can be delayed up to 12 hours (continuously variable not stepped). Similarly the switch-on time can be delayed. This is a beautiful unit, size 5½ x 3½ x 2½ in. deep. Metal encased, glass fronted with chrome surround. Offered at **£2.40** plus 23p postage and insurance.



Mains Connector

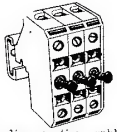A quick way to connect equipment to the mains safely and firmly—L, N, and E, coded to new colour scheme; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7/029 cables. 65p each.



FLOURESCENT CONTROL KITS

Each kit comprises seven kits—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—10-20 w. £1. Kit B—50-40. £1. Kit C—80 w. £1.20. Kit D—65 w. £1.20. Kit E for 8ft. 125 w. tube £1.75. Kit F for 6ft. 6in. and 12in. miniature tubes £1. Kit G for 2ft. 12 w. miniature tube £1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and E 23p on first kit then 15p for each kit ordered. Kit F 23p then 23p for each kit ordered. Kit G 18p on first kit then 15p on each two kits ordered.

BLANKET SWITCH

Double pole with neon let into side so luminous in dark. Ideal for dark room light or for use with waterproof element. In plastic case 30p each. 3 heat model 40p.



BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching on for varying time periods, thus giving a complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using up to 1 amp. Listed at **£1.40** each we offer these while our stocks last at only **65p** each.

REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types: Miniature. 1in. long x approximately ¼ in. diameter. Will make and break up to ½ amp to 300 volts. Price 13p each. £1.20 dozen. Standard. 2in. long x ¼ in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 10p each. 80p per dozen. Flat. Flat type, 2in. long, just over ¼ in. thick, approximately ¼ in. wide. The Standard Type flattened out, so that it can be fitted into a square or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 80p each. £2 per dozen. Small ceramic magnets to operate these reed switches 9p each. 80p per dozen.

HIGH CAPACITY ELECTROLYTICS

Brand new, not ex-equipment. 100 mfd. 25v. 4p each. 40p doz. 250 mfd. 50v. 16p each. £1.65 doz. 400 mfd. 40v. 22p each. £2.30 doz. 500 mfd. 12v. 10p each. £1.05 doz. 500 mfd. 25v. 18p each. £1.50 doz. 500 mfd. 50v. 23p each. £2.40 doz. 500 mfd. 350v. 43p each. £4.50 doz. 1000 mfd. 12v. 15p each. £1.50 doz. 1000 mfd. 18v. 17p each. £1.70 doz. 1000 mfd. 64v. 37p each. £4 doz. 2000 mfd. 25v. 34p each. £3.95 doz. 5000 mfd. 12v. 24p each. £2.40 doz. 10,000 mfd. 6v. 29p each. £3 doz. 10,000 mfd. 15v. 43p each. £4.50 doz. 15,000 mfd. 10v. 53p each. £5 doz. 90,000 mfd. 5v. £1.10 each. £11 doz. 70,000 mfd. 15v. 42p each. £20 doz. 3 amp 15v Battery Charger Kit—comprising 230/40 mains transformer with 3 amp secondary and 3 amp rectifier £1.15 plus 23p post. 12 volt 1½ amp Power Pack. This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd/50 smoothing. Price **£1.40**. Sonotone Stereo Cartridge. Turnover type, ref. No. 19 T1. This fits most British pick-ups and is a really excellent reproducer. Limited quantity. £1. 5 amp 3 pin Sockets. These are always good stock, you never know when you will need some. Famous make, brown bakelite, standard size, 12 for 65p plus 23p post. Ditto but with switch. 12 for £1 plus 23p post. 15 amp sockets, flush mounting. Bakelite, cream, less switch. 6 for £1.

Bakelite Panels, many thicknesses. We have just taken delivery of approximately 10 tons of bakelite in varying thicknesses from 2in. to a few thou. If you have a need for any of this then we would be glad to supply. The thickest is very heavy and could be used, for instance, as a bed for a motorised unit. Medium thickness is useful for front panels of instrument, etc. Cut to your size price is 30p per lb. plus 80p cutting charge plus carriage. 2 amp 3 pin Switched sockets for surface mounting, brown bakelite. Made by famous maker. 13p each or £1.20 dozen.

100 assorted Silicon Rectifiers G.P. and switching diodes. Small and very small sizes. A real snip for experimenters, 65p per 100.

HI-FI SPEAKERS (15, 30, 40 & 100W)

FULL FIVE INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwell—Power Handling 15 watts R.M.S. Cone Modified fibre—Freq. response 30-10,000 c.p.s.—Specify 3 or 15 ohms—Mains resistance 60 c.p.s.—Chassis Diam. 12in.—12½in. over mounting lug—Baffle hole 11in. Diam.—Mounting holes 4, holes—1in. diam. on pitch circle 1¼ in. diam.—Overall height 4½ in. A 26 speaker offer for only **£4** plus 27p p. & p. 12in. 40 watt £27 carr. 33p. 15in. 25 watt £28 carr. 33p. 18in. 100 watt **£19.50** carr. 21.50.



INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard and second of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over **£5**. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 5p upwards with circuit and technical data of each. Complete parcel only **£1** post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**

THIS MONTH'S SNIP 24-HOUR ELECTRIC TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours. 5 amp changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 23p. Additional time contacts 50p pair.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 12 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work. £2 less post **£2.25** with fitted 13 amp plug; **£2.40** with fitted 15 amp plug, plus 23p P. & I.



BARGAIN OF THE YEAR

MICROSONIC KEYCHAIN RADIO

7 transistor Keychain Radio in very pretty case, size 2½ x 2½ x 1¼ in.—complete with soft leather zippered bag. Specifications: Circuit 7 transistor superheterodyne. Frequency range: 530 to 1600 Kc/s. Sensitivity: 5 mv/m. Intermediate frequency: 468 Kc/s or 455 Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only **£1.25** less batteries plus 13p. post & for £2.75 post free. Pair of rechargeable batteries and charger 85p.



4 AMP VARIAC CONTROLLERS

With this you can vary the voltage applied to your circuit from zero to full mains without generating undue heat. One obvious application therefore is to dim lighting. Ex equipment but little used—as good as new offered at approx. half price. **£5** plus 75p. post and ins.




19 PIECE SOCKET SETS

Complete with wall or bench rack. Most useful sizes from ¼" to 1½" 80p plus 23p post and insurance.



HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price **£5.75** plus 23p post and insurance. Don't miss this terrific bargain.

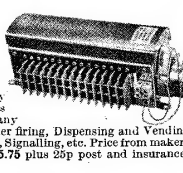

Where postage is not stated then orders over 45 are post free. Below 45 add 20p. Semi-conductors add 5p post. Over 41 post free. S.A.E. with enquiries please.

CONTROL DRILL SPEEDS

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. **£1.50** plus 13p post and insurance. Made up unit also available. **£1.90** plus 13p post & p.



DRILL CONTROLLER

500 ohm. operates speaker or meters. 30 useful in intercom or similar circuits. 33p ea. £3.60 doz.


PROTECT VALUABLE DEVICES FROM THERMAL RUNAWAY OR OVER-HEATING: Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the thermostat part of the heat sink. Motors and equipment generally can also be protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 150 deg. F. or with the dial removed range setting is between 50 to 300deg. F. Price 50p.



THERMOSTAT WITH PROBE This has a sensor attached to a 15A switch by a 14in. length of flexible capillary tubing—control range is 20°F to 150°F so it is suitable to control with heating and liquid heating especially when in buckets or portable vessels as the sensor can be raised out and lowered into the vessel. This thermostat could also be used to sound a bell or other alarm when critical temp. is reached in stack or heap subject to spontaneous combustion or if liquid is being heated by gas or other means not controllable by the switch. Made by the famous Teddington Co., we offer these at 65p each. Postage and insurance 14p.



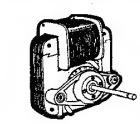MAINS MOTOR Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one then 5p for each one ordered.



NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 80p doz. Plastic push-rod suitable for operating. 5p each, 45p doz.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—1 pole, 12 way. All at 18p each, £1.80 dozen, your assortment.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

MICRO SWITCH

5 amp. changeover contacts, 8p each, £1 doz. 15 amp. Model 10p each or £1.05 doz.




ELECTRONICS (CROYDON) LTD
Dept. PW, 266 London Rd., Croydon CRO 2TH
Also 102/3 Tamworth Road, Croydon

COMET

HI-FI DISCOUNT WAREHOUSES

DRIVE-IN CAR PARK

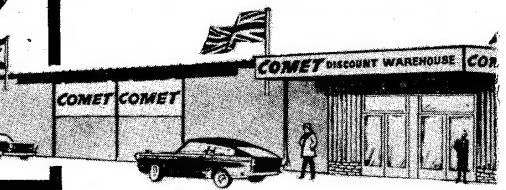

STEREO AMPLIFIERS

	Rec. Retail Price	Comet Price
ARMSTRONG 821	86-00	44-50
*DULCI 207	26-00	17-50
DULCI 207M	32-00	22-25
FERROGRAPH F307	59-00	48-00
GOODMANS 890	54-00	39-50
LEAK Stereo 30 Plus	56-50	44-75
LEAK Stereo 30 Plus, in teak case	62-50	49-50
LEAK Stereo 70	69-00	55-00
LEAK Stereo 70, in teak case	75-00	59-50
*LINEAR LT 66	21-00	17-00
METROSOUND ST20	36-00	28-00
PHILIPS RH 591	79-00	61-50
PHILIPS RH 592	52-00	39-50
PHILIPS RH 580	29-00	23-00
PIONEER SA500	62-10	43-00
PIONEER SA700	98-00	70-00
PIONEER SA900	136-10	97-00
PIONEER Reverberation	45-50	33-00
ROGERS Ravensbourne	59-50	47-00
ROGERS Ravensbourne (cased)	64-00	50-00
ROGERS Ravensbrook Mk. II	47-50	38-00
ROGERS Ravensbrook (cased) Mk. II	52-50	42-00
SINCLAIR 2000	35-00	26-00
SINCLAIR PROJECT 60 1/2 X Z30/PZ3	23-90	17-00
SINCLAIR PROJECT 60 1/2 X Z50/PZ4	34-86	25-50
SINCLAIR Newcast	61-95	46-00
SINCLAIR 3000	45-00	36-00
TELETON 203E	28-75	20-00
TELETON SA 206 (new release)	29-00	20-00
VOLTEX 100w. Stereo Discotheque, 8 electronically mixed inputs	185-00	139-00

Starred items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges.

TUNERS

*ARMSTRONG 523 AM/FM	53-76	45-00
*ARMSTRONG 524 FM	41-99	35-00
ARMSTRONG M8 Decoder	9-50	8-00
*DULCI FMT.7 FM	26-00	22-00
DULCI FMT.7S Stereo	35-00	29-95
GOODMANS Stereomax	52-25	39-50
LEAK Stereotic Chassis	66-50	52-00
LEAK Stereotic in teak case	72-50	59-00
PHILIPS RH 680	47-00	38-00
PHILIPS RH 681	38-00	30-50
PIONEER TX500 AM/FM	77-94	64-00
PIONEER TX900 AM/FM	153-69	125-00
ROGERS Ravensbourne	61-69	50-00
ROGERS Ravensbrook Mk. II	45-00	40-00
ROGERS Ravensbrook (cased)	51-26	43-00
*SINCLAIR 2000	26-73	19-25
SINCLAIR Project 60	25-00	21-00
TELETON 6T 101	45-50	34-00
TELETON 201X FM	36-00	30-00


All above Tuners are complete with MPX Stereo Decoder except where starred.

TUNER/AMPLIFIERS

AKAI AA 8500	229-00	181-00
AKAI 6600	142-53	112-00
ARENA R500	82-00	67-00
ARENA 2400	90-30	72-00
ARENA 2600 Stereo AM/FM	111-30	94-00
ARENA 2700	105-00	85-00
ARENA T1500F	72-45	60-00
ARENA T9000	303-45	258-00
ARMSTRONG M8 Decoder	9-50	8-00
ARMSTRONG 525	91-89	77-00
ARMSTRONG 528	104-71	87-00
GOODMANS Module 808 35w. R.M.S.	95-00	75-00
GOODMANS 3000	77-73	53-00
PHILIPS RH 700	139-00	112-00
PIONEER SX770 AM/FM	160-43	126-00
PIONEER SX900 AM/FM	194-74	150-00
PIONEER 440	111-10	89-00
*TELETON F200	51-50	32-00
TELETON 7 AT 20	105-00	80-00
TELETON 10AT1 150w. RMS	160-00	109-00
TELETON TF550	79-50	56-00
*TELETON R3000 with Speakers	63-25	50-00
TELETON CR55	120-00	95-00
WHARFEDALE 100.1	149-00	119-00

Starred items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges.

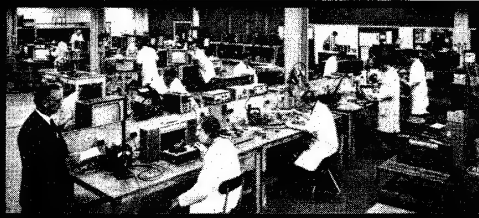All the above Tuners and Tuner/Amplifiers include MPX Stereo Decoder with the exception of Armstrong where decoder is extra as listed.



COMET for after-sales service
THROUGHOUT THE U.K.

Pictured, Service Dept. at Clough Rd., Hull also at Leeds, Stockton, Goole, Wakefield, Doncaster, and Bridlington

PICKUP ARMS

	Rec. Retail Price	Comet Price
GOLDRING Lenco L75	12-33	10-50
GOLDRING Lenco L69	9-29	7-00
SME 3009 with S2 Shell	34-47	28-00
SME 3012 with S2 Shell	36-71	31-50

CARTRIDGES

GOLDRING 800	13-00	7-50
GOLDRING 800H	10-69	8-00
GOLDRING 800E	18-88	12-25
GOLDRING 800 Super E	28-61	20-00
*GOLDRING CS90 Stereo	5-20	4-25
*GOLDRING CS91/E	7-81	6-25
*GOLDRING G650	9-00	5-25
EMPIRE 100ZEX	63-00	52-50
EMPIRE 999VE/X	44-50	36-00
EMPIRE 999TE/X	27-60	22-50
EMPIRE 999SE/X	21-00	17-50
EMPIRE 999E/X	16-50	13-00
EMPIRE 999X	11-50	9-25
EMPIRE 909E/X	12-85	10-25
EMPIRE 909X	8-46	7-50
EMPIRE 90E/X	9-75	8-00
ORBIT Magnetic NM 22	Special Price	2-90
PICKERING V15 AC2	8-46	7-50
ORTOFON SL15E	29-65	23-75
ORTOFON 2X15K Transformer	7-00	5-25
SHURE M3DM	7-41	5-25
SHURE M31E	12-05	9-50
SHURE M32E	11-10	8-75
SHURE M32-3	10-20	8-00
SHURE M44-5	11-10	8-50
SHURE M44-7	10-20	8-00
SHURE M-44C	10-20	8-00
SHURE M44E	12-05	9-50
SHURE M95E	12-85	10-25
SHURE M75G	17-80	14-00
SHURE M75-6	16-70	13-00
SHURE M75EJ	19-45	16-00
SHURE M75E-95G	23-15	18-00
SHURE M75E	21-30	16-00
SHURE M75E/D19	23-15	19-00
SHURE V15-11	40-76	30-00
SHURE V15-11-7	36-90	29-00

Starred cartridges above are ceramic. All others are magnetic.

TURNTABLES


GARRARD SP25, Mk III fully wired with Goldring G800 Magnetic Cartridge. Complete with base, plinth and cover	Special Price 21-98
GARRARD 2025 fully wired with Sonotone 9TA HC Cartridge complete with base and cover	Special Price 15-50
GOLDRING 705P turntable, complete with Goldring G880 cartridge, base and cover	25-00 15-95
DUAL 1219 transcription	60-40 50-00
DUAL 1209 transcription	42-62 35-00
GARRARD SP25 Mk III	16-45 11-90
GARRARD SL65 B	21-25 15-50
GARRARD SL75 B	38-95 28-50
GARRARD SL95 B	53-27 38-50
GARRARD 401	36-07 26-50
GARRARD SL72 B	32-77 26-90
GARRARD 3500, with GKS Cartridge	17-23 12-90
Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500	Special Price 4-00
GARRARD 40B	13-84 10-97
GARRARD AP 75	28-88 21-50
GOLDRING 705P with 850 Cartridge and Cover	26-00 23-90
GOLDRING GL69 Mk. II	26-63 22-50

	Rec. Retail Price	Comet Price
GOLDRING GL69 P Mk. II	35-14	29-50
GOLDRING GL75	36-41	33-90
GOLDRING GL75 P	46-94	41-90
GOLDRING CS90-plinth and cover for G99	4-21	3-50
GOLDRING G99	11-45	9-90
GOODMANS 3025	26-00	23-90
MCDONALD MP 60	37-74	26-90
MCDONALD 610	16-55	12-25
Base and Cover for MCDONALD MP 60 and 610	Special Price	4-50
PHILIPS 228	20-00	17-00
PHILIPS GA 146	31-50	25-00
PHILIPS 217	33-00	28-00
PHILIPS 202 Electronic	69-00	57-50
PIONEER PL 12A with base & cover	49-33	37-95
PIONEER PL11	57-90	39-00
THORENS TD125	8-85	7-00
THORENS TX 25 cover	79-04	64-95
THORENS TD150A Mk. II	46-16	35-95
THORENS TD125AB	120-20	100-00
THORENS TD150AB Mk. II	49-96	42-95
THORENS TX11 Cover	4-43	3-95

SPEAKERS

ARENA HT 16	13-00	10-95
B & W Model 70	139-50	115-00
B & W DM3	63-00	53-00
B & W DM1	32-00	25-50
CELESTION Dilton 120	24-00	19-00
CELESTION Dilton 15	32-00	25-50
CELESTION Dilton 25	65-00	52-00
GOODMANS Minister	29-00	21-20
GOODMANS Magister	35-00	33-00
GOODMANS Maxim	20-39	16-75
GOODMANS Mezzo 3	34-00	26-50
GOODMANS Magnum K2	44-00	33-00
KEF Concord	45-50	33-00
KEF Concerto	53-50	42-00
KEF Creta	22-17	18-00
KELETRON KN 500 4 speaker system (pair)	23-00	17-95
KELETRON KN 700 4 speaker system (pair)	27-50	21-95
KELETRON KN 1000 4 speaker system	19-25	14-95
KELETRON KN 1500 4 speaker system	24-75	19-95
KELETRON KN 2000 4 speaker system	28-75	21-95
LEAK 200	24-85	18-80
LEAK 300	32-50	23-95
LEAK 600	49-50	36-90
LOWTHER Acousta (with PM6)	45-50	38-50
LOWTHER Acousta (with PM7)	53-00	46-00
LOWTHER Ideal Barite	35-50	30-00
METROSOUND HFS 20	18-50	13-50
METROSOUND HFS 10 (pair)	27-44	22-90
PHILIPS RH481	11-00	9-25
PHILIPS RH492	13-00	10-00
SINCLAIR O16	8-98	8-00
STE-MA 275 3 speaker system	23-10	15-00
WHARFEDALE Speakers		
Airedale	69-50	56-00
Denton	19-95	15-90
Super Linton	24-95	20-50
Melton	35-50	25-50
Dovedale 3	45-50	32-50
Rosedale	65-00	52-50
Triton (pair)	59-90	46-90
Unit 3 speaker kit	13-00	10-50
Unit 4 speaker kit	18-00	14-25
Unit 5 speaker kit	26-00	20-50
CHASSIS SPEAKERS		
GOODMANS Axiette 8	8-10	6-50
GOODMANS Twinaxlette 8	9-17	7-50
GOODMANS Axiom 10	9-16	7-75

(OVER 1,520 sq. yds.)

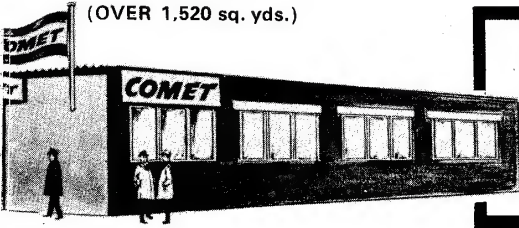

OVER 1000 ITEMS ALWAYS IN STOCK ALL FULLY GUARANTEED— WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

	Rec. Retail Price	Comet Price
GOODMANS Axiom 80	28-31	23-75
GOODMANS Axiom 201	14-45	10-95
GOODMANS Axiom 301	20-70	15-75
GOODMANS Audiom 8P	5-60	4-25
GOODMANS Audiom 10P	6-00	3-55
GOODMANS Audiom 51	13-05	9-75
GOODMANS Audiom 61	18-95	14-00
GOODMANS 12P	12-87	10-00
GOODMANS 15P	20-00	16-97
GOODMANS Audiom 18P	34-00	26-97
GOODMANS Twin Axiom 10	10-23	8-25
GOODMANS ARJ 172	4-50	3-50
GOODMANS Trebax 100	8-00	6-00
GOODMANS Trebax 5K/20XL	8-40	6-50
GOODMANS Midax	12-95	9-50
GOODMANS ARJ 100	3-55	2-00
GOODMANS Crossover Networks		
XO/950/5000	9-75	7-25
GOODMANS Crossover Networks		
XO/950	7-40	5-75
GOODMANS Crossover Networks		
XO/5000	2-65	2-00
WHARFEDALE 8 in. Bronze/R5/DD	5-00	4-00
WHARFEDALE Super 8/RS/DD	8-50	7-00
WHARFEDALE Super 10/RS/DD	14-00	11-50
WHARFEDALE WMT 1 Matching Transformer	0-84	0-75

HI-FI STEREO SYSTEMS (complete)

	Rec. Retail Price	Comet Price
ARENA MR15	145-00	115-95
ALBA UA652	47-50	33-95
ALBA UA682	62-99	47-95
BUSH System 749/748/764	102-65	82-85
DECCA Sound 903	72-50	59-95
DECCA Sound 904	72-50	60-95
DECCA Sound 1203	97-50	72-95
DECCALAN 5, complete with stand.	65-50	52-95
EKCO SRG 909	88-50	68-95
EKCO ZUS	165-00	135-00
FERGUSON 3422	84-70	68-95
FERGUSON 3424	123-15	105-00
FERGUSON 3245	138-2	112-95
FIDELITY Music Master UA2	43-00	35-95
FIDELITY Music Master UA1	98-00	82-95
GOODMANS 3000 Suite	140-45	92-95
H.M.V. 2415	129-70	104-95
H.M.V. 204/5/6	202-85	169-95
K.B. KA1250, complete with two 3-way speakers	72-00	56-00
K.B. KA1250, complete with two 651 speakers	80-00	63-95
LEAK 30/GOLDRING/WHARFE-	182-65	142-95
DALE	218-75	169-95
LEAK 70/THORENS/WHARFEDALE	126-75	99-95
MARCONI Unit 4	77-45	66-95
MARCONI Unit 3	89-00	69-95
METRO SOUND Stereo 1010	77-32	65-95
PHILIPS GF823	51-90	41-95
PHILIPS GF824	69-50	56-95
PHILIPS GF833	67-50	55-95
PHILIPS GF834	88-00	73-95
PHILIPS GF417	99-50	82-95
QUAD/THORENS/GOODMANS	372-78	312-75
TELETON 8-track Stereo	52-25	45-95
TELETON 2580F, with Stereo Radio	75-00	59-95
TELETON CMS400, with Stereo Radio	102-50	89-95
TELETON CRIOT 2025/1003, with Stereo Radio	82-10	45-95
TOSHIBA SP8507	248-00	175-00
ULTRA 6405	78-75	66-95
TELETON Stereo 8-track Tape Audio System complete	82-05	46-00

TAPE RECORDERS AND TAPE DECKS

AKAI M10L	245-05	189-00
AKAI X200D	190-00	150-95
AKAI X5000 W L	177-98	140-00

	Rec. Retail Price	Comet Price
AKAI X330	342-57	269-00
AKAI X-330D	312-56	245-00
AKAI X-360	380-08	284-00
AKAI X-360 D-deck	318-92	243-00
AKAI 1805D	199-42	167-00
AKAI 1710L	89-85	65-95
AKAI CR60 8-track stereo recorder	115-03	90-95
AKAI CR80D 8-track stereo tape deck	95-00	79-95
AKAI 4000 4-track Stereo	124-90	99-95
AKAI 4000 D 4-track Stereo deck	89-95	69-95
BUSH TP 50 Cassette Tape Recorder	29-40	24-95
BUSH TP 70 Cassette Battery/Main Tape Recorder	29-95	23-75
BUSH Discassette DCT0	121-05	110-00
FERGUSON 3282	101-80	82-95
FERGUSON 3245 Twin track	37-05	29-95
FERGUSON 3245 4-track	43-00	33-95
FERGUSON 3247 4-track Stereo	48-45	38-95
FERGUSON 3248 4-track	54-30	41-95
FERROGRAPH 722	242-54	202-00
FERROGRAPH 724	242-54	202-00
FERROGRAPH 702/W 2 track tape deck	207-35	168-00
FERROGRAPH 704/W 4 track tape deck	207-35	168-00
GOLDRING C200L Cassette	39-90	29-95
GRUNDIG TK 141 (4-track)	61-85	49-95
GRUNDIG TK 121 (Twin-track)	58-85	43-95
GRUNDIG TK 146 (4-track Auto)	68-14	53-95
GRUNDIG TK 149 4-track	57-63	47-95
PHILIPS 2202	29-90	23-95
PHILIPS 2205 Cassette Tape Recorder	43-15	34-95
PHILIPS 4404 4-track stereo recorder	95-00	73-95
PHILIPS 4407 4-track stereo recorder	110-00	89-95
PHILIPS 4302 Twin Track Auto	39-00	32-00
PHILIPS 4307 4-track	49-50	38-95
PHILIPS 4500 4-Track Stereo Tape Deck	128-00	98-95
PHILIPS 4408 4-track Stereo tape	109-00	86-95
PHILIPS N4308	60-50	47-50
PYE Cassette Recorder/Radio (Batt. Mains)	45-50	38-95
TELETON FXB 510 D 4-track Stereo	62-50	47-95
TELETON TRC 130 cassette, with VHF/AM radio, Battery/mains twin motors	39-50	29-95
TELETON TC110 cassette, battery/mains	27-50	19-95
TOSHIBA GT 840 S	110-00	89-95
TOSHIBA GT 601V Twin Track	45-15	25-95
TOSHIBA 850 SA	94-00	59-95

BASES AND COVERS

GARRARD WBI Base	3-86	3-25
GARRARD WB4 Base	5-69	4-75
GARRARD SPC 1 Cover	3-74	3-00
GARRARD SPC 4 Cover	4-44	3-75
SPECIAL OFFER OF BASE AND COVER TO FIT		
GARRARD SP25, SL55, SL65B and 3800	Special Price	4-00
GOLDRING Plinth 75	8-52	7-00
GOLDRING Plinth 69	8-52	7-00
GOLDRING Covers for 69P and 75P	4-21	3-50
THORENS TX25 (for TD125AB)	8-22	6-50
THORENS TX11 Cover	4-11	3-75
Base and Cover for TD 125	15-18	12-50
SME Plinth System 2000	39-20	31-25
MOTORBOARDS only	4-95	3-00

TEAK CASES

Leak 70/30 Amp. case	7-50	6-50
Leak Tuner case	7-50	6-50
Leak Double case for amp. & tuner	10-50	8-95

COMPLETE HI-FI SYSTEMS

Completely wired, mounted and ready for use

	Rec. Retail Price	Comet Price
TELETON Stereo 8 track tape Audio system complete with speakers..	52-25	46-00

GARRARD SP 25, Mk. III mounted in base, plinth and cover with GOLDRING G800 Cartridge, Teleton 303 or 205 Stereo Amplifier 12 watts RMS, and 2 KELETRON KN500 Speakers, each speaker is a 4 speaker system ..	88-33	58-95
---	-------	-------

PIONEER PL 12 turntable, Goodmans Maxamp, Shure M55E Cartridge, 2 Kellotron KN 700 speakers (each speaker cabinet contains 4 speakers)	144-38	105-00
--	--------	--------

GOLDRING GL 69P Mk. 11 mounted in base with hinged lid, GOLDRING G800 Cartridge, Rogers Ravensbrook Amplifier in Teak case, Two Wharfedale Super Linton Speakers	151-25	115-95
--	--------	--------

GOLDRING GL 75P mounted in teak base with hinged perspex cover complete with GOLDRING G800E Cartridge, Leak Stereo 30 Plus Amplifier in Teak case, 2 GOODMANS Mezzo 3 Speakers	200-50	154-20
--	--------	--------

THORENS TD 150AB Mk. II with TX11 dust cover, SHURE M55E Cartridge, LEAK Stereo 70 Amplifier in Teak case, 2 Wharfedale Dovecote 3 Speakers	226-87	175-00
---	--------	--------

THORENS TD 125AB Electronic Turntable complete with cover, SHURE V15-11 Cartridge, GOODMANS Maxamp, GOODMANS Stereoamp AM/FM Tuner, 2 GOODMANS Magister Speakers	422-48	309-00
--	--------	--------



All in-stock items delivered by **SECURICOR** WITHIN 72 HOURS

(Add £1.50 only for Securicor delivery)
ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

Open daily to the public from 9-0 A.M. until—
5-30 P.M. MON.
1-0 P.M. TUES.
8-0 P.M. WED.
8-0 P.M. THUR.
9-0 P.M. FRI.
5-30 P.M. SAT.
Customers are welcome to call - Ample car parking facilities

Complete Price List FREE on request!

COMET HIGH FIDELITY DISCOUNT WAREHOUSES

(Dept. P.W.) Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 407906 and 407877
(Dept. P.W.) 68A Armley Rd. (Artist St.), Leeds LS12 2EE Tel. 32035 (4 lines)
(Dept. P.W.) Teesway, Portrack Lane, North Teesside Industrial Estate, Teesside, KTS18 2RH Tel. 66132/65215

(Service Dept., New Road Side, Horsforth, Leeds)
Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closes for press. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) or, if Securicor delivery required, add £1.50 only. Make cheques, Money Orders payable to "COMET".

This MONTH'S Best Buy . . .



AKG K50 Dynamic Stereo headphones

Complete with spare ear muffs.
 Total (value £10.40) Our Price **£5.90** + 23p p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last.

- * High-fidelity reproduction due to broad frequency response (20-20,000Hz)
- * Substantially increased stereo effect
- * Headphones fit the head gently and do not shift
- * Earpieces fit ears snugly (Cardanic suspension)
- * Tone quality superior to conventional loudspeakers.
- * Only expensive studio loudspeakers can match the reproduction quality of the K50.
- * Music can be reproduced at concert hall volume (1), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.



GARRARD SP25 mk II £11.50 Plus 50p carriage

Normal price £15.57
 Single record playing unit. Features include cue and pause and automatic pick-up return and switch off.
 Wired with mains cable and 5ft. twin screened stereo cable, 5 pin din plug. 53p extra.
 AP75 Complete with base and cover £25 plus 75p carriage.

PLUGS ?



- Pack 107 5-Pin Din 20p
- Pack 108 5-Pin Din 15p
- Pack 135 1/2" Jack 25p
- Pack 130 1/2" Jack Stereo 48p
- Pack 103 Loudspeaker Plug 15p
- Pack 100 Phono Plug 6p
- Pack 230 3-Pin Socket 23p
- Pack 236 5-Pin Socket 30p
- Pack 234 Loudspeaker Socket 30p
- Ready-made Leads
- 3-pin to 3-pin Din 63p
- 3-pin to open end 53p
- 3-pin to 5-pin Din 80p
- 5-pin to open end 65p
- 5-pin to 4 phono plugs 93p
- Speaker lead Din to spade 12ft 30p. Extension lead Din plug to socket 12ft 65p
- All leads approx. 6ft. in length. Post free, by return.



PLINTH & COVER £5.25

Unbeatable Value plus 50p p. & p
 Suitable for AT60; SP25; 3000; 2500; 3500. Superb finish. Spindle can be left in position with cover on. Cover of neutral smoke tint perspex.
 Also available for AP75; SL5; SL75 £6.88 plus 50p carr.

Replacement Stereo **DIAMOND STYL**
 8TA 9TA 9TAHC
 GP91 ST4 ST9
 EV28 GC8 **75p** each
 others on request p. & p. 13p

Countdown SPEAKER

Teak Cabinet
£12 insurance & carr. 38p



A speaker of outstanding specifications and technical merit. Solid teak cabinet size: 14" x 10" x 6". Originally designed for use with our Countdown stereo budget system but now available separately.

EMI low matched loudspeaker set 450

Our price **£3.75** inc. 25p p. & p.

13 1/2" x 8 1/2" elliptical loudspeaker and independent high frequency units with associated crossover network. Frequency range 55 to 13000Hz. The cone of the bass unit has a surround designed for high travel giving freedom from distortion when operated at low frequencies.
 Also 350 KIT 20W Frequency range: 20 to 20,000Hz. **£7.50**
 Normal price £12.50 plus 40p p & p
 Also 150 KIT 10W **£2.50** plus 40p p & p
 3, 8 or 15 ohms



SINCLAIR Project 60

SAVE nearly £5 Normal price £23.90

Designed for building into plinths etc., complete with two 230 Output stages **£19** plus 50p carr.

(20 watt) and power supply unit. Send S.A.E. for full technical brochure.

SINCLAIR 2000 AMPLIFIER SAVE £6.30 Our price **£24.15**

Magnetic cartridges

Diamond **£4.75** (Fitted Diamond Styl) styli plus 13p p. & p. Today's value £6. Stylus replacement can be carried out without removing cartridge. Fully guaranteed.
 Ronette 105 Stereo cartridge (Sapphire 78 Diamond LP) £1.25 13p. p. & p.



SONOTONE Cartridge . . .

(Fitted Diamond Styl) (Ceramic) // at price 24.10
 Sensitivity: 9TAHC 55mV/cm/sec rms minimum at 45° at 1,000Hz measured on Decca SXL2057 **£2.50** plus 13p p. & p.

J. J. FRANCIS
 (WOOD GREEN) LTD
 123 ALEXANDRA ROAD, HORNSEY,
 LONDON, N.8. Tel: 01-888 1662

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the **practical way.**

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable **TECHNATRON Self-Build Outfit** take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

. . . and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

You LEARN—but it's as fascinating as a hobby

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

New Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of "OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO". This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.

FREE



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 372B, ALDERMASTON COURT, READING RG7 4PF

POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. 372B, Aldermaston Court, Reading RG7 4PF
 Please send books and full information — free and without obligation.




NAME AGE

ADDRESS

OCCUPATION

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

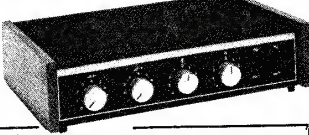HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response $\pm 20\text{dB}$ 12-20,000 Hz. Sensitivity: better than 20mV into 1M Ω . Full power bandwidth: $\pm 3\text{dB}$ 12-15,000 Hz. Bass boost approx. to $\pm 12\text{dB}$. Treble cut approx. to -16dB . Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2". Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES
AMPLIFIER KIT £10-60 P. & P. 15p
POWER PACK KIT £3-00 P. & P. 25p
CABINET £3-00 P. & P. 25p
(Post Free if all units purchased at same time)

Also available ready built and tested £20-50. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide fading facilities for medium powered Hi-Fi Discophone use, etc.

FANTASTIC 'POLY PLANAR' WATER-TYPE WIDE RANGE ELECTRODYNAMIC SPEAKER

Size only 11 3/4" x 14 1/2" x 1 1/4" deep. Weight only 19 ozs. Can replace cone speakers in any application and is particularly useful for those with limited space. Extremely rugged and shockproof. Operating temperature—20°F to 175°F. Power handling 10 watts r.m.s. (30 watts peak). Impedance 8 ohm only. Response 40 Hz-20 KHz. Can be mounted on ceilings, walls, doors, under tables etc. and used with or without baffle. Send S.A.E. for full details. ONLY £6-75 each. P. & P. 25p

MAGNAVOX DESK TYPE MOVING COIL MICROPHONE. Medium imp. Brand New. Price £10-10 P. & P. 10p
SINGLE HEADPHONE. With aluminum headband. Approx. 200 ohm, 25p. P. & P. 8p
CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity. 5p. P. & P. 8p

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE £1-05. P. & P. 8p
HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity. £1-05. P. & P. 12p

PIANO KEY TYPE SWITCHES. 3 press buttons plus 1 cancel button. Each of the 3 sections contains 6 s.p.c.o. (total 48 s.p.c.o.). Brand new—limited quantity only. Original manufacturing cost £1-37 1/2. OUR PRICE 75p. P. & P. 13p (3 or more post free).

HONEYWELL MICROSWITCHES. S/P. G/O. Push button action. Rating 250v. A.C. at 15 amps. Size approx. 1 1/2" x 1/2" x 1/2". 25p each. P. & P. 6p (2 or more post free).

SPECIAL OFFER! PLESSEY TYPE 59 TWIN TUNING GANG. 400pF + 146pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 k Ω i.f.c. I.F. spec approx. 2 x 1 x 1 1/2". Only 43p P. & P. 13p.

TELESCOPE AXIAL WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to 22 1/2in. approx. Maximum diameter 1in. 25p each. P. & P. 6p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-20-240v. Secondary combinations 0-10-15-20-25-30-35-40-60v. half wave at 1 amp, or 10-0-10. Compact design, all on 2amps full wave. Size 3in. long x 3 1/4in. wide x 3in. deep. Price £1-75 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 0-0-9 at 600mA. 70p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1-38. P. & P. 18p. Tapped Primary 200-220-240v. Sec. 21.5v. at 600mA. 85p. P. & P. 13p.

BATTERY CHARGER TRANSFORMERS. 200/240v. input. Nominal output for 6 or 12v. batteries 3 amps. Size approx. 3" x 2 1/2" x 2 1/2". Brand New. Price £1-05. P. & P. 25p.

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive design. Front. Size 16 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitter with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.
OUR PRICE £8.40 Carr. 50p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8-50 Carr. 50p

LOUDSPEAKER BARGAINS

3" 4 ohm 50p. P. & P. 8p. 5in. 3 ohm 80p. P. & P. 15p. 7 x 4in. 3 ohm £1-05. P. & P. 20p. 10 x 6in. 3 or 15 ohm £1-40. P. & P. 30p. E.M.I. 8 x 6in. 3 ohm with high flux magnet £1-62. P. & P. 20p. E.M.I. 13 x 8in. 3 ohm with high flux ceramic magnet £2-10 (15 ohm £2-25). P. & P. 30p. E.M.I. 13 x 6in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network £4-20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parastatic tweeter) 8 ohm £2-25 P. & P. 30p.

BRAND NEW. 12in. 15w. Hi/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiLux ceramic ferrobar magnet assembly £5-50. P. & P. 38p. Guitar models: 35w. £4-80. 35w. £3-50. E.M.I. 31in. **HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 93p each. P. & P. 13p.

12in. **"RA" TWIN CONE LOUDSPEAKER.** 10 watts peak. 12 or 15 ohm £1-88. P. & P. 30p.
35 OHM SPEAKERS 3in. 70p. P. & P. 13p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexform earmuffs. Wired and fitted with standard stereo j in jack plug. Frequency response 80-15,000Hz. Matching impedance 8-16 ohms. PRICE £2-85. P. & P. 15p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U., Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 3/4". Brand new complete with instructions. Price 88p. P. & P. 13p.

BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REEF. Cited mono $\frac{1}{2}$ stylus and cartridge for LP/78. ONLY £1. P. & P. 13p.

QUALITY RECORD PLAYER AMPLIFIER MK II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £3-75 P. & P. 30p
ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £4-48 P. & P. 30p

DELUXE QUALITY PORTABLE R/P CABINET MK II. Uncut motor board size 14 1/2" x 12in. clearance 2in. below. 3 1/2in. above. Will take above amplifier and any H.S.E.R. or SP25. Size 18 x 15 x 8in. PRICE £3-98. P. & P. 48p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £7-97 P. & P. 45p. Also available ready built and tested complete with add. input sockets, £9-97. P. & P. 45p.


BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 75p. V18/10p 50p; OC71 25p; OC76 50p; AF117 15p; 2G339 (NPN) 15p.
Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 £1-25; ORP12 Cadmium Sulphide Cells 50p. All post free.

VERY POWERFUL COMPACT MOTOR

For 12v. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Ideal in operation with high starting torque. Overall size approx. 1 1/2" x 1 1/2" dia. Free shaft 3/8" dia. x 1/2". Useful for Model Makers, etc. ONLY 38p. each P. & P. 5p.
3 or more post free (A few 6v. versions also available)

HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/4in. FIVE for 50p. P. & P. 10p.

DE LUXE STEREO AMPLIFIER

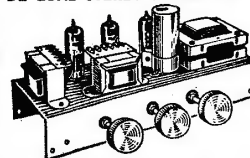

A.C. mains 200-240 v. U.S. 115 v. heavy duty fully isolated main transformer with full wave rectification giving adequate u.f.c. smoothing with negligible hum.

Valve line up:—2 ECL86 Triode Pentodes, 1 x E280 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11 1/2" w. x 4 1/2" d. Overall height including valves 5". Ready built and tested to a high standard. PRICE £8-92 P. & P. 40p.

4-SPEED RECORD PLAYER BARGAINS
Main models. All brand new in maker's original boxes.
LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER. With stereo cartridge £7-97 Carr. 33p.

STYLISH PLANTER UNIT FOR ABOVE with rigid plastic cover. £5-75 complete P. & P. 45p.
LATEST GERRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60 etc. S.A.E. for latest Prices! PLANTY Units cut out for Gerrard Models, 1025, 2025, 3000, 3000, 3500 etc. With rigid transparent plastic cover. Special design enables above models to be used with cover on mono equipment. Also suitable for housing AT60 and SP25. OUR PRICE £5-75 complete. P. & P. 45p.

LATEST ACOS GPB1/180 mono compatible cartridge with $\frac{1}{2}$ stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.
ACOS EL4 Single sided mono cartridge for LP & EP. ONLY 50p. Post Free.

SONOTONE SPACIO COMPATIBLE STEREO CARTRIDGE $\frac{1}{2}$ stylus Diamond and LP and Sapphire 78. ONLY £2-50 P. & P. 10p.

Also available fitted with Twin Diamond T/O stylus for Stereo LP. ONLY £2. P. & P. 10p.

LATEST ROSETTE T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. £1-63 P. & P. 10p.
LATEST ROSETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

HIGH GAIN TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TAI
Peak output in excess of 1 1/2 watts. All standard British components.
Built on printed circuit panel size 6 x 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GERT14 or 81 Mullard AC128D) and matched pair of AC128 9v. 9 volt operation. Everything supplied, wire, battery clips, solder, etc. Comprehensive ease to follow instructions and circuit diagram 15p (Free with Kit). All parts sold separately. **SPECIAL PRICE £2-45 P. & P. 15p.**
Also ready built and tested, £2-75. P. & P. 15p.


3-VALVE AUDIO AMPLIFIER HA24 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone control giving bass and treble lift and cut. Negative feedback line. Output 44 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4-75. P. & P. 30p.
HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA24 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £2-98. P. & P. 30p.

HARVERSON'S SUPER MONO AMPLIFIER. A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and heavy output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.
FEW ONLY. BARGAIN PRICE £7.75 P. & P. 30p

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

CHROMOSOMIC SOUND OPERATED LIGHT DISPLAY

This compact unit (size 8 1/2" x 6 1/2" x 8" high) is connected directly across the speaker output of an amplifier, it will then convert audio signals into a spectacular three colour light display (500 watts light output each colour) Send S.A.E. for further details. **£18.50** P. & P. 88p



CRESCENT


RADIO LTD

11 & 40 MAYES RD
LONDON N22 6TL
888-3206

PLEASE NOTE PRICES IN DECIMALS


TRANSFORMER SCOOP

Primary 220, 250 v. fused.
Secondary 220 v. at 50mA
6.3v at 1 amp.
Overall size 2 1/2" x 2" x 2 1/2" high.
63p each.
P. & P. 15p.




BARGAIN COMPUTER BUMPER BOARDS

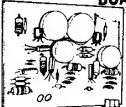Many Resistors, Condensers, Diodes and Transistors (minimum of 4 transistors on each board).
5 BOARDS FOR 120p. Post Free.




ACOS STETHOSCOPE

Used but in good condition. For personal listening and monitoring with tape recorders, transistor sets and record players. 200 ohm DC resistance. 5 ft. lead.
30p. Postage 5p.




CHROME TV STAND

Stand would make an ideal base for a coffee table and is a bargain at **163p.** Post 25p




SOLID STATE BLOCK MODULES

Phono pre-amp E1311 input 100k; gain 25dB max out 3 volt; max input 50mV.
Tape pre-amp as above E1313.
Power amp E1314 input 1,000 ohms gain 20dB 300mW.
Organ tone osc E1315 tone freq. 200-1k Hz output 50mW. All above modules 9 volt. Dual flasher E1318 flash time 1-4 secs power 6 volt. Lamp 6v 150mA. All at **£1.25 P. & P. 10p**




LIGHT DIMMER

The unit comes complete with MK Ivory Front Plate and Control Knob, when used in place of Light Switch it will control your room lighting from, off to full brightness. Power—up to 300 watts interference suppressed
£2.75 + P. & P. 8p.




MOTOR

Rated up to 11.5 volt 400mA. Size 1 1/2" long. 7/8" dia. Shaft 1/8" long Post **43p**



TUAC HIGH POWER AMPLIFIER

True 100 watt output.
Studio switch, for lower power work, but with same tone.
Over 30dB of treble boost and full bass response.
Full power — four ohms
10-30,000 Hz response ideal for bass guitar work
Negligible distortion right up to full output
Price **£89.00** Postage 50p
FULL 12 MONTH GUARANTEE




COMPONENT CENTRE

8" x 8" one sided printed circuit board 10p each
BY100 type resistor 800 v/750mA 18p each
4-pin transistor holders ... 8p each
2 1/2" 80 ohm loudspeaker ... 30p each
2 1/2" 8 ohm loudspeaker ... 35p each
2 1/2" 25 ohm loudspeaker ... 38p each
1/2 battery holders (blue plastic) ... 5p each
10 ohm w/w pots ... 13p each
OC1 double heat clips ... 3p each
Tape recorder rev. counters ... 25p each
Please include P. & P.

STEREO HEADPHONES

All Types 8 ohm
SH550 ... £2.38
DH225 Dits. ... £2.38
SD17D ... £4.00
G2222-w/ih volume controls on each ear £5.50
SDH205V-Good quality with volume controls £2.50
Postage—20p on all types.




G.E.C. RATCHET RELAY

No RELIA/008/07 C61—375 Ω 3-make break contacts. 1-changeover. All New and Boxed.
30p. each. Post 5p.


FLICK SWITCHES

250 volt 3A. Single Pole on/off. 1 1/2" nylon Toggle.
18p Plus Postage 5p



DWELL TIME UNIT

These small units contain the following components:
700 ohm DPDT relay with base, 1/16" 250v. paper, 0.01µF 400v. paper, 30µF 50v. electrolytic, 3 diodes OC200 transistor, a 2N2925 type transistor unmarked, a skeleton pre-set pot, 4 pin dim plug & socket, 4 foot of 4 core screen. All housed in a small neat metal box. Can be made into many timing devices.
43p + P. & P. 8p



PADGETTS RADIO STORES

OLD TOWN HALL, LIVERSEDGE, YORKS

TEL. HECKMONDWIKE 4285

40 ONLY. The much sought after Sighting Computer Mark XIV.A. For the model maker. Condition Good. £2.50p. Carriage £1.00.

AMPLIFIER UNIT TYPE A1418. Complete with 6Z4 and 6V6GT valves 250/230 volt. 50 cycle. Transformer, Clean Condition, Untested. £1.25p. Carriage 75p

AIR POSITION INDICATORS. Contains Gears, Ball Races, Dimmer Units, Lamps. Four numbered controls, 24 volt Motor etc. Great interest to the model makers. In good condition, 75p. Carriage 50p.

GROUND POSITION INDICATOR. Contains 24 volt lamp, Prisms Mirror, Gears Could interest schools & model makers. 75p. Carriage 75p.

NEW BOXED UNIT TYPE B197. Contains two Toggle D.P.S.T. switches, also one Press Toggle D.P.S.T. Sixteen Miniature, 500 Ohm. Pre-set Pots RX/TX switches etc. 25p. P. & P. 22p. £3.00 per dozen. Carriage paid.

TOGGLE SWITCHES. Ex Units D.P.D.T. 10p. D.P.S.T. 5p. S.P.S.T. Spring Loaded 10p. D.P.S.T. Press Button Spring Loaded 10p. P. & P. on any switch 4p. Doz. Post Paid.

G.P.O. RELAYS EX-UNITS. 400 Ohms and 600 Ohms 50p per doz. P. & P. 25p. Sample Relay 6p. P. & P. 5p.

MINIATURE BRASS LAMP HOLDER. 10p. P. & P. 5p. 90p per doz. Post Paid. Base Board Type.

RECLAIMED T.V. TUBES with 12 months Guarantee. 17" AW 43/88 £1.50p. MW 43/69 £1.50p. AW 43/88 £2.00. Carriage and Insurance on any tube £1.00.

12 CHANNEL COMPLETE UNTESTED T.V. SETS. £2.50p Carriage and Insurance £1.50.

SPEAKERS REMOVED FROM T.V. SETS. All 3 Ohm and P.M. 6x4. 15p. 7x4 25p. 8x24 25p. Post on any Speaker 20p.

VALVE LIST—Ex Equipment 3 months guarantee. Single valves. Post 8p, over 3 valves P. & P. Paid.

ARF12	5p	EP50	5p	30F5	15p	PY81	5p	6P28	25p
EB91	4p	EP80	3p	PCL84	20p	PY82	8p	20D1	10p
EF85	15p	EP91	4p	PCL82	20p	PZ30	25p	20P1	25p
EBF80	15p	EV86	25p	PCL88	25p	U191	25p	20P3	15p
EC051	15p	FOC84	10p	PL36	35p	U201	25p	30P4	25p
EC082	15p	FOC80	10p	PL81	30p	6BW7	10p		
ECL80	10p	30P12	25p	PY33	25p	6U4	25p		

NEW VALVES!

Guaranteed and Tested 24-HOUR SERVICE

R5	27	30PL13	76	EB91	11	EF184	30	PCF802	44	R19	81
IS5	21	30PL14	87	EB03	38	EL83	48	PCF805	54	U26	85
IT4	18	COH35	85	EBF89	90	EL84	24	PCL85	38	U26	83
384	28	DAC32	83	EC031	17	EY51	85	PCL84	35	U191	80
3V4	37	DAF91	22	EC032	20	EY86	81	PCL86	42	U251	70
6J30L2	57	DAF95	95	EC033	23	EZ30	29	PCL86	40	U229	70
6AQ5	25	DF33	87	ECF80	25	EZ31	23	PFL200	54	UABC80	80
6BW7	57	DF91	16	ECF82	88	ET61	46	PL38	49	UBF89	31
6F23	71	DF96	85	EOH35	27	KT86	82	PL81	48	UCC85	88
6F25	40	DK23	83	EOH81	38	N78	85	PL82	30	UCR81	88
2L6GT	28	DK91	87	EOL80	33	PC86	49	PL83	49	UCL82	84
30C15	69	DK92	41	ECL82	31	PC88	49	PL84	81	UCL83	49
30L15	60	DL84	37	EP85	28	PC089	46	PT32	54	UY85	27
30L17	71	DL86	38	EP86	31	PC089	50	PT32	54	Z77	88
30P4	60	DY36	38	EP89	23	PCF80	29	PY82	25		
30P19	60	DY87	28	EP91	12	PCF86	45	PY80	35		
30P11	61	EABC80	31	EF183	27	PCF801	32	PY801	35		

Postage on 1 valve 5p, on 2 or more valves 8p per valve extra. Any parcel insured against damage in transit 5p extra. Office address, no callers.

GERALD BERNARD
83, OSBALDESTON ROAD, STOKES NEWINGTON, LONDON, N.16

If you have difficulty in obtaining

PRACTICAL WIRELESS

Please place a regular order with your newsagent or send 1 year's subscription (£2.65) to Subscription Department, Practical Wireless, Tower House, Southampton St., London, W.C.2.

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 8½p per word (minimum 12 words), box number 7½p extra. Semi-displayed setting £6 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

MISCELLANEOUS

We stock all those components and materials required by the home Hi-Fi constructor, including speaker grille fabrics, BAF wadding, Peerless speaker kits, Helme Cabinet Kits, cross-over networks, inductors, etc. Special offers also available. Send 4 x 3p stamps NOW for your copy of our new fully illustrated catalogue (catalogue cost refunded against purchases over 50p). No callers please, mail-order ONLY.

AUDIOSCAN Dept. PW5
4, PRINCIPLES SQUARE
HARROGATE, YORKS.

12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts. 12 ins 8 watt Tube. Ideal for Caravan, Tent, Emergency Lighting etc. Fully Transistorised, Low Battery Drain, With ON/OFF Switch and 12v Socket to Run other Lights or 12V Equipment.

Unbeatable at **£3.30** post paid
or in kit form **£2.90**

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 32 output, new and boxed **£3.65** POST PAID

SALOP ELECTRONICS Callers welcome
23 Wyle Cop Shrewsbury, Shropshire S.A.E. for lists

MUSICAL MIRACLES

WAA-WAA Pedal. Complete kit of all parts, robust cabinet, mechanism & instructions. Huge sales, well proven design. Only £2.45 complete. Or built & tested £4.75 post free.

Rhythm Box. Build your own from our pre-built electronic circuit modules, e.g. box giving waltz, foxtrot etc., cost under £11.

Organ Percussion units £14. Bass pedal and other fascinating effects, fuzz, reverb etc.
Send 15p for list. D.E.W. Ltd.,
254 Ringwood Rd., Ferndown, Dorset.

DAILY UFO FLIGHT PATTERNS (British, American), 37½p. UFO Map, S. England, 37½p. TV Notes on UFO Detection, and Optical Circuits, 50p. Radar & Electronic Publications, "Highlands," Needham Market, Suffolk.

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond Surrey.

MISCELLANEOUS

(continued)

MODULES. Epoxy resin moulded, size 12mm x 30mm dia approx. Written guarantee. Data supplied to make a variety of projects.

M1. AUDIO AMP. 1 watt output. 7½-15v supply, requires speaker, volume control and battery. £1.25.

M2. INTERCOM AMP. Requires only speaker, switch and battery to make a very sensitive intercom. etc. 90p.

M3. AUDIO TONE GENERATOR. Can be used for signal injector, organ, morse practice, etc., adjustable frequency. 55p.
A. MANLEY, 13 Randisbourne Gardens, Bromley Road, London, S.E.6.

AE 396

PICK-UP CONVERSION KIT

To replace E.M.I. Double 'C' cartridge, comprising pick up head shell, turn-over holder and dual sapphire cartridge. Mono only. Full D.I.Y. instructions supplied.

£3.72

Send stamp for comprehensive lists of transformers, condensers, resistors, cartridges and tape heads.

R. D. I. LTD.,
Chilton Works, Garden Road,
Richmond, Surrey.

THE NEW

ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 2p stamp.

ENAMELLED COPPER WIRE

S.W.G.	Per 1½ lb reel	Per 1lb reel
18-22	£0.62½	£0.92½
23-30	£0.65	£0.97½
31-35	£0.67½	£1.02½
36-40	£0.82½	£1.32½
41-44	£0.97½	£1.62½

Orders despatched by return of post. Please add £0.12½ per item P. & P.

Supplied by: Banner Transformers, Brooks St., Higher Hillgate, Stockport, Cheshire.

TRADE ENQUIRIES INVITED

BUILD IT in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

LOUDSPEAKER ENCLOSURES, hand made, teak veneered, below wholesale prices. 01-445 2451. London STD anytime. SLD.

MISCELLANEOUS

(continued)

ENGINEERING SERVICE for constructors. Lathe work, milling, sheet metal, castings, etc. S.A.E. for details, Chelmsford Machine Tool Company, P.O. Box 55, Chelmsford CMI 2AU.

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

AUSTRALIAN READERS! SEND S.A.E. FOR ELECTRONICS CATALOGUE. HOBIPAK, P.O. Box 224, Carlton South, 3053, Victoria, Australia.

MORSE MADE !! EASY

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 send 4p stamp for explanatory booklet to:

G3CHS (BOX 11),
45 GREEN LANE, PURLEY, SURREY

SAMWELL HUTTON TV Wobulator type 41B, £22.50. Marconi beat frequency oscillator Model TF 1951, £15. Marconi signal generator model TF 144G/4, £20. Telephone 01-449 1769.

YUKAN SELF-SPRAY so professional, the world's best spray

Get these **air drying GREY HAMMER** OR **BLACK WRINKLE (CRACKLE) finishes** NOW!

Yukan Aerosol sprays combine with fine quality durable easy instant spray. No stove baking required. Hammer's available in grey, blue, Modern Eggshell Black, Wrinkle (Crackle) all in 150 cc. or 400 cc. or 800 cc. carriage paid, per push-button self-priming can. Also durable, heat and water resistant Black Matt finish (300p. self-priming can only). The carriage paid.

SPECIAL OFFER: I can plus optional transferable snap-on trigger handle (value 30p) for 90p. carriage paid. Choice of 13 self-spray plain colours and primer (prior car query) also available. Please enclose cheque or crossed P.O. for total amount direct to:

Dept: M4 YUKAN, 307A, EDWARDS ROAD, LONDON, W2 1EN

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Open all day Saturday, Closed Thursday afternoon

LADDERS

VARNISHED TIMBER LADDERS from manufacturer. Lowest prices anywhere. 15½ ft. extd. £6.20, 17ft. ext. £6.50, 20ft. ext. £7. 21½ ft. ext. £7.75, 24½ ft. ext. £8.90, 29ft. ext. £10.25, 31½ ft. triple ext. £12.25, 36ft. triple ext. £16. Carr. 80p. Free lists. Also Aluminium Ext. & Loft Ladders. Callers welcome.—(Dept. W.L.S.) Home Sales, Baldwin Road, Stourport, Worcs. Tel: 02-995 2574. Placing order on C.O.D.



TELEVISION AND RADIO TRAINING

(DAY ATTENDANCE COURSES)

This private College provides theoretical and practical training in Radio & TV Servicing. Courses of one years' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Radar and Radio Transmission are also available following the TV course. Write for prospectus to:—
London Electronics College, Dept B/4, 20 Penywern Road, Earls Court, London, S.W.5
 Tel. 01-373 8721

R.T.E.B. Certs., City & Guilds. Colour TV, Radio, Computers, Radio Amateurs' Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—FREE. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, Dept. 137K, Aldermaston Court, Reading RG7 4PF.

A.M.S.E. (Elec.), City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on 'Satisfaction or Refund' terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio & TV, etc. Send for full details and illustrated book—FREE. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, Dept. 168K, Aldermaston Court, Reading RG7 4PF.

MEN! You can earn £50 p.w. Learn Computer Operating. Send for FREE brochure—London Computer Operators Training Centre, C94 Oxford House, 9-15 Oxford Street, London, W.1.

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

SITUATIONS VACANT

Radio Operators

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1971 and subsequent years.

Specialist training courses lasting approximately 8 months are held at intervals. Applications are now invited for the course starting in September 1971.

Salary Scales

During training with free accommodation provided at the Training School:

Age 21	£848 per annum
22	£906
23	£943
24	£981
25 and over	£1,025

On successful completion of course:—

Age 21	£1,073 per annum
22	£1,140
23	£1,207
24	£1,274
25 (highest age point)	£1,351

then by 6 annual increments to a maximum of £1,835 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad.

Applicants must be United Kingdom residents normally under 35 years of age at start of training course, and must have at least 2 years operating experience or PMG qualifications. Preference given to those who also have GCE 'O' level or similar qualification. Exceptionally well qualified candidates aged from 30-40 may also be considered.

Interviews will be arranged throughout 1971.

Application forms and further particulars from:

RECRUITMENT OFFICER (TRO 37)

Government Communications

Headquarters,

Oakley, Priors Road,

CHELTENHAM, Glos. GL52 5AJ

Tel: Cheltenham 21491 Ext 2270

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON SW8

SITUATIONS VACANT

(continued)

FIELD/BENCH ENGINEER required for Hi-Fi firm in Wimbledon. Must drive. Good salary and prospects. Please telephone 01-540 6545.

EAGLE INTERNATIONAL require Audio Engineers; excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact Mr. Morrow 01-636 0961.

SERVICE SHEETS

SERVICE SHEETS. Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. **TELRAY, 11 Maudland Bank, Preston.**

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each, Manuals from 50p.

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

C. CARANNA

71 BEAUFORT PARK LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

SERVICE SHEETS

(continued)

TRADER SERVICE SHEETS

30p. each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND LONDON WC2

Make	Model	Radio/TV

1970 List now available at 10p. plus postage

If list is required indicate with X

From

Address

enclose remittance of..... (and a stamped addressed envelope) s.a.e. with enquiries please

MAIL ORDER ONLY (February PW)

RADIO, TELEVISION over 3,000 models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London W.6. SHE 8441.

RADIO/TV SERVICE SHEETS and MANUALS

S.A.E. with enquiries please. Mullard Valve and Semiconductor Data Book, 25p. Mazda Valve and Tube Data Booklet, 25p. Brimar Valve and Teletubes Data List, 20p. Resistor Colour Code Indicator, 15p.

BELL'S TELEVISION SERVICES Albert Place, Harrogate, Yorks HG1 4QA Tel. 0423-86844

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 15p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex.

METAL WORK

METAL WORK: All types cabinets, chassis, racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

Queen's Award to Industry

A PROUD DAY FOR REDIFON

THE Queen's Award to Industry for 1970 was formally presented to Redifon Limited and Redifon Air Trainers Limited on June 8 by Field Marshal Sir Gerald Templer, Her Majesty's Lieutenant for Greater London.

New marine radio telephone

MARINE Division has introduced a new SSB radio-telephone for operation in the marine 2 MHz band. It is designed to satisfy all current and future international regulations covering the phasing out of DSB transmissions, and to meet type approval.

TEST ENGINEERS

£1144-£1500+

Continuing expansion means we need more test engineers with the practical experience and real technical knowledge to work on the alignment and testing of HF and VHF equipment.

Theoretical and practical experience of semi conductors, SSB and frequency synthesis will be a great advantage.

Age is not important, since initial earnings will be directly related to experience.

You could start at £1144, but with more experience this could be in excess of £1500.

Benefits include Pension, Life Assurance, 3 weeks holiday. Ring or write with brief details to: Norman Manion, REDIFON LIMITED, Broomhill Road, Wandsworth, London SW18. 01-874 7281

REDIFON

A Member Company of the Redifuson Organisation



Redifon

REDIFON LTD. has won an order from Cable and Wireless to supply radio transmitting and receiving equipment for a new ground-to-air service in the Seychelles, where an airport is under construction for the first regular air service to the islands by land-based aircraft. Valued at over £25,000, contract also includes the provision of transmitters for a radio beacon which, while operating in the aeronautical

A NEW MILITARY RADIO STATION

A NEW 100 watt SSB (single sideband) military radio station, developed by the Communications Division is now in quantity production and delivery of an order valued at £136,000 for the Royal Air Force has already been completed.

RECEIVERS & COMPONENTS

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards **50np** + 7np P. & P. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for **£1. P. & P.** 18np. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board + components. 2 boards (4 x OC28) **50np** + 6np P. & P.

9 OAS, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for **£1** + 25np P. & P.

LARGE CAPACITY ELECTROLYTICS
1000MFD 30V }
16000MFD 12V } **40np** + 6np P. & P.
or **£3.50** per doz. Carr. 50np

250 MIXED RESISTORS **62np**
‡ & ‡ watt.

150 MIXED HI STABS **62np**
‡, ‡ & 1 watt 5% and better.

EXTRACTOR/BLOWER FANS (PAPST)

100 CFM 2800 RPM 4 1/2 in x 4 1/2 in x 2 in. Ideal for kitchen extraction, instrument cooling, etc., etc. **£2.5** + 25np P. & P. 240V AC 50Hz.

DIODES ex EQPT; SILICON
1 Amp 1000 PIV. 4 for **50np.**
20 Amp 150 PIV. 4 for **£1.** + 5np P. & P.

BARGAIN RELAY OFFER
Single pole change over silver contacts. 25V to 50V. 2.5kΩ coil. 8 for **50np.** + 5np P. & P.

KEYTRONICS mail order only
52 EARLS COURT ROAD,
LONDON W8 **01-478 8499**

5 WATT R.M.S. I.C. (10 WATT^{PEAK}) PA246 £2.49

Complete with amplifier details inc. how NOT to damage them through misuse

LOW NOISE HIGH STABS

‡ watt 5%, all E24 values from 4.7Ω to 10MΩ. 3 for 5d (2p). min. 2 dozen.

P. & P. on all orders 6p.

**MANY BARGAINS
SEND FOR LISTS
CHROMASONIC ELECTRONICS**

56 Fortis Green Road, London, N.10.

AERIAL BOOSTERS

We make four types of r.f. high gain transistorized pre-amplifiers:

Wideband Radio Type L10 £2.50

This covers the Medium and Short Wave.

V.H.F. F.M. Radio Type L11 £3

This covers the V.H.F. radio band.

V.H.F. Television Type L12 £3

Please state Band and I and III.

U.H.F. Television Type L45 £3

Tunable over the U.H.F. band.

S.A.E. for Details.

VALVE BARGAINS

Any 5-45p; 10-60p; 100-25.50; ECC82
ECL80, EF80, EF85, EF183, EBF89, EB91,
EY86, PCC84, PCC89, PC97, PCF80,
PCF86, PCL82, PCL83, PCL84, PCL85,
PL36, PY35, PY81, PY82, PY801, PY800,
30L15. Postage & packing 10p.

7 day Money Back Guarantee.

VELCO ELECTRONICS

62 Bridge St, Ramsbottom, via Bury,
Lancs.

Kits for P.W. CONSTRUCTIONAL ARTICLES

Amateur Bands Communications Receiver £25.85, p.&p. 35p.
(All 3-parts available separately). **Wide Range R.F. Detector** £9.64,
p.&p. 18p. **Signal Injector Tracer** £3.95, p.&p. 18p. **Trojan Top Band
Transceiver** (excluding o/p and matching transformer and speaker)
£35.56 p.&p. 35p. Kits also available for **Hi-Z Voltmeter** and **Workshop
Oscilloscope**

F. & B. ELECTRONICS 5, Staple Inn, Holborn Bars, W.C.1

Stella Nine Range Cases

Manufactured in Black, Grey, or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

LIST OF PRICES AND SIZES

Width	Depth	4" Height	6" Height	7 1/2" Height
6 1/2"	3 1/2"	90p	£1.05	£1.23
6 1/2"	4 1/2"	96p	£1.23	£1.40
8 1/2"	3 1/2"	£1.05	£1.40	£1.40
8 1/2"	6 1/2"	£1.40	£1.74	£2.00
10 1/2"	7 1/2"	£1.88	£2.28	£2.45
12 1/2"	3 1/2"	£1.40	£1.74	£2.03
12 1/2"	5 1/2"	£1.85	£2.25	£2.43
12 1/2"	8 1/2"	£2.30	£2.74	£2.93
14 1/2"	3 1/2"	£1.65	£2.03	£2.25
14 1/2"	9 1/2"	£2.73	£3.50	£3.65
16 1/2"	6 1/2"	£2.45	£2.93	£3.24
16 1/2"	10 1/2"	£3.15	£4.05	£4.45

Cases—Post 25p. per order.

Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2 1/2" Walls

6" x 3"	33p	10" x 7"	51p	14" x 3"	44p
6" x 4"	34p	12" x 3"	40p	14" x 9"	84p
8" x 3"	39p	12" x 5"	45p	16" x 6"	64p
8" x 6"	46p	12" x 8"	64p	16" x 10"	95p

Chassis—Post 15p. per order.

Discounts available on quantities.

E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD

STOCKPORT - CHESHIRE

Tel: 061-480 2179

A CORNUCOPIA OF COMPONENTS!

Scarce valve, selected T.V. components, Speakers, Cabinets, Computer panels—long leads NOT printed circuits. Transistors, resistors—new and recovered. State requirements. S.A.E. (F.S.) for details. MAILMART, 6 Eastbourne Road, Pevensey Bay, Sussex.

MICROCIRCUITS

709	47p	741	85p	PA230	92p
PA234	87p	PA237	£1.57	D40C1	87p
SL402A	£1.80	MEL11	47p	DIL Conn.	30p
7410	28p	7420	28p	7430	28p

TRANSISTORS

ME0402	21p	ME0412	30p	ME4101	11p
ME4102	12p	ME6101	15p	MP8111	35p
2N5172	9p	2N4059	15p	2N3085	65p

RECTIFIERS

1N4001	7p	1N4003	9p	1N4005	12p
1N4002	8p	1N4004	10p	1N4006	14p
FL4002	10p	PL4003	11p	PL4004	12p
W005	37p	W02	40p	PD40	62p

40583 Diac Trigger Diode 28p

JEF ELECTRONICS (P.W.S.),

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only. C.W.O. P.&P. 5p per order, Overseas 40p. Money back if not satisfied.

BRAND NEW COMPONENTS by return. Electrolytics 15 or 25V 1-10 mfd. 3.5p; 20-100 mfd. 4p; Mylar Film 100V 001, 002, 005, 01, 02 2p; 04, 05, 1 2.5p; Mullard miniature Carbon Film Resistors E12 Series 1/2 W. 10-10MΩ 8 for 5p. Postage 5p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

EX-GOVT. COMMUNICATIONS RECEIVERS, calibrators, signal generators, components, etc., with money back guarantee. SAE list. Callers welcome, please phone first.—P. R. Gollidge, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

£5 TELEVISIONS £5

Delivered anywhere in Great Britain

17" 12 channel. Complete & tested. Good working order. Carriage and ins. £1

17" Untested T.V.s 12 channel **£1.50** Carriage **£1.** All makes.

TUBES! TUBES!

Guaranteed 6 months

17" (48/88 only)	£1.50
19" All makes	£2.00
25"	£2.50
19" Bonded	£3.50
28" Bonded	£4.50

Plus 50p carriage

SPAKERS PK 3 ohm perfect ex-T.V. (minimum order two 6" round, 8" by 2" rectangular, 4" by 4" oval—12ip each. Add 7ip per speaker postage and packaging.

VALVES EX EQUIPMENT

EB91	5p	EY86	17p	PCF80	71p	PY81	15p
EB99	12p	80ZL13	80p	PC89	12p	PY800	15p
OC828	18p	680L2	18p	POL85	22p	PY83	71p
EC180	71p	80L16	18p	PCL84	17p	PY83	22p
EF90	18p	80P4	18p	PCL82	17p	U191	17p
EF85	18p	PC97	17p	PCL88	17p	6P28	17p
EF183	18p	PCF80	17p	PCL83	18p	30PL1	22p
EF184	18p	PC84	71p	PL36	22p	80P12	90p
				FL81	17p	80P5	15p

On two valves or more 5p postage and packing.

UHF TUNERS TO SUIT FERGUSON 850 900 Chassis **£2-50p.** P. & P. 50p

Dept. T.S.

THORNBURY TRADE DISPOSALS

Thornbury Roundabout, Leeds Rd., Bradford. Telephone 665670

COMPLETE RANGE of receivers by Trio, Lafayette, Hallicrafters, etc. Chassis, panels, cabinets, S.A.E. for lists. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263 7829.

WANTED

CASH PAID for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS,** 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

WE BUY New Valves and Transistors. State price: **A.D.A. MANUFACTURING CO.,** 116 Alfreton Road, Nottingham.

WANTED
(continued)

WANTED NEW VALVES, televisions, radiograms, transistors, etc. **STAN WILLETTS**, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

TOP PRICES PAID for NEW VALVES popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

HIGHEST CASH PRICES for Tape Recorders, 9.30-5. Immediate quotations. 01-472 2185.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return
WILLIAM CARVIS LTD.
103 North Street, Leeds 7

HOME IMPROVEMENT

THE FACTS

You will find them all in **PRACTICAL HOUSEHOLDER HOMEOWNER'S ANNUAL 1971**, out now. This tenth, and latest, edition is chock-a-block with expert advice on ways of improving the comfort and value of your home. There are up-to-the-minute instructions on decorating your home, beautifying it with mirrors, choosing colour schemes, reducing noise, installing central heating and many more useful and fascinating articles. **PRACTICAL HOUSEHOLDER HOMEOWNER'S ANNUAL** saves you time, money and trouble. You'll wonder how you managed without it!

PRACTICAL HOUSEHOLDER HOMEOWNER'S ANNUAL 1971

128 Big-value picture pages packed with money saving ideas

OUT NOW 25p

BRAND NEW AR88D COMMUNICATIONS RECEIVERS. AC mains input 110 volts or 250 volts. Frequency in 6 bands 535 kc/s up to 32 megs, output impedance 200-500 ohms. Complete with crystal filter noise limiter B.F.O. HF tone controls. Price £80 including spare set of valves, headphones and manual.

COMPUTER BOARDS Min 30 transistors and diodes and rods, etc. 10 boards at 50p plus 12p p.p.; 25 boards at £1.12 plus 22p p.p.

BARGAIN PARCELS 14lb at £1.46 plus 32p p.p.; 28lb at £2.76 plus 52p p.p.; 56lb at £4.50 plus £1.25 p.p. Contain pots, Res. Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £225. Lucky Dip Service.

FURZILL BEAT FREQUENCY OSCILLATOR 0-10 kc/s, 110/250 volt. Good condition complete with spares. £5.50 plus £1.25 p.p.

VHF Receiver, Type 715, less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tunable 12 volt input, not tested; complete with valves and speaker. £3 plus £1 p.p.

VHF AERIAL TUNING UNITS consisting of the following: 1" x 500 microammeter; 1 small 2-gang 75 pF capacitor. 1 various large wattage resistors for dummy load. Pair gears B.N.C. type sockets. Will tune 10 mtrs with 25/30 watts R.F. input. Size only 5 1/2" x 4 1/2" x 5" Sealed. Price £1.97 plus p.p. 25p

CRYSTALS AS NEW: Hc 6u, 5,345; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,500; 2,295 Kc/s and 10 x J465 Kc/s. 50p each plus 8p. p.p.

SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS: 10% tolerance & 1 watt. Preferred values in packets of 10. Our price 50p per 100, 50p per 200, £1.35 per 300, 500 at £2.12. Our selection. p.p. 8p per 100 and 2p per extra 100.

TRIMMER BARGAINS. These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details; Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice. Trimmers without Xtal—80p per doz. plus 17p p.p. Trimmers with Xtal—75p per doz. plus 17p p.p. Also 20 PF min. brand new air-spaced. 50p per doz. plus 17p p.p.

HRO MIX IN NEW CONDITION with 5 general coverage coil units including spare set of valves less power supply. Tested £25 p.p. £1.50.

ANY HEIGHT AERIAL TUBULAR SECTIONS 1/2 dia x 3 ft. long. Brass screw in type, copper coated and painted. New 20p each, p.p. 5p. Minimum order 6.

SIGNAL GENERATORS OSCILLATOR No. 2. Size 12in. x 8 1/2in. x 9in. Ideal for VHF work. 20-80 Mc/s. Functions are AM/CW. Deviation up to 40 Kc/s. RF meter. Measuring levels: RF output 1 microvolt to 100 microvolts set. Mod-set carrier controls. Good condition with accessories: 230V AC 12V DC. £30 plus 75p p.p.

R209 RECEIVER AM/CW/FM 1-20 mc/s, four bands vernier tuning, 12 volt D.C. Input tested and working. Price £15, p.p. £1.

AERIALS NEW CONDITION. Whip type 4ft. 25p, 11ft. 62p, 14ft. 77p. Used condition 4ft. 20p, 14ft. 52p. All collapsible type p. and p. 4ft. 10p, rest at 17p. Bases for above 25p, p.p. 2/6. New matching unit coax connection for above 30p, p.p. 5p.

Huge release of valves for the 62 set TX/RX, in original rubber packing consisting of QV04/7 x 61M, ABE12 etc, 10 valves in all at the bargain price as seen. 87p plus 17p p.p.

New Headphone and Mike rubber muff type. Low impedance. 87p. p. & p. 17p.

Magnetic Transducers new, price 87p post and packing 10p.

New Aerial Wire on boards 7/22 uncovered. Length 75ft. 40p, 90ft. 47p, 100ft. 55p, p.p. 12p.

New small fuse boxes 250 volts 15 amps. 87p each post and packing 15p.

Headphones, ex Gov. DLR No. 5 high impedance New 87p 17p p.p. Used condition 62p 17p p.p.


Meters moving coil ex equipment, good condition. Also 20 amp DC, 40 amp DC, and RF Therm-Couple Meters 0-1 amp and 0-2.5 amp, 2in. diameter. 50p post and packing 25p.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY


A. H. THACKER,
Radio Dept.,
HIGH STREET, CHESLYN HAY,
Nr. Walsall, Staffs.

Fingers

The more 'fiddly' the job, the more you depend on your finger-tips. Make sure minor burns and blisters don't rob them of their skill. Apply **BURNEZE**, pronto! This unique scientific aerosol cools the heat out of a burn in just 8 seconds, anaesthetizes pain, reduces swelling. **BURNEZE** - the clever tip for burnt finger-tips. From chemists.

 **Potter & Clarke Ltd**
Croydon CR9 3LP

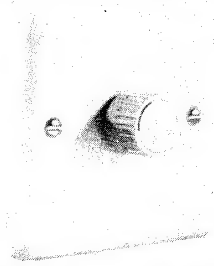Vary the strength
of your lighting with a
DIMMASWITCH



The **DIMMASWITCH** is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the **DIMMASWITCH** matches modern electric fittings. The bright chrome control knob activates an on-off switch and controls 40-600 watts of all lights except fluorescent at mains voltages from 200-250 V. 50 Hz. The **DIMMASWITCH** has built-in radio interference suppression. Price: £3-20 plus 10p post and packing. Kit Form: £2-70 plus 10p post and packing. Please send C.W.O. to:-

DEXTER & COMPANY
1 ULVER HOUSE, 19, KING STREET,
CHESTER CH1 2AH Tel: 0244-25883,
As supplied to H.M. Government Departments,
Hospitals, Local Authorities, etc.

Please mention
PRACTICAL WIRELESS
when replying to
advertisements

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office
When sending cash with order, please include 12p net in £ for postage and handling
MINIMUM CHARGE 12p net. No C.O.D. orders accepted

PLEASE NOTE THAT THE VALUES OFFERED BELOW ARE NOT NECESSARILY OF U.K. ORIGIN

PLEASE NOTE THAT ALL PRICES ARE IN DECIMAL PARTS OF £, I.E. IN NEW PENCE

Retail Shop
65 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANgham 8403
Open all day Saturday

0A2	0.38	6A95	0.55	6BW6	0.65	10C2	0.50
0A3	0.48	6A93	0.35	6E1	0.51	10D1	0.55
0B2	0.35	6AR6	0.40	6E5	0.50	10D2	0.40
0B3	0.60	6AS5	0.35	6E6G	0.30	10P1	0.90
0C3	0.38	6AS7G	0.30	6E11	0.38	10P9	0.50
0D2	0.35	6B76	0.30	6E13	0.33	10P13	0.45
0E2T	0.38	6AUG	0.25	6E14	0.65	10L1	0.45
1C1P1	6.00	6AV6	0.30	6E15	0.65	10LD11	0.60
1L4	0.20	6AW8A	0.55	6E18	0.45	10P13	0.55
1E4	0.35	6B6A	0.25	6E23	0.60	10P14	1.10
1R5	0.25	6B6E	0.30	6E24	0.75	12A8B	0.60
1R8	0.27	6B75	0.80	6E25	0.75	12A0C	0.40
1S5	0.25	6B76	0.50	6E26	0.50	12A15	0.45
1T4	0.25	6B76	0.45	6E29	0.60	12A06	0.45
1U4	0.27	6B76	0.45	6E34	0.20	12A70	0.40
1V5	0.60	6BK7A	0.55	6E50T	0.30	12A77	0.33
1Y2	0.45	6B85	0.43	6E77	0.45	12A76	0.30
1Y2B	0.40	6E96	0.40	6E60T	0.55	12A77	0.30
2D21	0.25	6BQ5	0.25	6K7	0.25	12A7V	0.33
3A4	0.35	6B85	0.65	6K8G	0.35	12A7V	0.50
3B2S	2.15	6B87	1.30	6K25	0.75	12A7X	0.30
3B3P1	2.75	6B76	0.55	6L6GT	0.45	12A77	0.70
3Q4	0.40	6B77	0.70	6L7	0.40	12B44	A0.55
3R4	0.35	6B76	0.25	6L18	0.45	12B46	0.35
3V4	0.45	6B26	0.35	6L20	0.60	12A77	0.70
4A40Y	0.60	6C4	0.32	6N7GT	0.40	12B26	0.85
5U4G	0.33	6C5CT	0.40	6P1	0.10	12B17	0.40
5U40B	0.42	6CA4	0.28	6P28	0.65	12B7V	0.55
5V4G	0.42	6B76	0.35	6R7	0.60	12A06	0.45
5Y3GT	0.32	6C36	0.30	6S47	0.40	12K7G	P0.35
5Z3	0.50	6C0D6A1.15	0.87	6S7	0.35	12Q7Q	0.30
6Z45	0.40	6C67	0.50	6S8K7	0.35	12S17	0.35
6Z912	0.75	6C16	0.35	6L7GT	0.35	1487	0.80
6A4B	0.45	6C16	0.50	6S8N7G	0.35	20D1	0.45
6A4FA	0.50	6C24	0.63	6S2Q	0.40	20L1	1.10
6A70	0.40	6C75	0.43	6S8K7	0.40	20L1	0.50
6A7H	0.50	6C75	0.45	6S7	0.40	20P4	1.10
6A8J	0.30	6D3	0.45	6U4GT	0.60	2P5	1.20
6AK5	0.80	6D08	0.75	6U5A	0.40	2P5C	0.60
6AK6	0.57	6D08	0.75	6X4	0.55	2L8G	0.45
6AL3	0.43	6D08	0.85	6X3GT	0.55	2Z24G	0.40
6AL5	0.20	6D84	0.75	6X8	0.55	2Z26G	0.65
6AM5	0.32	6E4S	0.58	6Y6G	0.65	30A1	0.45
6AM6	0.33	6E4S	0.58	6Y6G	0.65	30C3	0.65
6AQ5	0.35	6E77	0.35	6Y6W	0.50	30C4	0.65

First Quality Fully Guaranteed



ELECTRONIC VALVES

30C15	0.80	85A2	0.40	DK96	0.42	KCC84	0.30
30C17	0.85	90AG	2.40	DL96	0.42	KCC85	0.40
30C18	0.75	90AV	2.50	DM100	0.45	KCC88	0.40
30F5	0.85	90C1	0.60	DY86	0.33	KCC89	0.50
30FL1	0.70	90CV	1.25	Y78	0.35	KCC91	0.20
30FL2	0.33	807	0.50	DY902	0.50	KCC189	0.60
30FL14	0.75	812A	2.50	ES8C2	0.65	KCP80	0.35
30L1	0.40	813	3.75	E130L	0.45	KCF29	0.35
30L15	0.85	866A	0.75	E180F	0.95	KCF86	0.65
30L17	0.80	864S	0.65	EAB08	0.65	KCP804.1.50	
30P12	0.80	8080	1.50	EAF42	0.35	KCH81	0.30
30P13	0.80	6146	1.50	EBC33	0.50	KCH85	0.40
30P13	0.75	6590	1.25	EBC41	0.55	ECH84	0.45
30P14	0.90	6939	2.15	EBC81	0.50	ECL90	0.40
35A3	0.55	7199	0.75	EBF30	0.45	ECL81	0.45
35C4	0.75	7360	1.80	EBF83	0.40	ECL82	0.35
35B5	0.65	7686	1.25	ECP89	0.30	ECL85	0.65
35C5	0.40	7895	1.25	EC53	0.50	EM34	0.60
35D5	0.70	9002	0.35	EC68	0.55	EM51	0.60
35L5GT	0.50	9603	0.50	EC88	0.60	ECL86	0.40
38W4	0.30	AZ1	0.45	EC90	0.33	ECLL90	
35Z3	0.60	AZ1	0.55	EC91	0.50	1.50	
35Z40	0.30	CB11	0.80	EC92	0.25	EP37A	0.60
35L5GT	0.40	CB15L	0.90	EC98	0.50	EF39	0.40
38A5	0.70	CV1	0.35	EC9010	3.25	EP40	0.50
50B5	0.45	DAF96	0.45	EC94	0.45	EF41	0.65
50C5	0.40	DF96	0.42	ECCS1	0.33	EF42	0.70
50CDDG15	0.45	DK32	0.55	EC92	0.25	EY83	0.40
50LACT0.50	0.50	DK92	0.50	ECC83	0.30	EF83	0.55

EP85	0.35	EY88	0.43	PCL88	0.90	U78	0.30
EP86	0.30	EZ40	0.45	PCL800	0.33	U191	0.75
EP89	0.28	EZ41	0.65	PCL801	0.70	U201	0.35
EP91	0.33	EZ80	0.25	PD500	1.50	U281	0.40
EP92	0.40	EZ81	0.28	PF86	0.60	U282	0.40
EP96	0.30	EY21	0.60	PF815	0.85	U301	0.40
EP97	0.65	GZ30	0.40	PFL2000.75		U403	0.50
EP98	0.65	GZ31	0.33	PL33	0.35	U404	0.40
EP183	0.30	GZ32	0.48	PL36	0.55	U61	1.00
EP184	0.35	GZ33	0.70	PL51	0.50	UABC80	
EP800	1.00	GZ34	0.80	PL82	0.45		
EP804	1.25	HABC800.45		PL83	0.45	UAF41	0.35
ER30	0.30	HK90	0.35	PL84	0.40	UAF42	0.55
EL33	1.25	K786	2.05	PL802	0.80	UBC41	0.50
ELK40	0.50	K788	2.00	PL604	0.80	UBC81	0.40
EL36	0.50	N78	1.45	PL608	0.90	UBF80	0.40
EL27	1.25	PABC800.40		PL609	1.30	UBP89	0.25
EL41	0.55	PC88	0.60	PL659	1.30	UBL1	0.50
EL42	0.58	PC88	0.60	PL801	0.80	UBL21	0.60
EL81	0.55	PC97	0.60	PMS4	0.50	UC92	0.35
EL83	0.42	PC90	0.48	PY31	0.30	UC85	0.40
EL84	0.25	PC84	0.40	PY80	0.35	UC89	0.55
EL85	0.43	PC88	0.40	PY81	0.30	UC89	0.40
EL86	0.40	PC88	0.55	PY82	0.30	UC89	0.75
EL90	0.35	PC88	0.50	PY82	0.30	UC89	0.75
EL88	0.85	PC189	0.55	PY88	0.35	UC81	0.35
EL360	1.15	PC808	0.85	PY88	0.40	UC81	0.80
EL303	1.00	PC806	0.80	PY600	1.00	UC82	0.25
EL301	0.65	PC828	0.90	PT800	0.50	UC83	0.50
EL222	0.30	PC828	0.35	PY801	0.50	UF41	0.60
EL250	0.75	PC818	0.55	PZ30	0.35	UF42	0.60
EM34	0.90	PC96	0.60	QQV2-6.215		UF43	0.60
EM40	0.40	PCF80	0.60	QQV02-9.0		UF43	0.60
EM51	0.60	PCF801	0.60	1.25		UF85	0.40
EM84	0.35	PC808	0.75	QQV02-20A		UF89	0.35
EM85	1.00	PC808	0.70	5.25		U141	0.65
EM87	0.55	PC808	0.70	TT21	2.65	U171	0.55
EN91	0.35	PCH2000.75		TT22	2.80	UM84	0.20
EV31	0.40	PCL81	0.50	U18/20	0.75	UM18	0.50
EV30	0.45	PCL82	0.35	U28	0.75	U171	0.55
EV41	0.60	PCL83	0.55	U38	0.75	UY4	0.45
EY83	0.55	PCL84	0.45	U31	0.45	UY82	0.50
EY85	0.40	PCL85	0.40	U32	1.50	UY85	0.90
EY87	0.43	PCL86	0.45	U75	0.30	W39	0.60
				U76	0.30	Z80A	0.90

TRANSISTORS

2N404	0.17	2S034	1.00	BC159	0.15
2N444A	0.25	2S102	0.40	BC175	0.25
2N606	0.20	2S104	0.50	BCY30	0.35
2N697	0.23	2S701	0.50	BCY33	0.25
2N698	0.40	2S702	0.50	BCY37	0.25
2N705	0.70	2S746	0.30	BCY72	0.20
2N706	0.15	AC113	0.15	BCW11	0.40
2N708	0.20	AC125	0.30	BD121	0.20
2N753	0.25	AC130	0.30	BD123	0.35
2N929	0.30	AC127	0.30	BF115	0.20
2N930	0.85	AC132	0.35	BF167	0.25
2N987	0.35	AC133	0.35	BF173	0.30
2N1131	0.40	AC150	0.35	BF184	0.25
2N1132	0.45	AC156	0.33	BF184	0.25
2N1184	1.25	AC157	0.20	BF185	0.30
2N1393	0.40	AC176	0.25	BF194	0.30
2N1802	0.25	AC176	0.25	BF195	0.15
2N1804	0.25	AC187	0.30	BF196	0.20
2N1805	0.25	AC188	0.30	BF197	0.20
2N1806	0.25	AC190	0.30	BFW87	0.30
2N1807	0.30	AC191	0.30	BFW88	0.25
2N1808	0.40	AC191	0.25	BFW89	0.23
2N1809	0.55	ACY20	0.20	BFW91	0.20
2N1813	0.25	ACY21	0.20	BFX88	0.25
2N1711	0.30	ACY22	0.15	BFY17	0.40
2N1755	0.75	AD140	0.80	BFY19	0.60
2N2147	0.45	AD149	0.50	BFY50	0.25
2N2160	1.25	AD161	0.35	BFY51	0.20
2N2217	0.40	AD162	0.35	BFY52	0.25
2N2218	0.40	AD174	0.25	BSY26	0.25
2N2219	0.45	AF115	0.30	BSY27	0.30
2N2869A	0.25	AF116	0.25	BSY28	0.30
2N2877	0.65	AF117	0.20	BSY65	0.20
2N2946	0.60	AF118	0.45	BSY95A	0.20
2N2965	0.40	AF125	0.25	OC18	0.75
2N2923	0.15	AF127	0.25	OC22	0.65
2N2924	0.15	AF178	0.40	OC23	0.60
2N2926	0.15	AF180	0.35	OC24	0.60
2N3052	0.50	AF181	0.35	OC25	0.40
2N3053	0.75	AF186	0.50	OC26	0.30
2N3133	0.55	AF229	0.40	OC28	0.60
2N3134	0.50	AF271	0.45	OC29	0.55
2N3291	0.20	ASV26	0.25	OC30	0.75
2N3292	0.15	ASV27	0.30	OC35	0.50
2N3293	0.15	ASV28	0.30	OC3	

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical
A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship
A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic
A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.
C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero
A.M.I.A.M.I.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production
Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional
A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General
C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education
Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT—SO COULD YOU

"My income has almost trebled... my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you... but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept D258, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



BIET

POST THIS COUPON TODAY

To: B.I.E.T., Dept D258, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name..... Age.....

Address.....

..... Occupation.....

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2.65 (£2.15s. 0u). PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES



HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

TRANSISTOR AMPLIFIERS

NEW RANGES NOW IN STOCK
(Leaflets Ref. Nos. 6 and 8)
Post etc. 20p

- 4-300 4 TR 9V 300mW £1.75
- 104 4 TR 9V 1V £2.12
- 304 4 TR 9V 3W £2.47
- 555 6 TR 12V 3W £2.75
- PA7 6 TR 16V 7W £3.62
- 608 6 TR 24V 10W £4.12
- 410 4 TR 28V 10W £4.97
- MPA12/3 6 TR 18V 12W £4.50
- MPA12/156 TR 36V 12W £5.25
- PZ30 9 TR 30V 20W £3.75
- PA25 10 TR (Sp) 25V £7.50
- P50 30V 40W £5.47
- PA50 12TR (Sp) 50W £9.50
- 100 100W with Power Supply £45.00
Post 45p

OPTIONAL POWER SUPPLIES

- P.500 Switchable (One or Two) for 104, 304 £2.62
- PS 20 Switchable (One or Two) for PA7 £3.47
- MU24/40 Switchable (One or Two) for MPA12/3 or MPA12/15 £4.50
- PZ5 for Z30 £2.97 or PZ6 for Z30 £3.97
- PZ8 for Z50 £2.97 Transformer £2.25
- P11 for 608 £2.87 P15 for 410 £2.62
- MU442 for 1 or 2 PA25 or 1 only PA50 £6.50

SINCLAIR PROJECT 60 PACKAGE DEALS

2xZ30 amplifier, stereo 60 pre-amp, PZ5 power supply, £19, Carr. 40p. Or with PZ6 power supply £21, Carr. 40p. 2xZ50 amplifier, stereo 60 pre-amp, PZ8 power supply, £21.50, Carr. 40p. Transformer for PZ8 £2.25 extra. Any of the above with Active Filter unit add £4.87 or with pair Q16 speakers add £16. Also new FM Tuner £23.

BUILD THIS VHF FM TUNER



5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.

Free Leaflet No. 3 & 7. TOTAL £6.97 p.p. 20p
Cabinet 100p, Decoder Kit £5.97, Tuning meter £1.75
Mains unit (optional) Model PS900 £2.47
Mains unit for Tuner and Decoder PS1200 £2.62


BUILD YOURSELF A QUALITY RADIO



Excellent printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in. speaker. Room filling power. Easy to build with terrific results. Two colour leather-sloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.
Total cost £6.98 p.p. 35p.
All parts sold separately.

Ask for leaflet No. 1.

HENELEC SELF-POWERED PRE-AMPLIFIERS

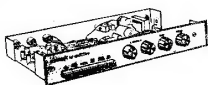

Designed for use with PA25 and PA50 Amplifiers. GOLD AND SILVER FINISH. Mains operated. Supplied with all plugs, etc. ADJUSTABLE OUTPUT UP TO 1 VOLT.

- ★ FET9/4. Mono with built-in mic-mixer. Accepts any ceramic or crystal cartridge. Plus tuner, tape, etc. Price £12.50 p.p. 20p.
- ★ FET154 STEREO (illus.). Magnetic cart. input, tuner, tape, etc. Beautiful stereo sound. Price £16.50 p.p. 25p

SLIM MODERN DESIGNS USING THE LATEST SILICON TRANSISTORS FET's and IC's. DIN SOCKETS, Etc. fitted. Self powered.

PUSH-BUTTON SELECTION. ±20dB BASS AND TREBLE BOOST & CUT
All inputs provided plus TAPE RECORD and REPLAY.

Also suitable for use with any power amplifier. Suggested types PA25, PA50, MPA12/3, MPA12/15

SIMPLICITY TO MOUNT—EASY TO USE—DESIGNED FOR QUALITY, PERFORMANCE AND PRICE
All units no soldering—just edge connectors and plugs AS SPECIFIED FOR MANY "PRACTICAL WIRELESS" 1970 PROJECTS

Electronic Components & Test Gear Centre
356 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre
354 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-402 5854

Electronic Organs, P.A. & Discotheque Centre
309 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-723 6963

Mail Orders. Special Bargain Shop, Industrial Sales
303 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-723 1008/9

OPEN 9 a.m. to 6 p.m. MONDAY TO SATURDAY — 9 a.m. to 1 p.m. THURSDAYS — OPEN ALL DAY SATURDAY

HI-FI TO SUIT EVERY POCKET



CHOOSE 100 STEREO FROM SYSTEMS and a complete range of individual units in stock—Demonstrations all day—visit our new HI FI Store. LOW CASH OR CREDIT/HP TERMS (Credit terms from £30 purchase—callers only).

FREE—Stock list No. 16 or 17 on request—BEST VALUE IN U.K.

HENRY'S LATEST CATALOGUE

Now 350 pages. WHY NOT SEND AWAY TODAY

- ★ COMPONENTS, TEST GEAR
- ★ EQUIPMENT, MODULES
- ★ SPECIAL OFFERS, etc. etc.

Everything for the constructor. Complete with 50p value discount voucher for use with purchase. Price 50p Post Paid.


- FREE 8 page Transistor, IC, Diode lists No. 36
- FREE 20 page Organs to Build brochure No. 9
- FREE Decks and Hi Fi Stock Lists No. 16/17
- FREE PA, Disco and Lighting List No. 18
- FREE Quotations for all Electronics—send list and S.A.E.

TEST EQUIPMENT FOR HOME, SCHOOL & PROFESSIONAL USE




- AF105 50k/volt multimeter (illus.). Price £8.50, p.p. 20p. Leather case £1.42.
- 200H 20k/volt. Price £3.87, p.p. 20p. Case 62p
- 500 30k/volt multi-meter. Price £8.87, p.p. 20p.
- Leather case £1.50.
- THL 33 2k/volt. Price £4.12, p.p. 15p.
- Leather case £1.15
- TE65 Valve voltmeter (illus.). Price £17.50 p.p. 40p.
- SE250B Pocket pencil signal injector. Price £1.75 Post Paid.

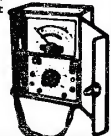- SE500 Pocket pencil signal tracer. Price £1.50 Post Paid
- TE20D RF generator Price £15, p.p. 40p
- TE22D Matching audio generator. Price £17, p.p. 40p.
- TE15 Grid dip meter. Price £12.50, p.p. 40p
- TO3 Scope 3" tube. Price £37.50, p.p. 50p.
- TE22 Audio Generator £17, p.p. 40p



NEW MINIATURE LOW COST AMPLIFIER

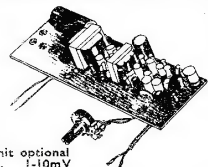


MODEL 4-300

9 volt operated or mains unit optional transformer (MT98 70p). 1-10mV adjustable sensitivity. PIP output for 3-8 ohms. Fitted volume control and leads. Size 5 1/2" x 1 1/2" x 1/2". Thousands of uses—takes magnetic, dynamic and crystal inputs direct. Output 300mW—very high gain—built in rectifier circuit.

PRICE £1.75 p.p. 15p
Complete with FREE leaflet No. 8.

STC TIME DELAY MODULE

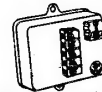

Ideal for experimenters, educational projects as well as for practical uses. Delay adjustable 3-15 secs. Operates 9-12 volts. Heavy Duty Relay Contacts. Complete with suggested applications sheet. Price £1.75 Post Paid.

GARRARD TAPE DECK




9 volt operated 2-speed tape deck fitted. Record/Replay 3 track. and Erase/Bias Cloc. Head. Complete with Oscillator/Record head circuit. Unit size 9" x 6 1/2" x 1 1/2" and 2 1/2" below motor board. Takes up to 4" spools. Supplied Brand New.

Price £9.97 P.&P. 35p 3 1/2" Tape 300" and spool 40p

25 WATT AND 50 WATT SILICON AMPLIFIERS

LOOK AT THE SPECIFICATIONS

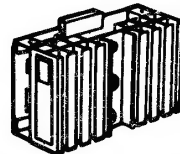- ★ At full power 0.3% distortion.
- ★ At full power—1dB 11c/s to 40 kc/s.
- ★ Response—1dB 11 c/s to 100 kc/s.
- ★ Rise time 2µ sec.
- ★ Short circuit proof plus limiting cct.



PA 25 10 transistor all silicon differential input 400mV sensitivity. 25 watts Rms into 8 ohms. Supplied with edge connector harness size 5" x 3" x 2".
PA 50 12 transistor version 50 watts Rms into 3 to 4 ohms. Size 5" x 3" x 4".
MU 442. Power supply or one or two PA 25 or one PA 50
PA 25 £7.50; PA 50 £9.50. MU 442 £6.00 P. & P. 20p each.