

# PRACTICAL WIRELESS

JULY  
1973

20p



**TREMOLO GENERATOR**

for  
**GUITARS**  
and

**ORGANS**


also:

**0-99 SECOND PROCESS TIMER  
EXTRA BANDS F.M. RECEIVER**
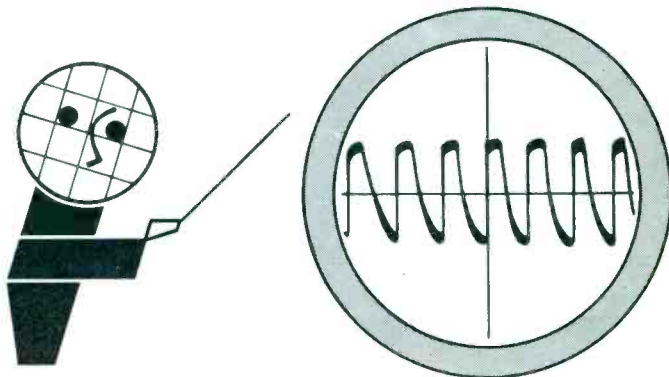
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
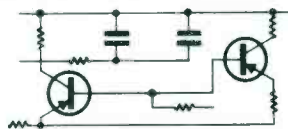
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**,  
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:  
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL73

**special free gift also to all our students**

# PRACTICAL WIRELESS

VOL. 49 NO. 3

ISSUE 797

JULY 1973

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

## EDITOR

Morris A. Colwell

## ASSISTANT EDITOR

Lionel E. Howes, G3AYA

## ART EDITOR

Peter Metalli

## TECHNICAL EDITOR

Eric Dowdeswell, G4AR

## PRODUCTION & NEWS EDITOR

Colin R. Riches

## SECRETARIAL

Jenny Maunder  
Jill Alflatt

Telephone 01-634 4292

## ADVT. MANAGER

Roy Smith

Telephone 01-634 4293

## CLASSIFIED ADVTs.

Colin R. Brown

Telephone 01-634 4301

## SUBSCRIPTIONS

Subscription Rates for one year to any part of the world £2.65 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477 Binders (£1-10) and Indexes (11p) can be supplied by the Binders Dept at the same address.

## BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

## COPYRIGHT AND QUERIES

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

## ● NEWS & COMMENT

216 FORMATIVE HABITS—Leader article and August preview

217 NEWS . . . NEWS . . . NEWS

229 TELEVISION—This month's attractions

230 PRODUCTION LINES—Products reviewed by Colin Riches

234 PRACTICALLY WIRELESS—Light hearted view by Henry

239 NEXT MONTH in Practical Wireless

254 ON THE AIR—Reports on Broadcast Bands

254 Short Wave—Malcolm Connah

257 Medium Wave—Charles Molloy

257 V.H.F./F.M.—Simon David

258 Amateur Bands, Short Wave/V.H.F.—David Gibson G3JDG

261 DEAR SIR—Readers' letters to the Editor

262 HOTLINES on recent developments—Ginsberg

## ● CONSTRUCTIONAL

218 EXTRA BANDS F.M. RECEIVER—F. G. Rayer

235 I.C. PROCESS TIMER (0-99 seconds)—G. H. Woods

240 TREMOLO GENERATOR for guitars and organs—R. Morgan

246 3-BAND TRANSMITTER, Part 2—V.F.O.—F. G. Rayer G3OGR

260 TAKE 20 No. 50 Electronic Siren—David Andrews

265 "P.W. TRICOLOUR" Mood Lighting System, Part 4—J. Budek

## ● OTHER FEATURES

225 MAGNETIC AMPLIFIERS, Part 1—I. R. Sinclair

233 I.C. OF THE MONTH, TBA435 Voltage Regulator—

L. A. J. Ireland

250 GOING BACK Equipment of yesteryear—

Colin Riches and Arthur Dow

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. Telephone: 01-634 4444.



# PACKAGE PRICE

# R.S.C. STEREO PACKAGE OFFERS

# HIGH FIDELITY UNITS

FOR ILLUSTRATED UNITS

**ONLY £39-99**

Carr. £1 00  
Or deposit £20-95  
and 9 monthly  
payments £4-92  
(Total £44-98)



R.S.C. A55 LOUDSPEAKERS

GARRARD 2025

LINEAR 505 AMP

Individual Rec. Retail Prices:

LINEAR 505 5 + 5 Watt Amplifier £18 25  
GARRARD 2025 Autochanger + K840A Cartridge £5 90  
Teak Veneer Plinth with Transparent Plastic Cover £10 92  
Pair A55 LOUDSPEAKERS (inc 8" x 5" 10,000 Gauss) £10 92  
**TOTAL £46 41**

**SEND S.A.E. FOR FREE COLOUR BROCHURE**

**SAVE £29-89**

MONARCH SPEAKERS

GOLDRING GL72

'SUPER 30' AMP

PACKAGE PRICE

**£108-25** Carr. £1-75

FOR ILLUSTRATED UNITS

Or deposit £15-00 and 12 monthly payments £8-78 (Total £120-86)  
GOLDRING GL72 Transcription Turntable + P.U.  
GOLDRING G800 Magnetic Cartridge  
DE-LUXE PLINTH with Roll-over Cover  
Pair R.S.C. MONARCH LOUDSPEAKERS  
R.S.C. SUPER 30 Mk III AMPLIFIER  
Total value of individual items listed above £138-14.

## FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT



Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround cone. Printed circuit cross-over assembly with ferrite cored coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc., and instructive diagrams, Frequency **£9-96** post Response 25 Hz-20 kHz. free Impedance 8-15 ohms

Or Dep. £2 & 9 mthly payments £1 02 7/11 £11 63/100

## SPIO1 HIGH FIDELITY PLAYER UNIT

Comprising Goldring G101 hi-fi single player unit fitted high fidelity free field magnetic stereo cartridge with diamond stylus. Belt driven Attractive design super-slim plinth and 'roll-over' transparent tinted plastic cover. Excellent value. Or Deposit £4-95 and **£34-95** Post 9 Monthly Payments of £3-75 (Total £38-70)

## RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. **COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £12-65** Carr. as illustrated £16-50 or dep. £2 and 9 monthly payments £1-88 (Total £18-92).



Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. **COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £12-65** Carr. as illustrated £16-50 or dep. £2 and 9 monthly payments £1-88 (Total £18-92).

## AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. **PLEASE STATE CHOICE.**

Exceptional performance at low cost.  
HF808T 8" 10W £2 88 HF120D 12" 15W £5 50  
HF102D 10" 10W £2 80 HF128 12" 15W £6 85  
HF120 12" 15W £4 95 HF126D 12" 15W £6 85



## FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality. In suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high tone response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω. **PLEASE STATE IMPEDANCE WHEN ORDERING: MODEL 803T 8" 15w. with parallel Tweeter. Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15. £3-70 £4-95**



## R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BML An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v and 90v, to battery range where A.C. mains 200/250v. 30c/s is available. **ASSEMBLED READY FOR USE £4-15**

## R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary. Primaries 200-250v. 50c/s. Screened

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.	
250v.-60mA, 6-3v. 2a	£1 10
250-0-250v.-60mA 6-3v. 2a	£1 16
FULLY SHROUDED UPRIGHT MOUNTING	
250-0-250v. 60mA, 6-3v. 2a, 0-5-6-3v. 2a.	£1 55
250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2 45
300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2 46
300-0-300v. 130mA, 6-3v. 4a. c.t., 6-3v. 1a.	£2 46
For Mullard 610 Amplifier	£2 95
350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2 46
350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2 95
425-0-425v. 200mA, 6-3v. 4a. c.t., 5v. 3a.	£5 49
425-0-425v. 200mA, 6-3v. 4a., 6-3v. 3a., 5v. 3a.	£5 49
450-0-450v. 250mA, 6-3v. 4a., c.t., 5v. 3a.	£5 60
450-0-450v. 250mA, 6-3v. 4a., c.t., 5v. 3a.	£6 00

TOP SHROUDED DROP-THERO TYPE	
250-0-250v. 70mA, 6-3v. 2a., 0-5-6-3v. 2a.	£1 49
250-0-250v. 100mA, 6-3v. 3-5a.	£1 71
250-0-250v. 100mA, 6-3v. 2a., 6-3v. 1a.	£1 75
250-0-250v. 80mA, 6-3v. 2a., 0-5-6-3v. 2a.	£1 81
200-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2 45
300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2 45
300-0-300v. 130mA, 6-3v. 4a., c.t. 6-3v. 1a.	£2 45
Suitable for Mullard 610 Amplifier.	£2 85
350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2 45
350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2 85
FILAMENT or TRANSISTOR POWER PACK	
6-3v. 3v. 1.5a. 55p; 6-3v. 2a. 60p; 6-3v. 3a. 85p;	
6-3v. 6a. £1 45; 12v. 1a. 61p; 12v. 3a. or 24v. 1.5a. £1 50; 0-9-18v 1 1/2a. £1 25; 0-12-25-42v 2a. £1 95.	

SELENIUM RECTIFIERS	
F.W. (Bridge) All output. D.C. input. Max. A.C. input 18v.	
1a, 28p. 2a, 39p. 3a, 55p. 4a, 72p. 6a, 88p.	
SMOOTHING CHOKES	
150mA, 7-10H, 250 Ω 77p; 100mA, 10H, 200 Ω 95p; 80mA, 10H, 350 Ω 95p; 60mA, 10H, 400 Ω 28p.	

## R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET

Only high grade components by leading manufacturers

- \* Push Button Selector Switching
- \* Jack Socket for Headphones
- \* Neon Indicator
- \* Satin Silver Finish Metal Fascia
- \* Solid State Circuitry
- \* Twenty Silicon Transistors
- \* Four Diodes, Four Rectifiers

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8 Ω. Frequency Response 7 Hz to 70 KHz ± 1/2 db.



**COMPLETE KIT (less cabinet). £27-50**  
Carr. 70p. Cabinet if req. £5 extra.

R.S.C. STEREO FM III TUNER, in cabinet. Visually matches Super 30 Mk. III **£37-50**

FACTORY BUILT UNIT INC. CABINET with 12 months' guarantee. Or Dep. £7 and 9 monthly payments £4-54 (Total £47-86). **£42-50**

## 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- \* Moderate size only 25 x 14 x 10in. approx.
- \* Response 30-20,000 c.p.s. Impedance 15 ohms
- \* Performance comparable with units costing considerably more Carr. 65p

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-60 and 9 monthly payments £2-64 (Total £28-36).



# RSC GROUP/DISCO UNITS



## PACKAGE OFFER

- Units listed below  
 (a) 100W POWER AMPLIFIER  
 (b) PAIR OF HI-FI HEAD-  
 PHONES  
 (c) MATCHING DYNAMIC  
 'MIKE' (attached to h'phone)  
 (d) PAIR 50 WATT SPEAKERS  
 Black Rexine covered  
 Cabinets Size approx.  
 18" x 18" x 8"  
 (e) RSC TDI DISCO CONSOLE

## RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 Mk.III turntables and Sospone of Acos Cartridges with diamond stylus. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vinyl covered Cabinet with lid. see illustration on left  
 Or Dep. £10 and 9 mthly pymts £8-80  
 (Total £71-80) Carr. £1-50

(a) (b) (c) (d) & (e) **£145**  
 Carr. £2-50

Terms Deposit £30 and 18 monthly payments of £8-00 (Total £174-00).

HEADPHONES MICROPHONE

TWIN TURNTABLE WITH PRE-AMP

## R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair  
 TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback howl characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £3 and 9 mthly payments £2-42 (Total £24-78) Carr. 65p. **£21-95**

TYPE C313 50 WATTS Low feedback characteristic. Fitted three 13" x 8" deep cone high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £5 and 9 mthly pymts £3-54 (Total £38-88) Carr. 85p. **£32-72**

TYPE C4100 100 WATTS inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx. 58 x 16 x 10" Acoustically filled and pressurised. Terms: Dep. £11 and 12 mthly. pyts. £5-80 (Total £80-80). **£71-50**

## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, Hum level -70dB. Response  $\pm 3dB$  30-20,000 c/s. All high grade components. Valves EP86, EP86, EC83S, EL34, EL34, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram. **£21-75**



Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. for mixing purposes. 200-250v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Twin-handled perforated cover £2-10. 12 MONTHS' GUARANTEE. Carr. 72p.

TERMS: Deposit £4 and 9 monthly payments of £2-27 (Total £24-43). Send S.A.E. for leaflet.

## LINEAR T40/60D 50W GROUP/DISCO AMPLIFIER

- ★ FULL MONITORING FACILITIES
- Individual Bass and Treble controls
- Twin Jack output sockets for speakers
- Input sockets for medium or high impedance Microphones or Guitar P.U.s and Crystal or Ceramic Gram. P.U.s
- ★ Frequency response 30-20,000 Hz.
- ★ Output overload protection plus double fusing
- FRONT PANEL (Jack inputs) Gram, Microphone/Guitar P.U. plus monitoring socket.
- CONTROLS Vol. (1) (2) (3) and (4), Bass, Treble, Master Vol., Monitor Selection Switch Gram (1) or (2), Mains Switch.

**£54-45** Carr. free  
 Or Deposit £7-50 and 9 monthly payments £8-00 (Total £61-80)




Simulated black rexine, plastic bonded metal case. ALSO STOCKED-LINEAR T80/100D £76-72

## FAL PHASE 50 MK.III AMPLIFIER 50 WATT.

Bold state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speakers 3 to 30 ohms. Size 17" x 7" x 7". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £7-25 & 9 monthly payments £8-82. Total £42-53. **£37-95** Carr. 82p.



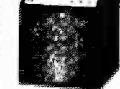
## RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker.



For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £8-95 and 12 monthly payments £4-89 (Total £67-63). Carr. Free S.A.E. for leaflet. UK Mainland **ONLY £59-95**
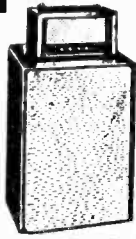
## RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting. ★ Two extra heavy duty 12in. 50w Loudspeakers. ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £15 & 9 monthly payments of £7-22. (Total £79-98.) Carr. £2 **£71-50**



## RSC GP30 HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group



A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £4-40 and 9 monthly payments of £2-75. (Total £29-15). **£25-85** Carr. 72p

NOW FIVE NEW BRANCHES  
**BOLTON** 23 DEANS GATE open shortly  
**NOTTINGHAM** 19/19A MARKET STREET  
**SUNDERLAND** 5 MARKET SQUARE  
**STOCKPORT** 8 LITTLE UNDERBANK  
**COVENTRY** 17 SHELTON SQUARE  
 NEW LARGER PREMISES AT HULL, DARLINGTON & NEWCASTLE See Addresses



HI-FI CENTRES LTD.  
 MAIL ORDERS & EXPORT ENQUIRIES TO:—  
 AUDIO HOUSE, HENCONNER LANE, LEEDS, 13. Tel: Pudsey (09735) 77631.  
 TERMS C.W.O. or C.O.D. No C.O.D. under £1. POSTAGE 89p EXTRA UNDER £2. 33p EXTRA OVER £2. 9p AS ORDER. TRADE SUPPLIED.  
 S.A.E. PLEASE WITH ENQUIRIES.  
 SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc.  
 MAIL ORDERS MUST BE SENT TO SHOPS

## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15" <b>£25-95</b> Dep. £8 and 9 mthly payments £2-49 (Total £28-41)	15" 60 Watt 14,000 gauss 8/15" <b>£14-75</b> Dep. £3-30 and 9 monthly payments. £1-50 (Total £18-80)	12" 50 Watt 13,000 gauss 15" <b>£11-99</b> Dep. £2 and 9 monthly payments £1-33 (Total £13-87) PAIR SUITABLE ALL PURPOSES

## FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free **£7-95** or Dep. £1-25 and 9 monthly payments 89p (Total £9-28).

## GROUP/DISCO EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK.III AMPLIFIER PR. FANE POP 25/2 25W L/SPEAKERS Terms: Deposit £7-50 and 9 monthly payments of £5-38 (Total £55-74) <b>£37-95</b> carr. £1-90 <b>£49-50</b> £1-10	F.A.L. PHASE 50 MK.III AMPLIFIER PR. FANE POP 60 L/SPEAKERS Terms: Deposit £10 and 9 monthly payments of £6-07 (Total £64-63) <b>£37-95</b> carr. £1-10 <b>£57-50</b> £1-10	F.A.L. PHASE 50 MK.III AMPLIFIER PAIR L12/20 25W L/S in cabinets Terms: Deposit £10 and 9 monthly payments of £6-52 (Total £68-88) <b>£37-95</b> carr. £1-35 <b>£61</b> £1-35	LINEAR T40/60D AMPLIFIER PAIR L12/20 SPEAKERS in Cabinets Terms: Deposit £10 and 9 monthly payments of £8-30 (Total £84-70) <b>£54-45</b> carr. £1-50 <b>£75</b> £1-50	F.A.L. PHASE 100 L/SPEAKERS 4 FANE POP 50 L/SPEAKERS Terms: Deposit £20 and 12 monthly payments of £8-63 (Total £123-58) <b>£89-85</b> carr. £1-76 <b>£110</b> £2
---	---	---	--	---

## HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH  
 L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50  
 Or deposit £4-50 and 9 monthly pymts. of £4-27. Total £42-93 **£37-95**

L12/20 12" 20-25 WATT 13,000 lines 15 ohms Dep. £2-50 & 9 mthly pymts £1-42 (Total £15-28) Carr. 65p. **£13-15**

L12/10 10-15 Watt vaneer finish cabinet 12" unit 8-15 ohm. Size approx. 14" x 14" x 9". Carr. 80p **£8-25**

CREDIT TERMS AVAILABLE ON PURCHASES OVER £8 (Kits Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

## R.S.C. Branches operate a 5-day week Open all day Saturday


- BRADFORD** 10 North Parade (Closed Wed.). Tel. 25349
- BOLTON** 23 Deansgate Tel: 33512 opens shortly
- BIRMINGHAM** 30/31 Great Western Arcade. Tel: 021-236 1279 (Closed Wed.)
- COVENTRY** 17 Shelton Square, The Precinct. Tel. 41361
- DERBY** 26 Osmonter Rd., The Spot (Closed Wed.)
- DARLINGTON** 19 Northgate (Closed Wed) Tel 68043
- EDINBURGH** 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
- GLASGOW** 326 Argyle St. (Closed Tues.). Tel. 248 4158
- HULL** 7 Whitefriargate Tel. 20505
- LEICESTER** 32 High Street (Closed Thurs.). Tel. 56420
- LEEDS** 5-7 County (Mecca) Arcade, Briggs (Closed Wed.). Tel. 28252
- LIVERPOOL** 73 Dale St. (Closed Wed.). Tel. 236 3573
- LONDON** 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629
- MANCHESTER** 60A Oldham Street, (Closed Wed.). Tel. 236 2778
- MIDDLESBROUGH** 106 Newport Rd. (Closed Wed.). Tel. 47096
- NEWCASTLE UPON TYNE** 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469
- NOTTINGHAM** 19/19A Market Street (Closed Thurs.). Tel: 48068
- SHEFFIELD** 13 Exchange Street (Castle Mark' Bldg.) (Closed Thurs.). Tel. 20716
- STOCKPORT** 8 Little Underbank. Tel: 480-0777.
- SUNDERLAND** 5 Market Sq. (Closed Wed.) Tel. 70573

TERMS Retail mail order subject to £1.00 minimum order.  
 Cash with order only. Trade and educational establishments  
 M/AC on application (minimum £5.00).  
 Postage 10p inland, 25p, Europe.  
 GUARANTEE: All goods carry full manufacturer's  
 warranty. Get in touch today for a complete  
 run-down of devices available from SCS (include SAE).



SCS COMPONENTS, P.O. Box 26,  
 Wembley, Middlesex HA0 1YY  
 The 'Professional' Amateur Supplier

## device of the month ZN414

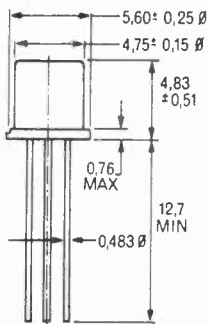


The Ferranti ZN414 is a complete a.m. radio circuit which operates from 1.1 to 1.8 volts and requires only battery, earphones and antenna plus a tuning capacitor and two decoupling capacitors. The ZN414 features: medium and long waveband, good stability on assembly, no setting up of IF coils, plus much more.

a complete a.m radio circuit for just

£1.20  
 +  
 VAT

## compatible device MFC 4000B

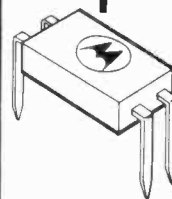

The Motorola 1/4-Watt Audio Amplifier is designed for the output stage of battery powered portable radios.

- \* 250 mW of Audio Output Power
- \* Low Standby Current—3.5 mA typical
- \* Low Harmonic Distortion
- \* Reduces Component Count in Portable Radios by Two Transformers and Two Transistors
- \* Eliminates Costly Component Matching Requirements


motorola 1/4 watt  
 audio amplifier  
 MFC 4000

50p  
 +  
 VAT
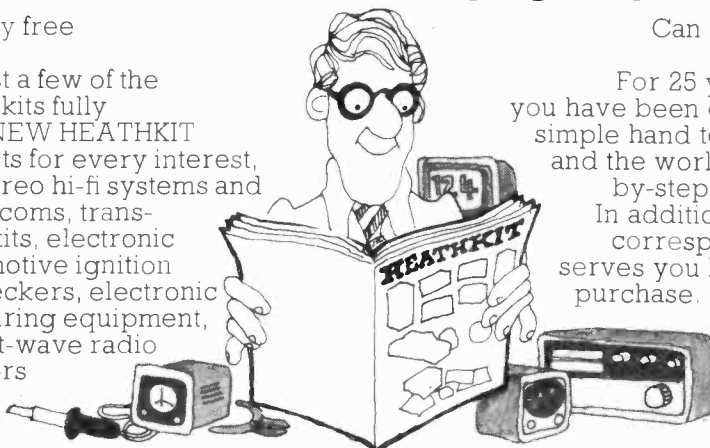
# We've written this book on kits

You can get a copy free

Below are just a few of the large selection of kits fully illustrated in the NEW HEATHKIT CATALOGUE - kits for every interest, every budget, stereo hi-fi systems and accessories, intercoms, transistor radios, tool kits, electronic calculators, automotive ignition analysers and checkers, electronic testing and measuring equipment, amateur and short-wave radio gear, metal locators - even a powerful battery charger.



Can you build a Heathkit?

For 25 years people just like you have been doing it - using a few simple hand tools, a soldering iron and the world-famous Heath step-by-step construction manual. In addition, a factory technical correspondence department serves you both before and after purchase. And, finally, building your Heathkit is fun, pure and simple ...

The coupon gets you started.



Please send me the FREE Heathkit catalogue

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

HEATH Dept. PW 07/73  
 Schlumberger Heath (Gloucester) Limited  
 Bristol Road, Gloucester GL2 6EE

## Another Great SHOPERTUNITIES Scoop!

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and **SEE** for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use. We're almost giving them away at only £18.50—mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! ★ Send quickly, after receiving goods test 7 days, refund if not delighted. Elegant black & chrome finish face, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer & sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. **VHF: FM/US, AM: LW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world!** Expensive **TURRET TUNER** side control waveband selection unit as expensive T.V.'s! Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries or direct through battery eliminator from 220/240V A.C. mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE 14ins x 10½ins x 4½ins overall approx.** Magnificently designed, made to give years of perfect service. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE**, manual with simple operating instructions & circuit diagram. **PLUS** Ultra sensitive earphone for personal listening. **ONLY £18.50** (with mains/battery eliminator £2 extra). **BOX, POST, ETC. 45p.—NO MORE TO PAY!** ★ **BUT WAIT**, for only 75p extra you get the sensational "**COMPUTERISED**" **WORLD TUNING GUIDE** (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K., when abroad. **NO GUESSING! NO MESSING!** **PLUS** Standard 'longlife' batteries. (Sorry—We cannot change these new radios for any earlier model purchased.)

## THOUSANDS OF MILES REDUCED TO INCHES? 1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! \*COMPUTERISED?

**THIS FANTASTIC  
EARTH SHRINKER**



YES, 24,901 miles  
SHRUNK TO ONLY 14 x 10½ x 4½  
inches approx?

**BRAND NEW  
FABULOUS ASTRAD 17**  
PORTABLE RADIO & COMMUNICATIONS  
RECEIVER



**WORLD WIDE  
RECEPTION  
& STATIONS POOR IN FRANCE  
FOUR CORNERS OF THE EARTH**

**28 TRANSISTORS  
AND DIODES!**  
**WAVEBANDS:**  
STANDARD LONG and MEDIUM  
**Plus 5 SHORT WAVEBANDS**  
**Plus ULTRA SHORT WAVES**  
(V.H.F. AM, FM, MW, LW, USW.)

**BATTERY MODEL £18.50** **BOX POST ETC. 45p**  
**MAINS/BATTERY ELIMINATOR £2 extra**

**FIRST TIME EVER!**  
\*NOW AVAILABLE WITH  
**fabulous "COMPUTERISED"  
WORLD TUNING GUIDE!**  
**NO MORE GUESSWORK**  
**INSTANT DATA** at your fingertips—  
enables you to **TUNE IN A FLASH!** to  
transmissions the world over!

**THIS OFFER ONLY FROM US!**

**BUY ONE FROM US!** **SAVE £21.60 NOW!**

**fabulous BRAND NEW SOLID STATE**

**BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER**

This equipment's got EVERYTHING!



**RECOMMENDED RETAIL PRICE £44**

**OUR PRICE £22.40** **CARR. ETC. 39p**

WITH REMOTE CONTROL MICROPHONE

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous **VHF, AM/FM Radio AND Cassette Tape Recorder & Player** combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V A.C. line cord.) Record & play back anything, anywhere! **RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE!** Wonderful features: ★ Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** ★ "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! ★ Separate ON/OFF and H.L.O. volume controls! ★ Heavy duty built-in speaker! ★ Earphone (for personal listening or "monitoring") and extension speaker sockets! ★ Remote control microphone! ★ Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes obtainable everywhere. **AND** the amazing built-in full circuit V.H.F. AM/FM Radio gives superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally, city and regional stations in every part of the country, plus B.B.C., National, V.H.F. Picks up dozens of foreign stations. **Fabulous in your car!** You could pay £££'s more for a Car Radio or Car Cassette player ALONE! £22.40, carr. etc. 39p.—**NO MORE TO PAY!** Complete with simple instructions, remote control microphone with optional microphone stand. **WRITTEN GUARANTEE.** Send quickly, after receiving goods test on mail order 7 day approval, refund if not delighted. Or call. **BONUS OFFER** Batteries and Cassette Tape 28p extra if required.

**FIRST TIME EVER! SAVE £15.21!**

**BRAND NEW AC/DC BATTERY/MAINS**

**Cassette TAPE RECORDER & PLAYER**

With remote control microphone.



**FIRST CLASS MAKERS**

**WE COULD CHARGE UP TO £26.97!**

**OUR PRICE £11.76** **POST ETC. 34p**

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! **NOW** a superb de-luxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £11.76!** Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the **BEST!** Expensive "**PIANO KEYBOARD**" **CONTROL PANEL** (or latest **MASTER SWITCH control**) and **AUTOMATIC LEVEL CONTROL**. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere.) **Amazing performance** ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—record anywhere, indoors or out! Runs on standard batteries **AND 220/240V AC** mains. Separate jacks for remote control microphone, etc. Size 9½in x 5½in x 2½in approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Recommended selling price £26.97!) **OUR PRICE ONLY £11.76, post etc. 34p.—NO MORE TO PAY!** ★ Send quickly, after receiving goods test on mail order 7 day approval—refund if not delighted. **BONUS OFFER** (one per customer)—Cassette tape, set of standard batteries **AND** microphone stand all for 55p extra, if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn store.)

**SHOPERTUNITIES LTD.**

Dept. WP/32, 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON, W12 8AQ (Thurs. 1, Late Night shopping Fri. 7).

Also at 37/39 HIGH HOLBORN (opp. Chancery Lane), LONDON, W.C.1 (Thurs 7 p.m.), BOTH OPEN MON TO SAT 9 A.M. TO 6 P.M.



# INTERFACE 73

is a Texas Instruments Technical Seminar

Enough said! So note the dates in your diary Tuesday June 12th, Wednesday June 13th, Thursday June 14th. Send this coupon now for the full INTERFACE 73 story and invitation. . . . To Texas Instruments Ltd., Seminar Centre MS21, Manton Lane Bedford MK41 7PA




## TEXAS INSTRUMENTS

Name

Company

Full Address

PW

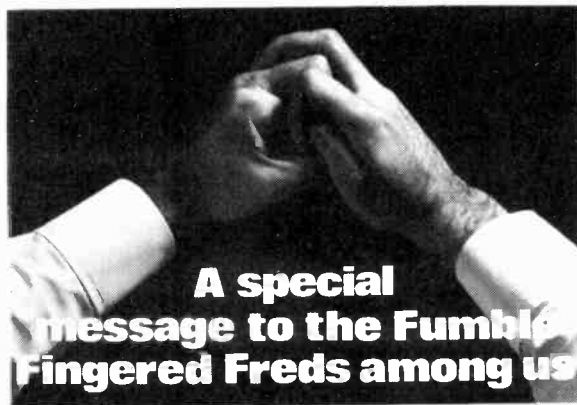

A special message to the Fumble Fingered Freds among us

## NEW STEPHENSPEAKERS

A new range of loudspeaker kits and cabinets with a style and specification for every purpose. You'll be cheating a bit if you tell your friends "made it myself". We supply superb craftsmen built fully finished cabinets in beautiful stain and scuff resistant vinyl in white or teak.

Just fit the speaker cloth (supplied) and screw in your speaker.

HIGH QUALITY AT LOW COST

Send for our free booklet "Choosing a Speaker"



STEPHENSPEAKERS, WILMSLOW AUDIO, Dept. 'PW', Swan Works, Bank Square, Wilmslow SK9 1HF

## VALVES

SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1-20. DAF96, DF96, DK96, DL96, 4 for £1-55.

1R5	-30	30FL12	-89	EBC90	-22	EY81	-36	PC185	-27	UAF43	-50
1S5	-25	30FL14	-65	EBF80	-32	EY85	-29	PCL84	-27	UBC41	-45
1T4	-20	30L1	-29	EBF83	-29	EY87	-29	PCL88	-80	UBF80	-34
3S4	-30	30L15	-70	EBF89	-29	EZ40	-39	PCL800	-89	UBF89	-32
3V4	-47	30L17	-70	ECC81	-20	EZ41	-89	PCL805	-37	UCB84	-32
5U4G	-31	30P4	-54	ECC82	-21	EZ80	-21	PEN A4	-77	UCC85	-25
5V4G	-35	30P12	-69	ECC83	-35	EZ81	-22	PEN36C	-70	UCF80	-20
6Y3GT	-30	30P19	-64	ECC85	-24	EZ90	-24	PL200	-46	UCH42	-53
5Z4G	-35	30PL1	-56	ECC804	-50	GZ30	-34	PL36	-48	UCH81	-20
6/30L2	-50	30PL13	-80	ECF80	-30	GZ32	-40	PL81	-43	UCL82	-22
6AM6	-16	30PL14	-80	ECH35	-55	KT41	-77	PL81A	-47	UCL83	-55
6AQ5	-24	35L6GT	-45	ECH42	-59	KT61	-65	PL82	-21	UF41	-52
6AT6	-20	35W4	-25	ECH81	-29	KT66	-78	PL83	-23	UF89	-20
6AU6	-20	35Z4GT	-25	ECH83	-38	LN319	-58	PL84	-20	UL41	-53
6BA6	-20	50CD6G	-68	ECH84	-35	LN329	-80	PL500	-58	UL84	-20
6BE6	-21	807	-55	ECL80	-30	LN339	-65	PL504	-58	UM84	-22
6BJ6	-41	AC/VP2	-77	ECL82	-29	N78	£1-05	PM84	-30	UY41	-29
6BW7	-50	B349	-70	ECL86	-35	PARC80	-31	PX25	-95	UY85	-23
6F14	-35	B729	-64	EF37A	-95	PC86	-44	PY32	-52	VP4B	-77
6F23	-68	CHL35	-67	EF39	-45	PC88	-44	PY33	-52	W77	-43
6F25	-50	CY31	-28	EF41	-57	PC96	-42	PV81	-25	Z77	-22
6J5GT	-20	DAF91	-25	EF80	-23	PC97	-25	PY82	-25		
6J7G	-24	DAF96	-38	EF85	-28	PC900	-29	PY83	-28	Transistors	
6V6GT	-28	DF91	-20	EF86	-30	PC884	-29	PY88	-33	AC107	-17
6X4	-30	DF96	-36	EF89	-28	PC885	-28	PY800	-31	AC127	-18
6X5GT	-28	DH77	-29	EF91	-18	PC888	-58	PY601	-31	AD149	-37
10F13	-53	DK91	-30	EF92	-30	PC889	-43	R19	-50	AP116	-20
12A7T	-20	DK92	-50	EP98	-70	PC1189	-48	R20	-70	AP116	-20
12AU7	-21	DK96	-45	EF183	-27	PC8805	-70	U25	-72	AF117	-20
12AX7	-22	DL92	-30	EF184	-29	PCF80	-26	U26	-64	AF125	-17
19BG6G	-75	DL94	-47	EH90	-36	PCF82	-33	U47	-73	AF127	-17
20F2	-67	DL96	-38	EL33	-65	PCF86	-48	U49	-70	OC82	-12
20F5	-24	EB31	-22	EL34	-50	PCF800	-28	U82	-31	OC45	-12
25L6GT	-19	DY87	-22	EL41	-54	PCF801	-28	U78	-30	OC71	-12
25U4GT	-57	DY802	-30	EL84	-23	PCF802	-29	U91	-55	OC72	-12
30C1	-26	EABC80	-32	EL90	-24	PCF805	-57	U93	-31	OC75	-12
30C15	-58	EAF42	-50	EL500	-62	PCF806	-56	U251	-61	OC81	-12
30C17	-78	EB91	-12	EM80	-38	PCF808	-65	U301	-58	OC8D	-12
30C18	-57	EBC33	-45	EM81	-38	PCL82	-20	U229	-66	OC82	-12
30F5	-24	EB341	-49	EM84	-26	PCL83	-65	U801	-75	OC82D	-12
30FL1	-65	EBC81	-30	EM87	-50	PCL84	-33	UABC80	-31	OC170	-23

## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

PRICES ARE INCLUSIVE OF VAT, ONLY POSTAGE IS EXTRA

Minimum post/packing on 1 valve 7p., on each additional valve, (3p. per. valve extra)

Any parcel insured against damage in transit 3p extra.





# 4 channel decoder modules

Tate 4-channel equipment decodes all quadrasonic matrix records and broadcasts and adds dimensional realism to ordinary stereo programme sources. It also controls 4-channel tapes when played through your system and CD-4\*\* records when used with a separate demodulator.

They are characterized by their ultra low distortion characteristics and six-pole wideband phase shift networks. These combine to produce an acoustic performance giving highly articulate sounds from the back as well as the front channels. The amplitude accuracy is better than  $\pm 1\text{dB}$  from 5Hz to 100KHz.

tate **2**




**High definition SQ\* quadrasonic decoder Fully built home constructor module** features: exclusive wide band phase shift network; distortion typically 0.04%. Ideal for use with other kit projects and even with the world's finest amplifiers.

Recommended retail price (excluding VAT) **£12.95**

Dimensions: 85 x 60 x 25mm

Operating Voltages: 18 - 30VDC at 11ma

tate **4**

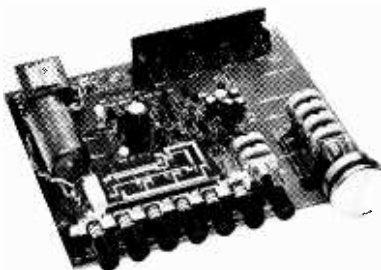

**High definition SQ\* quadrasonic decoder Fully built home constructor module** featuring **wide band** matrix decoding circuit board with integrated power supply, switching, master gain and exclusive rear level control.

Recommended retail price (excluding VAT) **£21.95**

Dimensions: 165 x 140 x 26mm

Operating Voltages: 110 - 240VAC at 3watts

## Specifications

Input Impedance	40K Ohms
Output Impedance	<300 Ohms
Phase Shift Network $90 \pm 10'$	20Hz-18KHz
Nominal Gain	Unity
Frequency Response $\pm 1\text{dB}$	5Hz-100KHz
Nominal Input Level	250mV rms
Nominal Distortion	0.025%
Clipping Point	2.5V rms
Distortion before Clipping	0.08% max.
Front Separation	>60dB
Rear Separation	>20dB

**Tate Audio Transmission Equipment Limited**  
5-7 Covent Garden Cambridge CB1 2HS England  
Telephone 0223 67873 Telex 81640

Reg. No. 105 9584

The only way to really understand the difference between ordinary stereo and SQ Quadrasonic sound is to hear it. However, if you remember the difference between mono and stereo upon hearing it for the first time, multiply the recollection of that experience by a factor of ten and you will be able to appreciate what is in store for you when you first hear SQ Quadrasonic sound.

Please send  **tate 2** at £14.25 each (including VAT)

**tate 4** at £24.15 each (including VAT)

I enclose cash/cheque/money order

Name (BLOCK LETTERS)

Address

PW73

\*TM CBS Inc. \*\*TM Victor Japan

# DUN G.W. SMITH & CO (RADIO) LTD

## TS60 POCKET MULTIMETER

High-precision at low-cost. Ranges: D.C. 15V, 150V, 1,000V (10,000 opt.), A.C. 15V, 150V, 100V (1,000 opt.), D.C. Current 150mA. Resistance 100k ohms. **£1.85. Post 15p.**



## AUDIOTRONIC MODEL ATM.1

Top value 1000 o.p.v. pocket multimeter. Ranges: 0/10/50/250/1000V. AC and DC. DC Current 0-1mA/100mA. Resistance 0/100k ohms. Decibels -10 to +22dB. 8 1/2 x 6 x 28mm. Complete with test leads. **£2.50. Post 15p.**



## MODEL 1092 TESTMETER

8,000 O.P.V. 0/5/15/150/300/1200 V. D.C. 0/6/30/300/600 V. A.C. 0/300µA/300 mA 0/10K/1 meg Ω. Decibels -10 to +16dB. **£2.75 each + 15p P. & P.**



## LT601 MULTIMETER

New style 20,000 o.p.v. pocket multi-meter. 5/25/50/250/500/2500 V. D.C. 10/50/100/600/1000V. A.C. 50µA/250mA. 6K/6 meg ohms. -20 to +22 dB. **£3.75. Post 20p.**



## MODEL TH-12

20,000 o.p.v. Overload protection. Slide switch selector 0/25/25/10/50/250/1000V. D.C. 0/10/50/250/1000V. A.C. 0/50µA/25/250mA. D.C. 0/3K/30K/30K/3 meg -20 to +60dB. **£4.97. Post 15p.**



## RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/20/250/1000V. D.C. 2.5/10/50/250/500/1000V. A.C. 10C Current 100mA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K/3M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. **OUR PRICE £25.97. P. & P. 25p.**



## HIKOI MODEL 730X

80,000 O.P.V. Overload protection. 8/30/60/300/600/1200 VDC. 12/60/120/600/1200 VAC. 60/µA/30 mA/300 mA. 2K/200K/2 megohms. -10 to +63dB. **£60. P. & P. 15p.**



## MODEL PL436

20k Ω/Volt D.C. 8k Ω/Volt AC. Mirror scale. 6/3/12/30/120/600 V. D.C. 3/30/120/600 V. A.C. 50/600µA/60/600 mA. 10/100K/1 Meg/10 Meg Ω -20 to +48dB. **£87. P. & P. 12p.**



## MODEL 500

30,000 O.P.V. with overload protection mirror scale 0/5/2.5/10/25/100/250/500/1,000V. D.C. 0/2.5/10/25/100/250/500/1,000V. A.C. 0/50µA/5/60/500mA. 12 amp. D.C. 0/60K/6 Meg/60 Meg Ω. **£28.87. Post paid.**



## HIKOI MODEL 750X

80,000 o.p.v. 43 ranges 0-0.3 to 1,200V D.C. 0.1 to 1,200V A.C. 0-3K/30 meg ohms. -10 to +17dB. **£8.97. Post 20p.**



## U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 667 o.p.v. 0/3/1.5/7.5/30/60/150/300/600/900 VDC and 70mV. 0/3/1.5/7.5/30/60/150/300/600/900 VAC. 0/300µA/1.5/6/15/60/150/600mA/1.5/6/15/60/150/600mA/1.5/6 AMP. A.C. 0/200 Ω/3K/30K Ω. Accuracy DC 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. **£9.50. P. & P. 25p.**



## HIKOI MODEL 700X

100,000 O.P.V. Overload protection. Mirror scale. 3/6/12/1.5/3/6/12/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600 1200 V. A.C. 15/30µA/3/6/30/60/150/300mA 6/12 AMP. D.C. 2K/200K/2 Meg/20 Meg ohm -20 to +63dB. **£18.50. P. & P. 20p.**




## MODEL C-7080 EN

Giant 6" mirror scale. 20,000 o.p.v. 0/25/1/2.5/10/50/250/1000V. D.C. 0/2.5/10/50/250/1000/5000V. A.C. 0/50µA/1/10/100/500mA/10 amp. D.C. 0/2K/200K/20 meg -20 to +60 dB. **£13.95. Post 30p.**


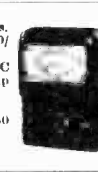
## 370 WTR MULTI-METER

Features A.C. current ranges. 20,000 o.p.v. 0/5/2.5/10/50/250/500 1000 V. D.C. 0/2.5/10/50/250/500/1000V AC 0/50µA/1/10/100mA/1/10 Amp D.C. 0/100mA/1/10 Amp AC 0/5K/50K/500K/5 MRΩ/50 MEG -20 +62dB. **£16. P. & P. 25p.**



## HT100B4 MULTI-METER

Features A.C. current ranges. 100,000 o.p.v. Mirror Scale, Overload protection. 0/5/2.5/10/50/250/500/1000 V. D.C. 0/2.5/10/50/250/1000 V. A.C. 0/10/25/50/125/250/500 MA/10 Amp. D.C. 10 amp. A.C. 0/2K/200K/2 MEG/20 MEG. -20 +62dB. **£12.60. P. & P. 25p.**



## KAMODEN 72 200 MULTIMETER

200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/0.08/3/3/30/120/600/1200V. D.C. 0/3/12/60/300/11,200V. A.C. 0/3µA/1.2mA/120mA/600mA/12A. D.C. 0/12A. A.C. -20 to +63dB. 0/2K/200K/2 meg/20 meg ohms. **£18.95. Post 30p.**



## THK LAB TESTER.

100,000 O.P.V. 6 1/2 in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K/Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000 V. A.C. Volts: 3, 10, 25, 50, 250, 500, 1,000V. D.C. Current: 10, 100µA, 10, 100, 500mA. 2.5, 10 amp. Resistance: 150, 10K, 100K, 10MEG, 100MΩ Ω. Decibels: -10 to +49 db. Plastic Case with Carrying Handle. Size: 7 1/2 in. x 6 1/2 in. x 3 1/2 in. **£18.95. P. & P. 25p.**



## Model S-100TR MULTIMETER TRANSISTOR TESTER

100,000 o.p.v. mirror scale/overload protection. 0/12/6/3/12/30/120/600 V DC. 0/6/30/120/600 V AC. 0/12/600µA/12/300mA/12 AMP DC. 0/10 K/1 MEG/100MEG. -20 to +50dB. 0-0.1-2 M.F.D. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. **£18.50. P/P 25p.**



## LB3 TRANSISTOR TESTER

Tests Ico and B. PNP/NPN. Operates from 9V battery. Complete with all instructions, leads and carrying handle. **£3.95. P. & P. 20p.**



## KAMODEN HM.350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and DC current. Amplification factor of PNP, PNP, transistors, diodes, SCR's etc. 4" x 4" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. **£12.50. Post 30p.**



## MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true A.C. beta in/out. Checks Ico. Checks diodes in/out. Checks SCR, etc. Beta H3 10 V. 500, Ico 2-50. Icbt 0-5000µA. 220/240 V A.C. operation **£17.50. Post 25p.**



## MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 330 ohms/Volt AC and DC. Accuracy 5% D.C. 1% AC. Scale length 165mm. 0/300/750µA 1.5/3/7.5/15/30/75/150/300/750mA 1/5/13/7.5/6MP DC 0/3/7.5/15/30/75/150/300/750mA 1/5/3/7.5/15/30/75/150/300/750V AC 0/75/150/300/750mV/1.5/3/7.5/15/30/75/150/300/750V DC 0/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out. Supplied complete with test leads, manual and test certificates. **£49.00. Post 50p.**



## TE-65 VALVE VOLTMETER

28 ranges D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. **£17.50. P. & P. 30p.** Additional probes available: R.F. £2-12; H.V. £2.50.




## KAMODEN HM. 720B F.E.T. V.O.M.

Input Impedance 10 meg ohms. Ranges: 0/25/1/2.5/10/50/250/1000V. D.C. 0/2.5/10/50/250/1000V. A.C. 0/25µA/2.5/25/250 MA. D.C. 1.5/20 to +62dB. 0/5K/50K/500K/5meg 500meg ohms. **£14.95. Post 30p.**


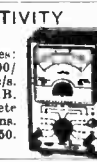
## TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0/0.003/1/3/1/30/10/30/300V. R.M.S. 4cps-1.2 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. **£17.50. Carr. 25p.**



## TMR MODEL 117 F.E.T. ELECTRONIC VOLTMETER

Battery operated, 11 meg input, 36 ranges. Large 4 1/2" mirror scale. Size 6 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0.3-1200V AC VOLTS 3-300V R.M.S. 8-0-800V P-P. DC CURRENT 12-12MA. Resistance up to 2000M ohm. Decibels -20 to +51dB. Complete with leads/instructions. **£17.50. P. & P. 20p.**



## MODEL L-55 FET V.O.M.

Input Impedance 10 meg ohms. 0/3/1.2/6/30/120/600V. D.C. 0/3/12/60/120/600V. A.C. 0/120µA/120mA. D.C. 0/1K/100K/10 meg/100 meg ohms. **£15.97. Post 15p.**



## KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1000 Meg ohms. 500 Volt Battery operated. Wide range clear meter 4 1/2" x 4". Complete with deluxe carrying case, batteries, instructions. **£19.95. Post 30p.**



## BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Size 18 x 200,000 Hz. Square 18 x 50,000 Hz Output max. +10 dB. (10 K ohms) Operation Internal batteries Attractive 2-tone case 7 1/2" x 2". Price **£17.50. Carr. 17p.**




## CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. IMP. Bandwidth 10MHz. Sensitivity at 100KHz VRMS/mm. 1-25; HOR. AMP. Bandwidth 500K Hz. Sensitivity at 100KHz, V R518/mm. 3-25; Preset triggered sweep 1-3,000µsec.; free running 20-200,000Hz in nine ranges. Calibrator plps. 220 x 300 x 430mm. 115-230V. A.C. operation. **£39.00. Carr. paid.**


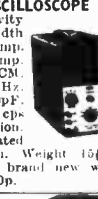
## TO-3 PORTABLE OSCILLOSCOPE

3in. tube. V amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 meg Ω 250V X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5cps-800KHz. Input Imp. 2 meg Ω 200V. Time base, 5 ranges 10 cps-300 kHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2lb. 220/240V. A.C. Supplied brand new with handbook. **£47.50. Carr. 60p.**



## RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5 mcs Pass Band Separator Y1 and Y2 amplifiers. Rectangular sin. x div. C.R.T. Calibrated triggered sweep from 2 µsec. to 100 milli-sec. per cm. Free running time base 50 cps-1 mcs. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual. **£87. Carr. Paid.**



## MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200KHz. Attenuator 0-111dB. 0-1dB step. Impedance 600 ohms. Max. Input power 30dBm. Size 180 x 90 x 25mm. **£12.50. Post 37p.**



## ARF-300 AF/RF SIGNAL GENERATOR

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine / square 10v. P-P. RF 100 KHz to 200 MHz. Output 1v. DC CURRENT 12-12MA. Resistance up to 2000M ohm. Decibels -20 to +51dB. Complete with instruction and leads. **£29.95. Post 50p.**





## UNR 30 RECEIVER



4 Bands covering 550 kc/s-30 mc/s  
FET, 8 Meter. Variable BFO for  
A.C. Brand new with instructions.  
Our Price **£15-75** Carr. 37p

## UR-1A RECEIVER



4 Bands covering 550 kc/s-30 mc/s  
FET, 8 Meter. Variable BFO for  
SBB. Built-in Speaker, Band-  
spread, Sensitivity Control, 220/  
240 v. A.C. or 12 v. D.C. 12 1/2 in. x  
4 1/2 in. x 7 in. Brand new with  
instructions.

Our Price **£25-00** Carr. 37p

## SKYWOOD CX203 RECEIVER



Solid state, 5 bands covering 200-  
420 KHz and 55 to 30 MHz.  
Illuminated slide rule dial. Band-  
spread, Aerial tuning, BFO, AVC,  
ANL, "8" meter, AM/CW/SS B.  
Integrated speaker and phone  
socket. 220/240 v. A.C. or 12 v.  
D.C. Size 325 x 266 x 150 mm.  
Complete with instructions and  
circuit.

Our Price **£32-50** Carr. 50p

## LAFAYETTE HA-600 RECEIVER



General coverage 150-400 kc/s, 550  
kc/s-30 mc/s, FET front end, 2  
mech. filters, product detector,  
variable B.F.O., noise limiter,  
8 Meter Bandspread, RF Gain,  
15in. x 9 1/2 in. x 8 1/2 in. or 12 v.  
220/240 v. A.C. or 12 v. D.C.  
Brand new with instructions.  
Our Price **£50-00** Carr. 50p

## TRIO 9R59DS RECEIVER



4 bands covering 550 kc/s to 30  
mc/s continuous and electrical  
bandspread on 10, 15, 20, 40 and  
80 metres. 8 valve plus 7 diode  
circuit. 4/8 ohm output and phone  
jack. SSB-CW, ANL, Variable  
BFO. 8 meter. Sep. bandspread  
dial. IF frequency 445 kc/s, audio  
output 1.5w. Variable RF and AF  
gain controls. 115/250 v. A.C.  
Size: 7 1/2 in. x 13 1/2 in. x 10 in.  
with instruction manual.

Our Price **£49-50** Carr. Paid.  
FULL RANGE OF TRIO STOCKED



## EMI LOUDSPEAKERS



Model 360. 13" x 8"  
with single tweeter/  
crossover. 20-20,000  
Hz. 15 watt RMS.  
Available 8 or 16  
ohms. £7-25 each.  
P. & P. 37p.  
Model 450. 13" x 8"  
with twin tweeter/  
crossover. 55-13,000  
Hz. 8 watt RMS.  
Available 8 or 16  
ohms. £8-62 each.  
P. & P. 25p.



## SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo book-  
shelf speakers. Delux  
streak veneer finish.  
Size 14 1/2" x 9"  
x 7 1/2". 8 ohms.  
8 watt RMS.

16 watt peak. Complete with DIN  
lead.

Our Price **£12-95** Carr. 50p

## HA-10 STEREO HEADPHONE AMPLIFIER



All silicon transistor  
amplifier oper-  
ates from mag-  
netic, ceramic or  
tuner inputs with  
stereo headphone  
outputs and separate  
volume controls for  
each channel. Oper-  
ates from 9v battery. Inputs  
5MU/100MU. Output  
50MW.

Our Price **£5-97** P. & P. 15p

## 1021 STEREO LISTENING STATION



For balanc-  
ing and gain  
selection of loud-  
speakers with addi-  
tional facility for stereo  
headphone switching.  
2 gain controls, speaker  
on-off slide switch, stereo head-  
phone sockets. 6" x 4" x 2 1/2".

Our Price **£2-25** P. & P. 15p

## MP7 MIXER PREAMPLIFIER



5 micro-  
phone inputs  
each with  
individual gain  
controls enab-  
ling complete mixing facilities.  
Battery operated, 9 1/2" x 5" x 3".  
Inputs: Mics: 3 x 3mV 50K; 2 x  
3mV 600 ohm. Phono meg. 4mV  
50K. Phono ceramic 100mV 1 meg.  
Output 250mV 100K.

Our Price **£8-97** P. & P. 20p

## HAND HELD 2-WAY WALKIE TALKIES

Industrial quality in robust metal  
cases. Battery operation. Volume  
and squelch controls. Call button  
and press to talk button. Tele-  
scopic aerial. Complete carrying  
cases.

2 channel **£52-50** Pair. Post 50p.  
300mW  
3 channel **£79-50** Pair.  
2 watt

Licence required for operation in  
U.K.

## HOMER INTERCOMS



Ideal for home,  
office, stores,  
factories, etc. Sup-  
ply and complete  
with batteries, cable and free  
instructions.  
2 Station **£2-97**, P. & P. 15p.  
3 Station **£5-25**, P. & P. 17p.  
4 Station **£6-62**, P. & P. 17p.

## FM TUNER CHASSIS



6 TRANSISTOR  
HIGH QUALITY  
TUNER  
ONLY  
6 x 4 x 2 1/2 in. 3 I.F. stages.  
Double tuned discriminator. Ample  
output to feed most amplifiers.  
Operates on 9V battery. Coverage  
88-108Mc/s. Ready built ready for  
use. Fantastic value for money.

Our Price **£5-95** P. & P. 12p

Stereo multiplex adaptors **£4-97**.

## SH628 STEREO HEADPHONES



Outstanding  
value. Soft  
ear-pads,  
adjustable  
headband.  
8-16 ohms.  
20-20,000  
Hz. Com-  
plete with lead and stereo plug.

Our Price **£1-87** P. & P. 30p

## TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive  
magnetic  
headset with  
soft earpads.  
Impedance  
2,600 ohms  
(d.c. 60  
ohms). Fre-  
quency response 200-4,000 Hz.

Our Price **£1-97** P. & P. 30p

## LHO2S STEREO HEADPHONES



Lightweight  
headphones  
with padded  
earpieces.  
4-16 ohms.  
20-20,000  
Hz. Com-  
plete with  
6 ft. cord and plug.

Our Price **£1-95** P. & P. 30p

## BH.001 HEAD SET AND BOOM MICROPHONE



Moving Coil. Ideal  
for language  
teaching, com-  
munications.  
Headphone imp.  
16 ohms. Micro-  
phone imp. 200  
ohms.

Our Price **£4-95** P. & P. 30p

## DH-085 DE-LUXE STEREO HEADPHONES



Features unique  
mechanical 2 way  
units and fitted  
adjustable lever  
controls. 8 ohm im-  
pedance 20-20,000  
cps. Complete with  
spring lead & stereo  
jack plug.

Our Price **£7-97** P. & P. 30p

## 4-CHANNEL STEREO HEADPHONES



TTC G3600.  
Soft vinyl  
covered head-  
cushion and  
earphones.  
Each ear-  
piece incor-  
porates two  
2" speaker units. Fitted 2/4 channel  
changeover switch. Impedance 4-16  
ohm. Frequency response 20-20,000  
Hz. Complete with 15 ft. coiled lead  
fitted two stereo plugs.

Our Price **£9-95** P. & P. 30p

Stereo multiplex adaptors **£4-97**.

## ROTEL BARGAIN!



Outstanding  
value. Soft  
ear-pads,  
adjustable  
headband.  
8-16 ohms.  
20-20,000  
Hz. Com-  
plete with lead and stereo plug.

Our Price **£6-75** P. & P. 30p

## ROTEL BARGAINS!



Soft leather  
ear cushions.  
Impedance  
8-16 ohms. 20-  
20,000 Hz. 15ft  
coiled lead.  
Brand new and  
boxed (List  
£9-95.)

Our Price **£6-75** P. & P. 30p

## STEREO AMPLIFIERS

RA310 15 + 15 watt **£24-95**  
RA610 32 + 32 watt **£21-95**  
RA801 40 + 40 watt **£22-95**  
RA1210 60 + 60 watt **£28-95**  
P. & P. 50p extra.

## AM/FM STEREO RECEIVERS

RX150 7 1/2 + 7 1/2 watt **£36-95**  
RX200 10 + 10 watt **£46-50**  
RX400 20 + 20 watt **£57-50**  
P. & P. 75p.

## UNREPEATABLE OFFER!



17+17 watts rms. Inputs for mag-  
netic and crystal phono, tuner,  
tape etc. Dual stereo speaker out-  
puts. Headphone socket. Full range  
of controls. (Rec. List Price **£59-50**)

## NIKKO TRM50 STEREO AMPLIFIER

Our Price **£39-95** P. & P. 50p



## AKAI BARGAINS

CASSETTE (P. & P. 50p)  
CR35D Deck **£44-45**  
CR85 Recorder **£57-75**  
CR85/CR88 Speakers **£67-95**  
GX40D Deck **£67-20**  
GX40 Recorder **£67-20**  
GX40T Deck/Receiver **£99-00**  
GX45 Deck **£78-25**  
GX46D Dolby Deck **£88-65**  
GX46 Recorder **£89-95**  
GX60D Deck **£87-65**  
GX65D Dolby Deck **£98-65**

CARTRIDGE (P. & P. 50p)  
CR81 Deck with amp. **£65-40**  
CR81D Deck **£55-80**  
CR81T Recorder/Receiver **£92-75**  
CR8088 4 channel Recdr. **£114-25**  
CR8088 4 channel Recdr. **£98-65**

TAPE (P. & P. 75p)  
4000D8 Deck **£59-95**  
4000D8 Dust Cover **£3-95**  
1721L Recorder **£80-35**  
X5000 Recorder **£82-50**  
X201D Deck **£108-20**  
GX220D Deck **£128-85**  
GX221D Deck **£138-40**  
GX280D Deck **£198-50**  
GX370 Deck **£211-50**

TAPE/CASSETTE (P. & P. 75p)  
GX1900D Deck **£144-50**  
TAPE/CARTRIDGE (P. & P. 75p)  
X1810D Deck **£138-40**

TAPE/CASSETTE/CARTRIDGE  
(P. & P. 75p)  
X20008D Recorder **£180-75**  
MICROPHONES (P. & P. 50p)  
ADM.11 Dynamic (pair) **£7-50**

STEREO RECEIVERS (P. & P. 75p)  
AA6300 20+20 watt **£81-95**  
AA8030 25+25 watt **£92-50**  
AA8080 40+40 watt **£117-50**  
AA8100 2 x 16 or 4 x 18 w. **£176-00**  
AA8500 65+65 watt **£160-50**

STEREO AMPLIFIERS  
(P. & P. 50p)  
AA5200 20+20 watt **£61-75**  
AA5500 30+30 watt **£78-50**  
AA5800 45+45 watt **£117-50**

STEREO TUNERS (P. & P. 50p)  
AT550 AM/FM **£60-50**  
AT580 AM/FM **£94-50**

4-CHANNEL UNIT (P. & P. 50p)  
S81 Synthesiser **£88-95**

SPEAKERS  
CR88 (pair) **£10-20**  
SW155 (each) **£51-00**

STEREO HEADPHONES  
ASB11 **£4-75**  
ASB20 **£7-30**  
ASB22 **£8-25**

## SPECIAL PURCHASE!

## FERGUSON EXPORT MODELS

FERGUSON 3408 STEREO  
TUNER AMPLIFIER  
Covers FM 88-108 MHz. Five push  
button tuning scales. 8+8 watts  
rms. Inputs for stereo ceramic  
cartridge and tape etc. Separate  
bass treble, balance and volume  
controls.

Our Price **£31-50** P. & P. 50p



FERGUSON 3416 STEREO  
TAPE DECK  
4 track. 7 1/2, 3 1/2 l.p.s. Stereo/  
mono record/play. 7" reels. Inputs  
for dynamic mikes, radio, gram.  
Complete with cover.

Our Price **£41-95** P. & P. 75p



# SAVE UP TO 33 1/3% OR MORE! GWS

## RECORD DECK PACKAGES



### Carriage and Packing 75p.

Complete units with Stereo cartridge ready wired in plinth cover.

GARRARD		
2025 TC/9TAHCD	£10.85	
SP25 111/G800	£15.95	
SP25 111/M44E	£16.45	
SP25 111/M44-7	£16.10	
SP25 111/M55E	£16.90	
SP25 111 Module/M75-6	£18.99	
AP76/G800	£23.95	
AP76/G600E	£25.95	
AP76/M44E	£24.95	
AP76/M55E	£25.85	
AP76/M75ED	£31.70	
AP76/M75EJ	£27.85	
AP76 Module M75-6	£26.95	
AP96 Module M75-6	£30.40	
ZERO 1008 Module/M93E	£41.85	

B.S.E. McDONALD		
210/SC7M	£6.85	
MP60/G800	£15.50	
MP60/TPD1/G800	£15.20	
MP60/M44-7	£16.40	
HT70/TPD1/G800	£18.80	

GOLDRING		
GL72/G800	£30.90	
GL75/G800	£33.80	
GL75/G800E	£36.75	

GOODMANS		
TD100/G800 Teak	£46.85	
TD100/G800 White	£48.80	

LEAK		
Delta/M75-6	£43.95	

PHILIPS		
GA105/GP200	£13.80	
GA150/GP200 Teak	£20.90	
GA150/GP400	£45.25	
GA308 (Less cartridge)	£23.95	
GA308 P.U.	£32.75	

PIONEER		
PL12D (Less cartridge)	£29.90	
PL16C (Less cartridge)	£41.25	
PL41D (Less cartridge)	£95.25	
PL50 (Less cartridge)	£39.90	
PL61	£102.75	
PLA35	£68.80	

THORENS		
TD160C/Ortofon M15E		
Super	£62.50	
TD125 AB/11/Ortofon		
M15E Super	£96.95	

WHARFEDALE		
Linton/M44-7	£23.70	

## RECORD DECKS



### Carriage and Packing 50p

B.S.E. McDONALD		
C114 Mini	£3.95	
C129 Mono	£5.50	
C137	£7.90	
G10/TPD1	£13.95	
610	£9.90	
610/TPD1	£14.85	
710	£19.20	
810	£24.50	
710/810 Plinth and Cover	£3.35	
MP60	£7.85	
MP60/G800	£10.25	
MP60/TPD1	£12.60	
MP60/TPD2	£11.25	
H770	£10.97	
HT70/G800	£13.60	
HT70/TPD1	£15.95	

CONNOISSEUR		
BD1 Kit	£3.65	
BD1 Chassis	£10.75	
BD1/SAU2/Plinth/Cover	£26.15	
BD2/SAU2/Chassis	£22.70	
BD2/SAU2/Plinth/Cover	£26.75	

GARRARD		
2025 T/C Stereo	£6.40	
SP25 III	£8.50	
SP25 IIII Acos GP104		
Ceramic	£5.50	
SP25/M75-6	£13.90	
AP76	£15.40	
SL65B	£11.15	
SL72B	£17.75	
SL95B	£25.25	
401	£23.60	
ZERO 100A	£30.80	
ZERO 100S	£27.95	

GOLDRING		
G99	£16.85	
G101P/C	£16.85	
GL69/2	£15.75	
GL72	£17.95	
GL72/P	£25.20	
Plinth 69/72	£5.85	
LID 72	£2.70	
GL75	£23.75	
GL76P	£29.30	
Plinth 75	£5.35	
LID 75	£2.97	
GL85P/C	£49.50	

THORENS		
TD125 II	£52.15	
TD125AB II	£78.55	
TX20	£5.30	
TD180A/II	£29.25	
TD180C	£43.95	

## PLINTHS AND COVERS

Carriage and Packing 50p		
Budget SP25 etc.	£3.95	
Budget 401/arm	£11.35	
Budget AP76/Zero 1008	£3.95	
Budget B.S.R.	£2.95	
Garrard WB1	£2.20	
Garrard SPC1	£2.20	
Garrard WB4	£2.25	
Garrard SPC4	£2.55	
BME2000 System	£26.40	

## SPECIAL GARRARD OFFERS!



4 speed autochanger unit fitted with stereo ceramic cartridge.  
**Our Price £4-95 Carr. 50p**



SP25 MK.II. 4 speed single record player fitted with Acos GP104 stereo ceramic cartridge.  
**Our Price £8-50 Carr. 50p**

## SINCLAIR PROJECT 60 PACKAGE DEALS



- 2 x Z30 Stereo 60/PZ5 £15.95 P. & P. 37p.
- 2 x Z30 Stereo 60/PZ6 £18.00 P. & P. 37p.
- 2 x Z50 Stereo 60/PZ8 £20.25 P. & P. 37p.
- Transformer for PZ8 £3.65.
- Active Filter Unit £4.45.
- Pair of Q16 Speakers £10.70
- Project 60 FM Tuner £14.95
- Sinclair Project 605 £20.97 P. & P. 37p.

All other Sinclair Products in stock  
2000 Amplifier £22.95  
3000 Amplifier £28.95  
2000/3000 Tuner £26.30  
Q830 Speakers £23.98 pair  
P. & P. 50p each of above items

## AUDIOTRONIC RANGE OF HIGH QUALITY EQUIPMENT



### ACP-8 8 TRACK CAR PLAYER

Attractive black and silver finish. 12v neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp. Complete with speakers, mounting brackets and instructions.

**ONLY £12-50 P & P 40p**



### ACR1 PUSH BUTTON CAR RADIO

Push button tuning of one LW and five MW stations of your choice. 12v pos. or neg. earth. Complete with speakers, mounting brackets and instructions.

**Our Price £8-95 P & P 50p**

### AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 16 1/2" x 8" x 3 1/2". AC 200/250v.

**PROCESS TWO**  
For use with cassette and tape recorders. Freq. res. 30Hz-20KHz ± 2dB. Off tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.

**Our Price £34-50 P & P 50p**



### LOW NOISE TAPE CASSETTES

Top Hi-Fi quality in library cases			
TYPE	5	10	25
C060	£1.29	£2.53	£5.99
C80	£1.85	£3.62	£8.59
C120	£2.29	£4.48	£10.68
P. & P. 15p.			post free




### ACR 3500 CAR RADIO

Manual tuning of Medium and Long waves. 12v pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

**Our Price £6-50 P & P 50p**

### ACA 55E ELECTRIC CAR AERIAL

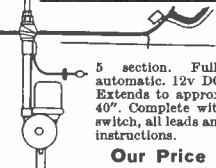

5 section. Fully automatic. 12v DC. Extends to approx. 40". Complete with switch, all leads and instructions.

**Our Price £5-95 P & P 50p**



**PROCESS FOUR**  
For use with semi-professional tape recorders. Freq. res. 30Hz-20KHz ± 2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

**Our Price £50-00 P & P 50p**

## MONATONE 6750 SYSTEM



AM/FM 4+4 watt stereo tuner amplifier, Garrard 2025 T/C, plinth and cover, stereo cartridge pair of matching speakers.

**Our Price £30-50 P & P £1-00**

## ALBANY HOUSE AM 108 SYSTEM



8+8 watt amplifier, Garrard SP25, plinth and cover, G800 cartridge, pair of Medway T138 speakers.

**Our Price £52-75 P & P £1-25**

## VAT

All prices are subject to 10% VAT (10p in the £)

**10% VAT**

Order with confidence by post - but remember to add 10% VAT (10p in the £) to total value of goods including carriage/packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY.

## SEND LARGE S.A.E. FOR FULL HI-FI DISCOUNT LIST

# G.W.SMITH & CO (RADIO) LTD

ALL MAIL ORDERS TO:  
11-12, PADDINGTON GREEN, LONDON W2 1LG. Tel: 01-262 6562  
PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

<b>CENTRAL LONDON</b>			
267, B. Tottenham Court Rd. W. 1	Tel: 01-580 0670	311, Edgware Road, W. 2	Tel: 01-262 0387
10, Tottenham Court Rd. W. 1	Tel: 01-437 2232	282, Edgware Road, W. 2	Tel: 01-223 4194
27, Tottenham Court Rd. W. 1	Tel: 01-636 3715	152/3, Fleet Street, E. C. 4	Tel: 01-353 2893
57, Tottenham Court Rd. W. 1	Tel: 01-580 3739	378, Harrow Road, W. 9	Tel: 01-286 9530
21, Old Compton Street, W. 1	Tel: 01-437 9369	<b>ESSEX</b>	
3, Little Street, W. C. 2	Tel: 01-437 8204	86, South Street, Romford.	Tel: Romford 20218
34, Little Street, W. C. 2	Tel: 01-437 9155	<b>SURREY</b>	
118, Edgware Road, W. 2	Tel: 01-723 9789	1048, Whitgift Centre, Croydon.	Tel: 01-881 3027
193, Edgware Road, W. 2	Tel: 01-723 6211	27 & 29, Eden Street, Kingston.	Tel: 01-948 7945
		32, Hill Street, Richmond.	Tel: 01-948 1461

### ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

Buy it with Access

**CREDIT TERMS FOR CALLERS (£50 and over)**

ALL EQUIPMENT IS BRAND NEW, FULLY GUARANTEED AND OFFERED WITH FULL AFTER SALES SERVICE

All items and prices are correct at 22-5-73 but subject to change without notice. E & O. E.



# The X25

## Why two shafts?

220-240 Volts or 100-120 Volts.

### Model X25

The leakage current of the X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live".

Tested at 1500v A.C. 25 watt. Fitted long-life iron-coated bit 1/8"

2 other bits available 3/32" and 3/16"

Price: £1.75 (rec. retail) P & P 8p



# "elementary"



One ceramic shaft to give you near-perfect insulation and negligible leakage current (only 3-5 microamps) so that you can safely solder delicate and expensive integrated circuits and transistors, even when "live"

Another shaft, of stainless steel, to give you the strength required of an everyday robust general purpose iron. Plus large volume long-life bits to store the enormous heat-capacity of the 25 watt element. Bits that do not stick (no screws or pins) and bits that slide over the element shaft to give you efficient heat transfer and a capacity equivalent to irons of 2-3 times the wattage.



### MODEL CCN

220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage.

Test voltage 400v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64".

PRICE: £1.95. P&P 5p



### MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder"

PRICE: £2.05 (rec. retail).

P&P 12p

### MODEL G

18 watt miniature iron, fitted with long life iron-coated bit 3/32" Voltages 240, 220 or 110.

PRICE: £1.95 (rec. retail). P&P 5p



All prices mentioned are exclusive of V.A.T.

### MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64", to 3/16". Voltages 240, 220, 110, 50 or 24.

PRICE: £1.75 (rec. retail). P&P 5p

### MODEL CN2


Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.

PRICE: £1.75 (rec. retail). P&P 5p

### MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, and "How to Solder" booklet.

PRICE: £2.60 (rec. retail), P&P 8p

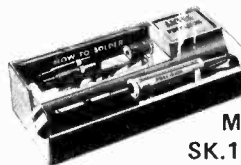

### MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE: £2.95 (rec. retail), P&P 12p



From radio or electrical dealers, car accessory shops or in case of difficulty direct from:—  
**ANTEX LTD. FREEPOST**  
 (no stamp required) **PLYMOUTH**  
**PL1 1BR. Tel: 0752 67377.**

- Please send the ANTEX colour catalogue.
- Please send the following: .....

I enclose cheque/P.O./Cash (Giro No. 2581000) Reg. No: 393594

NAME .....

ADDRESS .....

PW7

# parts for PRACTICAL WIRELESS projects

After many requests, Electro Spares are now supplying lists of components for ALL the projects featured in "Practical Wireless", commencing this month. Just forward an S.A.E. (Preferably 9" x 4" minimum) stating which project is of interest to you—we will forward an individually priced list of components required. No need to buy a full kit—you need only purchase the parts you require at any one time.

All Electro Spares supplied components are new, branded products of reputable manufacturers and carry full makers guarantee.

We regret we cannot supply lists for projects published before this issue.

"ONE SOURCE" BUYING MAKES SENSE—IT CAN SAVE YOU TIME, MONEY AND POSTAGE.

## "p.e." f.m. varicap stereo tuner

Electro Spares offer a kit of high quality parts to the published specification for this remarkable tuner, featured in "Practical Electronics" May 1973.

Features include push button "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy "no problem" construction, requiring only a few simple setting up adjustments with a D.C. Voltmeter. Uses NEW pre-set modules for R.F. and I.F. Circuits—no circuit alignment. High efficiency Integrated Circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator. Fibre Glass P.C. Board, neat slimline cabinet with brushed aluminium front panel, push buttons etc. etc.

**IDEAL FOR USE WITH THE "TEXAN," "GEMINI" AND ANY GOOD QUALITY STEREO AMPLIFIER**

Please send large S.A.E. for full details.

## "p.e. gemini" stereo amplifier

**QUALITY HI-FI FOR THE HOME CONSTRUCTOR**

30 Watts per channel into 8 ohms! Total Harmonic Distortion 0.02%! Frequency Response (-3 dB) 20Hz-100kHz!

We are still continuing to supply components for this fabulous Amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the Home Constructor—we can supply a Booklet containing full specification, complete constructional information wiring diagrams, fault finding guide, etc. etc. Price 55p, plus 4p postage.

Our **New Low Price List** is supplied with each booklet, or supplied separately on receipt of a large S.A.E.

**FOR PEOPLE WHO REQUIRE THE BEST, IT HAS TO BE THE "p.e. gemini".**

Note Our New Address—With New Mail Order Department For Quick, Efficient Service.

**PLEASE PAY US A CALL—VISITORS WELCOME. NO PARKING PROBLEMS**

 **Electro-Spares**  
288, ECCLESALL ROAD,  
SHEFFIELD, S11 8PE

"THE COMPONENT CENTRE OF THE NORTH"



**for fast, easy  
reliable soldering**

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

## EASY-TO-USE DISPENSERS



**Size 5**  
Savbit alloy  
18 swg, 18p  
(illustrated).  
**Size 19A**  
60/40 alloy  
18 swg, 18p  
**Size 15**  
60/40 alloy  
22 swg, 22p

## IDEAL FOR HOME CONSTRUCTORS


**Size 1** cartons in 40/60, 60/40  
and Savbit alloys  
in 7 gauges 25p



**Size 12**  
for Service  
Engineers and  
Electricians.  
75ft of 18 swg  
Savbit alloy. 75p



## NEW! BIB WIRE STRIPPER AND CUTTER

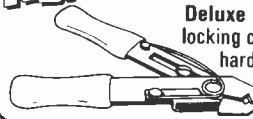

**Deluxe Model 9** Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T.  
From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to  
**Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP**

## 4 CHANNEL STEREO CONVERTER



**TRANSFORMS  
YOUR STEREO  
SYSTEM INTO  
SENSATIONAL  
QUADRAPHONIC  
SOUND**

Create a new dimension in sound — sound that engulfs you with natural realism from every corner of your room. Simply wired to your amplifier or Tuner/Amp.

speaker outputs and again into 4 speakers. Neat inc. carr. V.A.T. styling with brushed effect console panel. Peak input power 50w into 8 ohms. Front Hi/Low Level 6dB. Phone jacks for input and output. Size: 6" x 3 1/4" d. x 2". Guaranteed. Callers welcomed for demonstration.

INTRODUCTION PRICE **£8.65**

**CCIL** LTD

(Dept. PW 5), 43 BARTHOLOMEW CLOSE,  
LONDON, EC1A 7HP. Tel. 01-600 3211.

## poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker  
Super-thin construction  
permits new installation ideas.



Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz  
Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 1-3/4" x 14-11/16". Weight: 19 ounces.

£7.50 each Stereo pair £14.50  
post free

**web europa**

P.O. Box 162, Watford WD1 1AA








# UNISOUND FOR THE NEW SOUND

AT  
**£26.12**

INC.  
VAT

It's the RT-VC system that screws together to save you pounds! Unisound comprises two superb speakers and an amplifier/record deck plinth—all beautifully finished in simulated teak. The stereo amplifier (4 watts per channel into 8 ohms) is based on the famous Mullard Unilex system brought up-to-date by RTVC using integrated circuits. Turntable is the proven Garrard 2025TC complete with stereo cartridge and tinted acrylic cover. Speakers are big EMI Twin-cone units all ready for mounting in their elegant cabinets, which simply need screwing and glueing together. Easy step-by-step instructions. £26.12 complete plus £1.40 packing + £1.40 post. Diamond Stylus £1.37 extra. Stereo headphones with adaptor £4.40 extra. Send for leaflet.

## AN RTVC EXCLUSIVE DESIGN

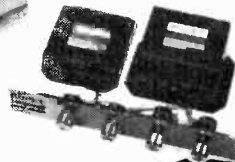

UNISOUND MODULES ONLY £7.65 + 55p. p. & p.

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.

# VISCOUNT III—Now 20 wa

If you can solder on printed circuit board you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions

## THE TOURIST PUSH BUTTON CAR RADIO KIT AN INCREDIBLE BUY

ONLY FROM **RTVC**



**£6.60**

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.


Apart from the output stage, which is an intergrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modularised IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7" wide, 2" high and 4½" deep.

\* Circuit diagram and comprehensive instructions 55p free with parts.

\* Fully retractable & lockable car aerial £1.37 post paid.

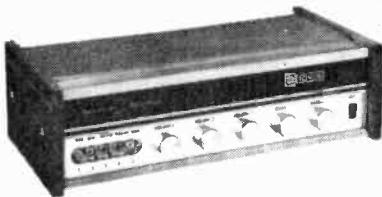**CAR RADIO KIT £6.60 p. and p. 55p**  
Speaker with baffle and fixing strips £1.65  
27 p. & p., post free if bought with the kit  
Send S.A.E. for leaflet.



## RELIANT Mk IV

AN ELEGANT 20 WATTS MONO AMPLIFIER FOR ONLY £13.50 (inc. VAT). IDEAL FOR YOUR DISCO.

\*5 Electrically Mixed inputs. \*3 Individual Mixing controls. \*Separate bass and treble controls common to all 5 inputs. \*Mixer employing F.E.T. (Field Effect Transistors).

\*Solid State Circuitry. \*Attractive Styling INPUTS 1. Crystal Mic or Guitar 9mV. 2.

Moving coil Mic. or Guitar 8mV Inputs. 3, 4 & 5

are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.)

All 250mV sensitivity. Output 20 watts into


8 ohms (suitable for 15 ohms).

**£13.50** p & p  
60p

Size approx. 12½ x 6 x 3½ ins.
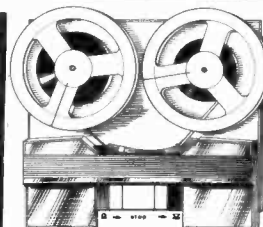
## SOUND 50

**45 WATT MONO AMPLIFIER.** Ideal for Disco Work. Output Power: 45 watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: **£31.35** 19½ x 10½ x 8ins. Amplifier £31.35 plus (inc. VAT) £1.65 p. and p.



## PE TAPE LINK CONSTRUCTORS

Suitable 3 speed tape deck, less heads. Caters up to 7ins. spools. 240V AC mains Un-**£4.00** used but store soiled hence plus no warranty. £1 p. & p.

All prices include VAT

**100 watts per channel RMS**

# VISCOUNT III AUDIO SYSTEM £49 COMPLETE

**PRICES: SYSTEM I**  
 Viscount III R 102 amplifier £24.20 + £1 p & p  
 2 Duo Type II speakers £14.00 + £2.20 p & p  
 Garrard SP25 Mk.III with  
 MAG. cartridge plinth & cover £18.00 + £1.75 p & p  
 total £56.20

Available complete for only £49 +  
 £3.50 p. & p.

**PRICES: SYSTEM 2**  
 Vicount R 102 amplifier £24.20 + £1 p & p  
 2 Duo Type III speakers £32.00 + £3.30 p & p  
 Garrard SP25 Mk. III with  
 MAG. cartridge plinth & cover £18.00 + £1.75 p & p  
 total £74.20

Available complete for £65 +  
 £4 p. & p.

20 + 20w. r.m.s. 40Hz to 40kHz ± 3dB. Total distortion at 10w. at 1kHz - 0.1%. This is real value for money! We have designed 2 systems and the heart of them both is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect, transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder.

For both systems we have chosen the famous Garrard SP25 Mk. III deck, with fitted magnetic cartridge, which comes complete with simulated teak plinth and tinted acrylic cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.



**SPEAKERS:** Duo Type II Size approx. 17in. x 10½in. x 6½in. Drive unit 13in. x 8in. with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £15.40 a pair (inc. VAT), £2.20 p. and p. Duo Type III Size approx. 23½in. x 11½in. x 9½in. Drive unit 13½in. x 8½in. with H.F. speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20KHz. Teak veneer cabinet. £35.20 a pair (inc. VAT) + £3.30 p. & p.  
**SPECIFICATION R102:** 20 watts per channel into 8 ohms (suitable 8-16 ohms.) Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 180mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within 1dB R.I.A.A. Radio 180mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Signal-to-noise ratio: (all controls at max.) -58dB. Cross talk better than -40dB on all inputs. Size approx. 13½in. x 9in. x 3½in. Send S.A.E. for fully illustrated brochure. 12 month's written guarantee.

**ONLY FROM US**


**TIMES OF OPENING:** Acton—Mon.—Sat. 9.30-5.  
 Closed all day Wed.  
 Edgware Rd.—Mon.—Sat. 9.30-5. Closed all day Thurs

**VISIT OUR SHOWROOMS** **RTVC**  
 Radio and TV Components (Acton) Ltd.  
 21c High Street, Acton, London W3  
 323 Edgware Road, London W2  
 Mail orders to Acton. Terms C.W.O.  
 Goods not despatched outside U.K.  
 All enquiries S.A.E.

## VISIT LONDON'S LIGHTHOUSE

*our lighthouse keeper  
wants to meet you!*

Jim Roche has been Imhofs Eddystone lighthouse keeper for a good few years now - so who better than he to guide you into the right channel, for an Eddystone communications receiver:

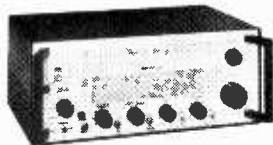

Model 1001 - general-purpose receiver with reception facilities for CW, MCW, AM and SSB. Provision for crystal control on 10 channels.

EC10 Mk II still 'Top of the Pops' in the modest price range of communication receivers. Embodies features usually only found in the more expensive designs.




**IMHOFS**

112-116 New Oxford Street  
London WC1A 1HJ  
telephone 01-636 7878 R81
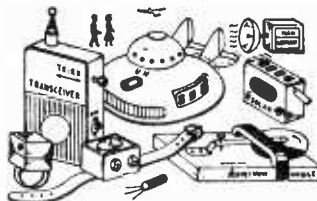
## PRINTED CIRCUIT KIT

BUILD 60 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2in x 2 1/2in. (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit: (10) Essential Design Data, Circuits, Chassis Plans, etc. for 60 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements.



EXPERIMENTER'S  
PRINTED CIRCUIT KIT

70p

Postage & Pack. 10p (UK)

Commonwealth:

SURFACE MAIL 15p

AIR MAIL 60p

Australia, New Zealand,  
South Africa, Canada

- (1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector.
- (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier.
- (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex.
- (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending).
- (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World.
- (10) 3 Subminiature Radio Receivers based on the "Tritexton" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62in x 0-95in x 0-25in. (11) Wristwatch Radio 1-15in x 0-80in x 0-55in. (12) Ring Radio 0-70in x 0-70in x 0-55in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone Amplifier. (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) "Photophone". (37) Light-Beam Transmitter. (40) Thyristor Drill Speed Controller. (41) Light Dimmer. (42) I.C. Pre-amplifier. (43) I.C. Amplifier. (44) I.C. Intercom. (45) I.C. Radio. (46) Raudive Voices Receiver. (47) Biofeedback Amplifier. (48) Brainwave Detector. (49) Proximity Switch. (50) Laser Projector.
- Plus 10 Photoelectric Circuits, Simple Alarms, Long Range Alarms, Projector, etc.

**YORK ELECTRICS, Mail Order Dept.**

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details and a brief description of all kits and Projects.

# Train for television

Course commences 5th September, 1973

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

**THE PEMBRIDGE COLLEGE OF ELECTRONICS**  
(Dept. PW4) 34a Hereford Rd., London W2 5AJ

ALL PRICES INCLUDE VAT

**BARGAIN PARCELS** 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 57½p p.p.; 56lb at £4.95 plus £1.37½ p.p. Contain pots, Res. Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save ££s. Lucky Dip Service.

**FANTASTIC BARGAIN.** New 6 inch tubes. E450 4/B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 09J 4½in. dia. Length 15in. Also 7BP7. All unused as new. Price £1.55 post paid.

**NEW HEAVY COAX CABLE** dia. ½" 70 ohms approx. 50ft. lengths £1.55, p. & p. 32½p. 100 ft. lengths £2.97, p. & p. 55p.

**AERIALS.** New Condition Whip Type, 4ft. 22p; 11ft. 82½p. all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 67½p. p. & p. 27½p.

**CRYSTALS AS NEW.** Hc 6u, 5,345; 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,295 Kc/s. 55p each plus 8p p.p.

**OUR SELECTION OF 6-Ex. Equ. METERS** consisting of 3in., 2½in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 27½p, minimum order of six.

**ANY HEIGHT AERIAL TUBULAR SECTIONS** ½" dia. x 3ft. long. Brass screw in ends, copper coated and painted. Good condition. 22½p p. & p. 5p each. Minimum order 6.

**TELE 'J' TELEPHONES AS NEW** £8.00 pair, p. & p. paid

**AS NEW AERIAL TUNER UNIT No. 6 RF**, consisting of 1½ inch 500 micro/ampmeter 3 gang tuner 75 PF geared BNC type socket size 5½" x 4½" x 5". Price £1.65, p. & p. 27½p.

**NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED** 90ft 50p. 100ft. 60p, p. & p. 22p.

**AERIAL MAST POLES** approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition, £1.10 each section. Carriage 37½p each section. ½" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1.10 + 32½p p.p.

**AS NEW 500ua PENNY SIZE METERS** complete with jack plug price £1.10 each, p. & p. 10p.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

**A. H. THACKER & SONS LTD.**

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.





TOP QUALITY — LOW COST



RADIO — STEREO EQUIPMENT



**P.R.40**  
SOLID STATE  
R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supercedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30 dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery), 12 months Guarantee. £10.12 V.A.T./Carr. paid.

**NEW!** HI-FI STEREO EQUIPMENT  
NOW AVAILABLE FROM CODAR—A COMPLETE RANGE OF QUALITY EQUIPMENT SELECTED BY US FOR TOP RESULTS AND MONEY VALUE—PLUS OUR BIG CASH DISCOUNTS!

SEND FOR FREE ILLUSTRATED BROCHURE NOW.



ON THE DESIGN STAFF—  
G3SZM G3IRE

**CODAR**

TELECOMMUNICATIONS AND ELECTRONIC  
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS  
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

Tel. 090-63-61901

BN15 - 8TZ



**CR70A**  
COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee. Complete ready built. £31.00 V.A.T./Carr. paid.

SEND FOR YOURS TODAY!  
FREE LEAFLETS ON REQUEST.

NOTE: These CODAR Receivers meet the B.R.E.M.A. specification for Communication Receivers. Some portable receivers being advertised as Communication Receivers do not meet these requirements.

**FIRST TIME EVER**  
at £42.50

**Solartron CD711S.2**  
Double Beam  
Oscilloscope d.c.—9MHz; 3mV-cm; trigger delay; crystal callibrator; 4in flat faced tube. In good working condition. Carriage £1.50.

**HARTLEY TYPE 13A**  
Only £18.00  
Double Beam oscilloscope TB2Hz-750kHz. Band width 5-5MHz. Sensitivity 33mV/cm. Calibration markers 100kHz and 1MHz. A completely reliable general purpose oscilloscope. Supplied with CIRCUIT DIAGRAM and Mains lead. Carr. £1.50.

As above. Complete with all accessories. £25.00. Carr. £1.50. Many other oscilloscopes available.

**GRATICULES.** 12cm x 14cm In High Quality plastic. 30p ea. P. & P. 5p.

**MODERN TELEPHONES** type 706. Two tone grey, £3.75 ea. The same but black, £2.75 ea. P. & P. 25p ea. Also **TOPAZ YELLOW** £4.50 ea. P. & P. 25p.

**STANDARD GPO DIAL TELEPHONE** (black) with Internal bell, 87p ea. P. & P. 50p. Two for £1.50. P. & P. 75p. All telephones complete with bell and dial.

**20Hz to 200kHz WB SINE AND SQUARE GENERATOR** Four ranges. Independent amplitude controls, thermostat stabilised. Ready to use. 9V supply required. £6.85 each. P. & P. 25p. (Not cased, not calibrated).

**MOTOR MIN SYNCHRONOUS** Size 1 1/2" x 2" x 3/4" 240V operation 3.6 RPM 25p each. P. & P. 5p.  
**5 MOVING COIL METERS** various £2 P. & P. 37p.

**WOBBLATOR**

Sweeps 8 to 45MHz ready to use. 6-3V a.c. required. £9 each. P. & P. 25p. (Not cased, not calibrated).

**CAPACITOR PACK**—50 Brand new components only 50p. P. & P. 17p.

**POTS**—10 different values. Brand new—50p. P. & P. 17p.

**COMPONENT PACK** consisting of 2-2 pole 2 amp push on/off switches; 4 pots, various, brand new; 250 resistors 1/4 watt, many high stabs, etc. Fine value at 50p per pack. P. & P. 17p.

**P.C.B. PACK S & D.** Quantity 2 eq ft—no tiny pieces. 50p plus P. & P. 20p.

**FIBRE GLASS** as above £1 plus P. & P. 20p.

**5 CRYSTALS** 70 to 90kHz. Our choice, 50p. P. & P. 15p.

Matched pairs, 50p per pair. P. & P. 15p.

**TRIMMER PACK.** 2 Twin 50/200pF ceramic; 2 Twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, 25p the lot. P. & P. 10p.

**ELECTRONIC TIMER UNITS**—wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only £2.50 incl. carriage.

**AMERICAN SCOPE** type USM24. A 10 meg scope—all min valves complete with circuit diagram. Mains input 115 volt 50 cycles therefore £20.00. Carr. £1.50.

**LIGHT EMITTING DIODES** (Red) from Hewlett-Packard. Brand New 38p ea. Holder 1p ea. Information 5p.

**PHOTOCELL** eqt OCP71—13p ea.  
**PHOTO-RESIST** type Clare 703. Two for 50p.

**DELIVERED TO YOUR DOOR** 1cwt of Electronic Scrap chassis boards, etc. No Rubbish. FOR ONLY £3.50.

**D.I.Y. TECHNICAL BOOKS**

- RADIO RECEIVER SERVICING GUIDE ..... £1.90
- 101 EASY HAM RADIO PROJECTS ..... £1.50
- 101 EASY AUDIO PROJECTS ..... £1.40
- RAPID T.V. REPAIR (224 pp) ..... £1.30
- ELECTRONIC GAMES AND TOYS YOU CAN BUILD ..... £1.40
- PAL RECEIVER SERVICING GUIDE (280 pp) ..... £3.50
- BASIC ELECTRICITY (6 VOLUMES, 630 pp, 600 ILLUS.) ..... £5.10
- ELECTRONIC DESIGNERS HANDBOOK ..... £3.40
- BASIC ELECTRONICS (6 VOLUMES, 674 pp, 700 ILLUS.) ..... £5.10
- ELECTRICITY, ELECTRONICS MADE SIMPLE ..... Each 95p
- RADIO HANDBOOK (896 pp) ..... £6.50
- 1-2-3-4 SERVICING STEREO AMPLIFIERS (240 pp) ..... £2.50
- MAKING & REPAIRING TRANSISTOR RADIOS, ADVANCED RADIO CONTROL, EASY WAYS TO SERVICE RADIO RECEIVERS, BEGINNERS GUIDE TO T.V. REPAIR, PRACTICAL HAM RADIO PROJECTS, HI-FI PROJECTS FOR THE HOBBYIST ..... Each £1.00
- HOW TO BUILD SPEAKER ENCLOSURES ..... £1.50
- HI-FI STEREO SERVICING GUIDE, 99 ELECTRONIC PROJECTS ..... £1.50
- 99 WAYS TO IMPROVE YOUR HI-FI ..... Each £1.50
- ELECTRONICS FOR THE BEGINNER, T.V. SERVICING MADE EASY, 101 QUES. & ANSWERS ABOUT AM, FM & SSB ..... Each £1.75
- HOW TO REPAIR SMALL APPLIANCES ..... £1.20

ADD 10% FOR POSTAGE AND PACKING  
WHEEL (PWJ), 41A ADELAIDE GROVE, LONDON, W12

**BAKER 12" MAJOR £9.90**

30-14500 cps. Double cone woofer and tweeter combination. Baker ceramic magnet assembly flux density 14500 gauss. Bass resonance 40 c.p.s. 20 watt RMS.

**MAJOR MODULE KIT £12.50**

30-17000 cps. with tweeter, crossover and baffle.



- Baker Loudspeakers**
- Regent 12" 15W £8.80
  - Major 12" 20W £9.90
  - Deluxe 12" 15W £11
  - Superb 12" 20W £16.50
  - Grp. 25 12" 25W £8.80
  - Grp. 35 12" 35W £9.90

ALL PRICES INCLUDE VAT

Baker Loudspeaker Co., Bensham Manor Passage, Thornton Heath, Surrey. Tel. 01-684 1665  
Loudspeakers Catalogue and Enclosure plan 5p

**CHILTMEAD LTD**  
7/9 ARTHUR ROAD, READING, BERKS.

(rear Tech. College) Tel.: Reading 582605/65916









# FORMATIVE HABITS

**D**URING the first 18 years of human life a great many natural developments take place which perhaps we take for granted. One of these is the shrugging off of juvenile behaviour characteristics and the adoption of a mature outlook to face the rigours of a competitive world.

When applied to a technical art such as broadcast entertainment, not only do programme standards alter, but also the medium by which they are conveyed. The obvious examples that spring to mind are the progressions through 405-line, 625-line, and colour television for one; acoustic gramophones, mono discs, 2-channel stereo and quadrasonic sound for another. In spite of a mixture of pessimism, cautiousness, apathy, or just plain rejection, developments in the methods and standards of technical achievement still win through.

But there is still a very interesting factor; that is a great reluctance, especially in the U.K., to shake off some of those formative habits. We still have 405-lines, mono discs (often forced to undergo processing to stereo status), and of more topical concern, medium wave broadcasting. Why? Or equally, why not? The very organisation that has been trying to convert us to v.h.f./f.m. for the past 18 years is still promoting broadcasting on m.w./l.w. Even more interesting—the IBA are now doing likewise. Why?

Have you bought or built an f.m.-only tuner in the light of the advice about improved reception of BBC programmes, only to find that you cannot receive the programmes that go out on a.m. only? Do you also find that reception in cars via f.m. is very difficult because of interference? Are you finding station separation on the medium wave more difficult? It is truly amazing that in spite of "progress" our broadcasting system is still bugged on occasions by major reception problems. (See letters on page 261.)

It is interesting to note that the BBC are experimenting with concurrent television and stereo radio programme material. Let's have more! Experiments are also going ahead on broadcasting quadrasonic sound, but we have not heard them yet.

In the meantime we will go on promoting v.h.f./f.m., especially for constructors. Mr. Ainslie's recent article was typically a popular project. Mr. Rayer describes a special receiver in this issue, that enables the experimenter to extend reception outside the usual 88–108MHz limits of a conventional dial. Future issues will provide state-of-the-art circuits of f.m. stereo. But we will not forget a.m. On the contrary we shall do all we can to provide constructors with limited experience some simple circuits to build, and at low cost too; more details about this next month.

M. A. COLWELL—*Editor*

**The August issue on sale 6th July, will include our new all-transistor oscilloscope specially designed for students, experimenters and constructors who want reliable performance coupled with simple construction. We shall also have a communications receiver and details of a new Databank scheme commencing in the autumn. Our autumn issues are being planned as the best yet for new projects and ideas on home entertainment. We would hate the idea of you missing them, so order your regular copies of *Practical Wireless* now. Further details on page 239.**

## NEWS...

### Mobile rally diary

**June 17**—Amateur Radio Mobile Society Rally, R.A.F. Cosford, Shropshire. Details from W. S. Barwick, 34 Malvern Rd., London, N.8.

**June 24**—West of England (Bristol City and County RSGB Group) Mobile Rally at Longleat. Further details of this popular rally can be obtained by dropping a line to A. H. Williams, G8CKJ, 58 Britannia Road, Kingswood, Bristol.

**July 1**—South Shields and District Amateur Radio Club's rally will be at Redwell School, Prince Edward Road, South Shields.

**July 8**—Cornish Rally at Treviglass County Secondary School, Newquay, Cornwall.

**July 8**—The Worcester and District Amateur Radio Club are organising the Upton-on-Severn Mobile Rally and further details can be obtained from B. A. Jones, G8ASO, 12 Woodside Road, Larkhill, Worcester, WR5 2EG.

**July 22**—Anglian Mobile Rally will be held at the Suffolk Showground Bucklesham Road, Ipswich. Readers can obtain further information by contacting C. J. Wantling, G3TNE, 15 Melplash Road, Ipswich, Suffolk, IP3 8QJ. Telephone Ipswich 75241.

**July 22**—Southdown Rally at Polegate, Wilmington.

**August 5**—Radio Society of Great Britain Mobile Rally at Woburn Abbey, Beds.

**August 12**—The Derby and District Amateur Radio Society are holding their 1973 rally at the usual venue i.e. Rykneld School, Bedford Street, Derby. There's ample inside accommodation if it rains and plenty of parking space for cars. In addition, there will be plenty of attractions for the XYL's and harmonics. If you want to know more, send a s.a.e. to Fred Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby, DE3 7GE.

**August 12**—Torbay Annual Mobile Rally will be held at Newton Abbot Rugby Club ground. There will be talk-in stations, the usual stands and various competitions. The contact for further gen is L. H. Webber, G3GDW, 43 Lime Tree Walk, Newton Abbot, Devon.

## MOS i.c.'s and their Applications

**T**HE latest book published by Mullard Ltd. is entitled "MOS Integrated Circuits and their Applications". It provides the reader with an introduction to these devices and should be ideal reading for designers unfamiliar with them and for electronic engineering students.

The construction, manufacture and characteristics of MOS i.c.'s are covered and the ways in which they can be used are fully explained.

A short description of the operation of the devices is followed by the explanation of the manufacturing processes of the various types of MOS i.c.'s. The static characteristics of the MOS transistor are examined and a description given of the static inverter which forms the basis of the gating elements used in MOS logic devices.

Switching characteristics are discussed and the main MOS static and dynamic logic circuits are examined.

Interface circuits are given and input/output protection devices described.

The final chapter deals with typical logic applications in which MOS i.c.'s can be used advantageously.

The book, cloth bound with 176 pages costs £2- and is obtainable from leading booksellers.

## Interface '73

**T**EXAS Instruments will again be holding their annual Seminar at the 'Talk of the Town' in London. It will be entitled "Interface 73" and will run for 3 days—June 12, 13 and 14. The same programme will be repeated each day.


In addition to presentations on Optoelectronics, Memories and Power Devices etc. Texas Instruments are expecting to make important policy statements on the Digital I.C. market.

## Audio Fair '73

**D**ATES are announced for the 1973 International Audio Festival and Fair and, for the first time since the exhibition moved to Olympia in 1969, it is to be open on a Sunday. Dates are October 23 to 28.
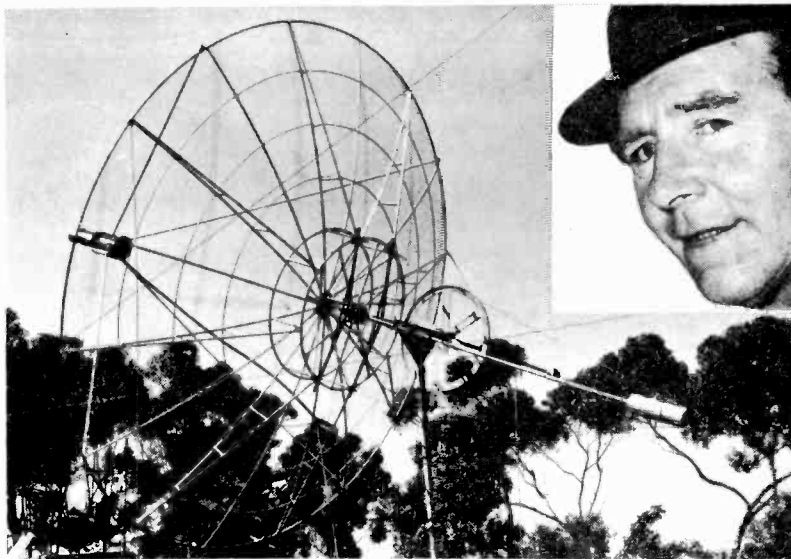
## An Aussie 'First'

**R**ON Wilkinson, VK3AKC is the first man in Australia to send a radio signal to America via the moon. He used the frequency of 1296MHz and the signal was received by the Crawford Hills UHF Group U.S.A.



The aerial used : a 20ft. parabolic dish.


## Circular aeriels for VHF

**E**MI has been awarded contracts to provide the Independent Broadcasting Authority with transmitting aerial systems for Britain's first commercial radio stations.

Altogether six systems are being supplied and they will cover five major cities throughout the country including London, Birmingham, Glasgow and Manchester. Transmissions from the new stations are expected to commence towards the end of 1973.

Two v.h.f. aeriels have been specified for London and Birmingham, which will be the first of their type in this country, utilising circular polarisation techniques. These techniques are used extensively in the United States to give improved reception for transistor and car radios.

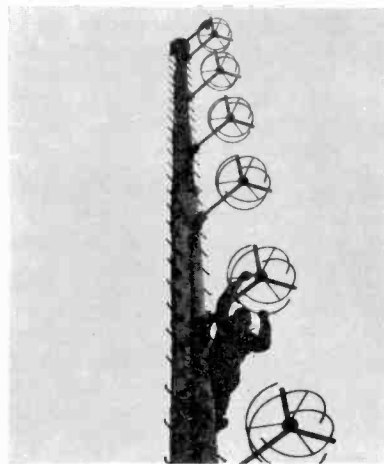The aerial system for London, which is 60ft. high, will be installed on the top of the 500ft. television tower at the IBA Croydon transmitting station. This aerial will transmit two programmes to the London area. The second v.h.f. system will be mounted on the 1000ft. mast at the Lichfield transmitting station, near Birmingham.



# extra bands

## Fm receiver

F. G. RAYER

**T**HE usual VHF receiver has a single VHF band covering those frequencies used for VHF broadcasting. The actual band varies with different receivers, but is often about 88-108MHz or so. This is usually obtained with fixed coils and a small ganged variable capacitor in conjunction with fixed capacitors and trimmers.

Experiments with a view to increasing coverage beyond that of popular VHF receivers show that the range can be extended in the HF direction by eliminating the parallel fixed capacitors and trimmers in the tuning circuits, as would be expected. For a reasonable inductance to capacitance ratio, tuning values of about 25pF are about the largest useable, but it is found that provided the layout gives the shortest possible leads, miniature plug-in coils are satisfactory, allowing extended coverage.

As trimmers would curtail coverage in the HF direction, and interchangeable coils are envisaged, separate tuning capacitors become almost essential. This eliminates ganging or alignment difficulties in this part of the receiver and works out quite satisfactorily because only the oscillator requires a reduction drive. The second tuning control is merely peaked for best results.

To facilitate alignment only two tuned circuits are used and since a single pair of plug-in coils will cover a band larger than the usual VHF range there is no need to fit other coils if not wanted.

The receiver intermediate frequency is 10.7MHz, so the second channel occurs at 21.4MHz from the wanted tuning frequency. As the tuned circuits have separate controls, some signals can thus be received at two positions of the oscillator tuning, depending on whether the oscillator frequency is 10.7MHz above or below the wanted signal. This is an effect which is unavoidable, if the advantage of separate tuning capacitors is to be retained, but it is not too important provided it is understood that this effect can arise.

In view of this, the bands given below are those of the oscillator coverage:

- Band 1 34—55MHz
- Band 2 45—72MHz
- Band 3 82—140MHz
- Band 4 110—180MHz

For general VHF use, Band 3 coils will be most suitable, the reception coverage then being approximately 72-130MHz, with the oscillator HF of the signal frequency.



### CIRCUIT

Fig. 1 is the circuit of the receiver, the rod aerial or feeder being taken to the primary of L1, which is tuned by VC1. L2 is the oscillator coil, capacitor VC2 having a ball drive and dial for tuning. L1 and L2 are miniature plug-in coils, for changing bands.

Tr1 is the dual-gate FET mixer, output from the drain going to IFT1. Transistors Tr3, Tr4 and Tr5 are the three 10.7MHz IF amplifiers, with double-tuned IF transformers. C8 and C11 are necessary to neutralise these stages. IFT4 is a ratio discriminator transformer with the matched diodes D1 and D2 the audio output being taken via R19 from the tertiary winding.

VR1 is the audio volume control feeding a 3-stage amplifier. A 2½in. speaker is incorporated for portable use, but the output jack allows a larger speaker or headphones to be plugged in.

The mixer and oscillator stages, with associated components, are built on a metal chassis but the IF and AF amplifiers are built as separate units on insulated boards.

### CHASSIS AND PANEL

The chassis is 8 x 4in. and is a universal chassis flanged member. For the case described, the panel is flat aluminium, 8 x 5in. Fig. 2 shows the underside of the chassis.

VC1 is mounted centrally and ¼in. clear of the chassis. The holder for L1 is placed so that the leads from pins 1 and 6 are as short as possible, as shown.

VC2 is mounted on a metal bracket and is set back to accommodate the ball drive. The holder for L2 must also be placed to allow very short leads to VC2. The ball drive requires a ¾in. or 1in. hole in the panel and its lug is fixed with a 6BA bolt. VC2 and the drive need to be lined up to give a smooth free movement. The listed drive has a flange and

# ★ components list

## Resistors

R1 100kΩ	R13 680Ω	R25 47kΩ
R2 2.2kΩ	R14 1kΩ	R26 3.3kΩ
R3 100kΩ	R15 33kΩ	R27 47kΩ
R4 1kΩ	R16 5.6kΩ	R28 12kΩ
R5 10kΩ	R17 1kΩ	R29 2.7kΩ
R6 10kΩ	R18 680Ω	R30 680Ω
R7 33kΩ	R19 100Ω	R31 2.2kΩ 5%
R8 5.6kΩ	R20 680Ω	R32 39Ω 5%
R9 680Ω	R21 680Ω	R33 5.6kΩ
R10 1kΩ	R22 4.7kΩ	R34 470kΩ
R11 33kΩ	R23 4.7kΩ	VR1 22kΩ log.
R12 5.6kΩ	R24 5.6kΩ	pot. with switch S1

All 10% 1/4W except R31 and R32, 5%

## Capacitors

C1 22pF	C11 5pF	C21 2μF 6V
C2 1000pF	C12 5000pF	C22 0.01μF
C3 5pF	C13 5000pF	C23 2μF 6V
C4 5pF	C14 5000pF	C24 100μF 12V
C5 5000pF	C15 5000pF	C25 2μF 6V
C6 0.01μF	C16 5000pF	C26 60μF 6V
C7 5000pF	C17 5000pF	C27 100μF 12V
C8 5pF	C18 330pF	
C9 5000pF	C19 330pF	
C10 5000pF	C20 0.01μF	

VC1 and VC2 25pF variable (Jackson C804)

## Semiconductors

Tr1 3N141	Tr4 OC170	Tr7 OC81D
Tr2 BF200	Tr5 OC170	Tr8/9 OC81
Tr3 OC170	Tr6 OC71	D1/2 OA79

## Miscellaneous

IFT1/2/3, (Denco IFT15). IFT4, (Denco RDT2). T1, (Home Radio TR64). T2, (Home Radio TR55A). Chassis, 8 x 4in. Universal chassis flanged member, panel 8 x 5in. (Home Radio). Valveholders B9A(2). Ball drive, (Jackson 4511/F). Dial 2½in. dia. (Bulgin). Veroboard 0.15in. matrix, and pins. Knobs. Coaxial socket. Speaker 3Ω, 2½in. dia. Jack socket (switched). L1/2, see text.

## ALIGNMENT GENERATOR

R1 22kΩ	R3 1kΩ	R5 5.6kΩ
R2 5.6kΩ	R4 22kΩ	
C1 5000pF	C3 0.01μF	C5 22pF
C2 1000pF	C4 47pF	

## Miscellaneous

Tr1, OC71. Tr2, AF117. T1, (Home Radio TR64). L1, (Denco 'Blue' Range 4, Valve type). S1/2 toggle, on/off. Chassis, 5 x 2in. universal chassis flanged member (Home Radio). Veroboard, pins.

the metal dial can be fixed with two very short 8BA bolts run into the tapped holes.

Wiring for Tr2 is shown in Fig. 2. Very short leads are essential to C4 and C5. The shield lead Sh is not connected. The oscillator may be tested by connecting a 9V battery to chassis and negative lead (observe the polarity shown). If this stage is oscillating, battery current, as indicated by a meter in one battery lead, will change when VC2 is shorted. If this stage does not oscillate, the receiver cannot work at all. A transistor of doubtful efficiency may oscillate at the lower frequencies but not in the 150-180MHz region. So the test can be made with all coils, and for all positions of VC2.

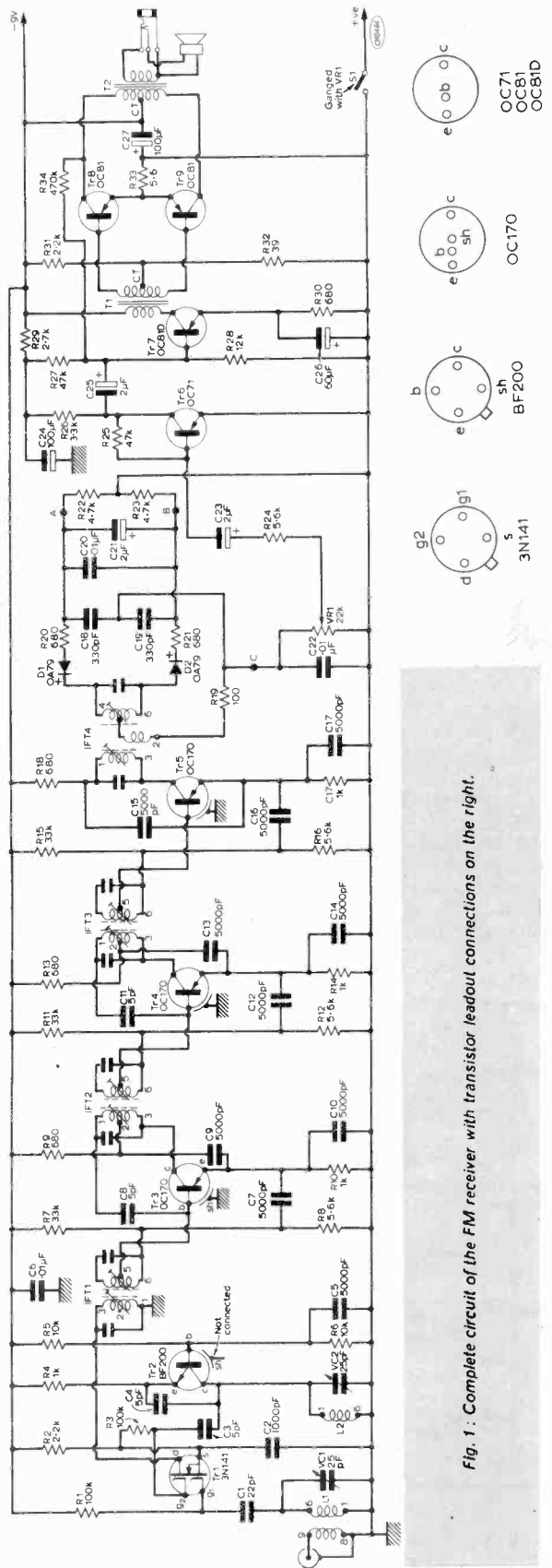


Fig. 1: Complete circuit of the FM receiver with transistor leadout connections on the right.

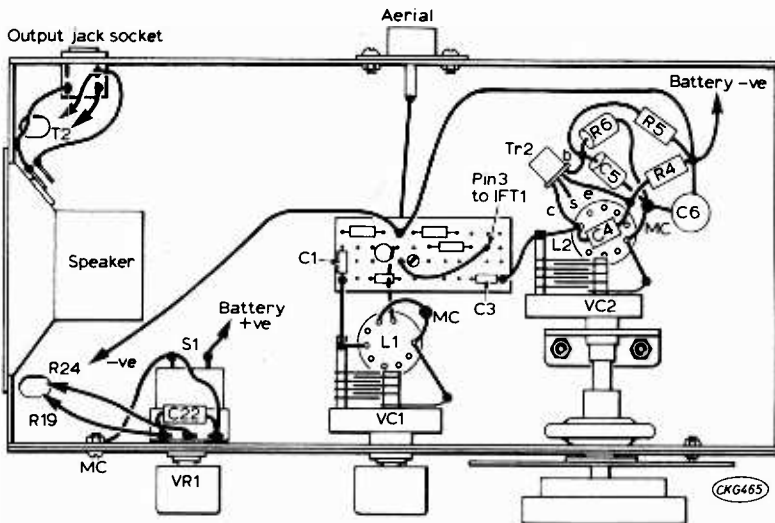


Fig. 2: Layout underneath the chassis with the tuned oscillator stage at the right. The mixer stage board (Fig. 3) is in the centre with its associated tuned circuit. The speaker is interconnected with the headphone jack socket mounted on the rear apron of the chassis.

## MIXER BOARD

This board is  $1\frac{7}{8} \times \frac{3}{4}$  in. of 0.15 in. matrix plain Veroboard, wired as in Fig. 3. A 6BA bolt, with extra nuts, allows the board to be locked to the metal chassis, with enough clearance to avoid any short circuits. This bolt forms the earth return.

The leads of C1 and C3 can be left projecting, to solder to VC1 and VC2. Also fit a pin or projecting lead for the negative connection, and a wire which can pass down through the board and chassis, to reach pin 3 of IFT1 on the IF amplifier.

Transistor Tr1 should be supplied with a shorting clip on its leads, and this **must not be removed** until the transistor has been soldered in place. First wire the board as in Fig. 3, omitting Tr1. Solder on the wires which will go to gate 1, gate 2, source and drain, and cut them to length and tin them. Tr1 is then inserted with its wires as shown. The leads can

be spread with a sharpened matchstick, but should not be touched with a metal or plastic tool, or the fingers. Solder source and drain leads. Then while holding iron and solder in contact with the lead from C1/R1, solder g1. In the same way, hold the iron and solder against the lead from R3, and solder g2. When the resistors are soldered to provide an external circuit from g1 and g2 to the source, the transistor is protected and the wire clip is removed. If g1 or g2 have to be unsoldered from R1 or R3, or these resistors have to be unsoldered, the transistor leads should first be bound with thin wire.

The board is fixed as in Fig. 2, and external connections are made. The co-axial aerial socket and output socket are fixed to the rear flange of the chassis so that the receiver can be tested out of its case.

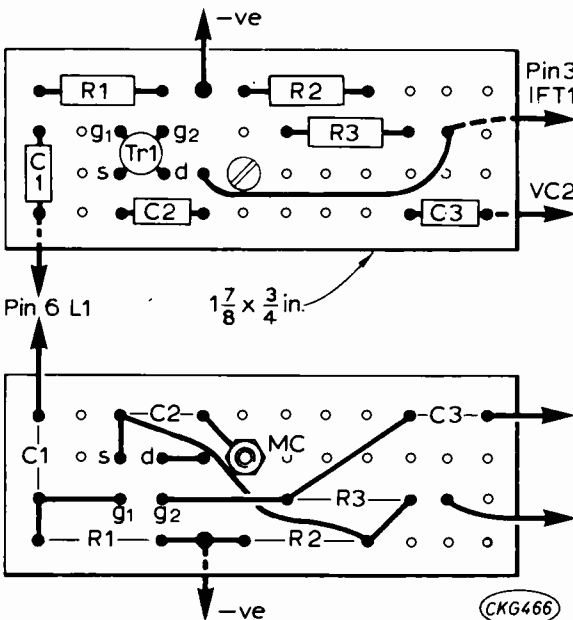


Fig. 3: Both sides of the mixer stage board.

## IF AMPLIFIER

This is assembled on a  $5\frac{1}{2} \times 1\frac{3}{4}$  in. board as in Fig. 4. First mark and drill holes for the IFT's and for the two  $\frac{1}{2}$  in. 6BA bolts. These, with additional nuts, form the chassis return and hold the board the metal chassis.


Leads should be short and direct, and insulated sleeving is put on where necessary. If  $\frac{1}{4}$  in. lengths of small diameter sleeving are put on the transistor leads this will prevent shorts and hold the transistors at a suitable height, while also identifying the wires.

Note that all the IFT screening cans are earthed. As the IFT's are prealigned, unnecessary disturbance of the cores is better avoided. When wiring D1 and D2, note that these may have a black ring to show positive. Polarity must be correct as a DC voltage is produced across C21.

Run a lead from pin 3 of IFT1 to a pin or wire, so that the wire from Tr1 can be soldered on later. A black lead, to go to battery negative, is soldered to R18, Fig. 4. A lead from R19 is provided, and will pass through the chassis to VR1.

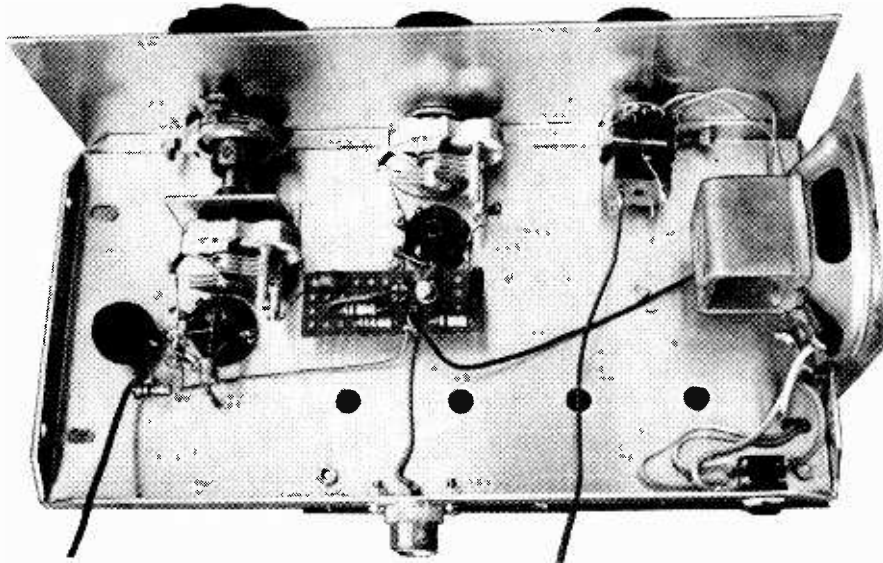If this section is tested with the board separate from the receiver, do not run a signal generator or other lead from pin 3 of IFT1 near the other IFT's or circuits, or instability may be caused which would not be present when the amplifier is fixed to the chassis.





View of the underside of the FM receiver which should be compared with Fig. 2.

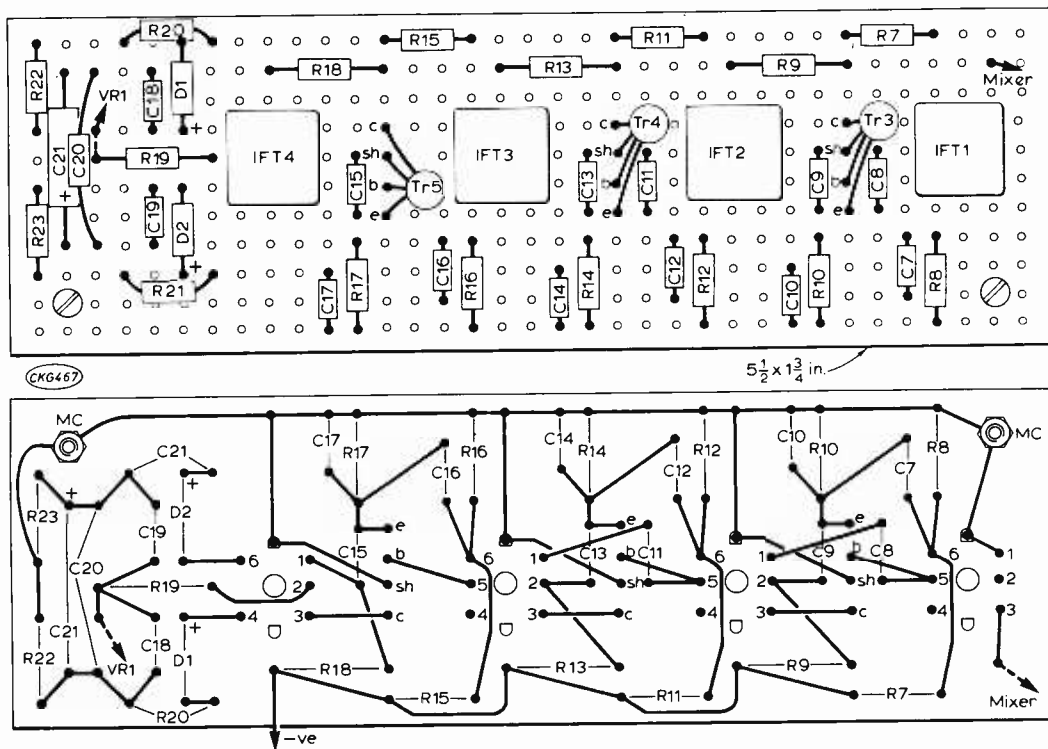


Fig. 4: The two sides of the IF amplifier board, shown actual size, illustrating component layout and wiring.

## IF ALIGNMENT

This can be carried out with the aid of a high-resistance voltmeter, or the 2-5V range of the usual type of multi-range meter, preferably with a resistance of 10kΩ/volt or better. It is assumed that if alignment equipment for FM receivers is available the means of employing this will be known, so the method of alignment described here is an alternate method.

Three test points are shown on the circuit, Fig. 1, and the multi-range meter is clipped to these for aligning the IF amplifier by this method. Initially, meter negative is clipped to A and meter positive to B. Maximum signal strength at the diodes will then produce maximum voltage from A to B, as shown by the meter. All the IFT cores are adjusted for maximum meter reading and each core should have quite a sharp tuning peak, seen by observing the meter while slowly turning the core.

For the second stage of adjustment, the meter is clipped from point C to chassis, the polarity being unimportant. The bottom core of IFT4 is then adjusted for minimum reading on the meter. In addition to the usual upwards movement of the meter pointer, some backwards movement can normally be seen. By rotating the lower core one way or the other, it should be possible to make the meter pointer move backwards or forwards from its minimum position. Set the core so that the meter shows this "zero". This completes the IF strip adjustment.

When making these adjustments, a properly fitting plastic trimming tool should be used. It is helpful to have a signal generator of the usual type employed with AM receivers and to tune this to 10.7MHz. A lead from the generator is placed near the receiver mixer, to secure sufficient input to allow an indication on the voltmeter as described. When the generator output is amplitude modulated, this will be heard in the speaker, but the adjustments described are made with the generator giving a CW output.

Unnecessary adjustment to the cores before obtaining results is best avoided, as they are approximately adjusted when the IFT's are manufactured. Should IFT's be used which are so far out of adjustment that no signal can pass through the IF strip, couple the signal generator to the base of the last IF amplifier and adjust the last IFT. Then transfer the generator input to the previous amplifier base and adjust the third IFT. After taking the input to the first IF amplifier base and adjusting the second IFT transfer the input to the mixer in the way described, and carefully check all the IFT's.

Where no signal generator is available, the only method is to tune the receiver until some signal is obtained, and to work on this by ear, adjusting all cores for best volume and the bottom core for best results with an FM transmission. This can prove reasonably satisfactory, unless the IF circuits are so far off tune that the strongest transmission available cannot be heard.

## INSTABILITY

With three IF stages and double-tuned transformers it is quite possible for IF instability to arise. This depends on the individual transistors, position and length of leads and similar factors. It is heard as whistling or hissing accompanying signals, or as oscillation liable to start when the IFT's are aligned, but which ceases when some cores are slightly staggered.

Where a small adjustment of some cores prevent this, and results are good, no modification is necessary. Otherwise, the trouble can be cured by placing a resistor between pin 5 of one or more IFT's and the corresponding base lead. This is most easily done by disconnecting the base wire from the pin, so that the resistor can be soldered directly to the pin, under the board. A similar result is achieved by placing a resistor in the lead from collector to pin 3 of the following IFT.

The values of the resistors are not very critical, except that unnecessarily large values will reduce gain. A number of small resistors from about 22Ω to 220Ω or so can readily be tried. In the original IF strip a value of 100Ω was used in the first stage, with 39Ω resistors for each of the following stages.

Though the amplifier can be tested and roughly aligned when clear of the receiver, final adjustments should be made with it fixed in its normal position. Four holes are required in the metal chassis, so that the lower cores can be reached. Final slight re-adjustment of IFT4 can be made by ear, when a transmission is tuned in. A simple 10.7MHz alignment generator is described later.

## COILS

Band 3 was covered with Denco miniature plug-in coils Range 7. A "Yellow" coil is used for L1 and "Red" coil for L2. This is the most generally useful band. Band 2 is covered by using a similar pair of coils, Range 6. The Range 5 coils, which have cores, cover Band 1. All these coils are the valve type. For Band 4, coils were wound using Denco plug-in formers. Place the former in a valve holder before soldering to the pins. L1 is 2½ turns spaced ½in. and tapped at 1 turn from pin 1, for pin 9. L2 is 1½ turns, spaced ½in. Both are 22swg or similar wire.

## AF AMPLIFIER

This is assembled on 0.15in. matrix Veroboard, in a similar way to the IF amplifier. The board is 2½in. x 2in. and both sides are shown in Fig. 5.

Transformer T2 has lugs which pass through slots, which can be made by drilling small holes closely together, and the lugs are twisted to hold the transformer to the board. Two ½in. 6BA bolts secure tags which form the chassis (positive) return.

The wiring of this unit should prove to be quite straightforward. Observe the polarity of electrolytic


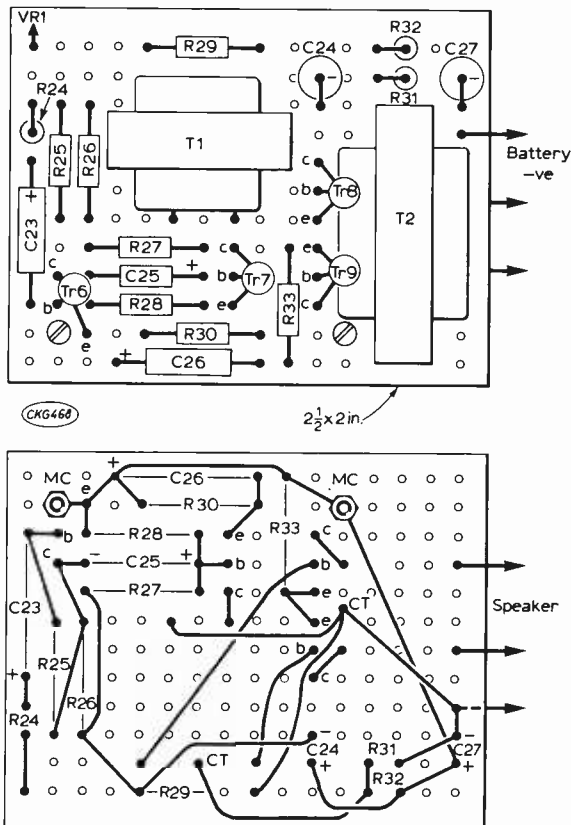


Fig. 5: Details of the audio amplifier board, full size.

capacitors and put sleeving on any leads where this is necessary to avoid short-circuits. Two thin flexible leads are soldered to the secondary tags of T2, for the speaker connections. A Veropin or projecting wire is provided for the connection to VR1 and another for fixing a black flexible lead for battery negative.

A great advantage of this circuit is that it provides quite high gain while the DC operating conditions of each stage are isolated from those of other stages. The specified transistors are readily available, but if similar types are to hand it is quite likely that they could be used. In some cases, the value of one or more resistors might have to be changed to suit the transistors. This is especially so in the output stage, where unsuitable values may cause high battery drain on the one hand, or very low drain with distortion, on the other.

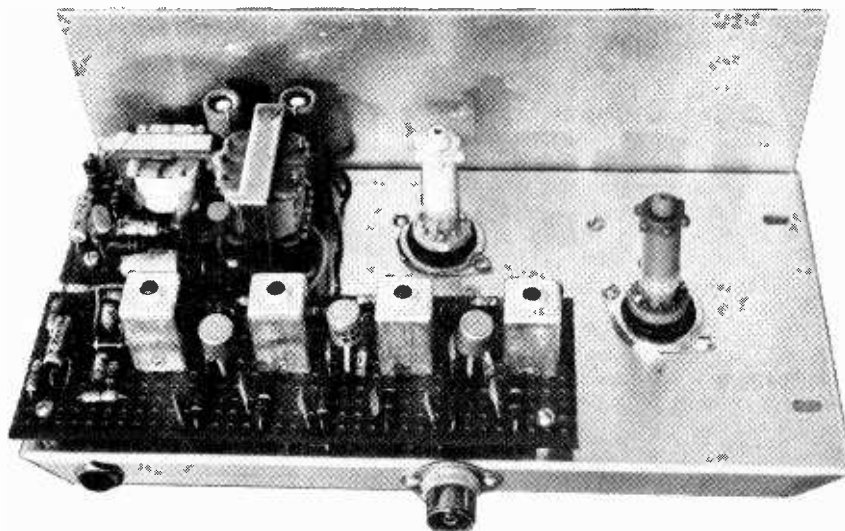It is quite a good plan to test the AF amplifier by itself, when it is completed. This is done by taking an AF input to the volume control VR1, which may be left in circuit to avoid overloading. The speaker and battery are connected when the amplifier should draw about 10mA, rising to 25-50mA or so with ample volume.



*This photograph shows the position of the IF and AF boards on top of the chassis.*

The negative feedback is not essential and R34 may be omitted or changed to between 470 and 680k $\Omega$ . If used, connect it from driver base to one output transistor collector at T2 primary. If volume falls slightly, this is correct. Should oscillation begin, transfer the connection to the other collector.

As the first AF stage is followed by two stages of amplification, a noisy transistor here will cause a hiss in the speaker. This was so in the amplifier shown and was traced to the use of a noisy, cheap surplus OC71 in the first stage. When this transistor was replaced, the noisy background ceased.

## CABINET

The cabinet is made from  $\frac{1}{4}$ in. plywood. Each side is  $5\frac{1}{4} \times 4\frac{1}{2}$ in. and the top and bottom are  $8\frac{5}{8} \times 4\frac{1}{2}$ in. An aperture to match the small internal speaker is cut in the right-hand side and covered with speaker gauze or similar material.

The parts are assembled with glue and panel pins. Four  $\frac{1}{4}$ in. strips are glued flush with the front edges, inside. The receiver can then be inserted as a complete unit from the back.

Bolts through the holes which are punched in the chassis flanges hold the receiver in the case. The back is thin plywood or paxolin, held by small wood-screws.

An extending telescopic rod aerial can be fixed to the left-hand side and connected by a short flexible lead to the co-axial socket. The latter can also be used for an external aerial.

## AERIALS


In those areas where VHF transmissions are normally well received a telescopic aerial or short wire should be quite adequate. The wire can be 2ft. to 6ft. or so long. The position of the receiver and aerial can influence volume, even with a vertical aerial.

It is also easy to try wires which are very long in terms of wavelength and part of the aerial system can then be out of doors. But with rather long wires the chances of 10·7MHz breakthrough are increased.

Best possible results are obtained by making a VHF type aerial of suitable dimensions for a chosen band. The aerial can then be high and in the clear outside, a co-axial down-lead going to the receiver. This can give a very great increase in signal strength.
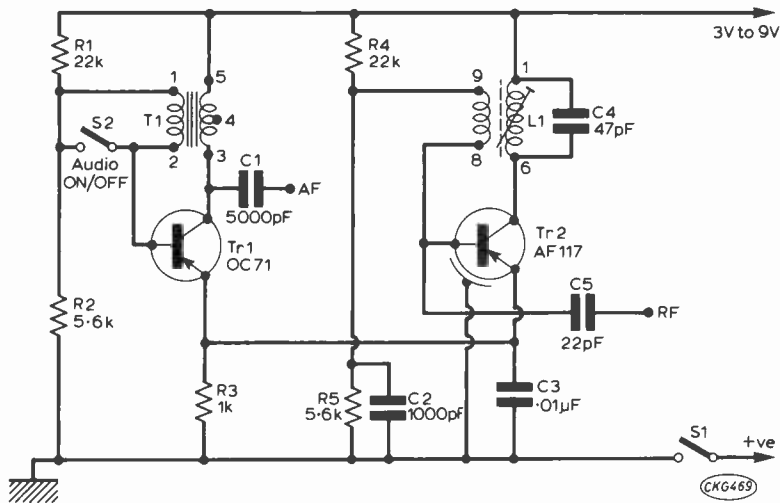
## ALIGNMENT GENERATOR

If necessary, a simple 10·7MHz alignment generator can be built using the circuit shown in Fig. 6. Tr1 is an audio oscillator and output from this may be taken, via the isolating capacitor C1, from the "AF" pin. This output may be useful for checking the AF circuits as well as providing amplitude modulation (and a certain amount of FM also) of the RF oscillator Tr2. The RF oscillator is tuned by means of the core of L1 and output can be had via C5 at the "RF" pin. Enough input to the IF strip may be obtained by just placing the generator near the circuits of IFT1.




◀ Fig. 6: Circuit diagram of the simple alignment oscillator providing RF or modulated RF at 10.7MHz.

▼ Fig. 7: Most of the components for the oscillator are mounted on the circuit board shown below.

Constructing this generator is straightforward. A 5in. x 2in. flanged "universal chassis" member has its flanges cut 2in. from one end, so that a 2 x 2in. section can be bent at right angles. Two toggle switches (S1 and S2) are mounted on this part, near the top and edges to clear the transformer T1.

The generator is assembled on a small piece of Veroboard, as in Fig. 7. Drill the board for the pins of L1 and T1 and for two 1/2in. 6BA bolts, which with extra nuts will provide the chassis return and allow the wired board to be mounted in the small chassis described. Two Veropins are inserted, at the points "AF" and "RF" so that leads can be clipped or soldered on, if wanted. If preferred, two small sockets could be mounted between the switches and be wired to these pins.

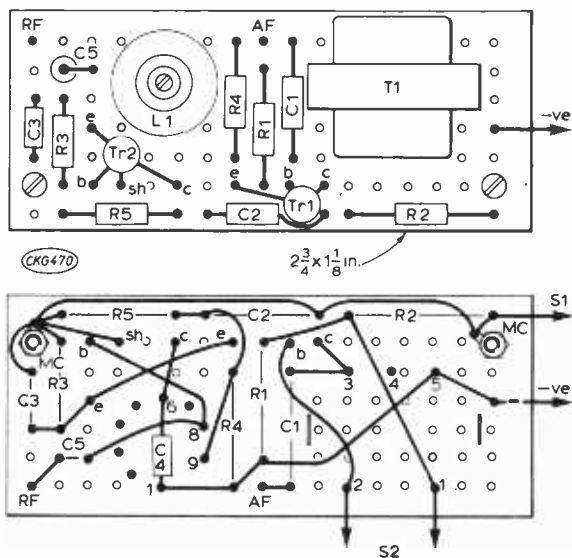
The circuit was found to operate with any battery from 3V to 9V. When S2 is open, an audio tone accompanies the signal, when this is tuned in. With S2 closed, no modulation is present. The modulated



signal is more easily found on a receiver or obtained through the IF amplifier, but the unmodulated signal is used for final alignment, in the way explained.

If an accurately calibrated receiver is available set this to 10.7MHz and rotate the core of L1 to tune the generator accurately to this, with S2 closed for final adjustment. If an accurately calibrated signal generator can be borrowed (but will not be available later) set the generator to 10.7MHz, tune this in on another receiver, and adjust L1 (with S2 closed) for zero beat.

With an FM receiver with 10.7MHz IF, place the alignment generator near this and adjust L1 to the correct frequency. If no such receiver is available, open S2 and place an insulated lead from the "RF" pin near the 1st IFT of the IF amplifier, which should give a strong enough signal for the core of L1 to be adjusted. Subsequently, reduce the coupling as much as possible, so that the IFT cores can be peaked as described, with S2 closed. There is no need for the IFT's to be exactly on 10.7MHz provided all the cores can be peaked and are still free to be moved either way. ■

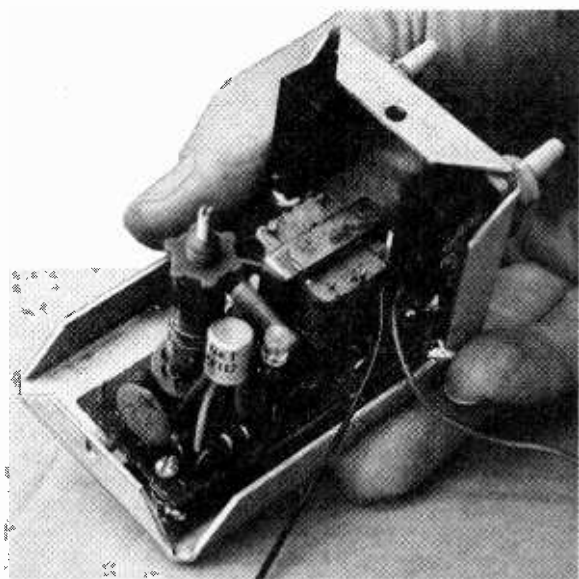

As can be seen here the oscillator is very small and is easy to construct.

# MAGNETIC AMPLIFIERS

PART 1

I. R. SINCLAIR

**A**mplification of d.c. and very low frequencies with very high gain, no valves or transistors, high output power capabilities—these are some of the advantages of magnetic amplifiers. Despite all these advantages, magnetic amplifiers are hardly ever used outside industrial electronics, yet they could be of great use in many amateur applications calling for low frequency amplification; applications such as motor speed control, photoelectric amplification; temperature control, or servo systems.

Probably the strongest reason for this is the lack of complete information on the working of a magnetic amplifier, textbooks either describing the amplifier as if magnetic theory were well known to the reader, or ignoring them altogether. This article sets out to fill the information gap.

## MAGNETIC CIRCUITS

One of the causes of the information gap is the way in which magnetism is taught in schools. We learn about magnetic poles and the simple "laws" of magnets as they were known 150 years ago, but nothing of the later developments in magnetic theory which made the solution of magnetic problems so much easier. We cannot, in this space, even attempt to outline the whole of modern magnetic theory, but we can take a look at the part of magnetism regarding magnetic materials and magnetic circuits which forms the basis of magnetic amplifiers.

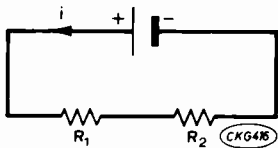


Fig. 1: Simple circuit to demonstrate Kirchoff's Second Law.

Figure 1 shows an electric circuit with a cell producing a current through two resistors in series. Now the voltage (electromotive force) across the cell is equal to the sum of the products of current times resistance for each resistance, or to use the mathematical form,  $V = R_1 \times i + R_2 \times i$ , which is Kirchoff's Second Law. This electric circuit is simple to deal with because the flow of current is exclusively in the circuit with no current flowing in the air around.

We can draw a very close comparison between the electric circuit of Fig. 1 and the electric magnetic circuit of Fig. 2, but with the exception that magnetic effects can be detected in the air around a magnet and do not confine themselves to the metal portion of the magnet. Designing magnetic circuits is rather like trying to design electric circuits to work in salt water; though the surroundings do not conduct so

well as the wires, they have a considerable effect, and current will flow even if there is a gap in a circuit.

If we imagine a magnet as a "cell", having two terminals and a **magneto-motive force** corresponding to the electromotive force of a cell, and the magnetic effect as a flow of magnetic current, or **flux**, then the similarity is obvious. Add to this the idea of **magnetic resistance** or **reluctance** for each piece of the magnetic circuit and we can make a Kirchoff's Law for the magnetic circuit.

$$MMF = R_1 \times N_1 + R_2 \times N_2$$

where R is **reluctance** (magnetic resistance) and N is **magnetic flux**.

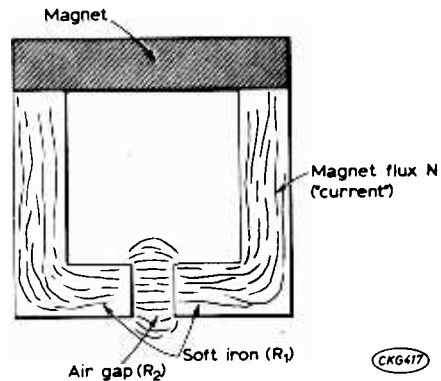


Fig. 2: The magnetic equivalent circuit of Fig. 1.

This idea is useful in the design of transformer cores, relays, and other electromagnetic devices but cannot be used as simply as Kirchoff's Law, because the reluctance is not as constant as the simple resistance of Kirchoff's Second Law, but varies with the flux. Despite this complication, however, the idea of a magnetic circuit is useful, especially since the greatest reluctance in most magnetic circuits is the air-gap (or any other gap not closed by magnetic materials) which is constant at any value of magnetic flux.

It is rather like the case of a circuit of several resistances in series, all about 100Ω but varying with current (as thermistors do) except for one which is about 15KΩ and which "swamps" the others. In the same way, the large reluctance of an air-gap in a transformer core makes design easier because it makes it unnecessary to bother too much about the precise reluctance of other portions of the circuit.

Incidentally, the idea of MMF is used mainly with electromagnets. When permanent magnets are incorporated in a magnetic circuit, as in polarised relays, they are treated as a "negative reluctance" which contributes flux, rather than as a source of m.m.f.



## MAGNETIC FIELD STRENGTH AND FLUX DENSITY

If we wind a solenoid and pass a measured current through it, we find that the magnetic effect, provided that no iron or other magnetic material is present, depends only on the current  $i$ , and the number of turns of the coil per unit length. For a very long coil, the magnetic field strength is simply  $H=N \times i$ , and  $H$  is measured in units of amperes/metre. As far as we are concerned this is a measure of the force which this solenoid would exert on a compass needle at a distance.

If a core of iron or any magnetic alloy is now placed inside the coil, the effect on a compass needle is greatly increased. The magnetic field has magnetised the iron, and the two different effects are adding together. We can measure this in the same way, but several old and confusing mistakes can be avoided if we measure this new effect by using **induction**. When a current changes in a coil which is wound on the same core as another, there is a voltage induced in both coils which is proportional to the number of turns and the rate at which current is changing. The quantity which changes the iron core is the **magnetic flux** which we met earlier and is measured in Webers or volt-seconds.

We find that the effect of a solenoid with an iron core can be measured by dividing the flux in the core by the area of cross-section of the core; this unit is called **flux-density**, and it is measured in Teslas ( $T=1$  Weber/ $m^2$ ) and given the symbol **B**.

## RELATION BETWEEN B AND H

If we set up the solenoid of the first example with an ammeter for measuring current, so that we can calculate  $H$  and a search coil close by connected to a flux meter so that we can measure  $B$ , we can place a magnetic material in the core of the solenoid and measure both  $B$  and  $H$  over a range of values. When we do so, we get a graph of the kind shown in Fig. 3. Starting from  $H=0$  and slowly increasing, the curve rises sharply and then flattens off until the rate of rise is equal to the rate of rise of  $H$ . When  $H$  is decreased again, the value of  $B$  does not take the same values as it did on the way up.

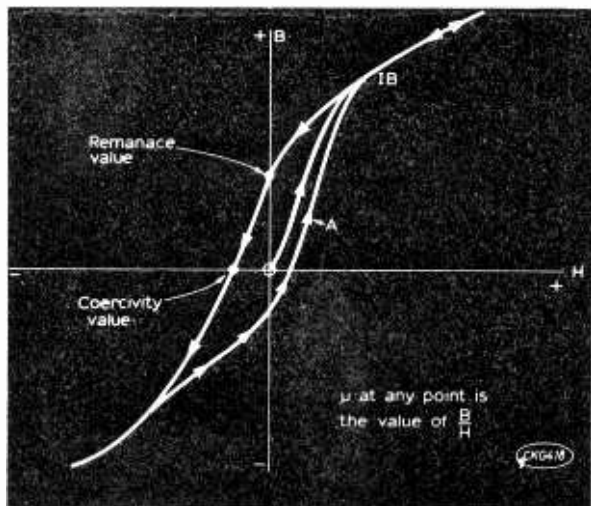


Fig. 3: Graph showing relation between 'B' and 'H'. (Note: For 'remance' read 'remance'.)

The value of  $B$  left when  $H=0$  again is called the **remance** and measures the ability of the material to be permanently magnetised. To reduce  $B$  to zero, an opposite value of  $H$  (called the **coercivity**) must be applied. As the values of  $H$  in the opposite direction are increased, the curve traced out becomes the opposite of the one previously traced, but the first portion of the graph is never traced again unless the iron can be completely demagnetised (by heating, for example) and the experiment repeated.

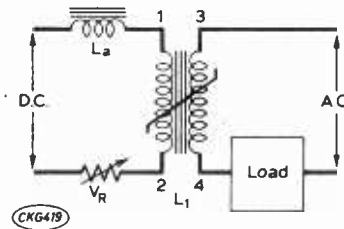


Fig. 4: Simple magnetic amplifier. The DC input to the 'primary' is not a mistake! See text.

The interesting portions of this curve, called a hysteresis curve, for our purposes are the steep sides and the flattened top. When the current in the coil is at a value corresponding to point A on the curve, the flux density changes considerably with a change of current, a condition which is ideal for a transformer or choke since it means the greatest possible reverse voltage, and so the maximum inductance. When the current in the coil is at a value above point B, the change of flux density is *very* much less, and the material of the core is said to be **saturated**. In this condition, an increase of current in the coil causes very little increase of flux density, very small induced voltage, and so very little opposition to change of current (low inductance) so that large currents can flow. A core which includes an air gap limits the flux density because of the reluctance of the air gap and so reduces the possibility of saturation, which can have serious effects in transformers. A core which consists of a circle of magnetic material will saturate easily because of its low reluctance.

Many text books quote the permeability of a magnetic material  $\mu$  as if it were a constant. As can be seen from the curve of Fig. 3, it is not a constant, but varies with the magnetic field strength, so that the only value which has any real meaning is the maximum permeability, the value of  $\mu$  at point A on our curve, because this indicates the usefulness of the material for a transformer core.

## A SIMPLE MAGNETIC AMPLIFIER

Figure 4 shows the circuit of the simplest form of magnetic amplifier. This consists of the choke  $L_1$  which is provided with two windings on a core of material which saturates easily (no air gap) and which has a very small area enclosed by the forward and return paths, meaning that the energy spent in magnetising and de-magnetising the core is not too large. Such a multiple winding choke (it is *not* a transformer, despite the similarity of the symbol) is termed a **reactor**. The winding marked 3, 4 is used as a choke in an a.c. secondary circuit, and the winding marked 1, 2 is used to apply magnetic flux to the core by passing a steady current. The winding 1, 2 is usually known as the **control winding**, and a


# SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT  
NEW & SECONDHAND MUSICAL INSTRUMENTS.  
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.
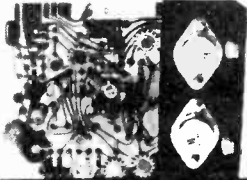
## SA25 - SA35 - SA100 LOW-PRICED AUDIO MODULES

FOR DOMESTIC  
& COMMERCIAL  
USE

New Versions using 3A  
'Plastic Power' Driver  
Transistors Now Available



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

**SA25 £2.95** carr. free

25 WATTS RMS. 7 transistors 7 diodes

**SA35 £4.45** carr. free

35 WATTS RMS. 7 transistors 7 diodes

**SA100 £10.90** carr. free

100 WATTS RMS. 11 transistors 8 diodes

ALL THREE MODULES HAVE OPEN & SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION & FAULTY INDUCTIVE LOADS. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRA-ORDINARILY LOW PRICES POSSIBLE.

### BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000 Hz ± 1dB
Distortion	0-2% at 1 kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75 dB
Supply voltage	SA25/35 25-45 volts SA100 40-70 volts
Size	4½" x 4" x 1" (SA100) 4" x 3" x 1" (SA25/SA35)

Circuits, connecting instruction and application data are supplied free with all modules.

### POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilized supply for 2 SA25/35	£4.90
PU70	Unstabilized supply for one or two SA100	£7.75 carr. 40p
PS45	Stabilized module for 2 SA25's or two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3.50 carr. 20p
PS70	Stabilized supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON  
GLASS FIBRE P.C. BOARD  
AND ARE SUPPLIED FULLY TESTED

Orders and personal shoppers to:

**SAXON ENTERTAINMENTS LTD., 327-331 Whitehorse Rd., W. Croydon, Surrey. CR0 2HS.**

Telephone 01-684 6385

Hours 9.30 a.m.-5.30 p.m.

TRADE & EXPORT ENQUIRIES INVITED

## OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE £13.90 + 20p carr. or with supply  
**£18.95** + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers, etc., and most other makes of mixer. It delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors.

### SPECIFICATION

Power output	120 watts into 8 ohms
Freq. response	20-20,000 HZ ± 2dB
Input sensitivity	200 mV into 10K
Construction	Fibreglass board
Size	8" x 4" x 4" (5" with supply)
Low distortion parallel push-pull output stage.	



**NEW** 160 watt version & supply **£27.90**

## SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100 watts. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.



**£8.90** carr. free



## THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3000 watt (3kw) this unit is unique for its price in that not only bass, middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in Tough Steel case for free mounting or panel fixing. Fully guaranteed.

**£19.75** carr. 30p

MONO VERSION £6.50 carr. 20p (As Illustrated. S.A.E. details 9 volt operation) Outputs up to 1 volt RMS



**£15.80** carr. 30p

## SAXON STEREO CONTROL UNIT

Two decks, and full headphone monitoring. The unit is mains operated and measures 17½" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE. (N.B.—Stereo only has mic input.)


## COMPLETE AMPLIFIERS

### CSE 100. £34.90 carr. free

This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups D.J.S., etc.



### SAXON 100 £48.50 carr. free

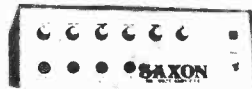

With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

### LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £5.95 carr. 30p. 15" 50W.8/15 ohm £14.50 carr. 50p.  
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p.

600 Watt 3 colour Light Boxes Smart Rexine finish £15 carr. free.

**A.K.G. MICROPHONES** suitable for disco, group or general P.A. use.  
D11 DHL IDEAL DISCO MIKE ONLY £9.45 (rrp £11.00).

SEND SAE FOR OUR A.K.G. PRICE LIST. DISCOUNTS ON ALL MICS.

All prices subject to VAT at standard rate

### TERMS OF BUSINESS

Cash with order (C.W.O.) For C.O.D. please add 35p extra, cash by regd. letter, please

**Why pay more - look at our Fantastic Bargain Offer!**

**PENTHOUSE**

**A COMPLETE AUDIO SYSTEM**

An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder, 4 wavebands Long/Medium/Short/VHF, 8 watts per channel (music power) output. The latest BSR C129 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units.

**OUR PRICE £55-00**



Credit terms £5 00 deposit plus £2.00 p. & p. followed by 12 payments of £4.80. Total Credit Terms £62.60 SEND £7.00 TODAY.

**BENSON**

**BENSON MW/FM/MPX STEREO 8 TRACK**


AM/FM radio with decoder for stereo radio with integral 8 track cartridge player. Portable for operation from internal batteries or A.C. mains or 12V Car/Boat cigar lighter socket. Unit divides into two for stereo reproduction.

Our price £39.95. Credit terms £5-00 deposit plus 12 monthly payments of £3.40 (Total £45.80), p. and p. £1.00. Send £6 Today!



UNIT DIVIDES TO GIVE 2 SEPARATE STEREO SPEAKERS

**THE AVON AUDIO SYSTEM**

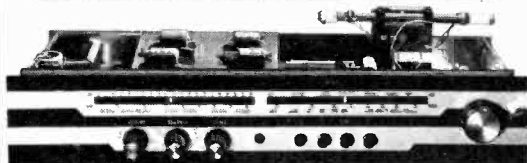

The uncabineted system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

BSR 4 SPEED STEREO/MONO RECORD CHANGER plays all types or 7in., 10in., and 12in. Mono or Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKER. These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.

EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45.74. OUR PRICE £35.00. Credit Terms £3.50 deposit plus £2 Post & Packing followed by 12 payments of £3.10 (Total Credit Terms £40.70) Don't miss this bargain.

SEND £5.50 TODAY

ALL EQUIPMENT COVERED BY 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

Please send me free details of your range

Name .....

Address .....

PW 7/73

LEWIS radio 100, Chase Side London N.14 Tel: 01-886 3733/9666

Post coupon NOW for... **FREE** leaflets



**ELECTRONIC ORGAN KITS**

★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £406.00. ★ Console—2 x 5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at £572.55. V.A.T. please add 10%—show separately on order.

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE, WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT, ELECTRICAL HOUSEHOLD APPLIANCES AND MUSICAL INSTRUMENTS.

**ELVINS ELECTRONIC MUSICAL INSTRUMENTS**

8, PUTNEY BRIDGE ROAD, LONDON, S.W.18  
TEL: 01-870 4949



**become a RADIO-AMATEUR!**

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

**free!**

Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL** P.O. Box 156, JERSEY

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

WB73 BLOCK CAPS please

choke La is wired in series with this winding to prevent a.c. being fed to the control voltage source through transformer action in the reactor.

Imagine that no d.c. is applied to the control winding. The winding 3, 4 then acts as a choke (providing that the current through it is not too large) so that only a fraction of the alternating voltage applied to the secondary circuit can appear across the load resistor. If now some current flows in the control winding, the condition can be reached where the sum of flux due to the control winding and flux due to current in the secondary winding cause the core to saturate. At saturation, the inductance of the secondary winding is very low and a high current flows in the load, so that the average current through the load increases. This is equivalent to shifting the bias conditions of the amplifier, and this shift in the operating point is shown by the curves of Fig. 5.

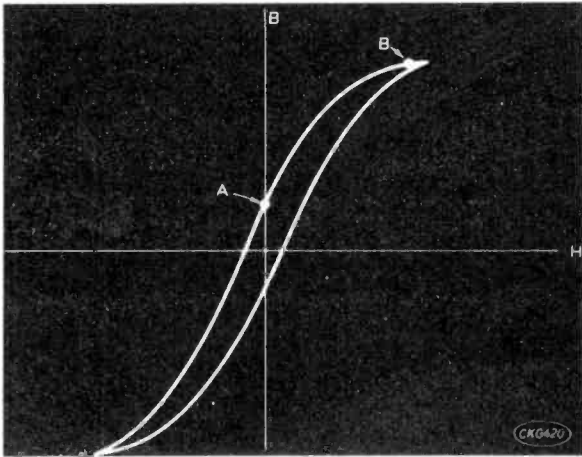


Fig. 5: At A,  $\mu = \frac{B}{H}$  is high, and the inductance of the coil (proportional to  $\mu$ ) is high. At B the reverse obtains.

This type of magnetic amplifier is known as a straight-saturating amplifier and is seldom used because the sensitivity is low and the waveform across the load is distorted. It does, however, illustrate well the principles involved in magnetic amplifiers, and is easy to construct. The current amplification produced is equal to the ratio of turns of the control winding to the turns of the secondary winding (that is, the same as the ratio of a conventional transformer); note that the step up is from d.c. in the control winding to a.c. in the secondary winding so that this offers a method of controlling a.c. by means of a d.c. source.

## SELF SATURATING MAGNETIC AMPLIFIERS

For many purposes, greater sensitivity and a better waveshape are required and these requirements have resulted in the self saturating magnetic amplifier, which uses the secondary current to contribute more to the saturation of the core. This is achieved by making the secondary current travel only in one direction in the core. If the core is already saturated by the control current the inductance is very low and the secondary current is unimpeded.

TO BE CONTINUED NEXT MONTH

# TELEVISION

## JULY ISSUE

### RENOVATING THE PHILIPS G6 CHASSIS

Continuing his series on renovating and fault finding in ex-rental colour chassis Caleb Bradley starts to work this month on the first Philips chassis. We've plenty of tricks to tell you on this one.

### DC RESTORATION CIRCUIT

Many single-standard monochrome chassis have a perfectly stable vision signal at the detector but then lose the black level through a.c. coupling in the video section. Keith Cummins has developed a circuit to give d.c. restoration at the c.r.t. cathode however. Development was undertaken using the popular BRC 1500 chassis but the circuit could be adapted for other chassis.

### WORKSHOP HINTS

Vivian Capel turns his attention to tuning capacitor gangs, both radio and TV receiver types, describing the fault conditions that arise and methods of dealing with them.

### COLOUR RECEIVER INSIGHT

Much insight into colour can be obtained by examining the wide variety of circuitry used in different chassis. This month we take a look at the Korting 51763 series which incorporates many novel features including an unusual ident stage and tube protection on the event of field collapse.

### FAULT FINDING GUIDE

This month John Law switches his attention to a typical i.f. panel (Bush TV141/Murphy V159 series) and describes the faults that arise and trouble-shooting procedures to be adopted in this part of the receiver.

### PLUS ALL THE REGULAR FEATURES

TO .....  
(Name of Newsagent)

Please reserve/deliver the JULY issue of TELEVISION (20p), on sale JUNE 18 and continue every month until further notice

NAME.....


ADDRESS .....

.....

# PRODUCTION LINES

colin riches

## 4D STEREO

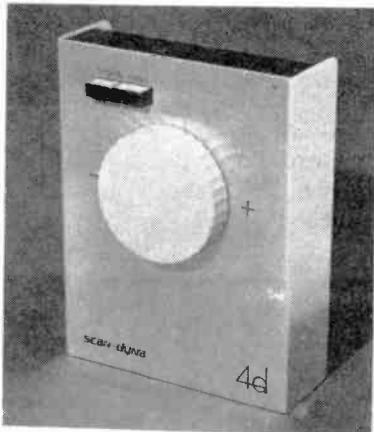

This is a Scan-Dyna 4d stereo unit. Used in conjunction with a stereo amplifier and 4 speakers, it damps the direct signals to two back speakers, permitting the reflected sounds from the back to be made


separate from the direct sound of the front two speakers.

The outputs from the amplifier channels are fed to the 4d unit. The four speakers are then plugged into DIN speaker sockets on the unit and the large knob can be rotated to control the volume of the back two speakers.

By use of the 4d unit, a 4-channel effect is produced which gives a very pleasing sound. In the unit (shown) the push-button marked "front" disconnects the back two speakers so that the stereo amplifier can operate as a normal 2-channel system. The push-button "test" is used to adjust correct balance between the two front speakers. One point of warning, however, it is essential that a correct phase connection is made between the amplifier and the 4d unit. Price is £12.90 plus VAT and your local hi-fi dealer should have 4d units in stock.
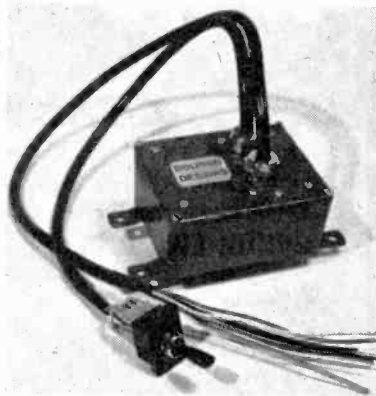
## ELECTRONIC IGNITION

A recently announced transistorised ignition system from Dolphin Designs has its casing made from diecast aluminium with a special epoxy finish. All metal parts are cadmium plated and connections are through watertight glands. All metals are plated to prevent electrolytic corrosion and the circuit is built on a fibreglass board with a double thickness of copper. The unit is designed for 12V cars with either positive or negative chassis.



A dash-mounted switch will revert the car to conventional ignition whilst driving either for comparison or the unlikely event of failure. The ignition system is priced at £12.95, plus 30p postage, plus VAT, and is available from: *Dolphin Designs, 59 Leighton Avenue, Leigh-on-Sea, Essex.*


## PEAK PROGRAMME METER

The PPM concept was developed by the BBC for checking modulation depths at transmitters, and the modern derivative (BS 4297) is used in the broadcasting and sound recording fields. The standards define attack and decay times and logarithmic meter scaling, with positive and negative peak detection as some sounds have + and - levels differing by up to 8dB. The drive circuit, produced by Surrey Electronics is for 1mA L.H. zero meters and is available as a kit at £8 or built and aligned at £12.

The attack time is 2.5mS, decay rate 1dB per 100mS and detection + and - peaks within 0.5dB. Display is a log. meter scale of 6 with 4dB divisions (-22 to +4) or BBC style 1 to 7. Accuracy is within 0.3dB and frequency response -0.5dB (20Hz-20kHz) -1.0dB (12Hz-30kHz). Input impedance is 100kΩ and supply is from +24V to 50V. Consumption is 25mA.


Ernest Turner special "ballistics" meters type 642 cost £9 and 643 £10.70. Further information from: *Surrey Electronics, 24 The High Street, Merstham, Redhill, RH1 3EA, Surrey.*

## ADVANCE ALPHA

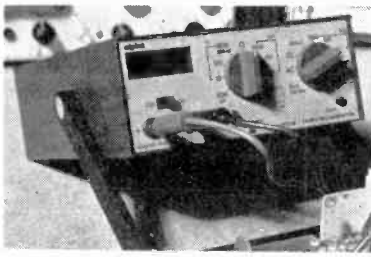

This digital multimeter from Advance costs £55. A total of 24 ranges indicate d.c. voltages from 1mV to 1kV, a.c. voltages from 1mV to 500V, d.c. and a.c. current from 0.1μA to 1A and resistance from 0.1Ω to 10MΩ.

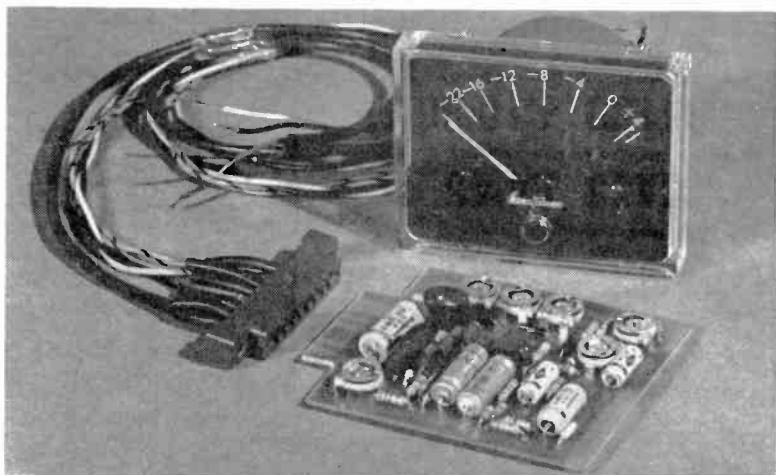Two other instruments in the Advance "pipeline" are the TC17 timer counter and DVM44 digital voltmeter. *Advance Electronics Ltd., Instrument Division, Raynham Road, Bishops Stortford, Herts.*








**I.L.P. (Electronics) Ltd**

# 100 WATTS!

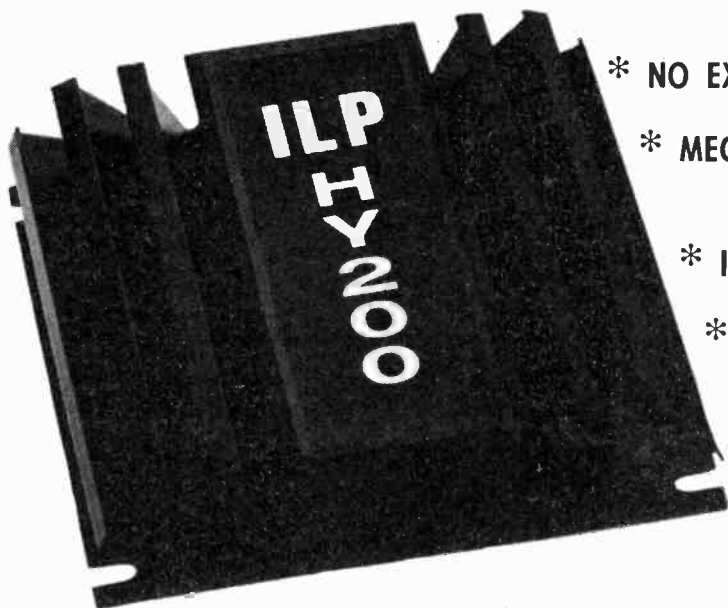

- \* NO EXTERNAL COMPONENTS
- \* MECHANICALLY & ELECTRICALLY ROBUST
- \* INTEGRAL HEATSINK
- \* HERMETICALLY SEALED UNIT
- \* ATTRACTIVE APPEARANCE
- \* LOW COST
- \* BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

**COMPLETE:** because the HY200 uses no external components!

**COMPLETE:** because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

**OUTPUT POWER:** 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE:** 10k $\Omega$ . **INPUT SENSITIVITY:** 0Dbm (0.775volt RMS). **LOAD IMPEDANCE:** 4-16 $\Omega$ . **TOTAL HARMONIC DISTORTION:** less than 0.1% at 100 watts, typically 0.05%. **SIGNAL : NOISE:** better than 75Db relative to 100 watts. **FREQUENCY RESPONSE:** 10Hz-50KHz  $\pm$ 1Db. **SUPPLY VOLTAGE:**  $\pm$ 45volts. **APPLICATIONS:** P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE:** £14.90 inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

Now available from one company are complete kits for many of the articles published in the Electronics, Radio and TV Journals. Examples of our range are:

**SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971) £9-50.** This kit includes all the parts for the assembly of this popular and reliable system. The hardware and the construction data are included.

**DRILL SPEED CONTROLLER (E.E. Aug. 1972)** Kit consists of resistors, rectifiers, thyristors and tag board as specified in the article, price £1-15. Kit with M.K. box, switch and plate included £2-30.

**ELECTRONIC PIANO (P.E. Sept. 1972)** We can supply the various sections for this article in kit form:—

**POWER SUPPLY £6-60,** including all semi-conductors, resistors, capacitors, transformer, heat sink and hardware less P.C.B.

**PREAMP AND TREMELO £3-20,** complete with switches hardware and electronic components, less P.C.B.

**MAIN AMP £4-20,** complete with IC-12, electronic components and P.C.B.

**13 PITCH BOARDS £39-50.** Kit contains all the resistors, capacitors and semiconductors as published, but not the P.C.B.'s or the inductor.

**LIGHT DIMMER.** Kit contains all parts including circuit and construction data, 480 watts, fully suppressed. Price £2-10.

**MUSIC MAKER ELECTRONIC ORGAN (P.W. Nov. 1972)** complete kit £4-40 or kit less resistors, P.C.B. and plastic box £2-80. Stylus not supplied.

**MIGHTY MIDGET (P.W. Jan. 1973)** kit contains all parts, less the battery, box and knob, £2-25.

**TRIFFID RADIO (P.E. Feb. 1973).** Kit includes all parts listed, less "tuning coil" and "miscellaneous components". £4-95. Ferrite rod and wire, optional extra at 50p, P.C.B. optional extra at 65p.

We shall be offering kits for most articles published in the popular electronics magazines and will be pleased to quote prices. Send for details of kits available (please enclose S.A.E.).

All kits sent post FREE, within the limits of the UK

We regret that prices shown do not allow for V.A.T. Please add 10% to your order.

Please note we reserve the right to withdraw kits without prior notification.




12 Lauderdale Road, London W.9.  
Telephone 01-286 0011 Telex 28479

# Electrokit

## SAVE TIME AND MONEY

LIST PRICE **£6-87** | OUR PRICE **£5-32**  
INCLUDING V.A.T.

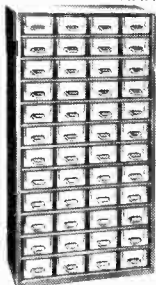

As supplied by us to **SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY.** Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21" x 11" x 6". Size of drawers 6" x 2" x 1". Other sizes available. Callers welcome Mon.-Sat. 9 a.m.-1 p.m. 2 p.m.-6 p.m. **NEW as illustrated OUR PRICE ONLY £5-32 plus 35p carriage on orders less than £10.** Money back guarantee. **SEND FOR FREE LISTS.**

## TRADE AIDS

(DEPT. PW12), 111 CHILTERN DRIVE,  
BERRYLANDS, SURBITON, SURREY  
01-399 4383

100 yds. Berrylands Railway Station.

## TRANSFORMERS

DOUGLAS GUARANTEED  
Prices include 10% VAT & P. & P.

Output V. & Amps	Ref. No.	Price	
12V x 2 250 mA x 2	MT111 CS**	£1-11	
12V x 2 500 mA x 2	MT213 CT**	£1-48	
12V x 2 1A x 2	MT 71 AT†	£1-58	
12V x 2 2A x 2	MT 18 AT	£2-59	
12V x 2 3A x 2	MT 70 AT	£3-20	
12V x 2 4A x 2	MT108 AT	£3-58	
12V x 2 5A x 2	MT 72 AT	£4-12	
12 or 24 volts			
30 volts. All tapped at 0-12-15-20-30V.			
Output Ref. No.	Price	Output Ref. No.	Price
500 mA MT112 CT†	£1-41	4A MT21 AT	£3-83
1A MT 79 AT†	£1-92	5A MT81 AT	£5-20
2A MT 3 AT	£2-78	8A MT88 AT	£7-50
3A MT 20 AT	£3-25	10A MT89 AT	£8-46
50 volts. All tapped at 0-19-25-33-40-50V.			
500 mA MT102 AT†	£1-84	3A MT105 AT	£4-75
1A MT103 AT	£2-55	4A MT106 AT	£6-02
2A MT104 AT	£3-78	5A MT107 AT	£8-87
60 volts. All tapped at 0-24-30-40-48-60V.			
500 mA MT124 AT†	£1-94	2A MT127 AT	£3-83
1A MT126 AT	£2-81	3A MT128 AT	£5-50

### AUTO-WOUND RANGE

Power output	Winding tapped at	Ref. No.	Price
20VA	0-115-210-240	XMT113 CT	£1-16
75VA	"	XMT 64 AT	£2-22
150VA	0-115-200-220-240	XMT 4 AT	£2-71
200VA	"	XMT 85 AT	£3-55
300VA	"	XMT 68 AT	£4-54
400V. Output at 50Hz.	Ref. ITS AT		Price
C-D Ignition System by R. M. Marston, Esq., Wireless World			£2-85

### EQUIPMENT RANGE


Sec. Output (r.m.s.)	Ref. No.	Price
3-0-3 V. 200 mA	MT238 CS**	£1-18
9-0-9 100 mA	MT 13 CS**	£1-18
12-0-12 50 mA	MT239 CS**	£1-18
20-0-20 30 mA	MT241 CS**	£1-18
0-20 x 2 300 mA x 2	MT214 CT**	£1-61
0-8-9 x 2 500 mA x 2	MT207 CT**	£1-77
0-15-20 x 2 500 mA x 2	MT206 AT**	£2-72
0-15-27 x 2 500 mA x 2	MT203 AT*	£2-02
0-15-27 x 2 1A x 2	MT204 AT*	£4-09
20-12-0-12-20 700mA (d.c.)	MT221 AT*	£1-51

AT Indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; \* with interwinding screen; † untapped 240V Primary; ‡ tapped at 210-240V; other Primaries tapped at 200-220-240V. Over 200 types in stock through agents or direct. Please send for lists.

DOUGLAS ELECTRONIC INDUSTRIES LTD.,  
Direct Sales Dept. (FW),  
Thames Street, LOUTH, Lincs. LN11 7AD

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION

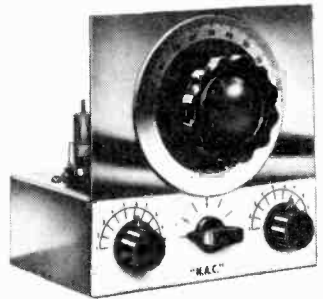


Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hains, etc.
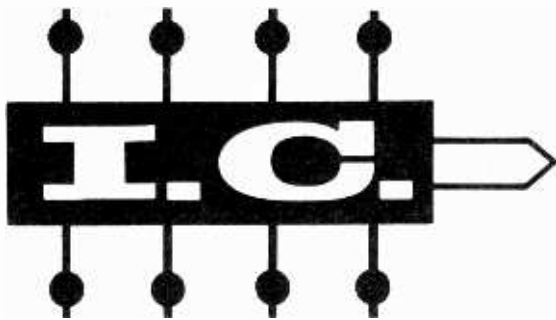
### NEW "DX" RECEIVER

Complete kit—price £3-95 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume." "I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, test report and order form. **EXCITING COMPETITION for Short-Wave listeners.** Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1



# OF THE MONTH

L.A.J. IRELAND

Number 39

## SGS TBA435 VOLTAGE REGULATOR

STANDARD portable transistorised equipment commonly operates from a 9 volt battery supply. When the occasion arises for such devices to be operated from a 12 volt supply, for example on a car battery, it is clearly necessary to provide some form of voltage dropper. This is not as simple as at first appears, due to the common use, for example, of class B output stages in portable equipment. Since it is not a constant current load, therefore, it is impossible to insert a simple resistor to provide the reduced supply voltage.

Neither is a potentiometer arrangement adequate, since it requires a standing current greater than the drain of the device in use. Zener diodes face a similar objection, and the integrated circuits available to date have generally required complex interconnections and several discrete components to set the required output voltage. Hence the advantages of the TBA 435, a simple three terminal device specifically designed to provide a fixed output voltage of 8.5 volts when operated from any power source between 10.5 and 20 volts. Its applicability to the problem of operating 9 volt transistorised equipment from automobile power supplies is obvious.

### Performance

The device is capable of supplying continuously a current of over 100mA. at the rated output voltage, representing an internal power dissipation of 0.75 watts, increasing to 4 watts if mounted on an

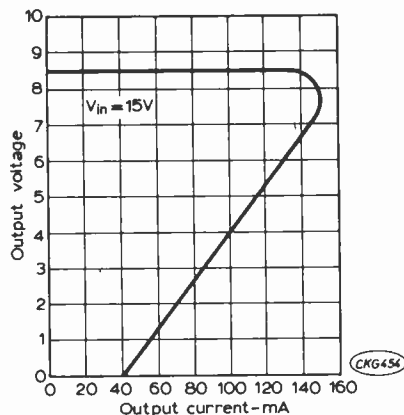


Fig. 1: Output regulation curve. Note action of protection circuit as rated current is exceeded.

adequate heat sink. The circuit is, of course, fully protected against overload and even short-circuit conditions, while maintaining the rated output voltage to within 1% over the design range.

The operation of the protection equipment is fully illustrated in Fig. 1, which clearly displays the drop in output voltage if an attempt is made to exceed a safe current. When in automobile use, it may be found advantageous to precede the regulator with an RF choke, to prevent ignition interference entering the system through the power supply lines. However, the IC itself has a capacity to reject ripple and high frequency noise by a factor of some 50dB, a property which is highly significant both for mobile and mains-driven equipment.

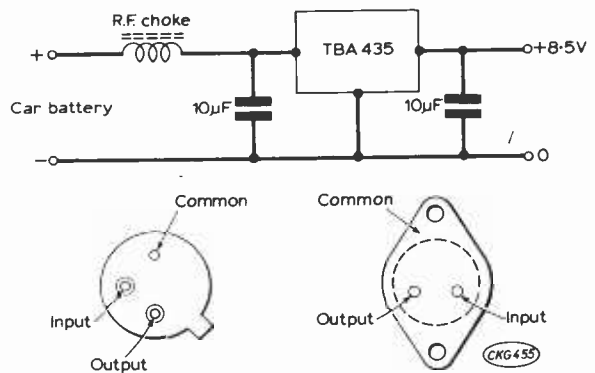


Fig. 2: Practical application of TBA435 and connections for 100mA and 600mA types.

It might be of interest to point out that the TBA 435 is merely one of a series of similar three-terminal integrated circuit voltage regulators with analogous operating parameters but with a range of output voltages. In any case where a power supply must provide a well regulated protected output at a fixed voltage, the appropriate unit from this series should certainly be evaluated for the application.

Type	TBA 625A	L 005	TBA 435	TBA 625B	L 036	TBA 625C	L 037
Output voltage	5	5	8.5	12	12	15	15
Rated current mA	100	600	100	100	600	100	600

Note: The NE555 reviewed in the May issue is made by Signetics and not SGS.

# practically wireless commentary by HENRY

No. 100

Ton Up

NOT until one of my colleagues and regular readers reminded me of the passage of time was I aware that this contribution is the hundredth Old Henry has made to PW. Have you really endured me that long?

Anniversaries are a time for recall and for resolution. Recall is a facet of Henry's waffling that may at times have seemed to take precedence. Resolution should be



*Brimming over with human kindness*

saved for innovatory dates, the Chinese New Year, the day after the annual holiday, any Monday morning . . .

Instead, if you'll bear with me, I would like to blast off about a couple of subjects that have recently roused my ire—and which, according to my critics, seem to exemplify Henry's approach to radio design, construction, and marketing.

First, the last. And I mean the retailer; your local friendly dealer, as the Radio & Television Retailers' Association would have us believe. Brimming over with the milk of human kindness, intent on social justice and the welfare of his customers, ineffably altruistic . . .

Believe me, the radio retailer who really cares; who came up from bright emitters and the days of the catswhisker; who will spend his precious spare time finding better ways of providing P.A. for the nearby Old Folks Club; whose advice is geared to needs and not mere profit: that chap is as rare as a fridge in an Eskimo's igloo!

Monthly, one reads glowing tributes in the enthusiast magazines from readers who, despairing of help from local dealers, took their gear to the manufacturer, and had satisfaction. I feel a bit wry about that—better that the manufacturer should give his local agent good backing.

I have even read examples of 'turn-around' repairs being done on equipment for which I have had outstanding parts orders for months, and can only think, with typical Henryesque cynicism, that the manufacturer was really thinking of his 'public image'. But that's another story.

As good an example as any of the way 'the trade' does not care was to be seen at Sonex, where Donald Aldous wore himself into the ground in organising a series of lectures. During the two trade days, attendance at the lectures was abysmally small.

Practically the only interest was shown when a quadrasonic demonstration was given, when the lecture theatre became half-filled.

I don't want to enter the surround-sound arena just now, but would agree that discrete four-channel is the only truly 'hi-fi' way of doing things: that, just as with gramophone records, mono/stereo, f.m. broadcasting, commercial radio, colour TV and any other technical innovation, compromise has resulted from the needs of compatibility, and we shall probably have some inadequate system ultimately foisted upon us.

The slogan seems to be: 'Never mind what's best. What can we get away with?'

Very few dealers are today happy to take in repairs. They will tell you that their service department is already stretched to the limit to service the stuff they sell. which, when you think about it, argues that either their workshop is under-staffed or the stuff they sell continually goes wrong.

The truth is that there is little

profit in service. The retailer does not regard good service as necessarily fostering goodwill. In our own establishment, the 'Boss' is fond of saying: 'One second complaint outweighs twenty well-done jobs.'

Which brings me to my second grievance . . . It is possible to make service pay, but only if it is run as a strictly economic business. And that, friends, entails our paying the true price for what we have done.

Take the case of the ordinary interconnecting lead. You can buy made-up packs of practically any plug or socket to any other for round about a pound, often less. But if you want a 'special' lead made by an otherwise busy engineer, you must expect to pay half as much again.

He has to fit this between other jobs, sort out matching more often than not, forage among the rubble for plugs and disentangle cable, set up his mini-vice and lick the end of his soldering iron, muttering incantations the while.

In a workshop like ours, where one of my colleagues waits till I am looking the other way, then 're-organises' all the drawers of



*muttering incantations the while*

small parts, it is lead-making that is most sick-making, and wildly uneconomic.

Perhaps that is why the small dealer no longer exists, and the package-seller who has taken his place shuns service: because we, you and I, are unwilling to pay our whack!



G.H. WOODS

**E**NLARGER timers generally rely mainly on charging or discharging capacitors through variable resistors and an appropriate switching circuit. These timers can give a good repeat accuracy of  $\pm 0.25$  seconds but actual settings can only be as accurate as can be manually calibrated, using a stop watch, in most cases no better than  $\pm 1/2$  second mid-range.

This IC Timer relies for its accuracy on the mains supply frequency; it has a very high repeat accuracy, requires no calibration and is switchable from 0.9-9 seconds in 0.1 second steps and 0.99 seconds in 1.0 second steps—the accuracy directly proportional to that of the mains. It has been my experience that the 0.9-9 second range is useful when printing in colour when filter changes dictate exposures of seconds and fractions of a second.

## CIRCUIT DESIGN

The circuit uses nine TTL i.c.'s. The timing is derived from 50Hz mains supply frequency which is obtained from the secondary of T1 Fig. 1 and fed via a capacitor C1 to a two transistor Schmitt trigger circuit the output of which goes to a control gate. The output from this gate goes to an SN7490, IC4 in Fig. 2, used as a divide by five. The 10Hz output from this goes to a divide by ten, IC5, to give 1Hz. Two more SN7490's, IC6 and 7, are used as divide by ten circuits; the BCD outputs of each one being decoded by an SN7442. The ten outputs of the SN7442's pass to the single pole twelve way wafer switches S2 and 3.

To start the timing sequence S1 is depressed which causes a logic pulse to be fed to the input of a flip-flop of an SN7472, IC3, one output of which goes to the control gate G1 so that 50Hz is applied to the driving circuit; and to gate G2 which is connected to gate G8 controlling the driving circuit. The other output of IC3 goes to the zero reset of the dividers IC4-7.

If, for instance, S2 is on position 4 and S3 on

position 5 then when 45 seconds have elapsed the outputs from the wafer switches are at logic 0 instead of logic 1 as they would have been before the beginning of the timing sequence. These two outputs are inverted using two nand gates G3 and 4 the outputs of which are applied to another nand gate G5 whose output will be at logic 0, when the 45 seconds have elapsed and at logic 1 at any other time.

The output is used to clear the flip-flop IC3 so causing it to revert to its original state which blocks the 50Hz clock pulses, clears the dividers IC4-7 and

## ★ components list

### Resistors

R1 47k $\Omega$	R5 47 $\Omega$
R2 2.2k $\Omega$	R6 4.7k $\Omega$
R3 2.2k $\Omega$	R7 27 $\Omega$
R4 3.3k $\Omega$	R8 150 $\Omega$

All  $\pm 10\%$

### Capacitors

C1 0.68 $\mu$ F	C2 1000 $\mu$ F	C3 10 $\mu$ F
-----------------	-----------------	---------------

All 12VW

### Integrated Circuits

IC1 SN7442	IC4 SN7490	IC7 SN7490
IC2 SN7442	IC5 SN7490	IC8 SN7400
IC3 SN7472	IC6 SN7490	IC9 SN7400


### Semiconductors

Tr1 BC108	Tr3 2N2926	D1 40430
Tr2 BC108	VR MVR5V (RS)	(400V 6A)
BR1 50V 1A bridge rectifier		
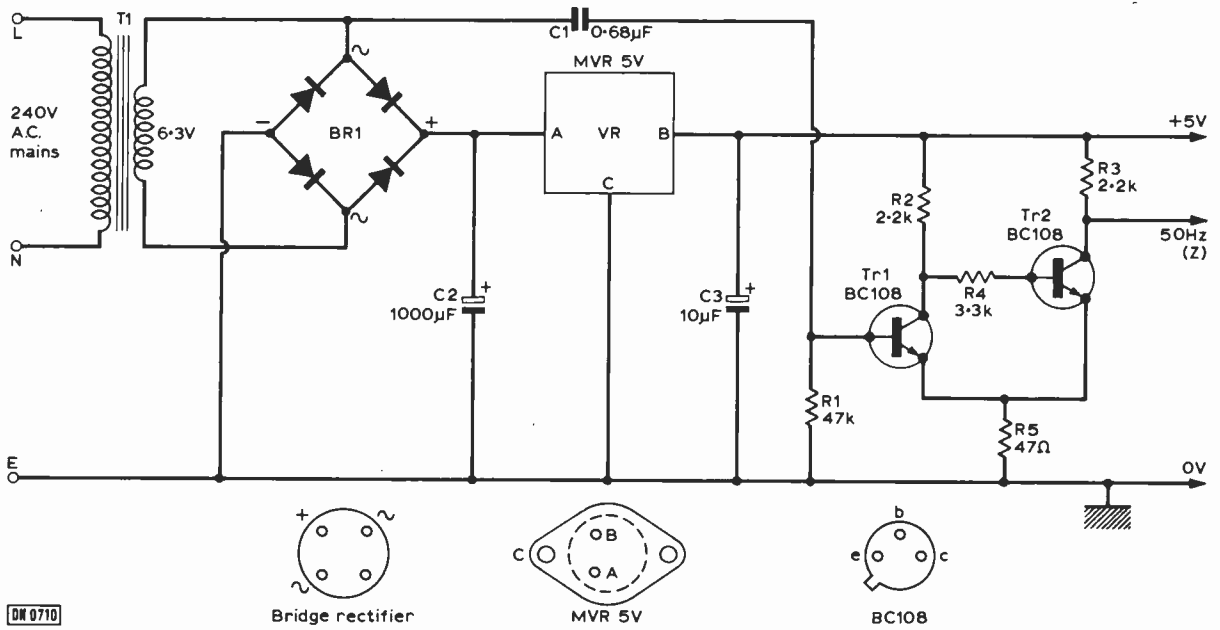
### Miscellaneous


T1, transformer 230/6.3V 1A. S1, SP biased toggle switch. S2 and S3, 2 x SP 12 way wafer switch. S4, SP changeover toggle switch. Veroboards,  $3\frac{1}{2}$  x  $3\frac{1}{2}$ in. 0.1in. matrix,  $3\frac{1}{2}$  x  $2\frac{1}{2}$ in. 0.1in. matrix. Veropins, knobs. Case 8 x 6 x 3in. with lid. Reed coil and switch for 3-5V operation.






▲ Fig. 1: Circuit of 5V stabilised power supply and two transistor Schmitt trigger arrangement.

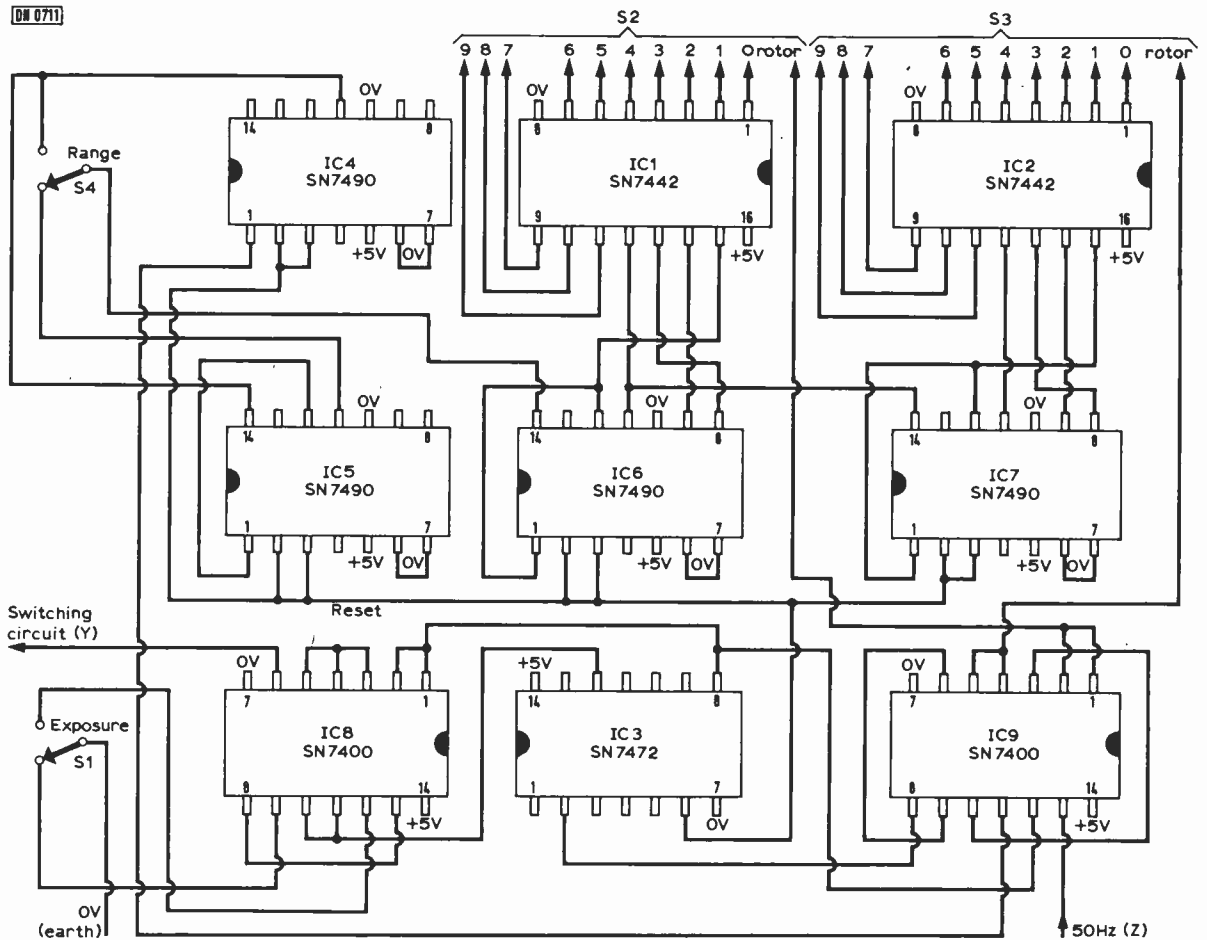▼ Fig. 2: Diagram of interconnections and supply leads for the nine integrated circuits.




switches the triac off via the reed switch. Two nand gates are connected so as to eliminate contact bounce at S1 (gates G6 and 7).

Switch S4 is an added facility which allows the circuit to count to ten seconds in 0.1 second steps and this is achieved by merely short-circuiting one of the divide-by-ten i.c.'s IC5 causing 10Hz to be applied to IC6 instead of 1Hz. When either or both wafer switches are set on positions 11 and 12, closing S1 switches the triac on which is held on until S1 is closed again; this facility allows the enlarger to be on for focusing.

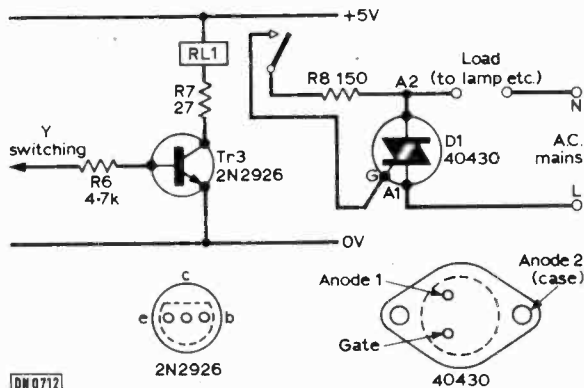


DW 0712

Fig. 3: Isolating stage using a reed relay to control the triac switch.

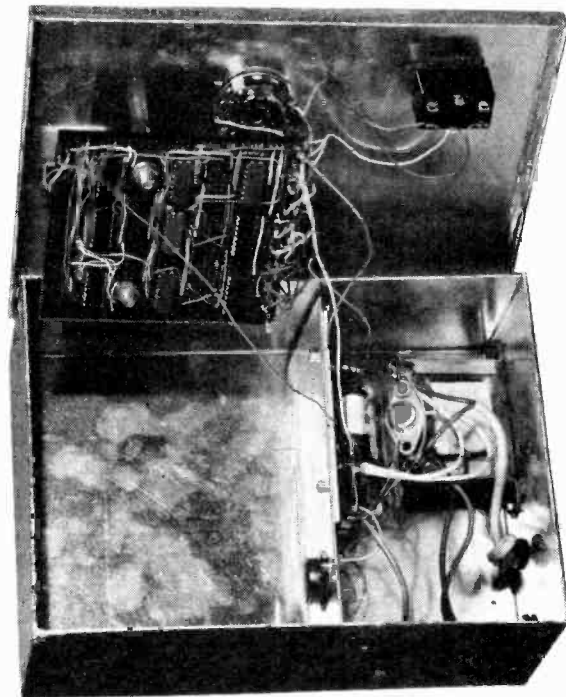

The IC board is mounted in the lid of the box on spacers to minimise the length of the wiring to the switches.

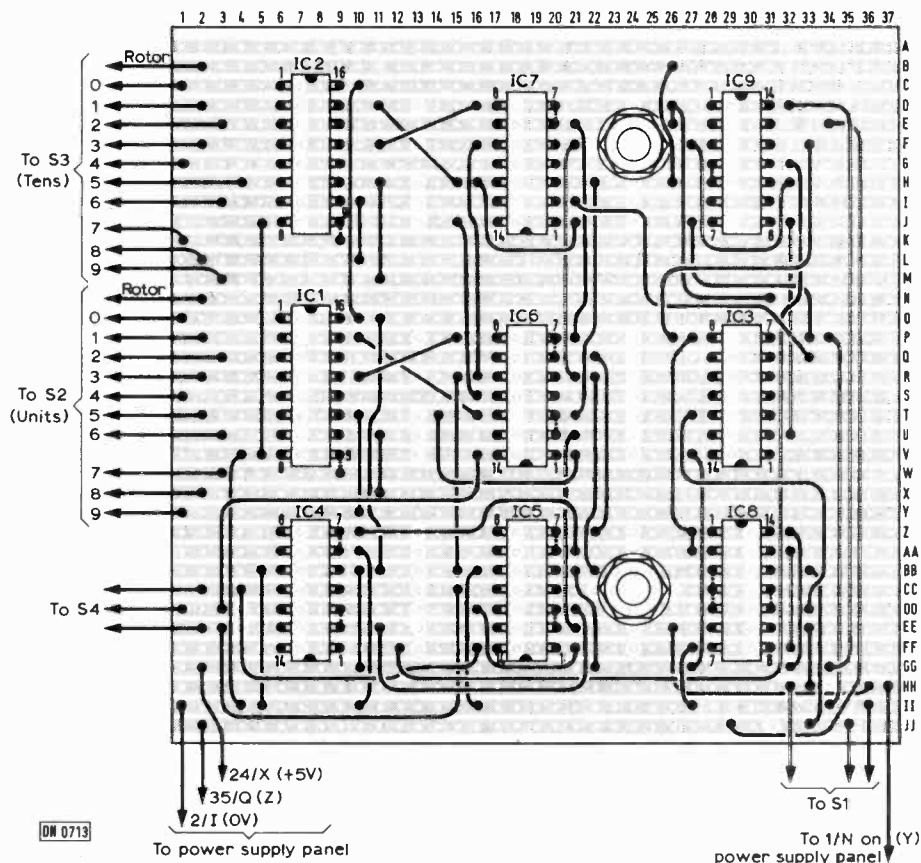

DW 0713

Fig. 4: Placement and wiring of the IC's on the veroboard panel. Note carefully all breaks in copper rails.


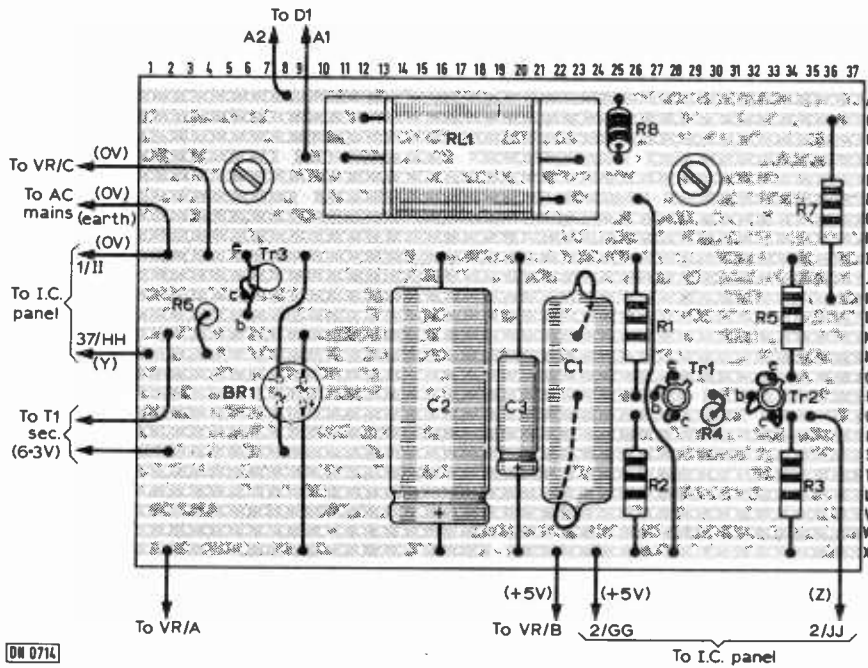


Fig. 5: Layout of panel carrying the power supply, Schmitt trigger circuit and reed relay.

Although the output of the final i.c. (IC8) to the switching circuit is compatible with the gate current required for the triac, the triac cannot be driven directly as it would mean that all the i.c.'s would be live and could not be earthed. In order to overcome this problem a reed relay is driven from IC8 and the triac switched from that. Unfortunately the reed relay used is not TTL compatible so an interface circuit consisting of a 2N2926 is used between IC8 and the reed relay, Fig. 3.

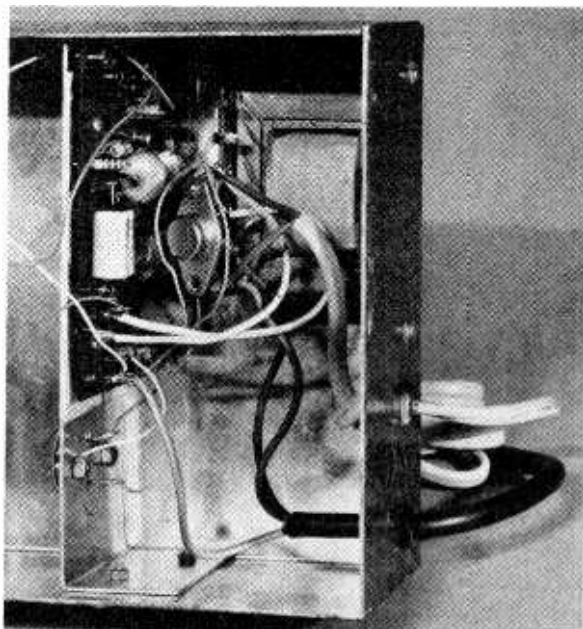

The panel of Fig. 5 is mounted on insulating spacers on the aluminium partition as well as the 5V regulator. The triac is mounted on a tag strip, part of the mains transformer.

Unfortunately, due to the high cost of i.c. holders (as much as twice the cost of some i.c.'s) they have not been used in the construction of this circuit. The i.c.'s have been mounted directly on to the 0.1in. matrix Veroboard, Fig. 4, care being taken not to allow the i.c.'s to get too hot although that is not much of a problem providing one solders them quickly and in rotation. The wiring between all components should be as short as possible (never any longer than 10in.) so as to prevent spurious triggering of the i.c.'s.

The construction is fairly straightforward, the whole unit being mounted in an aluminium box. The switches S1-4 are mounted on the lid as is the IC board, held by 2in. long 2BA nuts and bolts with spacers to provide a stand off so that the wires from S2 and S3 to the pins on the i.c. board are as short as possible. For convenience the triac was mounted on the transformer which was bolted to the case.

The power supply reed relay and interface circuit for the triac are mounted on Veroboard, Fig. 5, which is fixed to a piece of aluminium fixed across the inside of the box.

When the wiring has been completed and checked thoroughly (without the triac connected) it is possible to test the timing.

The switches S2 and S3 should be set to each of their positions and the timing tested: if it is not correct then one should look for faulty connections, missing drilled holes in Veroboard and solder bridges. When testing the timing it is important that the triac is not connected. Use a meter on the reed switch.

Because of the fact that the triac cannot be driven directly from the i.c.'s it is necessary to use an interface circuit. The i.c. board output goes to a resistor and transistor which switches hard-on when it receives a logic 1 voltage and a reed relay is energised which provides the gate current for the triac to turn on. Using a reed relay in this way the i.c.'s are completely isolated from the mains.


# IN NEXT MONTH'S

# PRACTICAL WIRELESS

PW
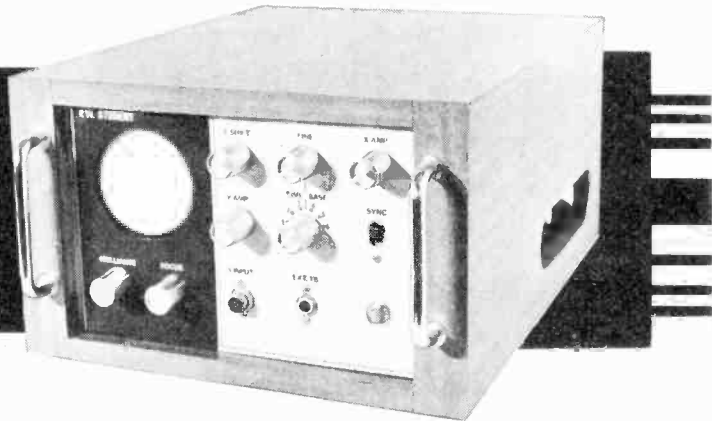
## 'Student' OSCILLOSCOPE

Simple to build. Inexpensive. One assembly board. Specially designed for students and all constructors who want an all-transistor 'scope for displaying simple waveforms.



plus

Details of a new series of articles, for readers who want to get started in construction of simple radio and electronics projects.



PW

FIRST DETAILS OF OUR NEW  
**DATA CARD SYSTEM**

TO BE LAUNCHED IN THE AUTUMN

## MINI COMMUNICATIONS RECEIVER



The "Mini-Comm" is just  $8 \times 4\frac{1}{2} \times 4$  in. and yet completely self-contained. Five transistors plus an audio module permit reception of AM, SSB and CW signals on the short wave bands.

DON'T MISS ANY ISSUE OF  
PRACTICAL WIRELESS  
AUGUST ISSUE ON SALE JULY 6th

# Tremolo gene



THE use of electronic devices to modify the sound of an electric guitar has become very popular in recent years, and the equipment of a guitarist often includes such devices as echo chambers, 'fuzz' boxes and 'wah-wah' pedals. This article describes a tremolo generator which can be used not only with electric guitars but also with most other electronic instruments.

## REQUIREMENTS


To add tremolo to a musical sound it is necessary to vary the loudness of the sound repeatedly at a very low frequency. In the terminology of electronics, this process is called *amplitude modulation*.

Figure 1 shows a block diagram of the tremolo generator. The input signal coming from the guitar has a more or less constant amplitude. The tremolo signal is generated by a low-frequency oscillator, whose output frequency and amplitude can be varied by means of foot pedals. The input and tremolo signals are fed into an amplitude modulator, whose output consists of the input signal with an amplitude which varies at the frequency of the tremolo signal.

Figure 2 shows oscilloscope traces of the signals involved. The input signal (a) is, in this case a, 400Hz wave generated by an audio signal generator. The tremolo signal (b) is a signal of much lower frequency, about 8Hz. The output signal (c) consists of the 400Hz input modulated at 8Hz.
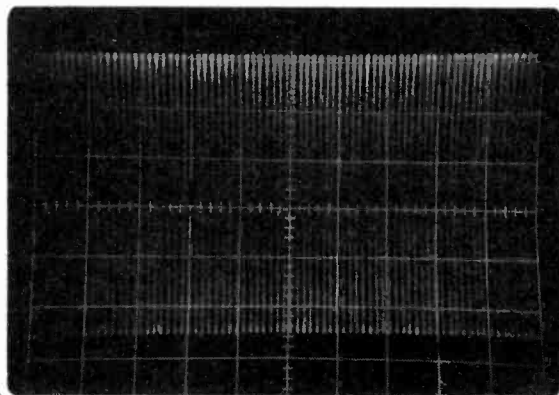
## CIRCUIT DESCRIPTION


The circuit diagram is shown in Fig. 3. It is easier to understand the circuit if the various sections are considered separately.





# erator

# for GUITARS and ORGANS

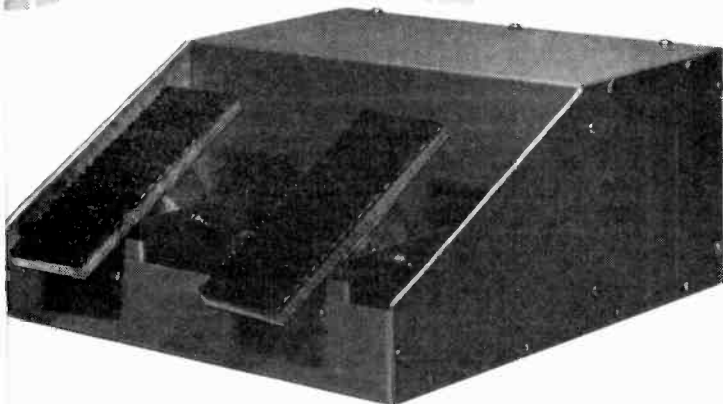

R. MORGAN


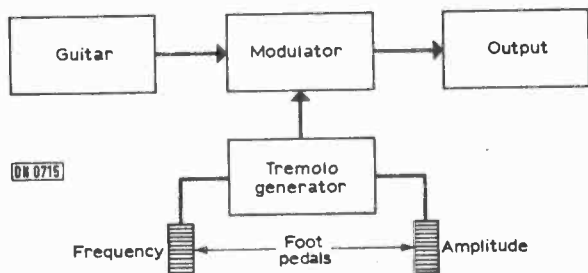
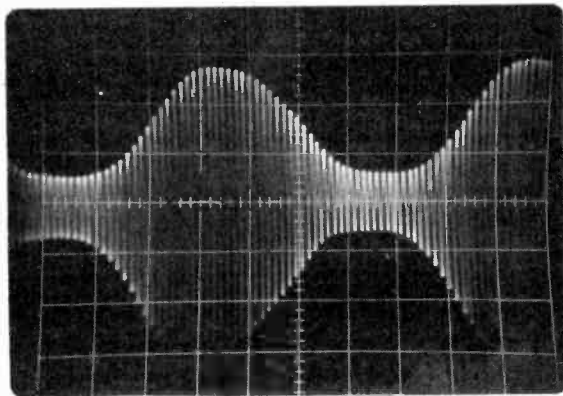


Fig. 1. Block diagram of the stages comprising the tremolo generator.

Fig. 2(a) left, shows an input signal of 400Hz from a signal generator while 2(b), centre, is a much lower frequency signal from the oscillator in the tremolo generator. The two signals are fed to a modulator stage producing the signal shown in 2(c), right.

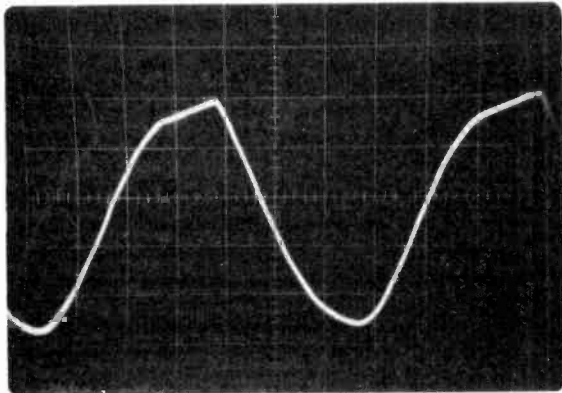

## Oscillator


The oscillator is required to produce a reasonably sinusoidal output at very low frequencies, from about 1Hz to 10Hz, and the usual circuit for this purpose is the Wien bridge oscillator. In Fig. 3 transistors Tr1 and Tr2 form a Wien bridge oscillator whose frequency is determined by resistors VR1+R3, VR2+R4, and capacitors C2, C3. The frequency can be varied over the required range by varying VR1 and VR2, which are ganged.

This type of circuit requires an amplitude controlling device to keep the output amplitude at a level low enough to avoid saturation of the transistors; without this the output increases to a point where severe distortion occurs. The usual amplitude control device is a thermistor, which can be expensive, but by suitable modification of the circuit it is possible to use a much cheaper device, namely a 6V bulb LP1.

The output of the oscillator is fed into a potentiometer, VR4, the setting of which determines how much of the oscillator output is fed into the next stage. Consequently VR4 acts as a modulation depth control.

## Modulator

The musical signal from the guitar is fed into Tr3 and amplified. The degree of amplification depends on the current through Tr3 and if this current is varied the amplitude of the output from Tr3 is also varied. The current through Tr3 is controlled by Tr4, so that when the oscillator signal is fed into Tr4, the current through Tr3 varies at the same frequency as the oscillator signal. Consequently the amplitude of the output from Tr3 also varies at the frequency of the oscillator signal. The output from Tr3 is therefore the musical signal modulated at the frequency of the oscillator.

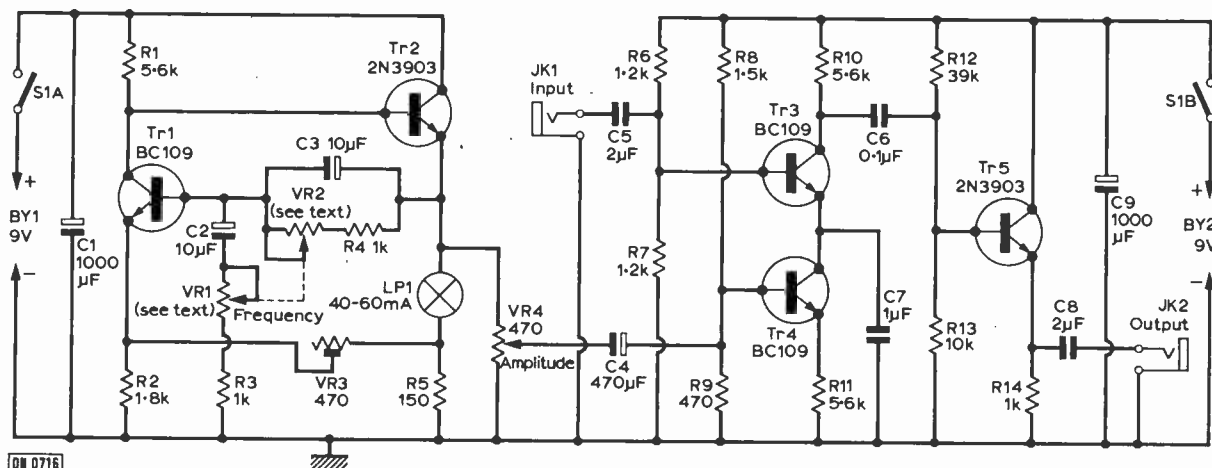

DN 0716

Fig. 3. Complete circuit diagram of the tremolo generator. Note that separate batteries are employed to avoid using expensive decoupling components.

## ★ components list

### Resistors

R1 5.6k $\Omega$	R6 1.2k $\Omega$	R11 5.6k $\Omega$
R2 1.8k $\Omega$	R7 1.2k $\Omega$	R12 39k $\Omega$
R3 1k $\Omega$	R8 1.5k $\Omega$	R13 10k $\Omega$
R4 1k $\Omega$	R9 470 $\Omega$	R14 1k $\Omega$
R5 150 $\Omega$	R10 5.6k $\Omega$	

All resistors  $\frac{1}{4}$ W 10%

VR1 50k $\Omega$  linear

VR3 470 $\Omega$  pre-set

VR2 50k $\Omega$  linear

VR4 470 $\Omega$  linear

See text for further information on potentiometers

### Capacitors

C1 1000 $\mu$ F	C4 470 $\mu$ F	C7 1 $\mu$ F (poly)
C2 10 $\mu$ F	C5 2 $\mu$ F (poly)	C8 2 $\mu$ F (poly)
C3 10 $\mu$ F	C6 0.1 $\mu$ F	C9 1000 $\mu$ F

All 12V or more working voltage

### Semiconductors

Tr1 BC109	Tr3 BC109	Tr5 2N3903
Tr2 2N3903	Tr4 BC109	

### Miscellaneous

Switch S1, double pole on/off. Jacks (2). Lamp LP1, 6V 40-60mA, with holder. Batteries PP9 or similar (2). Veroboard 12 x 2 $\frac{1}{2}$  in. (minimum) 0.1 in. matrix, and pins. Metal for casework.

### Meccano Parts

Name	Part No.	No. Off
Axle Rod 4 in.	15b	3
Axle Rod 3 in.	16b	1
Axle Rod 2 in.	17	1
Pinion $\frac{3}{4}$ x $\frac{1}{2}$ in.	25	2
Gear wheel $1\frac{1}{2}$ in.	27	2
Nuts and bolts	37	1 pkt.
Double angle strip $2\frac{1}{2}$ x $\frac{1}{2}$ in.	48a	4
Slotted strip $5\frac{1}{2}$ in.	55	4
Collar and screw	59	7
Couplings	63	3
Plates $5\frac{1}{4}$ x 2 $\frac{1}{2}$ in.	70	2
Sprocket chain	94	1
Sprocket wheel $\frac{3}{4}$ in.	96a	2
Bellcranks	128	4

## Output stage

The modulator output is at a high impedance and suitable for feeding directly into amplifiers with a high impedance input, i.e. all valve amplifiers and most transistor amplifiers. However, some transistor amplifiers have low-impedance inputs and if the modulator is used with such an amplifier an impedance-conversion stage is needed. The addition of such a stage makes the output suitable for all amplifiers, whether of high or low impedance, and there are certain other advantages such as a reduced level of mains hum. The output stage in the present design is an emitter-follower formed by Tr5.

## Power supply

If several parts of a circuit are fed from one power supply, there is a danger of unwanted interaction between one part of the circuit and another, due to voltage variations, unless the supply is de-coupled by means of a resistor and capacitor. When a circuit is designed to run at very low frequencies, as is the case here, the de-coupling capacitor has to be very large and therefore very expensive. A much cheaper solution is to use separate batteries for each part of the circuit. In the present design two batteries are used, one for the oscillator and the other for the rest of the circuit.

## CONSTRUCTION

The electronics are built on a piece of 0.1in. matrix Veroboard, 11 $\frac{3}{8}$  x 3 $\frac{3}{4}$ in. A suggested layout is shown in Fig. 4, but the layout is by no means critical and can be altered if necessary to suit components of different sizes and shapes. Constructors who are not used to building on 0.1in. Veroboard should take care to avoid bridging between the copper strips, by avoiding the use of too much solder.

The two sections of the circuit are almost completely separated electrically by severing all the copper strips where indicated, **except for the negative rail**, using a Vero spot cutter or a  $\frac{1}{16}$ in drill, or alternatively, with a sharp knife. The transistor leads are rather short and constructors who are inexperienced in soldering are advised to hold the leads with a pair of fine-nosed pliers during soldering, at a point between the solder joint and the body of the transistor.

Care should be taken to connect the input and output jack sockets correctly, with the negative rail to

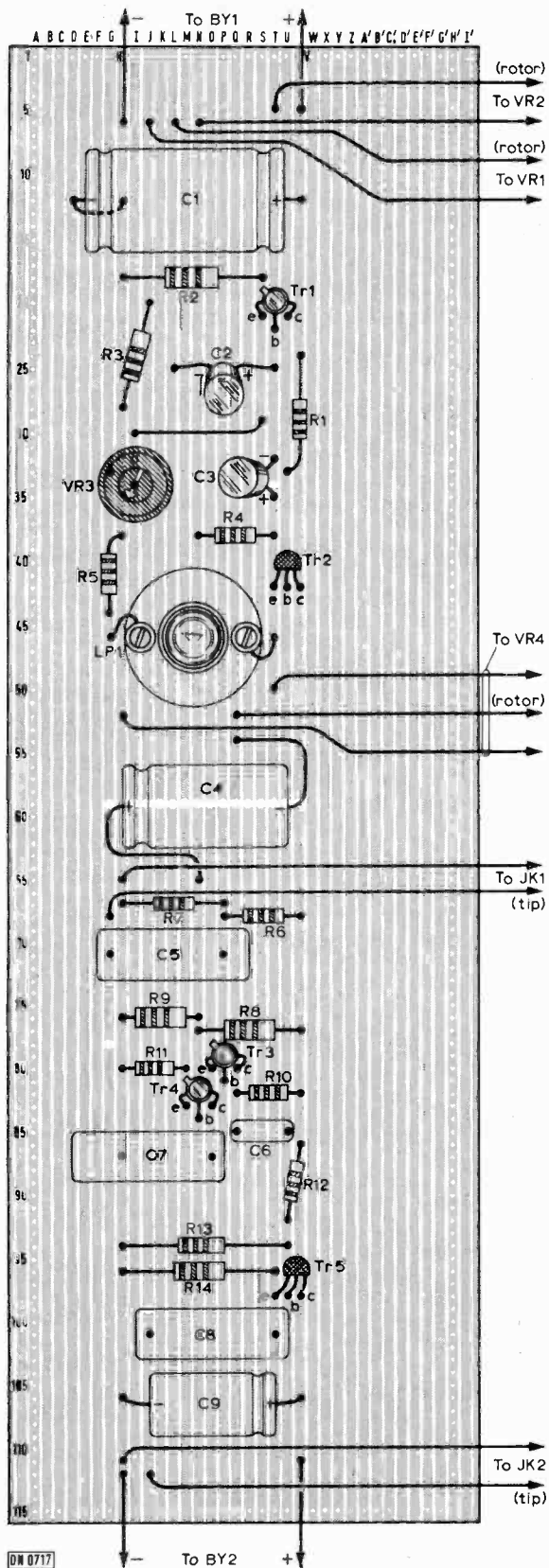


Fig. 4: Layout of the circuit board. Breaks in copper rails are best made before fitting components.

the socket contact which touches the outer conductor of the jack plug. If a mistake is made in this, an embarrassing amount of hum may be induced.

Potentiometers VR1 and VR2 are ganged linear controls. While ordinary carbon potentiometers are satisfactory, it is preferable to use wire-wound potentiometers because they have a much longer life and are less liable to noise. Ganged wire-wound controls are not easy to obtain, and for that reason the present design uses two ordinary single potentiometers with their spindles connected together. The mechanical details of this linkage using Meccano parts are shown in Fig. 5a. Because the two controls are "back to back", the connections may appear to be a little unusual, but if Fig. 5a is followed there should be no difficulty.

The mechanical linkages between the foot pedals and the controls are worth considering in some detail.


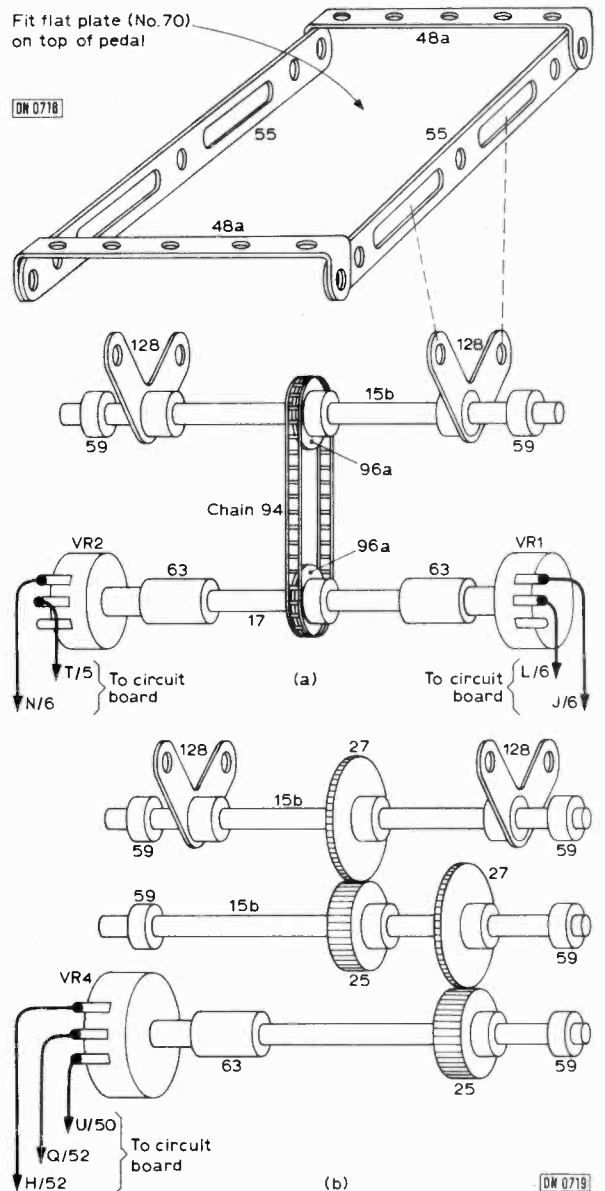


Fig. (5a), top, shows the assembly of the Meccano parts and potentiometers comprising the tremolo frequency pedal. Fig. (5b), bottom, is the pedal assembly for the tremolo depth control.

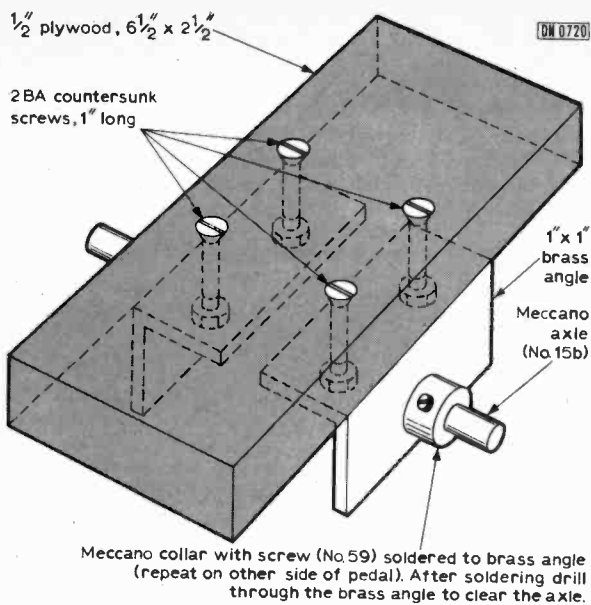

Meccano collar with screw (No.59) soldered to brass angle (repeat on other side of pedal). After soldering drill through the brass angle to clear the axle.

Fig. 6: Details of the foot pedals which were eventually fitted to the prototype unit.

It is not possible to rotate one's foot through more than about 60° without discomfort, while an ordinary potentiometer can rotate through about 300°. In the case of VR1 and VR2 a variation in resistance from zero to about 10kΩ is required and this can be achieved simply by using one end of the track of a 50kΩ potentiometer. In the case of VR4 it is necessary to use almost all the available rotation of the potentiometer so a 4 to 1 gear ratio is needed between the pedal and the control spindle. Meccano provides a simple and cheap way of building the linkage, and a suggested arrangement is shown in Fig. 5b.

From experience it was found that a sturdier pedal assembly was desirable and two were constructed, as in Fig. 6. They were each covered with corrugated rubber sheet.

A piece of equipment of this sort is subjected to a certain amount of rough treatment, and it is important to build a strong framework capable of withstanding abuse. A suggested design of framework is shown in Fig. 7.

The circuit board can be fixed with spacers to the back of the case. The on/off switch and the input and output sockets are fixed to the left-hand side panel. The two batteries are held in place by a metal bracket.

A view of the partially assembled casework showing the circuit board mounted along the back with input and output jacks and on/off switch at the left hand side. The two batteries are located by the partition at the right. Pedal movement is restricted by the pedal housing, if constructed as in Fig. 7.

## TESTING AND ADJUSTMENT

When the construction has been completed, and the circuit checked carefully, the unit is ready for testing and adjustment. It is useful to have an oscilloscope for this purpose, but it is not essential. Because of the use of two batteries, each part of the circuit can be tested separately.


### Oscillator

The first job is to set the position of the frequency pedal. Slacken off the grub-screws holding the short axle between VR1 and VR2 and turn the spindles of the potentiometers VR1 and VR2 to the **minimum** resistance position. Push the foot pedal to the extreme end of its movement, and tighten up the grub screws. Check that the potentiometers rotate smoothly when the pedal is moved. Leave the pedal near the middle of its travel.

The next adjustment is to set the position of the modulation depth pedal. Slacken off the grub-screw of the cogwheel which drives the spindle of VR4. Rotate the spindle to bring the slider to the **earthed** end of the track. Push the foot pedal to the extreme end of its movement, and tighten up the grub screw. Check the rotation of the potentiometer when the pedal is moved and once again leave the pedal near the middle of its travel.

Connect the oscillator battery (not the modulator ends of VR4. Set the timebase of the oscilloscope to a slow scan (about one trace per second if possible) and the input sensitivity to about 1 volt for full deflection. If an oscilloscope is not available, put the unit in a partially darkened room in a position where the lamp LP1 can be seen easily.

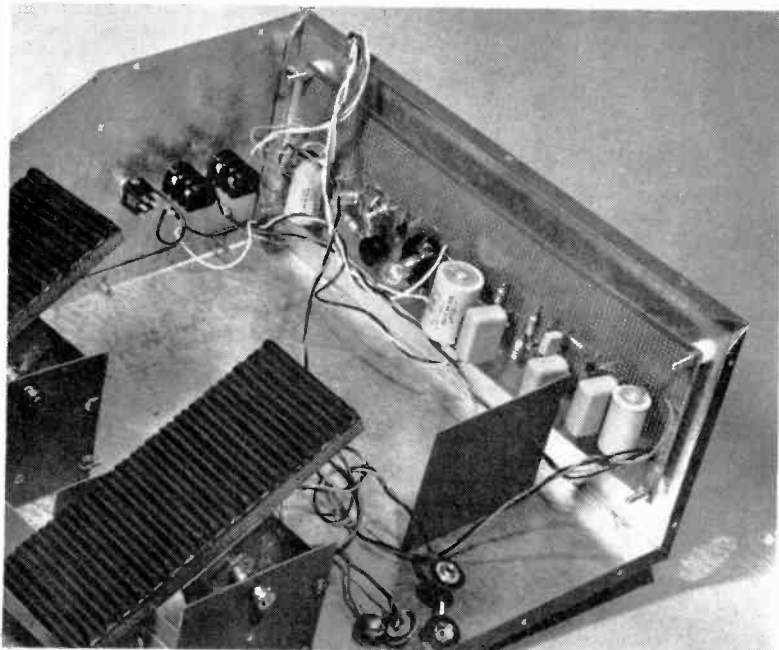Connect the oscillator battery (not the modulator battery) and switch on. Adjust the preset potentiometer VR3 until the circuit starts oscillating, as evidenced by the trace on the oscilloscope or by a dull pulsating glow in the lamp LP1. Move the frequency pedal to bring VR1 and VR2 to a high-resistance position. The frequency should drop to about 1Hz or less. If the circuit stops oscillating,



Material... 16 swg. dural or steel.  
When cutting allow for bends.

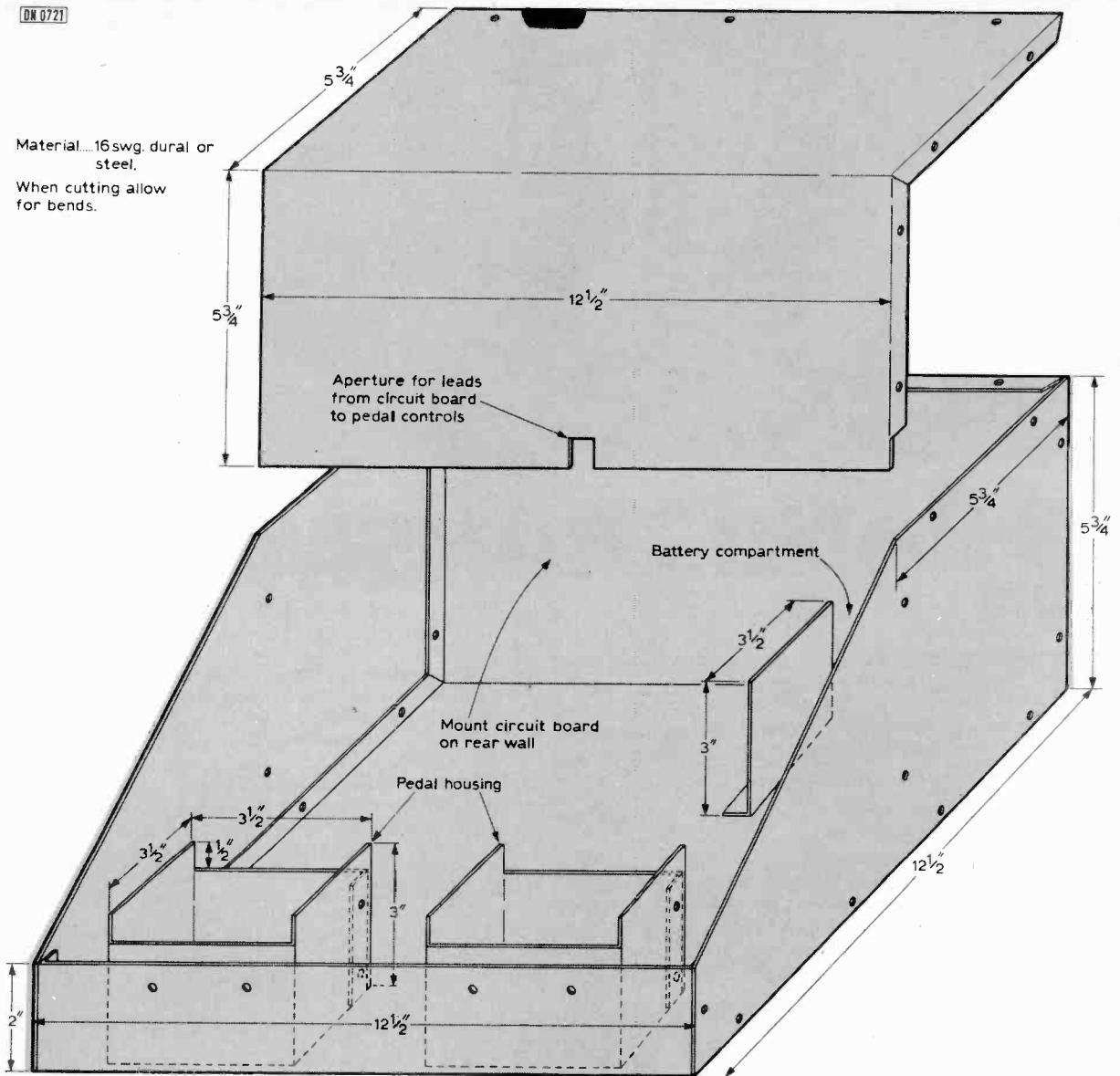


Fig. 7: Details of the casework housing the tremolo generator.

re-adjust VR3. Gradually raise the frequency by means of the frequency pedal and check that the oscillator works correctly over the required range of frequency; if it shows any sign of stopping, re-adjust VR3. The ideal position for VR3 is one in which the oscillation is just able to continue over the whole range of frequency, but the setting is not very critical. Finally, switch off.

**Modulator**

Disconnect the oscillator battery and connect the modulator battery. Plug the guitar lead into the input socket and plug the output into the guitar amplifier. Switch on and check that the volume is satisfactory and that there is no distortion of the sound. If all is well, no further adjustment is needed. If there is noticeable distortion, it is probably due to overloading of the modulator, and this can most


easily be prevented by connecting a resistor of a few kilohms in series with the input, between the input jack and C5.

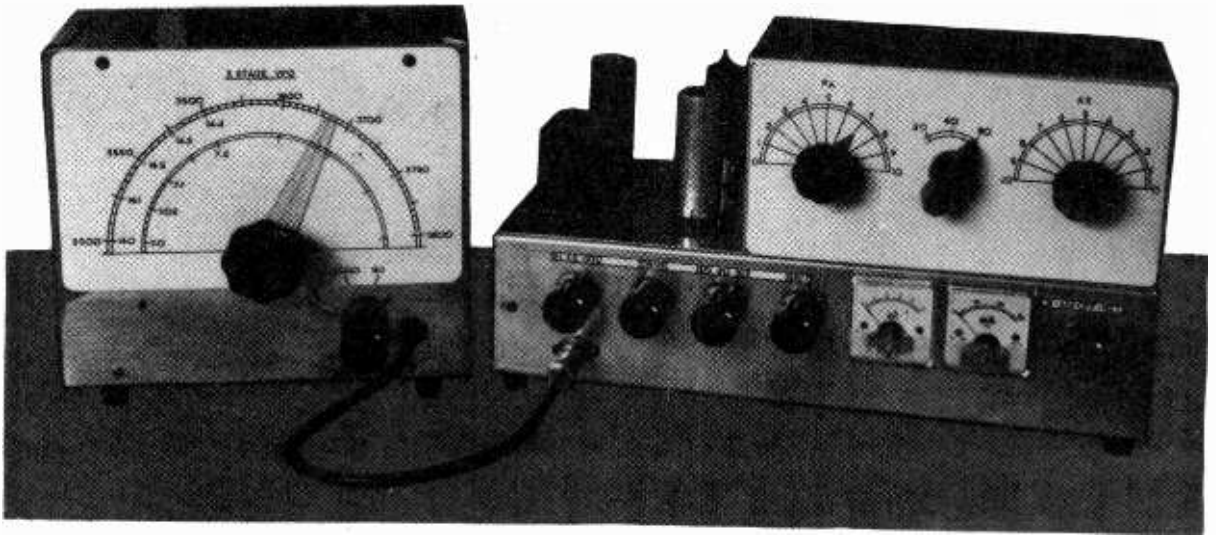**OPERATION**

Connect both batteries, the guitar and the amplifier. Switch on and adjust the positions of the pedals while playing long chords. The effect of the tremolo generator on the sound should now be apparent.

The guitarist may like to try the tremolo effect in conjunction with other devices. It appears to be particularly effective when used with a 'fuzz' box. It seems that better results are obtained when the 'fuzz' box is placed between the guitar and the tremolo generator, rather than between the tremolo generator and the amplifier, but this is a matter for experiment.





# 3-BAND TRANSMITTER

## PART 2

F. G. RAYER G30GR

**T**HOUGH this VFO is particularly intended for use with the transmitter described last month it can be employed for the frequency control of any similar transmitter. The VFO has a straight-forward circuit which can give reliable and excellent results.

### CIRCUIT

Fig. 1 is the circuit which uses a 6C4 as a Clapp oscillator, the HT to this stage being regulated by the OA2 voltage regulator. The valve capacitances are shunted by the large value capacitors C2, C3, and C4, so this type of circuit proves to be stable and trouble-free.

Components in the VFO stage are enclosed in a metal box on the chassis and this complete screening avoids any difficulties from stray feedback. The whole VFO is in turn enclosed in a metal box or case.

A 6BH6, V2, is a buffer-amplifier which also frequency doubles for working on 7MHz and 14MHz. On 3-5MHz resistor R6 forms the anode load. Output to the transmitter is by a co-axial lead plugged into the socket which is provided on the transmitter. The latter also supplies power for the VFO. When working on 14MHz, the crystal oscillator stage of the transmitter acts as a second doubler.

Coil L1 and capacitor VC1 tune 3500-3800kHz and output frequencies are fundamental or doubled which makes the VFO calibration easy.

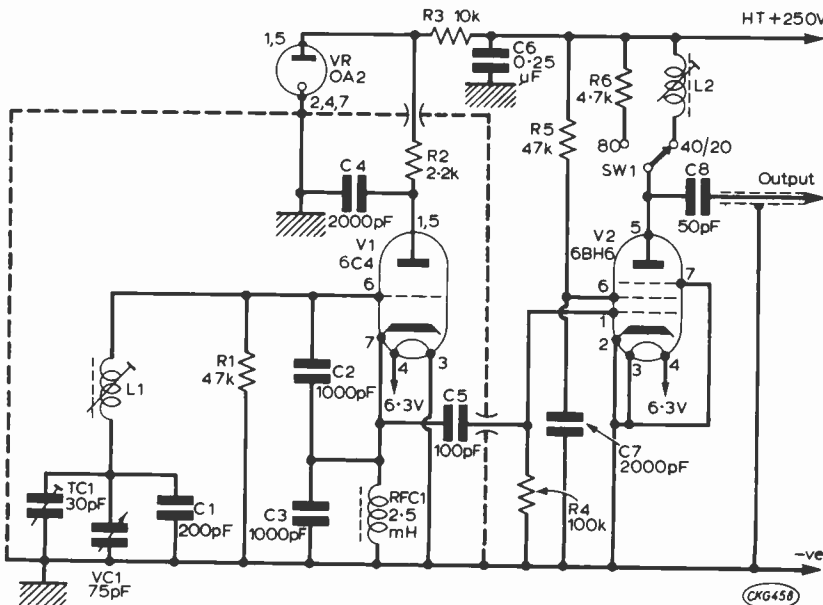


Fig. 1: Circuit of the two valve variable frequency oscillator. The power for the VFO is taken from the main transmitter, described last month. Components associated with the 6C4 oscillator valve are shown within the dotted enclosure.

## VFO BOX

The variable frequency oscillator coil L1 and associated components are completely enclosed in a box, Fig. 2 which is very easily made from "universal chassis" members. A flanged member 8 x 3in. is taken and a V-shaped notch is cut in each flange 2in. from the end. A right-angled bend can now be made 2in. from each end. A sharp bend is best obtained by holding the member firmly on a piece of wood just large enough to rest between the flanges, and with one edge level with the bending line. This gives a U-shaped piece 2in. high and 4in. wide. The front is closed by attaching a 4 x 2in. flanged plate with four bolts. After all assembly is finished, a flat back plate 4 x 2in. is fixed on with self-tapping screws.

Tuning capacitor VC1 is mounted on the front flanged plate as in Fig. 2 and the ball drive is put on. Its lug is held with a long bolt with spacer, or extra nuts.

Trimmer TC1 is fixed on a small bracket under a hole, so that it can be adjusted from above with a screwdriver. Tag-strips are used to anchor R2, C5 and RFC1. The coil L1 is positioned as shown, with its core adjusting screw projecting from the top of the box.

Wiring and components in the box should all be rigid.

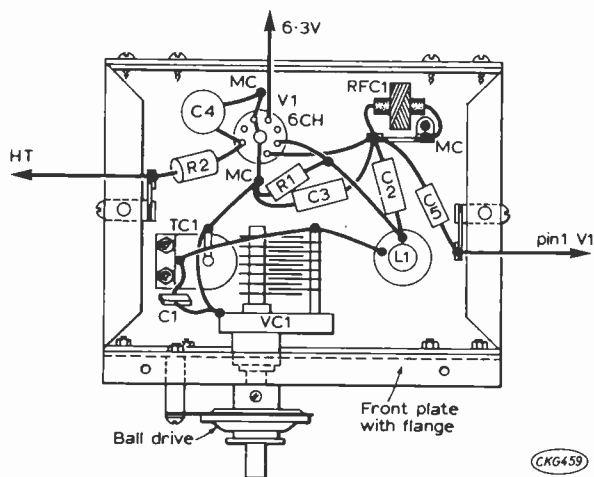


Fig. 2: Layout and wiring of components within the separate oscillator box.

Coil L1 is wound on a cored former, 1/2in. in diameter and 1 1/4in. long, with 30 turns of 26swg enamelled wire, closewound. The winding is started as near to the top or pin end of the former as possible. The former can be lightly smeared with a suitable adhesive (Denfix) before winding. The end is secured with cotton and adhesive.

The VFO can be tested by applying heater and HT voltages (about 150V) and adjusting TC1 and L1 for suitable coverage. With VC1 almost fully closed, L1 core is rotated to obtain 3.5MHz. VC1 is then set almost fully open, and TC1 is adjusted for 3.8MHz. One adjustment modifies the other, so this needs to be repeated several times. Sufficient coupling to a receiver is obtained by placing the aerial lead near the VFO.

Final calibration should be with the aid of a 100kHz crystal marker or equally accurate frequency

## ★ components list

### Resistors

R1 47kΩ 1/4W	R3 10kΩ 3W	R5 47kΩ 1W
R2 2.2kΩ 1/4W	R4 100kΩ 1/4W	R6 4.7kΩ 1W

### Capacitors

C1 200pF 1% SM	C6 0.25μF 350V
C2 1000pF 1% SM	C7 2000pF disc
C3 1000pF 1% SM	C8 50pF SM
C4 2000pF disc	TC1 30pF trimmer
C5 100pF SM	VC1 75pF variable

### Valves

V1 6C4	V2 6BH6	VR OA2
--------	---------	--------


### Miscellaneous

Valveholders B7G (3) with screens (2). Ball drive, knobs. Single pole 2 way switch. Formers, 1/2in. dia. with cores, (2) (Denco). RFC 1, miniature choke 2.5mH. VFO box: Universal chassis member, 8 x 3in., flat plate 4 x 2in., flanged plate 4 x 2in. Panel: plate 8 x 7in. Chassis: plate 8 x 4in. Case: flanged plates 8 x 4in. (2) 7 x 4in. (2) Home Radio.

standard. This will give calibration marks at 3.5, 3.6, 3.7 and 3.8MHz. Tuning the receiver to the second harmonic of the VFO will give 3.55MHz (at 7.1MHz) and so on, while the fourth harmonic will give calibration for the 20m band. When the VFO is being calibrated, or is in use with a transmitter, the higher frequency bands are direct multiples of the 3.5MHz band frequencies, so working with and marking the scales is very straightforward.
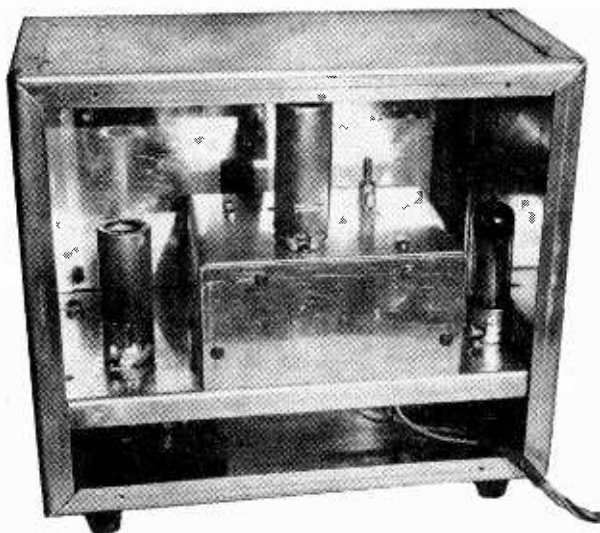
## CHASSIS AND CASE

The main chassis is a universal chassis flanged member 8 x 4in. This allows similar members to be used for the top and bottom of the VFO case, with 7 x 4in. flanged members for the sides. The front is a flat plate 8 x 7in.



Rear view of VFO shows position of oscillator stage on main chassis.

Fig. 3: Details of layout on top of main chassis. The oscillator can be checked and roughly calibrated before the box is fitted to the top of the chassis. RF output and power supply wires pass down through a hole in the chassis.

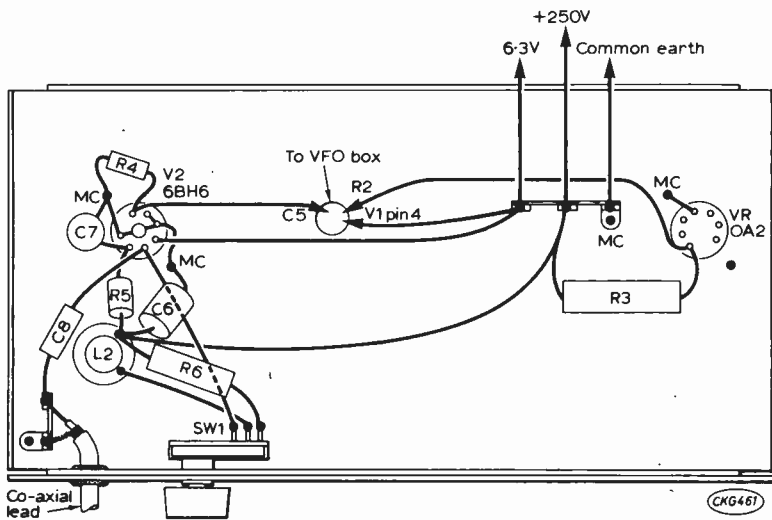
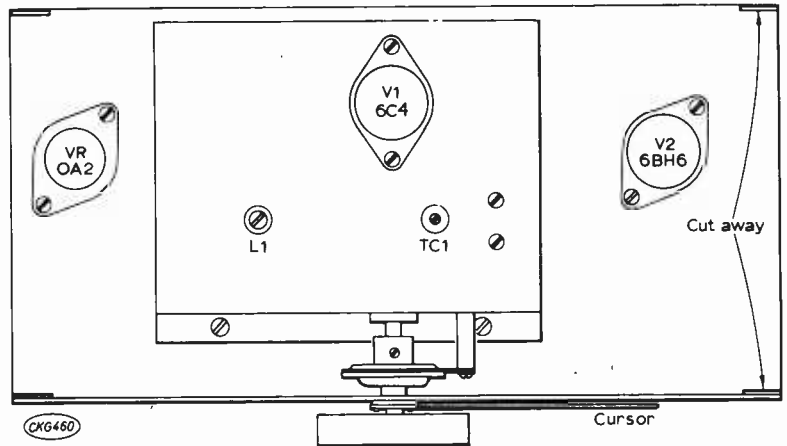


Fig. 4: Underneath the chassis showing the wiring of the buffer/multiplier stage and voltage regulator for the oscillator stage. The co-axial lead, bottom left, to the transmitter must be as short as possible. Power supply leads are taken to a 3-pin plug matching the socket on the transmitter.

The long flanges of the chassis member are first cut away at each corner just sufficiently to allow this item to fit *inside* the flanges of the members which form the sides of the case. The chassis is bolted so that its top surface is 2in. above the bottom edge of the 8 x 7in. panel plate. Voltage regulator VR and V2 are placed as in Fig. 3, and the wired VFO box is bolted in this position and its back closed with the 4 x 2in. plate.

## WIRING

Fig. 4 shows components and wiring under the chassis, with leads passing through a hole for heater, regulated HT and the connection from C5 to the grid of V2.

A tag strip holds flexible leads for 6.3V, 250V and common chassis return. These three leads can be about 18in. long and they are soldered to the pins of the 3-way plug, which fits the transmitter power outlet. Power switching of the VFO is controlled by the CW/AM/OFF/NET switch on the transmitter.

The VFO output lead is about 9in. of low-loss co-axial cable, passing through a grommet in the front panel and anchored at a tag strip. The VFO output

position is adjacent to the transmitter VFO input socket, so a long co-axial lead is not required or desirable. A long lead here may cause difficulty in resonating L2, or in securing adequate drive, due to its capacitance and possibly losses in the high impedance anode and grid circuits.

L2 has 38 turns of 32swg enamelled wire close-wound on a 1/2in. diameter former with adjustable core. The winding should begin as near to the tagged end of the former as possible.

The VFO should be tested before completing the case. It was found stable when used without the case, but the latter improves screening and rigidity. When the case is assembled, a short screwdriver is necessary to reach L1, L2 and TC1.

To assemble the case, put the side members with their flanges in the slots provided. The bottom and top can then be put into place, and are bolted to the sides. The case is checked for squareness, and the panel is correctly positioned. Holes for self-tapping screws are then drilled through the panel and side flanges, so that the panel can be secured. It is best to drill both panel and flange with a bit suitable for the self-tapping screws to hold, then use a larger bit, on the panel holes only for clearance.

The flanges of the member forming the chassis are bolted to the sides of the case.

## USING THE VFO

For operation on 80m, VFO, driver and PA switches are all set to the 80m position. With the transmitter control switch at "Net" grid current should be shown by the transmitter meter and the carrier should be

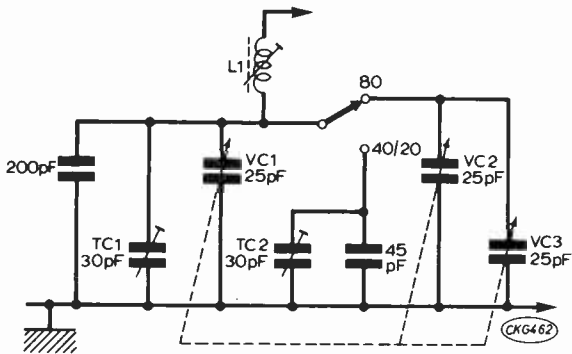


Fig. 5: Modified oscillator circuit to improve bandsread coverage on the higher frequency bands.

found on a receiver at the VFO frequency. The transmitter driver stage screen grid potentiometer will need to be turned back considerably to keep grid current down to the correct level.

For working on 40m, place the VFO switch at 40/20m and the transmitter switches at 40m. L2 may need adjusting as mentioned for 20m.

When first testing the VFO on 20m, tune to about 14.2MHz. Set the VFO switch at 40/20m and both transmitter switches at 20m. With the control switch at "Net" rotate the core of L2 for maximum grid current as shown by the transmitter meter. On all bands tune the PA grid for maximum grid current, adjusting this to a suitable level with the drive potentiometer.

## CALIBRATION

The scales are marked so that the higher frequency bands are direct multiples of the low frequency band. So 3.5MHz is also 7.0MHz and 14.0MHz. As mentioned this greatly simplifies calibration.

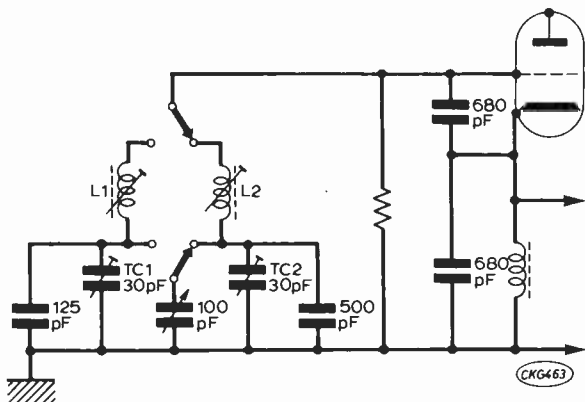


Fig. 6: Suggested circuit to give full scale coverage on all bands, 1.8-28MHz.


With this method of covering higher frequency bands only a smaller part of the tuning spread is used for 40m and 20m. During experimental use of

the VFO, two methods were employed to spread the tuning on the HF bands. These may be of interest, though they were not used in the completed VFO.

The method shown in Fig. 5 gives coverage of 3.5-3.8MHz on one range for 80m. On the other range the VFO tunes from 3.5-3.6MHz, giving coverage of 7.0-7.2MHz and 14.0-14.4MHz with almost the full 180-degree rotation of the tuning capacitor.

With the switch at 80m, VC1, VC2 and VC3 are all in parallel, forming a 75pF variable tuning capacitor, with TC1 and the 200pF capacitor as before.

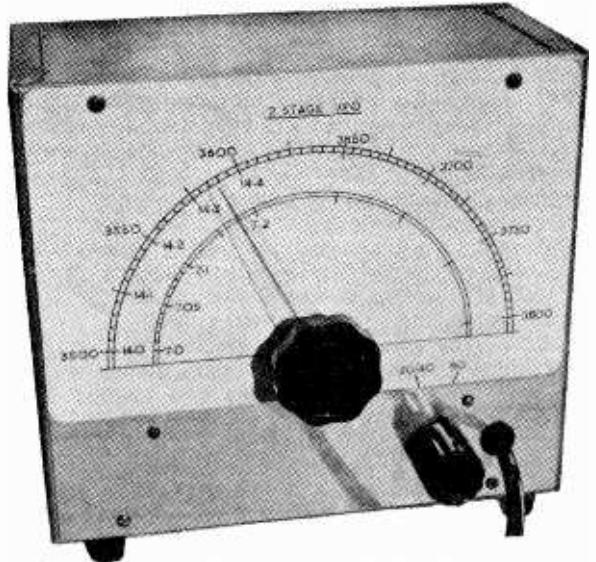When the switch is on 40/20, TC2 with its parallel fixed capacitor substitute for VC2 and VC3 and coverage is restricted to that of VC1, that is 3.5-3.6MHz, giving actual ranges of 7.0-7.2MHz and 14.0-14.4MHz.



A closer look at the VFO dial calibration.


A Jackson miniature 25pF 3-gang capacitor was used. TC2 is adjusted so that 3.5MHz falls on the same tuning position, with the switch at 80m or 40/20m. The 80m range has to be individually calibrated. The 20m range is the second harmonic of the 40m range.

Fig. 6 shows a modification used for some considerable time in conjunction with an all-band transmitter. With the switch placing L1 in circuit, TC1 is adjusted for coverage of 1.75-2.0MHz. This is for Top Band (160m) and 80m, the 1.75-1.9MHz portion of the band being doubled for 3.5-3.8MHz. L1 is 60 turns of 36swg enamelled wire, closewound on a 1/2in. diameter cored former.

When the switch places L2 in circuit, coverage is from 7.0-7.2MHz. This gives operation at the fundamental frequency of 7.0-7.1MHz for 40m. For 20m, 7.0-7.2MHz covers 14.0-14.4MHz, with doubling. This same VFO band provides 21.0-21.4MHz for 15m and 28.0-28.8MHz for 10m.

Where the transmitter has few frequency multiplying stages this arrangement is very useful indeed. When the transmitter covers all bands with the minimum of circuits, it is helpful to fit a 4-way switch for V2 in the VFO. In addition to the untuned load, coils for 3.5MHz, 7MHz and 14MHz may then be selected, giving a choice of VFO outputs, with only tripling required to reach 21MHz, or doubling for 28MHz. ■

# GOING BACK...

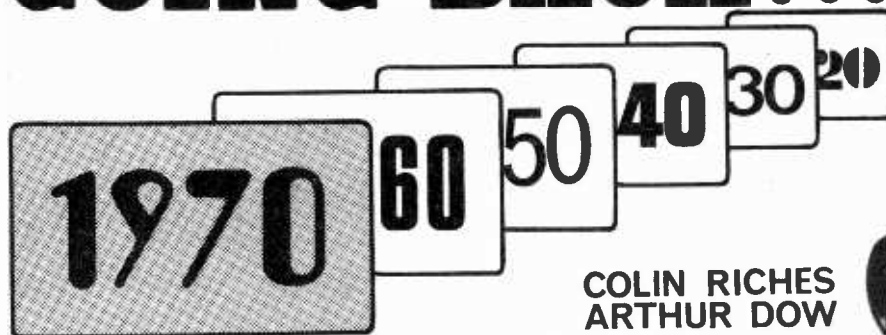

COLIN RICHES  
ARTHUR DOW



Following our review in the April issue of the extensive collection of vintage wireless equipment belonging to George Weston of Auckland, New Zealand, we received a copy of a letter sent to Mr. Weston by Mr. W. W. Barnes, G2FI, of Wadhurst in Sussex, who began his career in wireless in 1917 when he was with the Royal Flying Corp. He rightly congratulates Mr. Weston for having stuck to his task of gathering together so much ancient gear in a part of the world where the amount of such equipment must be very limited.

Mr. Barnes joined the Philips Company in 1926 and stayed with them for many years, mainly in their Servicing Department, and thus was able to offer some additional information on the 2510 and 2515 receivers that we pictured in the April issue. These sets were made at Eindhoven in Holland but when sent to England were fitted with Mullard valves and the type numbers changed to 2511 and 2516 respectively! Needless confusion does not seem to be the prerogative of the modern society! The 2511 was the first domestic receiver having two HF stages to appear on the English market and, according to Mr. Barnes, was far ahead of its time. It was built 'like a battleship' and reputedly was just as heavy! Obviously the forerunner to the AR88!

Mr. Barnes recalls feeding the output of a 2511 into a pair of PX4's which fed a mains energised 18in. loudspeaker. The speaker and its power supply alone weighed 48lbs.! We understand that the current copy of the Philips News Sheet refers to a letter from a customer saying his 2515 is still in use and functioning perfectly. Mr. Barnes built his own two-HF-stage receiver in 1922 from a design published in the old 'Modern Wireless'. However it was unstable to the extent that the coils had to be wound with resistance wire to 'hold it down'.

## Transatlantic DX

Another old-timer from the ranks of the amateur fraternity is George Tagg, G8IX, now of Stoke-on-Trent, who has been good enough to trust us with the original negatives and photographs of the wireless gear that he operated over fifty years ago, in 1919/20 to be precise. He was then a Leading Telegraphist at HM Wireless Telegraphy station at Mount Pearl, St. John's, Newfoundland and the equipment in use included a Model L receiver and a Poulsen Arc transmitter. (If anyone has any information on this receiver we would be glad to hear from them.)



George Tagg seen here at St. John's, Newfoundland, is still active on the air as G8IX.

Remarkably enough the best DX included contacts with the station at Pembroke Dock. George recounts taking photographs of Alcock and Brown before their epoch-making Transatlantic flight and also making special transmissions and test signals for them while they prepared their equipment.

## Early Courtesies

Our collection of photographs of 'very ancient stations' has been swelled by a contribution from Mr. S. D. Mason of Torquay whose station was active in 1910! It doesn't take much work on the office slide rule to realise that Mr. Mason is now a proud 80 years of age. In those early days he was located at Forest Gate in London and his call sign was just a simple 5SV. The preamble to his licence ran 'To all whom these presents shall come, the Post Master General the Rt. Hon. Herbert Samuel sends greetings... etc.' ... obviously a unique document one would be very happy to possess.

Morse and telephony were both used at 5SV to work other stations in the Ilford and Barking areas but seemingly the ship's operators in the Royal Albert Docks were not very favourably impressed by the virtually untuned spark gap at 5SV! The aerial was a twin wire inverted L but only 30ft. long which must have been very short compared with the wavelength in use at the time.

At the beginning of the First World War all Mr.



# LARGE STOCKS ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new & to makers specs.

# ELECTROVALUE

## Electronic Component Specialists

### TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power 80p  
AC153K pnp germanium low power 32p  
AC176K npn germanium low power 32p  
AD181 npn germanium medium power 42p  
AD182 pnp germanium medium power 40p  
AF139 pnp germanium UHF 40p  
BC107 13p; BC108 12p; BC109 13p;  
BC167 11p; BC168 9p; BC169 11p } (npn)  
BC177 81p; BC178 18p; BC179 21p;  
BC257 12p; BC258 11p; BC259 13p } (pnp)  
Standard groupings available.  
BD185 npn med power 39p  
BD186 pnp med power 39p  
**DIODES**  
OA20, OA91, OA95 each 6p  
OA200 8p; OA202 10p  
Other semiconductor  
AC128 17p; AF117 35p  
BFY51 18p

Full lists and technical data will be found in Catalogue No. 6. See also amendments list.


### SIEMENS' THYRISTORS

0-8A 400V 85p, 600V 90p  
3A 400V 70p, 600V £1.02

**ZENER DIODES** full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

### DIN PLUGS & SOCKETS

by Hirschmann, 3A rating

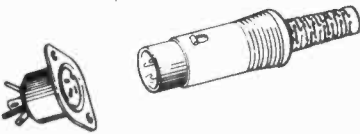


2 way 12S socket 10p; plug 12p. 3 way scr. socket 10p; plug 12p. 3 way scr. socket 12p; plug 16p.

### TRANSISTOR ACCESSORIES

To3 cover 7p  
Heat sinks 1°C/W, type 6W1, undrilled 60p
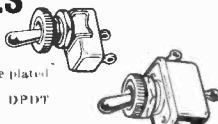
### SWITCHES

1011C 8PST toggle 20p;  
409 DPDT toggle 29p. (These are chrome plated-2.5A rating)  
7201 Sub-miniature DPDT 250V a.c./2A 48p




### ROTARY SWITCHES

Rotaries Miniature Moka-switch (in assembly kit form) Shaft 48p.  
Wafers, MBB-2P5W, 1P11W, 2EM-1P12W, 2P6W, 3P4W, 4P3W, 6P2W, each, 32p

### WAVECHANGE SWITCHES

1P12W, 2P6W, 3P4W, 4P3W, each 24p

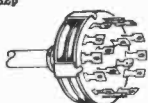

### ELECTROLYTIC CAPACITORS

AXIAL LEAD Prices subject to amendment by the manufacturer.

Rated voltage:	3V	6.3V	10V	16V	25V	40V	63V	100V
Capacity $\mu$ F:								
0.47								7p
1.0								7p
2.2								7p
4.7				7p				7p
10				7p				7p
22				7p				7p
47				7p				8p
100				7p				8p
220				7p				10p
470				7p				12p
1000				8p				17p
2200				8p				20p
4700				8p				23p
10,000				8p				24p
				37p				40p

### Polycarbonate —5% Tolerance

250V up to 0.1 $\mu$ F; 100V/0.1 $\mu$ F and above.  
0.01; 0.012; 0.015; 0.018; 0.022; 0.027; 0.033; 0.047; 0.056; each 4p.  
0.068; 0.082; 0.1; 0.12; 0.15 each 4p.  
0.18; .22; each 5p.  
0.27; 0.33; 5p. 0.39 7p. 0.47 8p. 0.56 10p.  
0.68 11p. 1 $\mu$ F 13p.  
Prices subject to amendment by the manufacturer.

**SILVERED MICA** non-polarised capacitors in 34 values from 2.2 pF to 680 pF, each 6p

### RESISTORS 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9 (see note below)	10 to 99	100 up
C	1/20W	5%	92 $\Omega$ -220K $\Omega$	E12	9	8	7.5
C	1/8W	5%	4.7 $\Omega$ -470K $\Omega$	E24	1	0.9	0.75
C	1/4W	10%	4.7 $\Omega$ -10M $\Omega$	E12	1	0.9	0.75
C	1/2W	5%	4.7 $\Omega$ -10M $\Omega$	E24	1.2	1	0.8
C	1W	10%	4.7 $\Omega$ -10M $\Omega$	E12	2.5	2	1.6
MO	1/2W	2%	10 $\Omega$ -1M $\Omega$	E24	4	3	2 net
WW	1W	10% $\pm$ 1/20 $\Omega$	0.22 $\Omega$ -3.9 $\Omega$	E12	7	7	6
WW	3W	5%	1 $\Omega$ -10K $\Omega$	E12	7	7	6
WW	7W	5%	1 $\Omega$ -10K $\Omega$	E12	9	9	8

Codes: C—carbon film, high stability, low noise.  
MO—metal oxide, Electrolox TR5, ultra low noise.  
WW—wire wound, Pleassey.

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.


Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order.)

★ Please remember to add V.A.T. to your order.

**IMPORTANT:** We regret that where substantial price increases have occurred in some items these are due to the increased costs of imported lines. S.A.E. brings amended list.
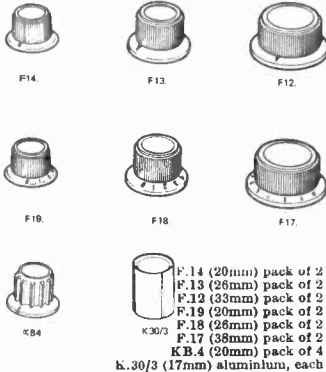
### KNOBBS

All grub screw fitting for 1" shafts. Black. For other types—see Catalogue No. 6, P. 54



F.14 (20mm) pack of 2 32p  
F.13 (26mm) pack of 2 38p  
F.12 (33mm) pack of 2 40p  
F.19 (20mm) pack of 2 32p  
F.18 (28mm) pack of 2 38p  
F.17 (38mm) pack of 2 40p  
K.B.A. (20mm) pack of 4 40p  
k. 30/3 (17mm) aluminium, each 24p

### IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 100's of semi-conductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc. information and equivalent tables, etc. Well illustrated (96 pages 5 1/2" x 8 1/2") 25p. post free with refund voucher for 25p. allowable on orders over £5 or more.

with  
**25p**  
refund  
voucher

### POTENTIOMETERS

Rotary carbon track, double wiper SINGLE P20 lin 100 $\Omega$  to 2.2M  $\Omega$  12p, P20 log 4.7K  $\Omega$  to 2.2 meg. 12p JP20 Log, 4.7K  $\Omega$  to 2.2M  $\Omega$  12p, Dual gang lin 4.7K  $\Omega$  to 2.2m  $\Omega$  42p; Dual log, 4.7K  $\Omega$  to 2.2m  $\Omega$  42p; Log/antilog, 10K, 22K, 47K, 1M  $\Omega$  only 42p; Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.


Only decades of 10, 22 & 47 available in ranges quoted.

**DUAL CONCENTRIC DP20** in any combination of P20 values, 60p; with switch, 72p.
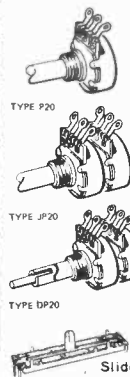
### SLIDER

Lin or log, 10K to 1meg. in all popular values, each 28p.  
Control knobs: blk/white/red/yel/or./blue/dk. grey/lt. grey, each 5p.

**CARBON SKELETON PRE-SETS**  
Small high quality, PR lin: 100 $\Omega$  220 $\Omega$ , 470 $\Omega$ , 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M  $\Omega$ . Vertical or horizontal mounting, 5p each.



All items offered for sale in accordance with our stated terms of business, copy of which available on request. Prices quoted DO NOT include V.A.T. Orders from U.K. customers must be accompanied by an additional 10% of net value for V.A.T.

**DISCOUNTS** Not allowed on net price items. 10% on orders for £5 or more, 15% on orders for £15 or more. Prices subject to alteration without prior notice.  
**PLEASE SEE LATEST AMENDMENT LIST. SEND S.A.E.**

**POSTAGE AND PACKING FREE**  
SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.

# ELECTROVALUE

(Dept. P.W. 6) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB  
Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 3603 Telex 264475

ENG. REG. NO. 1047788. R.O. 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT OPEN 6 DAYS A WEEK. 9.00 a.m. - 6.00 p.m.



TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD. 163 MITCHAM ROAD, LONDON SW17 9PG 01-672 3137/9080


**PRE-AMPLIFIER £4.22**



All Tuac audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into the various wide range tone control circuits, producing superb sound quality from any signal. Previous range still available.

- VA08 — Vol, Treb, Mid and Bass Controls. HI £4.22 I.M.P.FET I/P. Suitable Mic, Guitar, Radio, Illus. Crystal/Ceramic P.U. Sensitivity 4mV.
- P. & P. 20p Treb +28dB at 18kHz, Mid +20-15dB at 4kHz, Bass +20-10dB at 40Hz.
- VA06 — Vol, Treb and Bass Controls. 8mV sensitivity. Treb +22-15dB at 12kHz, P. & P. 20p Bass +18dB at 40Hz.
- MVA01 — Vol, Tone, Vol, Tone Controls. Ideal for £4.50 Disco. Suitable for Mic I/P. Sensitivity P. & P. 20p 2mV. Tone range +25dB at 12kHz to +20dB at 40Hz.
- AMF01 — Auto Mic Over-ride for Disco use. Feed £4.40 Deck and Mic Pre-amps in. Auto fade P. & P. 20p O/P to main Amp. 30mV operating level. Depth and Vol Controls.


**POWER AMPLIFIER £15.18**

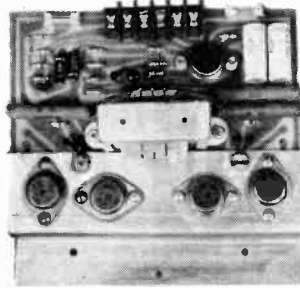

**TRI00W with RCA output transistors—150w device 2N6254**

**TP100W** £15.18 P. & P. 45p. Illus. **TP50W** £10.36 100 Watts r.m.s. continuous sine wave into 8Ω. 30mV input into 3kΩ full power frequency response 10Hz-20kHz ± 2dB. Hum and noise better than -70dB. T.H.D. at 100 Watts 2%. This rugged circuit incorporates a special layer wound driver transformer to give increased reliability under all conditions. Short and open circuit proof. An external heatsink area is required. Just bolt on the module. **PS100** 50 Watts r.m.s. continuous sine wave into 8-15Ω. With 115 Watt RCA 2N3055 output transistors. Specification as TP100W.


**POWER SUPPLY £9.10**

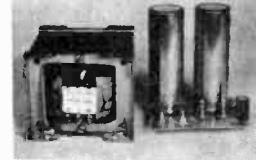

100 W, R.M.S. sine. 200 W, R.M.S. square. £28.50 + p & p Trade & export enquiries welcome.

- PS100**— 100 Watt Power Supply for one TP100W £9.10 Module. Complete as illus. above.
- PS50** 50 Watt Power Supply for one TP50W £6.86 Module. Similar to illus. above. Postage and Packing 50p each.
- PSU2**— 40V, 250mA. Pre-amp/Disco Mixer £2.95 Supply. P. & P. 25p.

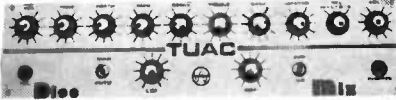**DISCOTHEQUE MIXER FEATURING AUTO-FADE**



Panel mounting Cut out 17 x 3 1/4 ins.

£22.00. P. & P. 50p. **PSU £2.95** Designed for the discerning D.J. of professional standard. Auto Fade is fitted as standard. Controls: Mic Vol, Tone, Over-ride depth, Auto Manual Sw. Tape Vol, L & R Deck Faders, Deck Volume, Treb. & Bass, H. Phon Vol, Selector, Master Vol, on/off sw.

**HIGH POWER AMPLIFICATION**



Suitable for Disco, P.A., Guitar etc. Rugged circuit, rugged case.

**LIGHT MODULATORS**

Triac controlled. Safety isolating input transformer. 0.5 Watt sensitivity with controls. **SILMB** 3 1000 Watt outputs. £17.45 Bass, Mid & Treb. **S2LMB** 1 1800 Watt output. £6.47 Operates on all frequencies. P. & P. 30p

ALL TUAC KITS ARE SUPPLIED COMPLETE WITH EASY TO FOLLOW WIRING INSTRUCTIONS AND CIRCUIT DIAGRAM. ALL PRICES INCLUDE VAT.

**LARGE S.A.E. WITH ALL ENQUIRIES PLEASE.**

ALL TUAC MODULES ARE READY ASSEMBLED ON GLASS FIBRE P.C. BOARD AND INDIVIDUALLY TESTED

New VAT EDITION



**Lasky's Audio-Tronics Catalogue 1973**

The new 1973 VAT edition of Lasky's famous Audio-Tronics catalogue will be available in early April—FREE on request. The 48 tabloid size pages—many in full colour—have been reprinted with VAT price changes for your convenience, together with many new items. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape Recording and Audio Accessories. Send for your copy now and see for yourself that VAT can mean a saving on many of the 1000's of items we offer.

**FREE** Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME .....

ADDRESS .....

PW13

LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1.

**PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDE, YORKS WF15, 6PQ**

TEL. HECKMONDWIKE 4285

THE T.V. GRAVEYARD OF THE NORTH, AS SEEN ON T.V. CLOSE TO THE MOTORWAY. PLENTY OF FREE PARKING SPACE. EST. 1935.

**SPECIAL OFFER**

1000 PYE 19" 13 Channel T.V. Sets. Brilliant Picture, Extra Slim Bench Tested. Sold with Money Back Guarantee. Hurry, have a second set at the price of £5.50. Plus carr. and ins. £1.80. FAMOUS R. & A. 7x4" Speakers ex T.V. 3 Ohm 2 1/2 Watt 50p. Post and Packing 12p.

COMPLETE UNTESTED T.V. SETS. With back and all valves. BBC 1 and ITV 17" 90° Tubes £1.10, 17" 110° Tube £2.20. 19" £3.30. Carr. and ins. on any set £1.75.

Reclaimed T.V. Tubes. All with 12 Months Guarantee, AW43/88 £1.65, MW43/69 £1.10, AW43/80, £1.65. Carr. and ins. on any tube £1.75.

1/2 Cwt. of ex Government Scrap Resistors, Panels and Gears, etc. 30p. Carr. 80p.


SPEAKERS REMOVED FROM T.V. SETS, all 3 Ohm 2 1/2 Watts. 7 x 4", 6 x 4", 8 x 2 1/2". All at 27p. Post and packing 12p.

TOP QUALITY TAPE. Reel to Reel 5" ST, 4 1/2" LP 55p, 5 1/2" LP 60p, 7" ST 66p, 7" LP 80p, Cassette Types C60 35p, C90 45p, C120 55p. Post on any tape 12p.

Japan Earpiece 8 Ohm Magnetic 3-5 12p. Ex Equipment Valves all tested on our Mullard Valve Tester before despatch. 3 months guarantee on all valves. Single Valves Post 3p, over Post Free.

ARP12	6p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF80	10p	PCL82	14p	UI91	20p
EBF89	15p	PCL83	15p	6BV77	12p
ECC81	12p	PCL84	15p	6U4	12p
ECC82	12p	PL82	10p	6F23	20p
EF91	5p	PL83	10p	20P1	15p
EY86	22p	PL36	17p	20P3	12p
EF183	20p	PY81	10p	30F5	12p
EF184	20p	PY801	17p	30FL1	20p
		PY800	17p		

ABOVE PRICES INCLUDE V.A.T.

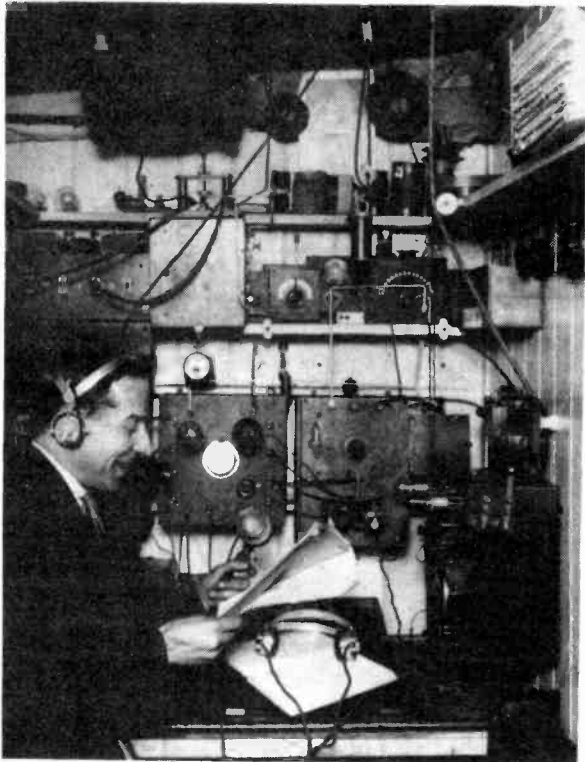

The spark gap at 5SV can be seen on the top shelf under the copper strip helix coil which 'tuned' the transmitter. Below is the 2-valve transmitter consisting of an oscillator and modulator.

Mason's equipment was impounded and he found himself with the Royal Naval Air Service at the White City in London, very close to the present site of the BBC TV service. After operating WT equipment from airships based at near-by Wormwood Scrubbs (another famous name!) 5SV passed to Manston for flying training and finished up with No. 3 Wing in France. Unfortunately Mr. Mason is no longer on the air, which is rather unusual. Generally the bug, having bitten, doesn't let go! At least not for long!

# Q4

is coming to  
**PW**

## Would you spend an hour a day to earn more money in Electronics- Television-Radio?

If you're willing to give up one hour or more a day we can help you get into the lucrative growth industries of electronics, television, radio.

And if you're already *in*, we can help you get on!

With our know-how and our wide experience in teaching, plus your determination to study, we can turn your interest into the technical knowledge you need for success. Once you've got the qualifications you need, you'll be in a good position to take full advantage of the opportunities which exist today in all fields of electronics - in television (colour and black/white) and in radio. (We teach you the theory and practice of valve and transistor portable circuits while you build your own 5 valve receiver, transistor portable and high grade test instruments).

With ICS you study at home - at your own pace, when *you* choose, in the time you've got available. Your ICS tutors will give you all the help and encouragement you need to pass any exams you want to take.

Don't waste another day. Take your first step *now* towards a better paid, more assured future. Send for your **FREE** Careers Guide today.

**ICS** your key to the door  
of opportunity

Tick or state subject of interest and post to:  
International Correspondence Schools, Dept. 232 P.  
Intertext House, Stewarts Road, London SW8 4UJ.

Subject of interest \_\_\_\_\_

- Society of Engineers Graduateship (Electrical Engineering)
- C & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificate in Technical Communication Techniques
- MPT General Certificate in Radio Telegraphy
- Audio, Radio & TV Engineering & Servicing
- Electronic Engineering, Maintenance, Engineering systems, Instrumentation & Control systems
- Computer Engineering and Technology
- Electrical Engineering, Installations, Contracting, Appliances
- Self-build radio courses

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_

Occupation \_\_\_\_\_

Age \_\_\_\_\_

Accredited by the Council for the Accreditation of Correspondence Colleges



## BROADCAST BANDS

### SHORT WAVE DX by MALCOLM CONNAH

**A** PART from the gems of information which can be gleaned from this monthly page, the best sources of DX information and station news are the DX programmes broadcast by many stations throughout the World.

The following list shows the times at which some of the more popular programmes are broadcast. In all cases the broadcasts are in English.

*Australia* "DXers Calling" is broadcast during the English transmissions on Saturday at 2130; Sunday at 0430, 0730, 1300 and 1530 and on Monday at 0215.

*Ecuador* HCJB in Quito broadcasts its "DX Party Line" programme on Monday at 0030, Tuesday at 0300 and 1930 and on Wednesday at 0900.

*Great Britain* The BBC's "World Radio Club" programme is broadcast over the normal World Service outlets at the following times: Sunday at 0815, Wednesday at 1330, Thursday at 2030 and Friday at 2345.

*Portugal* Adventist World Radio transmit a programme of DX News compiled by our own World DX Club at 0935 on Sundays on 9670kHz.

*Sweden* The "Sweden Calling DXers" programme is 25 years old this year but can be referred to as the "granddaddy" of DX programmes. The programme is broadcast every Tuesday and takes up half an hour of the normal English programmes.

*Switzerland* "Swiss Shortwave Merry-go-Round" is broadcast in all the English transmissions of the Swiss B.C. on the 2nd and 4th Saturdays of the month.

### Readers' Logs

The first item in this section this month comes from **John Godwin** of Rugeley in Staffordshire. John reports hearing *Radio New Zealand* between 0600 and 0800 on 11780kHz on his pre-war HRO receiver and "Joystick" antenna.

The transmitter power of *Radio New Zealand* is only 7½kW and reception in this country is fairly difficult. Well done John!

**Alexander Morton** of Framlingham in Suffolk has two receivers, a Bush AC2, 5 valve domestic and a VEF-204 10 transistor portable. His log included:

5920 R. Kiev, in English at 1930.

9023 *Voice of Iran* in English at 2000.  
9690 R. Pakistan with news in English at 1815.  
9745 HCJB, Quito, Ecuador, DX Partyline at 0900.  
10040 *Voice of Vietnam*, Hanoi, news in English.  
15415 R. Kuwait in English at 1630.  
17895 R. Portugal in English at 1345.

**Ian Gordon** of Rubery, Birmingham has managed to extract signals from the following stations out of the central heating radiator which he use as an aerial and coax them into his Codar CR70A receiver:

9005 R. Iran in English at 2015.  
9570 R. Australia at 0730.  
9655 R. Damascus, Syria in English at 2050.  
9670 *Adventist World Radio* at 0940.  
9745 R. Baghdad, Iraq in English at 1950.  
11675 R. Pakistan in English at 2035.  
11710 RAE, Argentina, s/on at 2300.  
11765 R. Australia, DXers Calling (Sun.), 0730.  
15012 *Voice of Vietnam*, Hanoi in English at 1815.  
17885 R. Japan, s/on at 0800 in English.

**Shaun O' Sullivan** of Keynsham (yes that's K-E-Y-N-S-H-A-M of Radio Luxemburg fame), Bristol, has a one valve 'H.A.C.' t.r.f. receiver and a two transistor amplifier connected to a 100 foot long-wire antenna. This combination enabled him to hear:

5930 *Radio Prague*, Czechoslovakia in English at 2135.  
5995 *Voice of America* in English at 2040.  
6160 *Radio Sofia*, Bulgaria in English at 2135.  
6190 *Vatican Radio* in English at 2100.  
7090 *Radio Tirana*, Albania in English at 2040.  
7100 *Radio Moscow*, USSR at 2110.

**Dave Gregory** of Plymouth in Devon has a Bendix RA-1 aircraft receiver and an 80 foot long-wire antenna, his log for the month included:

7100 R. Pakistan in English at 2200.  
9125 Test transmission from *Panama City* at 0035.  
9535 *Swiss B.C.*, Berne in English at 1530.  
9725 *Kol Israel* noted at 2140.  
9770 R. Baghdad, Iraq at 2045.  
11640 R. Bangladesh in English at 1800.  
11755 AIR, Delhi in English at 2230.  
11805 *Radio Finland* noted at 1910.  
11880 *Radio Sweden* in English at 1230.  
11900 RSA, South Africa in English at 1115.  
15175 *Radio Norway* noted at 2200.

### DX Clubs

The Youth DX Club International (YDXCI) which was mentioned in this column last month has announced that the maximum age of its members will be 17 years. The membership fee is £1.20 which includes the cost of sending the magazine to any country. The address for membership enquiries is YDXCI, Bartletts, Culmstock, Cullompton, Devon.

## PRICES NOW INCLUDE VAT

### SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transformers in push-pull. Full wave rectification. Output approx. 13 watts

r.m.s. into 8 ohm. Frequency response 13Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE  $\pounds$ 11.60. P. & P. 25p.

### DE LUXE STEREO AMPLIFIER



A.C. mains 200-240 V. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate

smoothing with negligible hum. Valve line up:—2 x ECL86 Triode Pentodes, 1 x E260 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono). Into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE  $\pounds$ 29.90. P. & P. 45p.

**POWER SUPPLY UNIT 200/240V.** A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 9v. and 12v. at 1 amp continuous (1 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hamner finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. PRICE  $\pounds$ 5.00. P. & P. 35p.

**BLACK ANODISED 16g. ALUMINIUM HEAT SINKS.** For TO3, complete with mica's and bushes. Size 2 1/2" x 3" approx. 28p pair. P. & P. 5p.

**HIGH GRADE COPPER LAMINATE BOARDS 8" x 6" 5 for 55p P. and P. 13p.**

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-45-50-60v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price  $\pounds$ 2.10. P. & P. 30p.

**MAINS TRANSFORMER.** For transistor power supplies. Fri 200/240v. Sec. 0-0-9 at 500mA.  $\pounds$ 1.00. P. & P. 13p. Fri 200/240v. Sec. 12-0-12 at 1 amp.  $\pounds$ 1.10. P. & P. 13p. Fri 200/240v. Sec. 10-0-10 at 2 amp.  $\pounds$ 1.65. P. & P. 30p.

**CENTRE ZERO MINIATURE MOVING COIL METER.** 100uA. For balance or tuning. Approx. size 1" x 1" x 1 1/2" deep. Limited number. 88p. P. & P. 10p.

#### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid enclosure size 1 1/2" x 1 1/2" x 1 1/2". Brand new complete with instructions. Price.  $\pounds$ 1.00 P. & P. 13p.

#### HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents	30p
Transistor Equivalents	30p
Transistor Characteristics	$\pounds$ 1.15
POST FREE	
All three together	$\pounds$ 3.80

Open 9-5.30 Monday to Friday, 9-5 Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

**RECORD PLAYER BARGAINS**  
Mains models. All brand new in maker's packing.  
**LATEST B.S.R. C109/C125 AUTOCHANGER UNITS** with latest stereo/mono compatible cartridge  $\pounds$ 7.80 + 50p P. & P.  
**GARRARD SP25 Mk III** with heavy precision machined die cast turntable  $\pounds$ 10.56, carr. 50p.

**PRECISION ENGINEERED PILLBOXES**  
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, 5165B, A700 etc. or B.S.R. C109, C125, A21 etc. back leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover).  
**NOW ONLY  $\pounds$ 4.95, P. & P. 35p.**

**LATEST ACOS GP91/180** mono compatible cartridge with 1/2 stylus for LP/EP/78. Universal mounting bracket.  $\pounds$ 1.50 P. & P. 35p.

**SONOTONE STARC COMPATIBLE STEREO CARTRIDGE** T/O stylus Diamond Stereo LP and Sapphire 78. ONLY  $\pounds$ 2.80 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP.  $\pounds$ 2.80. P. & P. 10p.

**LATEST BOWTIE T/O STEREO/COMPATIBLE CARTRIDGE** for EP/LP/78.  $\pounds$ 1.65 P. & P. 10p.  
**LATEST BOWTIE T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono stereo records on mono equipment. Only  $\pounds$ 1.50 P. & P. 10p.

**QUALITY RECORD PLAYER AMPLIFIER MK II**  
A top quality record player amplifier employing heavy duty double wound mains transformer. ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE  $\pounds$ 44.40 P. & P. 40p.  
ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE  $\pounds$ 25.95 P. & P. 50p.

### SPECIAL OFFER ! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynal front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two E.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 16 ohms impedance.

**OUR PRICE  $\pounds$ 9.25 Carr. 70p**  
Cabinet Available Separately  $\pounds$ 4.85 Carr. 65p  
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter  $\pounds$ 7.15 Carr. 70p

**HARVERSON'S SUPER MONO AMPLIFIER**  
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.  **$\pounds$ 3.30** P. & P. 35p BARGAIN PRICE

**LOUDSPEAKER BARGAINS**  
5in. 3 ohm  $\pounds$ 1.06, P. & P. 10p. 7 x 4in. 3 ohm  $\pounds$ 1.15, P. & P. 20p. 10" 8in. 2 or 15 ohm  $\pounds$ 1.90, P. & P. 30p. E.M.I. 8" 5in. 3 ohm with high flux magnet  $\pounds$ 1.80, P. & P. 20p. E.M.I. 13 1/2" 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm  $\pounds$ 3.50, P. & P. 30p. R.M.I. 13" 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network  $\pounds$ 4.65, P. & P. 30p. E.M.I. Ceramic magnet heavy duty tweeter. Approx 3 1/2". Available 3 or 8 or 15 ohms.  $\pounds$ 1.95 + 15p P. & P.  
**BRAND NEW 12in. 15w. H/D Speakers.** 3 or 15 ohms. Current production by well-known British maker. Now with Hifux ceramic ferrobar magnet assembly  $\pounds$ 7.50. Guitar model: 25w.  $\pounds$ 7.50 35w.  $\pounds$ 9.35. P. & P. 40p



#### SPECIAL OFFER!

**LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS**

With large ceramic magnet and plasticised cone surround. 8 ohm impedance.  $\pounds$ 70. P. & P. 25p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3, 8 or 15 ohm  $\pounds$ 45. P. & P. 30p.

35 ohm SPEAKERS 3in. only 70p P. & P. 13p.

**"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER**

Size 1 1/2" x 1 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceiling, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only  $\pounds$ 6.55 each. P. & P. 25p.

**VNAIE & REKINE SPEAKERS & CABINET FABRICS** app. 54 in. wide. Our price 85p yd. length. P. & P. 10p per yd. (min. 1 yd.). S.A.E. for samples.

#### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable softfoam ear-muffs. Wired and fitted with standard stereo 3 1/2 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE  $\pounds$ 2.80, P. & P. 10p.

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE  $\pounds$ 1.15, P. & P. 10p

## HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



**NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASY CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibreglass printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts, no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response  $\pm$ 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M  $\Omega$ . Full power bandwidth:  $\pm$ 3dB 12-15,000 Hz. Bass boost approx. to  $\pm$ 12dB. Treble boost approx. to  $\pm$ 16dB. Negative feedback 18dB over main amp. Power requirements 30v. at 1.0 amp. Overall Size 12" w x 8" d x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.  
**AMPLIFIER KIT** .....  $\pounds$ 11.55 P. & P. 18p  
**MAGNETIC INPUT COMPONENTS 33p extra**  
**PCB WAFER PACK KIT** .....  $\pounds$ 2.80 P. & P. 35p  
**CABINET** .....  $\pounds$ 4.85 P. & P. 35p

(Post Free if all units purchased at same time)  
Full after sales service.  
Also available ready built and tested  $\pounds$ 23.10. Post Free.  
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will also provide mixing and fading facilities for medium powered Hi Fi Discotheque use, etc.



**WAVE AUDIO AMPLIFIER HA34 MK II.** Designed for HI-FI reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4" d x 4 1/2" h. Incorporates ECC83, EL84, E260 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm


speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc. built and tested for only  $\pounds$ 25.50. P. & P. 35p.

**EGG "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc.  $\pounds$ 4.80. P. & P. 40p.

British made solid state all silicon stereo amplifier. 15 watts rms per channel output. Fre. res. 20Hz to 20KHz. Suitable for magnetic or ceramic pickup tape mic. etc. built in switcheable scratch filter, rumble filter and loudness control. 60 m/m alder controls for bass, treble and volume. 10 way push button function, selector switch. This amplifier has specification and performance usually only found in amplifiers costing twice as much. Each amplifier supplied, tested and fully guaranteed. Finished in the most attractive contemporary style teak cabinet, Size 16 1/2 in x 8 in x 4 in. Makers recommended price  $\pounds$ 46.36. (inc. VAT) Our price (while stocks last)  $\pounds$ 35.76 (inc. VAT) + 75p. p. & p. Send SAE for full details of specification.
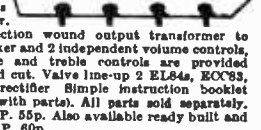
#### 10W WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 10 watts into 8 ohms. Uses two ECL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-16  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up: 2 EL84s, ECC82, EF86 and E280 rectifier. Simple instruction booklet 10p + SAE (Free with parts). All parts sold separately. ONLY  $\pounds$ 28.80 P. & P. 55p. Also available ready built and tested  $\pounds$ 19.10 P. & P. 60p.



(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES



### SINCLAIR PROJECT 60

Z30 £3-50  
 Z50 £4-25  
 PZ5 £3-97  
 PZ6 £6-40  
 Project 60  
 tuner £16-80  
 AFU £4-50  
 PZ8 £6-00



Stereo 60 £7-80  
 2000 Amp £22-00  
 Transformer for PZ8 £2-05


**EXECUTIVE CALCULATOR £30-00**

**PROJECT 60 KIT £2-50**  
 Our extremely popular kit contains the extra capacitors, din plugs and sockets, cable and fuse-holder needed to complete Project 60.

**IC RADIO CHIP TB851 £2-10**  
 The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amp, wide range AGC circuitry and voltage stabilizer. With data £2-10. Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1-75.
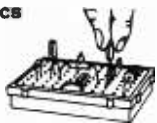
### S-DECS AND T-DECS

S-DECS £1-44  
 T-DECS £2-88  
 µ-DEC A £3-00  
 16 diil IC carriers £1-20



### SINCLAIR SUPER IC12

ONLY £2-00



Max. supply volts 28. Power 6 Watts rms. Complete with free printed circuit board and 44 page instruction book.

**SWANLEY IC TOMORROW £2-50**  
 The World's most powerful IC amplifier. Similar to the above but operates at 35 volts max. supply and gives 12 Watts rms output. Manufactured for us by a leading semiconductor company. Supplied with our instructions and a 6 month guarantee, but no printed circuit.

**KITS FOR IC12 AND IC TOMORROW**  
 Except for the power kits and speakers, all items suit both integrated circuits.

**DELUXE KIT**  
 includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-45. Stereo version with balance control £3-30.

**BASIC KIT**  
 Contains components for the P.C. board and volume and simple tone controls. Mono version £1-25. Stereo version with balance control £2-80.

**POWER UNITS FOR THE IC12**  
 A set of components to construct a 28V 0.5 Amp power supply £2-27. Also suitable Sinclair PZ5 fully constructed £3-97.

**POWER KIT FOR IC TOMORROW**  
 A set of components to construct a 35V 1 Amp power supply £2-97.

**LOUDSPEAKERS FOR THE IC12**  
 Specially chosen for the IC12. 5" 8 ohm £1-00. 5" x 8" 8 ohm £1-45. 10" x 8" 15 ohm £2-27.

**PREAMPLIFIER KITS**  
 Type 1 for magnetic pickups, mics and tuners. with 3 position equalization switch. Mono model £1-20. Stereo model £2-20. Type 2 for ceramic or crystal pickups. Mono 60p. Stereo £1-20. SEND S.A.E. FOR FREE LEAFLET ON KITS

### BATTERY ELIMINATOR BARGAIN £3-40

Introducing the most versatile battery eliminator ever offered, with a high current output that makes it suitable for operating most battery tape recorders, record players, cassette recorders and shavers. Input 200/240V. Output voltage selected by front panel switch may be set to 3V, 4.5V, 6V, 7.5V, 9V and 12V at 500 ma. Housed in a very strong, attractive, plastic case and fully guaranteed for 12 months.



### SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent  
 Post 10p per item. Please add 10% extra to total cost of order for V.A.T. Official credit orders welcome from schools etc. Full lists 10p post free. Mail order only. No callers please.



## TRANSCEIVERS

Due to warehouse clearance we have for disposal, few only Transreceivers No. 62 Mk. 2, made by Pye for the Navy and Army. Using a total of 11 valves. 1 RF and 2 I.F. stages. A.V.C., BFO, covering 1.5 Mc/s to 10 Mc/s. (approx. 200 to 30 metres) in two switched bands. Can be used on RT or CW M.O. or Crystal. A very good internal ATU made of a rotating silver wire coil, tunable over the complete range, suitable for aerials 4ft. to 100ft., internal P.U. for 12 volt D.C. A meter is fitted for checking voltages. A.V.C. etc. Housed in a metal water-proof case, approx. size 18" x 10 1/2" x 12 1/2". Supplied in as new condition, being either re-built by Army Signals or store-soiled new set. In cartons two spare valves, circuit, price £17-50, carriage £2. Suitable hand telephone with spring coil plus transmitter switch in handle. Modern. £1-50.

**CRYSTAL CALIBRATOR No. 10.** Range 500 kc/s. to 10 Mc/s., up to 30 Mc/s. on Harmonics. Size: 7" x 7 1/2" x 4". Power 300 volts HT. 12 volts L.T. The Calibrator can plug into a Power Socket on the 62 Trans-Receiver which it was normally used with. Supplied in good used condition with circuit, £2-50, Post 50p. or BRAND NEW IN CARTON, £5-00, 50p. post.

All enquiries include S.A.E. Terms; cash with order or uncrossed P.O. as these will be returned if items out of stock. Please add 10% VAT

## JOHNS RADIO

424 BRADFORD ROAD,  
 BATLEY, YORKS.

Phone: Batley 7732

### EX COMPUTER PC PANELS

2 x 4 in. packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors plus data. 10 boards 50p (9p)

### SPECIAL BARGAIN PACK

25 boards for £1 (25p).  
 Panels with 4 Power transistors sim OC28 50p (9p)

### ELECTROLYTICS

10,000µ 75v, 68,000µ 16v, 4 1/2 x 2 in. dia., 25,000µ 25v, 20,000µ 30v, 5,000µ 90v, 35,000µ 15v, 8,000µ 55v, 4 1/2 x 3 dia. 50p (15p)  
 15,000µ 15v, 10,000µ 35v, 4 1/2 x 2 in. dia. 30p (10p), 2,000µ 25v wire end 15p (5p).  
 12 for £1-50 (15p)

8 BLACK TOGGLEs dpst 50p (8p)

250 MIXED CAPACITORS 60p (8p)

250 MIXED RESISTORS 60p (8p)

150 HI-STAB RESISTORS 60p (8p)

200 SI PLANAR DIODES 50p (5p)

SUB. MIN. CO-AX PLUGS & SKTS. 4 pairs 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES 8 for 50p (8p)

ASSORTED RELAYS 8 for £1 (12p)

MIN. GLASS NEONS 12 for 50p (5p)

10 WAY TERMINAL BLOCKS 10 for 55p (5p)

Q-H BULBS 12v 55w 50p (5p)

Postage and package for each item shown in brackets.

Please add 10% VAT to prices.

## KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD  
 LONDON W8. 01-478 8499

## Beginner's Guide to Colour Television

2nd Edition Gordon J. King

The reader is guided through the principles of NTSC and PAL to an understanding of the method of operation of the PAL system from aerial to display tube. The author, noted for his crisp and lucid style, has completely revised this edition which will be of immense value to all who wish to understand how colour television works.

1973 208 pp, illustrated  
 0 408 00101 1 £1-95

## Elements of Linear Microcircuits

T. D. Towers

Based on a series of articles written for *Wireless World*, the book gives practical guidance on the commercially available linear microcircuit devices, and on the handling of these sensitive circuits within an assembly. The emphasis throughout is on applications and on the everyday problems of designing.

1973 116 pp, illustrated  
 0 592 00077 X £2-80

## Television Engineers' Pocket Book

6th Edition

Revised by P. J. McGoldrick

Extensively revised and updated, the sixth edition of this popular book provides an essential summary of all the basic facts, circuit techniques and technical data likely to be required for servicing either colour or monochrome receivers.

1973 376 pp, illustrated  
 0 408 00102 X £2-50

Obtainable through any bookseller or from the Publishers

## The Butterworth Group

88 Kingsway, London WC2B 6AB  
 Showroom: 4-5 Bell Yard, London WC2





## MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

**B**ILL JARVIS (Luton) has received direct from the BBC "20 BBC Local Radio Stations" which gives details of locations and power.

**R. Howard** (East Runton) has sent the following log of BBC Local Radio Stations heard at his QTH in Norfolk—Radio Blackburn on 854kHz; Radio Sheffield 1034kHz; Leeds 1106kHz; Newcastle-on-Tyne 1457kHz; Teeside (Stockton) 1594kHz. He also reports hearing La Coruna, Spain on 638kHz; AFN Bremerhaven 1142kHz and Radio Sud, Andorra on 818kHz. Andorra is a small independent state situated in the Pyrenees between France and Spain. Its other medium wave outlet is Radio Andorra on 701kHz and both stations will verify a correct reception report written in English, with a colourful QSL card. It appears that Andorra no longer broadcasts on the short waves and it is only on the medium waves that the DXers can hear broadcasts from this mini-republic. Reception reports should be sent to Radio Andorra, B.P.I, 66720 Andorra-la-Vieille,

## VHF/FM DXing

by SIMON DAVID

**F**IRST of all, my thanks to all those readers who wrote to me; I shall try to pick out interesting points from as many letters as my modest half-page allowance will permit and combine these with any news items that are useful.

Many of you take Band 2 seriously as DXers and this is really the basis on which this feature was started, but there are times when weather conditions, particularly in the summer months, can produce some odd twitterings even on the usual entertainment programmes from local stations.

**Mr. C. Rahn** of Chesterfield has made a study of reception conditions and confirms that humid overcast atmospheres and very warm temperatures bring in some long distant signals. Of course, it is of little help if conditions are cooler en route, so when you have one of those sultry sticky days and the weatherman says that this is spread over the whole country, forget the lawn mower and switch on your f.m. receiver.

It does help to have a multi-element array and if you can arrange for it to be rotated easily, then you are in for a mixed bag of DXing. Mr. Rahn has four aeriels: a roof 'H' set to Sutton Coldfield; an indoor 'H' rotatable; a piece of unscreened wire about 1ft. long; and an indoor telescopic. The most fruitful, of course, is the rotatable which brings in most of the BBC local radio stations from afar, plus numerous foreign stations. However, even Caen 95.6MHz was picked up by the telescopic. His tuner is the Omega ST-300C with a stereo decoder A1005M (G. W. Smith). Now with his new "weapon", a 6-element rotatable, he is getting even better results.

There were disturbances on April 1st due to an aurora borealis. Although not visible due to overcast skies, the effects on v.h.f. broadcasting were a

Andorra for the transmissions on 701kHz and to Sud Radio, B.P.7 Andorra-la-Vieille, Andorra for those on 818kHz. Remember to include an International Reply Coupon (obtainable from main Post Offices) to cover return postage and to ensure a reply.

**D. O. French** (Stroud Green, London) is unable to hear the religious broadcasts from Trans World Radio Monte Carlo on 1466kHz because of interference from the BBC Radio London station on 1457kHz which transmits from Brookmans Park. He expects TWR to increase power on 1466kHz from 400kW to 1000kW by the end of 1974. TWR will then join the growing list of medium wave broadcasters that use powers of a megawatt or more. Others include Radio Bucharest, Rumania on 1052kHz; El Beida, Libya 1124kHz and Tripoli, Libya 1250kHz both of which are easily heard in the UK after dark; Batra, Egypt 1106kHz; Skopje, Yugoslavia 809kHz; West Germany on 1421kHz and Radio Luxemburg 1439kHz. Other more distant stations that have been heard in the UK include Riyadh, Saudi Arabia on approx. 588kHz; Quazvin, Iran 841kHz (now with 2000kW); Rajkot, India on 1070kHz; Urumchi, China 1525kHz (usually in Russian with jamming) and the Voice of America Thailand 1580kHz in English at 2200hrs GMT. There is also the 1000kW outlet at Calcutta, India on 1130kHz which has been heard by the writer during July at 2200hrs GMT with sign-on at the start of its Chinese programme. It is worth looking for this station between the burble on 1133kHz and Barcelona/Libya on 1124kHz.

"burbling" note on continental stations, detected by Mr. R. Ham in Sussex on 42 and 72MHz. These noises also interfered with television on channels 3, 4 and 5.

The target for most DXers is to see how far into Europe one can penetrate on Band 2. Mr. G. P. Stanbury tells a fascinating tale involving an Antiference 4-element with two extra directors, a Rigonda "Symphony" radiogram with home made tuning meter in place of the magic eye, the f.e.t. preamplifier from April's P.W., and a rotatable aerial mounted on a cable controlled pulley system. In spite of some backlash, he has heard at his home in Chelmsford, Essex, many BBC stations as far away as North Hessay Tor and Wenvoe.

Continental pick-ups include five Dutch and three Belgian stations on Dutch network RTB-BRT, the latter being Aalter on 90.4, 95.7, 98.6MHz and Veltem on 89.5 and 93.7MHz. West German stations received include Langenberg and BFBS Cologne. There are local disturbances including a 400ft. hill and a police transmitter half a mile away that almost swamps the continentals at times. There is, he says, a local river board authority transmitter which appears to be "ill-matched to its damp string!"

One of the problems of DXing in residential areas is the interfering reflections from neighbouring aeriels, and badly aligned tuners without i.f. traps on the aerial can cause trouble. Mr. Stanbury appeals to all users to fit i.f. traps to keep the i.f. on a leash and I would endorse this wholeheartedly.

In the May article I mentioned rejection filters to suppress adjacent channels; the Wolsey Model No 2 covers 40 to 100MHz range with maximum rejection of 45dB. Most good aerial dealers should have these for around a fiver. Finally, the IBA have announced on their medium wave test transmissions on 557kHz that v.h.f. tests start in the autumn on 95.8MHz (entertainment), 97.3MHz (news).



## AMATEUR BANDS

### SHORT WAVES

by **DAVID GIBSON, G3JDG**

**A** good month for the persistent listener and some good DX loose on all bands—a fair assessment of the Amateur bands these past few weeks. Eighty metres has yielded such little treasures as ZL2BT and DU1EJ, and even 7MHz has seen fit to part with items like VK5CX and 5R8BD. Good DX on twenty and fifteen but the surprise came from 28MHz which has had spasmodic bursts of life. When this happened the DX was usually 599+ or 5 & 9+. Goodies on 28MHz logged include TU2DD, VP2LI and ZM1HV.

Occasionally one hears of an Amateur station accused of causing interference (QRM) to other receiving equipment, usually television. If this happens, the Amateur involved will take steps to solve the problem and help effect a cure for such QRM.

The boot is now on the other foot. There seems to be a marked increase in the number of intruders into the Amateur bands. Not only this but worse; the interference caused by these illegal intruders is deliberate. Other Hams have reported this also.

**John Bagley** (Birmingham) comments that we should find out where the QRM is originating from and then refuse to work Amateurs in that country(ies). It might, perhaps, be better to do exactly the reverse—make a point of working these localities and then diplomatically raising the question openly on the air i.e., “Do you suffer from QRM OM there seems to be a strong source somewhere in your area?”. The RSGB has set up an Intruder Watch. Perhaps its findings could be published?

A couple of hot tips have arrived. Listen 14250—14300kHz at 1230hrs. at weekends for YA1AH and YA0CDR. There is a net on Friday mornings (14250-14300kHz) called the Arabian Nights (Knights) Net. Stations from VK and ZL frequently call in.

Apparently that XG prefix heard by many mystified souls earlier this year was used by XE1J. Something to do with a 450th anniversary. Another callsign was changed because of the seventh Games held in Panama City. When will G stations get in on this callsign changing act? There are many events in England which merit an instant change of callsign:

hearing the first hedgehog; Noddy's birthday.

In the April issue I asked the real G4GJ to “stand up”. Well, he has! Operational from Bingley in Yorkshire since 1945 this station has a daily sked (not weekends) with G3CJS on 3680kHz. These stations have been doing some experiments with loop aerials.

**Lionel Outridge** (Canterbury) read my remarks re 4 metres (70MHz), and promptly built a converter using dual-gate MOSFET's (r.f. and mixer) plus a MPF102 crystal oscillator. Lionel says that a nearby BBC relay on channel 5 puts out a string of 50Hz modulated carriers right across the 70.1—70.3MHz band which makes reception difficult. (Who do you report the BBC to?). Other equipment is a FRDX400 and an indoor dipole. Stations received on 70MHz; G3—AJS, FDW/P, FIJ, FZL, IIR, JEQ/P, LVK, LVP, LVP/M, LVP/P, OHH, OQT, ORH, ORH/M RUA/P, TDM/P, VER/P, VHH, VPK, VPS/P, WMR/P, YCN, YTM, ZFP, ZRH, plus GB3SU, G4BLN, GW4ABR/P, GW4BGG/P and G6SG. So the band isn't morgue. How about a few more of us breathing life into it?

Anyone hear 5GAA, HA25KFZ or O1KA? **Gareth George** (Cheltenham) did and asks what, whom, who or where? (Perhaps someone else heard the first hedgehog?). Receiver is an HRO with a 100ft. long wire. A twiddle on twenty brought: EA3GN, EA5FQ, EA7QG, IT9JC, JA6BEE, JA6NPF, JA6YG, JA7BJA, JX1AK, JX5AZ, JY6UMS, OD5FB, VK3OC, VK3BJB, W7MTL/P, ZL2AAW, ZL2BFU, ZM2KG, ZK2BD all on s.s.b.

Thirteen-year-old **Chris Jones** is alive and well and living in West Bromwich. He also bagged: EA3WZ, IT9FKS, JA3XKJ, W6CYU, all with a CX203 and 70ft. end fed on twenty metres s.s.b.

We stop this 14MHz revelry to bring you a news flash: a two metre log has been received. Guilty party is one **David Noakes** who resides at Cranbrook in Kent. Using an f.e.t. converter (i.f. 28-30MHz), Trio JR310 and a 6-over-6 slot-fed he logged: F1AGY, F1CCP, F6CKU, G3AMF, G3FAB, G3RPZ, G3WKS/P (Rutland), G3YOA, G8BXX/P, G8CIW, G8CLY/P, G8FUF, G8FPR, G8GTD/P.

**Derrick Dance** (Roxburghshire), CR7OA, PR40 pre-electrode, a.t.u. and 264ft. end fed sends in a nice log of stations heard on topband. On c.w.: DJ3CY, GI3YFY, GW3RTR, OH1SJ, OL1AOH, OL1AQL, OL5AQK, plus several GM, OK1 and OK2 stations. On 160 metres s.s.b.: GM4BBL (Shetlands), GW3UCB, GW3ZQN, W4BIF, OE5KE.

At the other end of the scale, **Derrick** reports these on 28MHz c.w.: DL0IGI (beacon station), F3NB, ZC4CY (new beacon), 3B8MS (beacon), 3D6AX, 4X4SK, 9H1CH. The s.s.b. signals on 28MHz came from: CR6AM, CR6LF, CR7IZ, EA8GZ, EA8IB, LU8AJJ, ZC4DS, ZE1AV, 4X4HF, 4X4NJ, 4Z4DZ, 4Z4LI, 9J2AY, 9J2TB and PY5UI on a.m.

Events during June include: June 9-10, four metre open contest; 10, d.f. qualifying round at High Wycombe; 16-17, Microwave Field Day; 17, WAB v.h.f. contest (phone); 23-24, First Topband contest; 24, d.f. qualifying round at Chelmsford. July 7-8, Jubilee v.h.f./u.h.f. contest.

#### BROADCAST BANDS

Short Wave Reports by 15th of the month to **Malcolm Connah, 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.**

Medium Waves Logs to **Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.**

VHF/FM Reports to **Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.**

#### AMATEUR BANDS

##### Short Wave/VHF

Logs in alphabetical order please by 15th of the month to **David Gibson, G3JDG, 12 Cross Way, Harpenden, Hertfordshire.**

# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

## COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE

ONLY £1.05

POST & PACKING 38p EACH

## TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

ONLY 27½p

POST & PACKING 16p



OVER  
**1,000,000**

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

**600,000** Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.  
Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc.  
Please state Audio NPN or Audio PNP when ordering.  
ALL AT 500 for £3-30, 1,000 for £5-50, 10,000 for £44 P. & P. 11p/1,000.

### OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulation.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.  
TYPE "G" NPN Silicon similar ZTX 300 range  
TYPE "H" PNP Silicon similar ZTX 500 range

**8 RELAYS FOR VARIOUS TYPES £1-10**  
P & P 27½

## FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

### TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	55p
B81	10	Reed Switches, mixed types large and small	55p
B84	200	Mixed Capacitors. Approx. quantity, counted by weight	55p
H9	250	Mixed Resistors. Approx. quantity counted by weight	55p
H7	40	Wirewound Resistors. Mixed types and values.	55p
H9	2	OC771 Light Sensitive Photo Transistor	55p
H28	20	OC2001/1/2/3 PNP Silicon uncodcd TO-5 can	55p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6.8 - 43V.	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	55p
H38	30	Short lead Transistors. NPN Silicon Planar types.	55p
H39	10	Integrated Circuits. 6 Gates BMC 962, 4 Flip Flops BMC 945	55p
H40	20	BFY50/2, 2N696, 2N1613 NPN Silicon uncodcd TO-5	55p
H41	2	Sil Power transistors comp pair BD131/132	55p

### UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	55p
B1	50	Germanium Transistors PNP, AF and RF	55p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	55p
H17	20	3 amp. Silicon Stud Rectifiers mixed volts	55p
H15	30	Top Hat Silicon Rectifiers. 750mA. Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	55p

### MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.10 each



### Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors: PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Charts supplied to give some information on the Transistors. Please ask for Pak P.1. Only 55p. 11p P & P on this Pak.



### A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Television.

This complete kit of parts costs £3.85, post paid.

A MUST for Colour T.V. Alignment.

### STEREO DECODER £4-95

A ready built unit, ready for connection to the I.F. stages of your existing FM Radio or Tuner Unit. A tell-tale light can be connected to show the presence of a Stereo transmission and correct operation of the Unit.  
The Unit is in the form of a small printed circuit, and no further alignment is necessary, as all preset adjustments have already been carried out at the factory.

It is recommended that a L.E.D. is used as the indicating light and a suitable device is available from us @ 33p.  
Supplied with necessary instructions and written guarantee.

**100,000**

Plastic Power Transistors in stock, more on way!  
**NOW IN TWO RANGES**

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.  
Range 1. VCE. Min 15. HFE Min 15.  
40 Watt 22p 20p 18p  
90 Watt 26p 24p 22p  
Range 2. VCE. Min 40. HFE Min 40.  
40 Watt 33p 31p 29p  
90 Watt 38p 36p 33p  
Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

### INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

### METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.  
Pocket Size 15p. Wall Chart 18p.

### LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16p each. Now new low profile 16 pin type at 18p each type

### BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

**B.P.1 Transistor Equivalents and Substitutes;** 40p  
This includes many thousands of British U.S.A., European and C.V. equivalents.

**The Iliffe Radio Valve & Transistor Data Book 9th Edition;** p. & p. 231p. 75p  
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of publications  
N.B. Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME .....

ADDRESS .....

ALL PRICES INCLUDE VAT  
MINIMUM ORDER 50p. CASH WITH ORDER  
PLEASE Add 11p post and packing per order  
OVERSEAS ADD EXTRA FOR POSTAGE

**BI-PRE-PAK LTD**

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DF

TELEPHONE: SOUTHEND (0702) 46344

CO. REG. No. 820919

# TAKE 20


DAVID ANDREWS

**A series of simple transistor projects, using not more than twenty components.**

**T**HIS month's project describes a siren that utilises a voltage controlled relaxation oscillator. The output of the oscillator is fed to a very simple loudspeaker driver stage comprising Tr3 and Tr4 connected as a super-alpha pair. Alternative output stages to provide higher power can be used provided they present a comparatively high input impedance.
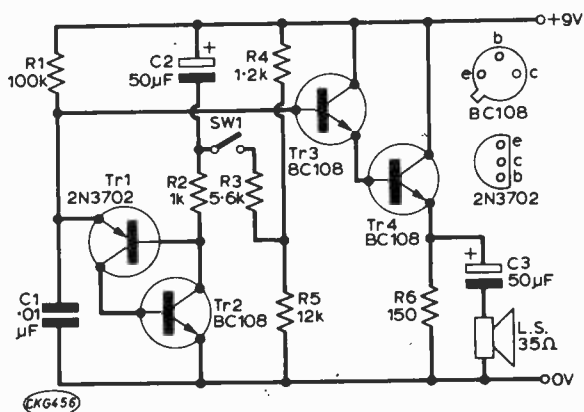
## Circuit

Tr1 and Tr2 form the active part of the oscillator. They can be almost any type of general purpose pnp and npn transistor respectively; but make sure they are connected the right way round. The fre-




The complete circuit of the electronic siren.

## ★ components list

R1	100kΩ	1p
R2	1kΩ	1p
R3	5.6kΩ	1p
R4	1.2kΩ	1p
R5	12kΩ	1p
R6	150Ω	1p
C1	0.01µF	4p
C2	50µF	10p
C3	50µF	10p
Tr1	2N3702	20p
Tr2	BC108	10p
Tr3	BC108	10p
Tr4	BC108	10p
SW1	Pushbutton switch	15p
		<b>95p</b>

No allowance is made for minimum order costs or for postage and packing and these points should be checked carefully before ordering.

## No. 50 ELECTRONIC SIREN

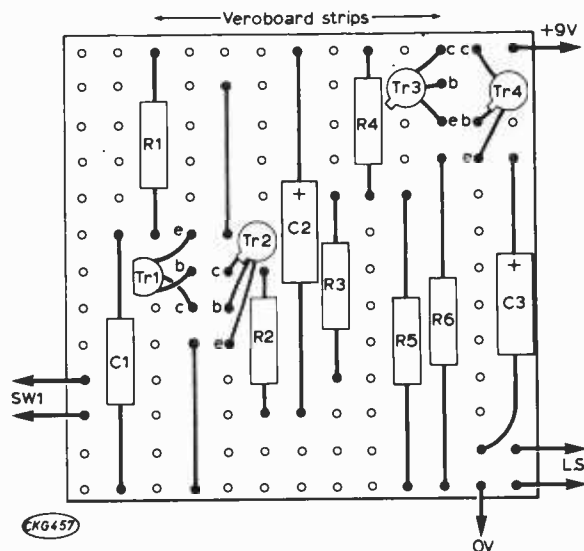

Suggested layout of components on a piece of veroboard.

quency of oscillation is set by the values of R1 and C1 together with the potential at the base of Tr1. In this instance the potential is determined by the network of R2, R3, R4 and R5 and is dependent on whether switch SW1 is open or closed. C2 serves to delay the build up and fall of this potential and gives a smooth change of frequency that gives rise to the siren "wail".

Assuming that SW1 is open and that the potential at Tr1's base is low, C1 will charge up through R1 until the base/emitter junction of Tr1 is forward biased. Not much charge is needed on C1 to arrive at this situation and it occurs very early on in the charging cycle. When Tr1 is turned on regenerative feedback occurs between Tr1 and Tr2 and the charge of C1 is shunted to negative through the circuit of Tr1's emitter and collector and Tr2's base and emitter; at the same time the collector of Tr2 is pulled down towards negative. Eventually base current into Tr1 ceases to flow and C1 is free to re-charge through R1 to repeat the cycle; the potential at Tr1's base returns to its original state. If this potential was higher it would take more time for C1 to reach a charge whereby the emitter of Tr1 became more positive than the base and thus the frequency of oscillation is reduced. By closing SW1 we force the potential to increase but this does not happen immediately and the rise is slowed up by the time constant given by C2. The frequency of oscillation reduces slowly to a minimum value set by the potential divider effect of R4 with R5. When the switch is opened the potential reduces slowly as the charge on C2 is bled to negative by the momentary spikes of current drawn by Tr2 through R2. While this happens the frequency of oscillation slowly increases.

—continued on page 261



Dear Sir,



## Shoreham Transmitters

I was interested to read Mr. Woodward's letter in your March issue. He complains that our transmitters at Shoreham "cause countless harmonics all the way down the medium wave band". The frequencies used at Shoreham are 692kHz (Radio 4), 1214kHz (Radio 1), and 1484kHz (Radio Brighton).

It is true that after the extensive wavelength changes last September a number of inter-modulation products were identified but the situation was quickly rectified. **G. H. Sturge** (*BBC Engineering Information Dept.*)

## Noises

... The fact remains that several miles from the transmitters, noises identifiable as Radio 1 can be heard loud and clear on 266 metres, 232 metres, and also on 1100 metres long wave on receivers ranging from small transistor radios to powerful communications receivers. The strength of these signals varies from day to day, and on some occasions I have heard Radio 1 very weak on 247 metres, and very strong on 323 metres.

In addition, Radio Brighton is always clearly audible on approximately 530 and 560 metres medium wave, as well as the intentional 202 metre wavelength.

My complaints have also been supported by the Horsham-based Southern Independent Radio Association, and the Brighton-based Southern Free Radio Campaign, both of which are responsible organisations, who are trying to improve the standards of broadcasting in this country.

Regarding the possibilities of covering the whole country on medium wave with a few kilowatts, the BBC should try using horizontal long-wire aerials instead of vertical masts. Using this method, the Independent Broadcasting Authority's test broadcasts on 539 metres medium wave cover large parts of the country, with a power of one kilowatt, despite the fact that a powerful Dutch pirate station is on 538 metres, directly underneath.

The IBA's transmitter is also audible in parts of Holland, over the aforementioned Dutch station. I also know for a fact that many on-shore pirate radio stations, notably Radio Jackie of London and Focus 240 of Worthing cover distances of as much as 30 miles, with the "massive" transmitter power of 7 watts! They also use efficient, long-wire aerials. **P. Woodward** (*Lancing, Sussex*).

## Corrective Action

... Following Mr. Woodward's further letter, we have carried out some further checks and measurements in the Brighton area. We found two spurious signals spaced about 80kHz above and below the frequency of Radio 1 (1214kHz). These signals were intermittent and of comparatively recent origin, and they were only present when a certain combination of equipment was in use at Shoreham. The necessary corrective action has now been taken, and we are grateful to Mr. Woodward

for drawing our attention to these signals.

We did not find any trace of a transmission of Radio 1 on Long Waves, or of Radio Brighton on 530 or 560 metres. But it may be worth pointing out that with a receiver i.f. of 'around 465kHz, the 'image' appears at approximately the frequencies mentioned, because

$$1484 - (2 \times 465) = 554\text{kHz} \\ (\text{i.e. } 542 \text{ metres})$$

$$1214 - (2 \times 465) = 284\text{kHz} \\ (\text{i.e. } 1058 \text{ metres}).$$

Such 'signals' are of course entirely the product of the super-het receiver, and do not exist as transmissions at all.

There is no point in going into great detail about the problems of medium-wave transmitting aerial design here, which are many and complex. I am afraid that the horizontal long-wire aerial which Mr. Woodward suggests is not suitable for serving very large areas by day and by night.

The IBA test transmissions are not made from such an aerial, and their relatively large coverage is due mainly to the high earth-conductivity of the area adjacent to the River Thames. Nevertheless the station does not serve large areas of the country nor is it intended to do so.

We understand that recordings made in Holland reveal the IBA signal as only just detectable in the presence of the pirate. It should also be remembered that there is a limit to the degree to which the service area of a station can be enlarged by increasing the power or using a different type of aerial, and the power necessary to serve a given area depends on very many factors, not the least of which is the level of interfering signals which must be overridden. **G. H. Sturge** (*BBC Engineering Information Dept.*)

## TAKE 20—Electronic Siren

—continued from page 260

### Operation

On initial switch-on it is possible to get no immediate high frequency oscillation and this problem can be overcome by temporarily shorting out R3 and when the audible tone is heard the shorting link can be removed. Varying the potential divider effect of R4 and R5 will set the minimum lowest frequency. The highest frequency, before complete cut off, is best set by C1. R1 could be adjusted to vary the range of frequency but this is undesirable

as it affects the working points of the two transistors.

The output is taken from the junction of R1 with C1 and this is a very high impedance point and if too much current is drawn by an external circuit C1 may never reach a charge at which regenerative triggering can occur. Hence the need for a reasonably high input impedance to the amplifier stage. The output waveform is a sawtooth and its amplitude decreases as the frequency increases which is quite effective in compensating for poor low frequency response of small loudspeakers.

The estimated cost to build this project is 95p, plus cost of the speaker, Veroboard, and VAT. ■

# HOTLINES

ON RECENT DEVELOPMENTS

**C**OMPUTERS are steadily becoming increasingly involved in our lives. Latest event to highlight this was the official opening of America's first computer-controlled petrol station which also boasts on-line credit checks. The motorist can pay cash or offer a credit card; the mini-computer will accept either. However, just like its human counterpart, man, the computer is happy to accept cash but wary of the credit card. When such a card is offered the computer will immediately check and verify it with the central computer files held in Atlanta. The petrol station is in the suburbs of Los Angeles. If the credit card offered to the computer is out of date, or has been stolen, then the computer will simply "pocket" the card and will refuse to return it. Now there's something you'd scarcely credit.

## ONE STEP AHEAD

A quick note to exponents of ESP (extra sensory perception). There is to be an International conference on "Electrical Signals from the Brain". It is to be held at Oxford University, August 28—30, 1973. Anyone got any brain waves?

## DEAF-BLIND HELP

In Hanover, there is a Centre for deaf-blind people. How do such unfortunate humans communicate? Feel or touch is an obvious answer. They can, for example, read Braille by feeling the raised dot impressions which make up the Braille alphabet. They cannot, of course, either see or hear television nor can they hear or answer a telephone call.

An ingenious system has been installed at the Hanover Centre which enables deaf-blind people to communicate directly with each other, over great distances—theoretically, anywhere in the world. Key to this system is the Braillomat. This machine produces a strip of paper with Braille alphabet letters or dot characters raised on it. Thus the deaf-blind person has only to run the strip of paper through his/her fingers to "read" the message. The Braillomat has a keyboard rather like a typewriter, but it is extremely simple in that it has only six keys—one key for each of the dots in the Braille alphabet pattern. The idea is that by connecting two of these machines together, two deaf-blind persons can "chat" happily. The tape output, incidentally, is rather like teletype or teleprinter tape.

It doesn't take too much imagination to see the potential here. Each deaf-blind person with a Braillomat could

contact other deaf-blind people by using the machines in conjunction with the telephone. But wait; how will they hear the telephone ring? In practice they don't have to because the inventors have thought of this problem. Their answer is a tiny unit which is carried on the person—rather like a radio paging bleeper. Instead of emitting a warning bleep when the telephone rings, the unit simply vibrates. What a wonderful application of electronics this is.

## THE "R.O.M."

Big international exhibitions are heavy going but often there are one or two very interesting items which crop up. At this year's Mesucora exhibition in Paris, one company exhibited a digital multimeter which incorporated a digital thermometer. Thus, in addition to the usual multimeter capability of measuring voltage, current and resistance, it offered the measurement of temperature also.

Unfortunately, as temperature rises, the transducer or sensor gives an output which does not follow a linear law and therefore cannot "change" degrees C directly into digital reading.

The solution used was to employ a ROM (read-only memory). This memory can be programmed to take certain correcting actions. For example; if the sensor was measuring 500°C and this, when fed directly to the digital display gave a reading of, say, 537, then the ROM could be programmed to compensate for this. Whenever a 500°C signal came in, the ROM would alter things by subtracting 37 from the answer before it was displayed.

Again, perhaps 600°C might read (fed direct) 671 and thus the ROM's programme would tell it, "If 600 in, subtract 71 to give 600 display". Thus the whole programme takes account of any input and processes it so that the "correct" temperature reading is shown digitally.

## INTEREST IN "ERNIE"

In the May article, the story about "ERNIE" might have implied that the name was derived from Ernie Harrison and possibly that Racal Electronics were connected with the Premium Bond selection equipment. We would like to record that the electronic equipment was developed by Plessey and that ERNIE is derived from Electronic Random Number Indicating Equipment, the original version being developed at the Post

Office Research Station, Dollis Hill, London. Mr. Harrison is Chairman of the Southern Region Industrial Savings Committee; Racal are not directly connected with ERNIE.

## FLAT-SCREEN TV

Last month I reported thin readout devices and suggested flat screen television. I have just come across a flat-screen cathode ray tube (c.r.t.) or, to be more precise, two inches deep. Its function (at present) is to display alpha numeric characters/messages and it does not use either electron guns or deflection plates. It is digitally addressed and the display forms 512 characters in a 5 × 7 matrix of dots. The screen measures 5.4 × 3.8 inches. It has an area cathode which emits a sort of blanket of electrons as opposed to the narrow beam normally associated with the more conventional (and very much longer) c.r.t.

Beam forming is achieved by a plate with some 20,000 holes in it. This "forms" the electron blanket into individual beams. These beams then have to pass through four plates each similar to the beam forming one. These plates are the switching mechanism by which characters are formed. The first two plates (of the four) determine the position of the characters on the screen while the remaining two determine the column and row.

A 75V positive potential will accelerate electrons through the holes in the switching plates, while a 50V negative potential will cut off the beam completely.

After travelling through the switching plates the electron beam(s) now pass through a final plate used for focusing. They then strike the phosphor screen thus creating an illuminated image. The very small thickness of this unique c.r.t. (2in.) has numerous obvious advantages.

Other advantages are also present which may not, at first sight, seem quite so obvious. Because the electron beam has such a very short distance to travel, the display is virtually immune to magnetic interference.

**Note:** This display, although it has been exhibited and is not an industrial secret, is not yet on the market although its appearance is believed to be imminent.

Ginsberg

# WEYRAD

## COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil .....	P50/1AC (For OC45)	P50/1AC (For AF117)	33p	Plus 10% V.A.T.
1st I.F. Transformer .....	P50/2CC (For OC45)	P51/1 (For AF117)	36p	
2nd I.F. Transformer .....	P50/2CC (For OC45)	P51/2 (For AF117)	36p	
3rd I.F. Transformer .....	P50/3CC (For OC45)	P50/3V (For AF117)	36p	
Rod Aerial .....	RA2W .....	72p		Plus 10% V.A.T.
Driver Transformer .....	LFDT4/1 .....	58p		
Output Transformer .....	OPT1 .....	58p		
Printed Circuit .....	PCA1 .....	58p		

## I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer .....	39p	Plus 10% V.A.T.
T41/2E	2nd I.F. Transformer .....	39p	
T41/3T	3rd I.F. Transformer .....	57p	
T41/3T	B.F.O. Coil .....	57p	

Details of these and our other components are given in an illustrated folder which will be supplied on request with postage please.

**WEYRAD (ELECTRONICS) LIMITED**  
SCHOOL STREET, WEYMOUTH, DORSET

## Ever had Component Problems?



1. Problems of choosing your components?
2. Problems of getting them quickly?
3. Problems of locating a supplier?



**CHEER UP!**

**HOME RADIO (COMPONENTS) LTD**  
have created a catalogue and an organisation that between them solve your problems simply & economically

**PUT US TO THE TEST**

FIRST YOU'LL NEED THE CATALOGUE.  
SEND COUPON with 77p CHEQUE or P.O.

The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

Please write your Name and Address in block capitals

Name \_\_\_\_\_

Address \_\_\_\_\_



HOME RADIO (Components) LTD. Regd. No. 912966 London  
Dept. PW, 234-240 London Road, Mitcham CR4 3HD

# NEVER AGAIN

AFTER MR. RISING PRICE EMERGES FROM THE 'FRIDGE, WILL OPPORTUNITIES LIKE THIS RECUR!!

PARTRIDGE PACKAGE PRICES ARE ACTUALLY LOWER THAN THE PRE-VAT PRICES OF THE ITEMS PURCHASED SEPARATELY. BUY A COMPLETE RECEIVING STATION FOR £66.55.

The Space Age WORLD RECORD award winning 7' 6" long All Band JOYSTICK VFA Antenna — JOYMATCH A.T.U. — TRIO RECEIVER or TRANSCIEVER — Matching HEADPHONES — A COMPLETE STATION IN ONE COMPACT PACKAGE — THE FLAT DWELLER'S DREAM I

JOYSTICK VFA £12.54 (A); JOYMATCH ATU 111 ★ or 111A £12.54 (B); JOYMATCH ATU LO-Z500 £18.10 (C).

## COMMUNICATIONS HEADPHONES £2.86 (D)

(All including V.A.T., carriage, packing, accessories & insurance.)

**PARTRIDGE PACKAGE No. 1**  
 9R59DS receiver ... .. £54.45  
 • Items (A); (B); (D) above .. £12.10  
 Complete Gen. Coverage Station .. .. £66.55

**PARTRIDGE PACKAGE No. 3**  
 9R599 receiver ... .. £293.50  
 • Items (A); (B); (D) above .. FREE  
 Complete Amateur RX Station £293.50

**PARTRIDGE PACKAGE No. 2**  
 JR310 receiver ... .. £27.50  
 • Items (A); (B); (D) above .. £7.70  
 Complete Amateur RX Station £30.20

**PARTRIDGE PACKAGE No. 4**  
 TS/PS515 Transceiver 180W £231.00  
 • Items (A); (B); (D) above .. FREE  
 Complete TX-RX Station .. £231.00

### BARCLAYCARD — ACCESS I

ALSO: SP5D SPKR. £4.95; OA2 MAINS STABILISER 74p.

**NEW:** World-wide reception on the amazing "DX—CRYSTAL SET" £2.20 including unique aerial.

## PARTRIDGE BUDGET LINE—

ARTIFICIAL EARTH—SOLVES YOUR EARTH PROBLEMS £5.28; AERIAL BANDSWITCH—TUNED AERIAL £5.28; A.T.U. KIT—FULL COVERAGE TX/RECEIVER £5.28; ASSEMBLED £6.38.

**NEW:** Instrument Cases, easily drilled in strong black rigid polystyrene. 5-7/8" x 3-1/2" x 2-1/2" only 20p.

(All including, V.A.T., carriage, packing, accessories & insurance.) Send 3p stamp for full illustrated details of Partridge Products. TIO brochures (state which) 3p stamp extra.

NO V.A.T. ON OVERSEAS ORDERS!

CARRIAGE & INSURANCE EXTRA OVERSEAS.

**BOX 5**  
**PARTRIDGE ELECTRONICS LTD.**  
**BROADSTAIRS, KENT**

Phone: 0843 62535 or 62839 cheap periods.

## P. C. BOARDS



Reverberation Unit PCB.

## FOR P.W. PROJECTS

All PCB's Fibreglass, Drilled, Roller-Tinned  
 Circuit and Layout Diagrams free with each PCB

**REVERBERATION UNIT (Nov/Dec 1972)**  
 PCB (2in x 1 1/4in). Specially designed to also hold Slider Pots with spacing compatible with published front panel £1.20  
 SET or R's, C's, S/C's, Slider Pots, Transformer £6.80

**8 WATT AMPLIFIER (Nov 1972)**  
 PCB (Mono—2 1/4in x 3in) 60p  
 R's, C's, Semiconductors: Stereo Set £7.70, Mono Set £3.90

**PRE-AMPLIFIER (Nov 1972)**  
 PCB (Stereo—3 1/4in x 7 1/4in) Specially designed to also hold all Pots, either rotary or slider, plus Selector Switch £1.50  
 R's, C's, Rotary Pots, Selector Switch, Semiconductors:  
 Stereo Set £5.20, Mono Set £2.50

**LOUDHAILER & SIREN (Dec 1972)—PRE-AMP & SIREN GENERATOR**  
 Set of R's, C's, Pot, Semiconductors PCB (2 1/4in x 2 1/4in) £2.20

**VIBRASONIC GUITAR PRE-AMP (Sept 1970)**  
 PCB (4in x 1 3/4in) for Mic Pre-Amp, 2-Guitar Pre-amp, Tremulant & Tone Controls, Master Volume. Specially designed to also hold Rotary or Slider Pots £2.30  
 Set of S/C's, R's, C's, Rotary Pots, LDR, Lamp, Coupling Transformer £7.75 Power Supply £2.80

**DIGITRONIC DIGITAL CLOCK (Mar 1973)**

PCB (1 1/2in x 3 1/4in) for 6-digit read-out 60p  
 POSTAGE: U.K. 10p any order. OVERSEAS at cost.

P.E. DESIGNS ALSO AVAILABLE—S.A.E. FOR FREE LIST.

V.A.T.: ADD 10% TO ALL U.K. ORDERS

## PHONOSONICS

DEPT. PW7, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW  
 MAIL ORDER ONLY

## FERRANTI Radio i.c. ZN414 only £1.32 WITH FREE DATA

BF869 15p	ZTX300 12p	ZTX502 17p	Z8178 55p
BF860 20p	ZTX301 12p	ZTX508 14p	Z8270 11p
BF861 15p	ZTX302 17p	ZTX604 45p	Z8271 11p
BF866 15p	ZTX303 14p	ZTX630 21p	Z8272 15p
BF867 25p	ZTX304 21p	Z8142 38p	Z8274 18p
BF868 20p	ZTX310 9p	Z8170 10p	Z8276 20p
ZTX107 8p	ZTX380 18p	Z8171 13p	Z8278 55p
ZTX108 8p	ZTX384 15p	Z8172 15p	* Zeners *
ZTX109 11p	ZTX500 12p	Z8174 17p	KSO80A to
ZTX214 15p	ZTX601 18p	Z8176 25p	K8180A 10p

All devices top grade, brand new, fully guaranteed. We specialize in Ferranti semiconductors and can supply any device. Postage & Packing 10p. Free over £2. Send S.A.E. for full list and data. All prices include V.A.T.

### DAVIAN ELECTRONICS

PO BOX 38, OLDHAM, LANCs. OL2 6XJ

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots / removable space dividers. Build up any size cabinet for wall, bench or table top.

**INTER-LOCKING PLASTIC STORAGE DRAWERS**

NEAT! HANDY! TIDY!

**DISCOUNT PRICES**

SINGLE UNITS (5" x 2 1/2" x 2 1/2") £1.25 Dozen  
 DOUBLE UNITS £2.15 Dozen  
 TREBLE (3D) £2.20 for 8

DOUBLE TREBLE 2 drawers in one outer case (6D2) £3.25  
 for 8 extra large size (6D1) £3.10 for 8, Carriage 35p Orders over £10 post free

**QUANTITY DISCOUNTS!** 5% in £1 for orders over £6, 7 1/2% over £10, 10% over £20. Quotation for large quantities.

**PLEASE ADD 10% VAT TO TOTAL REMITTANCE.**

**IVORYET LIMITED** (Dept. PW7), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

5 SIZES ALL INTERLOCK



# TRICOLOUR

## Mood Lighting System

PART FOUR

JUREK BUDEK\*



—continued from the June issue

As the load increases, the suppression of radio frequency interference becomes more difficult. Many sophisticated and very effective circuits have been published and are on the market, but very often they are prohibitive to the normal user because of their high cost.

The suppression filter used in this article is very simple, inexpensive and quite effective. It is suitable for total loads up to 900 watts, and consists of one bifilar wound ferrite core filter choke and 0.1μF capacitor as shown in Fig. 23.

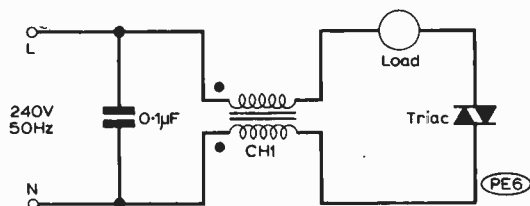


Fig. 23: The suppression circuit used in the mains input supply to the lamp dimming control unit.

The normal symmetrical currents generate magnetic fields which are self cancelling. However, symmetrical currents, caused by radio frequency interference are attenuated.

### Assembly

Pay attention to the correct polarity of capacitors, diodes, transistors and triacs. Mount the pulse transformer in correct way, i.e. to avoid sideways fixing.

The three core mains lead enters at the rear of the chassis (Fig. 20, page 54, May issue) and is connected to the junction terminal block.

Thereafter, the connections to the junction terminal block are as indicated in the printed circuit board wiring layout diagrams in this issue. It is pointed out that the mains 'earth' lead (E terminal) should preferably be taken directly to the control unit chassis. In Fig. 20 (May issue) this was shown soldered to the 'earth' side of the printed circuit board layout.

When the printed circuit board is mounted in the chassis metalwork, the 'earthy' side of the foil is connected to the metalwork via the mounting spacers, thus ensuring continuity of the chassis-p.c. foil earth system.

Therefore, the mains earth lead (common) and the earth lead from tag 1 on the lamps output socket SK1 may be conveniently taken to a chassis earth tag which may be mounted under one of the metal bolts that hold socket SK1 in position.

The socket SK1 is wired otherwise as shown in Fig. 20.

The three triacs, CSR3, CSR4 and CSR5, are in all instances bolted directly to the common heat sink

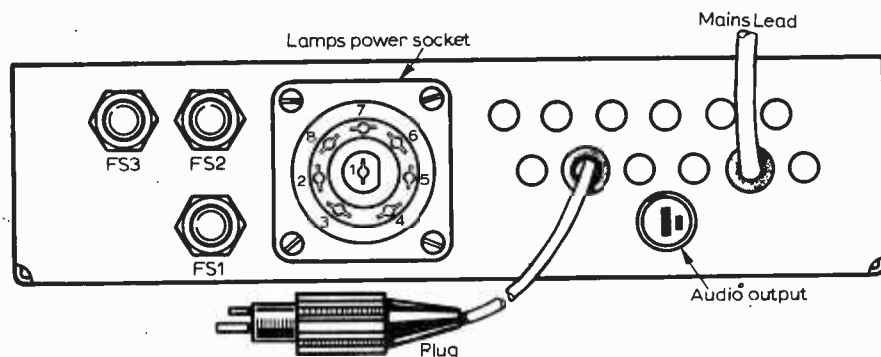


Fig. 24: Rear view of the P.W. Tricolour. The DIN plug and socket are the audio signal feed points—to amplifier output and loudspeaker.

\* Texas Instruments Ltd.



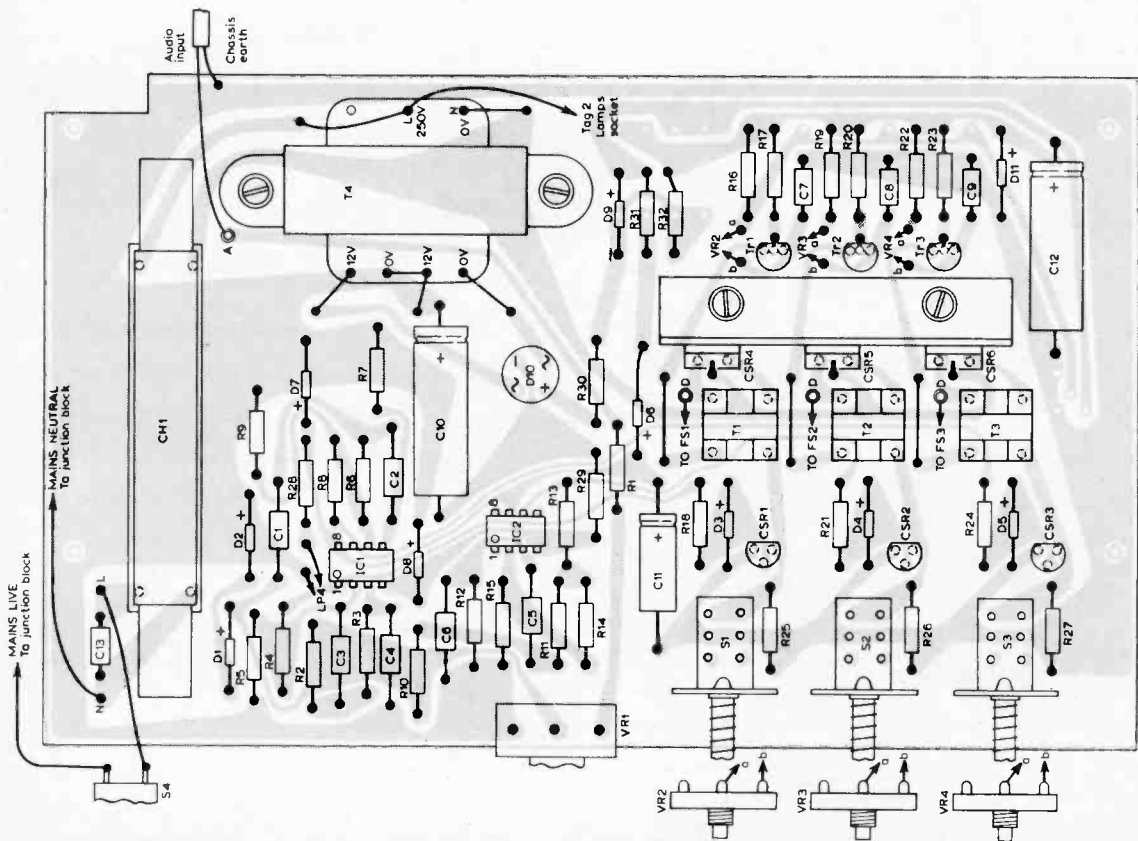


Fig. 25: Component layout for the lamp dimming version of the P.W. Tricolour on the Mk II printed circuit board. Refer to the April and June 73 issues for component details.

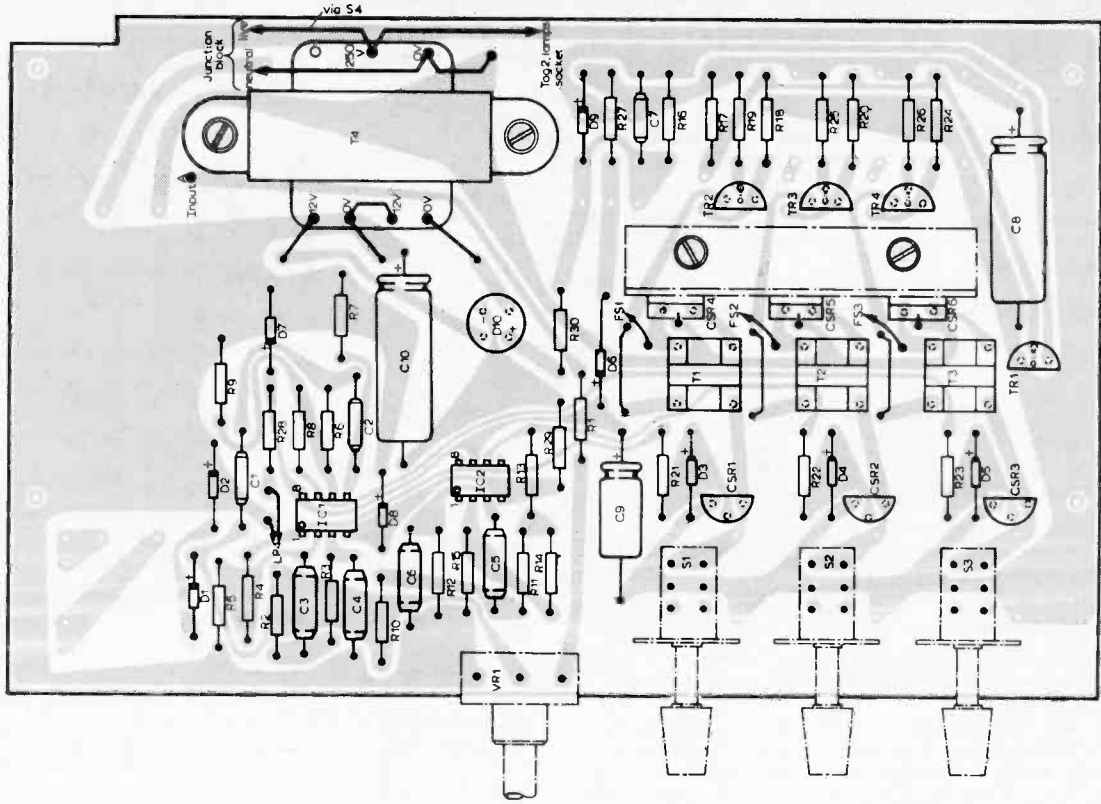


Fig. 26: Component layout for the zero voltage version of the P.W. Tricolour on the Mk II printed circuit board. Refer to the April 73 issue for component details.

# Build yourself a TRANSISTOR RADIO

## ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

**£9.35**

P. P. & Ins. 52p

Overseas P. & P. £1.05)



## ROAMER EIGHT Mk I


NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£7.68** P. P. & (Overseas P. & P. £1.05) Ins. 47p.


## ROAMER SEVEN MK IV

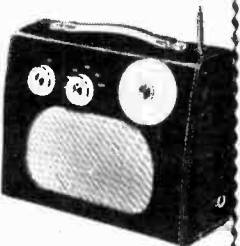

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

Total building costs **£6.58** P. P. & (Overseas P. & P. £1.05) Ins. 47p.

## ROAMER SIX

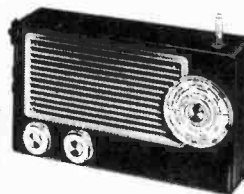

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 Trawler band plus an extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Easy build plans and parts price list 25p (FREE with parts).

Total building costs **£4.38** P. P. & (Overseas P. & P. £1.05) Ins. 31p


## POCKET FIVE



3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5½ x 1½ x 3½in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2.50** P. P. & (Overseas P. & P. 65p) Ins. 24p

## TRANSONA FIVE

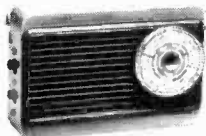


5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2.75** P. P. & (Overseas P. & P. 65p) Ins. 25p

## TRANS EIGHT

8 TRANSISTORS and 3 DIODES

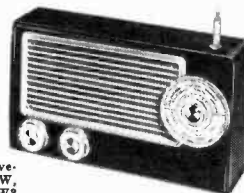

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

Total building costs **£4.95** P. P. & (Overseas P. & P. £1.05) Ins. 33p

## NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three ¼" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

Parts price list and easy build plans 25p (FREE with parts).

All parts including **£6.05** P. P. & Case and Plans Ins. 33p

(Overseas P. & P. £1.05)

FULL AFTER SALES SERVICE

\* Callers side entrance "Lavelle's" Shop  
\* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

PLEASE NOTE: ALL PRICES NOW INCLUDE VAT

## RADIO EXCHANGE CO

61a HIGH ST., BEDFORD, MK40 1SA. Tel. 0234 52367  
Reg. no. 788372

I enclose £..... please send items marked.

ROAMER TEN  ROAMER SEVEN   
ROAMER EIGHT  TRANS EIGHT   
TRANSONA FIVE  ROAMER SIX   
POCKET FIVE  EDU-KIT

Parts price list and plans for

Name .....

Address .....

PW54

VALVES		All prices in pounds and new pence																						
1A7GT	45	6BA6	25	6J6	20	7C5	11-13	12R7	40	37	40	DAF91	30	EBL31	11-50	EL34	50	N78	11-50	PL500	30	U403	60	
1D5	50	6BE6	30	6J7M	45	7C6	75	14H7	50	42	DAF96	45	EC90	33	EL41	60	N108	11-50	PL504	50	U404	60		
1H5	50	6BH6	75	6J7G	30	7D5	60	19AQ5	50	50B5	50	DCC90	11-35	EC81	35	EL42	65	O2	38	PL508	50	U901	11-18	
1NSGT	55	6BJ6	45	6J7GT	45	7H7	50	30D1	50	50C5	50	DCC30	55	EC82	30	EL84	25	OC3	38	PL509	11-60	UACB80	40	
1R5	55	6BR7	80	6K7M	35	7S7	22-25	20L1	11-10	50L6GT	55	DF70	45	EC83	30	EL93	35	OZ4	40	PL802	95	UAF24	55	
1R4	40	6BR9	70	6K7G	35	7Y4	65	20P4	11-10	75	DF92	20	EC84	30	EL99	45	PC86	60	PX4	22-50	UBC41	60		
1R5	50	6BWA	85	6K8M	60	10C2	35	20P5	11-20	78	DF96	45	EC85	40	EM80	45	PC88	60	PX25	22-50	UBC81	40		
1T4	30	6BW7	80	6K8G	40	10F1	75	25L6GT	50	85A2	50	DH77	35	EC88	40	EM81	60	PC97	50	PY33	63	UBF80	40	
3A4	30	6C4	33	6K8GT	50	10F3	60	25Y5	65	180B2	60	DK32	45	EC89	35	EM84	35	PC84	40	PY81	30	UBF89	35	
3A4	30	6C5G	35	6L6GT	50	10F9	60	25Z5	60	180C4	60	DK92	45	EC92	40	EM88	40	PC89	50	PY82	35	UBF84	45	
3Q4	40	6C6	45	6L6	50	10F18	50	25Z5GT	55	801	60	DK99	55	EC81	30	EZ35	40	PC8189	60	PY500	11-00	UCF80	55	
3Q5	50	6CD6G	11-25	6L18	45	10L11	65	25Z6	65	807	60	DK99	55	EC83	45	EZ40	50	PCF82	35	PY800	40	UCF42	70	
3B4	50	6CH6	60	6Q7G	40	10L13	60	30C1	30	813UBA	11-35	DL92	35	EC80	45	EZ41	50	PCF84	60	PY801	50	UCB81	40	
3V4	35	6CW4	65	6Q7GT	43	11E3	11-00	30C15	80	866A	75	DL93	40	EC83	70	EZ81	29	PCF801	60	R19	50	UCB82	35	
5R4GY	75	6E5	11-00	68A7M	40	12A76	30	30C17	90	94	DL94	48	EL86	40	EZ82	29	GY501	80	PCF802	50	S130	11-75	UF41	60
5V4G	35	6F1	70	68GT	40	12A75	35	30C18	90	1625	55	EL87	50	EZ83	30	H300	80	PCF805	60	SP4	50	UF81	60	
5V4G	45	6F8G	90	68H7M	40	12A77	30	30FL1	75	5783	30	EL88	45	G230	40	H309	45	PCF806	70	SP41	11-00	UL41	65	
5Y3GT	40	6F6G	35	68J7GT	30	12A78	30	30FL12	11-20	7193	30	EL89	45	G232	48	H309	45	PCF807	80	SP42	11-00	UL42	65	
5Z4G	40	6F8G	50	68K7GT	30	12A79	30	30FL14	85	7475	50	EL90	45	G234	60	H309	45	PCF808	85	SP61	75	UL84	40	
6J30L2	60	6F11	40	68L7GT	35	12B26	40	30L15	85	A61	48	E88CC	65	E41	65	K761	11-75	PCL84	45	SU25	11-00	UY21	50	
6A7	75	6F13	45	68N7GT	35	12B8GT	35	30L17	80	ATP4	45	E90	20	E45	25	K762	11-75	PCL85	40	SU210	75	UY41	48	
6A8G	40	6F14	70	68Q7GT	40	12E1	23-00	30P4	11-12	ATP5	60	EAB30	35	E49	25	K763	11-75	PCL86	45	T41	11-00	UX85	40	
6AK5	35	6F23	85	6I4GT	65	12J5GT	20	30P12	80	ATP7	60	EAF42	55	E49	25	K764	11-75	PCL86	45	T41	11-00	UX85	40	
6AM3	35	6F25	11-00	6I6GT	11-00	12J7GT	50	30P19	85	AU2	44-00	EB91	20	E49	25	K765	11-75	PCL86	45	T41	11-00	UX85	40	
6AM6	33	6F28	65	6V6G	30	12K7GT	40	30PL1	75	AU5	75	EB33	50	E49	25	K766	11-75	PCL86	45	T41	11-00	UX85	40	
6A05	38	6F32	25	6V6GT	40	12Q7GT	40	30PL14	90	AZ31	56	EB34	45	E49	25	K767	11-75	PCL86	45	T41	11-00	UX85	40	
6A87G	85	6G6	35	6X4	35	12K8GT	50	30PL13	93	AZ1	55	EB34	45	E49	25	K768	11-75	PCL86	45	T41	11-00	UX85	40	
6A76	35	6H6	23	6X5GT	40	12R27	35	35L5	70	CC135	60	EB38	40	E49	25	K769	11-75	PCL86	45	T41	11-00	UX85	40	
6A76	35	6J5M	50	6X5GT	40	12R27	35	35L5	70	CC135	60	EB38	40	E49	25	K769	11-75	PCL86	45	T41	11-00	UX85	40	
6B4G	11-00	6J5GT	30	7B6	70	12R37	50	35Z3	70	CY30	45	EBF89	30	E49	25	K769	11-75	PCL86	45	T41	11-00	UX85	40	
6B8G	25	6J6GT	30	7B7	50	12R37	50	35Z5	70	CY31	45	EBL1	11-00	E49	25	K769	11-75	PCL86	45	T41	11-00	UX85	40	
												EBL21	60	E49	25	K769	11-75	PCL86	45	T41	11-00	UX85	40	

Transistors		Integrated Circuits																			
1N914	07	AC128	20	BY100	15	NKT713	25	OC44	17	7430	20	7474	40	74100	22-50	74157	11-80				
1B113	25	AC129	20	BZ768	15	OA70	10	OC45	12	7432	42	7475	55	74107	50	74170	11-80				
1B202	22	AC130	20	CR1-40	17	OA71	10	OC87	60	7433	70	7476	45	74110	80	74174	22-00				
2N302	22	AC131	20	DD003	15	OA81	08	OC88	60	7437	65	7480	40	74111	11-45	74175	11-80				
2N302	22	AC132	20	GET102	30	OA85	12	OC89	65	7438	65	7482	87	74118	11-00	74176	11-80				
2N404	20	AC133	20	GET7882	25	OA91	07	OC71	12	7440	23	7483	51	74119	11-90	74180	11-95				
2N697	15	AC134	20	AE115	25	OA211	30	OC72	20	7441	22	7484	90	74121	60	74191	11-95				
2N706	10	AC135	20	KJ100A	20	OA2201	50	OC81	10	7442	75	7486	45	74122	11-35	74192	11-90				
2N1132	25	AC136	20	MJE250	27	OA2207	47	OC81D	20	7443	30	7487	70	74123	11-35	74193	11-90				
2N1305	22	AC137	20	MJE250	27	OA2210	35	OC82	25	7444	30	7487	70	74124	11-35	74194	11-90				
2N2147	75	AC138	20	MJE3055	87	OA2224	45	OC82D	20	7445	30	7487	70	74125	11-35	74195	11-85				
2N2160	60	AC139	20	NKT212	27	OA2241	25	OC70	25	7446	48	7487	70	74126	11-35	74196	11-85				
2N2218	20	AC140	20	NKT214	15	OA2242	23	OC71	30	7447	30	7487	70	74127	11-35	74197	11-90				
										7448	48	7487	70	74128	11-35	74198	11-80				
										7449	45	7487	70	74129	11-35	74199	11-80				
										7450	45	7487	70	74130	11-35	74200	11-80				
										7451	30	7487	70	74131	11-35	74201	11-80				
										7452	30	7487	70	74132	11-35	74202	11-80				
										7453	30	7487	70	74133	11-35	74203	11-80				
										7454	30	7487	70	74134	11-35	74204	11-80				
										7455	30	7487	70	74135	11-35	74205	11-80				
										7456	30	7487	70	74136	11-35	74206	11-80				
										7457	30	7487	70	74137	11-35	74207	11-80				
										7458	30	7487	70	74138	11-35	74208	11-80				
										7459	30	7487	70	74139	11-35	74209	11-80				
										7460	30	7487	70	74140	11-35	74210	11-80				
										7461	30	7487	70	74141	11-35	74211	11-80				
										7462	30	7487	70	74142	11-35	74212	11-80				
										7463	30	7487	70	74143	11-35	74213	11-80				
										7464	30	7487	70	74144	11-35	74214	11-80				
										7465	30	7487	70	74145	11-35	74215	11-80				
										7466	30	7487	70	74146	11-35	74216	11-80				
										7467	30	7487	70	74147	11-35	74217	11-80				
										7468	30	7487	70	74148	11-35	74218	11-80				
										7469	30	7487	70	74149	11-35	74219	11-80				
										7470	30	7487	70	74150	11-35	74220	11-80				
										7471	30	7487	70	74151	11-35	74221	11-80				
										7472	30	7487	70	74152	11-35	74222	11-80				
										7473	30	7487	70	74153	11-35	74223	11-80				
										7474	30	7487	70	74154	11-35	74224	11-80				
										7475	30	7487	70	74155	11-35	74225	11-80				

**RST VALVE MAIL ORDER CO.** TELEX 946708 Open to callers 9am-5pm Mon-Sat. From 1st April 1973 all orders sub-  
 16a WELLFIELD ROAD, LONDON SW16 2BS Closed Saturday from 1pm-3pm. ject to V.A.T. at applicable rate.  
 Express postage 1p per transistor, over 10 post free. Integrated Circuits & Valves 5p, plus 1p for each additional item, over £5.00 post free. This must be added to your order including postage.

**TRANSISTORISED** F.M. tuner head with A.M. gang, slow motion drive. 88-108Mc, with circuit diagram. £2.30p.

**PINNACLE LOW NOISE CASSETTES** C60-50p/C90-75p C120-£1.

**P-C BOARDS** (not computer panels)  
 1 off 6 transistors single wave band  
 1 off 4 transistor audio  
 1 off 3 transistor £1.60 the three.

Encapsulated bridge rectifier (lit used 3 3mdh) 100 PIV 2 amps. 50p each, 3 for £1.35.

Transistor F.M. Stereo Multiplex Decoder. Size: 5 1/2 x 2 1/2 x 1 1/2. As used in well known British stereo units with circuit. £3.75.

**GARRARD SP25 MK. II** less Cartridge. £10.00.

**10 VOLUME CONTROLS** consisting of 2 off each.  
 100K log. ganged L/S-20K log. ganged L/S.  
 470K log. D/P Switch-10K lin. L/S-50K lin. L/S. £1.35.

**4 PHONO SOCKETS ON PANEL.** 10 panels for £1.25.

<

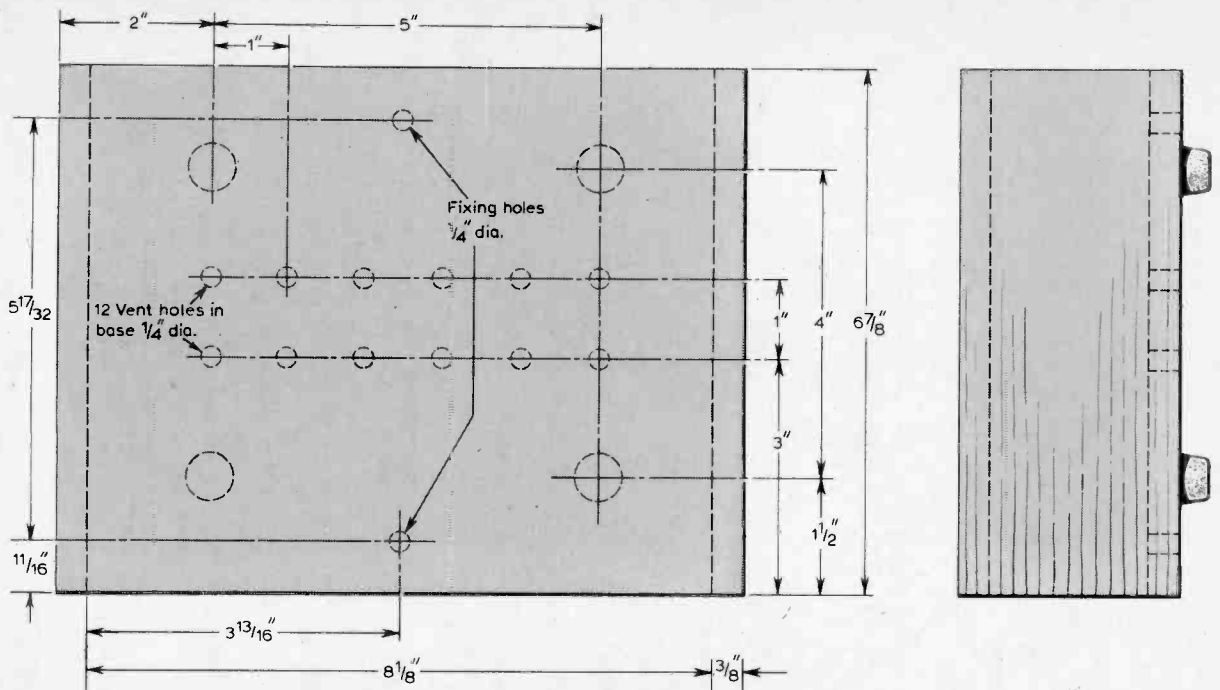


Fig. 27: Cabinet details for the P.W. Tricolour.


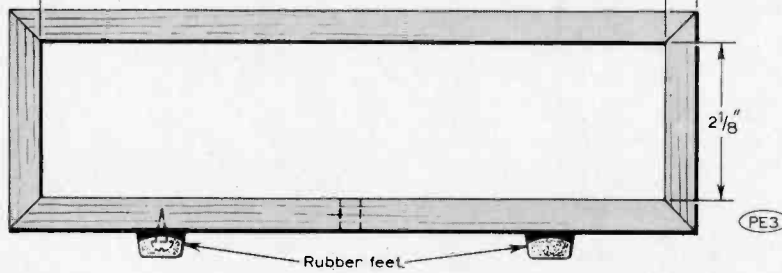
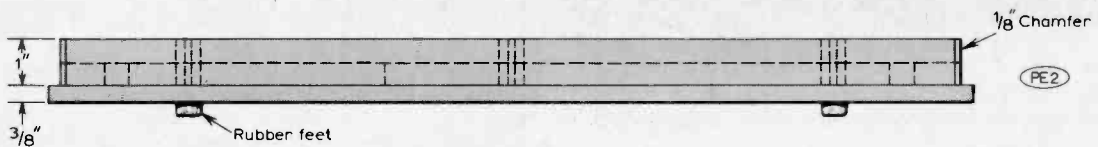


Fig. 28: Details of the base unit for the lamps.

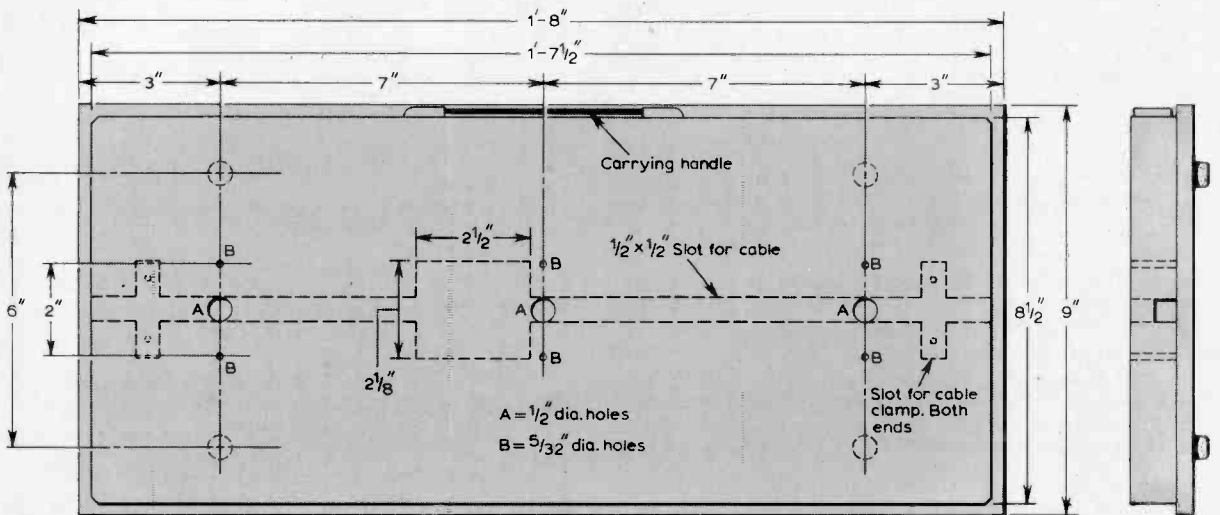

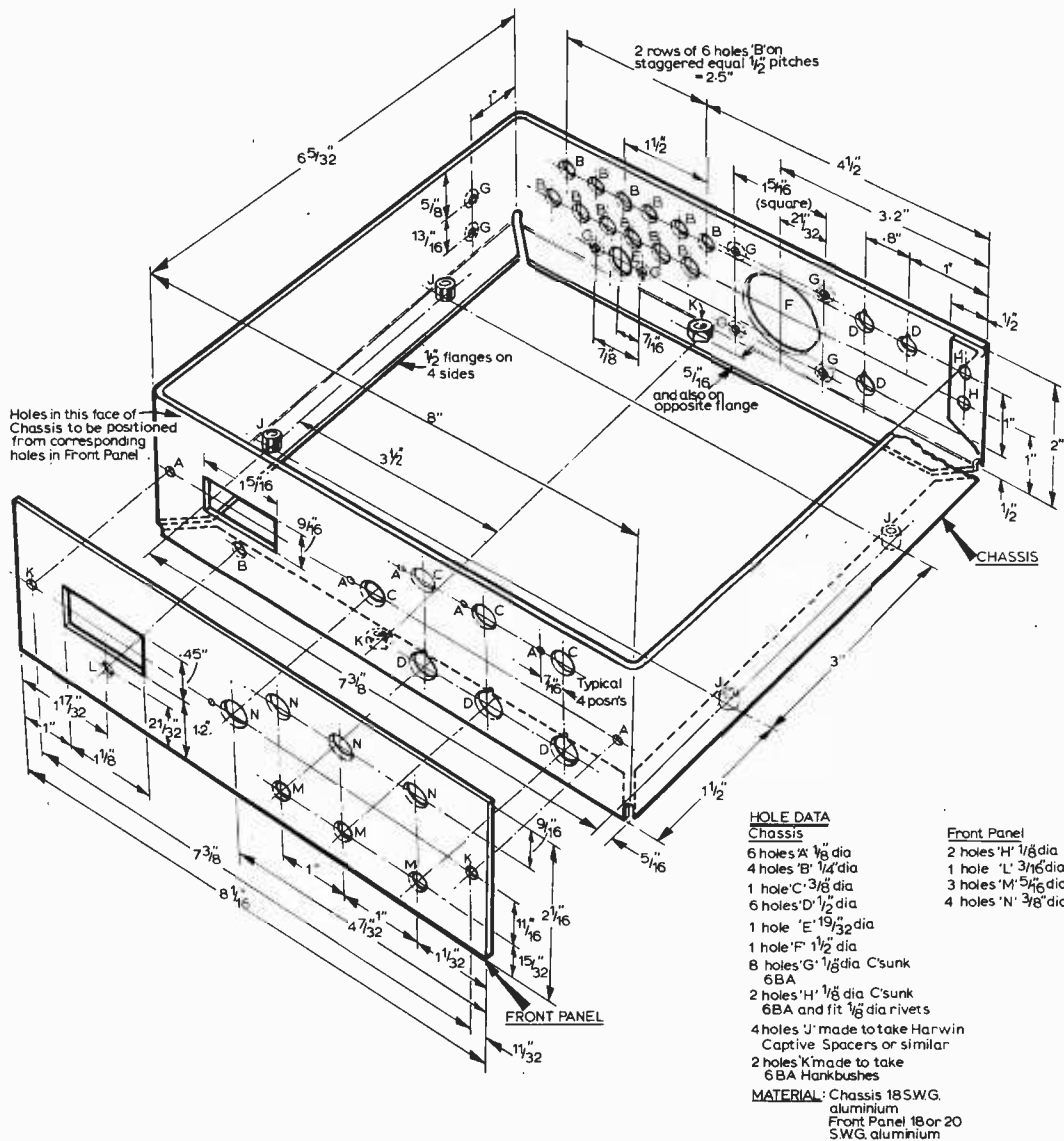


Fig. 29: Front panel and chassis metalwork details for the lamp dimming version. The heat sink is identical to that given in the May issue. Note that the two holes marked 'K' on the front panel should have been given as 'H'.

using 4BAx1/4in. bolts and nuts. No insulating washers are used. The heat sink is held in position on the printed circuit board by 4BAx1/4in. bolts and nuts.

The lamp dimming controls, VR2, VR3 and VR4 are wired as shown in Fig. 25, the left hand tag on each control is unused. These tags should be carefully positioned so that they do not touch or short to adjacent components.

The Bulgin socket (SK1) and plug (PL1) are numbered on their mouldings to conform with Fig. 20.

Having completed the units and checked the lamp wiring to the multiway lamps socket—1-Earth, 2-Common, 4-Bass, 6-Middle and 8-Treble, check if any of the lamps come on, after the supply has been switched on. If so, there may be a component wrongly positioned in the filter circuit or a solder bridging around the triac or thyristor. If no lamp

lights, press on the override switches; the lamps should come on, and if not, change over the lamps, check interconnecting wiring and switching circuits i.e. triac and thyristors.

Finally, play some music. If any of the lamps do not work, check all the components in the relevant filter circuit for dry joints etc.

It should have been pointed out in the captions to Figs 24 and 27 (part 3, last month) that each division of the graphic scale represented 1cm. In the list of components applicable to Fig. 25 the value of R1 (page 184) should have been given as 15kΩ.

It would appear that in some copies of the May issue, one of the I.C. connections (IC1) in Fig. 9 was missing. The missing number is '1'. On the same diagram a figure '13' appears between the middle and treble outputs. This should be ignored.



# TRANSISTORS

1 DOCKYARD, STATION ROAD, OLD HARLOW, ESSEX  
Phone Harlow 37739

P/P 10p. Price list S.A.E. (Saturday callers welcome)

**ALL PRICES INCLUDE VAT**

## 74 Series TTL




1 25		1 25		1 25		1 25	
8N7400	16p	8N7423	55p	8N7450	16p	8N7489	6-05p
8N7401	16p	8N7425	55p	8N7451	16p	8N7490	74p
8N7402	16p	8N7427	49p	8N7453	16p	8N7491	1-10p
8N7403	16p	8N7428	77p	8N7454	16p	8N7492	74p
8N7404	16p	8N7430	16p	8N7460	16p	8N7493	74p
8N7405	16p	8N7432	49p	8N7470	83p	8N7494	58p
8N7406	38p	8N7444	94p	8N7472	33p	8N7495	85p
8N7407	38p	8N7437	72p	8N7473	41p	8N7496	95p
8N7408	20p	8N7438	72p	8N7474	41p	8N74100	1-80p
8N7409	20p	8N7440	16p	8N7475	50p	8N74104	1-08p
8N7410	17p	8N7441	74p	8N7476	44p	8N74105	1-08p
8N7411	27p	8N7442	74p	8N7480	73p	8N74107	44p
8N7412	38p	8N7443	1-43p	8N7481	1-32p	8N74110	61p
8N7413	32p	8N7445	1-43p	8N7482	97p	8N74111	1-37p
8N7414	38p	8N7446	8-00p	8N7483	1-20p	8N74118	1-10p
8N7417	47p	8N7448	1-07p	8N7484	1-10p	8N74119	1-47p
8N7420	16p	8N7447	1-10p	8N7485	8-98p	8N74121	44p
8N7422	55p	8N7448	1-10p	8N7486	30p	8N74122	1-54p

\* Devices may be mixed to qualify for Price Breaks  
\* 100 Plus less 10% off 25 plus break
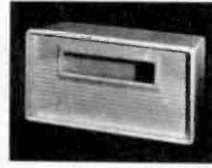
# £19.50 ELECTRONIC DIGITAL CLOCK

(For complete kit of parts including case.)



This 4 digit 24 hour clock is available to readers at this special price. Parts would normally cost over £25. Kit of parts includes twelve IC's, indicators, and a smart white plastic case.

## Electrolytic Capacitors

4 VOLT		16 VOLT		40 VOLT	
47µF	6½p	15µF	6½p	100µF	6½p
100µF	6½p	33µF	6½p	100µF	9p
220µF	6½p	68µF	6½p	150µF	10p
330µF	6½p	150µF	8p	220µF	11p
1000µF	13p	220µF	9p	470µF	11p
4700µF	29p	680µF	17p	680µF	25p
		1000µF	17p	1000µF	25p
		1500µF	25p	2200µF	44p
		2000µF	43p		
6-3 VOLT		25 VOLT		63 VOLT	
33µF	6½p	10µF	6½p	1µF	6½p
68µF	6½p	22µF	6½p	2-2µF	6½p
150µF	6½p	47µF	6½p	4-7µF	6½p
470µF	11p	100µF	8p	6-8µF	6½p
680µF	13p	150µF	8p	10µF	6½p
1500µF	18p	220µF	10p	22µF	6½p
2200µF	18p	470µF	10p	68µF	10p
3300µF	26p	1000µF	10p	100µF	11p
10 VOLT		40 VOLT		100 VOLT	
22µF	6½p	6-8µF	6½p	1µF	6½p
47µF	6½p	15µF	6½p	2-2µF	6½p
100µF	6½p	33µF	6½p	4-7µF	6½p
220µF	8p	68µF	8p	6-8µF	6½p
330µF	10p	100µF	8p	10µF	6½p
470µF	11p	150µF	8p	22µF	6½p
1000µF	11p	220µF	10p	68µF	10p
1500µF	20p	470µF	10p	100µF	11p
2200µF	24p	1000µF	10p	150µF	13p

## BARGAIN PACKS

Unmarked Packs	
Pack of 25 IN4148	55p
51p	
Pack of 10 BC108	55p
BC107 (Plastic can)	55p
Pack of 10 Plastic BC109	55p
Pack of 10 BC168	55p
BC168 (unmarked) but tested	
2N2646 (unmarked) 33p each	
Pack of 10 2N2926G	55p
unbranded but tested	
Unmarked but fully tested 2N3055	38p
1-9 10 plus	27p
FULLY MARKED TYPES	
AD161, AD162 M/P	
1-9 10 plus	58p
BC107-BC108 BC109	
1-9 10-99 100 plus	9p 8p 8p
BC 182L-3-4-212-4 1-3 10 plus	9p 9p 8p
AC127 or AC128	
1-9 10 plus 100 plus	13p 12p 11p
ZENER DIODES	
400 M/W 5% Miniature BZY 88 Range	
All voltages 3-3 - 33 Volt 8p each	
1 watt 5% All voltages 6-8 - 200 Volts 14p each	
10 watt 5% All Voltages 7-5 - 100 Volts 61p each	

## Linear Integrated Circuits

301 DIL	50p	723c DIL	99p
301 TO99	55p	723c TO99	95p
301 8 PIN DIL	46p	741c 8 PIN DIL	89p
301A DIL	69p	741c 14 PIN DIL	89p
301A TO99	89p	741c TO99	41p
301A 8 PIN DIL	86p	747c DIL	40p
307 DIL	89p	748c DIL	39p
307 TO99	89p	748c TO99	41p
307 8 PIN DIL	86p	1437 DIL	1-27p
308 TO99	6-40p	1458 TO99	1-27p
308A TO99	6-40p	3046 DIL	84p
799c DIL	86p	7503 DIL	1-27p
799c TO99	81p		



## Transistors

AC107	16p	BC138	38p	BF260	28p	OC44	14p	Diodes & Rectifiers	
AC128	14p	BC142	38p	BF299	18p	OC45	14p		
AC127	15p	BC143	38p	BF330	18p	OC70	28p		
AC128	15p	BC144	30p	BF390	31p	OC77	14p		
AC142K	22p	BC145	26p	BFX84	25p	OC72	14p		
AC141K	20p	BC147	9p	BFX85	35p	OC81	14p		
AC176	15p	BC148	9p	BFX86	22p	OC83	22p		
AC187	18p	BC149	9p	BFX87	28p	OC84	28p		
AC187K	20p	BC153	16p	BFX88	28p	TIP294	53p		
AC188	13p	BC154	17p	BFY30	21p	TIP30A	64p		
AC188K	20p	BC157	18p	BFY51	17p	TIP31A	84p		
ACY17	24p	BC158	17p	BFY52	17p	TIP32A	78p		
ACY18	21p	BC159	14p	BFY64	30p	TIP33	1-10p		
ACY19	26p	BC167	13p	BFY90	72p	TIP34A	1813p		
ACY20	22p	BC168	11p	BFZ20	19p	OC46	28p		
ACT21	25p	BC189	11p	CA07	22p	TIP35A	1-54		
ACY22	18p	BC177	18p	CA26	35p	TIP36A	29-53		
ACY39	68p	BC179	16p	CA28	81p	TIP36A	1894p		
AD140	40p	BC182L	9p	CA50	17p	23-19			
AD142	44p	BC183L	9p	MP8111	35p	TIP41A	79p		
AD143	38p	BC184L	9p	MP8112	42p	TIP42A	91p		
AD149	38p	BC186	33p	MP8113	35p	2N708	15p		
AD180	60p	BC212L	11p	MP8121	35p	2N930	28p		
AD161	28p	BC213L	11p	MP8122	44p	2N1131	22p		
AD162	28p	BC214L	11p	MP8123	50p	2N1132	28p		
AD M/P	50p	BC258	9p	NKT211	28p	2N1613	22p		
AF114	14p	BC259	9p	NKT212	28p	2N1711	28p		
AF115	14p	BC287	14p	NKT214	28p	2N2904	40p		
AF116	14p	BC300	16p	NKT217	28p	2N2904A	44p		
AF117	14p	BC301	16p	NKT219	28p	BA145	22p		
AF118	92p	BC301	32p	NKT271	20p	BA146	14p		
AF124	27p	BC302	30p	NKT274	20p	BA148	14p		
AF139	30p	BC303	50p	NKT275	25p	BA149	14p		
AF239	41p	BC304	40p	NK T403	71p	2N3063	16p		
AL100	77p	BCY70	17p	NK T405	53p	2N3064	35p		
AL102	68p	BCY71	37p	NK Y603F	29p	2N3065	44p		
AL103	55p	BCY72	17p	68P	46p	2N2905	44p		
ASY22	31p	BD123	68p	NKT613G	67p	2N3663	57p		
ASY26	40p	BD130	50p	33p	2N3702	9p	OA5	19p	
AU103	99p	BD131	68p	NKT674	28p	2N3703	9p	OA9	19p
AU110	11-10	BD132	90p	NKT677G	33p	2N3704	9p	OA10	24p
AU111	77p	BD135	42p	24p	2N3705	9p	OA47	9p	
BC102	9p	BD138	57p	NKT713	32p	2N3708	9p	OA70	8p
BC108	9p	BD141	11-87	NKT773	27p	2N3707	9p	OA73	11p
BC109	9p	BD142	50p	OC19	55p	2N3708	9p	OA79	8p
BC113	15-14p	BF159	33p	OC20	55p	2N3709	9p	OA81	8p
BC116	18p	BF173	29p	OC23	38p	2N3710	9p	OA85	11p
BC125	19p	BF177	29p	OC25	28p	2N3711	9p	OA90	8p
BC126	25p	BF178	29p	OC28	38p	2N3714	17p	OA91	8p
BC132	18p	BF179	35p	OC29	35p	2N3810	28p	OA91	8p
BC134	16p	BF194	15p	OC35	38p	40361	60p	OA95	8p
BC135	16p	BF195	15p	OC38	38p	40362	60p	OA95	8p
BC137	16p	BF244	27p	OC41	14p	40836	60p	OA200	11p

## MULLARD POLYESTER'S

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
250V P.C. mounting: 0-01µF, 0-015µF, 0-22µF, 33p, 0-33µF, 0-47µF, 0-068µF, 4p, 0-1µF, 4p, 0-16µF, 0-22µF, 51p, 0-33µF, 7p, 0-47µF, 91p, 0-68µF, 18p, 1-0µF, 14p, 1-5µF, 22p, 2-2µF, 27p

**MULLARD POLYESTER CAPACITORS C296 SERIES**  
400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 21p, 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 31p, 0-047µF, 0-068µF, 0-1µF, 41p, 0-15µF, 61p, 0-22µF, 81p, 0-33µF, 12p, 0-47µF, 14p, 180V: 0-01µF, 0-015µF, 0-22µF, 0-033µF, 0-47µF, 0-068µF, 3p, 0-1µF, 81p, 0-16µF, 41p, 0-22µF, 51p, 0-33µF, 61p, 0-47µF, 81p, 0-68µF, 12p, 1-0µF, 141p.

## VOLUME CONTROLS

Potentiometers  
Carbon track 500 Ω to 2-2M Ω  
Log or Linear  
Single 13p. Dual gang (stereo) 44p  
Single type with D.P. switch 13p extra.

## SLIDE POTENTIOMETERS

58mm, TRACK  
SINGLE GANGED, LOG or LIN 1k to 1M.  
45p each  
TWIN GANGED, LOG or LIN 1k to 500k.  
66p each.

## CARBON SKELETON PRESETS

Small high quality type (linear only).  
All values 100-5 meg ohms.  
-1 watt 5p each  
-2-5 watt 6p each

## VEROBOARD

0-15	0-1
Matrix	Matrix
2½in x 3½in	19p
2½in x 5in	28p
3½in x 3in	28p
3½in x 5in	35p
5in x 17in (plain)	94p
Vero Pins (bag of 36), 22p	
Vero cutter, 50p; Pin insertion Tools (0-1 and 0-15 matrix) at 61p.	

## SLIDE SWITCH

BPST 11p each. D.P.D.T. 13p each.

## MINIATURE NEON LAMPS

240V or 110V 1-4 5p, 5 plus 41p each.

## MINITRON DIGITAL INDICATOR TYPE 3015F

Reads 0-9 and decimals  
(Data Sheet on request)  
**ONLY £1.50**  
16 DIL Socket 83p  
Driven by 7447 £1.05

## RECTIFIERS

**NEW**  
ALL  
SILICON!



**PRACTICAL  
WIRELESS**

**ELECTRONIC IGNITION SYSTEM**

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P. Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, supplied with de-luxe kit only, refundable on purchase of kit.

Suitable for 12v systems with Pos. or Neg. earth.

Price: Standard Kit .....£7.97 U.K. Post Free  
De-Luxe Kit .....£9.62 U.K. Post Free

Quantity Discounts:  
Trade and Overseas 1-5 Nett 6-9 Less 10%  
Enquiries Invited 10-49 Less 15% 50-99 Less 20%  
Mail Order Only 100-999 Less 25% 1000 up Less 30%

**PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING.**

**DABAR ELECTRONIC PRODUCTS**

98A LICHFIELD STREET,  
WALSALL, STAFFS. WS1 1UZ  
Tel. Walsall 34365

**FELSTEAD ELECTRONICS (PW 70)**  
LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas, and with all orders on request). Cash with order only—No C.O.D. or Caller service. Charges (Min. 7p) in brackets after all items apply to G.B. and Eire only. Regret orders under 30p plus charges unacceptable. S.A.E. please for enquiries or cannot be replied to. Overseas, including Eire and Channel Isles, orders less 10% off prices below, which include V.A.T. **RECORDING TAPE:** Finest quality/value British Mylar available: **STANDARD 5" 600ft.** 40p, 5 1/2" 900ft. 55p; 7" 1200ft. 62p; **LONG PLAY 5" 900ft.** 55p; 5 1/2" 1200ft. 62p; 7" 1800ft. £1.00 (Charges for 5" and 5 1/2", singles 9p, two to four 8p each; five and over 33p the lot.) For 7", one or two 11p each reel, 3, 4 and 5 reels 33p the lot, 6 reels and over 33p the lot.) Other sizes and accessories in list. **CASSETTES:** Two types, Both in Library Cases, C60 33p, C90 45p, C120 72p. Deluxe Types: C60 55p, C90 72p, C120 99p. (Charges for both types, under 5, 8p each, 5 for 17p. All quantities over 5, 22p the lot.) **CARTRIDGES** all with standard fittings and styl. Stereo-compatible Mono GP91/8C 98p; **STEREO GP93 £1.25**, Stereo Ceramic GP94 £1.75. (All at 7p each.) Comparatives shown in List, with more types inc. Sonotone 9TAHC, Stereo Ceramic Diamond £1.70 (7p). **DIAMOND STYLII:** single tip types: Acoo GP37, GP59, GP65/67, GP71, BBR TC8/LP/ST; COLLARO O.P. and DC284, GARRARD GC2, GC8, GC810, GC812, RONETTE BF40, O.P. and T. PHILIPS 3301 (3060, 3066, 3302, 3304), 3010/12/13/15, SONOTONE 19T/20T AL AL AT 32p. **SAPPHIRE 18p (7p).** **DIAMOND DOUBLE TIP TURNOVER TYPES** (78 sap. on other side). For ACOO GP73, GP91 (for cartridges GP93, GP94 etc.) GP918C (for stereo compat. types) GP104 BBR 8T4 (8T3, 8T5), 8T9 (8T8), 8T12/14/15, SONOTONE 8TA, 9TA, 9TAHC. PHILIPS 3306 3310, 3224, 3228/22 GP280. GARRARD GCM21, and 22, GC823, GK825 and 26, GCM21T and 22T, GCM24T GC823. GK826T and 26T, GCM31, GC836, GC838, GC838, K840A, K841B ETC. ALL AT 88p (7p). **SAPPHIRE 32p (7p).** **DOUBLE DIAMOND STYLII:** same dia STYLII tip each side, no 78) All types £1.25 (7p). **SAPPHIRE DOUBLE STYLII TIPPED 32p (7p).** **DIAMOND STYLII GOLDDRING REPLACEMENTS:** (G800, G800H & G850, £2.25 each. G800E, £3.75 (8p each). **PICK-UP WIRE:** super thin flex screened, sheathed, TWIN 7p per yard, 4-core 18p per yard (either up to 6 yds. 7p). Over, charges paid. **MICROPHONES:** CRYSTAL: LAPEL 1 1/2", clip/hand, lead 3-5mm jack plug 38p (9p). CM20 Cream Plastic hand 88p (9p); "MIC 45". Curved metal hand grip £1.10 (11p) ALL with leads. **DYNAMIC:** Excellent Mike, 50K Ω, only 3 1/2" long, black/chrome, switched, lead with 2.5 and 3.5 mm jack plugs £1.87 (8p). Cardiod Ball, 50K/600 Ω built in volume control, on/off switch, special 2000 Ω lead, the best value anywhere at £2.80 (33p); Uni-dir mesh ball 50K/600 Ω jack plug cable, adaptor, £5.28 (33p); Omni-dir. Ball mesh, 50K, cable adaptor, jack plug, £4.29 (33p each). **SPEAKERS:** Very popular 12" ROUND, fitted tweeter, 3, 8 or 15 ohms (state which) £2.06 (33p) or pair for stereo £4.65, charges paid. **SMALL 2 1/2", 3 Ω, 8 Ω or 64 Ω** (state which) 41p (9p). More speakers in List. **HEADPHONES:** High resistance 2000 Ω adjustable £1.10 (11p). **EARPIECES:** with lead and min. 3-5mm or 3-5mm (state which) jack plug. **MAGNETIC 12p.** CRYSTAL (3-5mm plug only) 28p (up to 6 for 8p any size). **SOLDERING IRON:** 811m, modern, British high speed, 8 1/2", all parts replaceable, highest quality, fully guaranteed £1.29 (11p). **TRANSFORMERS:** Sub-min 11 x 11 x 12mm. OUTPUT (3 1/2 for OCT8, etc.) 16p or DRIVER 17p (Up to 12 for 7p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5yds. Assta. coils. **SOLID CORE 16p (7p).** **FLEXIBLE CORE 18p (9p).** **RETRACTABLE FLEXIBLE LEADS (CURLIES)** with phono plug each end, or phono plug one end, phono socket at the other (state which) 8T, 30p; 12T, 53p (either 7p). **VIBRATORS:** 12v/4 pin non-synch 121HD4, 2 1/2" ex. pins, 88p. **SAME** but 3 1/2" ex. pins, USA, 184p; 12v/7 pin synch. (12SR7) 2 1/2" ex. pins, 72p (9p any type). **MAINS BATTERY ELIMINATORS:** Two models, both 240v A.C. input. Suit most radios and cassette recorders/players with front switch, pilot lights, mains and output leads. Model 8C, 3, 6, 7 1/2 and 9v 400mA. stabilised with multi-output adaptor £5.60 (35p). Model N.R. has additional 12v output and 15 500mA £6.00 (35p).

OUR LIST (see heading) has added to the above items Cartridge and StylII Comparisons Special Non-repeatable Offers, Aerials, Diodes, Transistors, Multi-Leads, Plugs, Socketts of many types, Speakers, Vol. Controls, Multi-testers, Mike Inserts, Neoms, Indicators, STEREO Headphones, Pocket Screwdriver Testers, Tel. Pick-ups, Wire, Cable, etc., etc.

# Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a

mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Training Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

Ring

**01-637 2171**

between 9 a.m. and 9 p.m. and ask for Mr PROUT

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.

Please give me further information.

Name

Address

Age  Phone  PW 7

**CONTROL DATA  
INSTITUTE**

**CONTROL DATA  
LIMITED**

The Training Division of one of the world's largest Computer manufacturers.

# THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

## BRAND NEW FULLY GUARANTEED DEVICES

Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p		
AC107	22	AD161	37	BC145	50	BD133	72	BF192	44	MAT120	21	2G308	39	2N2148	63	2N3083	51	2N4059	11
AC113	22	AD162	37	BC147	11	BD136	44	BF193	44	MAT121	22	2G309	39	2N2160	66	2N3084	51	2N4060	13
AC115	26	AD161 &		BC148	11	BD136	44	BF194	28	MAT122	46	2G339	22	2N2192	39	2N3085	55	2N4061	13
AC117K	22	AD162 (MP)		BC149	13	BD137	50	BF185	33	MPT104	41	2G339A	18	2N2193	39	2N3391	18	2N4062	13
AC122	13			BC150	20	BD138	55	BF188	44	MPT105	41	2G344	20	2N2194	39	2N3391A	18	2N4284	19
AC125	19	ADT140	55	BC151	22	BD139	61	BF194	13	OC19	39	2G345	18	2N2217	24	2N3392	16	2N4285	19
AC126	19	AF114	27	BC152	19	BD149	66	BF195	13	OC20	70	2G371	18	2N2218	22	2N3393	16	2N4286	19
AC127	19	AF115	27	BC153	31	BD155	88	BF196	18	OC22	42	2G371D	13	2N2219	22	2N3394	16	2N4287	19
AC128	19	AF116	27	BC154	33	BD176	66	BF197	18	OC33	46	2G374	19	2N2220	24	2N3395	19	2N4288	19
AC132	16	AF117	27	BC157	20	BD177	66	BF200	50	OC34	62	2G374	19	2N2221	22	2N3402	23	2N4289	19
AC134	16	AF118	39	BC158	13	BD177	72	BF222	1-05	OC25	42	2G377	33	2N2222	22	2N3403	23	2N4290	19
AC137	16	AF124	33	BC159	13	BD178	72	BF257	50	OC26	28	2G378	18	2N2268	19	2N3404	31	2N4291	19
AC141	16	AF125	28	BC160	50	BD179	77	BF258	66	OC28	55	2G381	18	2N2369	16	2N3405	46	2N4292	19
AC141K	19	AF126	31	BC161	55	BD180	77	BF259	94	OC29	55	2G382	18	2N2369A	16	2N3414	17	2N4293	19
AC142	16	AF127	31	BC167	18	BD185	72	BF262	61	OC35	46	2G401	33	2N2371	27	2N3415	17	2N4294	13
AC145K	19	AF139	33	BC168	13	BD186	72	BF263	61	OC36	55	2G414	33	2N2412	27	2N3416	31	2N4295	35
AC151	17	AF178	33	BC169	13	BD187	77	BF262	39	OC41	22	2G417	23	2N2446	22	2N3417	31	2N4296	35
AC154	22	AF179	55	BC170	18	BD188	77	BF271	33	OC42	27	2N388	39	2N2711	23	2N3525	83	2N4549	44
AC155	22	AF180	55	BC171	16	BD189	83	BF272	88	OC44	16	2N388A	61	2N2712	23	2N3646	10	2S901	55
AC156	22	AF181	50	BC172	16	BD190	83	BF273	39	OC45	14	2N404	22	2N2714	23	2N3702	11	2S302A	46
AC157	27	AF186	50	BC173	16	BD196	94	BF274	39	OC70	11	2N404A	31	2M2904	19	2N3703	11	2S302	46
AC158	22	AP239	41	BC174	16	BD196	94	BF275	66	OC71	11	2N624	46	2N2904A	23	2N3704	12	2S303	61
AC160	22	AL102	72	BC176	24	BD197	89	BF289	30	OC72	16	2N927	54	2N2905	23	2N3705	11	2S304	77
AC167	22	AL103	72	BC177	21	BD198	93	BF292	62	OC74	16	2N928	46	2N2906A	23	2N3706	10	2S305	93
AC168	27	ASV26	28	BC178	21	BD199	1-05	BF285	33	OC75	17	2N939	50	2N2906	17	2N3707	12	2S306	93
AC169	16	ASV27	28	BC179	21	BD200	1-05	BF286	24	OC76	17	2N939	14	2N2906B	20	2N3708	8	2S307	93
AC170	22	ASV28	28	BC180	27	BD206	88	BF287	27	OC77	28	2N967	15	2N2907	22	2N3709	10	2S321	62
AC172	27	ASV29	28	BC181	27	RD206	88	BF288	24	OC81	17	2N968	27	2N2907A	24	2N3710	10	2S322	46
AC178	31	ASV30	28	BC182	11	BD207	1-05	BF290	22	OC81D	17	2N969	39	2N2923	16	2N3711	10	2S322A	46
AC179	31	ASV31	28	BC182L	11	BD206	1-05	BF291	22	OC82	17	2N706	9	2N2924	16	2N3819	31	2S323	62
AC180	19	ASV32	28	BC183	11	BDY20	1-10	BF292	24	OC84	22	2N707	22	2N2925	16	2N3820	55	2S324	77
AC180K	22	ASV34	28	BC183L	11	BF115	27	BFY43	19	OC83	22	2N708	13	2N2926(G)	14	2N3821	89	2S325	77
AC181	19	ASV35	28	BC184	13	BF117	50	BFX25	94	OC84	22	2N711	33	2N2926(Y)	12	2N3823	31	2S326	77
AC181K	22	ASV36	28	BC184L	13	BF118	77	BXS19	17	OC139	22	2N717	39	2N2926(R)	11	2N3903	31	2S327	77
AC187	24	ASV37	28	BC186	31	BF119	77	BXS20	17	OC140	22	2N718	27	2N2926(R)	11	2N3904	33	2S701	46
AC187K	22	ASV38	28	BC187	31	BF121	50	BYS25	17	OC169	28	2N718A	55	2N2926(B)	11	2N3905	31	40361	44
AC188	34	AS221	44	BC207	12	BF123	55	BYS26	17	OC170	28	2N726	31	2N3010	77	2N3906	30	40362	50
AC188K	22	BC107	12	BC208	12	BF126	50	BYS27	17	OC171	28	2N727	31	2N3011	16	2N4058	13		
ACV17	28	BC108	10	BC209	13	BF127	55	BYS28	17	OC200	28	2N743	22						
ACV18	28	BC109	11	BC212L	12	BF152	61	BYS29	17	OC201	31	2N744	22						
ACV19	22	BC113	11	BC213L	12	BF153	50	BYS30	20	OC202	31	2N914	16	AA119	9	BY133	23	0A70	8
ACV20	22	BC114	17	BC214L	16	BF154	50	BYS39	20	OC203	28	2N918	33	AA120	9	BY164	55	0A79	8
ACV21	22	BC115	17	BC225	28	BF155	77	BYS40	31	OC204	28	2N929	23	AA129	9	BY X 38/30	46	0A81	8
ACV22	22	BC116	17	BC226	28	BF156	55	BYS41	31	OC206	39	2N930	28	AA130	10	BYZ10	39	0A85	10
ACV27	20	BC117	12	BCY30	27	BF157	81	BYS42	14	OC309	44	2N131	22	AA131	11	BYZ11	33	0A90	7
ACV28	21	BC118	11	BCY31	29	BF158	61	BYS95A	14	OC711	48	2N132	24	BA100	11	BYZ12	33	0A91	7
ACV29	39	BC119	33	BCY32	33	BF159	86	Bul105	2-20	ORP12	48	2N1302	16	BA116	23	BYZ13	28	0A95	8
ACV30	31	BC120	88	BCY33	24	BF160	44	CI11E	55	ORP60	44	2N1303	16	BA126	24	BYZ16	44	0A200	7
ACV31	31	BC125	13	BCY34	28	BF162	44	C400	33	ORP61	44	2N1304	19	BA148	16	BYZ17	39	0A202	8
ACV34	23	BC126	20	BCY70	18	BF163	44	C407	28	P346A	22	2N1305	19	BA154	13	BYZ18	39	8D10	6
ACV35	23	BC132	13	BCY71	20	BF174	44	C424	22	P397	46	2N1306	23	BA155	16	BYZ19	31	8D19	6
ACV36	31	BC133	20	BCY72	18	BF165	44	C425	55	ST140	14	2N1307	23	BA156	16	CG62	13	1N34	8
ACV40	19	BC135	13	BCZ10	22	BF167	24	C426	39	ST141	19	2N1308	26	BY100	17	(OA91 Eq.)	6	1N34A	8
ACV41	20	BC136	17	BCZ11	28	BF173	24	C428	22	T1843	33	2N1309	26	BY101	13	CG651	5	1N34B	7
ACV44	39	BC137	17	BCX12	28	BF176	39	C441	33	UT46	30	2N1613	22	BY105	19	(OA70-OA70)	7	1N916	7
AD130	42	BC138	44	BD121	66	BF177	39	C442	33	2G301	21	2N1711	22	BY114	13	Eq.)	7	1N414B	7
AD140	53	DC140	33	BD123	72	BF178	33	C444	39	2G392	21	2N1869	35	BY126	16	OA5	39	1S021	11
AD142	53	DC141	33	BD124	58	BF179	33	C450	24	2G393	21	2N1869	50	BY127	17	OA5SL	23	1S951	7
AD143	42	DC142	33	BD131	55	BF180	33	MAT100	21	2G394	27	2N1893	41	BY128	17	OA10	39		
AD149	55	DC143	33	BD132	66	BF181	33	MAT101	22	2G396	44	2N2147	79	BY130	18	OA47	8		

Cut these 3 pages out and keep for reference

### NEW COMPONENT PAK BARGAINS

Qty.	Description	Price
C 1	250 Resistors mixed values approx. count by weight	0-55
C 2	250 Capacitors mixed values approx. count by weight	0-55
C 3	50 Precision Resistors 1%, mixed values	0-55
C 4	75 W Resistors mixed preferred values	0-55
C 5	5 Pieces assorted Ferrite Rods	0-55
C 6	2 Tuning Gangs, MW/LW VHF	0-55
C 7	1 Pack Wire 60 metres assorted colours	0-55
C 8	10 Reed Switches	0-55
C 9	3 Micro Switches	0-55
C10	15 Assorted Pots & Pre-Sets	0-55
C11	5 Jack Sockets 3 x 3-5m 2 x Standard Switch Types	0-55
C12	40 Paper Condensers preferred types mixed values	0-55
C13	20 Electrolytics Trans. types	0-55
C14	1 Pack assorted Hardware - Nuts/Bolts, Grommets etc.	0-55
C15	6 Mains Switches, 2 Amp	0-55
C16	20 Assorted Tag Strips & Panels	0-55
C17	10 Assorted Control Knobs	0-55
C18	4 Rotary Wave Change Switches	0-55
C19	3 Relays 6-24V Operating	0-55
C20	4 Sheets Copper Laminate approx. 10" x 7"	0-55

Please add 10p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19 & C20.

### JUMBO COMPONENT PAKS

MIXED ELECTRONIC COMPONENTS  
Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs in weight. Price Incl. P. & P. £1.65 only.  
Especially good value

**BRAND NEW POST OFFICE TYPE TELEPHONE DIALS**  
ONLY 83p each



### THE NEW S.G.S. EA 1000 AUDIO AMP MODULE \*Guarantee

**3 Watts**  
R.M.S.  
ONLY **£2-89** each

Module Tested and Guaranteed.  
Qty. 1--9 £2-89; 10--25 £2-50 Price each. Larger quantities noted on request. Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.



**Plus much more-- send now for the BI-PAK "component catalogue"**  
5p to cover postage, etc.

**SYSTEM 12 STEREO**

Each Kit contains two Amplifier Modules, 3 watts RMS, two loudspeakers, 15 ohms, the pre-amplifier, transformer, power supply module, front panel and other accessories, as well as an illustrated stage-by-stage instruction booklet designed for the beginner.

Further details available on request.

**ONLY £18-64 FREE P. & P.**

## NOW-TURN OVER FOR MORE FANTASTIC OFFERS

# The largest selection

## NEW LOW PRICED TESTED S.C.R.'s

PIV 1A	3A	5A	7A	10A	16A	30A
TO-18	TO-68	TO-68	TO-68	TO-68	TO-48	TO-48
50	0-28	0-28	0-39	0-39	0-52	0-55
100	0-28	0-37	0-52	0-52	0-55	0-64
200	0-39	0-41	0-54	0-54	0-63	0-87
400	0-48	0-52	0-82	0-82	0-74	0-83
600	0-59	0-63	0-75	0-75	0-85	1-07
800	0-70	0-77	0-88	0-88	0-99	1-32
						1-65
						4-40

## SIL. RECTS. TESTED

PIV 300mA	750mA	1A	15A	5A	10A	30A
50	0-04	0-06	0-06	0-08	0-16	0-23
100	0-04	0-07	0-06	0-10	0-18	0-26
200	0-06	0-10	0-07	0-16	0-22	0-27
400	0-07	0-15	0-08	0-22	0-30	0-41
600	0-08	0-18	0-11	0-26	0-38	0-50
800	0-11	0-19	0-12	0-28	0-41	0-61
1000	0-12	0-28	0-16	0-38	0-51	0-70
1200		0-37		0-42	0-63	0-83

## TRIACS

V BOM 2A	6A	10A
TO-5	TO-6	TO-48
\$p	\$p	\$p
100	33	55
200	55	66
400	77	82

## DIACS

FOR USE WITH TRIACS
BR100 (D32) 41p each

## FREE

One 50p Pak of your own choice free with orders valued \$4 or over.

**BRAND NEW TEXAS GERM. TRANSISTORS**  
Coded and Guaranteed

Pak No.	EQVT
T1 8 203713	OC71
T2 8 D1374	OC75
T3 8 D1216	OC81D
T4 8 20381T	OC81
T5 8 20382T	OC82
T6 8 20344B	OC94
T7 8 20346B	OC45
T8 8 20378	OC78
T9 8 20399A	2N1302
T10 8 20417	AF117

All 56p each pak

**D1899 NPN SILICON DUAL TRANSISTOR**  
(Similar to 2N2060)

1	25	100+
0-28	0-28	0-28

**ND 120 NIXIE DRIVER TRANSISTOR**  
Suitable replacement for BEX 21, C.407, 2N 1893 120vcb.

1	25	100+
0-19	0-17	0-16

Sil. Trans. suitable for F.E. Organ. Metal TO-18 Eqt. ZTX300 51p each. Any Qty.

**GF 100 TO3 METAL CASE GERMANIUM**  
V<sub>be</sub>=-80V, V<sub>ceo</sub>=-50V, I.C.=10 amps, P<sub>tot</sub>=30W, h<sub>fe</sub>=30-170.  
Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0-48	0-44	0-40

**GP 300 TO3 METAL CASE SILICON**  
V<sub>be</sub>=-100V, V<sub>ceo</sub>=-60V, I.C.=15 amps, P<sub>tot</sub>=115W, h<sub>fe</sub>=20-100fT, -1MHz. Suitable replacement for 2N 3055, BDY 11 or BDY 20.

1	25	100+
0-55	0-53	0-51

**AD161/162 PNP M/P COMP GERM TRANS.**  
OUR LOWEST PRICE OF 60p PER PAIR

## FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-33V. 400mV (DO-7 Case) 15p ea. 1 1/2W (Top-Hat) 20p ea. 10W (SO-10 Stud) 38p ea.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100IV. 99p each

2 Amp. BRIDGE RECTS. 50 v RMS 35p each  
100 v RMS 41p ..  
400 v RMS 81p ..  
Size 16 mm x 16 mm.

UT 46 UNIJUNCTION TRANSISTORS  
Direct replacement for T18 4Strand BEN 3000 also electrically equivalent to 2N2646

1	25	100+
0-30	0-28	0-22

## CADMIUM CELLS

ORP12 48p  
ORP60, ORP61 44p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N70678. BST-27/29/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20	For	0-55
50	For	1-10
100	For	1-92
500	For	8-25
1000	For	14-30

SIL. G.M. DIODES \$p  
300mW V<sub>0</sub> 30. -0-85  
40PIV(Min.) 100. 1-10  
Sub-Min. 500. 5-50  
Full Tested 1,000 9-90  
Ideal for Organ Builders.

R 2400 TOR NPN SILICON HIGH VOLTAGE  
V<sub>be</sub>=-250V, V<sub>ceo</sub>=-100V, I.C.=6 amps, P<sub>tot</sub>=30W, h<sub>fe</sub>=typ.30 fT=5MEHz.

1	25	100+
0-55	0-50	0-44

## 2N3055

115 WATT SILICON POWER NPN 55p EACH

B1P 19/20 TO3 NPN PLASTIC SILICON  
V<sub>be</sub>=-100V, V<sub>ceo</sub>=-50V I.C.=10 amps. P<sub>tot</sub>=50W, h<sub>fe</sub>=typ. 100 fT=3MHz B1P 19/20 Matched Pair.

1	25	100+
0-37	0-35	0-32

## KING OF THE PAKS Unequaled Value and Quality

### SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-55
U 2	60 Mixed Germanium Transistors AF/RF	0-55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-55
U 4	4 Germanium Transistors like OC81, AC128	0-55
U 5	60 200mA Sub-Min. Silicon Diodes	0-55
U 6	30 Sil. Planar Trans. NPN like BBY95A. 2N706	0-55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000V	0-55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-55
U 9	20 Mixed Voltage, 1 Watt Zener Diodes	0-55
U10	20 BA750 charge storage Diodes DO-7 Glass	0-55
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0-55
U12	12 Silicon Rectifiers Epoxy 600mA up to 800 PIV	0-55
U13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0-55
U14	150 Mixed Silicon and Germanium Diodes	0-55
U15	25 NPN Sil. Planar Trans. TO-5 like BFY61, 2N897	0-55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-55
U19	25 Silicon NPN Transistors like BC108	0-55
U20	12 1 1/2 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-55
U21	30 AF Germanium Alloy Transistors 2G300 Series & OC71	0-55
U22	30 MADT's like MHz Series PNP Transistors	0-55
U23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-55
U24	25 300 MHz NPN Silicon Transistors 2N708, BBY27	0-55
U25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-55
U26	12 NPN Germanium AF Transistors TO-1 like AC127	0-55
U27	10 1 Amp SCR's TO-5 can, up to 600 PIV CRB1/25-600	1-10
U28	15 Plastic Silicon Planar Trans. NPN 2N2928	0-55
U29	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0-55
U30	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0-55
U31	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-55
U32	30 Silicon PNP Alloy Trans. TO-5 BCY26 2B302/4	0-55
U33	25 Silicon Planar Transistors PNP TO-18 2N2906	0-55
U34	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0-55
U35	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0-55
U36	30 RF Germ. PNP Transistors 2N1803/5 TO-5	0-55
U37	10 Dual Transistors 6 lead TO-5 2N2906	0-55
U38	40 VHF Germanium PNP Transistors TO-1 NKT867, AF117	0-55
U39	25 Sil. Trans. Plastic TO-18 A.F. BC118/114	0-55
U40	20 Sil. Trans. Plastic TO-5 BC115/116	0-55
U41	7 3A SCR. TO66 up to 600PIV	1-10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

**SILICON PHOTO TRANSISTOR TO-18 Lens end**  
NPN Sim. to BF 25 and P21.  
BRAND NEW. Full data available. Fully guaranteed.  
Qty. 1-24 25-99 100 up  
Price each 49p 44p 38p

**F.E.T.'S**

2N3819	81p	2N5458	35p
2N3920	55p	2N5459	44p
2N3921	89p	BFW10	89p
2N3823	31p	MPF105	41p

### NEW 6th EDITION

**TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 99p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

## QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q1	20 Red spot transistors PNP	0-55
Q2	16 White spot R.F. transistors PNP	0-55
Q3	4 OC 77 type transistors	0-55
Q4	6 Matched transistors OC44/45/81/81D	0-55
Q5	4 OC 75 transistors	0-55
Q6	5 OC 72 transistors	0-55
Q7	4 AC 128 transistors PNP high gain.	0-55
Q8	4 AC 126 transistors PNP	0-55
Q9	7 OC 81 type transistors	0-55
Q10	7 OC 71 type transistors	0-55
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0-55
Q12	3 AF 116 type transistors	0-55
Q13	3 AF 117 type transistors	0-55
Q14	3 OC 171 H.F. type transistors	0-55
Q15	7 2N2928 Sil. Epoxy transistors mixed colours	0-55
Q16	2 GET880 low noise Germanium transistors	0-55
Q17	6 NPN 2 x ST.141 & 3 x ST.140.	0-55
Q18	4 MADT'S 2 x MAT.100 & 2 x MAT.120	0-55
Q19	3 MADT'S 2 x MAT.101 & 1 x MAT.121	0-55
Q20	4 OC 44 Germanium transistors A.F.	0-55
Q21	4 AC 127 NPN Germanium transistors	0-55
Q22	20 NKT transistors A.F. H.F. coded.	0-55
Q23	10 OA 92 Silicon diodes sub-min.	0-55
Q24	8 OA 81 diodes	0-55
Q25	15 IN914 Silicon diodes 75 PIV 70mA	0-55
Q26	8 OA95 Germanium diodes sub-min IN69	0-55
Q27	2 10A PIV silicon rectifier BR403R.	0-55
Q28	2 Silicon power rectifiers BYZ 13	0-55
Q29	4 Silicon transistors 2 x 2N896, 1 x 2N897, 1 x 2N898	0-55
Q30	7 Silicon switch transistors 2N706 NPN	0-55
Q31	6 Silicon switch transistors 2N707 NPN	0-55
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0-55
Q33	3 Silicon NPN transistors 2N1711	0-55
Q34	7 Silicon NPN transistors 2N2369, 600MHZ. (code F397)	0-55
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0-55
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0-55
Q37	3 2N3053 NPN Silicon transistors	0-55
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0-55

## ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales—  
Conversion of Frequency and Wavelength.  
Calculation of L, R and Z of Tuned Circuits.  
Resonance and Self Inductance. Area of Circles, Volume of Cylinders, Resistance of Conductors, Weight of Conductors, Decibel Calculations, Angle Functions, Natural Logs and e<sup>x</sup> Functions, Multiplication and Division, Squaring, Cubing and Square Roots, Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 22 cm x 4cm. Complete with case and instructions. Price each: £8.99

## INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	-12 x 7400	0-55	UIC46	-5 x 7446	0-55	UIC86	-5 x 7486	0-55
UIC01	-12 x 7401	0-55	UIC47	-5 x 7447	0-55	UIC90	-5 x 7490	0-55
UIC02	-12 x 7402	0-55	UIC48	-5 x 7448	0-55	UIC91	-5 x 7491	0-55
UIC03	-12 x 7403	0-55	UIC49	-12 x 7450	0-55	UIC92	-5 x 7492	0-55
UIC04	-12 x 7404	0-55	UIC51	-12 x 7451	0-55	UIC93	-5 x 7493	0-55
UIC05	-12 x 7405	0-55	UIC52	-12 x 7452	0-55	UIC94	-5 x 7494	0-55
UIC06	-8 x 7406	0-55	UIC54	-12 x 7454	0-55	UIC95	-5 x 7495	0-55
UIC07	-8 x 7407	0-55	UIC60	-12 x 7460	0-55	UIC96	-5 x 7496	0-55
UIC10	-12 x 7410	0-55	UIC70	-8 x 7470	0-55	UIC100	-5 x 74100	0-55
UIC13	-8 x 7413	0-55	UIC72	-8 x 7472	0-55	UIC121	-5 x 74121	0-55
UIC20	-12 x 7420	0-55	UIC73	-8 x 7473	0-55	UIC141	-5 x 74141	0-55
UIC30	-12 x 7430	0-55	UIC74	-8 x 7474	0-55	UIC151	-5 x 74151	0-55
UIC40	-12 x 7440	0-55	UIC75	-8 x 7475	0-55	UIC154	-5 x 74154	0-55
UIC41	-5 x 7441	0-55	UIC76	-8 x 7476	0-55	UIC193	-5 x 74193	0-55
UIC42	-5 x 7442	0-55	UIC80	-5 x 7480	0-55	UIC199	-5 x 74199	0-55
UIC43	-5 x 7443	0-55	UIC81	-5 x 7481	0-55			
UIC44	-5 x 7444	0-55	UIC82	-5 x 7482	0-55	UICXI	-25 Assorted	
UIC45	-5 x 7445	0-55	UIC83	-5 x 7483	0-55			74's 1-65

Packs cannot be split, but 26 assorted pieces (our mix) is available as PAK UIC X1.

**BI-PAKS NEW COMPONENT**

# -the lowest prices!

## 74 Series T.T.L. I.C.'s



BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

		25	100+	1	25	100+	1	25	100+
SN7400	0-17	0-18	0-18	SN7450	0-17	0-18	0-18	SN74141	0-74
SN7401	0-17	0-18	0-18	SN7451	0-17	0-18	0-18	SN74145	0-86
SN7402	0-17	0-18	0-18	SN7453	0-17	0-18	0-18	SN74150	0-20
SN7403	0-17	0-18	0-18	SN7454	0-17	0-18	0-18	SN74151	0-10
SN7404	0-17	0-18	0-18	SN7460	0-17	0-18	0-18	SN74153	0-81
SN7405	0-17	0-18	0-18	SN7470	0-32	0-29	0-27	SN74164	0-82
SN7406	0-39	0-34	0-31	SN7472	0-32	0-29	0-27	SN74165	0-81
SN7407	0-39	0-34	0-31	SN7473	0-41	0-39	0-36	SN74166	0-81
SN7408	0-20	0-19	0-18	SN7474	0-10	0-48	0-46	SN74168	0-88
SN7409	0-20	0-19	0-18	SN7475	0-50	0-49	0-46	SN74169	0-88
SN7410	0-17	0-16	0-15	SN7476	0-44	0-43	0-42	SN74161	0-93
SN7411	0-28	0-27	0-26	SN7480	0-74	0-71	0-64	SN74162	0-84
SN7412	0-39	0-34	0-31	SN7481	0-32	0-27	0-21	SN74163	0-84
SN7413	0-32	0-29	0-27	SN7482	0-96	0-95	0-94	SN74164	0-88
SN7414	0-48	0-44	0-42	SN7483	0-21	0-21	0-16	SN74165	0-88
SN7417	0-48	0-44	0-42	SN7484	0-21	0-21	0-16	SN74166	0-88
SN7420	0-17	0-16	0-15	SN7485	0-28	0-28	0-23	SN74167	0-88
SN7422	0-55	0-53	0-50	SN7486	0-35	0-34	0-33	SN74175	0-81
SN7423	0-55	0-53	0-50	SN7489	0-26	0-26	0-25	SN74176	0-82
SN7425	0-55	0-53	0-50	SN7490	0-74	0-71	0-64	SN74177	0-82
SN7426	0-60	0-46	0-44	SN7491	0-10	0-10	0-05	SN74180	0-20
SN7427	0-60	0-46	0-44	SN7492	0-74	0-71	0-64	SN74181	0-20
SN7428	0-77	0-70	0-68	SN7493	0-74	0-71	0-64	SN74182	0-20
SN7430	0-17	0-16	0-15	SN7494	0-85	0-82	0-76	SN74183	0-86
SN7432	0-60	0-46	0-44	SN7495	0-85	0-82	0-76	SN74190	0-20
SN7433	0-88	0-83	0-77	SN7496	0-98	0-98	0-86	SN74191	0-20
SN7437	0-71	0-68	0-66	SN74100	0-82	0-78	0-71	SN74192	0-20
SN7438	0-71	0-68	0-66	SN74104	0-07	0-04	0-04	SN74193	0-20
SN7440	0-17	0-16	0-15	SN74105	0-07	0-04	0-04	SN74194	0-20
SN7441	0-74	0-71	0-64	SN74107	0-44	0-42	0-40	SN74195	0-20
SN7442	0-74	0-71	0-64	SN74110	0-81	0-69	0-55	SN74196	0-20
SN7443	0-43	0-38	0-32	SN74111	0-38	0-27	0-21	SN74197	0-20
SN7444	0-43	0-38	0-32	SN74118	0-10	0-10	0-05	SN74198	0-26
SN7445	0-21	0-15	0-13	SN74119	0-49	0-38	0-31	SN74199	0-26
SN7446	0-27	0-24	0-21	SN74121	0-44	0-41	0-38	Terminal Pos Volt Reg. T.O.3	
SN7447	0-10	0-07	0-05	SN74122	0-54	0-43	0-41	Plastic O/P 1.5 Amps. μA7805	
SN7448	0-10	0-07	0-05	SN74123	0-08	0-27	0-26	5V. & μA7812 12V. 0-76 each	

### ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type No.	Price
BP930	13p 12p 11p
BP932	14p 13p 12p
BP933	14p 13p 12p
BP935	14p 13p 12p
BP936	14p 13p 12p
BP944	14p 13p 12p
BP945	28p 27p 24p
BP946	18p 17p 14p
BP948	28p 27p 24p
BP951	72p 68p 61p
BP962	13p 12p 11p
BP963	44p 42p 39p
BP964	44p 42p 39p
BP967	44p 42p 39p
BP969	44p 42p 39p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

### LINEAR I.C.'s—FULL SPEC.

Type No.	Price
BP 201C—BL201C	70p 59p 50p
BP 701C—BL701C	70p 55p 50p
BP 702C—BL702C	70p 55p 50p
BP 702—72702	58p 50p 44p
BP709—72709	40p 38p 33p
BP 709P—μA709C	40p 38p 33p
BP 710—72710	50p 48p 44p
BP 711—μA711	50p 48p 44p
BP 741—72741	55p 50p 45p
μA703C	81p 29p 27p
TAA 263	77p 66p 61p
TAA 293	89p 83p 77p
TAA 350	0-87p 0-74p 0-65p

S.G.S. EA1000 02-90p

## NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015F Minitron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2-3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	0-187	0-170	0-150

All indicators 0-9 + Decimal point. All side viewing. Full data for all types available on request.

### BTL MICROLOGIC CIRCUITS

	Price each
Epoxy TO-5 case	1-24 25-99 100 up
uL900 Buffer	38p 36p 29p
uL914 Dual 2 1/2 gate	38p 36p 29p
uL923 J-K flip-flop	55p 51p 49p

Date and Circuits Booklet for IC's Prices 8p.

### DUAL-IN-LINE SOCKETS.


14 & 16 Lead Sockets for use with DUAL-IN-LINE I.C.'s. TWO RANGES PROFESSIONAL & NEW LOW COST.

PROF. TYPE No.	1-24	25-99	100up.
T80 14 pin type	33p	30p	28p
T80 16 " "	39p	35p	33p
LOW COST No.			
BP8 14	17p	15p	12p
BP8 16	18p	16p	13p

## BI-PAK DO IT AGAIN! 50W pk 25w (RMS)

0.1% DISTORTION!  
HI-FI AUDIO AMPLIFIER

### THE AL50

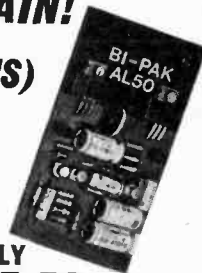

★ Frequency Response 15Hz to 100,000—1dB.

★ Load—3, 4, 8 or 16 ohms.

★ Distortion—better than 0.1% at 1KHz.

★ Signal to noise ratio 80dB.

ONLY  
**£3.58p each**


★ Supply voltage 10-35 Volts.

★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.

FULLY BUILT—TESTED—GUARANTEED.

## STABILISED POWER MODULE SPM80

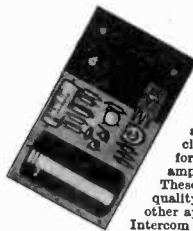

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 16 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Main Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including—Disc Systems, Public Address, Intercom Units, etc. Handbook available, 10p

PRICE £3.25

TRANSFORMER BMT80 £2.15 p. & p. 28p.

## STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable base and treble controls.

### SPECIFICATION

Frequency Response	20Hz - 20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs :	1. Tape Head
	1.25 mV into 60K Ω
	2. Radio, Tuner
	35 mV into 60K Ω
	3. Magnetic P.U.
	1.5 mV into 60K Ω

All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.

Base Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters :	100Hz
	8KHz
Signal/Noise Ratio	better than -65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm x 82mm x 35mm

ONLY £13.15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006  
Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail.

Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back



# ESSENTIAL BOOKS FOR RADIO AMATEURS

## A GUIDE TO AMATEUR RADIO

by Pat Hawker  
G3VA

Extensively revised, this new (15th) edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby.  
90p post paid

## TELEVISION INTERFERENCE MANUAL

by B. Priestley  
G3JGO

The causes of interference to TV receivers are examined, and ways in which they can be overcome are suggested in this latest RSGB publication.  
90p post paid

## AMATEUR RADIO TECHNIQUES

by Pat Hawker  
G3VA

4th Edn. 256 pages. A source book for many useful circuits and aerials. An ideas book aimed at extending the reader's awareness of new devices and techniques.  
£1.80 post paid

## RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's UK origin ensures easy availability of components. Complete coverage of technical and constructional fields.  
£4.10 post paid

These are just four of a complete range of technical publications, log books and maps for the Radio Amateur. Send s.a.e. for complete list

## RADIO SOCIETY OF GREAT BRITAIN


35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688



# BI-PRE-PAK

## 5W AMP for only £1.98

(inclusive of P.&P. and VAT)

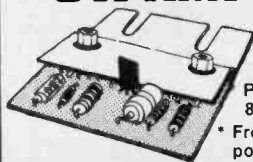

- \* Nominal 12-14V
- \* Distortion typically 0.5%
- Power output into 3 ohms = 5W, 8 ohms = 2W, 15 ohms = 1W
- \* Frequency response at 3dB points 10Hz to 30KHz

- \* Sensitivity (with/without tone control) 130mV
- \* Quiescent current 100mA \* Full power 3 ohms (650mA)

This matchbox sized amplifier will run satisfactorily from a 12V car battery. Can also be used for portable voice reinforcement such as public functions where mains supply is not accessible. A small mains unit is available. Two amplifiers are ideal for Stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders.

**Cheapest in the U.K. Built and tested.**

I enclose £..... for ..... amplifiers

Name .....

Address .....

# BI-PRE-PAK

Co. Regn. No. 820919

Dept. D, 222/224 West Rd., Westcliff-on-Sea, Essex, SS0 8DF

Tel: Southend (0702) 46344

## BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON S.W.17 01-672 3984

**CARTRIDGES**—Stereo Sonotone 9TA H/C Diamond £2.47, Ronette S105 Medium Output £1.40, S106 High Output £1.40, Acos GP93/1 Sapphire £1.95, GP94/1 Sapphire £1.95, Japanese equivalent to B.S.R. TC8s £1.80.

**CARTRIDGES**—Mono GP91 Stereo Compatible £1.29, B.S.R. TC8H Jap. equivalent £1.29.

**HI-FI STEREO HEADPHONES** Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms, frequency range 20-20,000 Hz 6ft. cord and standard stereo plug. Only £3.57.



**STEREO HEADPHONE JUNCTION BOX** Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 3 position switch to give headphones only, speakers only, speakers and headphones. Only £1.74.

**VYNAIR** Widths from 50 to 54in., 95p yd. off roll. 1/2 yard 57p. Send 5p stamps for samples. All prices inclusive of post and packing.

### AUTOMATIC EMERGENCY SUPPLY

250v 50Hz—150 watt inverter. Full kit of parts excluding meter. Circuit as appeared in December P.W. Complete kit—£16.95 + 80p P. & P.

### OTHER INVERTERS AVAILABLE IN KIT FORM

150 Watt—£13.50 + 60p P. & P. 75 Watt—£7.80 + 60p P. & P.  
300 Watt—£17.90 + 85p P. & P. 40 Watt—£5.20 + 40p P. & P.  
25 Watt—£2.60 + 20p P. & P.

All above operate from 12v. battery and give 250v.—50Hz. Output. 24 volt types are also available, alternative outputs or taps can be supplied. Transformers and/or Transistors can be supplied separately.

### SPECIAL OFFER

12v. Fluorescent lights, suitable for tents, caravans, houses or secondary lighting for factories, hotels, etc. 12 Inch—8 watt—£3.40 post paid. 21 Inch—13 watt—£4.20 post paid. Large discounts available for quantities.

### BATTERY CHARGER KIT

10 Amp Charge Current—£5.50+40p P. & P.  
(Consists of Transformer and Rectifiers.)

## ASTRO ELECTRONICS

6, BARNES ROAD, CHESTERFIELD, DERBYSHIRE



Another  
winner!

# fane MODE ONE

# HIGH FIDELITY LOUDSPEAKER KIT



Recommended  
retail price

**£9.39**

including V.A.T.

Please  
send S.A.E  
for fully  
descriptive  
leaflet.

Consisting of a Fane Model 803 ultra-low resonance 8" speaker unit with PVC cone surround, and a Fane Model 303 high frequency pressure tweeter together with a printed circuit cross-over assembly with ferrite cored coils.

**SPECIFICATION OF UNITS**

	Model 803	Model 303
Overall Diameter	8"	3"
Natural resonance	30Hz	—
Main resonance	*35Hz	1200Hz
Magnet Pole Diameter	1"	3/4"
Magnet Flux Density	13,000 gauss	10,000 gauss
Frequency response	30Hz-8kHz	10kHz-17kHz
Impedance	8-15 ohms	8-15 ohms
Power Handling	*15 watts	*15 watts

Very easy to assemble, this boxed kit comes with acoustic foam damping material, panels, screws, wire, wiring diagrams and instructions to provide a remarkable loudspeaker assembly—a pair is ideal for stereo.

CABINETS for the 'Mode One' are available in Teak veneer finish. SIZE 15 1/2" x 10 1/2" x 9".

\*When used with above cabinet.

Distributors to the wholesale  
and retail trade  
**LINEAR PRODUCTS LTD.**  
Electron Works, Armley, Leeds  
LS12 3SA. Tel. 630126

Manufactured by  
**FANE ACOUSTICS LTD.**  
Hick Lane, Batley, Yorkshire.  
Tel. Batley 6431

**G. F. MILWARD** 369 Alum Rock Road, Birmingham B8 3DR.

Tel. 021-327 2339

<p><b>TRANSISTORS</b></p> <p><b>Output Transistors</b></p> <p>BD 112 .. 25p OC 36 .. 50p BD 145 .. 25p</p> <p><b>Small Signal N.P.N.</b></p> <p>BC 108 .. 10p BC 109 .. 10p BF 194 .. 10p</p> <p><b>Transmitting Types</b></p> <p>BFR 64 .. £1 BKY 89A .. £5 BLY 93A .. £9</p> <p><b>Microwave Varactor Diodes</b></p> <p>BXY 27/28/32/35/36/37/38/39/40/41 .. £1</p> <p><b>Microwave Detector</b></p> <p>CAY 10 .. £5</p> <p><b>Microwave Mixer</b></p> <p>CL 7331 .. £20</p> <p><b>Microwave Gunn Effect Oscillator</b></p> <p>CL 8370 .. £10 CL 8380 .. £10 CL 8390 .. £10 CL 8470 .. £40</p> <p><b>Microwave Tunnel Diodes</b></p> <p>AEY 13 .. £5 AEY 18 .. £10</p> <p><b>R.F. Transistors</b></p> <p>BF 180 .. 20p BF 194 .. 10p AF 124 .. 20p</p>		<p><b>Field Effect Transistors</b></p> <p>BFW 12/13/14 .. 25p</p> <p><b>Micro-miniature N.P.N.</b></p> <p>BFS 16R .. 10p LDA 400/403/480/482 .. 10p</p> <p><b>Infra-red Transmitters</b></p> <p>CQY 11A .. £4 CQY 12A .. £10</p> <p><b>Light-sensitive Trans.</b></p> <p>OCF 70 .. 20p</p> <p><b>Complementary Drivers, 2 watts (per matched pair) 30p. a pair.</b></p> <p><b>INTEGRATED CIRCUITS</b></p> <p>TBA 500 Luminance I.C. .. £1 TBA 510 Chrominance I.C. .. £1 FEQ 101 84bit Memory .. £1</p> <p>7401 .. 12p 7410 .. 12p 7420 .. 12p 7440 .. 12p 7453 .. 12p 7470 .. 84p 7472 .. 84p 7473 .. 52p 7474 .. 32p 7482 .. 88p 7483 .. 88p 7490 .. 52p 7491 .. 74p 7492 .. 84p 7493 .. 88p 7495 .. 88p 5400 .. 10p 6404 .. 10p</p>		<p><b>NEW! NEW! NEW! NEW!</b></p> <p>An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.</p> <p>Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.</p> <p>Light sensitive aerosol spray .. £1.00 plus Developer and Etchant .. 50p postage</p> <p><b>NEWER THAN NEW! I</b></p> <p>Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.</p> <p>75 mm x 100mm .. 33p 150mm x 100mm .. 66p 150mm x 200mm .. £1.32</p> <p><b>Epoxy-Resin</b></p> <p>75mm x 100mm .. 22p 100mm x 150mm .. 44p 150mm x 200mm .. 88p</p> <p><b>Copper-clad Fibre Board</b></p> <p>12in x 6in .. 45p</p> <p><b>Copper-clad Epoxy Resin Board</b></p> <p>12in x 6in .. 25p</p> <p><b>MULLARD POLYESTER CAPACITORS</b> 500,000 in STOCK!!!</p> <p>.001µf .0018µf .0058µf .015µf .012µf .0022µf .01µf .033µf .0015µf .0027µf .012µf .082µf</p> <p>20p dozen; 75p-100; £5-1,000; £40-10,000 15µf .15µf .22µf .39µf .68µf 20p dozen; £1-100; £5-50-1,000; £50-10,000</p>		<p><b>VEROBOARD</b></p> <p>2 1/2in x 1in x 0.15in .. 6p 3 1/2in x 2 1/2in x 0.15in .. 16p 3 1/2in x 3 1/2in x 0.15in .. 20p 5in x 2 1/2in x 0.15in .. 20p 5in x 3 1/2in x 0.15in .. 28p 17in x 2 1/2in x 0.15in .. 55p 17in x 3 1/2in x 0.15in .. 74p 3 1/2in x 2 1/2in x 0.1in .. 21p 3 1/2in x 3 1/2in x 0.1in .. 24p 5in x 2 1/2in x 0.1in .. 23p 5in x 3 1/2in x 0.1in .. 28p</p> <p>Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0.1 or 0.15) 36 for 18p. Special Offer Pack consisting of 8 2 1/2in x 1in boards and a Spot Face Cutter—50p. "ODDS &amp; ENDS"—1p sq in.</p> <p><b>ERIE MONOLITHIC CERAMIC CAPACITORS</b> 3p each; 20p dozen; £1-75 per 100</p> <p>10pf 68pf 560pf 15pf 100pf 820pf 22pf 150pf 680pf 33pf 220pf 1,000pf 39pf 330pf 47pf 470pf</p>	
<p><b>£1</b> 100 1/2 WATT RESISTORS 100 CERAMIC CAPACITORS 100 DIODES</p> <p>POSTAGE 15p      PACK No. 1</p>	<p><b>£1</b> 1 VERO-BOARD CUTTER 8 2 1/2 in. x 1 in. x .15 BOARDS 50 SQ. INS. "ODD PIECES" VERO</p> <p>POSTAGE 15p      PACK No. 3</p>	<p><b>£1</b> 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BCT108 ETC.</p> <p>POSTAGE 15p      PACK No. 5</p>	<p><b>£1</b> 8 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS &amp; CAPACITORS</p> <p>POSTAGE 25p      PACK No. 7</p>				
<p><b>£1</b> 100 RESISTORS 100 CERAMIC CAPACITORS 100 POLYSTYRENE CAPACITORS</p> <p>POSTAGE 15p      PACK No. 2</p>	<p><b>£1</b> 100 RESISTORS 100 CERAMIC CAPACITORS 50 MULLARD POLYESTER CAPACITORS</p> <p>POSTAGE 15p      PACK No. 4</p>	<p><b>£1</b> 1 TRANSISTORISED SIGNAL TRACER KIT 1 TRANSISTORISED SIGNAL INJECTOR KIT</p> <p>POSTAGE 15p      PACK No. 6</p>	<p><b>£1</b> 100 RESISTORS 100 CAPACITORS (ASSORTED TYPES)</p> <p>POSTAGE 15p      PACK No. 8</p>				
<p><b>POSTAGE (MINIMUM) 15P PER ORDER</b></p>				<p><b>ALL GOODS PLUS 10% V.A.T.</b></p>			

### TRANSISTORS, ZENER DIODES etc.

**Fully guaranteed  
Individually packed  
VALVES**

B19H	£1.75	ECB84	40p	OA2	30p	OCT1	12p	IN823A	£1.30	3N154	95p	BC108	10p	GET115	45p
CY31	31p	ECH200	56p	OB2	30p	OCT2	80p	IN4785	50p	3N159	£1.45	BC113	10p	GET115	50p
DAF98	40p	ECL80	38p	PABCSO	38p	OCT7	80p	OZM75	35p	9F85	20p	BC118	20p	GEX66	£1.50
DF96	40p	ECL82	31p	PC87	41p	OCT8	25p	OZM10	32p	12FR60	78p	BCY73	15p	NKT222	20p
DK95	48p	ECL86	38p	PC84	36p	OA73	7p	OC76	25p	IZT5	67p	BF115	25p	NKT304	50p
DL94	40p	EKF30	40p	PC89	45p	OA74	7p	OC81	20p	IZT10	63p	BF173	20p	RA5310AF	
DL98	40p	EKF37A	£1.15	PC8189	49p	OA79 (6D15)	10p	OC81D	20p	2G385	51p	BFY51	20p	SD915	28p
DM70	27p	EKF40	40p	PC8760	75p	OC81DM	20p	2G403	61p	40688	£1.25	BFY52	20p		
DY86	29p	EKF41	75p	PC8780	25p	OC82	20p	2N918	37p	40689	£1.40	BFY59	20p		
DY87	28p	EKF80	22p	PC892	41p	OC82DM	30p	2N918	37p	40692	25p	BFY59	20p		
DY802	48p	EKF83	49p	PC864	54p	OC83	25p	2N1306	25p	AD127	25p	BSY29	25p		
EB8CC/01	£1.06	EKF85	31p	PC8760	40p	OC83B	15p	2N1307	25p	AC128	20p	BU100	£1.30		
EB8CC	37p	EKF85	27p	PCF201	60p	OC84	25p	2N1241	£1.50	AC176	20p	BZ13	25p		
E180CC	90p	EKF89	25p	PCF801	40p	OC84	20p	2N1241	£1.50	AC176	20p	BZ16	25p		
E181CC	90p	EKF91	27p	PCF802	45p	OC86	25p	2N2904A	25p	AC178	20p	BZ16	25p		
E182CC	£1.08	EKF95	31p	PCF805	80p	OC88	48p	2N2989	£4.00	AD149	35p	CRS1/10	25p		
EA50	18p	EKF183	28p	PCF808	60p	OC88	48p	IN25	60p	AD181	35p	CRS1/20	35p		
EA8C80	27p	EKF184	31p	PCF806	60p	OC92	50p	IN43	10p	AD181	35p	CRS1/35	45p		
EAF42	46p	EKF184	31p	PCF808	60p	OC92	50p	IN70	7p	AD181	35p	CRS1/40	48p		
EB91	16p	EKL34	45p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/05	30p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/10	35p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/15	35p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/20	38p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/30	45p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/35	48p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/40	50p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/45	52p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/50	55p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/55	58p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/60	60p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/65	62p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/70	65p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/75	68p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/80	70p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/85	72p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/90	75p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS3/95	78p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/00	80p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/05	82p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/10	85p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/15	88p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/20	90p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/25	92p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/30	95p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/35	98p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/40	100p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/45	102p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/50	105p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/55	108p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/60	110p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/65	112p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/70	115p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/75	118p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/80	120p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/85	122p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/90	125p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS4/95	128p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/00	130p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/05	132p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/10	135p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/15	138p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/20	140p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/25	142p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/30	145p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/35	148p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/40	150p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/45	152p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/50	155p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/55	158p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/60	160p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/65	162p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/70	165p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/75	168p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/80	170p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/85	172p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/90	175p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS5/95	178p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/00	180p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/05	182p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/10	185p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/15	188p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/20	190p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/25	192p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/30	195p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/35	198p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/40	200p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/45	202p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/50	205p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/55	208p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/60	210p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/65	212p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/70	215p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/75	218p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/80	220p		
EB91	16p	EKL41	47p	PCH200	60p	OC98	25p	IN77	12p	AD181	35p	CRS6/85</			



**MAINS MOTOR**  
Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 75p. Postage 20p for first one then 10p for each one ordered.

**MUSIC ON TAPE**

A further buy enables us to offer these at an even lower price—namely 65p each or 5 for £2.50. Send for list of titles. We can't repeat when sold out.

**BALANCED ARMATURE UNIT**

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits, 37p each, 10 for £3.85.



**CAR ELECTRIC PLUG**

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system, 48p each or 10 for £3.76.



**12 VOLT 11 AMP POWER PACK**

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price £8.80, plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps — maximum load 250W—that is from 5 amp at 40V to 15amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £6.33 plus 65p post.

**MAINS RELAY BARGAIN**

Special this month are some single, double pole change-over relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. Good British Make. Unused. Size approx. 1 1/2" x 1". Open construction.

Single pole 25p each 10 for £2.48  
Treble pole 35p each 10 for £3.67



**MINIATURE WAFER SWITCHES**

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 2 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 25p each.

**CONNECTING WIRE**

7-0078 Copper conductors. 500 metre drums available in the following colours:—Red/Brown—Yellow—Green/Grey—Blue/Green—Red/Orange—Green/White—Grey/White—Blue/Orange—Brown/Red—Brown/White—Red/Grey—Blue/Grey—Blue/Brown. Price £2.90 per drum plus 40p post. State alternative colours. Ditto—but with 200 metres. Price £1.38 per drum plus 20p. Ditto—but with 100 metres. Price 83p per drum.

**DOOR SWITCH**

As fitted to refrigerators, etc. Switches off as door closes. White 17p each. Black 15p each.

**GOODMANS P.M. SPEAKERS**

8" x 6" hi flux 15 ohm coil very suitable for use with Mullard Unilux stereo amplifier or with the EP9000 on it's own. £1.65 plus 20p post each.

7" x 4" also 15 ohm and suitable for use with the EP9000—not quite such good quality of course. Price £1.05 each.

**SOIL HEATING KIT**

Suitable for garden frame or propagating shelf, etc. Comprises 40 watt mains transformer, heating wire, connection strip and insulated wire with connection diagram. £1.65 plus 20p post.

**DOUBLE ENDED MAINS MOTOR**

This is a very quiet running induction motor, with two special features—one is that it has feet for easy fixing and the other is it has a good length of spindle coming from each end. So it could drive two things at once—or with simple slide attachment could reverse direction. 55p each or 10 for £4.95.

**U.V. LIGHTING**

Useful for flaw detection in metals and for looking for water marks, etc., also for fitting over tropical fish tanks. African plants and other indoor plants which must have U.V. for healthy growth. The outfit comprises of a 12" U.V. tube—choke—starter holder and tube ends. Price £2.20 plus 20p post.

**80 WATT TUBULAR ELEMENTS**

Brass encased with beaded flex ends. Standard replacements in most absorption refrigerators but also has dozens of other uses. 28p each or 10 for £1.48.



**MULLARD AUDIO AMPLIFIERS**  
All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 500mW power output 75p. Model 1172 750mW power output 84p. Model EP9000 4 watt power output £1.60. EP9001 twin channel or stereo pre amp. £1.98 10% discount if 10 or more ordered.


**CENTRIFUGAL BLOWER**

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet, or for removing flux smoke when soldering etc., etc. A real bargain at £9.05.



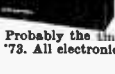**GOOD COMPANION I.C. VERSION**

We can now offer this again in I.C. version using Ferranti ZN414 and Mullard AF Module 1172. Cabinet size approx. 11in. wide x 8in. high x 3in. deep. Complete assembly instructions—Excellent tone wood cabinet £5.75 + 25p post & ins.



**MIGHTY MIDGET**

Probably the tiniest possible radio, as described in Practical Wireless, January '73. All electronic parts £2.20 post paid.


**THIS MONTH'S SNIP**

**HORSTMAN 24 HOUR TIME SWITCH**

With 6 position programmer. When fitted to hot water systems this could programme as follows:—

0	Off	00	Central Heating
1	Twice daily	01	
2	All day	02	
3	Twice daily	03	Twice daily
4	All day	04	All day
5	Continuously	05	Continuously

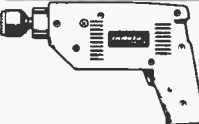Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated—Size 3" x 3" x 2" deep—Price £3.85 each. As illustrated but less case.



**PORTABLE ELECTRIC DRILL**

Very superior quality made by a famous Dutch Toolmaker. Model No. ASM 830 300w - 2 speed 2200/3000. With 1/2" chuck and chuck key, also separate side handle and hammer facility for dealing with concrete, etc. An equivalent British made drill would cost £15-00. £10-90—similar model but without the hammer attachment £8.76. Have either model on approval for 7 days.



**DISTRIBUTION PANELS**

Just what you need for work bench or lab. 4 x 18 amp. sockets in metal box to take standard 13 amp. fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2.60 plus 20p post and ins.


**CAPACITOR DISCHARGE CAR IGNITION**

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for an improved and even more efficient version (Practical Wireless, June). Price £2.55 plus 20p post. When ordering please state whether for positive or negative systems. De-luxe model including printed circuit board etc. £7.85.



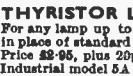**24-HOUR TIME SWITCH**

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. £2.75 post and ins. 25p. Additional time contacts 55p pair.



**THYRISTOR LIGHT DIMMER**

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2.95, plus 20p post and insurance. Industrial model 5A £2.30.

**BATTERY CONDITION TESTER**

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—nicad—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prods. Price £2.48 plus 20p postage.

**SPIT MOTOR**

200-250v Induction Motor, driving a carter gear box with 1 1/2" of output drive shaft running at 5 revs per minute. Intended for roasting chickens, also suitable for driving models—windmills, coloured disc lighting effect, etc. etc. £2.04 plus 20p post and insurance.

**TERMS:** 10% discount if ten of an item ordered, send postage where quoted—other items, post free if order for these items is £6.00 otherwise add 80p.



**DRILL CONTROLLER NEW IKW MODEL**

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.65. 15p post and p. Made up model also available. £3.75.

**MAINS TRANSISTOR POWER PACK**

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PPI, PPS, PPA, PFB, PFT, PPO, and others. KIT comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real amp only £1.10.

**SWITCH TRIGGER MATS**

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24" x 18" £1.54  
18" x 10" £1.10

**PP3 BATTERY CHARGER**

Almost 3 times the life can be obtained from PP3 battery if you recharge from the mains—this ready to use charger with instructions only 55p.

**15A ELECTRICAL PROGRAMMER**

Learn in your sleep: Have radio playing and kettle boiling as you awake switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.15 + 20p p. & p. or with glass front, chrome bezel, 83p extra.

**BAKELITE INSTRUMENT CASE**

Size approx. 8 1/2" x 3 1/2" x 2" deep with brass inserts in four corners. This is a very strong case suitable to house instruments and special rigs, etc. Price 60p each. Pixolin lid 11p extra.

**ROCKER SWITCH**

18 amp self-fixing into an oblong hole. Size approximately 1" x 1 1/2" 9p each, 10 for 81p.

**THERMAL CUTOUT**

A miniature device 3/4" dia. on one screw fixing mount—can be used for motor overload protection—fire alarm—soldering iron—switch off, etc., etc. 15 amp contacts open with flame—radiant or conducted heat. 11p each or 10 for 99p.

**HONEYWELL PUSH BUTTON MICRO SWITCHES**

As used in some vending machines, etc. Each switch is a change-over type rated at 15 amps 250V A.C. Intended for panel mounting with fixing nuts and single black push knob. Single change-over switch 28p. Double switch 42p. Triple switch 61p.

**KETTLE ELEMENTS**

Made by the famous A.E.I. Co. Complete with washers and combined fixing ring and plug around. Normal 2 round pin and flat pin earth connection and overload reset push button. 2 Models—1 1/2" (approx.) suitable for Swan and other similar models—1 1/4" (approx.) suitable for G.E.C., Hotpoint, etc. All quick bolt 2 1/2 Kw elements at 240v. Price £1.38 each.

**MAINS TRANSFORMER BARGAIN**

Standard mains 240v input Secondary 1.4v 9 amp intermittent 5 amp continuous. Price 55p.

**BULGIN 4 PIN PLUG & SOCKET**

Plug has shielded pin and flex entry and socket for panel mounting. 83p per pair. Ditto—but 3 pin—28p per pair.

**MACLAREN THERMOSTAT**

Make and break 20 amp A.C. with the sensor probe coupled by 2 feet capillary covering range of 10—100cc—complete with large engraved control knob. Price 83p.

**J. BULL (ELECTRICAL) LTD.**  
(Dept. P.W.) 7 Park Street, Croydon CRO 1YD  
Callers to: 102/3 Tamworth Road, CROYDON

# Sinclair Project 60

## Now—the Z.50 Mk.2

with built-in automatic transient overload protection

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symmetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50; circuitry has been re-designed, making this versatile high performance amplifier better than ever.



with free manual  
£4.48

### Z.30 the power amplifier for quality and economy



with free manual  
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm (3 1/8 x 2 1/4 x 1/2). Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.


### Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you. If it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.
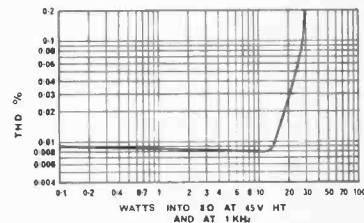
### Brilliant new technical specifications

Input impedance 100 K $\Omega$   
Input (for 30w into 8 $\Omega$ ) 400mV  
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better  
Distortion 0.02% up to 20W at 8 $\Omega$ . See curve  
Frequency response 10Hz to more than 200 KHz  $\pm$  1dB  
Max. supply voltage 45v (4 $\Omega$  to 8 $\Omega$  speakers) (50v 15 $\Omega$  speakers only)  
Min. supply voltage 9v  
Load impedance — minimum: 4 $\Omega$  at 45v HT  
Load impedance — maximum: safe on open circuit



## Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

# sinclair

SINCLAIR RADIONICS LTD., R.O. London Road, St. Ives, Huntingdonshire, PE17 4HJ (Phone St. Ives 4311) Reg. No. 699483 England

# the world's most advanced high fidelity modules

## Stereo 60 Pre-amp/control unit




Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

**SPECIFICATIONS—Input sensitivities:** Radio — up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A. curve  $\pm 1$ dB: 20 to 25,000 Hz. Ceramic p.u. — up to 3mV. Aux — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE  $\pm 12$  to  $-12$ dB at 10KHz. BASS  $\pm 12$  to  $-12$ dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed. **£9.98**

## Power Supply Units The new PZ.8 Mk.3

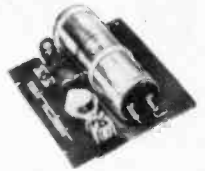

The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage—45.

PZ.8 Mk.3—£7.98

(Mains transformer, if required) £5.98

PZ.5 30v. un stabilised

(not suitable for Project 60 tuner) £4.98

PZ.6 35v. stabilised

(not suitable for IC. 12) £7.98

## Project 60 Stereo F.M. Tuner




The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

**SPECIFICATIONS—Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz **Sensitivity:** 7 $\mu$ V for lock-in over full deviation. **Squelch level:** Typically 20 $\mu$ V. **Signal to noise ratio:** >65dB. **Audio frequency response:** 10Hz — 15KHz ( $\pm 1$ dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 $\mu$ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum **Operating voltage:** 25—30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**
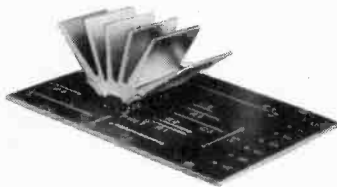
## Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

### SPECIFICATIONS

**Output power:** 6 watts RMS continuous (12 watts peak). 6—8 $\Omega$ . **Frequency Response:** 5Hz to 100KHz  $\pm 1$ dB. **Total Harmonic Distortion:** Less than 1%. (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

**£2.98** Post free

## Project 605



the easy way to  
buy and build  
Project 60  
without  
soldering

Project 605 in one pack contains: one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free

**£29.95**

All you need for a superb 30 watt high fidelity stereo amplifier

## Order form

Please send

enclose cash/cheque/money order.

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

PW7  
SINCLAIR RADIONICS LTD., R.O. London Road,  
St. Ives, Huntingdonshire, PE17 4HJ

**sinclair**

ADD 10% V.A.T. ON PRICES ON PAGE OPPOSITE AND ABOVE

# Practical Wireless Classified Advertisements

## Aerials

**BAINES for High Frequency Aerials**  
 UHF Multibeams by J. Beam  
 MBM 10 £2-40 MBM 18 £3-19 MBM 30 £4-29 MBM 46  
 £5-60 MBM 70 £11-00 Aerial Rotator £22-00  
 FM for Mono or Stereo  
 Dipole £1-54 FM/H £2-20 FM 3 £3-30 FM4S £6-10  
 FM6S £8-58  
 Masthead Amplifiers by SAC  
 Single stage £6-60 Two stage £8-80 Wideband £7-70  
 Co-ax 5p and 9p. Postage paid on all items except  
 accessories for which a SAE will bring full details.  
 VAT included on all above.  
 11 Dale Cres Tupton Chesterfield S42 6DR—  
 Telephone 863755

## Service Sheets

**SERVICE SHEETS, Radio, TV etc.,**  
 8,000 models. Catalogue 15p. S.A.E.  
 enquiries. Telray, 11 Maudland Bank,  
 Preston.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS,  
 RECORD PLAYERS, TRANSISTORS,  
 STEREOGRAMS, RADIOGRAMS,  
 CAR RADIOS)  
 Only 40p each

**PLEASE ENCLOSE LARGE S.A.E.**  
**WITH ALL ENQUIRIES & ORDERS**  
 Otherwise cannot be attended to

(Uncrossed P.O.'s please, original  
 returned if service sheets not available.)

**C. CARANNA**  
 71 BEAUFORT PARK  
 LONDON, N.W.11

We have the largest supplies of Service  
 Sheets (strictly by return of post). Please  
 state make and model numbers alternative.

Free TV fault tracing chart or TV list on  
 request with order.

Mail order or phone 01-458 4882

**SERVICE SHEETS for Televisions,**  
**Radios, Transistors, Tape Recorders,**  
**Record Players, etc., from 5p with free**  
**Fault-Finding Guide. S.A.E. orders/**  
**enquiries. Catalogue 15p. Hamilton**  
**Radio, 47 Bohemia Road, St. Leonards,**  
**Sussex. Telephone Hastings 29066.**

## Books and Publications

### RadioBOOKS

Handbk of Transistor Equip and Substitutes	45p
Handbook of Tested Transistor Circuits	45p
Rad & Electr Colour Codes and Data Chart	20p
Hi Fi, PA & Disco Amplifier Design H.bk.	80p
Boys Bk of Crystal Sets and Simple Circuits	23p
How to make FM & TV Aerials, Bands 1,2,3	23p
Radio Servicing for Amateurs	45p
High Fidelity Loudspeaker Enclosures	45p
Practical Tape Recording Handbook	35p
Practical Stereo Handbook	35p
Practical Radio Inside Out	45p
Transistor Circuits Manual No. 1	20p
Transistor Circuits Manual No. 2	20p
Coil Design and Construction Manual	35p
Radio TV and Electronics Data Book	30p
Transis Circuits for Radio Controlled Models	45p
Pract Transistor Audio Amplifiers, Book 1	25p
Transistor Test Equip and Servicing Manual	30p
Handbook of Simple Transistor Circuits	40p
Modern Transistor Circuits for Beginners	45p
Sound and Loudspeaker Manual	55p
Resistor Colour Code Disc Calculator	15p
Manual Transistor Audio Amplifiers	45p
Practical Car Radio Handbook	35p
Radio TV and Industrial Tube & Valve Equip.	45p
Practical Transistor Novelty Circuits	45p
Television Servicing Vol. 1	95p
Television Servicing Vol. 2	95p
Television Servicing Vol. 3	70p
Television Servicing Vol. 4	95p
Using an Oscilloscope	80p
Servicing Transistor Radio Receivers	85p
Television Timebase Circuits	£1.10p
Pal-D Colour Receiver Questions & Ans.	78p

All prices include postage & packing  
 FREE lists of other titles avail on request. Send to:

**RADIO BOOK SERVICE**  
 40 Elwill Way, Beckenham BR3 2RZ

**DENCO CLACTON LIMITED**  
 355-7-9 Old Road  
 Clacton-on-Sea, Essex

Catalogue 20p post paid  
 S.A.E. All enquiries

**SHORT WAVE MAGAZINE, now in its**  
**36th year and published monthly,**  
**covers the whole field of Radio**  
**Amateur transmission and reception**  
**including regular news features (DX,**  
**VHF, Clubs and SWL) and the design,**  
**construction and operation of AMA-**  
**TEUR Radio equipment of every type.**  
**Cover price 25p at newsagents. Specimen**  
**copy 30p post free, first class.**  
**Annual subscription £3-00 (or £2-75**  
**second class posting) year of 12 issues.**  
**—Circulation Dept. (P.), Short Wave**  
**Magazine Ltd., 55 Victoria Street,**  
**London SW1H 0HF. (Tel: 01-222 5341/2)**

## TRANSISTOR DATA

### THE INTERNATIONAL TRANSISTOR DATA MANUAL

1973 EDITION is now ready. Data on upwards  
 of 18,000 transistors of international origin.  
 £5-25 plus 35p post & packing in the UK.  
 Brochure available. Order direct from

**SEMICON INDEX LTD.,**  
 Freepost, Wokingham, Berks. RG11 2AY.

**DIGITAL COMPUTER LOGIC and**  
**Electronics. Four volume self-instruc-**  
**tional course. £2-95 including p & p.**  
**Money back assurance. Cambridge**  
**Learning (PW), 8a Rose Crescent,**  
**Cambridge.**

## Wanted

**TOP PRICES PAID for NEW VALVES**  
 popular T.V. and Radio types.

**KENSINGTON SUPPLIES (C),**  
 367 Kensington Street, Bradford 8,  
 Yorkshire.

**WE BUY New Valves, Transistors and**  
**clean new components, large or small**  
**quantities, all details, quotation by**  
**return. WALTON'S, 55 Worcester**  
**Street, Wolverhampton.**

**WANTED: Third I.F. Transformer for**  
**Heathkit A.F.M.I Tuner. 18 St Ed-**  
**munds Road, Stowmarket, Suffolk.**

## Situations Vacant

**MEN!**  
**£50 p.w.**  
**can be yours**

Jobs galore! 144,000 new computer  
 personnel needed by 1977. With  
 our revolutionary, direct-from-  
 America, course, you train as a  
 Computer Operator in only 4 weeks!  
 Pay prospects? £2500 + p.a.  
 After training, our exclusive ap-  
 pointments bureau—one of the  
 world's leaders of its kind—intro-  
 duces you FREE to world-wide  
 opportunities. Write or phone  
 TODAY, without obligation.

**London Computer Operators**  
 Training Centre

**M99, Oxford House**

**9-15, Oxford Street, W.1.**

**Telephone: 01-734 2874**

**127, The Piazza, Dept. M99,**

**Piccadilly Plaza, Manchester 1.**

**Telephone: 061-236 2935**

## SERVICE SHEETS MANUALS BOOKS

**SERVICE SHEETS 40p plus S.A.E. ★ SERVICE SHEET CATALOGUE 20p**  
 OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS  
 RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

### NEW BOOKS & PUBLICATIONS

Fault Location Exercises in Radio & TV Servicing by K.J. Bohlman, Volume 1	£0.80
Fault Location Exercises in Radio & TV Servicing by K.J. Bohlman, Volume 2	£1.35
How to get the best out of your Tape Recorder, 3rd Edition by P.J. Guy	£1.50
HOW TO MAKE WALKIE-TALKIES for licensed operation by T.D. Zedd	£0.40
EASY WAY TO SERVICE RADIO RECEIVERS by L. Sands, 176 pages	£1.00
ELECTRONICS FOR THE BEGINNER by J.A. Stanley, 192 pages	£1.75
MECHANICS COURSE IN RADIO, TV & ELECTRONICS 222 (433)	
FIRST YEAR. Principles and Calculations by B. Fozard	£0.50
PART 1. Electronic Systems by G.N. Patchett	£0.85
PART 2. SECOND YEAR. Electronic Systems by G.N. Patchett	£0.95
PART 2. THIRD YEAR. Electronic Systems by G.N. Patchett	£2.00
TRANSISTOR SUBSTITUTION HANDBOOK 12th Edition, 176 pages, by H.W. Sams	£1.40

★ SPECIAL OFFER AT THE REDUCED PRICE OF £1.50 POST FREE ★  
 1972 EDITION OF "WORLD RADIO TV HANDBOOK" Usually £2.80.

NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good prices paid

Send large S.A.E. for FREE booklists and book pamphlets on Radio, Television & Electronics.

NOTE. Postage on all books is now 5p up to £1.00. Orders over £1.00 POST FREE. (UK only)

**BELL'S TELEVISION SERVICES**  
 ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844





# Your talent can earn you money!

## As a Radio Rentals T.V. Engineer

How's about combining your hobby with your work? You can you know—by joining Radio Rentals to be trained as a T.V. Engineer.

You'll certainly be working towards a better future with more chances of promotion, and have more opportunities to use your talents.

You'll be well paid, and qualify either for a company vehicle, or alternatively, a generous car

allowance.

What's more, you'll be working with one of the friendliest, and most successful T.V. Rental teams in the country. Radio Rentals, with more branches in the U.K. than any other firm.

There are vacancies in the London Areas now, to find out all details now ring **675 0191** and ask for **Mr J. Canning** or write to: **Mr J. Canning, Area Liaison Engineer, Radio Rentals, 83 High Road, Balham, S.W.12.**



# Radio Rentals

## Courses

### LAUNCH INTO A CAREER FROM YOUR HOBBY



Study for B.Sc. in **COMMUNICATION ENGINEERING** at **PLYMOUTH POLYTECHNIC** courses commence September 1973.



The Senior Registrar,  
Ref. EE(B),  
Plymouth Polytechnic,  
PLYMOUTH PL4 8AA.

## Educational

**RADIO, TV, RTEB Certs., City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit).** Thousands of successes. Details of home study courses and illustrated book—FREE. BIET (Dept ZL BPW 27), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

**CIE, AMSE, City & Guilds, etc.** Thousands of exam successes. Postal courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept ZL BPW 38), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

**GO TO SEA** as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

## Ladders

**LADDERS** 24½ ft £9.80. Carr 80p. (Please add 10% V.A.T. to total order). Leaflet. Home Sales Ladder Centre, (WLS) Haldane, Halesfield (1) North, Telford, Salop. Tel: 0952 586644.

## Receivers and Components

**TV LINE OUTPUT TRANSFORMERS** Tidman Mail Order Ltd., 236 Sandycombe Rd., Richmond, Surrey. TW9 2EQ. 01-948 3702.

**ELEVEN BAND RADIO. SW1-4 (4-30 MHz).** Marine, LW, MW, FM, PB (76-86). Aircraft (108-136). PB (148-174). Battery/Mains. BFO. AGC. Squelch Control. Output: 1-3W. 15in x 10in x 5½in, £66. Eight Band Model, with BFO, £42. Four Band, MW, FM. Aircraft. PB. £15. SAE. Full Lists. Langtons Radio, High Street, ROCESTER, Staffordshire, Tel. 388.

**TAPE-HEAD** reconditioning service. Guaranteed satisfaction. Send worn head with £2 to: Sara Electronics, Fawkham Avenue, Longfield, Kent.

**STAND AND INSPECTION** magnifiers, ideal for the inspection of printed circuits, etc. S.A.E. for list from Revor Optical, 36 Baker Street, London W.1.

## TAPE HEADS

Send stamp for lists.  
**R.D.I. Ltd.**  
Chilton Works,  
Garden Rd.,  
Richmond,  
Surrey,  
TW9 4NS

For valve and transistorized recorders from £2 ea.

## PRECISION

### POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.

0.47µF: ±5% 80p: ±2% 40p: ±1% 50p  
1.0µF: ±5% 40p: ±2% 50p: ±1% 60p  
2.2µF: ±5% 50p: ±2% 60p: ±1% 75p  
4.7µF: ±5% 70p: ±2% 90p: ±1% 81-15  
6.8µF: ±5% 90p: ±2% 81-15: ±1% 81-60  
10µF: ±5% 81-15: ±2% 81-60: ±1% 81-80  
15µF: ±5% 81-60: ±2% 88-10: ±1% 88-70

### TANTALUM BEAD CAPACITORS

Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (78 capacitors) £5.

**NEW—TRANSISTORS. BC107, BC108, BC109.** All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178—35p each or 3 for £95p.

**POPULAR DIODES IN914—7p each, 8 for 50p; 18 for £1. IN916—9p each, 6 for 50p, 14 for £1. IS44—5p each, 11 for 50p, 24 for £1.** All brand new and marked.

**NEW LOW PRICE—400 mW Zeners** Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5 mA. All new and marked. Price 9p each, 6 for 50p, 14 for £1.00 Special offer 6 off each voltage (66 zeners) £4.25

**RESISTORS.** Carbon film ½W 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 9p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

**440V A.C. CAPACITORS.** 0.1µF, size 1½in x ½in, 25p; 0.25µF, size 1½in x ½in, 30p; 0.47 and 0.5µF, size 1½in x ½in, 35p; 1.0µF, size 2in x ½in, 45p; 2.0µF, size 2in x 1in, 75p each.

**SILICON PLASTIC RECTIFIERS 1.5 Amp** Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

5p post and packing on all orders below £5. Please add 10% VAT to all orders. **MARCOTRADING** (formerly V. Attwood) Dept. W.6, The Maltings, Station Road, Wem, Salop

### 5-N-CHANNEL FETs 3819E—£1

Full specification devices complete with data and circuit details for building voltmeter, timer, ohmmeter, etc. Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

### REDHAWK SALES LIMITED

45 Station Road, Gerrards Cross, Bucks. Mail Order only

**MINI MAINS PACK KIT.** Safe double wound mini transformer, silicon rects., 1000µF smoothing. Delivers 9V d.c., 120mA. Components with data sheet; pack buildable to size of PP6 etc. battery. £0.90+U.K. post 5p. By mail only from **AMATRONIX LTD.**, 396 SELSDON RD., SOUTH CROYDON, SURREY, CR2 0DE.

# Trompus electronics

ALL BRAND NEW, no rejects. Money back warranty. 5V DIGITAL INDICATOR. 0-9DP socket and filter £1.45. LED TYPE 4" 0-9DP DIL \$2.25 ea. LIGHT EMITTING DIODES. All with data and panel clip. TIL 209 1/4" dia 28p. Red 1" dia type 33p. Green 75p. INFRA RED beam LEO £1.10. T68 GAS detector £1.69. ULTRA-SOUND TRANSDUCERS \$2. DALO PCB resist marking pen 60p. Copper board 12" x 6" \$RBP 40p. FeC etch PAK 13p. INTEGRATED CIRCUITS: with data if required. IC LITE SWITCH: Photo amp/trigser 40ma / 11-20 relay or TTL 87p. Dll relay £1.10.



## IC digital clock

MOS/LSI type 28 pin 4 or 6 digit 12/24 hr. Chip with socket £18. PCB £1.69. KIT \$21.49. 741 Dll 8 pin 28p, 709 14p, Dll 28p, 748 39p, 710 88p. 555 TIMER mono/astable osc. clock 93p. REGULATORS: 11A 5 to 20V £1.49. 723 57p.

RECEIVER ZN414 £1.19. 2nd Rn kit £1.99. 1310 stereo decoder for tuner \$2.69. Kit \$3.45. 74N TTL: Gates 7400 etc. 14p ea. 7413 97p. 7441 73p. 7447 £1.09. 7490 59p. 7492 67p. 74121 45p. DIL SOCKETS: lo or hi profile 8/14/16 pin 13p. SEMICONDUCTORS 2N3055 40p. BC107 8p. BC108 8p. BC109 8p. BC147/8/9 10p. BC167/8/9 13p. BC177/8/9 15p. BC182/3/4 10p. BC212/3/4 11p. BCY70/72 13p. BD131/2 55p. BFY50/51/52 13p. T1848 UJT 24p. 2N706 11p. 2N2869 15p. 2N2928 0/5p. 2N2846 49p. 2N3053 17p. 2N3614 55p. 2N3702/3/4/5/6/7/8/9/10/11 All 8p ea. FETS: 2N3819 27p. 2N3823 28p. SCR 400V 1A 23p. 4A 55p. TRANSFORMER: 1A 6 & 12V £1. CAPACITORS: Disc 22pf to 0.1µf 4p. 25V electrolytic 10, 50, 100 µf 5p. 1000 µf 15p. PRESETS 5p ea. RESISTORS 1/4W. 5% 11p ea. CARBON POTS 12p ea. Dual 40p. Switch + 12p.

**FLUORESCENT LIGHTS 12VOLT £2.79**  
13" 8 watt fully built with diffuser.



## TRIO

All TRIO equipment available i.e. 9R-5908 Rx \$49.50. JR310 Rx. \$75. Also CODAR gear PR40 \$5.90. Multiband Rx kit £18.20. CR70A Rx \$27.50. V.A.T. You must add 10% (1/10) to all prices. FREE CAT. S.A.E. Data sheets. 8p ea. P.&P. 8p CWO. P.O. BOX 29, BRACKNELL, BERKS.

## COMPUTER PANELS

Type A: 4 Mullard OC35, 4 GET103 etc. 50p (5p). Type B: 3 Mullard OC30 on heat sink, 3 OC78, 6 OC42 etc. 40p (5p). Type C: 2 Mullard OC35, 2 OC78, 6 OC42 etc. 80p (5p). Type D: 4 Mullard OC38, 8 GET103 etc. 60p (5p). One of each £1.50 (10p). Parcel of 12 high quality panels, including power transistors, I.C.'s, trim pots etc. only £2 (30p). 7lb of lower quality £2 (40p).

## CASED AMPLIFIERS

2 x ECC83, EL84, EZ80 valves on 12 x 5 x 3" chassis in 14 x 13 x 9" cabinet with 7 x 4" 3Ω speaker and non-standard single motor tape deck. Tested with circuit £2 (£1 up to 250 miles, £1.25 over). Suitable Cassettes £1 (25p). Spare tape heads 40p.

## 7lb BARGAIN PARCELS

Contains hundreds of components—resistors, capacitors, pots, switches, xtals, P.C. boards, tag strips, lots of odds and ends. Amazing value at £1.85 (35p).

Ferric Chloride, 1lb 40p (15p); 10lb \$3.50 (50p). BC107-9 5p. 12 3055 8p. 7413 8 pin DIL or TO99 28p. 10 + 25p; Resistor Packs: 350 Carbon 60p (15p), 100 1 & 2% Hi-stabs 60p (5p), 150 Mixed Capacitors 60p (15p).

## GREENWELD (PW2)

24 Goodhart Way, West Wickham, Kent. Shop at 21 Deptford Broadway S.E.8 (next to old cinema). 01-692 2002. SAE list, enquiries. Post in brackets, small parts 3p. All prices exclude V.A.T.

## U.K. ORDERS—ADD VAT TO TOTAL

MICROCIRCUITS: 709 28p; 710 36p; 723 57p; 741 32p; 748 37p; PA230 70p; SL402A £1; FET Op. Amp. £1.62. TRANSISTORS: 2N696 14p; 2N697 14p; 2N706A 11p; 2N1613 16p; 2N1711 16p; 2N2218 19p; 2N2219 19p; 2N2219A 19p; 2N2904 17p; 2N2926 RED 6p; ORANGE 7p; YELLOW 8p; GREEN 9p; 2N3053 15p; 2N3055 40p; 2N3055 35p; 2N3702 10p; 2N3703 10p; 2N3704 10p; 2N3705 9p; 2N3706 9p; 2N3709 8p; 2N3710 9p; 2N3711 9p; 2N4058 12p; 2N4059 9p; 2N4061 11p; 2N4062 11p; AC107 28p; AC126 12p; AC127 12p; AC176 15p; ACY17 23p; ACY21 17p; AF114 14p; AF115 14p; AF116 14p; 2N3055 40p; AF124 22p; BC107A 8p; BC109B 8p; BC109C 8p; BC125 14p; BC147A 9p; BC167A 10p; BC168B 9p; BC169B 10p; BC177 13p; BC178 12p; BC179 16p; BCY70 13p; BCY71 22p; BD142 35p; BF115 26p; BF194 13p; BFX29 24p; BFX84 20p; BFX86 15p; BFX87 24p; BFX88 15p; BFY50 15p; BFY51 15p; BFY52 15p; BL47A 40p; BX20 12p; OC44 12p; OC45 12p; OC71 12p; OC72 12p; OC81 18p; OC83 24p. ME SERIES AVAILABLE. RECTIFIERS: 1 amp—50V 3p; 100V 4p; 200V 4p; 400V 5p; 800V 6p; 1,000V 7p. ZENERS BZY88 SERIES: 2-7V to 33V, 8p each. DIODES: IN916 4p; OA90 6p; OA200 7p; OA202 8p. SCR IR122Z (400V 5A) £1.14. LED PANEL LAMP with Bush and Data 28p. CARBON FILM 1/4W. 5% RESISTORS: £12 values 22Ω to 2.2MΩ 1p each or 7p per 10 of ONE VALUE. DALO ETCH RESIST FILLED FIBRE TIP PEN 80p. MINIATURE METAL GLAZE RESISTORS 1/4W 5% 4p each. 1kΩ THERMISTOR 9p; 2N3819 26p. MEF104 22p. TESTED TRANSISTOR CIRCUITS BOOKLET 40p. ITT POCKET MULTIMETER, 27 ranges, £17. (Above prices on April 16th. Check our list.)

**JEF ELECTRONICS (P.W.7)**  
York House, 12 York Drive, Grappenhall, Warrington WA2 2EJ  
Mail Order Only.  
C.V.O. P. & P. at cost. 10p min. List free.

World-wide acclaim, the incomparable  
**GLOBE-KING**  
V.H.F. & S.W. KITS  
Precision standard, inexpensive, low-cost valve and transistor Kits for Short-Wave 10-350 m. V.H.F. 80-180 M/cs. Ideal for beginners with unique "Easy-Build" diagrams and simplified instructions. Send to-day for free literature price list and order form, kindly enclose stamped addressed envelope (Overseas: Int. Reply Coupon). Direct to the sole manufacturers:  
**JOHNSONS (RADIO)**  
SHAW ST., WORCESTER.  
WR1 3QQ  
Please note new address, city centre. Pioneers in DX radio—Established for over 30 years.  
(A JOHN BANNER COMPANY)

**BRAND NEW COMPONENTS** by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10mfds—4p, 22, 47—4 1/2 p. (50V—5p.) 100—5 1/2 p. (50V—7p.) 220—6p. (50V—9p.). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V—8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—2p. 0.04, 0.05—3p. 0.068, 0.1—3 1/2 p. Polystyrene 63V. E12 series 10 pf.—1,000 pf.—2p. 1,200 pf.—10,000 pf.—3p. Miniature Highstab resistors, 5%, E.12 series—Carbon Film 1/2 W 1Ω—10MΩ (10% over 1 Meg.) Metal Film 1/2 W 10Ω—2.2MΩ and 1W. 27Ω—10MΩ all 3 1/2 p each. Postage 8p. The C.R. Supply Co., 127 Chesterfield Rd., Sheffield S8.

**NEW MODEL V.H.F. KIT MK2**  
Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.  
Only £3.50 + p.&p 10p U.K. only.  
Illustrated catalogue of selected kits and components, 20p inc. V.A.T. P&P free.  
**ALL PRICES PLUS 10% VAT**  
Galileo Trading Co., 12, Burs Way, Corringham, Stanford-Le-Hope, Essex. SS17 9DE

**TRANSISTOR AMPLIFIER 80c.** Vol/Tone Control Panel 75p. 465 K/CS IF Panel 75p. Wavechange-OSC Panel 75p. LW-MW Rod Aerial 25p. Colour Television, Cromas Panels £3.50. IF Panels £3.00. EHT Tripler Panel £1.08. Control Panel ON/OFF + Vol/Brightness Controls £1.00. Archer, 9 Pine Grove, Maidstone, Kent.

# THE TEXAN



Designer approved Kit only £28.50  
Instructions only 35p

- Pack 1. RESISTORS ..... 80p
  - Pack 2. SMALL CAPS ..... £1.50
  - Pack 3. LARGE CAPS ..... £1.40
  - Pack 4. SUNDRIES ..... £2.50
  - Pack 5. SWITCHES ..... £1.00
  - Pack 6. CONTROLS ..... £1.45
  - Pack 7. SEMI COND. .... £2.25
  - Pack 8. TRANSFORMER .... £4.95
  - Pack 9. P.C. BOARD ..... £2.50
  - Pack 10. CHASSIS, etc. .... £4.20
- Post extra—parts available separately  
Send for list and technical spec.

- Kits also available for
- ★ Radio Control Systems
  - ★ Digital Clock Systems
  - ★ Integrated Circuit Amplifiers (to 50W)
  - ★ Hi-Fi Pre-amps
  - ★ Stabilized Power Supply Units

**TELERADIO HI FI, 325 Fore Street, Edmonton, London N.9 01-807 3719**  
CLOSED ALL DAY THURSDAY

BUILD THE **TREASURE TRACER MK III** Metal Locator

- Vericap tuning
- Excellent sensitivity and stability
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- Thoroughly professional finish
- You only need soldering iron, screwdriver pliers and snips.
- Completely new design
- Send s.a.e. for leaflet

Complete kit **£12-50** Built, tested and guaranteed **£13-75**  
Post 35p Post 35p  
MINIKITS ELECTRONICS, 35b LANGLEY DRIVE, WANDSWORTH, LONDON SW18 2LN. (Mail order only)

**TRANSISTOR AMPLIFIER 80c.** Vol/Tone Control Panel 75p. 465 K/CS IF Panel 75p. Wavechange-OSC Panel 75p. LW-MW Rod Aerial 25p. Colour Television, Cromas Panels £3.50. IF Panels £3.00. EHT Tripler Panel £1.08. Control Panel ON/OFF + Vol/Brightness Controls £1.00. Archer, 9 Pine Grove, Maidstone, Kent.

**COMPONENTS GALORE.** Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 + 10p P & P C.V.O. to Caledonian Components, Fosterton Firs, Strathore Road, Thornton, Fife.

**TRANSISTOR BARGAINS.** Similar to BC107/8/9, BC168/9, 10 for 30p, 25 for 65p, 50 for £1.05. Individually tested, unmarked. Post/Package 5p. Mail Order only. 7 Walton Dene, Aylesbury, Bucks.

## TV'S COLOUR TV'S

Reserviced, perfect working order, repolished.

19in. DECCA	£110
19in. GEC 2028	£115
19in. THORN 2000	£120
25in. DECCA	£125
25in. RBM PHILIPS	£130
25in. THORN 2000	£135

One month comprehensive written guarantee. These are cash and collect prices. Delivery quotations by phone

## MONO UHF

Fabulous TVs. No rubbish, from good source. Repolished cabinets. Many working. Recent transistorised models, incl.:

BUSH TV 148U, TV 166, TV 176
PHILIPS, style 70 and 210
PYE & ECKO 858 chassis
THORN 950, 1400, GEC Concorde from £12 each

Valve UHF models inc.:  
BUSH push-button, THORNE 850,  
SOBELL, 1000, etc. from £5

## U.H.F. TUNERS

For FERGUSON 850, 900 chassis but adaptable for most D/STD chassis £2-50 each, c/w postage included. Send s.a.e. for lists of tubes, tvs, valves, etc. For England:

TRADE DISPOSALS, 1043 Leeds Road, Bradford. Tel. Bradford 665670  
For Scotland:

TRADE DISPOSALS, Unit 5, Peacock Cross INDUSTRIAL ESTATE, 32 Burnbank Road, Hamilton. Tel. Hamilton 29511/2

## VALVE LIST

ALL VALVES FULLY TESTED

One valve postage 3p. Over 5 valves postage paid.

DY86-87	12½p	PCF80	5p	6F23	15p
EB91	15p	PCF86	15p	6/30L2	15p
ECC82	10p	PCF805	25p	30F5	10p
EC C85	20p	PCL82	12½p	30FL1	20p
ECL80	7½p	PCL83	12½p	30PL1	20p
EF80	7½p	PCL84	12½p	30PL13	17½p
EF183	10p	PCL85	20p	MANY MORE	
EF184	10p	PCL86	17½p	AVAILABLE	
EH90	15p	PFL200	25p	S. & W.	
PC86	20p	PL36	20p	ELECTRONICS	
PC88	20p	PL504	20p	114 Burnley	
PC900	10p	PY800	12½p	Road	
PCC84	5p	PY801	25p	Rawtenstall	
PCC189	7½p	UY191	17½p	Rosendale	
PCC805	15p	U26	10p	Lancs.	

TUNBRIDGE WELLS, Components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

UNUSED RESISTORS and Capacitors 250 of each, including high stabs and electrolytics. Only £1.50. Trade enquiries invited. 676 Foxhall Road, Ipswich, Suffolk.

COMPONENTS AND HARDWARE, new and used, for P.W. circuits, S.A.E. for list. David Coulam, Tathwell, Louth, Lincs.

## Miscellaneous

# Darned Electronic Wizardry

by Dewtron

Famous kits, e.g. waa-waa complete kit £2-95; Fuzz kit £4-75, auto rhythm modules P & P 20p min Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 251 Ringwood Road, Ferndown, Dorset.

ENGRAVING. Give your Fascia Panels that professional look. Have the letters machine engraved. 3p per letter, minimum order 50p. Plus P & P. Colourstones, 9 Broadway Close, Harwell, Berkshire.

ALUMINIUM SHEET to individual sizes or in standard packs, 3p stamp for details. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warwick.

## BEDFORD ELECTRONICS

2 Grove Place, Bedford

Bedford 51961

YOUR LOCAL

COMPONENTS SUPPLIER

MAKE YOUR OWN printed circuits kit containing 1lb etchant, resist, 150 sq. in., copper laminate, brush and instructions—75p. Ferric chloride 2lb 60p, 4lb £1-00. Copper laminate offcuts, useful sizes S.R.B.P. and Fibreglass 500 sq. in. 80p. 1000 sq. in. £1-37. Post free. C.W.O. Malpas Electronic Developments, 94 Larch Grove, Malpas, Newport, Mon. NP1 6LA.

QUALITY ½ track R/P Heads, mounted in Mumetal Case. 55p each. 117 Horton Road, Brighton BN1 7EG.

## "AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS"

because this Ministry approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECKET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5-80 (inc. VAT) NOW (S.A.E. for details) 'MAIL ORDER ONLY'

TO: 'BOFFIN PROJECTS'

DEPT. KW2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

GLASS FIBRE P.C. BOARD. Large supplies available 1/16in single sided one ounce copper 2p per 3 sq. inches (under 1 foot). 75p per sq. ft. (over 1 foot). 1/16in double sided one ounce copper 1p per sq. inch (under 1 ft.), £1 per sq. ft. (over 1 foot). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, The Firs, Small-worth Lane, Garboldisham, Diss, Norfolk.

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd. Stratford-on-Avon, Warwks.

## 12 VOLT FLUORESCENT LIGHTS

As illustrated By Thorn/AEI



Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at: 12 ins. 8 watt £3-86 post paid 21 ins. 13 watt £4-82 post paid

Callers welcome.

For lists or enquiries, large s.a.e. SALOP ELECTRONICS, 23 WYLE COP SHREWSBURY, SHROPSHIRE.

BUILD IT in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

## NEW VALVES!

GUARANTEED AND TESTED

24-HOUR SERVICE

PRICES INCLUDE VAT

1R5	-88	30P19	-53	6CX82	-17	EL33	-83	PCF86	-44	PY801	-30
1R5	-83	30P11	-54	6CX83	-21	EL41	-85	PCF801	-27	U19	-27
174	-18	DAP91	-23	6CX85	-31	EL84	-20	PCF802	-38	U26	-64
384	-28	DAP96	-35	6CX85	-48	EM80	-80	PCF805	-55	U26	-64
3V4	-46	DF91	-18	6CH42	-56	EM81	-85	PCL82	-28	U191	-54
6/30L2	-48	DF96	-35	6CH81	-26	EM84	-80	PCL83	-58	U261	-60
6AT6	-18	DH77	-18	ECL80	-27	EY86	-97	PCL84	-31	U329	-65
6AQ5	-23	DK91	-28	ECL82	-27	EZ80	-19	PCL85	-36	UAB30	-29
6EW7	-48	DK96	-43	ECL86	-32	EZ81	-21	PCL86	-35	UFP89	-23
6F1	-57	DL92	-28	EF39	-43	KT61	-63	PFL200	-45	UCC85	-32
6F23	-84	DL94	-46	EF41	-56	KT66	-75	PL36	-45	UCH42	-56
6F25	-49	DL96	-36	EF80	-22	N78	£1-00	PL81	-41	UCH81	-28
12A07	-17	DY86	-21	EP85	-26	PC86	-42	PL82	-29	UCL82	-30
2BL0GT	-18	DY87	-21	EP86	-27	PC88	-42	PL83	-31	UF41	-49
30C16	-56	DY802	-23	EP89	-24	PC97	-34	PL84	-33	UY83	-23
30C17	-73	EAB30	-28	EP91	-15	PC900	-22	PL800	-56	UL41	-52
30C18	-55	EBC33	-43	EP92	-26	PC84	-27	PL504	-56	UL84	-27
30F5	-60	EBC41	-47	EP183	-25	PCC89	-41	UY81	-23	UY41	-87
30FL1	-59	EBP89	-27	EP184	-27	PCC189	-46	PY82	-23	UY85	-22
30FL14	-63	ECC81	-18	EH90	-33	PCF80	-25	PY800	-20	W77	-42

Post/Packing on 1 valve 7p. plus 3p. per valve on each extra valve. Any parcel insured against damage in transit 3p. extra. Office address, no calls.

GERALD BERNARD

83 Osbaldeston Road, Stoke Newington, London N.14

## ELEKON SPECIALS

ELECTROLYTIC CAPACITORS µF/V: 250/25, 2000/35, 2200/25, 4700/16, 8000/30, 10,000/15, 10,000/25, 16 + 16/50, 100 + 100/40. All at 25p each, post free. 16 + 16/350, 32 + 16/350, 40 + 40/250, 50 + 50/300, 80 + 80/450, 100 + 100/385, All at 25p each, post free. 2000/50, 2500/50, 5000/50, 10,000/50, 12,500/50. 50p each, post free.

VISCONOL EHT CAPACITORS. -001µF 20KV 50p. -01µF 5KV 40p. -01µF 10KV 50p. -02µF 5KV 40p.

HUNTS METALLISED FILM REVERSIBLE ELECTROLYTIC CAPACITORS 8µF 63V Type ML 30 wire-ended, 25p each. Also 10µF 63V, same price.

SOXSOL DE-SOLDER BRAID. 9ft length 50p, 20 ft length £1-00.

SUBMINIATURE PLUG-IN CRYSTALS FOR RADIO CONTROL. 26-945MHz and 27-025 MHz. 70p each.

ADD 10% V.A.T. TO TOTAL ORDER.

ELEKON ENTERPRISES  
224a St Paul's Road, Highbury Corner, London N.1



# LOUDSPEAKER BARGAINS

Fane Pop 100 watt 18" 8/15 ohm	£21.45
Fane Pop 60 watt 15" 8/15 ohm	£12.26
Fane Pop 50 watt 12" 8/15 ohm	£10.17
Fane Pop 25/2 25 watt 8/15 ohm	£5.94
Fane Pop 15 12" 15 watt 8/15 ohm	£4.40
Fane 122/10a or 122/12	£9.90
Fane Crescendo 15" 8 or 15 ohm	£27.50
Fane Crescendo 12" 8 or 15 ohm	£24.20
Fane 8" d/cone 808T 8 or 15 ohm	£2.64
Fane 8" d/cone, roll surr. 807T 8 or 15 ohm	£3.16
Baker Group 25 3, 8 or 15 ohm	£6.00
Baker Group 35, 3, 8 or 15 ohm	£7.50
Baker De Luxe 12" d/cone	£9.62
Baker Major	£7.50
EMI 13 x 8 3, 8 or 15 ohm	£2.25
EMI 13 x 8 type 150 d/cone 3, 8 or 15 ohm	£2.58
EMI 13 x 8 type 450 t/tw 3, 8 or 15 ohm	£3.85
EMI 13 x 8 type 350 8 ohm	£8.25
EMI 64" 93850 4 or 8 ohm	£2.80
Elac 9 x 5 59RML09 15 ohm	£2.53
Elac 9 x 5 59RMLL4 8 ohm	£2.53
Elac 64" d/cone 6RM220 8 ohm	£2.59
Elac 64" d/cone, roll surr. 6RM171 8 ohm	£3.22
Elac 4" tweeter TW4 8 or 15 ohm	£1.21
Celestion PS8 for Unilex	£2.16
Celestion MFL000 25 watt horn 8 or 15 ohm	£10.45
Elac 5" 3 ohm	£1.75
Elac 7" x 4" 3 or 8 ohm	£1.52
Elac 8" x 5" 3, 8 or 15 ohm	£1.93
Wharfedale Bronze 8 RS/DD	£3.11
Wharfedale Super 8 RS/DD	£5.50
Wharfedale Super 10 RS/DD	£9.80
Goodmans 8P 8 or 15 ohm	£3.80
Goodmans 10P 8 or 15 ohm	£4.49
Goodmans 12P 8 or 15 ohm	£11.55
Goodmans 15P 8 or 15 ohm	£17.05
Goodmans 18P 8 or 15 ohm	£29.70
Goodmans Twinaxiom 8	£6.79
Goodmans Twinaxiom 10	£7.61
Goodmans Axent 100	£6.60
Eagle DT33 dome tweeter 8 ohm	£4.95
Eagle HT15 tweeter 8 ohm	£3.46
Eagle CT5 tweeter 8 ohm	£1.21
Eagle MHT10 tweeter	£3.30
Eagle CT10 tweeter	£1.92
Eagle Xovers CN23, 28, 216	£1.10
Kef T27	£4.67
Kef T15	£5.50
Kef B110	£6.16
Kef B200	£7.42
Kef BL39	£10.72
Kefkit 2	£24.75
Richard Allan 12" d/cone 3 or 15 ohm	£2.20
Richard Allan 8" 3, 8 or 15 ohm 10" x 6" 3, 8 or 15 ohm	£2.27
8" x 5" 3 or 8 ohm	£1.38
7" x 4" 3 or 8 ohm	£1.38
3" 8 ohm or 80 ohm	£.65
2 1/2" 64 ohm	£.65
Speaker matching transformer 3, 8 or 15 ohm	£1.10
Adastra Hiten 10" 10 watt 8 or 15 ohm	£2.80
Adastra Top 20 12" 25 watt 8 or 15 ohm	£6.32
Stephenspeaker kits and cabinets—send for illustrated brochure and list of recommended speakers.	
Car stereo speakers—ask for leaflet.	
PA/Disco amplifiers (carr. and ins. £1.00):	
Baker 100 watt	£46.00
Linear 30/40	£25.00
Linear 40/60	£30.00
Linear 80/100	£50.00
FREE with speaker orders over £7 "Hi-Fi Loudspeaker Enclosures" book.	
All units guaranteed new and perfect. Prompt despatch.	
Carriage and insurance 25p per speaker. (Tweeters and Crossovers 15p each.)	
All prices quoted inclusive of V.A.T.	

**WILMSLOW**  
**AUDIO, Dept. PW**  
 Swan Works, Bank Square,  
 Wilmslow, Cheshire, SK9 1HF

# OMNIA PRODUCTS



## STABILIZED AUTO ADAPTOR

### For CAR-CARAVAN-BOAT

Stabilised 6, 7.5 & 9v from single unit. Battery operated cassette recorders, radios etc., powered by 12v car battery through this ingenious electronic Adaptor. Constant stabilised power means apparatus in use is always working at maximum efficiency—and no more 1.5v, 9v etc batteries to buy. Only £3.95 (p.p 12p).  
 FOR THE HOME: Voltage Converters 220-240v AC to 6, 7.5 & 9v DC: 2:00mA £2.50, 400mA £3.00. Leads (optional) 60p (State plug required). All prices include VAT.

25 Wilbury Gardens Hove Sussex

### AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45—UHF 825, B42—VHF 405, B11—VHF RADIO

### VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3.30—  
 ECC82, ECL80, EB91, EBF80, EF80, EF85, EF183, EF184, EY86, PCC84, PCC80, PCC180, PC97, PCF80, PCF85, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL38, PL81, PL504, PY33, PY82, PY800, PY801, 30L15.

### 19" UHF/VHF (BBC2) £6.00

Thorn-850 or Pye, with set of spare valves. Carriage £2.00 (Untested).

### 100 MIXED RESISTORS—85p

± to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Capacitors up to 500MFD—£1.10 (our choice).

### BARGAINS PARTS

Transistor UHF Tuners—£2.00, 500K-ohms V/C with Switch—20p. 50 mixed Tuner Valves—£2.25. Brand New Transistors BF115, BF173, BC171, BC183, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order Money back guarantee. S.A.E. for leaflets.

### ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036

## AUDIO POWER AMPLIFIERS

10W	—	£4.00	} 1 OFF PRICES
25W	—	£8.00	
50W	—	£11.00	

### GENEROUS QUANTITY DISCOUNTS AVAILABLE

DETAILS FROM:  
**PHOTAIN CONTROLS LTD.**  
 Randalls Road, Leatherhead, Surrey

PRICES DO NOT INCLUDE VAT Tel: 72776/75517 STD CODE 037-23

**CONSTRUCTION AIDS**—Screws, nuts, spacers etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd., Stratford on Avon, Warwks.

# FREE!



## FULLY ILLUSTRATED CATALOGUE

### AMAZING QUALITY

Our superb catalogue is printed in easily read type. It has dozens of clear pictures and illustrations of thousands of the kinds of components you use.

### SPEEDY SERVICE

Write now and we will be delighted to forward a copy to you by return of post.

### PHONE ANY TIME

You can phone for your free catalogue whenever it suits you. Out of office hours leave your name and address on our answering machine.

### £1 FREE

When you receive your catalogue you will find out how you can obtain one pounds worth of goods absolutely free!

### PLUS

Free post and packing in U.K. Every item sold guaranteed brand new and marked by the manufacturer.

Phone 037 42 79033 or Write:—MAPLIN ELECTRONIC SUPPLIES P.O. BOX No. 3 RAYLEIGH ESSEX SS6 8LR



LED's:		
TIL302 4 for		£10
6 for		£14
DL34 4 digits		£15
TIL360 6 digits		£18
TIL209 4 for		£1
50 for		£10
Equivalent may be supplied as stocks levels dictate		
'SPECIAL'		
Green/Red LED matched pair		£1
<b>CALCULATORS</b>		
Advance Mini		£45
Advance Exec. 8		£45
Advance Exec. 16-1		£95
Advance Exec. 16-2		£110
Post & Packing I.C.'s. LED's, 10p. KITS, CALC's, METERS 50p.		
I.C.'s		
MM5311 Clock		£12.50
ZN414 Radio		£1.10
Sig555 Mono/astab.		£0.90
CA3082 7-seg. driv.		£2.10
KITS (incl. I.C. sockets		
Calculator		£41
Digitronic (6)		£36
Digitronic (4)		£32
Bywood clock kit		£34
ADD 10% VAT TO ALL ORDERS		
LATEST! New Digital Clock I.C.'s available with alarms. S.A.E. for details. Complete kits with PCB & displays £24.00.		



You may telephone your order and pay by ACCESS.

ANSAFONE—24-hour service.

**BYWOOD**  
 ELECTRONICS  
 181 EBBERS ROAD, HEMEL  
 HEMPSTEAD, HERTS. 0442 62757

## B.H. COMPONENT FACTORS LIMITED

**SPECIAL RESISTOR KITS** (±w 5% or ±w 5% CARBON FILM)  
 10E12 Kit: 10 of each E12 value, 10 ohms—1M, a total of 610, £3.10 net  
 25E12 Kit: 25 of each E12 value, 10 ohms—1M, a total of 1,525, £7.20 net

**POLYESTER CAPACITORS MULLARD C280 250V**  
 μF: 0-01, 0-015, 0-022, 0-033, 0-047, 3½p each; 0-068, 0-1, 0-15, 4½p each;  
 0-22, 5½p; 0-33, 6p; 0-47, 9p; 0-68, 11p; 1-0, 15p; 1-5, 22p; 2, 25p.

**MULLARD POLYESTER CAPACITORS C396 SERIES**  
 160V: (μF) 0-01, 0-015, 0-022, 2½p; 0-047, 0-068, 3½p; 0-1, 0-15, 4½p;  
 0-22, 5p; 0-33, 6p; 0-47, 7½p; 0-68, 11p; 1-0, 12½p.  
 400V: (μF) 0-001, 0-0015, 0-0022, 0-0033, 0-01, 2½p; 0-015, 0-033, 3½p;  
 0-068, 4½p.

**MINIATURE ELECTROLYTIC CAPACITORS MULLARD C426 SERIES** (6p each)  
 (μF/V) 1/63, 4/40, 8/40, 10/40, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10,  
 80/16, 80/25, 100/6-4, 125/16, 200/6-4, 200/10, 320/6-4, 125/10.  
**MULLARD C437:** (μF/V) 64/64, 10p; 160/25, 10p; 160/40, 12p; 640/6-4,  
 10p; 1600/6-4, 16p.

**ELECTROLYTIC CAPACITORS.** Tubular and large can  
 (μF/V) 2-5/50, 3p; 4/10, 10/25, 16/15, 20/25, 25/15, 25/25, 40/6, 64/10, 200/6,  
 250/10, 5p; 10/6, 10/50, 25/50, 32/50, 50/10, 64/25, 100/25, 6p; 50/50, 64/40,  
 250/15, 1,000/3, 7p; 100/50, 250/25, 400/10, 500/10, 500/12, 640/10, 1,000/6, 9p;  
 500/25, 11p; 500/50, 14p; 1,000/12, 11p; 1,000/25, 2,000/12, 2,500/12, 17p;  
 1,000/50, 39p; 2,000/25, 27p; 2,500/25, 33p; 2,500/50, 62p; 3,000/50, 72p;  
 5,000/50, 94p; 1,000/100, 66p; 8/350, 14p; 16/350, 19p; 32/350, 25p.

**MINIATURE CERAMIC PLATE CAPACITORS**  
 50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390,  
 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8. (μF) 0-01, 0-015, 0-022, 0-033,  
 0-047, 2½p; 0-1, 30V, 4½p; 0-1, 100V, 5½p.

**CARBON FILM RESISTORS** ±w 5%, 10 ohms—2.2M, ±w 5%, 10 ohms—  
 1M, 1p each or 100 for 62p; 1,000 for £4.50.

**METAL FILM RESISTORS** ±w 5%, 10 ohms—10M, 1½p each or 100  
 for £1-10. "15E12 KIT (15 each value 10Ω—1M) £8"

Veroboard	0-1	0-15
2½ x 5in	26p	28p
2½ x 3½in	26p	19p
3½ x 5in	32p	33p
3½ x 3½in	28p	28p
2½ x 1in	7p	7p
2½ x 5in (plain)	—	14p
2½ x 3½in (plain)	—	12p
5 x 3½in (plain)	—	12p
Insertion tool	59p	59p
Track cutter	44p	44p
Pins, pkt. 25	10p	10p

IN4001	6½p	QUANTITY DISCOUNT
IN4002	7½p	SPECIAL BULK BUY PRICES
IN4003	9½p	ARE AVAILABLE BY
IN4004	9½p	QUOTATION FOR LARGE
IN914	7p	PROJECTS AND TRADE.
μL914	35p	S.C.R.
OC71	13p	50V IA 29p 3A 33p
OC75	17p	100V IA 33p 3A 40p
OC83	20p	400V IA 50p 3A 60p

Screened wire, m	5½p
Twin screened wire, m	10p
Stereo s.c. wire, m	10p
Connecting Wire, all colours	2½p
Neon bulb 90V wire ended	5 for 24p
Preset skeleton pots 1K—1M	6p

ALL PRICES INCLUDE V.A.T.  
 C.W.O. only. P. & P. 10p on orders below £5.  
 Discount: £10—10%, £20—15%.  
 Export Order enquiries welcome (VAT free)

Dept. P.W. 61, CHEDDINGTON ROAD, PITSTONE  
 Near LEIGHTON BUZZARD, BEDS. LU7 9AQ  
 Tel.: Cheddington 668446 STD. (0296) GIRO No. 331 7056  
 Inquiries—S.A.E. Catalogue FREE. Callers please phone first.

## COMPARE OUR PRICES

**Speaker Bargains**  
 E.M.I. 13 x 8 In 3, 8 & 15 OHMS  
 PLAIN .. £2.00  
 Type 380-20 watt with Tweeter .. £2.25  
 8 OHM p. & d. 37p .. £7.25  
 TWIN TWEETER .. £3.50  
 8 x 5 In 3, 8 & 15 OHMS .. £1.10  
 7 x 4 In 3 & 8 OHMS .. 90  
 FANE 8" 8 OHM DUAL CONE .. £2.10  
 CELESTION 8" 15 OHM .. £1.40  
 BAKE GROUP 25 12" 25 .. £3.75  
 WATT 8 or 15 OHM .. £3.75  
 2½" 8 or 64 OHM p. & p. 10p. .. 45  
 POSTAGE 25p per SPEAKER

**Kit-Form Cabinets Teak**  
 (17" x 10" x 6") with a 13" x 8"  
 or 8" CUT OUT .. £2.75  
 18 x 11 x 9 with 13" x 8" cutout  
 for EM1 350 .. £3.70  
 (12" x 12" x 6") with a 8" x 5" or  
 8" CUT OUT .. £2.25  
 (PLEASE SPECIFY CUT OUT)  
 Add 35p per Cabinet for p. & p.

**Cartridges with standard fittings & styl**  
 GOLDRING G850 .. £2.80  
 GOLDRING G800 .. £2.40  
 ACOS GP91/2SC or GP91/  
 35C STEREO COMPAT-  
 IBLE .. 90  
 ACOS GP94 STEREO CER. .. £1.50  
 ACOS GP95 STEREO CRY. .. £1.15  
 ACOS GP96 STEREO CER. .. £1.50  
 9THAC SONOTONE STEREO  
 CERAMIC (DIAMOND) .. £1.70  
 9THAC/G SONOTONE  
 STEREO CER. (DIAMOND) .. £1.70  
 SLIMLINE .. £1.70  
 ACOS GP97/2C MONO CRY. .. 65  
 ACOS GP97 COMP. CRY. .. 65  
 19-TI SONOTONE STEREO .. 60  
 CRYSTAL .. 60  
 POSTAGE 5p per CARTRIDGE

**Microphone Bargains**  
 MIC45 "ACOS" metal case,  
 crystal hand .. 95  
 CM 20 Crystal Hand .. 45  
 DX143 Dynamic, cassette-  
 type stick .. £1.00  
 CM70 PLANET stick metal,  
 switch crystal .. £1.45  
 DM160 Dynamic uni-dir, ball  
 metal .. £3.75  
 UD130 50K/600 OHM uni-dir,  
 ball m. .. £4.50  
 TW209 LESSON DUAL IMP  
 ball metal, uni-dir. .. £5.75  
 CONDENSER MIKE uni-dir.  
 800 OHM .. £7.95  
 GUITAR MIKE .. 45  
 LAPEL TYPE, crystal .. 40  
 POSTAGE 17p each.

**Battery Eliminators**  
 240v input 6 or 9v d.c. output  
 at 150 mA .. £1.00  
 240v input 6, 7½ or 9v output  
 at 300 mA .. £2.00  
 12v d.c. input for cars, fits in  
 lighter socket) 6, 7½ or 9v  
 d.c. output at 300 mA .. £2.50  
 P. & P. 10p

**Tapes — "MYLAR" base finest  
 quality British made.**  
 5" 600 ft 36p 5½" 1800 ft 85p  
 5" 900 ft 45p 7" 1200 ft 85p  
 5" 1200 ft 60p 7" 1800 ft 80p  
 5½" 900 ft 49p 7" 2400 ft 85p  
 5½" 1200 ft 55p  
 POSTAGE 9p each.

**PLASTIC LIBRARY CASES**  
 for 5in Reels 16p  
 5½in Reels 19p  
 7in Reels 21p  
 P. & P. 5p each

**THIS MONTH'S SPECIAL OFFER**  
 PLINTH to suit GARRARD 2025, SP25, etc. Teak finish complete with  
 perspex cover. Our price £3.20. P. & P. 50p.

SEND 25p FOR COMPLETE CATALOGUE Add 10% VAT on prices, inc. P. & P.

## RIVERSDALE ELECTRONICS

Mail Order Department W7/73, P.O. Box 470, Manchester M66 4BU  
 ALL OUR MERCHANDISE IS FULLY GUARANTEED

## INDEX TO ADVERTISERS

Antex Ltd...	205	Felstead Electronics	272	R.D.I.	283
Astro Electronics	276	Fi-Comp Electronics	268	Radio Component Specialists	211
B. H. Components Factors Ltd...	287	Galleon Trading	283	Radio Book Services	282
Baines, R.	282	Gladstone Radio	278	Radio Exchange Co. Ltd.	267
Baker Loudspeakers Ltd.	212	Greenwell Electronics	284	Radio & T.V. Components (Acton) Ltd	208, 209
Bedford Electronics	285	HAC Shortwave Products	232	Radio Society of Great Britain	276
Bells' Television	282	Harverson Surplus Co. Ltd.	255	Readers Radio	198
Bentley Acoustic Corporation Ltd.	204	Heath (Gloucester) Ltd.	196	Redhawk Sales	283
Bernard, Gerald	285	Henry's Radio Ltd.	207, Cov. iv	Riversdale Electronics	287
B.I.E.T.	268 Cov iii	Home Radio (Components) Ltd.	263	RSC (Hi-Fi Centres) Ltd.	194, 195
Bi-Pak Semiconductors	273, 274, 275	I.C.S.	253	R.S.T. Valve Mail Order Co.	268
Bi-Pre-Pak Ltd.	259, 276	I.L.P. (Electronics) Ltd.	231	S.C.S. Components	196
Boffin Projects	285	Imhois	210	S. & W. Electronics	285
British National Radio & Electronic School	Cov ii, 228	Ivoryet Ltd.	264	Salop Electronics	285
Broadway Electronics	276	Jef Electronics	284	Saxon Entertainment	227
Bull, J. (Electrical) Ltd.	279	Johns (Radio) Ltd.	256	Smicon Index Ltd.	282
Bush & Meissner	204	Johnson (Radio)	284	Sinclair Radionics Ltd.	280, 281
Butterworth & Co. (Pub.) Ltd.	256	K.V.A. Electronics	204	Shopertunities Ltd.	197
Bywood Electronics	286	Kensington Supplies	286	Smith, G. W. & Co. Ltd.	200, 201, 202, 203
C.C.I.L. Ltd.	206	Keytronics	252	Surpnetronics	268
Caranna, C.	282	Lasky's Radio Ltd...	252	Swanley Electronics	256
Chiltmead Ltd.	212	Lewis Radio	228	Tate Audio Transmission Equipment Ltd.	199
Chromasonic Electronics	213	Linear Products Ltd.	277	Teleradio Co. Ltd.	284
Codar	212	London Computer Operators Training Centre	282	Texas Instruments	198
Colomor Electronics Ltd.	278	Maplin Electronic Supplies	286	Thacker, A. H. & Sons Ltd.	210
Comet High Fidelity Discount Warehouses	214, 215	Marco Ltd.	283	Trade Aids	232
Control Data Institute	272	Milward, G. F.	277	Trade Disposals	285
D.E.W. Ltd.	285	Minikits Electronics	284	Trampus Electronix	284
Dabar Electronic Products	272	Multicore Solders Ltd.	206	Trannies	271
Davian Electronics	264	Omnia Products	286	Tuac Ltd.	252
Denco	282	Partridge Radio Store	252	Web Europa	206
Douglas Electronic Industries Ltd.	232	Partridge Electronics Ltd.	264	West London Direct Supplies	204
Electrokit	232	Pembridge College	210	Weyrad (Electronics) Ltd.	263
Electronic Design Associates	278	Phononics	264	Wheel	212
Electronic Mail Order	286	Phyotain Controls	286	Wilmslow Audio	198, 286
Electrosparcs	206	Plymouth Polytechnic	283	York Electronics	210
Electrovalue	251	Padgetts Radio Store	252	Z & I Aero Services	288
Elekon Enterprises	285	Partridge Electronics Ltd.	264		
Elvins Electronic Musical Instruments	228	Pembridge College	210		

Head Office and Warehouse  
44A WESTBOURNE ROAD  
LONDON W2 5SF  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 12 $\frac{1}{2}$  p in £ for postage and handling  
MINIMUM CHARGE 15np. No C.O.D. orders accepted  
Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

0A2 0.40	6ASTG 0.85	6F13 0.60	10D1 0.85
0A3 0.48	6AT6 0.88	6F14 0.70	10D2 0.75
0B2 0.40	6AU6 0.80	6F15 0.45	10F1 0.55
0B3 0.70	6AV6 0.40	6F18 0.80	10F9 0.85
0C3 0.40	6AW8A 0.65	6F23 0.90	10F8 0.80
0D3 0.40	6BA6 0.25	6F24 0.80	10L1 0.60
1B3GT 0.45	6BE6 0.32	6F25 1.00	10LD11 0.70
1L4 0.25	6BF6 0.56	6F26 0.35	10P13 0.75
1R4 0.50	6BH6 0.75	6F28 0.70	12AB5 0.70
1R5 0.45	6BJ6 0.55	6GK6 0.80	12AC6 0.80
1R6 0.30	6BK7A 0.75	6J4 0.80	12AB5 0.60
184 0.80	6BN5 0.45	6J8GT 0.40	12AL5 0.55
1T4 0.30	6BN4 0.60	6J8 0.30	12AQ5 0.55
1U4 0.40	6BQ5 0.85	6J7 0.45	12AT6 0.40
1U5 0.75	6BR8 0.75	6K47T 0.80	12AT7 0.40
1V2 0.55	6BS7 1.35	6K6GT 0.75	12AU7 0.45
1X2B 0.55	6BW6 0.90	6K7 0.45	12AU7 0.35
2D21 0.40	6BW7 0.90	6K8G 0.45	12AV6 0.45
3A4 0.45	6BK6 0.25	6K25 0.75	12AV7 0.70
3A5 0.75	6BZ6 0.45	6LGT 0.55	13AX7 0.33
3B4 0.40	6C4 0.35	6L7 0.45	12B47 0.75
3V4 0.70	6C5GT 0.55	6L18 0.80	12B4A 0.85
5R4GY 0.75	6CB6 0.40	6LD20 0.60	12BAC 0.45
5U4G 0.40	6CD8GA 0.30	6N7GT 0.55	12BA7 0.50
5V4G 0.80	6CG7 1.60	6Q7 0.50	12B6 0.50
5Y3GT 0.45	6CH6 0.60	68A7 0.45	12B7 0.50
5Z5 0.75	6CL6 0.60	68G7 0.45	12E1 1.00
5Z4G 0.95	6CU6 0.80	68K7 0.50	12K5 8.00
6/30L2 0.40	6CW4 0.70	68L7GT 0.45	12G7GT 0.45
6AB4 0.45	6CY5 0.90	68W7 0.45	12G7GT 0.45
6AFA 0.60	6CY7 0.75	68Y7 0.55	12H87 0.50
6AG5 0.85	6D3 0.55	68R7 0.50	20D1 1.00
6AJ5 0.45	6DC6 0.80	6T8 0.35	20L1 1.10
6AJ8 0.30	6DK6 0.60	6U4GT 0.75	20P1 0.80
6AK5 0.40	6DQ8B 0.75	6UG7 0.70	20P4 1.15
6AK6 0.60	6DS4 1.25	6A8 0.45	20P5 1.10
6AL5 0.45	6EA 0.80	6V8GT 0.45	25C5 0.60
6AL6 0.80	6EH7 0.30	6X4 0.40	25B6GT 0.50
6AM6 0.37	6EJ7 0.35	6X6GT 0.45	25Z4G 0.55
6AQ5 0.85	6EWS 0.70	6X8 0.45	25Z6GT 0.75
6AQ6 0.70	6F1 0.75	6Y6G 0.50	30A5 0.60
6AR5 0.55	6F5 0.75	6Y8 0.45	30A6 0.60
6AR6 0.65	6F6G 0.75	6Z5 0.80	30A3 0.40
6AS6 0.50	6F11 0.50	10C2 0.60	30C1 0.30
			30C15 1.00

First Quality Fully Guaranteed



ELECTRONIC VALVES


30C17 1.10	90AG 2.40	DY86 0.25	ECC88 0.40
30C18 0.90	90AV 2.50	DY87 0.35	ECC89 0.50
30F6 1.00	90C1 0.75	DY89 0.37	ECC91 0.30
30F11 0.80	90CV 3.40	E80F 1.25	ECC189 0.65
30FL12 1.10	807 0.50	E80C 1.00	ECC807 1.00
30FL14 0.90	813 4.00	E180F 1.00	ECCF80 0.35
30L1 0.40	886A 0.35	E10F 0.90	ECCF82 0.35
30L15 0.95	8842 0.70	EABC800.35	ECCF90.41.45
30L17 0.85	6080 1.75	EAF42 0.60	ECH43 0.75
30P12 1.00	6146 1.80	EBC33 0.60	ECH81 0.30
30P19 0.95	6146B 0.50	EBC41 0.65	ECH43 0.45
30P11 0.95	6360 1.85	EBC84 0.35	ECH84 0.45
30P13 1.10	6939 3.25	EBF80 0.40	ECL80 0.50
30P14 1.25	7199 0.85	EBF33 0.40	ECL81 0.70
35A3 0.60	7886 1.50	EBF89 0.50	ECL82 0.35
35A5 0.75	7895 1.50	EHL81 1.80	ECL83 0.70
35B5 0.65	A2993 2.80	EC53 0.50	ECL84 0.55
35C5 0.60	AZ1 0.80	EC80 2.55	ECL85 0.55
35D5 0.75	AZ31 0.55	EC86 0.60	ECL86 0.40
35L6GT 0.75	CBLL 0.90	EC88 0.60	ECLL800
35W4 0.40	CBLS1 1.00	EC90 0.35	EP37A 1.00
35Z5 0.75	CY1 0.80	EC92 0.45	EP40 0.50
35ZAG 0.40	CY31 0.50	EC93 0.60	EP41 0.55
35ZSGT 0.70	DAF96 0.50	EC95 1.00	EP42 0.70
50A5 0.80	DP96 0.50	EC98 0.50	EP80 0.80
50B5 0.70	DK92 0.70	EC98 0.55	EP86 0.35
50C5 0.80	DK96 0.80	ECC81 0.40	EP86 0.35
50CDG1.20	DL96 0.55	EC92 0.35	EF89 0.85
50EH8 0.55	DM70 0.80	ECC93 0.35	EF91 0.37
50L6GT 0.60	DM160 0.95	ECC84 0.30	EP92 0.25
86A2 0.55	DY51 0.55		

EP95 0.40	GZ34 0.60	PF818 1.00	U901 0.55
EP97 0.55	HABC800.55	PF1000.55	U40S 0.70
EP98 0.75	HK90 0.50	PL33 0.40	U404 0.70
EP183 0.30	KT66 2.35	PL36 0.55	U401 0.80
EP184 0.35	KT77 1.00	PL81 0.50	UABC80
EP804 1.25	KT88 2.25	PL92 0.45	
EK90 0.32	N78 1.60	PL93 0.45	UAF41 0.70
EL34 0.80	PAABC800.40	PL94 0.40	UAF42 0.50
EL36 0.50	PC86 0.60	PL302 0.95	UB41 0.65
EL41 0.75	PC88 0.60	PL504 0.75	UBC41 0.55
EL81 0.55	PC92 0.50	PL508 0.90	UBC81 0.45
EL83 0.50	PC97 0.50	PL509 1.10	UBF80 0.40
EL84 0.25	PC900 0.48	PL801 1.00	UBF89 0.40
EL88 0.40	PC84 0.40	PL802 0.96	UBL1 0.70
EL90 0.42	PC35 0.40	PM84 0.50	UBL21 0.70
EL92 0.15	PC38 0.55	PY81 0.35	UC92 0.45
EL93 0.15	PC89 0.55	PY83 0.63	UC85 0.45
EL94 0.15	PC189 0.60	Y80 0.40	UCF80 0.70
EM71 0.80	PC808 0.95	Y81 0.30	UCH21 0.60
EM80 0.45	PC806 0.95	Y82 0.35	UCH2 0.70
EM85 0.50	PCF80 0.30	Y83 0.38	UBL1 0.40
EM84 0.35	PCF82 0.35	Y88 0.40	UCL81 0.60
EM85 1.00	PCF84 0.60	Y800 1.00	UCL82 0.35
EN91 0.40	PCF86 0.60	Y801 0.47	UCL83 0.65
EN91 0.40	PCF87 1.10	Y801 0.50	UF9 0.55
EN91 0.40	PCF801 0.50	ZP30 0.38	UF11 0.60
EN91 0.40	PCF802 0.50	QQV02-4	UF41 0.65
EN91 0.40	PCF805 0.90	UF2 0.25	UF43 0.65
EN91 0.40	PCF806 0.75	QQV03-10	UF43 0.65
EN91 0.40	PCF808 0.90	1.25	UF80 0.35
EN91 0.40	PCF809 0.90	TT21 3.80	UF85 0.40
EN91 0.40	PCF810 0.90	TT22 4.00	UF89 0.40
EN91 0.40	PCF811 0.90	U18/20 0.75	UL41 0.65
EN91 0.40	PCF812 0.90	U26 0.85	UL84 0.48
EN91 0.40	PCF813 0.90	U28 0.85	UM84 0.30
EN91 0.40	PCF814 0.90	U31 0.70	UYN 0.50
EN91 0.40	PCF815 0.90	U37 6.50	UY11 1.00
EN91 0.40	PCF816 0.90	U52 0.40	UY41 0.48
EN91 0.40	PCF817 0.90	U76 0.40	UY82 0.80
EN91 0.40	PCF818 0.90	U78 0.40	UY86 0.48
EN91 0.40	PCF819 0.90	U91 0.75	W279 0.75
EN91 0.40	PCF820 0.90	U98 0.75	XC12 0.60
EN91 0.40	PCF821 0.90	U201 0.80	Y63 0.75
EN91 0.40	PCF822 0.90	Y801 0.85	Z759 3.60
EN91 0.40	PCF823 0.90	Y822 0.55	Z803U 1.25

## TRANSISTORS

2N696 0.15	AC128 0.15	BD121 0.65
2N697 0.15	AC132 0.35	BD124 0.60
2N698 0.30	AC153 0.20	BD131 0.75
2N705 0.70	AC154 0.15	BD132 0.80
2N706 0.10	AC157 0.17	BF115 0.30
2N708 0.15	AC169 0.10	BF157 0.18
2N753 0.25	AC177 0.17	BF199 0.45
2N929 0.90	AC187 0.25	BF179 0.80
2N930 0.20	AC188 0.25	BF180 0.80
2N947 0.20	ACY17 0.25	BF181 0.30
2N1121 0.25	ACY18 0.20	BF184 0.20
2N1132 0.25	ACY19 0.25	BF195 0.20
2N1184 0.25	ACY20 0.20	BF196 0.18
2N1302 0.17	ACY21 0.20	BF196 0.14
2N1303 0.17	ACY22 0.10	BF196 0.12
2N1304 0.20	AD140 0.50	BF197 0.12
2N1305 0.20	AD149 0.45	BF200 0.35
2N1306 0.25	AD161 0.45	BFW87 0.25
2N1307 0.25	D162 0.35	BFW89 0.25
2N1308 0.25	ADZ11 1.25	BFW89 0.25
2N1309 0.25	ADZ12 1.25	BFW91 0.20
2N1613 0.17	AF114 0.17	BFX88 0.20
2N1711 0.20	AF115 0.17	BFY17 0.40
2N1786 0.75	AF116 0.17	BFY19 0.25
2N9147 0.75	AF117 0.17	BFY20 0.25
2N9160 0.60	AF118 0.20	BFY21 0.20
2N9217 0.25	AF125 0.20	BFY52 0.20
2N2218 0.20	AF127 0.20	BSY26 0.17
2N2219 0.20	AF180 0.35	BY927 0.15
2N2399A 0.15	AF181 0.25	BSY98 0.17
2N2477 0.65	AF186 0.40	BSY98 0.20
2N2646 0.40	AF239 0.38	BSY96A 0.10
2N2905 0.25	AFZ11 0.45	OC16 0.50
2N2923 0.15	AFZ12 1.00	OC22 0.50
2N2924 0.13	AS Y26 0.25	OC23 0.60
2N2926 0.10	AS Y27 0.20	OC24 0.60
2N3053 0.60	AS Y28 0.25	OC25 0.35
2N3084 0.50	AS Y29 0.30	OC29 0.35
2N3085 0.60	AS Y54 0.25	OC29 0.60
2N3133 0.25	AS Z15 0.70	OC35 0.50
2N3134 0.25	AS Z16 0.70	OC36 0.45
2N3391 0.17	AS Z17 0.75	OC42 0.20
2N3392 0.17	AS Z18 0.75	OC44 0.15
2N3393 0.15	AS Z20 0.25	OC45 0.10
2N3394 0.15	AS Z21 0.40	OC70 0.10
2N3395 0.20	AUY10 1.00	OC71 0.12
2N3402 0.15	BC107 0.10	OC72 0.12
2N3403 0.15	BC108 0.10	OC73 0.20
2N3404 0.25	BC109 0.10	OC75 0.15
2N3414 0.20	BC113 0.10	OC78 0.15
2N3415 0.15	BC118 0.20	OC78 0.25
2N3417 0.25	BC134 0.20	OC78D 0.20
2N3702 0.10	BC147 0.10	OC81 0.20
2N3703 0.10	BC148 0.10	OC81D 0.20
2N3704 0.13	BC149 0.12	OC83 0.20
2N3707 0.13	BC159 0.15	OC139 0.80
2N3709 0.10	BC158 0.15	OC140 0.35
2N3710 0.10	BC175 0.20	OC141 0.60
2N3819 0.35	BC196 0.25	OC170 0.25
2N3906 0.25	BCY30 0.25	OC171 0.25
28702 0.50	BCY31 0.30	OC200 0.20
28746 0.25	BCY32 0.25	OC201 0.30
AC115 0.10	BCY34 0.30	OC202 0.65
AC125 0.30	BCY72 0.15	OC203 0.40
AC126 0.20	BCZ10 0.30	OC204 0.40
AC127 0.17	BCZ11 0.40	

## MULTIMETERS MADE IN USSR

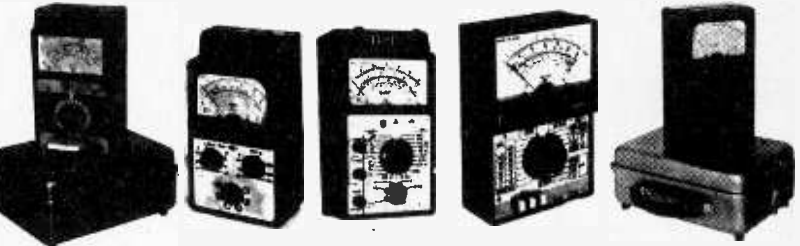

Prices of these exceptionally well made instruments range from £4.95 to £10.50. Please write for illustrated catalogue.

## SYNCHROSCOPE TYPE C1-5



Made in USSR  
3-in tube fitted with telescopic viewing hood, giving bright display in full daylight. Sensitivity 10nV/mm (narrow band) to 30mV/mm (wide band).  
Bandwidth 10 o/s-10 mc/s. Triggered sweep pre-set at 1-2.5-10-30-100-300-1000-3000 usec per stroke.  
Free-running time base 20 o/s to 200kc, with built-in crystal calibrator providing timing marks at 0.5-2-1.5-20-100 u sec.  
Amplitude calibrator directly calibrated in volts.  
Input attenuator 1-10-100.  
Power supplies 127/230v AC.  
PRICE \$39.00. Packing and carriage £1.50.

Series BZX61 1-watt ZENER Diodes  
Available in: 7.5-8.2-11.15-16-24-27-30-33-36-62-68 volts. \$0.20 each.

DIODES		
OA5 0.25	OA81 0.07	
OA6 0.15	OA85 0.07	
OA7 0.18	OA86 0.15	
OA10 0.20	OA90 0.07	
OA47 0.08	OA91 0.07	
OA70 0.07	OA95 0.07	
OA75 0.07	OA200 0.07	

## MINIATURE SILICON HALF-WAVE WIRE-ENDED RECTIFIERS

IN4002	100 p.i.v.	1A	0.07
IN4004	400 p.i.v.	1A	0.08
IN4006	600 p.i.v.	1A	0.15
IN4399	1000 p.i.v.	1-5A	0.35
IN4608	1000 p.i.v.	3-0A	0.50
BY101	450 p.i.v.	1-1A	0.15
BY105	500 p.i.v.	1-1A	0.15
BY127	1250 p.i.v.	1A	0.12
DD000	50 p.i.v.	500mA	0.15
DD006	400 p.i.v.	500mA	0.25
DD058	800 p.i.v.	500mA	0.25

## VALUE ADDED TAX

THE ABOVE PRICES DO NOT INCLUDE V.A.T. WHEN REMITTING CASH WITH ORDERS PLEASE ADD 10% OF THE VALUE OF GOODS INCLUDING POSTAGE AND HANDLING AS SOME OF THE ITEMS STILL CONTAIN THE PROPORTION OF PURCHASE TAX. RESPECTIVE AMOUNT WILL BE REFUNDED.



# FREE!

## Over 150 ways to engineer a better future



**HIGHER PAY**      **A BETTER JOB**  
**SECURITY**

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BPW06 Aldermaston Court, Reading RG7 4PF.

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/sia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £22.65. PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.** Everything you need to know

about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

**CUT OUT THIS COUPON**  
Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL A.S.E. (Mech.) Boiler Inspect. & Operation C & G Eng. Crafts C & G Fabricat. Diesel Eng. Eng. Inspection Eng. Metallurgy Inst. Eng. & Tech. Inst. Motor Ind. Mainten. Eng. Mechanical Eng. Sheet Metal Work Welding	<input type="checkbox"/> Man. Prod.—cont. Quality Control Salesmanship Storekeeping Work Study Works Management A.M.I.E.D. Design of Elec. Machines Die & Press Tool Design Electrical Draughtsmanship Gen. Draughtsmanship Jig & Tool Des. Tech. Drawing	<input type="checkbox"/> Constructional-cont. Building Building Drawing Build. Foreman Carpentry & Join. Civil & Municipal Engineering Constructional Engineering Constructional Surveyors Institute Clerk of Works Council Eng. Geology Health Eng. Hydraulics Inst. of Builders Inst. Works & Highway Sup. Painting & Dec. Public Hygiene Road Engineer. Structural Eng. Surveying
<input type="checkbox"/> ELECTRICAL & ELECTRONIC A.M.S.E. (Elec.) C & G Elec. Eng. C & G Elec. Inst. C & G Elec. Tech. Computer Elect. Elec. Maths Elec. Science Electronic Eng. Electrical Eng. Install. & Wiring Meters & Measuring Instruments	<input type="checkbox"/> RADIO & TELECOMMUNICATIONS Colour TV C & G Radio/TV/Electronics C & G Telecomm. Tech. Prac. Rad. Elec. (with kit) Radio Amateurs Exam. Radio Servicing & Repairs Radio & TV Eng. Trans. Course TV Main. & Serv.	<input type="checkbox"/> GENERAL Agricultural Eng. Council of Eng. Inst. Farm Science General Educat. Gen. Plastics Pract. Maths Pract. Slide Rule Pure & Applied Maths Refrigeration Rubber Tech. Sales Engineers Tech. Report Writing Timber Trade University Ent.
<input type="checkbox"/> MANAGEMENT & PRODUCTION Auto. Control Computer Prog. Electronic Data Processing Estimating Foremanship Inst. Cost & Man. Accountants Inst. Marketing Management Metrication Motor Trade Man. Network Plan. Numerical Cont. Operational Research Personnel Man. Planning Eng. Production Eng.	<input type="checkbox"/> AUTO & AERO Aero Eng. A.M.I.M.I. A.E.C. Cert. Auto Engineer. Auto Repair C & G Auto. Eng. Garage Management MAA/IMI Dipl. Motor Vehicle Mechanics CONSTRUCTIONAL A.M.S.E. (Civil) Architecture	<input type="checkbox"/> G.C.E. 58 'O' & 'A' LEVELS SUBJECTS Over 10,000 group passes

Coaching for many major exams. including ONC, C & G, etc.

**POST TODAY FOR A BETTER TOMORROW**

To B.I.E.T., Dept. BPW06 Aldermaston Court, Reading RG7 4PF      QN BPW06

NAME .....  
Block Capitals Please  
ADDRESS .....

OTHER SUBJECTS ..... AGE .....

Accredited by C.A.C.C.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

# Henry's

## YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

### BUILD THE TEXAN

★ FREE TEAK CABINET with complete kits!

**FEATURES.** New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

**HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES** - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

**FACILITIES.** On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector; Mag. P.U Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).  
Constructional details Ref. No. 21 30p

SPECIAL KIT PRICE **£28.50** P & P 45p  
COMPLETE WITH FREE TEAK CABINET  
Designer approved kits distributed by Henry's!

### 20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)



P.W. Tricolour as per April/May June 1973. Parts list on request (52A).

★ SLIM DESIGN WITH SILVER TRIM  
Overall chassis size 14 1/2" x 6" x 2" high

### LOW COST HI-FI SPEAKERS



E.M.I. Size 1 3/4" x 8 1/2". Large Ceramic Magnet.  
**TYPE 150** 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.  
**TYPE 150 TC** Twin cone version £2.75. Post 22p.  
**TYPE 450** 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3.50. Post 25p.  
**TYPE 350** 20 watt with tweeter and crossover. 8 and 15 ohms. £7.50. Post 28p.



**POLISHED CABINETS** 150, 150TC 450 £4.60. Post 30p.  
**ASSEMBLED IN POLISHED CABINETS** (8 ohms)  
**SERIES 6** (Assembled 150 T/C) per pair £16.50. Post 70p  
**SERIES 8** (Assembled 450) per pair £18.95. Post 70p

### TEST EQUIPMENT

Just a selection!

- SE250B Pocket Pencil Signal Injector £1.90
  - SE500 Pocket Pencil Signal Tracer £1.50
  - THL33D Robust 2K/Volt £4.35 with case £4.95
  - 5015 Grid Dip Meter 440 KHz-280 mHz £13.45
  - TE10 30 KJV Multimeter £9.25 With leather case £10.50
  - 200H 20K/V Multimeter £4.20. With case £4.95
  - AF105 50K/V Multimeter £8.50. With case £9.50
  - U4341 AC/DC Multimeter with transistor tester with steel case £10.50
  - TE20D RF Generator 120KHz-500MHz £16.50. Carr. 35p
  - TE22D Audio Generator 20Hz-200KHz £17.50. Carr. 35p
  - CI-5 3" Pulse Scope 10Hz-10mHz £39.00. Carr. 50p
  - TE65 Valve Voltmeter 28 ranges £17.50. Carr. 40p
- ALL NOMBREX MODELS IN STOCK



### ML-3 MW/LW TUNER to BUILD



Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". TOTAL COST TO BUILD £4.85. Post 15p. All parts sold separately. Leaflet No. 6

### "BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning. 600 mW push-pull output. Fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.  
TOTAL COST TO BUILD £7.98 p.p. 32p. (Battery 22p).

### PA-Disco-Lighting


UK's Largest Range—Write phone or call in. Details and demonstrations on request.



- DJ30L 3 Channel sound to light unit, 3kW. £29.50
- DJ40L 3 channel Mic (built-in) to light, 3kW. £38.75
- DJ70S 70 watt Disco amp/mixer. £49.75
- DISCOAMP 100 watt amp/mixer, £68.85
- DJ105S 30 watt Disco amp/mixer, £32.25
- Anti-Feedback Quality Mic., £11.50
- DJ500 50 watt PA Amplifier £43.95
- DJ700 70 watt £52.75
- DJ1000 100 watt £63.00
- GROUP 300 150 watt rms "Group" Valve Amplifier £86.00
- FIBRE OPTICS LIGHTING. — MICS. EFFECTS. PROJECTORS. SPOTS. DIMMERS — STANDS. MIXERS. SPEAKERS. Everything for PA — Disco — Lighting.
- FREE Stock List Ref. No. 18
- PORTABLE DISCOS — DETAILS ON REQUEST
- CREDIT TERMS FOR CALLERS
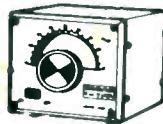
### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO.  
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.  
TOTAL £6.97, p.p. 20p. Mk. I Decoder Kit £5.97.  
Built IC Decoder £6.50. Tuning meter unit £1.75.  
Mains unit for Tuner and/or Decoder P56/12 £3.25. Post 20p



### SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!

- Z30 £3.57; Z50 £4.37
- STEREO 60 PZ5 £3.97
- £7.97; PZ8 £4.77
- PZ6 £6.37;



Transformer for PZ8 £2.95  
Active Filter Unit £4.45  
Stereo FM Tuner £16.95  
IC12 £1.80; Q16's £15 pr.  
Post etc. 20p per item

**PACKAGE DEALS** Post 25p  
2xZ30, Stereo 60, PZ5 £15.95  
2xZ30, Stereo 60, PZ6 £18.00  
2xZ50, Stereo 60, PZ8 £20.25  
Transformer for PZ8 £2.95  
PROJECT 605 KIT £19.95

### ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

### IC RECEIVER

ZN414 Radio integrated circuit as featured in Practical Wireless, January 1973. Article Reprint Ref. No. 19 10p. Price £1.20.

### BATTERY TAPE DECK

Garrard 9 volt Tape Deck with heads, etc. As previously advertised. Limited quantity. £9.50, post 30p.

### LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish Italian. £1.36 per course. £5.00 per set of four.

### DISCO SPOTBANK

3 channel Disco Spotbank for use with any psychedelic lighting display. £12.75, p. & p. 35p.

### HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES. FREE—24 page detailed brochure (Ref. No. 17). You can see the savings!

### HIGH QUALITY CASSETTES

The best UK low noise tapes but at a special price. 'Living Sound' cassettes meet the highest international standard (IEC 94A). Fantastic price savings.

	3 for	6 for	10 for
C60	1.00	1.80	2.80
C90	1.32	2.54	4.20
CI20	1.62	3.15	5.00

Full guarantee. Extra paid Made by EMI especially for Henry's.

### ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and new I.C. circuits. £5.90 per pair. Post 10p

### MARROT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO  
'17' High Impedance £2.00  
'18' Med. Imp. £2.00  
'36' Med.-Low Imp. £3.50  
Erase Heads for above 75p  
'63' 2 track mono- £1.75  
Hi Imp.  
'43' Erase Head for above 75p

### 7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)  
XN3, XN13, GN6 0-9 side view with data, 85p.  
GNP-7, GNP-8 0-9 side view with decimal points and data, 95p  
3015F 7 seg £2 each. £7 per 4 with data.  
12 and 24 hour clock circuits Ref. No. 31 15p.

### Miniature Amplifier

5 transistor. Complete with knobs. Fitted volume and sensitivity control, 9 volt operated. £1.75 each P/P 15p.

### Quality Slider Controls


60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 50K, 100K, 250K, 500K. 1 meg, Log and Lin. 40p each, 10K, 25K, 50K, 100K, 250K, Log and Lin ganged, 60p each.

## CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

Post Paid 55p (40p FOR CALLERS)  
PLUS! FIVE 10p VOUCHERS

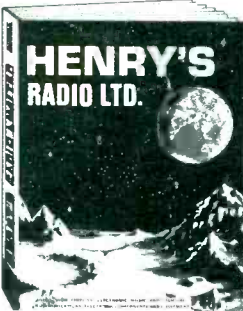Send to this address—HENRY'S RADIO LTD. (Dept. PW) 3 ALBEMARLE WAY, LONDON, E.C.1.—for catalogue by post only. All other mail and callers to "303" see below.



## VAT

All prices are exclusive of 10% VAT which must be added to all orders inc. carr/packing. (Note: Catalogue is not subject to VAT).

See earlier page of this magazine for transistors, I.C.'s and Semi Conductor prices—latest list Ref. no. 36 on request. E. & O.E.

# Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381  
354-356 High Fidelity and Tape Equipment 01-402 5854/4736  
309 PA-Disco-Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW

Open: 9 am-6 pm  
6 days a week  
(309 closed Thursday)  
All stores open all day Saturday