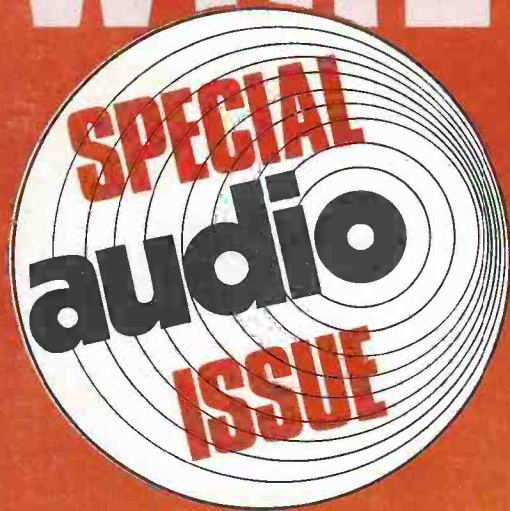


# PRACTICAL WIRELESS

NOVEMBER  
1974

25p



**ADD-ON STEREO  
HI-FI UNITS**

**ALSO:-**

**Section 2 of the  
P.W. BUYERS' GUIDE**

**AND**

**CONCLUDING THE**

**P.W. TELE-TENNIS**  
- FINAL ADJUSTMENTS



**SCRATCH & RUMBLE FILTER**



**TONE  
CONTROL UNIT**

# NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit  
Build these projects without soldering iron or solder


- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator.
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.

**Total Building Costs**  
**£7-23** P P & Ins. 44p  
(Overseas P & P £1-85)  
(+ 8% VAT 57p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/4" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).

## NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

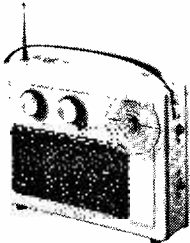


Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors. 3 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/4". Parts Price List and Plans 30p. (Free with parts).

**Total Building Costs** **£6-95** P P & Ins. 44p  
(Overseas P & P £1-85)  
(+ 8% VAT 55p)
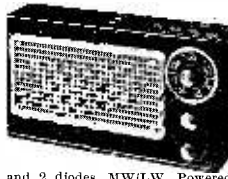
## NEW Everyday Series

Build this exciting New series of designs



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/4" approx. Parts Price List and Plans 15p. Free with parts.

**Total Building Costs** **£2-95** P P & Ins. 30p  
(+ 8% VAT 23p)  
(Overseas P & P £1-25)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans 15p. Free with parts.


**Total Building Costs** **£3-60** P P & Ins. 30p  
(+ 8% VAT 29p)  
(Overseas P & P £1-25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW. Trawler Band, SW1, SW2, SW3. Powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans 20p. Free with parts. Overseas P & P £1-05.

**Total Building Costs** **£4-08** P P & Ins. 31p  
(Overseas P & P £1-85)  
(+ 8% VAT 32p)

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

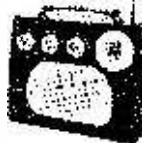


7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 3 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

**Total building costs** **£6-98** P P & Ins. 47p  
(Overseas P & P £1-85) (+ 8% VAT 36p)

## ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

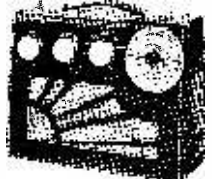


10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeakers. 9 Tunable Wavebands. MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band.

Built in Ferrite Rod Aerial for MW/LW. Chrome plated 7 section Telescopic Aerial can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).


**Total building costs** **£8-50** P P & Ins. 62p  
(Overseas P & P £1-85) (+ 8% VAT 68p)
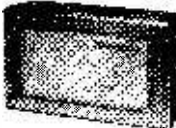
## POCKET FIVE

NOW WITH 3" LOUD-SPEAKER. 3 Tunable wavebands, M.W. L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/4" approx. Plans and Parts Price List 15p (Free with parts).



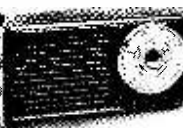**Total Building Costs** **£2-50** P P & Ins. 26p  
(+ 8% VAT 20p)  
(Overseas P & P £1-25)



## TRANSONA FIVE

NOW WITH 3" LOUDSPEAKER. Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 15p (Free with parts).


**Total Building Costs** **£2-75** P P & Ins. 26p  
(+ 8% VAT 21p) (Overseas P & P £1-25)

## TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/4in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

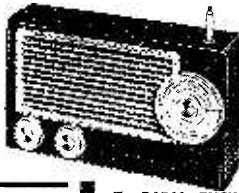**Total building costs** **£4-48** P P & Ins. 33p  
(+ 8% VAT 36p)  
(Overseas P & P £1-25)



## ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2. Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/4in. approx. Plans and parts price list 25p (FREE with parts).

**Total building costs** **£3-98** P P & Ins. 31p  
(+ 8% VAT 32p) (Overseas P & P £1-85)

## "EDU-KIT"



Build Radios, Amplifiers, etc. from easy stage diagrams.

Five units including master unit to construct.

Components include: Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine Tone 3" Moving Coil Speaker; Terminal Strip; Ferrite Rod Aerial; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

**Total building costs** **£5-50** P P & Ins. 33p  
(Overseas P & P £1-85) (+ 8% VAT 44p)

## RADIO EXCHANGE LTD

★ Callers side entrance "Lavelis" shop.  
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA  
Tel.: 0234 52367. Reg. No. 788972.

I enclose £..... for .....

Name .....

Address .....

(Dept. PW11.)

# PRACTICAL WIRELESS

VOL. 50 NO. 7  
ISSUE 813  
NOVEMBER 1974

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

## EDITOR

Lionel E. Howes, G3AYA

## ASSISTANT EDITOR

Eric Dowdeswell, G4AR

## ART EDITOR

Peter Metalli

## PRODUCTION & NEWS

EDITOR Colin R. Riches

## PROJECTS SUB-EDITOR

Geoffrey C. Arnold

## TECHNICAL ARTIST

Alan Martin

## SECRETARIAL

Susan King

01-634 4292

## ADVERTS. MANAGER

01-634 4293

Roy Smith

## CLASSIFIED ADVERTS.

01-634 4301

Colin R. Brown

Published by IPC Magazines Ltd.,  
Fleetway House, Farringdon Street,  
London EC4A 4AD. Tel. 01-634 4444

## SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.25 and to the rest of the world £4.35 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.34) and indexes 30p (inc. VAT) can be supplied by the Binders Dept at the same address.

## BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

## COPYRIGHT AND QUERIES

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

## ● NEWS & COMMENT

- 602 EXHIBITIONS?!—Leader article
  - 603 NEWS... NEWS... NEWS and December preview of PW.
  - 609 NEXT MONTH IN PRACTICAL WIRELESS
  - 636 PRODUCTION LINES—Products reviewed by *Colin Riches*
  - 637 TELEVISION—Coming in the December issue
  - 642 HOTLINES on recent developments by *Ginsberg*
  - 649 ON THE AIR Amateur Bands—*Eric Dowdeswell G4AR*
  - 650 Medium Waves—*Charles Molloy*
- PW AT THE AUDIO FAIR—see pages 633 and 635**

## ● CONSTRUCTIONAL

- 604 FM AERIAL PRE-AMPLIFIER—*Keith Cummins*
- 607 "SANDOWN" FM STEREO TUNER PART 2—*J. R. W. Ames, B.Sc. and M. J. Carey, B.Sc.*
- 621 TELE-TENNIS Part 5—*M. J. Hughes, M.A.*
- 625 TAKE 20 No. 65 Electronic Pushbutton Switch—*David Andrews*
- 626 ADD-ON STEREO HI-FI UNITS—*A. Foord*
- 638 EXPERIMENTAL WORKSHOP RC Filters—*M. J. Hughes, M.A.*

## ● OTHER FEATURES

- 617 SWITCH ON SOMEBODY!—*Geoffrey Smith*
- 634 SPECIAL PRODUCT REPORT—Heathkit SW-717G Medium and Short Wavebands Receiver
- 637 TECHNICROSS No. 7
- 645 IC OF THE MONTH—National Semicon LM1820N AM Superhet

**PLUS BUYERS' GUIDE to Radio and Electronic Components—PART 2**

## STAFF CHANGES

**Lionel Howes has been appointed Editor of Practical Wireless and of our associate magazine Television. Eric Dowdeswell has been appointed Assistant Editor of Practical Wireless.**

# HUGE DISCOUNTS

**ON LEADING BRAND HI-FI ALL RSC PRICES INCLUDE VAT LOW DEPOSIT CREDIT TERMS**

\*Full labour and material guarantees for 12 months

	List Price	RSC Price
WHARFEDAILE DENTON	£42.31 Pr.	£29.95
WHARFEDAILE LINTON	£52.39 Pr.	£38.95
LEAK 250 SPEAKERS	£65.48 Pr.	£42.00
LINEAR 202 AMPLIFIER	£39.23	£24.95
ROTEL RT222 AM/FM Tuner	£50.57	£36.95
ROTEL RT322	£73.16	£53.50
ROTEL RX150 A Tuner/Amp	£77.09	£54.95
LEAK 2000 Tuner/Amp	£165.70	£134.95
Wharfedale Denton Tun/Amp	£93.28	£59.95
RANK 150a Stereo System	£139.90	£79.95

Also Shure Cartridges, Basf Tape, Koss H/Phones, etc. Prices of above correct at Sept 25 1974

## AKAI TAPE UNITS

Model	Rec. Price	All £1 carr.
GXC 36D	£110.72	£72.50
GXC 38	£147.19	£104.95
GXC 38D	£137.38	£97.95
GXC 46D	£157.59	£109.95
GXC 40T	£186.09	£135.95
GXC 75D	£199.90	£142.95

## GXC 510D

Model	Rec. Price	£189.90	£135.95
GXR 82D	£122.65	£89.95	
4000 DS	£130.12	£94.95	
4000 DB(Dolby)	£196.27	£139.95	
1721 L	£118.58	£84.95	
CR 81D	£98.10	£69.95	
CS33D	£105.81	£75.95	

**GOLDRING GL72 T/Table & G800 £29.95** (Approx. value £46) Carr. 75p  
**GOLDRING GL75 T/Table & G800 £34.95** (Approx. value £65) Carr. 85p  
**PIONEER PL12D T/Table on plinth & cover £41.75** List £61.90  
**BSR TD8S 8 track player. Special price £14.95**  
**T/TABLES with MAGNETIC CARTRIDGE/PLINTH & COVER**  
**GARRARD SP25 MK IV with G850 Special Price £19.95** (Carr. £1)  
**MCDONALD MP60 with G800 or G850 " " £19.95** (Carr. £1)  
**RANK BD2000** Rec. Price £67.27 **£48.95** (Carr. £1)

## FANE HI-FI LOUDSPEAKERS AT APPROXIMATELY HALF-PRICE

UNREPEATABLE OFFER BRAND NEW BOXED FULLY GUARANTEED for High-Fidelity NOT Group Disco use Available by Mail Order only due to small quantities of some models. SAE for leaflets. Please state impedance required.

Model	Price	Model	Price	Model	Price	Model	Price	Model	Price
505	£2.73	806	£2.56	121/10	£3.17	138/10LR	£2.50	138/15TLR	£4.96
506	£2.61	1001	£4.37	121/10T	£3.97	138/10TLR	£2.68	101/10A	£4.27
507	£1.08	1002	£4.19	121/11	£3.68	138/11	£3.65	101/11A	£3.64
508	£1.00	1005	£3.45	121/11T	£3.78	138/11LR	£3.97	101/11A	£3.74
801	£3.93	1006	£3.50	121/15	£4.61	138/13	£3.83	122/10	£3.17
802	£3.69	1008	£2.93	121/15LR	£5.33	138/13LR	£4.15	122/10A	£5.49
802T	£3.82	1001LR	£5.09	138/10	£2.18	138/15	£4.51	122/10LR	£6.08
805	£3.25	1005LR	£4.37	138/10T	£2.31	138/15LR	£4.83	122/10T	£5.49
								122/14LR	£9.19
								162/12	£10.94

## RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control  $\pm$  12db. Treble Control  $\pm$  13db. Selector switch for Crystal P.U. or Tape/Radio. For speaker output impedances of 3 - 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £12.95 Carr. Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £16.95 or dep. £2.12 and 8 monthly payments £2.12 (Total £19.08)

## AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE. Exceptional performance at low cost.

HF808T	8"	10W	£2.55	HF120D	12"	15W	£6.50
HF102D	10"	10W	£3.65	HF120L	12"	15W	£7.95
HF120	12"	15W	£5.95	HF126D	12"	16W	£8.50

## FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15  $\Omega$ . PLEASE STATE IMPEDANCE REQUIRED List £4.42 **£3.99**  
**MODEL 808T 8" 15w.** with parasitic Tweeter. Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15  $\Omega$ . List £6.33 **£5.50**

## HI-FI 8" x 5" 7 watt SPEAKERS

with parasitic Tweeter 8 ohm imp. P.p. 20p **£1.25**

## R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET Only high grade components by leading manufacturers

- \* Push Button Selector Switching
- \* Jack Socket for Headphones
- \* Neon Indicator
- \* Satin Silver Finish Metal Fascia
- \* Solid State Circuitry
- \* Twenty Silicon Transistors
- \* Four Diodes, Four Rectifiers

Send S.A.E. for full descriptive leaflet.

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8  $\Omega$ . Frequency Response 7 Hz to 70 KHz  $\pm$  1  $\frac{1}{2}$  dB.

COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £4.90 extra. Assembled unit in cabinet **£22.50**

## R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED.

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.	TOP SHROUDED DROP-THRO' TYPE
250v, 60mA, 6-3v, 2a	250-0-250v, 70mA, 6-3v, 2a, 0-5-6-3v, 2a
250-0-250v, 60mA, 6-3v, 2a	250-0-250v, 100mA, 6-3v, 3a
	250-0-250v, 100mA, 6-3v, 2a, 6-3v, 1a
	350-0-350v, 80mA, 6-3v, 2a, 0-5-6-3v, 2a
	250-0-250v, 100mA, 6-3v, 4a, 0-5-6-3v, 3a
	300-0-300v, 100mA, 6-3v, 4a, 0-5-6-3v, 3a
	300-0-300v, 130mA, 6-3v, 4a, c.t., 6-3v, 1a
	350-0-350v, 100mA, 6-3v, 4a, 0-5-6-3v, 3a
	300-0-300v, 100mA, 6-3v, 4a, 0-5-6-3v, 3a
	300-0-300v, 130mA, 6-3v, 4a, c.t., 6-3v, 1a
	Suitable for Mullard 610 Amplifier
	350-0-350v, 150mA, 6-3v, 4a, 0-5-6-3v, 3a
	WILMINGTON or TRANSISTOR POWER PACK
	6-3v, 1a, £7.75; 6-3v, 2a, £8.95; 6-3v, 3a, £1.45p;
	6-3v, 6a, £2.25; 12v, 1a, 80p; 12v, 3a, or 24v, 1a
	1-5a £2.25; 0-9-18v 1 1/2a £1.95; 0-12-25-42v 2a £2.75.

## HI-FI SPEAKER ENCLOSURES

TEAK VENEER Carr. 50p. Sizes approx. per enc. Cut for 8in. spkr. **£5.95**  
 SE10 25 x 16 x 9in. Cut for 10in. and Tweeter **£8.95**  
 SE12 25 x 16 x 9in. Cut for 12in. and Tweeter **£8.95**

## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 Gauss 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range **£7.50** Carr. 45p  
 OR SENIOR 15 WATT INCLUDING **£7.95** Carr. 50p  
 HF126 15,000 GAUSS SPEAKER

## R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Response 30-20,000 c.p.s. -2dB. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. O/P rating I.H.F.M. Enclosed enamelled case 9 1/2 x 2 1/2 x 3 1/2 in. Silver finish fascia 10 1/2 x 3 1/2 in. COMPLETE KIT, wiring diagrams and instructions. **£7.95** Carr. 40p. FACTORY BUILT **£10.95**

## R.S.C. TA12 MKIII 6.5+6.5 WATT STEREO AMPLIFIER

Fully Transistorised. Hi-Fi o/p of 6.5 watts per channel. Optimum performance with any crystal or ceramic P.U. Cartridge, Bass Tuner, Tape Rec. etc. Input Sel. Switch, Bass, Treble, Vol. & Bal. Controls. COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS **£12.95** Carr. 40p.  
 Factory built with 12 mths guarantee **£16.61** Or in Teak Veneer housing **£19.55** Dep. £2.50 & 8 mthly pymts **£22.50** (Total £28.50).

## AUDIO FIDELITY FRI SPEAKER KIT

Response 30Hz-15KHz. Rating 15 watts in sealed cabinet. Imp. 8-15 ohms. 8" Bass Unit with P.V.C. Cone surround (or ultra low resonance. Pressure Tweeter. Printed Circuit. Inductive/Capacitive Cross-over. Damping Material, Screws, Terminal Panels. Carr. each **£10.78**  
**SPECIAL OFFER £14.99** Pair 50p Carr. Free.

## 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx.  
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms  
 Performance comparable with COMPLETE KIT units at twice the cost **£25.95** Carr. 75p  
 Deposit £4.71 and 8 monthly payments £3.12 (Total £29.87)  
 Consists of (1) 12in. 15w Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) Dome Pressure Tweeter. (5) 6L6, KT66, etc. for 3 or 15  $\Omega$ . (6) Handmade Teak veneered cabinet. (7) Circuit and full instructions.

## CHARGER TRANSFORMERS 0-9-15v, 1 1/2a £1.75

CHARGER TRANSFORMERS 0-9-15v, 1 1/2a £1.75	SELENIUM RECTIFIERS F.W. (Bridged)
2 1/2a. £1.95; 3a. £2.40; 5a. £2.45; 6a. £2.75; 8a. £3.40	All 6/12v. D.C. output. Max. A.C. input 18v.
AUTO (Step Up/step DOWN) TRANSFORMERS	1a, 39p, 2a, 49p, 3a, 65p, 4a, 81p, 6a, 97p.
0-110/120v. 200-230-250v. 50-80 watts £2.50, 150 watts, £4.50 250 watts £5.50; 500 watts £8.50	L.F. CHOKES
OUTPUT TRANSFORMERS	150mA, 7-10H, 250 $\Omega$ £1.10; 100mA, 10H, 200 $\Omega$ 85p
Push-Pull 8 watts EL84 to 3 or 15 $\Omega$ £1.45	60mA, 10H, 400 $\Omega$ 35p.
Push-Pull 10 watts 6V6, 3-5-8-15 $\Omega$ £2.25	
Push-Pull EL84 to 3 or 15 $\Omega$ 10-12 watts £2.25	
Push-Pull Ultra Linear for Mullard 610, etc. £2.75	
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 $\Omega$ £3.20	
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 $\Omega$ £5.50	



# RSC 100 watt DISCO SYSTEM



50 WATT SPEAKER  
50 WATT SPEAKER  
TWIN TURNTABLE WITH PRE-AMP and POWER AMPLIFIER

AT FANTASTIC LOW PRICES!

Complete with lid HEADPHONES MICROPHONE

Units listed below  
(a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier.  
(b) PAIR OF HI-FI HEAD- PHONES  
(c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)  
(d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 8"  
(e) (b) (c) & (d) **£149-95**  
Carr. £3-00

**RSC TDI DISCO CONSOLE**  
Incorporating twin Garrard SP25 or BSR MP60 type turntables and Sonotone or Acos Cartridges with diamond stylus. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid, see illustration on left.  
Or Dep. £6-00 and 18 fortnightly pymts. £4-22 (Total £54-96) Carr. £1-50  
**£75-00**

DEP. £19-95 & 19 fortnightly. payments of £7-87 (Total £169-48).

## DISCOMASTER TWIN TURNTABLE POWER CONSOLE

Garrard SP25 or McDonald MP60 turntables. Sonotone or Acos cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit **£11-48** and 18 fortnightly payments **£5-74** Carr. £2-50 (Total £114-80) **£99-95**

**R.S.C. COLUMN SPEAKERS** IDEAL FOR VOCALISTS AND PUBLIC ADDRESS  
All types 15 Ohms covered in Rexine and Vynair  
**TYPE C132 30-40 WATTS** Fitted two exceptionally efficient, low feedback howl characteristic high flux 12" x 8" x 20 watt speakers. Terms: Dep. **£3-95** and 8 m'thly payments **£2-67** (Total **£25-81**) Carr. 65p.  
**TYPE C8/70 70 WATTS.** Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 64" x 14" x 11". Dep. **£5-11** and 8 m'thly pymts. **£5-11** **£39-95** (Total **£45-99**) Carr. 85p

## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEED High flux ceramic magnets. ALL CARRIAGE FREE.  
**'POP' 100** 18" 100Watt 14,000 gauss 8/15Ω **£29-95**  
Dep. **£3-80** and 8 m'thly payments **£3-80** (Total **£34-20**)  
**'POP' 60** 15" 60 Watt 14,000 gauss 8/15Ω **£16-95**  
Dep. **£2-12** and 8 m'thly payments **£2-17** (Total **£19-58**)  
**'POP' 50** 12" 50 Watt 13,000 gauss 15Ω **£12-95**  
Terms for pairs Dep **£3-90** & 8 m'thly pymts **£2-16** Total **£29-18**  
**PAIR SUITABLE ALL PURPOSES**

**FANE POP '55'** 12" 60 watt 15000 gauss 8-15Ω **£15-99**  
**PH50 Power Tweeter** 50w with rec. filter for improved vocal sound **£5-95**

**FANE SPEAKERS 'POP' 25/2 12 in. 30 WATT**  
Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free **£8-95**  
CREDIT TERMS (PAIRS ONLY) Dep. **£2-80** & 8 m'thly pymts. **£2-30** (Total **£21-20**).

## GROUP EQUIPMENT PACKAGE OFFERS

**F.A.L. PHASE 50 MK. III AMPLIFIER** **£43-95** PACKAGE PRICE  
**FE. FANE POP 50'S ROW L/SPEAKERS** **£17-90** carr.  
Terms: Deposit **£7-85** and 8 monthly payments of **£7-05** (Total **£60-15**) **£61-85** **£56-95** £1-10  
**F.A.L. PHASE 50 MK II AMPLIFIER** **£43-95** PACKAGE PRICE  
**FE. FANE POP 40 L/SPEAKERS** **£25-90** carr.  
Terms: Deposit **£22-00** and 12 monthly payments of **£4-20** (Total **£72-40**) **£69-85** **£63-95** £1-10  
**F.A.L. PHASE 50 AMPLIFIER** **£43-95** PACKAGE PRICE  
**FAIR L12/20 SPKRS (in Cabinets)** **£25-90** carr.  
Terms: Deposit **£22-00** and 12 monthly payments **£4-20** (Total **£72-40**) **£69-85** **£63-95** £2-00

## ALL RSC PRICES INCLUDE VAT


INTEREST CHARGES REFUNDED on Credit Purchases settled in 3 months

**MINSTREL 8W GUITAR AMP.**  
Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 4 watts R.M.S. Continuous. 3 Jack inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity.  
Terms: Deposit **£4-40** and 8 monthly payments **£2-67** (Total **£25-78**) Carr. free **£19-95**

**FANE CRESCENDO SPEAKERS**  
Full range available at ALL BRANCHES
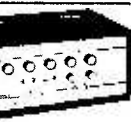
## FAL PHASE 50 Mk. III AMPLIFIER 50 WATT

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speaker's 8 to 15 ohms. Size 17" x 7" x 7 1/4". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit **£5-75** & 8 monthly payments **£2-75**. Total **£51-75**. Carr. Free **£43-95**



## RSC PHANTOM '50'

Combined 50W Amplifier and 12in. Loudspeaker.  
For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle.  
Terms: Deposit **£6-30** and 8 monthly payments **£6-30** (Total **£67-51**). Carr. £1-50  
SAB for leaflet UK Mainland **ONLY £49-95**  
SPECIAL PRICE for limited period



## HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH  
**L125 50 WATT** Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50  
Or deposit **£5-11** and 8 monthly pymts. of **£5-11** Total **£46-99**  
**L12/25G 12" 95 WATT** 13,000 gauss cabinet 12" unit 8-15 ohm  
Lines 15 ohms Terms for Pairs. Dep **£3-22** & 8 m'thly pymts **£3-22** (Total **£29-88**) Carr. 55p. **£12-95**  
**L22B/15W 15" Veneered cabinet 15" unit 8-15 ohm** Approx. 14" x 14" x 9". Carr. 65p. Terms for Pairs. Dep. **£2-05** & 8 m'thly pymts **£2-05** (Total **£18-45**) **£7-95**

## REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 50w Peak O/P rating. Not for Bass Guitar.  
★ Two Fane heavy duty high flux 12in. spkrs.  
★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit **£7-98** & 18 fortnightly payments of **£3-99** (Total **£78-80**). Carr. £2-50 **£69-95**  
**REGENT 50B** for Bass Guitar and general purposes. Or Dep. **£9-18** & 18 fortnightly payments **£4-59**. (Total **£81-80**). Carr. £2-50 **£79-95**

## GP30 AMPLIFIER For Guitar, Vocal or Instrumental Group

A 4 input, 2 vol. control HI-FI 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet.  
Terms: Deposit **£5-58** and 8 monthly payments of **£3-58** (Total **£34-22**). Carr. 75p. **£29-95**

## C4/100 HEAVY DUTY COLUMN SPEAKERS

Suitable for Public Address or Vocal and Instrumental Groups. Fitted four 12" 50 watt speakers. Robust attractive Vynide covered cabinet 58" x 16" x 10" approx. Limited stocks at SPECIAL PRICE **£1-50** **£95-95**  
Or Dep. **£20** and 12 m'thly pymts **£3-80** (Total **£68-80**).

## DISCO LIGHTING AT KEEN PRICES

NEW BRANCHES AT  
**BOLTON, COVENTRY DONCASTER, PRESTON and STOCKPORT**

## FAL DISCO PRE-AMPLIFIER

Mic. Jack & Tape inputs. Independent Vol. Control Std. 200-250v A.C. Mains operation **£18-50**

## TITAN 18" 100W SPEAKERS

15 ohms (List £33) Carr. 75p **£25-95**

**R.S.C. BRANCHES OPERATE A 5-DAY WEEK**  
OPEN ALL DAY SATURDAY  
**BRADFORD** 10 North Parade (Closed Wed.) Tel. 25349  
**BRADFORD** 23 Deansgate. (Closed Wed.) Tel. 33512  
**BIRMINGHAM** 30/31 Great Western Arcade.  
**COVENTRY** 17 Shelton Square, The Precinct. Tel. 021-236 1279 (Closed Wed.)  
**DERBY** 97 St. Peter's Street. (Closed Wed.) Tel. 25983  
**DARLINGTON** 19 Northgate (Closed Wed.) Tel. 41361  
**GLASGOW** 328 Argyle St. (Closed Tues.) Tel. 248 4158  
**HULL** 7 Whitefriargate (Closed Thurs.) Tel. 20305  
**LEICESTER** 32 High Street (Closed Thurs.) Tel. 56420  
**LEEDS** 5-7 County (Mecca) Arcade, Briggate (Closed Wed.) Tel. 28252  
**LIVERPOOL** 73 Dale St. (Closed Wed.) Tel. 236 3573  
**LONDON** 238 Edgware Road, W.2. (Closed Thurs.) Tel. 723 1629  
**MANCHESTER** 60A Oldham Street (Closed Wed.) Tel. 47096  
**MIDDLEBROUGH** 106 Newport Road (Closed Wed.) Tel. 47096  
**NEWCASTLE UPON TYNE** 24 Newgate Shopping Centre (Closed Wed.) Tel. 21469  
**NOTTINGHAM** 19/19A Market Street (Closed Thurs.) Tel. 48068  
**PRESTON** 41 Friargate Walk, St. Georges Shopping Centre (Closed Thurs.) Tel. 51979  
**SHEFFIELD** 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.) Tel. 20716  
**STOCKPORT** 8 Little Underbank (Closed Thurs.) Tel. 480-0777  
**SUNDERLAND** 5 Market Sq. (Closed Wed.) Tel. 70573



Barclaycard and Access accepted  
All items subject to availability. Prices correct at 25.9.74 E. & O.E.

MAIL ORDERS & EXPORT ENQUIRIES TO—  
AUDIO HOUSE, HENCONNER LANE, LEEDS, 18. Tel: Pudsey (09735) 77681.  
MAIL ORDER MUST NOT BE SENT TO SHOPS  
TERMS C.W.O. or O.O.D. No O.O.D. under £1.  
POSTAGE 40p PER ORDER OR AS QUOTED.  
TRADE SUPPLIED.  
S.A.E. PLEASE WITH ENQUIRIES.

# ESSENTIAL BOOKS FOR RADIO AMATEURS

## TEST EQUIPMENT for the radio amateur

by **H. L. Gibson, CEng, MIEE, G8CGA**

Explains in detail the theory behind modern measurement techniques, and describes many items of equipment of special interest to the home constructor. Topics include signal sources, attenuators, oscilloscopes, swept measurements, aeriads and transmission lines. Detailed instructions are given for the construction of many items of test gear.  
120 pages £2.15 post paid

## TELEPRINTER HANDBOOK

by **D. J. Goacher, G3LLZ, and  
J. G. Denny, G3NTT**

A brand new book covering all aspects of modern teleprinter techniques. Full descriptions and maintenance data for all widely-used machines, together with design and use of ancillary equipment. Definitely a book for the teleprinter enthusiast's work bench.  
376 pages £5.40 post paid

## A GUIDE TO AMATEUR RADIO

by **Pat Hawker, G3VA**

This extensively revised 15th edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby, it covers technical, operating and licensing matters.  
96 pages Price 95p post paid

## RADIO AMATEURS' EXAMINATION MANUAL

by **G. L. Benbow, G3HB**

The standard book for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination. Fully up-to-date to meet the present examination syllabus requirements.  
96 pages Price 95p post paid

These are just four of a complete range of technical publications, log books and maps for the radio amateur. Send a large s.a.e. for the complete list.

The **RSGB** is the national society representing all **UK** radio amateurs. Membership is open to all interested in the hobby: write to the **General Manager** and ask for full details.



## RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688

# ADCOLA SOLDERING KITS

## INCLUDES THE FAMOUS 'INVADER' SOLDERING INSTRUMENT

**£4.73**  
INCLUDES VAT  
POSTAGE  
FREE!



A quality soldering kit at a price which may never be repeated due to rising costs. The kit comprises of the renowned Invader Soldering Tool (high safety standards low leakage with easily removable bits). Two spare specially shaped bits (heavy duty and P.C.B. work). Safety stand with bit storage provision, dispenser of multi cored solder, and hints and tips soldering leaflet, all in a presentation styrene pack. Attach your plug and solder with Adcola.



**POST NOW TO!**

ADCOLA PRODUCTS LTD, ADCOLA HOUSE GAUDEN ROAD, LONDON, SW4 6LH  
V. A. T. REGD. No. 235 6153 72 REGD. No. 442762

ENCLOSING P/O, CHEQUE FOR SOLDERING KITS/£  
NAME

ADDRESS

# PE SCORPIO Mk 2 ignition system kit new from ELECTRO SPARES

- \* 6 OR 12 VOLT
- \* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System—with a big plus over all the other kits—the PE Scorpio Kit is designed for both positive and negative automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well. Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages.

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn

#### Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.  
Ready Made Unit £14.75 inc. VAT and p & p.  
State 6V or 12V system.

Send SAE now for details and free list.

#### FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics', Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

#### 'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

# ELECTRO SPARES



The Component Centre of the North  
288 ECCLESALL RD., SHEFFIELD S11 8PE (C)  
Tel: Sheffield (0742) 668888

# Guest Speaker


## The Castle 8.RS.DD.



A highly sensitive, full range eight inch unit designed for use in the recommended cabinet, or one of similar dimension.

Suitable for use with good quality stereo installations, tape recorders, car radios, public address and background music systems, it has a frequency range of 50 to 20,000 kHz - the lower limit variable with increases in cabinet volume. Recommended retail price is £9.00 excluding VAT.

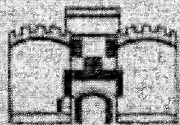*Aluminium Völké Coil  
High Flux 14,000 Oersted's Ceramic Magnet  
Roll Surround  
Double Diaphragm  
8" Die-cast Chassis  
8 ohms Impedance  
15 Watt DIN Power Handling*



# Castle Acoustics Limited

Park Mill, Shortbank Road,  
Skipton, Yorks. Tel: Skipton 5333

# THE NEW NELSON-JONES FM TUNER



**PUSH-BUTTON VARICAP DIODE TUNING (6 Position)**

('WW' JUNE '73)

Exclusive Designer Approved Kits

What are the important features to look for in an FM tuner kit? Naturally it must have an attractive appearance when built, but it must also embody the latest and best in circuit design such as:-

- MOSFET** front end for excellent cross modulation performance and low noise.
- 3 GANG** tuning for high selectivity.
- VARICAP** tuning diodes in back to back configuration for low distortion.
- CERAMIC** filters for defined IF response.
- INTEGRATED** circuit IF amplifiers for reliability and excellent limiting/AM rejection.

- PHASE LOCKED** Stereo decoder with Stereo mute, see below
- LED** fine tuning indicators.
- PUSH BUTTON** tuning (with AFC disable) over the FM band (88-104)
- IC STABILIZED** and S/C protected power supply.
- CABINET** double veneered against warp.

The Nelson-Jones Tuner has all of these features and many more, and more importantly the design is fully proven not just with a few prototypes but with many thousands of working tuners spread across the world.

Typ. Specn: 20 dB quieting 0-75uV, Image rejection -70dB.I.F. Rejection -85 dB.


Basic tuner module prices start as low as **£12.31**, with complete kits starting at **£26.95** (mono) + P.P. 65p, and of course all components are available separately.

Our low cost alignment service is available to customers without access to a signal generator. Please send large SAE for our latest price lists which details all of the many options and special low prices for complete kits. All our other products remain available.

**PORTANT AND HAYWOOD PHASE LOCKED DECODER** (W.W. Sept. '70). Still the lowest distortion P.L. decoder available. THD typically 0.05% (at Nelson-Jones Tuner O/P level)! Supplied complete with Red LED.


Price **£7.02** when bought with a complete N-J tuner kit or **£8.29** if bought separately (P.P. 21p). **PLEASE NOTE.** Existing tuners are readily convertible and kits/parts are available for this purpose.

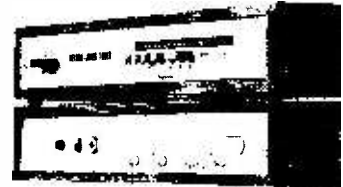**TEXAN AMPLIFIER.** We have designed the tuner case and metalwork to match the Texan amplifier (see photograph). Complete designer approved Texan kits are available at **£30.78** plus P.P. 65p including Teak Sleeve.


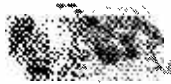
## NEW LOW COST STEREO TUNER Available as basic or complete kits

Basic stereo tuner **£15** post free.  
Basic mono tuner **£12** post free.  
6 position push button units with integral pots **£2.92**.



No alignment required. Mullard LP1186 front end module used with Ceramic IF and IC amplifier. Push button tuning (6 position) with Interstation Mute, restricted range AFC, single LED tuning indicator, phase locked IC decoder, and complete metalwork and veneered cabinet. Complete with IC regulated PSU and full assembly instructions. (Mechanically identical to N-J Tuner).

**TYP. SPECIFICATION**  
2uV for 30dB S/N  
Image rejection 40dB  
IF rejection 65dB

**PRICE Complete stereo kit £28.42**  
**Complete mono kit £24.19**  
P. & P. 65p

VAT at 8% is included in all prices

**INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW Phone Swadlincote (028387) 5432 Telex 377106**



# TRAMPUS ELECTRONICS LTD

58-60 GROVE ROAD, WINDSOR, BERKS.

FAST SERVICE SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15P. EUROPE 25P. OVERSEAS 65P.

MONEY BACK IF NOT SATISFIED. LARGE STOCKS. LOW PRICES. ALL BRAND NEW TOP GRADE FULL SPEC DEVICES. CALLERS WELCOME.

CATALOGUE/LIST FREE SEND S.A.E.

### Digital Displays



- MINITRON 3015F
- 0-9DP £1.15 ea
- LED 0.3" digit
- 0-9DP £1.49 ea
- JUMBO LED 0.6"
- 0-9DP £2.25 ea
- LIQUID CRYSTAL
- 6 digit £18

- 702 OPA 60p
- 703 RF/IF 75p
- 709 TO99 21p
- 709 DIL 14 25p
- 710 DIL 14 30p
- 720 Radio £1.99
- 723 Regulator 40p
- 741 TO99 10p
- 741 DIL8 30p
- 741 DIL14 31p
- 747 Dual 741 80p
- 748 DIL 8 35p
- 1505 IC A/D Converter £7
- 7805 IA5V £1.39
- 7808 IA8V £1.69
- 7812 IA12V £1.69
- 7815 IA15V £1.69
- 76009 3W AF 75p
- 76013 6W AF £1.39
- 8038 Sig Gen £3
- CA3046 60p
- LM301 OPA 40p
- LM307 OPA 49p
- LM508 HiBoPa 50p
- LM509K Reg. £2.10
- LM371 RF/IF £2
- LM372K AF/IF £2
- LM373 50p
- LM377 2x2W £2.99
- LM380 2W AF 99p
- LM811 2xpre. £2
- LM822 amp £2
- LM3900 4xOPA 69p

- MFC4000 1k Af 35p
- MFC4060 54p
- MFC6030 40p
- MFC6040 40p
- MFC8010 £1.10
- MFC8040 £1.10
- NE531 15V/us £2
- NE536 Fet OPA £2
- NE540 Driver £1
- NE546 AM Rx £1.50
- NE550 2v ref 79p
- NE551 TIMER 67p
- NE555 Dual £1.20
- NE561 TTL £3.15
- NE564 TTL £3.15
- NE565 TTL £3.10
- NE565 LED £2.10
- NE566 Jen £2.49
- NE567 uude £2.09
- NE7209 709 20p
- NE72741 741 31p
- NE72748 748 35p
- SN76151 £1.20
- SN76660 PMIF £1
- SN76611 IF £1.15
- TAD 100 & IF £1
- 4V00E 23
- 4N402T £1.75
- 5K403 Servo £2.50
- 2N414 AM Rx £1.09

**SPECIAL OFFERS**

741 29p MFC4000 35p  
555 67p 2N414 £1.09

BC107, BC108, BC109 9p ea  
2N3055 39p Three for £1  
115W/TO3 or 90W plastic  
2N3819E 16p 2N3053 17p  
BFY50/51/52/53 all 18p  
LASOVrect 4p ea IN914 4p

### LEDS 14P.

- MINI PIN SOURCE OR RED DIFFUSE
- LEDS. 209 STYLE. NO CLIP. 14P ea
- TIL209 RED LED & CLIP 17P ea
- ORIG 1" RED LED & CLIP 18P ea
- BAG & GREEN LEADS:
- MINI 25P ea. BIG & CLIP 35P ea
- INFRA RED LED £1.25/777 35P.
- PS12 PHOTO IC/amp/switch £1.

### DIGITAL CLOCK

- NOS INTEGRATED CIRCUITS.
- AYS1224 4 DIGIT CLOCK supplied with 14pin socket & data £4.25
- MMS511/14 6 DIGIT CLOCK with 28 pin socket & data £7.50
- 3DIGIT DVM AYS3500 £7.50
- 4DIGIT COUNTER/DRIVER £7.50

### CASSETTE mechanics £12.50

- STEREO CASSETTE MECHANISM.
- As used in imported types costing £100. Only requires a case & electronics. Heads supplied. Send for data 15p.
- MC1303 £1.20
- MC1306 £1.48
- MC1310 & LED £2.69
- MC1312 SQamp £2.50
- MC1330 60p
- MC1339 50p
- MC1350 55p
- MC1351 70p
- MC1352 70p
- MC1357 11p
- MC1358 8p
- MC1375 £1.15

### IC's & Semiconductors

### 7400 TTL

- 7400 etc gates 16p
- 7413 schmitt 51p
- 7447 driver £1.29
- 7470/72 20p
- 7473/74/76 20p
- 7475 20p
- 7476 20p
- 7490 Counter 60p
- 7492 Counter 60p
- 74121 mono 25p
- 74141 driver 20p
- Full range in Cat.

### vero

- VERO PINSx36 25p.
- 1" PER CLAD VEROBOARD 0.1"
- 21x5" 27p, 21x31" 24p, 31x31" 27p, 31x5" 29p, 31x17" £1.50
- DIL IC's BOARDS 6x4" £1.50
- 24 way edge connector 60p
- 36way 90p. PLAIN 31"x17" £1
- FACE CUTTER 43p. PEC ETCHANT

### BALOPEN69p

- PRINTED CIRCUIT BOARD KIT £1.69
- COPPER BOARD 6x4" 40p.
- DESOLDER BRAID reel 59p
- HEATSINKS
- 5f/TO5 & 18f/TO18 5p ea.
- TV4 12p. TV3/TO3 16p. 4Y1/TO3 29p
- CAPACITORS
- 22pf to 0.1uF 4p ea. ELECTROLYTIC
- 25V 2/10/50/100uF 6p. 100uF 20p
- PRESETS VERT: 5p. RESISTORS 55¢ 11p

### POTS AB or EGIN

- ROTARY: 12p. SWITCH 13p. DUAL 38p.
- SLIDERS: SINGLE 26p. DOUBLE 48p.
- SWITCHES: SPST 18p. DPDT 25p.
- MINI 1" SPST 39p. PUSH 39p.
- BENCH POWER SUPPLY 3-12V 11.
- DIN PLUGS all 13p ea. Sockets 9p
- TRANSFORMERS 1A 6/12V £1.34
- BHA 0002 MODULE 15WATT AMP £5
- EAL000 4W AF MODULE £2.49
- 8W/12V FLUORESCENT LIGHT £3

### OIL sockets

- PROFESSIONAL GOLD PLATED
- 4 GREY NYLON
- \*14 or 16 PIN ONLY 15p each.
- TA6 1/400V 55p
- C107D1 SCR 4A/400V 55p
- SC146D TRIAC 10A 400V 75p



# SAVE OVER £36 NOW!

**FIRST TIME EVER!** A Genuine **'MEMORY'** POCKET CALCULATOR  
**\*YOURS FOR UNDER 1/3<sup>RD</sup> OF IMPORTERS RECOMMENDED SELLING PRICE!**

Whether you're a business man, an atomic scientist, a shopkeeper, a housewife or a schoolboy—the **004 "MEMORY" CALCULATOR IS FOR YOU!**

THE INCREDIBLE NEW WORLD SHATTERING  
**004 "MEMORY" POCKET SIZE ELECTRONIC CALCULATOR**  
**ONLY £15.47** POST 50p INCLUDES V.A.T. NO MORE TO PAY!



**Full Business, Scientific & All Basic Mathematical Functions**

Basic Arithmetic, Chain Calculations, Percentages, V.A.T. Calculations, Net Values, Interest simple and compound, Depreciation, Mortgages and hire purchase interest and payments, Counting for stock-taking, Currency conversion, Taxation calculations, Statistics, Electronics, etc., etc., Squares, Powers of Numbers, Square Root, Reciprocals, Logarithms, Hyperbolic Functions, Equations, Physics Calculations, Sum of Product, Polynomials, Computer Maths, nTH Roots, Trigonometric and Inverse Trigonometry Functions, Exponential Functions, etc., etc., etc.

- Amazing "Brain Button" allows random MEMORY Access
- MASSIVE entry and recall capacity
- Never overflows or loses information
- Problems entered as they are spoken
- Large eight digit display
- Fully floating decimal point
- Automatic minus sign
- Automatic true credit balance plus or minus
- Percentages with automatic net value, plus or minus
- X Constant on all four functions
- Correction of entry & function entry errors
- Correction of decimal point position
- Last answer can be recalled even after clearing

**SAVE OVER £36!**  
Importers recommended price £51.79!

**NEW V.A.T. PROBLEMS SOLVED!**

The incredible new 004 "MEMORY" Calculator heralds the beginning of a new era in pocket-size electronics! And, thanks to a special arrangement we have made with the suppliers, you can be among the first in this country to own one **AND SAVE OVER £36 INTO THE BARGAIN!** Brilliantly designed! Manufactured to the highest standards! So much is incorporated into this incredibly compact product of advanced modern science it's almost unbelievable! Only 2 1/4 x 4 1/2 x 3/8 in. overall approx. So small & light-weight you can slip it into your pocket or handbag & not know it's there at all! Yet wonderful also on Desk Top, in the office, shop or home. Extremely reliable & robust. Designed to give years of perfect service. Bold, clear visual display reading. Large, well-spaced keys for fast accurate use with utmost ease. The most intricately complicated calculations completed in a wink with miraculous "space-age" electronic accuracy! Everything worked out with utter simplicity! Accountant, schoolboy or professor, the 004 "Memory" Calculator has a virtually limitless capacity to solve your every mathematical problem! Works off standard batteries (obtainable everywhere) also works off 220/250v. A.C. Mains using mains battery eliminator (available as optional extra). Brand spanking new. Complete with Owner's Manual, Quick Reference Guide, simple instructions with working examples, and **WRITTEN GUARANTEE, ONLY £15.47, post etc. 50p.** Standard battery & special protective carry case 50p extra. Mains battery eliminator £2.50 extra, if required. Buy one, or buy as many as you like! What an investment! At this incredible price you just can't lose. You save £££'s & £££'s! Send quickly, test on 7 days Mail Order approval from receipt of goods. Refund if not delighted. Or call at either store.

Order by post to Uxbridge Road or call at either store.  
**Callers: ACCESS & BARCLAY CARDS ACCEPTED**  
 Bargains galore at both stores—**(COMMERCIAL TRAVELLERS NOTE: Merchandising office at Holborn)**

## SHOPERTUNITIES LTD.

Dept WP/40, 164 UXBRIDGE ROAD, (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thur. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.



**for fast, easy reliable soldering**  
 Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

**EASY-TO-USE DISPENSERS**

**Size 5**  
 Savbit alloy 18 swg, 32p (illustrated).

**Size 19A**  
 60/40 alloy 18 swg, 34p

**Size 15**  
 60/40 alloy 22 swg, 36p

**IDEAL FOR HOME CONSTRUCTORS**

**Size 1** cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 56p

**Size 12** Reel for Service Engineers and Electricians. 18 swg Savbit alloy £1.72

**BIB WIRE STRIPPER AND CUTTER**

**Deluxe Model 9** Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex.

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to **Bib Hi-Fi Accessories Limited, Hemel Hempstead, Herts HP2 7EP**

# Train for television

Course commences 8th January, 1975

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

**THE PEMBRIDGE COLLEGE OF ELECTRONICS**  
 (Dept. PW7 34a Hereford Rd., London W2 5AJ)

**Wire Wound Resistors.** Our selection of mixed values. 30 for £1.50, 100 for £4.00.

**Audio Amplifier Module.** Mullard LP1173, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2.50.

**Ferguson Stereogram chassis** Model 3357, all transistor, medium long, VHF/FM, 3 watts per channel S/M, with connection data, less tuning scale, £20.

**Crystals HC6U:** 52 03333 MHz: 52-02500: 52 01667: 51-56667: 51-58330: 37-76250: 37-75000: 12-895-8: 12-891-6: 12-700-0: 9-458-33: 9-456-25: 9-455-55: 9-533-33: 9-531-94: 9-530-55: 9-090-62: 9-087-5: 9-096-87: 50p each.

**Electrolytics.** 32/32/32µF, 325v, 2" 1½" 35p: 2000µF 30v, 2½" 1" 25p: 2000µF 35v 3" 1" 30p: 470µF 100v 3" 1½" 25p: 2000 2000µF 25v 2" 1½" 35p: 30,000µF 25v 4½" 2½" 50p: 700µF 200v 3½" 1½" 30p: 16 16µF 275v 1½" 1" 20p: 40 40µF 275v 3" 1" 20p: 4500 900 900µF 30v 2½" 1½" 50p: 4000µF 35v 3" 1½" 40p: 200 100 50 100µF 325v 3" 1½" 50p: 4000µF 18v 2" 1" 20p: 470µF 25v 1½" 1" 15p.

**Matched pair of bookshelf speakers.** Teak finish, size 12" x 8" x 5", 8 + 5 8" ohms ceramic, 5 watts RMS. Complete with din leads. £11.00 pair.

**Thorn TV IF chassis,** 950 series (less valves), £1.75.

**UHF 625 transistor push button tuner** (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, £3.25. **Light Dependent Resistors** (RCA sq3536) 30p each, 4 for £1.00.

**P-C Boards** (not computer panels) 1 off 6 transistor single wave band. 1 off 4 transistor audio. 1 off 3 transistor £1.60, three boards.

**Rank EVR Teleplayer colour transistor panels,** type and components on new panels listed as follows, £2.50, each panel. Z605—14 off BC148: 2 RCA ca3054 (ic): 1 crystal 4-433618 MHz—Z607—12 off BC148: 1 BC108: 1 BC158: 1 RCA ca3046 (ic), 1 RCA ca3045 (ic): Z608—23 off BC148: 2 BC158—Z612—12 off ME4103: 2 BC-251B: 1 BFY50.

**Mains Droppers,** 10 mixed values, £1.00.

**Edgewise Level meters,** 200µA, size ½" overall. 50p.

**Chrome Plastic knobs,** 3 types, 4 off each with spring clip, £1.25.

**Die Cast Boxes,** 4½" x 3½" x 3" 95p: 8½" x 5½" x 2" £1.20. 8½" x 5½" x 4" £1.70.

**Aluminium Chassis,** 7½" x 5½" x 2½" 70p: 10" x 7½" x 2½" 85p. 11" x 7½" x 2½" 95p.

**BSR P128,** similar to HT70 single play, with heavy die cast turntable, less cartridge, £11.00.

**Transistorised FM tuner head,** with A.M. gang, slow motion drive 88-108 Mcs, with circuit diagram, £2.30.

**Mono Amp Transistorised (Mains)** Ideal for record player 8 ohms 2 watts. £3.50.

**Ferguson Stereogram Chassis.** MW/LW VHF with tuning scale (5+5 watts sine wave) 15 ohms £28.50.

ALL ITEMS INCLUDE VAT


All items post paid in GREAT BRITAIN

**SURPLECTRONICS**

216 LEAGRAVE ROAD,  
LUTON, LU3 1JD, BEDS.

## Thick Film I.C. Audio Amplifiers

### S.T.K. SERIES

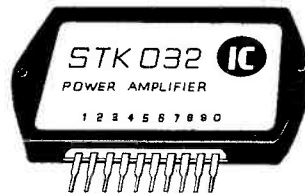

PRICES INCLUDE VAT AND P&P.

STK 011 | 10W (RL=4 ohm) | £3.14 ea.

STK 025 | 35W (RL=4 ohm) | £5.41 ea.

STK 032 | 45W (RL=4 ohm) | £6.92 ea.

**EX-STOCK!**

SEND P.O. OR CHEQUE WITH ORDER TO:

### Guest Distribution

Redlands, Coulsdon, Surrey, CR3 2HT. United Kingdom.

TEL: 01-668 7151 TELEX 946880



## Quality Loudspeaker Systems at half price

Direct from manufacturer as supplied by us to the trade.

Finished in natural Teak veneer 15 watt 8ohm speaker system containing Goodmans 8" bass + 3" tweeter speakers.


Cabinet size 20" high x 12" wide x 8½" deep.

Price, £16.00 per pair incl. VAT.

plus £1.25 packing and carriage U.K. (50p only if collected from Rugby).

Please send cash with order direct to:—

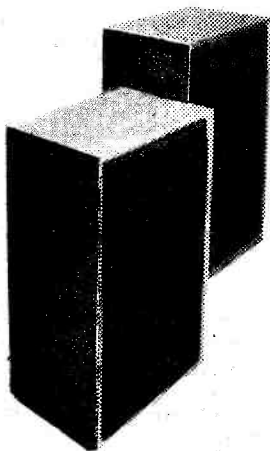Ben Ford (Hi-Fi Cabinets) Ltd.  
58 Somers Road Industrial Estate,  
Rugby,  
Warwickshire. Tel: 0788-78213



# Crescent Quality Components

74 SERIES TTL		
7400	80p	7473 41p
7401	80p	7474 41p
7402	80p	7475 68p
7403	80p	7476 44p
7404	80p	7486 49p
7408	80p	7489 24.75
7409	80p	7490 88p
7410	80p	7491 41.10
7413	81p	7492 88p
7420	80p	7493 88p
7430	80p	74100 22.87
7441	81p	74121 45p
7442	81p	74122 88p
7445	41-90	74141 41-10
7447	41-45	74154 41-62
7447A	41-80	74192 23-15
7448	41-50	74193 23-53
7470	85p	74196 41-73



**LIGHT EMITTING DIODES**

TH 209 (Red) With Clip	85p each
TH 209 (Green) With Clip	85p each
TH 209 (Yellow) With Clip	90p each
Mled 500 T092 Type	18p each

**LED READOUTS**

Litronic DL707 3 Character 14 Pin Dtl.	22.00
DL701 as above but ± 1	22.00
DL747 6 Character	22.82

**Minikron**

3015 7 Segment 16 Pin Dtl	41-18
2015G as above but ± 1	41-18

**Clock Chip**

CT7001 MOS/LSI Digital Clock/Calendar Chip	Plus
Full Circuits and Information Leaflet	23.95
Circuits and Information Sheet	15p
Lit 704 Led Display for above	41-85
Or 4 for	25-25

**WAFER SWITCHES**

1 Pole 12 Way	
2 Pole 2 Way	
2 Pole 3 Way	
2 Pole 4 Way	
2 Pole 6 Way	
3 Pole 4 Way	
4 Pole 3 Way	

25p each



**POTENTIOMETERS**

All types 1" and less diameter

Singles	Dual
5K Log or	5K
10K Lin Less	10K
25K Switch	25K Less
50K 15p each	50K Switch
100K	100K 45p each
250K Double	250K
500K Pole	500K
1M Switch	1M
2M	2M 80p each

**PRE SETS**

Sub Miniature Skeleton Type 0-1 Watt. Horizontal Mounting 100, 250 and 500 ohm, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, and 1M ohm 8p each

**MAINE TRANSFORMERS**

Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded flying leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high. Fixing centres: 2 1/4"

TR1 20-0-20v 100 m/a	
TR2 12-0-12 v 100 m/a	All
TR3 9-0-9 v 100 m/a	240 Volt
TR4 6-0-6 v 100 m/a	Primary
TR5 9-0-3 v 100 m/a	

Our Price 41.23 each

**200/250v MAINE RELAY**

Heavy duty contacts 2-500 ohm coil. All new and unused D.P.D.T. maine relays 80p. Carr. Free. Special quantity 240 per 100 off.

**MINIATURE RELAYS**

Brand new range of British made Relays, Size 1 1/4" x 1" x 1/2". All two changovers with 250V 1.5A contacts and suitable for fitting on 1m Veroboard.

Type	Volts	Current	Ohms	All
27/A	12v	17mA	700	
21/A	12v	28mA	430	80p
12/A	6v	33mA	185	each

**DOUGLAS TRANSFORMERS**

All types are standard 240 volt primary. MT 102 ct. 0 = 19 = 25 = 33 = 40 = 50 at 500M/A

MT237cs 20-0-20 at 150M/A	22.00 each	21.25
MT247cs 20-0-20 at 30M/A		21.05
MT240cs 15-0-15 at 30M/A		21.05
MT239cs 12-0-12 at 50M/A		21.05
MT238cs 3-0-3 at 200M/A		21.05

**POWER PACKS**

PPI Switched 3-6-7 1/2 - 9 volt 400M/A Transistor and Zener Stabilised On/Off Switch and Polarity Reversal Switch, in a black metal case 25.25 each.

PP2 Switched 6-7 1/2 - 9 volt Battery Eliminator, Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders 22.75 each (Double type 23.00).

PP3 Car converter. From 12v Pos. or Neg. to = 6-7 1/2 - 9 volt. Easy to fit and transistor regulated 22.50 each



**VEROBOARD**

	-1	-15	Plain -15
2 1/2 x 3 1/2	32p	24p	15p
2 1/2 x 5	34p	34p	18p
3 1/2 x 3 1/2	34p	34p	
3 1/2 x 5	39p	45p	
17 x 2 1/2	1.48p	77p	60p
17 x 3 1/2	1.45p	1.16p	75p
17 x 5	1.85p		1.10p

**Pin insertion tool** 72p

**Spot face cutter** 52p

**Pkt. 38 pins (state -1 or -15)** 25p

**LOUDSPEAKERS**

2 1/2" 8 ohm	50p
2 1/2" 40 ohm	50p
2 1/2" 80 ohm	50p
1 1/2" 8 ohm	ceramic 21.25
1 1/2" 8 ohm dual cone	ceramic 22.50
1 1/2" 8 ohm dual cone	ceramic 22.75
7" x 4" 8 ohm	ceramic 41.60
8" x 5" 8 ohm Permanent Magnet	41.60



\*EMI 1 1/2" x 8" 450 Kit 22.75

\*EMI 1 1/2" x 8" 350 Kit 8 ohm 27.50

**FANS ULTRA HIGH POWER LOUDSPEAKERS**

*Pop 25/2 30 watt 150 ohm 12"	28-18
*Pop 55 60 watt 8/15 ohm 12"	41-40
*Pop 50 50 watt 15 ohm 12"	41-81
*Pop 60 60 watt 8/15 ohm 15"	41-40
*Pop 100 100 watt 8/15 ohm 18"	427-90

\* Carr. on L/S over 18 x 8 and 12" 50p per L/S.

**ALUMINIUM CHASSIS**

Four-sided with corner plates. All are 2 1/2" deep.

	L	W	H	
6" x 3"	42p	12" x 5"		86p
6" x 4"	45p	12" x 8"		87p
8" x 3"	45p	14" x 3"		85p
8" x 6"	57p	14" x 9"		97p
10" x 7"	70p	16" x 6"		90p
12" x 5"	57p	16" x 10"		41.15

**ALUMINIUM BOXES**

Metal project boxes give your work a professional finish

	L	W	H	
AB7	2 1/2	5 1/2	1 1/2	40p
AB8	4	4	1 1/2	40p
AB9	4	2 1/2	1 1/2	40p
AB10	4	5 1/2	1 1/2	45p
AB11	4	2 1/2	2	40p
AB12	3	2	1	35p
AB13	6	4	2	55p
AB14	7	5	2 1/2	68p
AB15	8	6	3	85p
AB16	10	7	3	95p
AB17	10	4 1/2	3	85p
AB18	12	5	3	95p
AB19	12	8	3	41.28

**ABS PLASTIC BOXES**

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

1005 = 105mm x 78mm x 45mm = 51p
1006 = 150mm x 75mm x 47mm = 85p
1007 = 184mm x 124mm x 80mm = 98p
1021 = 106mm x 74mm x 45mm (sloping front) = 50p

**BARGAIN BOARD**


Components galore for the experimenter Ex Computer boards with Resistors, Capacitors and useful Transistors - at least 4 transistors per board. Five boards 21.00.

**CLEAR PLASTIC PANEL METERS**

Size 50mm x 46mm x 35mm these meters require a 38mm hole for mounting.

ME6	=0 to 50 micro amp Full Scale
ME7	=0 to 100 micro amp Full Scale
ME8	=0 to 500 micro amp Full Scale
ME9	=0 to 1 m/a Full Scale
ME10	=0 to 5 m/a Full Scale
ME11	=0 to 10 m/a Full Scale
ME12	=0 to 50 m/a Full Scale
ME13	=0 to 100 m/a Full Scale
ME14	=0 to 500 m/a Full Scale
ME15	=0 to 1 amp Full Scale
ME16	=0 to 50 volts A.C. Full Scale
ME17	=0 to 300 volts A.C. Full Scale
ME18	= "S" Meter
ME19	= "VU" Meter

OUR PRICE 23.00

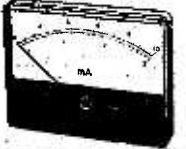

**Q-MAX SHEET METAL PUNCHES**

The easiest and quickest way of punching holes in sheet metal (up to 1.625mm Mild Steel)

DECON DALO 33PC ETCH RESIST PEN	SIZE	PRICE	
The Decon Dalco 33PC	3/8"	68p	Key
	1/2"	75p	"T" 6p
	5/8"	83p	
	3/4"	83p	Key
	7/8"	88p	"A"
	1"	88p	6p
	1 1/8"	88p	
	1 1/4"	90p	

**OUR PRICE 80p**

**ADD LUXURY TO YOUR CAR**

with a motor driven car aerial

SPEC: *	5 section	1 1/2"	21.05	Key
*	extended length 100cm	1 1/2"	21.10	"B"
*	Length under fender 40cm	1 1/8"	21.43	10p
*	Cable length 120cm	1 1/8"	21.50	
		2"	22.05	Key
		2 3/32"	22.30	"C" 13p
		2 1/2"	24.10	Key
		2 3/8"	25.25	"B"
		3"	28.10	20p

Fixed complete with supplied bracket and control switch 22.75

**1" SQUARE PUNCH complete with key 22.10**

**STOP PRESS**

BIA0002	15 watt Amp Module	22.50
NE55	Timer I.C.	75p
MCI310P	Stereo Decoder I.C.	22.00
7305	Regulator	21.49
TIP 29A		55p
TIP 30A		65p
BC107		10p
BC108		10p
BC109		10p



**I.C. SOCKETS**

D.I.L.	
8 pin	
14 pin	14p
16 pin	

**CABLE LESS SOLDERING IRON WAHL "ISO - TIP"**

- \* Completely Portable
  - \* Heats in 5 seconds
  - \* Solders up to 150 joints or more per charge
  - \* Recharges automatically in its own stand
  - \* No AC leakage or induced current to damage delicate components
  - \* Heats to 700 deg. F.
  - \* Fine Tip for delicate and general purpose soldering
  - \* Only 8" long and weighs just 6 ozs.
- OUR PRICE 29.75 (spare bits are available)

**BARGAIN BOX**

Loud buzzer mounted in a metal box complete with two U2 battery size holder.

Designed and can be used as a fire alarm but is ideal as a door or Morse code practice buzzer.

Approx. size - 2 1/2" x 6 1/4" x 1 1/2".

OUR PRICE - 50p.

**U.K. POSTAGE 15p UNLESS OTHERWISE STATED**

**V.A.T. Please add 8% to all Totals**

**CRESCENT RADIO LTD.**


All mail to 11 MAYES ROAD, WOOD GREEN, LONDON N22 6TL

Phone: 01-888 3206

Callers Welcome at 15 Mayes Road & 13 South Mall, Edmonton N9.

If you construct You should own one. **CRESCENT CATALOGUE** Price 20p.

# PRINTED CIRCUIT BOARD TRANSFER SYSTEMS

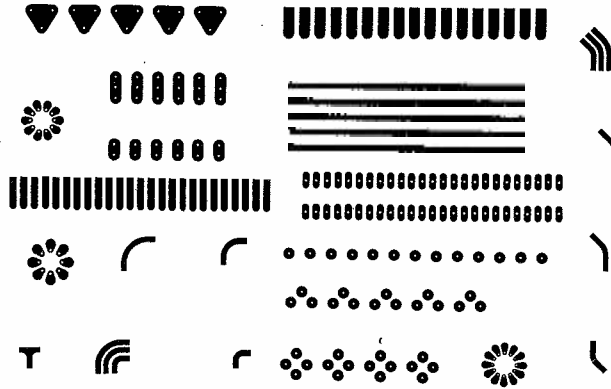

Acid resistant transfers for direct application to P.C. Board. This is a new approach to printed circuit board manufacture, giving a professional finish with all details that an electronics engineer would require, including all drilling positions automatically marked.

Ideal for single unit boards or small quantities. All at a very low cost—for example an average 6" x 4" layout would cost less than 30p, and the time taken under one hour, including etching to complete.

The system is simple, briefly it consists of 10 sheets of self adhesive acid resistant transfers made in required shapes—i.e. edge connectors, lines, pads, dual in line I.C.'s, 8-10-12. T.O.S Cans, 3-4 lead transistors, etc., etc., which only require pressing into the required positions on the printed circuit board before etching.

The printed circuit transfer system is a genuine offer to the public and industry. A full money back guarantee is sent with each order, trade prices on application.


#### List of Prices

Complete system including post and VAT .....	£2.00
Individual sheets .....	22p
Sample sheet .....	22p
Copper laminate (boards) size 6" x 4½" 6 sheets.....	50p
(with six months guarantee)	

Printed circuit board PCB transfer systems patent applied for.

**E. R. NICHOLLS, 46 LOWFIELD ROAD, STOCKPORT, CHESHIRE**

TELEPHONE NUMBER: 061-480-2179

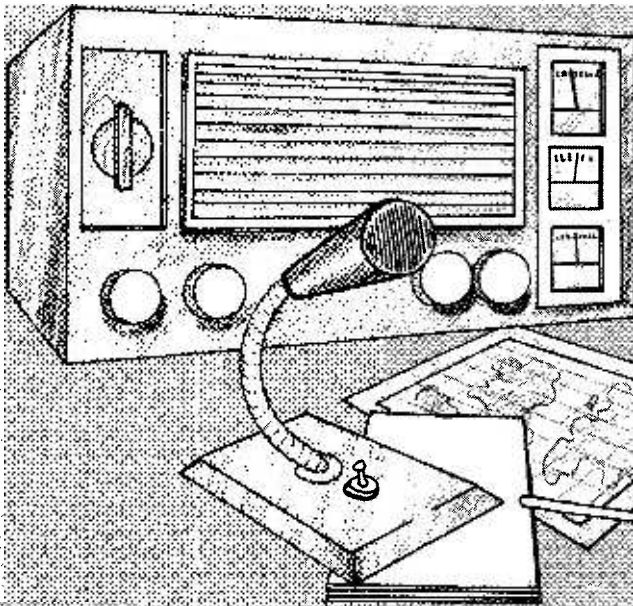

## Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

**Free!**

Brochure, without obligation to:  
**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept.,**  
 P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

WB 114


Block caps please







I.L.P. (Electronics) Ltd

# SHEER SIMPLICITY!

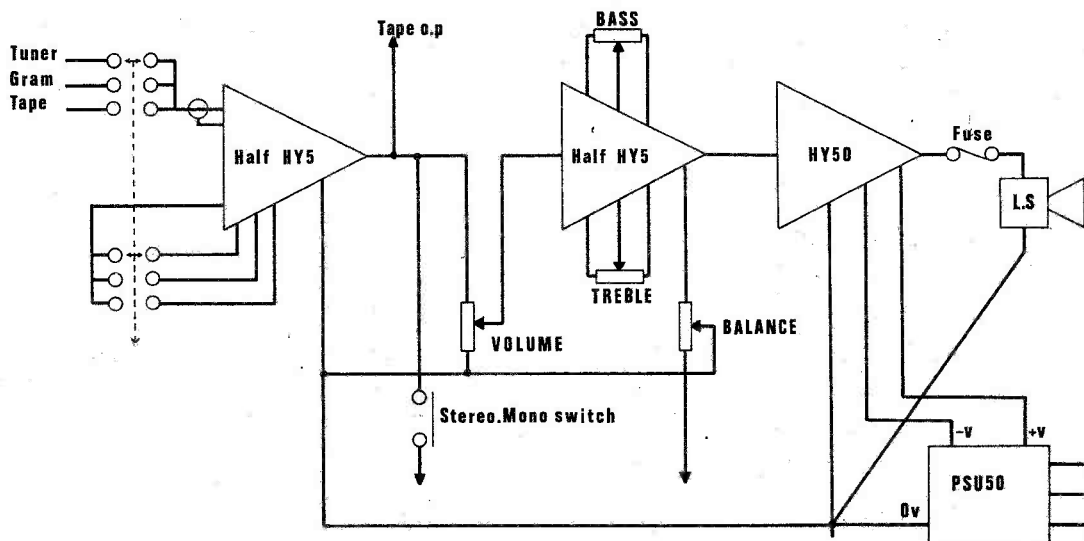

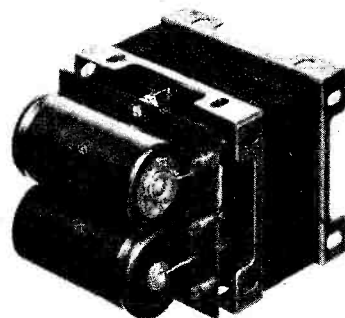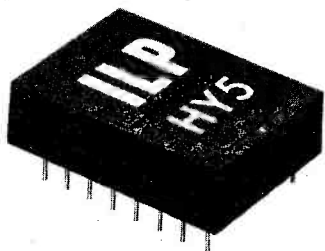MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

**TECHNICAL SPECIFICATION**

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3-100mV; Input Impedance 47k $\Omega$  at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble  $\pm$  12db at 10kHz; Bass  $\pm$  12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage:  $\pm$  16-25V.

**PRICE £4.50**

- 36p VAT  
P. & P. free

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

**TECHNICAL SPECIFICATION**

Output Power: 25W RMS into 8k $\Omega$ . Load Impedance: 4-16k $\Omega$ . Input Sensitivity 0db (0.775V RMS). Input Impedance: 47k $\Omega$ . Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz  $\pm$  3db. Supply Voltage:  $\pm$  25V. Size: 105 x 50 x 25mm.

**PRICE £5.98**

- 48p VAT  
P. & P. free

The PSU50 can be used for either mono or stereo systems.

**TECHNICAL SPECIFICATIONS**

Output voltage: 25V. Input voltage: 210-240V. Size: L. 70, D. 90, H. 60mm.

**PRICE £5**

- 40p VAT  
P. & P. free

**TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS**

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT


CANTERBURY (0227) 63218

**CUSTOM CABINETS, 331 High Street, Rochester, Kent. Tel: Medway (0634) 404199**

**Speaker Cabinets in kit form represent HUGE SAVINGS**



2' x 12" Cabinet

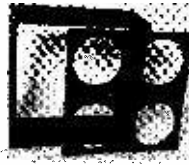

4' x 12" Cabinet



Disco Console (includes lid not shown)  
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!

Kits are available in all specifications and all the kits contain everything you need as follows:-

- 1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and 1 baffleboard with speaker cutout
- 2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
- 3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!

**PRICE & TYPE LIST**

Type	Size	Price manufactured	Kit price
2 x 12" (illustrated above)	36" x 18" x 13" x 3/4"	£19.50	£12.50
4 x 12" (illustrated above)	31" x 31" x 13" x 3/4"	£24.50	£17.50
4 x 12" P.A. Column	48" x 27" x 13" x 3/4"	£30.00	£21.50
1 x 18"	31" x 31" x 13" x 3/4"	£24.50	£17.50
1 x 15" with two top horn cutouts	36" x 20" x 13" x 3/4"	£21.00	£13.50
Mini Disco (state deck cutout BSR, GARRARD etc.)	33" x 20" x 10" x 1/2"	£20.00	£13.00
Maxi Disco (illustrated) (state deck cutout BSR, GARRARD etc.)	42" x 20" x 10" x 1/2"	£25.00	£18.50

Please ask for quotation on any other type or size of cabinet you may require.

**ALL OUR PRICES INCLUDE VAT AND UK DELIVERY**

**PC ETCHING KIT**

Contains 1lb Ferric Chloride, 100 sq. ins. copper-clad board, DALO etch-resist pen, abrasive cleaner, etching dish & instructions, all for only £3.30

**RESISTORS & CAPACITORS**

500 assorted resistors £1.35. 2500 4x12, 150 poly. ceramic, mica etc capacitors 80p.

**VEROBOARD**

100 sq. ins. assorted sizes and pitches (no tiny pieces) £1.10.

**3W TAPE AMPLIFIERS**

Polished wooden cabinet 14 x 13 x 9" containing a sensitive (20uV) 4 valve amplifier with tone & volume controls. Gives 3 watts output to the 7 x 4" 3Ω speaker. Also a non-standard tape deck. Supplied in good working condition with circuit. Standard mains operation. £4.50. Suitable cassette £1.10. Spare head 33p. Tape (ex-computer) 75p. Amplifier chassis only, complete and tested (2x ECC83, EL84, EZ80) and speaker £3.

**VERSATILE POWER UNIT**

Contains mains transformer, 2A thermal cut-out and bridge rectifier. Will give 1.7-10.5V output with 2 extra capacitors (supplied) £1.20. Also available as model garage with switch, lamp, jack plug etc. (Used for 'Hot Wheels') £1.70.

**LEO III COMPUTER**

Arriving late-October. All parts available, including 3000 reels tape, 1/2" decks, power units, etc.

All prices shown include 8% VAT and postage (mainland only) SAE list, enquiries.

**GREENWELD ELECTRONICS (PW8)**

Mail order dept., wholesale/retail shop 51 SHIRLEY PARK ROAD, SOUTH-AMPTON. Tel 0703 772591. Other retail shops at 21 Deptford Broadway SE8, Tel 01-892 2009 and 38 Lower Addiscombe Road, Croydon. Callers Welcome.

**FERRIC CHLORIDE**

Anhydrous technical quality to Mill Spec in 1lb double sealed packs. 1lb 80p, 3lbs £1.65, 10lbs £4.45, 100lbs £35.

**PO AMPLIFIER UNIT**

Contained in steel case 5 1/2 x 5 x 3 1/2" are 2xGET118 transistors on heat sinks, 3 pot cores, 2 30V zeners, 4 audio transformers, 1% resistors & caps. With circuit diagram £1.

**7lb BARGAIN PARCELS**

Hundreds of new components—Pots, resistors, capacitors, switches, + PC boards with transistors and diodes, and loads of odds and ends. Amazing value at only £2.30.

**COMPUTER PANELS**

3lbs asstd £1.40, 7lbs £2.65, 56lbs £15. Pack containing 500 components with at least 50 transistors 95p, 12 High quality panels with power transistors, trim pots, IC's etc £2.50. Thousands of boards at shops for callers from 5p.

**SLOT METER**

Ex-Pay TV, takes 10p pieces, has 3 digit mechanical counter, coin counter, Sangamo-Weston impulse movement, nylon gearing, switch, etc. Only £1.20.

**MISCELLANEOUS**

Transformer, Mains pri 16-0-16V with 9V tap sec 1 1/2A £2. Post office 4 digit counters 60p. Balanced armature earpieces, use as mic or spkr 20Ω impedance 30p. 2N3055 35p. 80 + 80 + 20uF 350V 15p. 10 for £1.15. Multimeters: good range in stock from £3.50.

**NEW**

ALL SILICON!



PRACTICAL WIRELESS

**ELECTRONIC IGNITION SYSTEM**

This Capacitor-Discharge Electronic Ignition System was described in *Practical Wireless*, and has proved extremely popular.

The kit is supplied with a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with AMP Electrical Spade Connector Block together with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. WE OFFER SILICON P.N.P. POWER DEVICES AT NO EXTRA COST! All components are available separately. Case size 4 1/2" x 3 3/4" x 2". Complete assembly and construction manual free with kit, available separately 25p.

SUITABLE FOR 12V SYSTEMS WITH NEG. OR POS. EARTH.

PRICE: **£9-50** U.K. ORDERS PLEASE ADD VAT

Quantity Discounts:

Trade and Overseas	1-5 Nett	6-9 less 10%
Enquiries Invited	10-49 less 15%	50-99 less 20%
Mail Order Only.	100-999 less 25%	1000 up less 30%

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING

**DABAR ELECTRONIC PRODUCTS**

98 LICHFIELD STREET

WALSALL, Staffs WSI 1UZ





# TRANSFORMERS

## SAFETY MAINS ISOLATING TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £
07	20	1 8	7.0 x 6.0 x 6.0	2.55 38
149	60	3 12	9.9 x 7.7 x 8.6	3.79 45
150	100	5 8	9.9 x 8.9 x 8.6	4.17 45
151	200	8 0	12.1 x 9.3 x 10.2	7.39 53
152	250	10 12	12.1 x 11.8 x 10.2	9.45 73
153	350	15 0	14.0 x 14.0 x 11.8	11.35 73
154	500	19 8	14.0 x 13.4 x 11.8	13.30 91
155	750	29 0	17.2 x 14.0 x 14.0	21.05 *
156	1000	38 0	17.2 x 16.6 x 14.0	27.20 *
158	2000	60 0	21.6 x 15.3 x 18.1	50.25 *

## AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.34 30
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.64 38
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	3.29 45
66	300	6 4	9.9 x 9.6 x 8.6	"	5.29 53
67	500	12 8	12.1 x 11.2 x 10.2	"	8.02 67
84	1000	19 8	14.0 x 13.4 x 14.3	"	13.50 91
93	1500	30 0	14.2 x 15.9 x 14.3	"	17.50 *
95	2000	32 0	17.2 x 16.6 x 14.0	"	25.35 *
73	3000	40 0	21.6 x 13.4 x 18.1	"	32.80 *

## CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2-pin outlets. 20VA £2.64 pp 38p  
500VA £9.50 pp 80p 1000VA £15.92 via B.R.S.

## TRANSFORMERS

### PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P £
111	0.5	0.25	8 4.8 x 2.9 x 3.5	0-12V at 0-25A x 2	1.34 23
213	1.0	0.5	1 4 6.1 x 5.8 x 4.8	0-12V at 0-5A x 2	1.58 30
71	2	1 2	7.0 x 6.4 x 6.1	0-12V at 1A x 2	2.09 38
18	4	2 2	8.9 x 8.0 x 7.0	0-12V at 2A x 2	2.60 38
70	6	3 3	8.9 x 8.0 x 7.7	0-12V at 3A x 2	3.52 45
108	8	4 5	9.9 x 8.9 x 8.6	0-12V at 4A x 2	3.96 45
72	10	5 6	9.9 x 9.6 x 8.6	0-12V at 5A x 2	4.67 53
116	12	6 6	12.1 x 9.9 x 10.2	0-12V at 5A x 2	5.61 53
17	16	8 8	12.1 x 9.9 x 10.2	0-12V at 8A x 2	6.62 60
115	20	11 8	14.0 x 12.1 x 11.8	0-12V at 10A x 2	10.20 73
187	30	15 15	18.2 x 12.1 x 11.8	0-12V at 15A x 2	13.70 85
226	60	30 32	0 17.2 x 15.3 x 14.0	0-12V at 30A x 2	22.50 *

### 30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.58 30
79	1.0	2 4	7.0 x 6.7 x 6.1	"	2.18 38
3	2.0	3 4	8.9 x 8.3 x 8.6	"	3.18 38
20	3.0	4 8	9.9 x 9.3 x 8.6	"	4.12 45
21	4.0	6 4	9.9 x 9.6 x 8.6	"	4.67 53
51	5.0	6 12	12.1 x 8.6 x 10.2	"	5.83 53
117	6.0	8 0	12.1 x 9.3 x 10.2	"	6.94 60
88	8.0	12 0	12.1 x 11.8 x 10.2	"	9.00 67
89	10.0	13 12	14.0 x 10.2 x 11.8	"	9.80 73

### 50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.09 38
103	1.0	2 12	8.3 x 7.4 x 7.0	"	3.08 38
104	2.0	5 8	9.9 x 8.9 x 8.6	"	4.26 45
105	3.0	6 12	9.9 x 10.2 x 8.6	"	5.79 53
106	4.0	10 10	12.1 x 10.5 x 10.2	"	7.41 67
107	6.0	12 0	14.0 x 10.2 x 11.8	"	11.00 67
118	8.0	18 0	14.0 x 12.7 x 11.8	"	13.40 85
119	10.0	25 0	17.2 x 12.7 x 14.0	"	17.60 *

### 60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60	2.12 38
124	1.0	4 4	8.9 x 7.7 x 7.7	"	2.97 38
127	2.0	6 4	9.9 x 9.6 x 8.6	"	5.40 45
125	3.0	8 12	12.1 x 9.9 x 10.2	"	7.11 60
123	4.0	13 12	12.1 x 11.8 x 10.2	"	9.20 67
40	5.0	12 00	14.0 x 10.2 x 11.8	"	10.83 73
120	6.0	15 8	14.0 x 12.1 x 11.8	"	13.35 85
121	8.0	25 00	14.0 x 14.7 x 11.8	"	15.01 *
122	10.0	25 0	17.2 x 12.7 x 14.0	"	19.60 *
189	12.0	29 00	17.2 x 14.0 x 14.0	"	21.60 *

## MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref. No.	MA	Weight lb oz	Size cm.	VOLTS	P & P £
238	200	2	2.8x2.6x2.0	3-0-3	1.40 10
212	1A, 1A	1	4 6.1x5.8x4.8	0-6-0-6	1.67 30
13	100	4	3.9x2.6x2.9	9-0-9	1.28 13
235	330, 330	4	4.8x2.9x3.5	0.9-0.9	1.42 19
207	500, 500	1	0 6.1x5.8x4.8	0-8-0, 0-8-9	2.23 30
208	1A, 1A	1	7.0x6.8x4.8	0.8-0.8-9	3.00 38
236	200, 200	4	4.8x2.9x3.5	0-15-0, 0-15	1.30 19
214	300, 300	1	4 6.1x5.8x4.8	0-20-0, 0-20	1.76 30
221	700 (D.C.)	1	8 7.0x6.1x6.1	20-12-0, 12-20	1.98 38
206	1A, 1A	2	12 8.3x7.7x7.0	0-15-20, 0-15-20	3.78 38
203	500, 500	4	8.3x7.0x7.0	0-15-27, 0-15-27	3.06 38
204	1A, 1A	3	4 8.9x7.7x7.7	0-15-27, 0-15-27	3.27 38

PLEASE ADD 8% FOR V.A.T. INCLUDING P. & P.

# BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

ALL PRICES INCLUDE VAT

**AERIAL MAST POLES.** Approx. 5ft. 2in. high, 2in. dia. Interlocking ends. Minimum order 3. As new, £1-25 (each) P. & P. 40p each.

**AERIALS.** As new. Whip Type 11ft. £1 each. Collapsible type. P. & P. 20p. New Bases for the above 75p, P. & P. 30p.

**PAIR OF 4 x 150A VALVES** complete with bases ex-equip not tested. Good condition £3, P. & P. 30p.

**BARGAIN PARCELS** 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 57p p.p.; 56lb at £4.95 plus £1.37 p.p. Contains pots, Res. Valves, Diodes. Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

**FANTASTIC BARGAIN.** New 6 inch tubes. E450 4/B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £2 post paid.

**TRANSISTOR BOARDS**—consisting of transistors, diodes and resistors etc. Long leads. Good value 12 for £1.00 (min. order) P. & P. 30p. Quotations for quantity.

**OUR SELECTION OF 6-Ex. Equ. METERS** consisting of 3in., 2½in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 30p, minimum order of six.

**NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED** 90ft £1, p. & p. 25p.

**AERIAL POLES** 4ft high 2" in diameter push-in type as new £1 each p. & p. 25p each minimum four.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

# A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

## ENGINEERS

# FREE



## YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

**CUT OUT THIS COUPON**  
**CHOOSE A BRAND NEW FUTURE HERE!**  
 Tick or state subject of interest. Post to the address below.

- Build-As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit)
- Electronic Engineering
- Computer Electronics
- Computer Programming
- General Radio and TV Engineering
- Radio Servicing, Maintenance and Repairs
- Transistor Technology
- CITY AND GUILDS Installations and Wiring
- CITY AND GUILDS Electrical Technicians
- CITY AND GUILDS Telecommunications
- Radio Amateurs' Exam etc. etc.

To ALDERMASTON COLLEGE Dept. BPW95, Reading RG7 4PF **BPW 95**

NAME (Block Capitals Please) \_\_\_\_\_  
 ADDRESS \_\_\_\_\_

Other subjects \_\_\_\_\_ Age \_\_\_\_\_  
 Accredited by C.A.C.C. Member of A.B.C.C.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**



# MAPLIN ELECTRONIC SUPPLIES

## ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

### THE DMO2

13 Master Frequencies on ONE tiny circuit board. **LOOK AT THESE AMAZING ADVANTAGES**

- ★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator.
- ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra.
- ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 37in. x 4 1/2in. ★ Very low power consumption.
- ★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.
- DMO2T (with tremulant) ONLY £14.25.
- DMO2 (without tremulant) £12.25.

★ S.a.e. please for full technical details.

Trade enquiries welcome.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.03 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

Keyboards: High quality adjustable type.

- Sloping front 49-note C to C £14.35
- Flat front 48-note F to E £14.35
- Contact Blocks GB2 (2 make contacts) 19p
- Palladium earth bar per octave length 15p
- Stop Tabs rocker type not engraved (white, red, grey or black) with DFDT switch 49p

### REVERBERATION UNIT

Enhances the sound of any electronic musical instrument. Ready built spring line driver module suitable for use with almost any spring line £5.94

Two types of spring line available:

- Short line £3.05
- Long line £7.59

S.a.e. please for details, leaflet MES 24

### BASIC ORGAN CIRCUIT


Leaflet MES 51 shows complete circuit for a basic fully polyphonic organ. Send only 15p for leaflet and start building now! **REMEMBER**—when you have built this organ you will later be able to use the same top quality component parts as the basis of a large sophisticated instrument with all the facilities you want. Watch our ads for details.

★ SAME DAY SERVICE


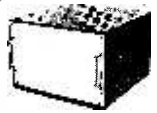
## Centurion

PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS



Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction.

Top, base, sides and detachable rear panel, blue hammer. Detachable aluminium front panel finished in white.

Model	W	H	D	Price
120	8	2 1/2	6	£2.87
220	8	6	3 1/2	£3.78
221	8	6	6	£4.07
320	12	8	12	£8.42

Chassis for model 320 £2.84 extra.

Please send s.a.e. for free illustrated leaflet.


## CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V Price	Mfd V Price
1 63 6p 68 6-3 6p	Mfd V Price
1 5 63 6p 68 16 6p	470 6-3 6p
2-2 63 6p 68 63 14p	470 10 14p
3-3 63 6p 100 10 6p	470 25 16p
4-7 63 6p 100 10 6p	470 40 25p
6-8 40 6p 100 25 6p	470 40 25p
6-8 63 6p 100 40 6p	680 6-3 14p
10 25 6p 100 63 16p	680 16 16p
10 63 6p 150 6-3 6p	680 25 25p
15 16 6p 150 16 6p	1000 4 14p
15 40 6p 150 25 6p	1000 10 16p
15 63 6p 150 40 14p	1000 16 25p
22 10 6p 150 63 16p	1000 16 25p
22 25 6p 220 4 6p	1500 6-3 16p
22 63 6p 220 10 6p	1500 10 25p
33 6-3 6p 220 16 6p	1500 16 25p
33 16 6p 220 25 14p	1500 16 25p
33 40 6p 220 40 16p	2200 6-3 25p
47 4 6p 220 63 25p	2200 10 28p
47 10 6p 330 4 6p	2200 6-3 25p
47 25 6p 330 10 6p	3300 6-3 25p
47 40 6p 330 16 14p	4700 4 28p
47 63 6p 330 63 28p	



## PLUGS AND SOCKETS

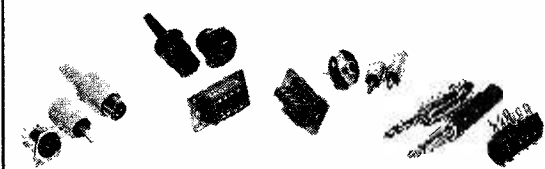

- DIN PLUGS**
  - 2 pin (1 flat) 8p
  - 3 pin 9p
  - 4 pin, 5 pin A 9p
  - (180°), 5 pin B pair 28p
  - (240°), 6 pin 10p
- MAINS**
  - P360 3 pin 1-5A chassis plug with line socket. Per pair 28p
  - SA 2190 3 pin 5A chassis plug 26p
  - SA 1862 Line socket for above 28p
- DIN Sockets**
  - 2 pin 6p
  - 3 pin, 4 pin, 5 pin 6p
  - A (180°), 5 pin B 13p
  - (240°), 7p, 6 pin 8p
- McMURDO**
  - RP8 8 way chassis plug 52p
- R88 8 way chassis socket 68p**
- PHONO**
  - Plug plastic 5p
  - Plug screened 12p
  - Chassis socket 4p
- JACK**
  - Std. 1" mono plug Plastic 13p
  - Screened 21p
- Std. 1" stereo plug Plastic 18p**
- Screened 30p**
- Open mono socket 1" 10p.
- Moulded mono socket 1" with 2 break contacts 14p.
- Moulded stereo socket 1" with 3 break contacts 18p.
- 3-5mm. plug plastic open socket 8p.

## WE KNOW YOU NEED IT!



The MES 1974 Catalogue is **STACKED** with dozens of tempting new lines. **BRIMMING OVER** with clear illustrations and detailed data. **WE'RE WAITING TO RUSH YOU A COPY.**


You'll be **IMPRESSED** with our **POST FREE** ordering system, **EXCITED** by our **BIG VALUE** discount vouchers, **AMAZED** by our **UNBEATABLE** speed of service. Take the first step towards real service **NOW!** Send **ONLY 26p** for our beautifully produced catalogue and leave the rest to us!

## OMNIUM GATHERUM

- PP3, 6 etc. battery clip dual min. 9p
- PP1, 9 etc. battery clip separate per pair 6p
- Pair crocodile clips 1 red, 1 black insulated sleeve. 10p
- Solder Multicores 22swg 10 metres 25p
- Silicone grease in special dispenser 20ml. 54p
- Red neon 240V panel mounting 23p
- Lacing Cord Strong rayon cored PVC 25m. 51p
- Panel fuse holders 20mm 20p; 1 1/2" 35p
- Transformers**
- LT700 min. output transformer Pri. 1-2k Ω Sec. 5 Ω 200mW 50p
- Sub-min. Mains Transformer 6-0-6V 100mA 95p
- 12-0-12V 50mA 85p
- Size: Both approx. 30 x 27 x 25mm.
- Min. Mains Transformer (Size: 46 x 31 x 38mm) 0-12V 250mA, 0-12V 250mA £1.36
- Mains transformer MT3AT Pri. 200-220-240V, Sec. 12-15-20-24-30V 2A £3.31
- Mains Transformer MT206AT Pri. 200-220-240V, Sec. 0-15-20V 1A, 0-15-20V 1A £3.98
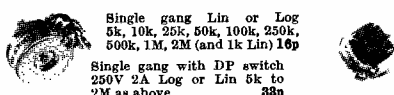
## POTENTIOMETERS

Rotary miniature carbon track 1" spindle.



- Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 16p
- Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 33p
- Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 48p.
- PRESETS**
- Sub-miniature 0-1W Vert or Horiz. 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 6p

**NE555V 8-pin DIL 69p**

## RESISTORS

- Carbon Film 1W 5% 1Ω to 1M; 10% 1-2M to 10M E12 1p
- Carbon Film 1W 5% 1.5Ω to 10G; 10% 1-2M to 10M E12 1p
- Carbon Film 1W 5% 11Ω to 910k E12 & E24 1p
- Carbon Film 1W 5% 10Ω to 10M E12 31p
- Metal Oxide 1W 2% 10Ω to 1M E12 & E24 4p
- Wirewound 21W 10% 0-22ohms to 0-47ohms E12 14p
- Wirewound 21W 5% 1ohm to 270ohms E12 12p
- E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades
- E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

## LINEARS

- CA3046 LH0042C, TO99 (TO5), FET 1/2p Op Amp 24.25p
  - LM301A. 8-pin DIL Op Amp 39p
  - MC1303L. 14-pin DIL Stereo Preamplifier £1.30p
  - MC1310P. 14-pin DIL FM Stereo Decoder (no coils needed) £3.15p
  - MF060. electronic attenuator £1.87p
  - MF08010. 8-pin base, 1W Audio Power Amp £1.37p
  - MF04000B 1/2 watt Audio Amp 38p
  - NE555V. 8-pin DIL, Precision Timer 69p
  - NE561B. 16-pin DIL, Phase Locked Loop £4.48p
  - SG3402N Amplifier/Multiplier £1.69p
  - SG1455D. 14-pin DIL Four Quadrant Analogue Multiplier £2.70p
  - µA723C. TO99 (TO5), 2 to 37V Voltage Regulator 75p
  - µA728C. 14-pin DIL, 2 to 37V Voltage Regulator 75p
  - µA741C. 8-pin DIL Op Amp 36p
  - µA741C. 14-pin DIL Op Amp 45p
  - µA747C. 14-pin DIL Dual Op Amp £1.00p
  - µA748C. 8-pin DIL Op Amp 39p
  - ZN414. TO5. TRF Radio £1.20p
- Full data, pin connexions, etc., on nearly all types listed in our catalogue. Price 25p

## SWITCHES

- Rotary with adjustable 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way. each 38p.
- Mains rotary DPST 250V 2A 20p
- Push to make non-locking 14p
- Toggle 250V 1-5A with ON/OFF plate 25p.
- High quality "sub-miniature" toggle switches
- SPDT 1-5A 204V AC 56p
- DPDT 1-5A 240V AC 75p
- DPDT 3A 240V AC 77p
- Four Pole DT 3A 240V AC £1.87
- Slide Sub-miniature DPDT 8p

**VAT** Please add 8% to the final total.

**Post & packing FREE in U.K.** (15p handling charge on orders under £1.) (First class post pre-paid envelope supplied free with every order.)

Orders and enquiries for catalogues to **MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. PHONE SOUTHERD (0702) 44101**

**NEW from A.S.P.**

**"SPASH PROOF"  
SAFETY TRANSFORMER**

750 VA Isolation Unit (Interwinding Screen) Housed in a tough Fibreglass case, with carrying handle. Complete with Heavy Duty 3 core power cable, splash proof outlet plug and socket, internal fuses 110 Volt and 240 Volt versions available. Price £26.80. Carriage £1.30

**2" and 4" PANEL METERS**


**2" 4"**  
SIZE: 60mm Wide x 45mm High x 40mm Deep. Movement I.R. Ohms  
0-50 micro A. 1250  
0-100 micro A. 380  
0-500 micro A. 170  
0-1 mA 170  
0-5 mA 170  
0-10 mA 170  
0-50 mA 170  
0-100 mA 0-5  
0-500 mA 0-5  
0-1 AMP 0-5  
0-2 AMP 0-5  
0-25 Volt 15K  
0-50 Volt 50K  
0-300 Volt 300K  
"g" Meter 170  
VU Meter 5250  
0-50 micro A. 1400  
0-100 micro A. 730  
0-500 micro A. 200  
0-1 mA 200  
0-5 mA 200  
0-10 mA 6  
0-50 mA 0-5  
0-100 mA 0-5  
0-500 mA 0-5  
0-1 AMP 0-5  
0-2 AMP 0-5  
15K  
50K  
300K  
200  
6250  
Ohms  
Ohms

VU Meters are complete with detectors. Modern wide view.  
Price 2" £2.95 Post 10p. Price 4" £3.95 Post 10p. Lamps 55p per set.

**1/2 watt CARBON FILM RESISTORS**  
1/2 watt at 70°C E 12 range 10Ω-1MΩ 5% tol above 470 KΩ 10% tol at 55p per 100.

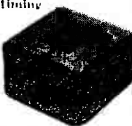**ELECTRONIC MAINS TIMER**

A reliable unit ideal for (Timing Bathroom/Toilet Ventilators Stairway Cloakroom Lighting etc.) Gives up to 30 mins delay before switching off. Delay 1-30 mins adjustable. Max Load 400VA or 1000 watts resistive. White Case 3 1/2" x 3 1/2" x 1 1/2". Fitting instructions included. Trade Price £5.80. Post 30p.



**MAINS KEYNECTOR**

The safe, quick, connector for electrical appliances. 13 Amp rating, fused, will connect a number of appliances quickly and safely to the mains. Ideal for fitting, demonstrating, window displays, etc. Warning Light, interlocked to prevent connecting when live. Trade Price: £3.25. Post 25p.



**TRANSFORMERS**

**SAFETY ISOLATING**

VA	Ref. No.	Price £	Price Plugs 2 Pin + 1 Earth	Price Open £	Post £
60	149	7.35	0.80	4.00	0.38
100	150	8.22	0.80	4.60	0.52
200	151	10.20	0.80	7.40	0.52
250	152	11.68	0.80	8.88	0.65
350	153	14.10	0.80	10.60	0.80
500	154	15.63	0.80	12.33	1.00
750	155	24.83	1.00	18.72	1.20
1000	156	32.19	1.00	26.50	1.20
1500	157	38.18	1.00	30.34	O.A.
2000	158	45.20	2.40	34.68	O.A.
3000	159	66.50	2.40	53.35	O.A.

**50 Volts**

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V.	Amps	Ref. No.	Price £	Post £
0-5	102	2.33	0.30	
1	103	3.00	0.38	
2	104	4.57	0.42	
3	105	5.20	0.52	
4	106	6.89	0.52	
5	107	11.17	0.67	
8	118	14.19	0.87	
10	119	15.47	0.97	

**60 Volts**

Prim. 230-240V. Sec. 24, 30, 40, 48, 60V.	Amps	Ref. No.	Price £	Post £
0.5	124	4.00	0.38	
1	126	5.90	0.38	
2	127	6.83	0.42	
3	125	6.84	0.52	
4	125	7.94	0.67	
5	4	8.90	0.67	
6	130	10.16	0.82	
8	121	13.58	1.00	
10	122	18.16	1.00	
12	189	18.00	1.10	

**12 & 24 Volts Prim. 200-240V.**

Amps	Ref. No.	Price £	Post £
12V 24V			
0-3	0-15	2.49	1.34
0-5	0-25	1.11	1.88
1	0-5	2.13	1.88
2	1	71	3.09
4	2	18	6.58
6	3	70	8.90
8	4	108	9.52
10	5	79	4.80
12	6	110	6.01
16	8	17	6.22
20	10	116	9.47
30	15	187	11.95
40	20	222	13.88
50	30	226	15.30

**30 Volts**

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.	Amps	Ref. No.	Price £	Post £
0-5	1	112	1.72	0.22
1	2	79	2.81	0.38
2	3	3	2.26	0.38
3	3	20	4.10	0.42
4	4	21	4.88	0.52
5	5	21	6.80	0.52
6	6	117	8.60	0.67
8	8	88	8.50	0.67
10	8	89	9.27	0.67

**MINIATURE AND EQUIPMENT**

Prim. 240V with screen.	Sec. 1	Sec. 2	Milliamps	Ref. No.	Price £	Post £
3-0-3	—	—	200	238	1.28	0.10
0-6	—	—	500	334	1.30	0.10
0-6	0-6	—	1000	212	1.93	0.22
9-0-9	—	—	100	13	1.23	0.10
0-9	0-9	—	330	330	2.48	0.10
0-9	0-8-9	—	500	307	1.75	0.22
0-8-9	0-8-9	—	1000	208	2.82	0.22
15-0-15	—	—	40	240	1.23	0.10
0-15	0-15	—	200	236	1.80	0.10
20-0-20	—	—	30	241	1.23	0.10
0-20	0-20	—	160	150	2.37	0.10
0-15-20	0-15-20	—	500	500	2.47	0.38
0-20	0-20	—	360	300	2.14	0.22
0-20	—	—	3500	NO SCREEN	1116	3.90
20-12-0 12 20	—	—	700 (D/C)	—	221	2.31
0-15-20	0-15-20	—	1000	1000	2.06	0.38
0-15-27	0-15-27	—	500	500	2.03	0.38
0-15-27	0-15-27	—	1000	1000	2.04	0.38

**PLASTIC CASED SILICON BRIDGE RECTIFIERS**

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 25p	50 P.I.V. 35p	100 P.I.V. 55p	60 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 45p	200 P.I.V. 55p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 55p	200 P.I.V. 85p
600 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 80p

ADD 10p P & P PER ORDER



**AUTO TRANSFORMERS**

Cased versions are 240 Volt Mains to 115 Volts, smart steel cased units coated in tough resin with power lead, fuse and 115 Volt American type socket up to 500VA, above 500VA cable entry.

VA	Ref. No.	Price £	Price Plugs 2 & 3 pin	Price Open £	Post £
Tapped at 115, 220, 240 Volts					
20	118	3.00	0.15	1.55	0.30
150	4	5.30	0.15	3.98	0.39
200	65	5.40	0.15	4.50	0.40
300	66	7.27	0.15	5.28	0.52
500	67	9.99	0.15	8.29	0.67
750	83	12.58	0.75	9.76	0.82
1000	84	15.70	0.75	12.40	0.82
1500	93	19.85	0.75	18.58	1.50
2000	95	30.10	1.44	28.05	1.50
3000	73	43.58	1.90	38.00	1.90

**POWER UNIT Type CC 12-05**

Output switched 3, 4, 5, 6, 7, 9 and 12 volts at 500 mA D.C. Operates from 240 V mains suitable for Radios, Tape Recorders, Record Players etc. Size 7.5 x 5.0 x 14.0cm. Price £3.65. Post 25p.



**A.S.P. LTD.**

DEPT PW11, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

**PLEASE ADD 8% FOR V.A.T.**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. I D have space dividers. Build up any size cabinet for wall, bench or table top.

**INTER-LOCKING PLASTIC STORAGE DRAWERS**

**NEAT! MESSY! TRY!**

**DISCOUNT PRICES**

SINGLE UNITS (5" x 2 1/2" x 2 1/4") £2.00 Dozen  
DOUBLE UNITS (5" x 5" Dozen. TREBLE (3D) £3.50 for 8  
DOUBLE TREBLE £4.90 for 8  
EXTRA LARGE SIZE (6D) £4.50 for 8.  
Carriage 40p. Orders over £10 post free.  
QUANTITY DISCOUNTS! 5% in £1 for orders over £15  
7 1/2% over £30, 10% over £50. Quotations for large quantities.  
**PLEASE ADD 8% VAT TO TOTAL REMITTANCE.**

**FLAIDLINE SUPPLIES** (Dept. PW11), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

5 SIZES ALL INTERLOCK

★ SPECIAL LOUSPEAKER SALE ★

**BAKER 12" MAJOR £8.50**  
30-14,500 cps. Double cone woofer. Baker ceramic magnet 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

**MAJOR MODULE KIT £10.95**  
30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 12 1/2in.

NOTE—When ordering state 3, or 8 or 15 ohms.

**BAKER LOUSPEAKERS 100% BRITISH MADE**


Regent 12 in. 15W £7.75	Group 25 12 in. 25W £7.75	New Group 50/12 12 in. 50W £12.95
Deluxe 12 in. 15W £9.75	Group 35 12 in. 35W £8.50	
Supert 12 in. 20W £13.80	Group 50 15 in. 50W £17.80	

**RADIO COMPONENT SPECIALISTS**  
337 WHITEHORSE ROAD, CROYDON  
ALL PRICES INCLUDE V.A.T. AND POST ALL GOODS IN STOCK



**TO THINK!**  
*I managed with a  
give-away catalogue  
-until I splashed  
out on a*

# HOME RADIO *Components Catalogue*

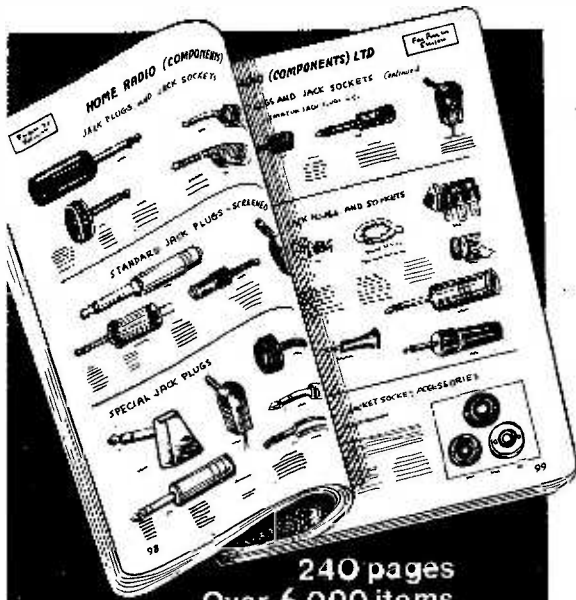

**240 pages  
Over 6,000 items  
Nearly 2,000 pictures**

Splashed out? *Invested* is more the word! It cost me just 98 pence (including packing and postage) and I saved more than that on my first order. And if I take into account the satisfaction I've gained from using such a comprehensive, clearly set out, well illustrated production, I've saved the outlay many times over. Think I'm exaggerating? Why not test it for yourself? The coupon below is just waiting to be filled in and sent off with your cheque or postal order. No need to keep it waiting any longer.

By the way, the catalogue contains 14 free Vouchers, each worth 5 pence when used against orders—so you can soon get the price of the catalogue back anyway, plus 5p towards the postage!

**65p. plus 33p POST AND PACKING**  
**Send off the coupon today. It's your first step to solving your component buying problems.**

The price of 98p applies only to customers in the U.K and to B.F.P.O. addresses.

Please write your Name and Address in block capitals

NAME .....

ADDRESS .....


.....

.....


HOME RADIO (Components) LTD., Dept. PW,  
234-240 London Road, Mitcham, Surrey CR4 3HD



Regd. No.  
912966 London

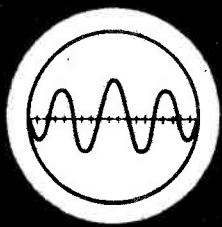

# TUAC

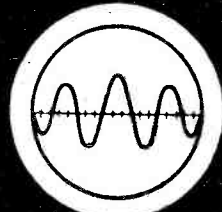

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
163 MITCHAM RD LONDON SW17 9PG 01-672 3137/9080

## TUAC DISCOTHEQUE MIXER WITH AUTO FADE



Designed for the discerning D.J. of professional standard Offering a vast variety of functions. Controls; Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification. Deck Inputs—50mV into 1mΩ; Deck Tone Controls—Treble +28 - 15dB at 12kHz. Bass +22 - 15dB at 40Hz; Mic input—200 ohms upwards. 2mV into 10kΩ; Mic Tone Control—Total Variation Treble 15dB. Total Variation Bass 10dB; Tape input—30mV into 47kΩ; Power Requirements—30-45 volts at 100mA.

**£26.50**


PANEL SIZE  
18 × 4½ in.  
DEPTH 3in.

### TUAC MAIN DEALERS

BRISTOL DISCO CENTRE, 86 Stokes Croft, Bristol 1. Tel. Bristol 41666.  
CALBARRIE AUDIO, 38 Cromwell Road, Luton Beds. Tel. Luton 411733.  
SOCODI, 9 The Friars, Canterbury, Kent. Tel. Canterbury 60948.  
WEC LIGHTING, 35 Northam Road, Southampton, Hants. Tel. Southampton 28102.  
CALLERS ONLY
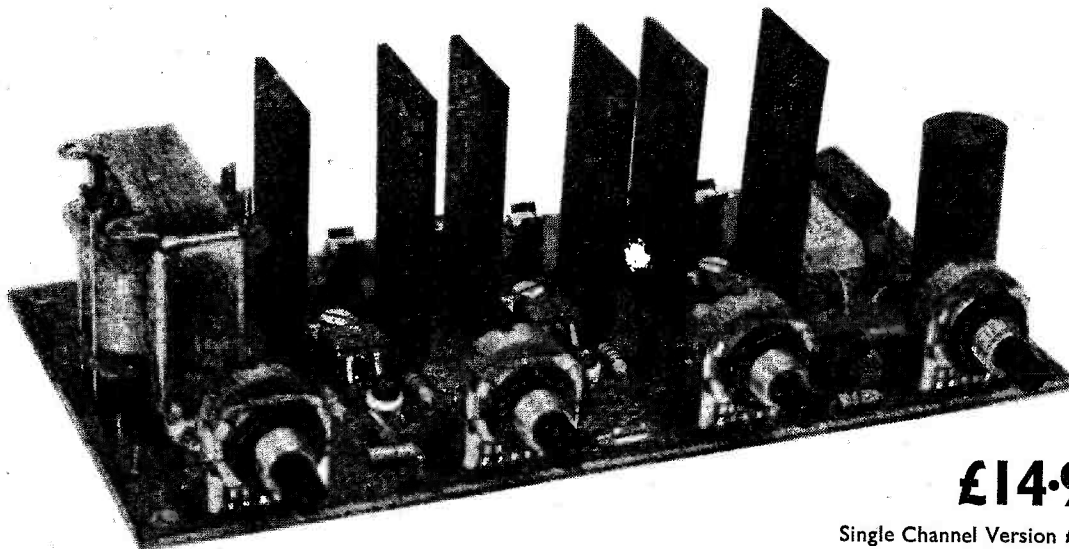
## NEW! 3 CHANNEL LIGHT MODULATOR

- R.C.A. 8 Amp Triacs ● 1000W per channel ● Each channel fully suppressed and fused
- Master control to operate from 1W to 100W ● Full wave control—12 easy connections



**£14.90**


Single Channel Version £6.60

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT  
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT · OPEN 6 DAYS A WEEK 9.30am - 6.00pm


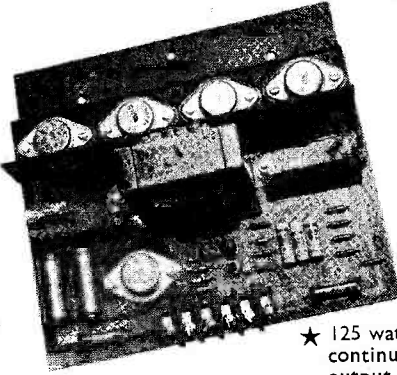
## NEW TUAC POWER MODULES

offering more power and quality than ever before.




Specification on all power modules:  
All output power ratings  $\pm 0.5$ dB;  
Output impedance 8-15 ohms; THD at full power 2% typically 1%;  
Input sensitivity 60mV into 10k $\Omega$ ;  
Frequency response 20Hz-20kHz  $\pm 2$ dB; Hum and noise better than -70dB.

**TP125**  
7 x 6½ x 3in  
**£17.00**

- ★ 125 watts RMS continuous sine wave output


- ★ 4 R.C.A. 150 watt 15 amp output transistors

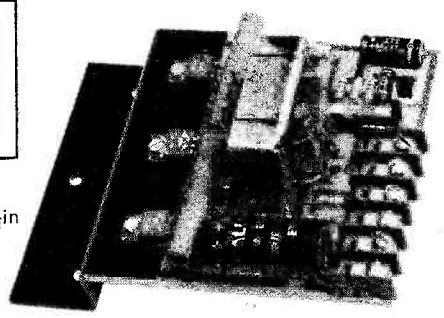

**TL30**  
4 x 5¼ x 2½in  
**£9.30**

- ★ 30 watts RMS continuous sine wave output
- ★ 2 R.C.A. 40 watt output transistor

- ★ Rugged layer wound driver transformer.
- ★ Short—Open—and Thermal overload protection
- ★ Only 6 connections

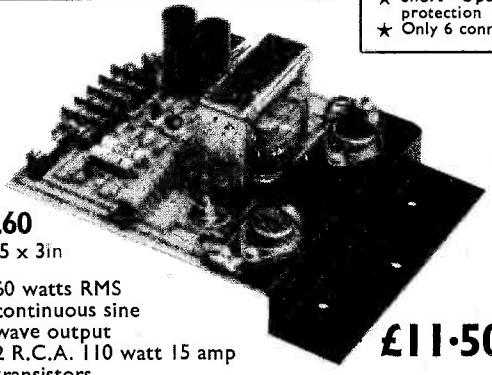

**TL60**  
5 x 5 x 3in


- ★ 60 watts RMS continuous sine wave output
- ★ 2 R.C.A. 110 watt 15 amp transistors

**£11.50**

**TL100**  
5 x 5 x 3in

- ★ 100 watts R.M.S. continuous sine wave output
- ★ 2 R.C.A. 150 watt 15 amp transistors

**£13.20**

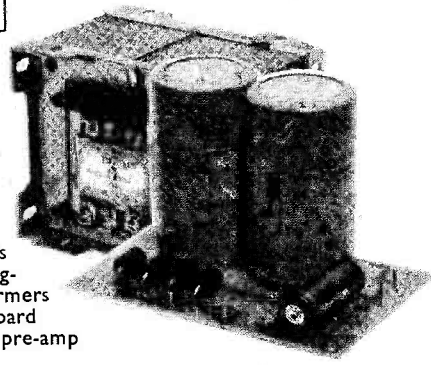

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

- PS 125  $\pm$  50 volts for one TP125 ..... **£11.50**
- PS 100  $\pm$  45 volts for one TL100 ..... **£10.50**
- PS 60  $\pm$  40 volts for one TL60 ..... **£9.30**
- PS 30  $\pm$  50 volts for one TL30 ..... **£6.85**
- PSU 2 for supplying disco mixer ..... **£4.65**

### PREAMPLIFIERS

All TUAC audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into various wide range tone control circuits producing superb sound quality from any signal.

**VA08** Vol. Treble, Mid and Bass controls. HI, IMP, FET, I/P. suitable Mid, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20—15dB at 1kHz. Bass +20—10dB at 40Hz. **£4.90**

**VA06** Vol. Treble and Bass controls. Sensitivity 8mV. Treble +28—15dB at 12kHz. Bass  $\pm$  18dB at 40Hz. **£4.15**

**AMFOI** TUAC Auto Fade Unit fades music when you speak. Auto Mic Over-ride for Disco use. Feed Deck and Mic Pre-amps in. Auto fade O/P to main Amp. 38mV operating level. Depth and Vol. Controls. **£4.90**




**ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING**


ACCESS & BARCLAY CARDS ACCEPTED · Just Send or Phone us Your Number · H.P. ARRANGED THROUGH PAYBONDS.

**G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR.**  
Tel. 021-327 2339

**12 VOLT FLUORESCENT LIGHTING**

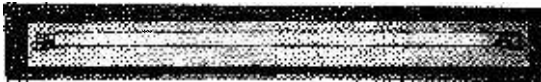

- INVERTER TRANSFORMERS 13/15 WATT (CIRCUIT INCLUDED) **70p**
- "CURRENT ECONOMY" TRANSISTOR (600 ma.) **50p**
- "MAXIMUM LIGHT" TRANSISTOR (1-3A) **50p**
- RESISTORS/CAPACITORS TO SUIT **15p**
- LAMP HOLDERS (LONG LEAD) **30p PAIR**
- (SHORT LEAD) **20p PAIR**
- WHITE ENAMEL CASE, 18" or 21" (Postage 30p) **70p**
- TUBE, 18"-15 WATT or 21"-13 WATT **45p**
- (NOTE:- TUBE ONLY SUPPLIED IF CASE ORDERED, TO PREVENT POSTAL DAMAGE)
- 13 WATT FITTING READY BUILT AND TESTED—INCLUDING TUBE (Postage 30p) **£3.75**
- Post/Packing 25p per order except where shown

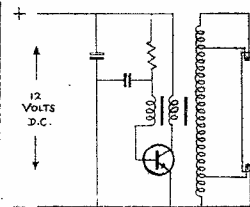

**NEW IMPROVED CIRCUIT!**  
Drives 21" 13 watt  
18" 15 watt  
or adaptable for  
2 x 12" 8 watt

**SMALL ELECTROLYTICS**

Ref. No.	Capacity	Voltage	Price
H8/3	3µF	50V	4p
H8/3A	4µF	50V	4p
H8/5	5µF	10V	4p
H8/6A	10µF	10V	4p
H8/8A	16µF	16V	4p
H8/9A	20µF	70V	4p
H8/10	22µF	50V	4p
H8/11	25µF	12V	4p
H8/12A	30µF	10V	4p
H8/13A	32µF	50V	4p
H8/14	40µF	25V	5p
H8/14A	40µF	16V	4p
H8/15A	40µF	35V	4p
H7/1A	50µF	10V	4p
H7/2A	64µF	2.5V	2p
H7/4	64µF	15V	4p
H7/9A	125µF	4V	4p
H7/10A	160µF	2.5V	3p
H7/11	160µF	25V	6p
H7/11A	150µF	16V	5p
H7/14	220µF	50V	10p
H7/14A	220µF	16V	6p
H7/15	220µF	25V	5p
H7/15A	220µF	35V	10p
H6/1A	250µF	4V	3p
H6/3A	320µF	2.5V	3p
H6/4	320µF	10V	4p
H6/5	330µF	25V	10p
H6/6A	330µF	35V	15p
H8/8A	470µF	35V	20p

POSTAGE 25p PER ORDER

**£1** 100 1/2 WATT RESISTORS  
100 CERAMIC CAPACITORS  
100 DIODES

**£1** 1 VERO-BOARD CUTTER  
5 1/2 in. x 1 in. x 15 BOARDS  
50 SQ. INS. "ODD PIECES"  
VERO

**£1** 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108 ETC.

**£1** 5 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS & CAPACITORS

**£1** 100 RESISTORS  
100 CERAMIC CAPACITORS  
100 POLYSTYRENE CAPACITORS

**£1** 100 RESISTORS  
100 CERAMIC CAPACITORS  
50 MULLARD POLYESTER CAPACITORS

**£1** 1 TRANSISTORISED SIGNAL TRACER KIT  
1 TRANSISTORISED SIGNAL INJECTOR KIT

**£1** 100 RESISTORS  
100 CAPACITORS (ASSORTED TYPES)

**NOTE:- ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)**

16 CHERRY LANE BRISTOL BS1 3NG **THE RADIO SHOP** TELEPHONE 0272-421196

**TRIACS**

1-6AMP PLASTIC TOS		6-5AMP ISOLATED TAB		10AMP ISOLATED TAB	
NAS0161W 100V	-27	NAS0651W 100V	-46	NAS1001W 100V	-63
NAS0161X 100V	-26	NAS0651X 100V	-44	NAS1001X 100V	-60
NAS0162W 200V	-30	NAS0652W 200V	-58	NAS1002W 200V	-76
NAS0162X 200V	-28	NAS0652X 200V	-56	NAS1002X 200V	-74
NAS0164W 400V	-40	NAS0654W 400V	-84	NAS1004W 400V	-1-09
NAS0164X 400V	-38	NAS0654X 400V	-80	NAS1004X 400V	-1-04
NAS0166W 600V	-55	NAS0656W 600V	-1-05	NAS1006W 600V	-1-34
NAS0166X 600V	-52	NAS0656X 600V	-1-00	NAS1006X 600V	-1-28

Devices with Internal Trigger have "W" suffix. "X" denotes Standard Triac.

**THYRISTORS**

1-6 AMP MIN. TOS		4 AMP ISOLATED TAB		6 AMP ISOLATED TAB	
NAS006P	50PIV -25	NAS106P	50PIV -26	NAS206P	50PIV -37
NAS006Q	100PIV -28	NAS106Q	100PIV -30	NAS206Q	100PIV -42
NAS006R	200PIV -31	NAS106R	200PIV -36	NAS206R	100PIV -50
NAS006S	400PIV -40	NAS106S	400PIV -57	NAS206S	100PIV -77
NAS006T	600PIV -52				

**8 AMP ISOLATED TAB**  
NAS306P 50PIV -41  
NAS306Q 100PIV -47  
NAS306R 200PIV -58  
NAS306S 400PIV -85

**16 AMP ISOLATED TAB**  
NAS806P 50PIV -50  
NAS806Q 100PIV -58  
NAS806R 200PIV -73  
NAS806S 400PIV -115

Quantity prices on application, S.A.E.

**CLOCK CHIP 7001** £8-95  
The unique 7001 represents a major breakthrough in Clock Chip design, incorporating many features available for the first time: 365 DAY CALENDAR - 12/24 HR. OPERATION - ALARM - SNOOZE ALARM - SIX DIGIT CAPABILITY - DIRECT DRIVE TO LED DISPLAY - CONTINUOUS OPERATION DURING MAINS FAILURES.  
Copy of data available—please send 10p stamp.  
Special kit comprising 1 7001 & 4 LED 7 segment displays and data sheets and socket **£15-40**  
704 LED—7 seg. display -3" **£1-50** each  
Please add 8% VAT to all listed prices. Postage & packing 15p per order. Send 10p for latest catalogue. Callers welcome.

**YOUR CAREER in RADIO & ELECTRONICS ?**

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio & Electronics School, Dept W.C. 114, P.O. Box 156, Jersey, C.I.

Please send FREE BROCHURE to

NAME ..... Block

ADDRESS ..... Caps.

..... Please

**BRITISH NATIONAL RADIO AND ELECTRONICS SCHOOL**

# Henry's

TRANSISTORS, VALVES AND SEMI-CONDUCTOR DEVICES ANY QUANTITIES UK'S LARGEST STOCKISTS


FREE NEW '74/75 SEMI-CONDUCTOR AND VALVE LISTS Ref No. 36 on request

**CASH & CARRY PRICES**  
FOR CALLERS or BY POST

G.B. Carr./Pack 15p per item.

Ref. No.	Description	Price
1	DI203 Telephone Amplifier—Suction	£4.95
2	DI201 Telephone Amplifier—Cradle	£7.50
3	TI206 2 Station Intercomm	£4.95
4	TI306 3 Station Intercomm	£9.95
5	TI406 4 Station Intercomm	£12.50
6	TAIA 2 Station Telephones Intercomm	£13.50
7	WI1.2 2 Station Wireless Intercomm	£18.20
8	DP303 Door Phone Intercomm	£7.00
9	PK3 ETCH your own printed circuits	£2.25
10	EA41 Reverberation amplifier	£11.75
11	US50 Ultrasonic switch	£12.75
12	XP4002 Photoelectric alarm system	£13.50
13	Solid state tachometer	£11.30
14	Power dash transistor assisted ignition	£13.50
15	Car auto lock	£2.75
16	4 amp 6-12 volt battery charger	£4.85
17	FF21 Car radio/cassette quad adaptor	£4.68
18	Fully disappearing car aerial	£2.00
19	Electric disappearing car aerial	£7.80
20	ET (F1009) Morse Code Key/Buzzer	£1.70
21	VH105 aircraft band converter	£4.50
22	LM300 50K Disco mic.	£12.95
23	DF508 50K Communications mic.	£5.75
24	Car lighter up to 12v voltage adaptors 300mA (state 6/7/9 volts)	£1.95 ea.
25	STC time delay module	£1.50
26	Gravenire 931A photo electric unit (with data)	£3.50
27	3 ch. 3 x 500 watt sound to light	£21.50
28	3 ch. 3 x 1000 watt sound to light plus override	£41.25
29	150w. light display projector with wheel	£23.50
30	MM1 (B2005) 4 channel 9 volt mixer	£4.20
31	MX100 deluxe 4 channel mixer	£6.78
32	H67 (C1320) Stereo headphones amplifier	£10.50
33	MP12 6-CH. Slider control mixer	£27.95
34	RE 208 stereo phone adaptor	£2.25
35	MD802 stereo phones	£2.20
36	CIS200 stereo phones	£2.75
37	CIS 250 stereo phones	£6.50
38	G1301 and G1305 stereo phone controls	£2.95
39	Car stereo speakers in pods. Special offer	£2.95 pr.
40	Crystal lapel microphone	£0.60
41	EI052 car speakers front/rear fadar	£1.00
42	Bib Groove Clean (Ref. No. 42)	£1.76
43	Bib Record care kit (Ref. No. 43)	£2.20
44	Bib cassette recorder care kit (Ref. No. 26A)	£1.96
45	Bib cassette Tape splicing kit (Ref. No. 24)	£1.64
46	BASF reel-reel Hobby Box	£2.40
47	2000 OHM headphones	£1.50
48	4000 OHM headphones	£1.55
49	Cassette Recorder Mic. (2½ x 3¼mm Plugs)	£1.85
50	420 ES Microscope	£5.70
51	UP050 Low cost 9 volt eliminator	£2.25
52	RE 527K Tape Head Demagnetiser	£1.50
53	Cambridge pocket calculator	£17.95
54	BC808 % Pocket calculator	£21.95
55	BC817 Memory pocket calculator	£28.95
56	BCM 850 % and memory calculator	£33.25
57	Sinclair scientific calculator	£27.20
57A	Sinclair Cambridge Memory	£23.95
58	Antex soldering iron kit (SKI)	£3.30
59	Bib record care kit (Ref. No. 59)	£1.17
60	5pc Chassis punch kits	£5.50
61	Longs desoldering tool	£5.50
62	1 amp in line mains suppressors	£2.50
63	B552 (E1013) 7 way stereo speaker switch	£2.20
64	Weller 8200D-PK expert gun kit	£6.20
65	'S' Dec breadboard	£1.98
66	'2' Dec breadboard	£4.29
67	'4' Dec breadboard	£7.50
68	'T' Dec breadboard	£3.65
69	Instant heat soldering gun	£2.30
70	40 watt soldering iron	£1.90

## ELECTRONIC COMPONENTS



(Post/Packing 15p per 1-6 items GB unless stated)

<b>Ceramic Filters</b> Miniature 10-7 MHz filters 40p pair. IC IF Unit CA3089 10-7 MHz IC 92 Sinclair 6 w. IC IC14 with data and PC board £2.10 Radio IC Chip ZN414 Radio IC with circuit £1.20	<b>Fibre optics</b> 0-01" diam. mono filament £5.50 per 100 metres 0-13" diam. 64 fibres £1 per metre 15m diam. mares tails £10.50 each Radio Control XTALS Matched pair for 465 KHZ IF £2.00 pr. for all superhet trans. RX's
<b>Strobe Tubes</b> ZFT8A (similar to 4A) £4.00 ZFT12A £5.00	<b>Handsets</b> Lightweight telephone handsets brand new complete with diagrams for intercomms £3.00 pr.
<b>7 segment indicators</b> 30 15F with data £1.70 ea Spring delay units	<b>MARRIOT TAPE HEADS</b> 4 TRACK MONO or 2 TRACK STEREO '17' High Impedance £2.50 '18' Med. Impedance £3.50 '36' Med. Impedance £5.00 Erase Heads for '17' '18' and '36' £1.00 '63' 2 track mono. High Imp. £1.75 '43' Erase Head for '63' 75p (Post, etc. 15p any quantity)
<b>HR42 9" twin spring</b> £3.30 <b>pp 20p HR16" twin spring</b> £6.85 pp 25p	
<b>IC Clock</b> MM 5314 single chip clock with CCT £9.00	
<b>Ultrasonic transducers</b> with data/circuits £5.90 pr	

### QUALITY CASSETTE TAPES

"Living Sound" Made specially for Henry's by EMP Tapes Ltd. 5 screw type with library case Post paid (GB)

	3 for	6 for	10 for	25 for
C60	£1.10	£2.00	£3.15	£7.50
C90	£1.47	£2.85	£4.65	£11.37
C120	£1.83	£3.54	£5.60	£14.00

### SPECIAL OFFER CASSETTE STORAGE

Rotating unit up to 32 cassettes stackable £3.60 pp 15p  
Car unit with bracket for 10 cassettes £2.80 pp 10p

### ELECTRONIC COMPONENTS & EQUIPMENT

More selection — bigger stocks of electronic components and equipment for supply purpose. Let us quote for your requirements (Please enclose large SAE with all enquiries)

### BUILD IT YOURSELF MULTI-KITS

Ready to use and use again. Educational and practical. All transistor circuits with full handbooks.

MW/LW Portable radio £7.98 pp 32p	MW/LW Radio tuner £5.25 pp 20p	9 volt regulated power supply £2.15 pp 15p	15 watt inverter £5.20 pp 30p	40 watt inverter £6.80 pp 40p	Sinclair micromatic radio £2.25 pp 15p	Sinclair Cambridge Calculator £13.84 post paid
590 SWR meter £9.47	630 STAB Power supply 6-12V 0.25-0.1A £9.24	690 DC motor speed Gov. £3.31	700 Electronic Chaffinch £7.92	707 Windscreen wiper timer £7.97	760 Acoustic switch £12.57	780 Metal Detector (electronics only) £10.91
790 Capacitive Burglar alarm £7.92	835 Guitar preamp. £4.99	840 Delay car alarm £6.99	875 CAP. Discharge ignition for car engine (-Vc Earth) £13.19	80 Scope Calibrator £2.65	255 Level indicator £6.98	525 120-160mHz VHF timer £11.31

## TEST EQUIPMENT MULTI-METERS



(carr./packing 35p)

U4324, 20kV with case	£9.25
U435, 20kV with steel case	£7.75
U4313, 20kV with steel case	£12.50
U4317, 20kV with case	£16.50
U4341, 33kV + transistor tester steel case	£10.90
U4323, 20kV plus INKH 465KHZ OSC with case	£7.70
ITI-2, 20kV/V slim type	£5.95
THL33D (L33DX) 2kV/V Robust	£7.50
TP55N, 20kV/V (Case £2.00)	£8.25
TP105 20kV/V	£6.25
TP405 20kV/V	£11.20
TW50K 50kV/V	£11.25
EPIOKN 10kV/V	£9.95
AF105 50kV/V Deluxe (case £1.90)	£12.50
S100TR 100kV/V Plus trans. tester	£22.50

### General Test Equipment

(† carr./pack 50p. \*carr./pack 30p unless stated)

#### New Revolutionary Super tester 680R 680R Multi-tester £18.50

#### Accessories

Transistor tester	£11.00
Electronic volt.	£18.00
Amplclamp	£11.95
Temp. probe	£11.95
Gauss meter	£11.95
Signal injector	£5.95
Phase Sequence	£5.95
EHT Probe	£5.95
Shunts 25/50/10A	£4.50


†3100 IMA Stripchart recorder £44.00  
†TE40 AC Multi voltmeter £19.75  
†TE15 Grid dip meter 400KHZ-28MHz £19.95  
†TE65 28 Range valve voltmeter £22.50  
†TK20D RF Generator 120-KHZ 500MHZ £18.95  
†TK22D AF Gen 20HZ-200KHZ £19.95  
†HM350 In circuit transistor tester £19.50  
†C3025 Deluxe meter 1-300 MHz £6.95  
†TI145 Compact transistor tester £14.75  
†G3-36 R/C osc. 20HZ-200 KHZ £19.75  
†C3042 SWR Meter £5.75  
†SE350A Deluxe signal tracer £12.95  
†SE400 Mini-lab in one tester £15.50  
†C1-5 Scope 500,000 KHZ (carr. £1) £43.00  
†C3043 S CH/F A meter 1-300 MHz £5.75  
Resistance sub box } 20p } £2.40  
Capacitor } }  
2 amp var. transformers (carr. £1) £6.95  
Radio activity counter 0-10 (carr. £1) £9.97

Mains unit for above (carr. 50p) £3.75

### PA-DISCO-LIGHTING Equipment

Without doubt UK's best range of modular and complete equipment, lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc FREE stock lists (Ref. No. 18) on request CALL IN AND SEE FOR YOURSELF AT HENRY'S DISCO CENTRE 309 EDGWARE ROAD 01-723 6963.

### ANTRON KITS



310 Radio control receiver £3.29	4-channel R/C trans £6.61	345 Superhet R/C receiver £6.61	615 Simple transistor tester £6.66	8v watt amplifier £4.50	120 1/2 watt amp £4.73	125 Stereo control unit £6.61
127 Noise reduction unit £9.55	157 Private TV loop Trans. £4.95	130 Mono control unit £4.16	605 Power Supply for 115 £5.31	610 Power supply for 120 £5.31		

615 Power supply for 2 x 120 £6.64	230 AM/FM aerial amplifier £3.29	240 Auto packing light £6.90	275 Mic. preamp £4.98	525C 120-160 MHz VHF tuner £11.31	5705 LF generator 10Hz-1mHz £21.45	5755 Sq. wave generator 20Khz £19.77
------------------------------------	----------------------------------	------------------------------	-----------------------	-----------------------------------	------------------------------------	--------------------------------------

590 SWR meter £9.47	630 STAB Power supply 6-12V 0.25-0.1A £9.24	690 DC motor speed Gov. £3.31	700 Electronic Chaffinch £7.92	707 Windscreen wiper timer £7.97	760 Acoustic switch £12.57	780 Metal Detector (electronics only) £10.91
790 Capacitive Burglar alarm £7.92	835 Guitar preamp. £4.99	840 Delay car alarm £6.99	875 CAP. Discharge ignition for car engine (-Vc Earth) £13.19	80 Scope Calibrator £2.65	255 Level indicator £6.98	525 120-160mHz VHF timer £11.31

**8% TO BE ADDED TO ALL ORDERS (Export VAT FREE)**

**FOR MORE ELECTRONICS, SEE BACK PAGE**

HENRY'S ELECTRONICS & HI FIDELITY CENTER NOW OPEN IN BRUSSELS, BELGIUM prices, VAT, stock etc subject to Belgian regulations

# Henry's RADIO

EDGWARE ROAD, W2

Electronic Centres  
404-406 Electronic Components & Equipment 01-402 8361  
309 PA-Disco Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road London W2 1RW  
Price correct at time of preparation. Subject to change without notice. E & O E

Hi Fi and Electronics Centres Open 9am-6pm

# DISCOUNTS UP TO 60%

## FANTASTIC OFFER



**GARRARD SP25 MKIV**  
Plinth & Cover  
Garrard SP25 MkIV deck, Goldring G800 Cartridge, Teak finished Plinth/Cover (Non Hinged) All Leads.  
**GLOBAL'S PRICE £19-80**  
Carr. & Ins. £1-93

**TURNTABLES**  
Please add £1.05 for p. & p. & Ins.  
Garrard SP25 MkIV Chassis £12-95  
Garrard 86SB P/C Cart (Hinged Cover) £47-50  
Garrard 86SB Chassis £22-40  
Garrard 401 Chassis £32-00  
Goldring 101 Mk II P/C G800 £22-50  
Goldring GL78 P/C G800 £39-15  
Goldring GL78 P/C G500 £43-95  
Goldring GL85 P/C £63-50

Pioneer PL 12D .. P.O.A.  
Sansul SR212 .. P.O.A.  
Thorens TD125 MkII .. £72-25  
Thorens TD125AB Mk II .. £111-95  
Thorens TD160 ABC .. £59-95  
Thorens TD165 ABC .. £52-95  
Transcripser Saturn With Vestigial Arm .. £63-95

**AMPLIFIERS**  
Please add £1.05 for p & p & Ins  
Amstrad Integra 4000 Mk II .. £24-45  
Amstrad IC2000 MkII .. £31-75  
Amstrad 8000 MkIII .. £17-95  
Benson 100A .. £22-95  
Benson 200A .. £29-95  
Metro-Sound ST20E MkII .. £26-15  
Metro-Sound ST40 .. £33-25  
Metro-Sound ST60 .. £46-75  
Sansul AJ101 .. P.O.A.  
Sinclair 2000 Mk III .. £29-95  
Sinclair 4000 .. £44-95  
Teleton GA202 .. £30-50  
Teleton SAQ206B .. £23-95  
Teleton SAQ307D .. £27-20

**COMBINATION UNITS**  
Please add £1.10 for p & p & Ins  
Goodmans Compact 80 (Teak) £131-15  
Goodmans Compact 90 .. £169-99  
Goodmans Compact 1-10 (Teak) .. £191-00

## TUNERS

Please add £1.05 for p & p & Ins.  
Amstrad MLX 3000 .. £24-95  
Eagle AA8 .. £45-95  
Eagle TST 152 .. £32-95  
Metro-Sound FMS 20 Mk II .. £33-35  
Teleton T300 .. P.O.A.  
Teleton ST202 .. £36-60  
Sinclair 2000 Mk III .. £29-85  
Sinclair 4000 .. £37-45

## TUNER/AMPLIFIERS

Please add £1.21 for p & p & Ins  
Amstrad 5000 .. £55-00  
Goodmans Module 80 .. £72-40  
Goodmans Module 90 .. £92-90  
Goodmans 1-10 Module .. £108-50

## SPEAKERS

Add £1.82 for p & p & Ins per Pair  
Amstrad 1500 .. £25-65  
Amstrad 2500 .. £29-60  
Celestion County .. £25-25  
Celestion Ditton 10 MkII .. £42-65  
Celestion Ditton 15 .. £65-50  
Celestion Ditton 25 .. £129-95  
Celestion Ditton 44 .. £108-45  
Celestion Ditton 66 .. £158-95  
Celestion Hadleigh .. £39-25  
Goodmans Dimension 8 .. £127-95  
Goodmans Havant SL .. £44-50  
Goodmans Magisters .. £107-75  
Goodmans Magnum K2 SL .. £84-85  
Goodmans Minister .. £36-90  
Goodmans Moxo 3SL .. £67-35  
Marsden Hall 110F/C .. £26-65  
Marsden Hall 150F/C .. £30-95  
Marsden Hall 200F/C .. £38-45  
Marsden Hall 300F/C .. £74-75  
Wharfedale Denton 2 .. £29-25  
Wharfedale Dovedale .. £77-80  
Wharfedale Glendale .. £52-85

## CARTRIDGES

Please add 12p for p & p & Ins  
Goldring G800 .. £3-85  
Goldring G800E .. £5-29  
Goldring G800 .. £3-40  
Shure V15 Type 3 .. £26-00  
Shure M75EJ Type 2 .. £7-75  
Shure M75EJ Type 2 .. £8-95  
Shure 91ED .. £8-10  
Shure M3D .. £2-99  
Sonnitone 9 TACHD .. £1-30

## FABULOUS OFFER



**AMSTRAD IC2000 MkII**  
**STEREO SYSTEM**  
Amstrad IC2000 MkII with increased power 25+25 watts amplifier. Complete with a pair of Amstrad Acoustra 2500 speakers, Garrard SP25 MkIV deck, G800 Cart, Plinth/Cover (Non Hinged) all leads.  
**GLOBAL'S PRICE £80-75**  
Carr. & Ins. £3-90

## STEREO HEADPHONES

Please add 42p for p & p & Ins.  
Koss K7/11 Red Devil .. £9-55  
Koss K6 .. £11-15  
Koss 747 .. £17-49  
Koss HV1 .. £19-05  
Koss HV1/LC .. £22-50  
Koss K7/11 Black .. £9-45  
Sennheiser HD414 .. £10-75

# GLOBAL AUDIO

Please Note Every effort is made to ensure prices listed are correct at time of going to press, but are subject to alteration without prior notice. (E&OE)

## FULL 12 MONTH AFTER SALES SERVICE

We give a **FULL 12 MONTH GUARANTEE** on all products purchased at any branch parts and labour absolutely **FREE**

### BIRMINGHAM

Two! Shopping Centre,  
1536 Coventry Road, Yardley  
Tel: 01-706 9949

### ESSEX

4 High View Parade,  
Redbridge Lane East,  
Woodford Avenue, Ilford.  
Tel: 01-550 1086

### LONDON

328 Edgware Road, W2.  
Tel: 01-262 3047  
174 Pentonville Road, N1.  
Tel: 01-278 1769  
120 Notting Hill Gate, W11  
Tel: 01-229 1437  
50 Stamford Hill, N16.  
Tel: 01-806 4699

### PORTSMOUTH

12 London Road, North End  
Tel: 0705 68321

### READING

46 Market Place,  
Tel: 0734 595331

### WATFORD

105 St Albans Rd. Tel: 39832

### H.P. FACILITIES

AVAILABLE FOR  
PERSONAL CALLERS ONLY  
**MAIL ORDERS**  
TO: 174 PENTONVILLE  
ROAD, LONDON, N1.  
Order with confidence.  
Send Postal Order,  
cheque, Money Order,  
Bank Draft, Giro or  
Cash by Reg. Mail.

**NO HIDDEN PRICES AT GLOBAL AUDIO - ALL OUR PRICES ARE SHOWN WITH VAT INCLUDED**

**PERSONAL CALLERS VERY WELCOME!**  
COMPARE OUR PRICES WITH ANY IN THE BOOK!  
OPEN MONDAY TO SATURDAY 9.30 am - 6 pm  
LATE NIGHT FRIDAY OPEN UNTIL 7 pm.

**PLEASE NOTE** All Cheques, Money Orders, Postal Orders, Bank Draft, or Giro to be made payable to **MAUTONFEAD LTD.**

# SPARKRITE Mk II

## Electronic Ignition... Better on all points

Because you keep your points!


The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly - with all the advantages and none of the disadvantages. No misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of norm, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds, if points go (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes. ● Up to 20% better fuel consumption. ● Instant all weather starting. ● Cleaner plugs - they last 5 times longer without attention. ● Faster acceleration. ● Faster top speeds. ● Coil and battery last longer. ● Efficient fuel burning with less air pollution.
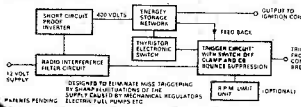
## The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system, and 6 page installation instruction leaflet.

WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!



Sparkrite Mk II - full capacitive discharge electronic system - not just a transistorised inductive discharge booster.

## PRICES

D.I.Y. Kit only £10.93 incl. VAT and P & P  
Ready Built Unit £13.86 incl. VAT and P & P  
(Both to fit all cars with coil/distributor ignition up to 8 cylinders).

We can supply units for any petrol-engined vehicle (boat, motorcycle etc) with coil/contact breaker ignition. Details on request. Call in and see us for a demonstration.

## ORDER NOW TO:

ELECTRONICS DESIGN ASSOCIATES  
(Dept PW 11) 82 Bath Street,  
Walsall WS1 3DE Phone 33652

Please supply:

- Sparkrite Mk.2 D.I.Y. Kit(s) at £10.93 each incl. VAT and P & P (Will make pos. or neg. earth).
- Sparkrite Ready Built Neg. Earth Unit(s) at £13.86 each incl. VAT and P & P
- Sparkrite Ready Built Positive Earth Unit(s) at £13.86 each incl. VAT and P & P

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I enclose cheque/P.O. for £ \_\_\_\_\_  
Send SAE for brochure.

# ELECTROVALUE

APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

Present

## top quality electronic components for price-minded buyers

112 p. CATALOGUE · FREE POSTAGE (U.K.) · ATTRACTIVE DISCOUNTS · SPECS. GUARANTEED

### A 100 OF THE BEST From our transistor stock

2N1307	47p	BC149C	14p
2N2646	51p	BC158B	15p
2N3053	26p	BC159	15p
2N3054	60p	BC167B	13p
2N3055	60p	BC168B	12p
2N3702	11p	BC169B	12p
2N3703	10p	BC169C	13p
2N3704	11p	BC179B	26p
2N3705	10p	BC182L	26p
2N3794	18p	BC184L	26p
2N3819	25p	BC212L	12p
2N4062	11p	BC214L	14p
2N4443	52p	BC257A	14p
2N5052	42p	BC259B	14p
2N5163	20p	BC758	30p
2N5459	32p	BD130	90p
40361	46p	BD131	48p
40392	44p	BD132	52p
40602	46p	BD135	37p
40636	£1-36	BD136	39p
40669	£1-10	BDY20	83p
AC128	17p	BF194	15p
AC151R	23p	BFR39	23p
AC153	27p	BRF79	23p
AC153K	37p	BFX29	33p
AC176	24p	BFX84	27p
AC176K	38p	BFY51	23p
AC187K	31p	BRV39	51p
AC188K	29p	BY164	45p
AD135	£1-92	C106S1	42p
AD136	£1-11	C106D1	62p
AD149	65p	C1406	78p
AD161	42p	MJ481	£1-20
AD162	40p	MJ491	£1-35
AF200J	70p	MJ2955	80p
AF239	60p	MJE371	35p
E1906	36p	MJE521	81p
BA138	31p	MJE2955	£1-12
BB103	24p	OA91	6p
BB105	34p	SD4	8p
BB109	18p	TIP31A	70p
BC107A	15p	TIP32A	80p
BC107B	15p	TIP41A	80p
BC108B	14p	TIP42A	£1-00
BC109B	18p	WO2	30p
BC109C	18p	ZTX300	14p
BC147A	12p	ZTX304	23p
BC147B	12p	ZTX300	14p
BC148B	12p	ZTX504	45p

### 100s MORE IN CATALOGUE 7

### BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14-90.

The size and weight of this product obliges us to charge 70p part cost of carr. in U.K. Equaliser Assembly, £2-30. Loudspeaker Unit 59RM109, £2-45. Cabinet Kit (to Baxandall design), £10-45. Cross-over choke for additional woofer to above, £15-50.

### DISCOUNTS

Available on all items except those shown with NETT PRICES 10% on orders from £5 to £14-99, 15% on orders £15 and over.

### FREE POSTAGE

In U.K. for pre-paid mail orders. For mail orders for £2 list value and under there is an additional handling charge of 10p. Overseas orders - carriage charged at cost.

Giro A/C No. 38/671/4002

### RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
(see note below)					
C	1/3	4-7-470K	1-3	1-1	0-9 nett
C	1/2	4-7-10M	1-3	1-1	0-9 nett
C	3/4	4-7-10M	1-5	1-2	0-97 nett
C	1	4-7-10M	3-2	2-5	1-92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-22-3-9Ω	11	10	8
WW	3	1-10K	9	8	6
WW	7	1-10K	11	10	8

Codes: C = carbon film, high stability, low noise. MO = metal oxide. Electrofil TR5 ultra low noise. WW = wire wound, Plessey.

Values: All E12 except C 1/3W, C 3/4W and MO 1/2W. E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances: 5% except WW 10% ± 0-05% below 10Ω and MO 1/2W 2%. Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order). Prices for 100 up in units of 100 only

### POTENTIOMETERS ROTARY, CARBON TRACK,

Double wipers for good contact and long working life

P-20 SINGLE linear 100 ohms to 4-7 megohms,	each 14p
P-20 SINGLE log. 4-7 Kohms to 2-2 megohms,	each 14p
JP-20 DUAL GANG 1in. 4-7 Kohms to 2-2 megohms,	each 48p
JP-20 DUAL GANG log, 4-7 Kohms to 2-2 megohms,	each 48p
JP-20 DUAL GANG Log/Antilog 10K, 22K, 47K, 1 megohm only,	each 48p
JP-20 DUAL GANG antilog 10K only	48p

2A DP mains switch for any of above 14p extra.

Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets, Type PR, horizontal or vertical each 8p

### SLIDER

Linear or log mono 4-7K to 1 meg, in all popular values each 30p

STEREO, matched tracks, lin. or log in all popular values from 4-7K to 1 meg, 60p

Escutcheon plates, mono, black, white or light grey, each 10p

Control knobs, blk/wht/red/yel/gm/ blue/dk. grey/lt. grey, each 7p

### ELECTROLYTIC CAPACITORS

Axial Lead	3V	6-3V	10V	16V	25V	40V	63V	100V
0-47	—	—	—	—	—	—	11p	8p
1-0	—	—	—	—	—	—	11p	8p
2-2	—	—	—	—	—	—	8p	8p
4-7	—	—	—	11p	—	—	8p	8p
10	—	—	—	—	—	—	8p	8p
22	—	—	—	—	—	—	8p	8p
47	8p	—	8p	8p	8p	8p	10p	13p
100	9p	8p	8p	8p	9p	10p	12p	19p
220	8p	8p	8p	8p	10p	10p	11p	17p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	18p	23p	26p	37p	41p	—	—
4,700	26p	30p	39p	44p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

### MINITRON DIGITAL INDICATORS

3015F Seven segment filament compatible with standard logic modules. 0-9 and decimal point: 9mm characters in 16 lead DIL. Suitable BCD decoder driver 7447 £1-20 3015G showing + or - & 1/4 dec. pt. £1-20

LEDs (Light Emitting Diodes) 25p  
Photo Cells, each 40p

### ANEX Soldering Irons

CN340	£1-95	Spare bits	32p
CCN240	£2-30	Spare bits	40p

### DESOLDER BRAID

6 ft strip 66p

### WAVECHANGE SWITCHES

1 pole 12 way; 2 pole 6 way  
3 pole 4 way; 4 pole 3 way each 29p  
TAG STRIP 28 way 11p

### NUTS, SCREWS, etc.

in lots of 100 each  
4BA NUTS 28p; 6BA NUTS 28p  
3/8" 4B SCREWS 28p; 1/2" 6BA SCREWS 24p  
Threaded pillars 6BA, 1/2" hexagonal £1-68  
£1-12

Plain spacers 1/2" round  
Other sizes available

### ENAMEL COPPER

### WIRE IN 2 ounce reels

16, 18, 20, 22 SWG 34p  
24, 26, 28, 30 SWG 40p

### DIN CONNECTORS

1 way loudspeaker	10p	Socket Plug	12p
3 way audio	10p	10p	12p
5 way audio 180	12p	15p	15p
5 way audio 240	12p	15p	15p
6 way audio	13p	15p	15p

### EV CATALOGUE 7

### 2nd printing—Green and yellow Cover

112 pages, thousands of items; illustrations; diagrams; much useful technical information. This 2nd printing has been updated as much as possible on prices. It costs only 25p post free including refund voucher for 25p for spending when ordering goods list value £5 or more.

### QUALITY GUARANTEE

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered for sale. Prices quoted do not include V.A.T. for which 8% must be added to total net value of order. Every effort is made to ensure the correctness of information and prices at time of going to press. Prices subject to alteration without notice.

## ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB  
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily: Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA  
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily: Sat. 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

All postal communications, mail orders etc. to Head Office at Egham address, Dept. EE11. S.A.E. with enquiries requiring answers.



# Radio Operators. How to see more of your wife without losing sight of the sea.



Join the Post Office Maritime Service. We have openings for Radio Operators at several of our coastal stations.

The work is just as interesting, just as rewarding as aboard ship, but you get home to see your wife and family more often. You need a United Kingdom General or First Class Certificate in Radiocommunications, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting pay for a man of 25 or over is £2,270, plus cost of living allowance with further

annual increases after that. Though we're happy to take people from 19 up.

In addition to your basic salary, you'll get an average allowance of £450 a year for shift duties and there are opportunities for overtime.

Other benefits include a good pension scheme, sick pay and prospects of promotion to Senior Management.

For more information, write to: ETE Maritime Radio Services Division (RC10), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London, EC1A 1AS.

Post Office  
Telecommunications


**WIRE RECORDERS** record only 24v DC I/P complete with spool of wire I/P level 15 Mill/V, running time 75 min spools 3½" dia by 1" would take 1" tape, wire speed 30" per sec in case size 5½ x 11 x 6" in good cond with instructions **£5.25. POWER UNITS** stabilised for use with BC221 freq meter mains I/P fits in battery box gives 135v & 6.3 with circ tested **£7.16 CONTAMINATION METERS** No. 1 · 1 to 10 Mill/Rongt per Hr meter indicator also sk for phones complete with mains P.U. & carrying case with instructions new boxed & tested **£6.10 CT38 ELECTRONIC MULTIMETERS** bench type for 240v mains these have 97 ranges of V, A, W, R, etc. with H/Bk tested **£23. BATTERIES** Lead Acid type 24v 25 amp/hr tapped at 2v steps in lightweight carrying container new with instructions **£10.40. AERIAL TUNING UNITS** ex A/C 2 to 18 Mc/s Tx type remote controlled contains 1000pf tun cond, large coil, meter, Ae c/o relay etc in case 8 x 7 x 14" **£5.15. ELEC CONDS** all heavy duty types with screw term new ex USAF 82,000uf 17.5v **£3. 44,000uf 27.5v £3. 8,400uf 10v 65p, 4,600uf 20v 65p, 1200uf 75v 80p, METER UNIT X** pointer type dual 115 Ua for use with 1155Rx approx 3" dia okay for Stereo Balance Ind new **£1.79. DIODES** 200 PIV 8 amps 4 for 70p, also 800 PIV 750 Ma 15 for **£1.10** new. **CRYSTAL OVEN** with 12 type Hc6/u holder can be removed **76p. UNI SELECTORS** coil 50v 25 way 4 bank with motoring contact **£2.50 TAG STRIPS** solder type 24 way new 10 for **40p PRESS GAUGE** elec scale 0 to 120 vehicle type new **55p. METERS** 1 Ma FSD 2½ sq scale knots **£1, 500 Ua scale 0 to 5 1½" dia £1.45. 500 Ua scale 0 to 5 2½" dia. £1.30 200 Ua scale 0 to 200 3½" dia £1.80. 50 Ma 2½ sq scale 0-50 £1.20.**

Above prices include VAT & Postage, S.A.E. for list or enquiry.

## A. H. SUPPLIES

57 MAIN RD. SHEFFIELD S9 5HL. Tel: 442278 (0742)

## CARBON SLIDE POTENTIOMETERS

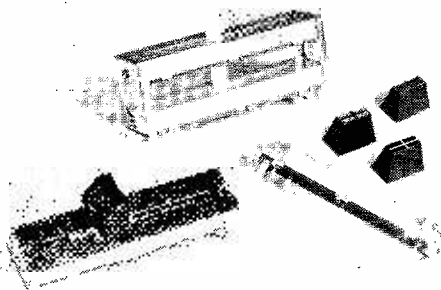

60mm Single Track including Black Knob **50p** (inc. V.A.T.), 60mm Twin Track including Black Knob **60p** (inc. V.A.T.), 60mm Quad Slide Potentiometers—Prices upon application. 1K, 5K, 10K, 25K, 50K, 100K, 500K ohms Log, Lin, Antilog. Metal Case. 3-2db Matched Track. 15mV Nominal Noise (B.S. 2122). Life Exceeds 20,000 cycles. Fixing Holes 2 x M3 on 80mm Centres.

Designed, Manufactured and Supplied by:—

## RIVLIN INSTRUMENTS LTD

DOMAN ROAD, CAMBERLEY, SURREY GU15 3DJ

Send cash with order to above address. Postage and packing 15p per order. Trade enquiries invited.

# C. T. ELECTRONICS

NOW AT 267 & 270 ACTON LANE, LONDON W4 5DG

Now open—our new components shop. These premises are very much larger and will enable us to have greater stocks than we already have. Having all the components under one roof will now guarantee you speedier service on the counter, and on the mail order side. We have an enormous range of components to choose from. If you are having problems getting your components then come along. We are open from 9.30 a.m. through till 6 p.m. Monday to Saturday. The nearest underground is Chiswick Park, and there are no parking restrictions.

## SEMICONDUCTORS

AC107	35p	BCY30	40p	MJ340	55p	OC36	85p	TIP41C	95p	2N2846	£1.50
AC125	35p	BCY31	55p	MJ481	85p	OC42	40p	TIP42C	£1.10	2N2804	25p
AC126	35p	BCY32	55p	MJ501	£1.20	OC44	£1.50	TIP43C	£1.10	2N2805	25p
AC127	27p	BCY33	85p	MJ201	£2.20	OC45	20p	2T7X107	15p	2N2826	12p
AC128	25p	BCY34	85p	MJ340	50p	OC70	15p	2T7X300	15p	2N2827	12p
AC176	27p	BCY36	85p	MJ370	75p	OC71	17p	2T7X500	15p	2N2828	12p
ACY17	25p	BCY39	£1.80	MJ201	£1.70	OC72	17p	2T7X511	20p	2N2829	12p
ACY18	25p	BCY40	85p	MJ250	65p	OC75	25p	2T7X504	50p	2N3055	25p
ACY19	30p	BCY70	22p	MPS2951	£1.95	OC76	25p	2T7X531	30p	2N3055	50p
ACY20	25p	BCY71	22p	MPS3055	85p	OC77	40p	2T7X550	25p	2N3232	75p
ACY39	55p	BD121	75p	MM1613	25p	IN65	25p	IN65	55p	2N3235	95p
AD140	85p	BD123	75p	MM1712	60p	OC83	25p	IN814	35p	2N3702	14p
AD149	85p	BD124	80p	MPP103	45p	OC84	25p	IN816	35p	2N3703	12p
AD161	40p	BD131	75p	(2N5457)	35p	OC139	30p	IN4001	8p	2N3704	12p
AD162	40p	BD132	75p	MPP104	45p	OC140	30p	IN4002	8p	2N3705	12p
AF114	25p	BD153	75p	(2N5458)	35p	OC171	30p	IN4004	10p	2N3707	12p
AF115	25p	BD156	75p	MPP105	45p	OC200	50p	IN4005	12p	2N3708	12p
AF116	25p	BDY11	£1.40	(2N5459)	45p	OC220	60p	IN4006	15p	2N3709	12p
AF117	25p	BDY17	£1.80	MPSA06	35p	OC291	75p	IN4022	15p	2N3771	£2.70
AF118	60p	BDY19	£1.85	MPSA16	30p	TIP29A	45p	IN4148	7p	2N3772	£2.75
AF172	30p	BF152	20p	MPSA56	35p	TIP30A	55p	2N699	25p	2N3773	£2.95
AS226	30p	BF194	14p	MPSU06	75p	TIP32A	45p	2N699	25p	2N3819	35p
AS221	30p	BF195	14p	MPSU06	75p	TIP32A	45p	2N699	25p	2N3820	35p
BA102	30p	BFX29	30p	NKT135	35p	TIP33A	£1.05	2N705	15p	2N3866	60p
BA112	30p	BFX84	30p	NKT222	25p	TIP34A	£1.85	2N705A	15p	2N3904	22p
BA114	30p	BFX85	30p	NKT222	25p	TIP34A	£1.85	2N705A	15p	2N3905	22p
BA156	15p	BFY08	30p	NKT404	80p	TIP38A	£2.75	2N709	15p	2N4058	12p
BC107	40p	BFX88	30p	NKT773	30p	TIP41A	75p	2N1132	25p	2N4059	12p
BC108	40p	BFY10	35p	NKT774	25p	TIP42A	90p	2N1302	15p	2N4060	12p
BC147	12p	BFY44	50p	OA5	20p	TIP29B	50p	2N1303	15p	2N4061	12p
BC148	12p	BFY46	50p	OA6	20p	TIP30A	55p	2N1304	15p	2N4128	17p
BC149	12p	BFY51	25p	OA7	10p	TIP31B	70p	2N1305	25p	2N4288	15p
BC149	12p	BFY52	25p	OA7	10p	TIP32B	82p	2N1306	25p	2N4287	15p
BC153	14p	BFY65	25p	OA79	12p	TIP33B	£1.12	2N1307	25p	2N4288	15p
BC157	14p	BFY69	25p	OA80	12p	TIP34B	£1.68	2N1309	25p	2N4289	15p
BC158	14p	BSW63	85p	OA90	10p	TIP35B	£2.81	2N1309	25p	2N4290	80p
BC159	14p	BSW68	85p	OA91	10p	TIP36B	£3.84	2N1613	25p	2N4444	£1.90
BC189C	14p	BSY95A	12p	OA210	10p	TIP41B	83p	2N1711	25p	2N4871	35p
BC183	14p	C126	40p	OA210	10p	TIP42B	95p	2N2147	70p	2N4920	80p
BC184	14p	BY100	15p	OA211	10p	TIP29C	71p	2N5190	65p	2N5191	£1.10
BC212	14p	BY126	20p	OC16	90p	TIP31C	85p	2N2218	25p	40360	50p
BC213	14p	BY148	20p	OC17	90p	TIP32C	85p	2N2219	25p	40361	50p
BC214	14p	BY164	65p	OC22	55p	TIP33C	£1.30	2N2222	20p	40362	50p
BC238	12p	IS100	15p	OC26	65p	TIP34C	£1.90	2N2224	20p		
BC239	12p	IS103	15p	OC28	65p	TIP35C	£3.20	2N2386	70p		

## S.C.R.s

CRS1/05	40p	2N2846	£1.50
CRS1/10	56p	2N2804	25p
CRS1/20	60p	2N2805	25p
CRS1/40	65p	2T7X107	15p
CRS1/60	90p	2N2807	25p
CRS1/80	90p	2N2826	12p
CRS2/10	62p	2N2827	12p
CRS3/20	82p	2N2828	12p
CRS3/40	90p	2N2829	12p
CRS7/400	£1.00	2N3055	50p
CRS16/100	85p	2N3055	50p
CRS16/200	90p	2N3232	75p
CRS16/600	£1.60	2N3235	95p
CRS16/800	£1.60	2N3702	14p
CRS16/1000	£1.60	2N3703	12p
CRS16/1200	£1.60	2N3704	12p
CRS16/1400	£1.60	2N3705	12p
CRS16/1600	£1.60	2N3707	12p
CRS16/1800	£1.60	2N3708	12p
CRS16/2000	£1.60	2N3709	12p
CRS16/2200	£1.60	2N3771	£2.70
CRS16/2400	£1.60	2N3772	£2.75
CRS16/2600	£1.60	2N3773	£2.95
CRS16/2800	£1.60	2N3819	35p
CRS16/3000	£1.60	2N3820	35p
CRS16/3200	£1.60	2N3866	60p
CRS16/3400	£1.60	2N3904	22p
CRS16/3600	£1.60	2N3905	22p
CRS16/3800	£1.60	2N4058	12p
CRS16/4000	£1.60	2N4059	12p
CRS16/4200	£1.60	2N4060	12p
CRS16/4400	£1.60	2N4061	12p
CRS16/4600	£1.60	2N4128	17p
CRS16/4800	£1.60	2N4288	15p
CRS16/5000	£1.60	2N4287	15p
CRS16/5200	£1.60	2N4288	15p
CRS16/5400	£1.60	2N4289	15p
CRS16/5600	£1.60	2N4290	80p
CRS16/5800	£1.60	2N4444	£1.90
CRS16/6000	£1.60	2N4871	35p
CRS16/6200	£1.60	2N4920	80p
CRS16/6400	£1.60	2N5191	£1.10
CRS16/6600	£1.60	40360	50p
CRS16/6800	£1.60	40361	50p
CRS16/7000	£1.60	40362	50p

## TRIACS

TXL228B 8A 400V	95p
SC40D	£1.40
SC40E	£1.65
SC45D	£1.70
SC45E	£2.10
SC50D	£2.42
SC50E	£2.70
DIAC	£2.50

## LINEAR I.C.s

LM309K SV, 1A, Volt. Age Reg	£2.10
LM723C 2.37V, 150mA Voltage Reg	£1.05
MFC400 250mV Audio	60p
TBA800 SWT. A/D L.	£1.50
709C Op Amp D.I.L. TO99	45p
741C Op Amp 814 D.I.L./TO99	55p
748C Op Amp D.I.L.	75p
747C Dual Op Amp	£1.20
ZN414 Radio I.C.	£1.25
TAD100 Radio I.C.	£1.90
Int. Filter	£1.90
CA301A	£1.55
CA301B	£1.00
CA302B	£1.00
CA303B	£1.20
CA304B	£1.00
CA307A	£1.60
CA3090Q	£4.85
MC1303	£2.20
SN7623 SW Audio I.C. with circuit	£1.75

## BRIDGE RECTIFIERS

WD2 1A 200V	38p
BY164 1-4A 200V	57p
MDA952Z	6A 100V 80p

## ZENER DIODES

BZ708 Series 400mV	12p
3V-30V 5% 1p	
1-5W range	25p
10W range	45p

## L.E.D.

TIL209	28p
HP5082	28p
MA2082R	25p
L.D.R.	
ORP12	60p
NE555 Timer	90p

## METAL BOXES

ALUMINUM BOXES IDEAL FOR VEROBORD WITH BASE AND P.K. SCREWS					
Box 4	4"	1 1/2"	High	50p	
Box 4	4"	2 1/2"	High	80p	
Box 4	4"	3 1/2"	High	110p	
Box 4	4"	4 1/2"	High	140p	
Box 4	4"	5 1/2"	High	170p	
Box 4	4"	6 1/2"	High	200p	
Box 4	4"	7 1/2"	High	230p	
Box 4	4"	8 1/2"	High	260p	
Box 4	4"	9 1/2"	High	290p	
Box 4	4"	10 1/2"	High	320p	
Box 4	4"	11 1/2"	High	350p	
Box 4	4"	12 1/2"	High	380p	
Box 4	4"	13 1/2"	High	410p	
Box 4	4"	14 1/2"	High	440p	
Box 4	4"	15 1/2"	High	470p	
Box 4	4"	16 1/2"	High	500p	
Box 4	4"	17 1/2"	High	530p	
Box 4	4"	18 1/2"	High	560p	
Box 4	4"	19 1/2"	High	590p	
Box 4	4"	20 1/2"	High	620p	

## ALUMINUM BOXES WITH SLOPING TOP PANEL—IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS

AB20	2" High at front 6" Slides to front	£2.80
AB21	2" High at front 6" Slides to front	£2.80
AB22	2" High at front 6" Slides to front	£2.80
AB23	2" High at front 6" Slides to front	£2.80
AB24	2" High at front 6" Slides to front	£2.80
AB25	2" High at front 6" Slides to front	£2.80
AB26	2" High at front 6" Slides to front	£2.80
AB27	2" High at front 6" Slides to front	£2.80
AB28	2" High at front 6" Slides to front	£2.80
AB29	2" High at front 6" Slides to front	£2.80
AB30	2" High at front 6" Slides to front	£2.80
AB31	2" High at front 6" Slides to front	£2.80
AB32	2" High at front 6" Slides to front	£2.80
AB33	2" High at front 6" Slides to front	£2.80
AB34	2" High at front 6" Slides to front	£2.80
AB35	2" High at front 6" Slides to front	£2.80
AB36	2" High at front 6" Slides to front	£2.80
AB37	2" High at front 6" Slides to front	£2.80
AB38	2" High at front 6" Slides to front	£2.80
AB39	2" High at front 6" Slides to front	£2.80
AB40	2" High at front 6" Slides to front	£2.80

## ALSO STOCKED

Electrolytic Capacitors Mullard, Sprague, Lorin etc  
Polyester, Polystyrene Silver Mica Capacitors etc  
Resistors 1/2W Potentiometers, carbon, wirewound  
Preset, Rectilinear multitrans Axial Soldering Irons  
switches, rotary, slide, toggle, etc Cable, veroboard

## \* \* \* SPECIAL OFFERS \* \* \*

MINIATURE MAINS TRANSFORMER. PRI 240V SEC 12V, 100MA Manuf., Hinchley Size 30 x 45 x 40mm F.C 53mm. Price 100-450, 1000-500 etc. 1,000-50p etc. 10,000-40p etc.	
3 CORE PVC INSULATED MAINS CABLE, GREY, 100-450, 1000-500 etc. Price 100-450, 1000-500 etc. 10,000-40p etc.	
50 GDE DUO O447 ELECTROFORMER. DOUGLAS Pk. 0.115 200, 220, 240 SEC 25-0-25-6V. 24A. £4.50 - 50p.	
240V. A.C. SOLENOID. Reversible operation; twin coil. Size approx 2 1/2 x 1 1/2 x 1 1/2 in. Price 100-450, 1000-500 etc. 10,000-40p etc.	
30 UNMARKED OC71 transistors £1.00	
25 UNMARKED 250mW Zenadode. 4.7V 5-1V 50. 2V. 7V. 9-1V 10V Measured and tested. Price 100-450, 1000-500 etc. 10,000-40p etc.	
Plate state voltage required £1.00	
50 GDE DUO O447 ELECTROFORMER. DOUGLAS Pk. 0.115 200, 220, 240 SEC 25-0-25-6V. 24A. £4.50 - 50p.	
TRANSFORMER PRI 0.115, 160, 225, 225, 245, SEC 35-0-35, 1.2A £4.50 - 50p. Price 100-450, 1000-500 etc. 10,000-40p etc.	
MULLARD TUBULAR CERAMIC IUF TRIMMERS (PROFESSIONAL) Type 982 801 0.8-2.2 pF } Price 10p etc. 991 0.8-1.3 pF } Price 10p etc.	
QUANTITY DISCOUNTS PLEASE TELEPHONE 801 0.8-2.2 pF } Price 10p etc. 991 0.8-1.3 pF } Price 10p etc.	
1000pF Feedthrough capacitor 5p etc. Miniature tubular P.C. trimmers 80p etc. 3-5 10pF 50p etc. 4p 0 Varley 700Ω relay 50p etc. £4.85 TO 5V VOLTAGE REGULATORS L005 5V 850mA L008 5V 850mA L037 15V 450mA £1.80 etc.	

## VEROBORD

# EXHIBITIONS ?!

**W**HAT is happening to the R.S.G.B. National Mobile Rally? This annual event, as many readers will be aware, took place in the grounds of Woburn Abbey during the month of August.

It was not the day of continuous rain that made the exhibition part of the rally a wash-out—attendance was good despite the climatic conditions. Apathy on the part of the organisers and many exhibitors resulted in dismal displays on nameless stalls.

Who were these nameless exhibitors? These people were, in effect, representatives of one of our greatest national activities—Amateur radio and the amateur electronics constructor. The question being asked was, “surely this is not the R.S.G.B. National Mobile Rally? I must have taken the wrong turning!”

Exhibitors displaying new equipment and those displaying ‘surplus’ gear were intermixed. Yours truly spent a considerable amount of time trying to find the whereabouts of various exhibitors, without avail. Little information was forthcoming—even from the R.S.G.B. stand itself! Well-established and respected manufacturers and distributors were conspicuous—by their absence. Who can blame them?

Someone had better pull up their socks or we may see the rapid demise of what should be, as the title implies, our *National Mobile Rally*.

Do you remember the Radio Communications or Hobbies Exhibitions sponsored by the Radio Society of Great Britain? They were held annually in the London area and were extremely popular. What happened to them.

Practical Wireless and other major organisations, gave their support on numerous occasions and we are justly proud of the part that we contributed by showing our flag, on behalf of the radio and electronic constructor.

This hobby of ours encompasses an exceedingly wide sphere in the field of electronics and it is the responsibility of the Editor and his staff—as a team—to balance the editorial contents of each issue—to cater for many tastes. The satisfaction that the constructor derives from ‘switching it on’ is extremely gratifying and indeed therapeutic. We are indeed fortunate in that we live in an era of component plethora. Of course, there are shortages in many areas, but we suggest that the pessimists cast a careful eye over the pages of our *1974/5 PW Buyers' Guide to Radio and Electronic Components*.

Many new items are included, each month by advertisers in their respective columns. Take a good look at the small print, you could be pleasantly surprised!

We shall be exhibiting at the 1974 International Audio Festival and Fair, Olympia, London. Many *PW* constructional projects will be on show, including unique constructional designs not yet published in this country. A further exciting development in the *PW Tele-Tennis* constructional project will also be unveiled.

Members of the editorial and advertising departments will be in attendance to deal with enquiries. We shall also have a limited number of free ‘give-aways’ to visitors.

Don't forget the *PW* slogan—*Stay tuned to PW* for full coverage of the finest and up-to-the minute constructional projects.

A date for your diary—*Practical Wireless*, Stand B12, International Audio Festival & Fair, Olympia, 28th October—3rd November inclusive.

LIONEL E. HOWES—Editor.

# NEWS...

## Crofton move

**C**ROFTON ELECTRONICS have moved. Their new address is: 124 Colne Road, Twickenham, Middlesex. (Tel: 898 1569).

## A foolproof Electric Lock

**S**OME quite clever ideas have appeared in journals for electronic locks. But our vote goes to a professional approach recently announced which, as far as we can see, is almost fool-proof. The code for this lock is carefully stored in a CMOS shift register memory. When the “electronic” key is inserted, the code in the key is interrogated by the lock which compares it with the code in its memory. If the two codes are identical the lock will open. The key itself contains another shift register with the identical code in its memory banks. Even a small 32-bit memory would provide a possible four million combinations.

When the key is inserted into the lock it activates a micro-switch. This causes the lock to transmit a series of pulses which in turn make the “key” enter its code into the lock for comparison.

Because the key does not emit signals (i.e. magnetic or sonic or anything else) it is impossible to “read” the code from the key. Again, any exploratory signals sent into the lock would immediately alter or destroy its memory (fail safe).

One last cunning asset. The speed of operation of the memory circuits in the lock is fast when opening the door with the correct key. But slow by “logic” standards. If you were to permutate all combinations possible by plugging some sort of pulsing device into the lock instead of the key—it would take well over a year to run through all the possible combinations. Sorry—not available on the market yet and that's all the information we can get at present.

**Not to be missed —**

**T**HE LATEST Heathkit Catalogue is now available free from: Heath (Gloucester) Limited, Bristol Road, Gloucester, GL2 6EE. Write, or phone Gloucester 29451, for a copy. Or if you happen to be in London or Gloucester, call in and collect one. The London Heathkit Centre is at 233 Tottenham Court Road, and the Gloucester showroom is next to the factory in Bristol Road.

The catalogue contains details of the very large range of electronic kits, many available for the first time in this country.

It talks in detail about kit building "The Heathkit Way" and shows how easy it is to build a Heathkit. Even a complete novice need have no worries as the instruction manual, with the aid of large pictorials and step-by-step instructions, leads you every step of the way.

Its 64 pages give details of many exciting models for home construction, ranging from a large selection of audio and Hi-Fi equipment through electronic calculators, digital electronic clocks, electronic thermometers, an ultrasonic burglar alarm, to test instruments for the electronic hobbyist and home car servicer. Even a 12 inch black and white portable television kit is available.

**Heathkit's Catalogue**

New kit models include an f.m. tuner with digital readout and computer tuner, a 4 channel SQ amplifier, a battery powered electronic thermometer and a de-luxe digital electronic clock with alarm. All models are available for cash or on extended credit terms through the very popular Heath Money Budget Plan. A free technical consultation service is in operation both before and after purchase.

**Hi-Fi Accessories by Bib**

**B**IB HI-FI Accessories Limited announce the publication of a comprehensive 16-page full colour catalogue, which illustrates and describes their very large range of hi-fi accessories which now comprises more than 70 products.

The catalogue has been designed so that it can be easily reprinted in foreign languages and arrangements are already in hand to print it in French, German and Italian.

For the UK market a single sheet retail price list is inserted in the catalogue.

*Bib Hi-Fi Accessories Ltd., PO Box 78, Hemel Hempstead, Herts, HP2 7EP.*

**Wolsey's Colour King at sea**

**W**OLSEY ELECTRONICS equipment is now being increasingly used on marine installations and the most recent of these, through Aerialwork Limited of Southampton, their agents for Southern England, has been the installation of a communal TV and radio system to the officers and crews quarters on the car ferry "Eagle". In order to receive various transmitters whilst at sea, a Wolsey Broad Band "Colour King" u.h.f. aerial and FM411 array were erected with a rotator motor and remote control unit. The aerials and mast were specially treated to withstand exposed sea conditions. The well-proved Wolsey "Mercury" amplifier was fitted and provision was made for a monochrome video cassette recorder and additional outlet points to public rooms should this be required at some future date.

The 11,500 ton "Eagle" which is controlled by one of the P & O Group of Companies—Southern Ferries—is the largest on/off car ferry to use the port of Southampton and operates a regular service to Lisbon, Algeiras and Tangier.

**You have been warned! Don't forget to order your copy of the December issue of *Practical Wireless* . . . look for your Free PW Miniature Screwdriver.**

**Start building the PW Kempton with our December issue. This is a quality stereo cassette player for your car; build yourself an inexpensive capacitance bridge that really works, and the third section of our 1974/5 PW Buyers Guide to Radio and Electronic Components will also be included in our December issue.**

**In the January 1975 issue of PW, we start the New Year with constructional series on radio control. Don't forget to place a permanent order with your newsagent, or write to our subscription department.**

**Further details of the December issue on page 609.**

# FM AERIAL pre-amplifier

KEITH CUMMINS


**L**ONG-DISTANCE reception of weak FM signals is possible provided that a high gain aerial is used and that the receiver has high sensitivity. Some older types of receiver lack the sensitivity of their modern counterparts and the use of an aerial amplifier can improve reception considerably.

We have to be careful in the use of such an amplifier however, since high gain is not the only pre-requisite. If the amplifier adds as much noise as it increases the signal, then we are no better off. The amplifier must have a good noise factor, that is, it increases the signal by a much greater amount than it increases the noise.

Another aspect we have to consider is the type of reception we expect, having provided the amplifier. If the incoming signal is very weak indeed then we may be able to improve it, but if it fades away to nothing, no amount of amplification will bring it back again. This situation can exist during fading conditions, when total cancellation of the signal at the aerial occurs because of multipath reception. An amplifier can be useful, however, since it shortens the time during which the signal is unusable. Imagine a threshold level below which the signal must not fall if a satisfactory signal-to-noise ratio is to be maintained; if the amplifier lifts the entire incoming signal, this can fall to a lower level before becoming unsatisfactory.
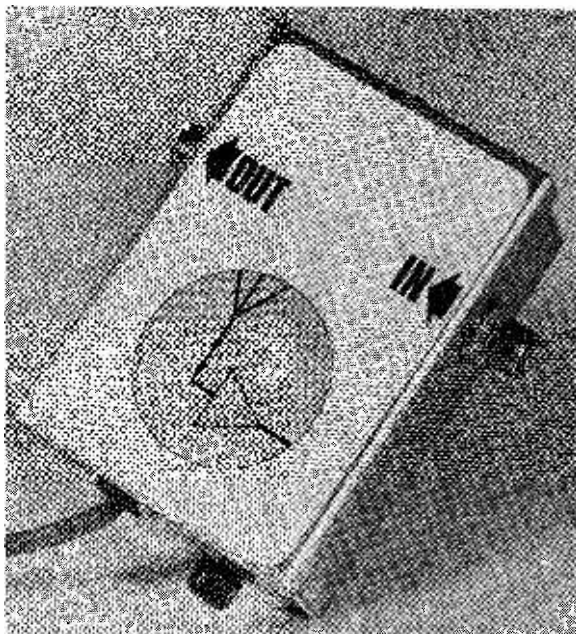
## CROSS MODULATION


The VHF FM band is becoming quite crowded and the weak signals we wish to amplify may be situated very close to a strong local transmission. Unless our amplifier is correctly designed, a strong possibility exists that cross-modulation will occur between the various signals present, due to the high amplitude of the local signals. The signals we wish to receive may then become completely lost in the mess which results. Once this has happened, it is impossible to



separate the signals again, so we must prevent such a thing happening in the first place.

Cross-modulation can not only occur in the amplifier but also in the input stages of the receiver. A valve receiver is far more tolerant of high input levels than its transistor counterpart. Too much amplification before the receiver's RF stage can therefore cause intermodulation and it will be seen that excessive gain can be a real disadvantage. Any aerial amplifier used for FM work should therefore not have so much gain that the local signals will cause cross modulation, have enough gain to substantially improve weak signals, and, itself, have

Fig. 1: The two FETs are connected in a cascode circuit, the first being an amplifier while the second is a buffer or isolating stage.

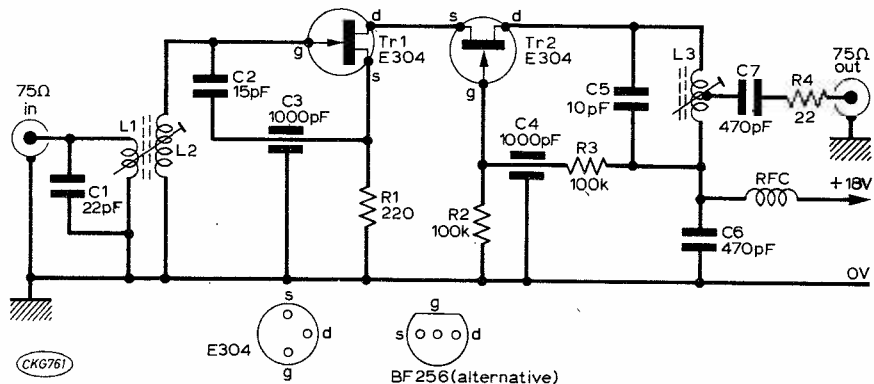



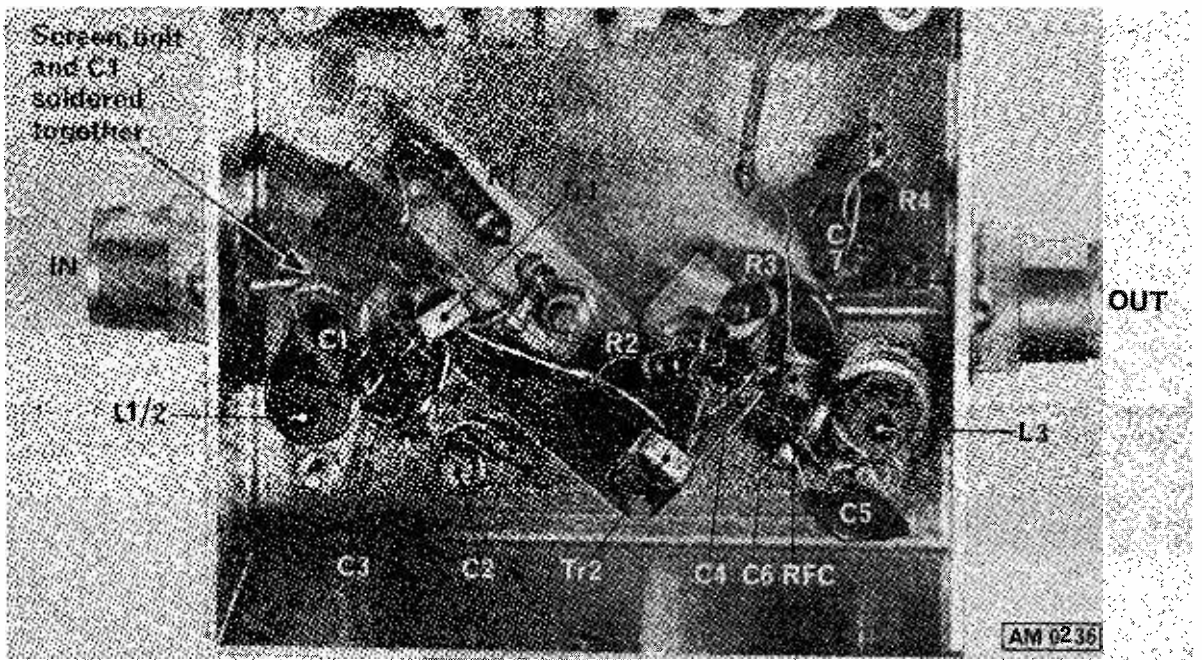


Fig. 2: This view of the amplifier shows all the components of Fig. 1. Most are mounted on either side of a metal screen to which earth returns can be soldered.

good cross-modulation characteristics. Above all, its signal-to-noise ratio should be as high as possible.

The cross-modulation requirements basically rule out the use of ordinary bipolar transistors. A very simple amplifier made up to prove the point produced a total jumble of signals which could not be separated. The use of field-effect transistors is much to be preferred, since they have a square law characteristic which helps prevent cross modulation from occurring.

## A PRACTICAL DESIGN

The circuit of Fig. 1 shows a very successful aerial amplifier using FETs in a cascode configuration. The 75 ohm aerial signal is fed to the aerial coil L1, which is tightly coupled to L2. C1 is included to improve the aerial matching resulting in a useful improvement in signal-to-noise ratio. The input circuit to the FET gate is tuned by C2 connected from gate to source of the FET, the source being decoupled to earth by the feed-through capacitor C3. This input configuration has been found to provide the optimum energy transfer from the aerial to the FET.

As in all cascode configurations, the first stage provides the gain while the second provides isolation from input to output, so preventing feedback and instability. It is possible to provide neutralisation over just one FET stage, but because of the bandwidth requirements of our amplifier, the neutralisation could not be optimised and so the gain would not be constant over the band.


The arrangement shown is a satisfactory compromise between gain and bandwidth so that a useful gain of 12 to 15dB is obtained over the range 88-98 MHz. The output tuned circuit consisting of C5 and L3 has a tapping for the output, which is taken to

the socket via C7 and R4. The input circuit required additional capacitive reactance to optimise the matching and it was found that the output circuit needed R4 to improve matching and prevent spurious instability. This could be the result of coupling the amplifier to the receiver by a coaxial cable less than half a wavelength long. The receiver's input impedance need not be entirely resistive.
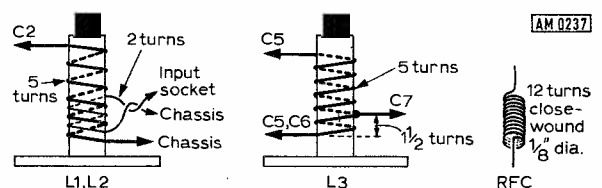
## CONSTRUCTION

A suggested layout is shown in Fig. 2. Great care should be taken when handling and connecting the FETs. The unit should not be attached to any other apparatus while undergoing construction and the soldering iron should be earthed. This will ensure that the devices are not subjected to voltages which might damage them. Information on the coils is given in Fig. 3.

Tuning is quite simple. An attenuator should be fitted in the aerial feed so that with the amplifier connected, a weak signal is received. The cores of




Note: L2 and L3 approx. 20 swg copper wire, spaced 1-diameter of wire. L1 insulated copper wire, interwound with L2.

Fig. 3: Details of the coils and the RFC. Follow information carefully to ensure coils will tune inside the FM band, using the adjustable cores.

# ★ components list

Resistors		
R1 220Ω	R3 100kΩ	R5 390Ω
R2 100kΩ	R4 22Ω	
All $\frac{1}{2}$ or $\frac{1}{4}$ W, 5 or 10%		
Capacitors		
C1 22pF SM	C5 10pF SM	
C2 15pF SM	C6 470pF SM	
C3 1000pF Feedthrough	C7 470pF SM	
C4 1000pF Feedthrough	C8 1000μF 30V	
Semiconductors		
Tr1 E304* or BF256*	D1 1N4002	
Tr2 E304* or BF256*	D2 ZF18 (zener 18V)	
* see text.		
Miscellaneous		
T1, transformer 240V/12+12V, F1, fuse 100mA and holder. Aluminium box (Type AB9) 4 x 2½ x 1½ in. Coaxial sockets (2). Coil formers, polystyrene ¼ in. dia. with cores.		

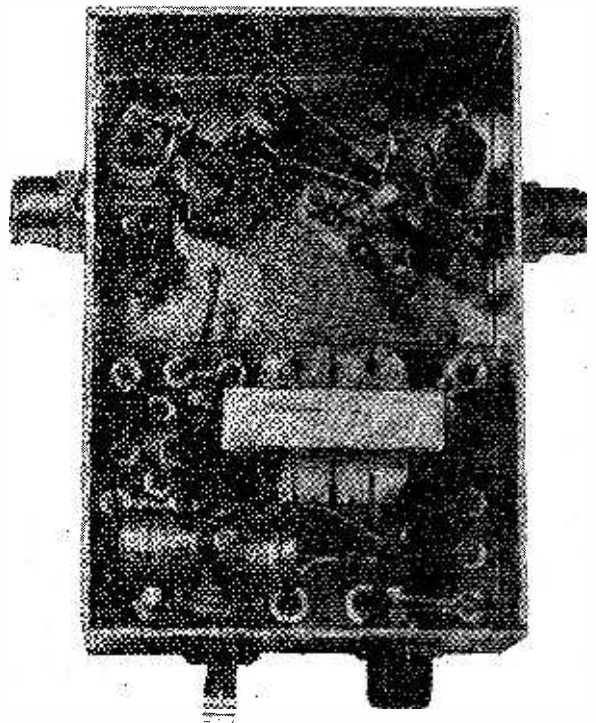

The finished pre-amplifier. The power supply board shown here was taken from a commercial pre-amplifier.

the coils can then be adjusted for optimum performance. They should be set to approximately half way out of the windings as a starting position.

## RESULTS

Results using the prototype are most encouraging. A Wolsey FM4 aerial is fitted to a 12ft mast attached to a chimney. Low-loss coaxial cable links the aerial to the amplifier, which is then connected to the Quad FM1 tuner. The receiving site is in Southern Hampshire and the aerial is beamed half way between London and Wrotham. There is virtually no difference between the reception of local signals from the Isle of Wight and those from Wrotham, including these stations' "local" transmissions, Radio Solent and Radio London. Capital Radio can be received, even though it is adjacent to Radio Solent. Mono reception of Capital is satisfactory 90% of the time; stereo about 50% at the time of writing. Other signals received are Radio Bristol, Radio Oxford and LBC which seems very consistent.

It should be pointed out that all long-range reception is vulnerable to interference from electrical apparatus such as vacuum cleaners and drills. The hash from a vacuum cleaner nearby may completely obliterate the distant signal despite all our efforts to receive it. The local oscillators of TV receivers operating on Band 1 may also radiate and

cause interference. This problem, however, is becoming less troublesome as more and more viewers move to UHF.

Reflected signals from aircraft appear in and out of phase with the main signal so cancelling at the aerial in a cyclic manner. This gives rise to drop-out of the signal accompanied by a "chuff-chuff" noise, something like a steam train. Despite these problems, however, worthwhile reception of distant signals is possible for a high proportion of the time, provided a good aerial is available.

Power for the amplifier can be obtained from a simple power pack as shown in Fig. 4 or, alternatively, two PP9 batteries may be used. The current drain is only 4mA, so battery life would be long.

The Siliconix FETs have been chosen for their excellent signal-to-noise ratio and they can be obtained from Atlantic Semiconductors, 143 Loughborough Rd, Leicester LE4 5LR. The alternative BF256 can be obtained from Ambit International, 37 High St., Brentwood, Essex CM14 4RH.

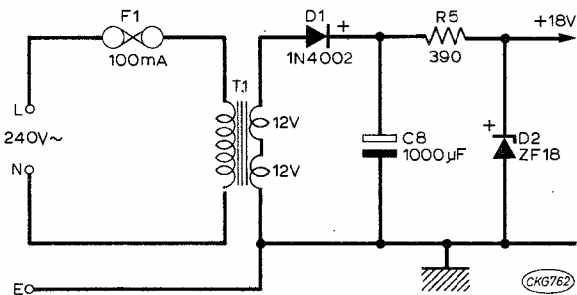


Fig. 4: Circuit of a suitable power supply for the pre-amplifier.

**PW 'DERBY'  
STEREO HEADPHONE AMPLIFIER  
AUGUST 1974**

Fig. 1: Bottom, right. "To R123/Tr103 base" should read 'collector'.

Fig. 1: In the symbol for Tr5 the collector should be the emitter, with arrowhead inwards (PNP). The emitter should be the collector, to base Tr6, C16 and D2. The diagram of the component layout, Fig. 8, is correct and not affected.

Fig. 9: On the DISC/RADIO switch S1, pole connection S1d should be marked R106, not R116.

# f. m. stereo tuner

## CONSTRUCTIONAL DETAILS

Construction of the tuner is very simple but it should not be undertaken by someone who has not had some previous experience in miniature electronic circuitry. The components are closely packed and may be damaged easily if overheated by a soldering iron.

Because of the high gain in parts of the circuit and the high frequencies involved, careful attention to the layout of the circuit is very important if instability is to be avoided and best performance obtained. Great care must be taken to ensure that no undesirable stray coupling can exist between sensitive parts of the circuit.

Fig. 4 shows the underside of a printed wiring board which has been designed to ensure stable operation and Fig. 5 shows the component side of the same board. This consists of a sheet of copper, or ground plane, broken only by bare patches where component leads pass through. The narrowness and close proximity of some of the conductors on this board, however, make it difficult to produce by normal 'kitchen table' techniques. Those readers who prefer to purchase a ready-made board may do so from the firm mentioned in the components list.

## SCREENING

Liberal use has been made of screening between circuits and it is with these screens that construction should begin. They consist of strips of double-sided copper-clad board 1" high with lengths as shown in Fig. 6.

Start with the screen marked AB and put a small blob of solder on the bottom corner at both sides at point B and, on the side facing the printed wiring board only, at point A. Then hold the screen in position and run solder between it and the board to tack it into place at the points at which the solder blobs were applied. When you are sure that the screen is vertical and in the correct position it may be finally fixed by producing a fillet of solder between both sides and the board. This can be done by running the soldering iron along in contact with board and screen whilst feeding in solder.

Repeat this process for screens CD, DE and FG but leave HJ until later to allow access to the IF compartment. Where two screens meet they should be joined by a fillet of solder in the same manner. Small marks are provided on the underside of the board to indicate the correct positions of the screens.

## TUNER HOUSING

Fig. 6 shows the completed tuner mounted in an 8 $\frac{3}{4}$ in x 5 $\frac{3}{4}$ in die-cast box with all component positions marked. Start by placing the board and transformer in the box where shown and centre-punching through the mounting holes. Drill and countersink 6BA holes for the board mounting bolts and 4BA holes for the transformer.

Holes should be drilled in the side of the box for the sockets for aerial input and audio output and for the 17 leadthrough insulators carrying connections to the front panel as listed in Table 1. Two further holes are required in the end of the box for the mains input grommet and fuseholder. The positions for these components are shown in Fig. 6 and the photograph of the tuner box which appeared in Part 1.

Mount all the components except the board, remembering to fix a couple of solder tags under one of the transformer mounting bolts. Connect two separate insulated wires to one of these earthing tags and route them close to the sides of the box to leadthrough terminals 14 and 17. Next connect wires to the two 12V terminals on the transformer and attach them to terminals 15 and 16. These wires carry current for the scale illuminating lamps on the control panel. Where a number of wires run together in close proximity it is convenient and tidy to make them up into a cable form.

TABLE 1

Leadthrough insulator No.	Connect to PCB point
1	X
2	M
3	SW M
4	SW
5	SS
6	SD OUT
7	SD IN
8	SQ OUT
9	SQ IN
10	LAMP
11	V
12	L
13	H
14	EARTH TAG
15	12 VAC (T301)
16	12 VAC (T301)
17	EARTH TAG

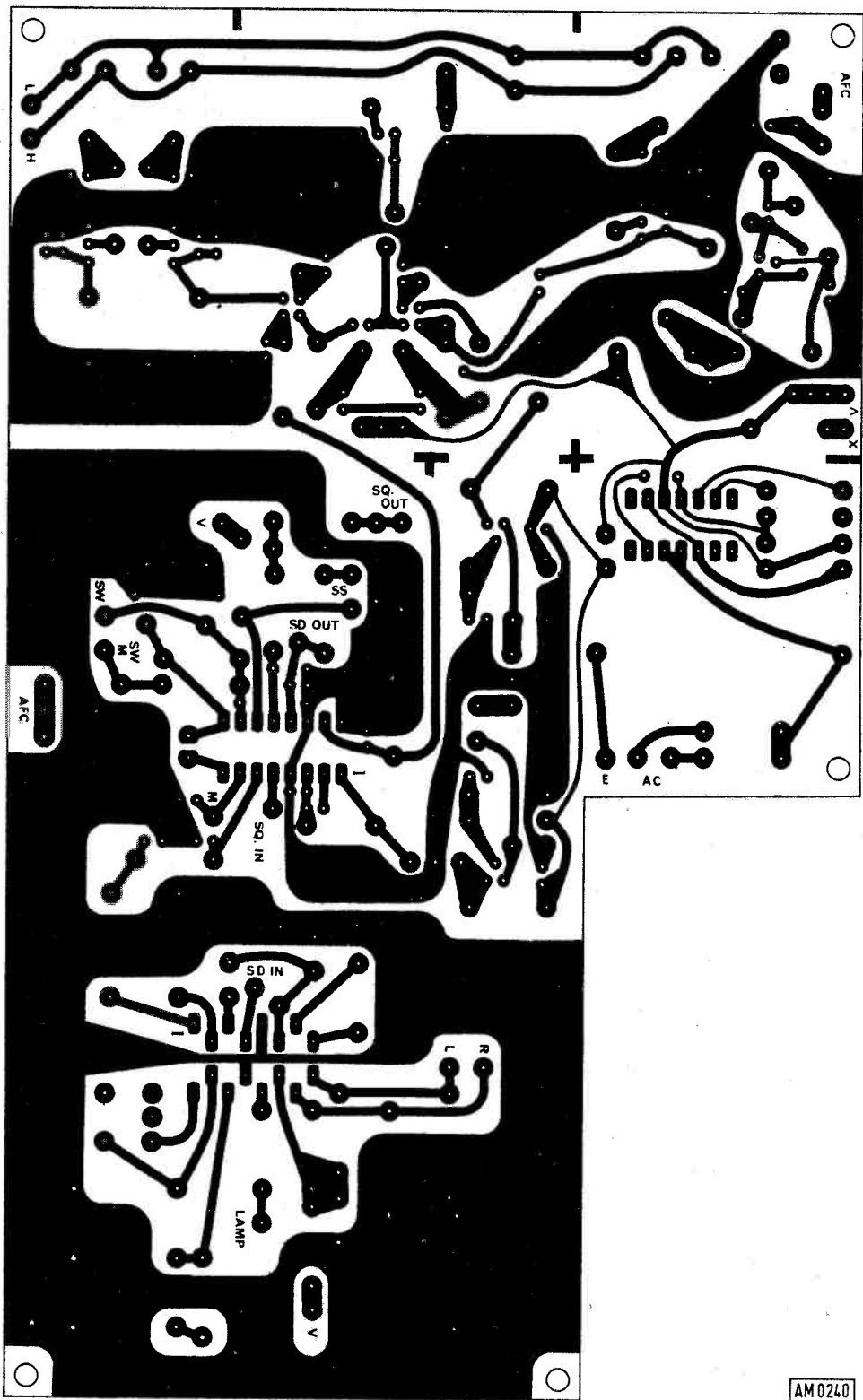


Fig. 4. Underside of printed circuit board, shown actual size.




# FREE!

**YOU HAVE BEEN WARNED!** Don't forget to order your copy **NOW**. The December issue of PW will carry your Free Miniature Screwdriver, invaluable in the home and in the electronic enthusiasts' workshop for adjusting miniature potentiometers, etc.

# IN NEXT MONTH'S PRACTICAL WIRELESS

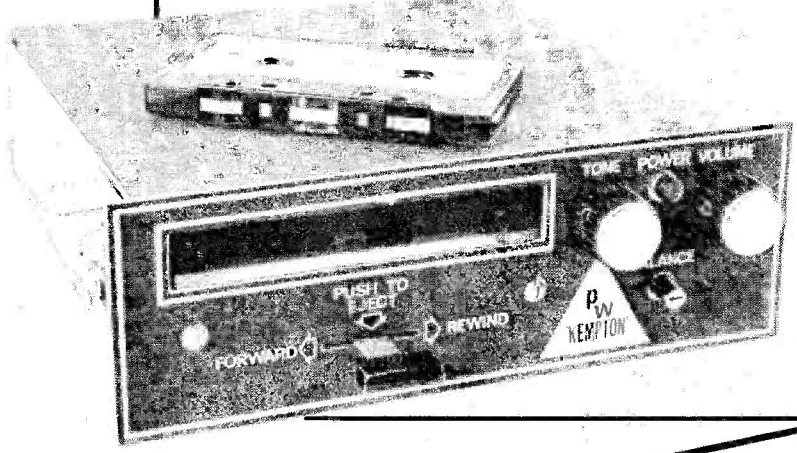
## PW 'KEMPTON' PART 1 CAR STEREO CASSETTE PLAYER



A quality stereo cassette player for your car. Using a Goldring-Lenco tape transport mechanism with automatic cassette ejection this design incorporates comprehensive noise suppression and gives a good 3 watts output per channel. The motor speed is electronically controlled and an automatic stop is included.

Also:-

### INEXPENSIVE CAPACITY BRIDGE

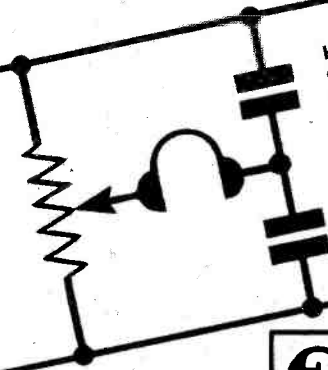

Hands up all those constructors with a box full of capacitors of unknown value... We thought so! Build the PW Inexpensive Capacity Bridge... measures capacitors in seconds, from a few picofarads to several microfarads.

1 PW B

2 PW Buyer

### 3 PW Buyers' Guide 74/5

We are sure that you have already found the first two parts of the Buyers' Guide to be of great interest, so don't miss the third section which will be included in the December issue of PW. The fourth and last section will appear in the January 75 PW thus completing a very valuable reference book.

MANY OTHER CONSTRUCTIONAL  
ARTICLES, SPECIAL FEATURES  
AND REGULAR COLUMNS.

**ON SALE IN NOVEMBER**



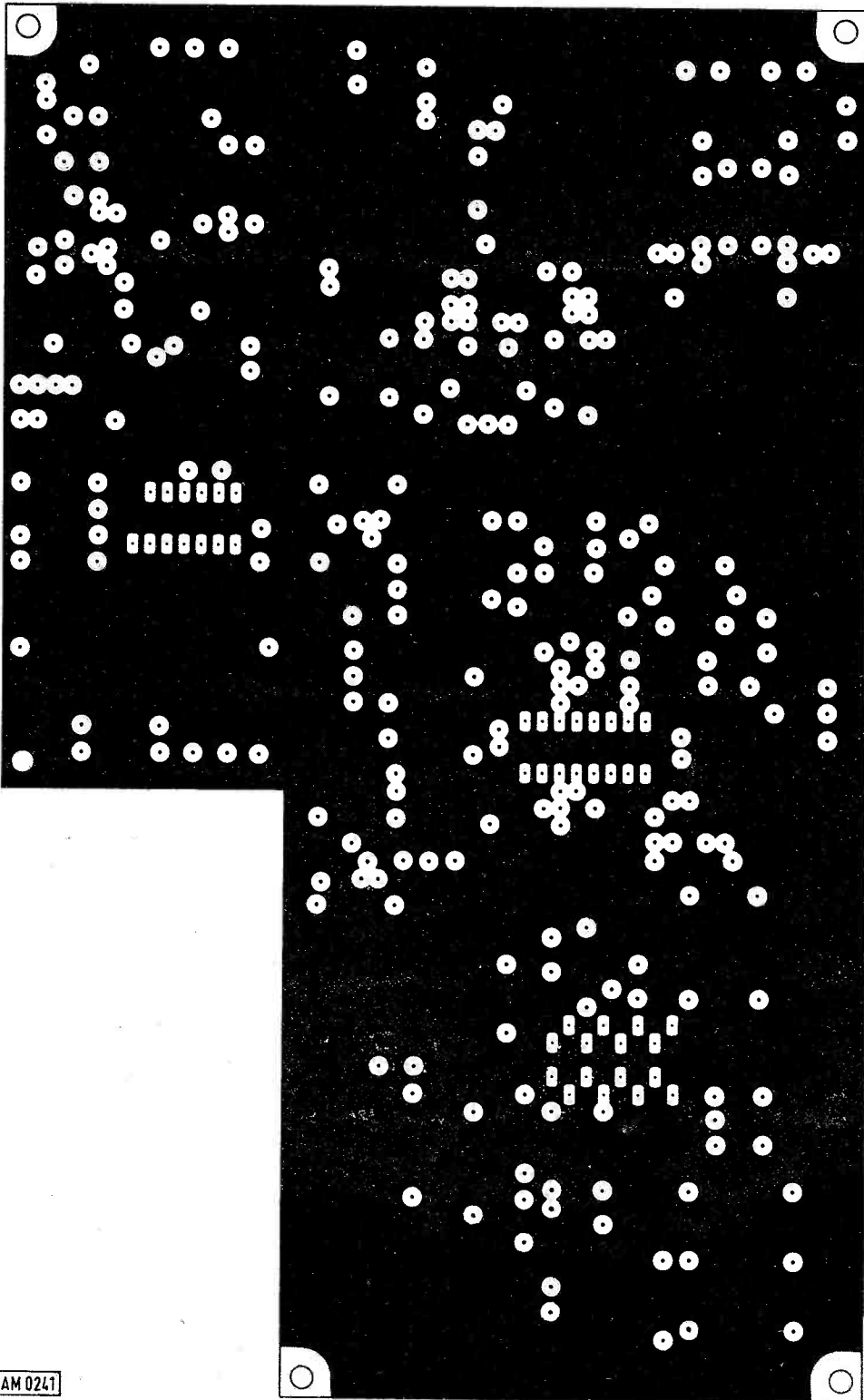




Fig. 6. Ground-plane side (top) of printed circuit board, drawn actual size.

# look!
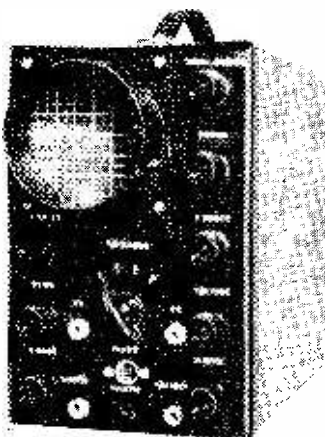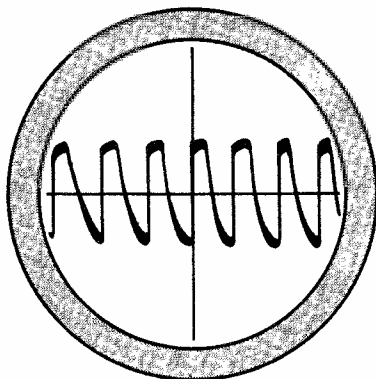
# electronics really mastered

**... practical  
... visual  
... exciting!**

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
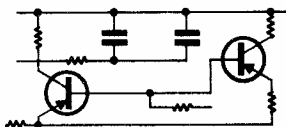
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW  
for  
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**,  
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:  
*we do not employ representatives*

NAME


**BLOCK CAPS**

ADDRESS

PLEASE WL 114

**special free gift also to all our students**

# BIG Discounts

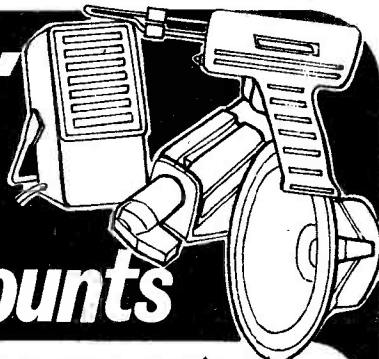

## ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£	GOODMANS 6½" 8 ohm		£
EMI 13" x 8" 3, 8 or 15 ohm	Plain	2-05	Dualcone	2-15	
With Co-Axial Tweeter	8 ohms only	2-20	ELAC 8" 8 ohm Dualcone	2-25	
Twin Tweeter		3-70	ELAC 8 ohm Dualcone 10 watt	3-50	
Type 350	8 or 15 ohm,	7-50	FANE 7" x 4" 3 or 8 ohm	1-00	
6½" 8 ohm, 10 watt		2-40	CELESTION 8" 15 ohm	1-55	
8" 8 ohm, 10 watt		3-75	ADASTRA 10" 8 or 15 ohm,	3-45	
12" 8 ohm, 20 watt		5-70	10 watt		
8" x 5" C/Mag. 5 watt		1-25	BAKER GROUP 25 12" 8 or	7-65	
8" x 5" Dualcone	8 ohm, 10 watt	2-45	15 ohm, 25 watt		
			P. & P.	30	
			5" 8 ohm, C/Mag.	85	
			2½" 8 ohm or 64 ohm	50	
			P. & P.	15	

TWEETER & CROSSOVER		£	Dome Tweeter 8 ohm, 30 watt		5-40
EMI 3½" or 8 ohm C/Mag		1-00	Crossovers CN23 (3 ohm),		
Cone Tweeter 8 or 15 ohm,	10 watt	2-40	CN23 (8 ohm), CN216 (16		
Cone Tweeter 8 ohm, 3 watt		1-45	ohm)		1-10
Horn Tweeter 8 ohm, 20 watt		6-40	P. & P.		10

KIT FORM CABINETS TEAK VENEER		£	18" x 11 x 9 with 13" x 8" cutout		4-25
12" x 12 x 6 with 8" 8" x 5" or	6½" and 3½" cut out.	2-45	for EMI 350		
17" x 10 x 9 with 8" or 13" x 8"	cutout	3-50	P. & P. ea.		45

MICROPHONES		£	CONDENSER MIKE 600 ohm,		9-35
CM70 Planet stick metal,	switch crystal	1-55	uni-dir		
DM160 Dynamic omni-dir.	ball metal	3-85	Cassette Stick Mike with R.		
UD130 50K/600 ohm, uni-dir.	ball metal	5-75	Control on/off switch		
			(2-5 & 3-5mm J/Ply)		1-45
			P. & P.		20

SOLDERING IRONS		£	X25 25 watt (low		1-90
ANTEX CN240 15 watt		1-90	leakage)		
SK 1 Kit (15 watt iron		3-30	P. & P.		10
2 spare Bib etc.)					

CARTRIDGES		£	BSR SC5M Stereo ceramic <th>2-70</th>		2-70
ACOS GP91/2SC or GP91/3SC	Stereo comp.	1-00	SX6H Stereo crystal		1-70
GP93/1 Stereo crys.		1-25	SX6M Stereo crystal		1-70
GP94/1 Stereo crys.		1-65	X5H Mono/stereo		1-40
GP95/1		1-35	X5M Mono/stereo		1-40
GP96/1		1-65	GOLDRING G800, G850 £3-85		£2-95
GP101		80	G800E		7-15
GP104		1-65	P. & P.		10p

SONOTONE		£	Sapphires 35 D. Diamond <th>1-25</th>		1-25
9THAC Stereo cer. diam.		1-70	Styli for GOLDRING G800 G850		1-95
19-TI Stereo crystal		80	G800E		3-95
			P. & P.		05

BATTERY ELIMINATORS		£	6, 7-5 or 9 d.c. output at		2-15
240v Input 6, 7-5 or 9 300mA		2-75	300mA		
12v d.c. input (specify output)			P. & P.		15

TAPES		£	7"		£
Stnd.	LP	DP	Stnd.	LP	DP
50p	65p	1-25p	85p	1-15p	2-10p
5½"	65p	80p	1-45p		
			P. & P. 1-3, 9p ea. 4 or more, lot 30p		

LOW NOISE CASSETTES		£	Cassette Head Cleaner <th>35p</th>		35p
C80	1-5	6-10	11-20		
C90	35p	33p	30p		
C120	45p	43p	40p		
	55p	52p	50p		

PLASTIC LIBRARY CASES		£	CASSETTE CASES		10p
For 5" Reels		18p	P. & P. 1-3, 5p ea. 4 or more, 20p		
5½" Reels		22p			
7" Reels		25p			

BIB ACCESSORIES		£	SPECIAL OFFER		£
Tape Editing Kit Ref. 23		1-25	SINCLAIR CAMBRIDGE		
Recording Tape		1-15	CALCULATOR (BATT.)		
Splicer Ref. 20		1-15	* 4½" x 2" x 11/16", wt. 3½ oz.		
Cassette Tape, editing Ref. 24		1-40	* Floating Dec. Point		
Cassette Salvage Kit Ref. 29		40p	* Algebraic Logic		
12's Cassette Case Ref. 34		£1-50	* 4 Operators with Constant		
Stylus Balance Ref. 32A		1-15	* 8 Digit Display		
Spirit Lever Ref. 46		50	Build £19-95		
Hi-Fi Stereo Test Cassette		1-90	Kit £14-95		
Groove-Kleen Record Cleaner		1-90			

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED. Subject to manufacturer increase and availability.

**Riversdale Electronics**  
Mail Order Department **PW11**  
P.O. Box 470, Manchester M60 4BU.

Brand new marked and tested ICs with full data and our own new applications booklet

LM380 2-3 W audio power amp 5 for £3.25 VAT extra  
LM381N HiFi stereo preamp 2 for £3.00 PP15p  
Mark all orders PW offer please and send to 37 High St., Brentwood, Essex CM14 4RH Valid whilst stocks last

# SPECIAL OFFER

See Also Our Advert Page 644

**ambit** international

## INTRODUCTORY OFFER

A V.C.O. by FHACHI 1Hz to 100kHz  
for £3-85p P. & P. 15p.

Size 2" L; 1½" W; ¾" H.

Input 12 to 24V DC (not centre tapped)  
18V input giving 10 volt constant amplitude output

Requires only a 1 meg ohm pot to tune entire range—or can be swept with a saw tooth input.

Enormous possibilities—music; synthesizers; filters; communications; frequency modulation etc.

Detailed application sheet with all purchases  
Sole Distributor.

## LOW FREQUENCY WOBBULATOR

Primary intended for the alignment of AM Radios Communication Receivers; Filters, etc. in the range of 250 KHZ to 5 MHZ, but can be effectively used to 30 MHZ. Can be used with any general purpose oscilloscope. Requires 12V AC input. Three controls—RF level sweep width and frequency. Price £3-50 A second model is available as above but which allows the range to be extended down in frequency to 20 KHZ by the addition of external capacitors. Price £11-50.

Both models are supplied connected for automatic 50 HZ sweeping. An external sweep voltage can be used instead. These units are encapsulated for additional reliability, with the exception of the controls (not cased not calibrated).

PLEASE ADD V.A.T. AT 8%  
OPEN 9 a.m. to 5.30 p.m. ANY DAY

**CHILTMEAD LTD**

7/9 ARTHUR ROAD, READING, BERKS.

(near Tech. College)

Tel.: Reading 582605/652916



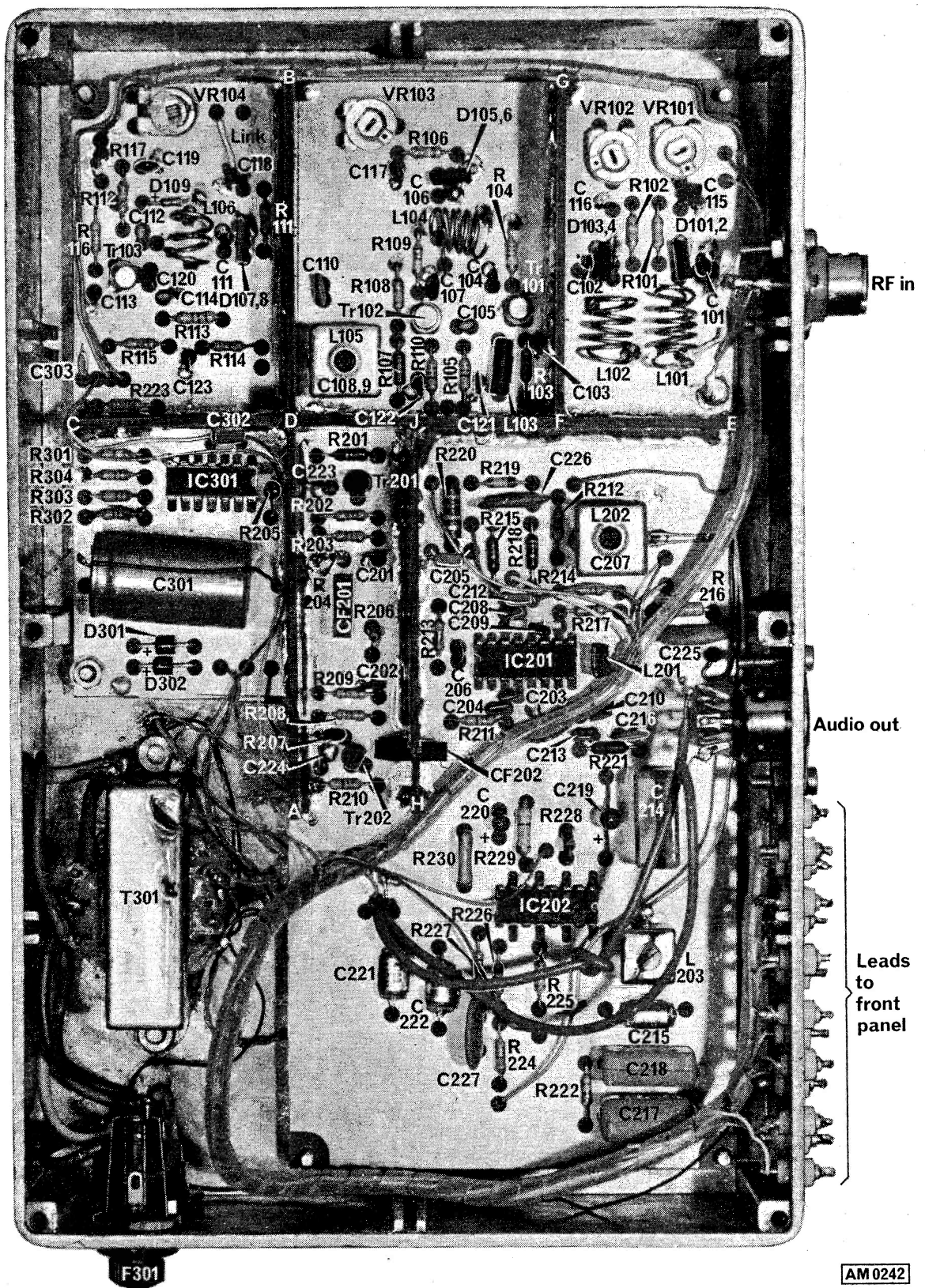


Fig. 6: Layout of components and Screens in the receiver.

NOTE—To correspond with the layout shown here, two alterations should be made to the circuit diagram, Fig. 2: (a) C216 should be connected between earth and the junction of R221/C214, not to pin 1 of IC202. (b) The top ends of R226 and R227 should be returned to the junction of R224/C227 and not direct to the +13V line.

AM 0242

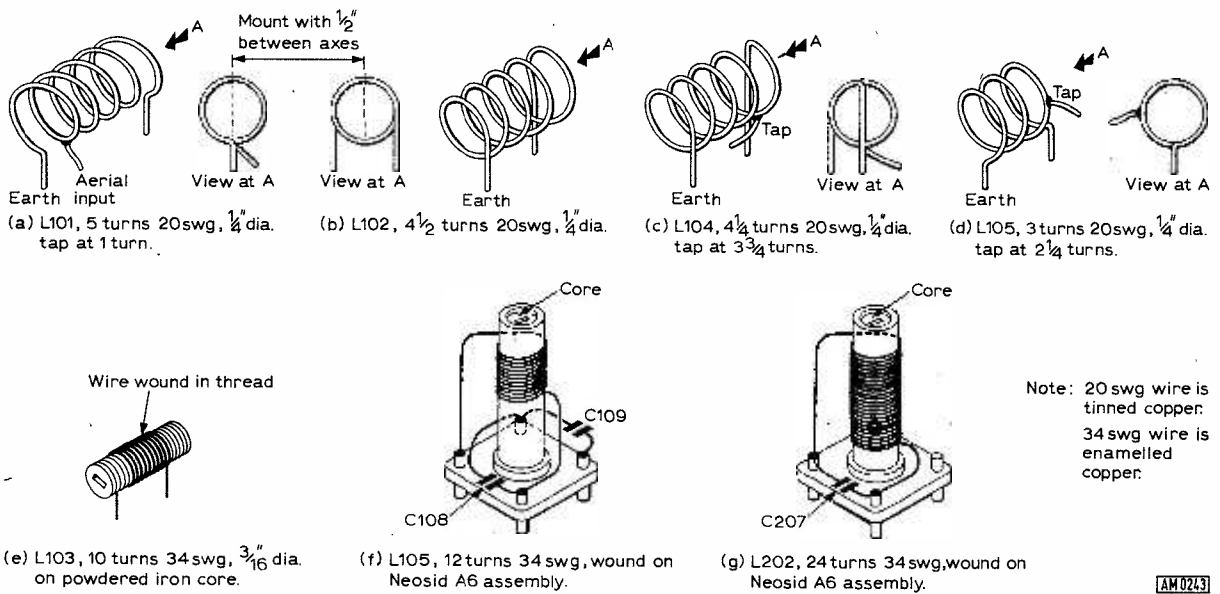


Fig. 7: Winding information for all coils.

## POWER SUPPLY

There are few components in the power supply section, but care must be taken to ensure that diodes D301, D302 and capacitor C301 are correctly connected. Mount and solder the power supply components shown on Fig. 6, but omit IC301 and R205 at this stage.

Now connect up the mains lead, fuseholder and transformer as indicated in the circuit diagram. Connect to the other earthed solder tag the mains earth, the transformer centre tap, the transformer screen and the pad marked 'E' on the underside of the board. The earth return for the rest of the circuit is via the board mounting bolt in the power supply section. For testing the board out of the box, a temporary earth link can be provided by a wire soldered to the ground plane and connected to a transformer earth tag. It is important that this earthing arrangement is adhered to as other arrangements may result in the appearance of 50Hz or 100Hz hum at the outputs of the tuner.

## TESTING

As an initial test connect a voltmeter across C301 and switch on. The meter reading should rise immediately to about +18V. If not, switch off and check the wiring and the polarity of D301, D302 and C301.

When this test is satisfactory switch off and insert IC301, ensuring that it is the correct way round. Solder the pins to the pads on the underside of the board using as little heat as possible. Pin 7 should also be soldered to the ground plane to complete the power supply earth return. Now connect the voltmeter to the junction of R302, R303 and switch on; the voltage will rise to about 13V. This completes the construction of the power supply.

Assembly of the remainder of the pcb is easier if the earth and AC leads from T301 are now disconnected, allowing the board to be completely removed from the box.

## FRONT END AND OSCILLATOR

Winding data for all of the coils is given in Fig. 7 and it is worth spending a little time in ensuring that they are made correctly so that the receiver is easy to align when construction is complete.

Mount the components in the positions indicated in Fig. 6 taking care that the coils are correctly positioned and that the active devices are soldered in correctly. All components should be positioned as close to the board as possible except for Tr103, which must be at least 1/4in from the ground plane, and the coils which should stand about 0.1 in clear of the board and all other components. Wires which are connected to earth should be soldered both above and below the board in the RF sections.

## IF SECTION

Earthed leads in this section are also soldered to both sides of the board, except for the centre pins of the ceramic filters which are only soldered to the underside. Treat the ceramic filters as you would active devices and apply as little heat as possible to their leads whilst soldering. Omit R205, located in the power supply section.

When the IF section is complete solder in the final screening partition HJ as described earlier.

## DEMODULATOR AND DECODER


It is most important that the integrated circuits in this section are inserted the right way round or an expensive failure may result when power is first applied. Fig. 6 shows the correct orientation. When soldering the pins of the integrated circuits, treat them as you would transistors and apply as little heat as possible whilst ensuring that the solder wets both of the surfaces to be joined.

Omit the power supply resistors R212, R224 so that initial testing may be carried out systematically from the front end. Finally make a connection

—continued on page 641



# BI-PRE-PAK Audio Bargains

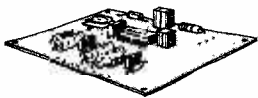


**STEREO  
DECODER**  
**£4.50**

incl. P. & P.

Ready-built unit, ready for connection to the IF stages of existing FM Radio or Tuner. The very latest 2nd Generation coil less integrated circuit design, operating on this phase locked loop system, offering even better stereo separation. Only owing to our bulk buying capacity are we able to offer this at the old price. LED stereo indicator lights available. **RED at 25p. GREEN at 40p.**

**3 W.R.M.S. I.C. AMP**  
**only £1.50**


incl. P. & P.  
Order Code I.C.A.1

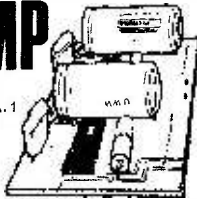

on P.C. Board with all components  
or 2 on one board for £2.60  
Order Code I.C.A.1/S

These amps. are supplied with a free booklet  
on connecting up, specifications and easy to  
build projects using the I.C.A.1

## 5W & 10W AMPS

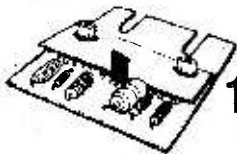

**5W ONLY £1.80**  
**10W ONLY £2.26**

incl. P. & P.

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2 1/4" x 1 1/4". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. **Cheapest in the UK. Built and tested.**

## Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit .15 edge connector.

**Stereo Pre-Amp 1 (Pre 1).** This unit is for use with low gain crystal or ceramic pick-up cartridges. **£1.10**

**Stereo Pre-Amp 2 (Pre 2).** This unit is for use with magnetic pick-up cartridges. **£1.55**

**Stereo Tone Control (STC).** This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. **£1.10**

**Instruction leaflet supplied with all units. Post and packing included in prices. VAT at current rate.**

I enclose £..... for..... Decoders/.....  
3W Amps/..... 5W Amps/..... 10W Amps/.....  
Stereo Pre-Amps 1..... Stereo Pre-Amps 2.....  
Stereo Tone Controls.....  
(Please insert quantities and delete those not applicable)  
Name.....  
Address.....

**BI-PRE-PAK** Dept. D, 222/224 West Road,  
Westcliffe-on-Sea, Essex SS0 9DF  
Telephone: Southend (0702) 46344  
Co. Regn. No. 820919

# We don't miss anything out, so you won't miss out.

Our 1214 Series stereo equipment comes to you in kit form. And, as you would expect, coming from Heathkit, they are absolutely complete kits. With nothing left out.

So you'll have all you need to build our superb AR-1214 stereo receiver. Or, if you'd prefer, a separate amplifier and tuner (the AA-1214 and AJ-1214).

The easy to understand instruction manual you'll get makes assembly beautifully straightforward.

And very enjoyable.



And the high performance of the 1214 Series means you won't miss out on listening pleasure in any way either.

From the stereo receiver, or separate amplifier, you'll get 15 watts r.m.s. a channel, with reproduction so good it makes many ready-made systems really sit up and listen.

For full details of the 1214 Series, the rest of our audio range, including speakers, and our many other kits, just post the coupon now for your free Heathkit catalogue.

Or call in at the London Heathkit Centre,  
233 Tottenham Court Road.

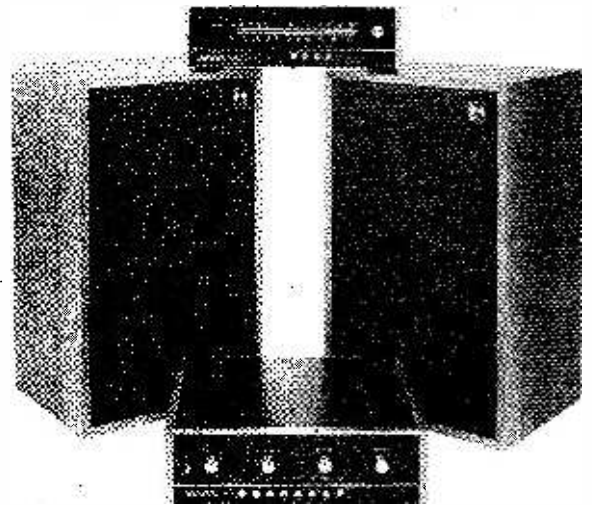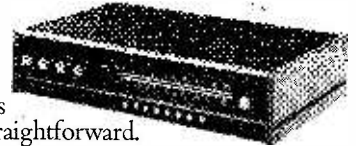Heath (Gloucester) Ltd., Dept. PW-114, Bristol Road,  
Gloucester GL2 6EE. Tel: (0452) 29451.



To: Heath (Gloucester) Limited, Dept. PW-114, Gloucester, GL2 6EE.  
Please send me my free Heathkit catalogue.

**HEATHKIT**



Name.....

Address.....

Postcode.....

HEATH

Schlumberger

Remember easy terms are available with the Heathkit Monthly Budget Plan.

### RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are:  
 7 track record playback heads 50p each.  
 4 track record playback heads 75p each.  
 Erase heads are also available separately  
 1 track 35p—4 track 55p.

### NEED A SPECIAL SWITCH

Double Lead Contact. Very slight pressure closes both contacts. 8p each, 10 for 75p Plastic pushrod suitable for operating. 6p each, 10 for 55p.

### 1 R.P.M. MOTOR & GEAR BOX

Made by the famous Chamberlain & Hookham Ltd. These could be made to drive clock or similar. Really robust reliable unit.  
 Price £1.10 each.

### AUTO-ELECTRICAL CAR AERIAL

With dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready-wired dashboard switch. £9.35 plus 25p post and insurance.

### MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Contains: mains transformer, smoothing and load resistors, condensers and instructions. Real snip at only £1.20.

### MINIATURE WAFER SWITCHES

1 pole, 2 way—4 pole, 2 way—3 pole, 4 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 25p each.

### MULTI-SPEED MOTOR.

Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000, 12,000 and 15,000 r.p.m. Size is 1 1/2 in. diameter and approximately 1 1/2 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price £1.00 plus 25p postage and insurance.

### SLIDE SWITCHES

Slide Switch, 2-pole changeover panel mounting by two 6BA screws. Size approx. 1in x 1in rated 250V lamp. 8p each, 10 for 75p. Ditto as above but for printed circuit 6p each 10 for 65p. Sub Miniature Slide Switch, DPDT 19mm (1in approx.) between fixing centres. 20p each 10 for £1.80. SP Change over spring return 250V 1 amp. 11p.

### ISA ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you wake a switch on lights to ward off intruders—have a warm house to come home to.

All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory logger. A beautiful unit. Price £2.15 + 20p p. & p. or with glass front, chrome bezel, 85p extra.

### BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits. 87p each.

### 12 VOLT 1 1/2 AMP. POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price £2.20 plus 20p post & packing. Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £6.33 plus 65p post.

### RESETTABLE FUSE


How long does it take you to renew a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only £1.10 each or £12 per dozen, specify 5, 10 or 15 amp—simply fit in place of switch.

### MIGHTY MIDGET

Probably the finest possible radio, as described in Practical Wireless January 1973. All electronic parts £2.20 post paid.
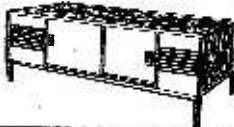
### STEREO RADIO CABINET

Long, Low and Modern. Teak veneered with sliding front and tapered legs. Speaker spaces each end. Size approx. 4ft. 2in x 15in x 15in. Probably cost over £20 to make. Our Price £8.10 each.



## THIS MONTH'S SNIPS

### AM/FM TUNER

Unit made by the American GEC company. 8 transistor, all-wired ready to work. Complete with tuner condenser, needs only scale and pointer. Tunes AM range 540 to 1620 KHz, FM range 88 to 108 MHz. Switches for on-off and AFC. Output for MXF or direct. Special snip price £25 plus 30p post. Three or more post free.

### 7 WATT STEREO AMPLIFIER

Again by the American GEC company. This has exceptionally good tone quality. Is complete with pre-amp and treble base, volume and balance controls. Also has mains smoothing circuit and rectifiers so requires only mains transformer. Output for 15 ohm speakers. Inputs for tuner, pick-up, mike, etc. Special snip price £6 plus 30p post. Three or more post free.

### DIGITAL DISPLAY UNIT 'DIGIVISOR'

A precision instrument consisting basically of a 12 volt lamp focused by a lens system to shine through a numbered scale onto a ground glass front screen, the number being selected by applying a different voltage of the coil. Overall size approx. 2 1/2 x 1 1/2 x 4 1/2". Price £3.50

### HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:—

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously

Suitable of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated. Size 3in. x 3in. x 2in. deep. Price £3.85 as illustrated but less case.



### TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters. Comprises motor, impeller, 2kW element allowing switching 1, 2kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £2.75. Don't miss this. Control Switch 44p. P. & P. 40p.



### MULLARD UNILEX STEREO SYSTEM

There is no doubt that it is a good system, we believe that for the money it is without comparison. We demonstrate gladly at our Tamworth Road depot. Prices of the individual items for this:—  
 1 Unilex Amplifier Ref. EP.9000 £1.80  
 1 Unilex Amplifier Ref. EP.9000 £1.80  
 1 Unilex Pre-Amp Ref. EP.9001 £1.98  
 1 Unilex Power Unit Ref. EP.9002 £2.58  
 1 Control panel kit with spun aluminium face and knobs £3.80  
 Or the complete outfit—£11.90 post paid.  
 Pair of 15 ohm speakers made by Goodmans are also available if required, price £2.30 the pair. No extra postage if ordered with the above, otherwise add 25p.



### SWITCH TRIGGER MATS

8 1/2in is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc.  
 24in x 18in £1.69  
 18in x 0in £1.21

### HORSTMANN "TIME AND SET" SWITCH

(A 20 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Two models 15 amp £1.98, 30 amp £2.58. P. & P. 25p each.

### SMOKE WILL KILL—GAS WILL KILL—FIRE WILL KILL

But, if you install SAGA (our smoke and gas alarm) your family will have the latest electronic protection against these killers. SAGA uses a fantastic electronic sensor which "smells" smoke and gas and sounds the alarm immediately. In a neat case measuring approx. 6" x 3 1/2" x 2 1/2". It has its own internal alarm, also a connector for additional bells. You just plug it in to the mains and hang it near the ceiling. SAGA uses so little electricity that it will hardly move the meter, leave it on always to give night and day protection. £6.99 plus 30p post.


### SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19.25.31.39 & 49 metre bands—kit contains chassis front panel and all the parts. £1.25—crystal earphone 35p.

**TERMS:—**  
 ADD 8% V.A.T.  
 Send postage where quoted—other items, post free if order for these items is £6.00, otherwise add 30p.
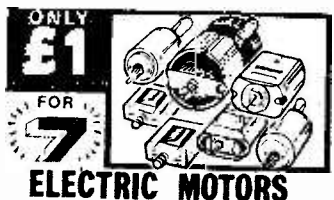
### CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by blange, air is blown into the equipment to be cooled, air out, mount it from centre using cable. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing fume smoke when soldering etc., etc. A real bargain at £2.95.



### ELECTRIC MOTORS

7 powerful battery motors as used in racing cars and power models. Output and types vary to make them suitable for hundreds of different projects—tools, toys, models, etc. All brand new reversible and for 10 to 12v. Bats., wiring diagrams included. Post and VAT 30p.  
**FREE** Details of how to make miniature power station.

### FERRITE RODS

For aerials, etc. The following types are in stock  
 Dia. 1/4", 4" long 15p, 5" long 15p. Dia. 3/8", 5" long 20p, 6" long 25p, 8" long 30p. Dia. 1/2", 4" long 20p, 5" long 25p, 6" long 30p, 8" long 40p.  
 Dia. 1", 6" long 35p; Ferrite Slab 3" long x 3/4" x 1/2"—20p.

### IMMERSION HEATERS BY REMPLOY

Standard fitting for domestic water tanks, made by the famous Remploy Company. Complete with sealing washers suitable for 200-240 volts A.C. Depth into tank 11in. 2kW or 3 kW £1.65 plus 20p each post and insurance.

### PC BOARD MARKER

Valve action fibre tipped marking pen filled with black ethyl resist—it's easy with this to make a perfect PC board, just draw straight on to the copper—allow 15 minutes to dry, then immerse in ferric chloride or other etchant on removal the circuit stands in high relief. 99p.

### TELESCOPIC AERIAL

For portable, car radio or transmitter. Chrome plated—six sections—extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 42p. KNUCKLED MODEL FOR P.M. 55p.

### TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless, August issue. £4.30 plus 20p post and insurance.

### MIDGET TWO GANGS

Tuning condenser as fitted to many Japanese and Hong Kong radios—probably 200p each section with 1/2" spindle with terminal-less trimmers. Price 35p. With trimmers 50p.

### NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XN.3 Price 99p each, 10 for £9.

### MAINS OPERATED SOLENOIDS

Model 2—small but powerful 1in. pull—approx size 1 1/2 x 1 1/2 in. 66p.  
 Model 4001—1in. pull. Model 21—2 x 1 1/2 in. 58p.  
 Model 471—1 1/2 in. pull. Size 3 x 2 1/2 x 2 1/2 in £1.98 plus 20p post and insurance.

### RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2.20, twin stethoscopy instead of earpiece 88p extra—post and ins. 20p.

## J. BULL (ELECTRICAL) LTD.

(Dept. PW), 102/3 Tamworth Road, CROYDON CRO IXX



# SWITCH ON SOMEBODY!

Geoffrey Smith

I'D better come clean at the start. I'm not a radio expert. I suppose I could say "Well, it's not my fault—I've got no sight and I'm a wheel-chair case with multiple sclerosis" but that would only be an excuse. In this country alone there are many severely disabled people who are capable and very knowledgeable radio amateurs.

Take Paddy, for instance, who's a Londoner. He's got a 45ft tower with a high gain 3-element rotary aerial, whatever all that is. He's also got a KW2000 transceiver, a KW1000 linear and a fistful of achievement certificates. He's totally blind, yet operationally he's as efficient as any sighted person. If this wasn't so, he wouldn't be a member of the First-Class Operators Club. This exclusive body limits its members to 500 top-notch morse code operators throughout the world. Paddy finds morse relaxing, after talking all day in his job as a bank telephonist.



... a friend who'll nudge me ...

Whilst operating he's also often using his tape recorder to make copies of a comprehensive course in radio. It's a voluntary job. He does it to help beginners in a national radio club for the disabled to study for their exams to get a transmitting licence. Actually, this is the course I've been floundering through but I find tape study tough going. What happens is that I come to a spot on the tape where I'm not sure what's meant, so I solve the problem by applying my own particular brand of logic. Usually I coast along through the next mile or so of tape before I gradually begin to realise that, way back, I came to some wrong conclusions, because

nothing is making sense any more. What I really need is a friend locally who'll nudge me back on to the right road.

I have to be honest, though, and admit that I have another difficulty. I'm a radio romantic. I marvel each time I'm reminded that there, dancing amongst the petunias in my garden, is music and speech from all over the world. Radiophonically speaking, the wonder of it clouds my thinking and makes the next process even less credible. That's the bit where these inaudible signals are channelled along a piece of copper wire, fed into a box, dissected and then rendered capable of being amplified to an ear-bursting loudness, in stereo if desired.



... music dancing in my garden ...

It's difficult to think of a better hobby than amateur radio for those who are on their own a good deal. At the flick of a switch a friend from the next street or the other side of the world can come into the room. Thanks to non-visual radio waves, the guest is certain not to feel awkward or embarrassed. I can't always say the same about people I meet in the High Street when I'm being pushed along in my wheel-chair in real live 3D colour.

## Bye Bye, Mr. Smith

When I'm around, people often become ill-at-ease and behave unnaturally. Conversations tend to go on above my head and the breeze wafts down to me such remarks as "Can he dress himself?" or "How does he pass the time?" Knowing I'm blind they're quite likely, on parting, to bend down, cup their hands round my ear and bellow "Bye Bye, Mr. Smith, pleased to see you looking so well!" If this action makes them feel particularly foolish then they may cap it by tapping me lightly on the head as we move away.

Well, of course, you don't get these problems with amateur radio, so I decided to look out for a short

wave receiver. A fellow I contacted said he had one to sell and would bring it round. In this transistor age I was expecting something small so I was very surprised to find it took two strong men all their time to huff and puff it into my den. After heaving it on to the top of a chest-of-drawers, one of them had to make a second trip to fetch the separate speaker unit. It was the owner who stayed behind and passed the time by telling me how sad he was to be losing his set. He'd gone and brought one of these new-fangled Japanese transceivers which slipped into one of his bureau drawers but the receiver part wasn't half as good as the one he was offering me, a pre-war Hallicrafters Super Skyrider SX-28. Its age, in fact, seemed to be its main selling feature. He assured me that the instruction manual, if not the set itself, was of considerable antique value!



... how sad to be losing his set ...

After the speaker had been hoisted into place on top of the set, and a temporary aerial erected, I was invited to move over and inspect the instrument. It certainly seemed impressive. It bristled with knobs, had a couple of capstan-like wheels and three little glass windows which, apparently, lit up like a doll's house. The main structure was built of metal, including the slotted lid which reminded me of an Edwardian pavement grating. The matching speaker was finished off in the same style with what felt like a metal footscraper bolted across its front! Still, it sounded good and the price seemed reasonable, so I bought it.

### Conversation piece

Right from the start it's been an interesting conversation piece. Strangers immediately find that their eyes are drawn to the corner where it stands. 'What's that?' they ask. When I explain that it's a Super Skyrider short wave radio made in Chicago when Al Capone was a lad, I never fail to get one of those drawn-in whistles. All in all it's been a good friend. When in good health its oscillations rose to the heights and plunged to the depths in grand style, vibrating everything vibratable in the room. Yes, it's certainly been a lively period-piece but sadly the breath's gone out of it now.

What happened was that a ham came from the town to these country parts for a few day's fresh air.

On learning that there was a short wave listener in the area, he looked me up for a chat. He also tuned my set and got it going well on all pistons. It made his day to hear his pals back home having a local chat across the town. After he'd gone I carried on listening to them until it was time to make lunch and tune in to "The World at One" on my domestic set. At two o'clock, though, my curiosity drew me back to the Hallicrafter. I wanted to know if they were still at it, but all I got when it warmed up on the frequency where I'd left them, was a spluttering, spitting noise. I mused to think that they were perhaps frying up a couple of transformers in oil for a light lunch. It was only as the smell, thick enough to taste, wafted across to me that I began to realise the seriousness of the situation. Hurriedly I snatched the mains plug out of its socket and then waited nervously by in my wheel-chair, hoping the set wouldn't burst into flames. Thankfully, it didn't. After a series of pings, twangs and cracks it gradually cooled off.

### Disposing of a Skyrider

My set is now something of a problem. There's no one in the house strong enough to move it but we don't want it to become a permanent fixture. My wife suggested that we should gradually disembowel it by taking bits out weekly and putting them in the dustbin until we're left with an empty shell. Personally I prefer to search for a couple of men who could take it down to the garden as it stands and bury it. It would be a more fitting end, I feel, for it to rest in a quiet corner where the radio waves could blow freely over it. What we really need, of course, is a little practical help and advice from a local radio enthusiast. Disabled people like to be independent but with the best will in the world there are some jobs they just can't do.



... the smell wafted across to me ...

This is why the radio club for the disabled, which I mentioned earlier, is always very pleased to welcome helpers who are fit and active enough to lend a hand occasionally. If you feel that you could give a little help at times to invalid radio enthusiasts who have struck a bad patch, write to Evelyn Boakes secretary of the Radio Amateur Invalid and Bedfast Club at RAIBC, Bristol Road, Cambridge, Glos. GL2 7BQ. It could be that someone disabled in your area is anxiously waiting now to have a chat with a knowledgeable, good-hearted chap like you! ■

## SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohm. Frequency response 12Hz-30kHz  $\pm$  3dB. Fully integrated pre-amplifier stage with separate Volume. Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Frequency approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high  $\times$  6" wide  $\times$  7 1/2" deep. AC 200/250V. **PRICE £11.80. P. & P. 50p.**

## DE LUXE STEREO AMPLIFIER



A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate hum.

Something with negligible hum. Valve line up: 2  $\times$  ECL86 Triode Pentodes, 1  $\times$  EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11"  $\times$  4". Overall height including valves 5". Ready built & tested to a high standard. **£10.22. P. & P. 50p.**

**POWER SUPPLY UNIT 200/240V.** A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 9v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finished metal case overall size 6"  $\times$  3 1/2"  $\times$  2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready to go. **PRICE £4.90 P. & P. 35p.**

**VYNAIR & REKINE SPEAKERS & CABINET FABRICS** apt. 54 in. wide. Our price £1.10 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

### HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide  $\times$  3in. deep  $\times$  6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. **£3.78 P. & P. 40p BARGAIN PRICE**

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in long  $\times$  3 1/2in wide  $\times$  3in. deep. **Price £2.31 P. & P. 40p.**

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. **£1.10. P. & P. 25p.** Pri. 200/240v. Sec. 12-0-12 at 1 amp. **£1.21. P. & P. 26p.** Pri. 200/240v. Sec. 10-0-10 at 2 amp. **£1.82. P. & P. 35p.**

**HI-GRADE COPPER LAMINATE BOARDS** 8"  $\times$  6". Five for 60p plus 30p P. & P.

**For personal callers only!** Limited number of stereo radio/gram chassis, covering LW/NW/FM bands. Mono radio and stereo gram. Overall size—approx. 16 1/2"  $\times$  W. 6 1/2"  $\times$  H. 8" Depth. 4 watts per channel output. only **£16.20.**

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.C.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz - 25kHz. Gain 26dB. Solid encapsulation size 1 1/2"  $\times$  1 1/2"  $\times$  1 1/2". Brand new complete with instructions. Price 95p. P. & P. 15p.

**HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES** A manual for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. **ONLY 40p. Post 5p.**

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents, 80p; Transistor Equivalents, 80p; Transistor Characteristics, £1.15; **POST FREE** All three together, **£2.60**

### NEW ISSUE

Thyratron, Triac, Diac etc. encyclopedias 95p. Post Free 8 pole 3 way 2 bank low loss Vaxley type switches 1 1/2" sections. Standard spindle, 2 switches 84p + 10p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday

Closed Wednesday.

A few minutes from South Wimbledon Tube Station.

# HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

## HARVERSON MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy stereo radio at this fabulous low price

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to "lock-on" station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12" wide  $\times$  8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). **Price £21.80 Post and Packing 50p.**

### STEREO-DECODER

Size 12"  $\times$  8"  $\times$  1 1/2" ready built. Pre-fitted and tested. Sens. 20-560 mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. **£5.00 plus 10p. P. & P.** Stereo beacon light if required **£4.00 extra.**



### SPECIAL BARGAIN OFFER!

Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. **Brand new. ONLY £7.98 + p. & P. 60p.**

### PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2020TC, 2500, 3000, 2500, 5100, SPS II and III, SL505B, A760 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12"  $\times$  14 1/2"  $\times$  3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). **NOW ONLY £4.78. P. & P. 70p.**

**LATEST ACOS GP/15C** mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. **£1.46. P. & P. 15p.**

**SONOTONE STAIC COMPATIBLE STEREO CARTRIDGE** T/O stylus Diamond Stereo LP and Sapphire 78. **ONLY £2.27. P. & P. 10p.** Also available fitted with twin Diamond T/O stylus for Stereo LP £2.78. P. & P. 15p.

**LATEST T/O STEREO / COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. **£1.60 P. & P. 15p.** **LATEST T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. **Only £1.47. P. & P. 15p.**

### QUALITY RECORD PLAYER AMPLIFIER MK. II

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC85, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide  $\times$  3in. deep  $\times$  6in. high. Ready built and tested. **PRICE £4.91. P. & P. 50p.** **ALSO AVAILABLE** mounted on board with output transformer and speaker. **PRICE £6.20. P. & P. 60p.**

### HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16" high  $\times$  10 1/2" wide  $\times$  6" deep. Fitted with E.M.I. Ceramic Magnet 1 1/2"  $\times$  3" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

**OUR PRICE £9.10** Carr. 90p  
Cabinet Available Separately **£4.88**, Carr. 90p  
Also available in 8 ohms with EMI 1 1/2"  $\times$  3" bass speaker with parasitic tweeter **£7.60**, Carr. 90p.

### LOUDSPEAKER BARGAINS

6in. 3 ohm **£1.25**, P. & P. 15p. 7  $\times$  4in. 3 ohm **£1.40**, P. & P. 20p. 10  $\times$  6in. 3 or 15 ohm **£2.10**, P. & P. 30p. E.M.I. 8  $\times$  6in. 3 ohm with high flux magnet **£1.70**, P. & P. 20p. E.M.I. 1 1/2"  $\times$  3in. with high flux ceramic magnet with parasitic tweeter 3 or 8 ohm **£3.80**, P. & P. 30p. E.M.I. 1 1/2"  $\times$  3in. 3 or 15 ohm with two inbuilt tweeters and crossover network **£4.85**, P. & P. 30p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. **£1.25 + 20p. p. & p.**

**BRAND NEW** Bakers Loudspeakers at substantial discounts. 12in. 15w. H/D Speakers, 3 or 8 or 15 ohms. State which. Current production by well-known British maker. Now with HiFlux ceramic ferrobar magnet assembly. Guitar models: 25w **£7.75**, 35w **£8.50**, P. & P. 45p.

12in. "RA" TWIN CONE LOUSPEAKER. 10 watts peak handling, 3 or 8 or 15 ohm (state which) **£2.70**, P. & P. 35p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2"  $\times$  14 1/2"  $\times$  1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. **Only £6.43 each.** P. & P. 34p.

## HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise, level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response  $\pm$  3dB 12-30,000 Hz Sensitivity: better than 60mV into 1M $\Omega$ . Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to  $\pm$  16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12"  $\times$  8"  $\times$  2 1/2".

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

**AMPLIFIER KIT** . . . . . **£11.94 P. & P. 30p** (Magnetic input components 33p extra)

**POWER PACK KIT** . . . . . **£3.46 P. & P. 40p**  
**CABINET** . . . . . **£2.46 P. & P. 40p**

(Post Free if all units purchased at same time)

Full after sales service

Also available ready built and tested **£24.60**. Post Free.

*Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc. and will then provide mixing and fading facilities for medium powered Hi-Fi Discogogue use, etc.*



### 3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2"  $\times$  4 1/2"  $\times$  4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£5.90. P. & P. 45p.**

**ESK '4004' AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc **£4.92 P. & P. 45p.**

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC85, EBF8 and EZ80 rectifier. Simple instruction booklet 15p + SAE (Free with parts!) All parts sold separately. **ONLY £8.60 P. & P. 60p.** Also available ready built and tested **£12.75 P. & P. 70p.**



### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-16,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. **PRICE £3.24. P. & P. 25p.**

**PRICES INCLUDE VAT at 8%**

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.



# CHROMASONIC electronics

Dept. 1  
56, Fortis Green Road, London, N10 3HN.  
telephone: 01-883 3705

**electronics** *Nuts, Bolts etc.* **electronics** *Cases* **CHROMASONIC electronics** *Loadspeakers*

**CHROMASONIC electronics** *Tuners* **CHROMASONIC electronics** *Boxes*

**CHROMASONIC electronics** *MC1310* **CHROMASONIC electronics** *Transformers*

**electronics** *MC1312* **Phase-Locked F.M. Stereo D** **CHROMASONIC electronics** *Inductors*

**CHROMASONIC electronics** *Veroboard* **CHROMASONIC electronics** *2N414*

**CHROMASONIC electronics** *An I.C. For The Constructor*


**24 HOUR TURNROUND NOW IN OPERATION**  
**ORDERS RECEIVED BY 3.0 p.m. DESPATCHED**  
**SAME DAY.**  
**CALLERS WELCOME**

## SPECIAL OPTO OFFERS

**NEW**

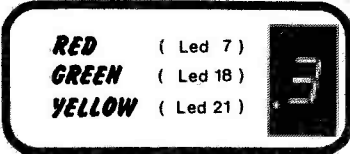**LOW COST**

All Common Anode, Left Hand Decimal Point  
Character Height 0.3"



- RED** ( Led 7 )
- GREEN** ( Led 18 )
- YELLOW** ( Led 21 )

**4 for £5.99**  
**5 for £7.45**  
**6 for £8.93**

### 0.125" diameter — T1L209 size

- 10 RED
- 10 GREEN
- 10 YELLOW
- 10 WHITE



Our Usual price	Special Pack Price
<del>£2.40</del>	£1.99
<del>£4.10</del>	£3.49
<del>£2.90</del>	£1.99
<del>£3.50</del>	£3.39

### 0.2" diameter — MLED650 size

- 10 RED
- 10 GREEN
- 10 YELLOW

Free snap-on plastic retainer with each order

<del>£2.80</del>	£2.39
<del>£4.50</del>	£3.99
<del>£3.90</del>	£5.99

### 0.175" diameter — T092 size

- 10 RED



<del>£1.70</del>	£1.39
------------------	-------

## VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH.  
 VAT INVOICES ON REQUEST.  
 P.&P. On U.K. Orders 15p., - Overseas Orders at Cost

THE POPULAR NEW ELECTRONIC GAME

# TELE- TENNIS

PLAYED ON THE TELEVISION SCREEN

PART 5

M. J. HUGHES MA

## Testing Board D

Build the circuit for Board D and install it on the sub frame with all the necessary interconnections (including those to the front panel) EXCEPT for the lead from the blanked ball output to Board E. Instead connect a temporary link between the last diode input of Board E and the BALL signal input to Board D. This will by-pass the ball-blanking and allow you to see the ball at all times to check that the ramps are working.

Set VR11 and VR12 to maximum resistance and switch on. You should immediately see the ball moving about the screen, but do not worry if it is stationary near one of the corners of the tennis court. You are bound to have to carry out a bit of lining up and you must follow the procedure to be described very carefully. It is not difficult but needs a little patience.

## Final Adjustments

Press the Ballboy button and the ball should jump to an approximately central position on the screen. Use VR3 and VR4 of Board A to get the ball as near to the centre as possible and then take your finger off the button. The ball will move obliquely across the screen and should rebound as it hits each base line.

It may be that the ball rises to the top left hand corner and stops before it reaches a base line; this means that the voltage control is not having sufficient effect on the ball's position. In this event use VR3 to move the ball from its stationary position until it just touches the top base. The ball will immediately start to move down the screen but will not move sideways. Now adjust VR4 so that the ball is in contact with the left base. All being well the ball should now move freely across the screen rebounding from all the bases.

If there are problems in getting the ball to reach both extremes of its vertical and horizontal travel you might have to bring the base lines in a little. Once this has been done check that the Ballboy freezes the ball's movement somewhere within the "court".

Now remove the temporary link from board E and connect the Blanked Ball output of Board D permanently to the last diode input to the mixer stage. Switch on and press Ballboy—almost certainly the ball will not be visible because it will be blanked off. Press the Service button on one side and hold it down for a few seconds. The ball should appear from that end's base after a brief delay. As soon as it appears try playing a brief game and check that the ball disappears when it hits an end base. Finally test the other end's service and then adjust the ball's speed with VR11 and VR12 to suit the standard of your play. When doing setting up adjustments it is always advisable to have the ball moving at its lowest speed.

## Installation

Now that the game is complete it only remains to finish off the installation within the case, using self tapping screws to secure the subframe. Make sure that the mains input lead is suitably clamped and that the earth wire goes to the case. Use two short lengths of 16 swg enamelled copper wire twisted together once or twice over three-quarters of an inch to provide the uhf output coupling capacitor. Using the centre core only of coaxial plug, connect one end of this capacitive lead to the output of the modulator. The other end goes direct to the output

—continued on page 641

## ★ components list

### FRONT PANEL & CASE

#### Potentiometers

VR13, VR14 5k $\Omega$  linear sliders

#### Switches (all push-button type)

S1, S2, S3 DP changeover, non-locking

S4 DP Push-ON/Push-OFF, 250 VAC rating

#### Miscellaneous

SK1 75 $\Omega$  panel mounting coax socket

SK2 50 $\Omega$  panel mounting coax socket (for video output if required)

Case including front panel; hinge for panel; mains-cable grommet and clamp; earthing tags; plastic feet.



# BRITAIN'S FASTEST SERVICE!

A SELECTION FROM OUR COMPREHENSIVE CATALOGUE



## ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	6p	BCY72	14p	D10 (NTGD10)	OC83	23p	2N1307	30p	7447	£1.50		
AC107	50p	BD124	75p		OC84	25p	2N1308	34p	7450	24p		
AC126	20p	BD131	40p	HP5082	29p	OC139	25p	2N1309	34p	7451	24p	
AC127	25p	BD132	40p	HS822-33	46p	OC170	25p	2N1559(CR1/		7453	24p	
AC128	24p	BD131/132	80p	HT841-33	£2.24	OC171	30p	401C	71p	7454	24p	
AC128/AC176	BDY20	44p	BF115	53p	HT861-33	£2.90	OC771M	42p	2N1711	15p	7460	24p
AC151	20p	BF163	35p	IR2160	95p	ORP60	50p	2N1893	54p	7472	54p	
AC152	25p	BF167	25p	IR220	46p	ORP61	50p	2N2218	33p	7473	54p	
AC153	26p	BF173	29p	IR284	£2.24	ORP69	50p	2N2218A	44p	7474	55p	
AC176	20p	BF177	25p	JA424	£2.08	PM7A2	£1.85	2N2219	38p	7475	54p	
AC153/176K	52p	BF178	31p	MC1303L	£1.75	PM7A6	£2.50	2N2219A	53p	7476	54p	
AC187K	17p	BF180	35p	MC1305P	£2.80	PN170	10p	2N2368	17p	7480	80p	
AC188K	23p	BF194	55p	MC1307P	£1.65	PN171	10p	2N2369	17p	7482	£1.04	
AC187/188K	40p	BF195	15p	MC1310P	£2.80	PN107	8p	2N2369A	17p	7483	£1.58	
ACY17	27p	BF196	15p	MC1330P	£2.00	PN108	8p	2N2484	42p	7486	39p	
ACY18	20p	BF200	35p	MC1352P	£2.00	PN109	8p	2N2646	45p	7490	34p	
ACY19	20p	BF254	14p	MC1466L	£4.20	PN3619 (2N3819)	20p	2N2904	44p	7491A	£1.54	
ACY20	20p	BF255	15p	MC1466L	£2.58		20p	2N2904A	49p	7492	£1.02	
ACY21	19p	BFX13	25p	MC4002P	£2.58	SL103A	50p	2N2905	65p	7493	90p	
ACY22	10p	BFX29	32p	MC4044P	£2.20	SL403A	50p	2N2905A	75p	7494	£1.36	
AD140	60p	BFX84	25p	MFC4000B	65p	(Rectifier)	60p	2N2924	18p	7495	96p	
AD149	60p	BFX85	34p	MFC6030	£1.63	SL803A	30p	2N2925	20p	7496	£1.78	
AD161	44p	BFX86	25p	MFC6040	£1.15	ST2	20p	2N2926	10p	74100	£1.97	
AD162	44p	BFX87	30p	MFC8010	£1.38	TAA263	£1.12	2N3053	24p	74107	62p	
AD161/162	85p	BFX88	24p	MFC8040	£1.24	TAA283	97p	2N3054	65p	74121	51p	
AF106	32p	BFY50	22p	MFC9020	£2.12	TAA310	£1.25	2N3055	65p	74141	£1.20	
AF114	27p	BFY51	19p	MJE571	12p	TAA320	75p	2N3228	£1.10	74150	£1.02	
AF115	27p	BFY52	20p	MJE520	65p	TAA861	45p	2N3391A	29p	74151	£1.32	
AF116	25p	BFY53	17p	MJE521	62p	TAD100	£1.97	2N3525	£1.04	74153	£1.62	
AF117	25p	BFY90	£1.20	MJE2955	£1.06	TAD110	£1.97	2N3702	14p	74154	£2.40	
AF118	25p	BFY99	£1.40	MJE3055	97p	TAA810S	£1.68	2N3703	12p	74155	£1.86	
AF124	25p	BFY86	£1.50	MJ480	77p	TIL112	£2.00	2N3704	12p	74156	£1.86	
AF125	24p	BR100	20p	MJ481	£1.25	TIL200	30p	2N3705	12p	74190	£2.16	
AF126	24p	BR193	45p	MJ491	£1.35	TP13A	60p	2N3706	12p	74191	£2.16	
AF139	47p	BXS19	16p	MJ802	£4.12	TP23A	70p	2N3707	12p	74192	£2.09	
AF186	50p	BXS20	16p	MJ802/MJ4502	TP41A	85p	2N3708	12p	74193	£2.09		
AF239	50p	BXS21	25p	MJ805	£3.56	T42A	£1.00	2N3709	12p	74196	£1.80	
AF279	59p	BSY27	25p	MJ900	£1.80	TIS43	30p	2N3710	12p	74197	£1.80	
AS526	25p	BSY29	25p	MJ1000	£1.50	TR1	20p	2N3711	12p	40250	68p	
AS527	30p	BSY95A	12p	MJ4502	£4.44	VA1039	15p	2N3773	£2.50	40309	40p	
AS528	22p	BT106	12p	MLM309K	£1.90	VA1040	15p	2N3819	28p	40310	60p	
AS529	30p	BTY79/400R	MPF102	37p	VA1066	15p	2N3820	60p	40311	42p		
EA108	15p	BY100	£1.80	MPF103 (2N5457)	VA1077	15p	2N3823E	20p	40312	62p		
BB103	30p	BY101	20p	MPF104	49p	W005	25p	2N3826	34p	40320	42p	
BB104	34p	BY127	22p	MPF104 (2N5456)	W01	26p	2N3866	£1.10	40360	55p		
BB105	28p	BZY88CV3	49p	W02	25p	2N3904	28p	2N3904	28p	40361	45p	
BC107	16p	to	MPF105 (2N5459)	W04	27p	2N3906	28p	2N4058	25p	40406	45p	
BC107/BC177	36p	BZX63CV0	10p	NE555V	78p	W08	41p	2N4060	13p	40407	40p	
BC108	16p	BZX61 C7V5	NE555V	78p	W08	41p	2N4060	13p	40408	54p		
BC108/BC178	36p	BZX61 C3V0	28p	NKT1033	66p	ZT107	12p	2N4061	13p	40409	62p	
BC109	32p	BZY93CV1	70p	NKT212	25p	ZT108	11p	2N4062	13p	40409	62p	
BC109/BC179	36p	BZY93CV12	70p	NKT213	25p	ZT300	13p	2N4441	70p	40410	62p	
BC109/BC179	36p	BZY93CV15	70p	NKT216	46p	ZT302	18p	2N4444	£2.20	40430	£1.13	
BC109C	36p	BZY93C18V	70p	NKT217	50p	ZT303	15p	2N4871	44p	40468A	44p	
BC117	15p	CA3004	£2.50	NKT218	50p	ZT304	23p	2N4990	66p	40511	£1.92	
BC140	30p	CA3011	£1.35	NKT223	27p	ZT314	11p	2N4991	48p	40575	£1.54	
BC147	12p	CA3013	£1.17	NKT274	18p	ZT330	18p	2N5457 (MPF103)	40p	40600	£1.46	
BC148	11p	CA3014	£1.37	NKT275	20p	ZT X501	14p	2N5458 (MPF104)	40p	40602	70p	
BC149	12p	CA3018	72p	NKT279A	12p	ZT X502	18p	49p	40603	70p		
BC157	15p	CA3020	£1.30	NKT351	75p	ZT X503	17p	2N5459 (MPF105)	40p	40669	£1.00	
BC158	15p	CA3028A	79p	NKT401	78p	IN914	45p	49p	40673	52p		
BC159	15p	CA3035	£1.37	NKT402	83p	IN9754	4p	2N5756	£1.20	40739	£1.50	
BC147/157	23p	CA3043	£1.57	NKT403	71p	IN4001	4p	2N6027 (D13T1)	4p	45p		
BC148/158	25p	CA3044	£1.28	NKT404	66p	IN4002	4p					
BC149/159	11p	CA3046	70p	NKT405	87p	IN4003	5p	3N84	£1.30			
BC167	10p	CA3048	£2.11	NKT406	69p	IN4004	7p	3N129	73p			
BC168	11p	CA3052	£1.62	NMC409	£1.00	IN4005	6p	3N140	92p			
BC169C	12p	CA3053	47p	NMC469	66p	IN4006	8p	3N152	92p			
BC177	20p	CA3065	£1.28	NMC505	£3.00	IN4007	9p	7417/O5	45p			
BC178	16p	CA3088E	£1.24	NTGD10	40p	IN4148	4p	7417/8D1L	34p			
BC179	20p	CA3089E	£1.94	OA10(NTGD10)	IN5400	14p	723/O5	£1.02				
BC182	14p	CA3090D	£4.23		MS404	18p	723/14D1L	£1.02				
BC182L	14p	CA3123E	£1.80	OA47	8p	MS408	25p	747/14D1L	46p			
BC183	13p	CD4000AE	55p	OA79	8p	IS44	4p	748/14D1L	39p			
BC183L	14p	CD4001AE	55p	OA90	6p	IS920	7p	3015F	£1.40			
BC184	17p	CD4007AE	55p	OA91	5p	IS940	6p	3015G	£2.00			
BC184L	16p	CD4009AE	£1.16	OA95	5p	2N404	23p	7400	24p			
BC212	16p	CD4011AE	55p	OA200	6p	2N696	15p	7401	24p			
BC212L	16p	CD4012AE	55p	OA202	7p	2N697	17p	7042	24p			
BC238	10p	CD4013AE	£1.11	OC25	45p	2N698	30p	7403	24p			
BC238/308	20p	CD4015AE	£2.92	OC28	78p	2N706	10p	7404	30p			
BC257	11p	CD4017AE	£2.92	OC29	79p	2N706A	12p	7405	30p			
BC258	10p	CD4018AE	£2.92	OC35	66p	2N708	16p	7408	30p			
BC259	12p	CD4020AE	£3.25	OC36	69p	2N911	50p	7409	30p			
BC307	10p	CD4021AE	£2.00	OC41	40p	2N914	20p	7410	30p			
BC308	10p	CD4027AE	£1.73	OC42	40p	2N918	42p	7413	35p			
BCY30	25p	CD4029AE	£4.12	OC44	20p	2N929	25p	7420	24p			
BCY31	48p	CD4049AE	99p	OC45	20p	2N930	28p	7425	26p			
BCY32	50p	CR1/051C	54p	OC71	20p	2N1131	24p	7430	24p			
BCY33	29p	CR1/401C	71p	OC72	20p	2N132	24p	7440	29p			
BCY34	25p	CRS3/05AF	OC75	OC75	25p	2N132	25p	7442	£1.98			
BCY38	30p	CRS3/40AF	£1.08	OC76	25p	2N1303	17p	7443	£1.74			
BCY58	18p	CRS3/40AF	OC77	OC77	40p	2N1304	24p	7444	£1.74			
BCY70	15p	CZ6	£1.53	OC81	20p	2N1305	24p	7445	£2.47			
BCY71	28p	CZ6	17p	OC81D	20p	2N1306	30p	7446	£1.74			

## TEST METER

This compact, robust Meter contains a transistorized amplifier enabling a very high input impedance to be achieved (at least 200K ohms per volt).  
**DC & AC Ranges** £27.50 each  
 Further details on request — ask for leaflet 06-351.

## LOGIC CHECKER

The fast effective way for checking Digital DIL IC's. Checks DIL gates, flip-flops, counters shift registers, decoders, etc., etc.  
 Clip on logic plates clarify circuit state.  
 No interference with circuit, input impedance responds to one TTL load.  
 Instant display by LED's.  
 Power supply automatically selected.  
 Full instructions supplied with each device at £25.85 each.

## INTEGRATED CIRCUIT TEST CLIP

Indispensable aid to the engineer working with DIL IC's. For use with both 14 & 16 lead packages. Clips on to device under test. Can be used as a removal tool. Accidental shorting of IC leads eliminated & Capacitance effects at HF are negligible.  
 £1.95 each

## INTEGRATED CIRCUIT PINS

The lowest priced IC mounting available. Pin Sockets come in a reel, just drill your board at required centres, drop in pins and solder, break off frame holders—your DIL mounting is complete!  
**Pin Sockets** 1,000 pieces £7.00  
**Pin Sockets** 100 pieces £1.00

## NE555V TIMER I.C.

As used in magazine articles including July Practical Wireless.  
**DATA AND CIRCUITS** 78p

## CA3123E Superhet System with RF Amp. IF Amp. Mixer, OSC. I.C. g.c. Detector and Voltage Regulator. Ideal for car radio applications.

**APPLICATION SHEET & DATA** 15p

## SEVEN WATT AUDIO AMP. I.C.

**TBA810S** £1.68  
 Featuring thermal protection. Ideal for car radio applications.  
**APPLICATION SHEET & DATA** 15p

## PACKAGED CIRCUITS

The complete range of Newmarket modules currently being featured in magazine articles. See catalogue for details.

## ANTEX SOLDERING EQUIPMENT

X25/240v 25w Iron. £2.15 SK2/240v 15w kit £3.40  
 MLX 12v 25w kit, essential for car tool kit £2.70  
 X50T 240v 50w temperature controlled £7.95

**ARROW** SPECIALISE IN EDUCATIONAL AND GOVERNMENT ORDERS  
 —See catalogue for further details.

**ARROW** SERVICE PLUS  
 10% DISCOUNT OVER £4. NO POSTAGE AND PACKING. TOP QUALITY PRODUCTS ALWAYS BY RETURN  
**COMPREHENSIVE CAT.** →

**Important Notice** "All prices are exclusive of V.A.T. Please add 8% V.A.T. to the final total of your order after deducting any discount which may be due"  
 V.A.T. REG. 246062672

**ARROW ELECTRONICS LTD.**

# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



## Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O.

only **99p** P & P 45p each

## TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

only **25p** POST & PACKING 16p

## Tested and Guaranteed Paks



B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, 1" long, 1/4" dia. High Speed P.O. type	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short lead Transistors, NPN Silicon, Planar types	50p
H39	6	Integrated Circuits. 4 Gates BMC 962, 2 Flip Flops BMC 945	50p
H41	2	Sil Power transistors comp pair BD131/132	50p
H63	4	2N3055 type NPN Sil. power transistors. Below spec. devices	50p
H64	4	3819 N Channel FETs 2N3819 in plastic case	50p



## Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	50p
B66	150	Germanium Diodes Min. glass type	50p
B83	200	Transistors, manufacturers rejects, AF, RF, Sil. and Germs.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p
H67	10	3819N Channel FETs plastic case type	50p

## Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1.00p** each

## Electronic Transistor Ignition £6.00

Complete kit p. & p. 11p

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

## Extension Telephones

Ideal for childrens toys **70p** each P. & P. 25p.

## New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available

Will align the colour guns on a colour T.V. receiver. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's tool box—and only measures 3" x 5 1/2" x 3".

Ready built unit only **£9.95** Complete kit **£7.95**

(includes p. & p. but no batteries)



## LM380 AUDIO IC

We have just received a large consignment of LM380 IC's. These are specially selected to a higher grade and are marked with the number SL60745

This fantastic little 3watt audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special price **£1.00** ea complete with data and projects book

## Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

## Our very popular 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can  
TYPE "B" PNP Silicon, plastic encapsulation  
TYPE "C" Germanium AF or RF  
TYPE "E" NPN Silicon plastic encapsulation  
TYPE "G" NPN silicon similar ZTX 300 range  
TYPE "H" PNP silicon similar ZTX 500 range

**8** RELAYS FOR VARIOUS TYPES P & P 27p **£1.00p**

## UHF TV Tuner Units

Brand new by a famous manufacturer

Data supplied **£2.50**

## Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.  
1-12 13-25 26-50  
40 Watt 20p 18p 16p  
90 Watt 24p 22p 20p

Range 2. VCE. Min. 40. HFE Min 40  
1-12 13-25 26-50  
40 Watt 30p 28p 26p  
90 Watt 35p 33p 30p  
Please state NPN or PNP on order.

HIGH SPEED MAGNETIC COUNTERS  
4 Digit (non-reset) 4 x 1 x 1 in ex G.P.O. 30p

## INTEGRATED CIRCUITS

We stock a large range of I.Cs at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

## METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 15p Wall Chart 18p

## LOW COST DUEL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile  
16 pin type at 17p each } type

## BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are void of V.A.T.

Send for lists of publications

## Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. only **50p**

Please send me the FREE Bi-Pre-Pak Catalogue I enclose large SAE with 5p stamp

NAME .....

ADDRESS .....

Please add current VAT rate

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 15p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

# BI-PRE-PAK LTD

Co Reg. No 820919

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND (0702) 46344.



A series of simple transistor projects, using not more than twenty components.

THERE are often occasions when it is desirable to control a circuit, or a piece of machinery, with push buttons. The classic case is the two button system for starting and stopping a lathe; when the green button is pressed the lathe starts running and continues to do so until the red button is pressed. These high power push button contactors are usually of an electro-mechanical design and rely on a relay tripping and latching itself "in" when the start button is pressed; pressing the stop button breaks the current through the relay coil and the relay drops out.

We can produce a simple circuit that will perform the same function for small currents and its applications are numerous. For remote switching of radios, burglar alarm trips, starting and stopping logic circuits or possibly in a domestic lighting system for switching lights on and off from different locations.

### Practical Circuit

The circuit is shown in Fig. 1 and to make the application general we are carrying out the switching of the external circuit via a relay, RL1. All the control circuitry is at low voltage but there is no reason why the relay should not control low power mains circuits if desired. To show how the system will respond to signals from more than one station we have built in two extra push buttons, S2 and S4, but for single station control these can be omitted. For more than two stations it is only necessary to parallel other push buttons with S1 and S2 for the "Start" function and an equivalent number of buttons with S3 and S4 for the "Stop" operation.

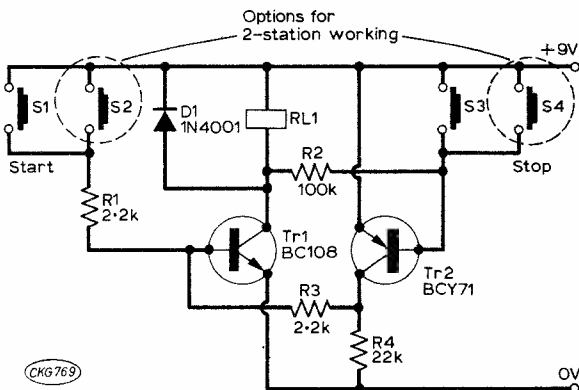


Fig. 1: Circuit of the switch with provision for additional stations.

The circuit is basically a bistable using complementary transistors; when one of the start buttons is pressed base current flows into Tr1 and the relay pulls in switching on the external circuit. Simultaneously the voltage at the collector of Tr1 falls to nearly zero and current then flows from the emitter of Tr2, through its base and via R2. Because of this

base current through Tr2 the latter transistor turns on and its collector voltage is pulled up to the positive rail. This action provides an alternative source of base current for Tr1 through R3 and when the finger is removed from the start button the relay is held in by this positive feedback loop. This switching action is very fast and once initiated cannot be reversed, hence the action is "once and for all" which means that very positive switching is produced so there is no possibility of contact bounce in the electronics (although this may not necessarily be the case with the relay contacts).

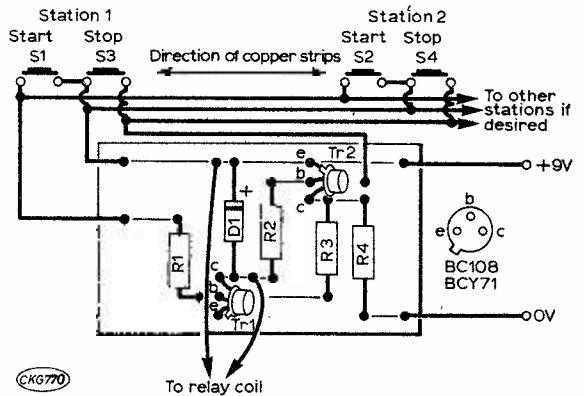



Fig. 2: Layout for 2-station switching, using Veroboard. No breaks are required in copper rails.

To get the relay to drop out it is only necessary to stop the base current flowing through Tr2 and this is done with the stop button(s) which shorts its base to +9V diverting any base current. D1 is present to protect the base/collector junction of Tr1 from the high reverse voltages that are produced by the inductance of RL1.

The relay can be of any type designed for low voltage (6 to 9 volts) operation but should have a coil resistance greater than 100 ohms. Conventional or reed relays can be used. Alternatively the relay and D1 can be replaced by a resistor in the range of 150 to 1000 ohms if all that is required is a logic signal, which can be extracted from the collector of Tr1. Another option is to replace it with a 6V 0.04A bulb or an LED, with a suitable limiting resistor if the circuit is to be used for visual indicating.

### ★ components list

R1	2.2kΩ	} or 1W 10%	Tr1	BC108
R2	100kΩ		Tr2	BCY71
R3	2.2kΩ		S1 etc.	Push buttons normally open.
R4	22kΩ		RL1	See text
D1	1N4001			

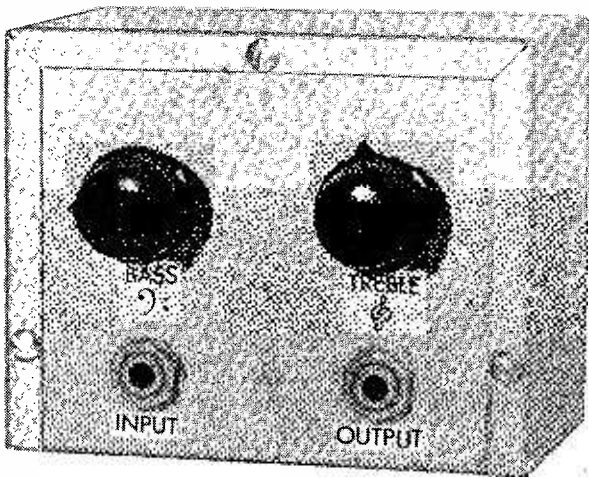

# ADD-ON STE

## \*TONE CONTROL UNIT

A. FOORD

THE tone control unit was designed for experimental audio application where tone controls may be required for signal equalisation. Two identical printed circuit boards are used but a single channel may be constructed if desired. For maximum flexibility volume and balance controls were not added to the unit, but these may be incorporated if required.

PERFORMANCE	
Input Resistance	15k $\Omega$
Output Resistance	Low
Midband Gain	Unity
Bass Control Range	$\pm 20$ dB at 20Hz
Treble Control Range	$\pm 11$ dB at 20kHz
Supply voltage nominally	18V but 12 to 24 V may be used

### CIRCUIT

The circuit for one channel is shown in Fig. 1. An emitter follower Tr1 gives a medium input resistance with a low output resistance driving a Baxandall type tone control circuit. This uses negative feedback around an integrated circuit to give well defined tone control characteristics. The DC bias for the integrated circuit is derived from the supply via R9 and R10. Capacitors C7 and C9 are decoupling components.

### CONSTRUCTION

The construction is straightforward, as shown in Fig. 2, with a separate board, Fig. 3, for each channel. Jack sockets Sk1 and Sk2 are common to both channels. Components for the second channel are listed as C101, etc, as is normal practice. Although a printed circuit was used in the prototype, a similar

CMG763

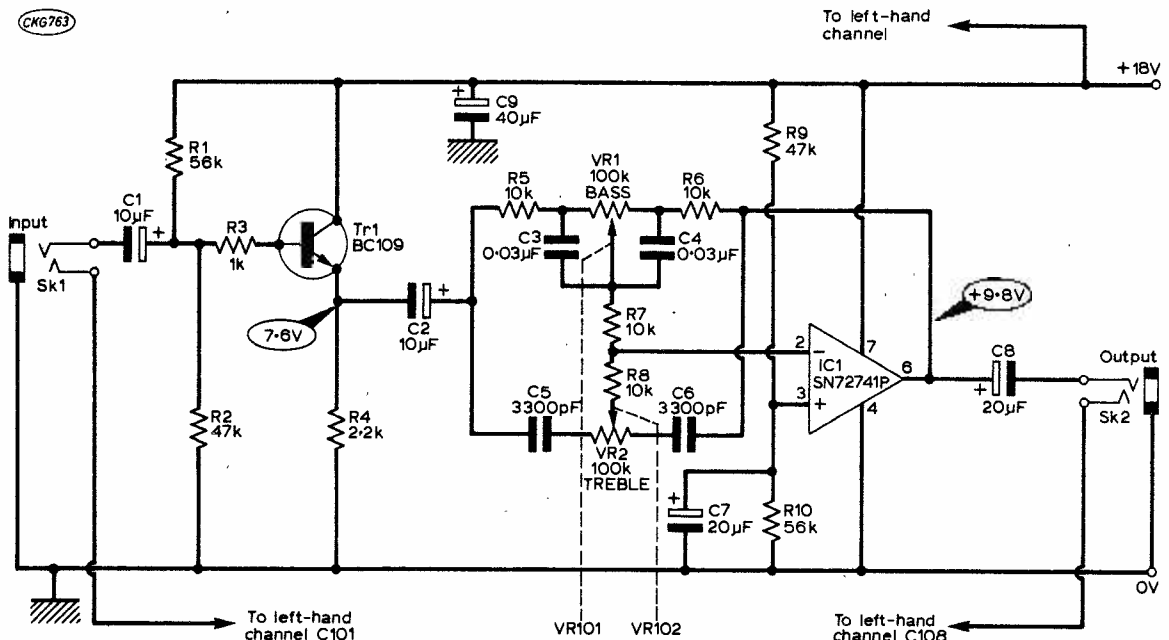


Fig. 1: Circuit of the Tone Control Unit with test voltages indicated. The right-hand channel is shown, the left-hand channel being similar.

Payment CWO, COD, PO, cheque, monthly a/c.


AE, CRIC, CRTE, CRY, DIAT, DILE, DIRE, DIS, DIT, DIZ, EAR, ESC, FUSE, HEAD, ICAM, ICCOM, ICDDL, ICECL, ICFM, ICOP, ICOSC, ICPCA, ICREG, ICVID, MOD, MOR, NEI, THE, THY, TRDA, TRDU, TRGE, TRHF, TRHV, TRPO, TRSI, TRSS, TRSW, TRY, VACC, VAEH, VAPE, VARX, VATX, VATV, VAY.

**CRESCENT RADIO LTD.**,  
11, Mayes Road, Wood Green, London, N22 6TL.  
MOC nil. CP 15p min in UK, overseas at cost. VAT inc.  
Orders by post, call, telephone.  
Payment CWO, PO, cheque, monthly a/c, AC, BC.

AE, AL, BAY, BAYC, BAYH, BELT, BOCA, BOOKS, BOXD, BOXO, BUSH, CAA, CACE, CAEL, CAFI, CAHV, CAPE, CAPA, CAPC, CAPS, CASM, CATA, CATR, CAV, CHA, CHK1, CHKR, COIA, COIF, COIX, COMA, CONA, CONC, CONE, CONM, CONW, CORD, COUP, CROC, DIAL, DIAC, DILE, DIRE, DIS, DIVC, DIZ, DPCC, DPLE, EAR, EHT, FED, FEP, FER, FUSE, GROM, GRUB, HAC, HEAD, HEAT, IND, INST, INSS, ICAM, ICCOM, ICCOU, ICDEC, ICDIV, ICDDR, ICDDL, ICECL, ICFM, ICLSI, ICMOD, ICMOS, ICMSI, ICMUL, ICOP, ICPCA, ICPLL, ICRAM, ICREG, ICROM, ICRTL, ICSEN, ICSSA, ICTIM, ICTRA, ICTTL, IH, JACK, KIT, KNOB, LET, LAMP, LEAD, LISD, LSA, LSM, MAI, MEP, MIS, MOD, MOR, NEI, NUB, OPT, PAD, PAS, PIN, PLSA, PLSB, PLSM, PLR, PLRW, PCBK, PCBU, POT, POTG, POTP, POTS, POTW, RECT, RELE, RES5, RES10, RES20, RESCF, RESMD, RESMO, RESVD, RESW, SC, SLE, SPR, SPH, SPT, SPTV, STUD, SUP, SWA, SWB, SWIK, SWL, SWM, SWRO, SWS, SWTO, SWW, TAG, TAGB, TAGS, TER, TERB, TES, TESP, THE, THY, TOH, TOS, TRAA, TRAH, TRAI, TRAL, TRAM, TRAP, TRAO, TRAT, TRGE, TRJF, TRMF, TRPO, TRSI, TRSS, TRSW, TRUJ, TRX, TRY, VAEH,

continued on page 38.


**JACKS AND PLUGS**

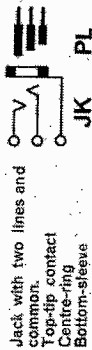

Jack with two lines and common.  
Top-tip contact  
Centre-ring  
Bottom-sleeve




Jack as above but with break contacts

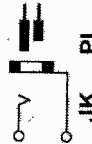

Jack with one line and common



Jack as above but with one break contact

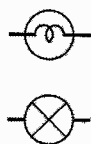

INCANDESCENT LAMPS INDICATING (left) AND ILLUMINATING (right)




LIGHT DEPENDENT VARIABLE RESISTANCE




LOUDSPEAKER

**ELECTROMAGNETIC RELAYS**

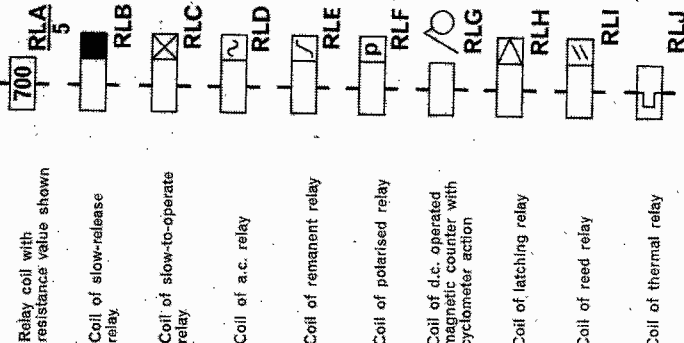

Relay coil with resistance value shown  
Coil of slow-release relay  
Coil of slow-to-operate relay  
Coil of a.c. relay  
Coil of remanent relay  
Coil of polarised relay  
Coil of d.c. operated magnetic counter with cyclometer action  
Coil of latching relay  
Coil of reed relay  
Coil of thermal relay

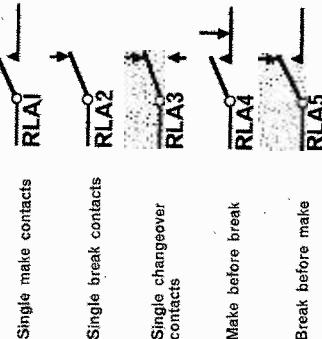**RELAY CONTACTS (SHOWN IN NEUTRAL POSITION)**



Single make contacts  
Single break contacts  
Single changeover contacts  
Make before break  
Break before make

**NEW RANGE OF FREQUENCY COUNTERS, DIGITAL CLOCKS, ETC. NOW AVAILABLE**

**Studio Electronics**  
15-17, Upper Street, London, N1 1UP

Directory Entry on page 12

**PEAT'S**

Public Address  
Electronic Parts  
Audio & Testgear  
Technical Books  
Tereo Systems

Also a postal service  
**Wm. B. Peat & Co. Ltd.**  
25-26 Parnell Street, Dublin 1, Ireland.

**SAME DAY SERVICE ON ALL EX-STOCK ITEMS!**  
MAIL ORDER AND WHOLESALE SUPPLIERS OF ELECTRONIC COMPONENTS.  
Send s.a.e. for up-to-date lists.

**MARCO TRADING**  
THE OLD SCHOOL, EDSTASTON,  
Nr. WEM, SHROPSHIRE

Telephone Number:  
WHYKALL (SHROPSHIRE) 464  
STD CODE 08872

Proprietors: Minicost Trading Ltd.

**LANCASHIRE**

**DAVIAN ELECTRONICS,**  
P.O. Box 38, Oldham, OL2 6XJ.

**TP** nil.  
**MOC** nil. **CP** 10p up to £2 order in UK, overseas at cost. **VAT** Inc.  
Orders by post. Exports.  
Payment CWO, COD, PO, cheque.

**DILE, DIRE, DIS, DIZ, ICAM, ICCOM, ICCOU, ICDEC, ICDDV, ICDTL, ICFM, ICESI, ICMSI, ICOP, ICSSA, ICTIM, ICTTL, LISD, OPT, PCB, SOL, THY, TRDA, TRDU, TRHF, TRHV, TRMP, TRPO, TRSI, TRSS, TRSW, TRV.**

**JEF ELECTRONICS,**

York House, 12 York Drive, Grappenhall, Warrington, WAA 4 2EJ.

**TP** 0925-64080.  
**MOC** nil. **CP** 11p in UK, overseas at cost, **VAT** extra.  
Orders by post only. Exports.  
Payment CWO, COD, PO, cheque, monthly a/c.

**DIAC, DILE, DIRE, DIS, DIZ, DPFI, FEB, HEAT, ICAM, ICCOU, ICCOM, ICDEC, ICDDV, ICDR, IGLSI, ICMSI, ICMSI, ICOP, ICEA, ICPLL, IGRAM, ICREG, ICROM, ICSEN, ICSSA, ICTIM, ICTTL, IH LEAD, POTR, RESI, RESCF, RESWV, TESP, THE, THY, TOS, TRDA, TRGE, TRHF, TRHV, TRUF, TRVF, TRVP, TRW, TRX, TRSS, TRSW, TRV.**

**LEICESTERSHIRE**

**ELEY ELECTRONICS,**

112 Groby Road, Glenfield, Leicester, LE3 8GL.  
**TP** 0533 (Leicester) 871522.  
**MOC** nil. **CP** at cost. **VAT** Inc.  
Orders by post, call, telephone. Exports.  
Payment CWO, PO, cheque, monthly a/c, A.C.

**BAY, BAYC, BAYH, BOOK, BOXO, BUSH, CAB, CAGE, CAEL, CAE, CAFE, CAFI, CAPE, CAPA, CAPS, CASM, CATI, CATR, CAV, CHA, CHK, CHKR, COIX, CONA, CONG, CONE, CONW, CONW, CONW, CONW, CONW, CRY, DIAT, DIAC, DILE, DIRE, DIS, DIT, DIVC, DIZ, DFCC, DPLI, DPLC,**

**EAR, FED, FER, FERT, FIG, FUSE, GROM, HEAD, HEAT, IND, INST, INSA, INSS, ICAM, ICCOM, ICCOU, ICDEC, ICDDV, ICDR, ICDTL, ICFM, ICESI, ICMSI, ICOP, ICSPA, ICPLL, ICREG, ICSSA, ICTIM, ICTTL, IH, JACK, KIT, KNOB, LAMP, LEAD LISD, LSA, LSM, MAG, MEP, MIS, MOR, MOT, NEI, NUB, OPT, PAD, PIN, PLSA, PLSG, PLSM, PLSR, PLSW, PCB, POT, POT, POTR, POTS, POTV, RECT, RELE, RELR, RESI, RES, RESI, RES10, RES20, RESCF, RESGT, RESMO, RESWV, SC, SLE, SLUG, SPA, STUD, SUP, SWB, SWL, SWM, SWRE, SWRO, SWS, SWTH, SWTO, SWUE, SWV, TAG, TAGB, TAGS, TER, TERB, TES, TESP, THE, THY, TRAA, TRAH, TRAI, TRAL, TRAM, TRAO, TRATR, TRGE, TRHF, TRHV, TRUF, TRVF, TRPO, TRSI, TRSS, TRSW, TRUJ, TRX, TRY, VAAC, VAEH, VAPE, VARX, VATX, VATY, VAX, VAV, VAZ, WCA, WSC, WCP, WEN, WMA, WMU, WMS.**

**LONDON**

**BARRIE ELECTRONICS,**

3 The Minories, London, EC3N 1BU.  
**TP** 01-488 3316.  
**MOC** nil. **CP** extra. **VAT** extra.  
Orders by post, call, telephone. Exports.  
Payment CWO, PO, cheque, monthly a/c, A.C, B.C.

**BAY, CONC, ICCOU, ICDEC, ICDDV, ICDR, ICDDL, ICESI, ICMSI, ICMSI, ICOP, ICTTL, PAD, RECT, RESI, RES2, RES3, RESCF, RESCQ, RESGT, RESMO, RESWV, TES, THY, TOS, TRAA, TRAH, TRAL, TRAM, TRAM, TRAO, TRGE, TRHF, TRHV, TRUF, TRMF, TRMP, TRPO, TRSI, TRSS, TRSW, TRUJ, TRX, TRY, VATX, WCA, WMA.**

**CHROMASONIC ELECTRONICS,**


56 Fortis Green Road, London, N10 3HN  
**TP** 01-600 0801.  
**MOC** nil. **CP** in UK from 10p, overseas at cost. **VAT** Inc.  
Orders by post, call, telephone.  
Export agent Pitt & Scott.  
Payment CWO, PO, cheque, monthly a/c.

Single-pole single throw on-off

(a) normally open

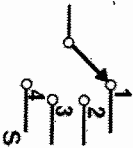(b) normally closed

Single-pole multi-way rotary switch with knob control and four paths



Double-pole changeover with rotary control knob or single toggle operating danged moving arms.




Single-pole slide switch with changeover operated by slider knob



Thermal switch with resistive sensing element



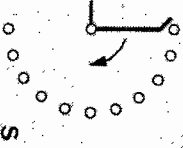Multi-way electro-magnetic coil operated rotary switch. Arrow shows direction of wiper motion (unselector)



Coil of above switch



**COLOMOR ELECTRONICS LTD.**  
170, Goldhawk Rd, London, W12  
valves, transistors, diodes, etc.

**24 HOUR SERVICE**  
Radio communications & telephone equipment.

Directory Entry on Page 18.

**Crescent Quality Components from CRESCENT RADIO LTD.**

Callers welcome at:  
15-17 Mayes Rd, Wood Green, London N22 6TL  
13 South Mall, Edmonton, London N9

Or send for our Mail Order Catalogue  
To: No. 11 Mayes Rd, Wood Green N22 6TL

**TELETYPE**

49-53 Pancras Road  
London NW1 2EP  
Tel. 01 857 7791

For a complete range of Oscillators, Signal Generators, Digital Voltmeters, Power Supplies, Pen Recorders, Multi-Channel Meters, etc. Please send for latest All Inclusive Directory from 30p discount

VARX, VATV, VAX, VAY, VAZ, WCA, WSC, WCP, WEH, WEN, WLI, WMA, WRE, WMS.

**C.T. ELECTRONICS.**

270 Acton Lane, London W4 5DG.  
**TP** 01-994 6275.  
**MOC** nil. **CP** 20p min up to £5 order, overseas 85p min.  
**VAT** extra.  
**Orders** by post, call, telephone. Exports.  
**Payment** CWO, COD, PO, cheque monthly a/c.

AE, BAY, BAYC, BAYH, BOCA, BOXD, BOXO, CAEL, CAEL, CAFE, CAFI, CAHV, CAPE, CAPC, CAPP, CAPS, CASM, CAPA, CAPC, CAPP, CAPS, CASM, CATA, CATR, CAV, CAHKR, COJA, CHKR, COIX, COMA, CONA, CONC, CONE, CONM, CONW, COUP, CROC, CRY, DIAC, DILE, DIRE, DIS, DIT, DIUM, DIVC, DIZ, EAR, FEP, FER, FERT, FIC, FUSE, GROM, GRUB, HAC, HEAD, HEAT, IND, INST, INSS, ICAM, ICCOU, ICDEC, ICDIV, ICDR, ICFCM, ICIMOD, ICMUL, ICOP, ICPA, ICREG, ICSSA, ICTIM, ICTRA, ICTTL, ICTV, JACK, KIT, KNOB, LAMP, LEAD, LISD, LSA, LSM, MEP, MIS, MOD, MOT, NEI, NUB, OPT, PAD, PIN, PLSA, PLS, PLSM, PLSR, PLSW, PCBE, PCBK, PCB, POT, POTG, POTP, POTS, POTW, RECT, RELE, RELR, RES1, RES2, RES3, RES10, RES20, RESCF, RESMO, RESVW, SLE, SPA, SUP, SWA, SWL, SWM, SWRE, SWRO, SWS, SWTO, SWWE, SWW, TAG, TAGB, TAGS, TER, TERB, TES, TESP, THE, THY, IOS, TRAA, TRAH, TRAL, TRAM, TRAMI, TRAP, TRAO, TRAT, TRDA, TRDU, TRGE, TRHF, TRHV, TRJF, TRMF, TRMP, TRPO, TRSI, TRSS, TRSW, TRUJ, TRUM, TRX, TRY, WCA, WSC, WCP, WEN, WMA, WMLU, WMS.




FIXED RESISTANCE (EUROPEAN STANDARD)



FIXED RESISTANCE (ALTERNATIVE SYMBOL)



FIXED RESISTANCE WITH TAPPED CONNECTION

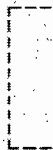


SCREEN AROUND A PART OF A CIRCUIT



SOLAR CELL



SUPPRESSOR

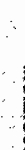

SWITCHES (SHOWN IN NEUTRAL POSITION)



Single pole on-off push button (normally off)




Single pole on-off push button (normally closed)

**LEVER OPERATED KEYSWITCH CONTACTS**



Make before break, non-locking

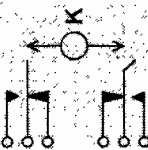

Changeover, non-locking Lever arm



Changeover locking



Double-pole single throw on-off switch (ganged moving arms or single toggle)

BAYC, BAYH, BOCA, BOXD, BOXO, CAEL, CAEL, CAFE, CAFI, CAHV, CAPE, CAPC, CAPP, CAPS, CASM, CATA, CATR, CAV, CAHKR, COJA, COIF, COIX, COMA, CONA, CONC, CONE, CONM, CONW, COUP, CROC, DIAC, DILE, DIRE, DIS, DIVC, DIZ, DPFI, DPGA, DPIC, DPLE, EAR, FEB, FED, FER, FIC, FII, FUSE, GROM, HEAT, INST, ICAM, ICCOM, ICCOU, ICDEC, ICDIV, ICDR, ICFCM, ICFSI, ICMOD, ICMOS, ICMIS, ICMUL, ICOP, ICOS, ICPA, ICPLL, ICREG, ICSSA, ICTIM, ICTRA, ICTTL, ICTV, ICVID, IH, JACK, KIT, KNOB, LAMP, LISD, LSA, MAI, MOD, NEI, NUB, OPT, PAD, PIN, PLSA, PLS, PLSM, PLSR, PCBE, PCB, POT, POTG, POTP, POTS, POTW, RECT, RES2, RES3, RES10, RES20, RESCF, RESGT, RESMD, RESMO, RESTF, RESVD, RESVW, SC, SLE, SPR, SPH, SWB, SWM, SWS, SWTO, SWTW, SWW, TAGB, TAGS, TER, TERB, TESP, THE, THY, TOS, TRAH, TRAI, TRAL, TRAM, TRAO, TRAT, TRDA, TRDU, TRGE, TRHF, TRHV, TRJF, TRMF, TRMP, TRPO, TRSI, TRSS, TRSW, TRUJ, TRX, TRY, VAEH, VAY, WCA, WCP, WEN, WMA.

**COLOMOR (ELECTRONICS) LTD.,**  
 170 Goldhawk Road, London W4.  
**TP** 01-743 0899.

**MOC** nil. **CP** in UK 22p up to £3 order, overseas at cost.  
**VAT** extra.  
**Orders** by post, call. Exports.

**PHONOSONICS**  
 25 KENTISH ROAD,  
 BELVEDERE, KENT  
 DA17 5BW

**PRINTED CIRCUIT  
 BOARDS, COMPONENTS,  
 KITS**

S.A.E. for Free List  
 Mail Order Only

**NEW MART  
 NELECTRONICS**

Mail Order Dept.  
 Belmont Street,  
 Monton, Eccles,  
 Manchester.  
 061-789 5268

**BRANCHES**  
**MANCHESTER** LIVERPOOL  
 30-32 Shudehill 15 Whitechapel  
 061 236 0738 051 236 0738

**LEEDS** SHEFFIELD  
 4 New Market St. 20 Pinston St.  
 0532 42708 0742 79308

**Hi Fi and component specialists**

**ELEY ELECTRONICS**  
 Surplus Supermarket Premises  
 102 Beatrix Rd., Leicester (off  
 Fosse Rd., Nth).

OPEN: Tuesday to { 10a.m.-2p.m.  
 Thursday { 4p.m.-5p.m.  
 Friday { 9a.m.-2p.m.  
 Saturday { 10a.m.-5p.m.

Valves — Components — I.C.'s —  
 Transistors — Surplus Equip-  
 ment — Transceivers — Test  
 Gear.

For Comprehensive List  
 of Components and  
 Component Packs send  
 S.A.E. to:—

**W.P. COMPONENTS**  
 7, Brook Avenue,  
 Edgware,  
 Middlesex, HA8 9XF

**YORK ELECTRICS.**  
 335A, Battersea Park Road, London  
 SW 11.

**TP** none.  
**MOC** nil. **CP** extra. **VAT** inc.  
**Orders** by post, call, Exports.  
**Payment** CWO, PO, cheque, monthly  
 a/c, AC, BC.

KIT, LISD, OPT, PCBK.



**ELECTRONIC BROKERS LTD.,**  
49 Pancras Road, London NW1,  
TP 01-837 7811.

**MOC** nil. **CP** extra. **VAT** extra.  
Orders by post, call, telephone. Exports.  
Payment CWO, PO, cheque, monthly  
a/c.

New and surplus instruments only. TES

**GARLAND BROS. LTD.,**  
Dentford Broadway, London, SE8 4QN,  
TP 01-692 4412.

**MOC** nil. **CP** UK only 20p min. **VAT** inc.  
Orders by post, call telephone.  
Payment CWO, PO, cheque, monthly  
a/c.

Directory entry page 43.

AE, AL, BAY, BAYC, BAYH, BELT,  
BOCA, BOOK, BOXD, BOXO, CAA,  
CAB, CACE, CAEL, CAFE, CAFI,  
CAHV, CAPE, CAPA, CAPC, CAPP,  
CAPS, CASM, CATA, CATR, CAV,  
CHA, CHKR, COIA, COIX, COMA,  
CONA, CONG, CONM, CONW,  
CORD, COUP, CROC, DIAC, DILE,  
DIRE, DIS, DIVC, DIZ, EAR, FEB, FED,  
FER, FIL, FUSE, GROM, HAC, HEAD,  
HEAT, IND, INST, ICCOM, ICCOU,  
ICDEC, ICIDI, ICDR, ICMD, ICOP,  
ICPA, ICSSA, ICTTL, IH, JACK, KIT,  
KNOB, LAMP, LEAD, LISD, LSA,  
LSM, MAI, MEP, MIS, MOD, NEI, NUB,  
OPT, PIN, PLSA, PLSG, PLSM, PLSR,  
PLSW, PCBK, PCBUI, POT, POTG,  
POTP, POTS, POTW, RECT, RELI,  
RELR, RES2, RES3, RES10, RES20,  
RESCF, RESCR, RESMD, RESWV,  
SLE, SPA, SPR, SPT, SPTV, SPTV,  
SRBP, STUJ, SUP, SWA, SWB, SWK,  
SWL, SWM, SWRE, SWRO, SWS,  
SWTH, SWTO, SWW, TAG, TAGB,  
TAGS, TER, TERB, TES, TESP, THE,  
THY, TOH, TOS, TRAA, TRAH, TRAL,  
TRAMI, TRAP, TRAO, TRATR, TRGE,  
TRHF, TRHV, TRJF, TRMF, TRMP,  
TRPO, TRSI, TRSS, TRSW, TRUJ,  
TRX, TRY, VAH, VAPE, VARX,  
VATX, VATY, VAY, WCA, WSC,  
WCP, WEH, WEN, WMA, WMU, WMS.

Orders by post, call, TP, TX, Exports.  
Payment CWO, PO, cheque, monthly  
a/c. AC, BC.

Directory entry page 43.

AE, BAY, BAYC, BAYH, BOCA, BOOK,  
BOXD, BOXO, BUSH, CAA, CACE,  
CAEL, CAFE, CAFI, CAHV, CAPE,  
CAPA, CAPS, CASM, CATA, CATR,  
CAV, CHA, CHKL, CHKR, COIA, COIF,  
COIT, COIX, COMA, CONA, CONG,  
CONE, CONM, CONW, COUP, CROC,  
CRY, DIAL, DIAG, DILE, DIRE, DIS,  
DIT, DIVC, DIZ, DPCG, DPLE, EAR,  
EHT, FEB, FED, FER, FERT, FIG,  
FUSE, HEAD, HEAT, IND, INST, INSA,  
ICAM, ICCOM, ICCOU, ICDEC, ICIDI,  
ICDR, ISIDL, ICECL, ICFM, ICMD,  
ICMU, ICOP, ICOSC, ICPA, ICPLL,  
ICRAM, ICRG, ICROM, ICRTL, ICSEN,  
ICSSA, ICTRA, ICTTL, IH, JACK, KIT,  
KNOB, LAMP, LEAD, LISD, LSA, LSM,  
MEP, MIS, MOD, MOR, MOT, NEI, OPT,  
PAD, PIN, PLSA, PLSG, PLSM, PLSR,  
PLSW, PCBK, PCBUI, POT,  
POTG, POTP, POTS, POTW, RECT,  
RELE, RELR, RELR, RES3, RESCF, RESCR,  
RESMO, RESVD, RESWV, SC, SLUG,  
SOL, SPR, SPT, SPTV, SPTV, SWA,  
SWB, SWM, SWL, SWM, SWP,  
SWRE, SWRO, SWS, SWTH, SWTO,  
SWTW, SWUE, SWW, TAG, TAGS,  
TER, TERB, TES, TESP, THE, THY,  
TOH, TOS, TRAA, TRAH, TRAI,  
TRAL, TRAM, TRAMI, TRAP, TRAO,  
TRATR, TRDA, TRDU, TRGE, TRHF,  
TRHV, TRJF, TRMF, TRMP, TRPO,  
TRSI, TRSS, TRSW, TRUJ, TRX, TRY,  
VACC, VAH, VAPE, VARX, VATX,  
VATY, VAX, VAY, VAZ, WCA, WSC,  
WCP, WEN, WMA, WMU, WMS.

**LASKY'S AUDIOELECTRONICS,**  
Audiotronic House, The Hyde Industrial  
Estate, London NW9 6UJ

TP 01-205 5651/3735.  
**MOC** nil. **CP** in UK extra, overseas—on  
application. **VAT** extra.

Orders by post, call on shops, telephone  
Exports.  
Payment CWO, PO, cheque, monthly  
a/c. AC, BC.

**AE, BAY, BAYC, BAYH, BOOK, CONA,  
CROC, EAR, HEAD, JACK, KIT, KNOB,  
LEAD, LSA, MEP, MOD, OPT, PIN,  
SWS, SWTO, TES, TRATR, WSC,  
WCP, WMA.**

**Partridge Electronics Ltd.,**  
P.O. Box 4, Broadstairs, Kent.  
TP 0843 (Thanet) 82535.

**MOC** nil. **CP** extra. **VAT** extra.  
Orders by post, call, telephone. Export.  
Payment CWO, COD, PO, cheque, AC,  
BC.

AE, BOXO, CATR, CAV, COIA, COIX,  
CONA, CONG, CROC, CRY, EAR,  
HEAD, KIT, KNOB, LSA, MEP, NUB,  
POT, SLE, SWA, SWRO, SWS,  
SWW, TAG, TER, TERB, VARX,  
WCA, WCP, WEN.

**PHONOSONICS**

25 Kentish Road, Belvedere, DA17 5BW.  
TP nil.  
**MOC** nil. **CP** 15p in UK, overseas at  
cost. **VAT** extra.

Orders by post Exports.  
Payment CWO, PO, cheque, monthly  
a/c.

BAYC, BOCA, CACE, CAEL, CAFI,  
CAPE, CAPC, CAPS, CASM, CATA,  
COIX, COMA, CONA, CONG, CONE,  
CONM, CONW, COUP, CROC, DIRE,  
DIS, DIZ, FED, FER, FERT, FUSE, IND,  
ICCOM, ICCOU, ICDEC, ICIDI,  
ICDR, ICIDI, ICOP, ICPA, ICRG,  
ICSSA, ICTTL, IH, JACK, KIT, KNOB,  
LET, LAMP, LEAD, MEP, NEI, POT,  
PIN, PLSA, PLSG, PLSM, PLSW,  
PCBE, POT, POTG, POTR, POTS,  
POTW, RECT, RELE, RELR, RES2,  
RES3, RES10, RESCF, RESMO, RESWV,  
SPA, SWA, SWB, SWL, SWM,  
SWRO, SWTO, SWW, TAGB, TAGS,  
THY, TRAL, TRGE, TRHF, TRJF,  
TRPO, TRSI, TRSS, TRSW, TRUJ,  
TRX, TRY, WSC, WCP, WEN

**TELESERVICE**

108 Camden Road, Tunbridge Wells,  
TN1 2QX.  
TP 0892 (Tunbridge Wells) 31803.  
**MOC** 44p. **CP** inc. **VAT** inc.

Orders by post, call, telephone.  
Payment CWO, PO, cheque.

AE, AL, BAY, BAYC, BAYH, BOCA,  
BOOK, BOXO, CAB, CACE, CAEL, CAFE,  
CAHV, CAPE, CAPC, CAPS, CASM,  
CATA, CATR, CAV, CHA, CHKR,  
COIA, COIX, COMA, CONA, CONG,  
CONE, CONM, COUP, CROC, DIAL,

DILE, DIOR, DIRE, DIS, DIUN, DIZ,  
EAR, FEB, FED, FER, FERT, FIL, FUSE,  
GROM, HAC, HEAD, HEAT, INST,  
INSS, JACK, KNOB, LAMP, LEAD,  
LISD, LSA, LSM, MAI, MIS, MOT,  
NEI, NUB, PIN, PLSA, PLSG, PLSM,  
PLSH, PCBK, PCBUI, POT, POTG,  
POTP, POTW, RECT, RELE, RES2, RES3,  
RES10, RESCF, RESMD, RESMO,  
RESCF, RESWV, SC, SLE, SRBP,  
SWS, SWM, SWS, SWTO, SWW, TAG  
TAGB, TAGS, TER, TERB, TESP,  
THY, TOH, TOS, TRAH, TRAI, TRAL,  
TRATR, TRGE, TRHF, TRHV,  
TRJF, TRMF, TRMP, TRPO, TRSI,  
TRSS, TRSW, TRUJ, TRUM, TRX,  
VAY, WCA, WSC, WCP, WEN, WMA,  
WMU, WMS.

**Ex-Stock Transformers**

**24 HOUR SERVICE**

Phone  
Kiln Country  
(0227) 52556

**1-24 £1.55 each**

Send for catalogue

**A.S.P. BYRE HOUSE - SIMMONDS RD. - CANTERBURY - KENT**



**SWLS - DEXERS - AMATEURS  
WHATSOEVER YOUR LOCATION**


PARTNDRIDGE offer you TOP CLASS  
PERFORMANCE using WORLD RECORD  
patented V.F.A. system!

DISCUSS YOUR PROBLEM WITH THE  
EXPERTS.


Send 5p stamp for brochure—

**PARTNDRIDGE ELECTRONICS LTD.**  
BOX P  
BROADSTAIRS, KENT CT10 1LD  
G3CED Tel. Thanet (0843) 82535 G3VFA



# REC HI-FI UNITS

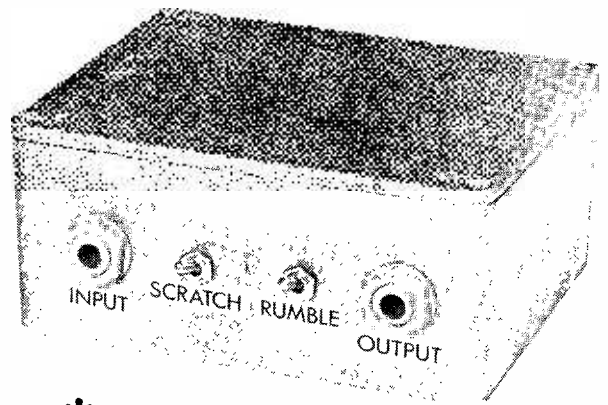


## \* SCRATCH AND RUMBLE FILTER

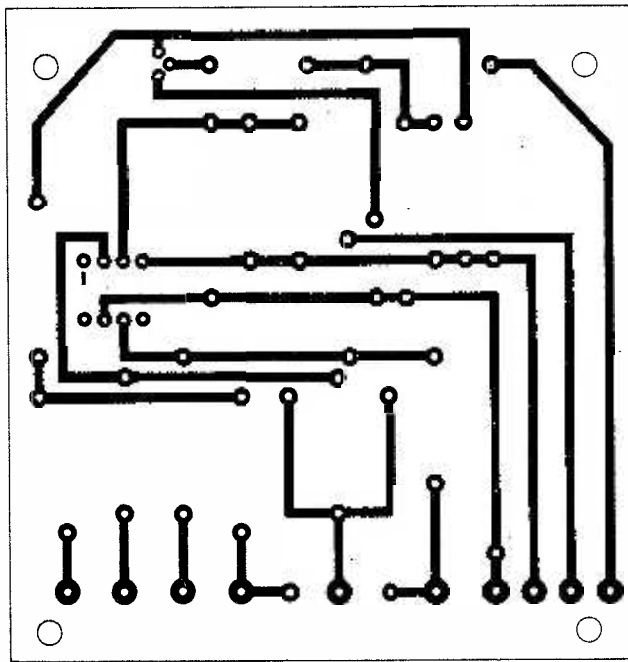


AM 0238A

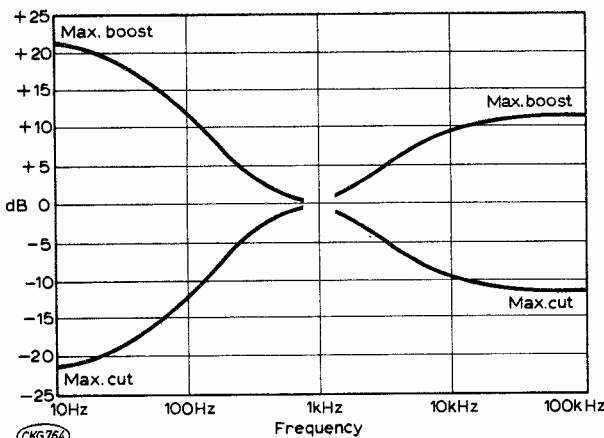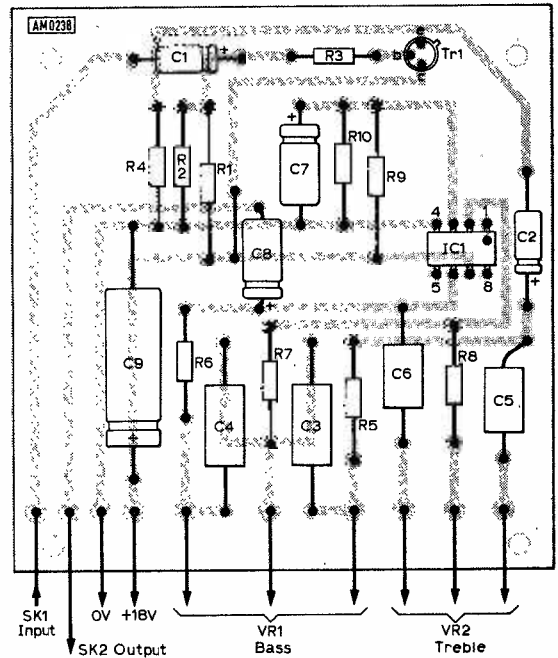

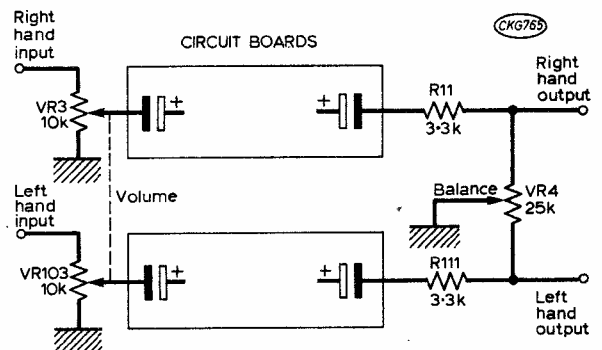Figs. 2 & 3; above, show the PCB actual size and layout of components on the PCB. Two such PCB's are required for a stereo unit. Fig. 4: left, indicates the performance of the tone controls. Fig. 5: below, shows how volume and balance controls can be added, if required.



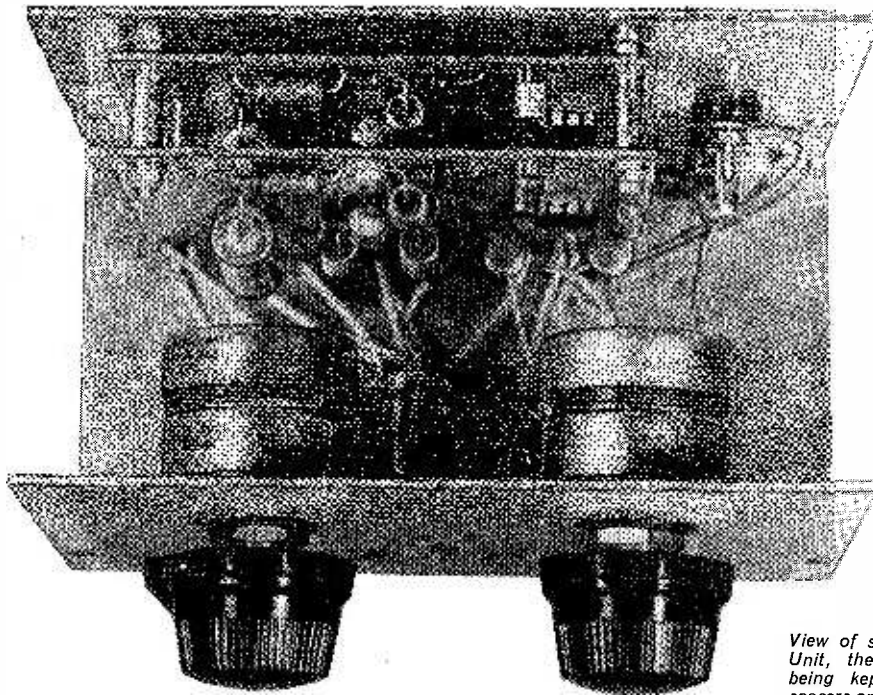

*View of stereo Tone Control Unit, the identical boards being kept well apart with spacers on the fixing bolts.*

layout using LEKTROKIT could be used if required. No detailed dimensions are given since this will depend on the constructor's individual requirements and the layout is not critical.

The DC voltages shown on the circuit diagram may be measured for the nominal supply voltage shown.

## ★ components list

### Resistors

R1	R101	56k $\Omega$	R7	R107	10k $\Omega$
R2	R102	47k $\Omega$	R8	R108	10k $\Omega$
R3	R103	1k $\Omega$	R9	R109	47k $\Omega$
R4	R104	2.2k $\Omega$	R10	R110	56k $\Omega$
R5	R105	10k $\Omega$	R11	R111	3.3k $\Omega$
R6	R106	10k $\Omega$			

All  $\frac{1}{4}$  or  $\frac{1}{2}$ W 5%

VR1/VR101 100k $\Omega$  linear dual gang

VR2/VR102 100k $\Omega$  linear dual gang

VR3/VR103 10k $\Omega$  log. dual gang

VR4 25k $\Omega$  linear

### Capacitors

C1	C101	10 $\mu$ F 16V
C2	C102	10 $\mu$ F 16V
C3	C103	0.03 $\mu$ F* 5% polycarbonate
C4	C104	0.03 $\mu$ F* 5% "
C5	C105	3300pF 5% polystyrene
C6	C106	3300pF 5% "
C7	C107	20 $\mu$ F 16V
C8	C108	20 $\mu$ F 16V
C9	C109	40 $\mu$ F 25V

(\* 0.033 $\mu$ F 'preferred' value)

### Semiconductors

Tr1	Tr101	BC109	IC1	IC101	SN72741P
					(or 741 or similar)

### Miscellaneous

Terminals (2). Case 5 x 4 x 3 in. or similar. Knobs (2).  
Jack sockets, stereo (2). PCB's (2).

If these DC conditions are correct then an AC signal may be applied to the unit and the overall performance checked. If no test equipment is available then a listening test must suffice. The tone control characteristics are shown in Fig. 4.

## VOLUME AND BALANCE CONTROLS

If required, volume and balance controls may be added as shown in Fig. 5. This will however depend on the application and the existing system. For maximum flexibility in experimental work it might be better to have completely separate controls for bass, treble and volume rather than have them ganged.

The balance control shown reduces the gain for each channel to 0.8 times the central value. However this should not present a problem because tone controls are usually inserted into a system at a point where adequate signals are available.

## SCRATCH & RUMBLE FILTER

This unit was developed for experimental audio applications where scratch and rumble filtering may be required to improve the results obtained from a record player or tape recorder. It was originally built as an "add on" stereo unit, although it could equally well be incorporated into a permanent system. The unit was designed on two identical printed circuit boards so that a single channel can be constructed if desired.

## THEORY

The basic scratch and rumble filters used here are shown in Fig. 6a and 6b respectively. The theoretical design of such circuits is complex and many variations are possible. The unity voltage gain amplifier shown will have a power gain because it has a high


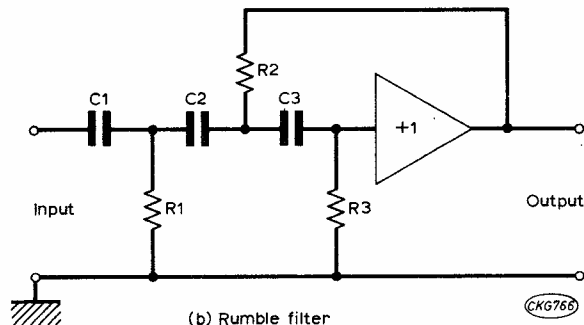
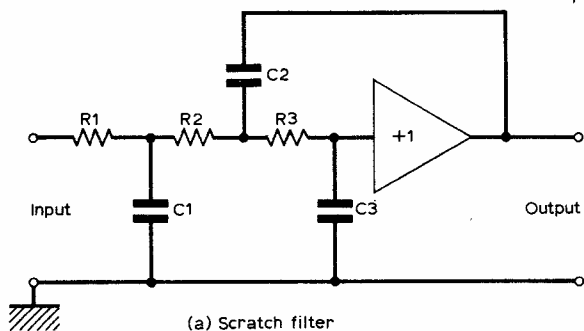


Fig. 6: (a) Basic circuit of a scratch filter. (b) shows the arrangement required for a rumble filter.

input impedance but a low output impedance. An emitter follower is sometimes used but an integrated circuit allows the unity gain to be more closely defined.

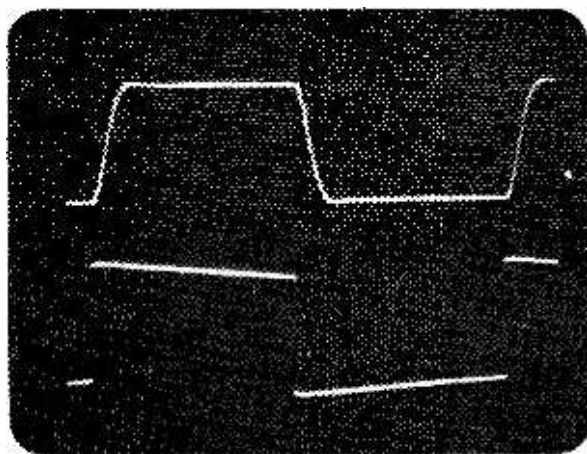For the scratch filter the capacitors have no effect at mid frequencies and the overall gain is unity. As the input frequency is increased C1 and C3 bypass the signal to earth and there is feedback from the output of the amplifier through C2 back to the input circuit. This arrangement gives a sharper 'turn-over'



These traces show the response of the filters to a 1kHz square wave input. Top, scratch filter only. Bottom, rumble filter only.

of the frequency response than would be possible using only passive components. Similarly, for the rumble filter, at mid frequencies the capacitors have a low impedance and the overall gain in unity. As the input frequency is decreased the capacitors increase in impedance and the output is reduced.

## CIRCUIT

In the practical circuit of Fig. 7 the amplifiers are formed by 741 integrated circuits. The output terminal pin 6 is connected directly to the inverting input pin 2. This gives the required non-inverting buffer with a high input impedance and a low output impedance. The right hand channel only is shown in Fig. 7 and the left hand channel is identical. Tr1 forms an emitter follower which corrects the DC bias for the integrated circuit. The rumble filter can be

—continued on page 633

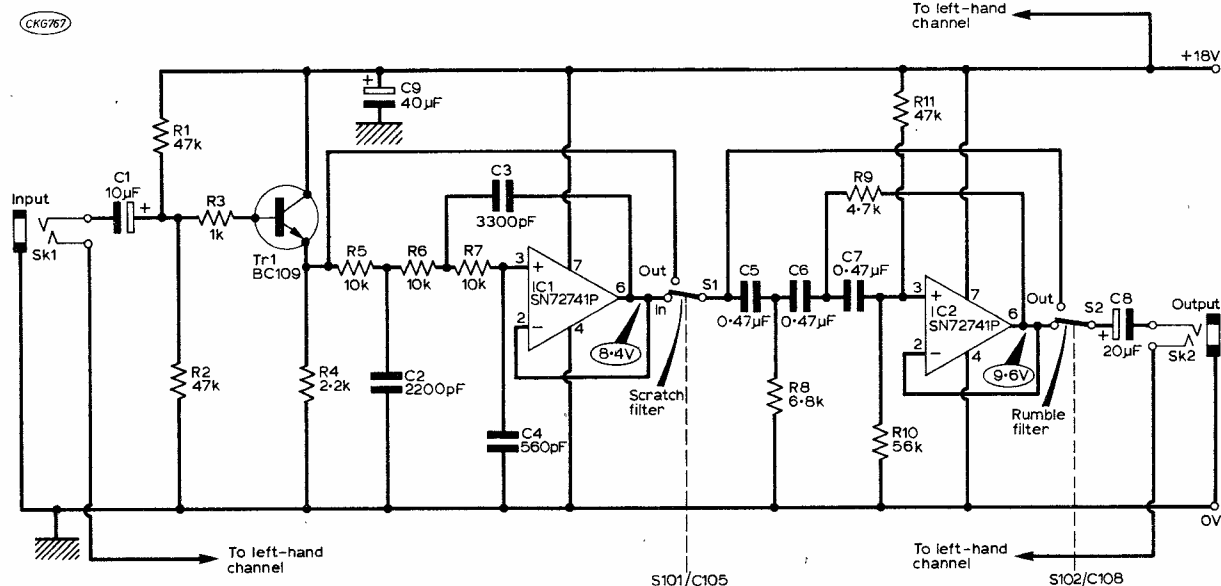


Fig. 7: Circuit of the right-hand channel of the complete Scratch and Rumble Filter for stereo.

Now two fascinating ways to enjoy saving money!

# NEW! Sinclair Scientific kit **£19.95** (INC. VAT)

## Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range — features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £32.35 (including VAT).

And as a kit it costs under £20!

## Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle *directly*

sin and arcsin,  
cos and arccos,  
tan and arctan,  
automatic squaring and doubling,  
log<sub>10</sub>, antilog<sub>10</sub>, giving quick access to x<sup>Y</sup> (including square and other roots),  
plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

## So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied — all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer — they're still exceptional value. Use the order form.

## Components for Scientific Kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

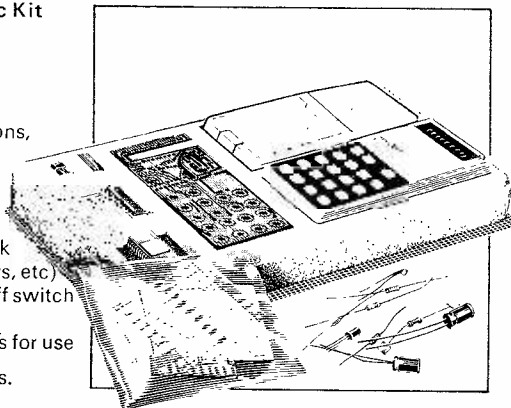

## Features of the Sinclair Scientific

- **12 functions on simple keyboard**  
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.


- **Scientific notation**  
Display shows 5-digit mantissa, 2-digit exponent, both signable.

- **200-decade range**  
10<sup>-99</sup> to 10<sup>+99</sup>.

- **Reverse Polish logic**  
Post-fixed operators allow chain calculations of unlimited length — eliminate need for an = button.

- **25-hour battery life**  
4 AAA manganese alkaline batteries (e.g. MN2400) give 25 hours continuous use. Complete independence from external power.

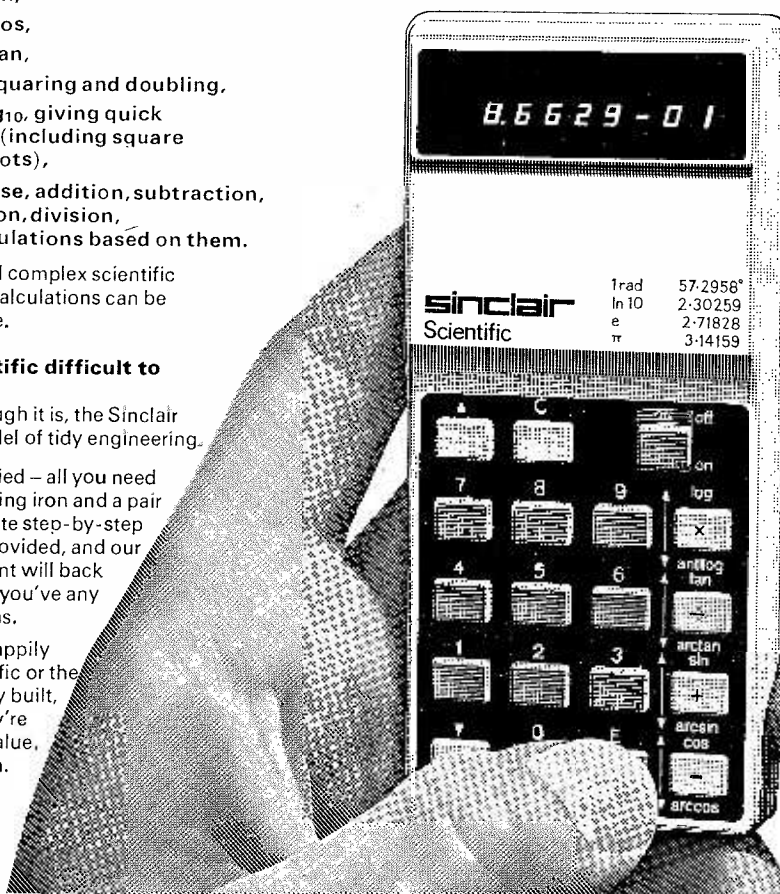- **Genuinely pocketable**  
4 1/3" x 2" x 11/16". Weight 4 oz. Attractively styled in grey, blue and white.





# Sinclair Cambridge kit

**Now only**  
**£14.95**  
 (INC. VAT)

At its new low price, the original Sinclair Cambridge kit remains unbeatable value.

In less than a year, the Cambridge has become Britain's most popular pocket calculator.

It's not surprising. Check the features below – then ask yourself what other pocket calculator offers such a powerful package at such a reasonable price.

## Components for Cambridge Kit

1. Coil
2. LSI chip
3. Interface chip
4. Thick film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet

Assembly time is about 3 hours.

## Take advantage of this

**money-back, no-risk offer today**  
 The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee any correctly-assembled calculator for one year. (This guarantee also applies to calculators supplied in built form.)

Simply fill in the preferential order form below and slip it in the post today.

## Scientific

Price in kit form £19.95 inc. VAT.

Price built £32.35 inc. VAT.

## Cambridge

Price in kit form £14.95 inc. VAT.

Price built £21.55 inc. VAT.

## Features of the Sinclair Cambridge



- Uniquely handy package. 4 1/3" x 2" x 11/16", weight 3 1/2 oz.
- Standard keyboard. All you need for complex calculations.
- Clear-last-entry feature.
- Fully-floating decimal point.
- Algebraic logic.
- Four operators (+, -, ×, ÷), with constant on all four.
- Powerful constant with separate 'K' button.
- Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £15.
- Calculates to 8 significant digits.
- Clear, bright 8-digit display.
- Operates for weeks on four AAA batteries.

To: Sinclair Radionics Ltd,  
 FREEPOST St Ives,  
 Huntingdon, Cambs. PE17 4BR

Please send me

- Sinclair Scientific kit at £19.95
- Sinclair Scientific built at £32.35
- Sinclair Cambridge kit at £14.95
- Sinclair Cambridge built at £21.55

All prices include 8% VAT.

\*I enclose a cheque for £....., made out to Sinclair Radionics Ltd, and crossed.

\*Please debit my \*Barclaycard/ Access account. Account number

--	--	--	--	--	--	--	--	--	--	--	--

\*Delete as required.

Signed \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_



Please print. FREEPOST – no stamp needed.

PW 11/74
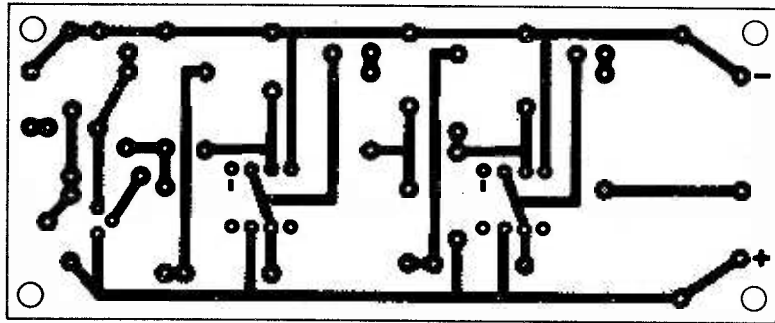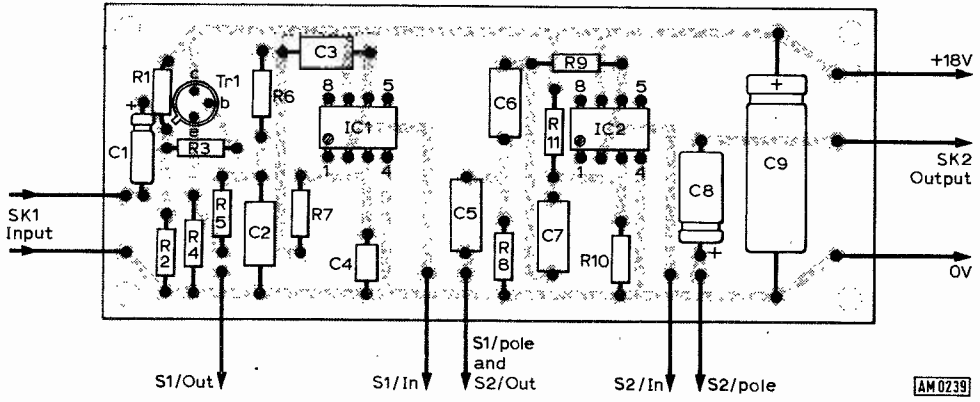
# sinclair

Sinclair Radionics Ltd,  
 FREEPOST St. Ives,  
 Huntingdon, Cambs. PE17 4BR.

Reg. No: 699483 England. VAT Reg. No: 213 8170 88.



Figs. 8 and 9 : Full size diagram of the PCB with component layout. Again, two PCB's are required for a stereo amplifier.

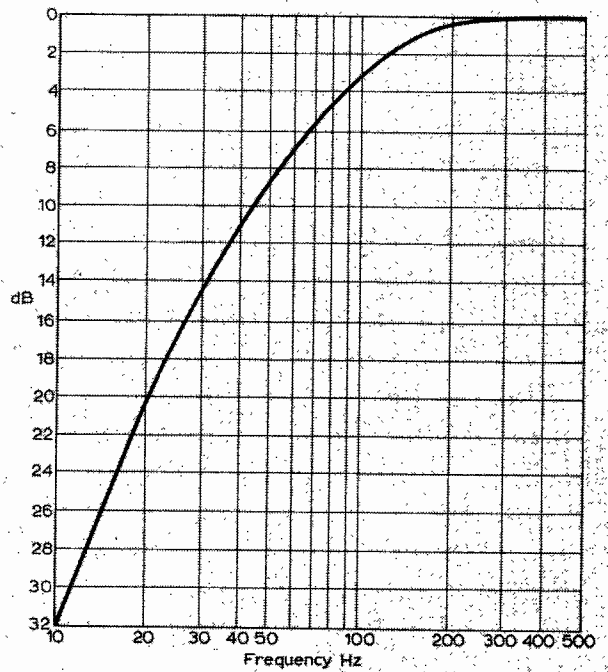
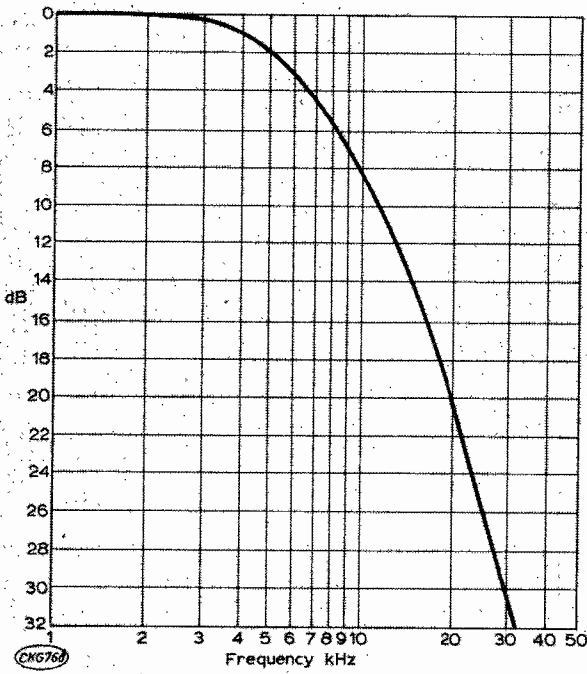


Fig. 10: left, frequency response of the scratch filter. The response of the rumble filter is shown on the right.

—continued from page 629

driven from the scratch filter or directly from Tr1. In the rumble filter R10 and R11 maintain the correct DC conditions for the circuit and their parallel resistance gives the R3 of Fig. 6b. Capacitors C9 and C109 are decoupling components.


## CONSTRUCTION

Construction is straightforward, as shown in Fig. 8 with a separate board, Fig. 9, for each channel. Sockets Sk1 and Sk2 are common to both channels. Components for the second channel are listed as C101, etc, as in normal practice. Although a printed circuit was used in the prototype, a similar layout using LEKTROKIT could be used if required. It is advisable to purchase the filter components before the layout is finalised as capacitor sizes vary and the types used were among the smallest available.

Although the 8 pin DIL versions of the 741 are specified in the article, it is worthwhile noting that the round package versions have the same pin connections and the leads can be spread to fit the printed circuit board if required. No detailed dimensions are given because this will depend on the box used, the size of which is not important.
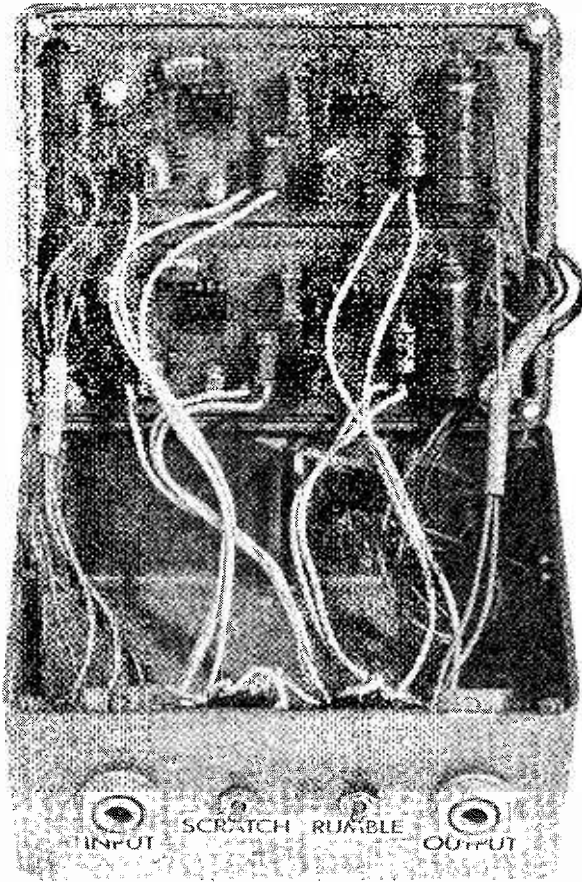
## TESTING

The DC voltages shown on the circuit diagram should be measured for the nominal supply voltage shown. If these DC conditions are correct then an AC signal may be applied to the unit and the overall performance checked. If no test equipment is available for this purpose then a listening test must suffice. The characteristics of the filters are shown in Fig. 10.



The finished Scratch and Rumble filter for a stereo set-up. The input impedance is 15kΩ and the output impedance low.

## ★ components list

### Resistors

R1	R101 47kΩ	R7	R107 10kΩ
R2	R102 47kΩ	R8	R108 6.8kΩ
R3	R103 1kΩ	R9	R109 4.7kΩ
R4	R104 2.2kΩ	R10	R110 56kΩ
R5	R105 10kΩ	R11	R111 47kΩ
R6	R106 10kΩ		

All  $\frac{1}{2}$  or  $\frac{1}{4}$ W 5%

### Capacitors

C1	C101 10μF 16V	C6	C106 0.47μF 5% PC
C2	C102 2200pF 5% PS	C7	C107 0.47μF 5% PC
C3	C103 3300pF 5% PS	C8	C108 20μF
C4	C104 560pF 5% PS	C9	C109 40μF
C5	C105 0.47μF 5% PC		

PS polystyrene    PC polycarbonate

### Semiconductors

Tr1 Tr101 BC109 ICI IC101 SN72741P or similar  
IC2 IC102 SN72741P or similar

### Miscellaneous

S1/S101 and S2/S102, each 2 pole 2 way toggle switch. Sk1/2 stereo jack socket (2). Printed circuit boards. Die cast aluminium box 4½ x 3½ x 2in. or similar. Terminals (2).

**WE SHALL BE GLAD  
TO SEE YOU  
ON  
STAND B12**

**INTERNATIONAL  
AUDIO FESTIVAL & FAIR**  
to be held at **OLYMPIA, London**  
from **28th October to 3rd November**  
1974.

**PW's  
'TELE-TENNIS'  
WILL BE  
IN OPERATION**

**SPECIAL  
PRODUCT  
REPORT**

**HEATHKIT SW-717G**

**MEDIUM  
AND SHORT  
WAVEBANDS RECEIVER**



THIS report applies to the Heathkit SW-717G, the latest model from the SW-717 range of receivers. The SW-717G shortwave receiver covers the medium waveband and three short wavebands. The receiver tunes continuously from 550kHz (550 metres) to 30MHz (10 metres) in four overlapping bands and will receive a.m., c.w. morse code or single sideband (s.s.b.) signals.

The Heathkit SW-717G is an all-semiconductor design with a selected 40673 dual gate MOSFET functioning both as r.f. amplifier-mixer in the front end of the receiver. The 40673 has wide signal handling capabilities together with lower noise. A separate local oscillator stage reduces 'pulling' and improves stability.

Ceramic filters are utilised in the i.f. stages, thus simplifying alignment. The i.f. response and therefore selectivity is optimised by the use of these filters.

Amplified a.g.c. is incorporated, thus yielding excellent control over the gain of the r.f./mixer and i.f. stages. Regeneration is utilised to improve selectivity in the c.w. s.s.b. mode and to a limited extent in the a.m. mode.



The degree of regeneration (and therefore selectivity) may be adjusted by a front panel control. This was found to be extremely useful when receiving 80 metre s.s.b. and c.w. signals.

An automatic noise limiter circuit affords a reduction in the levels of impulse noise interference. The audio stages consist of audio preamplifier and driver, followed by a complementary push-pull output stage (pnp-npn silicon devices) which in turn feeds either an internal loudspeaker or a socket for headphones/external speaker.

A ferrite rod aerial is utilised for medium waveband reception and is automatically selected by the wavechange switch. On short waves there is provision for connecting an external aerial for optimum performance.

Bandspread tuning on all wavebands is an extremely useful tuning aid, especially when searching for those weak DX signals. A tuning meter indicates relative signal strength.

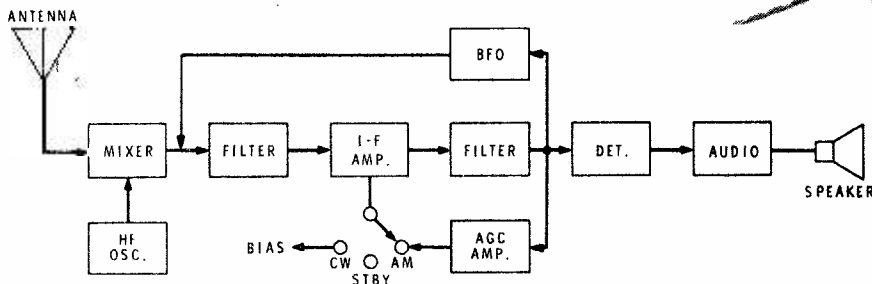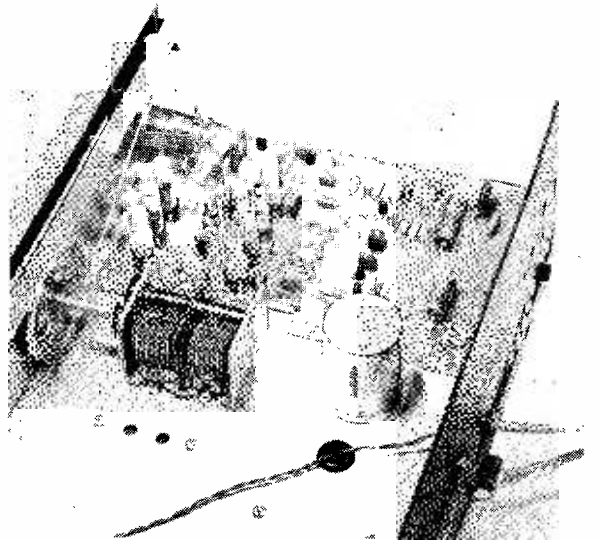The assembly manual for the Heathkit SW-717G is an excellent and informative work. The assembly instructions are clear and concise and the accompanying sketches



The block diagram, left, indicates the function of each stage of the SW-717G. The photograph, above, shows the completed printed circuit board fitted to the chassis.

## MANUFACTURER'S SPECIFICATION

### Frequency coverage:

Band A—550kHz to 1500kHz,  
Band B—1.5MHz to 4.0MHz,  
Band C—4.0MHz to 10.0MHz,  
Band D—10.0MHz to 30.0MHz.

### Sensitivity:

Band A—10 $\mu$ V (ferrite rod aerial)

### S/N + N for 3 $\mu$ V input

Band B 30dB average (h.f. to l.f.)	30dB down
Band C 25dB average (h.f. to l.f.)	24dB down
Band D 15dB average (h.f. to l.f.)	15dB down

### Image average

### Selectivity:

4kHz at 3dB down  
12kHz at 30dB down.

### Meter:

Indicates relative signal strength. **Headphone socket:** low impedance headphones or external loudspeaker (25 $\Omega$ ). **Loudspeaker:** built-in. **Controls:** Volume with on/off switch. **Mode:** (a.m., Standby, c.w./s.s.b.). **BFO, Main Tuning. Bandspread Tuning. ANL (on/off).**

### Transistor complement:


40673 r.f. amplifier and mixer, MP105 local oscillator, 2N5308 i.f. amplifier, 2N5232A i.f. amplifier and a.g.c. amplifier, 2N3393 audio pre-amplifier, X29A829 audio driver, S2090/S2091 audio output stage (complementary pair).

### Power requirements:

Transformer operated, full wave bridge rectifier 120V a.c. or 240V a.c. 50/60Hz.

### Dimensions:

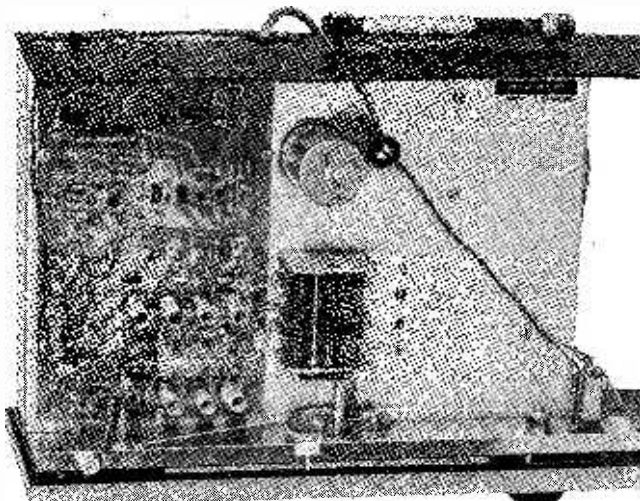14.5in. wide, 5.75in. high, 10in deep. Weight 7lbs.



The ferrite rod aerial for the medium wave band is fitted to the outside of the back of the cabinet, at the top in the photograph.

fed with 75 $\Omega$  coax) the following amateur s.s.b. stations were heard at good strength on the 80M amateur band during July this year, (The reviewers' favourite band). ZL3GS, PY2FOA, ZL4KF, PY2FUS, all at good signal strengths. In addition many stations from the USA and Canada were logged over a week of early morning listening. On the 20M band, most parts of the world were logged including VP8. If one remembers that the majority of amateur band signals emanate from low power transmitters (compared with BC stations) the performance of the SW-717G is indeed impressive.

No problems were encountered during assembly (assembled by the reviewers' young son) and the receiver, after initial tests, worked immediately upon switching on—in fact, before alignment.

The main tuning drive utilises a spring-loaded reduction system. Tuning is positive and there is negligible backlash. Tuning the shortwave bands was a pleasure, especially when using the bandspread control.

The Heathkit SW-717G kit is well engineered, the chassis and other metalwork is first class. A printed circuit board facilitates assembly.

In addition to the assembly manual, a kit builders' guide is included which, amongst many other things, gives comprehensive illustrative details on how to solder!

At £33.50 (including VAT and carriage) the Heathkit SW-717G is extremely good value for money. Its excellent performance and sensitivity surprised your reviewer, who incidentally has been both swl and licensed amateur for a total of 35 years!

An illustrated brochure with complete circuit details is available—upon request from Heathkit. The complete assembly manual is also available. The cost is 50p which is deductible when purchasing the kit.

HEATHKIT (GLOUCESTER) LTD, GLOUCESTER, GL2 6EE, ENGLAND.

detailing step-by-step assembly cannot be faulted. Everything that the newcomer or beginner requires for assembly in easy-to-read stages is there. Alignment, often the bogey of the beginner constructor, is covered in a straightforward manner. Details are given for alignment both *with* and *without* test instruments. As a matter of interest, the reviewers' young son used the '*without instrument*' alignment procedure and on checking with instruments—no extra adjustment was required. Quite remarkable, but after all Heathkit Ltd., have been in this business for a very long time.

A technical consultancy service is operated by Heathkit—queries are answered either by telephone or letter—what more could you ask?

Performance figures do not really convey much to many beginners or newcomers to shortwave listening. What he really wants to know is, how well it works. Well, judge for yourself. In conjunction with a wire aerial (132ft. trap dipole

MAKE A NOTE—NOW ! AT OLYMPIA 28 OCT-3 NOV

## 1974 INTERNATIONAL AUDIO FESTIVAL AND FAIR

Times:—Monday 28 Oct, 12 noon-9 p.m. Tuesday 29 Oct to Saturday 2 Nov, 10 a.m.-9 p.m.

ALSO ! Sunday 3 Nov, 11 a.m.-7 p.m.


PW's STAND IS B12



# PRODUCTION LINES

colin riches

## CASSETTE STORAGE UNIT

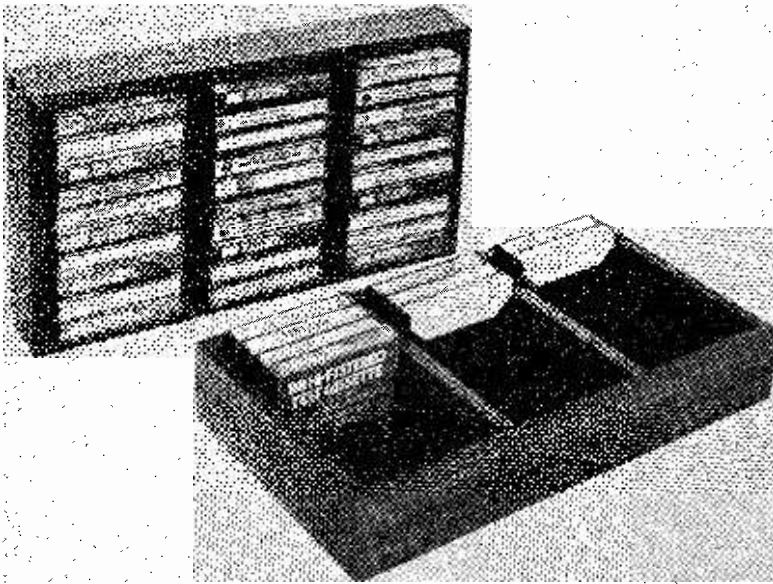

**T**HIS jolly useful piece of furniture—for that is what my wife, Margaret, called it when she saw the lovely teak finish—is something that's been wanted for a long time.

It holds 30 compact cassettes which fit into plastic inserts—thus enabling them to be removed quickly and easily without touching each other.

The rack, made by Bib Limited, measures 15 $\frac{3}{4}$ in wide, 9in high and 2 $\frac{1}{2}$ in deep. It can be used either standing up or laying flat (as the picture shows) and comes complete with four self-adhesive protective base feet.

The price, excluding VAT, is £4.26 and you should see them in most hi-fi and record shops.

If you would like further information on this, or any other accessories, write to Bib for their full-colour catalogue. The address is: *Bib HiFi Accessories Limited, P.O. Box 78, Hemel Hempstead, Herts HP2 7EP.*

## RECHARGEABLE CELLS

**T**HE Ever Ready Co. market a good selection of rechargeable cells. They are nickel cadmium devices and come in a range of sizes and capacities which makes them ideal for driving transistor tape recorders, battery shavers and such like.

The main features of the nickel cadmium electrochemical system are (1) flat voltage curve—the cell voltage being substantially constant throughout the discharge cycle; (2) high rate discharge—the cells are capable of and specially suited to this type of use; (3) overcharge capability—the cells can accept long-term overcharging at prescribed rates; (4) wide temperature range—the cells will operate from  $-30^{\circ}\text{C}$  to  $+50^{\circ}\text{C}$ .

If you would like some more gen and a price list contact *Mr. K. G. Banks, The Ever Ready Co. (Great Britain) Limited, Spa Road, Hockley, Essex SS5 4AH.*


## CURVE TRACER

**W**ITH this device you can check operating parameters of any discrete semiconductor with your oscilloscope.

The IT-1121 curve tracer from Heath is just connected to any scope with a horizontal sensitivity of 0.5V/div and vertical sensitivity of 1V/div.

Devices such as bipolar transistors, diodes, SCR's, triacs and FET's can be inspected or tested. Extra leads are supplied for in-circuit testing or checking large devices.

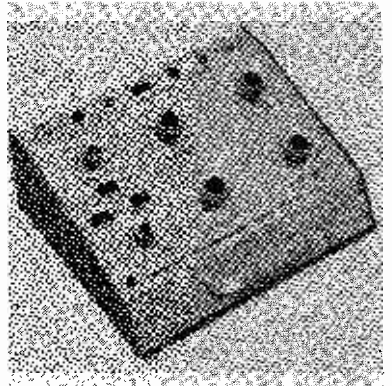With the IT-1121, you can display fundamental parameters like gain (beta) leakage, breakdown voltage, saturation, forward conduction voltage, output admittance, linearity, capacitive effects, temperature effects, etc.



In kit form, the unit costs £52.95 (this includes 8% VAT and delivery). Assembled price is £127.45.

Further gen and free catalogue from *Heath (Gloucester) Ltd., Gloucester GL2 6EE.*


## GRUNDIG CUT PRICES

**G**RUNDIG have cut the prices of two of their most popular car radios. The WK2503 l.w./m.w. push button receiver with tone control now costs £29.16 (rec. retail price including VAT).

The 3-band model WK3001 with manual tuning and push-button tone control now retails at £20.

Grundig tell us that in spite of these price reductions, there are no changes to the two receivers.

# PW TECHNICAL CROSS PUZZLE No. 7

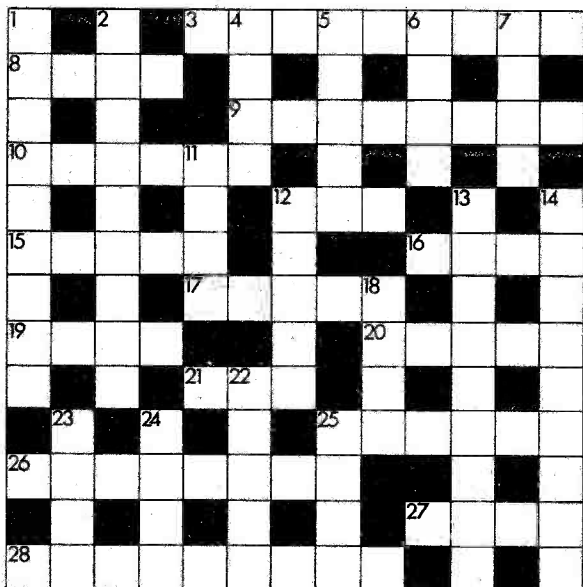

## ACROSS

- 3 A brief farewell to this band? (5, 4)
- 8 Plans to correct Pam's distortion? (4)
- 9 Disc-jockeys in bowlers? (8)
- 10 Has no longer got it taped? (6)
- 12 Group receiver fixed (3)
- 15 Bewilder with a complicated circuit? (5)
- 16 The spiral of electricity charges (4)
- 17 Beams over the television? (5)
- 19 Much of a rectifier from a friend? (4)
- 20 Marine ultrasonics, like Richard said (5)
- 21 Often an extreme state of modulation (Abbrev.)
- 25 One in the eye for the TV screen? (6)
- 26 Manufacturer for BBC's American sound? (8)
- 27 Chief part of a main conductor? (4)
- 28 Singular example of personal reception (9)

## DOWN

- 1 It seems to resist more after induction (9)
- 2 Is it a receiver or some other mechanism? (9)
- 4 Disapproval expressed of surface noise (4)
- 5 It has current for hi-network induction (5)
- 6 Bit of a blow to prepare for 16 Across? (4)
- 7 Love radio shows when she's in them? (4)
- 11 Woolly sound from their ramshackle designs! (4)
- 12 Extra volume instruction finishes employees (5)
- 13 Milkman in electricity storage business? (9)
- 14 Valve charges passed by this device? (9)
- 18 Glass shutter mechanism (4)
- 22 Intuition about hunting a switch? (5)
- 23 Large networks contain hereditary element (4)
- 24 Speed up for such jazz? (4)
- 25 An indication of call-up? (4)

FOR AMUSEMENT ONLY  
ANSWERS NEXT MONTH

# TELEVISION

## IN THE NOVEMBER ISSUE

### BUILD A BLACK-LEVEL CLAMP

Most monochrome receivers use a.c. coupling at some point in the video circuits. The result of this is that the black level shifts as the average picture content changes. In consequence the contrast range is compressed as dark areas become lighter and dark detail is lost. D.C. Restoration can help but the best answer to the problem is to use a driven clamp. The circuit described—with full constructional details—was devised for use in the Thorn 950 Mk. II chassis but should work in almost any monochrome receiver using a valve video output stage. Accurately timed pulses derived from the line output stage are used to drive the clamp.

### RASTER CORRECTION IN 110° COLOUR RECEIVERS

New circuits have had to be devised for pin-cushion distortion correction in the new generation of 110° colour receivers. This means extra knobs for the devoted knob-twiddler to try out. As the methods of correction used are quite novel however it is important to know what the circuitry is doing. The message from Harold Peters in this issue is reassuring however: "don't panic, it's easy!"

### CHANNEL IDENTIFICATION WITH VARICAP TUNERS

One of the problems of the DX-TV enthusiast or those seeking extra channels with a varicap tuner is that no accurate indication of the channel selected is provided. Accurate channel identification in electronically tuned sets can be provided however by means of the simple and inexpensive meter circuit to be described this month.

### PLUS ALL THE REGULAR FEATURES

TO .....  
(Name of Newsagent)

Please reserve/deliver the NOVEMBER issue of  
TELEVISION (25p) and continue every month until  
further notice.

NAME .....

ADDRESS .....

# EXPERIMENTAL WORKSHOP

M. J. HUGHES M.A.

## LEARNING BY PRACTICAL PROJECT STEPS

### PART 12—R C FILTERS

**C**APACITORS behave, to some extent, like resistors in a.c. circuits in that they exhibit a form of resistance to current flow. Unlike a straightforward resistance the effect produced by a capacitor depends on the frequency of the current trying to flow through it. To distinguish between this special sort of resistance and the conventional type—with which we are all very familiar—we call the capacitor's resistance **reactance**. Strictly speaking it should be called **capacitive reactance**.

A capacitor allows high frequency signals to flow through it more easily than low frequency signals therefore we can say that the reactance of a capacitor decreases as frequency increases. The actual value of the capacitor (microfarads or picofarads) also controls the reactance. The higher the capacitance the lower the reactance. The effect of frequencies is superimposed on the relationship between capacitance and reactance hence we can derive a simple formula for calculating the reactance of any capacitor at any frequency.

$$X_c \text{ (capacitive reactance)} = \frac{1}{2\pi fC}$$

where the reactance is in Ohms,  $f$  is in Hz and  $C$  in Farads

Although reactance has units of ohms just like resistors we cannot simply add the reactance of a capacitor to the value of a resistor when they are connected in series because a phenomena known as **phase shift** occurs in such a circuit when a.c. signals flow—we shall be saying more about this next month—therefore we have, again, another simple formula for calculating the nett value of the two in series.

$$Z = \sqrt{R^2 + X_c^2}$$

$Z$  is called **impedance** and again is measured in ohms

So long as we deal with the effective resistance to a.c. of the circuit as a whole in terms of **impedance** we can use values of d.c. resistance or capacitive reactance in voltage divide calculations just as if we were dealing with resistors in d.c.

The only thing to remember is that one set of calculations is only valid for one particular frequency.

The frequency dependence of reactance is very useful to us because it enables us to tailor the frequency response of circuits—we can design and build filters which will pass, or block, signals having preselected frequency ranges. In this part we shall look at just one area where this application is well known—tone controls in audio amplifiers.

If we feed a set of a.c. signals of different frequencies into the circuit of Fig. 82 the reactance of the capacitor decreases as frequencies increase; if this is combined with the total circuit impedance for each frequency we care to consider we can work out what the output voltage would be as a fraction of the input voltage by a simple potential divide calculation.

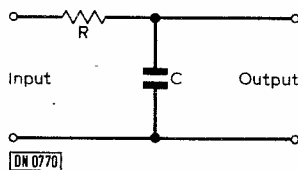


Fig. 82: Basic circuit for a top cut filter.

We would find that for a fixed amplitude input signal the output voltage would fall as the frequency of the signal increased. If you have the inclination you could work this out by taking any pair of values for  $C$  and  $R$  and using the equations we have just mentioned. If you were to do this you would find that a doubling in frequency would halve the output voltage thus we arrive at the statement that an RC filter stage of this type has a falling response to frequency with a factor of 2 (or 6dB) per octave. Because the circuit attenuates high frequencies we call this a **top cut filter** and it is very often used as a "mellowing" circuit for low price record players and radios.

You can see—or rather, listen to—the effect of a circuit based on this principle by making up the project shown in Fig. 83. In this circuit we have an oscillator in the shape of a multivibrator (Tr1 and Tr2) the frequency of which can be adjusted


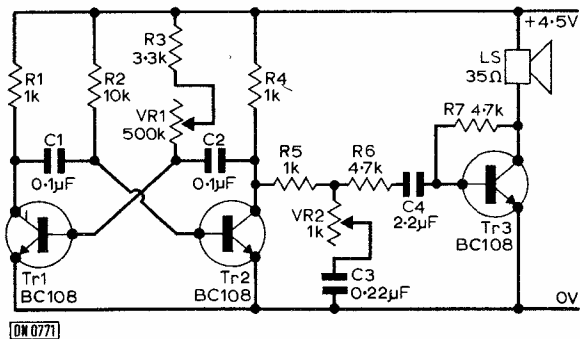


Fig. 83: left, demonstration circuit of a top cut filter. R7 should be selected to produce a quiescent voltage of 2V at the collector of Tr3. Fig. 85: below, shows basic bottom cut network.

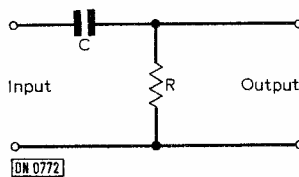

by VR1. We have designed it to run at quite low frequencies but the square wave output is very rich in harmonic content. If this were listened to in its raw state the wave produced would sound rich and throaty—rather like a clarinet. If we remove some of the high frequency harmonics with a filter the sound becomes more mellow with flutelike qualities.

R5 in conjunction with VR2 and C3 form the top cut filter (R6 and C4 are only there to give us effective coupling to the loudspeaker driver stage). VR2 allows us to change the total circuit impedance and thus alter the potential divide effect of C3—this effectively shifts the frequency at which the filter starts to take effect. A high value for VR2 will reduce the top cut action (in simple terms you could imagine it as divorcing the capacitor from the rest of the circuit!). Reducing the value of VR2 to zero gives maximum top cut effect.

Make up the circuit on T Dec as shown in the layout; be careful that the collector of Tr3 is approximately mid rail—to do this you might have to vary the value of R7 slightly. With VR2 set to maximum resistance you should hear the clarinet type of sound already described and reducing it should mellow the signal considerably. Ideally you need as large a loudspeaker as possible to get the best effect. Try different frequency settings of the oscillator and at the same time substitute different values for C3 in the range of 0.01µF to 1.0µF.

While you have the circuit built you can easily investigate the properties of a bottom cut (or bass cut) filter. The basic circuit is shown in Fig. 85. Note that the capacitor and resistor have changed places; at high frequencies the capacitor provides very little series reactance hence attenuation of these frequencies is small but for low frequencies the capacitor increases the circuit's impedance and the potential divide action between the resistor and the impedance is quite significant—hence the low frequencies are attenuated.

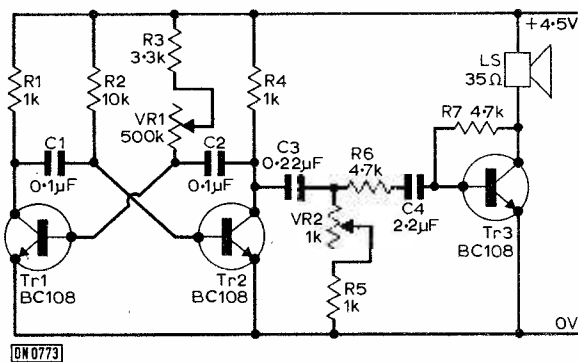


Fig. 86: This circuit of the bottom cut filter is similar to Fig. 83 except that the positions of the components C3 and R5 are interchanged.

By reducing the low frequencies of the square wave we effectively draw more attention to the high harmonics and the sound becomes very raspy or harsh. Control over the degree of filtering is provided by VR2 which is now, effectively, divorcing R5 from the rest of the circuit; the lower the value of VR2 the greater the filtering effect.

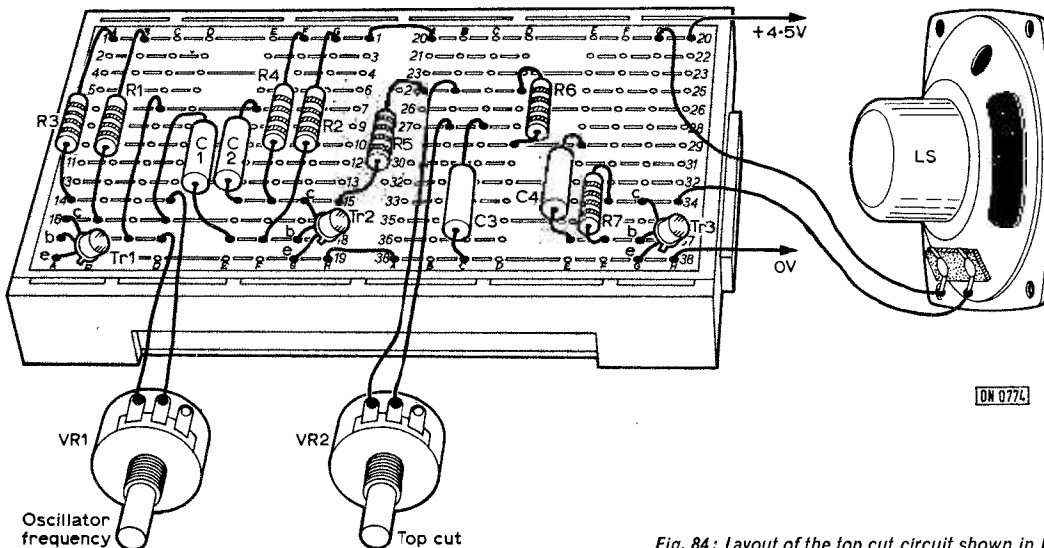


Fig. 84: Layout of the top cut circuit shown in Fig. 83.

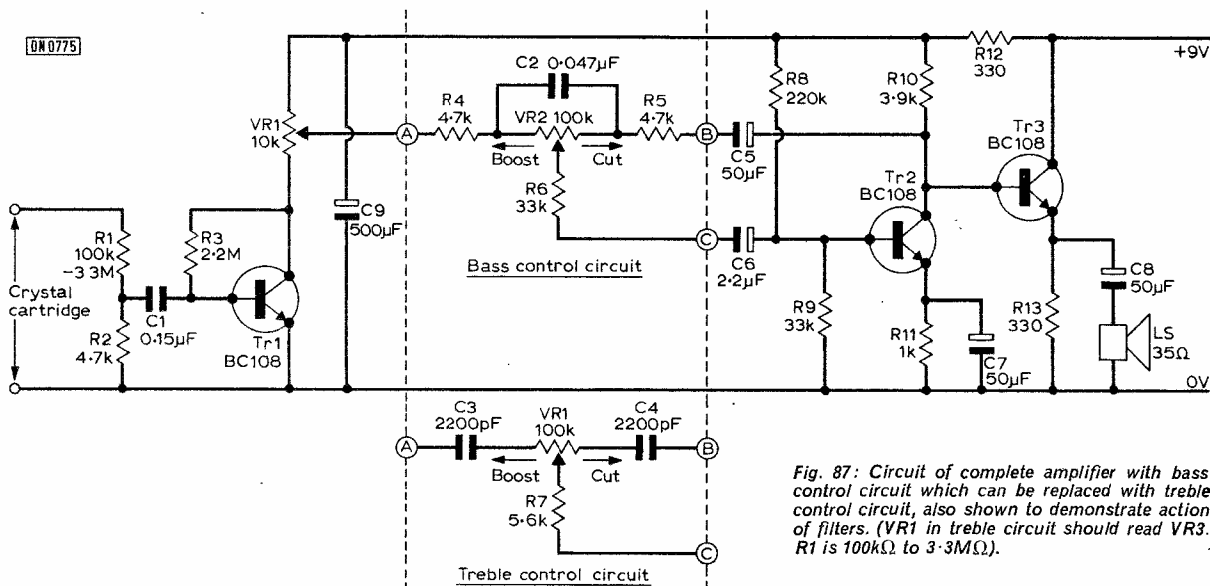


Fig. 87: Circuit of complete amplifier with bass control circuit which can be replaced with treble filter, also shown to demonstrate action of filters. (VR1 in treble circuit should read VR3. R1 is 100kΩ to 3.3MΩ).

Both these types of circuit are used in simple tone control applications and they frequently form part of the tone forming circuits of electronic organs as the experimenter should make very clear. There is a fundamental problem with this type of circuit; it operates by *removing* part of the signal and the signal that is left is always of lower energy than that which went into the filter. Such a filter cannot by any stretch of the imagination be considered as one which, for example, "improves" the bass of an amplifier. In practice, of course, one can cut the treble and then turn up the volume control of the amplifier; this will enhance the bass frequencies but the enhancement is caused mainly by the extra gain from the amplifier. The filters we have just described come into the category of **passive filters**.

In most high-fidelity amplifiers we like to be able to cut or enhance each end of the audio frequency range with single controls. This means that our

filter must be somewhat more complex—we need to turn to **active filters**. These are circuits which will range from giving preferential amplification to certain frequencies through a central "neutral" condition—in which the input signal is unaltered—to a condition which reduces the signal from the range of frequencies in question.

A demonstration circuit incorporating such a bass filter is shown in Fig. 87. This circuit is for a very simple record player amplifier; the circuitry around Tr1 and Tr3 has already been described earlier in the series. The active filter is centred on Tr2. The values of R4, R5, C2 and VR2 have been carefully selected so that when VR2 is set in its mid position the gain of Tr2 stage is approximately unity at a frequency of 1 kHz.

The wiper of VR2 receives two signals; one is the direct input signal coming through R4 and the other is a negative feedback signal from R5. When the

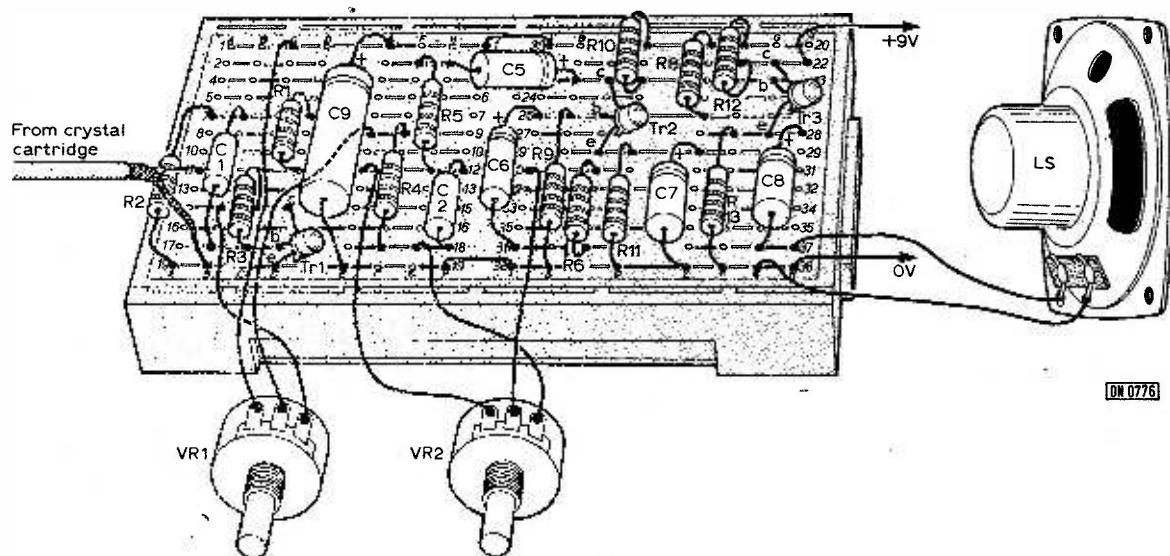


Fig. 88: Layout of the amplifier shown in Fig. 87 with the bass control circuit components inserted.



wiper is at the left hand end of its track (in the boost position) the wiper sees the input signal unmodified by any reactive elements but C2 feeds back high frequency signals from the collector of Tr2. These signals are out of phase with the input and effectively reduce the amplitude of high frequency signals at the wiper. Because we have removed the series effect of VR2 to the input signal its overall amplitude will be larger and this fact in conjunction with the attenuation of high frequencies provides a bass boost. When the wiper is at the right hand end of its track C2 provides a reactive path for the input signal and will, of course, pass high frequency signals preferentially. By cutting out the effect of VR2 on the feedback signal the overall negative feedback is considerably increased and the nett effect is a lowering of the stage gain to low frequencies—in other words the bass will be cut.

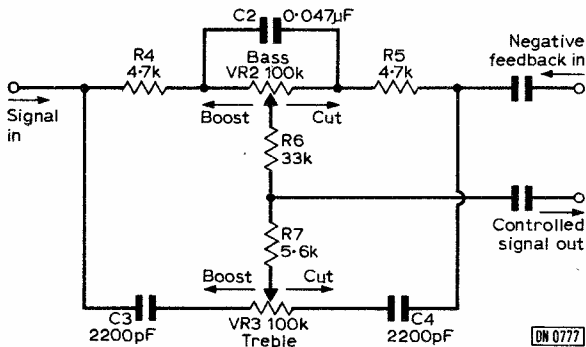


Fig. 89: A combined feedback tone control circuit designed by Baxendall, frequently found in audio amplifiers.

By connecting a crystal cartridge to the input (selecting R1 to prevent overload distortion) you should be able to hear the effect of this circuit quite clearly, if a reasonably good loudspeaker is used.

You can, at the same time, experiment with a treble boost/cut circuit—also shown in Fig. 87. The extra network simply substitutes for the circuit between the dotted lines at connections A B and C. Again the gain of the stage at 1kHz will be about unity when VR3 is set mid way. When the wiper is at the left hand end C3 passes high frequencies and the negative feedback, overall, is low thus giving a boost to high frequencies; when it is at the right hand end the extra series resistance of VR3 reduces the input signal and the negative feedback of high frequencies through C4 is also increased. This gives rise to treble cut.

In practice these two circuits would be combined as we have shown in Fig. 89 providing the amplifier user with virtually independent control of both the low and high frequency ends of the audio spectrum with the centre frequency (1kHz) unaffected. Such a network is sometimes named after its original designer—Baxendall. You might like to try building the complete network on a piece of Veroboard together with Tr2 and its bias components; the complete stage should be capable of insertion in almost any type of amplifier at the volume control stage, if you wish to improve the tone control arrangements.

To be continued

socket on the back of the case. When this is done use Araldite to hold the twisted wires together.

Now connect a short lead between the case and the 0V rail of Board E, as shown in Part 2. This must be the **only** link to chassis in the whole system. Under **no circumstances** should the metal case of the modulator be allowed to come into electrical contact with the main system's chassis—this will put a dead short across the power supply.

The prototype has proved to be quite robust, having stood up to a lot of travelling and to use at an exhibition. Little adjustment has been needed apart from the initial setting up described in the above paragraphs. However, should it be necessary to carry out adjustments the design allows easy access to all the preset potentiometers. When doing this be careful not to catch the back of your hand on the pins of the mains switch which will, of course, be live.

### Corrections to Overall components list

(page 235 of July issue)

1. Polystyrene capacitor quantities:  
1000pF should read 2.  
2200pF should read 5.  
Diode types:
2. 1N4004 should read 1N4001, although either type is satisfactory in this circuit.

### SANDOWN PART 2—continued from page 614

between the earth planes on the top and bottom of the board by passing a piece of wire through the hole near to the connecting pad marked 'SW' and soldering it to both sides of the board.

## WIRING UP

Connect wires to the leadthrough insulators on the side of the box and route them in a cable form as shown in Fig. 6. Table 1 shows the point on the board to which each wire should be connected. Leave enough wire to allow the board to be removed from the box without disconnecting the cable. If any meters or switched facilities are omitted the appropriate wires may be left out and the necessary connections made directly on the board. Re-connect the wires from the transformer, including the temporary earth lead from the ground plane to the earth tag, in readiness for testing.

Next month we will give constructional details for the front panel, together with final test and alignment procedures.

### EDITORIAL VACANCY ON PW

PW invites applications, in writing, for the position of Technical Sub-Editor on the magazine. Previous experience of editing technical material, correcting proofs and article make-up highly desirable. A general knowledge of electronics should be coupled with an interest in the problems of the home-constructor. Applications should be addressed to the Editor.

# HOTLINES

ON RECENT DEVELOPMENTS

## VERY FISHY

MANY moons ago (1972 to be precise) RCA announced details of an improved type of TV camera tube—a silicon intensifier type. Having wondered ever since about the applications (other than military) I checked. Would you believe it, one application is the detection of fish from a flying aircraft and at night time too!

Apparently sea plankton glows very slightly and this is detectable by the silicon intensifier. The fish disturb the plankton when they swim near it and thus the fish can be seen from an aircraft flying at some thousands of feet. Before anyone thinks this a little crude, I should add that, so sensitive are these tubes, the observers can even tell the actual species of fish involved.

## SO SARIE!

But it's not only American companies which design and manufacture interesting devices. An example of something from England is Sarie—the brain child of EMI Electronics Ltd. This simple name hides a most ingenious semi-automatic radar identification equipment.

Think of a foreign ship, steaming along and watching British naval exercises. The foreign ship will be using its radar to keep an eye on the whole operation. But such an observer can be disguised and so can its radar equipment. Such disguises don't fool Sarie. She is a passive receiving system which looks round for any signals. Once she spots a radar signal she immediately displays this on a digital/alpha numeric LED readout. Radars are known and classified by characteristics—size of the pulse, width of pulse, duration, frequency etc etc.

The previous approach was to first pick up the radar signal, then examine it on an oscilloscope and try to measure the characteristics. Having eventually done all that, it was necessary to hunt through a huge

list of radars trying to match up the characteristics and thus, finally, identify the radar.

This can now be done by Sarie—in a few seconds. The signal received (on standard receiving equipment) is simply fed into Sarie. She immediately shows all radars in her memory which have characteristics like those being received. These signals are arranged in order of likelihood. Further information is then derived from the signal and Sarie will eliminate the "probables" leaving the identified radar on the screen plus all the information about its characteristics. The significance of this can be appreciated already. However, whereas at sea during an exercise, the identification of a foreign radar can be a casual affair, think of a missile. To spend several minutes hunting through lists could be the last hunt you ever did! Sarie holds a unique place in U.K. electronics—she allows the listener to be listened to.

## MORE CCDS

Charge coupled devices (CCDS) showed great promise as solid state television camera tubes. Some systems have already been marketed which employ CCD sensors. Fairchild, for example, have a television camera about the size of a packet of 20 cigarettes. Versatility of the CCD technique is now being realised in other areas and perhaps the most prominent is that of using it in a computer memory. Various systems already exist—tape, magnetic disc and drums etc. Drums are popular and can store large amounts of information. Now, the memory scene is being upset, because the CCD memory seems to offer a quite fantastic edge on anything else—so far! Comparing CCD memories with drums illustrates the point. An American company is currently working on a CCD memory which can store some eight million bits of information. To store the same amount of information a drum would

need to be bigger and heavier. The CCD device weighs only one eighth, measures only one tenth and consumes only one sixtieth of the power which a comparable drum system would use. Remember too that the CCD device is solid state, no moving parts, no maintenance. The desk top computer will soon be old hat and we will end up with wrist watch computers if things carry on at this pace. Perhaps those 007 gimmicks aren't so far fetched after all.

## SNAP

The photographic fraternity among us may be heading for an era where no film exists—no negatives. The hint is that amateur photographers of the future will sport a video camera recording direct on to magnetic tape. The age of hand-held consumer video cameras is about to dawn and already the electronics companies are gearing up to provide all the necessary equipment. The latest item of interest comes from BASF who has developed a cassette system using magnetic tapes with a playback time of 90 minutes. The tape has 28 tracks and reverses automatically in a fraction of a second when the end of one track is reached. Rumours tell of a two-hour tape under development. The interesting thing about the BASF approach is that it is a major departure from the conventional rotating heads along angled tracks. The BASF system uses the reverse; longitudinal tracks and fixed head.

The electronics for the consumer video camera is an expensive affair and has to be very much cheaper before it becomes a marketable proposition. However, with the development of CCDs (those devices again) a solid-state cine camera could well be just round the corner.

*Ginsberg*

# NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

**EXPRESS POSTAGE**

5p for 1 Valve.  
Each additional Valve add 2p.

DM70	0-53	EP80	0-48	PC86	0-75	PL84	0-68	30CL15/			
DY51	0-85	EP83	1-03	PC88	0-75	PL84	0-88	PCF800	1-05		
DY86/7	0-45	EP85	0-43	PC900	0-58	PL606	1-05	30C17			
DY86/2	0-45	EP86	0-90	PC88	0-52	PL509	1-55	30C18/			
EA80	1-00	EP89	0-81	PC88	0-52	PL802	0-98	PCF805	0-90		
EB91	0-85	EP91	1-30	PC88	0-52	PL802	0-98	30F5/EP818			
EC81	0-75	EP92	1-40	PCF201	0-87	U26	1-00	30FL1/			
EF80	0-60	EP95	1-25	PCF800	0-65	U191	1-00	PCB800	0-75		
EF83	0-68	EP182	0-60	PCF86	0-65	U193	0-85	30FL2	0-75		
EF99	0-58	EP184	0-60	PCF200	0-85	U8C81	0-70	30FL12	1-05		
EC86	0-75	EH90	0-56	PCF801	0-85	U8C81	0-70	30FL14	0-85		
EC88	0-77	EL34	0-92	PCF801	0-85	U8C81	0-70	30L11/PC84			
EC89	0-75	EL36	1-05	PCF801	0-85	U8C81	0-70	30L15/PC805			
EC89/2	0-45	EL81	0-90	PCF806	0-65	U8C81	0-70	30L17	0-90		
EC89/3	0-45	EL84	0-47	PCH200	0-88	U8C81	0-70	30P4MR	1-30		
EC89/4	0-55	EL85	0-55	PCH202	0-88	U8C81	0-70	30P12/PC801			
EC89/5	0-55	EL86	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/6	0-55	EL87	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/7	0-55	EL88	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/8	0-55	EL89	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/9	0-55	EL90	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/10	0-55	EL91	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/11	0-55	EL92	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/12	0-55	EL93	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/13	0-55	EL94	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/14	0-55	EL95	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/15	0-55	EL96	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/16	0-55	EL97	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/17	0-55	EL98	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/18	0-55	EL99	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/19	0-55	EL00	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/20	0-55	EL01	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/21	0-55	EL02	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/22	0-55	EL03	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/23	0-55	EL04	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/24	0-55	EL05	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/25	0-55	EL06	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/26	0-55	EL07	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/27	0-55	EL08	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/28	0-55	EL09	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/29	0-55	EL10	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/30	0-55	EL11	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/31	0-55	EL12	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			
EC89/100	0-55	EL81	0-55	PCH202	0-88	U8C81	0-70	30P19/PC802			

# NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

AZ1	0-75	EP39	1-20	N78	3-50	PY500	1-10	6P28	0-
-----	------	------	------	-----	------	-------	------	------	----

AMBIT FOR CLOCK CHIPS: CT 7001 £10.00

*Ambit the PLL people:*

NE560B £3.19  
 NE561B £3.19  
 NE562B £3.19  
 NE565A £2.75  
 NE566V £2.55  
 NE567V £2.75

*Ambit for radio ICs:*

CA3123E £1.40  
 CA3089E £1.90  
 TBA651 £1.82  
 uA753 £0.99

*Ambit for displays:*

(All LED 7 seg types)

SLA1 .33" red £1.50  
 SLA11 .33" green £1.50  
 SLA21 .33" yellow £1.50  
 SLA7 .33" red £1.25  
 plus many others

*Ambit for lots more besides*

Our catalogue is gaining momentum, and contains much of interest to any technologically minded persons - we have devices for most occasions.

All our devices are BRAND NEW GUARANTEED TYPES available in OEM quantities. We do not sell any seconds. Catalogue 25p - now refundable with £5+ worth of purchases. Don't forget that we are here to talk about applications - and have a wealth of experience in all that we sell. (Plus several hundredweight of data at your disposal - through our datacopy service.)

All prices exclude VAT. Post and packing 15p.

**ambit**  
 international

37 HIGH STREET  
 BRENTWOOD  
 ESSEX CM14 4RH  
 Tel: (0277) 216029  
 Telex: 995194

*Ambit for TOKO COILS*  
 CFT 455/470 B/C 0.45  
 CFU 470C 0.50  
 MFH 41/71T 1.35  
 CFS10.7 0.40  
 KACSK586HM 0.30  
 many others available

*Ambit for Larsholt and TOKO FM modules:*

FM Tunerset - the high quality RF/IF module with features of £60 tuners £20.00  
 TOKO EF5603 ultra quality varicap head £8.40

*Ambit for TTL:*

7400 19p 7402 19p 7413 44p  
 7446 £1.50 7447 £1.45  
 7448 £1.50 7490 65p  
 74121 55p 74192 £1.45

# Tele-Tennis

As described in Practical Wireless

Play the game that's sweeping the nation. You've seen it in pubs, clubs and arcades—now you can play it in the comfort of your own home.


Plugs into the aerial of your V.H.F. 625 Black & White or Colour television. No internal connections to your T.V. set. Does not interfere with other T.V. programmes. Built from 6 neat sub-sections, purchase a complete kit or sub-section at a time.

All parts available separately including P. C. boards, case and ready punched and slotted fascia panel.

S.A.E. for full details.

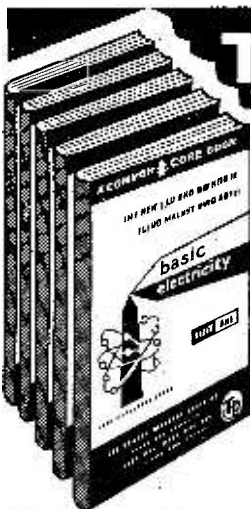**DABAR ELECTRONIC PRODUCTS**

98 LICHFIELD STREET  
 WALSALL, Staffs WS1 1UZ



# The Pictorial Method

## BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

### WHAT READERS SAY

These books make interesting reading of a complicated subject.

*A.V. Andover*

I am delighted with these marvellous manuals, they are so easy to follow: well done.

*W.A. Cheltenham*

These manuals are extremely clear and easy to understand.

*L.L. Pontefract*

The Basic Electricity volumes were readily understood by my 13 year old son.

*J.B. Wolverhampton*

**YOUR 100% GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....


BASIC ELECTRICITY 5 parts £5.30   
 BASIC ELECTRONICS 6 parts £6.40   
 BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.

**YOUR 100% GUARANTEE.** If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME .....  
 BLOCK LETTERS  
 FULL POSTAL.....  
 ADDRESS .....

**POST NOW FOR THIS OFFER!**

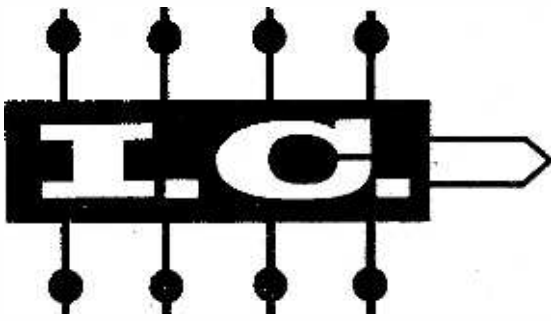

# OF THE MONTH

## Number 48 National Semicon LM1820N AM Superhet

**I**NTEGRATED circuits are becoming much more widely used in all types of radio receiver. As experience is gained by the collaboration of the semiconductor and receiver manufacturers, the devices produced become more and more complex internally as it becomes possible to incorporate more functions into a single device. At first sight one might expect that such ICs would be of use mainly to the receiver manufacturer rather than to the

amateur enthusiast. However, the complex internal circuitry allows the use of simplified external circuits, which is very suitable for the amateur constructor!

Manufacturers design devices primarily for the high volume user but it is very pleasing to note that the devices are now being made available to the amateur constructor almost as soon as they reach the large manufacturer.

This month's device is the National Semiconductor's LM1820N superhet AM radio receiver which incorporates all the active devices required between the aerial and the audio detector diode. It can be used in receivers up to about 30MHz.

The 14 pin dual-in-line device contains two amplifiers, one as an RF stage and one as an IF amplifier, a mixer-oscillator, an AGC detector and a zener diode voltage regulator. Most of the external components used consist of tuned circuits, the selectivity depending entirely on these circuits and not on the IC itself. In addition, a detector circuit and an audio amplifier are required; an IC audio amplifier will normally be employed so that the whole receiver is as compact as possible.

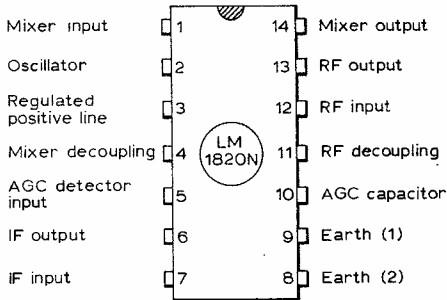


Fig. 1: Pin connections for the LM1820N.

Fig. 2: below, circuit for receiver using ganged permeability tuning.

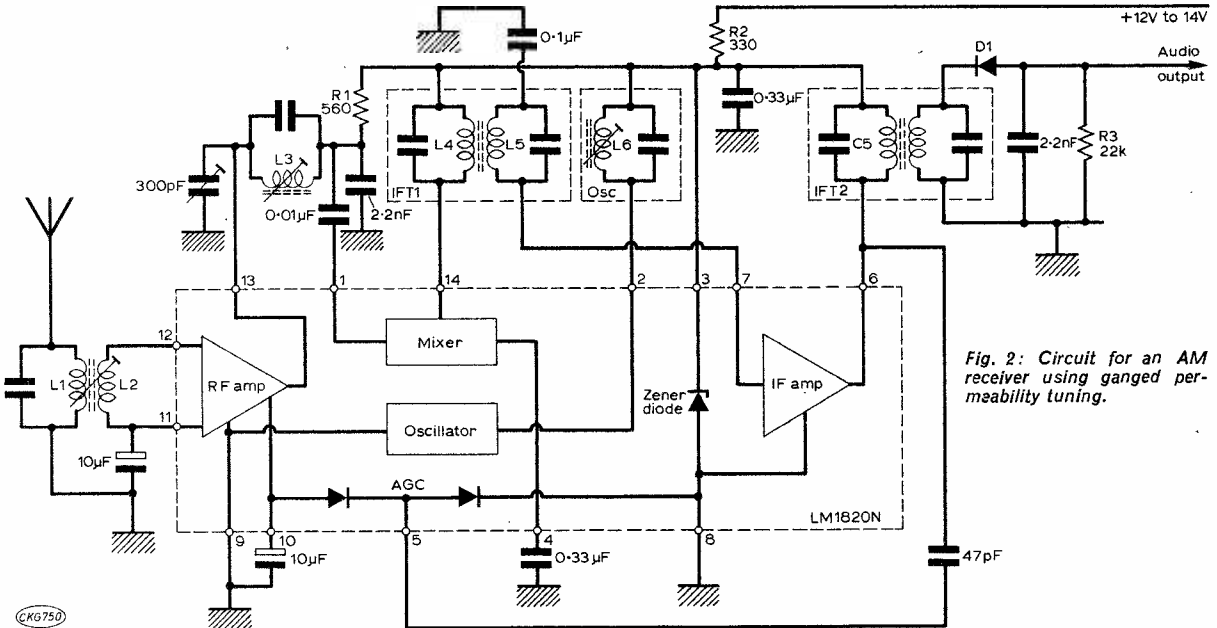


Fig. 2: Circuit for an AM receiver using ganged permeability tuning.



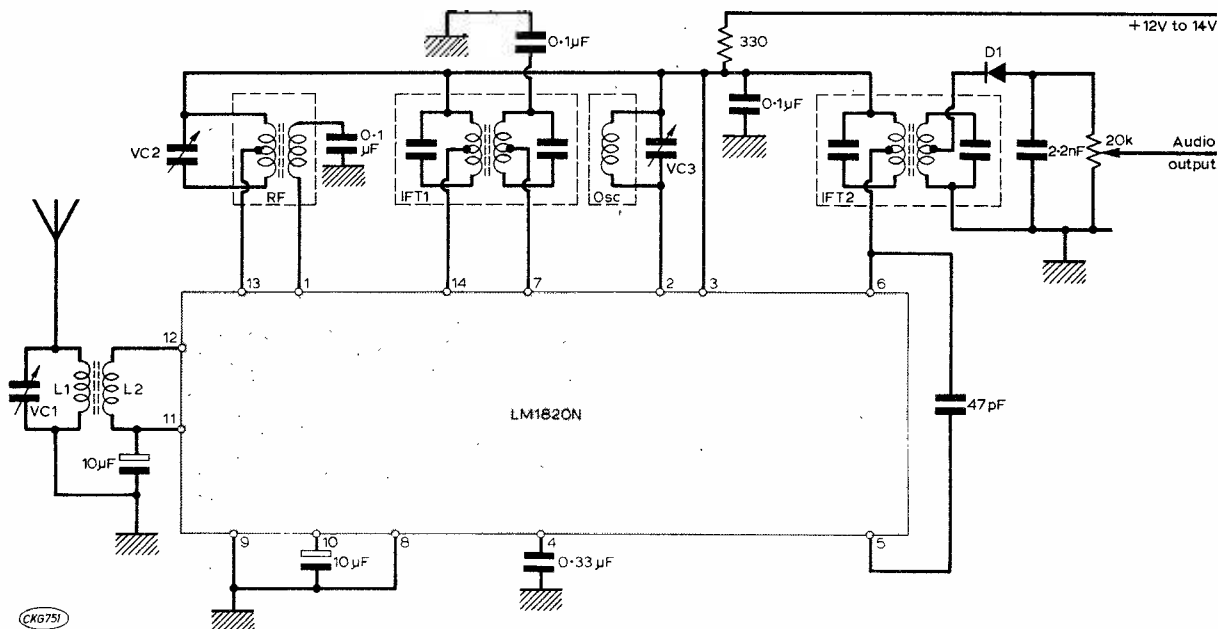


Fig. 3: Receiver with variable capacity tuning, VC1/2/3 being ganged.

## CIRCUITS

The pin connections of the LM1820N are shown in Fig. 1. A typical receiver circuit (excluding the audio amplifier) is shown in Fig. 2 together with the internal circuitry of the LM1820N in the form of a block diagram. It can be seen that the inputs and outputs of the RF and IF amplifier stages are brought out to separate pins. This improves the versatility of the device, since one could, for example, omit the receiver RF stage and use the amplifier for another purpose.

The circuit of Fig. 2 is designed for permeability tuning. That is, the iron dust cores of the aerial tuned circuit L1, the RF tuned circuit L3 and the oscillator tuned circuit L6 move simultaneously into or out of the three coils to tune the receiver.

The component values shown are the ones tried by the writer, since no values are shown on the receiver circuit in the manufacturer's data sheet. For simplicity only one waveband is shown in Fig. 2, but it is not difficult to employ a number of switched coils for L1, L2, L3 and L6 to provide a number of switched wave bands.

## POWER SUPPLY

The absolute maximum supply line voltage is 16V, but it is wise to regard the circuit design maximum voltage as 14V so as to allow a reasonable margin of safety. An internal zener diode is connected between pins 3 and 8 so it is important to note that a resistor must be connected between the positive supply line and pin 3 or the supply voltage will be connected directly across the zener. Unlike most ICs there is no direct connection between the receiver positive line and any pin of the LM1820N.

The zener diode stabilises the pin 3 voltage at about 7.1V. The total supply current required is about 18mA and it follows that a resistor R2 of about 330Ω should be connected between pin 3 and the receiver positive supply line for typical supply voltages of about 12 to 14V. The device will, in fact, function

when the supply voltage is below the zener voltage. The maximum permissible current into pin 3 is 35mA and the maximum dissipation at temperatures up to 25°C is 850mW.

The output of the RF amplifier stage at pin 13 is connected internally to the collector of an npn transistor. The current required by this transistor passes through the resistor R1 and L3 in the circuit of Fig. 2. The mixer output (pin 14) is also connected to the collector of an internal npn transistor, obtaining its current through the primary of IFT1.

The steady component of the voltage at pin 2 should be equal to the potential at pin 3, accomplished by connecting a tuned circuit between the pins. This circuit resonates at the oscillator frequency.

The output of the mixer stage at pin 14 feeds IFT1 and the signal from this is fed into the IF amplifier through pin 7. The output from this amplifier at pin 6 is fed into IFT2. The secondary of the transformer feeds the detector diode D1 which provides the audio output. R3 may be replaced with a 20kΩ volume control.

The IF output from pin 6 is fed to the AGC input pin 5. The two internal diodes act as a peak-to-peak detector. The resulting AGC control voltage is smoothed at pin 10 and provides a suitable time constant in controlling the gain of the RF stage.

## VARIABLE CAPACITY TUNING

The amateur constructor may find it easier to use the LM1820N in the type of circuit shown in Fig. 3 in which tuning is carried out by means of a three-gang variable capacitor, VC1, VC2 and VC3. The RF coil L3 is tapped which leads to a simpler and more efficient circuit. (The coil L3 of Fig. 2 was not tapped because this can cause problems with permeability tuning.) One could also consider the possibility of using semiconductor variable capacitance diodes for tuning purposes.

—continued on page 650

# Marshall's

A. Marshall & Son (London) Limited Dept. PW  
42 Cricklewood Broadway London NW2 3HD Tel: 01-452 0161  
& 85 West Regent Street Glasgow G2 2QD Tel: 041-332 4133

**Everything you need is in our new catalogue available now price 20p**

Trade and export enquiries welcome

## SPECIAL TELE TENNIS KITS

We are now able to offer at special prices all the components listed in the July 1974 Practical Wireless for the Tele Tennis Project. As per parts list we can supply:—Resistor packs £1 + P & P 20p. Potentiometer packs £1.25 + P & P 20p. Capacitor packs £3.10 + P & P 20p. Semiconductor packs £14.50 + P & P 20p. IC Holders £4.50 + P & P 20p. Transformer £1.15 + P & P 20p. We offer a still further reduction in price with all packs purchased together—£23.50 + P & P 30p.

Type	Price	Type	Price	Type	Price	Type	Price
SN7400	16p	SN7437	35p	SN7483	£1.20	SN74154	£1.66
SN7401	16p	SN7438	35p	SN7484	95p	SN74155	£1.55
SN7401AN	38p	SN7440	16p	SN7485	£1.58	SN74157	£1.09
SN7402	16p	SN7441	85p	SN7486	45p	SN74160	£1.58
SN7403	16p	SN7442	85p	SN7490	65p	SN74161	£1.58
SN7404	24p	SN7445	£1.59	SN7491	£1.10	SN74162	£1.58
SN7405	24p	SN7446	£2.00	SN7492	75p	SN74164	£2.01
SN7406	45p	SN7447	£1.30	SN7493	65p	SN74165	£2.01
SN7407	45p	SN7448	£1.50	SN7494	85p	SN74167	£4.10
SN7408	25p	SN7450	16p	SN7495	80p	SN74174	£1.80
SN7409	33p	SN7451	16p	SN7496	£1.00	SN74175	£1.29
SN7410	16p	SN7453	16p	SN7497	£2.16	SN74176	£1.74
SN7411	25p	SN7454	16p	SN74107	43p	SN74180	£1.44
SN7412	28p	SN7460	16p	SN74118	£1.00	SN74181	£5.18
SN7413	50p	SN7470	30p	SN74119	£1.92	SN74190	£1.95
SN7416	45p	SN7472	38p	SN74121	57p	SN74191	£1.95
SN7417	30p	SN7473	44p	SN74122	80p	SN74192	£2.05
SN7420	30p	SN7474	48p	SN74123	72p	SN74193	£2.30
SN7423	37p	SN7475	59p	SN74141	£1.00	SN74196	£1.58
SN7425	37p	SN7476	45p	SN74145	£1.44	SN74197	£1.58
SN7427	45p	SN7480	75p	SN74150	£1.44	SN74198	£3.16
SN7430	16p	SN7481	£1.25	SN74151	£1.10	SN74199	£2.88
SN7432	45p	SN7482	87p	SN74153	£1.09		

**Our new Glasgow shop is now open**  
Prices correct at August 1974, but all exclusive of V.A.T.  
Post and Package 20p postage and package charges

## Popular Semi-conductors

2N696	22p	2N3707	13p	AD142	50p	BC309	10p	LM709	48p
2N697	16p	2N3708	70p	AD143	45p	BC237	21p	TO 99	38p
2N698	40p	2N3715	£1.50	AD161	45p	BC238	19p	80IL	35p
2N1302	45p	2N3716	£1.80	AD162	45p	BCV770	17p	14DIL	35p
2N1309	19p	2N3771	£2.20	AD161	pr	BCV71	22p	LM723C	90p
2N1304	16p	2N3772	£1.80	AD162	pr	BCV72	13p	SN74193	£2.30
2N1305	24p	2N3773	£2.65	AF109R	40p	BD123	32p	TO 99	40p
2N1306	31p	2N3819	37p	AF115	24p	BD131	40p	8DIL	40p
2N1307	22p	2N3820	38p	AF124	30p	BD132	50p	14DIL	14p
2N1308	25p	2N3823	£1.42	AF125	30p	BD135	42p	LM747	£1.00
2N1309	36p	2N3904	27p	AF126	28p	BD136	49p	LM7805	£2.00
2N1671	£1.44	2N3905	45p	AF127	28p	BD137	55p	MC1310	£2.92
2N1671A	£1.54	2N4036	63p	AF139	39p	BD138	63p	MJ480	90p
2N1671B	£1.72	2N4037	42p	AF178	55p	BD139	71p	MJ481	£1.14
2N1671C	£4.32	2N4126	20p	AF179	65p	BD140	87p	MJ490	98p
2N2102	50p	2N4289	34p	AF180	58p	BF115	25p	MJ491	£1.38
2N2147	78p	2N4921	73p	AF239	51p	BF116	23p	MJE340	45p
2N2148	94p	2N4923	83p	AF240	72p	BF117	43p	MJE355	£1.12
2N2160	60p	2N5190	92p	AF279	54p	BF154	16p	MJE3955	68p
2N2218A	22p	2N5191	95p	AF280	54p	BF163	32p	NE555V	70p
2N2219	24p	2N5192	£1.24	BC107	16p	BF180	35p	OC28	76p
2N2219A	26p	2N5192	£1.46	BC108	15p	BF181	34p	OC71	12p
2N2221	18p	2N5195	£1.46	BC109	19p	BF184	30p	OC72	13p
2N2221A	21p	2N5457	49p	BC147	12p	BF184	12p	SC35D	£1.68
2N2222	20p	2N5458	45p	BC148	13p	BF195	12p	SC36D	£1.46
2N2222A	25p	2N5459	49p	BC149	13p	BF196	13p	SC40D	£1.89
2N2646	55p	40361	49p	BC167B	13p	BF197	15p	SC41D	£1.32
2N2904	22p	40362	48p	BC168B	13p	BF198	18p	SC45D	£1.89
2N2904A	24p	40363	88p	BC169B	11p	BF200	40p	SC46D	£1.96
2N2905	24p	40406	44p	BC169C	13p	BF238	22p	SC50D	£2.60
2N2905A	26p	40407	33p	BC182	12p	BF239	22p	SC51D	£2.39
2N2906	19p	40408	50p	BC182L	12p	BFX30	30p	SLA14A	£1.80
2N2906A	21p	40409	52p	BC183	09p	BFX84	24p	TAA263	£1.00
2N2907	28p	40410	52p	BC183L	09p	BFX85	24p	TBA800	£1.50
2N2907A	24p	40411	25p	BC184	11p	BFX87	30p	TBA910	£1.50
2N2926	11p	40602	46p	BC184L	11p	BFX88	28p	TIP29A	49p
2N3053	32p	40604	56p	BC121K	10p	BFX89	25p	TIP30A	58p
2N3054	60p	40669	1.00	BC212L	16p	BFY19	62p	TIP31A	62p
2N3055	75p	AC117	20p	BC214L	16p	BFY51	23p	TIP328	£1.01
2N3441	97p	AC126	20p	BC237	09p	BFY52	21p	TIP33A	£1.81
2N3442	£1.69	AC127	20p	BC238	09p	BFY59	60p	TIP34A	£1.51
2N3415	10p	AC128	20p	BC239	09p	BRY30	48p	TIP35A	£2.90
2N3416	15p	AC151V	25p	BC257	09p	CI060	65p	TIP36A	£3.70
2N3417	21p	AC152V	17p	BC258	09p	CA3020A	1.80	TIP42A	90p
2N3702	11p	AC153K	25p	BC259	13p	CA3046	70p	TIP2995	93p
2N3703	12p	AC176	18p	BC301	£2.12	CA3048	£2.11	TIP3055	60p
2N3704	14p	AC176K	40p	BC301	34p	CA3089E	£1.96	ZTX300	12p
2N3705	12p	AC187K	23p	BC307	10p	CA3090E4	23p	ZTX300	20p
2N3706	9p	AC188K	34p	BC308	09p	LM301A	46p	ZTX500	15p



## "I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

# Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby! Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

**No soldering—yet you learn faster than you ever dreamed possible.**

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

**So fast, so easy, this personalised course will teach you even if you don't know a thing today!**

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

**Send now for FREE 76 page book—see how easy it is—read what others say!**

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

**POST TODAY FOR FREE BOOK**

To: ALDERMASTON COLLEGE  
DEPT. BPW 85  
READING RG7 4PF

QH BPW85

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

**no extras**  
all prices inc VAT  
FREE delivery

BARCLAYCARD

Buy it with Access



High Quality  
Construction  
Kits, stocked  
at all branches  
Send for  
catalogue!

**AMPLIFIERS**

Teleton SAQ3078 - 8 watt £27.00  
Rotel RA211 £42.95  
RA311 £54.95  
RA611 £86.95  
Leak Delta 30 £54.75  
Samsui AU101 £48.25  
AU505 £74.95  
Sinclair 2000 £34.95  
Sinclair 4000 £45.95

**TUNERS & RECEIVERS**

Leak Delta FM £58.75  
Sinclair 2000/4000 Tuner £34.95  
Rotel RX150A Tuner/  
Amp. £59.95  
Rotel I52A £69.95  
RT222 £42.75  
Samsui  
210 AM/FM/MPX £84.25  
310 AM/FM/MPX £99.50  
350A AM/FM/MPX £106.95

**RECORD DECKS**

SP25 Mk III £11.00  
Garrard SP25 MkIV £12.95  
BSR MP60 £11.00  
BSR Invicta P & C/SC7M £9.95  
Garrard  
SP25 MkIV P & C G/800 £21.00  
AP76 Module £30.00  
Goldring GL78 P & C/  
G800E £59.95  
Connoisseur  
BDI Kit £13.50  
BD2 Chassis/SAU2 £32.50  
SAU2 £14.25  
SCUI £5.95  
Plinth & Cover for Garrard  
SP25 MkIV Mk. III  
2025TC £3.95

**TAPE DECKS (Insurance 2.00)**

Akai  
4000DS Reel to Reel £93.95  
4000DB Reel to Reel  
Dolby £149.50  
1721L Special Offer £77.95  
GXC36D £82.00  
GXC38D £103.95  
CS33D £79.95  
Akai CR81D 8-track Rec.  
player £73.95

**SPEAKERS**

Wharfedale  
Denton 2 (pair) £33.00  
Linton 2 (pair) £42.95  
Linton 2 Kits (pair) £19.95  
Glendale 3 Kit (pair) £36.95  
Dovedale 3 Kit (pair) £59.95

**Chassis Speakers**

EMI (Plain) 13in x 8in,  
3, 8 or 15 ohm Bass unit £2.30  
with Single Tweeter  
(only Bohm) £2.45  
with Twin Tweeter £3.95  
Type 350 Kit 15 watt 8 ohm £8.25  
13in x 8in Bass unit  
15 watt 8 ohm £4.95  
8in x 5in 5 watt 3, 8 or  
15 ohm £1.50  
8in x 5in 10 watt  
Dualcone 8 ohm £2.50  
6 1/2" 10 watt 8 ohm £2.65  
8in 10 watt 8 ohm £3.90  
12in 20 watt 8 ohm £6.95  
Fane Bin 4 or 15 ohm £2.25

Fane 7in x 4in 3 or 8 ohm £1.20  
Elac 8in 8 ohm Dualcone £2.50  
Elac 10in 8 ohm Dualcone £3.75  
Goodman 6 1/2in 8 ohm  
Dualcone £2.40  
Baker Group 25 12in 8 or  
15 ohm £7.95  
Adastra "Top 20" 12in  
25 watt 8 or 15 ohm £8.25  
Adastra "Hi-Ten" 10in  
10 watt 8 or 15 ohm £3.60  
Also 5in 8 ohm speaker  
2 1/2in 8 or 64 ohm  
speaker £0.50  
Wharfedale  
Denton 1 £26.75  
Denton 2 £30.00  
Linton 2 £38.95  
Dovedale 3 £42.95  
Glendale 3 £58.95  
Kingsdale 3 £60.95

**SPEAKER CABINETS IN  
KIT FORM (Teak Veneer)**

12in x 8in x 6in  
(8 x 5 or 7 x 4 cutout) £2.50  
14in x 12in x 9in  
(8 x 5, 8", 6 1/2" & 3 1/2") £3.75  
18in x 11in x 9in  
(8" x 3 1/2" or 13 x 8) £4.50  
22in x 14in x 9in  
(12" & 3 1/2" or 13 x 8) £6.25

**TWEETERS & CROSSOVERS**

EMI 3 1/2" c/magnet in 3 or  
8 ohm £1.25  
Cone Tweeter 10 watt  
8 or 15 ohm (K2006) £2.50  
Cone Tweeter 3 watt  
8 ohm (K2003) £1.55  
Horn Tweeter 8 ohm  
(K2007) £6.50  
Dome Tweeter 8 ohm  
(K2011) £5.50  
2-way Crossovers (CN23,  
CN28, CN216) £1.20  
3-way Crossover (CN38) £2.75

**CARTRIDGES & STYLII**

ACOS	Cart. £	D/D Styli £
GP91/2SC or 3CS (ster. comp)	1.10	1.25
GP93/1 or 95/1 ster. cryst.	1.35	1.25
GP94/1 or 96/1 ster. ceram.	1.75	1.25
GP101 cryst. comp.	90	—
GP104 ster. ceram.	1.75	1.25
BSR X5M or X5H cryst. comp.	1.75	1.25
SX6M or SX6H cryst. ster.	2.00	1.25
SC5M ster./ceram.	2.75	1.25
SONOTONE 9TAHC or 9TAHC/G (Diam.)	1.85	1.25
3509 Magnetic	1.90	1.25
AUDIO TECNICA AT55	1.95	—
EMPIRE 999 REX	3.95	—

**GOLDRING**

G850	2.95	1.95
G800	3.95	1.95
G800H	3.95	1.95
G800E	6.99	3.95
SHURE M44G	4.75	3.45
M55E	5.50	4.25
M75ED Type 2	10.75	6.99
M15EJ Type 2	8.75	4.99
V15 Type 3	29.95	—

**MICROPHONES**

UD130 50K/600 ohm  
uni-dir. ball metal £5.95  
UD147 £9.25  
Condenser Mic. 600 ohm  
uni-dir £9.50  
Cassette Stick Mic. with  
R/Control £1.60  
Mic-Mixers Mono/stereo £5.50  
AKAI ADM14 £5.95

**HEADPHONES**

Rotel  
RH430 £4.75  
RH 630 £7.75  
RH 700 £11.50  
Koss  
K711 £10.95  
KR0711 £10.95  
K6 £11.50  
K6LC £14.00  
KO727B £16.00  
KO747 £20.75  
HVI £21.95  
PRO4AA £26.95  
PRO54 £29.95  
K6LCO £26.00  
Samsui SS10 £14.20  
Headphone adaptor  
(junction box) £2.50  
extension lead 2ft curly £1.35

**CASSETTES**

	C40	C60	C90	C120
Low Noise	—	35p	45p	55p
Philips	—	50p	69p	105p
Memorex	55p	65p	85p	120p
Ampex (360)	45p	55p	70p	99p
Ampex (20-20+)	59p	65p	99p	135p
Chromium Dioxide	—	99p	140p	—
Cassette Head Cleaner	—	—	45p	—
Ampex Head Cleaner	—	—	Demag	£1.65
Cassette Racks (hold 6)	—	—	—	£0.45
Cassette Rotating Racks (hold 20)	—	—	—	£3.50
Cassette Carrying Case (BIB) (hold 12)	—	—	—	£1.60

**8-Track Cartridge Blanks**

Ampex	C40	C64	C80
	80p	95p	£1.10
8-track H/Cleaner Demagnetiser	—	—	£1.90
8-track Carrying Cases (BIB)	—	—	£1.65

**TAPES & CASSETTES**

	Stnd	LP	DP	Cases
5"	55p	65p	1.00	20p
5 1/2"	65p	75p	1.35	25p
7"	80p	110p	1.85	30p
High frequency Ampex	—	—	—	—
5"	—	1.40p	1.55p	—
7"	—	1.90p	2.95p	—
AKAI Metal Reel 7"	—	—	—	£1.99

**CALCULATORS**

Sinclair Cambridge Build £19.95  
Scientific £29.95

**SINCLAIR PROJECT 80**

Stereo Pre-amp. £11.95  
Active Filter Unit £6.95  
Z40 15 watt Amp £5.45  
Z60 25 watt Amp £6.95  
P25 Power Supply for 240 £4.98  
P26 Power Supply for 240 £7.98  
P28 Power Supply for 260 £7.98  
FM Tuner £11.95  
Stereo Decoder £7.45  
Q16 Speaker £7.10

**PORTABLE RADIOS**

Vega Jade £5.75  
Vega Zircon £8.25  
Vega Sapphire £7.25  
Vega VEF206 £13.95  
Micado LM/MW/FM/SSW  
Murphy £18.95  
B833 MW/VHF £9.95  
BA838 LW/MW/VHF  
M/Batt £18.50  
MA5003 Head Set  
Radio LW £7.95  
Bush  
VTR165 LW/MW/VHF £22.00  
VTR127 LW/MW/VHF £15.50  
VTR178 VHF/MW/2SW/  
AIR M/Batt £27.50  
VTR175 LW/MW/VHF £13.95  
VTR188 LW/MW/VHF/  
2SW M/Batt £31.95  
BY5661 LW/MW/VHF £14.95

**CLOCK RADIOS**

Bush CR128 LW/MW £13.60  
Bush CR232 MW/VHF £24.95  
Murphy MV5600  
MW/VHF £22.95

**CASSETTE RECORDERS**

Murphy BA206 £16.95  
Bush TP66 M/Batt £25.75  
Murphy BA200 M/Batt £22.75  
Bush BT8504 (miniature) £25.50

**RADIO CASSETTES**

(Mains/Batt.)  
Micado 8155 AM/FM £25.95  
Murphy BA209 MW/VHF £33.50

**STEREO RECORD PLAYER & SYSTEM**

Bush SPR58 £29.50  
Bush SPR59 £31.50  
Bush A1005 £56.50  
Hanimec H101 £39.95  
Hanimec HRC5060 8-track  
AM/FM/MPX + Speaker £116.95

**CAR AUDIO**

Bush Car Cassette BT8501 £36.75  
Hitachi Car Radio  
VM702R LW/MW £16.50  
KM1510 LW/MW/VHF £32.50  
Hitachi Car Cassette  
CS114 £45.00

ALL ITEMS SUBJECT TO  
MANUFACTURERS INCREASE  
AND AVAILABILITY


**PERSONAL CALLERS  
WELCOME**

ALL MERCHANDISE FULLY GUARANTEED

**NEWMART**  
ELECTRONICS

Mail Order Dept PW/II  
Belmont St, Monton,  
Eccles, Manchester.  
Tel: 061-789 5268

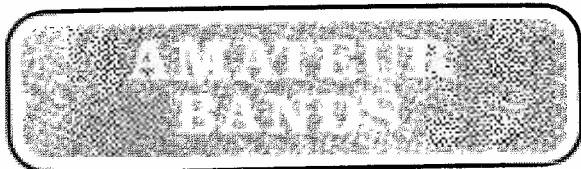Manchester  
30-32 Shudehill. tel 061-832 7710  
Leeds  
4 New Market St tel 0532 42708  
Liverpool  
15 Whitechapel tel 051-236 0738



by Eric Dowdeswell G4AR

LOOK to your laurels, my lads! Pride of place this month goes to Julie Rose (Warley, West Midlands) who has sent in any excellent log. Her Dad handed over his version of the PW 'Progressive' receiver to Julie and she's spent most of her spare time in the last couple of years listening on the amateur bands, aided and abetted by a No. 19 set bought for 10p at a jumble sale! Clever Dad removed the TX and VHF bits and fitted up a power pack and output stage. A Yaesu FR50B is in the offing, if Santa gets the message in time!

### And now-SSTV!

Paul Barker (Sunderland) made me sit up with his reception reports on SSTV (slow scan TV) stations he had 'seen'! Equipment includes a home-made electrostatic monitor and an MK Products electromagnetic monitor which has recording facilities. Receivers include an FRDX500, Trio JR310 and Sony TFM1600. The aerials are 15 and 20m dipoles and a six element Yagi on 2m. Paul is to be congratulated on getting away from the SSB/CW routine and it is to be hoped that others may follow his example and 'look' into the possibilities of SSTV. Sorry about that!

John Porter (Baslow, Derbys) queries the SQ prefix heard of late. Just another of those silly 'change for change's sake', I'm afraid. Some SP anniversary I understand. The habit is very common nowadays especially in contests, no doubt netting the user a few extra million points since the country/prefix chaser cannot afford not to work him 'just in case' he is a new one!

Tony Price BRS33946 (Brierly Hill, Staffs) will have to have another go at the RAE. Hard luck Tony, but I'm sure the exam experience will have been worthwhile. I'm glad to see you haven't given up amateur radio in favour of stamp collecting! Tony reports that WB4SPG is hoping to activate Saipan in the Pacific 10 to 15 October, mostly CW but some SSB on 80, 40 and 20m. Tony also logged TG9GI who was

running just 5 watts of SSB. That's really QRP, although the call is always worth a couple of extra S points! By the way, Tony uses a Collins 75A4 (lucky him!) and a TA32 for 10, 15 and 20m.

Alan Rae (Glasgow) concentrated on 40m SSB this time. He and his fellow members of the West of Scotland ARS are very aggrieved on having the club's KW2000 stolen recently. Stan Sharred (B'ham) is still finding useful DX on 160m in the height of summer (I must be joking!) including ZB2AY for a new one. Michael Crimes (Exeter) was pleased to change his 9R59DS for a Yaesu FR50B but says 'no more VHF until the converter's IF is changed' so he was forced to listen on HF for a change.

### Congratulations

Graham Nicholls (Banbury) is just 16 and really off to a flying start in amateur radio having just passed his RAE, and probably his code exam by now. He says 'can copy 20wpm in my head' so writing it down at 12wpm shouldn't present much of a problem. How wise of him to go for the Class A licence from the start and have the run of all the bands even though he is interested only in 70cm and 2m at the moment. Graham's version of the G3HBW 2m converter reached out to OE3QMD/P and his F3PH/F3FC converter caught DL3BSA which isn't bad with bedroom yagis! He can always hang his socks on them when conditions are duff! Max France (Warrington) sent in a very impressive first log of 80m SSB heard on his R107 with either a 60ft horizontal wire or a 30ft vertical and a home-made ATU.

### SSB-the hard way

Tim Charles (Colchester) plucked up courage to tell me that he is only 15 but a dedicated listener to the amateurs. His Teleton 702 portable hasn't got a BFO so 'I resolve SSB and CW by superimposing a local carrier from another receiver'. He does the same with his modified Bush 90A covering the HF bands between them. Oh well! As Tim says 'one day I'll have to make up a simple BFO'. It would be easier!

Not much space for personal chat this month! Any 9R59DS experts out there??? Several readers complain of excessive hum when using headphones, perhaps not entirely unexpected since these low impedance headsets are probably intended for hi-fi stereo reception and respond well to the 100Hz ripple frequency! A capacitor, around 0.5/1µF in series with headset might help reduce the bass response.

### Log Extracts

Julie Rose:- 80m CT2BN C31FO EL7F FP0YY (0530) VK3DN VP2LH ZL2AKK ZL2BT ZL3GS ZL4KS ZP5AL 40m EA7PW 7X2AN 20m HI8MOG 5X5NK.

#### BROADCAST BANDS

Short Wave and VHF/FM reports by the 15th of the month to The Editor, Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

#### AMATEUR BANDS

Logs covering any amateur bands in band/alphabetical order by the middle of the month to Eric Dowdeswell G4AR, Silver Fir, Leatherhead Road, Ash-lead, Surrey, KT21 2TW.

**P. Barker:-** 20m C31BL F0CH/FC HM1BK HZ1SH KC4AAC (Antarctica) KC6SX KV4BW R1A, R2C etc (Russian contest calls) VE8DC (Ellesmere Is.) VQ9BP XT2AA 15m TR8SS ZE4JS ZS3TP **Seen on 20m SSTV:-** DL3DW DK2MH DK5EL F8KW G3VGU K1OKW YU2CDS YV1AQE.

**J. Porter:-** 20m CR4BS CX1JR FG7TD HC1WP KG4NY TU2DV VP2VS (Tortola) 15m KZ5WA ZP5AN.

**T. Price:-** 20m C02FA CR4BS DUIXKE HK0BKX KG4GO KH6IJ KL7MF KM6DZ KS6DH KW6HF TG9GI ZL4BX (2300) 15m H18EJH.

**A. Rae:-** 40m CM7EG CX3UE M1C PJ2CW ZS3PT.  
**S. Sharred:-** 160m EP2BQ GD3WPS/P WA8IJI ZB2AY 80m 5Z4LW CE6EZ FY7YF ZS1MH 40m HC1XG TI2PZ VK3MR 20m 5T5MG DU1NRS FG7XC FL8OM HRIJBS KL7BJW 15m CX2CA TR8CQ.

**M. Crimes:-** 20m VU2DK 15m LU9HG VQ9GP CE3AQW IS0SQF.

**G. Nicholls:-** 2m DC8CB DK6QK GD8EX1 GM8AGU/P HB9QQ LX1DU OE2CAL/P OK1WSG/P OZ1OL All SSB. 70cm DL3SBA DL7SGN F9FT G3KMS G8BGU All SSB.

**M. France:-** 80m CE6EC CP8CX CR3WB EP2VJ FY7AU TJ1EZ TR8AI VP2SAF VP5KG VP8NP ZD9GD 4S7PB 8P6CX 9M2BX.

**T. Charles:-** 80m PY4TK ZL3FA ZL3PX ZL4KF 40m TG9PW VK2WC YV4ZA ZL3DR ZL4BO ZL4CM. CW stations in bold, remainder SSB.

DXers in the UK often hear North America on the medium waves during the winter months when a path of darkness falls across the North Atlantic before midnight. The band becomes quieter after 2300hrs GMT when a number of European broadcasters close down for the night and this is the time to hunt for Canadians, which are the first to appear. Listen for CBN in St John's Newfoundland on 640kHz; CJON also in St John's on 930kHz; CHER Sydney, Nova Scotia on 950kHz and CBA in Moncton, New Brunswick on 1070kHz. These stations are heard regularly in the UK when conditions are favourable. Propagation is variable on this path so if nothing is heard at the first attempt then try again a few evenings later. As midnight approaches stations in the United States can be heard. Look for WOR in New York City on 710kHz; WNEW also in NYC on 1130kHz; WCAU Philadelphia on 1210kHz and WKWB Buffalo NY on 1020kHz. An outdoor aerial or a medium wave loop aerial should be used for this type of DXing as it is unlikely that North America will be heard at any strength with a portable receiver and internal aerial.

**David Birch** (Trowbridge, Wilts) has been busy on the medium waves with his VTO transistor radio. He reports hearing Vatican Radio on 1529kHz; Trans World Radio, Montecarlo on 1466kHz; and programmes in English from West Germany on 1268kHz, Warsaw on 1502kHz and the Voice of America on 1295kHz at 2100hrs GMT. Our regular reporter **Brendon McNamee** who lives in Portrush, Northern Ireland has been DXing with his Sharp BZ-23 receiver. His log includes Radio Tirana, Albania on 1394kHz; Radio Prague on 1286kHz and RTE Dublin on 1250kHz.

We wish to thank those readers who have sent in reports for the Short Wave Broadcast and VHF/FM bands, we hope to resume publication of these features as from next month.



## MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

**C**hristopher Owens (Stoke-on-Trent) has a Bush PB12 receiver and a 15ft outdoor aerial. His medium wave log includes Radio Carlisle on 755kHz; Radio Blackburn on 854kHz; Radio Derby on 1115kHz; Piccadilly Radio, Manchester on 1151kHz; IBA Birmingham also on 1151kHz and Radio Humberside on 1484kHz. Christopher asks for information about French and German broadcasts on the low frequency end of the medium wave band. Guide to Broadcasting Stations published by Butterworth is available in most bookshops. It lists the majority of European stations on the medium waves together with a few of the more distant ones that are heard regularly and it is a good guide for the newcomer to the band.

**Christopher Hall** of St Julians in Malta who has been trying to pick up the BBC on the medium waves with his Telefunken multiband receiver, asks for information about medium wave propagation. During the daytime reception is by the ground wave only and the range, even of high power stations is limited. After dark the radio waves are reflected by the ionosphere and they can travel quite a considerable distance provided there is a path of darkness between transmitter and receiver. Reception of the UK in Malta on the medium waves should be possible after dark provided a selective receiver and an outdoor aerial are used.

## IC OF THE MONTH—continued from page 646 PERFORMANCE

The RF input resistance at pin 12 is typically 1k $\Omega$ . The transconductance of the RF stage at 1MHz with a 100 $\mu$ V signal at pin 12 is about 120mmho, but decreases with the applied AGC and, at higher frequencies, with the frequency. The mixer input impedance is typically 1.4k $\Omega$  whilst the mixer transconductance is about 2.5mmho with a 1MHz 1mV input signal at pin 1. The oscillator voltage at pin 2 is about 1.7V RMS.

If the IFT between pins 14 and 7 is replaced by a suitable ceramic filter, a better response curve should be obtainable. Ceramic filters operating at the normal IF frequency of about 455kHz can provide a response curve with a flat, broad top for good quality reproduction, but with the steep sides required for the reception of a weak signal close to a much more powerful one. If such a ceramic filter is employed, a single tuned circuit may be used for IFT2.

For broadcast band reception on the medium and long wave bands, a ferrite rod aerial could be employed instead of L1 and L2 of Figs. 2 and 3. However, the LM1820N is really intended for more critical applications. The Fairchild equivalent is the  $\mu$ A720DC while the NE546A is the equivalent in the Signetics range.

ICs and coils available from Ambit International, 37A High Street, Brentwood, Essex CM14 4RH. ■

# Trannies LTD.

4 BUSH HOUSE, HARLOW, ESSEX

Retail shop open  
9.30 to 5.30 Monday to Friday

**ALL PRICES FULLY INCLUSIVE OF VAT**

## SEMICONDUCTORS

### TRANSISTORS—DIODES—RECTIFIERS—THYRISTORS—TRIACS—74 SERIES—IC's—THERMISTORS


<b>Transistors</b>	BA145 24p	BCY30 58p	ME04075 34p	NKT773 34p	2N930 22p	<b>Ther-</b>	IN5407 28p	7437 77p	74154 22.20
AA119 7p	BA154 14p	BCY31 60p	ME0491 23p	NKT773 30p	2N1131 26p	<b>mistors</b>	IN5408 24p	7738 77p	74155 21.75
AC107 25p	BA156 18p	BCY70 17p	ME0492 23p	OA5(GH5001) 19p	2N3132 26p	VA10668 15p	400mW Zener	7440 22p	74156 21.75
AC126 22p	BAX16 8p	BCY71 27p	ME0493 21p	OA10 24p	2N3202 26p	VA10658 15p	Diodes	7441 81p	74157 21.84
AC127 18p	BC107 14p	BCY72 14p	ME1001 15p	OA10 24p	2N1303 30p	VA10656 15p	3.3v to 33v 15p	7442 81p	74160 22.18
AC128 13p	BC108 14p	BD124 14p	ME1002 17p	OA47 9p	2N1304 35p	VA10657 15p		7443 81p	74161 22.18
AC141 25p	BC109 14p	BD131 52p	ME1075 15p	OA90 6p	2N1305 38p	VA1089 14p	<b>Thyristors</b>	7444 81p	74162 22.18
AC141k 25p	BC113 18p	BD132 57p	ME1100 20p	OA91 6p	2N1306 47p	VA1040 14p	1 amp	7445 81p	74163 22.18
AC142 22p	BC114 19p	BD131 M/P	ME1120 20p	OA95 6p	2N1307 47p	VA1077 15p	50v	7446 81p	74164 22.18
AC142k 22p	BC115 19p	BD132 / 11.18	ME2001 15p	(HG1005) 7p	2N1308 23p	VA1100 14p	100v	7447 81p	74165 22.18
AC151 23p	BC117 26p	BDY20 91p	ME2002 18p	OA200 9p	2N1309 26p	<b>Bridge</b>	200v	7448 81p	74166 22.18
AC152 25p	BC125 17p	BF167 25p	ME2003 18p	OA202 9p	2N1310 26p	<b>Rectifiers</b>	400v	7449 81p	74167 22.18
AC153k 38p	BC126 17p	BF173 25p	ME2004 18p	OA19 55p	2N1613 24p	1 amp	50v	7450 81p	74168 22.18
AC153k M/P	BC128 19p	BF177 27p	ME2005 18p	OA19 55p	2N1711 25p	2 amp	50v	7451 81p	74169 22.18
AC176k 38p	BC137 18p	BF178 24p	ME2006 18p	OC25 45p	2N2218 48p	5 amp	50v	7452 81p	74170 22.18
AC176k 42p	BC140 35p	BF179 38p	ME2007 18p	OC28 45p	2N2219 48p	10 amp	50v	7453 81p	74171 22.18
AC176 24p	BC147 18p	BF194 18p	ME2008 18p	OC29 69p	2N2219a 48p	1 amp	100v	7454 81p	74172 22.18
AC187 22p	BC148 11p	BF195 18p	ME2009 18p	OC35 65p	2N2484 46p	2 amp	100v	7455 81p	74173 22.18
AC187k 22p	BC149 18p	BF244 27p	ME2010 18p	OC41 20p	2N2646 51p	5 amp	100v	7456 81p	74174 22.18
AC188 22p	BC157 17p	BF254 19p	ME2011 18p	OC44 20p	2N2904 25p	10 amp	100v	7457 81p	74175 22.18
AC188k 22p	BC158 18p	BF259 24p	ME2012 18p	OC44 20p	2N2904a 25p	5 amp	400v	7458 81p	74176 22.18
AC197 22p	BC159 18p	BF264 24p	ME2013 18p	OC70 23p	2N2904a 25p	10 amp	400v	7459 81p	74177 22.18
AC198 22p	BC167 18p	BF265 24p	ME2014 18p	OC71 18p	2N2905a 25p	5 amp	50v	7460 81p	74178 22.18
AC199 22p	BC168 18p	BF266 24p	ME2015 18p	OC72 18p	2N3053 28p	10 amp	50v	7461 81p	74179 22.18
AC200 22p	BC169 18p	BF267 27p	ME2016 18p	OC75 24p	2N3055 28p	5 amp	100v	7462 81p	74180 22.18
AC201 22p	BC177 23p	BF268 27p	ME2017 18p	OC81 28p	2N3702 11p	10 amp	100v	7463 81p	74181 22.18
AC202 19p	BC178 21p	BF269 27p	ME2018 18p	OC81 28p	2N3703 11p	5 amp	100v	7464 81p	74182 22.18
AD140 67p	AD142 67p	AD143 67p	ME2019 18p	OC82 28p	2N3704 11p	10 amp	100v	7465 81p	74183 22.18
AD142 67p	AD143 67p	AD144 67p	ME2020 21p	OC83 24p	2N3705 11p	5 amp	100v	7466 81p	74184 22.18
AD143 67p	AD144 67p	AD145 67p	ME2021 21p	OC84 28p	2N3706 11p	10 amp	100v	7467 81p	74185 22.18
AD149 65p	BC184 12p	BFY30 11.15	ME2022 18p	OC84 28p	2N3707 11p	5 amp	100v	7468 81p	74186 22.18
AD161 46p	BC212 18p	BY100 17p	ME2023 18p	TIP29a 64p	2N3708 11p	<b>Silicon</b>	7400 20p	7469 81p	74187 22.18
AD162 46p	BC213 15p	BY127 17p	ME2024 18p	TIP30a 64p	2N3709 11p	<b>Rectifiers</b>	7401 20p	7470 81p	74188 22.18
AD161 M/P	BC214 15p	BF210 39p	ME2025 18p	TIP31a 77p	2N3710 11p	IN4001 7p	7402 20p	7471 81p	74189 22.18
AD162 55p	BC215 15p	BF211 39p	ME2026 18p	TIP32a 77p	2N3711 11p	IN4002 7p	7403 20p	7472 81p	74190 22.18
AF114 25p	BC256 18p	BF212 38p	ME2027 18p	TIP33a 77p	2N3712 11p	IN4003 8p	7404 20p	7473 81p	74191 22.18
AF116 20p	BC259 15p	BY213 28p	ME2028 18p	TIP34a 77p	2N3713 11p	IN4004 8p	7405 20p	7474 81p	74192 22.18
AF116 20p	BC267 14p	CA07 19p	ME2029 18p	TIP35a 23.18p	2N3714 20p	IN4005 10p	7406 20p	7475 81p	74193 22.18
AF117 20p	BC268 18p	MA8001 36p	ME2030 18p	TIP36a 24.07p	2N3819 27p	IN4006 11p	7407 20p	7476 81p	74194 22.18
AF124 29p	BC269 14p	MA8002 40p	ME2031 18p	TIP41a 88p	2N4292 11p	IN4007 11p	7408 20p	7477 81p	74195 22.18
AF125 29p	BC270 15p	MA8003 40p	ME2032 18p	TIP42a 11.10p	2N4296 11p	IN4008 11p	7409 20p	7478 81p	74196 22.18
AF126 29p	BC271 15p	ME0401 33p	ME2033 18p	TIP43a 11.10p	2N4306 17p	IN4009 11p	7410 20p	7479 81p	74197 22.18
AF127 29p	BC272 15p	ME0402 33p	ME2034 18p	TIP44a 11.10p	2N4306 17p	IN4010 11p	7411 20p	7480 81p	74198 22.18
AF128 29p	BC273 15p	ME0403 33p	ME2035 18p	TIP45a 11.10p	2N4306 17p	IN4011 11p	7412 20p	7481 81p	74199 22.18
AF129 29p	BC274 15p	ME0404 33p	ME2036 18p	TIP46a 11.10p	2N4306 17p	IN4012 11p	7413 20p	7482 81p	74200 22.18
AF239 62p	BC298 24p	ME0404/1 19p	ME2037 18p	TIP47a 11.10p	2N4306 17p	IN4013 11p	7414 20p	7483 81p	74201 22.18
AF279 75p	BC300 41p	ME0404/2 19p	ME2038 18p	TIP48a 11.10p	2N4306 17p	IN4014 11p	7415 20p	7484 81p	74202 22.18
AY826 39p	BC301 40p	ME0411 22p	ME2039 18p	TIP49a 11.10p	2N4306 17p	IN4015 11p	7416 20p	7485 81p	74203 22.18
AY827 50p	BC302 36p	ME0412 21p	ME2040 18p	TIP50a 11.10p	2N4306 17p	IN4016 11p	7417 20p	7486 81p	74204 22.18
AY828 39p	BC303 49p	ME0413 19p	ME2041 18p	TIP51a 11.10p	2N4306 17p	IN4017 11p	7418 20p	7487 81p	74205 22.18
AY829 45p	BC304 39p	ME0414 19p	ME2042 18p	TIP52a 11.10p	2N4306 17p	IN4018 11p	7419 20p	7488 81p	74206 22.18
BA111 35p	BC341 39p	ME0422 25p	ME2043 18p	TIP53a 11.10p	2N4306 17p	IN4019 11p	7420 20p	7489 81p	74207 22.18
BA115 10p	BC461 45p	ME0463 23p	ME2044 18p	TIP54a 11.10p	2N4306 17p	IN4020 11p	7421 20p	7490 81p	74208 22.18
			ME2045 18p	TIP55a 11.10p	2N4306 17p	IN4021 11p	7422 20p	7491 81p	74209 22.18
			ME2046 18p	TIP56a 11.10p	2N4306 17p	IN4022 11p	7423 20p	7492 81p	74210 22.18
			ME2047 18p	TIP57a 11.10p	2N4306 17p	IN4023 11p	7424 20p	7493 81p	74211 22.18
			ME2048 18p	TIP58a 11.10p	2N4306 17p	IN4024 11p	7425 20p	7494 81p	74212 22.18
			ME2049 18p	TIP59a 11.10p	2N4306 17p	IN4025 11p	7426 20p	7495 81p	74213 22.18
			ME2050 18p	TIP60a 11.10p	2N4306 17p	IN4026 11p	7427 20p	7496 81p	74214 22.18
			ME2051 18p	TIP61a 11.10p	2N4306 17p	IN4027 11p	7428 20p	7497 81p	74215 22.18
			ME2052 18p	TIP62a 11.10p	2N4306 17p	IN4028 11p	7429 20p	7498 81p	74216 22.18
			ME2053 18p	TIP63a 11.10p	2N4306 17p	IN4029 11p	7430 20p	7499 81p	74217 22.18
			ME2054 18p	TIP64a 11.10p	2N4306 17p	IN4030 11p	7431 20p	7500 81p	74218 22.18
			ME2055 18p	TIP65a 11.10p	2N4306 17p	IN4031 11p	7432 20p	7501 81p	74219 22.18
			ME2056 18p	TIP66a 11.10p	2N4306 17p	IN4032 11p	7433 20p	7502 81p	74220 22.18
			ME2057 18p	TIP67a 11.10p	2N4306 17p	IN4033 11p	7434 20p	7503 81p	74221 22.18
			ME2058 18p	TIP68a 11.10p	2N4306 17p	IN4034 11p	7435 20p	7504 81p	74222 22.18
			ME2059 18p	TIP69a 11.10p	2N4306 17p	IN4035 11p	7436 20p	7505 81p	74223 22.18
			ME2060 18p	TIP70a 11.10p	2N4306 17p	IN4036 11p	7437 20p	7506 81p	74224 22.18
			ME2061 18p	TIP71a 11.10p	2N4306 17p	IN4037 11p	7438 20p	7507 81p	74225 22.18
			ME2062 18p	TIP72a 11.10p	2N4306 17p	IN4038 11p	7439 20p	7508 81p	74226 22.18
			ME2063 18p	TIP73a 11.10p	2N4306 17p	IN4039 11p	7440 20p	7509 81p	74227 22.18
			ME2064 18p	TIP74a 11.10p	2N4306 17p	IN4040 11p	7441 20p	7510 81p	74228 22.18
			ME2065 18p	TIP75a 11.10p	2N4306 17p	IN4041 11p	7442 20p	7511 81p	74229 22.18
			ME2066 18p	TIP76a 11.10p	2N4306 17p	IN4042 11p	7443 20p	7512 81p	74230 22.18
			ME2067 18p	TIP77a 11.10p	2N4306 17p	IN4043 11p	7444 20p	7513 81p	74231 22.18
			ME2068 18p	TIP78a 11.10p	2N4306 17p	IN4044 11p	7445 20p	7514 81p	74232 22.18
			ME2069 18p	TIP79a 11.10p	2N4306 17p	IN4045 11p	7446 20p	7515 81p	74233 22.18
			ME2070 18p	TIP80a 11.10p	2N4306 17p	IN4046 11p	7447 20p	7516 81p	74234 22.18
			ME2071 18p	TIP81a 11.10p	2N4306 17p	IN4047 11p	7448 20p	7517 81p	74235 22.18
			ME2072 18p	TIP82a 11.10p	2N4306 17p	IN4048 11p	7449 20p	7518 81p	74236 22.18
			ME2073 18p	TIP83a 11.10p	2N4306 17p	IN4049 11p	7450 20p	7519 81p	74237 22.18
			ME2074 18p	TIP84a 11.10p	2N4306 17p	IN4050 11p	7451 20p	7520 81p	74238 22.18
			ME2075 18p	TIP85a 11.10p	2N4306 17p	IN4051 11p	7452 20p	7521 81p	74239 22.18
			ME2076 18p	TIP86a 11.10p	2N4306 17p				



# R T V C FOR AUDIO ON A BUDGET

## PUSH BUTTON CAR RADIO KIT

### The Tourist II

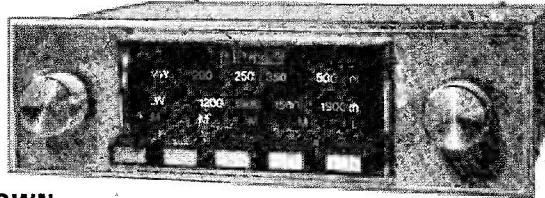

**NO SOLDERING  
REQUIRED!**

#### NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

**Car Radio Kit £7.70 + 55p p & p**

Tourist Mk.1 kit still available—  
price **£6.60+55p. p & p.**  
See July issue for full specification


#### Technical specification :

- (1) **Output** 4 watts R.M.S. output. For 12 volt operation on negative or positive earth.
- (2) **Integrated circuit** output stage, pre-built three stage IF Module.

**Controls** volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide, 2" high and 4 $\frac{5}{16}$ " deep approx

**Speaker** including baffle and fixing strip **£1.65+23p. p & p.**

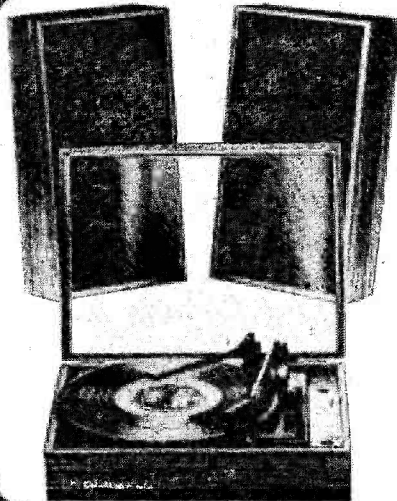**Car Aerial** Recommended — fully retractable and locking **£1.37+20p. postage & packing**



## \* STEREO 21 QUALITY SOUND FOR LESS THAN £20.00

Stereo 21, easy to assemble audio system kit. No soldering required.

Includes :- BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two speakers with cabinets.

**Amplifier module.** Ready built with control panel, speaker leads and full, easy to follow assembly instructions.


**Specifications :** For the technically minded :-

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel.

Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. **Overall Dimensions.** Speakers approx. 15 $\frac{1}{2}$ " x 8" x 4". Complete deck and cover in closed position approx. 15 $\frac{1}{2}$ " x 12" x 6".

Complete only **£19.95 + £1.60 p & p.** Extras if required. Optional Diamond Stylus **£1.37.**

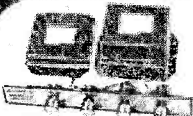Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**




## BUILD YOUR OWN \* STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

**£7.64 + 55p. p & p**

## 8 TRACK CARTRIDGE PLAYER\*

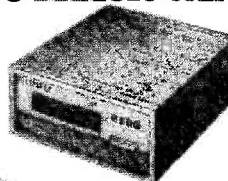

Elegant self selector push button player for use with your stereo system.


Compatible with Viscount III system, Unisound module and the Stereo 21.

Technical specification Mains input, 240V, Output sensitivity 125mV

Comparable unit sold elsewhere at £24.00 approx. Yours for only

**£10.95 + 90 p & p**

# COMPLETE\* STEREO SYSTEM

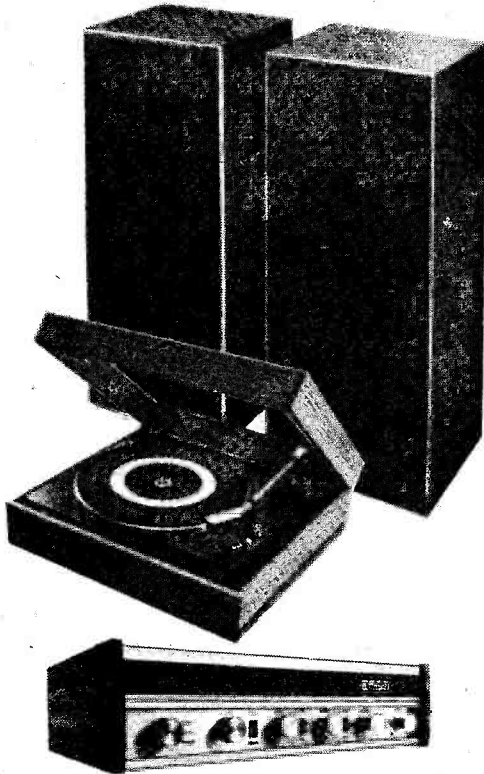

## System 1. £51.00

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.

System 1 includes:

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification

20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0-1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within  $\pm 1$ dB R.I.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass:  $+12$ dB to  $-17$ dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble  $+12$ dB to  $-12$ dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx.  $13\frac{3}{4}'' \times 9'' \times 3\frac{3}{4}''$ .

Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers - Enclosure size approx.  $17\frac{1}{2}'' \times 10\frac{1}{2}'' \times 6''$  in simulated teak. Drive unit  $13'' \times 8''$  with parasitic tweeter. 10 watts handling.

Complete System £51.00

## System 2. £69.00

Viscount III amplifier (As System 1)

Garrard SP 25 Mk III deck (As System 1)

Two Duo Type IIIA matched speakers - Enclosure size approx.  $31'' \times 13'' \times 11\frac{1}{2}''$

Finished in teak veneer. Drive units approx.  $13\frac{1}{2}'' \times 8\frac{1}{2}''$  with  $3\frac{1}{4}''$  HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20KHz.

Complete System £69.00

### PRICES: SYSTEM 1

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
<b>total:</b>	<b>£59.20</b>

Available complete for only:

**£51.00**  
+ £3.50 p & p


### PRICES: SYSTEM 2

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type III A speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
<b>total:</b>	<b>£84.20</b>

Available complete for only:

**£69.00**  
+ £4.00 p & p

# EMI SPEAKERS AT FANTASTIC REDUCTIONS

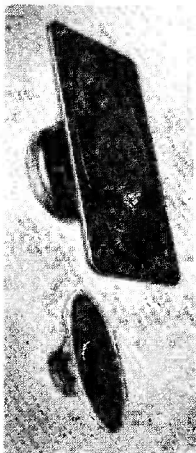

### 20 WATT SPEAKER SYSTEM

System consists of a  $13'' \times 8''$  (approx) elliptical woofer unit with a  $8'' \times 5''$  (approx.) mid range unit incorporating parasitic tweeter and crossover components.

Technical Specification:

Bass Unit

Flux density-100 K, speech coil- $1\frac{1}{2}''$ , Cone, Triple laminated paper with P.V.C. surround.

Mid Range Unit

Flux density-33K, speech coil- $1''$  with parasitic tweeter.

Power Handling

20 watts R.M.S., impedance - 8 ohms, frequency response - 20 Hz to 18,000 Hz.

**OUR PRICE**  
**£6.60.** Complete  
+ 90p p & p.



### 15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms.  $3''$  voice coil.

Recommended retail price £40.80.  
**OUR PRICE £18.70 + £1.50 p & p**



### 950 KIT

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz. Huge  $19'' \times 14''$  (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame. The four 10,000 gauss tweeters, each  $3\frac{1}{2}''$  dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil  $2''$ , others 0-5". Recommended list price £44.00.

**Special Offer**  
**OUR PRICE £19.50 + £1.50 p & p**

FOR DISCO PAGE AND DETAILS OF HOW TO ORDER - TURN OVER...


# PORTABLE DISCO CONSOLE

**INCORPORATES:** Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges.

The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record.

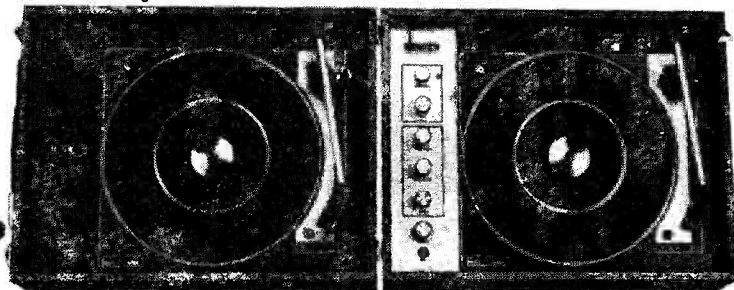The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.



## TECHNICAL SPECIFICATION:

**Pre-amp** - Output - 200mV. Auxiliary inputs - 200mV and 750mV into 1 meg.

**Mic input** - 6mV into 100K. 240 volt operation.

**Turntables capacity** - 7", 10" or 12" records.

**Rumble, wow and flutter** - Rumble - Better than -35dB. Wow - Better than 0.2%. Flutter - Better than 0.06% (Gaugmont kalee meter).

**Finish** - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

**Console size** - Unit Closed - 17 3/4" x 13 3/4" x 8 3/4" (approx.)

Unit Open - 35 3/4" x 13 3/4" x 4 1/4" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging diamond spun control knobs with matching control panel.

**Yours for only £45.00 + £3.50 P. & P.**


# DISCO 50


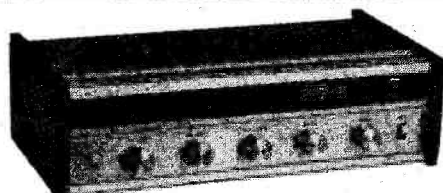
## 45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 1/4" x 10 1/2" x 8" (approx.) Amplifier £27.50 + £1.50 p. & p.

**Special Offer:** Disco 50 plus two 15" E.M.I. speakers type 14A/780 (as illustrated on previous page) Complete £55.00 + £4.00 p&p.



# DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.

**Outputs** 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

**Inputs** \*4 electrically mixed inputs. \*3 individual mixing controls.

\*Separate bass and treble controls common to all 4 inputs.

\*Mixer employing F.E.T. (Field Effect Transistors) \*Solid State circuitry.

\*Attractive styling.

## INPUT SENSITIVITIES

-Input - 1.) Crystal mic, guitar or moving coil mic, 2 and 10mV.

(Selector switch for desired sensitivity).

-Inputs - 2), 3), 4). Medium output equipment - ceramic cartridge, tuner,

tape recorder, organs, etc. - all 250mV sensitivity. AC Mains, 240V operation.

Size approx: 12 3/4" x 8" x 3 3/4".

**£15.00 + 60p. post & pack.**



## DO NOT SEND YOUR CARD

Just write your order giving your credit card number

● Mail orders to Acton. Terms C.W.O.  
All enquires Stamped Addressed Envelope.  
Goods not despatched outside U.K.

● Leaflets available for all items listed thus ✕  
Send stamped addressed envelope.



Radio and TV  
Components  
(Acton) Ltd.

21 High Street, Acton, London W3 6NG  
323 Edgware Road, London W2

Personal \_\_\_\_\_ Edgware Road: 9a.m.-5.30p.m. Half day Thurs.  
Shoppers \_\_\_\_\_ Acton: 9.30a.m.-5p.m. Closed all day Wed.

**Fully guaranteed  
Individually packed  
VALVES**

A1065	£1.25	6CL82	35p	KT66	£2.50	PY81	40p
AR8	55p	6CL83	70p	KT88	£3.00	PY82	40p
ATP4	50p	6CL86	45p	MH4	75p	PY83	40p
B12H	£3.00	EP36	65p	ML6	65p	PY88	45p
CT31	50p	EP37A	70p	QAZ	45p	PY500	£1.00
DA36	50p	EP38	£1.20	QAZ2	45p	PY800	45p
DF96	50p	EP40	75p	PAB180	40p	PY801	50p
DK96	70p	EP41	65p	PC57	50p	QV03-10	40p
DL92	40p	EP80	30p	PC600	50p	QV03-11	£1.40
DL96	60p	EP83	£1.25	PC84	40p	QV06-40A	40p
DY86/87	40p	EP85	35p	PC85	40p	QV06-40B	40p
EP86	35p	PC88	60p	PC89	60p	QV06-40C	40p
DY802	40p	EP89	30p	PC89	60p	QV06-40D	40p
EP800/01	40p	EP91	45p	PC118	£1.10	QV06-40E	40p
EP92	50p	EP92	50p	PC120	40p	QV06-40F	40p
EP93	50p	EP95	40p	PC121	40p	QV06-40G	40p
EP94	50p	EP96	40p	PC122	40p	QV06-40H	40p
EP97	40p	EP98	35p	PC123	40p	QV06-40I	40p
EP99	40p	EP100	35p	PC124	40p	QV06-40J	40p
EP101	40p	EP102	35p	PC125	40p	QV06-40K	40p
EP103	40p	EP104	35p	PC126	40p	QV06-40L	40p
EP105	40p	EP106	35p	PC127	40p	QV06-40M	40p
EP107	40p	EP108	35p	PC128	40p	QV06-40N	40p
EP109	40p	EP110	35p	PC129	40p	QV06-40O	40p
EP111	40p	EP112	35p	PC130	40p	QV06-40P	40p
EP113	40p	EP114	35p	PC131	40p	QV06-40Q	40p
EP115	40p	EP116	35p	PC132	40p	QV06-40R	40p
EP117	40p	EP118	35p	PC133	40p	QV06-40S	40p
EP119	40p	EP120	35p	PC134	40p	QV06-40T	40p
EP121	40p	EP122	35p	PC135	40p	QV06-40U	40p
EP123	40p	EP124	35p	PC136	40p	QV06-40V	40p
EP125	40p	EP126	35p	PC137	40p	QV06-40W	40p
EP127	40p	EP128	35p	PC138	40p	QV06-40X	40p
EP129	40p	EP130	35p	PC139	40p	QV06-40Y	40p
EP131	40p	EP132	35p	PC140	40p	QV06-40Z	40p
EP133	40p	EP134	35p	PC141	40p	QV06-40AA	40p
EP135	40p	EP136	35p	PC142	40p	QV06-40AB	40p
EP137	40p	EP138	35p	PC143	40p	QV06-40AC	40p
EP139	40p	EP140	35p	PC144	40p	QV06-40AD	40p
EP141	40p	EP142	35p	PC145	40p	QV06-40AE	40p
EP143	40p	EP144	35p	PC146	40p	QV06-40AF	40p
EP145	40p	EP146	35p	PC147	40p	QV06-40AG	40p
EP147	40p	EP148	35p	PC148	40p	QV06-40AH	40p
EP149	40p	EP150	35p	PC149	40p	QV06-40AI	40p
EP151	40p	EP152	35p	PC150	40p	QV06-40AJ	40p
EP153	40p	EP154	35p	PC151	40p	QV06-40AK	40p
EP155	40p	EP156	35p	PC152	40p	QV06-40AL	40p
EP157	40p	EP158	35p	PC153	40p	QV06-40AM	40p
EP159	40p	EP160	35p	PC154	40p	QV06-40AN	40p
EP161	40p	EP162	35p	PC155	40p	QV06-40AO	40p
EP163	40p	EP164	35p	PC156	40p	QV06-40AP	40p
EP165	40p	EP166	35p	PC157	40p	QV06-40AQ	40p
EP167	40p	EP168	35p	PC158	40p	QV06-40AR	40p
EP169	40p	EP170	35p	PC159	40p	QV06-40AS	40p
EP171	40p	EP172	35p	PC160	40p	QV06-40AT	40p
EP173	40p	EP174	35p	PC161	40p	QV06-40AU	40p
EP175	40p	EP176	35p	PC162	40p	QV06-40AV	40p
EP177	40p	EP178	35p	PC163	40p	QV06-40AW	40p
EP179	40p	EP180	35p	PC164	40p	QV06-40AX	40p
EP181	40p	EP182	35p	PC165	40p	QV06-40AY	40p
EP183	40p	EP184	35p	PC166	40p	QV06-40AZ	40p
EP185	40p	EP186	35p	PC167	40p	QV06-40BA	40p
EP187	40p	EP188	35p	PC168	40p	QV06-40BB	40p
EP189	40p	EP190	35p	PC169	40p	QV06-40BC	40p
EP191	40p	EP192	35p	PC170	40p	QV06-40BD	40p
EP193	40p	EP194	35p	PC171	40p	QV06-40BE	40p
EP195	40p	EP196	35p	PC172	40p	QV06-40BF	40p
EP197	40p	EP198	35p	PC173	40p	QV06-40BG	40p
EP199	40p	EP200	35p	PC174	40p	QV06-40BH	40p
EP201	40p	EP202	35p	PC175	40p	QV06-40BI	40p
EP203	40p	EP204	35p	PC176	40p	QV06-40BJ	40p
EP205	40p	EP206	35p	PC177	40p	QV06-40BK	40p
EP207	40p	EP208	35p	PC178	40p	QV06-40BL	40p
EP209	40p	EP210	35p	PC179	40p	QV06-40BM	40p
EP211	40p	EP212	35p	PC180	40p	QV06-40BN	40p
EP213	40p	EP214	35p	PC181	40p	QV06-40BO	40p
EP215	40p	EP216	35p	PC182	40p	QV06-40BP	40p
EP217	40p	EP218	35p	PC183	40p	QV06-40BQ	40p
EP219	40p	EP220	35p	PC184	40p	QV06-40BR	40p
EP221	40p	EP222	35p	PC185	40p	QV06-40BS	40p
EP223	40p	EP224	35p	PC186	40p	QV06-40BT	40p
EP225	40p	EP226	35p	PC187	40p	QV06-40BU	40p
EP227	40p	EP228	35p	PC188	40p	QV06-40BV	40p
EP229	40p	EP230	35p	PC189	40p	QV06-40BW	40p
EP231	40p	EP232	35p	PC190	40p	QV06-40BX	40p
EP233	40p	EP234	35p	PC191	40p	QV06-40BY	40p
EP235	40p	EP236	35p	PC192	40p	QV06-40BZ	40p
EP237	40p	EP238	35p	PC193	40p	QV06-40CA	40p
EP239	40p	EP240	35p	PC194	40p	QV06-40CB	40p
EP241	40p	EP242	35p	PC195	40p	QV06-40CC	40p
EP243	40p	EP244	35p	PC196	40p	QV06-40CD	40p
EP245	40p	EP246	35p	PC197	40p	QV06-40CE	40p
EP247	40p	EP248	35p	PC198	40p	QV06-40CF	40p
EP249	40p	EP250	35p	PC199	40p	QV06-40CG	40p
EP251	40p	EP252	35p	PC200	40p	QV06-40CH	40p

AC 113	AF 139	BBY 27	OA 202	OC 200	2N 3033
AC 126	AF 178	BBY 38	OA 200	OC 206	2N 3034
AC 127	AF 186	BBY 39	OC 22	OC 206	2N 3034
AC 128	AF 187	BBY 39A	OC 22	OC 206	2N 3034
AC 176	AF 212	BYZ 16	OC 25	OC 25	2N 3390
AC 181	ASX 26	CRS 1/10	OC 26	OC 26	2N 3391
AC 187	ASX 27	CRS 1/20	OC 28	OC 28	1N 28A
AC 19	ASX 28	CRS 1/30	OC 29	OC 29	1N 25
AC 20	BC 108	CRS 1/40	OC 35	OC 35	1N 32A
AC 21	BC 118	CRS 1/10	OC 36	OC 36	1N 28A
AC 29	BC 119	CRS 3/20	OC 42	OC 42	1N 43
AC 30	BC 136	CRS 3/30	OC 44	OC 44	1N 70
AC 40	BC 137	CRS 3/40	OC 45	OC 45	1N 277
AD 149	BC 148	CRS 25/25	OC 70	OC 70	1N 4150
AD 161	BC 172	CRS 25/25	OC 73	OC 73	1N 4149
AD 162	BC 172A	CRS 25/25	OC 78	OC 78	1N 4149
AD 171	BC 212A	CRS 25/25	OC 81	OC 81	1N 4149
AD 172	BC 212A	CRS 25/25	OC 82	OC 82	1N 4149
AD 173	BC 212A	CRS 25/25	OC 82D	OC 82D	1N 4149
AD 174	BC 212A	CRS 25/25	OC 82DM	OC 82DM	1N 4149
AD 175	BC 212A	CRS 25/25	OC 83	OC 83	1N 4149
AD 176	BC 212A	CRS 25/25	OC 83A	OC 83A	1N 4149
AD 177	BC 212A	CRS 25/25	OC 83B	OC 83B	1N 4149
AD 178	BC 212A	CRS 25/25	OC 83C	OC 83C	1N 4149
AD 179	BC 212A	CRS 25/25	OC 83D	OC 83D	1N 4149
AD 180	BC 212A	CRS 25/25	OC 83E	OC 83E	1N 4149
AD 181	BC 212A	CRS 25/25	OC 83F	OC 83F	1N 4149
AD 182	BC 212A	CRS 25/25	OC 83G	OC 83G	1N 4149
AD 183	BC 212A	CRS 25/25	OC 83H	OC 83H	1N 4149
AD 184	BC 212A	CRS 25/25	OC 83I	OC 83I	1N 4149
AD 185	BC 212A	CRS 25/25	OC 83J	OC 83J	1N 4149
AD 186	BC 212A	CRS 25/25	OC 83K	OC 83K	1N 4149
AD 187	BC 212A	CRS 25/25	OC 83L	OC 83L	1N 4149
AD 188	BC 212A	CRS 25/25	OC 83M	OC 83M	1N 4149
AD 189	BC 212A	CRS 25/25	OC 83N	OC 83N	1N 4149
AD 190	BC 212A	CRS 25/25	OC 83O	OC 83O	1N 4149
AD 191	BC 212A	CRS 25/25	OC 83P	OC 83P	1N 4149
AD 192	BC 212A	CRS 25/25	OC 83Q	OC 83Q	1N 4149
AD 193	BC 212A	CRS 25/25	OC 83R	OC 83R	1N 4149
AD 194	BC 212A	CRS 25/25	OC 83S	OC 83S	1N 4149
AD 195	BC 212A	CRS 25/25	OC 83T	OC 83T	1N 4149
AD 196	BC 212A	CRS 25/25	OC 83U	OC 83U	1N 4149
AD 197	BC 212A	CRS 25/25	OC 83V	OC 83V	1N 4149
AD 198	BC 212A	CRS 25/25	OC 83W	OC 83W	1N 4149
AD 199	BC 212A	CRS 25/25	OC 83X	OC 83X	1N 4149
AD 200	BC 212A	CRS 25/25	OC 83Y	OC 83Y	1N 4149
AD 201	BC 212A	CRS 25/25	OC 83Z	OC 83Z	1N 4149



**ALL valves guaranteed**

68A	50p	1906	£6.80	2051	£1.00
68A7GT	40p	1915	£1.40	3033	£3.00
68C7GT	40p	20P3	60p	6057	75p
68C7	50p	20P4	£1.10	6060	70p
68C7	55p	25L6GT	70p	6064	£1.00
68C7GT	35p	30C15	£1.00	6065	£1.00
68K7	55p	30C17	£1.00	6080	£2.30
68L7GT	50p	30C18	90p	6146	£2.95
68N7GT	50p	30C15	£1.00	6146	£2.25
68Q7	55p	30PL1	£1.00	8020	£5.00
68Q7	60p	30PL2	£1.00	9001	£5.00
68Q7	65p	30PL2	£1.00	9002	£5.00
68Q7	70p	30PL2	£1.00	9003	70p
68Q7	75p	30PL2	£1.00	9004	35p
68Q7	80p	30PL2	£1.00	9004	35p
68Q7	85p	30PL2	£1.00	9004	35p
68Q7	90p	30PL2	£1.00	9004	35p
68Q7	95p	30PL2	£1.00	9004	35p
68Q7	100p	30PL2	£1.00	9004	35p
68Q7	105p	30PL2	£1.00	9004	35p
68Q7	110p	30PL2	£1.00	9004	35p
68Q7	115p	30PL2	£1.00	9004	35p
68Q7	120p	30PL2	£1.00	9004	35p
68Q7	125p	30PL2	£1.00	9004	35p
68Q7	130p	30PL2	£1.00	9004	35p
68Q7	135p	30PL2	£1.00	9004	35p
68Q7	140p	30PL2	£1.00	9004	35p
68Q7	145p	30			

# ITS HERE! THE SUPER **PARTRIDGE PACKAGE** COMPLETE RADIO COMMUNICATION RECEIVING STATION

FOR ANY  
LOCATION  
AT HOME,  
CAMPING,  
BOATING ETC.

THE TREND LEADER **QR666 TRIO** SOLID STATE GEN. COVERAGE RECEIVER £139.62 delivered **FREE** (our risk), with **FREE** matching headphones—OR—**COMPLETE STATION** on the air in seconds—delivered (our risk) for **£157.58** **THE SUPER PARTRIDGE PACKAGE** comprises:—

- **QR666** receiver, 170kHz–30MHz, all bands, all modes. AM, SSB, CW, (opt. FM) for Mains, batteries, DC ext., a truly beautiful receiver for all purposes.
- **FREE** matching headphones, lightweight, comfortable, hygienic.
- World Record All Band patented **VFA** aerial in gold stove enamel, hammer finish (7' 6" long when assembled!)
- Made to match the **QR666**—the **JOYMATCH 111B** A.T.U. in gold stove enamel hammer finish case.
- All necessary cables.

**JOYSTICK VFA + JOYMATCH 111B** (for Trio, Eddystone, Yaesu Musen etc. receivers & LP.TX. **£29.58 del.**

**JOYSTICK VFA + JOYMATCH LO-Z 500** (with RF meter. Transmitting 500W P.EP input) **£36.27 del.**

**JOYSTICK VFA + JOYMATCH LO-Z 500X** (No RF meter. Transmitting 500W P.EP input) **£33.59 del.**

**JOYMATCH** tuned **AERIAL SYSTEM** for ANY M.W. and S.W. communications or solid state receiver **£5.87 del.**

**JOYMATCH** Artificial Earth for M.W. and S.W., as used on North Sea Oil Rigs **£5.87 del.**

Communications Headphones 8 ohm (suitable most modern comm. receivers) **£3.39 del.**

**VALVES:** Complete replacement set for 9R59DS & 9R59DE **£4.75 del.**

**AERIAL WIRE,** heavy duty 16 SWG enamelled aluminium, per 10 metres **£0.59 del.**

Send 4½p stamp for complete brochure **PARTRIDGE** and **TRIO**.



BOX 5 **PARTRIDGE**  
BROADSTAIRS KENT ENGLAND  
**ELECTRONIC LTD**


G3CED — G3VFA

FOR EXPERT ADVICE AND INFORMATION

Telephone: 0843 62535 or 62839  
evenings and weekends
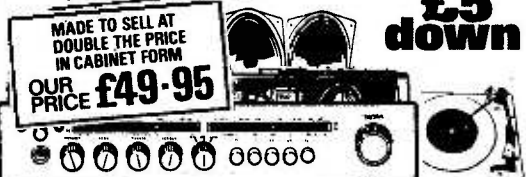
## QUALITY STEREO SOUND.

ALMOST **½ PRICE OFFER!** SOLENT AUDIO SYSTEM



**MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM**  
**OUR PRICE £49.95**  
**£5 down**

\*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. Power output 7 watts R.M.S. per channel (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8½" x 3¼". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49.95. Credit Sale £5.00 deposit 9 monthly payments of £5.75 (Total Credit price £56.75). P. & P. £2.50. Send £7.50 today.

Chassis only available for cash at £35.00.  
Full 12 months Guarantee.  
CALLERS WELCOME.

Stereo headphones supplied with every order.

**LEWIS radio** PW 11/74 100 CHASE SIDE SOUTHGATE LONDON N14 5PL Telephones: 01-886 9666/3733

## MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Rotary and Slide Switches, IP's, Tag Strips, Drive Drums, Coil Formers, Wire, Grommets, Relays, Pulley Wheels, Magnets, Transistor Panels, etc. Save yourself £'s on these well selected parcels, 6lb net weight £1.00, p.p 50p.

Brand New Wire-wound Resistors 1-7 watts, mostly Plessey GWS-1-3-5-7. Good selection. 100 for £1.00, p.p. 20p.

Mullard Ferrite Cores LA3 50p, LA4 75p, LA2100 50p.

SPECIAL OFFER. Metallised Polyester Capacitors by Erie, Mullard, etc. Values include -01/160V, -01/250V, -015/160V, -022/160, -033/160, -047/160V, -068/160V, -1/160-250V, -22/160V, etc. This is a bargain not to be missed. 100 for £1.50, p.p. 20p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene, Tremendously good selection. 300 for £1, p.p. 20p. Please add 8% V.A.T.

Mail Order Only.

**XEROZA RADIO,**  
1, EAST STREET, BISHOPS TAWTON, DEVON.

## MODULAR POWER AMPLIFIERS

**50 WATTS RMS.**

Power Output .... 50 watts rms 4Ω **£6.95 INC.**  
25 watts rms 8Ω **VAT, P & P.**

**H.T. Requirements** 25 to 65 volts  
**Power Response** ..15 Hz to 40kHz ± 3dB  
**T.H.D.** ..... < 0.25% (typical 0.15%) @ 1kHz  
**Input Sensitivity** .... 500mV  
Stereo pre-amp with 4 inputs, slider controls & illuminated input selection available shortly.

## ELLIOTT BLUNT AUDIO LTD.

40 York Street, Twickenham, Middx. Tel: 01-891-1692



# YATES ELECTRONICS

(FLITWICK) LTD.

DEPT P.W., ELSTOW STORAGE DEPOT  
KEMPSTON HARDWICK  
BEDFORD

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue sent free on request, 10p stamp  
appreciated.

PLEASE ADD 8% VAT

## RESISTORS

±1W and ±1W PIHER.  
±1W 2% ELECTROSIL.

Power watts	Tolerance	Range	Values available	Price
1	5%	4.7 Ω - 2.2M Ω	E24	1p
1	10%	3.3M Ω - 10M Ω	E12	0.8p
1	2%	10 Ω - 1M Ω	E24	3.5p
1	10%	1 Ω - 1M Ω	E12	1p
1	5%	4.7 Ω - 1M Ω	E12	0.8p
1	10%	1 Ω - 10 Ω	E12	5.5p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Piher resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5k Ω to 2M Ω, log or linear (log ±1W, lin ±1W).  
Single, 14p. Dual gang (stereo), 49p. Single D.P. switch, 29p.

## SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.  
mounting (0-1 matrix).  
Sub-miniature 0.1W, 6p each. Miniature 0.25W, 7p each.

## TRANSISTORS

AC107 16p	BC109 14p	BD115 75p	BF337 46p	ZTX300 18p
AC126 18p	BC115 16p	BD116 60p	BFY50 22p	ZTX302 20p
AC127 18p	BC116 15p	BD124 81p	BFY51 22p	ZTX341 18p
AC128 18p	BC117 25p	BD131 60p	BFY52 22p	ZTX500 18p
AC141K 22p	BC125 15p	BD132 64p	BRY39 41p	ZTX503 25p
AC142 25p	BC142 24p	BD140 66p	MJE340 47p	2N2646 60p
AC165 20p	BC143 21p	BDY32 57p	MJE370 68p	2N2904 28p
AD161 42p	BC147 12p	BF115 32p	OC26 90p	2N2905 32p
AC187 22p	BC148 12p	BF158 22p	OC28 90p	2N2926 12p
AC188 22p	BC149 12p	BF159 22p	OC35 90p	2N3053 31p
AC193K 28p	BC153 18p	BF160 23p	OC42 16p	2N3054 60p
AD140 53p	BC154 18p	BF161 26p	OC44 12p	2N3055 60p
AD143 73p	BC157 15p	BF164 22p	OC45 12p	2N3702 15p
AD149 70p	BC158 15p	BF177 28p	OC70 12p	2N3703 14p
AD161 42p	BC159 15p	BF177 28p	OC71 12p	2N3704 20p
AD162 42p	BC169 15p	BF178 43p	OC72 12p	2N3705 20p
AF114 25p	BC171 13p	BF179 41p	OC85 12p	2N3706 19p
AF115 25p	BC172 22p	BF180 42p	OC87 12p	2N3707 20p
AF116 25p	BC177 20p	BF181 32p	OC88 12p	2N3708 20p
AF117 25p	BC182 15p	BF182 41p	OC72 12p	2N3709 19p
AF118 50p	BC182L 16p	BF183 43p	ORP12 65p	2N3710 19p
AF121 50p	BC183 15p	BF184 32p	TIP29A 49p	2N3711 19p
AF126 50p	BC183L 16p	BF185 32p	TIP30A 58p	2N3819 32p
AF127 50p	BC184 18p	BF194 14p	TIP31A 62p	2N4062 25p
AF139 53p	BC186 25p	BF195 17p	TIP32A 74p	40360 46p
AF178 48p	BC187 25p	BF196 15p	TIP33A 98p	40361 43p
AF180 50p	BC212 13p	BF197 16p	TIP34A 148p	40362 45p
AF186 30p	BC212L 15p	BF200 40p	TIP41A 79p	40363 88p
AF239 48p	BC214L 19p	BF259 25p	TIP42A 90p	40406 44p
BC107 13p	BCY70 21p	BF262 26p	TIP43 35p	40486 90p
BC108 13p	BD112 52p	BF263 26p	ZTX108 18p	

## ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

## WIRE WOUND POTS. 3W, 10

25, 50Ω and decades to 100kΩ, 50p.

## DIODES

### RECTIFIER

DIODE	VOLTS	CURRENT	SIGNAL	PRICE
BY127	1250V	1A	OAS5	7p
IN4001	50V	1A	OAS9	5p
IN4002	100V	1A	OAS9	5p
IN4004	400V	1A	OAS20	7p
IN4006	800V	1A	IN4148	5p
IN4007	1000V	1A	BA114	8p

## SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.  
SINGLE 10K, 25K, 100K log. or lin. 50p.  
DUAL GANG, 10K + 10K etc. log. or lin. 60p.  
KNOB FOR ABOVE, 12p.  
FRONT PANEL, 90p.

18 Gauge panel 12in x 4in with slots cut for use  
with slider pots. Grey or matt black finish complete  
with fixings for 4 pots.

## BRUSHED

### ALUMINIUM

### PANELS

12in x 6in. 37p.

12in x 2½in. 14p.

9in x 2in. 12p.

## THYRISTORS

2N5060	50V 0.8A	65p	106F	50V	5A	55p
2N5064	200V 0.8A	80p	106D	200V	5A	80p

## HEATSINKS—REDPOINT

2W	24p	4W	45p	TO5 Clip	5p	TO1 Single	5p
3W	36p	6W	60p	TO18 Clip	5p	TO1 Double	8p

## TRANSFORMERS All have 240V primary

MT30/2	0-12-15-20-24-30V	2A	£3.85
MT50/±	0-12-15-20-24-30V	±A	£2.50
MT50/±	0-19-25-33-40-50V	±A	£3.15
MT50/2	0-19-25-33-40-50V	2A	£4.20
MT60/±	0-24-30-40-48-60V	±A	£3.30
MT60/±	0-24-30-40-48-60V	±A	£4.80
MT60/2	0-24-30-40-48-60V	2A	£6.50

## MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. Mounting: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 3½p. 0.068μF 4p. 0.1μF 4½p. 0.15μF 5p. 0.22μF 5½p. 0.33μF 7p. 0.47μF 9p. 0.68μF 12p. 1.0μF 14½p. 1.5μF 22p. 2.2μF 26p.

## MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 3p. 0.04μF, 0.05μF, 0.068μF, 0.1μF, 6p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

## ELECTROLYTIC CAPACITORS

(μF/V) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p. 47/63, 100/40, 150/25, 220/25, 330/10, 470/6.3, 7p. 68/63, 150/40, 220/40, 330/16, 1000/4, 10p. 470/10, 680/6.3, 11p. 100/63, 150/63, 220/63, 1000/10, 12p. 470/25, 680/16, 1500/6.3, 13p. 470/40, 680/25, 1000/16, 1500/10, 2200/6.3, 18p. 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6.3, 4700/4, 21p.

## SOLID TANTALUM BEAD CAPACITORS

0.1μF	35V	2.2μF	35V	22μF	16V	12p
0.22μF	35V	4.7μF	35V	33μF	10V	
0.47μF	35V	6.8μF	25V	47μF	6.3V	
1.0μF	35V	10μF	25V	100μF	3V	

## VEROBOARD

2½ x 3½	0.1	0.15	Standard screened	32p	2.5mm insulated	13p
2½ x 5	26p	28p	Standard insulated	18p	3.5mm insulated	13p
3½ x 3	28p	28p	Stereo screened	44p	3.5mm screened	22p
3½ x 5	28p	28p	Standard socket	15p	2.5mm socket	14p
3½ x 5	34p	34p	Stereo socket	22p	3.5mm socket	14p
17 x 2½	95p	77p				
17 x 3½	130p	108p				
17 x 3½ (plain)	86	72p				
17 x 2½ (plain)	—	51p				
2½ x 5 (plain)	—	18p				
2½ x 3½ (plain)	—	15p				
Pin insertion tool	62p	62p				
Spot face cutter	52p	52p				
Pkt. 50 pins	20p	20p				

## JACK PLUGS AND SOCKETS

Standard screened	32p	2.5mm insulated	13p
Standard insulated	18p	3.5mm insulated	13p
Stereo screened	44p	3.5mm screened	22p
Standard socket	15p	2.5mm socket	14p
Stereo socket	22p	3.5mm socket	14p

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plug 12p. Socket 8p.  
4 way screened cable, 26p/metre.  
6 way screened cable, 32p/metre.

## BATTERY ELIMINATOR

9V mains power supply. Same size as PP9 battery. £1.70

## HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF	16p	0.047μF	16p	0.22μF	25p
0.022μF	14p	0.1μF	20p	0.47μF	36p

## POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series Values, 4p each.

## SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs oxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector. Detector GDI £2. Smoke and Gas Detector Kits, mains operated with audible alarm £5.60. Mains operated Meter Indicator £7.90. Mains/Battery Gas Leak Detector £12.60. 12.24V Battery operated £8.40. 12V Battery operated Two Remote Sensors £12.80. NOTE: The battery operated kits incorporate our patented circuit to minimise battery drain. Typically 120mA for 12V. These kits contain all parts required with the exception of case. Suitable case mains operated kit £1.60. Battery operated kits £5.

## PRINTED BOARD MARKER

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief. 97p

## METERS

2" Scale-500μA, 1mA, 10mA, 100mA £3.30

## BULGIN MAINS CONNECTORS

3 Pin 1½A	Chassis Plug	18p	3 Pin 1½A	Chassis Socket	30p
	Line Socket	22p		Line Plug	24p
3 Pin 3A	Chassis Plug	24p	3 Pin 3A	Chassis Socket	34p
	Line Socket	28p		Line Plug	40p
3 Pin 5A	Chassis Plug	24p			
	Line Socket	32p	2 Pin 5A	Line Plug	20p

## THERMISTORS

VA1005	15p
VA1026	15p
VA1033	15p
VA10555	15p
VA10665	15p
VA1077	15p
R53	£1.25

## ROTARY MAINS SWITCH

D.P. 2A 35p

## LINEAR IC's

709	14 pin DIL	40p
741	8 pin DIL	40p
741	14 pin DIL	38p
723	14 pin DIL	95p
747	14 pin DIL	85p
748	8 pin DIL	45p

## WAVECHANGE SWITCH 33p

1p 12W, 3p 4W, 2p 2W, 2p 6W, 4p 3W

DIL Sockets 14 pin and 16 pin 16p



# The largest selection

## BRAND NEW FULLY GUARANTEED DEVICES

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	0-20	AD162	0-39	BC149	0-18	BD124	0-76	BF181	0-33	MAT121	0-22	2G306	0-44	2N2180	0-66	2N3055	0-85	2N4059	0-11
AC113	0-20	AD161	0-20	BC150	0-20	BD131	0-85	BF182	0-44	MJE2065	0-95	2G309	0-35	2N2182	0-39	2N3059	0-18	2N4060	0-13
AC115	0-22	AD162(MP)	75	BC151	0-22	BD132	0-86	BF183	0-44	MJE3055	0-82	2G310	0-39	2N2183	0-39	2N3061	0-18	2N4061	0-13
AC117K	0-32	AD170	0-55	BC152	0-19	BD133	0-72	BF184	0-28	MJE3440	0-55	2G319	0-22	2N2194	0-39	2N3092	0-16	2N4062	0-13
AC122	0-18	AF114	0-27	BC153	0-31	BD135	0-44	BF185	0-33	MFF102	0-46	2G339A	0-18	2N2217	0-29	2N3393	0-16	2N4284	0-10
AC125	0-19	AF115	0-27	BC154	0-33	BD136	0-44	BF187	0-40	MFF104	0-41	2G344	0-20	2N2218	0-22	2N3394	0-16	2N4285	0-10
AC126	0-19	AF116	0-27	BC157	0-20	BD137	0-50	BF189	0-38	MFF105	0-41	2G345	0-18	2N2219	0-22	2N3395	0-16	2N4286	0-10
AC127	0-20	AF117	0-27	BC158	0-13	BD138	0-55	BF194	0-18	OC23	0-70	2G371B	0-16	2N2220	0-24	2N3402	0-23	2N4287	0-10
AC128	0-20	AF118	0-39	BC159	0-13	BD139	0-51	BF195	0-18	OC22	0-52	2G373	0-19	2N2222	0-22	2N3404	0-21	2N4288	0-10
AC132	0-16	AF124	0-33	BC160	0-50	BD140	0-66	BF196	0-16	OC23	0-54	2G374	0-19	2N2268	0-19	2N3405	0-46	2N4290	0-10
AC134	0-16	AF125	0-33	BC161	0-55	BD155	0-88	BF197	0-16	OC24	0-62	2G377	0-33	2N2369	0-16	2N3414	0-17	2N4291	0-10
AC137	0-16	AF126	0-31	BC167	0-13	BD175	0-66	BF200	0-50	OC25	0-42	2G378	0-18	2N2369A	0-16	2N3415	0-17	2N4292	0-10
AC141	0-20	AF127	0-31	BC168	0-18	BD176	0-66	BF222	\$1.05	OC26	0-42	2G381	0-18	2N2411	0-27	2N3416	0-31	2N4293	0-10
AC141K	0-32	AF139	0-33	BC169	0-18	BD177	0-72	BF257	0-60	OC28	0-55	2G382	0-18	2N2412	0-27	2N3417	0-31	2N4294	0-10
AC142	0-20	AF178	0-55	BC170	0-13	BD178	0-72	BF258	0-66	OC29	0-55	2G401	0-33	2N2846	0-23	2N3614	0-21	2N4295	0-10
AC142K	0-28	AF179	0-55	BC171	0-16	BD179	0-77	BF259	0-94	OC29	0-55	2G411	0-33	2N2847	0-23	2N3617	0-21	2N4296	0-10
AC151	0-17	AF180	0-55	BC172	0-16	BD180	0-77	BF262	0-61	OC35	0-45	2G414	0-33	2N2848	0-23	2N3618	0-21	2N4547	0-35
AC154	0-22	AF181	0-55	BC173	0-16	BD185	0-72	BF263	0-61	OC36	0-55	2G417	0-28	2N2712	0-23	2N3615	0-82	2N4548	0-35
AC155	0-22	AF186	0-55	BC174	0-16	BD186	0-72	BF270	0-89	OC41	0-22	2N388	0-39	2N2714	0-23	2N3616	0-82	2N4549	0-35
AC156	0-22	AF239	0-41	BC175	0-24	BD187	0-72	BF271	0-83	OC42	0-27	2N388A	0-61	2N2904	0-19	2N3644	0-10	2N6221	0-75
AC157	0-27	AL102	0-72	BC177	0-21	BD188	0-77	BF272	0-83	OC43	0-27	2N404	0-17	2N2905	0-23	2N3702	0-10	2N6222	0-75
AC165	0-22	AL103	0-72	BC178	0-21	BD189	0-83	BF273	0-89	OC45	0-14	2N404A	0-31	2N2905	0-23	2N3703	0-18	2N6223	0-75
AC166	0-22	ASV26	0-28	BC179	0-21	BD190	0-83	BF274	0-89	OC70	0-11	2N524	0-46	2N2905A	0-23	2N3704	0-14	2N6224	0-75
AC167	0-22	ASV27	0-28	BC180	0-27	BD195	0-94	BFW10	0-66	OC71	0-11	2N527	0-54	2N2906	0-17	2N3705	0-13	2N6225	0-75
AC168	0-27	ASV28	0-28	BC181	0-27	BD196	0-94	BFX29	0-80	OC72	0-16	2N598	0-46	2N2906A	0-20	2N3706	0-13	2N6226	0-77
AC169	0-18	ASV29	0-28	BC182	0-16	BD197	0-99	BFX24	0-24	OC74	0-16	2N599	0-50	2N2907	0-24	2N3707	0-14	2N6227	0-77
AC176	0-22	ASV50	0-28	BC182L	0-16	BD198	0-99	BFX25	0-24	OC76	0-17	2N696	0-14	2N2907A	0-24	2N3708	0-09	2N6228	0-77
AC177	0-27	ASV51	0-28	BC183	0-16	BD199	\$1.05	BFX26	0-24	OC77	0-17	2N697	0-17	2N2908	0-14	2N3709	0-10	2N6229	0-77
AC178	0-31	ASV52	0-28	BC183L	0-16	BD200	\$1.05	BFX27	0-27	OC78	0-22	2N698	0-27	2N2909	0-16	2N3710	0-10	2N6230	0-77
AC179	0-31	ASV54	0-28	BC184	0-22	BD205	0-88	BFX28	0-24	OC81	0-17	2N699	0-39	2N2926	0-16	2N3711	0-10	2N6232	0-46
AC180	0-22	ASV55	0-28	BC184L	0-22	BD206	0-88	BFY59	0-22	OC81D	0-17	2N706	0-09	2N2926(G)	14	2N3819	0-01	2N6232A	0-66
AC180K	0-32	ASV56	0-28	BC185	0-16	BD247	\$1.05	BFY51	0-22	OC82	0-17	2N706A	0-10	2N2926(Y)	12	2N3820	0-65	2N6232B	0-66
AC181	0-22	ASV57	0-28	BC187	0-31	BD208	\$1.05	BFY52	0-22	OC83	0-22	2N706B	0-13	2N2926(X)	11	2N3821	0-39	2N6232C	0-77
AC181K	0-32	ASV58	0-28	BC207	0-12	BDY20	\$1.10	BFY53	0-19	OC83	0-22	2N711	0-09	2N2926(Z)	11	2N3822	0-39	2N6232D	0-77
AC187	0-24	ASV73	0-28	BC208	0-12	BF115	0-27	BSX19	0-17	OC139	0-22	2N717	0-39	2N2926(B)	11	2N3903	0-31	2N6232E	0-77
AC187K	0-25	ASV71	0-44	BC209	0-13	BF117	0-50	BSX20	0-17	OC140	0-22	2N718	0-27	2N3010	0-77	2N3904	0-33	2N6232F	0-77
AC188	0-24	BC107	0-14	BC212L	0-14	BF118	0-77	BSY25	0-17	OC169	0-28	2N718A	0-55	2N3011	0-16	2N3905	0-31	2N6232G	0-77
AC188K	0-25	BC108	0-14	BC213L	0-14	BF119	0-77	BSY26	0-17	OC170	0-28	2N726	0-31	2N3058	0-19	2N3906	0-31	2N6232H	0-77
AC197	0-28	BC109	0-15	BC214L	0-18	BF121	0-50	BSY27	0-17	OC77	0-28	2N727	0-31	2N3064	0-07	2N4061	0-13	40362	0-50
AC198	0-22	BC113	0-11	BC225	0-28	BF123	0-55	BSY28	0-17	OC200	0-28	2N743	0-25						
AC199	0-22	BC114	0-17	BC226	0-39	BF125	0-50	BSY29	0-17	OC201	0-31	2N744	0-22						
AC200	0-22	BC115	0-17	BC301	0-30	BF127	0-55	BSY38	0-20	OC202	0-31	2N914	0-16						
AC201	0-22	BC116	0-17	BC302	0-27	BF128	0-61	BSY39	0-20	OC203	0-28	2N918	0-33	Type Price	Type Price	Type Price	Type Price	Type Price	Type Price
AC202	0-22	BC117	0-17	BC303	0-18	BF129	0-60	BSY40	0-20	OC204	0-28	2N929	0-23	AA119	0-09	BY128	0-17	OA10	0-15
AC203	0-22	BC118	0-11	BC304	0-40	BF154	0-50	BSY41	0-31	OC205	0-28	2N930	0-23	AA120	0-09	BY130	0-18	OA17	0-08
AC208	0-21	BC119	0-33	BC440	0-34	BF155	0-77	BSY95	0-14	OC206	0-44	2N930	0-23	AA129	0-09	BY133	0-28	OA70	0-08
AC209	0-39	BC120	0-38	BC460	0-40	BF156	0-53	BSY95A	0-14	OC209	0-44	2N131	0-44	AA131	0-09	BY140	0-45	OA71	0-08
AC230	0-31	BC125	0-18	BCY30	0-27	BF157	0-61	CI11E	\$2.20	OC211	0-48	2N132	0-24	AA132	0-11	BY139/300	0-45	OA81	0-08
AC231	0-31	BC126	0-20	BCY31	0-29	BF158	0-61	CI11E	0-55	OC212	0-48	2N132	0-16	AA133	0-11	BY140	0-39	OA85	0-10
AC232	0-31	BC127	0-20	BCY32	0-38	BF159	0-66	C400	0-33	OC213	0-48	2N1303	0-16	AA134	0-11	BY141	0-39	OA90	0-07
AC233	0-31	BC128	0-20	BCY33	0-40	BF160	0-44	C401	0-33	OC214	0-48	2N1304	0-19	AA135	0-11	BY142	0-39	OA91	0-07
AC234	0-31	BC129	0-20	BCY34	0-28	BF162	0-44	C424	0-33	OC215	0-48	2N1305	0-19	AA136	0-11	BY143	0-39	OA95	0-08
AC235	0-31	BC130	0-20	BCY35	0-18	BF163	0-44	C425	0-55	OC216	0-48	2N1307	0-23	AA137	0-11	BY144	0-39	OA96	0-08
AC236	0-31	BC131	0-13	BCY36	0-28	BF164	0-44	C426	0-39	OC217	0-48	2N1308	0-26	AA138	0-11	BY145	0-39	OA97	0-08
AC237	0-31	BC132	0-17	BCY71	0-22	BF165	0-44	C428	0-39	OC218	0-48	2N1309	0-26	AA139	0-11	BY146	0-39	OA98	0-08
AC238	0-31	BC133	0-17	BCY72	0-22	BF166	0-44	C428	0-39	OC219	0-48	2N1310	0-26	AA140	0-11	BY147	0-39	OA99	0-08
AC239	0-31	BC134	0-13	BCY73	0-22	BF167	0-44	C441	0-33	OC220	0-48	2N1311	0-22	AA141	0-11	BY148	0-39	OA100	0-08
AD130	0-42	BC140	0-33	BCZ10	0-28	BF170	0-39	C442	0-33	OC221	0-48	2N1312	0-22	AA142	0-11	BY149	0-39	OA101	0-08
AD140	0-53	BC141	0-33	BCZ11	0-28	BF171	0-39	C443	0-33	OC222	0-48	2N1313	0-22	AA143	0-11	BY150	0-39	OA102	0-08
AD142	0-53	BC142	0-33	BCZ12	0-28	BF172	0-39	C444	0-33	OC223	0-48	2N1314	0-22	AA144	0-11	BY151	0-39	OA103	0-08
AD143	0-42	BC143	0-33	BD115	0-68	BF177	0-39	C450	0-24	OC224	0-48	2N1315	0-22	AA145	0-11	BY152	0-39	OA104	0-08
AD145	0-55	BC145	0-30	BD116	0-68	BF178	0-33	C451	0-24	OC225	0-48	2N1316	0-22	AA146	0-11	BY153	0-39	OA105	0-08
AD149	0-55	BC147	0-11	BD121	0-66	BF179	0-33	C452	0-24	OC226	0-48	2N1317	0-22	AA147	0-11	BY154	0-39	OA106	0-08
AD161	0-39	BC148	0-11	BD123	0-72	BF180	0-33	MAT100	0-21	OC227</									

# -the lowest prices!

## P.W. TELE-TENNIS KIT OF PARTS

Including all resistors, capacitors, semi-conductors, I.C. sockets, switches and transformer

Our Usual Price £27.50

### SPECIAL OFFER

£23.50 incl. V.A.T. and P. & P.

We regret free pack not applicable to this offer

#### ND 120 NIXIE DRIVER TRANSISTOR.

Suitable replacement for BSX 21, C 407, 2N 1893 120evb.

1	25	100+
0-19	0-17	0-18

Sil. trans. suitable for P.E. Organ. Metal TO-18

Eqvt. ZXK900 6p each. Any Qty.

#### GP 100 TO3 METAL CASE GERMANIUM

V<sub>beo</sub> = 80V. V<sub>ceo</sub> = 50V. I<sub>C</sub> = 10 amps. P<sub>tot</sub> = 30W. h<sub>fe</sub> = 80-170.

Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0-47	0-44	0-40

#### GP 300 TO3 METAL CASE SILICON

V<sub>beo</sub> = 100V. V<sub>ceo</sub> = 60V. I<sub>C</sub> = 15 amps. P<sub>tot</sub> = 115W. h<sub>fe</sub> = 20, 100T, = 1MHz. Suitable replacement for 2N 3055, BDY 11 or BDY 20.

1	25	100+
0-55	0-53	0-51

#### NEW 8th EDITION 250 pages

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. £1.85 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

SIL. G.P. DIODES 4p  
300mW 30 0-55  
40PIV(Min.) 100 1-85  
Sub-Min. 500 5-50  
Fully Tested, 1,000 9-90  
Ideal for Organ Builders.

### AD161/162

M/P COMP GERM. PNP TRANS. OUR LOW. BEST PRICE OF 75p PER PAIR.

## LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS ADVERTISEMENTS

PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-33V. 400mV (DO-7 Case) 12p ea. 1 1/2W (Top-Hat) 18p ea. 10W (SO-10 Stud) 32p ea.

## 555 I.C. 75p each

### MAMMOTH I.C. PACK

APPROXIMATELY 200 PIECES ASSORTED MANUFACTURERS FALL-OUT INTEGRATED CIRCUITS INCLUDING LOGIC 74 SERIES LINEAR and AUDIO AMPLIFIERS

MANY CODED also SOME UNKNOWN TYPES - YOU TO IDENTIFY

PAK NO. M.I.C. 200

PRICE £1.25 per PAK including p & p & V.A.T.

### QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price 4p
Q1	20 Red spot transistors PNP	0-55
Q2	16 White spot R.F. transistors PNP	0-55
Q3	4 OC 77 type transistors	0-55
Q4	6 Matched transistors OC44/45/81/81D	0-55
Q5	4 OC 75 transistors	0-55
Q6	5 OC 72 transistors	0-55
Q7	4 AC 128 transistors PNP high gain	0-55
Q8	4 AC 126 transistors PNP	0-55
Q9	7 OC 81 type transistors	0-55
Q10	7 OC 71 type transistors	0-55
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0-55
Q12	2 AF 116 type transistors	0-55
Q13	2 AF 117 type transistors	0-55
Q14	3 OC 171 R.F. type transistors	0-55
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0-55
Q17	5 NPN 2 x ST.141 & 3 x ST.140	0-55
Q18	4 MADD'S 2 x MAT 100 & 2 x MAT 121	0-55
Q19	3 MADD'S 2 x MAT 101 & 1 x MAT 102	0-55
Q20	4 OC 44 Germanium transistors A.F.	0-55
Q21	4 AC 127 NPN Germanium transistors	0-55
Q22	20 NKT transistors A.F. R.F. coded	0-55
Q23	10 OA 202 Silicon diodes sub-min.	0-55
Q24	8 OA 81 diodes	0-55
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0-55
Q26	8 OA95 Germanium diodes sub-min IN69	0-55
Q27	2 10A PIV Silicon rectifiers IS42ER	0-55
Q28	2 Silicon power rectifiers BYZ 13	0-55
Q29	4 Silicon transistors 2 x 2N896, 1 x 2N897, 1 x 2N898	0-55
Q30	7 Silicon switch transistors 2N706 NPN	0-55
Q31	6 Silicon switch transistors 2N708 NPN	0-55
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0-55
Q33	3 Silicon NPN transistors 2N1711	0-55
Q34	7 Silicon NPN transistors 2N2369, 500MHz (code P397)	0-55
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0-55
Q36	7 2N3846 TO-18 plastic 300 MHz NPN	0-55
Q37	3 2N3055 NPN Silicon transistors	0-55
Q38	7 NPN transistors 3 x 2N3703, 2 x 2N3702	0-55

### KING OF THE PAKS Unequaled Value and Quality

## SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price 4p
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-55
U 2	Mixed Germanium Transistors AF/RF	0-55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-55
U 4	Germanium Transistors like OC81, AC128	0-55
U 5	60 200mA Sub-Min. Silicon Diodes	0-55
U 6	30 Sil. Planar Trans. NPN like BSY95A, 2N705	0-55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000 0-55	
U 8	80 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-55
U10	20 BA750 charge storage Diodes DO-7 Glass	0-55
U11	PNP Sil. Planar Trans. TO-5 like 2N1122, 2N2904	0-55
U13	30 PNP-NPN Sil. Transistors OC200 & 28 104	0-55
U14	150 Mixed Silicon and Germanium Diodes	0-55
U15	NPN Sil. Planar Trans. TO-5 like BFY81, 2N697	0-55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-55
U19	Silicon NPN Transistors like BC108	0-55
U20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-55
U21	20 AF, Germanium Alloy Transistors 2G300 Series & OC71	0-55
U23	MADD'S like MHz Series PNP Transistors	0-55
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-55
U25	25 300 MHz NPN Silicon Transistors 2N708, BSY27	0-55
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-55
U29	10 1 Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	1-10
U32	25 Zener Diodes 400mV DO-7 case 3-15 volts mixed	0-55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0-55
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-55
U36	Silicon Planar NPN Transistors TO-5 BFY75/51/52	0-55
U37	30 Silicon Alloy Transistors 80-3 PNP OC200, 35322	0-55
U38	20 Fast Switching Silicon Trans. 2N1302/5 TO-5	0-55
U39	30 RF, Germ. PNP Transistors 2N1302/5 TO-5	0-55
U40	10 Dual Transistors 6 lead TO-5 2N2080	0-55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC118/114	0-55
U44	20 Sil. Trans. Plastic TO-5 BC118/116	0-55
U45	7 3A SCR. TO66 up to 600PIV	1-10
U46	20 Unijunction transistors similar to T1843	0-55
U47	10 TO220AB plastic triacs 50V 8A	£1.10
U48	9 NPN Sil. power transistors like 2N3055	£1.10
U49	12 NPN Sil. plastic power trans. 60W like 2N2924/2926	£1.10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

### FREE

One 55p Pak of your own choice free with orders valued £4 or over

### CADMIUM CELLS

ORP12 48p

### SIL. RECTS. TESTED

PIV 300mA 750mA 1A	1-5A 3A	10A 30A
50 0-05 0-06	IN4001 0-05 0-08 0-15 0-21 0-80	
100 0-05 0-07	IN4002 0-06 0-10 0-17 0-23 0-75	
200 0-06 0-10	IN4003 0-07 0-12 0-23 0-26 1-00	
400 0-08 0-15	IN4004 0-08 0-15 0-30 0-28 1-85	
600 0-08 0-17	IN4005 0-10 0-18 0-36 0-45 1-90	
800 0-12 0-18	IN4006 0-11 0-20 0-35 0-55 2-10	
1000 0-14 0-30	IN4007 0-12 0-25 0-45 0-85 2-50	
1200 - 0-35		0-30 0-58 0-75 3-00

### NEW LOW PRICED TESTED S.C.R.'s

PIV1A 3A 5A 5A 7A 10A 16A 30A
TO5 TO86TO66TO64TO48TO48TO48TO48
50 0-26 0-28 0-39 0-39 0-52 0-55 0-59 1-27
100 0-28 0-37 0-52 0-62 0-55 0-64 0-70 1-54
200 0-39 0-41 0-54 0-54 0-63 0-67 0-83 1-76
400 0-48 0-52 0-62 0-62 0-74 0-83 1-03 1-93
800 0-69 0-63 0-75 0-75 0-85 1-07 1-38
800 0-70 0-77 0-88 0-88 0-99 1-32 1-65 4-40

### DIACS

FOR USE WITH TRIACS	BR100 (D32) 25p each
10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each	

### TRIACS

VBOM 2A 6A 10A	TO-5 TO-6 TO-48	D	P	4p
100	33	55	58	
200	55	66	99	
400	77	88	1-21	

### INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No. Contents Price	Pak No. Contents Price	Pak No. Contents Price
UIC00 - 12 x 7400 0-55	UIC46 - 5 x 7446 0-55	UIC90 - 5 x 7490 0-55
UIC01 - 12 x 7401 0-55	UIC48 - 5 x 7448 0-55	UIC91 - 5 x 7491 0-55
UIC02 - 12 x 7402 0-55	UIC50 - 12 x 7450 0-55	UIC92 - 5 x 7492 0-55
UIC03 - 12 x 7403 0-55	UIC51 - 12 x 7451 0-55	UIC93 - 5 x 7493 0-55
UIC40 - 12 x 7404 0-55	UIC53 - 12 x 7453 0-55	UIC94 - 5 x 7494 0-55
UIC04 - 12 x 7406 0-55	UIC54 - 12 x 7454 0-55	UIC95 - 5 x 7495 0-55
UIC06 - 8 x 7406 0-55	UIC50 - 12 x 7450 0-55	UIC96 - 5 x 7496 0-55
UIC07 - 8 x 7407 0-55	UIC70 - 8 x 7470 0-55	UIC100 - 5 x 74100 0-55
UIC10 - 12 x 7410 0-55	UIC72 - 8 x 7472 0-55	UIC121 - 5 x 74121 0-55
UIC20 - 12 x 7420 0-55	UIC73 - 8 x 7473 0-55	UIC141 - 5 x 74141 0-55
UIC30 - 12 x 7430 0-55	UIC74 - 8 x 7474 0-55	UIC181 - 5 x 74181 0-55
UIC40 - 12 x 7440 0-55	UIC76 - 8 x 7476 0-55	UIC184 - 5 x 74184 0-55
UIC41 - 5 x 7406 0-55	UIC80 - 5 x 7480 0-55	UIC192 - 5 x 74192 0-55
UIC42 - 5 x 7442 0-55	UIC81 - 5 x 7481 0-55	UIC199 - 5 x 74199 0-55
UIC43 - 5 x 7443 0-55	UIC82 - 5 x 7482 0-55	
UIC44 - 5 x 7444 0-55	UIC83 - 5 x 7483 0-55	UICXI - 25 Assorted
UIC45 - 5 x 7445 0-55	UIC86 - 5 x 7486 0-55	74's £1.65

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

2 Amp. BRIDGE RECTS.	50 v RMS 85p each
100 v RMS 40p	
200 v RMS 45p	
400 v RMS 50p	
1,000 v RMS 55p	
Size 16 mm x 16 mm.	

D1699 NPN SILICON DUAL TRANSISTOR (Similar to 2N2060)	1 25 100+	0-28 0-26 0-24
---	-----------	----------------

LINEAR INTEGRATED CIRCUIT PAKS	ULIC709 10 x 709	ULIC710 7 x 710	ULIC741 7 x 741	ULIC747 5 x 747	ULIC748 7 x 748
	0-55	0-55	0-55	0-55	0-55

# BI-PAK

Giro No. 388-7006 Please send all orders direct to warehouse and despatch department

P.O. BOX 6, WARE, HERTS  
Postage and packing add 15p. Overseas add extra for airmail.  
Minimum order 55p. Cash with order please.  
Guaranteed Satisfaction or Money Back



# Newnes - Butterworths

## Books on Radio, TV, Electronics etc . . .

- BEGINNER'S GUIDE TO ELECTRONICS—3rd Edn. Squires and Deason £1-90
- BEGINNER'S GUIDE TO RADIO—7th Edn. King. £1-00
- BEGINNER'S GUIDE TO TELEVISION—5th Edn. King. £1-60
- BEGINNER'S GUIDE TO TRANSISTORS. Reddihough. £1-00
- FM RADIO SERVICING HANDBOOK—2nd Edn. King. £3-00
- FOUNDATIONS OF WIRELESS AND ELECTRONICS—8th Edn. Scroggie. £3-00, limp £1-80
- 110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR. Marston. Cased £1-80, limp £1-20
- 110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR. Marston. Cased £1-80, limp £1-20
- 110 THYRISTOR PROJECTS USING SCRs AND TRIACS. Marston. Cased £2-40, limp £1-40
- PRACTICAL WIRELESS CIRCUITS—18th edn. The Technical Staff of 'Practical Wireless'. £1-20
- PRINCIPLES OF TRANSISTOR CIRCUITS—4th edn. Amos. Cased £3-00, limp £1-50
- QUESTIONS AND ANSWERS ON ELECTRONICS. Brown. £0-75
- QUESTIONS AND ANSWERS ON INTEGRATED CIRCUITS. Hibberd. £0-75
- QUESTIONS AND ANSWERS ON RADIO AND TELEVISION—3rd Edn. Hellyer. £0-75
- QUESTIONS AND ANSWERS ON TRANSISTORS—3rd Edn. Brown. £0-75
- RADIO AND ELECTRONIC HANDBOOK. Wilding. £1-20
- RADIO VALVE AND TRANSISTOR DATA—9th Edn. Ball. £0-75
- RAPID SERVICING OF TRANSISTOR EQUIPMENT—2nd Edn. King. £1-90
- TRANSISTOR POCKET BOOK. Hibberd. £1-40
- 20 SOLID STATE PROJECTS FOR THE CAR AND GARAGE. Marston. Cased £1-80, limp £1-20
- 20 SOLID STATE PROJECTS FOR THE HOME. Marston. Cased £1-60, limp £1-00
- WIRELESS SERVICING MANUAL—10th Edn. Cocking. £1-50

All these books, and many more, are available from

## BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, YORKSHIRE. Telephone: 0423-55885

Please add 10% for Postage and Packing on all books. Send large S.A.E. for FREE booklists. Open until 6 pm Daily and 8 pm Saturday

## BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX  
All prices inclusive of V.A.T. Telephone 6743

0B2	40	6BC8	80	6L7	50	1Q7GT	45	35ZAGT	70	E80CC	2-80	RCL83	70	EY91	58	PCL82	86	UBF89	40	Transistors	AF115	17	BYZ12	28
0Z4	47	6BE6	85	6L18	55	128C7	50	35Z8GT	75	E80F	1-20	ECL84	80	EZ40	70	PCL83	86	UBL21	77	& Diodes	AF117	21	BYZ13	38
1A3	45	6BH6	75	6L19	3-00	128G7	40	43	1-00	E83F	1-20	ECL85	80	EZ41	75	PCL84	49	UC92	45	1N4744	15	AF121	38	
1A6GT	50	6BJ6	55	6LD20	75	128H7	35	50B5	85	E88CC	75	ECL86	40	EZ80	28	PCL85	47	UC95A	75	2N4004	20	AF124	28	
1A7GT	85	6BQ7A	55	6N7GT	80	128J7	44	50C5	45	E92CC	1-00	EF22	1-50	EZ81	28	PCL86	60	UC98	45	2N986	58	AF125	19	
1B8GT	50	6BR7	1-00	6Q7G	50	128K7	85	50D6C1	1-25	E180F	1-00	EF23	1-50	GZ32	54	PEN45	30	UCF80	70	2N1756	55	AF126	20	
1H8GT	55	6BR8	1-50	6Q7GT	80	128L7	75	80E8B	85	E192CC	1-00	EF24	1-50	GZ37	1-00	PEN46	50	UCF81	40	2N2147	94	AF180	58	
1L4	68	6C7	1-40	6Q7MT	55	1A37	85	80L46	85	E146	85	EF25	1-00	HZ81	25	PEN48	30	UCF82	38	2N2813	48	BA115	15	
1N6GT	45	6BW6	90	6R7G	80	1A57	80	85A2	80	E450	87	EF26	1-00	HZ82	80	PEN49	30	UCF83	65	2N3053	88	BA129	14	
1R5	45	6BW7	74	6R7M	75	19A4	50	85A3	1-00	E476	1-00	EF27	1-00	HZ83	80	PENDD	30	UCF84	70	2N3121	276	BA130	11	
1R4	38	6BZ6	49	6SA7	44	19G6	1-40	90A9	2-50	EABC80	38	EF28	1-00	HZ84	80	PEN49	30	UCF85	40	2N3703	21	BA131	17	
1U4	40	6CB6A	40	68C7GT	38	20D4	2-00	90C1	75	EAC91	75	EF29	37	HL1D	82	PEN50	40	UCF86	35	2N3709	22	BC107	14	
1U5	75	6C4	35	68G7	44	20P2	75	90C2	2-40	EAF42	75	EF30	37	HL42	70	PEN50	40	UCF87	50	2N3709	22	BC108	14	
1D1	40	6C6	40	68HT	44	20L1	88	10B32	75	EAF61	75	EF31	37	HL43	70	PEN50	40	UCF88	50	2N3709	22	BC109	11	
2GK5	55	6C8	1-50	68J7	55	20P3	80	10B37	80	EAF61	75	EF32	37	HL44	70	PEN50	40	UCF89	50	2N3709	22	BC110	11	
2X2	50	6CD6G	1-25	68K7GT	44	20P4	1-00	807	59	E81	20	EF33	1-00	HZ85	80	PEN50	40	UCF90	50	2N3709	22	BC111	28	
8A4	50	6CG8A	75	68Q7GT	45	20P5	1-80	4033X	6-00	EBC41	75	EF34	37	HL45	70	PEN50	40	UCF91	50	2N3709	22	BC112	28	
8D4	40	6CH6	1-18	6V6G	1-00	27A6G	60	6702	80	EBC1	85	EF35	37	HL46	70	PEN50	40	UCF92	50	2N3709	22	BC113	28	
8Q4	60	6CL6	1-15	6V8GT	45	27B6G	60	6087	1-00	E8F80	89	EF36	37	HL47	70	PEN50	40	UCF93	50	2N3709	22	BC114	28	
8Q4GT	55	6CL8A	80	6K4	40	20Y6G	70	6080	1-00	E8F83	48	EF37	37	HL48	70	PEN50	40	UCF94	50	2N3709	22	BC115	28	
8B6	45	6CM7	75	6X6GT	40	28Z4G	35	6087	1-00	E8F89	40	EF38	37	HL49	70	PEN50	40	UCF95	50	2N3709	22	BC116	28	
4QB6	55	6C8U5	75	7B6	75	28Z6	80	7475	1-00	E85	44	EF39	37	HL50	70	PEN50	40	UCF96	50	2N3709	22	BC117	28	
6C8S	55	6CW4	1-00	7B7	70	28Z6G	70	9002	50	E86	70	EF40	37	HL51	70	PEN50	40	UCF97	50	2N3709	22	BC118	28	
8R4GY	80	6DE7	75	7H7	75	28D7	1-00	9006	30	E88	70	EF41	37	HL52	70	PEN50	40	UCF98	50	2N3709	22	BC119	28	
5U4G	40	6DT6A	75	7R7	80	80A5	65	AC/PE9	93	E89	45	EF42	37	HL53	70	PEN50	40	UCF99	50	2N3709	22	BC120	28	
5V4G	54	6EW6	75	7Y4	75	30C15	50	AC/PE9	93	ECC33	1-50	EF43	37	HL54	70	PEN50	40	UCF100	50	2N3709	22	BC121	28	
5Y3GT	45	6E5	1-00	7A4	80	30C17	80	DD	95	ECC36	95	EF44	37	HL55	70	PEN50	40	UCF101	50	2N3709	22	BC122	28	
5Z3	40	6E1	70	9D7	85	AC/PE9	93	AC/PE9	93	ECC38	1-00	EF45	37	HL56	70	PEN50	40	UCF102	50	2N3709	22	BC123	28	
6Z4GT	45	6F6G	50	10C2	85	80F5	80	AC/TH1	41	ECC31	34	EF46	37	HL57	70	PEN50	40	UCF103	50	2N3709	22	BC124	28	
6Z4GT	45	6F13	55	10DR7	75	30FL1	75	A160	1-00	ECC82	33	EF47	37	HL58	70	PEN50	40	UCF104	50	2N3709	22	BC125	28	
6J80L2	80	6F14	75	10F1	75	30FL2	75	ATP4	50	ECC83	33	EF48	37	HL59	70	PEN50	40	UCF105	50	2N3709	22	BC126	28	
6A8G	1-25	6F18	55	10F9	85	30FL2	1-00	AZ1	80	ECC84	30	EF49	37	HL60	70	PEN50	40	UCF106	50	2N3709	22	BC127	28	
6AC7	49	6F23	80	10F15	55	30FL3	55	AZ31	60	ECC85	40	EF50	37	HL61	70	PEN50	40	UCF107	50	2N3709	22	BC128	28	
6AN8	27	6F24	35	10LD11	70	30P4	75	D91	85	ECC86	85	EF51	37	HL62	70	PEN50	40	UCF108	50	2N3709	22	BC129	28	
6AQ5	45	6E7	85	10C18	80	AC/PE9	93	AC/PE9	93	ECC87	85	EF52	37	HL63	70	PEN50	40	UCF109	50	2N3709	22	BC130	28	
6AR5	55	6H6GT	25	12A6	45	30PL1	65	8F86	85	ECC189	40	EF53	37	HL64	70	PEN50	40	UCF110	50	2N3709	22	BC131	28	
6A8J	1-00	6J5GT	45	12A6	50	30PL13	85	DK40	70	ECC190	40	EF54	37	HL65	70	PEN50	40	UCF111	50	2N3709	22	BC132	28	
6AT5	45	6J6	30	12BA6	45	30PL14	1-10	DK92	90	ECC191	2-10	EF55	37	HL66	70	PEN50	40	UCF112	50	2N3709	22	BC133	28	
6AU6	30	6J7G	30	12BE6	50	30PL15	90	DK96	80	ECC192	1-00	EF56	37	HL67	70	PEN50	40	UCF113	50	2N3709	22	BC134	28	
6AV6	45	6J8A	70	12BH7	60	36A3	65	DL96	55	ECC193	38	EF57	37	HL68	70	PEN50	40	UCF114	50	2N3709	22	BC135	28	
6AW8A	85	6K7C	80	12BI	3-00	36D5	65	DM70	80	ECC194	44	EF58	37	HL69	70	PEN50	40	UCF115	50	2N3709	22	BC136	28	
6AX4	75	6K8G	45	12BTGT	55	36EGT	75	DM71	1-00	ECC195	85	EF59	37	HL70	70	PEN50	40	UCF116	50	2N3709	22	BC137	28	
6BG8	30	6L1	2-00	12K5	1-00	35W4	50	DY87/6	85	ECC196	85	EF60	37	HL71	70	PEN50	40	UCF117	50	2N3709	22	BC138	28	
6BA6	28	6L6GT	58	12K7GT	45	35Z3	75	DY802	38	ECC197	85	EF61	37	HL72	70	PEN50	40	UCF118	50	2N3709	22	BC139	28	

MATCHED TRANSISTOR SETS—  
LE15 (AC113, AC154, AC157, AA120) 55p  
per pack. 1—OC81 & 2—OC81, 47p.  
1—OC44 & 2—OC45, 47p. 1—OC82D &  
2—OC82 55p. Set of 3—OC83-78p.

VALVES ALSO REQUIRED FOR CASH. LOOSE OR BOXED, BUT MUST BE NEW. OFFERS MADE BY RETURN.  
All goods are insured and subject to the standard 90 day guarantee. Cash or cheque with order only. Despatch charges—Orders below £5, add 10p per order up to three items, each additional item 5p extra. Orders between £5 and £10 add 25p total. Orders over £10 are post free. Same day despatch. Any parcel insured against damage in transit for only 3p per parcel extra. Terms of business free on request. Many others in stock too numerous to mention.  
Please enclose S.A.E. for reply to any correspondence.

**SINCLAIR CALCULATORS**



Cambridge Memory £20.95 (£1.95)  
 Cambridge Assembled £15.95 (£1.55)  
 Sinclair Scientific £22.45 (£2.05)  
 Executive with Memory £26.25 (£2.53)  
 Executive £22.75 (£2.25)

**FERRANTI ZN414**

IC radio chip with data £1.20 (22p). Also available kit of extra parts to complete a radio £2.45 (42p). Send sae for free leaflet.

**SINCLAIR PROJECT 80**

AFU £5.95 (70p)

Z40 £4.65 (51p)

Z60 £3.95 (70p)

Q16 £8.70 (77p)

P25 £4.28 (49p)

P26 £6.95 (82p)

P28 £6.95 (82p)

Decoder £8.45 (75p). Trans for P28 £3.35 (50p)

Tuner £3.95 (£1.08). Stereo 80 £3.95 (£1.08)

Project 805 P.O.A. Project 805SQ P.O.A.



**ECONOMICAL QUADRAPHONICS**

Introducing the Naplex QA10

self contained matrix

quadrasonic synthesizer.

Just feed the output of any

stereo system (including

Project 80 or 60) into it and

hook on 4 speakers to obtain

the latest experience in

sound. Send sae for free

leaflet. Only £10.15 (£1.10).



**SINCLAIR SUPER IC12**

6W rms power.

With 44 page

booklet and

printed circuit

£1.80 (40p)



**NEW SINCLAIR IC20**

High power IC audio amplifier chip. P.O.A.

**DELUXE KIT FOR THE IC12**

Includes all parts for the printed circuit and

volume, bass and treble controls needed to

complete the mono version £1.60 (25p). Stereo

model with balance control £3.60 (42p).

**IC12 POWER KIT**

Supplies 28V 0.5 Amps £2.67 (47p)

**LOUDSPEAKERS FOR THE IC12**

5" x 8" £1.10 (27p). 5" x 8" 8 ohm £1.55 (37p).

**PREAMP KITS FOR THE IC12**

Type 1 for magnetic pickups, mics and tuners.

Mono model £1.35 (24p). Stereo model £2.40 (32p).

Type 2 for ceramic or crystal pickups.

Mono 65p (18p). Stereo £1.30 (24p).

SEND SAE FOR FREE LEAFLET ON KITS

**BATTERY ELIMINATOR**

**BARGAINS**

The most versatile

battery eliminator ever

offered. Switched out-

put of 3, 4½, 6, 7½, 9

and 12V at 500mA

£3.90 (57p).

Other eliminators stocked:

250mA:—3 way switched model giving 6, 7½ and

9V £2.25 (55p).

50mA:—6V £1.95 (40p). 9V £1.95 (40p). 7½V

cassette type £2.50 (40p). Double 6V+6V

£2.50 (40p). 9V+9V £2.50 (40p).

500mA:—Heavy duty deluxe models 6V £2.78

(55p). 7½V £2.78 (55p). 9V £2.78 (55p).



**S-DECS AND T-DECS**

S-DeC £1.98 (31p)

T-DeC £3.63 (47p)

µ-DeC A £3.99 (51p)

µ-DeC B £6.99 (81p)

IC carriers:

16 dill: plain 81p (15p)

With socket £1.77 (25p)

10 TO5: plain 78p (15p). With socket £1.68 (24p).

Experiment guides: A £1.50 (26p). B £1.77 (29p).

C 90p (18p). D £2.40 (35p). E £4.20 (53p).



**SWANLEY ELECTRONICS**

PO BOX 68, SWANLEY,

KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and new VAT. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.



**WILMSLOW AUDIO**

**THE Firm for speakers!**

**SPEAKERS**

- Baker Group 25 3, 8 or 15 ohm £7.75
- Baker Group 33 3, 8 or 15 ohm £8.50
- Baker Group 50/12 8 or 15 ohm £12.50
- Baker Deluxe 12" d/cone £10.75
- Baker Major £8.50
- Baker Regent £7.75
- Baker Super £14.50
- Baker Auditorium 12 £12.50
- Celestion MHT10 horn £10.95
- Celestion P578 for Unilux £12.00
- Celestion G12M 8 or 15 ohm £15.00
- Celestion G12H 8 or 15 ohm £24.00
- Celestion G15C 8 or 15 ohm £33.00
- Coral 6 1/2 d/cone roll surr. 8 ohm £2.50
- Coral 8" d/cone roll surr. 8 ohm £2.25
- EMI 13 x 8, 3, 8 or 15 ohm £2.50
- EMI 13 x 8 150 d/c 3, 8 or 15 ohm £3.75
- EMI 13 x 8 450 t/w 3, 8 or 15 ohm £8.25
- EMI 13 x 8 type 350 8 or 15 ohm £6.60
- EMI 13 x 8 20 watt base £2.00
- EMI 6 1/2" 93650 4 or 3 ohm £2.50
- EMI 5" 98132CP 8 ohm £2.50
- EMI 8 x 5 d/cone, roll surr 10 watt EMI 2 1/2" tweeter 97492AT .65
- Eagle DT33 30 watt tweeter £5.45
- Eagle HT15 horn tweeter £3.80
- Eagle CT5 cone tweeter £1.75
- Eagle CT10 tweeter 8 or 16 ohm £2.45
- Eagle MHT10 horn tweeter £3.80
- Eagle crossover CN23, CN28, CN216 £1.50
- Eagle FR4 £5.30
- Eagle FR65 £8.35
- Eagle FR8 £10.65
- Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm £2.80
- Elac 6 1/2" 6RM171 d/c roll surr. £3.50
- Elac 6 1/2" 6RM220 d/cone £2.85
- Elac 4" tweeter TW4 £1.21
- Elac 10" d/cone 0RM239 8 ohm £2.85
- Elac 8" 8CSI75 3 ohm £2.50
- Fane Pop 15 watt 12" £4.80
- Fane Pop 25/2 25 watt 12" £6.95
- Fane Pop 40 watt 10" £8.50
- Fane Pop 50 watt 12" £11.00
- Fane Pop 55 12" 90 watt £12.50
- Fane Pop 60 watt 15" £13.00
- Fane Pop 100 watt 18" £22.50
- Fane Crescendo 12A 100 watt 12" £29.00
- Fane Crescendo 12B bass £29.00
- Fane Crescendo 15" 100 watt £36.00
- Fane Crescendo 18" 150 watt £7.00
- Fane 801T 8" d/c roll surr. £7.00
- Fane 807T 8" d/c roll surr. £3.85
- Fane 808T 8" d/c £2.75
- Fane 701 twin ribbon horn £35.00
- Fane 910 horn £12.75
- Fane 920 horn £33.00

- Goodmans 8P 8 or 15 ohm £3.00
- Goodmans 10P 8 or 15 ohm £3.30
- Goodmans 12P 8 or 15 ohm £12.95
- Goodmans 12P-D 8 or 15 ohm £16.75
- Goodmans 12P-G 8 or 15 ohm £15.75
- Goodmans Audiomax 12AX 100 watt £37.50
- Goodmans Audiomax 15AX £40.00
- Goodmans 15P 8 or 15 ohm £21.00
- Goodmans 18P 8 or 15 ohm £26.00
- Goodmans Midax 750 £18.00
- Goodmans Axent 100 tweeter £7.25
- Goodmans Audiom 100 12" £12.00
- Goodmans Axlom 401 12" £17.25
- Goodmans Twinaxiom 8 £8.25
- Goodmans Twinaxiom 10 £9.00
- Keft T27 £5.25
- Keft T15 £6.00
- Keft B110 £7.00
- Keft B200 £8.00
- Keft B59 £12.75
- Keft DN8 £2.00
- Keft DN12 £2.00
- Keft DN13 £2.75
- STC4001G super tweeter £6.19
- Richard Allan CG8T 8" d/c r/surr. £6.35
- Wharfedale Super 10RS/DD £9.80
- 2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm .65
- 2 1/2" 75 ohm .50
- 7" x 4" 3 or 8 ohm £1.40
- 8" x 5" 3 or 8 ohm £1.50
- 10" x 6" 3, 8 or 15 ohm £2.30

**SPEAKER KITS**

- Baker Major Module each £10.75
- Fane Mode One each £9.90
- Goodmans D1H 20 pair £22.00
- Helme XLK 25 pair £14.85
- Helme XLK 30 pair £39.95
- Helme XLK 50 pair £39.95
- Keftit 2 each £23.50
- Keftit 3 each £34.00
- Richard Allan Twinkit each £8.95
- Richard Allan Triple 8 each £13.75
- Richard Allan Triple each £19.95
- Richard Allan Super Triple each £23.75
- Wharfedale Linton 2 kit pair £19.25
- Wharfedale Glendale 3 kit pair £34.50
- Wharfedale Doveclade 3 kit pair £52.50

**PA/DISCO AMPLIFIERS**

- (carr. and ins. £1)
- Baker Major 100 watt £49.75
- Linear 30/40 £30.00
- Linear 40/60 £35.00
- Linear 30/100 £58.95
- Linear 100 watt slave £44.00
- Eagle PA range in stock—ask for catalogue.

**Free with speaker orders over £7—**

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, speaker kits 75p each (£1.50 pair) tweeters and crossovers 20p.

**ALL PRICES QUOTED INCLUDE VAT.**

**WILMSLOW AUDIO (Dept. PW)**

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF  
 Discount Radio, PA, Hi-Fi: 10 Swan St. Wilmslow  
 Send stamp for free booklet "Choosing a Speaker"



**Cassettes**

The best buy!

Agfa Low Noise Cassettes

AT LESS THAN HALF PRICE!


**AGFA HIGHDYNAMIC SUPER**

**AGFA STEREO-CHROM CHROMIUM DIOXIDE**

	1	5	10
C60	37p	£1.80	£3.50
C90	50p	£2.48	£4.95
CT20	63p	£3.10	£6.20
C60+6	50p	£2.40	£4.70
C90+6	68p	£3.35	£6.60
CT20	99p	£4.90	£9.80
C60	1	5	10
C90	85p	£4.20	£8.30
	£1.08	£5.35	£10.60

SAME DAY DESPATCH. P. & P. 15p per order

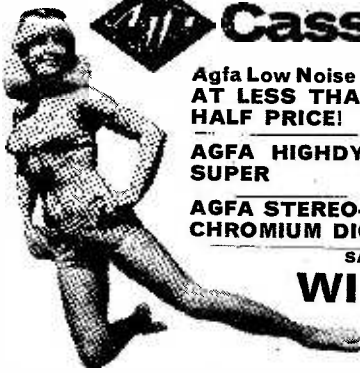**WILMSLOW AUDIO**  
 (DEPT. PW)  
 10 SWAN STREET, WILMSLOW,  
 CHESHIRE, SK9 1HF



Cut-price prerecorded cassettes—send stamp for list



GIRO NO. 331 7056  
C.W.O. only P. & P. 10p on orders below £5  
Discount: £10-10%, £20-15% (except net items)  
Export Order enquiries welcome (VAT free)

Official Orders accepted from  
Educational & Government Departments  
ALL PRICES INCLUDE VAT AT 8%

**SPECIAL RESISTOR KITS** (Prices include post & packing)

10E12 1/4W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.58 net  
10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.77 net  
25E12 1/4W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.19 net  
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.28 net  
5E12 1/4W KIT: 5 of each E12 value, 10 ohms—212, a total of 305 (METAL FILM 5%), £2.80 net  
Due to current world shortages, resistor kits may contain some wattage and value substitutions.

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1.2µF, 1.5µF, 1.5pF, 5pF, 23p, 2.2µF, 26p.

**MULLARD POLYESTER CAPACITORS C296 SERIES**  
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1.2µF, 1.5µF, 1.5pF, 5pF, 23p, 2.2µF, 26p.

**MINIATURE CERAMIC PLATE CAPACITORS**  
160V: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1.2µF, 1.5µF, 1.5pF, 5pF, 23p, 2.2µF, 26p.

**POLYSTYRENE CAPACITORS 160V 5% (P.F.)**  
10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 47p.

**RESISTORS**

CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%					
W. Type Range	1-99	100-499	500-999	1000+	Size mm
↓ CF 22-1M	1	0-75	0-60	0-55	2-4x7-5
↓ CF 22-2M2	1	0-75	0-60	0-55	3-9x10-5
↓ CF 22-1M	1	0-75	0-60	0-55	5-5x16
↓ MF 10-2M7	2	1-54	1-32	1-1	3x7
↓ MF 10-2M2	2	1-43	1-21	0-99	4-2x10-8
↓ MF 10-10M	3	1-98	1-81	1-65	6-6x17-5
2 MF 10-10M	4-5	3-52	3-08	2-75	6-6x17-5

For value mixing prices, please refer to our catalogue. (price in pence each).  
VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

**PRESET SKELETON POTENTIOMETERS**  
MINIATURE 0-25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω  
SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 5p each.

**B. H. COMPONENT FACTORS LTD.** (P.W.) 61 CHEDDINGTON ROAD, PITSTONE NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ  
Tel.: Cheddington 668446 (Std. Code 0296)  
CATALOGUE No. 3 20p

**Miniature Mullard Electrolytics**

1.0µF 63V	61p	68µF 16V	61p
1.5µF 63V	61p	68µF 63V	12p
2.2µF 63V	61p	100µF 10V	61p
3.3µF 63V	61p	100µF 25V	61p
4.7µF 63V	61p	100µF 63V	14p
6.8µF 63V	61p	150µF 63V	15p
8.0µF 40V	61p	220µF 6-4V	61p
10µF 16V	61p	220µF 10V	61p
10µF 25V	61p	220µF 16V	8p
15µF 63V	61p	220µF 33V	21p
15µF 16V	61p	330µF 63V	25p
15µF 63V	61p	470µF 6-4V	9p
22µF 20V	61p	470µF 40V	20p
22µF 10V	61p	680µF 16V	15p
33µF 63V	61p	680µF 25V	25p
33µF 16V	61p	1000µF 16V	20p
33µF 63V	61p	1500µF 25V	25p
47µF 10V	61p	1500µF 6-4V	15p
47µF 15V	61p	1500µF 16V	25p
47µF 20V	61p	2200µF 10V	25p
47µF 63V	8p	3300µF 6-4V	26p

**VEROBOARD 0-1 0-15**

2 1/2 x 5"	36p	36p
3 1/2 x 3 1/2"	33p	25p
3 1/2 x 4 1/2"	42p	46p
2 1/2 x 3 1/2"	36p	36p
2 1/2 x 5" (Plain)	—	19p
2 1/2 x 3 1/2" (Plain)	—	16p
2 1/2 x 5" (Plain)	—	29p
Insertion tool	73p	73p
Track Cutter	56p	56p
Pins, Pkt. 25	22p	22p

**POTENTIOMETERS**  
Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 161p Dual Gang 46p. Log single with switch 26p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p, 45mm, 47p, 60mm, 55p.

**DIODES**

IN4001 61p	DIN 2 Pin	12p
IN4002 71p	3 Pin	13p
IN4003 9p	5 Pin 180°	16p
IN4004 9p	Std. Jack	20p
IN4005 12p	2.5mm jack	13p
IN4006 14p	Phono	6p
IN914 7p	DIN 2 Pin	10p
IN916 7p	DIN 3 Pin	10p
BA10A 10p	5 Pin 180°	12p
OA5 42p	5 Pin	18p
OA47 9p	Std. Jack	15p
OA81 11p	2.5mm Jack	13p
OA200 8p	Phono	6p

**ELECTROLYTIC CAPACITORS. Tubular & Large Cans**  
(µF/V): 1/25, 2/25, 4/25, 4-7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 61p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/100, 88p, 2000/25, 30p, 2000/100, 93p, 2500/25, 38p, 2500/50, 61p, 5000/25, 65p, 5000/50, £1.08.

**TRANSISTORS**

AC127 161p	BC212L 12p
AC128 22p	BC213L 12p
BC107 11p	BC214L 17p
BC108 12p	OC44 16p
BC109 13p	OC71 13p
BC148 12p	OC81 16p
BC149 12p	OC170 23p
BC182L 12p	TIS43 33p
BC183L 12p	2N2922 11p
BC184L 13p	2N3702 11p

**Integrated Circuits**

µA709C 49p	Stereo Screened Wire, Metre	12p
µA741C 50p	Connecting Wire. All colours, Metre	21p
µA723C 98p	Neon Bulb, 90V Wire Ended	5 for 24p
ZN414 43p	Panel Neon. 240V Red, Amber, Clear	20p


**SCREENED WIRE, METRE**  
Twin Screened Wire, Metre 12p  
Stereo Screened Wire, Metre 12p  
Connecting Wire. All colours, Metre 21p  
Neon Bulb, 90V Wire Ended 5 for 24p  
Panel Neon. 240V Red, Amber, Clear 20p

**ZENER DIODES**  
Low cost 400mW Tol±7%  
All values E24 series 3V-30V  
1-24 25-99 100-499 1000-3000  
9p 7p 6p 5p

**METALLISED PAPER CAPACITORS**  
250V: 0.05µF, 0.1µF, 0.2µF, 0.25µF, 0.5µF, 7p, 1µF, 9p, 500V: 0.025, 0.05, 0.1, 0.2, 0.25, 7p, 0.5, 9p, 1000V: 0.01, 0.025, 0.05, 0.1, 0.2, 0.25, 13p, 0.047, 0.1, 1.5, 0.22, 23p, 0.47, 34p.

**MULTIMETER U4323**  
22 Ranges plus AF/IF Oscillator 20,000 Ω  
Vdc—0-5-1000V in 7 ranges  
Vdc—2-5-1000V in 6 ranges  
Idc—0-05-500mA in 5 ranges  
Resistance—50Ω-1MΩ in 4 ranges  
Accuracy—5% of F.S.D.  
OSCILLATOR—1 KHz and 465 KHz (A, M) at approx. 1 Volt.  
Size—160 x 97 x 40mm.  
Supplied complete with carrying case, test leads and battery.  
PRICE £8.30 net p & p 25p.

**MULTIMETER U4341**  
27 Ranges plus Transistor Tester, 16,700Ω/Volt. Overload protected.  
Vdc—0-3-900V in 8 ranges.  
Vdc—1-5-750V in 6 ranges.  
Idc—0-06-600mA in 5 ranges.  
Iac—0-3-300mA in 4 ranges.  
Resistance—2KΩ-2MΩ in 4 ranges.  
Accuracy—dc—2½%, ac—4% of F.S.D.  
Ihf—10-350 in 2 ranges.  
Size—115 x 215 x 90mm.  
Complete with steel carrying case, test leads, and battery.  
PRICE £11.30 net p & p 30p.

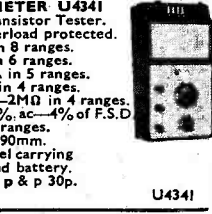


**MULTIMETER U4313**  
33 Ranges. Knife edge with mirror scale, 20,000Ω/Volt. High accuracy, mVdc—75mV.  
Vdc—1-5-600V in 9 ranges.  
Vdc—1-5-600V in 9 ranges.  
Idc—0-06-120mA in 5 ranges.  
Idc—0-6-1500mA in 6 ranges.  
Iac—0-6-1500mA in 6 ranges.  
Resistance—1KΩ-1MΩ in 4 ranges.  
db scale—10 to +12db.  
Accuracy—dc—1½%, ac—2½%  
Size—115 x 215 x 90mm.  
Complete with steel carrying case, test leads, and battery.  
PRICE £13.40 net p & p 30p.

**NEW CAPACITOR KITS**  
C280 Kit—PC Mounting polyester 250V. 5 of each value: 0-01 0-022, 0-047, 0-1, 0-22µF, 2 of 0-47, 1µF. £1.30 net.  
C296 Kit—Tubular polyester, 400V. 5 of each value: 0-01, 0-022, 0-047, 0-1, 0-22µF, 2 of 0-47µF. £1.30 net.  
Ceramic Kit—square plaquette 50V. 5 each value: 22, 33, 47, 100, 220, 330, 470, 1000pF, 2200, 4700pF, 0-01µF, £1.30 net.  
250V Paper Kit—Tubular metal case. 3 of each value: 0-05, 0-1, 0-25, 0-5, 1µF. 90p net.  
500V Paper Kit—Tubular metal case. 3 of each value: 0-025, 0-05, 0-1, 0-25, 0-5µF. 90p net.  
1000V Paper Kit—Tubular metal case. 3 each value: 0-01, 0-025, 0-05, 0-1µF. £1.10 net.

**MULTIMETER U4324**  
34 Ranges. High sensitivity, 20,000Ω/Volt. Overload protected.  
Vdc—0-6-1200V in 9 ranges.  
Vdc—3-900V in 8 ranges.  
Idc—0-06-3A in 5 ranges.  
Iac—0-3-3A in 5 ranges.  
Resistance—25Ω-5MΩ in 5 ranges.  
Accuracy—dc and R—2½% of F.S.D.  
ac and db—4% of F.S.D.  
Size—167 x 98 x 63mm.  
Supplied complete with storage case, test leads, spare diode, and battery.  
PRICE £9.95 net p & p 25p.

**MULTIMETER U4313**  
33 Ranges. Knife edge with mirror scale, 20,000Ω/Volt. High accuracy, mVdc—75mV.  
Vdc—1-5-600V in 9 ranges.  
Vdc—1-5-600V in 9 ranges.  
Idc—0-06-120mA in 5 ranges.  
Idc—0-6-1500mA in 6 ranges.  
Iac—0-6-1500mA in 6 ranges.  
Resistance—1KΩ-1MΩ in 4 ranges.  
db scale—10 to +12db.  
Accuracy—dc—1½%, ac—2½%  
Size—115 x 215 x 90mm.  
Complete with steel carrying case, test leads, and battery.  
PRICE £13.40 net p & p 30p.

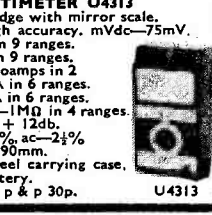

**S-DeC**  
S-DeC £2.14  
T-DeC £3.92  
µDeC "A" £4.30  
µDeC "B" £7.53

**PANEL METERS**  
2" scale  
100µA £3.75  
500µA  
1mA All at 5mA  
10mA £3.75  
100mA  
500mA  
1A

**FELSTED ELECTRONICS (PW84), LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE SK8 4EE**

**STYLII** Replacements for virtually all ACOS, BSR, COLLARO, GARRARD, PHILIPS, RONETTE, SONOTONE. Single Tip: Sapphire 19p, Diamond 37p. Double Tip: Can be ST/LP+78 or ST/LP+ST/LP Sapphire 37p, Double Tip: Diamond ST/LP+78 or ST/LP+78 65p, Diamond ST/LP+Diamond ST/LP £1.25. For GOLDRING Diamond 8800, 8800H and 8850 at £2-10 each, 8800E at £4-10. FREE LIST (FOR SAE) FULL DETAILS STYLII AND CARTRIDGE EQUIVALENTS including SURE, PICKERING, AUDIO PICK-UPS. Charges 10p any quantity.

**CARTRIDGES.** All with stylus and fittings. Replacements for ACOS GP/91 SC (Stereo-compatible series) at £1.05, GP93 Stereo at £1.45, GP94 Stereo Ceramic at £1.98; for RONETTE DC4008CM (Speed change switch at front for GP67, TCS & c) at £1.25; for BSR X3H, X5H and X5M at £1.35 each, X5H and X5M at £1.70 each. TC8H at £1.50, TC8 Stereo, 3 pins. £2.15; charges 10p any quantity.

**RECORDING TAPE.** ALL FINEST BRITISH MYLARS 5" 609 ft. 20p; 5" 900 ft. 55p; 5 1/2" 1200 ft. 75p; 7" 1800 ft. £1.05. Charges for 5" and 5 1/2", 1-4, 13p each; 5 and over, 35p the lot. Charges for 7", 1-3 15p each, 4-5 85p the lot, 6 and over 40p the lot.

**SPEAKERS 2T1,** 3, 8 or 64 ohms (state which) 55p. Charges 10p each.

**CONNECTING WIRE.** Pkts. of 5 coils, asstd. cols., each 5 yds. Solid core 10p (10p charges). Flexible 21p (10p charges).

**EARPIECES.** Magnetic. 2-5 or 3-5mm plug (state which) 15p. CRYSTAL (3-5mm only) 35p (all 10p up to 6).

**VIBRATORS.** 7 pin SYNCH. (12SR7 type) 75p. 4-pin NON-synch (121HD4) 45p (all 10p each).

Send SAE for free stylus, cartridge and components list. All prices include VAT. (Some delay possible in dealing with orders, &c. between Oct. 23rd and Nov. 8th)

**poly-planar**  
20-Watt Full Range Speaker

Completely replaces the conventional cone speaker  
Super-thin construction permits new installation ideas.


Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz  
Sensitivity: 85 dB/1m for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 1-3/4" x 1-11/16". Weight: 19 ounces.

£7-50 each Stereo pair £14-50  
INCLUSIVE OF VAT AND POSTAGE

**web europa**  
P.O. Box 162, Watford WD1 1AA



# Quadraphonic Project 80

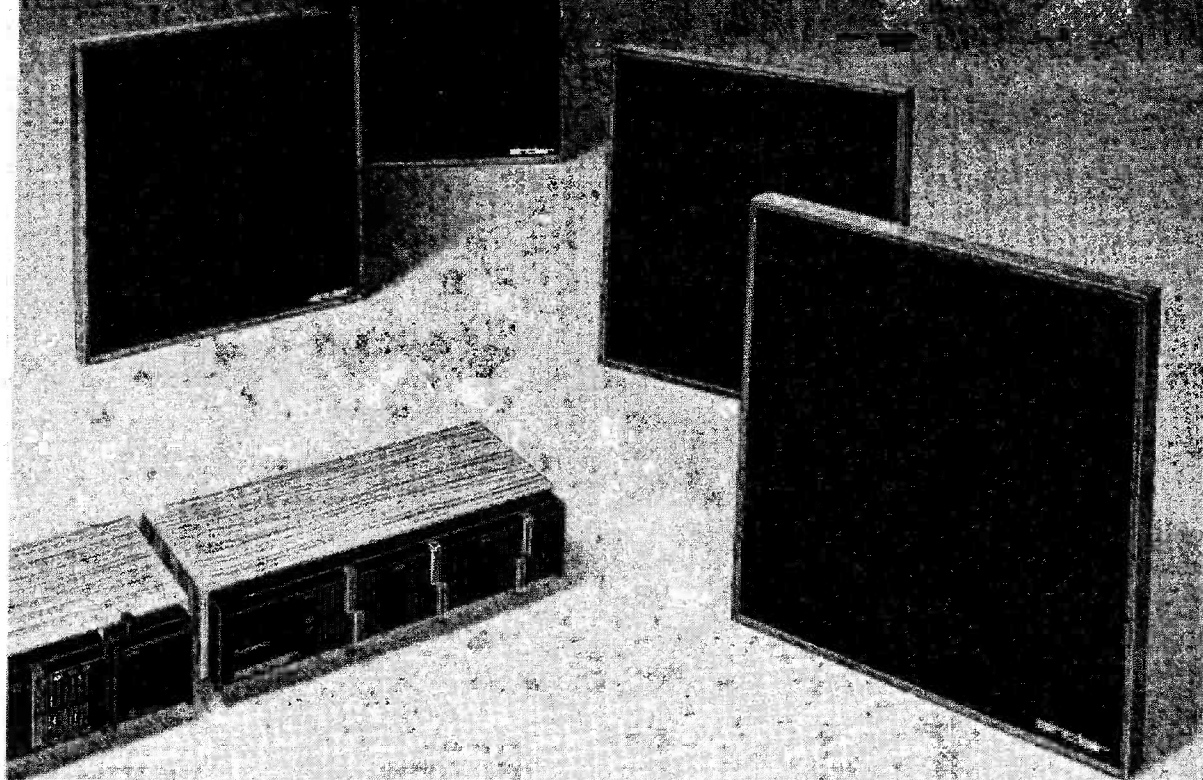

Sinclair's 4<sup>th</sup> dimension in high fidelity

## Project 80

The slim modules for building stereo hi-fi with FM

## Project 805

Project 80 made even easier to build

## Project 805SQ

The add-on assembly that gives you quadraphony

## Q16 Loudspeakers

The square speakers for 4 channel listening

### Four channel listening has arrived!

Thanks to Project 80 versatility and marvellous compactness, adding two more channels is easy, efficient and economical – you simply add on Project 805SQ, or select the necessary modules from the Project 80 range detailed on the fourth page of this advertisement. Another way is to start with the new Project 805 (which is Project 80 complete in one pack) and add 805SQ to it. Our technicians have adopted the CBS SQ matrix principle to carry the rear left and right channels since it is already clearly the most widely used method in quadraphonic recordings. The decoder, however, can be modified to discrete systems without difficulty. Sinclair suitability for quadraphonics by no means stops with Project 805SQ. The Q.16 – always a superb loudspeaker in its own right – becomes one of the best ways of creating effective ambience without taking up too much space or money. Project 80 quadraphonic modules are ready now for you to enjoy both stereo and true quadraphonics right away with better reproduction from mono records as well.



Stereo 80 pre-amp/control unit



Project 80 F.M. tuner



Project 80 stereo decoder



Project 80 active filter unit




Project 805Q quadraphonic decoder

**sinclair**



# Forward with Project 80 into

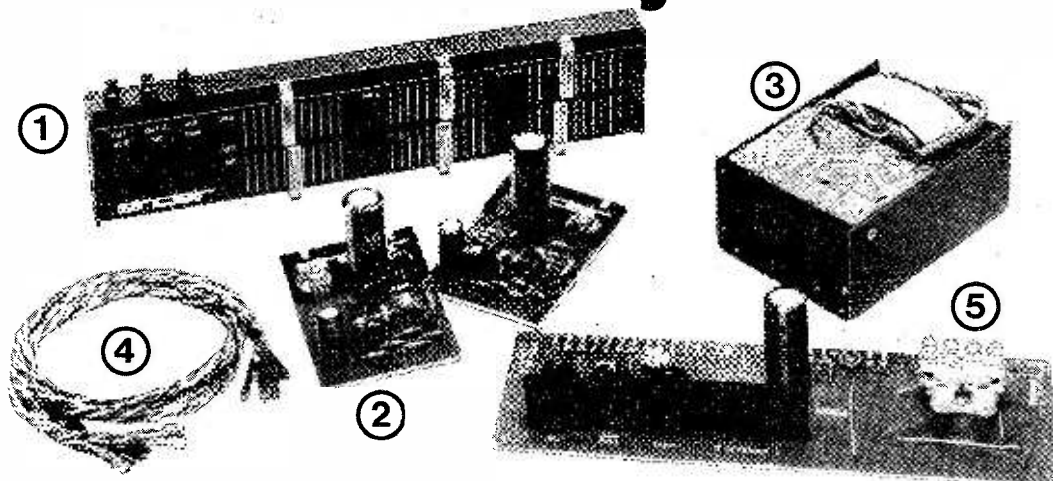

*Everything you want in one pack to build the world's most advanced modular hi-fi WITHOUT SOLDERING*

- 1 Stereo 80 Control Unit  
For mag. and ceramic cartridges, radio and tape.
- 2 Project 80 power amplifiers  
Two Z.40s to give 8/8 watts R.M.S. output per channel.
- 3 Power supply unit  
One PZ.5.
- 4 Connecting wires  
All wires plus nuts, bolts, screws etc.
- 5 Project 805 Masterlink  
For input and output connections.
- 6 Mains switch block and instructions manual (not illustrated).

## This is Project 80 made even easier to build

You have seen how the marvellously compact Project 80 modules (only 2" high,  $\frac{1}{2}$ " deep) are so adaptable and easy to install. Now, with Project 805, this wonderful system is made easier still to put together. In this, you have not only all the Project 80 modules in one pack for building a 8/8 watt R.M.S. hi-fi amplifier — there is also a loom of colour coded wires cut to length and tagged for clipping on so that you don't even have to solder! Input and output connections go via the 805 Masterlink panel. With the explicit stage-by-stage large 32 page instructions manual included, it becomes easy for anyone, no matter how inexperienced to install an ultra-modern assembly so advanced in appearance and design that it sets brand new concepts in domestic hi-fi — and of course, you can convert to quadraphony just whenever you wish by adding 805SQ. Only Sinclair know-how and manufacturing facilities could hope to bring you such quality and versatility.

### TAGGED WIRES CUT TO LENGTH · NO SOLDERING

# Project 805

## the complete ready-to-build hi-fi STEREO AMPLIFIER

Project 805 comprises a Stereo 80 Pre-amp/Control Unit with input for both magnetic and ceramic cartridges, radio, tape; separate bass and treble cut/lift, and volume controls 2 x Z.40 power amplifiers, PZ.5 power unit, 805 Masterlink, wire loom, instructions manual, etc. down to nuts, bolts and washers. For technical specifications, see fourth page of this advertisement.

# £39.95


+£3.20 VAT (R.R.P.)

# sinclair




SINCLAIR RADIONICS LTD.  
London Rd, St. Ives, Huntingdon PE17 4HJ  
Telephone St. Ives (0480) 64646

# true quadraphonics... *NOW!*

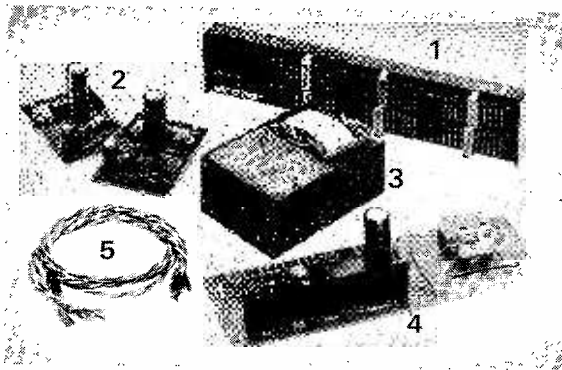

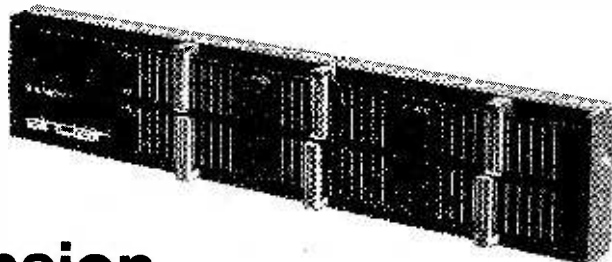1. Project 80SQ decoder with controls.
2. Two Z.40 power amplifiers.
3. PZ.5 power pack.
4. Project 80Q Masterlink unit.
5. Wire loom, with clip-on tags – NO SOLDERING!
6. (Not illustrated) Instructions manual, nuts bolts, washers, etc.

The most effective and economical way to enjoy this spectacular breakthrough in hi-fi listening




## Add a fourth dimension to your stereo sound

It's so simple to convert to quadraphonics when you already have Project 80, or are about to start with Project 805. Project 805SQ is a complete add-on system at the heart of which is the Project 80SQ decoder. It uses the CBS.SQ matrix principle, by now the widest used method of containing four sound channels within the groove of the record. Project 805SQ includes two power amplifiers, power supply unit, connecting wire loom, 805Q Masterlink, switch block and instructions manual. The 80SQ decoder (also obtainable separately) has independent tone and volume slider controls on the two rear channels for matching true four channel sound to domestic environment. Project 805SQ is money saving too since you do not have to scrap existing Project 80 equipment to enjoy the newest and most exciting form of home listening in the entire history of sound, and your Project 80 quadraphonic assembly is compatible with stereo and mono records.

- Frequency response  $\pm 3\text{db}$  15 Hz-25kHz
- Rated output 100mV
- S/N ratio 58dB
- Distortion 0.1%
- Power requirements 22-35 volts
- Phase shift network  $90^\circ \pm 10^\circ$  100 Hz-10kHz
- Adaptable to discrete (CD4) use



# Project 805SQ

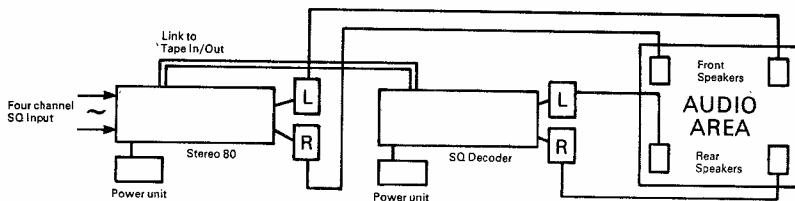

The output from any good stereo cartridge feeds into Stereo 80 and passes via the tape outlet to the 80SQ decoder. Here the signal is separated into its constituent 4 channels, those for the front being accepted by the Stereo 80, those for the rear going from the decoder to the two additional power amplifiers and speakers.

**£44.95**

+£3.60 VAT (R.R.P.) \*

**Guarantee** If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair Appointed Stockists also offer this guarantee. Should any defect arise in normal use within 2 years, we will service it without charge. For damage arising from mis-use a nominal charge will be made.

Project 80 quadraphonic modules may be purchased separately if required. The Project 80SQ decoder may be used with any other amplifier having tape and monitoring facilities. Z40 or Z60 power amps can be used as required.

# The Project 80 programme to date

**KEEP THIS PAGE FOR HANDY REFERENCE USE THE PRIORITY ORDER FORM IN CASES OF DIFFICULTY**

## Stereo 80 pre-amp/control unit



260×50×20mm (10½×2×¾ ins.) separate slider controls on each channel for treble, bass and volume. INPUTS – Mag. P.U 3mV (RIAA corrected) ceramic – 300mV, Radio 100mV, Tape 30mV. S/N ratio 60dB. Frequency range – 20Hz to 15KHz ± 1dB. OUTPUTS – 2.5V rms max (30V supply) and tape plus AB monitoring. PRESS BUTTONS for P.U., Radio and Tape. Operating power – 20 to 35V. Black case with white indications.

**£13.95** +£1.12 VAT (R.R.P.)

## Project 80 F.M. tuner



Size 85×50×20mm (3½×2×¾ ins.). Tunes 87.5 to 108MHz. DETECTOR – I.C balanced coincidence (I.C equivalent to 26 transistors) Distortion – 0.2% at 1KHz for 30% modulation. SENSITIVITY – 5 microvolts for 30dB quieting. Output – 300mV for 30% modulation. Aerial imp. – 75 Ω or 240-300 Ω. Dual Varicap tuning. 4 pole ceramic filter. Switchable A.F.C. Operating power 23-30 volts.

**£13.95** +£1.12 VAT (R.R.P.)


## Project 80 stereo decoder

Size 47×50×20mm. For adding to Project 80 FM tuner. With one I.C equal to 19 transistors, and LED indicator which glows on tuning in stereo signal.



**£8.95** +72p VAT (R.R.P.)
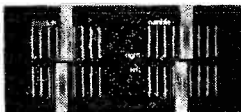
## Project 80 active filter unit (A.F.U.)



Size 108×50×20mm. Useful where there is need to eliminate unwanted high frequencies (scratch, whistle, etc) or low (rumble). Voltage gain – minus 0.2dB. Frequency response (filter at zero) 36Hz to 22KHz. H.F cut (scratch) variable from 22KHz to 5.5KHz 12dB/octave slope. L.F cut (rumble) – 28dB at 28Hz, slope 9dB/octave.


**£7.45** +60p VAT (R.R.P.)

## Project 80 power amplifiers

Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced.
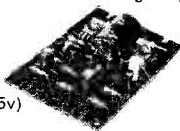
### Z.40

Size – 55×80×20mm  
9 transistors  
Input sensitivity – 100mV  
Output – 12 watts RMS continuous into 8 Ω (35V)  
Frequency response – 10Hz – 100KHz ± 1dB  
S/N ratio – 64dB  
Distortion – 0.1% at 10 watts into 8 Ω at 1KHz  
Power requirements – 12 to 35 volts



**£5.95** +48p VAT (R.R.P.)

### Z.c0

Size – 55×98×20mm  
12 transistors  
Input sensitivity – 100-250mV  
Output – 25 watts RMS continuous into 8 Ω (50V).  
Distortion – 0.02% at 10W/8 Ω/1KHz  
Frequency response – 10Hz to more than 200KHz ± 3dB  
S/N ratio – better than 70dB  
Built-in protection against transient overload and short circuiting  
Load impedance – 4 Ω min; max. safe on open circuit



**£7.45** +60p VAT (R.R.P.)

## Power-supply units

**PZ.5** Unstabilized. 30 volts. Suitable for Z.40 assemblies, etc.

**£5.95** +48p VAT (R.R.P.)

**PZ.6** Stabilized. Output voltage adjustable between 20 and 50 volts approx. Protecting fuse.

**£8.95** +72p VAT (R.R.P.)

**PZ.8** Stabilized. Output adjustable from 20 to 60V. approx. Re-entrant current limiting makes damage from overload or even shorting impossible. Without mains transformer.


**£8.45** +68p VAT (R.R.P.)



**Project 805 (previous pages)** **£39.95** +£3.20 VAT (R.R.P.)

**Project 805SQ quadraphonic add-on kit** **£44.95** +£3.60 VAT (R.R.P.)

## Project 80SQ quadraphonic decoder

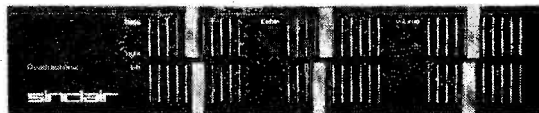


Size 260×50×20mm, matching Stereo 80 in style. Connects with tape socket on stereo 80 or similar facility on any stereo amplifier. Frequency response 15Hz to 25KHz ± 3dB. Distortion 0.1%. S/N ratio 58dB. Rated Output – 100mV. Separate bass and treble slider controls on each channel, also volume. Phase shift network 90° ± 10°, 100Hz to 10KHz. Operating power – 22-35V.

**£18.95** +£1.52 VAT (R.R.P.)
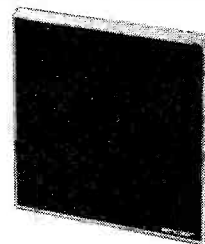
## Sinclair Q.16 loudspeaker

An original and uniquely designed speaker of outstanding efficiency. Balanced sealed sound chamber and special driver assembly. Loads up to 14 W./R.M.S. 8 ohms imp. Size 248mm square×120mm deep. Pedestal base. All-over black front, teak surround.



**£8.95** +72p VAT (R.R.P.)

**sinclair**

Sinclair Radionics Ltd.,  
London Road St. Ives  
Huntingdonshire PE17 4HJ  
Telephone St. Ives (0480) 64311  
R.O. St. Ives: Reg No. 6994583 Eng.

**USE THIS PRIORITY ORDER FORM IN CASES OF DIFFICULTY**

To Sinclair Radionics Ltd.  
Please send, (carriage paid in U.K.)

NAME .....

ADDRESS .....


For which I enclose £..... cash/  
cheque/money order INCLUDING V.A.T.

PW11

LISTEN TO

**CODAR**® THE WORLD!

★ **CR70A**

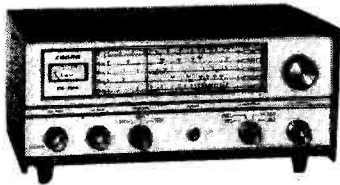

**COMMUNICATION RECEIVER**

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Mer. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ **IMPORTANT NOTE**

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your order receipt, sent by return.


★ **MADE TO ORDER!**

**£34.14!**

VAT PAID  
CARR. 87p




★ **P.R.40** ★

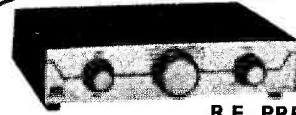

**£10-93!**  
VAT PAID  
CARR. 32p

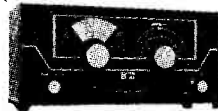**R.F. PRESELECTOR**

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee...



**MULTIBAND-6** ★

**SHORT WAVE RECEIVER KIT**

**£16-90!** CARR. 43p

All transistor T.I.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship / Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandspread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

ILLUSTRATED LEAFLETS FREE ON REQUEST

ON THE DESIGN STAFF—  
G3SZM G3IRE

**CODAR**®

TELECOMMUNICATIONS AND ELECTRONIC  
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS  
GOVERNMENTS

**VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX**

Tel. 090-63-61901

BN15 - 8TZ



**LOGIC  
LEISURE  
LTD**

**build your  
own t.v.  
game**

**Complete kit available or P/C board only.** First time available, the real T.V. Game in kit form as supplied to the amusement trade with five bat angles, fully automatic ball, digital score read out on screen and also simulated sound.

Please send stamped addressed envelope for details and prices to:—

**LOGIC LEISURE LIMITED, Kingfisher House, 68 Park Road, New Barnet, Herts.**


Telephone: 01-440-9173/4 Telex: 264397

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 12p per word (minimum 12 words), box number 30p extra. Semi-displayed setting £10.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London. EC4A 4AD for insertion in the next available issue.
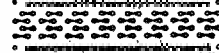
## THE MAKERS OF BEC CABINETS NOW INTRODUCE:-

**PAD-STRIP P.C. BOARD**  
Tinned for easy soldering and made of Fibre Glass.



A new approach to a standard P.C. Board. Simply look at any circuit layout, draw it out as you see it on Pad-Strip. Then make it . . . as simple as that . . . and only 23p and a S.A.E.  
Full details with each board.

**I.C. TEST RIG PADS**  
Fibre Glass and Tinned for easy soldering.



TO 12

DIL 16

Experimenters fit fly leads to take off pads and use your I.C.'s over and over again. Also small circuits can be built on the DIL 16. Price either type.  
**13p and a S.A.E.**

And of course BEC Cabinets



- GB11 14" x 2" x 6" £3-75
  - GB1a 9" x 2" x 6" £3-35
  - GB2 14" x 3" x 7" £4-25
  - GB3 14" x 4" x 9" £4-75
  - GB4 14" x 6" x 9" £7-50
- Plus 45p P & P.  
S.A.E. with enquiries

V.A.T. at 8% included in all prices.  
We also make custom made Facia Panels and P.C. Boards.

**H.M. ELECTRONICS (P.W.S)**  
275a, Fulwood Road.,  
Sheffield S10 3BD.  
Tel. 669676

## Aerials

**GENUINE FULL SIZE**  
**18 element TV aerial**  
as used by leading TV companies

**FOR ONLY £2.20**

ITV, BBC1, BBC2, BBC4, BBC5, BBC6, BBC2016, BBC2

**SOUND TO LIGHT CONVERTORS** 3-channel, 1.5 kW £18, 3 kW £25, single channel £9; Sequencer £93; Strobes from £19; Projectors from £24; etc. Call or mail Aarvak Electronics, 98A West Green Road (Side Door), London N15 5NS. 01-800 8656.

**G.E.C. BRT 400** general coverage communications receiver. Very good condition, £55. **BACK NUMBERS** of P.W. also available. Oct. '65 to Mar. '69 (some missing). Lucas, 29 Myton Crescent, Warwick. Tel: Warwick (0926) 42196.

**VALVES, VALVES & MORE VALVES.** Large stocks 1950-1974, many obsolete. Also available many types of transistors and stylis. Price lists available, 15p. Cox Radio, The Parade, East Wittering, Sussex. West Wittering 2023.

## Official Appointments

# The Hatfield Polytechnic

**TECHNICIAN** for Psychological Laboratory for maintenance and construction of a variety of electronic, mechanical, audio-visual and medical equipment. The person appointed will work with a Senior Technician. Applicants should preferably hold an appropriate Intermediate or National Certificate or City and Guilds qualification, but this is not essential. Further study is encouraged and day release facilities are available.

Salary on a scale rising to £1889 per annum including a local weighting allowance and threshold agreement.

Application form and further details from the Staffing Officer, The Hatfield Polytechnic, P.O. Box 109, Hatfield, Herts., or ring Hatfield 68100, Extn. 309

Please quote ref: 542

## Situations Vacant

**MEN!**  
**£70p.w.**  
**can be yours**

Jobs galore? Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

**London**  
**Computer Operators**  
**Training Centre**

172, Oxford Road

9-15, Oxford Street, W.1.  
Telephone: 01-734 2874

## Educational

### C AND E EXAM

Make sure you succeed with an ICS home study course for C and E Electrical Installation Work & Technicians. Radio/TV/Electronics Technicians. Telecomms Technicians and Radio Amateurs.

### COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

### TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits.

Get the qualifications you need to success. Free details from: International Correspondence Schools, Dept. 732X, Intertext House, London SW8 4UJ. Or phone 01-622 9911.

**GO TO SEA** as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

## Books and Publications

### Technical Books - Radio & Electronics

Handbook of Tested Transistor Circuits.....	£0-40
Radio Servicing for Amateurs.....	£0-20
Radio TV and Electronics Data Book.....	£0-25
Coil Design and Construction Manual.....	£0-30
How to Solve Solid State Circuit Troubles.....	£1-75
Transistor Circuits Manual No. 1.....	£0-15
Transistor Circuits Manual No. 2.....	£0-15
Jack Darr's Service Clinic.....	£1-35
Transistor Circuits for Modern Test Equipment.....	£0-60
Rad & Electr Colour Codes and Data Chart.....	£0-15
Handbk of Transistor Equiv. and Substitutes.....	£0-40
Hi Fi, PA & Disco Amplifier Design Hndbk.....	£0-75
Radio Servicing Problems.....	£0-45
Electronic Circuits for the Amat. Photographer.....	£0-60
Handbook of Simple Transistors for the Home.....	£0-35
How to build Solid State Audio Circuits.....	£1-75
Sound and Loudspeaker Manual.....	£0-50
TV Technicians Bench Manual.....	£2-50
Radio TV and Industrial Tube & Valve Equiv.....	£0-40
Audio Amplifiers.....	£0-53
Television Servicing Vol. No. 1.....	£0-85
Television Servicing Vol. No. 3.....	£0-60
Television Servicing Vol. No. 4.....	£0-85
Radio Technicians Bench Manual.....	£3-00
Servicing Transistor Radio Receivers.....	£0-75
Television Timebase Circuits.....	£1-00
2nd Book of Hi Fi Loudspeaker Enclosures.....	£0-60
Manual of Electronic Circuits for the Home.....	£0-50
Modern Crystal Set Circuits for Beginners.....	£0-35
Electronic Novelties for the Motorist.....	£0-50
2nd Book of Transistor Equiv. & Substitutes.....	£0-95
Handbook of Electronic Musical Novelties.....	£0-50
Transistorised Novelties for Hi Fi Enthusiast.....	£0-35
Fault Location Exercises in Rad. & TV Vol.1.....	£0-80
Fault Location Exercises in Rad. & TV Vol.2.....	£1-35
Colour TV Picture Faults.....	£2-50
Practical Transistor Novelty Circuits.....	£0-40
Boys Book of Practical Radio & Electronics.....	£0-60
Radio Receiver Construction using ICs & Transis.....	£0-60
ICs & Transistor Gadgets Construction Handb'k.....	£0-60
Integrated Circuits Equiv. & Substitutes Hbk.....	£0-75

**FREE!** \*\*\*\*\*  
\* A 'Resistor Colour Code Disc Calculator' \*  
\* (Invaluable to the keen radio constructor!) \*  
\* OFFERED FREE ON REQUEST FOR ORDERS £3 AND OVER \*  
\* PLEASE ADD 10% FOR POSTAGE & PACKING \*  
**RADIO BOOK SERVICE**  
40 Elwill Way, Beckenham BR3 2RZ

**UFO CHARTS.**—Wave Prediction, 49p; Daily Flight Pattern, 44p; Map, 44p; TV UFO Detection, 2 Optical Circuits, 55p; Propulsion Theory, 55p; Gravity Theories, 55p. Circuits: Transistor Optical, 66p; Radiation/Optical, 40p; Microdetector with memory, LSI, 75p. R. & E., Highlands, Needham, Suffolk.

**ANTIQUÉ WIRELESS ENTHUSIASTS.** For valves, spares, service data and complete sets 1920-1950, contact Tudor Rees, 18 Brook Road, Mangotsfield, Bristol. Tel: 0272-565238.

**TV TECHNIC PUBLICATIONS.** Unique format godsend to engineers. Suitable Hams / Instructors. Circular plus sample page request. Turner (M.W.), 16 Jersey St., Newark, Notts NG24 4NE.

## Receivers and Components

### CRATA F.M. TUNER

Pack 1.	1. Resistors	36p
	2. Capacitors	£1-70
	3. Semi Conductors	£5-85
	4. Inductors & filters	£7-00
	5. Chassis & hardware	£5-00
	6/7. A.M. Parts	£3-65

### TEXAN 20 + 20W AMP.

Pack 1.	1. Resistors	80p
2/3.	Capacitors	£3-65
4.	Sundries	£2-50
5.	Switches	£1-00
6.	Potentiometers	£1-45
7.	Semi Conductors	£8-25
8.	Transformer	£6-95
9.	Printed Circuit	£2-50
10.	Chassis	£3-00
11.	Cables	40p

### V.A.T. EXTRA

add 20p p/p etc. except transformer (35p)

S.A.E. for lists

**TERERADIO ELECTRONICS,**  
325-7 Fore Street, Edmonton,  
London N9 0PE 01-807-3719  
Closed Thursdays

## ALLARD ELECTRONICS

Branded Components—Full Specification

TRANSISTORS	SCR's	DIODES	Price
AC125/4/7/8	0-15 CRS1/05	1N914	0-05
AD140/145	0-49 CRS1/20	1N4001/2/3/4/08	
AD161/162	0-57 CRS1/40	1N4005/6/7/8/06	
AF114/5/6/7	0-15 CRS3/40		
AF118	0-85 CRS7/400		
BC107/8/9	0-08 CRS16/100		
BC147/8/9	0-10 CRS16/200		
BC182/3/4	0-10 CRS16/600		
BC215/3/4	0-11 I.C's		
BCY70/1/729-15	1-15 TBA800		
BD131/132	0-85 free data		
BF194/5/6	0-13		
BFY30/51/52/53	0-16		
BY127	0-25		
MLF870	0-62		
MJ1371	0-73		
OC28	0-50		
OC35	0-50		
OC38	0-50		
TTL209	0-82		
2N2218	0-19		
2N2906	0-13		
2N2926 all	0-11		
2N3053	0-15		
2N3054	0-50		
2N3055	0-44		
2N3702/3/4	0-10		
2N3703/6	0-10		
2N3707/8/9	0-10		
2N3819	0-29		

### BRIDGE RECTIFIERS—

Price each

D.I.V. 1A 2A 4A 6A

50v 0-24 0-34 — 0-64

100v 0-24 0-39 0-54 0-69

200v 0-27 0-44 0-58 0-79

400v — 0-49 0-64 0-89

600v 0-28 0-74 —

299/301 BALLARDS LAE

LONDON N12 8NP

MAIL ORDER ONLY Telephone enquiries:  
01-445 5188 Cash with order. Add V.A.T.  
Orders under £2 plus 12p P. & P.

250mA Cartridge Fuses 1½", 90p per 100.  
Unused Carbon Resistors. 100 different 45p your choice 70p per 100.  
Unused W/W Resistors—100 assorted £1-10.  
150 Assorted Capacitor Mixture, 85p.  
15b. 8 to 2BA Nut & Bolt mixture Brass 32p Steel 28p.  
20 Assorted Potentiometers Unused £1-15.  
Ex Government Standard Jack Plugs 4 for 55p.  
New 6 volt 36 watt SBC Bulbs 70p per doz.  
Earphones Ex. Govt. 70p per pair.  
Modulator Speech Amplifier Unit for Transmitters. New & Boxed 16½" x 8½" x 9½". 8 valves. Meter. Carbon & Dynamic Mike inputs. £4-50.  
(All postage included in price.)  
**SOUND SYSTEMS OF SUFFOLK**  
676 Foxhall Rd., Ipswich, Suffolk IP3 8NQ



## Precision Polycarbonate Capacitors


All High Stability - Extremely Low Leakage

440V AC (±10%)		63V Range	
0.1µF (14" x 4")	80p	±1%	±2%
0.22µF (14" x 4")	50p	±1%	±2%
0.25µF (14" x 4")	68p	1.0µF	68p
0.47µF (14" x 4")	71p	2.2µF	80p
0.5µF (14" x 4")	75p	4.7µF	11.80
0.68µF (27" x 1")	80p	6.8µF	11.84
1.0µF (27" x 1")	81p	10.0µF	22.00
2.0µF (27" x 1")	11p	15.0µF	42.76

TANTALUM BRAD CAPACITORS - Values available:  
 0.1-0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V;  
 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V;  
 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V.  
 ALL at 10p each, 10 for 85p, 50 for 24.

TRANSISTORS:		BC183/183L		BFY50	
BC107/8/9	9p	BC184/184L	12p	BFY51	20p
BC114	12p	BC212/212L	14p	BFY52	20p
BC147/8/9	10p	BC647/553A	12p	AF178	30p
BC183/18	12p	BF194	12p	OC71	12p
BC182/182L	11p	BF197	12p	2N3055	80p

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 80p;  
 1N916 5p, 6 for 45p, 14 for 80p; 1844 5p, 11 for 50p,  
 24 for 81.00, 1N4148 6p, 6 for 27p, 12 for 45p; 1N4001  
 5p; 603 6p; 603 6p; 604 7p; 605 7p; 606 3p; 607 8p;  
 607 8p; 608 8p; 609 8p; 610 8p; 611 8p; 612 8p; 613 8p;  
 614 8p; 615 8p; 616 8p; 617 8p; 618 8p; 619 8p;  
 620 8p; 621 8p; 622 8p; 623 8p; 624 8p; 625 8p;  
 626 8p; 627 8p; 628 8p; 629 8p; 630 8p; 631 8p;  
 632 8p; 633 8p; 634 8p; 635 8p; 636 8p; 637 8p;  
 638 8p; 639 8p; 640 8p; 641 8p; 642 8p; 643 8p;  
 644 8p; 645 8p; 646 8p; 647 8p; 648 8p; 649 8p;  
 650 8p; 651 8p; 652 8p; 653 8p; 654 8p; 655 8p;  
 656 8p; 657 8p; 658 8p; 659 8p; 660 8p; 661 8p;  
 662 8p; 663 8p; 664 8p; 665 8p; 666 8p; 667 8p;  
 668 8p; 669 8p; 670 8p; 671 8p; 672 8p; 673 8p;  
 674 8p; 675 8p; 676 8p; 677 8p; 678 8p; 679 8p;  
 680 8p; 681 8p; 682 8p; 683 8p; 684 8p; 685 8p;  
 686 8p; 687 8p; 688 8p; 689 8p; 690 8p; 691 8p;  
 692 8p; 693 8p; 694 8p; 695 8p; 696 8p; 697 8p;  
 698 8p; 699 8p; 700 8p; 701 8p; 702 8p; 703 8p;  
 704 8p; 705 8p; 706 8p; 707 8p; 708 8p; 709 8p;  
 710 8p; 711 8p; 712 8p; 713 8p; 714 8p; 715 8p;  
 716 8p; 717 8p; 718 8p; 719 8p; 720 8p; 721 8p;  
 722 8p; 723 8p; 724 8p; 725 8p; 726 8p; 727 8p;  
 728 8p; 729 8p; 730 8p; 731 8p; 732 8p; 733 8p;  
 734 8p; 735 8p; 736 8p; 737 8p; 738 8p; 739 8p;  
 740 8p; 741 8p; 742 8p; 743 8p; 744 8p; 745 8p;  
 746 8p; 747 8p; 748 8p; 749 8p; 750 8p; 751 8p;  
 752 8p; 753 8p; 754 8p; 755 8p; 756 8p; 757 8p;  
 758 8p; 759 8p; 760 8p; 761 8p; 762 8p; 763 8p;  
 764 8p; 765 8p; 766 8p; 767 8p; 768 8p; 769 8p;  
 770 8p; 771 8p; 772 8p; 773 8p; 774 8p; 775 8p;  
 776 8p; 777 8p; 778 8p; 779 8p; 780 8p; 781 8p;  
 782 8p; 783 8p; 784 8p; 785 8p; 786 8p; 787 8p;  
 788 8p; 789 8p; 790 8p; 791 8p; 792 8p; 793 8p;  
 794 8p; 795 8p; 796 8p; 797 8p; 798 8p; 799 8p;  
 800 8p; 801 8p; 802 8p; 803 8p; 804 8p; 805 8p;  
 806 8p; 807 8p; 808 8p; 809 8p; 810 8p; 811 8p;  
 812 8p; 813 8p; 814 8p; 815 8p; 816 8p; 817 8p;  
 818 8p; 819 8p; 820 8p; 821 8p; 822 8p; 823 8p;  
 824 8p; 825 8p; 826 8p; 827 8p; 828 8p; 829 8p;  
 830 8p; 831 8p; 832 8p; 833 8p; 834 8p; 835 8p;  
 836 8p; 837 8p; 838 8p; 839 8p; 840 8p; 841 8p;  
 842 8p; 843 8p; 844 8p; 845 8p; 846 8p; 847 8p;  
 848 8p; 849 8p; 850 8p; 851 8p; 852 8p; 853 8p;  
 854 8p; 855 8p; 856 8p; 857 8p; 858 8p; 859 8p;  
 860 8p; 861 8p; 862 8p; 863 8p; 864 8p; 865 8p;  
 866 8p; 867 8p; 868 8p; 869 8p; 870 8p; 871 8p;  
 872 8p; 873 8p; 874 8p; 875 8p; 876 8p; 877 8p;  
 878 8p; 879 8p; 880 8p; 881 8p; 882 8p; 883 8p;  
 884 8p; 885 8p; 886 8p; 887 8p; 888 8p; 889 8p;  
 890 8p; 891 8p; 892 8p; 893 8p; 894 8p; 895 8p;  
 896 8p; 897 8p; 898 8p; 899 8p; 900 8p; 901 8p;  
 902 8p; 903 8p; 904 8p; 905 8p; 906 8p; 907 8p;  
 908 8p; 909 8p; 910 8p; 911 8p; 912 8p; 913 8p;  
 914 8p; 915 8p; 916 8p; 917 8p; 918 8p; 919 8p;  
 920 8p; 921 8p; 922 8p; 923 8p; 924 8p; 925 8p;  
 926 8p; 927 8p; 928 8p; 929 8p; 930 8p; 931 8p;  
 932 8p; 933 8p; 934 8p; 935 8p; 936 8p; 937 8p;  
 938 8p; 939 8p; 940 8p; 941 8p; 942 8p; 943 8p;  
 944 8p; 945 8p; 946 8p; 947 8p; 948 8p; 949 8p;  
 950 8p; 951 8p; 952 8p; 953 8p; 954 8p; 955 8p;  
 956 8p; 957 8p; 958 8p; 959 8p; 960 8p; 961 8p;  
 962 8p; 963 8p; 964 8p; 965 8p; 966 8p; 967 8p;  
 968 8p; 969 8p; 970 8p; 971 8p; 972 8p; 973 8p;  
 974 8p; 975 8p; 976 8p; 977 8p; 978 8p; 979 8p;  
 980 8p; 981 8p; 982 8p; 983 8p; 984 8p; 985 8p;  
 986 8p; 987 8p; 988 8p; 989 8p; 990 8p; 991 8p;  
 992 8p; 993 8p; 994 8p; 995 8p; 996 8p; 997 8p;  
 998 8p; 999 8p; 1000 8p; 1001 8p; 1002 8p;  
 1003 8p; 1004 8p; 1005 8p; 1006 8p; 1007 8p;  
 1008 8p; 1009 8p; 1010 8p; 1011 8p; 1012 8p;  
 1758 8p; 1759 8p; 1760 8p; 1761 8p; 1762 8p;  
 1763 8p; 1764 8p; 1765 8p; 1

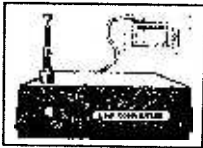

### UHF TO VHF CONVERTER

As most high level transmissions are now moving to UHF this unit enables their reception without the necessity of an expensive receiver.

The unit will receive frequencies in the range 420-470 MHz or to customers requirements and allows any VHF radio to receive UHF transmissions.

To operate: Connect crocodile clip to any VHF radio aerial, in the down position, switch converter on, tune VHF radio to 100-108 MHz on dial and receive UHF communications band.

The converter is of rigid metal construction and housed in a strong plastic case. The circuitry uses tuned lines in oscillator and RF circuits facilities are made for peaking I.F. output between 100-108 Mc/s. Power supply is from an internal 9 volt battery.

Unit dimensions: App. 6" x 3" x 1"; aerial 6". An interesting feature is that the converter can be used to feed several VHF radios enabling a number of UHF channels to be received simultaneously.

**CONVERTER, ready to use — £25.50**

MAIL ORDER. C.O.D. (Reg., P. & P., 45p)

The illustration features a converter in use, with crocodile lead connected.

## MULLHALL ELECTRONICS

ARDGLASS, Co. Down, BT30 7SF Tel. 033 684 461

### MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0-06-3A — 6 Ranges.

A-AC 0-3-3A — 5 Ranges.

V-DC 0-6-1200 V — 9 Ranges.

V-AC 3-300 V — 8 Ranges.

Freq. in the range of 45 to 20KHz.

Resistance: 500 Ohm to 5 MOhm.


5 Ranges. Decibel: —10 to +12dB.

Accuracy: ± 2.5% DC. ± 4% AC

Dimensions: 167 x 98 x 63 mm.



Only **£8.85**

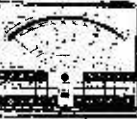

### SUPRETESTER 608R ICE

10 Fields — 80 Ranges: Plus

a lot of accessories for

measurements of 500A-AC

100 A/DC — Temperature-

50C to +200C — Magnetic

fields up to 15 KGauss-

Phase Indicator— EHT 25kV

Electronic Volt Ohm- meter

Transistor Diode Tester etc.

Dimensions: 123 x 95 x 32 mm-

300 grams 20kOhm Accuracy

1% DC. Ask for free catalogue

**£18.50**

Accessories Extra

### ALPHANUMERIC NIXIE TUBES B7971

The Alpha-numeric NIXIE tube has the ability to display all the letters of the alphabet

numerals 0 thru 9 and special characters in a single tube.

From the standpoint of both readability and

electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits

including ★ All DC operation ★ Uniform, continuous line characters of equal height

★ Memory with simple solid state drive circuits

★ Readability in high ambient light—200 foot-

lamberts brightness ★ Long life with no loss of brightness

★ Character height 2½ in.



Price only **99p** each plus 16p P/P.

### SPECIAL OFFER

The Sinclair Scientific.

Logs, trig and arith-

metic. All at the touch

of a button.

At last there's a pocket calculator

which gives you log and trig

functions instantly.

Full 12 function machine

With the functions available on the Scientific

keyboard, you can handle directly logs, anti-

logs, sin and arcsin, cos and arccos, tan and

arctan, automatic squaring, automatic doubling,

xy (including square and other roots), plus, of

course, addition, subtraction, multiplication,

division and any calculations based on them.

7-digit scientific notation, 200-decade range,

Reverse Polish logic and 26-hour battery life.

Send for further information. **£27.50**

Add 8% VAT to all items + 35p P & P

ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 2QB

Tel: 01-837 7781



## TREASURE TRACER

### MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Complete kit **£9.80** Built tested and guaranteed **£13.75**  
 P & P 45p — 13p VAT P & P 45p — 11p VAT  
 MINIKITS ELECTRONICS, 35a LANGLEY DRIVE, LONDON E11 2LN (Mail Order Only)

## PSYCHEDELICATESSEN

is the only way to describe the *paradise* of Freaky gear now available from Boffin. Look!

**KITS**

No Licence Exam Transmitter/Receiver **£6.40**  
 Variable-rate, Bright-Flash, Pocket Mini-Strobe **£2.40**

**READY-MADE MODULES**

Maxi-Volt Spark Generator (½ inch spark), 15,000 Volts! **£1.35**  
 Experimental Mini Dream-Lab-ratory **£2.20**  
 Sensitive non-anatomical electronic Stethoscope **£2.20**  
 Electronic 'Voice-Thrower' **£2.20**  
 Ghost-Hunting Aid **£2.20**  
 People Detector **£2.20**  
 Experimental Water-Fone **£4.40**  
 Psychedelic Meditation Aid **£2.20**  
 Bird-Watchers Remote Monitor **£2.20**  
 Psychological Cross-Eyed Ears Device **£4.40**  
 Super Sound-Catcher **£2.20**

(All prices include VAT, packing & postage)

Send remittance to:

**BOFFIN PROJECTS**  
 4 Cunliffe Road, Stoneleigh Ewell, Surrey  
 (Mail order U.K. only)

Or for more details, send 20p for lists, plus free design project sheet

# Synthesiser

## "Sounds Supreme"

### by Dewtron (VAT extra.)

Famous kits, e.g. waa-waa complete kit £3.50; Fuzz kit £5.50 P & P 25p under £10. Ring Modulator modules £9. 'Mister Bassman' Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

P.W. TENNIS. 12.NE555. 16.7400  
 24.IN914. 2.BC108. £11 inclusive. Island  
 Devices, P.O. Box 11, Margate, Kent  
 CT9 1QX.

### GADGETS GALORE!!

Alarms — Test Gear — Musical Instruments  
 Timers — Audio — Disco — Sound Effects

★ READY BUILT + TESTED ★

Sample prices: Signal Injector £1.95  
 Signal Tracer £2.95

Prices include U.K. Postage and Batteries  
 — Mail Order Only — S.A.E. list to:

**G.K. SERVICES,**  
 83 Westdale Road, London SE18 3BQ

**AIRCRAFT TYPE** servo position indicator and transmitter. Can be used for aerial direction indication. £1 (40p) per set. S.A.E. for details and list of ex-equipment components. Eldun Electronics, 16 Raven Road, Timperley, Cheshire.

**PRINTED CIRCUIT MANUFACTURERS** offer P.W. Project P.C.B.'s, 70p each. Also, Production, Design, Artwork, Photography, Electroplating, Screen-printing, Tinning, Undertaken. Estimates by return or phone W.K.F. Electronics, Welbeck St., Whitwell, Worksop, Notts. Tel. 695.

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from heavy duty PVC faced steel, choice of 212 types, send for free list. Bazelli Instrument Cases, Dept 25, St. Wilfrids, Lane, Halton LA2 6LT, Nr. Lancaster.

**PRINTED CIRCUIT BOARDS.** Any P.C.B. published in Practical Wireless/Electronics, E.T.I., W.W. etc. Any month any year. In fibreglass at 5p/sq. in. Postage free (min 50p). Also Artwork and/or photography undertaken. S.A.E. for full details. P.W. Tele-Tennis £5.50. P. Lancaster, 11 Chesterton Road, Cambridge, Cambs. CB4 3AD.

**SUPER SPACER PACKS** containing 150 assorted spacers ¼-¾ at ½ long, 4 at 6BA clearance types plus 150 mixed 4 at 6BA screws, nuts, and washers to fit. 600 brand new top quality components for only £2.50 plus 20p postage. Lists 7p. Electro-Mech Products, 7 Chantry Avenue, Bideford, Devon.

**AERIAL WIRE.** High quality PVC covered multi-strand copper, 50ft 60p (10p), 75ft 86p (13p), 100ft £1.19 (15p), 150ft £1.77 (24p), 200ft £2.36 (26p), 250ft £2.95 (28p), 300ft £3.54 (31p). Egg insulators 12p pair (6p). P&P in brackets. S.A.E. all enquiries. A.I. Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

**LOW COST I.C. MOUNTING.** Lengths of 100 I.C. pin sockets, 60p (p & p 5p). Quantity rates, SAE details & sample. L.E.D. (MLED500), 20p each. (post paid). P.K.G. Electronics, "Oak Lodge", Tansley, Derbyshire.

**JOYMATCH A/B:** Better than Big Set performance from your transistor radio! "Non-existent" stations come in like local. Big saving in battery costs. Quality greatly improved. High rise flat problem solved. Refund if not delighted £5.71. Partridge Electronics Ltd., Broadstairs, Kent.

**MULLARD 10W RMS AUDIO AMPLIFIER MODULES.** Brand new, for 24 volt 4 ohm operation. Tremendous offer, absolutely no extra components or hardware required. Supplied with circuit and full data for simple operation. £2.65 INCLUSIVE. LTE, 46 Minehead Road, South Harrow, Middx. Mail order only.

**AUDIOSCAN**, the "do-it-yourself" speaker mail-order specialists. High fidelity speaker kits, chassis units, sound absorbent, grille fabric and much more. Send 7p in stamps for bargain list to: Audioscan, Dept. PW-6, 4 Princes Square, Harrogate, Yorks.

**PRECISION** turned steel nuts 8, 6, 5, 4BA 20p per 100. 2BA 23p per 100. 0.T1.BA 36p per 100 P & P 17p. C. Cooke, 66 Park Road, Enfield Wash, Middx EN3 6SR.

**HARDWARE SUPPLIES.** Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers etc. Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes etc. 7p for list. Remar Constructor Services, 29 Shelbourne Road, Stratford on Avon. Warwick. CV37 9JP.

**ENERGY CRISIS?** The distant Radio Station powers your World's first DX-CRYSTAL SET; general coverage, with Aerial and Earpiece £3.56. Costs nothing to run. Partridge Electronics Ltd., Broadstairs, Kent.

### Ladders

**LADDERS 'Special Offer'.** Unvarnished triples. 9ft 7in closed—23ft 1in extd. £18.52 delivered. Home Sales Ladder Centre (WLS2) Haldane (North) Halesfield (1) Telford, Shropshire. Tel: 0952-586644 and pay at the door.

Please mention  
**PRACTICAL  
WIRELESS**  
when replying to  
Advertisements

### AERIAL BOOSTERS £3.30

We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF, RADIO

### VALVE BARGAINS

Any 5—50p, 10—75p, 50—£3.30 :—  
ECC82, ECL80, EB91, EBF89, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, EH90, PC88, PC86.

### TV COLOUR VALVES

PL508, PL509, PY5001A, 25p EACH.  
Press Button U.H.F. Tuners—£2.50.  
Rotary U.H.F. Tuners—£2.00.

### PLUGS—SOCKETS

Price per item, in brackets for ten  
**CO-AX PLUGS** 6p (50p) Socket surface 7p (60p), Connectors 4p (35p).

### D.I.N. PLUGS

2 pin, 3 pin and 5 pin 20p (£1.65).  
**JACK PLUGS.** Standard 18p (£1.50), 3.5 mm 10p (80p), 2.5 mm 10p (80p).

All prices include V.A.T. P. & p. 10p per order. Money back refund. S.A.E. for leaflet

### ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036.

# verobox



## ALUMINIUM ENCLOSURES

- 6 standard sizes available from your local retailer.
- Made from precision extrusions with integral board guide slots
- Finned sides improve appearance and radiate heat.
- Parallel sides for ease of component mounting.



### VERO ELECTRONICS LTD.

Castleigh, Hants. SO5 37R.  
Tel: Chandler's Ford 2352 Telex: 47551

Subsidiaries and Agents  
throughout the World

## BUILD A PROFESSIONAL TELEVISION CAMERA

Complete kits available as designed by "Mullard" Includes a comprehensive construction manual, lens tube and lens at £60.00 + VAT. Lens and tubes also available from stock. UHF Modulator Kits at £7.19 including P. & P. & VAT. Allows standard domestic TV to be used as monitor (Modulator also suitable for TV Tennis and other similar games).

Send 5p stamp for illustrative brochure and price sheet.


## GROFTON ELECTRONICS

124 Colne Road, Twickenham, Middlesex TW2 6QS.  
Tel. 01-898-1569

### NEW IMPROVED

## MAINS INTERCOM


NO BATTERIES  
NO WIRES

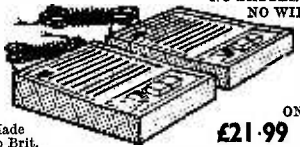

Made in Brit. Safety & Telecom. Standards, Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal-clear communication from room to room. Operates over a 2-mile range. On/Off switch, Vol. control. Useful as office intercom, baby alarm, invalid. No G.P.O. licence reqd. Full price ref. If returned in 10 days. 12 months service guarantee. P. & P. 60p.

ONLY £21.99 per pair + VAT £1.76
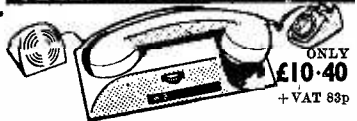
## NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £10.40 + VAT 85p

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £11.50 + VAT 92p. P. & P. 48p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW11)  
169 KENSINGTON HIGH STREET, LONDON, W.8

### TRANSISTORS (p. & p. 10p.)

All new and full spec.  
BC107/8/9, BC147/8/9, BC157/8/9 all 9p  
BF180 25p, BF182/3 40p, BF184 17p,  
BF187 13p, BFW10 55p, 741 8DIL 34p,  
BF336 35p, 2N3771 £1.10

### EX COMPUTER PC PANELS

4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data 25 boards £1 (30p)  
Dural extruded heatsinks, 10D outline, black anodised, drilled for 4 x TO3 transistors 5 x 4 x 1 1/4 40p (15p)  
Sim. to above but for 8 x TO3 5 x 8 x 1 1/4 70p (27p)

### ELECTROLYTICS

15,000µ 30v	65p (22p)
30,000µ 25v	65p (22p)
4,000µ 70v, 3,600µ 40v 4 x 2"	55p (15p)
5,000µ 35v	40p (12p)
20A 100 p1v Si recs.	4 for £1 (12p)
3A 100 p1v Si recs	4 for 50p (8p)
250 mixed resistors	60p (13p)
250 mixed capacitors	60p (11p)
150 mixed HI-STABS	60p (11p)
200 Si planar diodes	60p (8p)
QH bulbs 12v 55w	50p (7p)

Postage and packing shown in brackets

ADD 8% VAT TO TOTAL

## KEYTRONICS

(Mail Order only)


44 EARLS COURT ROAD  
LONDON W8. 01-478 8499

# SAXON

Money saving high performance audio equipment  
DIRECT FROM OUR OWN FACTORY

## GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- |   |               |               |  |
|---|---------------|---------------|--|
| <b>SA35</b><br>35W RMS 25-50V<br>7 transistors, 7 diodes.   | <b>£5.45</b>  | Carriage free | ★ 25Hz-25kHz<br>★ 0.2% distortion<br>★ Noise—80dB<br>★ 500mV into 20K                    |
| <b>SA50</b><br>50W RMS 25-65V<br>7 transistors, 7 diodes    | <b>£6.90</b>  | Carriage free | ★ 4-16 ohms<br>★ Simple wiring<br>★ Short and open circuit proof<br>★ Continuously rated |
| <b>SA100</b><br>100W RMS 45-70V<br>11 transistors, 6 diodes | <b>£10.90</b> |               | ★ Top-grade components   |
- 120 watt module complete with built-in supply—extra heavy duty £19.75 Carr. 60p**

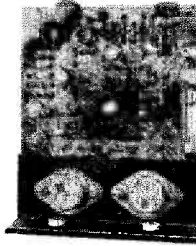

THE SA100 MODULE

## POWER SUPPLIES

### UNSTABILISED

- |             |                         |              |              |
|-------------|-------------------------|--------------|--------------|
| <b>PU45</b> | Suits 2 SA35 or 1 SA50  | <b>£4.90</b> | Carriage 30p |
| <b>PU70</b> | Suits 2 SA50 or 2 SA100 | <b>£7.75</b> | Carriage 40p |

### STABILISED

- |             |                        |              |               |
|-------------|------------------------|--------------|---------------|
| <b>PS45</b> | Suits 2 SA35 or 2 SA50 | <b>£3.50</b> | Carriage free |
| <b>MT45</b> | Transformer for above  | <b>£3.50</b> | Carriage 30p  |
| <b>PS70</b> | Suits 2 SA100          | <b>£4.90</b> | Carriage free |
| <b>MT70</b> | Transformer for above  | <b>£4.90</b> | Carriage 40p  |

N.B. PS70 is not suitable for the SA50

## Mk II STEREO DISCO MIXER £19.75 Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble, Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep.



## DISCO MODULE £8.00 Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: h/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



## 3-CHANNEL SOUND-LITE £22.50 Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



ADD 10% VAT TO ALL ORDERS

**SINGLE CHANNEL VERSION £7.50 Carr. free**  
Recently reduced in price due to increasing demand handles 1kW. Full wave operation


## MULTI-PURPOSE MIXERS

**M4HL £18.50 Carr. 50p**  
**M6HL £27.50 Carr. 50p**

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.
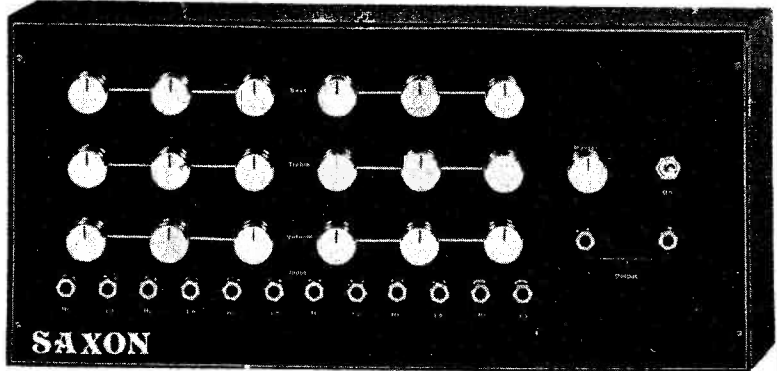
## VA30 CHANNEL MODULE £3.50 Carr. free


This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)



## SAXON CSE 100 COMPLETE AMPLIFIER

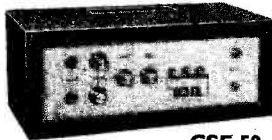**£34.90 Carr. free**

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinylite case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



**CSE 50 £29.50 Carr. free**



sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

Four individually controlled FET input stages plus wide range bass and treble controls. 120V of speech and music output from twin loudspeaker

## SAXON 100 COMPLETE AMPLIFIER

**£53.00 Carr. free**

**SAXON 50 £37.50 Carr. free**

CALLERS AND MAIL ORDER:

## SAXON ENTERTAINMENTS LIMITED

327-333 WHITEHORSE ROAD • CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m. 5 p.m. — LUNCH 12.30 1.30 p.m. MAIL ORDER DESK: 10 a.m. 3 p.m.  
24-HOUR ANSWER SERVICE TEL. 01-684 6385

SEND 10p FOR OUR NEW 26-PAGE MANUAL which gives full details of the above products.

TERMS OF BUSINESS: C.W.O. or C.O.D. on receipt of 50p C.O.D. charge.

Please include S.A.E. with all enquiries.

VAT at 8% must be added to all orders including postage and carriage charges.

# TWO NEW ADDITIONS TO FANE 'POP' RANGE LOUDSPEAKERS

## POP 40 10" 40 Watt

Impedance  
8-15 ohms  
Gauss 14,000  
Voice Coil  
Diam. 1 1/2in  
Fitted  
Tweeter Cone  
Range  
50-15,000 Hz

Rec. Retail Price  
inc. VAT

**£10.95**




Also for those who can  
afford the very best  
For Instrument Reproduction

## CRESCENDO '12' B

Two Super Sensitive Models  
Ideal for Lead Guitar etc.  
12" 75 Watt 2" Pole Diam. Gauss 20,000
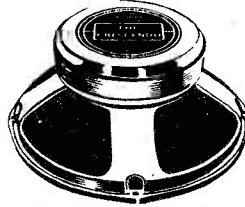
## CRESCENDO '15'

General Purpose  
15" 100 Watt 2" Pole Diam. Gauss 20,000



Rec.  
Retail  
Price

CRESCENDO '12' B

**£38.48**

Rec.  
Retail  
Price

CRESCENDO '15'

**£46.59**

There is also a 12" Crescendo  
Speaker for General Purpose  
Public Address, and a 12" and 15"  
for Bass Guitar etc.

Please send S.A.E. for leaflet on  
'POP' or 'CRESCENDO' Range Speakers

## POP 55 12" 60 Watt

Impedance  
8-15 ohms  
Gauss 15,000  
Voice Coil  
Diam. 2in

Range  
50-9,000 Hz  
AN ALL PURPOSE  
UNIT OF HIGH  
SENSITIVITY

Rec. Retail Price  
inc. VAT


**£15.99**


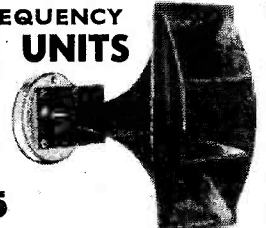
## HIGH FREQUENCY HORN UNITS

MODEL 910

Rating 25 to  
50 watts  
according to  
filter capacity



**£15.95**

inc. VAT

MODEL 920 (as illustrated) Rating with  
recommended filter  
100 watts

**£39.95**  
inc. VAT

Brief details of other 'POP' Speakers  
Rec. Retail

POP '15' 12" 15 Watt **£6.30**

1" Voice Coil inc. VAT

POP '25/2' 12" 30 Watt **£8.95**

2" Voice Coil inc. VAT

POP '50' 12" 50 Watt **£12.95**

2" Voice Coil inc. VAT

POP '60' 15" 60 Watt **£16.95**

2" Voice Coil inc. VAT

POP '100' 18" 100 Watt **£31.00**

3" Voice Coil inc. VAT

Distributors to Wholesale and Retail Traders—**LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.**  
Manufacturers enquiries to—**FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS**  
Prices shown correct at Sept 2, 1974

## H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

### 1974 "DX" RECEIVER

Complete kit—Price **£4.30** (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume."—"I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valver." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other E.W. Kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue of kits & components. Test Report available. **EXCITING COMPETITION** for Short-Wave listeners. Send stamped envelope for details.


"H.A.C." SHORT-WAVE PRODUCTS  
P.O. BOX No. 16, EAST GRINSTEAD,  
SUSSEX RH19 3SN

## MAINS UNITS for all types of TRANSISTOR EQUIPMENT

### RUN YOUR TAPE RECORDER OFF AC MAINS

Mains unit supplied complete and ready to plug into your cassette-recorder. (State voltage, make and type of plug required. If in doubt send diagram of recorder socket).

**ONLY £2.97**

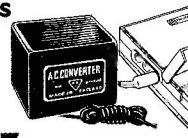

### CAR OWNERS

Buy a British Made battery eliminator for your car.

This unit enables you to run your cassette tape recorder from the car whilst travelling. It is easily fitted and comes complete with fitting instructions. Please state make of cassette, voltage and type of plug required.



Price **£2.65**

### MAINS UNIT FOR TRANSISTOR RADIO ONLY

For single outputs, 6v or 9v **£2.42**.  
For two separate outputs, 6v + 6v, or 9v + 9v, **£2.97** per unit. (Please state outputs required).

All units are completely isolated from mains by double wound transformer ensuring 100% safety.

ALL PRICES INC VAT & P. & F

BRITISH MADE

FULL REFUND IF NOT COMPLETELY SATISFIED

R.C.S. PRODUCTS (RADIO) LTD.

(Dept. P.W.J.)

36 Raymond Ave., South Woodford  
London, E18 2HG

HOMER 2 STATION KE550 INTERCOM **£3.95**

HILLS HI010ISM STEREO HEADPHONE WITH VOL-UME CONTROLS 30-18,000Hz

8Ω **£4.50**

JB3 HEADPHONE JUNCTION BOX **£1.37**

CAR STEREO SPEAKERS 8Ω **£4.50**

15ft Coiled Headphone ext. cable **£1.45**

20ft Coiled Guitar ext. cable **£1.50**

VYNIAR SPEAKER CLOTH

Black or Black & Silver **60p**

Sizes 18in x 25in **£1.10**

36in x 25in **£2.10**

36in x 50in **£2.20**

SOLDERING IRONS

CEN240 15watt **£2.08**

X25 25watt **£1.80**

Replacement Elements **£1.16**

Replacement Bits **40p**

S73 Stand **96p**

CARTRIDGES

Acos GP91-3SC Mono Crystal Compat. **95p**

GP93-1 Stereo Crystal **£1.30**

GP96-1 Stereo Ceramic **£1.70**

Sonotone 9TAMC Diam. **£1.95**

CASSETTE TAPE RECORDER

DYNAMIC MICROPHONE **£1.50**

Telephone Pickup Coil **45p**

Small Crystal Lapel Microphone **55p**

AC-DC Mains Adaptor 250Volt

4, 6, 7.5 and 9 Volt at 300mA **£2.95**

Visit our Warehouse for your requirements of Resistors, Capacitors, Transistors, ICs, Speakers, Metal Boxes, Headphones, Inter-coms, Meters, Audio Cables, Cartridges, Microphones, Wide Range of Plugs and Sockets, etc.

All prices include V.A.T.

Plus add 10% for P/P

Minimum Order **£1.00**

## HILLS COMPONENTS LTD

DEPT PW11 UNIT No. 6

MELINITE INDUSTRIAL ESTATE

BRIXTON ROAD, WATFORD, HERTS

WD2 5SL TEL WATFORD 27711



# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER, CALLERS SATURDAYS ONLY

C.W.O. Please. P. & P. add 15p to orders under £3. Prices exclusive of VAT

## TRANSISTORS (All Components Brand New and Fully Guaranteed)

AC125 14p	BC148/9 11p	MJE520 52p	TI29 43p	2N2894 30p	DIODES
AC128/7 14p	BC181 11p	MPF102 35p	TIP30 48p	2N2906 15p	AA120 10p
AC128 14p	BC183/4 11p	MPF103 35p	TIS43 25p	2N2907 15p	BY100 15p
AC176 14p	BC212 11p	MPF104 35p	ZTX107 10p	2N2926 5p	BY164 35p
AC187/8 12p	BC213/4 11p	MPF105 36p	ZTX108 10p	2N3953 20p	BYZ11 25p
ACV17 35p	BCV70 15p	OC26 42p	ZTX109 11p	2N3954 42p	OA5 39p
ACV19 24p	BCV71 15p	OC28 55p	ZTX300 13p	2N3955 50p	OA9 10p
ACV20 24p	BCV72 15p	OC35 48p	ZTX301 13p	2N3702/311p	OA79 10p
ACV21 25p	BD121 £1.00	OC41 15p	ZTX302 18p	2N3703/412p	OA81 8p
ACV22 19p	BD131 45p	OC42 15p	2N1131 20p	2N3705/610p	OA85 10p
AD140 48p	BD132 45p	OC44/45 12p	2N1132 20p	2N3707 10p	OA90/1 8p
AD149 48p	BDV19 £1.95	OC70/71 12p	2N1307/8 20p	2N3708/9 7p	OA200/1 6p
AD161 35p	BF184/5 15p	OC72 12p	2N1303/4 24p	2N3819 25p	PL4001 9p
AD162 35p	BF198 16p	OC74 22p	2N1305/6 24p	2N3903/4 15p	PL4004 9p
AF114/5 14p	BFY50 20p	OC81 12p	2N1307 26p	2N3905/6 17p	PL4007 12p
AF116/7 14p	BFY51 20p	OC82 15p	2N1671B 99p	2N4444 £1.80	1N914 5p
AF118 40p	BFY52 20p	OC83N 20p	2N1990 45p	ZENER	1N4001/2 6p
BC107 10p	BFY53 17p	OC140 60p	2N2217 23p	BZY88	1N4003/4 7p
BC108 10p	BSX29 40p	OC201 80p	2N2218A 20p	400mW	1N4005 7p
BC109 10p	MJE370 63p	OC202 80p	2N2203 75p	3-V-33V	1N4006/7 8p
BC147 11p	MJE371 63p	OC204 65p	2N2483 25p	1p each	1N4148 5p

## ICs TTL 74 SERIES

7400 18p	7427 37p	7472 28p
7401 18p	7428 43p	7473 37p
7402 16p	7430 18p	7474 37p
7403 16p	7432 37p	7475 55p
7404 20p	7433 43p	7476 37p
7405 18p	7437 43p	7480 69p
7406 39p	7438 43p	7481 £1.10
7407 39p	7440 18p	7482 96p
7408 21p	7441 75p	7483 £1.10
7409 24p	7442 75p	7484 95p
7410 20p	7443 £1.20	7485 £1.87
7411 22p	7444 £1.20	7486 38p
7412 20p	7445 £1.89	7490 69p
7413 28p	7446 £1.48	7491 99p
7414 60p	7447 £1.30	7492 99p
7416 35p	7448 £1.18	7493 69p
7417 35p	7450 18p	7494 80p
7420 18p	7451 18p	7495 80p
7422 75p	7453 17p	7496 99p
7423 38p	7454 17p	7497 £3.98
7425 38p	7460 18p	74104 60p
7426 28p	7470 28p	74105 59p

## LINEAR ICs

709C DIL/TO99 35p
723C DIL/TO99 80p
741 C 3 pin 41p
741 C 14 pin 41p
747C 85p
747C 85p
748C 85p
7805 (Reg.) £1.65
CA3020 £1.40
CA3069 £1.95
CA3046 80p
CA3075 £1.65
CA3090Q £3.50
MFC400B 40p
MC305 £1.70
MC724P 50p
MC1303L 50p
MC1304P £1.60
MC1310P £2.75
MC1710CG 40p
NE555 65p
TAD100 £1.35
TBA800 £1.59
ZN414 £1.15

## OPTO ELECTRONICS

Minitrans 3015F £1.20
OC270 40p
OC271 40p
OC272 40p
OC500 40p

## POWER SUPPLIES

470 C AC/DC O/P 6, 7, 8, 9V 300mA (4 way adaptor for radio, cassettes etc.) Price £2.15 p. & p. 15p
DC/DC /O/P 6, 7, 9V 300mA I/P 12V. Plugs to Cigarette Lighter price £1.95 p. & p. 15p.

## DIL SOCKETS

8, 14, 16 pin 15p each
------------------------

## POLYESTER CAPACITORS. Axial lead type.

400V: 0.001µF, 0.0015µF, 0.002µF, 0.003µF, 2µF, 0.0047µF, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 3p, 0.047µF, 0.068µF, 0.1µF, 4p, 0.15µF, 0.22µF, 7p, 0.33µF, 10p, 0.47µF, 13p, 160V: 0.1µF, 0.15µF, 4p, 0.22µF, 5p, 0.33µF, 8p, 0.47µF, 7p, 0.68µF, 10p, 1µF, 13p, 250V: 0.22µF 6p, 0.68µF 12p, 0.33µF 8p, 0.47µF 9p, 2.2µF 18p.
Radial lead P.C. type: 250V: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 3µF, 0.1µF, 4p, 0.15µF, 4p, 0.22µF, 0.33µF, 5p, 0.47µF, 7p, 1.0µF, 11p, 1.5µF, 15p, 2.2µF, 18p.

## ELECTROLYTIC CAPACITORS. Miniature axial lead type.

63V: 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 20µF, 22µF, 47µF, 68µF 6p; 100µF, 10p; 25V: 33µF, 68µF, 100µF, 150µF, 220µF, 11p; 470µF, 13p; 680µF, 13p; 1,000µF, 24p; 2,200µF, 33p; 3,000µF, 39p; 3,500µF, 39p; 16V: 40µF, 100µF, 125µF, 250µF, 6p; 1,000µF, 1,500µF, 16p, 10V: 4µF, 5p, 60µF, 10p, 1,000µF, 14p, 2,200µF, 18p.
--

## CERAMIC CAPACITORS

50V d.c. Plaquette body 25mm leads. Range: 5pF-10,000pF. Price 2p each. 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.1µF.
--

## POTENTIOMETERS AB Carbon Track

10k and linear values. 1kΩ-2MΩ Single gang 15p
5KΩ-500KΩ Single gang 25p
5KΩ-2MΩ Dual gang 42p

## SLIDER POTENTIOMETERS

0-25V Log and linear 5KΩ-500KΩ Single Gang 40p
10KΩ-100KΩ Dual Gang 55p
KNOBs for above Black or Silver 10p

## BRIDGE RECTIFIERS

1A 50V 20p	100V 1 Amp 30p
1A 100V 21p	400 1A 45p
1A 200V 21p	600V 1A 45p
1A 600V 25p	200V 3A 55p
2A 50V 40p	300V 5A 75p
2A 200V 40p	600V 7A 95p
2A 600V 54p	
4A 200V 45p	
4A 600V 70p	
6A 200V 68p	
6A 600V 87p	

## THYRISTORS

100V 1 Amp 30p
400 1A 45p
600V 1A 45p
200V 3A 55p
300V 5A 75p
600V 7A 95p

## ALUM. BOXES

2 1/2" x 3 1/2" x 1 1/2" 45p
4" x 4 1/2" x 1 1/2" 45p
4" x 2 1/2" x 1 1/2" 45p
4" x 5 1/2" x 1 1/2" 48p

## VEROBOARD

0-1	Pitch	0-15	0-15
		plain	14p
2 1/2 x 3"	30p	32p	15p
2 1/2 x 5"	32p	32p	15p
3 1/2 x 3"	32p	32p	15p
3 1/2 x 5"	38p	38p	26p
2 x 17"	98p	75p	55p
3 x 17"	139p	105p	79p
5 x 17"	173p		105p




Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2 5SF  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 0.15 in £ for postage and handling  
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop.  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

## AC/DC MULTIMETER TYPE U4324

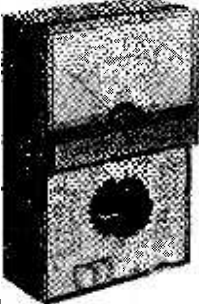

33 ranges up to  
3 Amps AC/DC;  
1200V DC, 900V  
AC, 500kΩ, +12  
db.

Sensitivity:  
20kΩ/V DC;  
4kΩ/V AC

Accuracy:  
±2.5% DC;  
±4% AC

Movement is protected by silicon diodes.

Dimensions 167×98×63 mm. Weight: 1.5lb.

PRICE: complete with test leads, instruction manual and fibre-board storage case £9.25. Packing & carr. £0.50.

## MULTIMETER TYPE U4323


Sensitivity: 20,000Ω/V.



7 D.C. Voltage ranges 0.5-1000V  
6 A.C. Voltage ranges 2.5-1000V  
5 D.C. Current ranges 0.05-500mA  
4 Resistance ranges 1kΩ-1mΩ  
Built-in oscillator providing AF output of 1kHz and I.F. output of 465kHz with an amplitude of 1 volt minimum.

Dimensions: 140×87×40 mm. Weight 0.5kg  
PRICE complete with leads and plastic storage case £7.70. Packing & postage £0.50

## AC/DC MULTIMETER TYPE U4313

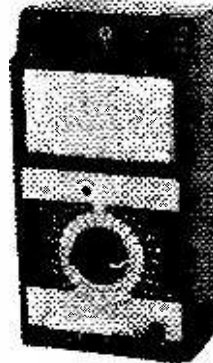


39 ranges:  
600μA to 1.5A  
AC  
60μA to 1.5A DC  
75mV to 600V  
DC  
1.5V to 600V AC  
1MΩ, 0.5μF, 12db  
Accuracy: 1.5%  
DC; 2.5% AC  
Sensitivity: 20k  
Ω/V DC; 2kΩ/V  
AC

Mirror scale 86mm long.

Dimensions: 115×215×90 mm, Weight 3.3lb.  
PRICE, complete with test leads, service manual and steel carrying case £12.50. Packing & carriage £0.50.

**ALL THE ABOVE INSTRUMENTS FEATURE TAUT SUSPENSION MOVEMENTS  
PRICES ARE EXCLUSIVE OF V.A.T.**
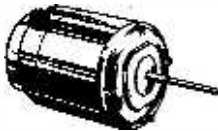
## "SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give DC., to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For A.C. (synchronous) operation at 120r, 50Hz. Speed 60 rpm at 60Hz, 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 1/4" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. **OUR PRICE ONLY £15**

### NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant. Ideal for P.C.'s  
Sizes: 12" x 12", 24" x 12", 24" x 24"; FULL SHEET 43" x 37" (11 sq ft). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.



### SMITHS RINGER-TIMER


Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P. & P.

### KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in desk sets, burgling devices, etc. Size (60 DB) 7/32" x 5/32" x 1/4"; (80 DB) 3/4" x 5/32" x 3/4". Equipment, all tested. £1.20 each. P. & P. FREE.

## Ultra PRECISION CENTRIFUGAL BLOWER

by Air Control Ltd.

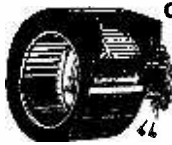

30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 A.C. Very powerful and silent running. 5 1/2" dia. 3" inlet dia. Outlet flange 3" x 2 1/2". **LIMITED NUMBER ONLY £8.95. P & P 40p.**

### MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "s l o w". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V AC. Pull at coil is approximately 1lb. £1. **FREE P. & P. Special quotes for quantities.**



### SOLENOIDS by WESTOOL

240AC type MM6. 3lb. pull, 2 1/2" x 1" x 1 1/2". Travel 1", 90p. each. P. & P. 10p.  
240AC type MM4. 2lb. pull, 1 1/2" x 1 1/2" x 1". Travel 3/4" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



### OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case)  
240 AC, 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p.  
Similar to above, 18rpm. £2.70. P. & P. 30p.  
110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.




## SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 5amp at 120v. 1/2amp at 240v. Size: (approx.) 1 1/2" long x 3/4" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8.80; 100 for £15.50. **FREE P. & P. over 10.**



## AMPEX 7.5v. D.C. MOTOR

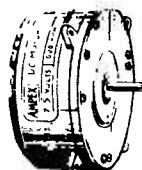

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 500rpm ± speed adjustment. Internal AF/RF suppression. 1/4" dia. x 1 1/2" spindle, motor 3/4" dia. x 1 1/2". Original cost £16.50. **OUR PRICE £3.30. P. & P. 25p.** Quantity available. Mu-metal enclosure available 75p each. **FREE P. & P.**

**ALL PRICES  
INCLUDE V.A.T.**

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

# ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD,  
LONDON, W2.  
Tel: 01-723 5667 01-402 5580

# FREE!

## Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call in on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course". Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects"—Student J.A.O. Dublin.

"My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". Student C.C.P., Bucks.

### FIND OUT FOR YOURSELF

These letters and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to Aldermaston College, Dept. BPW80, Reading RG7 4PF.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



**CUT OUT THIS COUPON**  
Tick or state subject of interest. Post to address below.

<b>MECHANICAL</b>	<b>DRAUGHTSMAN-SHIP</b>	Construction Surveyors Institute L.C.S.I. <input type="checkbox"/>
Society of Engineers— <input type="checkbox"/>	Institute of Engineering Designers (A.M.I.E.D.) General <input type="checkbox"/>	City & Guilds General Building (all branches) Heating & Vent. Inst. Clerk of Works <input type="checkbox"/>
A.M.S.E. (Mech) <input type="checkbox"/>	Draughtsmanship <input type="checkbox"/>	Site Surveying <input type="checkbox"/>
Institute of Engineer & Technicians (A.M.I.E.) <input type="checkbox"/>	Elec. Draughtsmanship <input type="checkbox"/>	Health Engineering <input type="checkbox"/>
<b>CITY &amp; GUILDS</b> <input type="checkbox"/>	Architectural Draughtsmanship <input type="checkbox"/>	Road Construction <input type="checkbox"/>
Gen. Mech. Eng. <input type="checkbox"/>	Technical Drawing <input type="checkbox"/>	Quantities <input type="checkbox"/>
Maintenance Eng. <input type="checkbox"/>		Estimates <input type="checkbox"/>
Welding <input type="checkbox"/>		Hydraulics <input type="checkbox"/>
Gen. Diesel Eng. <input type="checkbox"/>		Structural Eng. <input type="checkbox"/>
Sheet Metal Work <input type="checkbox"/>		
Eng. Inspection <input type="checkbox"/>		
Eng. Metallurgy <input type="checkbox"/>		
<b>ELECTRICAL &amp; ELECTRONIC</b>	<b>RADIO &amp; TELE-COMMUNICATIONS</b>	<b>GENERAL</b>
<b>CITY &amp; GUILDS</b>	City & Guilds Telecoms. <input type="checkbox"/>	Agricultural Eng. Council of Eng. Institutions <input type="checkbox"/>
Gen. Electrical Engineering <input type="checkbox"/>	Gen. Radio & TV Eng. <input type="checkbox"/>	Farm Science <input type="checkbox"/>
Electrical Installations <input type="checkbox"/>	Radio Amateurs Exam <input type="checkbox"/>	Plastics <input type="checkbox"/>
Computer Electronics <input type="checkbox"/>	Radio Servicing <input type="checkbox"/>	Supplementary courses for Nat. Certificates. <input type="checkbox"/>
Electronic Eng. <input type="checkbox"/>		
Practical Radio & Electronics (with kit) <input type="checkbox"/>		
<b>MANAGEMENT &amp; PRODUCTION</b>	<b>AUTOMOBILE &amp; AERONAUTICAL</b>	
Institute of Cost & Management Acctns. <input type="checkbox"/>	Institute of the Motor Industry A.M.I.I. <input type="checkbox"/>	
Computer Programming <input type="checkbox"/>	MAJIMI City & Guilds Auto Eng. <input type="checkbox"/>	
Works M'nt <input type="checkbox"/>	Gen. Auto Eng. <input type="checkbox"/>	
Works Study <input type="checkbox"/>	Motor Mechanics <input type="checkbox"/>	
Gen. Production Eng. <input type="checkbox"/>	Auto Diesel Eng. <input type="checkbox"/>	
Estimating & Planning <input type="checkbox"/>	Garage M'nt <input type="checkbox"/>	
Storekeeping <input type="checkbox"/>	ABC Aero Engineering Exams <input type="checkbox"/>	
Management Skills <input type="checkbox"/>	Gen. Aero Eng. <input type="checkbox"/>	
Quality Control <input type="checkbox"/>		
	<b>CONSTRUCTIONAL</b>	Coaching for many exams, including C & G <input type="checkbox"/>
	Institute of Building L.I.O.B. <input type="checkbox"/>	
	A.B.T. Clerk of Works <input type="checkbox"/>	

**G.C.E.**  
—choose from 58 'O' & 'A' level subjects

## POST TODAY FOR A BETTER TOMORROW

To Aldermaston College, Dept. BPW80, Reading RG7 4PF BPW80

NAME.....  
Block capitals please  
ADDRESS.....  
.....  
.....

OTHER SUBJECTS.....  
.....  
..... AGE.....

Accredited by C.A.C.C. Member of A.B.C.C

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. Publisher's subscription rate (including postage): for one year UK £3-25, Overseas £4-35. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.


# Henry's

## SO MUCH MORE - AND YOU PAY LESS VAT WITH HENRY'S LOW PRICES

UK's No. 1 for Electronics and Hi Fi
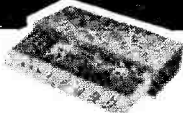
### You can build the Texan and Stereo FM Tuner TEXAN 20 + 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC board, Gardners low field transformer, 6-IC's, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15½" x 2½" x 6½" mains operated. Free teak sleeve with every kit. **£28.50 (GB post paid).**



**STEREO FM TUNER** Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 2½" x 6½". Complete kit with teak sleeve **£21.00 (GB post paid).**

**JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!**



### TRANSISTORISED MODULES

#### Tuners - Power Suppliers - Amplifiers

AMPLIFIERS (All single channel unless stated)	£ p
4-300 9 volt 300 MW O/P 3-8 OHM, 1-10 MV I/P Special Offer	1-75
2004 9 volt 250 MW O/P 3-8 OHM, 10-100MV I/P	2-70
104 9 volt 1 watt O/P 8-16 OHM, 10 MV I/P	3-10
9 volt 3 watt O/P 4-8 OHM, 10 MV I/P	3-95
555 12 volt 3 watt O/P 8-16 OHM, 150 MV I/P	4-10
555ST 12 volt 1½ + 1½ watt O/P 8 OHM, 150 MV I/P Stereo module	5-10
E1208 12 volt 5 watt O/P 4-16 OHM, 25-50 MV I/P	5-95
608 24 volt 10 watt O/P 4-8 OHM, 30-50 MV I/P	5-10
410 28 volt 10 watt O/P 8 OHM, 160 MV I/P	9-95
620 45 volt 30 watt O/P 4-8 OHM, 150 MV I/P	4-95
Z60 30/35 volt 15 watt O/P 4-8 OHM, 100 MV I/P	5-45
Z40 45/50 volt 25 watt O/P 4-8 OHM, 100-250 MV I/P	6-95
SA6817 24 volt 6 + 6 O/P 8 OHM 100 MV I/P Stereo module	10-20
<b>AMPLIFIERS with controls</b>	
E1210 12 volt 2½ + 2½ watts 8 ohms, Stereo	8-25
R 500 Mains 5 watts 4-16 ohms, Mono	6-30
SAC14 Mains 7 + 7 watts 8 ohms, Stereo	11-75
SAC30 Mains 15 + 15 watts 8 ohms, Stereo	14-95
CAO38 9 volt 1½ + 1½ watts 8 ohms, Stereo	6-95
CAO68 12 volt 3 + 3 watts 8 ohms, Stereo	10-50



FM Modules	£ p
Mullard LP 1186 FM tuner (front end) with data 10.7 MHZ O/P	4-85
Mullard LP 1185 10.7 MHZ IF unit with data	4-50
Gorler Permeability FM tuner (front end) 10.7 MHZ O/P	4-20
<b>FM and AM tuners and decoders</b>	
FM 5231 (tu 2) 6 volt fm tuner	7-95
TU3 12 volt version (FM use with Decoder	7-95
SD4912 Stereo Decoder for Tu 3, 12 volt	4-80
SP62H 6 volt stereo FM tuner	7-95
A1007 9 volt MW-AM tuner	11-95
Sinclair 12/45 volt FM tuner stereo recorder for above	7-45
A1018 9 volt FM tuner in cabinet	13-95
A1005M (S) 9-12 volt Stereo decoder FM for above	7-50
1062 12 volt Stereo decoder general purpose	6-50

All models fitted dials supplied with instructions

PREAMPLIFIERS	£ p
Sinclair Stereo 60 Preamp with controls	6-75
E1300 Cart/Tape/Mic Inputs 9 volt Module	2-85
E1310 Stereo 3-30 mV mal cart 9 volt	4-75
FF3 Stereo 5 mV tape head 9 volt	4-95
3042 Stereo 5-20 mV Mag. cart. mains	5-95
EQ25 Mono 3-250 mV Tape/Cart/Flay 9 volt	5-95
<b>Power Supplies Mains input (* chassis-rest cased)</b>	
470C 6.75/9V 300 MA w/whad's r's 2.25	7-80
*P1081 45V 0.9A	
P500 9 volt 500 MA	3-20
HC244R 3.75/7.5/9v. 400 MA	7-15
SE101A 3.6/9/12V. 1 amp stabilised	12-75
*P11 24v. ½ amp. 3-30	3-30
*P15 28v. ½ amp	3-30
*P1080 12V 1A 4-70	7-80
*P1076 3.4/6.7/9/12V. ½ amp	4-20
SE800A 1-15 VOLT 0-1A stabilised	17-50

### SINCLAIR MODULES & KITS

SINCLAIR PROJECT 80	£ p	PACKAGE DEALS (carr. packg 35p)	£ p
ST80 Stereo preamplifier	11-95	2 x Z40 ST80 PZ5	25-00
Audio Filter Unit	6-95	2 x Z60 ST80 PZ6	27-75
Z40 15 Watt Amplifier	5-45	2 x Z60 ST80 PZ8-trans	34-40
Z60 25 Watt Amplifier	6-95	Sinclair Special Purchases	
PZ5 Power Supply for 1 or 2 Z40	4-98	*Project 60 stereo preamp	£6-75 (post 20p)
PZ6 Power Supplies (5 Tab) for 1 or 2 Z40	7-98	*Project 605 Kit	£19-95 (post 25p)
PZ8 Power Supplies (5 Tab) for 1 or 2 Z60	7-98	Cambridge calculator kit	£13-84 (post 15p)
TRANSFORMER FOR PZ8	3-95	Sinclair Cambridge Memory	£25-95
FM TUNER	19-95	Cambridge Calculator built	£18-13 (post 15p)
STEREO DECODER	7-95	Cambridge Scientific built	£27-20 (post 15p)
IC20 power amp kit	7-95	All above post paid (GB only)	
PZ20 power supply for 1 or 2 IC20	5-45		

**TRANSISTORS/SEMICONDUCTORS**  
UK's largest stockists of branded guaranteed devices at low prices.  
**EXTRA DISCOUNTS**  
Any one type. Extra 10% for 12 | 15... 25 | 20... 100 |  
The above also applies to mixed SN74 series IC.  
Get your free stock list now—new '74-75 edition now available (Ref. No. 36).

### EXCLUSIVE DECCA KELLY SPEAKERS

12 watt speaker tweeter systems 8 in bass midrange, Melinex domed HF radiator plus crossover. Built into veneered cabinets size 18x12x6½ in. PRICE £19.50 pair (carr., etc. £1-00)




### EMI SPEAKERS SPECIAL PURCHASE

13 in x 8 in chassis speakers (Carr./packing 30p each or 50p pr.)  
\*150 TC 10 watts 8 ohms twin cone **£2.20**  
\*450 10 watts 4, 8, 15 ohm with twin tweeters and crossover **£3.85** each  
EY15 watt 8 ohm with tweeter **£5.25**  
350 20 watt 8, 15 ohm with tweeter **£7.80** ea.  
\* Polished wood cabinet **£4.80** carr., etc. 35p each or 50p pair.


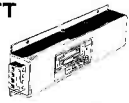
### PHILIPS 8 WATT FLUORESCENT UNIT

**EXCLUSIVE PURCHASE**  
Brand new Philips 12 volt operated 8 watt fluorescent tube units for standby lighting. Complete with tube and instructions. Price **£3.50** p & p 25p.



### EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load. 30 volt max. DC operation, complete with data. Price **£1.50** each or 2 for **£2.85**. Printed Circuit Panels. 50p



### UHF TV TUNERS

625 line receiver UHF transistorised tuners FM UK operation. Brand new. (Post packing 25p each).  
TYPE C variable tuning **£2.50**  
TYPE B 4-button push-button (adjustable) **£3.50**



### JOSTY KITS IN STOCK

(Post etc. 15p each)	£ p
AE20 Mono Transistor Amp.	5-61
AF25 Mono Trans. Pre-amp.	3-20
AF30 Mono Trans. Pre-amp.	3-20
AF35 Mono Trans. Pre-amp.	2-43
AF80 Mono Trans. Pre-amp.	4-86
AF305 Intercom	7-68
AF310/2 Mono Amplifier (for Stereo use two)	7-56
M160 Multivibrator	2-19
M1302 Transistor Tester	8-34
M191 Vu-Meter	5-37
M192 Stereo Balance Meter	5-94
LF380 Quadrophonic Device	8-43
AT60 Psychedelic Light Control, Single Ch.	10-82
AT65 Psychedelic Light Control, 3 Chan.	16-53
AT25 Window Wiper Robot	5-82
AT30 Photo Cell	
AT50 Switching Unit	6-69
AT55 400W Triac Light Dimmer Sp. Cont.	5-19
AT56 2-200W Triac Light Dimmer Sp. Cont.	6-75
AT5 Treble Unit for Guitars, etc.	8-10
H F61 Diode Detector	3-87
HF65 Frequency Modulated FM Transmitter	3-21
HF75 FM Trans. Receiver	3-66
HF310 FM Tuner Unit	16-31
HF325 De-luxe FM Tuner Unit	26-34
HF330 Stereo Decoder for use with HF310/325	10-56
GP310 Stereo Pre-amp (for use with 2 AF310)	22-98
GP312 Basis Circuit Board	10-02
GP304 Basis Circuit Board	5-33
HF380 Aerial Amp. for LW to VHF	6-03
HF395 Broadband Aerial Amp. 2-10	
NT10 Power Supply 100mA 9V Stab. & 12V Unstable	6-27
NT300 Professional Stab. Power Supply	13-17
NT310 Power Pack 2 x 15 volt 2A	5-64
NT305 Voltage Converter	5-64
NT330 Power Pack AF310/ GP304	6-27
NT315 P/5 240V ac to 4-5-15V dc. 500mA	12-06
AE1 Output Stage 100mV	1-56
AE2 Pre-amplifier	1-32
AE3 Diode-receiver	2-05
AE4 Flasher	1-26
AE5 A stable Multivibrator	1-14
AE6 Monostable Multivibrator	1-11
AE7 RC Generator	1-08
AE8 Bass-filter	1-06
AE9 Treble-filter	1-06
AE10 CCIR-filter	1-06

### FREE STOCK LISTS

No. 36 Transistors/valves/semiconductors No. 18 Disco-lighting—high power sound No. 17 Hi-Fi Tv-Tape Equipment. Send large stamped addressed envelope with all enquiries.

### HENRY'S HOME ENTERTAINMENT CENTRES

London  
354/6 Edgware Rd. W2 01-402 5854  
376/8 Edgware Rd. W2 01-723 2564  
372 Edgware Rd. W2 01-402 8140  
120 Shaftesbury Ave. W1 01-437 9692  
230 Tottenham Court Rd. W1 01-580 1785  
144 Burnt Oak B'way, Burnt Oak, Edgware 01-952 7402  
190/4 Station Rd., Harrow, Middlesex 01-863 7788  
Out of Town  
256 Banbury Rd., Summertown, Oxford (0865) 53072  
55 Gloucester Rd., Bristol 7 (0272) 45791

### SUPPLIERS OF ELECTRONICS FOR OVER 30 YEARS 8% VAT TO BE ADDED TO ALL ORDERS VAT-UK

# Henry's RADIO

EDGWARE ROAD, W2

Electronic Centres  
404-406 Electronic Components & Equipment 01-402 8381  
309 PA-Disco-Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW  
Prices correct at time of preparation. Subject to change without notice. E.&O.E

Hi Fi and Electronics Centres Open 9 am - 6 pm