

PRACTICAL WIRELESS


MAY
1975

30p

NEW!
the
All Electric
Wireless
FIRST TIME PUBLISHED

PW APOLLO series PART 1

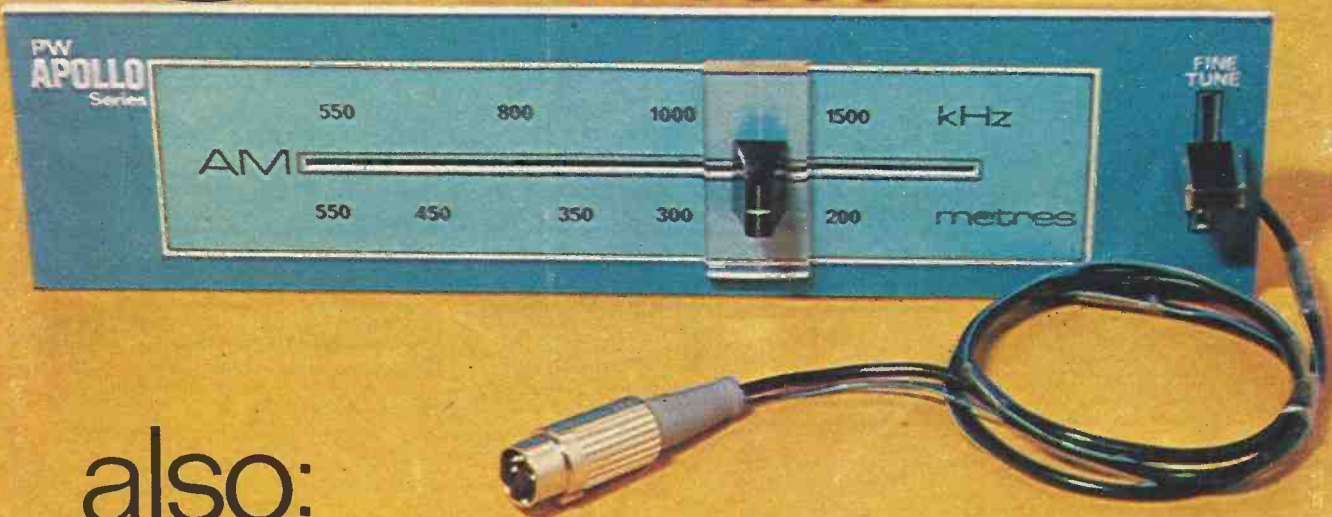TRIPLE VARICAP MEDIUM WAVE TUNER/RECEIVER



also:

**CAR WIPER DELAY UNIT
MODEL TRAIN CONTROLLER**

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ 5 Transistor Push Pull Amplifier.
- ★ Batteryless Crystal Radio.
- ★ Signal Tracer.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ One Transistor Radio.
- ★ Signal Injector.
- ★ 5 Transistor Short Wave Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 4 Transistor Tester NPN-PNP.
- ★ Electronic Metronome.
- ★ 3 Transistor Regenerative Radio.
- ★ 4 Transistor Push Pull Amplifier.
- ★ Electronic Noise Generator
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.


Total Building Costs

£7-23 P P & Ins. 44p
(Overseas Seamail P & P £2-35)
(+ 8% VAT 57p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3½" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6½ yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 55p free with parts.

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

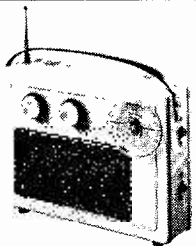


Nine Transistors, 9 Tuneable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors, 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9½" x 7" x 2½" approx. Parts Price List and Plans free with parts.

Total Building Costs £6-95 P P & Ins. 44p
(+ 8% VAT 55p) (Overseas Seamail P & P £2-35)


POCKET FIVE

NOW WITH 3" LOUD-SPEAKER

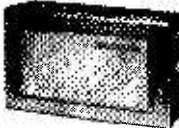

3 Tuneable wavebands, M.W. L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3½" approx. Plans and Parts Price List free with parts.

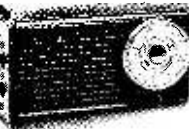Total Building Costs £2-50 P P & Ins. 36p
(+ 8% VAT 20p) (Overseas Seamail P & P £1-70)



TRANSONA FIVE NOW WITH 3" LOUDSPEAKER

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List free with parts.

Total Building Costs £2-75 P P & Ins. 36p
(+ 8% VAT 21p) (Overseas Seamail P & P £1-70)

TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tuneable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

Total building costs £4-48 P P & Ins. 40p
(+ 8% VAT 36p) (Overseas Seamail P & P £2-00)

ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tuneable Wavebands: MW, LW, SW1, SW2, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Plans and parts price list free with parts.

Total building costs £3-98 P P & Ins. 40p
(+ 8% VAT 32p) P & P £2-00)

NEW Everyday Series

Build this exciting New series of designs

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5½" x 2½" approx. Parts Price List and Plans free with parts.

Total Building Costs £2-95 P P & Ins. 36p
(+ 8% VAT 23p) (Overseas Seamail P & P £1-70)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 2" loudspeaker, etc. MW/LW coverage. Push Pull output. Parts Price List and Plans free with parts.

Total Building Costs £3-60 P P & Ins. 36p
(+ 8% VAT 29p) (Overseas Seamail P & P £1-70)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans free with parts.


Total Building Costs £4-08 P P & Ins. 38p
(+ 8% VAT 32p) (Overseas Seamail P & P £2-00)

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

7 Tuneable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price list and plans free with parts.

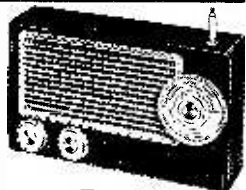Total building costs £6-98 P P & Ins. 47p
(+ 8% VAT 56p) (Overseas Seamail P & P £2-50)



ROAMER TEN Mk 2


WITH VHF INCLUDING AIRCRAFT

Now with free earpiece and switched socket. 10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeaker.

9 Tuneable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band.

Built in Ferrite Rod Aerial for MW/LW. Chrome plated 6 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p free with parts.

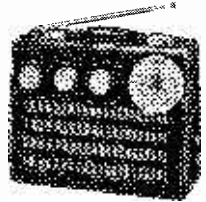Total building costs £9-50 P P & Ins. 52p
(+ 8% VAT 76p) (Overseas Seamail P & P £2-50)



"EDU-KIT"

Build Radios, Amplifiers, etc., from easy stage diagrams.

Five units including master unit to construct.

Components include:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three ½" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

Total building costs £5-50 P P & Ins. 35p
(+ 8% VAT 44p) (Overseas Seamail P & P £2-35)

RADIO EXCHANGE LTD

★ Callers side entrance "Lavelle's" shop.
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
Tel.: 0234 52367. Reg. No. 788372.

I enclose £..... for

Name

Address

(Dept. PW5.)

PRACTICAL WIRELESS

VOL. 51 NO. 1

ISSUE 819

MAY 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Sam Lewis B.Sc. (Eng.)

PRODUCTION & NEWS EDITOR

Colin R. Riches

TECHNICAL SUB-EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Jenny Maunder
Susan King

ADVERTS MANAGER

01-634 4293 Roy Smith

CLASSIFIED ADVERTS

01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.85 and to the rest of the world £4.95 (\$13.50 USA/CAN) including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.34) and indexes 30p (inc. VAT) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 20 FACT NOT FICTION—Leader article
- 21 NEWS... NEWS... NEWS...
- 25 LETTERS—Readers comment
- 42 HOTLINES on recent developments by *Ginsberg*
- 43 NEXT MONTH IN PRACTICAL WIRELESS
- 52 PRODUCTION LINES by *Colin Riches*
- 62 TELEVISION—coming in the May issue
- 66 ON THE AIR
- 66 Amateur Bands—*Eric Dowdeswell, G4AR*
- 69 Broadcast Bands—Medium Waves—*Charles Molic*,
- 69 Broadcast Bands—Short Waves—*Derek Bell*

● CONSTRUCTIONAL

- 22 MODEL TRAIN CONTROLLER—*John Lewis*
- 26 P.W. 'EASYBUILD' ELECTRONIC ORGAN—Part 3—*M. J. Hughes, M.A., C.Eng., MIERE*
- 37 CAR WIPER DELAY UNIT—*J. B. Harvey, B.Sc.*
- 44 P.W. 'APOLLO' Series—Varicap Receiver—Part 1—*W. Poel*
- 54 2 VHF CONVERTERS—Part 2—*G. Severn*
- 57 TAKE 20, No. 70—LED FLASHER—*David Andrews*

● OTHER FEATURES

- 51 GOING BACK—Earlier days of Wireless—*Colin Riches*
- 61 SPECIAL PRODUCT REPORT—SINCLAIR DM2 Digital Multimeter

HUGE DISCOUNTS

ON LEADING BRAND HI-FI ALL RSC PRICES INCLUDE VAT
LOW DEPOSIT CREDIT TERMS
 Full labour and material guarantees for 12 months
 List Price RSC Price

WHARFEDALE DENTON II £47.50 Pr. **£31.95**
 „ **DENTON I (White)** £33.78 Pr. **£22.95**

WHARFEDALE LINTON £59.75 Pr. **£39.95**
 „ **LINTON Spkr Kit** £28.90 Pr. **£19.50**

LEAK 2030 L/Spkr £83.99 Pr. **£69.00**
LEAK 2060 L/Spkr £72.54 Ea. **£57.50**
FANE MODE ONE Spkr Kit £23.98 Pr. **£18.95**
WHARFEDALE LINTON

Amplifier £68.04 **£49.95**

LINEAR 202 Amplifier £39.23 **£24.95**
ROTEL RX150A Tun/Amp £84.50 **£59.95**
ROTEL I52 Tuner/Amp £94.50 **£67.95**
ROTEL I54A (Quad) Amp £144.85 **£89.95**
ROTEL 202 Tuner/Amp £107.50 **£77.95**
ROTEL RT222 AM/FM Tuner £59.90 **£42.50**
ROTEL RT 322 £84.50 **£59.95**
LEAK 2000 Tuner/Amp £178.16 **£149.50**

Also Shure Cartridges, Bass Tape, Koss H/Phones, etc.
 Prices of above correct at Mar 14 1975

AKAI TAPE UNITS

	Rec. Price	RSC Price		Rec. Price	RSC Price
CS 30D	£91.23	£64.95	GXC 510D	£199.39	£135.95
GXC 36D	£116.24	£72.50	GXR 82D	£128.77	£92.95
GXC 38	£154.53	£109.95	4000 DS	£136.59	£97.95
GXC 38D	£144.23	£102.95	4000 DB (Dolby)	£196.27	£139.95
GXC 46D	£165.47	£115.95	1722 L	£146.37	£105.95
GXC 40T	£195.35	£139.95	CR 81D	£98.10	£69.95
GXC 75D	£209.89	£149.95	CS33D	£111.08	£79.95
GOLDRING GL72 T/Table & G800	£29.95			(Approx. value £46)	Carr. 75p
GOLDRING GL75 T/Table & G800	£34.95			(Approx. value £65)	Carr. 85p
PIONEER PL12D T/Table on plinth & cover	£41.75			List	£61.90
T/TABLES with MAGNETIC CARTRIDGE/PLINTH & COVER					
GARRARD SP25 MK IV with G850	Special Price £23.95			(Carr. £1)	
RANK BD2000	Rec. Price £67.25	RSC Price £48.95		(Carr. £1)	

FANE HIGH FIDELITY SPEAKERS

Limited number at approx. 1/3 off list prices.

Model	Special Price	Model	Special Price
5" 501	8 ohms £5.20	12" 122/14*	8 & 15Ω £11.50
8" 804*	8 ohms £3.65	12" 122/14LR	8Ω £12.95
10" 1005LR	15Ω £5.75	12" 122/17*	8 & 15Ω £12.95

Available by Mail Order carr. free or may be ordered through Branches
 *Basic models made to individual specification of equipment manufacturers

HI-FI 7 Watt LOUDSPEAKERS fitted Parasitic Tweeter Imp 8Ω
 8" x 5" **£1.25 ea.** 6 1/2" **£1.45 ea.** 8" **£1.85** Carr. 20p

GENERAL PURPOSE 3-4 Watt SPEAKERS Imp 8Ω
 4" 88p. 5" or 6" x 4" 95p. 8" x 5" 99p Carr. 20p

HI-FI SPEAKER ENCLOSURES Teak veneer Carr. 50p.
 Sizes approx. per enc.

ME8 13 x 9 1/2 x 6 1/2in. **£3.95**
JEB 16 x 11 x 9in. **£5.95** } Both cut for 8in. speaker
SE10 25 x 16 x 9in. Cut for 10in. and Tweeter **£8.95**
SE12 25 x 16 x 9in. Cut for 12in. and Tweeter **£8.95**

AUDIOTRINE HI-FI SPEAKER SYSTEMS
 Consisting of matched 12in. 11,000 Gauss 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£6.95** Carr. 45p
 OR SENIOR 15 WATT INCLUDING **£8.95** Carr. 50p
HF123 13,000 GAUSS SPEAKER

R.S.C. TA6 6 Watt HI-FI AMPLIFIER
 200-250v. AC mains operated. Response 30-20,000 c.p.s. -2dB. Separate Bass and Treble 'in and out' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 8-15 ohm spkrs. Max. sensitivity 5mV. O/P rating I.H.F.M. Enclosed enamelled case 9 1/2 x 2 1/2 x 5 1/2in. Silver finish fascia 10 1/2 x 3 1/2in. Complete kit, wiring diagrams and instructions. **£7.95** Carr. 40p. **FACTORY BUILT £10.95**

R.S.C. TA12 MKIII 6.5+6.5 WATT STEREO AMPLIFIER
 Fully transistorised, Hi-Fi o/p of 6.5 watts per channel. Optimum performance with any crystal or ceramic P.U. Cartridge, Radio Tuner, Tape Rec. etc. Input Sel. Switch, Bass, Treble, Vol. & Bal. Controls. **COMPLETE KIT OF PARTS WITH FULL £12.95** Carr. 40p.
WIRING DIAGRAMS & INSTRUCTIONS
 Factory built with 12mths guarantee **£16.61** Or in housing **£19.55** Dep. £2.50 & 8 monthly pymts **£22.50** (Total £22.50).

RSC G66 MkII 6.6 WATT high quality STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12dB. Treble Control ± 13dB. Selector switch for Crystal P.U. or Tape/Radio. For speaker output impedances of 3 - 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. **COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT** and **COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS** **£12.95** Carr. 40p
 Or **FACTORY BUILT IN TEAK VENEERED CABINET** as illustrated **£16.95** or dep. £2.12 and 8 monthly payments £2.12 (Total £19.08)

AUDIOTRINE HIGH FIDELITY SPEAKERS
 Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.

Exceptional performance at low cost.

Model	8"	10"	12"	15"	18"	15W	45-50
HF808T	8"	10"	12"	15"	18"	15W	45-50
HF102D	10"	12"	15"	18"	15W	47-95	
HF120	12"	15"	18"	15W	45-85	12"	15W 45-80

AUDIO FIDELITY MODEL 80 HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 8-15 Ω. **£4.50 ea. £7.98** pr.
MODEL 83 8" 15w. with Parasitic Tweeter. £5.99 ea. **£10.95** pr.
 Response 25 Hz to 15 KHz. Gauss 13,000 Imp 8-15Ω.

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET
 Only high grade components by leading manufacturers

- * Push Button Selector Switching
- * Jack Socket for Headphones
- * Neon Indicator
- * Satin Silver Finish Metal Fascia
- * Solid State Circuitry
- * Twenty Silicon Transistors
- * Four Diodes, Four Rectifiers

Send S.A.E. for full descriptive leaflet.

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8Ω. Frequency Response 7 Hz to 70 KHz ± 1 1/2 dB.

Assembled unit in cabinet **£42.50**



COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £4.90 extra.
£22.95

AUDIO FIDELITY FRI SPEAKER KIT

Response 30 Hz-15 KHz. Rating 15 watts in sealed cabinet. Imp. 8-15 ohms. 8" Bass Unit with P.V.C. Cone surround for ultra low resonance. Pressure Tweeter. Printed Circuit. Inductive/Capacitive Cross-over. Damping Material. Screws, Terminal Panels.

£11.78 Carr. Free. **SPECIAL OFFER £15.99** Pair Carr. 60p



R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED. Impregnated and Interleaved where necessary. Primaries 200-250v. 50/0s. Screened

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.	TOP SHOULDED DROP-THRO' TYPE	CHARGER TRANSFORMERS 0.9-16v. 1 1/2a. £1.75, 2 1/2a. £1.95; 3a. £2.00; 5a. £2.45; 6a. £2.75; 8a. £3.00	SELENIUM RECTIFIERS P. W. (Bridged)
250v. 30mA, 8.3v. 2a. £1.50	250-0-250v. 70mA, 6.3v. 2a., 0-5-6.3v. 2a. £2.25	AUTO (Slap UP/Slap DOWN) TRANSFORMERS	All 6/12v. D.C. output. Max. A.C. input 15v.
250-0-250v., 60mA 6.3v. 2a. £1.60	250-0-250v. 100mA, 6.3v. 3a. £2.50	0-110/120v. 200-250-250v. 50-50 watts £2.50	1a. 25p. 2a. 45p. 3a. 65p. 4a. 81p. 6a. 97p.
FULLY SHOULDED UPRIGHT MOUNTING	250-0-250v. 100mA, 6.3v. 2a., 0-5-6.3v. 2a. £2.25	150 watts, £4.50 250 watts £5.50; 500 watts £8.50	L.F. CHOKES
200-0-250v. 60mA, 6.3v. 2a., 0-5-6.3v. 2a. £2.25	250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 2a. £3.75	OUTPUT TRANSFORMERS	150mA, 7-10H, 250 Ω #1-10; 100mA, 10H, 200 Ω #50; 60mA, 10H, 400 Ω #35p.
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £3.75	300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 2a. £3.75	Std. Pentode 5000-3 Ω or 700-3 Ω 95p	
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £3.75	300-0-300v. 130mA, 6.3v. 4a., c.t. 6.3v. 1a. £4.50	Push-Pull 8 watts EL84 to 3 Ω or 15 Ω £1.45	
300-0-300v. 130mA, 6.3v. 4a., c.t. 6.3v. 1a. £4.50	500 suitable for Mullard 610 Amplifier £4.50	Push-Pull 10 watts 6V6, 5-5-8-15 Ω £2.25	
For Mullard 610 Amplifier £4.50	300-0-300v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £3.75	Push-Pull 15 watts 6X4, 3 or 15 Ω 15 watts £2.25	
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 2a. £3.75	350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £4.50	Push-Pull Ultra Linear for Mullard 510, etc. £3.75	
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £4.50	FILAMENT or TRANSISTOR POWER PACK	Push-Pull 15-15 watts, sectionally wound 6L6, KT66, etc., for 3 or 15 Ω £2.20	
425-0-425v. 200mA, 6.3v. 4a., c.t. 5v. 3a. £8.50	Types 6-3v. 1.5a. 95p; 6-3v. 2a. 95p; 6-3v. 3a. 1.45; 6-3v. 4a. 2.25; 12v. 1a. 95p; 12v. 3a. or 24v. 1.5a. 2.25; 0-9-18v. 1 1/2a. £1.95; 0-12-25-42v. 2a. £2.75.	Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω £5.50	
425-0-425v. 200mA, 6.3v. 4a., Twice 5v. 3a. £8.70			
450-0-450v. 250mA, 6.3v. 4a., c.t. 5v. 3a. £9.00			

RSC 100 watt DISCO SYSTEM

50 WATT SPEAKER **50 WATT SPEAKER**

TWIN TURNTABLE WITH PRE-AMP. and POWER AMPLIFIER

AT FANTASTIC LOW PRICES!

Complete with lid **HEADPHONES MICROPHONE**

Units listed below
 (a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier
 (b) PAIR OF HI-FI HEAD- PHONES
 (c) MATCHING DYNAMIC 'MIKE' (attached to h' phone)
 (d) PAIR 50 WATT SPEAKERS
 Black Rexine covered Cabinets Size approx. 18" x 12" x 8"
 (a) (b) (c) & (d) Carr. £3-00

£159-95

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BBE MP60 type turntables and Sonotone or Acos Cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £19-95 and 18 fortnightly payments £8-61

£79-95

DEP. £19-95 & 18 fortnightly. Payments of £9-11 (Total £183-93).

STEREO VERSION
 of Above System
 Or DEPOSIT £29-95 and 18 fortnightly pymts. £11-11 (Total £289-95) Carr. £3-60

£199-95

TD25 STEREO VERSION OF ABOVE
 Terms DEPOSIT £15 and 18 fortnightly payments £8-51 (Total £138-18) Carr. £1-80

£115-00

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £109-95 Carr. £2-00

Garrard SP25 or McDonald MP60 turntables. Sonotone or Acos cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £19-95 and 18 fortnightly payments £8-61 (Total £188-58)

STEREO VERSION £145 or **DEPOSIT £20** and 18 fortnightly pymts £8-15 (Total £160-70). Carr. £3

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 16 Ohms covered in Rexine and Vynair

TYPE C38 40-50 WATTS Incorporating three exceptionally efficient 8" speaker units. Terms: Dep. £2-95 and 8 monthly payments £2-87 (Total £25-91) Carr. 65p. **£21-95**

TYPE C8/70 70 WATTS. Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £5-11 & 8 mthly pymts. £5-11 **£39-95** (Total £45-99) Carr. 85p

FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 15Ω
£31-95	£17-95	£13-95
Dep: £5-80 and 3 mthly payments £2-80 (Total £25-20)	Dep. £3-17 and 8 monthly payments. £2-17 (Total £20-58)	Terms for pairs Dep £2-90 & 8 mthly pymts £2-16 Total £21-18

FOR BASS GUITAR, ELECT. ORGAN, ETC. **PAIR SUITABLE ALL PURPOSES**

ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

SUPER MINSTREL 10 W GUITAR AMP.

Incorporating Tremolo and 18" x 8" or 10" Speaker. Output 10 watts E.M.S. Continuous. 3 Jack inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity. Terms: DEPOSIT £8-78 and 8 monthly payments £3-00 (Total £30-78) Carr. free **£26-73**

FANE CRESCENDO SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES

'POP' 25/T 12" 25W. PH50 HIGH POWER TWEETER

Dual cone. 15 ohm Imp. (Not for Bass Guitar use) **£9-95**

with 2 to 4 mfd. Non elect. filter available 55p. Rating 50 Watt Imp 8Ω **£6-65**

D40 FULL RANGE 40 WATT POWER SPEAKER KIT £21-00

Consisting of 12" 40 watt Bass Unit, HPX1 200w Cross-over and PH50 Tweeter. Rating 40w R.M.S. Imp. 8 ohms. Terms: Deposit £5-99 and 8 mthly payments £2-50. (Total £25-99)

FAL MAESTRO COMBINED 30W AMP. AND 18" SPEAKER £48-60 Carr. Free

For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass, TREMOLO with associated controls. Attractively finished in black with silver-finished fascia. Compact size fitted carrying handle. Deposit £28-60 and 8 mthly payments £5-75 (Total £54-60)

RSC 'PHANTOM 50' Rating 50 watts. 3 inputs, 2 vol. controls. Bass, Treble, Presence £55-00 Carr. £1-50

Terms: Deposit £8-00 & 8 mthly. pymts. £6-75 (Total £38-08).



HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE VYNIDE AND VYNAIR FINISH

L12/2 50 WATT Fitted pair of 12" 30 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50

Or deposit £5-11 and 8 monthly pymts. of £5-11. Total £45-99

L18/25G 12" 25 WATT 15,000 lines 15 ohms Terms for Pairs. Dep. £2-82 & 8 mthly pymts £2-82 **£12-95** Carr. 55p.

L12/10 10-16 Watt Veneered cabinet 12" unit 8-15 ohm. Approx. 14" x 14" x 8" Carr. 65p. Terms for Pairs. Dep. £2-05 & 8 mthly pymts £2-06 (Total £18-45). **£7-95**

FAL PHASE 50 Mk. III AMPLIFIER 50 WATT

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speaker's 8 to 15 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £28-60 & 8 monthly payments £5-75. Total £34-60. Carr. Free **£48-60**



NOW AVAILABLE I.S.E. CA 127 JINGLE MACHINES £79-95

Terms: DEPOSIT £8 and 18 fortnightly payments £4-61 Total £91-98

REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 60w Peak O/P rating. Not for Bass Guitar. ★ Two Fane heavy duty high flux 12in. spks. ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £29-95, & 18 fortnightly payments £74-95 (Total £24-15) (Total £24-65). Carr. £2-50

REGENT 50B for Bass Guitar and general purposes. Or Dep. £10-85 & 18 fortnightly payments £4-78. £84-95 (Total £20-69). Carr. £2-50

GP30 AMPLIFIER

For Guitar, Vocal or Instr. Group. Gram, Radio or Tape. 4 inputs. 2 Vol. Controls. Current Valves. Peak o/p rating. Strong Vynide covered cabinet with carrying handles. Black/Silver Facia. Neon Indicator. For 200-250v A.C. For 3 or 15 Ω speakers. Send S.A.E. for leaflet. Terms: Dep. £5-58 & 8 mthly pymts £2-68 (Total £24-28) Carr. 75p **£29-95**

LIQUID WHEEL from PROJECTORS £24-75

COMPLETE PULSAR £99-95

'SOUND TO LIFE' SYSTEM

AT A WORTHWHILE SAVING ON INDIVIDUAL UNITS purchased separately. Terms: Deposit £11-48 and 18 fortnightly payments £5-74. (Total Credit Price £114-80). Super 8L Unit. 1000 watt per channel. Manual overrid buttons. 2 spotbanks with 8 bulbs (3 sep. colours) 5 yd and 10 yd leads, fitted plugs. Units sold sep.

FAL DISCO PRE-AMPLIFIER

T/Table mixing inputs. Headphone Vol. Control. Std. 200-250v A.C. Mains operation **£18-50**

REGENT '50' AMP.

As supplied with Regent 50x or 50B. Terms: DEP. £5-11 and 8 mthly pymts £5-11 (Total £45-99) Carr. £1 **£39-95**

NEW BRANCHES AT BOLTON, COVENTRY DONCASTER, PRESTON and STOCKPORT

OPEN ALL DAY SATURDAYS (5 Day Week)

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
 BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
 BIRMINGHAM 30/31 Great Western Arcade. Tel. 621-236 1279 (Closed Wed.).
 COVENTRY 17 Shelton Square, The Precinct. Tel. 25083
 DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41381
 DARLINGTON 19 Northgate (Closed Wed.). Tel. 88043

HI-FI CENTRES LTD.

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs). Tel. 63069
 EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
 GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158
 HULL 7 Whitefriargate (Closed Thurs.). Tel. 30505
 LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
 LEEDS 6-7 County (Mecca) Arcade, Briggate. (Closed Wed.). Tel. 28252
 LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
 LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1829

MAIL ORDERS & EXPORT ENQUIRIES TO:-
 AUDIO HOUSE, HENWOOD LANE, LEEDS, 18. Tel: Pudsey (09785) 77881.
 MAIL ORDERS MUST NOT BE SENT TO SHOPS
 TERMS G.W.O. or C.O.D. No G.O.D. under #1.
 POSTAGE 40p PER ORDER OR AS QUOTED.
 TRADE SUPPLIED.
 S.A.E. PLEASE WITH ENQUIRIES.

MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2776
 MIDDLESBROUGH 105 Newport Road (Closed Wed.). Tel. 47095
 NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469
 NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48083
 PRESTON 41 Friargate Walk. St. Georges Shopping Prec. Tel. 51979
 SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20719
 STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777
 SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70578

If you're interested in electronics You'll like the **NEW LITESOLD SUPER IRONS**

We've been supplying the electronics industry with soldering irons for many years and we have now put all our experience into an iron for the electronics enthusiast.

The new LITESOLD SUPER IRONS have all the features you have been looking for; a neon indicator which glows only when the supply is connected correctly and the iron is safely earthed, an unbreakable nylon handle, a burn-proof mains lead, a special oxydised binding, a long life element. A range of bit shapes to suit every job and a special bench stand are also available.


There are three SUPER IRONS the S90 12 watts for miniature jobs at £4.77 the S142 20 watts for medium jobs at £4.85 the S187 24 watts for heavy jobs at £4.89 and the special spring stand at £2.24.

If you want an economy iron, the Litesold Standard is the one for you. Model 90 12 watts at £2.97 Model 142 20 watts at £3.02 Model 187 24 watts at £3.15

Get your LITESOLD SUPER IRON direct from

Light Soldering Developments Limited
97-99 Gloucester Road Croydon Surrey
Telephone 01-689 0574

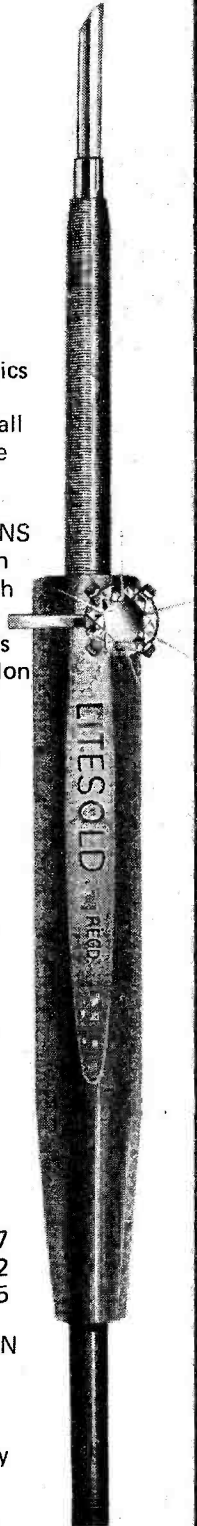All prices include postage, packing and VAT but not the diamond ring.



ELECTROVALUE

The best of all!

CATALOGUE 7 ISSUE 3

with 25p refund voucher

Up-dated Price & Product Information

112 pages plus cover As comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 25p for spending on orders list value £5 or more **SEND NOW FOR YOUR COPY BY RETURN 30p** post paid it's an investment in practical money-saving and reliability!

PRICES as shown in our latest catalogue (No. 7, issue 3) having been maintained until March 31st are now reviewed only at 3-monthly intervals as from April 1st. This is instead of making day-to-day price changes.

DISCOUNTS apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders list value £15 or more.

FREE POST AND PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.

QUALITY GUARANTEE. All goods are sold on the understanding that they conform to maker's specification. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Section 215, 28, ST JUDES RD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603; Telex 264475. Shop hours: 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours: Daily 9-5.30 pm; 9-1 pm Sats.

ALLARD ELECTRONICS

New Branded Components—Full Specification—Guaranteed

Transistors	I.C's	Price ea.	SPECIAL OFFER	
AO125/6/7/8	709C (DIL or TO)	0.27	This month only	
AD140/149	723C (DIL or TO)	0.50	NE555	
AD161/162	741C TO	0.38	Price each 0.49	
AF114/5/8/7	741C DIL	0.26	POTENTIOMETERS—CARBON TRACK	
AF118	748C TO	0.44	Lin. or Log. 3" Bush—Spindle 2" F.M.F.	
BC107/8/9	748C DIL	0.26	5K to 2 Meg Single 0.16 ea.	
BC147/8/9	LM309K	2.00	5K to 2 Meg Single with D/P sw. 0.38 ea.	
BC167/169	TBA300	0.95	10K to 2 Meg Dual with D/P sw. 0.82 ea.	
BC168	ZN414	1.05	Log. only 0.82 ea.	
BC212/3/4	S.C.R.'s		T.T.L's	Price ea.
BCY70/1/2	CRS1/05	0.80	7400/1/2/3	0.14
BD131/132	CRS1/10	0.56	7404/5	0.18
BF194/5/6	CRS1/20	0.60	7406/7	0.38
BFY50/1/2	CRS1/40	0.45	7408	0.15
MJE370	CRS3/40	0.55	7409	0.15
MJE371	ZENERS		7416/7	0.34
2N2218	BZY88 all voltages	0.09	7428	0.37
2N2906	BZX61 series	1.3w	7432/3	0.38
2N2926 all		0.17	7436	0.27
2N3053	ALL-BOXES		7441/2AN	0.75
2N3054	2 1/2 x 6 1/2 x 1 1/2"	0.44	7470/72	0.27
2N3055	4 x 4 x 1 1/2"	0.44	7473/74	0.32
2N3702/3/4	4 x 2 1/2 x 2"	0.44	7475	0.47
2N3706/6	3 x 2 x 1"	0.38	7480	0.44
2N3707/8/9	6 x 4 x 2"	0.60	7482	0.75
2N3819	7 x 5 x 2 1/2"	0.70	7483	0.38
2N3819	VEROBOARD		7484	0.90
TIP29a	1 Matrix	Price ea.	7486	0.37
TIP30a	1 Matrix	0.30	7490	0.47
TIP31a	2 1/2 x 3 1/2"	0.34	7491AN	0.80
TIP32a	2 1/2 x 5"	0.34	74119	1.68
TIP41a	3 1/2 x 3 1/2"	0.32	74141	0.90
TIP42a	3 1/2 x 5"	0.38	I.C. SOCKETS	
	2 1/2" x 1 1/2"	0.95	DIL	
	3 1/2 x 1 1/2"	1.25	8 pin 0.14	
	Pins 25 per pack	0.15	14 pin 0.15	
			16 pin 0.17	
			DIODES	
			1N914/	
			1N4148	
			1N4001/8	
			SPEAKERS	
			7" x 4" PANE	
			3-8-15 ohm	
			0.85 each	

Send for FREE CATALOGUE. Listing over 2,900 items. S.A.E. please. Quantity Discounts

DEPT. W.5, 299/301 BALLARDS LANE, LONDON N12 8NP

MAIL ORDER ONLY. Cash with order. Orders under £3 plus 15p. P. & P. Add VAT to total

Europe's Largest Hi-Fi Retailers



give you:-

- GREAT CHOICE
- BIG VALUE
- BIG NAMES
- 29 STORES to give you BIG SERVICE



TMK 200 MULTIMETER KIT

Build yourself a quality 20000 opv. multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test leads and instructions. Ranges: 0/0.6/6/30/120/600/1200V D.C. 0.6/30/120/60/600mA. Resistance: 0/10/100K/1/10 Meg ohms. Decibels: -20 to +63dB. Size: 90 x 150 x 35mm



OUR PRICE £7.95 P&P 30p.

AUDIOTRONIC Model ATM1

Top value 1,000 opv pocket multimeter. Ranges: 0/10/50/250/1,000 Volt AC and DC. DC current 0.1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.



OUR PRICE £3.25 P&P 15p

AUDIOTRONIC MODEL ATM5

Jewel movement, attractively moulded case with slide ohms adjustment. Ranges: 0.3/15/150/300/1200V AC. (2500 opv). 0.6/30/300/600V DC. (5000 opv). DC 300uA/0.300mA DC. Resistance: x10 & x100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.



OUR PRICE £4.50 P & P 20p

MODEL C720ZEN

20,000 op.v. DC. 10,000 op.v. AC. Mirror Scale. 5/25/50/250/500/1000/2500V. DC. 10/50/100/500/1000V. A.C. DC Resistance x10, x1000 (30C centre scale) DC Current 50uA/2.5mA/250mA. -20 to +68dB.



OUR PRICE £6.95 P & P 30p

ASK LASKYS
about test equipment

U435 MULTIMETER

20,000opv. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1.5/25/100mA/0.5/2.5A DC. 5/25/100mA/0.5/2.5A AC. Resistance: 0.3/3/30/300 ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.



OUR PRICE £8.75 P&P 30p

U4323 MULTIMETER

20,000opv. Simple unit with audio/IF amplifier. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/25/50/100/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: x10, x100, x1,000, x10,000 (50Z, 50KZ, 5K1, 50K1 centre scale) Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.



OUR PRICE £8.00 P&P 30p

MODEL C7208FM

30,000 opv DC. 15,000 opv AC. -6/3/15/60/300/600/1200 V. DC. 6/30/120/600/1200V. A.C. DC Resistance x1, x10, x100, x1000 (50C centre scale) DC Current 30uA/3/30/600mA. -20 to +63dB.



OUR PRICE £8.95 P & P 30p

U4324 MULTIMETER

High sensitivity, overload protected. Ranges: 0.6/1.2/3/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.



OUR PRICE £9.85 P&P 30p

U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 253 x 94 x 35mm. Complete with carrying case, leads and fuses.



OUR PRICE £14.00 P&P 30p

HIKOKI 730X

30,000 opv. Overload protection. 6/30/60/300/600/1200V DC. 12/60/120/600/1200V AC. 30mA/100mA/300mA. 2Meg/200K/2 Meg Ohm. -10 to -63dB.



OUR PRICE £7.50 P&P 30p.

U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 5570pV. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/200uA/1.5/6/15/150/600mA/1/1.5/6A DC. 0.1/1.5/6/15/60/100/600mA. 1.5/6A AC. 0.2/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.



OUR PRICE £10.75 P&P 50p

HIKOKI 750X VOLT-OHM-IMPEDANCE TESTER

43 ranges: 0-0.3/0.6/1.5/3/6/12/30/60/150/300/600/1200V DC. 0-3/6/15/30/60/120/300/600/1200V AC. Current: 0-30/60uA/1.5/3/15/30/150/300 mA/6/12A. Resistance: 0-3/300k/3/30Mohms. Decibels: -10 to +17dB. Output: 50,000 opv DC. 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.



OUR PRICE £11.95 P&P 40p

TMK MODEL TW50K

46 ranges, mirror scale, 50k/V DC. 50k/V AC. DC Volts: 0.125/0.25/1/2.5/5/10/25/50/125/250/500/1000V. AC Volts: 1.5/3/15/25/50/125/250/500/1000V. DC current: 25/50/100/250/500/1000mA/5/10A. Resistance: 10k/100k/1 Meg/10 Meg ohms. -20 to +81.5dB.



OUR PRICE £12.50 P&P 20p

MODEL C7080EN

Giant 6" mirror scale. 20,000 opv. 0/0.25/1/2.5/10/50/250/1000/5000V DC. 0/2.5/10/50/250/100/500/1000V AC. 0/50uA/1/10/100/500mA/10A DC. 0/2k/200k/20 Meg. -20 to +50dB.



OUR PRICE £19.95 P&P 35p

MODEL 500

30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/5/50/500mA. 12A DC. 0/60k/6 meg/60 Meg ohms.



OUR PRICE £13.95 Carr. paid

MODEL AS.1000 VOM

100,000 opv. Mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10uA/6/60/300mA/12 mA DC. 200k/2M/200 Meg Ohm. -20 to +17dB.



OUR PRICE £17.50 P&P 30p.

KAMODEN HM720B FET VOM

Input impedance 10 Megohms. Ranges: 0.25/1/2.5/10/50/100V DC. 0/2.5/10/50/250/1000V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohms



OUR PRICE £22.50 P & P 40p

KAMODEN 360 MULTIMETER

High sensitivity DC 100kohm/V AC 10kohm/V 5" mirror scale. Overload protection. Ranges: 0.5/2.5/10/50/250/1000V DC. 0.5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/10/100k ohms/10/100M ohms. Decibels -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads.



OUR PRICE £17.50 P & P 40p

Model HT10084 MULTIMETER

Overload protection, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 100uV. Polarity change switch. Ranges: 0.5/2.5/10/50/250/1000V AC. DC resistance 0-20/200k/2/20 Meg ohms. DC current: 0/250uA/2.5/25/250 mA/10A. AC current: 0-10A. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.



OUR PRICE £19.50 P&P 40p

370WTR MULTIMETER

Features AC current ranges. 20,000opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100mA/1/10A DC. 0/100mA/1/10A AC. 0/5/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB.



OUR PRICE £19.95 P&P 30p

U4317 MULTIMETER

High sensitivity instrument for field and laboratory work. Knife edge pointer. 36mm. mirror scale. Overload protection. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/5/10/50/100/250/500mA/1/5A AC. Resistance: 0.5/10/100/200 ohms/1/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.



OUR PRICE £17.00 P&P 40p.

KAMODEN 72.200 Multitester

High sensitivity tester. 200,000 opv Overload protected. Mirror scale. Ranges: -0/0.6/3/3/30/120/600/1200V DC. 0/3/12/60/120V AC. 0/12A AC. -20 to +63dB. 0/2k/200k/2 Meg/200 Megohms.



OUR PRICE £22.50 P&P 30p

MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter protection. 0/3/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V DC. 0/30uA/8/80/300mA/12 Amp. 0/10k/1m/10m/100 Meg Ohms. -20 to +17 dB.



OUR PRICE £12.50 P&P 30p.

L84 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.



OUR PRICE £4.50 P&P 20p

KAMODEN TT35 TRANSISTOR TESTER

High quality instrument to test reverse leak current and DC current. Amplification factor of PNP, PNP, diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.



OUR PRICE £17.50 P & P 40p

U4341 Multimeter & Transistor Tester

27 ranges. 16,700 opv. Overload protected. Ranges: 0.3/1.5/6/30/60/150/300/900V DC. 3/6/30/150/300/750V AC. Current: 0.06/0.6/6/60/600mA/3A AC. Resistance: 0.06/0.6/2/6/20/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.



OUR PRICE £11.00 P&P 30p.

5100TR MULTIMETER TRANSISTOR TESTER


100,000opv. Mirror scale. Overload protection. 0/0.1/2/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0.1/2/600uA/12/300mA/6/12A DC. 0/10k/1 Meg/100 Meg. -20 to +50dB. 0.01-0.2 MFD Transistor tester measures Alpha, Beta and ICO. Complete with instructions, batteries and leads.



OUR PRICE £19.95 P&P 25p

SWR METER Model SWR3

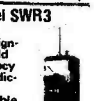Handy SWR meter. Transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52 Ohms. 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.



OUR PRICE £4.25 P&P 30p

C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm: 0.1-25. HOR. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/mm: 0.3-25. Preset triggered sweep 1-3000uSec. Free running 20-200 kHz in 100Hz steps. 220 x 360 x 430mm. 115-230V AC.



OUR PRICE £44.00 Carr. paid

ALL PRICES EXCLUDE VAT

Also see following pages

SEW PANEL METERS

SEW PANEL METERS ARE STOCKED AT OUR
3 LISLE ST., 311 EDGWARE RD., & 152 FLEET
ST., BRANCHES or order by post.

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.
Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

Your nearest
LASKYS

store, call in or
send for our 32
page Price list and
brochure

Complete
the coupon below.

CENTRAL LONDON

481 OXFORD ST. 01-493 8641
3 LISLE ST. WC2 01-437 8204
34 LISLE ST. WC2 01-437 9155
118 EDGWARE RD. W2 01-723 9789
193 EDGWARE RD. W2 01-723 5211
207 EDGWARE RD. W2 01-723 3271
311 EDGWARE RD. W2 01-262 0387
346 EDGWARE RD. W2 01-723 4453
382 EDGWARE RD. W2 01-723 4194
109 FLEET ST. EC4 01-353 5812
152/3 FLEET ST. EC4 01-353 2833
10 TOTENHAM CT. RD. 01-637 2232
27 TOTENHAM CT. RD. 01-636 3715
33 TOTENHAM CT. RD. 01-636 2405
42/45 TOTENHAM CT. RD. 01-636 0845
257/8 TOTENHAM CT. RD. 01-580 0670

ESSEX

86 SOUTH ST. ROMFORD 20218
205/206 CHURCHILL WEST,
VICTORIA CIRCUS, SOUTHWEND 0702 612241

GLOUCESTERSHIRE

16/20, PENN ST. BRISTOL 0272-20421

KENT

53/57 CAMDEN RD., TUNBRIDGE WELLS
0692-23242

LEICESTERSHIRE

45 MARKET PLACE, LEICESTER
0533-537 070

NORTHAMPTONSHIRE

73 ABINGTON STREET,
NORTHAMPTON 0604-35753

NOTTINGHAMSHIRE

5.7 LOWER PARLIAMENT STREET,
NOTTINGHAM

OXFORDSHIRE

16 WESTGATE SHOPPING CENTRE, OXFORD
0865 722870

STAFFORDSHIRE

30 WULFRUM WAY, WOLVERHAMPTON
0902-23384

SURREY

1046 WHITGIFT CENTRE, CROYDON
01-681 3027
38/40 EDEN ST., KINGSTON 01-546 1271
32 HILL ST., RICHMOND 01-948 1441

WARWICKSHIRE

116 CORPORATION ST., BIRMINGHAM
021-236 3503

ALL BRANCHES OPEN FROM
Sun to Sat 10.00 A.M. to 5.00 P.M.

OUR CUSTOMER
SERVICES DIVISION are glad to help
with answer all your enquiries—

just ring 01-200 1321

EXPORT Personal services
arranged for overseas visitors.
Goods specially packed, insured
and dispatched by air, wherever
most exclusive of V.A.T.
Payment by bank transfer,
certified cheque, postal order
or money order in any
CURRENCY

BARCLAYCARD
& ACCESS

Please your order
to 01-200 0037 or
call into any branch

NO DEPOSIT TERMS
available on most goods
for personal callers

CHEQUES TO THE VALUE OF £30.
ACCEPTED FROM PERSONAL SHOPPERS
WITH BANKERS CARD. IN OTHER CASES
AND FOR AMOUNTS IN EXCESS OF £30.
PLEASE ALLOW TIME FOR CLEARANCE.

BANKERS DRAFTS ACCEPTED
All prices correct at 4/3/75 but
subject to change without notice E.&O.E.


A member of the
Audiotronic Group of Companies

CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£3.90
100uA	£3.86
200uA	£3.80
500uA	£3.75
50-0-500uA	£3.89
100-0-1000uA	£3.80
1mA	£3.76
5mA	£3.75
10mA	£3.76
50mA	£3.75
100mA	£3.75
500mA	£3.75
1A DC	£3.76
5A DC	£3.75
10A DC	£3.75
5V DC	£3.75

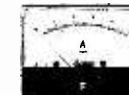10V DC .. £3.75
20V DC .. £3.75
50V DC .. £3.75
300V DC .. £3.75
15V AC .. £3.85
50V AC .. £3.85
VU Meter .. £4.00




CLEAR PLASTIC MODEL SW100

Size: 100 x 60mm

50uA	£4.70
100uA	£4.60
500uA	£4.40
50-0-500uA	£4.60
100-0-1000uA	£4.65
1mA	£4.40
1A DC	£4.40
5A DC	£4.40
20V DC	£4.40
50V DC	£4.40
300V DC	£4.40


150V AC .. £4.55
300V AC .. £4.55
VU Meter .. £5.00



EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.25
100uA	£4.20
200uA	£4.15
500uA	£4.10
50-0-500uA	£4.20
100-0-1000uA	£4.15
1mA	£3.96
300V AC	£4.40
VU Meter	£4.40




MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

50uA	£8.70
100uA	£8.10
500-0-500uA	£8.10
1mA	£7.80
1-0-1mA	£7.80
1A DC	£7.80
5A DC	£7.80
15V DC	£7.80
10V DC	£7.80
5V DC	£7.80

20V DC .. £7.80
500mA/5 DC .. £7.80
300V DC .. £7.80
500mA/5 DC .. £7.80
5V/50V DC .. £7.80
5V/15V DC .. £7.80
1/5A DC .. £7.80




CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm


50uA	£8.40
100uA	£8.35
200uA	£8.30
500uA	£8.40
50-0-500uA	£8.55
100-0-1000uA	£8.50
500-0-5000uA	£8.55
1mA	£8.35
1-0-1mA	£8.35
5mA	£8.35
10mA	£8.35
50mA	£8.35
100mA	£8.35
500mA	£8.35
1A DC	£8.35
5A DC	£8.35
15A DC	£8.35
30A DC	£8.35
50A DC	£8.35
10V DC	£8.35
20V DC	£8.35
50V DC	£8.35
150V DC	£8.35

300V DC .. £5.40
15V AC .. £5.45
300V AC .. £5.45
S Meter 1mA .. £5.35
VU Meter .. £5.70
1A AC .. £5.35
5A AC .. £5.35
10A AC .. £5.35
20A AC .. £5.35
30A AC .. £5.35



240° Wide Angle 1mA METERS


MW1-6 60 x 60 mm
£6.50 P & P 15p
MW1-8 80 x 80 mm
£8.90 P & P 15p



YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-260V.
MODEL S260 BENCH MOUNTING

1A	£10.50	50p
5A	£17.50	£1.00
8A	£30.35	£1.00
10A	£33.75	£1.00
12A	£35.40	£1.00
20A	£55.00	£1.50
25A	£95.00	£1.50
40A	£120.00	£1.50



ALL PRICES EXCLUDE VAT


*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

50uA	£4.40
100uA	£4.36
200uA	£4.30
500uA	£4.25
50-0-500uA	£4.35
100-0-1000uA	£4.30
1mA	£4.20
5mA	£4.20
10mA	£4.20
50mA	£4.20
100mA	£4.20
500mA	£4.20
1A DC	£4.20
5A DC	£4.20
10A DC	£4.20
5V DC	£4.20

10V DC .. £4.20
20V DC .. £4.20
50V DC .. £4.20
300V DC .. £4.20
15V AC .. £4.30
50V AC .. £4.30
VU Meter .. £4.50




CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA	£3.30
100uA	£3.25
200uA	£3.20
500uA	£3.10
50-0-500uA	£3.25
100-0-1000uA	£3.20
500-0-5000uA	£3.05
1mA	£3.05
5mA	£3.05
10mA	£3.05
50mA	£3.05
100mA	£3.05
500mA	£3.05
1A DC	£3.05
5A DC	£3.05
10V DC	£3.05
50V DC	£3.05
300V DC	£3.05
15V AC	£3.15

300V AC .. £3.15
S Meter 1mA .. £3.05
VU Meter .. £3.50
1A AC .. *£3.05
5A AC .. *£3.05
10A AC .. *£3.05
20A AC .. *£3.05
30A AC .. *£3.05




CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£3.00
50-0-500uA	£3.15
100-0-1000uA	£3.10
500-0-5000uA	£2.85
1mA	£2.85
1-0-1mA	£2.85
2mA	£2.85
10mA	£2.85
100mA	£2.85
500mA	£2.85
1A DC	£2.85
5A DC	£2.85
20A DC	£2.85
50A DC	£2.85
100A DC	£2.85
3V DC	£2.85
10V DC	£2.85
15V DC	£2.85

20V DC .. £2.85
50V DC .. £2.85
100V DC .. £2.85
150V DC .. £2.85
300V DC .. £2.85
750V DC .. £2.85
1A DC .. £2.85
2A DC .. £2.85
5A DC .. £2.85
10A DC .. £2.85
30V AC .. £2.85
50V AC .. £2.85
100V AC .. £2.85
300V AC .. £2.85
S Meter 1mA .. £3.10
VU Meter .. £3.30




CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.60
100uA	£3.55
200uA	£3.50
500uA	£3.45
50-0-500uA	£3.55
100-0-1000uA	£3.50
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
10A DC	£3.40
5V DC	£3.40

10V DC .. £3.40
20V DC .. £3.40
50V DC .. £3.40
300V DC .. £3.40
15V AC .. £3.40
50V AC .. £3.40
300V AC .. £3.40
VU Meter .. £3.75




POSTAGE & PACKING 15p

CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£4.05
100uA	£3.95
200uA	£3.90
500uA	£3.85
50-0-500uA	£3.95
100-0-1000uA	£3.90
500-0-5000uA	£3.80
1mA	£3.80
1-0-1mA	£3.80
5mA	£3.80
10mA	£3.80
50mA	£3.80
100mA	£3.80
500mA	£3.80
1A DC	£3.80
5A DC	£3.80
10A DC	£3.80
15A DC	£3.80
20A DC	£3.80
30A DC	£3.80
50A DC	£3.80
100A DC	£3.80
500A DC	£3.80
1000A DC	£3.80
150V DC	£3.80

30V AC .. £3.80
50V AC .. £3.80
100V AC .. £3.80
150V AC .. £3.80
300V AC .. £3.80
500V AC .. £3.80
S Meter 1mA .. £4.20
VU Meter .. £4.20




BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.60
100uA	£4.55
500uA	£4.30
50-0-500uA	£4.55
100-0-1000uA	£4.50
1mA	£4.30
1A DC	£4.30
5A DC	£4.30
20V DC	£4.30
50V DC	£4.30
300V DC	£4.30
300V AC	£4.40
VU Meter	£4.80

S Meter 1mA .. £3.40
VU Meter .. £3.90
1A AC .. *£3.40
5A AC .. *£3.40
10A AC .. *£3.40
20A AC .. *£3.40
30A AC .. *£3.40




CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3.80
100uA	£3.60
200uA	£3.45
500uA	£3.30
50-0-500uA	£3.45
100-0-1000uA	£3.40
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
10V DC	£3.40
20V DC	£3.40
50V DC	£3.40
300V DC	£3.40
15V AC	£3.50
30V AC	£3.50

S Meter 1mA .. £3.40
VU Meter .. £3.90
1A AC .. *£3.40
5A AC .. *£3.40
10A AC .. *£3.40
20A AC .. *£3.40
30A AC .. *£3.40




BAKELITE MODEL MR 65

Size: 80 x 80mm

25uA	£5.40
50uA	£4.10
100uA	£4.05
500uA	£3.75
50-0-500uA	£4.05
100-0-1000uA	£4.00
500-0-5000uA	£3.70
1mA	£3.70
1-0-1mA	£3.70
5mA	£3.70
10mA	£3.70
50mA	£3.70
100mA	£3.70
500mA	£3.70
1A DC	£3.70
5A DC	£3.70
10A DC	£3.70
15A DC	£3.70
20A DC	£3.70
30A DC	£3.70
50A DC	£3.70
100A DC	£3.70
500A DC	£3.70
1000A DC	£3.70
15V DC	£3.70
20V DC	£3.70
50V DC	£3.70
150V DC	£3.70

300V DC .. £3.80
30V AC .. £3.70
50V AC .. £3.70
150V AC .. £3.70
300V AC .. £3.70
500V AC .. £3.70
VU Meter .. £4.20
1A AC .. £3.70
5A AC .. £3.70
10A AC .. £3.70
20A AC .. £3.70
30A AC .. £3.70
50A AC .. £3.70
100A AC .. £3.70
500A AC .. £3.70
1000A AC .. £3.70



TO LASKYS CUSTOMER SERVICES DIVISION
Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me the following items

TOTAL PURCHASE PRICE (inc. P & P and VAT)

Please send me your 32-page price list
I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is

Name

Address

Signature

Registered in England No. 347947 at 12 Lower Grosvenor Place, London SW1 0EX

PE SCORPIO Mk 2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original Scorpio Electronic Ignition System - with a big plus over all the other kits - the Electro Spares Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car or motor cycle.

When your Scorpio Mk. 2 is installed, you instantly benefit from all these Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only **£10.85** inc. VAT and p & p.
Ready Made Unit **£13.65** inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

PE FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only **£28.50** inc. VAT and p & p.

PE GEMINI STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from **£50** to **£60** inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 9p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE(B)
Tel: Sheffield (0742) 668888



ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£	ELAC 6 1/2" 8 ohm Dualcone ...	£ 2.25
EMI 13" x 8" 3 or 8 ohm Plain	2.05	With Co-Axial Tweeter	ELAC 8" 8 ohm Dualcone ..	2.30
8 ohms only ..	2.20	Tweeter & Crossover 3, 8	ELAC 8 ohm Dualcone 10 watt	3.50
or 15 ohm ..	3.95	Type 350	7" x 4" 3 or 8 ohm ..	1.00
8 or 15 ohm, ..	7.95	6 1/2" 8 ohm, 10 watt	ADAstra 10" 8 or 15 ohm,	3.55
8" 8 ohm, 10 watt	2.80	8" 8 ohm, 10 watt	10 watt ..	3.55
12" 8 ohm, 20 watt	6.70	8" x 5" C/Mag. 3, 8 or	BAKER GROUP 25 12" 8 or	7.95
8" x 5" Dualcone	1.40	15 ohm 5 watt	15 ohm, 25 watt ..	7.95
8 ohm, 10 watt	2.55	8" x 5" Dualcone	5" 8 ohm, C/Mag. ..	.85
			2 1/2" 8 ohm or 64 ohm ..	.55
			P. & P. ..	.15
TWEETER & CROSSOVER				
Cone Tweeter 8 or 15 ohm,	2.80	Crossovers CN23 (3 ohm),		
10 watt ..	1.45	CN28 (8 ohm), CN216 (16		
Cone Tweeter 8 ohm, 3 watt	6.40	ohm) ..	P. & P. ..	1.30
Horn Tweeter 8 ohm, 20 watt	5.80			
Dome Tweeter 8 ohm, 30 watt	5.80			
KIT FORM CABINETS TEAK VENEER				
12 x 12 x 6 with 8" x 5" or	3.40	18 x 11 x 9 with 8" x 3" or	4.75	
6 1/2" and 3 1/2" cut out. ..	4.25	13" x 8" cutout for EMI 350	P. & P. ea. ..	.50
17 x 10 x 9 with 8" or 13" x 8"				
cutout ..				
MICROPHONES				
CM70 Planet stick metal,	1.55	TW209 ..	5.75	
switch crystal ..		CONDENSER MIKE 600 ohm,	9.35	
DM160 Dynamic omni-dir.	4.80	uni-dir ..		
ball metal ..	6.40	Cassette Stick Mike with R.	1.50	
UD130 50K/600 ohm, uni-dir.		Control on/off switch		
ball metal ..		(2.5 & 3.5mm J/Ply)	P. & P. ..	.30
SOLDERING IRONS				
ANTEX CN240 15 watt ..	2.00	X25 25 watt (low	2.00	
SK 1 Kit (5 watt Iron	3.40	leakage) ..	P. & P. ..	.15
2 spare bits etc.) ..				
CARTRIDGES & STYLII				
ACOS GP91/2SC or 3SC ster.	1.00	SONOTONE	9TAHC or 9TAHC/G Diam.	1.90
comp. ..		3509 Ster. ceram. Diam. ..	1.90	
GP93/1 or 95/1 ster.	1.35	GOLDRING G650 ..	2.85	
cryst. ...		G800 ..	3.95	
GP94/1 or 96/1 ster.	1.75	G900E ..	6.90	
ceram. ...		P. & P. ..	.15	
GP101 cryst. comp. ..	1.80	D. Diamond Stylil for above ..	1.25	
GP104 ster. ceram. ..	1.80	G900/G850 ..	1.85	
BSS X5M or X5H cryst. comp.	1.80	G800E ..	3.85	
SX6M or SX6H cryst.	1.85	P. & P. ..	.05	
comp. ...				
SC5M ster. ceram. ..	2.70			
CALCULATORS SINCLAIR				
Cambridge ..	12.95	Scientific ..	10.95	
Cambridge with memory	17.95			
BATTERY ELIMINATORS				
240V Input 6, 7.5 or 9 ..	2.85			
BATTERY ELIMINATORS				
240V Input 6, 7.5 or 9 ..	2.85			
TAPES				
Std. LP	DP			
5" 50p	85p	1.00p		
5 1/2" 65p	80p	1.40p		
7" 80p	1.10p	1.80p		
PLASTIC LIBRARY CASES				
For 5" Reels ..	18p			
5 1/2" Reels ..	22p			
7" Reels ..	25p			
P. & P. 1-3, 9p ea. 4 or more, lot 35p				
LOW NOISE CASSETTES				
1-5	6-10	11-20	Cassette Cases	10p
C60	35p	33p	Cassette Head Cleaner	40p
C90	45p	43p	P. & P. 1-5, 5p ea. 6-10, 20p lot.	
CI20	55p	52p	11-20, Post Free.	
BIB ACCESSORIES				
Tape Editing Kit Ref. 23	1.35	WHARFEDALE SPEAKER BARGAINS		
Recording Tape		Linton 2 Kit (pr)	£ 19.95	P&P 1.50
Splicer .. Ref. 20	1.15	Glendale 3 Kit (pr)	33.50	2.00
Cassette Tape, editing Ref. 24	1.50	Dovedale 3 Kit (pr)	52.00	2.00
Cassette Salvage Kit Ref. 29	.45	Denton 2 Speaker (pr)	30.00	2.50
Stylus Balance Ref. 32A	1.20	Linton 2 Speaker (pr)	39.50	2.50
Spirit Lever .. Ref. 46	.50	Dovedale 3 Speaker	42.00	2.50
Hi-Fi Stereo Test Cassette	2.10	(each) ..	57.00	3.50
Groove-Kleen Record Cleaner	1.90	Kingsdale 3 Speaker	59.95	4.00
P. & P. ..	.15p	(each) ..		

Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED.
Subject to manufacturer increase and availability.

Riversdale Electronics

Mail Order Department **PWS**

P.O. Box 470, Manchester M60 4BU.



for fast easy reliable soldering

EASY TO USE DISPENSERS AND REELS

IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7ft 6 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5
32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.72



ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32



Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



For soldering fine joints




Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 19 s.w.g. (1.22mm) Ersin Multicore Solder. Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER

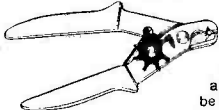

Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter. Model 8B.80p

NEW SOLDER WICK




Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited,

Sole U.K. Sales Concessionaires, P.O. Box 78 Hemel Hempstead, Herts. HP2 7EP

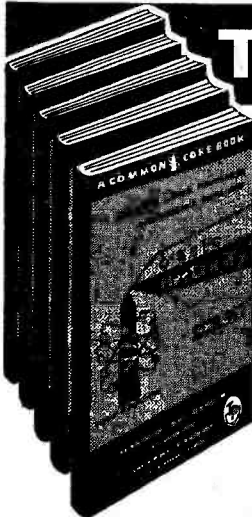Prices shown are recommended retail excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 15p P&P. Prices and specifications subject to change without notice.



The Pictorial Method

BASIC ELECTRICITY (5vols) BASIC ELECTRONICS (6vols) BASIC TELEVISION (3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

These manuals have played an important part in my career. *K.W. West Drayton*

My only regret is that I should have purchased these manuals years ago. *C.B. West Wickham*

I have studied many books but have learned more from Part One than from anything else. *B.A. Reading*

These books create a sound basis on which to build a successful future. *R.G. Gt. Yarmouth*

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £6.50
BASIC ELECTRONICS 6 parts £7.50
BASIC TELEVISION 3 parts £4.25

Tick Set(s) required. Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS
FULL POSTAL.....
ADDRESS

POST NOW FOR THIS OFFER!

MAPLIN

ELECTRONIC SUPPLIES

Get your 1975 CATALOGUE!

132 Big Pages

Includes dozens of useful & interesting circuits you can build; data; hundreds of pictures, transistor equivalents list and hundreds of new lines. Packed with information. Only 40p.

NEW SHOP NOW OPEN, details below

SUPERSONIC SAME-DAY-SERVICE - MEANS QUALITY COMPONENTS - FAST!

● RESISTORS

CARBON FILM
 1/4W 1Ω to 1M: 5%, 1M2 to 10M: 10% E12
 1/4W 10Ω to 10k: 5%, 1M2 to 10M: 10%
 E12 11Ω to 010k: 5% E12 & E24 1p each

METAL OXIDE
 1/4W 10Ω to 1M: 2% E12 & E24 4p each

WIREWOUND
 5W 0-22Ω, 0-27Ω, 0-33Ω, 0-47Ω:
 10% 1Q5% 17p each
 1-2Ω to 270Ω: 5% E12 18p each
 Other ranges stocked. See our catalogue for details.
 E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades.
 E24: 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades.

● POTENTIOMETERS

Rotary miniature carbon track 1/4" spindle.
 Values available: 5k, 10k, 20k, 50k, 100k, 250k, 500k, 1M, 2M.
 Log. Single-gang 17p
 Lin. Single-gang (+ 1K) 17p
 Log. or Lin. Single-gang with switch 38p
 Log. or Lin. Dual-gang without switch 54p
 Slider 60mm track. Metal-cased: overall length 86-15mm (knob extra 7p)
 Values available: 1k; 5k; 10k; 25k; 50k; 100k; 250k; 500k; 1M; 2M.
 Lin. Single Gang 38p
 Log Single Gang 38p
 Lin or Log Dual Gang 45p
 Presets: 0-1W Vertical or Horizontal.
 100Ω, 220Ω, 470Ω, 1k, 2k2, 4k7, 10k, 22k, 47k, 100k; 220k, 470k, 1M 7p each

● CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd	V	Price	Mfd	V	Price
1-5	63	6p	68	6.3	6p
1-5	63	6p	68	16	6p
2-2	63	6p	68	63	14p
3-3	63	6p	100	4	6p
4-7	63	6p	100	10	6p
6-8	40	6p	100	25	6p
6-8	63	6p	100	40	6p
10	25	6p	100	63	18p
10	63	6p	150	6.3	6p
15	16	6p	150	16	16p
15	40	6p	150	25	25p
15	63	6p	150	40	28p
22	10	6p	150	63	19p
22	25	6p	220	10	16p
22	63	6p	220	10	6p
33	6.3	6p	220	16	6p
33	16	6p	220	25	15p
33	40	6p	33	40	6p
47	4	6p	220	63	25p
47	10	6p	230	4	6p
47	25	6p	330	10	6p
47	0	6p	330	16	14p
47	63	6p	330	63	28p
			4700	4	28p

● MAINS CONNECTORS

P360 3-pin 1.5A Chassis Plug with Line Socket 33p
 SA2190 3-pin 5A Chassis Plug 25p
 SA1862 Line Socket for SA2190 28p
 P437 3-pin 5A Chassis Socket with Line Plug 68p

● TRANSISTORS & DIODES

AC197	18p	BY126	13p
AC138	18p	BY127	13p
AC176	17p	BY164	48p
AD161/162 MP	BZY88 series 93p		
BA100	8p	MPP102	38p
BA145	22p	OA81	6p
BC107	10p	OA200	10p
BC108	10p	OC71	20p
BC109	13p	SC146D	88p
BC109C	15p	T1S43	28p
BC142	23p	WO05	30p
BC143	26p	WO4	38p
BC147	15p	IN314	4p
BC148	10p	IN4001	6p
BC149	12p	IN4002	6p
BC168C	12p	IN4003	7p
BC169C	12p	IN4004	7p
BC178	17p	IN4005	8p
BC182L	10p	IN4006	8p
BC183L	12p	IN4007	8p
BC184L	12p	IN4148	4p
BC212L	14p	2N1302	20p
BC213L	15p	2N1303	20p
BC214L	18p	2N1304	30p
BCY71	22p	2N1711	24p
BD181	45p	2N2219	25p
BD182	54p	2N2646	45p
BD181/BD132	2N2905	38p	
MP	2N29260	without switch 54p	
BD135	38p	Ye	12p
BD139	46p	Gin	12p
BD140	59p	2N3053	18p
BF268	35p	2N3055	48p
BF269	25p	2N3819	22p
BFX20	30p	2N5459	51p
BFX30	38p	7400	16p
BFX34	30p	7413	39p
BFX85	39p	7447	11.10
BFX87	30p	7473	54p
BFX88	25p	7474	45p
BFY50	20p	7490	93p
BFY51	22p	7493	98p
BFY52	20p	74121	38p
L.E.D. RED			
2mcd 1/2" only			15p
Panel mtg. clip			6p
(Other colours and 7-seg. displays) in our catalogue.			

● INTEGRATED CIRCUITS

CA3046 (14-pin DIL)	69p
LH0042CH (TO99)	24.25
MC1310P (14-pin DIL)	25.50
MC1496 (UA796) (14-pin DIL)	78p
MFC4000B	58p
MFC400	65p
NE555V (8-pin DIL)	65p
SC1495 (14-pin DIL)	22.70
SG3402 (14-pin DIL)	11.69
TBA8108	11.00
UA741C (8-pin DIL)	38p
UA741C (14-pin DIL)	45p
UA747C (14-pin DIL)	11.05
UA748C (8-pin DIL)	38p
ZN414 (TO18)	11.20

VOLTAGE REGULATORS
 UA7805 5V 1.5A (TO3) £1.75
 UA7815 15V 1.5A (TO3) £1.75
 MVR 5V, 12V, 15V, 500mA (TO3) £1.60
 UA78M05 5V 500mA (Plastic power) £1.05
 UA78M15 15V 500mA (Plastic power) £1.05
 UA78L05 5V 100mA (TO92) 80p
 UA78L15 15V 100mA (TO92) 80p
 UA78ZC Variable 2 to 37V (TO99 or 14-pin DIL) 75p
 Our catalogue contains application circuits and data for all the above I.C.'s and many more

● DISCOUNTS

Details in our catalogue. Start collecting MESS Discount Vouchers NOW!

● SWITCHES

Rotary adjustable stop, 1 pole, 2 to 12 way; 2 pole, 2 to 6 way; 3 pole, 2 to 4 way; 4 pole, 2 or 3 way 38p each
 Slide Sub-min DPDT 9p
 Slide Min. DPDT 13p
 Push to make Non-locking SPST 14p
 Push-on, Push-off Locking DPST 250V 4A 38p
 Rocker White DPST 250V 10A 40p
 Rotary Mains DPST 250V 2A 20p
 Toggle with ON/OFF plate DPDT 250V 1.5A 25p

BCD OUTPUT SLIDE SWITCH
 Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue. £1.38

● PLUGS & SOCKETS

DIN	PLUG	CHASSIS SOCKET
2-pin	8p	6p
3-pin	9p	7p
4-pin	10p	7p
5-pin A (180°)	10p	7p
5-pin B (240°)	10p	7p
6-pin	10p	8p

JACK PLUGS
 1in. Std. Mono Plastic Barrel 13p
 1in. Std. Mono Metal Barrel 22p
 1in. Std. Stereo Plastic Barrel 18p
 1in. Std. Stereo Metal Barrel 25p
 2.5mm Plastic Barrel 9p
 2.5mm Metal Barrel 15p
 3.5mm Plastic Barrel 9p
 3.5mm Metal Barrel 15p

JACK CHASSIS SOCKETS
 2.5mm Open-type metal 9p
 1/2" Std. Mono Open-type metal 9p
 1/2" Std. Mono Moulded with 2 break contacts 14p
 1/2" Std. Stereo Open-type metal 15p
 1/2" Std. Stereo Moulded with 3 break contacts 21p

● TRANSFORMERS

LT700 min. output. Pri. 1k2; Sec. 5Ω 200mW 50p
 Sub-min mains 6.0-6V 100mA 95p;
 12.0-12V 50mA 85p
 (Size both approx. 30 x 27 x 25mm)
 Min. mains
 0-6V 500mA, 0-6V 500mA 21.55
 0-12V 250mA, 0-12V 250mA 11.55
 0-20V 150mA, 0-20V 150mA 11.55
 0-24V 125mA, 0-24V 125mA 11.55
 Mains MT3AT: Sec: 12-15-20-24-30V 2A £3.98
 Mains MT206AT: Sec: 0-15-20V 1A, 0-15-20V 1A £3.98

● ORGAN CONSTRUCTION

A Full Scale Electronic Organ that you can Build to Your Own Specification.

FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS

Leaflet MESS 51: Price 15p, describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument.
 Leaflet MESS 52: Price 5p continues the description of the MESS 50 series organs and shows you how to add a second keyboard with lots more stops.




● THE AMAZING DMO2

A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4k to 8k (highest) or 2k to 4k or 1k to 2k, etc. right down to 16Hz to 32Hz! And this new compatible design is even smaller!—only 3.5in x 3.7in including gold-plated edge connexion.
 DMO2T includes built in variable depth and rate frequency shift tremulant.
 DMO2 £12.95 DMO2T £14.25
 SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1.80 each or 6 for £9.94 or 12 for £18.16.
 Keyboards high quality, fully sprung.
 Flat-front 48-note F to E £15.95
 Sloping-front 49-note C to C £15.95
 Sloping-front 61-note C to C £20.44
 Spring pedal with 10k log. pot £6.33
 *Well Line Unit (Short) £3.05
 *Spring Line Unit (Long) £3.29
 *Reverberation Driver Module £5.34
 * S.A.E. please for full details: leaflet MESS 24. Gold-clad phosphor-bronze wire 30p per yd. Palladium earth bar 15p per octave length. Contact Blocks 2-make (GB2) 22p
 Stop Tabs rocker type not engraved (white, red, grey or black) with DPDT switch 58p

SPECIAL OFFER
 15 BC108C £1.00
 All brand new marked I.T.T. Guaranteed full spec. highest gain group.

"ELECTRONICS TODAY INTERNATIONAL" 4600 SYNTHESISER

We stock all parts for this brilliantly designed synthesiser. This includes all the P.C.B.s, metalwork and drilled and printed front panel giving a truly professional finish. Authoritative opinions agree the E.T.I. International Synthesiser is technically superior to most of today's models. Complete constructional details in our booklet, available shortly. S.A.E. please for price list and specification.
 We also stock all parts for the P.E. Synthesiser and Minisonic.

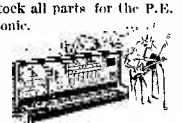

P.O. BOX 3, RAYLEIGH, ESSEX. Tel.: Southend-on-Sea (0702)44101
 SHOP NOW OPEN: 284 LONDON ROAD, WESTCLIFF-ON-SEA, ESSEX
 VAT Please add 8% to the final total. Post and packing FREE in U.K.
 (15p handling charge on orders under £1).
 First-class post pre-paid envelope supplied free with every order.

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed

Pak No.	Eqvt
T1 8 2G3713 OC71	
T2 8 1D1374 OC75	
T3 8 1D1216 OC81D	
T4 8 2G381T OC81	
T5 8 2G382T OC82	
T6 8 2G344B OC44	
T7 8 2G345B OC45	
T8 8 2G3378 OC78	
T9 8 2G3399A 2N1302	
T10 8 2G417 AP117	

All 54p each pak

ND 150 NIXIE DRIVER TRANSISTOR.
Suitable replacement for BSX 21, C 407, 2N 1893 12veb.

1	25	100+
0.19	0.17	0.16

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 5p each. Any Qty.

GP 100 T03 METAL CASE GERMANIUM TRANSISTOR.
V_{beo}=30V, V_{ceo}=50V. I.C.=10 amps. P_{tot}=30W. I_{fe}=30-170. Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0.47	0.44	0.40

GP 800 T03 METAL CASE SILICON TRANSISTOR.
V_{beo}=100V, V_{ceo}=60V. I.C.=15 amps. P_{tot}=115W. I_{fe}=20, 100T_{fe}=1MHz. Suitable replacement for 2N 3055, BDY 11 or BDY 20.

1	25	100+
0.55	0.53	0.51

NEW 9th EDITION Over 300 Pages TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. £2.30 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N708/8, BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20	For	0.54
50	For	1.08
100	For	1.92
500	For	8.25
1000	For	14.30

SIL. G.F. DIODES 2p
300mw 30 0.55
40FV(Min.) 100 1.65
Sub-Min. 500 5.50
Fully Tested 1,000 9.90
Ideal for Organ Builders.

ADI161/162
M/P COMP. PNP GERM. TRANS. OUR LOW-EST PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS ADVERTISEMENTS PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-33V. 400mV (DO-7 Case) 9p ea. 1½W (Top-Hat) 18p ea. 10W (80-10 Stud) 82p ea.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q1	20 Red spot transistors PNP	0.54
Q2	16 White spot R.F. transistors PNP	0.54
Q3	4 OC 77 type transistors	0.54
Q4	6 Matched transistors OC44/46/81/81D	0.54
Q5	4 OC 75 transistors	0.54
Q6	5 OC 72 transistors	0.54
Q7	4 AC 128 transistors PNP high gain	0.54
Q8	4 AC 129 transistors PNP	0.54
Q9	7 OC 81 type transistors	0.54
Q10	7 AC 71 type transistors	0.54
Q11	2 AC 127/128 Complementary pairs PNP/PNP	0.54
Q12	3 AF 116 type transistors	0.54
Q13	3 AF 117 type transistors	0.54
Q14	3 OC 171 H.F. type transistors	0.54
Q15	2 NCT 127/128 Complementary pairs mixed colours	0.54
Q16	5 NPN 2xST.141 & 3xST.140	0.54
Q17	4 MADT'S 2xMAT 100 & 2xMAT 120	0.54
Q18	3 MADT'S 2xMAT 101 & 1xMAT 121	0.54
Q19	4 OC 44 Germanium transistors A.F.	0.54
Q20	4 AC 127 NPN Germanium transistors	0.54
Q21	20 NKT transistors A.F. R.F. coded	0.54
Q22	10 OA 202 Silicon diodes sub-min	0.54
Q23	8 OA 81 diodes	0.54
Q24	15 IN914 Silicon diodes 75 PIV 75mA	0.54
Q25	8 OA95 Germanium diodes sub-min IN 89	0.54
Q26	2 10A PIV Silicon rectifiers 154251L	0.54
Q27	2 Silicon power rectifiers BYZ 13	0.54
Q28	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0.54
Q29	3 Silicon switch transistors 2N706 NPN	0.54
Q30	8 Silicon switch transistors 2N708 NPN	0.54
Q31	3 PNP Silicon transistors 2x2N1131, 1x2N1132	0.54
Q32	3 Silicon NPN transistors 2N1711	0.54
Q33	7 Silicon NPN transistors 2N2369, 500MHz (code P397)	0.54
Q34	3 Silicon PNP TO-5. 2 x 2N2904 & 1x2N2905	0.54
Q35	7x2N3646 TO-18 plastic 300 MHz NPN	0.54
Q36	7x2N3053 NPN Silicon transistors	0.54
Q37	3 NPN transistors 3x2N3703, 2x2N3702	0.54

555 I.C. 65p each

All prices include V.A.T.
MAMMOTH I.C. PACK
APPROXIMATELY 200 PIECES ASSORTED MANUFACTURERS FALL-OUT INTEGRATED CIRCUITS INCLUDING LOGIC 74 SERIES LINEAR and AUDIO AMPLIFIERS MANY CODED also SOME UNKNOWN TYPES - YOU TO IDENTIFY
PAK NO. M.I.C. 200
PRICE £1.25 per PAK including p & p & V.A.T.

1975 CATALOGUE NOW READY 10p

NEW LOW PRICED TESTED S.C.R.'s

PIV 1A	3A	5A	5A	7A	10A	16A	30A
705	T066	T066	T064	T048	T048	T048	T048
50 0-25	0-25	0-39	0-39	0-52	0-55	0-59	1-27
100 0-25	0-37	0-52	0-52	0-55	0-64	0-70	1-54
200 0-39	0-41	0-54	0-54	0-63	0-67	0-83	1-76
400 0-48	0-52	0-62	0-62	0-74	0-88	1-03	1-93
600 0-59	0-68	0-75	0-75	0-85	1-07	1-38	-
800 0-70	0-77	0-88	0-88	0-99	1-32	1-65	4-40

2N3055
115 WATT SIL POWER NPN 45p EACH

Pak No.	Contents	Price
UIC00	= 5 x 7446	0.54
UIC01	= 5 x 7448	0.54
UIC02	= 5 x 7449	0.54
UIC03	= 5 x 7491	0.54
UIC04	= 5 x 7492	0.54
UIC05	= 5 x 7493	0.54
UIC06	= 5 x 7494	0.54
UIC07	= 5 x 7495	0.54
UIC08	= 5 x 7496	0.54
UIC09	= 5 x 7496	0.54
UIC10	= 5 x 74100	0.54
UIC11	= 5 x 74123	0.54
UIC12	= 5 x 74141	0.54
UIC13	= 5 x 74151	0.54
UIC14	= 5 x 74154	0.54
UIC15	= 5 x 74193	0.54
UIC16	= 5 x 74199	0.54
UIC17	= 5 x 7482	0.54
UIC18	= 5 x 7485	0.54
UIC19	= 5 x 7486	0.54
UIC20	= 5 x 7486	0.54
UIC21	= 5 x 7486	0.54
UIC100	= 5 x 7486	0.54

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.54
U 2	60 Mixed Germanium Transistors AF/RF	0.54
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.54
U 4	40 Germanium Transistors like OC81, AC128	0.54
U 5	60 200mA Sub-Min. Silicon Diodes	0.54
U 6	30 Sil. Planar Trans. NPN like BS795A, 2N708	0.54
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000V	0.54
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.54
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.54
U10	20 BAY56 charge storage Diodes DO-7 Glass	0.54
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.54
U12	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0.54
U13	150 Mixed Silicon and Germanium Diodes	0.54
U14	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0.54
U15	10 3 Amp Silicon Rectifiers Stud Type up to 1000V	0.54
U16	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.54
U17	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.54
U18	25 Silicon NPN Transistors like BC108	0.54
U19	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.54
U20	30 AF Germanium Alloy Transistors G3300 Series & OC71	0.54
U21	30 MADT's like MHz Series PNP Transistors	0.54
U22	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.54
U23	25 300 MHz NPN Silicon Transistors 2N708, BSY27	0.54
U24	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.54
U25	10 1 Amp SCR's TO-5 can. up to 600 PIV CR81/25-600	1.08
U26	25 Zener Diodes 400mV DO-7 case 3-18 volts mixed	0.54
U27	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.54
U28	30 Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	0.54
U29	25 Silicon Planar Transistors PNP TO-18 2N2906	0.54
U30	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0.54
U31	30 Silicon Alloy Transistors 80-2 PNP OC200, 2S322	0.54
U32	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.54
U33	30 R.F. Germ. PNP Transistors 2N1303/5 TO-5	0.54
U34	10 Dual Transistors 6 lead TO-5 2N2060	0.54
U35	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0.54
U36	20 Sil. Trans. Plastic TO-5 BC115/116	0.54
U37	7 3A SCR, TO66 up to 600PIV	1.08
U38	20 Unijunction transistors similar to T1648	0.54
U39	10 TO220AB plastic triacs 50V 6A	£1.08
U40	9 NPN Sil. power transistors like 2N3055	£1.08
U41	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	£1.08

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

FREE	SIL. RECTS. TESTED
One 55p Pak of your own choice free with orders valued £4 or over	PIV 300mA 750mA 1A 1.5A 5A 10A 30A 50 0.05 0.06 1N4001 0.05 0.08 0.15 0.21 0.80 100 0.05 0.07 1N4002 0.06 0.10 0.17 0.23 0.75 200 0.06 0.10 1N4003 0.07 0.12 0.22 0.25 1.00 400 0.08 0.15 1N4004 0.08 0.15 0.30 0.38 1.35 600 0.09 0.17 1N4005 0.10 0.18 0.36 0.45 1.95 800 0.12 0.19 1N4006 0.11 0.20 0.38 0.55 2.10 1000 0.14 0.30 1N4007 0.12 0.25 0.48 0.65 2.50 1200 - 10.35 0.30 0.58 0.75 3.00
CADIUM CELLS	DIACS
ORP12 48p	FOR USE WITH TRIACS. BR100 (DS2) 25p each 10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each
NEW LOW PRICED TESTED S.C.R.'s	TRIACS
PIV 1A 3A 5A 5A 7A 10A 16A 30A 705 T066 T066 T064 T048 T048 T048 T048 50 0-25 0-25 0-39 0-39 0-52 0-55 0-59 1-27 100 0-25 0-37 0-52 0-52 0-55 0-64 0-70 1-54 200 0-39 0-41 0-54 0-54 0-63 0-67 0-83 1-76 400 0-48 0-52 0-62 0-62 0-74 0-88 1-03 1-93 600 0-59 0-68 0-75 0-75 0-85 1-07 1-38 - 800 0-70 0-77 0-88 0-88 0-99 1-32 1-65 4-40	VBOM 2A 6A 10A TO-5 TO-66 TO-4M D D D 5p 100 33 55 88 200 55 66 99 400 77 83 1.21

Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS
Postage and packing add 20p Overseas add extra for airmail.
Minimum order 55p. Cash with order please.
Guaranteed Satisfaction or Money Back

2 Amp. BRIDGE RECTS.
50 v RMS 35p each
100 v RMS 40p "
200 v RMS 45p "
400 v RMS 50p "
1,000 v RMS 55p "
Size 16 mm x 16 mm.

D1699 NPN SILICON DUAL TRANSISTOR (Similar to 2N2060)
1 25 100+
0.28 0.26 0.23

LINEAR INTEGRATED CIRCUIT PAKS MANUFACTURERS FALL-OUTS

ULIC709	10 x 709	0.54
ULIC710	7 x 710	0.54
ULIC741	7 x 741	0.54
ULIC747	7 x 747	0.54
ULIC748	7 x 748	0.54



TRAMPUS

Electronics Ltd.
WINDSOR, BERKS
58/60 GROVE RD.
SEND C.M.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 60p.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME.
CATALOGUE/LIST FREE SEND SAE.
BARCLAYCARD & ACCESS X POST.

Digital Displays



SLA7 RED LED 0.3"
DIGIT 0-9DP 89p ea
GREEN&YELLOW £1.40
JUMBO LED 0.6" 747
DISPLAY £2.25 ea.
3015F 0-9DP £1 ea.
ZENON FLASH TUBE
£4. Data 15p.

LEDS red 13P

LEDS 209 STYLE ONLY 13p ea
TTL 209 WITH CLIP RED 15p ea
TTL 211 & CLIP GREEN 29p ea
LARGE 0.2" CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR 2" ORANGE 29p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81P

TEC12 PHOTO AMP/SCMITT/RELAY
DRIVER or LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12V MADE IN UK
8 WATT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MM5311/4 6 DIGIT CLOCK £7

CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder
with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 DIL14 29p LM377 2x2W£2.87
555 TIMER 54p LM380 2W AF 89p
703 RP/IF 28p LM381 2xPre £2
709 T099 23p LM3900 4XOPA69p
709 DIL 14 28p MC1303 £1.20
710 DIL 14 34p MC1306
3015F 0-9DP £1 ea. MC13108LED£2.65
741 DIL 8 27p MC1312 SQ £2.10
741 DIL 14 29p MC1330
741 T099 29p MC1339 2xPre £1
747 2x741 70p MC1350 55p
748 DIL 8 33p NE536 fetOPA £2
7805 5V £1.40 NE540 Driver £2
7812 & 15 £1.40 NE550 2vRef 79p
78013 6W AF £1 NE555 Timer 55p
8038 SIG GEN £3 NE556 2x" £1.20
CA3028 £1 NE560 PLL £3.15
CA3046 55p NE561 PLL £3.15
CA3048 £2 NE562 PLL £3.19
CA3052 £1.50 NE565 PLL £2.69
CA3054 £1 SN72709 709 28p
LM300 2-20V £2 SN72741 741 26p
LM301 OPA 45p SN72748 748 33p
LM304 0-40V £3 SN76660 1P £1
LM307 OPA 48p SN76611 1F£1.25
LM308 H180 95p TAD110 & 1P £2
LM309K 5V £1.45 TB810 7WAF 99p
LM372 1P £1.80 ZN414 RK £1.09

SPECIAL OFFERS

2N3055 FULL HIGH SPEC 115W 37p
741C 8PIN DIL 37p.MFCA000B 33p
NE555 TIMER 55p.ZN414 RK £1.09
BC109 9p.2N3819e 18p.BFY51 15p

79N TTL

7400 GATES 13p 7473/74/76 29p
7404 INVERT 17p 7475 45p
7401/2/10etc14p 7490 52p
7413 SCMITT 31p 7491/2/3/4 39p
7440 BUFFER 14p 74121 11
7447 DRIVER 89p 74121 32p
7470 & 7472 29p 74123 59p
74141(&7441)73p

TRANSISTORS & DIODES

Price each
AC127 & 128 16p MATCHING 16p
AC187 & 188 19p INS, RUSH SET10p
AD149 43p TIP 41 70p
AD181 & 162 33p TIP 42 85p
BC107 & 108 9p TIP 2955 90p
BC109 10p TIP 3055 55p
BC147/8/9 10p TIS43 3002N264£
BC157/8/9 12p ZTX108&301 13p
BC167/8/9 12p IN4001 4p
BC177/8/9 18p IN4004 & 7 7p
BC182/3/4/44L10p IN4148 & 914 4p
BC212/3/4/44L11p 2N697 14p
BCY70/1/2 17p 2N70688 11p
BD131 & 132 39p 2N2646 UJT 32p
BRF1 2N2904 & 5 20p
BRF50/51 23p 2N2926royg 9p
BRF80/51 23p 2N3053 17p
BRF88 250V 29p 2N3055 115W 37p
BFY50/1/2 15p 2N3563 & 64 16p
BSX19/20/21 16p 2N3614 49p
MJE2955 90p 2N3702 & 3 9p
MJE3055 65p 2N3704 & 5 10p
MPS131 PUT 49p 2N3706 & 7 9p
OAG1 OAG1 6p 2N3708 & 9 8p
OAG1 & OAG1 6p 2N3710 & 11 10p
TIP 29 & 30 52p 2N3819E FET 16p
TIP 31 & 32 52p 2N3823E FET 17p
TIP 31 & 32 52p 2N3904/5/6 15p
FULL SELECTION IN OUR FREE LISTS.

NEW TRAMPUS FULL SPEC PAKS

PAK A 10 RED LEDS our choice £1
PAK B 4 741 OP AMP £1
PAK C 4 2N3055 £1.D 12 BC109 £1
PAK E 10 BC182 £1.F 12 2N3704 £1
PAK G 8 BFY51 £1.H 9 2N3819e£1
PAK J 9 2N3053 £1.K 40 1N914 £1

BZY88 400mW 1A/50V SCR 36p
ZENER DIODES 9p TAG1/400 55p
BRIDGE RECT C106 & 7 SCR D1
1A 50V 20p 4A/400V 53p
BR100 DIAC 25p SC146D TRIAC
10A 400V 75p

vero

VERO PINS:36 26p.
COPPER CLAD VERBOARD 0.1"
24"x5" 29p 24x3 1/2" 26p.31x3 1/2"31p.
3 1/2"x5" 31p 3 1/2x 1 7/8" £1.50
DIL IC's BOARDS 6x4 1/2" £1.50
24 way edge connector 60p.
36 way 90p. PLAIN 3 1/2"x1 7/8" £1.
FACE CUTTER 45p.FEC ETCH PAK 50p

DALOPEN 69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK REF 69p
DECON DESOLDER BRAID NEEL 59p

HEATSINKS

5F/T05 & 18F/T018 5p ea.TV4 15p.
TV3/T03 16p.EXTRUDED 4" 4Y1 29p.
TGS308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.
ELECTROLYTIC:10/50/100 uf in
10v 5p.25v 6p.50v 8p.2u/10v 9p.
1000 uf/25v 18p.200/500 25v 9p.

POTENTIOMETERS (POTS) AB or EGIN

LN or LOG ROTARY 13p.SWITCH 14p
DUAL 45p.SLIDERS 29p.STEREO 57p
KNOBS 7p.PRESETS 6PRESISTORS 14p
SWITCHES: SPST 18p. DPDT 25p.

DIN PLUGS ALL 12p. SOCKETS 10p.
ALI CASES AB5/AB7 50p.AB13 65p.
TRANSFORMERS 1A 6v6v or 12v12v
Only £1.34.100mA type CT 75p.

OIL sockets

TEXAS GOLD
LOW PROFILE ea
8,14, & 16 PIN 13p
SOLDERCON STRIPS
100 PINS 50p.IK £3.



Train for television

Course commences September 8th 1975

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:
Name _____
Address _____

THE PEMBRIDGE COLLEGE OF ELECTRONICS
(Dept. PW1) 34a Hereford Rd., London W2 5AJ

8 PIN DIL 741's

Full spec of course
10+ 26p 100+ 21p
25+ 23p 250+ 20p

555 TIMERS

3+ 60p 25+ 46p
10+ 50p 100+ 43p

PC ETCHING KIT

Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO etch resist pen, abrasive cleaner, etching dish and instructions. £3.30.

FERRIC CHLORIDE

Anhydrous to Mil-spec in 1lb double sealed packs. 1lb 90p, 3lbs £1.80; 10lbs £4.65.

COMPUTER PANELS

Large quantity always available. 3lbs assorted £1.60, 7lbs £2.85, 56lbs £15.
12 High quality panels with IC's, Trim pots, Power Transistors, etc. £2.65.

PACK WITH 50 14 PIN DIL DTL IC'S

£1.20. Pack with 20 multi-turn trim pots + other parts £1.10. Pack with 5 1A 200V SCR's + 60 other parts 60p.

PRICE INCREASES

Price increases, which we regret, are due to higher postal, packaging and advertising costs. Prices include 8% VAT and inland postage. SAE list. Computers, components and equipment always wanted for cash.

GREENWELD ELECTRONICS (PW5)

Mail order dept., retail/wholesale shop
51 SHIRLEY PARK ROAD, SOUTHAMPTON SO1 4FX. Tel. (0703) 772501
Also callers welcome at 21 Deptford Broadway SE8. Tel. 01-692 2009 and 38 Lower Addiscombe Road, Croydon. Tel. 01-688 2950.

no extras
all prices inc VAT
FREE delivery



ALL ITEMS SUBJECT TO
MANUFACTURERS INCREASE
AND AVAILABILITY
**Personal
Callers are
Welcome!**

**High Quality
Construction
Kits, stocked
at all branches
Send for
catalogue!**

AMPLIFIERS

Rotel RA211 £43.95
RA311 £54.95
RA611 £86.95
Sansui AU101 £48.25
AU505 £74.95
Sinclair 4000 £50.00
Linton Mk. II £59.95

TUNERS & RECEIVERS

Sinclair 4000 Tuner £43.95
Rotel RT222 £42.75
Pioneer SX434 £99.00
Rotel RX150A Tuner/
Amp. £59.95
Rotel 152 £69.95
Sansui
210 AM/FM/MPX £75.50
310 AM/FM/MPX £99.50
441 AM/FM/MPX £91.95

RECORD DECKS (Ins. 50p.)

Garrard SP25 MkIV £15.25
BSR MP60 £12.95
BSR Invicta P & C/SC7M £9.95
Garrard
SP25 MkIV P & C G/800 £25.00
Goldring GL78 P & C/
G800E £59.95
Rank Domus BD 2000/
Rex 999 Cart. £50.00
Connoisseur
BDI Kit £13.50
BD2 Chassis/SAU2 £32.50
SAU Arm £14.25
SCUI Cartridge £5.95
Pioneer FL12D £43.50

TAPE DECKS (Insurance 2.00)

Akai
4000DS Reel to Reel £93.95
4000DB Reel to Reel
Dolby £149.50
GXC36D £83.00
GXC38D £103.95
CS33D £79.95
Akai CR8ID 8-track Rec.
player £73.95
GXC82D £93.95

SPEAKERS

Chassis Speakers
EMI (Plain) 13in x 8in,
3 or 8 ohm Bass unit £2.30
with Single Tweeter
(only 8 ohm) £2.45
Tweeter and Crossover
3, 8 or 15 ohm £4.25
Type 350 Kit 15 watt 8 ohm £8.25
13in x 8in Bass unit 15 watt
8 ohm or 15 ohm £5.45
8in x 5in 5 watt 3, 8 or
15 ohm £1.70
8in x 5in 10 watt
Dualcone 8 ohm £2.95
6 1/2" 10 watt 8 ohm £2.65
8in 10 watt 8 ohm £4.50
12in 20 watt 8 ohm £6.95
8in 4 or 15 ohm £2.25
7in x 4in 3 or 8 ohm £1.30
Elac 6 1/2" 8 ohm 10 watt £2.65
Elac 8in 8 ohm Dualcone £2.70
Elac 10in 8 ohm Dualcone £3.75
Baker Group 25 12in 8 or
15 ohm £8.25

Adastra 'Top 20' 12in
25 watt 8 or 15 ohm £8.25
Adastra 'Hi-Ten' 10in
10 watt 8 or 15 ohm £3.70
Also 5in 8 ohm speaker £0.95
2 1/2in 8 or 64 ohm
speaker 60p

**WHARFEDALE SPEAKER
BARGAINS**

Denton 1 pr. £26.75
Denton 2 pr. £32.00
Linton 2 pr. £40.75
Glendale 3 pr. £60.95
Kingsdale 3 ea. £64.95
Dovedale 3 ea. £44.95

KITS

Linton 2 pr. £20.95
Glendale 3 pr. £35.95
Dovedale £55.50

**SPEAKER CABINETS IN
KIT FORM** (Teak Veneer)

(Ins. 50p. per pair)
12in x 8in x 6in
(8 x 5 or 7 x 4 cutout) £3.25
14in x 12in x 9in
(10", 8 x 5, 8", 6 1/2" & 3 1/2") £4.25
18in x 11in x 9in
(8" x 3" or 13 x 8) £5.25
22in x 14in x 9in
(12" & 3" or 13 x 8) £6.95

TWEETERS & CROSSOVERS

Cone Tweeter 10 watt
8 or 15 ohm (K2006) £2.95
Cone Tweeter 3 watt
8 ohm (K2003) £1.55
Horn Tweeter 8 ohm
(K2007) £6.50
Dome Tweeter 8 ohm
(K2011) £5.75
2-way Crossovers (CN23,
CN28, CN216) £1.40
3-way Crossover (CN38) £2.85

CARTRIDGES & STYLII

ACOS	Cart. £	D/D Styli £
GP91/25C or 3CS (ster. comp)	1.10	1.25
GP93/I or 95/I ster. cryst.	1.35	1.25
GP94/I or 96/I ster. ceram.	1.75	1.25
GP10I cryst. comp.	90	—
GP104 ster. ceram.	1.95	1.25
BSR X5M or X5H cryst. comp.	1.95	1.25
SX6M or SX6H cryst. ster.	2.10	1.25
SC5M ster./ceram.	2.85	1.25
SONOTONE 9TAHC or 9TAHC/G (Diam.)	1.95	1.25
3509 Magnetic	1.95	1.25
AUDIO TECNICA AT55	1.95	—
EMPIRE 999 REX	3.95	—
GOLDRING G850	2.95	1.95

G800 3.95 1.95
G800H 3.95 1.95
G800E 6.99 3.95
SHURE
M44G 4.95 3.95
M55E 6.25 4.95
M75ED Type 2 11.75 8.25
M15EJ Type 2 9.75 6.25
V15 Type 3 32.25 —

MICROPHONES

UD130 50K/600 ohm
uni-dir. ball metal £6.75
UD147 £9.25
Condenser Mic. 600 ohm
uni-dir. £9.50
Cassette Stick Mic. with
R/Control £1.65
Cass. Stiek Mic. with
R. control (Philips type) £2.00
Mic-Mixers Mono/stereo £5.50

HEADPHONES

Rotel
RH430 £4.75
RH 630 £7.75
RH 700 £11.50
Kokoi
K711 £11.50
KRO711 £10.95
K6 £13.00
K6LC £14.95
K0727B £16.75
K0747 £21.50
HV1 £21.95
PRO4AA £29.25
PRO54 £29.95
K6LCC £26.00
Sansui SS10 £16.75
*Headphone adaptor
(Junction box) £2.75
extension lead 2ft curly £1.50

CASSETTES

	C40	C60	C90	C120
Low Noise	—	35p	45p	55p
Philips	—	55p	75p	110p
Memorex	65p	79p	110p	155p
Ampex (360)	45p	55p	75p	99p
Ampex (20-20+)	59p	65p	99p	135p
Chromium Dioxide	—	99p	140p	—
Cassette Head Cleaner	—	45p	—	—
Ampex Head Cleaner	—	Demag	£1.65	—
BIB Stereo Test Cassette	—	£2.15	—	—
Cassette Racks (hold 6)	—	£0.45	—	—
Cassette Rotating Racks (hold 20)	—	£3.50	—	—
Cassette Carrying Case (hold 18)	—	£1.95	—	—
8-Track Cartridge Blanks C40 C64 C80	—	80p	95p	£1.10
Ampex 8-track H/Cleaner Demagnetiser	—	£1.90	—	—
8-track Carrying Cases (BIB)	—	£1.65	—	—

TAPES

	Stnd	LP	DP	Cases
5"	55p	65p	1.00	20p
5 1/2"	65p	86p	1.35	25p
7"	80p	110p	1.85	30p
High frequency Ampex	—	—	—	—
5"	—	1.40p	1.55p	—
7"	—	1.90p	2.95p	—
AKAI Metal Reel 7"	—	—	£2.10	—

CALCULATORS

Sinclair Cambridge Build £12.95
Sinclair Cambridge with
memory £17.95
Scientific £19.95

SINCLAIR PROJECT 80

Stereo Pre-amp. £12.95
Active Filter Unit £7.25
Z40 15 watt Amp £5.75
Z60 25 watt Amp £7.25
P25 Power Supply for 240 £5.45
P26 Power Supply for 240 £8.45
P28 Power Supply for 260 £8.25
FM Tuner £12.95
Stereo Decoder £8.45
Q16 Speaker £7.75
IC20 Stereo Amp. Kit £7.45
PZ20 Power Kit £5.25

PORTABLE RADIOS

Vega Jade £5.95
Vega Sapphire £8.75
Vega VEF206 £15.50
Selena LM/MW/FM/SSV £20.95
Murphy
B833 MW/VHF £9.95
BA838 LW/MW/VHF
M/Batt £18.50
MA5003 Head Set
Radio LW £7.95
Bush
VTR165 LW/MW/VHF £22.00
VTR127 LW/MW/VHF £15.50
VTR175 LW/MW/VHF £13.95
VTR188 LW/MW/VHF/
2SW M/Batt £31.95
BY5661 LW/MW/VHF £14.95

CLOCK RADIOS

Bush CR128 LW/MW £13.60
Bush CR232 MW/VHF £24.95
Murphy MV5600
MW/VHF £22.95
Vega Signal 2 wave band £9.95

CASSETTE RECORDERS

Bush TP66 M/Batt £25.25
Murphy BA200 M/Batt £22.75
Bush BT8504 (miniature) £25.50
Mains Battery Cass. £15.50

RADIO CASSETTES

(Mains/Batt.)
Murphy BA209 MW/VHF £33.50

**STEREO RECORD PLAYER
& SYSTEM**

Bush A1005 £56.50
Hanimex HRC5060 8-track
AM/FM/MPX+Speaker £116.95

CAR AUDIO

Hitachi Car Radio
WM702R LW/MW £16.50
KM1510 LW/MW/VHF £32.50
Hitachi Car Cassette
CS114 £45.00
Hitachi AM/FM & Cassette
CSW 217 £57.00
Battery Eliminators 240 in
6, 7.5 or 9 volt output £2.95

ALL MERCHANDISE FULLY GUARANTEED

**NEWMART
ELECTRONICS**

Mail Order Dept PW 5
Belmont St, Monton,
Eccles, Manchester.
Tel: 061-789 5268

Manchester
30-32 Shudehill. tel 061-832 7710
Leeds
4 New Market St tel 0532 42708
Liverpool
15 Whitechapel tel 051-236 0738

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. Telephone 6743

OB2	.40	6BA6	.35	6L1	8.00	12K5	1.	35W4	.50	DM70	.80	PCF806	.50	UBF80	.40	Transistors	AF117	.21	BY213	.28	
OC2	.47	6BC6	.80	6L6GT	.58	12K7GT	.50	35Z3	.75	DM71	1.50	PCL82	.38	UBF89	.40	& Diodes	AF121	.33	BY214	.25	
IA8	.45	6BE6	.35	6L7	.55	12Q7GT	.45	35Z4GT	.70	DY87G	.35	PCL83	.45	UB21	2.00	1N4744	.15	AF124	.28	FSY41A	.25
IA8GT	.50	6B16	.80	6L8	.55	12R6GT	.50	35Z6GT	.70	DY87G	.35	PCL84	.40	UC29	.45	2N404	.20	AF125	.19	OA9	.10
1A7GT	.65	6B16	.85	6L9	2.00	12R6GT	.40	42	4.00	EB8CC	2.20	PCL85	.47	UC28A	.75	2N896	.58	AF128	.20	OA10	.47
1B3GT	.80	6BK7A	.60	6L9D	.75	12SHY	.35	43	1.00	EB9F	1.40	PCL86	.55	UC28B	.45	2N1756	.55	AF129	.58	OA47	.11
1B3GT	.80	6BQ7A	.55	6N7GT	.60	10R17	.44	50B5	.85	EB9F	1.30	PCL87	.80	UC28C	.50	2N2147	.94	AF186	.61	OA70	.17
1H4	.28	6BR7	1.50	6Q7G	.80	12BQ7	.85	50C5	.60	EB8CC	.75	PCL88	.40	UC28D	.40	2N2997	.95	BA115	.15	OA73	.17
1N6GT	.85	6BR8	1.50	6Q7GT	.80	12BRT	.75	50D06G	1.25	EB2CC	.60	UC142	.75	UC28E	.45	2N2369	.15	BA116	.20	OA79	.10
1R5	.45	6BR7	1.40	6Q7M	.55	14H7	.55	60B8B	.75	EB8CF	1.00	PEN46	.50	UC28F	.40	2N3055	.38	BA128	.14	OA81	.10
1R4	.38	6BW6	.30	6R7G	.60	14B7	.50	60L6GT	.85	EB9CC	1.25	PEN48	.50	UC28G	.45	2N3121	.97	BA129	.17	OA85	.09
1U4	.60	6BW7	.70	6R7M	.75	19AQ5	.50	60S45	.60	EB148	.58	PEN49	1.00	UC155	.55	2N3703	.21	BA135	.17	OA90	.14
1U8	.75	6BZ6	.49	6BA7	.44	19G6	6.00	65A2	.80	EA9	.37	PEN4D	.70	UC156	.55	2N3709	.22	BC107	.14	OA91	.10
2D21	.45	6C4	.40	6D7GT	.33	20F2	.75	90A6	2.50	EA7E	1.00	FL33	.50	UC157	.45	2A119	.17	BC108	.14	OA95	.10
2GK6	.55	6C5G	.50	6E7G	.44	20L1	1.10	90C1	7.00	EA8C	1.00	FL36	.50	UC158	.40	2A120	.17	BC109	.14	OA200	.10
2X2	.60	6C6	.40	6E8T	.44	20P2	.80	90C6	2.40	EAC9Y	.75	FL38	.50	UC159	.45	AA129	.17	BC113	.28	OA202	.11
3A4	.50	6C9	1.00	6E9T	.55	20P4	1.00	100P2	2.75	EAF42	.75	FL39	.50	UC160	.40	AA123	.20	BC115	.28	OA204	.11
3D4	.40	6C10G	1.25	6E9GT	.44	20P5	1.30	100P2	2.75	EAF42	.75	FL40	.50	UC161	.40	AA123	.20	BC116	.28	OA205	.11
3Q4	.40	6C10A	.75	6E9GT	.45	20A6G	.60	100P2	2.75	EAF42	.75	FL41	.50	UC162	.40	AA123	.20	BC117	.28	OA206	.11
3Q5GT	.85	6C16	.65	6V4G	.17	20L6G	.60	100P2	2.75	EAF42	.75	FL42	.50	UC163	.40	AA123	.20	BC118	.28	OA207	.11
3B4	.40	6C18A	.80	6V6GT	.45	20Y5G	.70	100P2	2.75	EAF42	.75	FL43	.50	UC164	.40	AA123	.20	BC119	.28	OA208	.11
3V4	.70	6CM7	.75	6X4	.40	20Z4C	.40	100P2	2.75	EAF42	.75	FL44	.50	UC165	.40	AA123	.20	BC120	.28	OA209	.11
4C6B	.55	6C25	.75	6X6GT	.45	20Z6	.80	100P2	2.75	EAF42	.75	FL45	.50	UC166	.40	AA123	.20	BC121	.28	OA210	.11
6CQ8	.85	6C2W4	1.00	7B6	.75	20Z6G	.70	100P2	2.75	EAF42	.75	FL46	.50	UC167	.40	AA123	.20	BC122	.28	OA211	.11
6R4GY	.80	6D5E7	.75	7B7	.70	20Z7	1.00	100P2	2.75	EAF42	.75	FL47	.50	UC168	.40	AA123	.20	BC123	.28	OA212	.11
6V4G	.40	6D5A	.75	7B7	.70	20Z8	1.00	100P2	2.75	EAF42	.75	FL48	.50	UC169	.40	AA123	.20	BC124	.28	OA213	.11
5V4G	.50	6R8W6	.75	7H7	.80	30C1R	.75	9006G	.30	EC85	.70	FL49	.50	UC170	.40	AA123	.20	BC125	.28	OA214	.11
5Y3GT	.45	6E25	1.00	7Y4	.75	30C1T	.70	ACFEN	1.00	EC85	.70	FL50	.50	UC171	.40	AA123	.20	BC126	.28	OA215	.11
6Z3	.75	6F1	.75	7Z4	.50	30C18	.70	AC2/PEN/	.70	EC92	.48	FL51	.50	UC172	.40	AA123	.20	BC127	.28	OA216	.11
6Z4G	.45	6F6G	.50	9D7	.65	30F5	.75	DD	1.00	EC33	1.50	FL52	.50	UC173	.40	AA123	.20	BC128	.28	OA217	.11
6Z4GT	.45	6F13	.70	10C2	.65	30F1A	.65	ACFEN	.60	EC35	.90	FL53	.50	UC174	.40	AA123	.20	BC129	.28	OA218	.11
6A9L	.60	6F2A	.60	6F2A	.75	30F12	.67	ACFEN	1.00	EC34	1.00	FL54	.50	UC175	.40	AA123	.20	BC130	.28	OA219	.11
6A9T	1.25	6F15	.85	10F1	.75	30F12L	.50	AL60	1.00	EC31	2.40	FL55	.50	UC176	.40	AA123	.20	BC131	.28	OA220	.11
6A97	.49	6F18	.55	10F9	.65	30F13	.55	ATP4	.60	EC32	.38	FL56	.50	UC177	.40	AA123	.20	BC132	.28	OA221	.11
6A96	.67	6F22	.70	10F18	.55	30F14L	.70	AZ1	.25	EC33	.33	FL57	.50	UC178	.40	AA123	.20	BC133	.28	OA222	.11
6A9E	.60	6F24	.85	10D1L1	.70	30F15	.70	AZ31	.60	EC34	.35	FL58	.50	UC179	.40	AA123	.20	BC134	.28	OA223	.11
6A95	.85	6F25	1.00	10P15	.65	30F17	.65	AZ41	.25	EC35	.40	FL59	.50	UC180	.40	AA123	.20	BC135	.28	OA224	.11
6A9K	.40	6F28	.67	10F14	2.00	30F4M1	.60	BL65	9.00	EC36	.55	FL60	.50	UC181	.40	AA123	.20	BC136	.28	OA225	.11
6A9L	.60	6F3A	.50	12A6	1.00	30F4M1	1.00	CL35	1.60	EC37	.60	FL61	.50	UC182	.40	AA123	.20	BC137	.28	OA226	.11
6A9M	.85	6G6G	.60	12ACG	.70	30F12	.65	GY1C	1.00	EC38	.65	FL62	.50	UC183	.40	AA123	.20	BC138	.28	OA227	.11
6A9N	.70	6G85A	.75	12AD6	.65	30F19'	.60	GY21	.50	EC39	1.80	FL63	.50	UC184	.40	AA123	.20	BC139	.28	OA228	.11
6A9Q	.45	6GK7	.65	12AE6	.65	30P4	.75	DAF9'	.30	EC40	.45	FL64	.50	UC185	.40	AA123	.20	BC140	.28	OA229	.11
6A9R	.60	6G9U	.75	12AT6	.40	30P11	.85	DAF96	.50	EC41	.45	FL65	.50	UC186	.40	AA123	.20	BC141	.28	OA230	.11
6A9T	1.00	6H6GT	.25	12AV6	.45	30P13	.95	DF30	.80	EC42	.45	FL66	.50	UC187	.40	AA123	.20	BC142	.28	OA231	.11
6A9V	.45	6H6T	.45	12AW6	.50	30P14	1.16	DF31	.80	EC43	.45	FL67	.50	UC188	.40	AA123	.20	BC143	.28	OA232	.11
6A9W	.30	6H6	.30	12BA6	.45	30P15	.80	DF36	.50	EC44	.25	FL68	.50	UC189	.40	AA123	.20	BC144	.28	OA233	.11
6A9Y	.45	6J7G	.30	12BE6	.50	35A5	.85	DK40	.70	EC45	.20	FL69	.50	UC190	.40	AA123	.20	BC145	.28	OA234	.11
6A9ZA	.95	6JUS8	.75	12BH7	.50	35C5	.75	DK92	.70	EC46	1.25	FL70	.50	UC191	.40	AA123	.20	BC146	.28	OA235	.11
6AX4	.75	6K7G	.30	12E1	3.00	35B5	.75	DK96	.60	EC47	.70	FL71	.50	UC192	.40	AA123	.20	BC147	.28	OA236	.11
6B9G	.30	6K8G	.45	12F7GT	.60	35L6GT	.75	DL96	.55	EC48	.33	FL72	.50	UC193	.40	AA123	.20	BC148	.28	OA237	.11

MATCHED TRANSISTOR SETS:-
LP15 (AC13, AC16, AC17, AA120) - 58p per pack. 1 - OC81 & 2 - OC81 47p.
1 - OC44 & 2 - OC45, 47p. 1 - OC2D & 2 - OC2E - 58p. Set of 3 - OC83 - 72p.

VALUES ALSO REQUIRED FOR CASH. LOOSE OR BOXED, BUT MUST BE NEW. OFFERS MADE BY RETURN.

All goods are unused and subject to the standard 90 day guarantee. Cash or cheque with order only. Despatch charges - Orders below £10 in value, add 25p for post and packing. Orders over £10 post and packing free of charge. Same day despatch. Any parcel insured against damage in transit for only 3p per parcel extra. Terms of business free on request. Many others in stock too numerous to mention.
Please enclose S.A.E. for reply to any correspondence.

RECHARGEABLE BATTERIES

CAN SAVE YOU A FORTUNE!

Bush & Meissner's two purpose-built battery chargers for economy minded enthusiasts:

The "KESTREL-DOWN" Charger for Alkaline rechargeable batteries, no-load voltage of 1.5-volts per cell, for the following sizes ALKALINE (All prices ex-VAT)

Equivalent to	Type	Capacity	PRICE
U2 size	SA-13D	2Ah	£1.75
U11 size	SA-14C	1Ah	£1.13
U7 size (pencil)	SA-15AA	0.3Ah	£0.56p

NICKEL-CADMIUM (All prices ex-VAT)

The "DAIMON" Charger* for Nickel-Cadmium batteries, no-load voltage of 1.25-volts per cell, for the following sizes

Type	Capacity	PRICE
NCC400	4Ah	£3.54
NCC200	2Ah	£2.48
NCC50	0.5Ah	£1.45

Charger designed to give optimum results with a specific type of cell. Never be without power, day or night.

*Note, under no circumstances must Alkaline batteries be used with the Daimon charger.

S.A.E. brings full details

Bush & Meissner

Importers & Distributors Dept 15260 275 West End Lane, London NW6 1QS 01-794-9611



BETTER GET 'SET'

FAMOUS NO. 19 SET TRANS/RECEIVER

TR50/51 2-8 MHz in 2 bands. 11 valve. 807 PA Power reqs 12VLT 275-VHT REC 500VMT. Rebuilt £12.50, Carr. £1.50.
Complete station 12 VDC PSU. Mic. Cables £23.50, Carr. £3.00.

POWER UNIT RECTIFIER No. 19 (Heavy Duty)

Mains 100/250V AC Tapped input 12 or 24vdc 6/7 amps output. Excellent for driving No. 19 and other battery equipment, also battery charger. Size 19" x 6 x 7. Only £8.50, Carr. £1.50.

TE76/CT52
A superb Miniature Oscilloscope £25, Carr. £2.50. Mains operation.

RE102 42/MAST
12-3' 6" x 2" sections WIRE GUYS STRAINERS in carry holdall £23.50, Carr. £3.50.

AERIAL RODS
3' x 1/2" screwed M & F ends 10 £2.25. Post 75p. 25 £5, Carr. £1.00.

AE101. Telescopic mast antenna £3.75. Carr. £1.25. List 25p refundable with purchase.

XTAL CALIBRATOR
No. 10
10MHz Harmonics 30 MHz £3.50 Post 50p.

No. 62 RC/TM 1.5-10MHz £15 Carr. £2. Add VAT 8% Prices and Carriage

Surplus Electronic Trading
P.O. BOX No. 19, HITCHIN, HERTS. SG4 8TN

250w Light Dimmers £2.60 (13p)

TRANSISTORS (p. & p. 8p.)

All new and full spec. BC107/8/9, BC147/8/9, BC157/8/9 all 9p BF180 25p, BF182/3 40p, BF184 17p, BF187 13p, BF190 55p, 741 8DIL 34p, BF336 35p, 2N3771 £1.10, 2N3544 50p, BD131 40p, 2N3055 45p, NE555 67p.

EX COMPUTER PC PANELS

4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data 25 boards £1 (30p)

ELECTROLYTICS

2,200µ 63v 35p (8p)
2,000µ 50v with clip 35p (8p)
4,700µ 63v 60p (12p)
15,000µ 30v, 68,000µ 16v 65p (22p)
30,000µ 25v 65p (22p)
4,000µ

MAINS TRANSFORMERS

All models 230-250 volt primaries

1V	1 amp (special)	1.75
2-4v	5 amp	.85
6-3v	2 amp	1.00
6-5v	3 amp	1.50
9v	1 amp	.95
9v	3-5 amp	1.95
12v	500mA	1.00
12v	1 amp	1.00
0-5v-0-6-5v	1 amp	1.35
18v	1 amp	1.25
20v	1 amp	1.00
24v	1 amp	1.50
24v	3 amp	3.50
12-0-12v	50mA	1.90
6-0-6v	50mA	1.90
8-0-8v	1/2 amp	1.35
18-0-18v	2 amp	3.50
25v	1 1/2 amp	1.95
50v 2 amp & 6-3v 1 amp		5.50
60v 5 amp & 5v 1 amp		7.50
27v	8 amp	4.50
30v	37 amp	22.00
80v tapped 75v & 70v	4 amp	5.50
230v-60mA & 6-3v	1.5 amps	1.75
275-0-275v at 90mA & 6-4v 3 amps		2.95

Charger Transformers

6v and 12v	2 amps	1.25
6v and 12v	3 amps	2.25
6v and 12v	5 amps	3.50

EHT Transformer 5Kv at 25mA (intermittent) 5.50

NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XNII Price \$9p each, 10 for \$9

OIL PUMP

Driven by Redmond Motor of approx. 1/20th horse power, pump originally intended for oil-fired boilers etc, with normal inlet and outlet pipes and unions. \$2-15 plus 30p post and insurance.

LIGHT DIMMER KIT

For dimming up to 250w without heat sink or 750w with heat sink. This comprises quadrac variable control potentiometer, condenser, resistors, tag strip for mounting and data. Price \$1.50.

RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable for closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and rectifier. 33p each.

AM/FM TUNER

Unit made by the American GEC company, 8 transistor, all-wired ready to work. Complete with tuner condenser, needs only scale and pointer. Tunes AM range 640 to 1620 KHz. FM range 88 to 108 MHz. Switches for on-off and AFC. Output for MXP or direct. Special snip price \$5 plus 30p post. Three or more post free.

7 WATT STEREO AMPLIFIER

Again by the American GEC company. This has exceptionally good tone quality. Is complete with pre-amp and treble base, volume and balance controls. Also has mains smoothing circuit and rectifiers so requires only mains transformer. Output for 15 ohm speakers. Inputs for tuner, pick-up, mike, etc. Special snip price \$5 plus 30p post. Three or more post free.

WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to make. \$2-75.



PORTABLE CABINET OFFER

A nicely made portable cabinet, soft padded black finish intended for portable stereo system. Dimensions as sketch. With motor board out for Garrard SF 25. This was obviously a very costly cabinet originally made for a deluxe record player. Offered at \$1-95 plus \$1 carriage free if bought with the Garrard or BBR record decks.



CAR CASSETTE POWER SUPPLY

To give stabilized output of 6 or 9v, complete kit contains 2 transistors—zener diode—zero board panel resistors and plastic case to house it with constructional data. \$2-50.

PLAY YOUR 8-TRACK CASSETTE FROM MAINS

12v, 700mA unit all assembled and in neat plastic case with mains lead and terminals, full wave rectifier and transformer has overload protection and is double insulated. One of today's best buys at \$2-60 + 35p VAT.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated to equal divisions for switch-setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips, thus 15 circuits may be changed per revolution. Drive motor is mains operated, 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £20 each. Special snip price \$2-50 plus 25p post and insurance. Don't miss this terrific bargain.

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in x 18in \$1-80 13in x 10in \$1-50

THIS MONTH'S SNIP

High compliance 8" round speakers suitable for 8-12 ohm outputs, these speakers have rubber mounted diaphragms and will handle up to 12.5 watts. Made originally for an expensive Decca hi-fi outfit, we offer at \$2-95 each or \$7-75 a pair plus 40p each postage.



STEREO RADIO CABINET

Long, Low and Modern. Teak veneered with sliding front and tapered legs. 2 speaker spaces each end. Size approx. 4ft 2in x 13in x 15in. Probably cost over £20-00 to make. Our price \$3-10 each.

HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously

Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact, there is no limit to the versatility of this Programmer. Mains operated. Size 3in x 3in x 2in deep. Price \$4-85 as illustrated but less case.



TAPE DECK

In metal case with carrying handle, heavy fly wheel and capstan drive. Tape speed 3 1/2. Mains operated on metal platform with tape head and guide. Not new but in good order. Price \$1-95 plus \$1 post and insurance.



TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. 2kW Model \$2-75. Don't miss this. Control Switch 44p plus VAT, P.&P. 40p.

SHORTWAVE CRYSTAL SET


Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19.25-31.39 metre bands—Kit contains chassis front panel and all the parts. \$1-25—crystal earphone 50p.

SPIT MOTOR

200-250V Induction motor, driving a Carter gearbox with a 1 1/2" output drive shaft running at 5 revs p.m. Intended for roasting chickens, also for driving models—windmills, coloured disc lighting effects, etc. \$2-50 plus 20p post and ins.

INFRA-RED BINOCULARS

Made for military purposes during and immediately after last war to enable night vision, vehicle drivers, etc. to see in the dark. The binoculars have to be fed from a high voltage source (5KV approx.) and providing the objects are in the rays of an infra-red beam, then the binoculars will enable these objects to be seen. Each binocular eye, technical data on which is available. The binoculars are unused, believed to be in good working order. In fact they were never issued and are still in original cases, but since they were made a long time ago, they can hardly be called new. Sold without guarantee. Price \$18-50 per set + \$1 carriage.

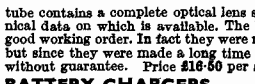

BATTERY CHARGERS

Famous Atlas in metal case with meter, output leads terminated by crocodile clips. For 6 or 15 amp. Recharge simply by changing plug on front panel. Ready built new and still in maker's original packing. Two models: 1 1/2 amp \$1-99 and 3-4 amp \$2-95. Please add 40p postage for one and 75p postage for two.



12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price \$2-50 plus 20p post & packing. Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop use. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price \$2-95 plus \$1-00 post.



TERMS—ADD 8% V.A.T.
Send postage where quoted—other items, post free if order for these items is £6-00, otherwise add 30p.

J. BULL (ELECTRICAL) LTD.
(Dept. PW), 102/103 TAMWORTH ROAD,
CROYDON CRO IXX

NEW ITEMS THIS MONTH

The bargains in this column are just some of the items which appeared in the December supplement to our catalogue. You can receive this catalogue and the next 12 supplements by sending \$1.

Laboratory volt meter, BS1. This is the conventional square case, size 7" x 7" x 3 1/2" with a leather carrying handle and rubber feet for horizontal and vertical standing. The meter is intended for horizontal use on the bench and has a mirrored scale. Hefty terminals along the top select the 3 ranges 0-150v, 0-300v and 0-600v D.C. Price \$6 plus \$1 post and insurance.

Laboratory amp meter, companion instrument to the above, but to read 0-20 amps 50 cycles, \$5 plus \$1 post and insurance.

Soil heating transformer, 4v, 5v or 6v output, very heavy duty secondary rated at 250 amps, price \$20 plus carriage \$2 first 100 miles then \$1 per 100 miles extra.


7 watt stereo/mono amplifier with usual switching and controls, in attractive teak style case, \$9. 3 core lead, 7" 6" long, ribbed, virtually non-kinkable 23/38 conductors, so OK for 8 amps. Price 10p each.

0-1 mA meter 2 1/2" square, flush mounting, English make ex equipment but perfect. \$1-75.

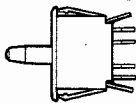0-100 microamp meter, as the above, but \$2-25. Solenoid 4-6v, size approx. 1" x 1" x 4" thick, twin coils give excellent pull. Mounted in frame but easily removable from this frame, fitted with lever giving approx. 1/4" push or pull. Price 30p each.

Gold cathode tube Swiss made "Elasta" type no. ER 12A. We have no technical information on this tube and if any reader has this we will be obliged for any information. Price of the tubes 30p each.

AC mains operated relay with single changeover 10 amp contacts, open type single screw fixing through the base. 50p each.



Push switch, metal push, normally on. These are replacements in many "break glass" fire alarms. Made by Arrow, contact rating 250v 5 amps. 30p each.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: 4EF4, 2F4, 2F7, 2F8 and others. Kit comprises main transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only \$1-50.

Push switch, double pole changeover contacts rated at 10 amps 250 volts made by the American Honeywell Co. A very reliable and robust switch with plenty of applications. Oblong plastic body, snap fitting into a hole size 1 1/2" x 1 1/2". Offered at only a fraction of its proper price, namely 20p each.

Double but single pole changeover, fits into a hole size 1" x 1". Price 15p each.

Double, but dished knob, 10p extra with knob.

Two new speakers, 5" round 8 ohm impedance 5 watt output, \$1-25 plus 20p post and \$1/2" mid-range 12 watt speaker, \$4 plus 40p post. (This is a GOODMANS speaker don't miss it).

AM/FM tuning condenser as fitted to many Japanese and Hong Kong portables, this has two main tuning sections and four trimmers, approx. size 1" x 1" x 1". 60p each.

Battery charger kit comprising 2 amp transformer, 2 amp full wave rectifier and 2 amp meter suitable for charging 6v or 12v. Special bargain price \$1-50 the kit plus 30p post.

MacDonald record auto-changer with cueing arm and ceramic stereo cartridge. This is a very superior auto changer and one we can thoroughly recommend. Limited quantity, special price \$7-95 plus \$1 post and insurance. Finish and cover (the plinth has to be modified very slightly) available, price \$4-95 plus \$1 post, or if you buy both together you can get a discount of \$1.

Instrument case measures 18" x 12" x 12". This is a very well-made case built up on an angled framework specially designed for instruments with rounded corners and edges. Into this framework fits the 6 panels. All panels are louvred for ventilation, side panels are also fitted with handles which drop down and in the down position are almost flush, the bottom panel has four rubber feet, the back panel has aperture for mains voltage adjustment panel and fuses, the front panel you provide yourself. These instrument cases would probably cost around \$15 each. We have approx. 100, not new but in very good condition and offer them at \$3 each plus carriage.

Battery condition testers. This is another item which has been set out of stock temporarily but we are pleased to say in stock again. Price now \$3-50.

RTVC

* COMPLETE STEREO SYSTEM

System 1a. £62.00

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel (40 watts peak). All systems include:

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket.

Specification:

20 watts per channel into 8 ohms 40W peak. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV at 1kHz into 47K, equalised within ± 1 dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics:* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".

Garrard SP 25 deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type IIa matched speakers - Enclosure size approx. 19 $\frac{1}{4}$ " x 9 $\frac{1}{2}$ " x 7 $\frac{3}{4}$ " in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling.

Complete System with these speakers £62.00 + £5.50 p & p.

System 2. £82.00

Viscount III amplifier (As System 1a)

Garrard SP 25 deck (As System 1a)

Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 $\frac{1}{2}$ " Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS, 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System with these speakers £82.00 + £6.50 p & p.



Scotland P & P Surcharge
System 1a £1.75 System 2 £3.50



PRICES: SYSTEM 1a

Viscount III R102 amplifier	£27.00 + £1.60 p & p
2 Duo Type IIa speakers	£26.00 + £5.50 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and cover	£21.00 + £2.80 p & p
total:	£74.00

Available complete for only: £62.00 + £5.50 p & p

PRICES: SYSTEM 2

Viscount III R102 amplifier	£27.00 + £1.60 p & p
2 Duo Type III speakers	£39.00 + £6.40 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and cover	£21.00 + £2.80 p & p
total:	£87.00

Available complete for only: £82.00 + £6.50 p & p

EMI SPEAKERS AT FANTASTIC REDUCTIONS



LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.

Specification - Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz - 20 KHz.

Our Price £29.00
(normally £56.97) + £5 p & p.

EMI 350 KIT

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

Complete with crossover Components and circuit diagram **£5.50 + £1 p & p.**

20 WATT SPEAKER SYSTEM*



System consists of a 13" x 8" (approx.) elliptical woofer unit with a 8" x 5" (approx.) mid-range unit incorporating parasitic tweeter and crossover components and circuit diagram

Technical Specification: Bass Unit: Flux density - 100 K, speech coil - 1 $\frac{1}{2}$ ". Cone. Triple laminated paper with P.V.C. surround. Mid-Range Unit: Flux density - 33 K, speech coil - 1" with parasitic tweeter. Power handling: 20 watts RMS, impedance - 8 ohms, frequency response - 20 Hz to 18,000 Hz.

Our Price £7.50
Complete + £1.35 p & p.

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3 $\frac{1}{2}$ " tweeter and matching crossover.

Easily put together with just a few basic tools. **Specification (each speaker):** Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000Hz. Size 20" x 11" x 9 $\frac{1}{2}$ " approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

£18.95 pair complete


+ £4.50 p & p. Complete with crossover Components and circuit diagram



DECCA STEREO AMPLIFIER CHASSIS

Specification: 4+4 watts into 8 ohms. Input Sensitivity 4mV into 47K (for magnetic cartridges). AC Mains only 240V. Controls - volume, bass, treble, on/off, mono/stereo switch. Chassis size 11" x 5 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " approx.

£5.95 + £1 p & p.

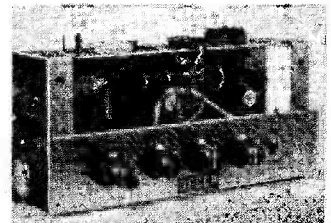

PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide 2" high

and 4½" deep approx. **£8.00** + 90p. p & p. Speaker including baffle and fixing strip **£1.65** + 37p p & p. Car Aerial Recommended — fully retractable **£1.37** + 32p p & p.

The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £7.00** + 90p p & p.

*STEREO 21 QUALITY SOUND FOR LESS THAN £20.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth

Includes — **BSR 3 speed deck**, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications — For the technically minded:

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs.

Overall Dimensions. Speakers approx. 15½" x 8" x 4". Complete deck and cover in closed position approx. 15½" x 12" x 6".

Complete only £19.95 + £2.60 p & p.

Extras if required. Optional Diamond Stylus **£1.37**.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£5.00**.

*DISCO AMPLIFIER



Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES — Input — 1). Crystal mic, guitar or moving coil mic. 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc — all 250mV sensitivity. AC Mains. 240V operation. Size approx: 12½" x 6" x 3½".

£17.00 + £1.15 p & p.

*8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21. Technical specification Mains input. 240V, Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx. Yours for only

£12.95 + £1.45 p & p.




BUILD YOUR OWN *STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7" x 4") **£9** + £1.50 p & p. **£7.64** + 90p p & p.

PORTABLE DISCO CONSOLE*

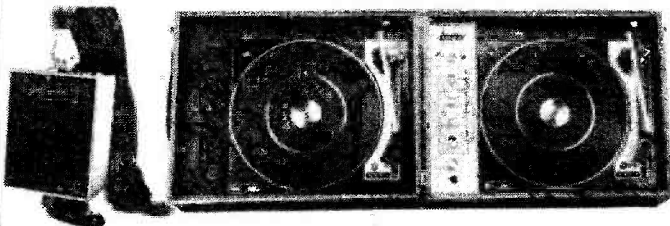

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:

Pre-amp — Output — 200mV. Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation. **Turntables capacity —** 7", 10" or 12" records. **Rumble, wow and flutter** Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kalee meter).

Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17½" x 13½" x 8½" (app.)
Unit Open — 35½" x 13½" x 4½" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only £49.00 + £5.60 p & p.



DO NOT SEND CARD
Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st March 1975 and subject to change without notice. All prices include V.A.T. at 8% rate.



21C HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personnal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

Fact~not Fiction

THE varicap silicon junction diode, with its variable capacity effect, has been with us for many years. There is widespread use of these devices in tuner heads for domestic VHF/FM and TV and UHF TV for automatic frequency control (AFC) and/or electronic tuning. The use of low-cost varicap diodes has been restricted to these applications because of the limited capacity swing they offer.

Numerous manufacturers with an eye on the market potential of this device, have been actively engaged in the development of varicaps that fulfil the special requirements of long and medium waveband receivers.

In recent months these long-awaited devices have been released by Motorola in several combinations. The MVAM1 triple varicap package forms the "heart" of the "PW Apollo" Triple Varicap Medium Wave Tuner/Receiver appearing in this issue.

Thus overnight, electronic tuning for long and medium waveband receivers is **fact** and **not fiction** for the home constructor. To this end, a new-style slider potentiometer was commissioned for the PW "All Electric Wireless" to simplify the tuning arrangements.

Remote control tuning is no problem. During tests on the prototype PW receiver, remote control tuning was achieved with the slider potentiometer connected to the receiver chassis via 30 metres (100 feet approx.) of cable!

The "PW Apollo" series will reveal, month by month, a number of fascinating applications utilising this new unique varicap package. Just to whet your appetite, this triple (or double) varicap device could be used in conjunction with a general coverage receiver and oscilloscope to give a spectral display of radio signals. Also, how about an electronic remote tuning car radio with the AM/FM radio unit tucked away safely in the car boot?

The applications of this new varicap package are numerous and we prophesy that it will bring about many radical changes and new ideas in electronic technology. The PW "All Electric Wireless" could set the trend and be the forerunner of a multitude of receiver designs that will now permeate our exploding technology.

Begin reading the facts in the "PW Apollo" series, Part 1 on page 44.

LIONEL E. HOWES, Editor.

Bentley Acoustic Corporation Ltd.

Following complaints from readers we have now received an undertaking from Bentley Acoustic Corporation Ltd., that their practice of deducting expenses from refunds made to readers has now ceased and we are assured that all future refunds will be made in full.

NEWS...

Write to them

THIS year seems to have got off to a relatively slow start when it comes to news of the latest happenings in the electronics world. The PW office usually receives a mountain of press releases that take a fair time to sort out. However, after thumbing our way through the correspondence that has arrived, and we must add, throwing out that more applicable to Nuclear Research Stations and the like, we've come up with the following pot-pourri of news, forthcoming events and a few noteworthy new components. It should be pointed out however, that the following are in a shortened form designed to 'whet the appetite'. If, therefore, more information is required, an address and sometimes the phone number of the firm concerned is given with the story. Write to them, not to PW!

Mail order success

DURING the last few months of last year, Chromasonic Electronics of North London (see advert. in this issue) announced their intention to start a return-of-mail service. In the months following, the firm states, not one letter received by 3pm has been left over for processing on the following day. They add that, in addition, telephone enquiries for technical or product price information are not discouraged, as is the case with many firms. Data sheets for semiconductors are also available and cost 6p, A4 size, plus postage.

Knowledge

IF any reader, thirsting for knowledge, wishes to attend an 'all in' three day symposium covering a wide range of test gear and techniques, then why not attend 'Test 75' at the University of Kent between July 7th and 10th. Cost is around £45 and correspondence should be sent to the Symposium Secretary, SERT, Faraday House, 8-10 Charing Cross Rd, London WC2H 0HP. Tel: 01-240 1152.

JVC moves

WE start with the news that JVC (UK), distributors of Hi-Fi and television products, have transferred to new premises. The move due to 'enormous growth since 1969' took place earlier this year with a new showroom, sales department, warehouse and service department. Location is now in the Eldonwall Trading Estate, Staples Corner, 6-8 Priestly Way, London NW2 7AF. Tel: 01-450 2621.




JVC's new premises in North London.

Hey Wack!

ANYONE out there live in Liverpool or surrounding district—Yes? Well, as from the 24th January BBC Radio Merseyside (95.8MHz) has been utilizing slant polarization. This, according to the BBC Engineering Department, is to improve reception for portable receivers and VHF car radios.

Another calculator

RECENTLY many companies have been jumping on the calculator bandwagon and although there is now a bewildering number to choose from, here's just one more!!! It's a desk-top model, designated the CBM1500 and hailing from the States. Functions include sin, cos, tan, arc, pi, and roots as well as straight-forward numbers. A memory is also included. Price is around the £70 mark and it can be obtained from *Guildford Tapes & Calculators, 1a Onslow St., Guildford, Surrey.*

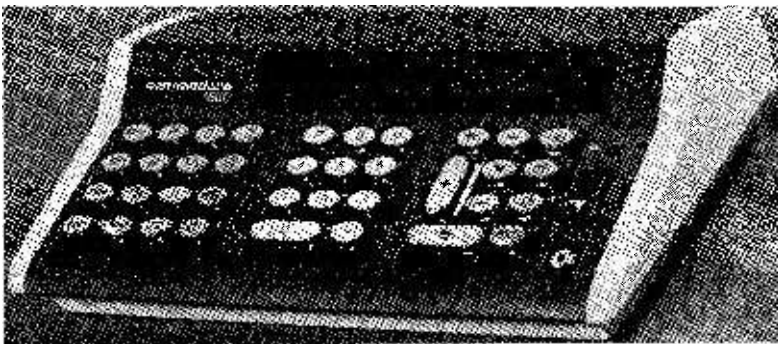

New desk-top calculator, the CBM1500 from Guildford Tapes & Calculators.

Radio notes

A QUICK note here for the amateur radio enthusiast. The Midland Amateur Radio Society will be staging the North Midlands Mobile Rally at Drayton Park, Tamworth, on Sunday 20th April. Further information from A. Walton (G3ZKQ), *Birmingham and Midland Institute, Birmingham 3.*

More Beeb cut-backs

ALTHOUGH possibly of more interest to the readers of our sister magazine, Television, it has come to our notice that the BBC, 'due to its financial position,' and the need to 'Save it', has found it necessary to curtail the BBC-2 trade test transmissions. Each weekday for about 5½ hours, installers, dealers and servicemen will be at a considerable inconvenience, particularly those installing new aerials and receivers. With the tremendous influx of cash due from the recent TV licence fee increase, one wonders what the BBC will do with all that extra money!

Radio Society get-together

THE RSGB 21st National VHF convention is to be held at the Winning Post Hotel, Whitton, Twickenham, Middlesex, on the 10th and 11th of May.

The programme comprises lectures and demonstrations on amateur space communications, microwaves and VHF propagation. Starting at 11am on the 10th, the lecture sessions are on Saturday afternoon and Sunday morning, with the Saturday evening taken up with a dinner dance.

The whole event costs £3 per person, or 80p for lectures and trade show only. Further details from RSGB, 35 Doughty Street, London WC1N 2AE, marking the envelope 'VHF Convention'.

Summer school

ESSEX University will be holding its annual Electronics Summer School for the week of July 7-11th and comprises two courses running simultaneously. The first course, ESS 8—Linear Circuit Design, is concerned with the use of transistors and operational amplifiers in linear applications. The second, ESS 9—Digital Circuit Design, concentrates on the use of the transistor as a switch and develops designs using integrated logic circuits.

A full laboratory programme backs up the topics covered in lectures, and tutorials are held to discuss the design for the practical sessions. Further information from Bob Mack, *Dep. of Electrical Engineering Science, University of Essex, Colchester, CO4 3SQ.*

Model Train Controller

JOHN LEWIS

SPEED controllers available to the general public are either mains or battery powered, both suffering inherent design faults. One of the overriding faults centres on the fact that it is based on a variable resistor placed between the supply and the tracks. It therefore follows that any control action which varies the speed of the train, also varies the current available to the motor and consequently the torque or pulling power. This is satisfactory at high speeds but at lower ones problems arise since it is here that one requires more pulling power in order to get the train started. What usually happens is that the control has to be well advanced before any movement occurs and then quickly turned back once the train is moving. This of course results in erratic and unrealistic motion of the train.

The author realised that this problem could be overcome by the use of a square wave of constant frequency and amplitude, but with a variable mark/space ratio. Fig. 1 shows what is meant. When the mark/space ratio is 50%, the time that the voltage is ON is the same as the time that the voltage is OFF, giving an average value of the voltage as shown. If the mark/space ratio is altered so that the ON time is increased, the average value of the voltage will rise and hence the train will speed-up. Conversely if the mark/space ratio is decreased the train will slow down. The motor integrates the pulses and interprets them as changes in voltage rather than current thus giving maximum torque at the required speed. In fact, with this arrangement it is possible to control the train from flat-out down to literally inching round the track, greatly increasing the realism.

THE INTEGRATED CIRCUIT

The controller is based on the inexpensive 555 integrated circuit. Basically it can be used either as a monostable or an astable circuit as shown in Fig. 2.




For those who are not familiar with its operation Fig. 3 may help. Internally there is the equivalent of two voltage comparators, a flip flop and an output stage. The comparator connected to pin 2 responds to a voltage of $\frac{1}{3}V_{cc}$, whilst the comparator on pin 6 responds to $\frac{2}{3}V_{cc}$. These comparators change the state of the flip-flop and hence the output.

If we look at the astable application which is the one used in this controller we see that both pin 2 and pin 6 are connected to the capacitor and so sense the voltage across it. The capacitor charges up via resistors R1 and R2 and when the voltage across it reaches $\frac{2}{3}V_{cc}$ the comparator on pin 6 will trigger and the flip-flop changes state, driving the output low. At the same time as this occurs, pin 7 is effectively shorted to earth and the capacitor now starts to discharge through R2. When the voltage across C2 reaches $\frac{1}{3}V_{cc}$ the comparator on pin 2 will be triggered, the flip-flop reset with the output going high and the earth to pin 7 removed. This means that C2 can start recharging again. The cycle repeats itself with the frequency being dependent on the values of C2, R1 and R2.

To calculate the frequency the formula

$$f = \frac{1.44 \times C2(\mu F)}{R1(k\Omega) + 2R2(k\Omega)}$$

is used. It can be seen that the values of R1 and R2

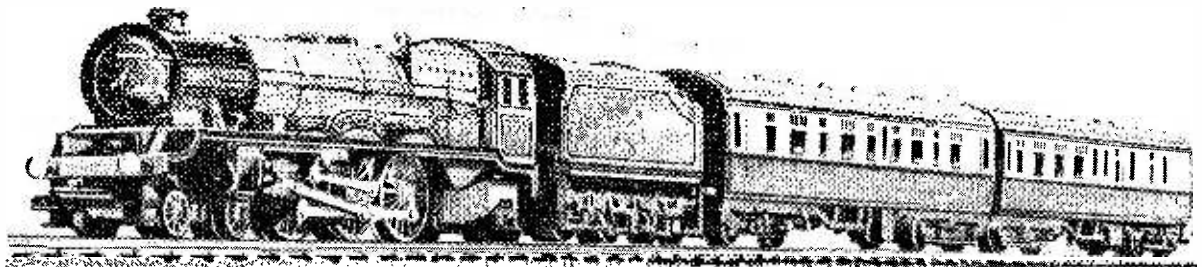

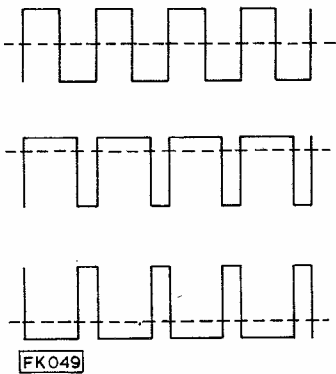


Fig. 1: Square waves of constant amplitude and frequency but with variable mark/space ratios.

will determine the time for which the output is either high or low. If R1 equals R2 then the charge up time will be twice that of the discharge time, since the capacitor charges up through both R1 and R2 but only discharges via R2. By choosing appropriate values one can get a mark/space ratio of 50% or more with the circuit shown. If a diode is added across pins 6 and 7 a duty cycle of less than 50% can be obtained, and if R1 and R2 are replaced with a variable resistor one can get a wide range of mark/space ratios.

The other feature of the IC is the reset available on pin 4, provided that the potential on this pin is maintained at more than 1V the circuit will operate normally. However if the potential falls to zero then the IC is inhibited and no output is obtained. It was decided to use this facility as an automatic short circuit protection.

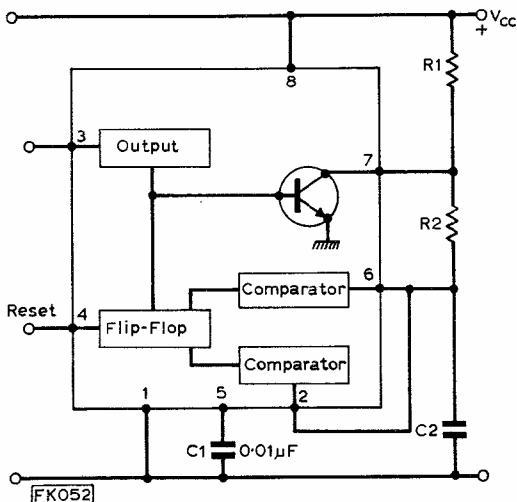


Fig. 3: Diagram of the 555 showing internal arrangement and external biasing components.

FINAL CIRCUIT

The final circuit can be seen in Fig. 4. The 555 is connected in the astable mode, with the diode added between pins 6 and 7. Using the values of C1 and VR1 shown a nominal frequency of 144Hz is obtained though the values could be altered should one wish to experiment with other frequencies of operation. The resulting square wave at pin 3 is used to drive

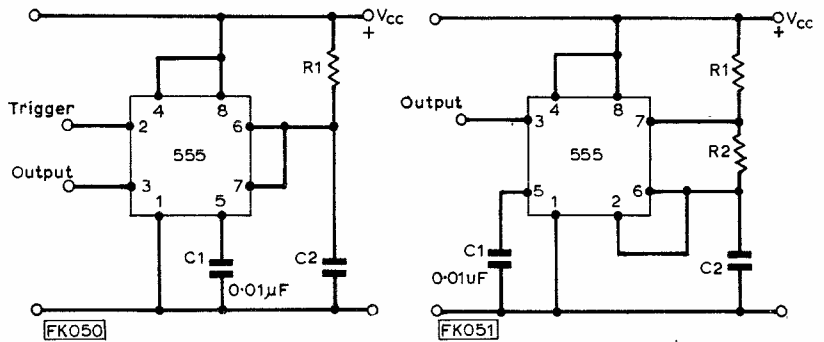


Fig. 2: The 555 integrated circuit connected in monostable and astable modes respectively.

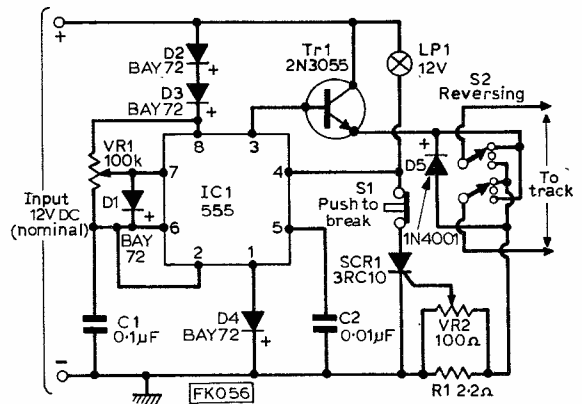


Fig. 4: Complete circuit of controller, showing automatic cut-out system, speed control potentiometer VR1 and reversing switch.

the base of the output transistor Tr1 while the output from its emitter is taken to the track via a reversing switch S2.

The return path of the current is through R1, a low value resistor which forms the sensing element of the short circuit protection. When the current flows through R3 a voltage drop is produced across this resistor depending on the current flowing, and is tapped off by VR2. This voltage is then applied to the gate of the thyristor SCR1. Without going into too much detail it will be remembered that a thyristor behaves like an open circuit switch passing negligible current until a suitable positive potential is applied to its gate. When this happens it turns on and conducts in a manner similar to a diode. The gate loses all control at this point and the thyristor stays on even though the gate bias is removed. The amount of potential required to trigger the thyristor varies from type to type and this is catered for by VR2.

If a short does occur on the track the current passing through R1 will increase, resulting in a higher voltage drop, and consequently the turning on of the thyristor. This lights the bulb, LP1, which indicates that something is wrong. With LP1 coming on the potential at the top of the thyristor drops from V_{cc} to almost zero, and since pin 4 is connected to this point the IC will be inhibited, and its output will drop, thus cutting off the power to the track. A push button S1, is provided to reset the circuit once the short has been removed. The diode D4 ensures

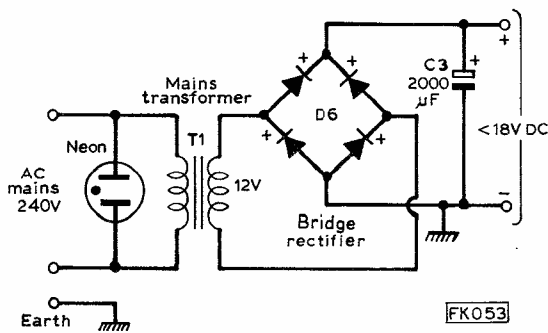


Fig. 5: Optional power supply, utilizing full-wave bridge rectification. Output must be less than 18V DC.

that the voltage presented at pin 4 is low enough to inhibit the IC, by raising the negative point of the IC, 0.6V above the negative rail voltage. The sensitivity of the protection circuit can be adjusted by VR2 enabling it to trigger should the train be excessively loaded. Once a fault has been cleared the reset button is pressed and the train will restart. On the prototype, VR2 was a normal pot, although obviously a skeleton preset would do the same job.

POWER SUPPLY

The circuit will work from any commercially produced 12V-18V DC supply which is adequately smoothed. If there are any doubts about the smoothness of the supply, include a 2000µF capacitor of at least 25V working across the output.

If required a simple DC power supply can be easily built and a suitable one is shown in Fig. 5.

SAFETY

Since the circuit is certainly going to be used by children, great care must be taken to ensure that it is electrically safe. Check that all main leads and transformer terminals are adequately insulated and the whole should be enclosed in a metal box which is earthed. On the prototype no mains switch was incorporated, only a neon indicator. The reasoning behind this is that it ensures that the controller is

★ components list

Resistors

- R1 2.2Ω 3W
- VR1 100kΩ linear potentiometer
- VR2 100Ω Trim potentiometer or skeleton type

Capacitors

- C1 0.1µF C2 0.01µF C3 2000µF 25V

Semiconductors

- Tr1 2N3055
- IC1 555—Signetics or Motorola
- SCR1 3RC10 or any general purpose thyristor rated at 0.5A and 25PIV.
- D1, D2, D3, D4 BAY72 or 1N914 or any general purpose silicon diode
- D5 1N4001
- D6 Bridge rectifier—any general purpose type rated at least 2A

Miscellaneous

- LP1 12V indicator lamp
- S1 switch—push to break
- S2 switch—toggle DPDT centre off.
- T1 Transformer—nominal 12V, 1.5A. Possible to use filament transformer and connect the two 6.3V windings in series.

Mains neon. Mains cable clamp and solder tag.
Metal box approx. 185 x 115 x 75mm (7½ x 4½ x 3in.)
Veroboard 0.1in. pitch 76 x 31mm (3 x 1¼in).

switched off and unplugged from the mains when not in use, and not merely switched off internally. However, opinions will differ and a suitable switch can be easily incorporated if desired. It is worth mentioning here the diodes D2 and D3 shown on the circuit diagram. In the prototype the power supply gave 19V under no-load conditions and the maximum working voltage of the 555 is 18V. Rather than mess around with a zener diode etc., it was decided to drop 1.2V just by using these diodes. Thus these and D4 ensure that the IC is actually running at 17.2V. If the supply is less than 18V under no-load conditions, D2 and D3 can of course be omitted. D5, which is across the reversing switch S2 is there to suppress the negative-going spike produced by the motor at the end of each pulse, which could damage Tr1.


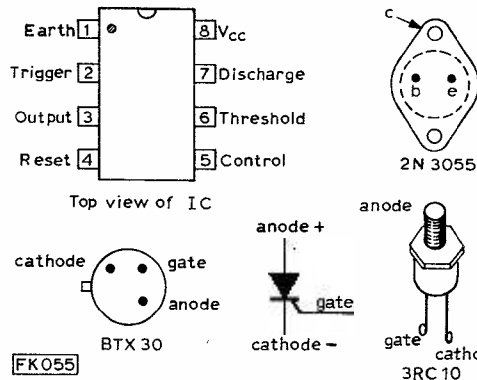
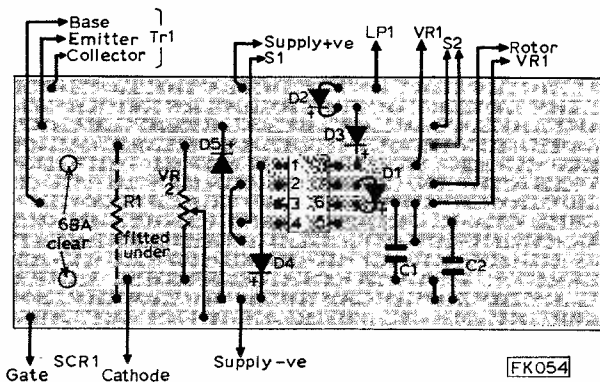


Fig. 6: Component layout on Veroboard, showing track breaks and external connections. Tr1 (2N3055) and SCR1 (3RC10) shown to the right must be fitted using insulating washers. Connections to the collector of Tr1 and anode of SCR1 are via solder tags.

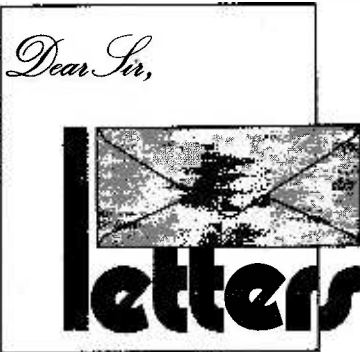

Oily waves

I feel I must write and protest at the tone of your editorial of March 1975 *Practical Wireless*.

I fail to see why you appear so "anti" about exchanges between North Sea oil rigs and their bases. Apart from 1625 kHz which is used by Ekofisk to work into Stavanger, all other off-shore installations work directly into British or Continental coast radio stations in the Maritime Service. The stations heard in the 80 metre band are exchanging traffic on ISB with Humber Radio or Wick Radio, or on SSB with Cullercoats or Stonehaven radio and thence by land line to shore based subscribers.

All these communications are taking place at the rate of 36p per minute and represent revenue to the Ministry of Post and Telegraphs. I fail to understand why any off-shore station should be expected to continually identify itself when the call is being monitored and charged by a coast station Radio Operator?

Life off-shore can be arduous and dangerous and the many oil rig and barge workers who may phone their wives during the evening should be entitled to a little privacy during the QSO. . . . they're paying enough for it!—**Stan Crabtree** G3OXC (Radio Operator, FORTIES ALPHA).

PW PSU mod

Having constructed a bench power supply unit to the same basic design as that described in PW, September 1973 by J. Lewis, B.Sc., I feel the following observation may be of use to your readers.

The author comments in the final paragraph: "a residual ripple . . . could be eliminated by

adding a 100 μ F capacitor. . ." I found that even a 1000 μ F made little difference when used with a particular piece of equipment which was sensitive to hum on the supply rails; I therefore added, to the circuit of Fig. 9 in the article, a 10 μ F 64V electrolytic, between pins 3 and 4 of the NE550A (negative to pin 4) thereby providing AC negative feedback and substantially reducing the hum (100Hz ripple).

I consider that a larger value would produce a greater improvement, but my unit is now sufficiently ripple free for my requirements.—**P. J. Brent** (Scotland).

Natural scale

I'm surprised at Mike Hughes! In his article on the PW Easybuild Electronic Organ, he states that "organ purists will wince" at the use of the equal temperament scale. This scale has been in use on keyboard instruments since the time of Bach. In fact it is in use in all musical instruments which are "pre-tuned" such as the clarinet, trumpet, oboe etc.

The idea behind the equal temperament scale is quite simple. The relationship between a note and the one an octave above, is that the higher note has twice the frequency of the lower. A violinist, in order to achieve this will in fact halve the length of his string. The frequency ratio for notes a fifth apart is 2:3. For notes a third apart it is 4:5 and so on.

In the equal tempered scale, as Mike Hughes says, there is an exact mathematical ratio between each half tone in the scale. This ratio is 1:0.594, and since there are twelve half tones to the scale, 1:0.594¹²=2. This makes the frequency ratio of the third 1:1.259 and not 1:1.25 as on the natural scale. Similarly the fourth ratio is 1:1.34 and not 1:1.33. The fifth becomes 1:1.498 instead of 1:1.5.

These differences are not enough to be noticed in ordinary circumstances, but violinists, and singers etc, when playing on their own, will play in the natural scale; and when with the piano or organ etc. will play equal tempered.

Incidentally, Bach was the first to write specifically for the equal tempered system in his "Well Tempered Clavier." — **P. G. Quartermain** (Sussex).

Cramped bands

Your editorial 'Thou shalt not listen' draws timely attention to a problem which is becoming increasingly frustrating to the DX listener. For about one year now, I have been very interested in long range reception on UHF TV and VHF radio.

I find that the ordinary VHF set offers good scope for DX work, except that the 88-108MHz band is cluttered with taxi and police signals. So much of the band is given over to these, that the broadcast band is "bunched" to such an extent that many stations use the same frequency, and others are so close to each other that the nearer ones eclipse the more distant.

Even with a six-element array, I cannot now receive Radio Humber-side because it is obliterated by Radio Piccadilly; RTE Kippure is wedged between Radio Merseyside and Radio Manchester and can only be heard by using screening. Radio Sheffield, on its lower frequency, is jammed by taxi calls, and on its higher frequency is jammed by the police.

Recently I picked up an interesting signal in Dutch. After waiting a long time for station identification, I was frustrated by a taxi firm which drowned out the station identification when it did come. (I still don't know which station I was listening to!)

All these problems could easily be solved by allocating the whole 88-108MHz band to broadcasting. Surely the police do not enjoy being overheard and would prefer to be on a virtually inaccessible band?

Which raises another question; What is to happen to Bands I and III when the 405 line TV service is phased out in a few years time? My own suggestion is that these channels should be allocated to educational television; schools broadcasts during the day and Open University in the evening.—**John T. Haines** (Lancs).

Ouch!

I thought you might be interested in the specification of a transistor radio seen in a mail order catalogue; "clear reception on 3 wavebands VHF/MW/LW. Clear 2 $\frac{1}{2}$ in. dynamic speaker giving 300kW output. Complete with earphone." —**R. Rix** (Norfolk).



PW 'Easybuild'
ELECTRONIC
ORGAN

M. J. HUGHES M.A., C. Eng. MIERE


This, the third part of the PW Easybuild Organ, carries on from the April issue, and covers in detail the keyboard wiring and the testing of the main PCB.

8FT PITCH

Readjust VR6 for maximum and adjust the pre-set VR5 until the signal level of the square wave output approximately matches that of the spike signal. To complete this rough setting up of the 8ft tones set the triangular wave slider VR8 to maximum. The sound should be more mellow but of similar amplitude to the square wave signal. Now adjust the pre-set control across the 8ft integrator VR7. Adjustment to its full extreme in one direction will have no effect but if its value is reduced to zero ohms the amplitude of the signal will fall abruptly to a very low level. Set it to the point just before the signal level starts to fall off which will prevent nasty keying noises when this tone is used. Now try mixing the different waveforms together to hear the general effect of the three signals in various proportions. Do not expect too much at this stage because we have yet to line up the 16ft. pitch.

16FT PITCH

Exactly the same procedure should be adopted by placing the lead from the 16ft. input pin on to a mid-frequency tone pad. Start with the spike waveform by advancing VR10 and adjust the preset VR9 until the level is approximately similar to the equivalent tone at 8ft pitch. Advance VR12 and use VR11 to set the level for the square wave. Finally, advance VR14 and adjust VR13 in exactly the same way as for the integrator pre-set at 8ft. pitch. Now experiment by connecting the 8ft. and 16ft. inputs to identical notes an octave apart at the same time, and listen to the full effect of the different tone colours produced by the main controls. When they are all advanced to maximum the loudspeaker might overload, in which case use the pre-set VR15 as a master control. Ideally the loudspeaker should be just on the edge of overloading when the volume control is at maximum. More will be said about this when dealing with the phono output.

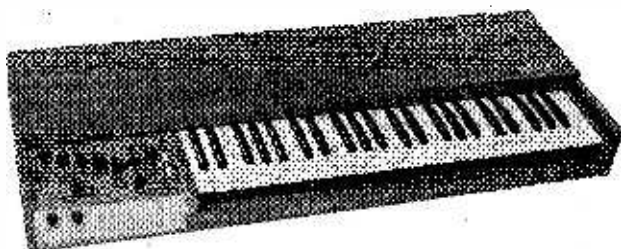

CALIBRATION

Check that the vibrato control functions correctly and roughly tune the master oscillator so that the organ is set to international pitch. Do this by adjusting C7 while listening to the tone from leadout number 23 (this should be International A at 440Hz), and can be checked against a piano (the A immediately above middle C) or against the BBC's morning radio test transmission.

When tuning, the tune control should be set midway. It may be that C7 has to be almost fully compressed to get the organ in tune. When correctly set up the tune control should shift the frequency by about one full tone, but this will vary slightly from one unit to another, depending on the internal capacitance of D1 and D2.

A wider degree of tune can be produced by reducing the value of R6 to about 4.7kΩ but this is not recommended because the vibrato effect will be too fierce when VR2 is set to its lowest frequency position.

The bulk of the electronics is now finished, the next stage is the assembly of the keyboard contacts and the wiring associated with them. This is a very repetitive operation and calls for a reasonable amount of patience and care.

KEYBOARD

Make sure that the correct components have been obtained. A 49 note C to C keyboard as specified will be required, together with 49 contact blocks. These blocks are very delicate and should be handled carefully to ensure that the fine gold-plated contact wires are not bent. Each block comprises four wires held

in position by the phenolic laminates and rivets. Fig. 10 shows such a block and the dotted lines show the disposition of the wires as they run through the centre.

For the purposes of description each wire should be designated with a letter 'a', 'b', 'c', and 'd'. Wires 'a' with 'b' form one contact pair and 'c' with 'd' the other; in every instance the pair a/b will be used to route signals into the 8ft busbar and c/d into the 16ft busbar.

The contacts are actuated when a key is pressed and the action can be checked by careful inspection of the underside of the keyboard. When a note is depressed the key pushes a small plastic actuating link out from under the keyboard. This is designed to push the wires 'a' and 'd' of each contact block into electrical contact with their corresponding 'b' and 'c' wires. One of the jobs that has to be done is to fix each contact block into position so that this simple mechanical action can be effected.

PALLADIUM BUSBARS

The blocks are so designed so that when a key is **not** pressed the signal coming from the tone generator is shorted to earth. To avoid the problems of connecting a separate earth lead to each switch assembly, use is made of an earth busbar. Each block has a small hole positioned near its "nose" and if inspected carefully it will be seen that the wires 'a' and 'd' exactly centre on the hole.

The keyboard suppliers will provide a special rod made from palladium which is designed to run through this hole, and through the equivalent holes of all the other contact blocks. This rod forms the earth busbar and it should be clear that under normal circumstances wires 'a' and 'd' are kept in contact with the rod by their own springiness. When it comes to inserting the rod, make sure that 'a' and 'd' wires are displaced **towards** their 'b' and 'c' counterparts so that the rod passes through the hole without hindrance and is on the correct side of the wires. Four palladium rods should have been obtained, each of which is about the length of one of the keyboard octaves.


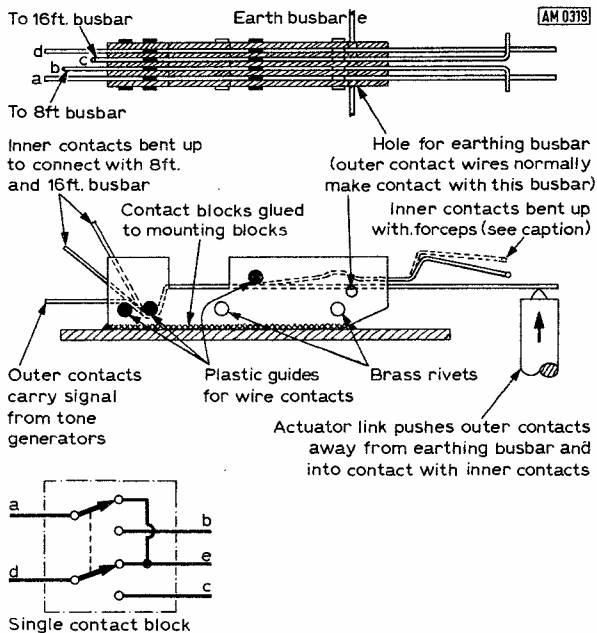


Fig. 10: Details of the keyboard switch assemblies (Kimber Allen)
NOTE. It is important, when a key is operated, that the outer contacts of the assembly break from the earth busbar before they make contact with the 8ft or 16ft busbars. These are adjusted by bending the "cranked" contacts away from the outer ones, with a pair of forceps, while operating each note in turn.

To make assembly easier, four SRBP plates (also obtainable from the keyboard suppliers) should be obtained. The contact blocks are glued on to these before the sub-assembly is screwed to the keyboard sub-frame.

KEYBOARD WIRING

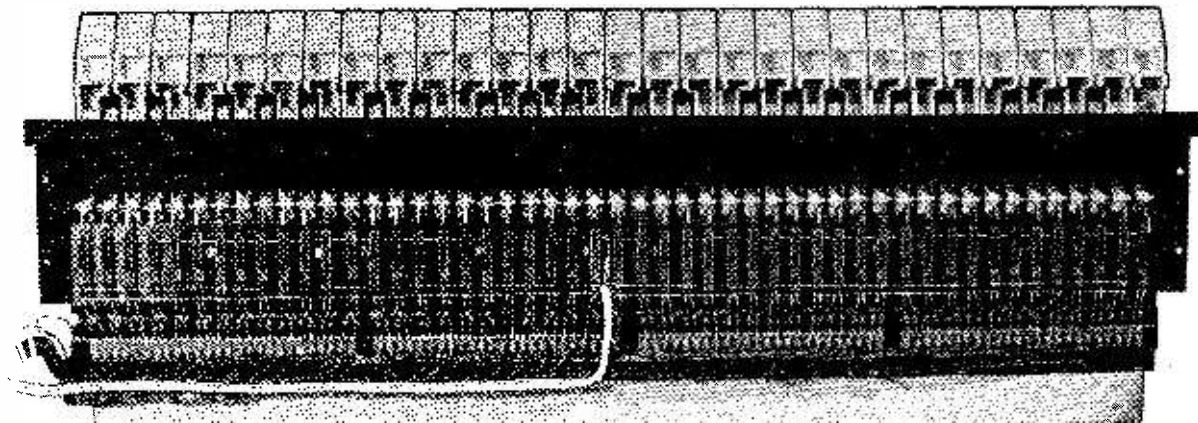The equivalent of 98 tag posts are required (strips with tags rivetted on 6mm ($\frac{1}{4}$ in) centres will do nicely) and these are used to terminate the 60 signal wires coming from the numbered positions on the main printed circuit board. Ideally there should be



Photograph of complete underside of organ keyboard, showing details of switch positioning, wiring and keyboard resistors.

one strip carrying 26 tags and three strips carrying 24 tags each. The tags are also used for routing the signals under the keyboard for the two pitches.

In principle a signal from the tone generator is terminated at one of the tag posts and a 100kΩ resistor feeds from that tag to the 'a' wire of the adjacent contact block. A connection is also made from that same tag post to the tag post for the same note an octave **higher**, but for this higher note key, the tag post corresponding to the 'd' contact wire should be used. A 100kΩ resistor bridges across from this latter tag to the 'd' contact. This looping from one octave to the next is how the signals are routed from the tone generator to give notes one octave apart (on the two pitches) when a single key is pressed.

A glance at the underside wiring diagram Fig. 11 and wiring schedule will show the general principle. The wires coming straight from the tone generator board go (in every case except the bottom octave) to the 8ft pitch contacts and the loop connections to the 16ft contacts of the identical note an octave higher. The bottom octave is slightly different because there is, of course, no lower octave from which to do the looping for the 16ft pitch connections. Instead there are eleven extra wires coming from the main board to look after the 16ft pitches for all this bottom octave **except for bottom 'c'**.

There are not quite enough notes to provide a 16ft pitch for the lowest C on the keyboard so the 8ft and 16ft contacts are simply looped together for this note. This is a slight nuisance but is a sacrifice one has to make for simplicity and low cost.

The wiring in Fig. 11 might look a little frighten-

ing but in actual fact it is very simple and only needs care and patience in the routing of the wires.

CONTACT ASSEMBLY

Before any thoughts of wiring however, the contacts must be assembled. To do this, turn the keyboard upside down and place the four SRBP plates exactly butting against each other on the wide flat portion of the keyboard sub frame; between the trough where the key pivots and the apertures for the actuator links. Slide the plates from side to side until the butt joint between the centre two plates **exactly** corresponds to the centre of the actuator link for the central 'C' of the keyboard. This should position the boards symmetrically about the mid-point of the keyboard.

Having obtained this position use a pencil to make marks on the boards which correspond to the centre lines of every actuating link of the keyboard. Use a set-square to project these marks across the board at every position and pencil in a centre line, this will mark where the contact block has to be glued into place. Draw another line 9.5mm ($\frac{3}{8}$ in) from the edge of the boards furthest away from the actuators which will act as a guide for positioning the blocks so that they line up with each other. This prevents problems when feeding the earth bus bar through the holes!

Using an epoxy resin glue (preferably the fast-setting variety) put a small smear of glue on the side of each contact block opposite the side having the rectangular notch and position each block

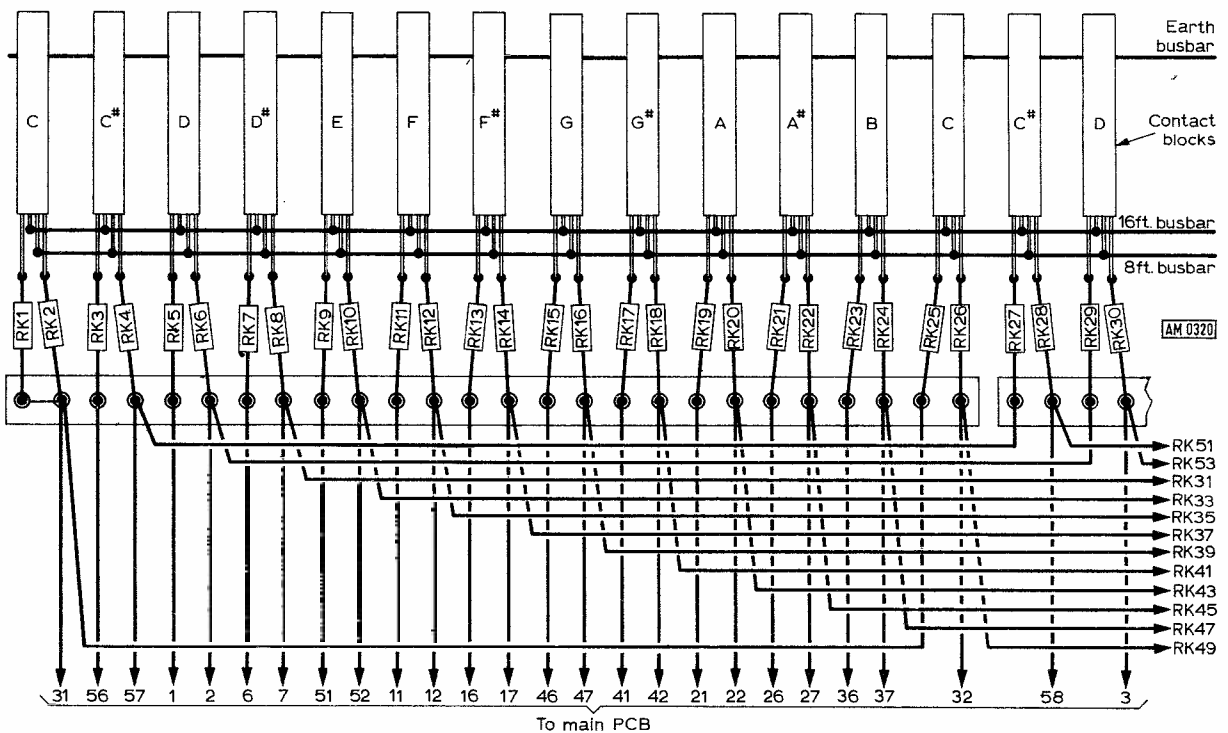


Fig. 11: Details of keyboard switch wiring, showing looping arrangements from one octave to another. This diagram shows only the bottom octave and the first two notes of the second octave, and therefore should be used in conjunction with the wiring schedule opposite.

Keyboard Resistors	PCB connections	Other keyboard connections	Note	Octave	Keyboard Resistors	PCB connections	Other keyboard connections	Note	Octave
RK1	31 ↑	RK25	C 16ft	* ↑	RK51	— ↑	—	C [♯] 16ft	↑
RK2	31 ↓	RK25	C 8ft		RK52	59 ↑	RK75	C [♯] 8ft	
RK3	56 ↓	—	C [♯] 16ft	Bottom octave	RK53	— ↑	—	D 16ft	↑
RK4	57 ↓	RK27	C [♯] 8ft		RK54	4 ↑	RK77	D 8ft	
RK5	1 ↓	—	D 16ft	Middle 'C' at 8ft pitch	RK55	— ↑	—	D [♯] 16ft	↑
RK6	2 ↓	RK29	D 8ft		RK56	9 ↑	RK79	D [♯] 8ft	
RK7	6 ↓	—	D [♯] 16ft	Middle 'C' at 16ft pitch	RK57	— ↑	—	E 16ft	↑
RK8	7 ↓	RK31	D [♯] 8ft		RK58	54 ↑	RK81	E 8ft	
RK9	51 ↓	—	E 16ft	Middle 'C' at 16ft pitch	RK59	— ↑	—	F 16ft	↑
RK10	52 ↓	RK33	E 8ft		RK60	14 ↑	RK83	F 8ft	
RK11	11 ↓	—	F 16ft	Middle 'C' at 16ft pitch	RK61	— ↑	—	F [♯] 16ft	↑
RK12	12 ↓	RK35	F 8ft		RK62	19 ↑	RK85	F [♯] 8ft	
RK13	16 ↓	—	F [♯] 16ft	Middle 'C' at 16ft pitch	RK63	— ↑	—	G 16ft	↑
RK14	17 ↓	RK37	F [♯] 8ft		RK64	49 ↑	RK87	G 8ft	
RK15	46 ↓	—	G 16ft	Middle 'C' at 16ft pitch	RK65	— ↑	—	G [♯] 16ft	↑
RK16	47 ↓	RK39	G 8ft		RK66	44 ↑	RK89	G [♯] 8ft	
RK17	41 ↓	—	G [♯] 16ft	Middle 'C' at 16ft pitch	RK67	— ↑	—	A 16ft	↑
RK18	42 ↓	RK41	G [♯] 8ft		RK68	24 ↑	RK91	A 8ft	
RK19	21 ↓	—	A 16ft	Middle 'C' at 16ft pitch	RK69	— ↑	—	A [♯] 16ft	↑
RK20	22 ↓	RK43	A 8ft		RK70	29 ↑	RK93	A [♯] 8ft	
RK21	26 ↓	—	A [♯] 16ft	Middle 'C' at 16ft pitch	RK71	— ↑	—	B 16ft	↑
RK22	27 ↓	RK45	A [♯] 8ft		RK72	39 ↑	RK95	B 8ft	
RK23	36 ↓	—	B 16ft	Middle 'C' at 16ft pitch	RK73	— ↑	—	C 16ft	↑
RK24	37 ↓	RK47	B 8ft		RK74	34 ↑	RK97	C 8ft	
RK25	— ↓	—	C 16ft	Middle 'C' at 16ft pitch	RK75	— ↑	—	C [♯] 16ft	↑
RK26	32 ↓	RK49	C 8ft		RK76	60 ↑	—	C [♯] 8ft	
RK27	— ↓	—	C [♯] 16ft	Middle 'C' at 16ft pitch	RK77	— ↑	—	D 16ft	↑
RK28	58 ↓	RK51	C [♯] 8ft		RK78	5 ↑	—	D 8ft	
RK29	— ↓	—	D 16ft	Middle 'C' at 16ft pitch	RK79	— ↑	—	D [♯] 16ft	↑
RK30	3 ↓	RK53	D 8ft		RK80	10 ↑	—	D [♯] 8ft	
RK31	— ↓	—	D [♯] 16ft	Middle 'C' at 16ft pitch	RK81	— ↑	—	E 16ft	↑
RK32	8 ↓	RK55	D [♯] 8ft		RK82	55 ↑	—	E 8ft	
RK33	— ↓	—	E 16ft	Middle 'C' at 16ft pitch	RK83	— ↑	—	F 16ft	↑
RK34	53 ↓	RK57	E 8ft		RK84	15 ↑	—	F 8ft	
RK35	— ↓	—	F 16ft	Middle 'C' at 16ft pitch	RK85	— ↑	—	F [♯] 16ft	↑
RK36	13 ↓	RK59	F 8ft		RK86	20 ↑	—	F [♯] 8ft	
RK37	— ↓	—	F [♯] 16ft	Middle 'C' at 16ft pitch	RK87	— ↑	—	G 16ft	↑
RK38	18 ↓	RK61	F [♯] 8ft		RK88	50 ↑	—	G 8ft	
RK39	— ↓	—	G 16ft	Middle 'C' at 16ft pitch	RK89	— ↑	—	G [♯] 16ft	↑
RK40	48 ↓	RK63	G 8ft		RK90	45 ↑	—	G [♯] 8ft	
RK41	— ↓	—	G [♯] 16ft	Middle 'C' at 16ft pitch	RK91	— ↑	—	A 16ft	↑
RK42	43 ↓	RK65	G [♯] 8ft		RK92	25 ↑	—	A 8ft	
RK43	— ↓	—	A 16ft	Middle 'C' at 16ft pitch	RK93	— ↑	—	A [♯] 16ft	↑
RK44	23 ↓	RK67	A 8ft		RK94	30 ↑	—	A [♯] 8ft	
RK45	— ↓	—	A [♯] 16ft	Middle 'C' at 16ft pitch	RK95	— ↑	—	B 16ft	↑
RK46	28 ↓	RK69	A [♯] 8ft		RK96	40 ↑	—	B 8ft	
RK47	— ↓	—	B 16ft	Middle 'C' at 16ft pitch	RK97	— ↑	—	C 16ft	↑
RK48	38 ↓	RK71	B 8ft		RK98	35 ↑	—	C 8ft	
RK49	— ↓	—	C 16ft	Middle 'C' at 16ft pitch					↑
RK50	33 ↓	RK73	C 8ft						

Main PCB to keyboard wiring schedule. Refer to Fig. 11 to begin with, in order to start the process going. Once begun, the wires going to the PCB, and the loop wires between tags, will follow in a logical sequence, as the wiring schedule above shows.

* Due to divider limitations, this note is the same on both 8ft and 16ft pitches.

exactly on the centre lines already drawn. Do not try gluing the block corresponding to the central "C" of the keyboard at this stage because it will be straddling a joint between two of the boards. NOTE; if fast-setting epoxy is being used do not mix up too much at a time because it will be found that it takes about ten minutes to position the twelve contacts on each board and the glue will be starting to go off as the first board is finished.

Set the contact assemblies to one side for the glue to harden. When they are really firm, drill a hole between the outer pair of contacts on each board to take self-tapping fixing screws. Next, offer the boards up to the keyboard so that the 'a' and 'd' wires of each contact block exactly rest over their corresponding actuating links. Press the boards down against the restraining action of the springiness in the contact wires and mark through the screw holes on to the metalwork of the keyboard frame. Again remove the boards and **very carefully** drill self-tapping holes in the metal where marked; do not allow the drill to break through the metal in an uncontrolled manner as damage may be caused to the underside of the plastic-covered keys.

Before screwing the contacts into place butt the two centre boards together on a flat surface and glue the final contact block across the butt joint. For added rigidity it is worth running a thin fillet of resin down each side of this block. Let this set really hard and then carefully screw the two central boards into place under the keyboard.

CONTACT EARTHING

Take two of the palladium rods and by carefully lifting each pair of 'a' and 'd' contacts, pass the rods through the earth busbar holes of the blocks that are in position—work from either end for each rod. Where the rods meet near the centre let them overlap by about 6mm ($\frac{1}{4}$ in) and solder them together. If necessary trim off the end of each rod so that they protrude by about 13mm ($\frac{1}{2}$ in) from the two extreme end contact blocks. Now screw the remaining two contact assemblies into position and insert the final two palladium rods from either end. Again, let them overlap the ends of the rods already in place and solder them together.

Now put bends in the shorter ends of the 'b' and 'c' wires for each contact block. The 'c' wire should be bent upwards until it is almost vertical and the 'b' wire up through about 45°. It will now be possible to get the test probes of a continuity test meter (ohms range on a multimeter) across the contact connections to test each one. This test is very important because clearing up problems at this stage will greatly simplify tests later on.

Although the keyboard must be kept upside down, make absolutely sure that none of the keys are depressed (use books to stand the keyboard off the working surface). Check that there is continuity between every 'a' and 'd' wire and the earth busbar. If any of them show open circuit, gently bend up the end of the contact wire that rests on the actuating link, so that the wire will settle itself further down inside the block assembly to touch the earthing bar.

Next, check that when a key is pressed there is continuity between the corresponding pairs of a/b and c/d contacts. Of course, continuity should be

broken when the key is released. Ideally, contact should be made when the key is depressed just over half of its total travel and the wires 'b' and 'c' carefully bent to allow this to happen. To make the organ easier to play each key should make contact at exactly the same degree of depression as its neighbour.

This completes the assembly and initial tests of the contacts. There is one more test to come but this must be reserved until some signals are available.

TAGSTRIP ASSEMBLY

Proceed to solder in the 8ft and 16ft busbars. These are simply lengths of straight tinned copper wire soldered to every contact block's 'b' or 'c' connection. One wire runs from the 'b' wire of the central "C" block and is soldered to every 'b' wire for the higher notes (this is the 8ft busbar for the top two octaves). Similarly another wire is run from the 'c' connection of the same block to all the higher note 'c' connections (16ft busbar for the top two octaves). Likewise two busbars run from the "B" below central "C" for 16ft and 8ft pitches for the bottom two octaves, a study of Fig. 12 should make these connections clear. Make sure that every connection is well made and that there are no dubious or dry joints.

It now remains to assemble the tag strips into position. The lengths of the strips should be such that there is a tag available for every 'a' and 'd'

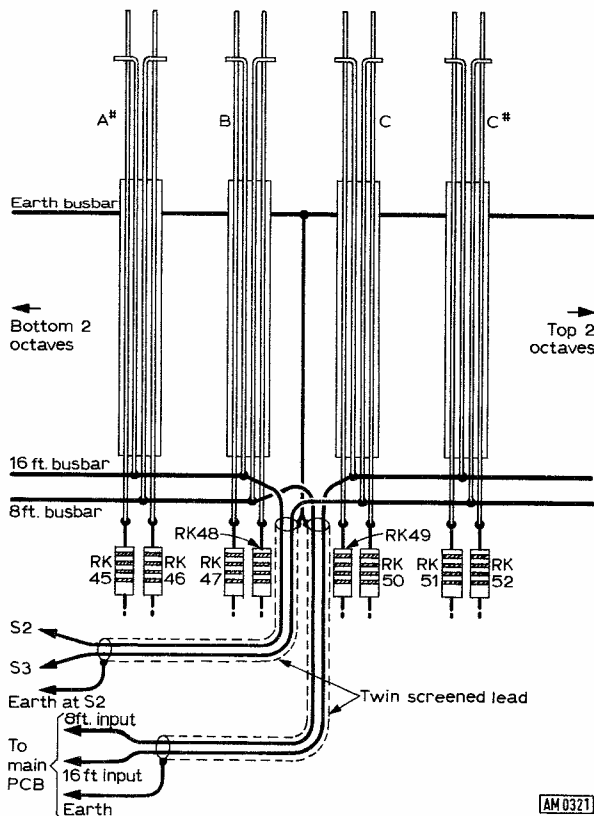


Fig. 12: Diagram showing orientation of contact blocks, busbars and wiring for the split keyboard switches.

New. Sinclair IC20.

20 watts stereo amplifier kit

for only £7.95 (plus VAT)



A build-it-yourself stereo power amplifier with latest integrated circuitry... 10 W RMS per channel output... full short-circuit and overheat protection.

Latest from Sinclair – the brand new IC20 power amp. It incorporates state-of-the-art integrated circuits – 2 monolithic silicon chips each containing the equivalent of over 20 transistors! These deliver 10 W per channel into 4 Ω speakers. And the IC20 has integral short-circuit protection and thermal cut-out – it's virtually indestructible!

How should I use the IC20?
Use the IC20 for converting your mono record player to stereo... for upgrading your existing stereo... for improving your car radio/tape player. The IC20 runs off a 9-24 V power supply. If you're running the IC20 off the mains, simply add a Sinclair PZ20 power supply (£4.95 plus VAT).

Using the IC20 to improve your car radio/tape player's quality and volume? Run the IC20 off the car battery direct. You don't need a separate power supply, and you're reducing the drain on the player's dry batteries.

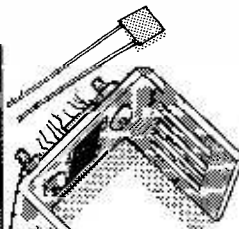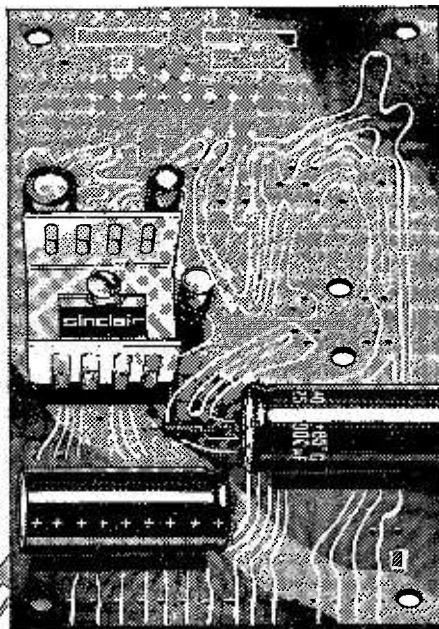A complete kit!
6 resistors
15 capacitors
2 ICs
2 heatsinks
Printed circuit board
Nuts and bolts



Typical performance of the IC20 stereo amplifier

Supply voltage: absolute maximum 24 V, minimum 6 V.
Current consumption: 24 V, no signal – 20 mA each channel.
18 V, 9 W into 4 Ω – 770 mA each channel.
Power output: 14 V supply, 4 Ω load, 10% distortion – 5½ W RMS per channel, 20 V supply, 4 Ω load, 10% distortion – 10 W RMS per channel.
Total harmonic distortion: at 50 mW, 4 Ω load, 20 V supply – less than 0.1%.
Input sensitivity: for 9 W into 4 Ω – 90 mV.
Frequency response: –3 dB at 40 Hz and 16 KHz.
Load impedance: 4 Ω or 8 Ω, but device is safe with any load.

Improve your audio equipment – today

Both the IC20 and the PZ20 are covered by the Sinclair one-year, no-quibble guarantee – if absolutely any defect arises, Sinclair will replace the whole unit – unconditionally.

You can find both the IC20 and the PZ20 at stores like Laskys and Henry's. But if you have any difficulty, send us a cheque direct and we'll send you an

IC20 and/or a PZ20 at once. 14-day money-back undertaking, naturally.

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: St Ives (0480) 64646

VAT Registration number: 213 8170 88.

sinclair

wire of all the contact blocks and ideally they should be in an exactly corresponding position on the opposite side of the pivot trough of the keyboard. In practice it is unlikely that tag strips having the correct pitch will be available but for the prototype it was found that standard "miniature" tag strips having 6mm ($\frac{1}{4}$ in) pitch would do, provided they were broken up into approximately octave lengths, the accumulative error in the pitch being taken up with a gap at the octave breaks.

One strip, to correspond to the bottom octave, should carry 26 tags and be centrally located between the "C" and the "C" an octave higher. A length of insulating strip (an old piece of blank Veroboard will do) should be cut and stuck with epoxy resin to the underside of the tag strip and, when set, the whole assembly should be glued into position opposite the contact blocks for the bottom octave. The ledge between the edge of the hinge and the pivot trough is an ideal place to stick the strips. The next three octaves should be dealt with by using strips each carrying 24 tags.

When all the tags are firmly glued into position all 98 keyboard resistors between the tags and their corresponding contact wires can be soldered in. All the resistors are 100k Ω and if an ohmmeter is available it's just as well to check each one before it is used. When using a large quantity of the same component there is always a chance that there may be an odd one out.

LOOP WIRING

Now comes the tedious bit. All the loop wires between the tags an octave apart must be connected up. Be very careful to start-off correctly by **triple checking** the following procedure.

Start by linking the two tags associated with bottom "C" and then run a lead of fine flexible insulated wire from the right hand pin of that pair to the left hand pin of the pair going to "C" an octave higher (i.e. from RK2 to RK25). Next, go from the right hand tag of bottom C# to the left tag of C# an octave higher (i.e. from RK4 to RK27). As long as the procedure is started off correctly there is little chance of error because the procedure is repetitive. There are no links to be made from top C# to higher frequency notes or any other notes in the topmost octave apart from C itself.

When making these loops cut the wires to exactly the right length and strip off exactly the right amount of insulation each time, then it will be found that the wires tuck down together very neatly. At the same time try to connect to the tags as far down them as possible (near to the insulating board) because there is still another wire to connect to most of the tags and space will be required to solder. Once the loops are in place the wires can be tied together to make the loom more robust, using waxed twine or alternatively black crochet thread.

PCB WIRING

The main wiring loom that runs from the printed circuit board to the keyboard has now to be constructed. Put the keyboard to one side and clear a nice amount of room to carry out the following

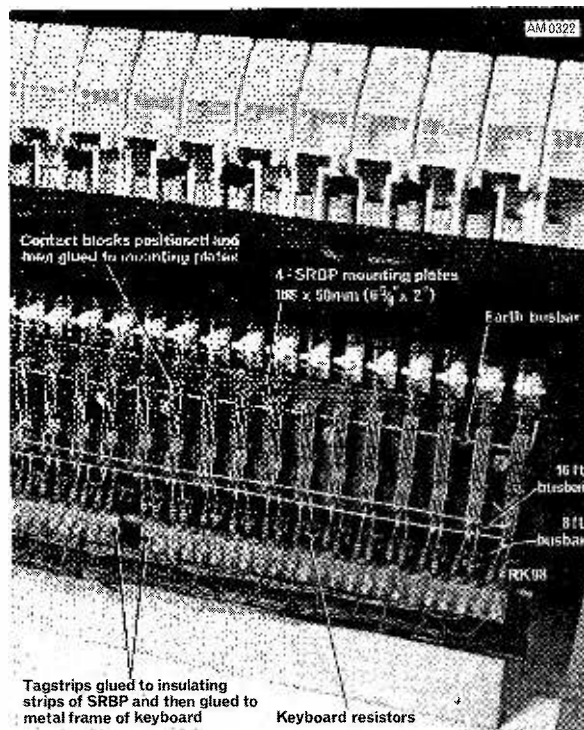


Fig. 13: Annotated photograph of prototype organ, showing close-up view of actual keyboard wiring and switch block assemblies.

wiring very methodically. First cut twelve 1.22m (4ft) lengths of fine connecting wire. Strip off 6mm ($\frac{1}{4}$ in) of insulation from one end of each piece. Pick up the lengths one at a time and with the first piece insert it through the hole numbered 35 on the PCB (insert it from the top side of the board) and solder it into place very carefully, taking care not to bridge any of the fine tracks with solder blobs. Cut off any excess wire at the joint.

This wire will, eventually, be connected to the tag going to the topmost "C" of the keyboard (at RK98); refer to the wiring schedule where it can be seen that the wire going into this point is numbered "35" to correspond with the printed board designations. Using sellotape and a small piece of paper make a flag carrying the number 35 and fix it to the free end of this wire. Take the next piece of wire and solder it to output 40 of the PCB and do likewise. Continue in this way, referring to the wiring schedule for details of which outlet the wire should go to and make sure that **every wire** has a correctly numbered flag on it.

Next, cut off twelve 910mm (3ft) lengths of wire and continue with the same procedure for the next octave down. When these are complete, cut a dozen wires each of 760mm (2 $\frac{1}{2}$ ft) in length, then 610mm (2ft) and finally 460mm (1 $\frac{1}{2}$ ft) for the bottom twelve notes. By the time the last dozen connections to the board are reached it will be found that the wires might tend to twist together. Try to avoid this happening. A good way is to let the wires

dangle over the edge of the table and make sure that they all run parallel from the board.

When this has been done, double check the wiring and ensure that there are no short circuits across the lead-outs on the board (use the ohmmeter as described in Part 2). As a check on the wiring, take each of the free ends of the wires in turn, bare them, one at a time, and check continuity between that wire and the numbered contact on the board that corresponds to the flag on the wire. Any dubious connections **must** be rectified.

Do not, at this stage, attempt to connect the free ends of the wires to the keyboard. Tie the groups of wires together into bundles of 12, corresponding to their different lengths, and then carefully put the board to one side and start building the cabinet. Final wiring is done when all the component parts are properly positioned within the final enclosure.

NOTES

On some main PCB layouts supplied by PW, it may appear that pins 1 and 2, reading clockwise, of IC5 are shorted together. This is incorrect, so on the PCB itself, very carefully run a sharp knife between the track of pin 1 and pad of pin 2 to clear.

The author has pointed out that the decoupling effect of R12 is excessive and can cause a supply line drop to the divider circuitry. This gives rise to apparent instability of the dividers at some settings of the Vibrato and Tune controls. It is therefore suggested that R12 be reduced to 10Ω or short circuited completely to overcome this problem.

In the components list published March 1975 values

of VR7 and C5 were incorrectly stated. They should have read:—

VR7 220kΩ miniature vert. preset.
C5 2200pF

The keyboard resistors designated R31-R128 in the components list, have been redesignated RK1-RK98 to simplify the description of the keyboard wiring.

Watford Electronics, 35 Cardiff Rd, Watford, Herts., have brought it to our attention that they are able to supply the complete semiconductor complement including the divider IC's AY-1-5051.

SCS Components of Northfield Industrial Estate, Beresford Avenue, Wembley, Middlesex, HA0 1YY, have informed us that as they are distributors for many semiconductor manufacturers, they too are in a position to supply the IC's for the Easybuild Organ. Telephone number for SCS components is 01-903 3168.

Just a quick reminder now for those readers interested in constructing their own PCB. PW is offering a full-size paper drawing of the PCB, showing track layout. For those who require one of these, please write, marking envelope "Easybuild Organ" to Practical Wireless, Fleetway House, Farringdon Street, London EC4A 4AD, and enclosing a PO or cheque for 25p and a 10 x 8in size S.A.E.

THE FINAL INSTALMENT, PART 4 NEXT MONTH, GIVES DETAILS OF CABINET CONSTRUCTION, FINAL WIRING UP AND TESTING.

MODEL TRAIN CONTROLLER—continued from page 24.

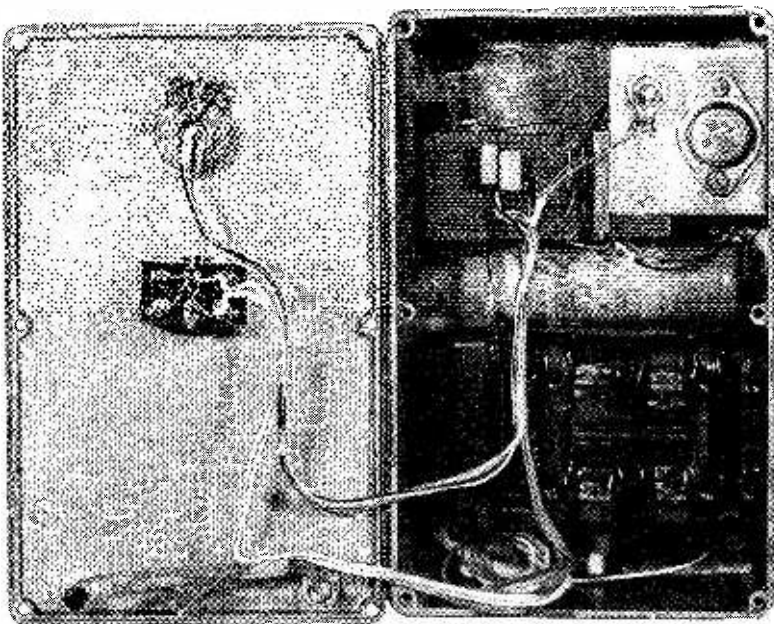



Fig. 7: Interior view of control box showing position of transformer, veroboard, output transistor, and, in the lid, the warning lights, reversing switch and control potentiometer.

LAYOUT

Component layout of the prototype is shown in Fig. 6, while Fig. 7 shows the diecast box, although any form of metal enclosure could be used. For children's use it was decided that the knob on VR1 should be as large as possible so that little fingers

could grasp it easily. After some use the reversing switch was replaced by a similar switch only this one had a centre off position making train driving much easier. With a little practice one can accelerate smoothly away from rest with quite large loads or even inch forwards and backwards with no difficulty.

PW

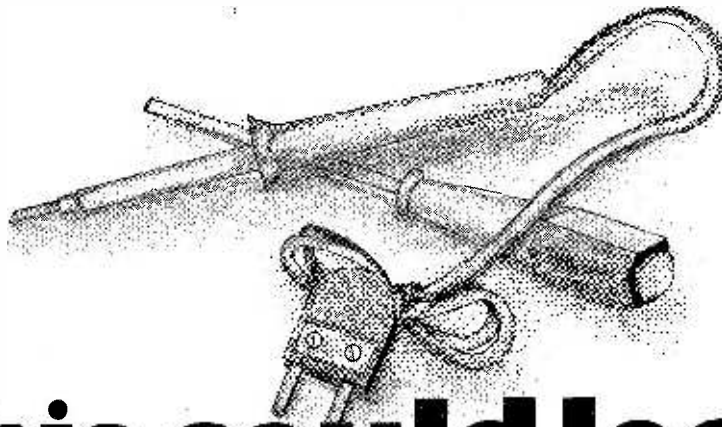

This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.


1

Build an oscilloscope.

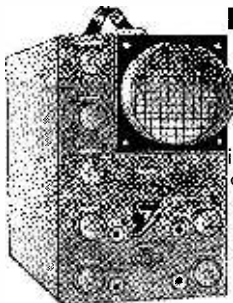

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2

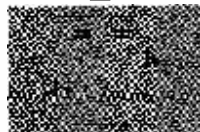

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3



Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS



FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

WAA

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept WL/55
P.O. Box 156, Jersey, Channel Islands.

NAME.....

ADDRESS.....

(Block caps please)



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£7-75
Baker Group 35 3, 8 or 15 ohm	£1-50
Baker Group 50/12 8 or 15 ohm	£12-50
Baker Deluxe 12" d/cone	£10-75
Baker Major " "	£8-50
Baker Regent " "	£7-75
Baker Superb	£14-50
Baker Auditorium 12	£12-50
Celestion M1000 horn	£10-50
Celestion PST8 for Unilux	£2-55
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G19C 8 or 15 ohm	£33-00
Coral 6 1/2" d/cone roll surr. 8 ohm	£10-55
Coral 8" d/cone roll surr. 8 ohm	£3-25
EMI 13 x 8 3, 8 or 15 ohm	£2-25
EMI 13 x 8 150 d/c 3, 8 or 15 ohm	£2-50
EMI 13 x 8 450 t/tw 8 ohm	£3-75
EMI 13 x 8 type 350 8 or 15 ohm	£8-25
EMI 13 x 8 20 watt base	£6-50
EMI 6 1/2" 93850 4 or 8 ohm	£3-00
EMI 5" 98132CP 8 ohm	£2-50
EMI 8 x 5 d/cone, roll surr 10 watt	£2-50
EMI 2 1/2" tweeter 97492AT	£65
Eagle DT33 30 watt tweeter	£5-45
Eagle HT15 horn tweeter	£3-90
Eagle CT5 cone tweeter	£1-75
Eagle CT10 tweeter 8 or 16 ohm	£2-55
Eagle MHT10 horn tweeter	£3-80
Eagle crossover CN23, CN28, CN216	£1-50
Eagle FR4	£5-30
Eagle FR65	£8-35
Eagle FR8	£10-95
Elac 9 x 5, 59RM109 15 ohm,	
59RM114 8 ohm	£2-80
Elac 6 1/2" 6RM171 d/c roll surr.	£3-50
Elac 6 1/2" 6RM220 d/cone	£2-85
Elac 4" tweeter TW4	£1-21
Elac 10" d/cone 10RM239 8 ohm	£2-45
Elac 8" 8CS175 3 ohm	£2-50
Fane Pop 15 watt 12"	£5-25
Fane Pop 25/25 25 watt 12"	£7-25
Fane Pop 40 watt 10"	£18-50
Fane Pop 50 watt 12"	£12-50
Fane Pop 55 12" 50 watt	£13-25
Fane Pop 60 watt 15"	£13-25
Fane Pop 100 watt 18"	£24-50
Fane Crescendo 12A 100 watt 12"	£29-00
Fane Crescendo 12B bass	£29-00
Fane Crescendo 15" 100 watt	£36-00
Fane Crescendo 18" 150 watt	£51-95
Fane 801T 8" d/c roll surr.	£7-00
Fane 807T 8" d/c roll surr.	£3-85
Fane 808T 8" d/c	£2-75
Fane 701 twin ribbon horn	£35-00
Fane 910 horn	£12-75
Fane 920 horn	£33-00

Goodmans 8P 8 or 15 ohm	£5-00
Goodmans 10P 8 or 15 ohm	£5-30
Goodmans 12P 8 or 15 ohm	£12-95
Goodmans 12P-D 8 or 15 ohm	£16-75
Goodmans 12P-G 8 or 15 ohm	£15-75
Goodmans Audiomax 12AX 100 watt	£37-50
Goodmans Audiomax 15AX	£40-25
Goodmans 15P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£36-00
Goodmans Midax 750	£16-00
Goodmans Axent 100 tweeter	£7-25
Goodmans Audiom 100 12"	£12-00
Goodmans Axion 401 12"	£17-25
Goodmans Twinaxiom 5	£8-25
Goodmans Twinaxiom 10	£9-00
Kef T27	£5-25
Kef T15	£6-00
Kef B110	£7-25
Kef B200	£35-25
Kef B139	£14-25
Kef DN8	£2-00
Kef DN12	£4-95
Kef DN13	£3-30
STC4001G super tweeter	£6-19
Richard Allan CG8T 8" d/c r/surr.	£6-35
2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm	
2 1/2" 75 ohm	£50
7" x 4" 3 or 8 ohm	£1-40
8" x 5" 3 or 8 ohm	£1-50
10" x 6" 3, 8 or 15 ohm	£2-30

SPEAKER KITS

Baker Major Modute	each £10-75
Goodmans Mezzo	pair £45-00
Goodmans DIN 20	each £9-75
Helme XLK 25	pair £22-00
Helme XLK 30	pair £14-95
Helme XLK 50	pair £39-95
Keffit 1	each £20-95
Keffit 3	each £36-75
Richard Allan Twinkit	each £8-95
Richard Allan Triple 8	each £13-75
Richard Allan Triple	each £19-95
Richard Allan Super Triple	each £23-75
Wharfedale Linton 2 kit	pair £19-25
Wharfedale Glendale 3 kit	pair £34-50
Wharfedale Dovedale 3 kit	pair £52-50

PA/DISCO AMPLIFIERS

(carr. and ins. £1)	
Baker Major 100 watt	£49-75
Linear 30/40	£30-00
Linear 40/60	£35-00
Linear 80/100	£58-85
Linear 100 watt slave	£44-00
Eagle PA range in stock—ask for catalogue.	

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 39p each, speaker kits 75p each (£1.50 pair) tweeters and crossovers 20p.

ALL PRICES QUOTED INCLUDE VAT.

WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF
Discount Radio, PA, Hi-Fi: 10 Swan St. Wilmslow
Send stamp for free booklet "Choosing a Speaker"



Cassettes

The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!

	1	5	10
C80	37p	£1-80	£3-50
C90	50p	£2-48	£4-95
C120	63p	£3-10	£5-20

AGFA HIGH DYNAMIC SUPER

	1	5	10
C80+6	50p	£2-40	£4-70
C90+6	68p	£3-35	£6-00
C120	99p	£4-90	£9-80

AGFA STEREO-CHROM CHROMIUM DIOXIDE

	1	5	10
C80	85p	£4-20	£8-30
C90	£1-08	£5-35	£10-60

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO

(DEPT. PW)
10 SWAN STREET, WILMSLOW, CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

NEW SINCLAIR

IC20

AMPLIFIER KITS

Send SAE for free reprint of IC20 booklet and data on kits.

IC20 10+10 Watt stereo amplifier kit with free 16 page booklet and printed circuit £6-95 (82p)
PZ20 power supply kit for above £4-45 (65p)
VP20 stereo volume, tone control and preamp kit for magnetic and ceramic pickups for IC20 £4-95 (72p)

SINCLAIR CALCULATORS AND MULTIMETERS



Sinclair Digital Multimeter DM2 £58-95 (£5-26)
Sinclair Scientific Assembled £16-95 (£1-70)
Cambridge Assembled £10-50 (£1-20)
Cambridge Memory Assembled £14-95 (£1-60)

CALCULATOR POWER SUPPLY

This 6V 500mA model runs any Sinclair or other 6V calculator from the mains. Never buy batteries again! £3-10 (65p)

FERRANTI ZN414

IC radio chip with data £1-20 (25p). Also available kit of extra parts to complete a radio £2-55 (47p)
Send sae for free leaflet


SINCLAIR PROJECT 80

AFU £6-38 (78p)
Z40 £5-12 (68p)
Z60 £6-38 (78p)
Q16 £7-21 (95p)
PZ5 £5-11 (73p)
PZ6 £7-79 (94p)
PZ8 £7-36 (90p)
Decoder £7-75 (89p). Trans for PZ8 £3-85 (70p)
Tuner £11-62 (£1-42). Stereo 80 £11-62 (£1-42)
Project 805 £29-95 (£3-00)
Project 805SQ £33-95 (£3-30)
Project 80 SQ Quad Decoder £15-95 (£1-28)



SINCLAIR SUPER IC12

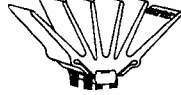6 Watt IC power amp and preamp. With 44 page booklet and printed circuit £1-80 (43p)



DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-80 (31p). Stereo model with balance control £3-90 (49p)

IC12 POWER KIT

Supplies 28V 0-5 Amps £3-07 (62p)

LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1-40 (44p). 5" x 8" 8 ohm £1-75 (57p)

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1-99 (50p). Stereo model £2-70 (36p). Type 2 for ceramic or crystal pickups. Mono 80p (23p). Stereo £1-60 (30p)

SEND SAE FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAINS


The most versatile battery eliminator ever offered. Switched output of 3, 4 1/2, 6, 7 1/2, 9 and 12V at 500 mA £3-90 (80p).



Other eliminators stocked:—
250mA:—3 way switched model giving 6, 7 1/2 and 9V £2-50 (65p).
50mA:— 4 1/2V £2-40 (40p), 6V £2-40 (40p), 9V £2-40 (40p), 7 1/2V cassette type £2-80 (50p). Double 4 1/2 + 4 1/2V £2-95 (50p). 6V + 6V £2-95 (50p), 9V + 9V £2-95 (50p).
500mA:— Heavy duty deluxe models 6V £3-10 (65p), 7 1/2V £3-10 (65p), 9V £3-10 (65p)

S-DECS AND T-DECS

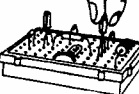S-DeC £1-98 (36p)
T-DeC £3-63 (52p)
µ-DeC A £3-99 (66p)
µ-DeC B £6-99 (86p)
IC carriers:—
16 dit: plain 8p (18p)
with socket £4-77 (28p)
10 TOS: plain 78p (18p). With socket £1-68 (27p)



SWANLEY ELECTRONICS

PO BOX 68, SWANLEY, KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and new VAT. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.

HAVE you ever driven a car in heavy mist or spotty rain (typical British weather!), and found that instead of providing a clear view the wipers merely smear the windscreen, making visibility even worse than ever? The reason for this is that the average car's windscreen wipers may function well in heavy rain, but, when it is only raining lightly not enough rain lands on the windscreen between one sweep of the wipers and the following one to lubricate the wiper blades as they travel across the screen.

The Car Wiper Delay Unit described here solves this problem and provides clear visibility in all types of rain. The wipers are allowed to sweep across the screen at their normal speed, but a delay is introduced, in between wiper sweeps, where the delay can be adjusted to suit the prevailing weather.

The circuit is suitable on all vehicles, whether positively or negatively earthed, equipped with

electrically driven self-parking wipers (i.e. virtually all vehicles, but apologies to owners of 100E's with vacuum driven wipers!).

CIRCUIT DESCRIPTION


The circuit is connected across the existing wiper switch as shown in Fig. 1, which shows the arrangement for a vehicle having a negative earth.

The wiper motor is normally connected via the ignition switch to the live terminal of the car battery, so that when the wiper switch is closed the other motor lead is earthed and the wipers are brought into operation.

A rotary switch is connected to the wiper mechanism which ensures that when the wipers are switched off the motor continues to run until the wiper blades are arked. This self-parking mechanism operates in conjunction with the Wiper Delay Unit and enables a cheap thyristor to be used in place of the relay which is usually found in simple timing circuits.

When S1 is closed, 12 volts appears across the circuit since there is a low resistance path through the motor armature to the battery live terminal and the current drawn by the circuit during the delay period is negligible.

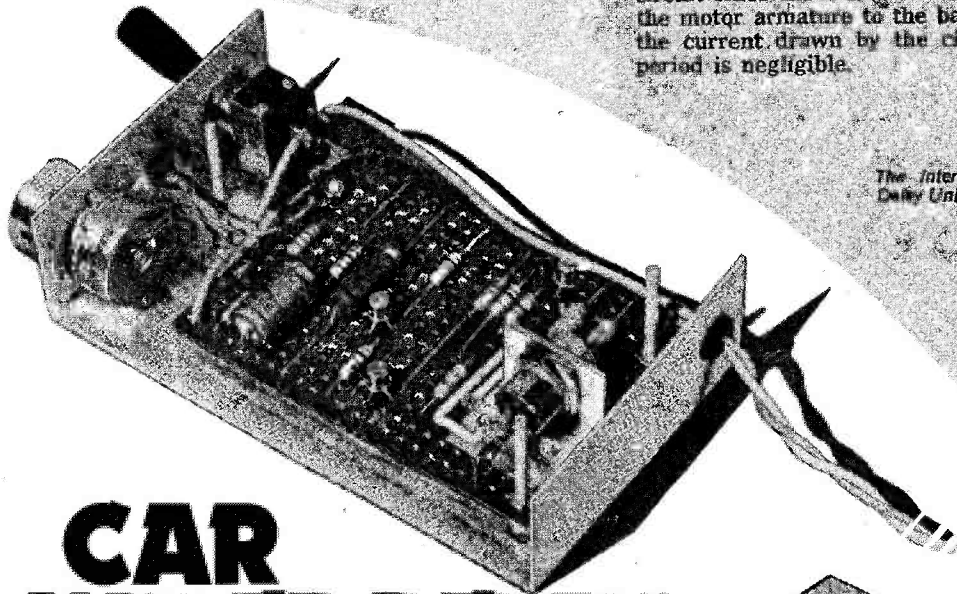The internal view of the Car Wiper Delay Unit is shown left



CAR WIPER DELAY UNIT

The completed unit with the cover fitted is shown right



J. B. HARVEY B. Sc.

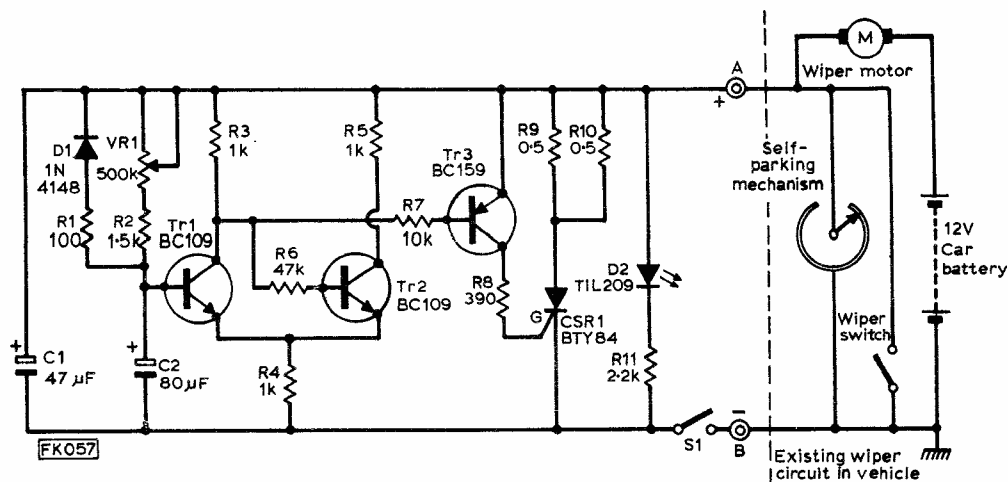


Fig. 1: The circuit diagram of the Car Wiper Delay Unit. The circuit to the right of the dotted line is typical for a car with negative earth and the wiper switch in the earth lead

The voltage across C2 is initially zero but rises exponentially due to the charging current through VR1 and R2. This voltage is monitored by the level detecting circuit consisting of Tr1 and Tr2.

SCHMITT TRIGGER

This part of the circuit is known as a "Schmitt trigger" and operates as follows. Initially Tr1 is cut off, since the voltage on C2 is low. Tr1 collector is high and is coupled via R6 to Tr2 base, so that Tr2 is turned hard on.

Since R4 and R5 are equal, the voltage at the junction of the two emitters is half the supply voltage i.e. 6 volts. Now when the voltage on the base of Tr1 approaches $(6 + V_{be})$ volts, i.e. 6.6 volts, Tr1 begins to conduct. Its collector voltage falls and Tr2 is turned off, causing Tr1 to conduct even harder until it is saturated.

The negative going voltage at the collector of Tr1 is applied via R7 to the base of Tr3, which amplifies the current available to drive the gate of the thyristor CSR1; thus the thyristor conducts and the wiper motor operates. R9 is included to protect the thyristor against current surge when the motor first conducts.

THYRISTOR OPERATION

When a thyristor is made to conduct it will continue to do so even if the gate current is removed until the anode current falls below a threshold known as the "holding current". Consequently if the Delay Unit were being used to drive, say, a lamp then the lamp would remain on until the current were interrupted by opening S1, and similarly if the wipers were not of the self-parking variety then they would continue to function. However, at this point the self-parking mechanism comes to the rescue.

A fraction of a second after the thyristor conducts the self-parking switch makes contact, shorting out points A and B. The switch thus diverts the motor current from the thyristor and removes the gate current, turning off the thyristor but allowing the wipers to complete one sweep of the windscreen. In addition C2 discharges through D1 and R1 in readiness for the next delay period. (R1 limits the discharge current to a safe value for D1.)

At the end of the sweep the self-parking mechanism switches off the wiper motor, 12 volts

is restored across the circuit and the cycle of events is repeated.

Capacitor C1 is included to protect the circuit against possible voltage spikes from the car's ignition circuits, although no trouble has been experienced in the prototypes.

DELAY PERIOD

The delay period is determined by the time taken for the voltage on C2 to reach 6.6 volts, and is approximately equal to $0.7 \times CR$ (C in farads, R in ohms). Thus with the components specified the maximum delay is 28 seconds.

A delay of several minutes may be obtained by increasing C2; e.g. 500 μ F gives three minutes. However, such a long delay is rarely required and adjustment in the most useful range of approximately one to ten seconds becomes very critical. VR1 should not be increased in value to obtain a greater delay since there may then be insufficient base current to turn on Tr1.

★ components list

Resistors

R1 100 Ω	R7 10k Ω
R2 1.5k Ω	R8 390 Ω
R3 1k Ω	R9 0.5 Ω 3W
R4 1k Ω	R10 0.5 Ω 3W
R5 1k Ω	R11 2.2k Ω
R6 47k Ω	

All resistors 5% $\frac{1}{4}$ W except where stated
VR1 500k Ω linear.

Capacitors


C1 47 μ F	25V elect.
C2 80 μ F	25V elect.

Semiconductors

Tr1 BC109 (or BC149)
Tr2 BC109 (or BC149)
Tr3 BC187 (or BC159)
D1 1N4148
D2 TIL209 light emitting diode
CSR1 BTY84 100V 12A (Henry's Radio)

Miscellaneous

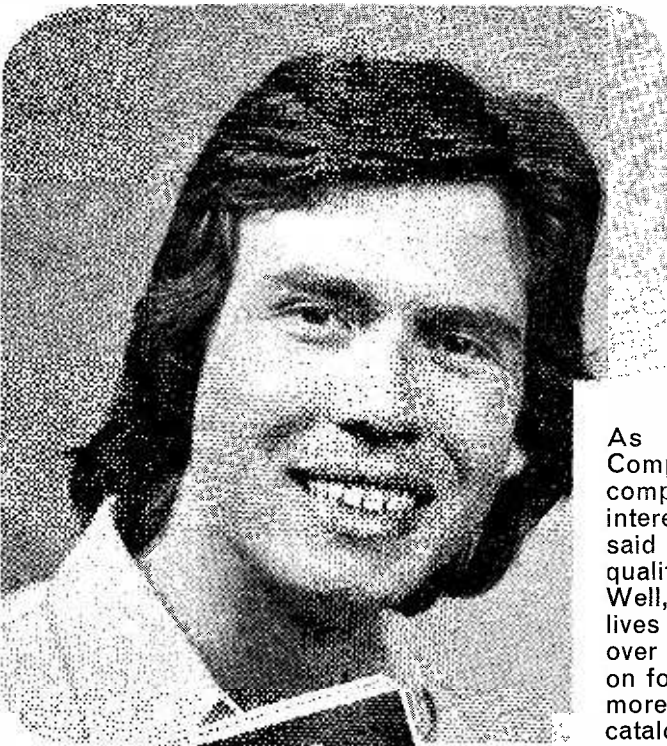Veroboard 63 x 95mm ($2\frac{1}{2}$ x 3 $\frac{3}{8}$ in), 0.15in matrix.
S1 Single pole on/off switch
Knob. Materials for case and heatsink.



kom-pre-hense-iv

As no doubt you've noticed, Home Radio Components Ltd. are always going on about how comprehensive their catalogue is! So out of interest I looked up the word in a dictionary. It said . . . "KOM-PRE-HENSE-IV, having the quality of comprising much; extensive; full."

Well, on that definition, the catalogue certainly lives up to their claim. In its 240 pages there are over 6,000 items listed and there must be getting on for a couple of thousand illustrations. What's more, to make it easy to find your way around, the catalogue is most carefully indexed, with cross references where necessary. Recently someone at Home Radio Components told me that they've sold over 150,000 copies of the catalogue. I'm not surprised! They also mentioned that many professional people in the world of radio and electronics regard it as a standard reference work. I don't know about the professionals, but I know lots of we amateur freaks would be quite lost without it.

But perhaps you have managed to struggle along so far without this invaluable catalogue. Why hamper yourself any longer? *Send off the coupon below with cheque or P.O. for 98 pence.* (65p plus 33p postage & packing). Every catalogue contains 14 vouchers each worth 5p when used as directed. This means that you can recover 70 pence, the whole cost of the catalogue plus 5p toward the postage. Needless to say, the catalogue is backed by a really good Mail Order Service.

65p. plus 33p POST AND PACKING

Send off the coupon today. It's your first step to solving your component buying problems.

The price of 98p applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME

ADDRESS

.....

.....

**HOME RADIO (Components) LTD., Dept. PW,
234-240 London Road, Mitcham, Surrey CR4 3HD**




(Regn. No.
London 912966)

HOME RADIO (Components) LTD Dept. PW, 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

LISTEN TO

CODAR® THE WORLD!

★**CR70A**

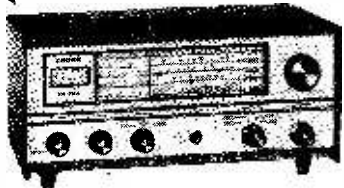

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning. Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ IMPORTANT NOTE

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your receipt, sent by return.

* Send now for details of educational and O.A.P. discounts!



ON THE DESIGN STAFF—
G3SZM G3IRE

CODAR®

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX
WORLD-WIDE MAIL ORDER—EXPORT QUOTES FREE. BNI5 - 8TZ




★**MADE TO ORDER!**

£37-15!

VAT PAID
CARR. 85p

P.R.40★

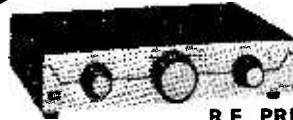

£10-93!

VAT PAID
CARR. 32p

R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee . . .



MULTIBAND-6★

SHORT WAVE RECEIVER KIT

£16-90! CARR. 43p

All transistor T.I.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship / Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandspread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

Principles of Transistor Circuits-5th Edition

S. W. AMOS

- Provides a clear and comprehensive account of the circuit applications of the sophisticated transistor devices now available.
- The edition has been revised to include important trends in the use of field effect transistors and integrated circuits in sound, television and digital equipment.
- Invaluable to aspiring circuit designers, students, home constructors; indeed anyone concerned with the applications of transistors should find the book of immense value.

320 pages 216 x 138 mm Illustrated ISBN 0 408 00160 7 (Cased) £5.50—0 408 00161 5 (Limp) £3.20

Beginner's Guide to Transistors—2nd Edition

J. A. Reddihough, revised by R. Sinclair

- A full revision has ensured that this second edition incorporates the latest developments in integrated circuits; logic principles have been introduced.

160 pages 192 x 126 mm Illustrated ISBN 0 408 00145 3 £1.80 February 1975

ORDER NOW FROM YOUR LOCAL BOOKSELLER

For full details of our books on Radio and Television write or telephone

Newnes-Butterworths, Borough Green, Nr. Sevenoaks, Kent

Telephone: Borough Green 884567—Ansacone: Borough Green 882442—Telex: 95678



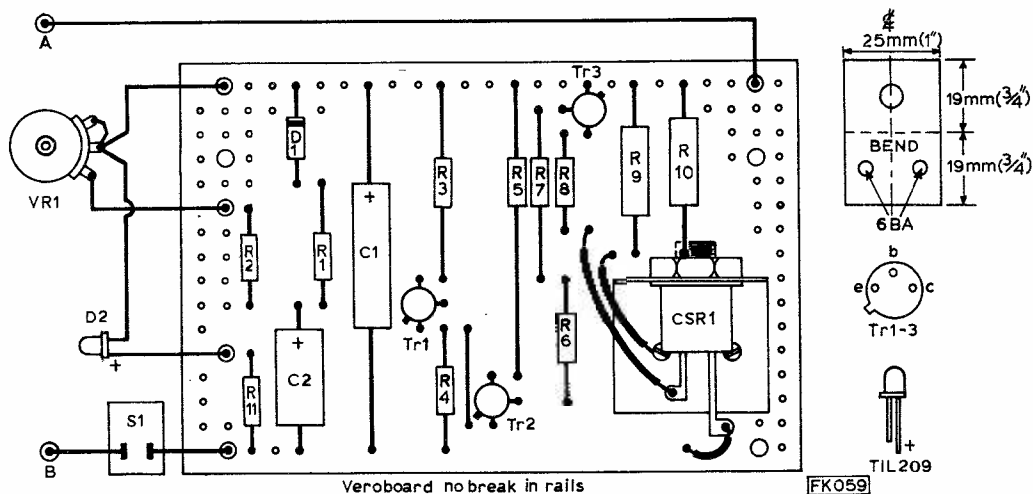


Fig. 2: Layout of the components on the Veroboard panel and interwiring details. The copper strips run horizontally. The connection to the thyristor anode is made via a solder tag on the heatsink

An indicator is optional, but useful to show when the Wiper Delay Unit is in operation: a small red light-emitting diode D2 was used in the prototype. LEDs have now become comparable in price to a bulb plus bulb-holder and are widely advertised; the one used in the prototype came complete with a little plastic clip for panel mounting.

A bulb could, of course, be used instead, but note that since the indicator will turn off during the course of each wiper sweep, the bulb or LED should be run at a reduced current to avoid distraction at night: hence the high value for R11.

CONSTRUCTION

The circuit may conveniently be constructed on a $3\frac{3}{4} \times 2\frac{1}{2}$ inch piece of 0.15 inch pitch Veroboard. If the layout in Fig. 2 is used then no track breaks will be necessary to accommodate the circuit, although care must be taken to ensure that any nuts and bolts used do not make contact with the tracks.

The thyristor is mounted on the board using a small bracket. Note that although the wiper motor typically draws 5A the thyristor and R9, R10 run quite cold, because they only conduct for a fraction of a second during each wiper sweep, the self-parking switch taking over for the rest of the sweep.

The thyristor specified is rated at 12A which is over twice the current drawn in this circuit. However it is readily available for less than 50p which is considerably cheaper than any thyristor in the 5A range, with the added bonus of substantial overload protection.

INSTALLATION

The method used to install the completed circuit will depend on the vehicle for which it is intended. The prototype was mounted in a simple box formed from two pieces of aluminium sheet and sprayed with aerosol paint to match the car: if this is done then it is a good idea to rough up the aluminium surface with fine glasspaper to improve paint adhesion. Alternatively the controls may be mounted directly onto the dashboard and connected to the circuit board by flying leads.

The circuit should be constructed so as to be entirely isolated from the car chassis, the earth connection being provided by a single lead from point A or B, depending on the polarity of the car's electrical system.

In view of the current drawn fairly thick wire should be used to connect up the Wiper Delay Unit to the vehicle. The circuit is identical for systems of either polarity, only the connections being different (see Fig. 3). Thus it is not necessary to construct another circuit if you exchange your elderly positively earthed car for a newer model with a negative earth. Neither is it necessary to have one side of the circuit at chassis potential: so long as the circuit is fully isolated from the chassis it may be used with a vehicle whose wiper switch is connected to the live side of the wiper motor, provided of course that the wipers are self-parking.

The circuit will work without modification in vehicles using 6 volt or 24 volt electrical systems, the delay time being almost independent of supply voltage.

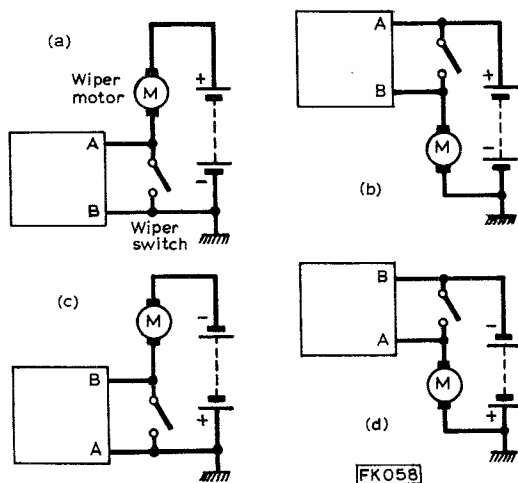


Fig. 3: Connections for the four types of wiper arrangements Negative earth encountered. (a) Negative earth, wiper switch in earth lead (b) normally earth, wiper switch in live lead (c) Positive earth, wiper switch in earth lead (d) Positive earth, wiper switch in live lead.

HOTLINES

ON RECENT DEVELOPMENTS

WATCH OUT

A few Ginsbergs' back I mentioned that it might be prudent to wait for a while if you were intending to purchase a digital watch. I advised this on inside information that a big digital watch price war was imminent in the US. Seems I was right. At a recent trade show, some watches were offered at \$75 (that's about £30 if you reckon \$2.5 to the £1). Bowmar has already introduced a two button watch with an led readout which gave the date in addition to the more usual hours and minutes. Note:—Bowmar is currently filing for bankruptcy in the US and rumours of a \$20 million loss are circulating and have already been reported in print in the States.

Keep an eye out for Timex who are already well-known for low-priced time pieces. They already have a liquid crystal watch with a less than \$90 price tag. I still say hang on—they should go a lot lower yet (more inside information; besides, remember calculators!).

ERE EAR!

How many times have you come across the sentence "Have you heard...?", or "Did you hear about... etc etc. Sad to say many human beings haven't heard—they're deaf. Way down in the inner ear are minute hair cells each of which "tunes" to different frequencies. Its a simple case of no hairs no hearing, or maybe the hairs are damaged or useless. Then, someone remembered that all the ear does, hair cells and all, is to feed minute electrical signals to the auditory nerve and hearing is established. Somewhere along the line it was reasoned that if only those minute signals could be correctly fed to the auditory nerve, the brain would never know what was sending them. Provided they were right, the brain would believe that it was receiving them from its old friend the ear.

Enter electronics. A system was devised for sending the necessary impulses to the auditory nerve. The results were successful yet disappointing. The upper frequency limit appeared to be around 300Hz and that certainly wouldn't fool the

brain. It wouldn't even permit the interpretation of speech.

Then, some scientists at Stanford University took an interest, and they've come up with—yes, you've guessed it, an electronic earhole; and it looks like being a winner. What was needed, they claimed, was not a single electrode, but four electrodes. The new circuit, a mixture of thick film and CMOS, promises to offer to the brain, frequencies up to 4kHz. Now this isn't good enough for listening to hi fi, but it does cover all the speech frequencies and if you've previously lived in a completely silent world that 4kHz upper limit is really something.

The tiny circuit is implanted but no electrodes are inserted through the skin. Instead, the inputs to the implant are sent over a minute radio link. The link also supplies the few milliwatts of power needed by the circuitry on the implant itself. The information as to which electrode receives which impulses, their amplitude, duration etc. is sent in using an ultrasonic link.

Externally, the "patient" carries a package which houses the microphone, ultrasonic link, the coding circuitry etc. By the end of this year the scientists hope to have the first "patient" hearing. It would, of course, be so easy to finish this story with a funny line, but I think a sincere round of applause would be much better.

ELECTRONIC FRANKENSTEIN

Still talking matters medical, I'm very interested to hear about Bell Labs and its involvement with lead poisoning. The Labs have come up with a very quick and easy way to check for lead poisoning and the instrument only takes one minute to perform the necessary tests. It requires only a tiny drop of blood, too. Once inside the machine, the blood sample is illuminated by a beam of blue light and the light emission is carefully measured. If excessive amounts of lead are present the blood will give off a red light which is of a specific frequency. The redness, or rather its intensity, is shown on a digital meter. Strangely,

the red light comes from a substance which the blood's haemoglobin makes, when lead is present, called zinc protoporphyrin. The instrument is so sensitive that it can detect down to five trillionths of a gram of zinc protoporphyrin in the single drop of blood required for the sample.

A very interesting aspect of this story is just why Bell Labs is bothering with human blood? Just what has blood got to do with electronics?

According to Bell, the scientists are extremely interested in understanding the electronic properties of large molecules. This interest extends to those molecules which control complicated metabolic and neurological processes in biological systems. Pity Baron Frankenstein isn't still alive unless...!

TIMER I.C.

It looks like another IC has arrived just to confuse the electronics-orientated amateur photographer, especially if he intends making up an electronic timer. Perhaps one of the most popular is the Signetics 555 chip. Now, Ferranti has launched its ZN1034E. The IC is a mixture of digital and linear technology all on the same chip. The company claims that only three external components are required and that accurate time periods provide ranges from milliseconds to weeks.

The chip contains an oscillator whose frequency is determined by an external capacitor and resistor. Output from the oscillator is fed to a divide-by-12 digital divider which can provide timing intervals up to 7,500 times the original time constant of the external capacitor and resistor. At 5V the chip consumes a modest 5mA and has a regulator built in. Temperature stability is claimed to be less than 0.01% /°C. The price of a one-off is £2.99p from one of the company's many distributors—NOT from Ferranti direct.

Ginsberg



Which?


Get them all with our
A relatively low cost, simple generator producing square, sine or sawtooth waveforms from 0.1Hz to 100kHz plus a further range giving useful signals up to 1MHz. Calibrated decade switches make the instrument particularly useful when used with an oscilloscope. Output may be positive or negative-going or symmetrical about earth. Output level, from a high impedance source, is 10V peak-to-peak, through an attenuator in steps down to 1mV.

**IN NEXT MONTH'S
PRACTICAL
WIRELESS**

DIGITAL WAVEFORM GENERATOR



Also DIRECT CONVERSION RECEIVER

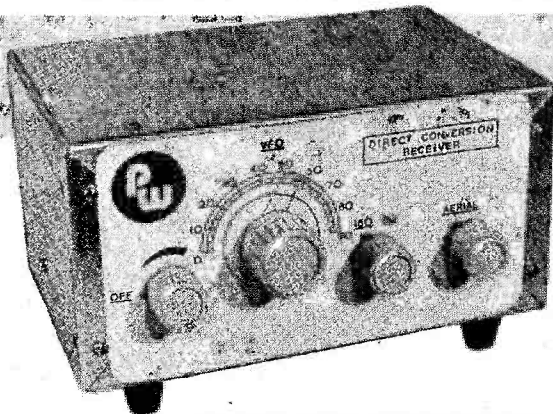

Although direct conversion receivers have been around for a long time published designs have been few. Ours covers the 160 and 80m amateur bands but the range can be extended quite easily.

and Repairing Hi-Fi Amplifiers

As the author points out, there is a right way and a wrong way to service solid state audio amplifiers, and the wrong way can prove expensive! We indicate the right way.

DON'T MISS THIS ISSUE! ~ ON SALE IN MAY

Pw APOLLO series

Part 1

TRIPLE VARICAP MEDIUM WAVE TUNER/RECEIVER



W. POEL*

THE variable capacity effect in silicon junction diodes has been known and exploited for some years. So far the use of varicap diodes has been restricted to UHF and VHF applications owing to the low capacitances of the available diodes. Now, for the first time, Motorola have developed an integrated circuit consisting of three varicap diodes whose capacitance values make them suitable for use at MW and SW frequencies.

This article describes a tuner which can be built using the new device. Various methods will be suggested for obtaining the tuning voltage so that the complete receiver can be used in a number of different ways including a domestic tuner amplifier, a portable receiver and a car radio.

VARICAP DIODE THEORY

The semiconductor diode is made up from two types of semiconductor material: one known as p-type which has a deficiency of free electrons (or an excess of "holes") and the other known as n-type which has an excess of free electrons.

When the two types are brought into contact an energy exchange takes place as the materials try to establish an electrical equilibrium. Some of the electrons move across the junction to fill the holes. This action produces an area devoid of free electrons or holes which is known as the depletion layer. With each side of the barrier at an opposite charge to the other, each side can be viewed as the plate

* *Ambit International.*

of a capacitor with the depletion layer forming the dielectric (see Fig. 1.1).

If a reverse bias is placed across the diode, charges will be drawn away from junction increasing the width of the depletion layer. In other words the plates of the capacitor will be moved apart, thus decreasing the capacitance. The diode may therefore be viewed as a voltage variable capacitor.


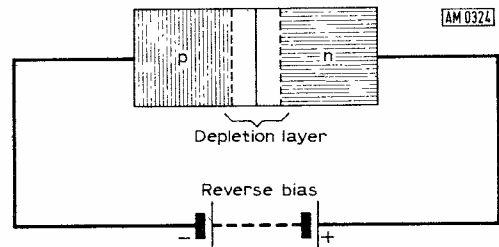


Fig. 1.1: As the reverse bias across a diode increases the width of the depletion layer increases and hence the junction capacitance decreases.

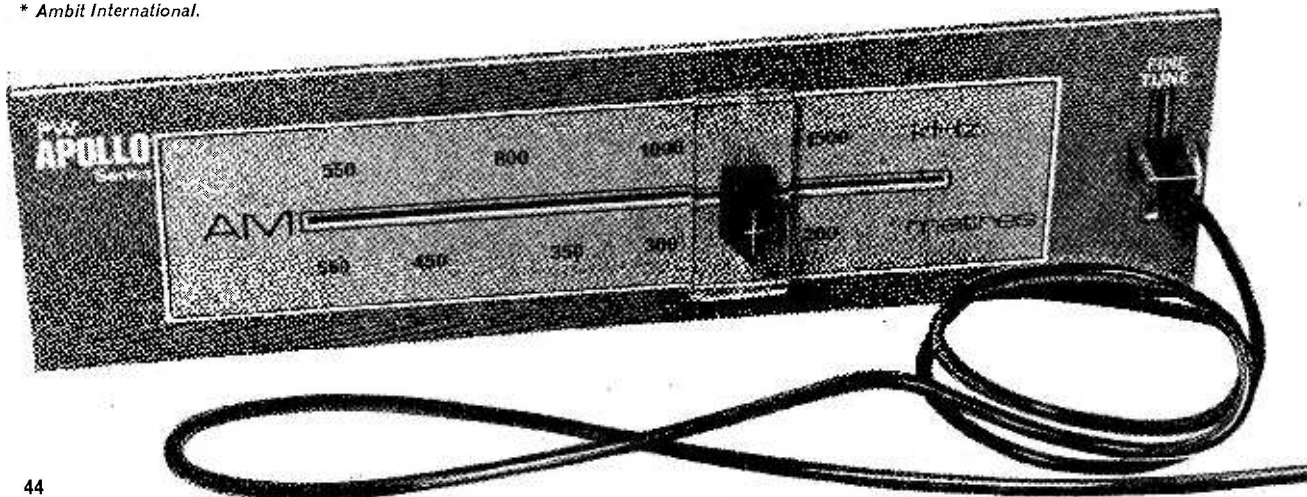All diodes exhibit this effect, the actual capacitance depending on the doping of the semiconductor material during manufacture and the area of the junction. A "varicap" diode is simply one where the degree of doping and geometry of the diode have been controlled to give predictable and repeatable capacitance variations as the bias is varied.





VARICAP DIODES FOR MW

The main limitation in the application of varicap diodes to lower frequencies (3 to 30MHz) has been the high cost of devices that are capable of giving a wide capacitance range. The well-known VHF diode, the BB104 has a maximum capacitance ratio of only 2.8 as the reverse bias is varied from 3 to 30V, the total capacity swing being about 55pF. This is completely inadequate for MW operation where swings of about 260pF are required.

Another crucial factor in producing varicap diodes for MW operation is the matching of the diodes to provide accurate tracking of the various stages (aerial, RF, and oscillator). The wide capacity swing means that very close tolerance has to be observed throughout the manufacturing process, causing prices to be high.

Because of the very large potential market for low cost, high capacitance varicap diodes several manufacturers have been trying to develop a suitable production process. Recently Motorola have produced two integrated circuits: the MVAM1 consisting of three matched diodes; and the MVAM2 which contains two.

The MVAM1 consists of three diodes with swings of greater than 400pF per diode and a capacitance ratio of 26 as the bias voltage is changed from 1 to 25V. They are matched to within $\pm 1.5\%$ over the entire range. Price is under £3.

The availability of these diodes means that the designer is no longer constrained by the mechanics of cord drives, scale gearing, etc.

To complete the innovation of electronic tuning, a new style of long throw slider potentiometer has been produced to simplify tuning and scale arrangements. A cursor can be attached to the wiper of the potentiometer to give a direct reading of stations without the need for complicated mechanisms.

Fig. 1.2 shows how the MVAM1 would be applied to a typical superhet tuner. Each diode will exhibit approximately the same capacitance swing, and since the oscillator will be running at the signal frequency plus the intermediate frequency according to conventional superhet practise, it will be necessary to reduce the effective capacity swing in the oscillator section so that it will track at $f_{\text{sig}} + f_{\text{IF}}$.

This is simply achieved by inserting a padder capacitor in series with the tuning diode, the exact value being determined by the value of the inductors employed in the various tuned circuits.

Some tracking error will be inevitable, but this can easily be kept to a tolerable level by careful design of coils.

To set the ends of the ranges for the diodes, a preset resistor is included at each end of the tuning slider.

The slider potentiometer is simply used to tap off a voltage which is applied to the diodes. It is not advisable to employ too low a bias voltage since the Q and cross modulation factors may be adversely affected.

VARICAP TUNER OPTIONS

Items such as preset station selectors, be they push-button or touch sensitive switches, can be employed in exactly the same way as they might be used at VHF.

Remote tuning is no problem: the tuning voltage can be fed down a long cable to a remote receiver with no adverse effect since it is strictly DC. Thus the receiver may be placed in a convenient spot where it is shielded from interference whilst the controls are close at hand.

Some of the other applications for the triple varicap diodes are in sweep generators and spectrum analysers, in self-tuning AM/FM receivers with band scanning and station hold facilities, and in transmitter low power stages, specifically in the oscillator where synthesis techniques are used.

MW TUNER

In order for the enthusiast to experiment with the new device a simple IC receiver will be described in detail. This requires a power supply of 9 to 12V plus a separate tuning bias for the varicap of up to 25V. Various power supplies will be described, the particular one that is chosen being up to the user.

The circuit of the tuner board is shown in Fig. 1.3. The IC used is available under various type numbers depending on manufacturer, NE546, LM1820, μ A720, or CA3123E, and provides all the active components for a superhet receiver.

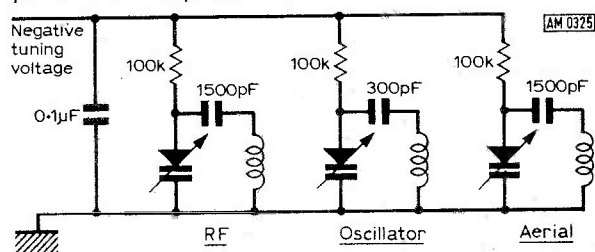


Fig. 1.2: The MVAM1 may be used with a conventional superhet circuit to control the tuned frequencies of the aerial, RF and oscillator stages.

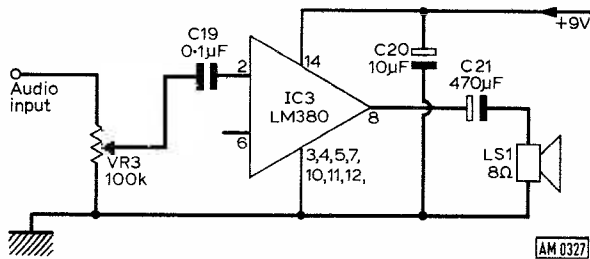


Fig. 1.4: A simple audio amplifier which can be used with the tuner.

A tuned RF stage is used which enhances selectivity and helps reception in the evening when local stations suffer from interference from adjacent frequencies from continental stations.

After the RF stage there is a conventional mixer stage followed by a ceramic filter which enhances IF selectivity. The IF amplifier then feeds into a detector transformer with a conventional silicon diode to detect the AM envelope. The audio output can then be fed into an external power amplifier or a simple amplifier can be incorporated into the design, a suggested circuit being shown in Fig. 1.4.

It is not recommended that substitutes for the specified coils be used.

CONSTRUCTION

When using ICs that operate in a linear mode at RF frequencies, it is virtually essential to use a printed circuit board if instability and associated problems are to be avoided. A suitable layout is shown in Figs. 1.5 and 1.6. On no account should Veroboard be used. Use a soldering iron of not more than 25W and avoid prolonged heating of IC pins.

The prototype which can be seen in the photographs was built as a battery-operated radio with the option of either pushbutton or remote slider tuning control. The pushbutton unit consists of six independently variable preset potentiometers one of

which is selected when a pushbutton is pressed. The common wiper output is taken to the tuning voltage input on the board via a changeover switch S2 used to select the remote slider potentiometer.

An internal 2W amplifier is incorporated within the case using the LM380 IC and its associated components (See Figs. 1.7 and 1.8). The speaker is mounted in the lid of the case.

An output socket is fitted at the back of the case to allow the connection of the remote slider tuner. The two outer connections to the slider can be commoned with the outer connections to the pushbutton unit but the wiper of the slider must be selected by the changeover switch. Twin-core screened cable was used to connect the slider potentiometers and the main unit.

A metal case was used since the radio was to be used with an external aerial via the coaxial socket on the back of the case. Should the constructor wish to use a ferrite rod aerial, the box must, of course, be plastic. Details of a suitable ferrite rod aerial, which is simply connected in place of the aerial coil T1, are given in Fig. 1.9.

The volume control and the on/off switch are the only controls mounted on the front panel.



A complete interwiring diagram for the receiver is shown in Fig. 1.10.

Should the constructor wish to use an external amplifier the output can be taken directly from the tuner board take-off point.

Ordinary rotary potentiometers can, of course, be used in place of the slider pots, but tuning is more difficult.

TUNING VOLTAGE

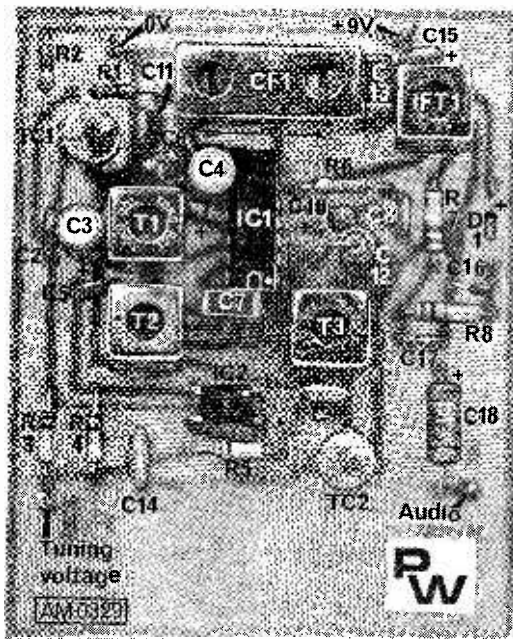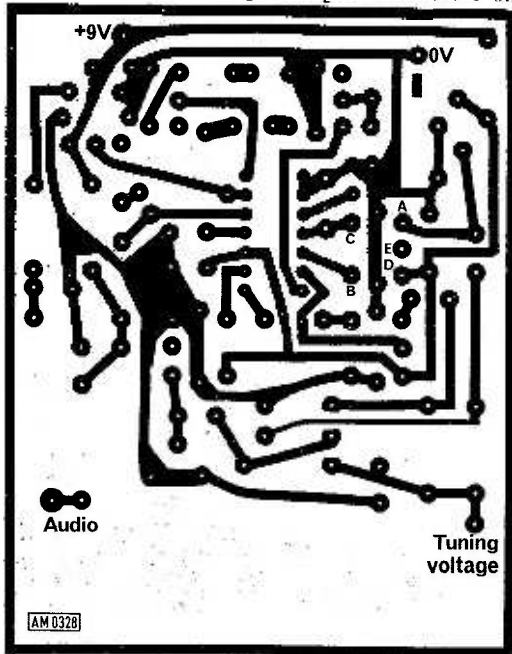In the circuit shown, a negative voltage is required for the diodes, so with the standard procedure of negative earth, this poses a few problems. Since the varicap diodes are reversed biased, the only current that flows is that through the tuning potentiometer.



Figs. 1.5 and 1.6: Full size printed circuit board layout for the tuner with component locations. The external aerial lead is connected on the reverse side of the board directly to T1 (E) to avoid stray pick-up.

tecknowledgegy

AMBIT has something more to offer the experimentally minded constructor. More than a unique range of inductive components, the best in radio linear integrated circuits, and our 'by return' service for all items in stock - and you cannot get much faster than that. We have tecknowledgegy. And plenty of it. Tecknowledgegy is the sort of data and information service that puts other component suppliers to shame.

So next time you want to buy a VHF tunerhead, a complete FM tuner set, or just one IC - wouldn't you like some tecknowledgegy to help you make certain that you are as well up in modern electronic technology as a component/information service that is as well informed as *AMBIT* ?

The ELECTRIC WIRELESS

The new Motorola varicap developments, the MVAM 1 & 2, represent the biggest advance in AM radio design since the introduction of the semiconductor. AMBIT has both types available, plus the sort of coil and filter backup that can only be available through the world's largest manufacturer of consumer radio inductors and filters. TOKO of course.

APOLLO PROJECT: the semiconductors: MVAM1, CA3123E, IN4148 package price £4.00

the coils and filter: YHCS11100AC2, 6A6371, Y18576AQ, CFU050D package price £1.40

the PCB: 75p the complete kit for the radio module: £8.00

the unique long slider: £3.00 the push button unit o/a

When you buy from AMBIT, we will keep you informed of all the latest developments in this new varicap technology.

and the rest:

Larsholt 7252 FM tuner set, a unique 'antenna to audio' system with a spec that includes 1uV for 26dB S/N muting, AFC, AGC, scan tune and lots more. Built and tested for £20.

TOKO EF5603 tunerhead. The very best from the range, with four signal frequency tuned circuits and MOS input stage. Built and tested for £8.40

TOKO EC3302. A low cost, but high performance varicap tunerhead with AFC compatible with any quad. det. IC IF system. Built and tested for £5

Larsholt 8319, the 'head' section of the 7252 tuner set; with AFC, AGC varicap control, dual MOSFET. Top quality Danish make for £7.74.

TOKO MT3302; the EC3302 with three stage FM and two stage AM mechanical geared tuning capacitor. FET input stage. Only £5.30.

91200 Our double linear phase filter FM IF system with the CA3089E.

Which means the lowest distortion FM IF with mute, Meter drive, AFC twin BBR3125N Built and T for £9

FM1185 A low cost FM IF with the CA3089E, ceramic filter, mute etc. Mini size and high spec for £4.35.

993090 The 'no compromise' top quality MPX stereo decoder with twin pilot tone filter, LED beacon audio preamps, & 100mV sensitivity. The best you can buy for £7.60.

91310 Lower cost MPX decoder, but still no corners cut with the module. Twin pilot tone filter, LED beacon, PLL IC. All for just £5.10.

Accessories for varicap FM radios:

illuminated edgewise panel meters scaled 88-104 (frequency) and with 0-10 (sig. Strength). £2.35ea £4.50pr.

A brief selection from the main information folder:

We haven't got space here to go into detail, so use our new short form list service, for a full list - for the price of a stamp. Coils for everything from audio to VHF, and plenty of stock from our 'by return' service.

Also linears, and other top technology electronic parts. Magnifier time: CA3089E including det. coil £1.94. CA3090AQ inc coil (2mH) £3.75. 8038CC Siggech chip and VCO £3.10. MC1310P PLL decoder only £2.20. 7800 voltage regs - see lists for gen. TOKO 455kHz mech filters £1.45. Ceramic filters for 455kHz 50p, and for 10.7MHz 40p each.

Linear phase filters BBR3125N for true 'no distortion' 10.7MHz IF amps £1.35 each, or £2.50 per pair. Also 560 series PLL, LM380/381, TBA810, TBA651, CA3123E, 1496, CT7001 clock chip, plus some IC accessories and hardware to make the service complete.

Terms: CWO please. All prices EXCLUDE VAT. P&P 15p per order. Min. Invoice £5.00. Min CWO £1.00 Catalogue (complete with stacks of data) 40p. OR send us an SAE for short form list and summary (FOC)

All enquiries to be accompanied by an SAE please. Please avoid burdening our phone service with requests that can be easily dealt with via post. All our goods are brand new and manufacturers first quality types. We sell no 'seconds' at all.

FROM ambit

AMBIT international 37 High Street, Brentwood, Essex. CM14 4RH tel: 0277 216029 tlx: 995194

★ components list

TUNER

Resistors

R1 47 Ω	R5 100k Ω
R2 330 Ω	R6 33k Ω
R3 100k Ω	R7 200k Ω
R4 100k Ω	R8 1k Ω
All $\pm 5\%$ $\frac{1}{4}$ W	R9 2.2k Ω
VR1 50k Ω 150mm linear slider Rivlin type WS 150 (Ambit)	
VR2 5k Ω linear slider	

Capacitors

C1 22pF	C10 0.47 μ F 35V tantalum
C2 1500pF	C11 0.047 μ F
C3 10 μ F 25V	C12 10 μ F 16V
C4 10 μ F 25V	C13 0.1 μ F
C5 1500pF	C14 0.1 μ F
C6 10 μ F 16V	C15 0.47 μ F 35V tantalum
C7 0.1 μ F	C16 4700pF
C8 56pF	C17 4700pF
C9 330pF	C18 4 μ F 40V
TC1 5–25pF miniature trimmer	
TC2 5–25pF miniature trimmer	

Semiconductors

D1 1N4148 or similar small signal diode
IC1 LM1820N (or CA3123E, μ A720 or NE 546)
IC2 MVAM1 (Ambit)

Inductors

T1 Toko 6A6408 (or ferrite rod, see text)	} (Ambit)
T2 Toko 6A6408	
T3 Toko Y18576A0	
IFT1 Toko YHCS11100AC2	
CF1 Toko CFU050D	

Miscellaneous

SK1 Coaxial socket
SK2 5-pin 180° DIN socket
S1 DPDT toggle switch
S2 Single pole changeover switch
B1 9V PP7
B2-B4 9V PP3 (3 off)
Printed circuit board
Six-way pushbutton varicap TV tuner unit, Imperial Metal Industries type 9932. Knob, twin-core screened cable, case.

AUDIO AMPLIFIER

VR3 100k Ω linear carbon
C19 0.1 μ F
C20 10 μ F 16V
C21 470 μ F 16V
IC3 LM380
LS1 8 Ω 3in speaker
Printed circuit board

If a 50k Ω potentiometer were used then with a 27V supply the current would be 500 μ A. This makes it quite feasible to use three PP3 batteries for the tuning bias, the use of batteries also alleviating the problems of smoothing and decoupling.

If the whole unit were to be run from the same set of batteries then the fluctuations in volume would cause variations in the supply voltage which would, in turn, affect the tuning voltage.

The most elegant method of supplying the necessary voltages is by using the 78 series of three-terminal voltage regulators. These are ICs which take the unregulated supply and turn it out at a predetermined voltage. In the circuit given, (Fig. 1.11) the main module supply is regulated by the 78L12, which is a 100mA low cost three pin 12V regulator, and tuning voltage by the 7924.

The overall stability is excellent, the set staying in tune over a wide temperature range.

SETTING UP


With all the components in place, check for solder bridges, dry joints, etc. Connect the audio amplifier, and then, having tested the voltages beforehand, connect the tuning supply and the main supply.

Set the tuning potentiometer to midway and adjust T1 (or slide the ferrite rod into the aerial coil) until some noise is heard from the AF section. (Holding on to the coil on the ferrite rod will assist in this procedure, as the effect of hand capacity will enhance the sensitivity.)

Although the IF coils are very nearly aligned, it may be necessary to adjust the tuning potentiometer until a strong local station is heard, then peak the detector coil by a slight turn of the core. Then trim the ceramic filter input and output transformers—this will need only a fraction of a turn.

If a signal generator covering IF frequency (470kHz) is available then loosely couple the output to the circuit and peak for maximum.

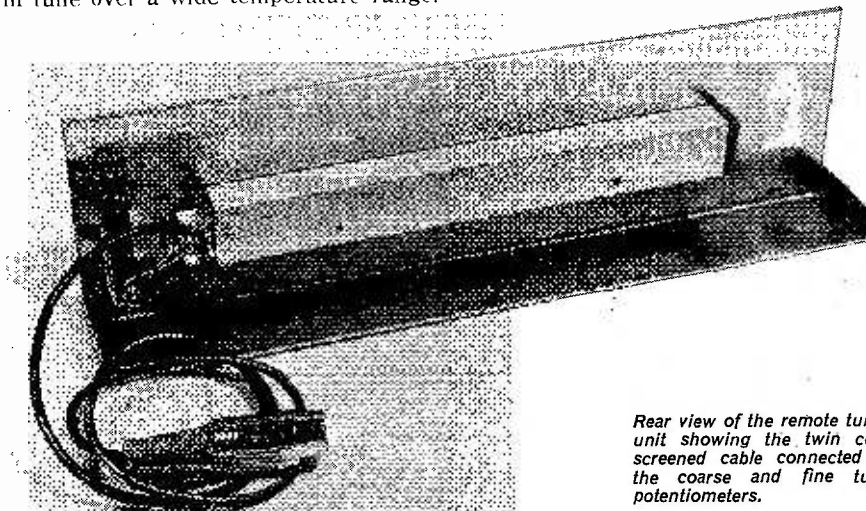To align the RF and aerial stages tune to the low frequency end of the medium wave and either find a station or, using the generator, slide the coil along the ferrite rod (or trim T1) for maximum output. A means of metering this is to monitor the voltage between the detector diode and earth, using a high impedance voltmeter. Note that the voltage goes increasingly negative with increasing signal.



Rear view of the remote tuner unit showing the twin core screened cable connected to the coarse and fine tune potentiometers.

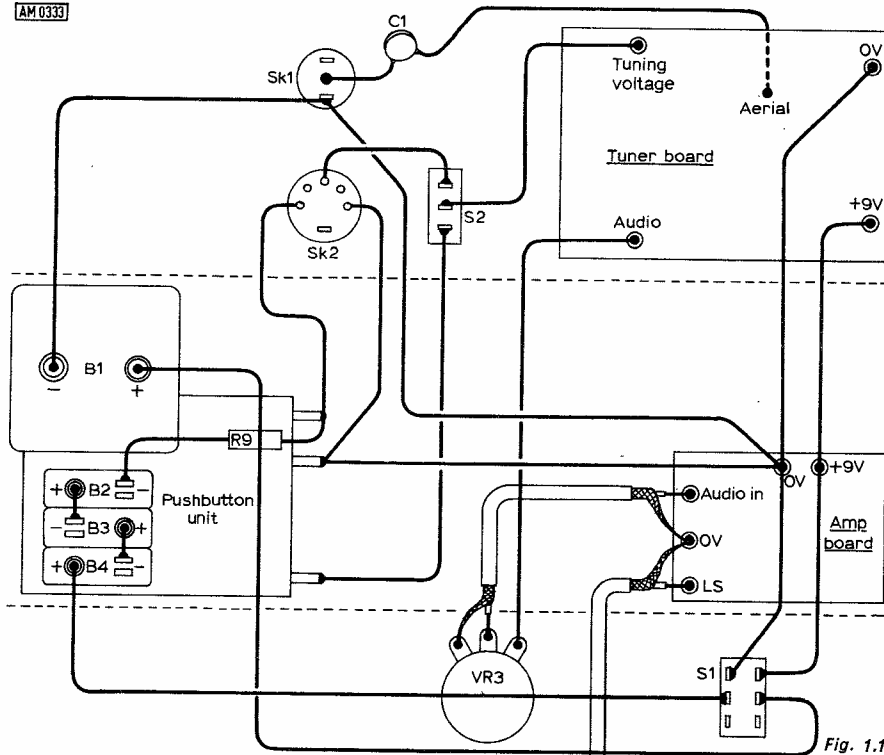


Fig. 1.10: Interwiring diagram of the Apollo receiver with an external aerial.

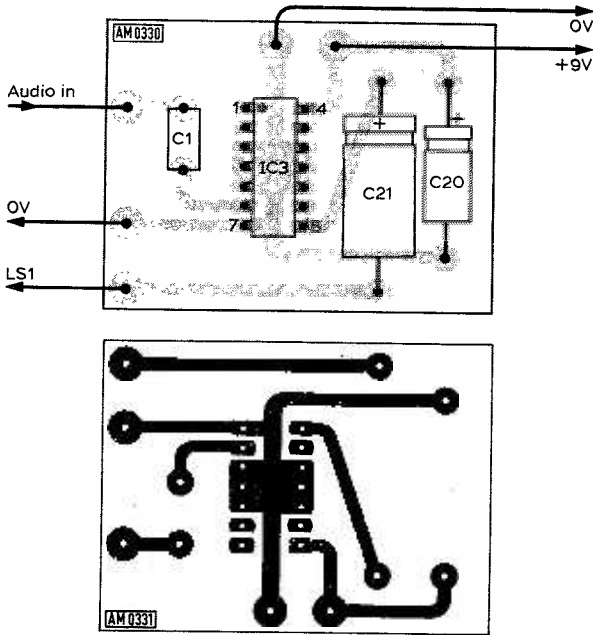


Fig. 1.7: Full size printed circuit board layout for the amplifier and Fig. 1.8 component location.

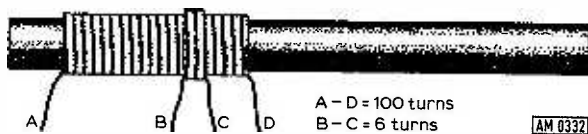


Fig. 1.9: Ferrite rod aerial winding details. The four leads are connected to the corresponding points on the tuner board and the external aerial connection (E) is not used.

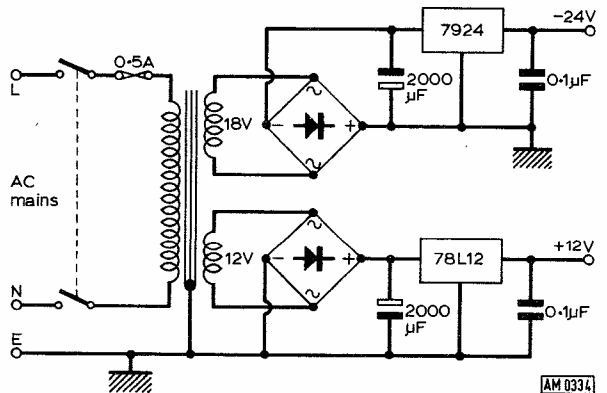


Fig. 1.11: A mains operated supply which will power the tuner and amplifier boards and give the required negative tuning voltage.


Trim the core in the RF stage transformer and then reset to the high frequency end of the MW band. Having established a signal, trim the capacitor in the aerial circuit for maximum. For this tuner the scale should be arranged so that the low end of the frequency range just covers 550kHz, and the high end covers 1500kHz.

Reference to your local papers should reveal the frequencies of local radio stations and these may then be used to provide markers. Alternatively, the signal generator or frequency counter may be used for calibration.

The actual frequency being received will be 470kHz less than the oscillator, in conventional superhet fashion.

NEXT MONTH THE USE OF THE TRIPLE VARICAP IN SWEEP OSCILLATORS WILL BE DISCUSSED

GOING BACK...

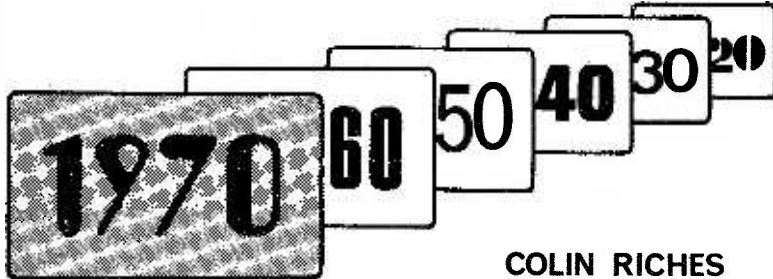

COLIN RICHES

Sir Oliver Lodge

EXPERIMENTS made by Hertz in the 1880's into the field of electromagnetic radiation through the ether inspired Lodge, who had already obtained repute as an eminent physicist. He amplified and developed the results obtained by Hertz and really pioneered work on coherers.

The detection of wireless signals using the coherer principle was largely due to Oliver Lodge, who in 1889 experimented with two metal spheres which were sited so close to each other that they were separated by a minute film of air.

When current was applied the passage of the spark made the spheres 'cohere'. All it needed to restore the spheres to their original highly resistive condition, was a slight mechanical shock or jolt.

Various pastes, liquids and

metal filings were used in later coherers and in 1890 Lodge used an electric bell in circuit to obtain the 'de-coherence' by vibrating the coherer itself.

In 1890 Lodge published his findings from experimenting with syntonic leyden jars and described the principle of tuning. What did not occur to Lodge at this time was the development of 'over the air' signalling as a serious competitor to the telegraph and telephone.

Marconi said years later that at that time there was no known method of creating electrical impulses powerful enough to project them any distance through the ether.

It had seemed to him that if the radiation could be increased and controlled (ie: tuned) it would be possible to signal across space for quite a distance.

Marconi's main problem was, that since the idea was so simple, why had no one else thought of doing it? We know now that Sir




Sir Oliver in his laboratory c. 1920.

Oliver had, in fact, missed the correct answer by a fraction.

1895 saw Lodge working with Dr. Alexander Muirhead and together they developed the Lodge-Muirhead system of wireless telegraphy.

The Lodge-Muirhead coherer which must have been amongst the most sensitive made, consisted of a sharp-edged steel wheel which just touched the surface of a pool of mercury covered with a thin film of oil. The wheel was driven by clockwork. High frequency oscillations were enough to break down the oil film while the continuously rotating wheel ensured that de-coherence took place as soon as the signal stopped.

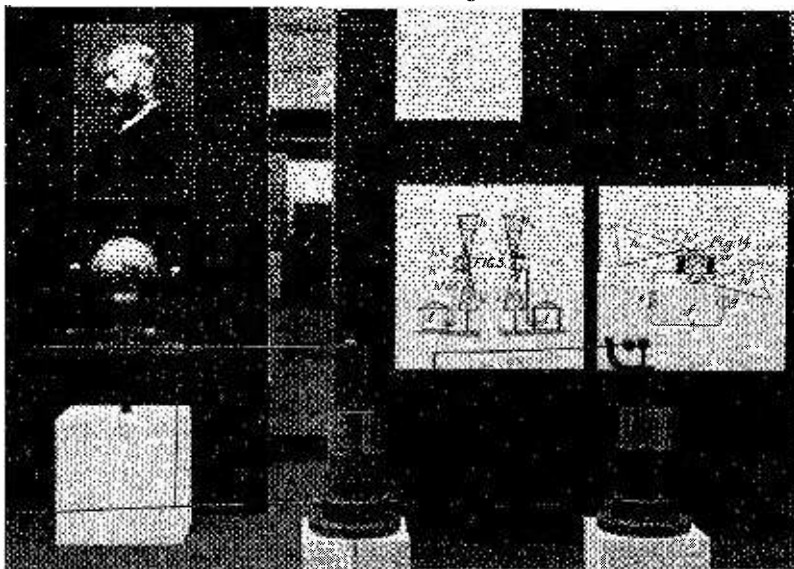In 1897, Lodge and Muirhead patented several of their ideas and in 1911, the Marconi Company acquired them. In that year, Sir Oliver was made a scientific adviser to the Marconi Co.



This Science Museum photo shows the display devoted to Sir Oliver in their radio gallery.

Points arising . . .

REACTION TIMER

April 1975. In the circuit diagram Fig. 1 page 1098, R3 should be shown as 27k Ω and R4 as 47k Ω . The component list is correct.

PW 'ASCOT' CASSETTE DECK

Part 3 April 1975. Note:—Fig. 5 Part 2 'collector' should read 'emitter'.

PRODUCTION LINES

colin riches

W.K.F. ELECTRONICS

In the March 1975 issue of Practical Wireless, we stated that printed circuit boards could be supplied at the price of 70p irrespective of size, etc.

This needs clarification. The 70p charge only applies to single page size (6in. x 8½in.) p.c.b.'s on SRBP and not fibre glass.

W.K.F. Electronics are prepared to quote separately for sizes larger than our single page size, i.e. Practical Wireless Electronic Organ main board £5-50 in fibre glass, with power

supply board. All boards are fully drilled and roller tinned.

Prices do not include postage and packing charges. As postal charges have once again been increased (and this applies to all mail order products) please add extra for postage—allowing approximately 10p per p.c.b. *W.K.F. Electronics, Welbeck Street, Whitwell, Worksop, Notts.*

TELE-TENNIS REPRINTS

These are still available from: Chief Cashier (P.W. Tele-Tennis) IPC Magazines, Tower House, Southampton St., WC2E 9QX. Price is 75p + 5p postage.

"EUROPA B"

The Solid State Modules "Europa B" is a 10 metre to 2 metre s.s.b. transverter. It is an updated version of the very successful "Europa". It is a linear transmit and receive converter for use with either a separate transmitter and receiver or transceivers. Any transmission mode fed into the unit is re-transmitted on 2m. When used with Musen, Sommerkamp or Yaesu gear the "Europa B" takes its power supply direct from the accessory socket on the h.f. equipment. When used in conjunction with other gear, the required voltages may be taken from the h.f. equipment or S.S.M.'s matching p.s.u.

The "Europa B" has a slightly different front panel, round knobs and an internal aerial change-over relay.

An SO 239 aerial socket is fitted.


The specification of the "Europa B" includes some of the following features: dual-gate MOSFETS in the receive converter, bipolar transistor oscillator chain; valves in transmit converter; low receive noise figure; ten times more accuracy on frequency because of the much closer tolerance crystal used in the oscillator section; 200W p.e.p. input; transmit drive requirement 100mW and receive converter gain -30dB.

Price, with valves is £88. Without valves £74. Valves required are: 2 off QQV03/10 and 1 off QQV06/40A.

Further details may be obtained from *Solid State Modules, 63 Woodhead Road, Solid, Lockwood, Huddersfield HD4 6ER.*


TELEFUNKEN CASSETTE DECK

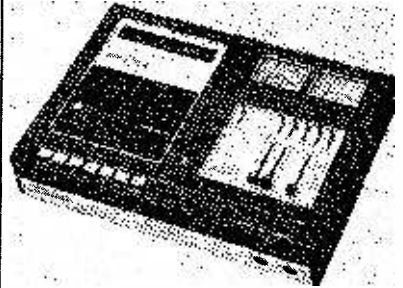The Telefunken MC3300 HiFi is a stereo cassette deck to DIN 45500 standard. It embodies the Dolby system for noise suppression, has an Electro CRO₂ tape selector, HNS audio head, i.e. maximum band modulability and automatic stereo recording level control with manual override. Speech/music changeover switch is coupled with Radio/microphone input selector. Features



include: 2 extra large illuminated peak voltage meters, also operational during playback. 3 slide controls for record left, record right and headphone volume. Headphone socket, speaker switch. Illuminated signals for record, playback, forward and rewind, stop, Dolby and CRO₂. 5 rocker switches for electrical function selection. Electronically governed d.c. motor. 3 digit memory counter (memory can be cut out). Electronic end-of-tape and interference detector with stop feature.

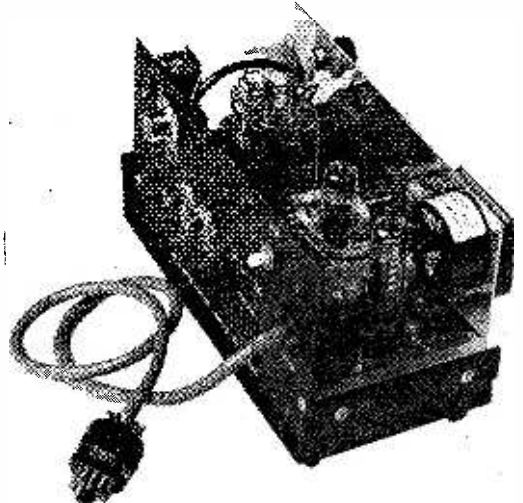
Frequency range with chromium dioxide tape is said to be 30-15000 kHz. Signal to noise ratio with chromium dioxide tape >57dB; Noise Suppression Dolby JC; wow and flutter; before tape <±0.18% and playback <±0.12%. Recommended Retail Price is £215.00 *AEG-Telefunken (UK) Ltd., Bath Road, Slough, SL1 4AW.*



JVC SPEAKERS

Model SK8, recently added to JVC's speaker range is designed for systems handling up to 25W r.m.s.

The cabinet houses an 8in. free-edge woofer and a 1in concave dome tweeter. An acoustic suspension principle is used to achieve a frequency response of 35Hz to 20kHz. Crossover frequency is 2.5kHz and fundamental resonance frequency 67Hz. Sound pressure level is quoted as 88dB/W (8Ω) at 1M. The SK8's are 17½in. high, 9¾in. wide and 8⅞in. deep. Recommended retail price is £38.50 each plus VAT. Further information may be obtained from *JVC (UK) Limited, Eldonwall Trading Estate, 6/8 Priestley Way, London, N.W.2.*

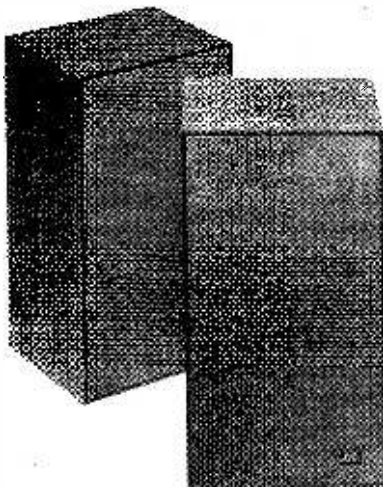

"DINO" MULTIMETER

The "Dino" multimeter, like the Dolomiti and Cito multimeters hails from the Chinaglia stable.

This 38-range meter has a basic sensitivity of 200kΩ/V d.c. and 20kΩ/V a.c.

The d.c. current ranges extend from 5μA right up to 5A, the voltage ranges from 100mV to 1.5kV, and the resistance ranges allow identification from 0.2Ω up to 1kMΩ. Indeed, in the one package this instrument provides most of the measuring requirements needed for modern semiconductor technology. A.C. ranges extend from 5mA to 5A and 5V to 1.5kV, whilst there are six dB ranges.

The Dino is built to the usual high Chinaglia standards with shock-proof ABS case, Class I, 40μA, 2.5kΩ movement mounted in sprung jewels and using a core-magnet system. Protection diodes guard the movement against overload. A full-view instrument face combined with anti-parallax mirror help avoid ambiguity of reading. Range switching is achieved using a simple five-position rotary switch in conjunction with separate range sockets for each selection.

A second version of the instrument is available with all the normal ranges, test leads and case, and with an additional internal universal signal injector. The USI version provides a modulated r.f. output rich in harmonics right up into the u.h.f. zones, making the instrument a simple dynamic analysis equipment capable of injecting a signal and observing the result.

A further optional extra is a 30kV probe to complete the TV servicing facility.


For further information contact *Alberto Coniglio, Chinaglia (U.K.) Ltd., 19 Mulberry Walk SW3 6DZ. Tel. 01-352 1897.*

SELF-ADHESIVE CABLE CLIPS

Special Products Distributors Ltd. who market a wide range of tools and equipment inform us that they can supply self-adhesive wiring clips. They grip instantly on any smooth surface to give a strong and permanent fixing—ideal for workshop and radio shack wiring! Insulation of the adhesive pad is said to break down at between 2.5 and 3kV. Price of the clips is £1.40 + VAT per hundred (size A)—up to ¼in dia. Size B £1.80 + VAT per 100 for ⅜in dia. wires. Further gen on these and other products from *Special Products Distributors Ltd., 81 Piccadilly, London W1V 0HL.*

TELE-TENNIS KITS

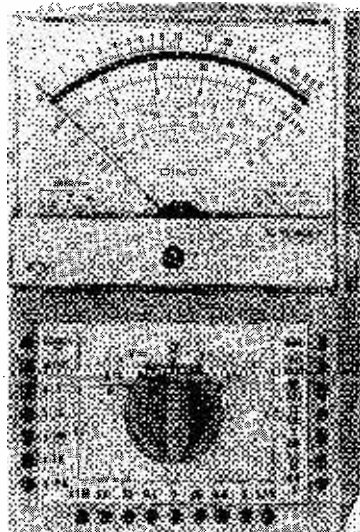Marshalls, who have branches in London and Glasgow tell us that they can now supply complete Tele-Tennis kits for £37, plus VAT and postage.—*A. Marshall and Son (London) Limited, Dept. P.W., 42 Cricklewood Broadway, London NW2 3HD (Tel. 01-452 0161).*



NEW CATALOGUES

Arrow Electronics have announced the 6th edition of their mail order catalogue. It contains details and prices of components, etc. ranging from neons to nuts and bolts and resistors to Mullard modules. For your free copy, send to *Arrow Electronics Ltd., 7 Coptfold Road, Brentwood, Essex CM14 4BN.*

The Studio Electronics catalogue has special emphasis placed on quadraphony and contains details of various electronic musical instruments. For a free catalogue, write to *Studio Electronics Ltd., P.O. Box 18, Harlow, Essex CM18 6SH.*

The 1975 Home Radio catalogue is now available. It contains a wealth of information on components and prices and is well-worth having on the bookshelf.—*Home Radio (Components) Ltd., 234-240 London Road, Mitcham, Surrey CR4 3HD.*

A new catalogue from Elvins gives details of prices of electronic organ components and kits. Send a stamped addressed envelope for a copy of the catalogue to *Elvins Electronic Musical Instruments, 12 Brett Road, Hackney, London E8 1JP.*


BBC CASSETTES

Latest cassette releases from the BBC include "Show of the Week" (includes Baby We Can't go Wrong—Cilla Black, Angel of the Morning—Olivia Newton-John). It's a stereo cassette RMC 4014. Bang on a Drum is a kiddies tape (stereo MRCM 004) which includes songs from Play School and Play Away.

Stereo MRCM 018 "Hits on a Harp" is David Snell playing popular numbers on a harp. It's a very pleasing sound and makes terrific background music.

RMC 4017 is a "Top of the Pops" stereo cassette which contains BBC TV's best of the pops available over recent months.

Finally, one for Dickens fans (MRCM 021)—one track features Ebenezer Scrooge (Patrick Magee) and supporting cast in a special dramatisation. The other side is Abel Magwitch (John Hollis)—the convict in *Great Expectations*. Both tracks, which feature full supporting cast, are ideal for introducing younger children to Dickens and should also hold the interest of older children (and Mums and Dads) who already know the stories.—*BBC, London W1A 1AA.*

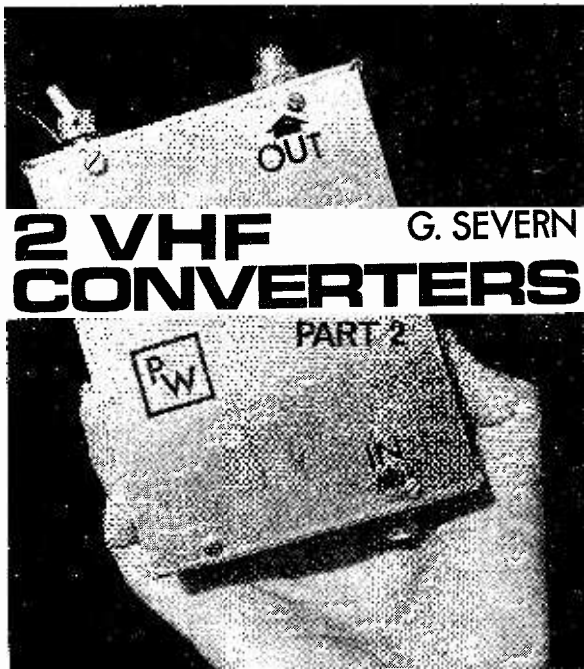

2 VHF CONVERTERS

G. SEVERN

CRYSTAL CONTROLLED CONVERTER

This employs a crystal oscillator and multiplier chain, RF stage and mixer. The crystal control results in frequency stability otherwise not obtainable combined with reliable read-out of frequencies on a calibrated receiver. As the oscillator frequency is fixed the receiver operates as a tunable IF. A screened communications type receiver with screened aerial input socket is thus almost essential, otherwise short wave transmissions over the tunable IF range will break through at considerable volume. A converter of this type is generally used for specialised reception over a narrow band, such as 144 to 146MHz, but it can be employed for some other frequencies.

In each case, reception can be in any mode catered for by the main receiver. The usual communications receiver will permit CW, AM and SSB reception which will be of advantage for 2m amateur signals. Few receivers will permit proper FM reception, though some will give "slope detection" of FM signals, which may be suitable for speech.

CIRCUIT

The aerial input goes to L1, with a tapping for impedance matching. A second tap supplies the source of the grounded gate FET RF stage Tr1, Fig. 4. This stage has less gain than a grounded source stage, does not need neutralising and is capable of broader band coverage. Coils L2 and L3 couple signals to the gate-protected mixer Tr2. The use of three signal-frequency circuits (L1, L2 and L3) helps remove spurious responses.

The oscillator Tr5 uses a 35MHz crystal doubling in each of the grounded base stages Tr4 and Tr3, so that L6 is tuned to 140MHz. This arrangement is intended for reception of 144-146MHz amateur band signals, tuning over the range 4-6MHz on the receiver. L4 in the mixer drain circuit is resonant

near 5MHz and L5 couples the output to the receiver, with a screened co-axial lead.

In converters of this type various output frequency ranges may be chosen. An output of 4-6MHz is likely to give quite open tuning with any receiver while a higher frequency, such as 14-16, 24-26 or 28-30MHz may be preferred where the receiver is efficient on these ranges and the scale is sufficiently open. A frequency sector which requires bandswitching the receiver is probably best avoided. Where an output other than 4 to 6 MHz is planned, the crystal, L10, L8, L6 and L4 must be modified to suit. The output frequency (L4) will be the difference between the signal frequency (L1 to L3) and final oscillator frequency (L6).

As the oscillator chain consumes about 20mA the converter is run from an external battery. Its main advantage lies in the frequency stability of this type of oscillator, avoidance of hand capacity and similar effects and the ability to re-tune on the receiver to a specific frequency.

RF MIXER BOARD

This board is shown in Fig. 5. Two tags MC fixed with $\frac{1}{2}$ in. 6BA bolts provide connecting points to the metal case. All connections between components should be as short as possible, noting that the "Tetfer" trimmers have tags which fit the 0.15 matrix board. Veropins are placed for L1, L2 and L3, the coils being wound with 20swg tinned copper wire, Fig. 6.

Coil L4 has 60 turns of 32swg enamelled wire wound in two layers, 40 turns being close wound, followed by 20 turns on a layer of tape. A further layer of tape is put on and L5 wound on top, Fig. 6.

★ components list

CRYSTAL CONTROLLED CONVERTER

Resistors

R1 270 Ω	R6 100k Ω	R11 150 Ω
R2 390 Ω	R7 39 Ω	R12 56k Ω
R3 120k Ω	R8 150 Ω	R13 5.6k Ω
R4 560 Ω	R9 68 Ω	
R5 220 Ω	R10 100 Ω	

All 5 or 10% $\frac{1}{2}$ or $\frac{1}{4}$ W

Capacitors

C1 1000pF	C8 1000pF
C2 1000pF	C9 1000pF
C3 100pF	C10 1000pF
C4 0.047 μ F	C11 1000pF
C5 10pF	C12 22pF
C6 3.3pF	C13 1000pF
C7 0.01 μ F	C14 10pF

Tubular or disc ceramic preferred.
TC1/2/3/4 10pF trimmers (Jackson 'Tetfer')

Semiconductors

Tr1 MPF102	Tr4 BC109
Tr2 40673	Tr5 2N706
Tr3 ZTX108	

Miscellaneous

Formers $\frac{1}{8}$ in. dia. (2) with cores (for VHF use).
Former $\frac{1}{8}$ in. dia with core (L4/L5). Veroboard
 $3\frac{1}{2} \times \frac{1}{2}$ in. and $3\frac{1}{2} \times 1\frac{1}{2}$ in. 0.15in. matrix. Universal
chassis $5 \times 4 \times 2$ in. with extra 5×2 in. flanged
plate and 5×4 in. flat plate (Home Radio) Co-axial
sockets (2) On/off switch. X1, crystal 35MHz (wire
leadouts) (Senator Crystals, 36 Valleyfield Rd.,
London, SW16 2HR).




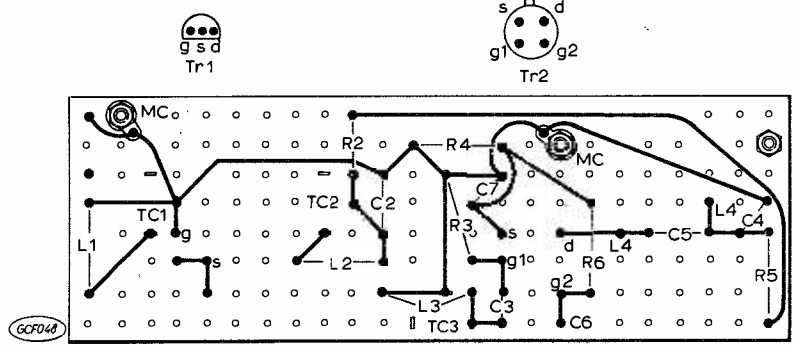
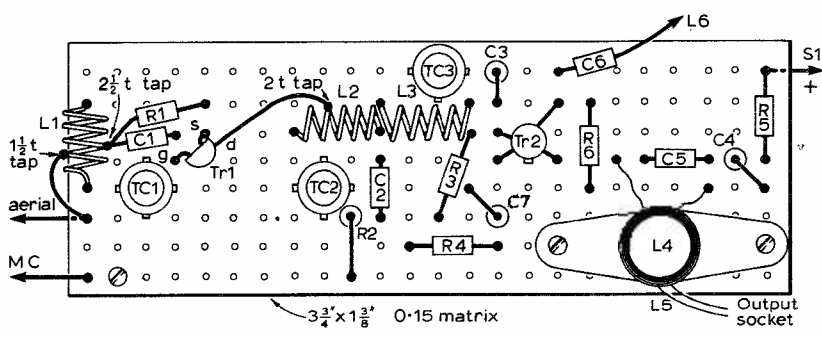
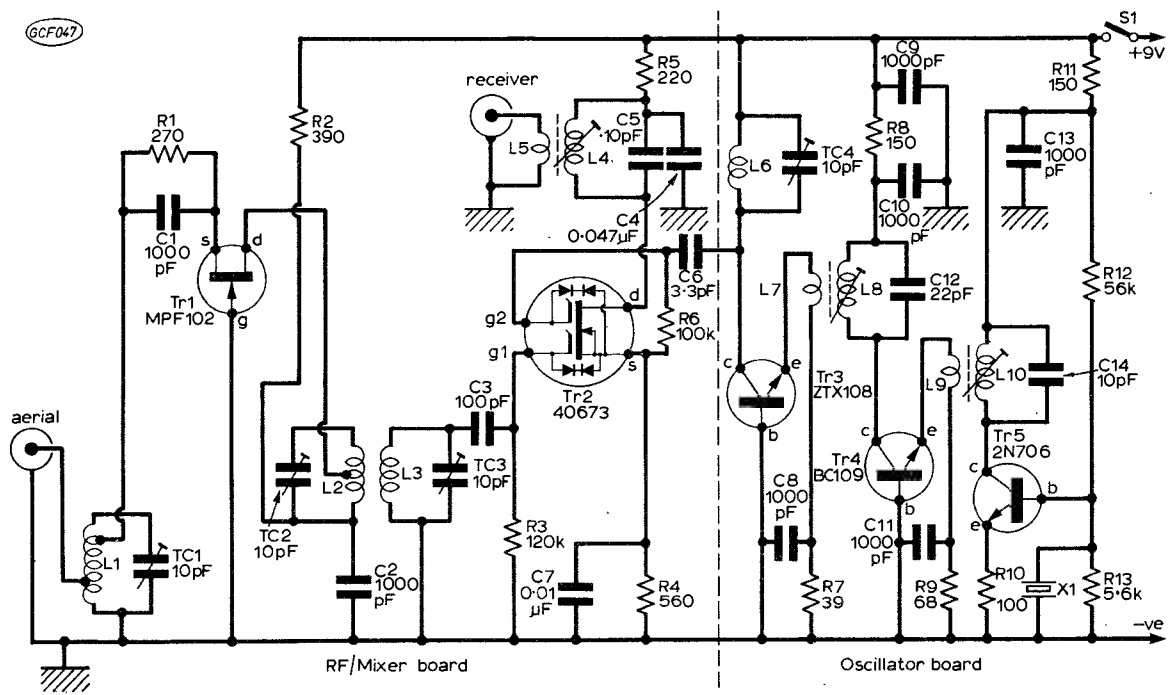
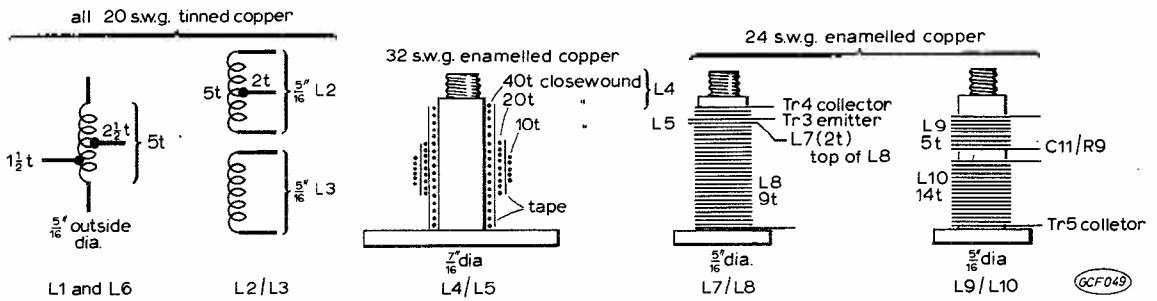


Fig. 4; above, is the more complicated circuit for the crystal controlled converter, constructed on two boards. Fig. 5; left, shows the RF/mixer circuit board, with the transistor lead-out connections. The second board is illustrated in Fig. 7. Fig. 6; below, gives winding information for the coils required in the converter.

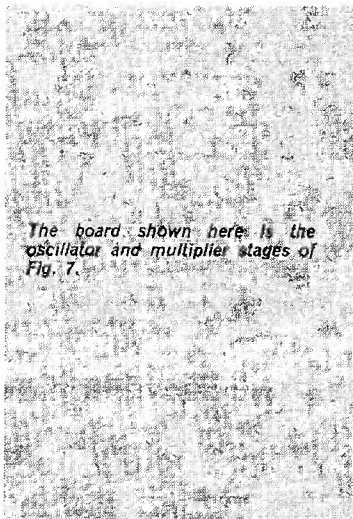

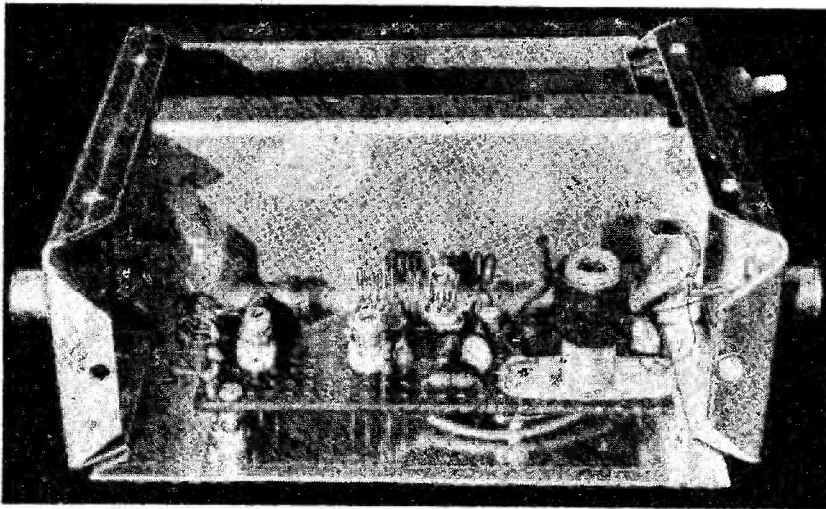

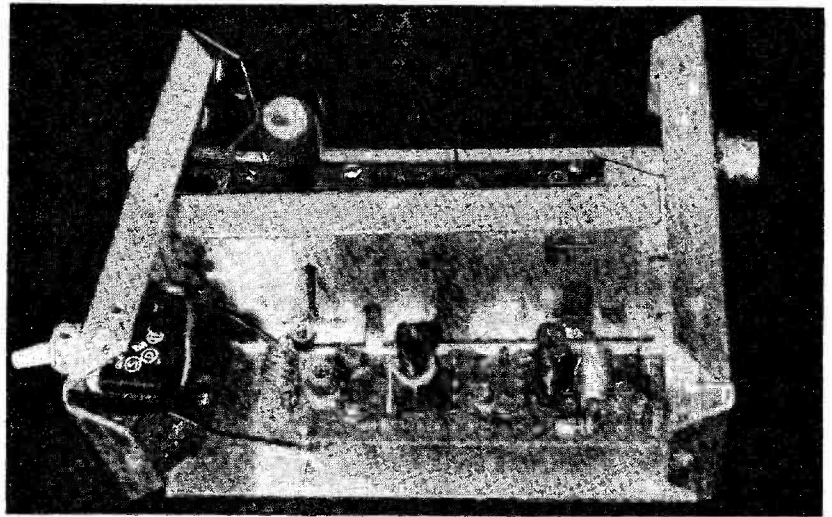The board shown here is the oscillator and multiplier stages of Fig. 7.



View of the RF/Mixer board of Fig. 6.

Note:—In Fig. 1, part 1, the symbols G1 and G2 on Tr1 should be reversed. Layout shown in Fig. 2 is correct.

This coil is then connected to the co-axial output socket and metal box utilizing a screened lead to keep down the strength of unwanted signals in the 4 to 6MHz range.

OSCILLATOR BOARD

The oscillator and multipliers are wired as in Fig. 7. All connections should be very short, including chassis returns such as to the base of Tr4 and Tr3 and from C11 and C8 to base. Coil winding information is given in Fig. 6.

CASEWORK

Cut $\frac{3}{8}$ in. from each flange of a 5 x 2 in. flanged plate so that this will fit inside the box ends. The 5 x 2in. screen is bolted centrally to the 5 x 4in. flat plate and the two 4 x 2in. flanged ends are fixed using bolts or self-tapping screws. Co-axial input and output sockets and on/off switch are fitted to these ends.

The flat plate is drilled for the bolts "MC" of the RF Mixer and oscillator boards. Each bolt has

two extra nuts so that they can be locked tightly, with adequate clearance under the boards. A lead passes from C6 through a hole in the screen to L6. The box sides and top are added only after the converter is tested and adjusted.

OSCILLATOR ADJUSTMENT

The easiest method of adjustment is to place an indicating wavemeter set to 35MHz near L10, and aligning the core of L10 until a deflection shows that oscillations are present. Set the core of L10 a little off the peak giving maximum RF or the oscillator may not start every time it is switched on.

Move the wavemeter set to 70MHz, near 18 and adjust the core for maximum indication. Repeat the same procedure at 140MHz with the trimmer TC4 and the wavemeter near L6. Later, L10, L8 and TC4 can be readjusted slightly for best results. The doubler chain output, with optimum tuning, is excessive for best results, causing unnecessary background noise. This is cured by slightly de-tuning for best reception.

—continued on page 58

TAKE 20

DAVID ANDREWS

No. 70 LED FLASHER

A series of simple transistor projects, using not more than twenty components.

THIS month's project came about after a request from a young lady for "something to liven up her appearance" at a New Year's Eve fancy-dress party. She wanted a gadget to cause small lights to flash on and off about her person but, for obvious reasons, whatever it was had to be small enough to be secreted away somewhere in her costume!

We offer the circuit for the benefit of other forward-thinking young ladies and anyone else who is interested in a very economic and novel twist to a well proven idea.

Circuit

To cut down on current consumption, and to prevent any possible overheating of the fine wires, which had to run around the lady's anatomy, it was decided to use general purpose LEDs which would give a good light output for currents of the order of 5 to 20mA. Quite clearly the project called for a multivibrator and after some thought transistors were ruled out, the main reason being that the final encapsulation would be too thick whereas a dual-in-line package integrated circuit, while taking up more or less the same area, would give a much thinner package for the end product.

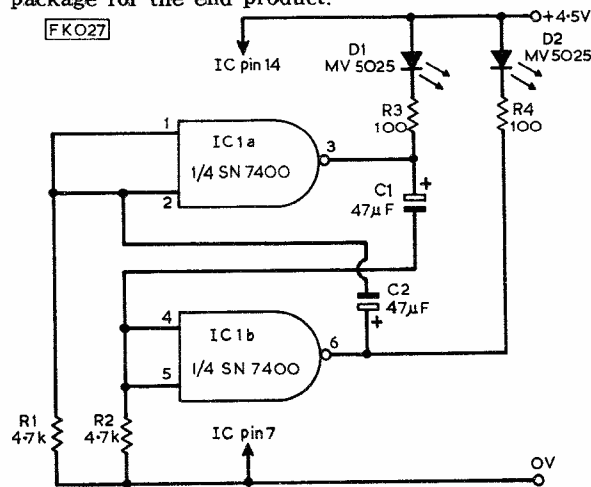


Fig. 1: Basic circuit using two gates of the IC.

By using a standard quad two input NAND gate (SN7400) it was found possible to make two such flashers from the single chip and by benefitting from the use of solid tantalum capacitors the whole circuit was housed on a piece of Veroboard approximately 1½ x 1in. The batteries (4.5V required) were three SP11 types soldered together in series, with ample interconnecting leads so that they could be discretely tucked away in various parts of the clothing without contributing too much to the bulk of the equipment.

The layout we are giving in this article is slightly larger than the prototype because we have included the LEDs on the same board and have laid out all the resistors horizontally, for clarity. Any other would-be party-goers could run pairs of 32 SWG enamelled copper wire from the board to the individual LEDs which can be sewn into the clothing.

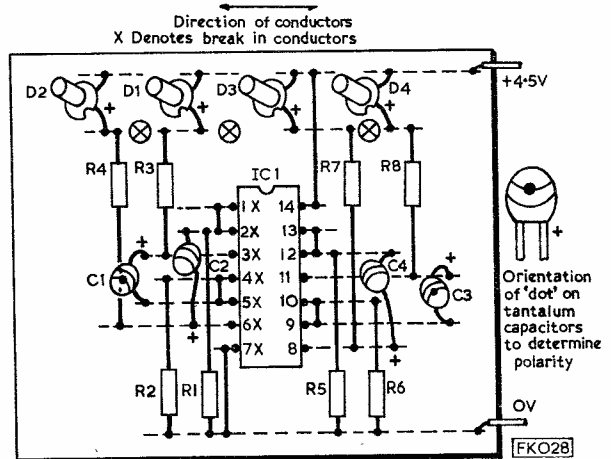


Fig. 2: Layout for complete unit with four LEDs.

The basic circuit for one of the flashers is shown in Fig. 1. Two of the gates from the package are cross coupled with capacitors C1 and C2 to form the multivibrator. Timing is controlled by these capacitors and the resistors R1 and R2 returned to the earth rail. To get reasonably low flashing speeds it is necessary to use large values of capacitance because it is undesirable to increase the values of R1 and R2 above that specified. With the values given the cycle lasts for approximately half a second. To alter the speed increase or decrease the values for C1 and C2 and leave the resistors as they are.

Initially it had been expected that it would be necessary to feed the output of each side of the multivibrator into each of the two remaining gates on the chip to act as buffers but after experimentation this was not found to be necessary. There was sufficient current available to drive the LEDs direct

★ components list

R1	4.7kΩ	R8	100Ω (see text)
R2	4.7kΩ	C1/C4	47μF 6V tantalum
R3	100Ω (see text)		(see text)
R4	100Ω (see text)	D1/4	MV 5025 (or G.P.
R5	4.7kΩ		Light emitting diode)
R6	4.7kΩ	IC1	SN7400
R7	100Ω (see text)		Piece of veroboard

SPARKRITE MK2


CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

Sparkrite Mk. 2 is a high performance, high quality, capacitive discharge, electronic ignition system. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and therefore eliminates the possibility of blowing the transistors or the SCR. (Many capacitive discharge ignitions are not completely foolproof in this respect.)


Sparkrite can therefore give you:
 up to 20% better fuel consumption, instant all weather starting, cleaner plugs - they last up to 5 times longer without attention, faster acceleration, higher top speeds, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

NOTE - FUEL CONSUMPTION:
 The fitting of a Sparkrite Mk. 2 should reduce fuel consumption although the amount of the reduction will vary. A fair estimate of the savings which could be expected based on reports by customers and upon our own experience, are as follows:
 any 4-cylinder vehicle, 10% improvement
 any 6-cylinder vehicle, 15% improvement
 any 8-cylinder vehicle, 20% improvement
 It is worth remembering that while fuel saving is important there are many other advantages to be gained from fitting a Sparkrite ignition system.

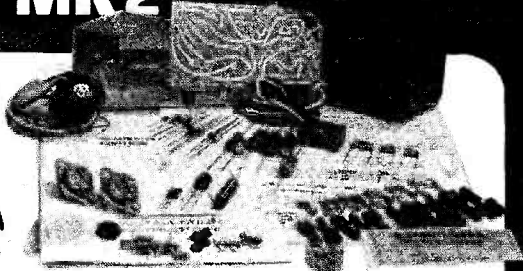*Voted best of 8
 ignition systems
 tested by leading
 Motoring Magazine*



THE KIT COMPRISES EVERYTHING NEEDED: Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink, top quality 5-year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicone grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.
WE SAY IT IS THE BEST SYSTEM AT ANY PRICE.

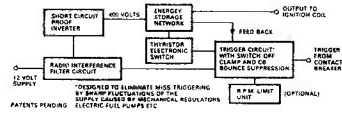

OPTIONAL EXTRAS
Electronic R.P.M. Limitation
 This can be included in the unit to prevent over revving, an advantage to most companies, hire firms, high performance drivers, etc.
Electronic/conventional Ignition switch.
 Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing, etc., and will also switch the ignition off completely as a security device. Includes: switch, connectors, mounting bracket and instructions. Cables excluded.

PRICES: D.I.Y. assembly kit £10.93*. Ready built unit £13.86* (both to fit all vehicles with coil/distributor ignition up to 8-cylinders).
 Switch for instant changeover from "Sparkrite" ignition to conventional ignition £2.79*. R.P.M. limiting control £2.42* (fitted in case on ready built unit, dashboard mounting on kit).
 * Including VAT, post and packing.
 We can supply units for any petrol-engined vehicle (boat, motorcycle, etc.) with coil/contact breaker ignition. Details on request.
CALL IN AND SEE US FOR A DEMONSTRATION.

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES

These project boxes are manufactured from 18-gauge aluminium and come complete with lids and screws. The prices shown include VAT (at 8%) but 18p should be added to the total order value for postage and packing.

Order No.	Length (in)	Width (in)	Height (in)	Price (inc. VAT)
7	5 1/2	2 1/2	2 1/2	47p
8	4	4	1 1/2	48p
9	4	4	2 1/2	46p
10	5 1/2	4	1 1/2	49p
11	5 1/2	4	2 1/2	46p
12	3	2 1/2	1	38p
13	6	4	2	58p
14	7	5	2 1/2	75p
15	8	6	3	83p
16	10	8	3	£1.14

Boxes can be made to any size but the minimum order for special sizes is 500. General trade enquiries welcome.

FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12V, 8W, fluorescent light. You will receive all of the necessary parts: white enamelled ready drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, end caps and cable, the fluorescent tube, nuts, bolts and washers, etc. and simple assembly instructions and operating instructions.

When complete the light has a wide variety of uses such as workshop and workbench illumination, garage lighting, emergency lighting, lighting for camping, caravanning or boating, as an inspection lamp and many more.

If you can't spare the time to put the light together then we will supply it ready built (for a few extra pence).

PRICES
 Assembly kit £3.19 (inc. VAT, post and packing).
 Ready built £3.78 (inc. VAT, post and packing).
 Diffuser 59p extra (inc. VAT, post and packing).

ORDER NOW

To: ELECTRONICS DESIGN ASSOCIATES DEPT. PW4
 82 Bath Street, Walsall WS1 3DE. Phone 33682

From: Name _____
 Address _____

Please Supply

Quantity	
	SPARKRITE Mk. 2 DIY assembly kits at £10.93
	SPARKRITE Mk. 2 ready built negative earth at £13.86
	SPARKRITE Mk. 2 ready built positive earth at £13.86
	Ignition changeover switches at £2.79
	R.P.M. Limit systems in the above units at £2.42
	Fluorescent light assembly kits at £3.19
	Fluorescent light built units at £3.78
	Diffusers for the above at 59p
	of number alum. boxes at
	of number alum. boxes at
	of number alum. boxes at

I enclose cheque/P.O. for £ _____ Cheque No. _____
 (Send S.A.E. if brochure only required)

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. ID have space dividers. Build up any size cabinet for wall, bench or table top.

INTER-LOCKING PLASTIC STORAGE DRAWERS

MEAT MARKET TODAY!

DISCOUNT PRICES

SINGLE UNITS 5" x 2 1/2" x 2 1/2" £2.00 Dozen

DOUBLE UNITS £3-50 Dozen. **TREBLE (3D)** £3.50 for 8

EXTRA LARGE SIZE (6D) £4.50 for 8.

Carriage 40p. Orders over £10 post free.

QUANTITY DISCOUNTS! 5% in £1 for orders over £15. 7 1/2% for orders over £30. Quotations for large quantities.

PLEASE ADD 8% VAT TO TOTAL RECEIVED.

FLAIDLINE SUPPLIES (Dept. PW5), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

TTL & SEMICONDUCTORS AT LOWER PRICES!

FAST DELIVERY **PRICES INCLUDE VAT (AT 8%)**

Type	1/24	25/99	100+	Type	1/24	25/99	100+	Type	1/24	25/99	100+
7400	0-14	0-13	0-12	7440	0-15	0-14	0-13	7486	0-30	0-26	0-25
7401	0-15	0-14	0-13	7442	0-89	0-83	0-58	7489	3-56	3-24	2-96
7402	0-15	0-14	0-13	7445	0-89	0-82	0-76	7490	0-45	0-44	0-41
7403	0-15	0-14	0-13	7447	0-89	0-79	0-76	7491	0-88	0-77	0-69
7404	0-18	0-16	0-15	7450	0-15	0-14	0-13	7492	0-51	0-46	0-42
7405	0-18	0-16	0-15	7451	0-15	0-14	0-13	7493	0-48	0-44	0-41
7408	0-18	0-16	0-14	7453	0-15	0-14	0-13	7495	0-88	0-61	0-57
7410	0-15	0-14	0-13	7454	0-15	0-14	0-13	7496	0-77	0-69	0-65
7412	0-24	0-19	0-17	7460	0-15	0-14	0-13	7497	0-34	0-31	0-29
7413	0-32	0-31	0-30	7472	0-28	0-25	0-23	7498	0-34	0-31	0-29
7417	0-30	0-29	0-28	7473	0-33	0-31	0-28	7499	0-88	0-61	0-57
7420	0-15	0-14	0-13	7474	0-33	0-31	0-29	7499	0-79	0-72	0-67
7427	0-27	0-25	0-22	7475	0-50	0-45	0-42	7499	0-89	0-81	0-76
7430	0-15	0-14	0-13	7476	0-34	0-31	0-29	7499	0-87	0-79	0-72
7432	0-27	0-25	0-22	7480	0-47	0-42	0-39	7499	0-89	0-81	0-76
7437	0-29	0-26	0-24	7483	0-89	0-80	0-74				


1N4148 ap, 1N4001 4p, 1N4002 5p, 1N4003/4 6p, ZTX107 10p, ZTX100C 11 1/2p.
 All devices full spec. by famous manufacturers. TTL MAY BE MIXED FOR QUANTITY PRICES. S.A.E. for catalogue (includes TTL pin layout guide). 10p P. & P. on orders under £2, otherwise POST FREE by 1st. class mail.

J. C. JONES (Dept. PW4)
46 BURSTELLARS, ST. IVES, HUNTINGDON PE17 4XX
 (Mail Order only)

**SPECIAL
PRODUCT
REPORT**

sinclair

DM2 digital multimeter

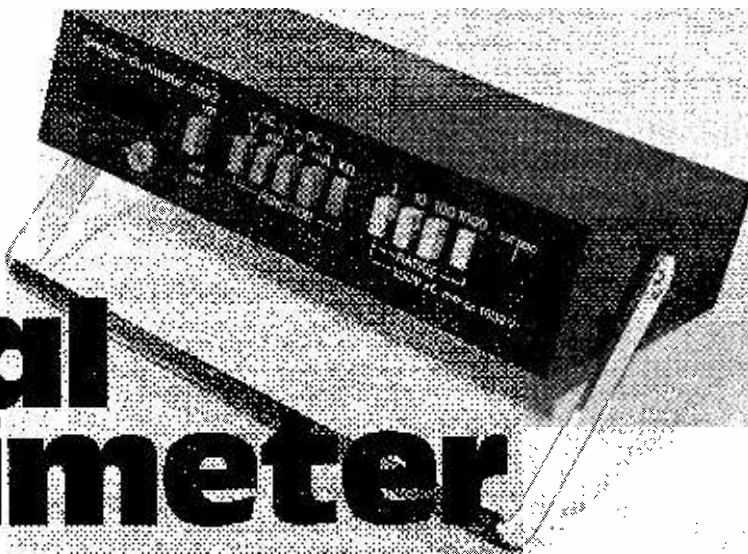

NOT very many years have passed since the appearance in this country of the first digital multimeter selling at under £100. Now a number are available at around £60—quite a drop even if you don't take into account the intervening fall in the value of the pound. As in the case of pocket calculators, the main factor behind this fall in price lies in the adoption of LSI techniques for the heart of the circuitry.

One of this new generation of digital multimeters is the DM2 by Sinclair Radionics—their second venture into the field. In common with most of the lower priced digital meters it uses an integrating converter, in this case one based on the dual-slope technique which offers a number of advantages over the simple system. A description of the basic principles of the dual-slope integration d.v.m. would probably be of interest to those not already familiar with them.

Dual slope integration

The unknown voltage V_x is applied to a voltage-to-current converter whose output charges a capacitor over a fixed time t_1/t_2 , see Fig. 1, controlled by a standard frequency oscillator. The voltage V_1 attained by the capacitor at the end of this fixed time is proportional to the unknown voltage V_x .

At time t_2 , the capacitor is disconnected from V_x and connected instead to a reference voltage of the opposite polarity, $-V_{ref}$. It will then discharge at a rate set by $-V_{ref}$ until its voltage reaches zero again at time t_3 . The period t_2/t_3 is thus proportional to V_1 , which was in turn proportional to V_x , so by measuring that period we will have an indication of the unknown voltage. The measurement is simply performed by feeding the output of the standard frequency oscillator to a digital counter via a gate which is arranged to open at time t_2 and close again at t_3 . By suitable scaling the counter will indicate directly the applied voltage.

Because the same oscillator both controls the charge period and measures the discharge time, its actual frequency is not important—the only requirement is that it should not change during the measurement. For similar reasons, the value of the capacitor is not critical; it just needs to have good short-term stability. Thus temperature changes and long-term drifts have little effect on the instrument's accuracy.

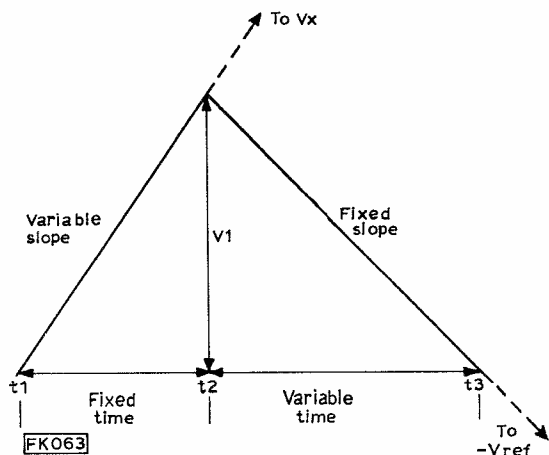



Fig. 1: The dual-slope integration technique.

Operating speed

Since integration by its very nature and definition takes time, integrating meters are not fast in operation. They are therefore unsuitable for applications where a rapidly fluctuating input is to be monitored, for instance where a control is to be set quickly to produce a certain voltage reading, or in data-logging systems where successive sampling of a number of input levels is required. To this cloud there is a silver lining, however, for this slow response will integrate out noise spikes which can upset faster reading instruments.


The Sinclair DM2 is a $3\frac{1}{2}$ digit instrument. For the benefit of those readers unversed in d.v.m. terminology, this means

SUPERSOUND 13 HI-FI MONO AMPLIFIER

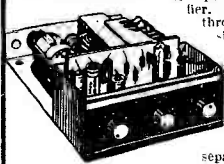

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3dB. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, esutchon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £12.50. P. & P. 50p.

DE LUXE STEREO AMPLIFIER

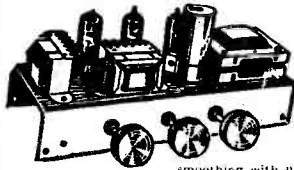

A.C. mains 200-240 v. Using heavy duty fully tested mains transformer - or with full wave rectification giving a.c. smoothing with negligible hum. Valve line up: 2 x ECL82 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w. x 4 1/2" h. Overall height including valves 6". Ready built & tested to a high standard. £10.75. P. & P. 30p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7.5v, and 9v, and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Haminer finish metal case overall size 6" x 3 1/2" x 2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £5-20 P. & P. 35p.

VYNAIR & BEXINE SPEAKERS & CABINET FABRICS sup. 54 in. wide. Our price £1-30 yd. length P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER
A super quality grain amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7 1/2" wide x 3 1/2" deep x 6 1/2" high overall. A.C. mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. £4-20 P. & P. 40p BARGAIN PRICE

FEW ONLY!
High grade mains transformer with grain orientated lamination. Primary 200/240 Secondary 18.5 volts at 0.6 amps and 4.6 v. high overall. Size 2 1/2" x 2 1/2" x 2" overall. £1-35 plus 25p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0.5-10-15-20-25-30-35-40-60v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.60 P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 0-9 or 500 mA. £1-25. P. & P. 25p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1-40. P. & P. 25p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2-00. P. & P. 35p.

3 VOLT RELAY
100 mA single pole normally closed. 2 for 60p + 15p P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER
For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-35KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price 1-20p. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES
A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.
Diode Equivalents, 90p; Transistor Equivalents, £1-00; Transistor Characteristics, £1-30; POST FREE All three together. £3-00
NEW ISSUE
Thyristor, Triac, Diac etc. encyclopedias £1-00. Post Free
8 pole 3 way 2 bank low loss Xaley type switches 11" sections. Standard spindle. 2 switches 65p + 10p P. & P.

HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy fabulous stereo radio at this fabulous low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to "lock-on" to an external drift. U stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12" wide x 8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £28-00 Post and Packing 50p.

STEREO-DECODER
SIZE 2" x 3" x 1/2" ready built. Pre-alignment and tested. Sens. 20-500 mV for 0-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5-40 plus 10p. P. & P. Stereo beacon light if required 40p extra.

SPECIAL BARGAIN OFFER!
Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £8-00 + p. & p. 60p.

LATEST Hi Sensitivity Uni-directional slim-line condenser microphone as used by many professional. Very low acoustic feedback. Available by impedance or low impedance. State which required. £13-50 plus 25p P. & P.

LATEST ACOS GP91/18C mono compatible cartridge with 1/2 stylus for LE/EP/78. Universal mounting bracket. £1-46. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal Mounting brackets and turnover stylus. 70mV per channel output. ONLY £1-75 + 10p P. & P.

SONOTONE STARC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-27 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2-76. P. & P. 15p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for LE/EP/78. £1-60 P. & P. 15p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-47. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II
A top quality record player amplifier employing heavy duty double wound mains transformer, EOC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 8in. deep x 6in. high. Ready built and tested. PRICE £5-50. P. & P. 50p.
ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £6-70. P. & P. 60p.

HI-FI LOUDSPEAKER SYSTEM MK II

Beautifully made, simulated teal finish enclosure with attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" 8" bass unit, H.F. tweeter and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm impedance (state which).
OUR PRICE £9.50 each Carr. 90p
Cabinet Available Separately £5.00. Carr. 90p
Also available in 8 ohms with EM1 13" x 8" bass speaker with parasitic tweeter £8.00. Carr. 90p.

LOUDSPEAKER BARGAINS


6in. 3 ohm £1-25. P. & P. 15p. 7 x 4in. 3 ohm £1-40. P. & P. 20p. 10 x 6in. 3 or 15 ohm £2-10. P. & P. 30p. E.M.I. 8 x 6in. 3 ohm with high flux magnet £1-70. P. & P. 20p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3-60. P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with inbuilt tweeter and crossover network £4-65. P. & P. 30p. E.M.I. tweeter. Approx. 35". Available 3 or 8 or 15 ohms. £1-80 + 20p. P. & P.

BRAND NEW Bakers Loudspeakers at substantial discounts. 12in. 16w. H/D Speakers, 3, 8 or 15 ohms. State which. (Current production by well-known British maker. Now with Illux ceramic ferrobar magnet assembly £7-50. Guitar models: 25w £7-50, 35w £8-50. P. & P. 45p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 192g. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £6-80 each. P. & P. 34p.

NOW ALSO AVAILABLE: 8" 10 watts, r.m.s. 20 watt peak 40Hz-20,000Hz. Overall depth 1 1/2". Ideal for Hi-Fi or for use in cars. £4-32 + 25p P. & P.

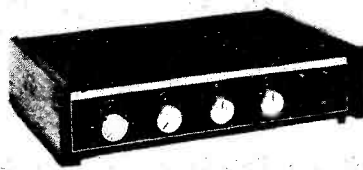HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise, level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 3 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1-0 amp. Overall size 12" w. x 8 1/2" x 2 1/2" h.

Fullly detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

AMPLIFIER KIT £12.96 P. & P. 30p
(Magnetic input components 33p extra)


POWER PACK KIT £4-32 P. & P. 40p
CABINET £4-32 P. & P. 40p

(Post Free if all units purchased at same time)

Full after sales service

Also available ready built and tested £28-08. Post Free.

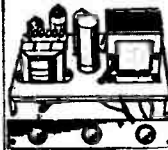Note: The above amplifier is suitable for feeding two mono sources into input \pm v. mikes, radio, turn record decks, etc. and will provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.




3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" h. Incorporates EOC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £6-50. P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc £5-50 P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls. And separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EOC83, EF85 and E280 rectifier. Simple instruction booklet 15p + SAE (Free with parts!) All parts sold separately. ONLY £10-25 P. & P. 60p. Also available ready built and tested £14-00 P. & P. 70p.

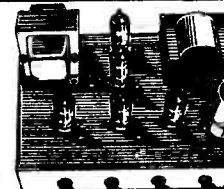

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3-50. P. & P. 25p.

PRICES INCLUDE VAT

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station.
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

**Fully guaranteed
Individually packed
VALVES**

A1065	1.25	ECL80	55p	GZ34	70p	PY80	40p
AR8	55p	ECL82	35p	GZ37	1.00	PY81	40p
ATP4	40p	ECL83	70p	KY26	2.50	PY82	40p
B12H	43.00	ECL86	50p	KT88	23.00	PY83	40p
CY31	50p	EF96	65p	MH4	75p	PY88	45p
DAF96	55p	EF37A	1.20	ML6	65p	PY500	1.00
DF96	55p	EF89	30p	OA2	45p	PY800	45p
DK96	70p	EF40	75p	OB2	45p	PY801	50p
DL2	40p	EF41	35p	PABC80	40p	QV03-10	1.40
DL96	60p	EF183	35p	PCF80	40p	QQV06-40A	28.00
DY86/87	EF83	1.25	PC900	50p	R19	60p	
DY802	45p	EF86	35p	PCC85	40p	RC1/400	60p
E88CC/01	1.20	EF89	30p	PCC88	60p	SC1/760	23.00
E180CC	70p	EF92	50p	PCF89	60p	SP61	75p
E182CC	70p	EF95	40p	PCF89	60p	TT21	25.00
EA50	40p	EF184	35p	PCF84	40p	U25	85p
EABC80	40p	EF1200	75p	PCF84	40p	U26	75p
EAF42	75p	EL34	70p	PCF86	60p	U27	60p
EB91	30p	EL36	60p	PCF201	75p	U191	75p
EB33	1.00	EL82	55p	PCF80	50p	U801	75p
EB41	75p	EL37	1.10	PCF80	50p	U802	75p
EBF80	40p	EL41	80p	PCF80	50p	U803	75p
EBF83	50p	EL41	80p	PCF80	50p	U804	75p
EBF89	40p	EL84	30p	PCF80	50p	U805	75p
EC52	35p	EL85	60p	PCF80	50p	U806	75p
EC81	40p	EL86	45p	PCL81	45p	UAF42	65p
EC82	35p	EL90	45p	PCL83	65p	UBC41	80p
EC83	35p	EL90	45p	PCL83	65p	UBF80	40p
EC84	35p	EL90	45p	PCL83	65p	UBF89	40p
EC85	40p	EM81	60p	PCL86	50p	UBL1	1.00
EC86	90p	EM80	50p	PCL80	60p	UBL21	70p
EC88	50p	EM84	40p	PCL200	70p	UCC85	45p
ECC189	70p	EM87	1.00	PL36	70p	UCH42	75p
ECF80	40p	EY51	45p	PL81	50p	UCH81	45p
ECF82	40p	EY81	45p	PL82	50p	UCL82	45p
ECF801	75p	EY86	40p	PL83	45p	UCL83	65p
ECH35	1.40	EY88	50p	PL84	45p	UF41	70p
ECH42	80p	EZ10	70p	PL504	80p	UF80	35p
ECH81	35p	EZ20	30p	PL508	1.00		
ECH83	45p	EZ81	30p	PL509	1.15		
ECH84	45p	EY301	75p	PL802	1.15		
				PY33	60p		

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

TRANSISTORS, DIODES etc.

AC 113	AF 139	BSY 27	OA 202	OC 200	2N 3053
AC 126	AF 178	BSY 38	OA2 200	OC 206	2N 3054
AC 127	AF 186	BSY 95A	OC 22	OC 206	2N 3055
AC 128	AF 172	BYZ 16	OC 25	OC 26	2N 3391
AC 176	ASV 26	CRS 1/10	OC 26	ZR 21	2N 3730
AC 19	ASV 27	CRS 1/20	OC 29	LN 25A	2N 3819
AC 19	ASV 28	CRS 1/30	OC 29	LN 25	2N 4088
AC 20	BC 108	CRS 1/40	OC 29	LN 32A	2N 4088
AC 28	BC 118	CRS 3/10	OC 36	LN 38A	2N 4061
AC 39	BC 119	CRS 3/20	OC 42	LN 43	2N 4785
AC 40	BC 136	CRS 3/30	OC 44	LN 70	2N 5295
AD 149	BC 137	CRS 5/40	O 45	LN 277	3N 128
AD 161	BC 148A	CRS 25/C25	OC 70	LN 415 1/2	3N 154
AD 162	BC 172A	GET 115	OC 73	LN 4149	3N 135
ADZ 11	BC 172	GET 116	OC 78	2N 466A	2N 303
ADZ 12	BC 212A	GEX 66	OC 78 D	2N 708	404
AF 114	BCY 31	NKT 222	OC 81	2N 918	2082
AF 115	BCY 33	OA 5	OC 82	2N 1304	40251
AF 116	BCY 72	OA 7	OC 82 D	2N 1305	40250
AF 117	BF 115	OA 70	OC 82 DM	2N 1307	0664
AF 118	BF 167	OA 71	OC 83	2N 1309	
AF 124	BF 185	OA 73	OC 130	2N 2062	
AF 125	BFY 51	OA 79	OC 140	2N 2147	
AF 126	BFY 52	OA 91	OC 170	2N 2411	
AF 127	BFY 90	OA 200	OC 172	2N 2989	

UF85	45p	1R5	40p
UF89	50p	1S4	30p
UL41	70p	1T4	30p
UL84	40p	1X2A	60p
UY41	45p	1X25	75p
UY85	40p	2D21	25p
VR105/30	45p	2K25	25.00
VR150/30	45p	3A4	60p
X61M	1.40	3D6	40p
X66	65p	3V4	85p
Z800U	22.70	5B255M	44.00
Z801U	22.70	5Z4	80p
Z900T	21.20	6A87	80p
1A3	55p	6AR6	70p
1L4	25p	6AX4GT	75p
		6AK5	40p
		6AK8	40p
		6AL5	30p
		6AL5W	55p
		6AM6	60p
		6AV4G	55p
		6B8E	40p

**V.A.T. —
Please add 8%
to all orders**

5Y3GT	55p	6AQ5	45p
6B76	65p	6AQ5W	70p
6BQ7A	60p	6A86	80p
6BR7	1.20	6AT6	45p
6BW7	1.00	6A7B	80p
6C14	40p	6AV6	45p
6C6	50p	6AX4GT	75p
6CB8	50p	6B8E	40p
6CH6	1.45	6B76	65p
6CL6	75p	6B77	55p
6D6	55p	6K5GT	60p
6E8	85p	6K25	1.00
6F7	1.10	6L6	1.90
6F8G	75p	6L6G	40p
6G23	90p	6L7G	40p
6F32	75p	6SA7	50p
6F33	23.50	6SA7GT	40p

6H6	35p
6J4WA	1.25
6J5GT	50p
6J6	80p
6J7	60p
6K7	55p
6K8	60p
6K9	60p
6L7	50p
6L8	50p
6L9	50p
6M7	50p
6M8	50p
6M9	50p
6N7	50p
6N8	50p
6N9	50p
6O7	50p
6O8	50p
6O9	50p
6P7	50p
6P8	50p
6P9	50p
6Q7	50p
6Q8	50p
6Q9	50p
6R7	50p
6R8	50p
6R9	50p
6S7	50p
6S8	50p
6S9	50p
6T7	50p
6T8	50p
6T9	50p
6U7	50p
6U8	50p
6U9	50p
6V7	50p
6V8	50p
6V9	50p
6W7	50p
6W8	50p
6W9	50p
6X7	50p
6X8	50p
6X9	50p
6Y7	50p
6Y8	50p
6Y9	50p
6Z7	50p
6Z8	50p
6Z9	50p

Colomat ALL valves guaranteed

6SU7-1	40p	25LGT	70p	6064	60p
6SG7	50p	30C15	1.00	6065	1.00
6SJ7	55p	30C17	1.00	6067	70p
6SK7GT	35p	30C18	90p	6068	22.30
6SK7	55p	30F5	1.00	6148	23.25
6SL7GT	50p	30FL1	1.00	6148B	23.25
6SN7GT	50p	30FL2	1.00	8020	25.00
6SQ7	55p	30P11	1.10	9001	25.00
6V6GT	50p	30P14	90p	9002	50p
6X4	40p	30L15	95p	9003	70p
6X6G	40p	30L17	95p	9004	35p
6X3GT	50p	30P12	1.00	9006	35p
6Y6G	90p	30P19	1.00		
6Z4	65p	30P11	95p		
6-30L2	90p	30P13			
7L7	80p		1.10	C.R. Tubes	
7Y4	80p	30P14	1.10	DG7-5	
9D6	40p	35L6GT	75p		1.10
11E2	26.00	35W4	50p	DG13-2	
12A6	55p	35ZAGT	70p		1.10
12AT6	45p	50C5	60p	MW13-35	
12AT7	40p	60CD6G			235.00
12AU7	35p		1.10	VCR139A	
12AV6	50p	75	1.00		28.00
12AX7	85p	75C1	75p	3BP1	24.50
12BA6	45p	76	75p	8D	29.00
12BE6	50p	78	70p	8S1	28.00
12BH7	50p	80	75p	8SL	29.00
12C8	55p	85A2	75p		
6BR7	1.20	6J5	65p		
6BW7	1.00	6J5GT	50p		
6C6	50p	6K7	55p		
6CB8	50p	6K8GT	80p		
6CH6	1.45	6K7	55p		
6CL6	75p	6K7G	30p		
6D6	55p	6K5GT	60p		
6E8	85p	6K25	1.00		
6F7	1.10	6L6	1.90		
6F8G	75p	6L6G	40p		
6G23	90p	6L7G	40p		
6F32	75p	6SA7	50p		
6F33	23.50	6SA7GT	40p		
6H6	35p				
6J4WA	1.25				
6J5GT	50p				
6J6	80p				
6J7	60p				
6K7	55p				
6K8	60p				
6K9	60p				
6L7	50p				
6L8	50p				
6L9	50p				
6M7	50p				
6M8	50p				
6M9	50p				
6N7	50p				
6N8	50p				
6N9	50p				
6O7	50p				
6O8	50p				
6O9	50p				
6P7	50p				
6P8	50p				
6P9	50p				
6Q7	50p				
6Q8	50p				
6Q9	50p				
6R7	50p				
6R8	50p				
6R9	50p				
6S7	50p				
6S8	50p				
6S9	50p				
6T7	50p				
6T8	50p				
6T9	50p				
6U7	50p				
6U8	50p				
6U9	50p				
6V7	50p				
6V8	50p				
6V9	50p				
6W7	50p				
6W8	50p				
6W9	50p				
6X7	50p				
6X8	50p				
6X9	50p				
6Y7	50p				
6Y8	50p				
6Y9	50p				
6Z7	50p				
6Z8	50p				
6Z9	50p				

MINIMUM POSTAL ORDER £1. PERSONAL CALLERS WELCOME.
OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K.
Postage Up to £2 12p, £2-23 22p. Over £3 post free. C.O.D. 25p extra.

29/41FT. AERIALS each consisting of ten 3ft., 7in. dia. tubular screw-in sections. 11ft. (8-section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect, in canvas bag. £7.50 new. Carriage £1.50.

VALVES AND TRANSISTORS
Telephone enquiries for valves, transistors and special retail trade and export 743 0899.

Colomar (Electronics) Ltd.
170 GOLDHAWK ROAD, LONDON W12.
Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

**YOUR CAREER in
RADIO &
ELECTRONICS ?**

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers


it has a four-digit display of which the first (most significant) digit can only be 0 or 1. A variation of this can occur where, as in the DM2, the leading (left hand) zero is suppressed to avoid displaying unnecessary information which might confuse the operator. In this case the first digit is either a blank or a 1. The result in either case is to extend the indication range of the instrument from 0-999 to 0-1999, a very useful extension requiring the minimum of additional circuitry.

The readout in the DM2 uses four 8mm (0.3in.) 7-segment I.e.d. displays; the necessary decoder and driver circuits are included in the custom LSI chip. Two sets of push-buttons select the five functions—a.c. voltage and current, d.c. voltage and current, and resistance—and the four range multipliers from 1 to 1000. Automatic dual-polarity operation is incorporated, as is automatic over-range and overload indication. In each case the relative information appears in the I.e.d. display on otherwise unused segments of the most significant digit.

Power supply

For convenience and portability, the instrument is battery powered, up to 60 hours of use being obtained with a single standard PP9 or equivalent. Sockets are provided at the rear of the instrument for an external power supply. This must provide a stable 9V with a current capability of 70mA average, 150mA surge. One minor criticism is that these sockets are unlabelled as to function or input requirements*. An instrument which is so easily operated is likely to be quickly separated from its operating instruction leaflet, which clearly

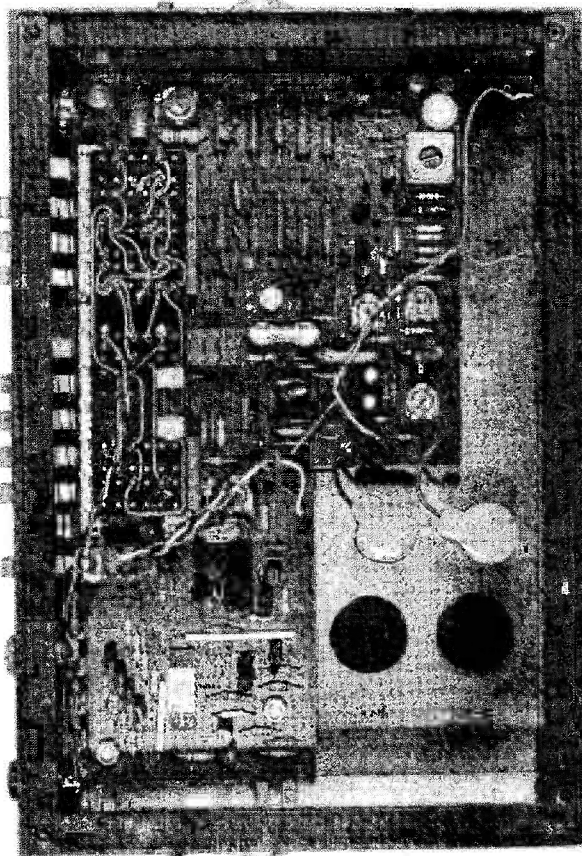* Sinclair tell us that these sockets will be clearly identified in future production.



This photograph shows the uncluttered interior layout. Interconnections on the push-button switch banks are made via a small subsidiary p.c.b.

★ Maker's specification

D.C. VOLTAGE

Range	Resolution	Accuracy
1V	1 V	0.3% ± 1 digit
10V	10mV	0.5% ± 1 digit
100V	100mV	
1000V	1V	

A.C. VOLTAGE

Range	Accuracy
1V	1.0% ± 2 digits
10V	
100V	2.0% ± 2 digits
1000V	

D.C. CURRENT

Range	Resolution	Accuracy
100µA	0.1µA	2.0% ± 1 digit
1mA	1µA	0.8% ± 1 digit
10mA	10µA	
100mA	100µA	
1000mA	1mA	2.0% ± 1 digit

A.C. CURRENT

Range	Accuracy
1mA	1.5% ± 2 digits
10mA	
100mA	
1000mA	2.0% ± 2 digits

RESISTANCE

Range	Measuring Current	Accuracy
1kΩ	1mA	1.0% ± 1 digit
10kΩ	100µA	
100kΩ	10µA	
1000kΩ	1µA	
10MΩ	0.1µA	2.0% ± 1 digit

* Maximum input on a.c. voltage is 500V.

† Additional ranges, obtained by special switching combinations.

TYPICAL TEMPERATURE COEFFICIENTS

D. ranges	0.03% per °C
A.C. ranges	0.05% per °C
Resistance ranges	0.05% per °C

OPERATING TEMPERATURE RANGE

0°C to +50°C

SIZE

Height	56mm (2.2in.)
Width	225mm (8.8in.)
Depth	155mm (6.1in.)
excluding knobs, feet and handle	

WEIGHT

1kg (2.2 lbs) excluding battery


warns that no more than 10V must be applied. This omission would seem to be a potential source of damage. A separate a.c. mains power unit giving a suitable 9V supply is available from Sinclair.

The basic measurement range of the instrument is 1V d.c., giving a resolution of 1mV with over-range to ±1.999V. A m.o.s.f.e.t. operational amplifier input stage achieves an input impedance of 100MΩ on this range; the voltage divider chain reduces this to 10MΩ on the other d.c. voltage ranges. A mean averaging a.c. to d.c. converter is used for the a.c. voltage and current ranges. Its frequency range is 20Hz-3kHz on voltage ranges up to 100V, 20Hz-1kHz on the 1000V and current ranges.

The DM2 can safely withstand a considerable overload on the lower voltage and current ranges, while fuse protection is incorporated for the current and resistance ranges.

continued on page 70

65

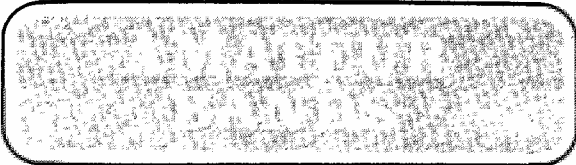

by Eric Dowdeswell G4AR

JUST a few words this month on the log extracts that appear at the end of this feature. Probably the majority of listeners to the amateur bands get drawn into the exciting race of hearing, and getting confirmation, of as many different countries as possible, thereby qualifying for various certificates and awards. The log extracts given here are designed to highlight the more unusual stations and prefixes that appear on the bands and thus enable vacancies to be filled in our 'wanted' list, be they countries or prefixes. Modern DXpeditions frequently take unto themselves a special call sign to make their appearance doubly attractive.

To those of you who are kind enough to send in logs for this column may I ask that you restrict your entries to stations that come within the above category? Six a month would be exceptional!

John Porter (Baslow, Derbys) concentrated on 20m CW and I wonder if John has noticed that his best DX tends to be in a north/south line as befits his east/west dipole. Could be missing something good off the ends! Tim Charles (Colchester) tells us about TI2CF due on from the Cocos Isles, for a rare one, with SSB on the usual bands plus CW on Top Band! Don't laugh, it's not impossible! Not long ago KV4FZ managed to work all continents (WAC) in eight hours on this band! Tim also mentions that the Gambia has dropped ZD3 in favour of C5.

Paul Heath (Wolverhampton) bemoans the "pretty hopeless reception other than 80m" but with an R1155 I'd tend to suspect the receiver rather than conditions! Paul is in the process of doing some rewiring to it so let's hope for better things. Mike Green (Northwich) suggests that Max France might do better with Oscar if he used crossed dipoles instead of verticals. Agreed, but even better is some simple way of tracking the satellite, perhaps a handheld aerial, in order to increase the period of reception. Andrew Swiffin A8603 (Cheadle) has now got a crystal-controlled converter for the HF bands, feeding into a PW design as a tuneable IF. This is a very efficient way of ensuring success on these frequencies if the main receiver is not too hot.

Paul Broadhurst (Near Clevedon) stuck to 80m and found A51TY in Bhutan and YB0AAG in Djarkarta for a couple of interesting prefixes. His 150ft wire feeds a Trio 9R59DS and PR40 pre-selector. Steve Blake (Aylesbury) has moved to "join the men up on VHF"! Hey, that's not nice at all! A 6-element Yagi feeds a converter into his Codar CR70A at 28 to 30MHz.

Graham Bleakley QSL/Publicity bod for the West of Scotland ARS GM4AGG reports demolition of the club's premises so write to him at 82 Ash Road,

Cumbernauld, Dumbartonshire for current details of venues and club meetings. Alan Rae (Glasgow) has now got his Morse up to a decent speed and found some goodies that he had previously missed. Those who take the trouble to learn the code are rewarded with a completely new world of interest, virtually another language. Roger London A8673 (London SE2) was one of several who copied the jungle outfit of HP1XJS/P/HP7 for an unusual catch, this time on 15m SSB.

Peter Walton (Llanfair P. G., Gwynedd) at 12 years of age is our latest recruit, with an Eddystone 358 and 85 ft of wire. Stephen Budd A8713 (Worthing) was worried at not being able to give me the frequencies of stations to better than 10kHz on his AR88. Not to worry Steve, since very few stations are crystal controlled nowadays. Listen for the sudden rise in the QRM, the DX will be underneath, in what was a quiet slot a few minutes previously! Again from Tim Charles, "phew, 45 minutes to copy out the log." This time I can't say that there are any ordinary ones in his list, ranging from 160 to 2m, with the exception of 10 and 15m. He likes to listen through the GB3PI repeater on 2m but finds it jammed up whenever there is a lift in conditions.

Graham Nicholls G4DLB (Banbury) has stuck to working stuff on 2m and 70cm on CW, SSB and FM and enjoyed the recent good conditions enabling him to get into SM on 2m and PA0 on 70cm. M. C. P. Bennett (Slough) mentions the CG3 stations, normally VE3, in Listowel, Canada, celebrating some town event! Any more candidates for the "How stupid can you get?" competition??

Log extracts

M. Green:— 80m HK3LT ZL1BCC 5U7AH 20m TU2DP VP8HZ JY9CR (POB 2788 Amman) 15m A4XFE HZ1AT VQ9BP

J. Porter:— 80m A2CCY 8P6ES 20m CT2BP PJ3SF ZD8TM 5T5FP 15m ZD8TM

A. Doherty:— 80m HC2YL VQ9M PZ1AE 20m VK9ZQ 8P6ES 15m EP2SN KV4AD 80m TA3HB VP9GD XW8FA YB0ABV 5U7AH

A. Swiffin:— 80m PJ3DO VU2DGD 20m CT3AR EA9FB VE8RCS

P. Broadhurst:— 80m A51TY CT2AE YB0AAG 5B4BC 9G1DY

S. Blake:— 2m F1DJR GI8EWM GM8FFX SM6DKU

P. Barker:— 80m A4XVB 20m PZ5FB TA2SC TJ1AD VS5MC 20m (SSTV) DJ4SS EA4DT HA2KRB I8MQC OH5RM YU2CDS

A. Rae:— 160m PY1RO 80m AP2KS ZB2CF ZL4KF

S. Budd:— 80m 7X0EEG 20m CR4BS FL8DA JY9CR VQ9BP 4W1GM 15m WB2POJ/VQ9

G. Nicholls:—2m worked ON5NY OZ10F SM7AED 70cm worked G3KMS GW3UCB/P

M. Bennett:— 80m A4XVC ET3ZU HK4WWB VS5MC 9M2BU 20m EL5G HR6SWA HV1CN HV3SJ TU2EP 15m A4XFU HZ1AT TJ1AD

M. Sole:— HZ1TA MII PY6AHM TR8DG XU1DX ZL3PE 3V8BU 40m ZL1AQ

T. Charles:— 160m KV4FZ KZ5WA VE1WE ST2AY W2KH WA4GTB W6UD WB8APH 80m FL8DN HC2TR KZ5WA KL7DRT KS4IZ TG8KT XE3LK YS2HM ZL1BEA 5N2ESH 5T5DY 8R1AG 40m CO2NV XE6WHK ZD3P ZL1FM 20m C5AR (Gambia) KC4AZ VP8NP XT2AE 2m DC2BE GC4ASO SM6FBQ

Stations SSB except those in bold which are CW.


SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35	£6.60	Carriage free	★ 25Hz-25kHz
35W RMS 25-50V			★ 0.2% distortion
7 transistors, 7 diodes			★ Noise—80dB
SA50	£8.50	Carriage free	★ 500mV into 20K
50W RMS 25-65V			★ 4-16 ohms
7 transistors, 7 diodes			★ Simple wiring
SA100	£12.50	Carriage free	★ Short and open circuit proof
100W RMS 45-70V			★ Continuously rated
10 transistors, 7 diodes			★ Top-grade components

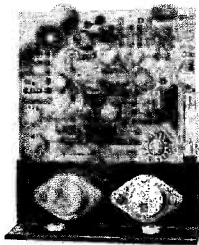120 watt module complete with built-in supply—extra heavy duty **£24.75** Carr. 60p



THE SA100 MODULE


POWER SUPPLIES

UNSTABILISED—READY WIRED & FUSED	
PU45	Suits 2 SA35 or 1 SA50 (4 ohm) £6.50 Carriage 50p
PU70	Suits 2 SA50 (8 ohm) or 2 SA100 £9.50 Carriage 60p
STABILISED	
PS45	Suits 2 SA35 or 2 SA50 (4 ohm) £5.50 Carriage free
MT45	Transformer for above £3.90 Carriage 50p
PS70	Suits 2 SA100 £6.50 Carriage free
MT70	Transformer or above £5.50 Carriage 60p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £29.50 Carr. 60p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, base, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep.

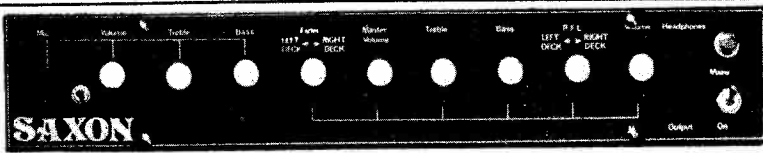

DISCO MODULE £12.50 Carr. 50p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: h/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £24.75 Carr. 50p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!


ADD 8% VAT TO ALL ORDERS



SINGLE CHANNEL VERSION £7.90 Carr. free
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation.

MULTI-PURPOSE MIXERS

M4HL £25.00 Carr. 60p **M6HL £35.00 Carr. 60p**
Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

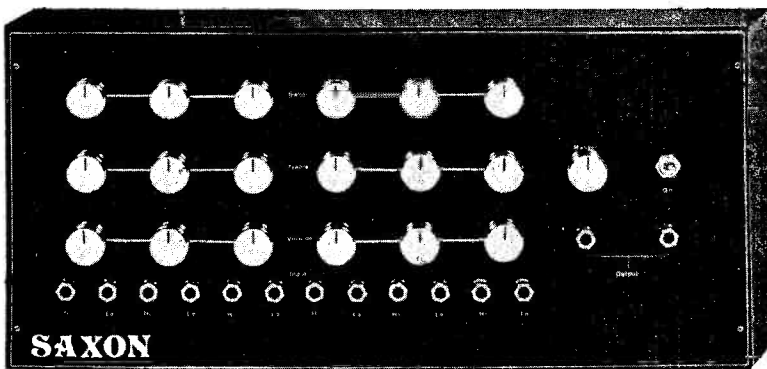

VA30 CHANNEL MODULE £3.90 Carr. free
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)

SAXON CSE 100 COMPLETE AMPLIFIER

£39.90 Carr. 60p

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE50 £33.00 Carr. 60p

NEW !!

SAXON MULTIMIX 100 £57.00 carr. £1.00

100W rms four inputs slider controls plus master slider. Wide range bass and treble controls. Fantastic value, ideal for complete disco's, groups, clubs etc. **SAXON MULTIMIX 50**—Exactly as above but 50W rms. **£45.00**

CALLERS AND MAIL ORDER

SAXON ENTERTAINMENTS LIMITED

327-333 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m.—5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.—3 p.m. 24-HOUR ANSWER SERVICE. TEL. 01-684 6385. TECHNICAL ENQUIRIES: 01-684 0098.

SEND 10p FOR OUR 26 PAGE MANUAL—full circuits & details.

TERMS OF BUSINESS: C.W.O. C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.


Please send S.A.E. with all enquiries.

VAT @ 8% must be added to all orders including carr. charges.

With a kit as complete as this, all you need add is a little time.



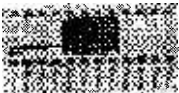You may have found, from past experience, that your definition of 'complete' is not quite the same as other people's. And your so called complete kit comes minus a cabinet, or knobs, or a multitude of other bits and pieces.



That won't happen with a Heathkit. Take our very popular digital alarm clock kit. Every part you need will be there, right down to the solder. And you'll also receive a very easy to understand instruction manual that makes light work of assembly.

In fact all you need are a few basic tools and a few enjoyable hours of your time.

After which you may like to try your hand at our AR-1214 stereo receiver. Or even a TV.



And how about an ultrasonic burglar alarm disguised as a book?

Or, for a bookful of other ideas, just clip the coupon and we'll send you the Heathkit catalogue.

Otherwise call in and see us at the London Heathkit Centre, 233 Tottenham Court Road.

Or at our showroom in Bristol Road, Gloucester.

You'll find it well worth your time.

Heath (Gloucester) Limited, Dept. PW-55,
Bristol Road, Gloucester, GL2 6EE.
Tel: Gloucester (0452) 29451.



To: Heath (Gloucester) Limited,
Dept. PW-55, Gloucester, GL2 6EE.
My free Heathkit catalogue, please.

Name _____

Address _____

Postcode _____

Remember easy terms are available
with the Heathkit Monthly Budget Plan.



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner
than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE DEPT. CPW05 READING RG7 4PF

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

Name _____

Address _____

POST CODE _____

CPW05

BIET

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



MEDIUM WAVE DX

by CHARLES MOLLOY

THE Newfoundland station CJON on 930kHz was my first Transatlantic DX contact ever, on November 9th. In January reception was fairly consistent and only on three of the nights that I stayed up to 0200 was the station unreadable" writes **Steve Whitt** from NW London. Steve uses an HRO communications receiver with a 40ft outdoor aerial to pull in his medium wave DX which includes CBM in Montreal on 940kHz with a news bulletin and WNEW in New York City on 1130kHz with a basketball commentary. Transatlantic reception in the UK starts about six hours after sunset and even during the summer months reception is possible for an hour before sunrise.

Roy Patrick reports again from his new QTH at Mackworth in Derby with a fine log of reception from both North and South America, West Africa and the Middle East. His receiver is a Trio 9R59D and he logged Morocco on 818kHz CJCH in Halifax, Nova Scotia on 920kHz at 0215, CJON St. John's on 930kHz at 0145, Radio el Mundo in Buenos Aires, Argentina on 1070kHz at 0240, Voice of America in Rhodes on 1259kHz with sign-on at 0300, Kuwait with Arabic music at 0250 on 1345kHz and Conakry in Guinea on 1403kHz at 0020. Roy mentions hearing a broadcast in Arabic on 1205kHz which is almost certain to be Radio Sanaa in the Yemen Arab Republic, a fine catch.

SHORT WAVE BROADCASTS

by **Derek Bell**

WE have been set a challenge this month by **John Godwin** from Rugeley. He wants us to try for, as he puts it, "the elusive ZL3" this is a 7 $\frac{1}{2}$ kW station in New Zealand. Mr. Godwin's method is to try Radio Australia on the 25m band to see if the path is open. Then he tunes 15kHz higher to 11780 and listens for a very weak signal. John reports that it usually has rapid flutter and that he has to have everything screwed up tight on his pre-war HRO receiver and dare not even breathe too deeply for fear of losing it! The best time is 0845 to 0930 and the address for a QSL is: New Zealand Broadcasting Corp., P.O. Box 2396, Wellington 1 N.Z., but please send two International Reply Coupons to pay for the return postage.

"Nothing special here but the best I can get." So says **Eric Chowanietz** of Braunstone, Leicester. He then goes on to list the following:

T.R.T. Voice of Turkey on 11880 at 2300

Radio Cairo on 9700 at 2245

Radio Finland on 9555 at 1620.

All this on a Fidelity Comet transistor set. Reader **Bob Stone** from Plymouth writes to enquire if any one knows of a "Radio Dominicana" on 5967. The only one I can trace is Radio TV Dominicana of Santo Domingo in the Dominican Republic. The trouble is that as far as I can see their only outlet is on the medium wave. **Christopher Hasman** is the

Harold Emblem of Mirfield in Yorkshire is still active on the medium waves with his Eddystone 730 receiver and medium wave loop aerial. He has logged four Canadian stations, CBN St. John's in Newfoundland on 640kHz, CBH in Halifax, Nova Scotia on 860kHz, CJON St. John's on 930kHz and CHNS in Halifax on 960kHz together with Radio Sahara in Spanish Sahara on 656kHz. Others include Radio Andorra on 701kHz, Bagdad on 760kHz, Yerevan, Armenia on 863kHz, Rajkot, India on 1070kHz and Conakry, Guinea on 1403kHz. Harold reports hearing Tashkent, Uzbekistan well at 0300hrs on 908kHz over Thourah, Iraq on the same frequency.

Fred Dinning of Dunlop, Ayrshire has sent an outstanding log of North American DX. Using his SP600 receiver, 6000ft(!) Beverage aerial and medium wave loop he logged 72 stations in Canada and the United States between 0300 and 0800 during the first week of January. The most notable logged are WMAQ in Chicago on 670kHz, WOR in New York City on 710kHz, WSB Atlanta, Georgia on 750kHz, WJR in Detroit on 760kHz, WBBM Chicago on 780kHz; WGY Schenectady, NY on 810kHz, WBAP Fort Worth in Texas on 820kHz, WCCO Minneapolis on 830kHz, WHAS Louisville, Kentucky on 840kHz, KOA Denver, Colorado on 850kHz, WWL New Orleans on 870kHz, WLS Chicago 890kHz, WCFL Chicago 1000kHz, KDKA Pittsburg on 1020kHz, WHO Des Moines on 1040kHz, CHUM Toronto on 1050kHz, KING Seattle on 1090kHz, KMOX St. Louis 1120kHz, KSL in Salt Lake City on 1160kHz and WOAI San Antonio, Texas on 1200kHz. Fred's log is an indication of the improved conditions on the medium waveband now that we are approaching the minimum of the sunspot cycle, expected in 1976. Medium wave DXers can confidently look forward to a return of the outstanding DX of ten years ago when a few of the more common North Americans were, on occasion, heard in this country on transistor portables.

proud new owner of a Bush VTR178 and he takes us into the realms of inner space by logging the last Russian space flight between 121 and 146 MHz. This was achieved using a BBGI TV aerial. Christopher also informs us that the US-Soviet joint flight in July will be using the same frequencies. However, sadly, the TV aerial has gone back to its rightful owner and Christopher is appealing for help.

An example of the "giveaway" comes from **Frank Allen** of Ilfracombe. On his QR666 he logged and QSLed Radio Pyongyang on 6576 at 2000 and they replied by sending two ten-inch double sided LP records of an opera based on a hospital at war, along with a multitude of books and stamps. The QR666, by the way, is the replacement for the phased out Trio 9R59DS and costs a lot more than the old workhorse! A self-confessed crystal-set addict is **Andrew McIntee** of The Schoolhouse, Craichie, Forfar. This gallant Scot owns three of them and has pulled in, among others:

Radio Messiah on 6050 at 1915.

This is a new one on me, can anyone give some more gen. **Arthur Bell** is no relation, honestly, but by chance he picked up PW and got hooked on the SW page. Being, as he says, a greenhorn he admits to being all at sea with the frequency figures. These are always in megahertz, Arthur, and the times are always twenty-four hour clock and given in Greenwich time only. The hertz equals one cycle per second, thus a megahertz equals the old megacycle.

The metre band system used by some stations, covers a small segment of the spectrum. For example, the twenty metre amateur band runs from 14 to 14.350 MHz or over 350kHz. Regarding a list of stations of the world, the "Radio and TV Handbook" published by Billboard Publications should fill the void. Finally, I can say, Arthur, that to log Radio Australia on an Astrad 17 is pretty good going!

A letter that came some time ago but unfortunately had to be held back was from **G. E. W. Hewlett**. This gentleman has been DXing since (would you believe) 1928! He built a one-valve receiver and later added it to another rig in order to improve them both. This was done by plugging the first set, as an RF amplifier, into the detector valve socket of the second. As a result of this a QSL came from VK3LR, or, as it later became, Radio Australia. Since then Mr. Hewlett has become a confirmed radio fan "down under" and can quote, at the drop of a hat, all the times and frequencies of this far-away station. In fact, Mr. Hewlett sometimes spends up to eight hours a day monitoring the VK's.

My enquiries recently about FEBA in the Seychelles seem to have borne fruit. I have beside me a logging by **Roy Wooden** of Staines who reports FEBA on 11715 and says that it puts out English on Tuesdays and Wednesdays from 1745 to 1800. However, Roy advises us to get in soon as the service to the Middle East will be phased out and more emphasis will be placed on the Far Eastern, South African and Indian Ocean islands, with, perhaps, the loss to us here in Europe of this signal.

Having written the above about "us here in Europe", I was surprised to have in the mail an air

letter from **David Samuel** in Johore Baru, Malasia. David comes to the aid of our recent enquirer who had a daughter in Thailand and sends the tip that perhaps she listens to the BBC World Service from the Malasia relay. Many thanks David for the welcome gen. Another reply to an enquiry comes from **John Dipré** of Stoke Newington, London. He would like to help our reader who was suffering from "anaemia" of the 60m band so, if Glenn Tobin is interested, John will make all as clear as crystal for him. John reports thirteen different countries on the band using a VEF204. Among them Honduras, Costa Rica, Togo and the Sudan. Pass your secret on, John, and we will all share it!

From the steel town of Sheffield comes **David Williams** to give us the low-down on the 2.5, 5, 10 and 15MHz fixed frequency time signals. He writes that the United States Bureau of Standards puts out signals on these frequencies from stations in Hawaii and Washington with IDs. on the hour. The voice ID from Hawaii is a woman (or xyl, as they say) and a man from Washington. Turning now to station news Radio Portugal recently announced that they are to stop QSLs until further notice, but that they hope to start a DX show soon, while Radio Baghdad has started to send out copper emblems with some of their QSLs. The one and only "Happy Station" on Sunday from Radio Nederland, has announced an alternate frequency of 5965, the old ORTF slot. RN has also been testing on 5955 from 0930 to 1050 and would like reports. A new DX show starts soon on Liverpool's local "Radio City." This station moves into VHF in February and the DX show is on the late night show, alternate Sundays, in the "wee small hours."

—continued from page 65

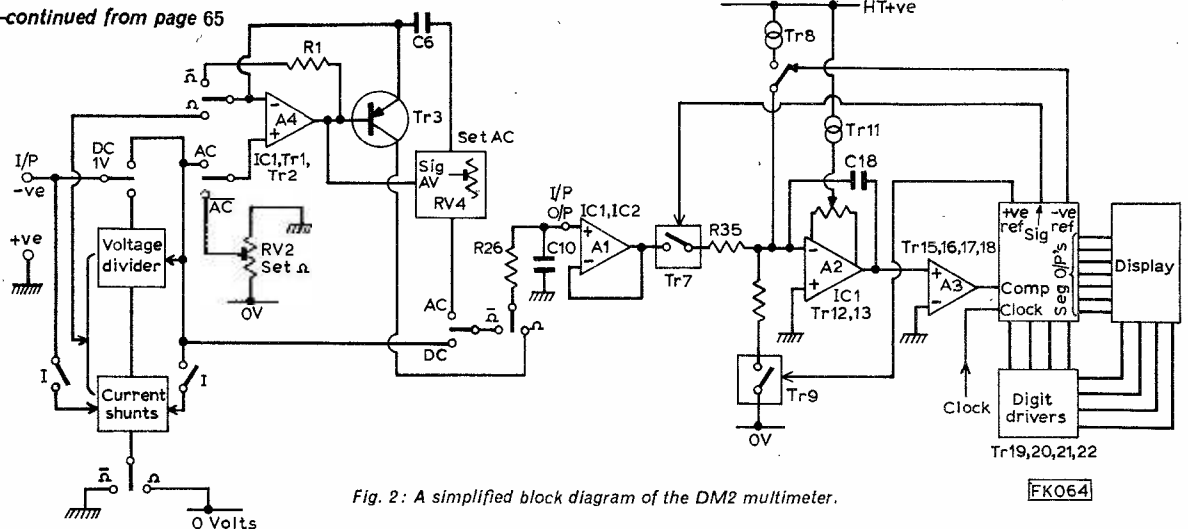


Fig. 2: A simplified block diagram of the DM2 multimeter.

Your reviewer has been using a DM2 for about three months for servicing and experimentation and has found it reliable and easy to use. The display is quite bright and is fitted with a violet filter to improve its contrast. Even so, if your workbench is near a window or has a good bench-lamp you will find that you need to tuck the meter away in a shady corner for easy reading.

Complete screening of the instrument is provided by the case, based on robust aluminium extrusions. The dual purpose handle/bench stand is useful, as is the optional carrying case which allows the DM2 to be used slung around the neck.

In the absence of any suitable instruments for comparison, I cannot really comment upon the accuracy of readings

obtained except to say that a selection of 1% resistors checked out well and other results were always "as expected".

Sinclair offer their usual year's guarantee on the DM2. As they put it, "If it stops working, send it back and we repair or replace it free of charge."

The Sinclair Multimeter DM2 is available from retailers or direct from Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire PE17 4HJ. Recommended retail prices are as follows:—

DM2 complete with battery and test leads £59 + VAT
Carrying case £5 + VAT
Mains converter £2.95 + VAT.

POWER UNIT Type A126

Supplying 6, 7.5 or 9 Volt DC at 200 mA. In moulded case forming a 2 pin 5A mains plug.



2 metre output lead with 4-way multiplex giving 2.1 and 3.5 mm sockets and 3.5 mm plug. Price £2.30. Post 10p.

2" and 4" PANEL METERS

SIZE: 60mm Wide x 45mm High x 40mm Deep. I.R. Movement

Ohms	0-50 micro A.	0-100 micro A.	0-500 micro A.	0-1 mA	0-5 mA	0-10 mA	0-50 mA	0-100 mA	0-500 mA	0-1 AMP	0-2 AMP	0-25 Volt	0-50 Volt	0-300 Volt	"g" Meter	VU Meter
1250	170	170	170	170	170	6	0.5	0.5	0.5	0.5	0.5	15K	50K	300K	170	5250
1400	200	200	200	200	200	6	0.5	0.5	0.5	0.5	0.5	15K	50K	300K	200	5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.15 Post 10p. Price 4" £4.15 Post 10p. Lamps 75p per set.

1/2 watt CARBON FILM RESISTORS

1 watt at 70°C E 19 range 10Ω - 1MΩ 5% tol above 470 KΩ 10% tol at 85p per 100.

C1000 MULTIMETER

Special Offer Compact General Purpose Mini Multimeter. Input Resistance 1000 ohms per volt



Ranges: AC Volts 0-15, 50, 250, 1000 V DC Volts 0-10, 50, 250, 1000 V DC Current 0-1 mA 0-100mA Resistance 0-150K ohms Size 60 x 24 x 90 mm Complete with Batteries, Test Prods, Instructions. Special price £3.25 Post 20p.

C1001 MULTIMETER

Input Resistance 20,000 ohms per volt Overload protection 150 μA movement, clear scale Ranges—AC Volts 0-10, 50, 250, 1000V DC Volts 0-5, 25, 125, 500, 2500V DC Current 0-50 mA Resistance 0-60 Kohms, 0-6 Mohms Decibels -20 to +22 dB Carrying Case, Test Prods and Batteries included. Size: 11.5 x 8.3 x 2.7 cm. Price £3.85. Post 20p.

TRANSFORMERS

CASED TRANSFORMERS

Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets, and are available with 110 volt or 240 volt output. (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices.

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA	Ref. No.	Price Cased	Price Plugs 2 Pin 1 Earth	Price Open	Post
60	149	7-35	0-20	4-00	0-38
100	150	8-22	0-20	4-60	0-52
200	151	10-20	0-20	7-40	0-52
250	152	11-68	0-20	8-88	0-65
350	153	14-10	0-20	10-80	0-60
500	154	15-88	0-20	12-38	1-00
750	155	24-83	1-00	18-72	1-20
1000	156	32-19	1-00	28-50	1-20
1500	157	38-18	1-00	30-34	O.A.
2000	158	45-20	2-40	34-88	O.A.
3000	159	68-50	2-40	53-35	O.A.

12 & 24 Volts Prim. 200-240V.

Amps	24V Ref. No.	Price	Post
0-3	0-15	2-42	1-84
0-5	0-25	1-11	0-22
1	0-5	2-13	1-58
2	1	7-71	2-09
4	2	18	2-58
6	2	70	3-80
8	4	108	4-20
10	5	75	4-80
12	6	116	5-21
16	8	17	6-22
20	10	116	9-47
30	15	187	11-95
40	20	232	13-22
50	30	226	15-30

30 Volts

Amps	Ref. No.	Price	Post
0-5	112	1-72	0-22
1	79	2-41	0-38
2	3	3-28	0-38
4	26	4-10	0-42
6	21	4-48	0-52
8	51	5-20	0-62
10	117	6-20	0-62
8	88	8-50	0-67
10	89	8-97	0-67

AUTO TRANSFORMERS

VA	Ref. No.	Price Cased	Price Plugs 2 & 3 pin	Price Open	Post
Tapped at 115, 220, 240 Volts	20	113	3-00	0-15	1-55
Tapped at 115, 200, 220, 240 Volts:	150	4	5-80	0-15	3-98
200	65	6-40	0-15	4-50	0-40
300	66	7-27	0-15	5-28	0-52
500	67	9-89	0-15	8-29	0-67
750	83	12-58	0-75	9-76	0-82
1000	84	15-70	0-75	12-40	0-82
1500	93	19-88	0-75	16-58	1-00
2000	95	30-10	1-44	22-05	1-00
3000	73	43-58	1-90	32-00	1-90

50 Volts

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V.	Amps	Ref. No.	Price	Post
0-5	102	2-83	0-30	
1	103	3-00	0-38	
2	104	4-67	0-42	
3	105	5-20	0-52	
4	106	6-89	0-52	
6	107	11-17	0-67	
8	118	14-19	0-97	
10	119	15-47	0-97	

60 Volts

Prim. 230-240V. Sec. 24, 30, 40, 48, 60V.	Amps	Ref. No.	Price	Post
0-5	124	2-08	0-38	
1	126	2-96	0-38	
2	127	4-63	0-42	
3	128	6-84	0-52	
4	123	7-94	0-67	
5	40	8-86	0-67	
6	120	10-15	0-82	
8	121	13-68	1-00	
10	122	18-15	1-00	
12	189	16-60	1-10	

MINIATURE AND EQUIPMENT

Prim. 240V with screen.	Volts	Sec. 2	Milliamps	Ref. No.	Price	Post
Sec. 1	3-0-3	0-6	200	238	1-23	0-10
	0-6	0-6	500	234	1-30	0-10
	0-6	0-6	1000	212	1-33	0-10
	0-9	0-9	100	235	1-42	0-10
	0-9	0-9	330	207	1-75	0-22
	0-9	0-9	500	208	2-80	0-30
	0-9	0-9	1000	1000	2-80	0-30
	15-0-15	0-15	40	240	1-23	0-10
	0-15	0-15	200	236	1-80	0-20
	20-0-20	0-20	20	241	1-23	0-10
	0-20	0-20	150	237	1-30	0-10
	0-15-20	0-15-20	500	205	2-47	0-38
	0-20	0-20	300	214	1-72	0-22
	0-20	0-20	3500	NO SCREEN	1136	3-00
	20-19-0-12-20	0-15-20	700 (D/C)	221	2-31	0-30
	0-15-20	0-15-20	1000	206	3-22	0-48
	0-15-27	0-15-27	500	203	2-73	0-38
	0-15-27	0-15-27	1000	204	3-52	0-38

PLASTIC CASED SILICON BRIDGE RECTIFIERS


One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 25p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 50p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 30p	400 P.I.V. 60p	600 P.I.V. 75p	400 P.I.V. 90p

ADD 10p P & F PER ORDER

PLEASE ADD 8% FOR VAT

POWER UNIT Type CC 12-05

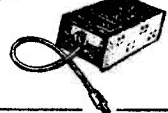Output switched 3, 4.5, 6, 7.5 and 12 volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players etc Size 7.5 x 5.0 x 1.4 Dcm. Price £3.95. Post 25p.



MINIATURE NEONS

6mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor 150K ohms for 240 Volt operation Price: Packet of 10 for 55p. Postage 10p.

A.S.P. LTD.

DEPT PW5, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

ELECTRONI-KIT

... educational kits of exceptional quality" (AUDIO mag. Dec. 1974)

BUILD AND REBUILD ANY NUMBER OF TIMES:

Radios, microphones, burglar alarms, inter-comms, ferrite detectors, solar cell, photoelectric cell, voice relay, electronic cats, birds, guns, organs, illuminometers, voltmeters, meters of all types, etc., etc., plus your own circuit designs.

COMPLETELY SAFE—suitable for all, from beginners on. 30 different projects £10-45, 100 different projects £20-45, over 150 £33-95. Add-on kits, spares, available too.

Prices include Manuals, Battery, p & p, VAT, etc. Cheque/PO (or 7p for catalogues) to DEPT. PW:

Satisfaction guaranteed.

ELECTRONI-KIT LTD, 408 St. John's Street, London, EC1. (01-278 4579)

FELSTEAD ELECTRONICS (PW91)


Longley Lane, Gatley, Cheshire SK8 4EE

STYLII AND CARTRIDGE REPLACEMENTS for

Single Tip Styli	Double (Turnover) Styli	G800H, G850, £2-10 ea. G800E, £4-10.
ACOS GP35 LP, GP27 LP, GP59 LP, GP65/67 LP, GP71/3 ST/LP, BSR TC8 ST/LP, ST19 ST/LP, COLLARO "O" LP, TKS8 LP, GARRARD GC2 LP, GC8 LP, GCE12 LP, GC810 LP, EV26 ST/LP, PHILIPS 3010 LP, 3016 LP, GP204/5 ST/LP, 3301/3060/3 ST/LP, SONETTE BF40, DC284 ST/LP &c, SONOTONE 19T/20T ST/LP, COST: S.A.P. 20p, D.I.A. 40p.	ACOS GP73, GP91, GP18C, GP96, GP104, BSR ST3/4, ST5/9/10, ST11/14/15, ST16/17/18, GARRARD GOM, GCS, GKS, K340/41 series, &c (give number), PHILIPS 3306, GP310, &c, SONOTONE 2T, 3T, 8TA, 9TA, 9TAC, 2509, 3509, SAP ST/LP + 78 or ST/LP + ST/LP 40p, D.I.A. ST/LP + S.A.P. 78 65p, DOUBLE DIA ST/LP + ST/LP £1.25.	Also Shure &c. see List CARTRIDGES For ACOS GP91 SC @ £1.20, GP93 @ £1.60, GP94 @ £2.20, BSE X3H, X5H, X5M @ £1.50, TCH, @ £1.60, SX5H and SX5M @ £1.80, TC/S (3 pins) £2.30, PHILIPS for 3306-3310, GP360 &c. @ £1.85, for 3234, 3238, GP290, @ £1.95, GARRARD KS40A (Sonotone 3509) @ £1.95. Other types available.

CHARGES—All STYLII up to 3 for 12p, CARTRIDGES 12p each. C.W.O. only PRICES INCLUDE VAT. SEND S.A.E. FOR FULL LIST OF ABOVE + ACCESSORIES, COMPONENTS, CASSETTES, TAPES, etc. There will be a delay in despatch of orders from May 1st to 18th

LOWE ELECTRONICS

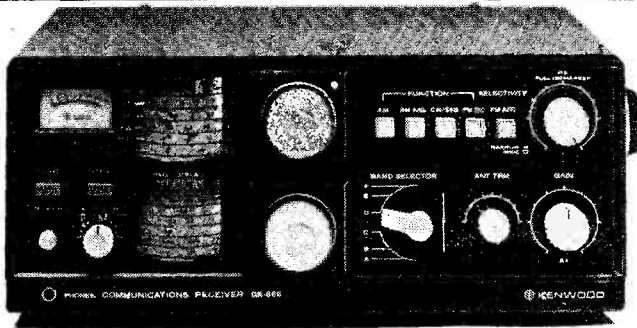


TRIO
QR666

SPECIFICATION 170-410
Frequency coverage 17-410kHz, 525-1250kHz, 1-25-3-0MHz,
3-7-50MHz, 7-5-18MHz, 18-30MHz (Dual conversion)
Bandspread 3-5-4MHz, 7-7-5MHz, 14-14-6MHz, 21-21-5MHz
(Dual conversion), 28-30MHz (Dual conversion)
Modes AM, USB, LSB, CW
Selectivity 2 position wide/narrow
Antenna 50-100Ω
Sensitivity 1μV for 10dB S/N (SSB/CW)
AF Output More than 1-5W into 8Ω. Internal speaker fitted
Power supply 100/117/220/240V ac 50/60Hz, External 12V dc.
Internal 12V batteries, Automatic changeover to
Internal supply in the event of mains failure
Dimensions (mm) 382 wide x 163 high x 322 deep
Weight 7-3kg (16-09 lbs)
Options 500kHz marker QR6MK, FM broadcast tuner
QR6FM

An all new receiver from the TRIO company providing general coverage reception 170kHz to 30MHz with calibrated bandspread for the amateur bands. Dual-gate MOSFETS for RF and mixer stages ensure high gain, good selectivity and first class A.G.C. characteristics.

Dual position selectivity gives two bandwidths to cater for all band conditions.

Use the QR666 at home, in the car or boat or truly portable; all catered for by the exclusive 3-way power supply. **PRICE £130 (VAT excl)**

We stock a great many products apart from those advertised month by month—everything in fact for the radio amateur operator. If you need more information, our complete catalogues are available free to callers. If you require them sending by mail, postal charges being what they are today, please send us 20p in stamps because that's what it costs to send them to you!

HEAD OFFICE 119 Cavendish Road, Matlock, Derbyshire. Tel. 2817 or 2430 9 a.m. to 9 p.m.

BRANCH OFFICES Goring Road, Steyning, Sussex. Tel. Steyning 814466

Soho House, 362-4 Soho Road, Handsworth, Birmingham. Tel. 021-554 0708

AGENTS

Alan GW3YSA, 35 Pen-Y-Waun, Efall Isaf, Nr. Pontypridd, Tel. Newton Llantwit 3809

John G3JYG, 16 Harvard Road, Ringmer, Lewes, Sussex. Tel. Ringmer 812071

Sim GM3SAN, 19 Ellismulr Road, Baillieston, Nr. Glasgow. Tel. 041-771 0364

OPENING HOURS: 9-5.30 TUESDAY TO SATURDAY INCLUSIVE

73 from BILL G3UBO/VE8DP, ALAN G3MME, JOHN G3PCY/5N2AAC, IAN G3ZCY



**become
a RADIO-AMATEUR!**

learn how to become a radio-amateur
in contact with the whole world. We give
skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS
SCHOOL** Dept. WB54, P.O. Box 156, JERSEY

NAME: _____
ADDRESS: _____

_____ BLOCK CAPS please

CJL PRICES INCLUDE P&P AND V.A.T.

- AERIAL**, telescopic, 15-120cm. £1.20
- AERIAL**, telescopic, h and v swivel, 15-80cm. . . £1.78
- BIB HI-FI ACCESSORIES**
- CASSETTE TAPE RECORDER CARE KIT** £1.95
- CASSETTE SPLICING AND EDITING KIT** . . . £1.50
- HI-FI STEREO TEST CASSETTE** £2.10
- 1" TAPE EDITING KIT** £1.35
- GROOV-KLEEN RECORD CLEANER** £1.85
- EARPHONE**, stethoscope style, 8 ohm dynamic . £1.00
- HAND DRILL** (Leytool), compact precision drill, 5/16" chuck. Gears totally enclosed. S/L bearings. £2.99
- INTEGRATED CIRCUITS**
- AUDIO POWER AMPLIFIER** (National) LM380 . £1.00
- A.M. RADIO RECEIVER** (RCA) CA3123E £1.40
- F.M. STEREO DECODER** (Motorola) MC1310P £2.80
- TIMER** (Signetics) NE555V £0.78
- VOLTAGE REGULATOR** (Fairchild) uA7805 £1.70
- VOLTAGE REGULATOR** (Signetics) NE550A £0.80
- D.I.L. SOCKETS** (Pk of 3) 8 or 14 pin. £0.50
- KEYNECTOR**, rapid connect to mains-single/multiple leads. Built-in piano switches, neon & 13A fuse £3.20
- LOCKFLEX RULE** (Rabone Chesterman), 3m/10ft precision pocket rule. Easy to read, 13mm/½" wide steel tape. Blade length lockable-power return. A superb rule £0.93
- MICROPHONE**, lightweight dynamic, remote start stop, 200 ohms, 100-10kHz, 6mV average output . £1.80
- MULTIMETER**, attractive design, Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA. R-150k . £4.95
- SIGNAL INJECTOR**, audio through video signals, excellent for servicing amplifiers, radio & tv . . £3.92
- SOLDERING IRON, 25 WATT** (Antex), X25, 240V, Very low leakage, 1/8" long life bit (interchangeable) £1.85
- 3/32" bit £0.45 3/16" bit £0.45 Element £0.95
- STAND**, ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits . £0.95
- SPEAKER**, miniature, 75mm dia, 8 ohms. . . £0.80

CJL CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

ALL OUR PRICES INCLUDE V.A.T.

£5.50 Post 25p.



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop complete with carriage. Base-plate. Size 11in x 8 1/2in. Turntable. Size 7in. diameter. A/C mains. 200/250V motor has a separate winding 14 volt to power a small amplifier. Three speeds. Plays all records.

COMPLETE STEREO HI-FI

Two full size loudspeakers 12 1/2 x 10 x 8 1/2in. Player unit clips to loudspeakers making it extremely compact. Overall size only 12 1/2 x 10 x 8 1/2in. 3 watts per channel, plays all records 3 1/2 rpm, 45 rpm. Separate volume & tone controls. 240V A.C. mains.



Attractive Teak finish Weight 13lbs. Bargain Price **£25** 85p carriage

SPECIAL OFFER

SMITH'S CLOCKWORK 15 AMP TIME SWITCH C-60 MINUTES
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home. Range, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Makers last list price £4.00. Brand new and fully guaranteed. **OUR PRICE £2.80** Post 25p



WEYRAD P50—TRANSISTOR COILS

RA2W Ferrite Aerial. 85p	Printed Circuit, PCA1. 85p
L.F. P50/200 470 kc/s. 40p	J.B. Tuning Gans. £1.20
3rd L.F. P50/300. 40p	Weyrad Booklet. 10p
Spare Cores. 3p	O.F.T.I. 65p
P50/1A. 60p	Driver Trans. LFDTA. 65p
Ferrite Rod 8 x 1/2in. 20p 6 x 1/2in. 20p 8 x 1/2in. 20p	

VOLUME CONTROLS 80 Ohm Coax 5p. yd.

5 K. ohms to 2 Meg. LOG or LIN. 1/8 20p. D.P. 35p. STEREO L/S 55p. D.P. 75p. Edge 5K.S.P. Transistor 25p

BRITISH AERIALS
AERIAL-AIR SPACED 40 yd. £2; 60 yd. £3.
FRINGE LOW LOSS
Ideal 625 & colour 10p yd.

8in or 10 x 6in ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm 10 watt. **£3.75** Each Post 52p

10 inch 12 watt Twin Cone, 8 ohm £4.50



E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) **£4.50** Post 25p



With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p **£2.95**

BOOKSHELF CABINET £6.60 Post 45p
Size 16 x 10 x 7in. teak finish

E.M.I. 18 x 8in. BASS WOOFER. 20 WATTS RUBBER CONE SURROUND. £5.50 Post 25p.

BLANK ALUMINIUM CHASSIS. 18 a.w.s. 2 1/2in. sides 6 x 4in. 45p; 3 x 6in. 55p; 10 x 7in. 65p; 12 x 8in. 65p; 14 x 8in. 90p; 16 x 8in. 90p; 12 x 8in. 50p; 16 x 10in. 21. **ALUMINIUM BOXES** 3 x 3 x 3in. 60p; 3 x 4 x 4in. 70p; 6 x 4 x 4in. 80p; 9 x 4 x 4in. 112; 4 x 4 x 4in. 80. **ALUMINIUM PANELS** 18 a.w.s. 6 x 4in. 12p; 8 x 6in. 10p; 14 x 8in. 20p; 10 x 7in. 24p; 12 x 8in. 25p; 12 x 8in. 24p; 16 x 6in. 24p; 14 x 9in. 40p; 12 x 12in. 47p; 16 x 10in. 60p

SPECIAL OFFER

100 ohm 80W Rheostat 2 1/2in. diam. Ceramic Former, screw terminals, 1/2in. diam. spindle. 95p, Post 25p.

RADIO COMPONENT SPECIALISTS

Minimum post 20p. Illustrated Brochure, Radio Books & Components Lists 10p.

ANOTHER R.C.S. BARGAIN!

ELAC 9 x 5in. HI-FI SPEAKER. TYPE 59RM. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE **£2.95**
10 WATT, 8 OHM. CERAMIC MAGNET.

R.C.S. STABILISED POWER PACK KITS
All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer. Input 200/240V a.c. Output voltages available 6 or 8 or 12 or 15 or 18 or 20V d.c. at 100mA or less.
PLEASE STATE VOLTAGE REQUIRED. **£2-20** Post Details S.A.E. Size 8 1/2 x 1 1/2 x 1 1/2in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v, or I.R.L. line 200-300V. d.c. operation. Size 1 1/2 x 1 1/2 x 1 1/2" Response 25 c/s. to 25 Kc/s, 28 dB gain. For use with valve or transistor equipment. **£1.25** Post Full instructions supplied. Details S.A.E. 20p

TEAKWOOD LOUDSPEAKER GRILLS. Will easily fit to baffle board. Size 12 1/2 x 10 1/2in—75p. 10 1/2 x 7 1/2in—45p.

E.M.I. WOOFER AND TWEETER KIT

Woofer 10 1/2 x 6 1/2in. Ceramic Magnet, 44oz. 13,000 lines. Tweeter 3 1/2in. square, 10,000 lines. Crossover condenser full instructions supplied. Impedance 8 ohms. Power 12 watts. **£5.75** Post 45p.

BRITISH FM/VHF TUNING HEART

98 to 108 M/Cs British made. 2 Transistors ready aligned requires 10-7 M/Cs I.F. Complete with tuning gang. Connections supplied but some technical experience essential **Our price £3.95** 10-7 M/Cs IF Strip 24-95
DECODER = 24-75

MAINS TRANSFORMERS

250-0-250 8mA. 6-3V 2amp. 25p	All post 25p
250-0-250 80 mA. 6-3V 3-5A. 6-3V 1A or 5V 2A. 25.00	25.00
350-0-350 80 mA. 6-3V 3-5A. 6-3V 1A or 5V 2A. 28.00	28.00
300-0-300V 120mA. 6-3V 4A C.T. 8-2V 2A. 24.25	24.25
MINIATURE 200V 20mA. 6-3V 1A. 21.00	21.00
MIDGET 220V 45mA. 6-3V 2A. 21.00	21.00
HEATER TRANS. 6-3V 1 amp 85p. 8 amp £1.20	85p. £1.20
GENERAL PURPOSE LOW VOLTAGE. Trapped outputs at 2 amp. 2, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V 24-00	24-00
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 24-00	24-00
2 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 26-00	26-00
3 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 27-50	27-50
5 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 29-75	29-75
3, 5, 8, 10, 13V 5 amp. £1.50; 6-0-6V 500mA 90p	1.50; 90p
9V 1 amp 95p 12V 300mA 75p 12V 500mA 85p 12V 750mA 95p. 10, 30, 40V 2 amp. £2.20 3V 3 amp. £2.40 3A £2.50. 20-0-20V 4A £3. 18V 1 amp. 85p. 18V 2 amp. £1.85.	95p. £2.20; 2.40; £2.50; 85p; £1.85
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W 24; 300W 27.50; 750W 41.5; 1000W 51.	24; 27.50; 41.5; 51
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2; 4 amp £4; 5 amp £4.50.	2; 4; 4.50
FULL WAVE BRIDGE CHARGER RECTIFIERS; 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.	40p; 55p; 85p

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals, Varnish impregnated. Fully enclosed in steel case with fixing feet. **OUR PRICE £12** 95p
Famous make. (Value £18) Carr. Charge.
Can be used as 800W auto transformers 240-110V. IDEAL FOR COLLECTOR TV. OR GARDEN POOLS.

NEW ELECTROLYTIC CONDENSERS

2/250V. 14p	100/25V .. 10p	50+50/800V .. 50p
4/250V. 14p	250/25V .. 14p	350+50/825 .. 85p
8/250V. 22p	500/25V .. 20p	32+32/850V .. 40p
16/350V 25p	100+100/275V 65p	32+32/450V .. 60p
32/450V 35p	150+200/275V 70p	32+32+32/350V 85p
32/500V 50p	8+8/450V .. 22p	22+32+18 .. 32/450V 35p
25/25V .. 10p	8+16/450V .. 25p	900/350V .. 95p
50/50V .. 10p	16+16/450V 40p	4700/83V .. 95p

LOW VOLTAGE ELECTROLYTICS


1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p. 500mF. 15V. 15p; 25V. 20p; 50V. 30p. 100mF. 15V. 20p; 25V. 35p; 50V. 47p; 100V. 70p. 1000mF. 6V. 25p; 85V. 42p; 50V. 57p. 2500mF. 50V. 65p; 2000mF. 25V. 47p; 50V. 65p. 5000mF. 6V. 25p; 18V. 42p; 25V. 75p; 35V. 85p; 50V. 95p.

MICRO SWITCH. Single Pole Change Over. 20p.
MICRO SWITCH. Sub Min 25p.

CERAMIC 1pF to 0.01mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-0-1 7p. 0-5 12p; 15V 15p; 25V 15V 15p. 500V-0-01 to 0-05 4p; 0-1 10p; 0-25 15p; 0-47 25p. TWIN GANG. "0-0" 200pF+175pF. £1.20; 500pF standard 75p; 365+365 with 25+25pF Slow motion drive 50p. TWIN GANG. 120pF 50p. 385pF 50p. SELECT WAVE, SINGLE 100P 80p; 20pF 55p; 50pF 55p. NEON PANEL. 1000V. 600V A.C. Dim. 25p. RESISTORS. 1W, 1/2W, 1W, 20%; 1/2W, 5p, 10 to 10M. HIGH STABILITY. 1/2W, 2%; 10 ohms to 6 meg. 10p. Ditto 5% Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each. VALVE OSCILLATOR COIL. Valve Type 85p.

NEW MODEL "BAKER LOUDSPEAKER" 12in. 50 watt GROUP 50/12 8 or 15 ohm high power full range. Professional quality. **£12.95**

BAKER MAJOR 12" £8-50

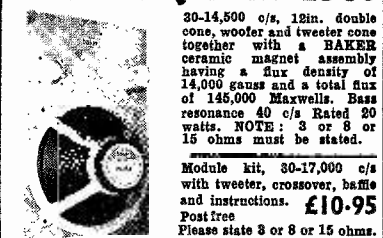

30-14,500 c/s. 12in. double cone woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£10.95**
Post free
Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
12 inch 25 watt 3 or 8 or 15 ohm	12 inch 35 watt 8 or 8 or 15 ohm	15 inch 50 watt 8 or 15 ohm
£7.75	£8.50	£17.80

TEAK VENEERED HI-FI SPEAKER CABINETS
For 12in or 10in. dia. speaker 20 x 13 x 9" £10-50 Post 75p
For 18 x 8in. or 8in. speaker 18 x 10 x 7" £6-00 Post 55p
For 8 x 5in. speaker 18 x 8 x 9" £4-95 Post 55p
For 6in. and tweeter 12 x 8 x 8" £4-00 Post 55p
LOUDSPEAKER CABINET WADDING 18in. wide, 20p ft

EMI 6 1/2in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Rubber cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns, Hi-Fi Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 1/2 40. Suitable Tweeter 22.00. **£4**

ELAC COIL TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s. to 12,000 c/s. Size 8 1/2 x 3 1/2in. deep. Rating 10 watt, 8 ohm Suitable **£1.90** Post 20p

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kc/s. 10W 8 ohm or 15 ohm £1.95
CROSSOVERS TWO-WAY 3000cps 3 or 8 or 15 ohm £1.50
LOUDSPEAKERS 3 OHMS. 7 x 4in. £1.25; 8 1/2in. £1.50. 8 x 6in. £1.90 8in. £1.75; 10 x 6in. £1.90; 10in. £2.00.
SPECIAL OFFER: 50 ohm 2 1/2in.; 2 1/2in. 35 ohm. 8in. 2in. dia.; 5in. dia. 6" x 4". **£1** TYP E EACH
15 ohm 3 1/2in. dia.; 6 x 4in.; 7 x 4in.; 8 x 6in. £1
8in. 2 1/2in.; 2 1/2in.; 3 1/2in.; 5in. dia. (8 x 4in. 8 ohm £1.50)
RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. diameter 4 watt £2.50. 10in. diameter 5 watt £2.95; 12in. diameter 6 watt £3.50.
VALVE OUTPUT TRANS. 40p; **MIKE TRANS.** 50-1 40p. Mike trans. mu metal 100-1 £1.25.

MAJOR 100 WATT ALL PURPOSE GROUP OR DISCO AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. **£49** Carr. £1.00
Separate treble and bass controls. 2-WAY MIXING IDEAL FOR DISCO OR P.A. 239.95

3-WAY CROSSOVER 950 CPS and 3000 CPS with leads ready assembled £1.95

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphones, records, tape and tuner with separate controls into single output. 9 watt. **£4.50**

TWO CHANNEL STEREO VERSION £5.95

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume, treble and bass controls 15v. **MAINS POWER PACK 23.** **£3.95**

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 15p COAXIAL OUTLET BOXES, surface, 35p. BALANCED TWIN FEEDER 300 ohms 7 yard. JACK SOCKET Std. open-circuit 15p, closed-circuit 25p. Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p. TAGE PLUGS Std. Chrome 20p; 8 5mm Chrome 12p. DIN SOCKETS Chassis 8-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 15p; 6-pin 25p. DIN PLUGS 3-pin 15p; 5-pin 25p. VALVE HOLDERS. 6p; CERAMIC 10p; CANS 5p.

REVERSIBLE 4 POLE MOTOR £2.25

1,400 r.p.m. Reversible 4W Watt, Post 25p spindle 1 1/2 x 7/16, size 3 1/2 x 3 1/2. As illustrated. With Cooling Fan 240V A.C. **E.M.I. GRAM MOTOR £1.00**
120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. Post 25p.

337 WHITEHORSE ROAD, CROYDON

Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

CHROMASONIC electronics

Dept. 1
56, Fortis Green Road, London, N10 3HN.
telephone: 01-883 3705

RESISTORS

The standard ranges of Resistors stocked are either E12 or E24 and the values are all in multiples of ten times the decade shown below. The E12 items are only those in bold type. The E24 items are both those in bold and light type.

10	18	33	56
11	20	36	62
12	22	39	68
13	24	43	75
15	27	47	82
16	30	51	91

CARBON FILM 1/1 watt \pm 5% tol. 2p ea.
E12 Series 10 Ω to 330K Ω

CARBON FILM 1/2 watt \pm 5% tol. 1p ea.
E24 Series 10 Ω to 10M Ω

CERMET THICK FILM 1/2 watt \pm 2% tol. 8p ea.
E12 series 56 Ω to 150K Ω

METAL OXIDE FILM 1/2 watt \pm 2% tol. 4p ea.
E12 series 10 Ω to 1M Ω

CARBON COMPOSITION 1/2 watt 4p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; \pm 0.5 tol.
5.6 ; 6.8 ; 8.2 \pm 10% tol.

CARBON COMPOSITION 1 watt 5p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; \pm 0.5 tol.
5.6 ; 6.8 ; 8.2 \pm 10% tol.

CARBON FILM 1 watt \pm 5% tol. 3p ea.
E12 series 10 Ω to 10M Ω

CARBON FILM 2 watt \pm 5% tol. 6p ea.
E12 series 10 Ω to 10M Ω

WIREWOUND 2 1/2 watt \pm 5% tol. 0.22 to 0.47/0.15/5p
E12 series \pm 10% " 1 to 270 Ω 13p

WIRE WOUND 5 WATT 13p ea.

1	25	250	1.5K
1	30	270	1.8K
1.8	39	300	2K
2.2	50	330	2.2K
2.7	60	350	2.5K
3.3	68	400	2.7K
3.9	75	470	3K
4.7	82	500	3.3K
5	100	560	3.5K
5.6	125	600	4.7K
6.8	133	680	5K
8.2	150	750	5.6K
10	180	820	5.6K
15	200	1K	6.8K
21	220	1.2K	8.2K

WIRE WOUND 10 watt 14p ea.
All the values shown in bold in the 5 watt range

WIRE WOUND 10 watt \pm 5% tol. 20p ea.
10K ; 15K ; 20K ; 25K

WIRE WOUND 15 watt 13p ea.
All the values from 10 Ω upward shown in bold in the 5 watt range.

POTENTIOMETERS




5K	250K	Log or Lin Less Switch (and 1K Lin)	14p
10K	500K	Log or Lin with Switch	24p
25K	1 Meg	Dual Less Switch	46p
50K	2 Meg	1 Meg Log only	57p
100K		10K Log + 10K Antilog Less Switch	



Sliders


10K	Single	33p
25K		
50K	DUAL	55p
100K		

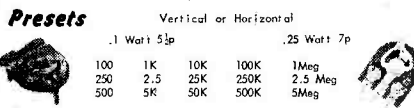

Presets

Vertical or Horizontal

.1 Watt 5p		.25 Watt 7p	
100	1K	10K	100K
250	2.5	25K	250K
500	5K	50K	500K
		5Meg	

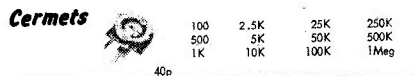

Cermets

100	2.5K	25K	250K
500	5K	50K	500K
1K	10K	100K	1Meg

VDR's &

Thermistors

CZ1	17p
CZ4	18p
CZ13A	18p
CZ19	18p
E298CDA258	13p
E298EDA258	13p
E298EDA260	13p
E298EDA262	13p
E298EDA265	13p
E298EDP268	13p
E298ZZ05	13p
E298ZZ06	13p
E299DDP336	14p
E299DDP338	14p
E299DDP342	14p
E299DDP348	14p
GL16	£1.21
GL23	£1.21
R53	£1.49
R54	£1.61
VA1005	16p
VA1026	16p
VA1033	16p
VA1034	16p
VA1039	16p
VA1040	16p
VA1053	16p
VA1055S	16p
VA1056S	16p
VA1064S	17p
VA1057S	19p
VA1067S	19p
VA1071	19p
VA1098	21p
VA1104	31p
VA1107	29p

CAPACITORS



Silvered Mica 350V.

Tol. \pm 0.5p	11p each	
2.2 pf	18pf	30pf
3.3 pf	20pf	35pf
5 pf	22pf	39pf
10 pf	25pf	47pf

Tol. \pm 1% 11p each

50pf	150pf	
56pf	82pf	180pf
68pf	100pf	200pf
75pf	120pf	220pf

12p each

250pf	330pf	560pf
270pf	390pf	680pf
300pf	470pf	820pf
	560pf	

17p each

1000 pf	1500pf	220pf
	1800pf	

26p each

2700pf	3600pf	5000pf
	4700pf	


33p each

6800pf	8200pf	10000pf
--------	--------	---------




Mixed Dielectric 600 Volts Wkg.

0.01 uF	8p	0.1 uF	9 p
0.022 uF	8p	0.22 uF	17p
0.033 uF	8p	0.47 uF	26p
0.047 uF	8p	1 uF	32p
0.068 uF	9p		

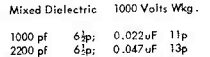

Mixed Dielectric 1000 Volts Wkg.

1000 pf	63p	0.022uF	11p
2200 pf	63p	0.047 uF	13p
3300 pf	7p	0.1 uF	13p
4700 pf	7p	0.22 uF	24p
0.01 uF	10p	0.47	35p

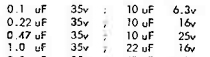

Solid Tantalum Beads all at 163p

0.1 uF	35v	10 uF	6.3v
0.22 uF	35v	10 uF	16v
0.47 uF	35v	10 uF	25v
1.0 uF	35v	22 uF	16v
2.2 uF	35v	47 uF	6.3v
4.7 uF	35v	100 uF	3v



Feed-through Ceramics

1000 pf 350v 6p


Disc Ceramics 750 Volt Wkg. all at 53p each

470 pf; 1000 pf; 5000 pf; 0.01 uF



Tubular HI-K Ceramics 750 Volts Wkg.

1000 pf	53p	3000 pf	53p
1500 pf	53p	5000 pf	53p
2000 pf	53p	0.01 uF	53p

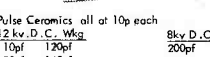

Pulse Ceramics all at 10p each

1.2 kv.D.C. Wkg	8kv D.C.	
10pf	120pf	200pf
22pf	140pf	220pf
68pf	150pf	250pf
82pf	100pf	270pf
100pf	200pf	300pf

CAPACITORS

Ceramic Plate

Mullard C333 Series 63 Volts Wkg.

all at 53p each

0.025pf	1.8 pf	2% 12 pf	42% 68 pf
2.2 pf	15 pf		82 pf
3.3 pf	18 pf		100 pf
3.9 pf	22 pf		120 pf
4.7 pf	27 pf		150 pf
5.6 pf	33 pf		180 pf
6.8 pf	39 pf		220 pf
8.2 pf	47 pf		270 pf
10 pf	56 pf		330 pf

Mullard 630 series 40 volts \pm 10% tol. 629 series 100 volts all at 53p each

390 pf	1000 pf	3300 pf
470 pf	1200 pf	3900 pf
560 pf	1500 pf	4700 pf
680 pf	1800 pf	* 10 nf
820 pf	2200 pf	* 22 nf
	2700 pf	

Erie Monolithic Ceramic 30 Volts Wkg.

27 nf 11p; 47 nf 13p; 100 nf 17p

Low Voltage Disc Ceramics all at 53p each

0.01 uF	18v	0.1 uF	30v
0.022 uF	18v	0.22 uF	6v
0.047 uF	18v	0.47 uF	3v

Mylar Film 100 Volts Wkg.

1000 pf	2p	0.05 uF	33p
2000 pf	2p	0.068uF	5p
5000 pf	2p	0.1 uF	5p
0.01 uF	3p	0.2 uF	63p
0.02 uF	3p	0.47 uF	7p
0.04 uF	3p		

MULLARD C295 Series 63 volts

Tolerance \pm 1%

6,800pf	(6.8nf)	Polyethylene	11p
8,200pf	(8.2nf)	C295 AH/D6X8	11p
13,000pf	(13nf)	C295 AH/D8X2	11p
18,000pf	(18nf)	C295 AH/D13K	15p
		C295 AH/D18K	15p
20nF	(.02uF)	C295 AH/D20K	15p
30nF	(.03uF)	C295 AH/D30K	18p
39nF	(.039uF)	C295 AH/D39K	18p
51nF	(.051uF)	C295 AH/D51K	25p

Polystyrene 160 volts Wkg. Tolerance \pm 1pf up to 33pf; \pm 5% 47pf up.

10 pf to 10,000 pf (0.01 uF) in multiples of: 10 ; 15 ; 22 ; 33 ; 47 ; 68.

Wima MKS. 0.22uF \pm 5% 100v 11p

Mullard C280 Series 250 Volts Wkg. Metallized Polyester Film

0.01 uF	33p	0.22 uF	53p
0.015 uF	33p	0.33 uF	7p
0.022 uF	33p	0.47 uF	9p
0.033 uF	33p	0.58 uF	12p
0.047 uF	33p	1.0 uF	14p
0.068 uF	4 p	1.5 uF	22p
0.1 uF	4p	2.2 uF	26p
0.15 uF	4p		

Mullard C281 series 400 Volts Wkg. Metallised Polycarbonate Film \pm 10%

0.01 uF	5p	0.1 uF	8p
0.015 uF	5p	0.15 uF	9p
0.022 uF	5p	0.22 uF	11p
0.033 uF	6p	0.33 uF	13p
0.047 uF	6p	0.47 uF	16p
0.068 uF	6p		


VAT INCLUSIVE PRICES AT 8% OVERSEAS CUSTOMERS DEDUCT 2/27 VAT INVOICES ON REQUEST P&P. ON U.K. Orders 15p Overseas Orders at Cost

CHROMASONIC electronics

Dept. 1
56, Fortis Green Road, London, N10 3HN.
telephone: 01-883 3705


INDUCTORS

Denco Maxi-Q Coils

Ferrite Rod Aerials


FRA1 Long & Medium Wave band (200p)
9p
FRA2 Long & Medium Wave band (200p)
9p

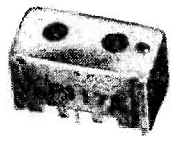Tuning Coils in two series:
Range
1 150 kHz to 400 kHz
2 515 kHz to 1.545 MHz
3 1.67 MHz to 5.3 MHz
4 5 MHz to 15 MHz
5 10.5 MHz to 31.5 MHz
6 30 MHz to 50 MHz
7 45 MHz to 78 MHz




Tuned Block Filter incorporating a Ceramic element. Pre-aligned to 470 Khz. 3db bandwidth 5Khz. Zin 100K. Zout 100K.
LP1175 £1.46

I.F. Transformers

I.F.T 13	465 kHz 1st & 2nd d/ tuned	70p	5p 10p 15p	£1.30 £1.30 £1.30
I.F.T 14	455 kHz final single tuned	70p	5p 10p 15p	£1.39 £1.39 £1.39
I.F.T 15	10.7 MHz d/ tuned	75p	5p 10p 15p	£1.39 £1.39 £1.39
I.F.T 16	1.6 MHz 1st & 2nd d/ tuned	65p	5p 10p 15p	£1.53 £1.53 £1.53
I.F.T 17	1.6 MHz Final s/ tuned	65p	100p	£1.53
I.F.T 18	455 kHz or 1.6 MHz d/ tuned	78p		


* 50 pf tuning, all others based on 300 pf.
Series A Transistor—75p each
Only available in ranges 1 to 5 inc. 4 Coils complete each range:
Blue - Aerial Coil
Yellow - R.F. Interstage
Red - Osc. Coil for 465 khz I.F.
White - Osc. Coil for 1.6 MHz I.F.
give range number ; letter 'T' & colour.

Series B Dual Purpose Coils 89p each
For FET or Valve Circuits
All ranges available
5 Coils complete each range:
Blue - Aerial
Yellow - Interstage R.F.
Green - R.F. plus reaction
Red - Osc. Coil for 465 khz I.F.
White - Osc. Coil for 1.6 MHz I.F.
(Note use Red instead of White for ranges 6 & 7.)

Chokes


We stock from 1µH to 19 mH
Check levels & prices when ordering

TUNING CONDENSERS

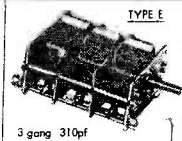

3 gang 310pf
E7-17



TYPE OO
208+170pf with screen & trimmers E2-99



DILECON
Slow Motion Drive Ratio 6:1 Ref: 4511



TYPE O
385pf E2-11
385 x 365pf E2-99

VEROBOARD



	COPPERCLAD	PLAIN	EXTRA
0.1"	0.15"	0.15"	P&P
2 1/2" x 1"	7p	7p	-
2 1/2" x 3 1/2"	26p	21p	17p
2 1/2" x 5"	30p	25p	13p
3 1/2" x 3 1/2"	30p	25p	-
3 1/2" x 5"	34p	34p	25p
17" x 2 1/2"	90p	69p	45p
17" x 3 1/2"	£1.21	75p	57p
17" x 5"		99p	10p

D.I.P. Breadboard 4.15" x 6.15" £1.40
VEROSTRIP (State .1" or .15") 30p
Pin Insertion Tool (State .1" or .15") 63p
Pin Face Cutter 51p
Terminal Pins in Pkts. of 50 (State .1" or .15") 22p

Details of I.C.'s, Rectifiers, Diodes, Bridges, Passive Components, LED's, Clocks; Triacs etc. can be seen on other pages and in issues of Wireless World, Practical Wireless; and Practical Electronics.

DIODES

AA119	10p	8Y103	22p	0A91	8p
AA120	10p	8Y105	16p	0A200	11p
AA129	10p	8Y126	10p	0A202	12p
BA100	10p	8Y127	16p	Z5120	8p
BA102	27p	8Y133	23p	Z5140	25p
BA110	44p	8Y184	54p	Z5141	42p
BA115	19p	8Y176	£1.62	Z5142	32p
BA144	20p	8Y182	£1.62	Z5170	10p
BA145	22p	8Y250	25p	Z5200	11p
BA148	22p	BZ270	27p	Z5271	10p
BA154	20p	Series		Z5278	36p
BA155	15p	BZ2Y88	11p	IN914	8p
BA156	10p	0A47		IN916	10p
BA161	10p	0A47		IN4009	7p
BB104	45p	0A79	10p	IN4148	5p
BB105B	41p	0A81	8p	IN4448	9p
BY100	16p	0A85	10p	IZS Series	8p
		0A90	8p		

TRANSISTORS

AC107	14p	BC213L	13p	D13V	52p	ZTX301	13p	ZN3707	12p
AC126	13p	BC214L	13p	D40N3	59p	ZTX302	17p	ZN3708	10p
AC127	13p	BC258	16p	MJ480	93p	ZTX303	16p	ZN3709	10p
AC128	13p	BC407	16p	MJ481	£1.18	ZTX304	21p	ZN3710	11p
AC176	15p	BCV70	17p	MJ490	£1.01	ZTX311	16p	ZN3711	11p
AC187	22p	BCV71	22p	MJ491	£1.42	ZTX312	10p	ZN3772	£2.00
AC187K	20p	BCY22	17p	MJ900	£1.42	ZTX341	22p	ZN3791	£2.55
AC188	22p	BD115	73p	MJ1000	£1.22	ZTX384	18p	ZN3819	27p
AC188K	22p	BD123	89p	MJ2955	£1.88	ZTX500	12p	ZN3821	81p
ACV17	39p	BD124	11p	MJ3055	£1.21	ZTX501	13p	ZN3828	99p
ACV17	38p	BD131	44p	MJ4000	£1.46	ZTX502	17p	ZN3902	16p
ACV20	22p	BD132	52p	MJ4010	£1.95	ZTX503	14p	ZN3904	19p
AD140	48p	BD132P2R	£1.17	MJ340	45p	ZTX504	42p	ZN3905	23p
AD149	48p	BD135	41p	MJE350	97p	ZTX531	22p	ZN3906	25p
AD161	37p	BD136	43p	MJE2955	£1.20	ZTX550	17p	ZN4056	13p
AD162	39p	BD201	£1.95	MJE3055	72p	ZN697	16p	ZN4059	19p
AD161/62MP	74p	BD202	£1.46	MPF102	27p	ZN706	13p	ZN4062	16p
AF114	17p	BF109	16p	MPF103	40p	ZN708	16p	ZN4289	19p
AF115	17p	BF115	25p	MPF104	44p	ZN914	24p	ZN4481	85p
AF116	17p	BF160	25p	MPF105	44p	ZN930	20p	ZN4442	£1.42
AF117	17p	BF167	24p	MPF106	49p	ZN1302	20p	ZN4443	£1.42
AF118	54p	BF173	24p	MPF111	22p	ZN1303	24p	ZN4444	£2.06
AF124	32p	BF178	28p	MP5U6	77p	ZN1305	24p	ZN4491	£1.41
AF139	34p	BF179	32p	OC28	49p	ZN1307	27p	ZN4507	11p
AF172	25p	BF180	32p	OC28	49p	ZN1308	34p	ZN4572	77p
AF239	40p	BF181	32p	OC35	49p	ZN1309	34p	ZN4591	77p
ASV26	32p	BF184	27p	OC36	49p	ZN1711	26p	ZN5194	91p
BC107	11p	BF185	27p	OC44	14p	ZN1718	£4.37	ZN5295	52p
BC108	11p	BF194	15p	OC45	14p	ZN1719	26p	ZN5374	91p
BC109	12p	BF195	17p	OC71	15p	ZN1879	52p	ZN5447	16p
BC117	22p	BF196	16p	OC72	15p	ZN2218	23p	ZN5449	16p
BC129	10p	BF197	16p	OC75	17p	ZN2219	38p	ZN5457	46p
BC148	10p	BF200	31p	OC76	27p	ZN2646	14p	ZN5458	43p
BC149	10p	BF248	27p	OC81	27p	ZN2646	14p	ZN5459	46p
BC157	13p	BF262	25p	OC83	25p	ZN2894	97p	ZN5459	46p
BC158	12p	BF263	25p	OC170	27p	ZN2904	32p	ZN5485	52p
BC159	14p	BF272	£1.19	OC171	32p	ZN2905	30p	ZN5485	52p
BC167	17p	BF597	23p	OC P17	£1.54	ZN2924	16p	ZN6068	44p
BC168	12p	BF598	20p	OC P22	12p	ZN2925	18p	ZN6069	51p
BC169	12p	BF598	20p	P1P26G	10p	ZN2926	10p	ZN6070	57p
BC171	20p	BFW10	45p	PI31	57p	ZN3019	17p	ZN6071	62p
BC172	17p	BFX 29	41p	PI31A	67p	ZN3054	15p	ZN6072	67p
BC177	22p	BFX88	26p	PI32A	79p	ZN3055	51p	ZN6073	67p
BC178	22p	BFY50	22p	PI41A	79p	ZN3375	£3.56	ZN6076	16p
BC179	24p	BFY51	22p	PI42A	97p	ZN3442	£1.19	ZN6111	54p
BC182L	11p	BFY52	£1.09	TIS43	33p	ZN3566	18p	ZN6268	60p
BC183L	12p	BR100	42p	TIS43A	36p	ZN3638	20p	ZN6440	99p
BC184L	12p	BRX39	43p	TIS91	32p	ZN3708	17p	ZN6553	87p
BC187	27p	BRX20	18p	ZTX107	10p	ZN3709	17p	ZN6553	87p
BC204	14p	BSX21	22p	ZTX108	10p	ZN3709	17p	ZN6553	87p
BC209	14p	BSY95A	14p	ZTX109	12p	ZN3705	12p	ZN6553	87p
BC212L	12p	BU105D	£1.95	ZTX300	12p	ZN3706	14p	ZN673	55p

REGULATORS

	100mA (TO-39)	500mA (TO-3)	500mA (ISOT-32)	1A (TO-220)
		20°C	0°C	
		+85°C	+70°C	
3V	TBA625A	L005T1 (MVR5V)	L129	TDA1405
	£1.03	£1.45	£1.39	79p
12V	TBA625B	L035T1 (MVR12V)	L130	TDA1412
	£1.03	£1.45	£1.39	79p
15V	TBA625C	L037T1 (MVR15V)	L131	TDA1415
	£1.03	£1.45	£1.39	79p

THYRISTORS SCR'S


V		800mA	4A	8A
30v	MCR102	32p	106p	39p
50v			106p	44p
60v	MCR103	44p		
100v	MCR104	49p	106A	48p
200v	MCR120	51p	106B	53p
400v			106D	67p
600v			106M	£1.50

DIGITAL SWITCH

BCD encoded digital switch
Reading 0 to 9. Suitable for digital clock alarm setting
DVM input scaling etc.

1 to 9. £1.49 each.

ALUMINIUM BOXES

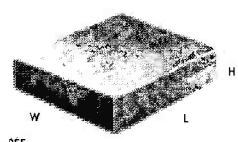

REF (No.)	(L)	(W)	(H)	PRICE	P&P
AB7	2 1/2"	5 1/2"	1 1/2"	45p	15p
AB8	4"	4"	1 1/2"	45p	15p
AB9	4"	2 1/2"	1 1/2"	45p	15p
AB10	4"	5 1/2"	1 1/2"	51p	15p
AB11	4"	2 1/2"	1"	45p	15p
AB12	3"	2"	1"	39p	15p
AB13	6"	4"	2"	61p	17p
AB14	7"	5"	2 1/2"	73p	17p
AB15	8"	6"	3"	92p	17p
AB16	10"	7"	3"	£1.05	20p
AB17	10"	4 1/2"	3"	92p	25p
AB18	12"	5"	3"	£1.04	25p
AB19	12"	8"	3"	£1.38	25p

8: VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT 2%
VAT INVOICES ON REQUEST.
P&P. On U.K. Orders min. 15p.. Overseas Orders at Cost

ENGINEERS FREE YOURSELF FOR A BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!
Tick or state subject of interest. Post to the address below.

Build-As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit) <input type="checkbox"/>	Electronic Engineering <input type="checkbox"/>	CITY AND GUILDS Installations and Wiring <input type="checkbox"/>
Computer Electronics <input type="checkbox"/>	Computer Programming <input type="checkbox"/>	CITY AND GUILDS Electrical Technicians <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	General Radio and TV Engineering <input type="checkbox"/>	CITY AND GUILDS Telecommunications <input type="checkbox"/>
Electrical Installations and wiring <input type="checkbox"/>	Radio Servicing, Maintenance and Repairs <input type="checkbox"/>	Radio Amateurs' Exam etc. etc. <input type="checkbox"/>
Electrical Draughtsmanship <input type="checkbox"/>	Transistor Technology <input type="checkbox"/>	
Electrical Mathematics <input type="checkbox"/>		

To ALDERMASTON COLLEGE Dept. EPW-03, Reading RG7 4PF **EPW-03**

NAME (Block Capitals Please) _____ POST CODE _____

ADDRESS _____

Other subjects _____ Age _____

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

QUALITY STEREO SOUND

SOLENT AUDIO SYSTEM

ALMOST 1/2 PRICE OFFER!

MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM

OUR PRICE **£49.95**

£5 down

*Stereo Tuner Amplifier chassis with AM,FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,00 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/2". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49.95. Credit Sale £5.00 deposit 9 monthly payments of £5.75 (Total Credit price £56.75). P. & P. £3.00. Send £8.00 today.

Chassis only available for cash at £35.00.

Full 12 months Guarantee.
CALLERS WELCOME.

Stereo headphones supplied with every complete order.

LEWIS radio PW/5/75 100 CHASE SIDE SOUTHGATE LONDON N14 5PL Telephones: 01-882-1644

THE FLEA THAT ROARS!!!

A good transmitting aerial IS a good receiving aerial—Accepted radio thinking and simple logic—if you can't hear 'em you sure can't work 'em Read what the **DX ITSELF** has to say about the "FLEA" powered 230cm long V.F.A.—operated continuously under "impossible" conditions—A stamp secures the evidence!!!

PARTRIDGE have a complete **VFA SYSTEM**, correctly terminated for your equipment ranging from modern communications gear to a modest solid state radio. Don't be satisfied with anything less than the **PARTRIDGE WORLD RECORD ANTENNA SYSTEM!** Make your selection from the list below:-

- (Each **SYSTEM** consists of the elegant gold stove enamelled 7' 6" VFA and a matching finish **JOYMATCH A.T.U.**, despatched direct by parcel post—our risk). (All prices delivered—our risk). Prices subject to alteration without notice.
- SYSTEM 'A'** for modern Communications Receivers £28.61
- SYSTEM 'D'** for other S.W. and M.W. receivers, all types £21.02
- SYSTEM 'J'** for TXs and TCVRs up to 500w PEP 160 thru 10m (pa inpt) £35.78
- JOYMATCH A.T.U.** kit (1.6 continuous to 30 mHz) £6.27
- JOYMATCH A.T.U.** kit (500 kHz continuous to 30 mHz) £6.27
- Either kit fully assembled £7.58
- JOYMATCH "Aerial Bandswitch"** tuned aerial. MW & SW £6.27
- SUPER SENSITIVE** general coverage DX-CRYSTAL SET that REALLY WORKS, not a toy, complete with Aerial and a sensitive matching Earpiece £3.95
- COMMUNICATIONS HEADPHONES**, 8 ohms, matches most modern Comm. Rxs. £4.02
- VFA Stack Lashing (Massive VFA support on chimney stack) £2.17
- JOYMATCH** Artificial Earth (ground) switch tuned £6.27
- A.G.T.U. Artificial Earth D.I.Y. add on unit for your A.T.U. £0.63
- Radials for the A.G.T.U. cut to required band, each £0.63
- "INVISIBLE AERIAL" wire, tough PVC covered tinned copper 22swg per 10m £0.63
- A.G.T.U. supplied fitted to **JOYMATCH A.T.U.'s** (less radials) £0.83
- FIELD STRENGTH METER**, (Japanese) £1.83
- VALVES**, complete set for 9R59DS & 9R59DE, including OA2 stabiliser £5.28


PARTRIDGE SUPER PACKAGE

COMPLETE RADIO STATION FOR ANY LOCATION £158.00
Comprising:—Trio QR666 Gen. Cov. RX, Headphones, V.F.A., System 'A', all connecting cables, del. (our risk)

Send 4½p stamp for details and expert advice.



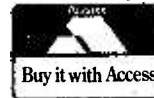Phone 0843 62535
or 62839
(after office hours)
G3CED G3VFA



BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

Bargains from our FREE Catalogue

20 large pages, filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 6p stamp for your FREE copy of 6th Edition by return. Meanwhile, for prompt delivery order from this month's ad. NOW.

TRANSISTOR PACKS ALL AT 50p EACH TESTED & GUARANTEED

- | | | | | | |
|-----|-----|--|-----|---|---|
| B79 | 4 | IN4007 Sil. Rec. diodes. 1,000PIV 1 amp. plastic | H39 | 6 | Integrated circuits 4 gates BMC 982, 2 flip flops BMC945 BD131/BD132 |
| B81 | 10 | Reed Switches, 1" long 3/4" dia. High-speed P.O. type | H41 | 2 | Complementary Plastic Transistors 40381 Type NPN Sil. Transistors TO-5 can comp. to H65 |
| H35 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked. | H65 | 4 | 40382. Type PNP Sil. Transistors TO-5 can comp. to H65 |
| H38 | 30 | Short lead, NPN Silicon Planar Ex Equipment. | H66 | 4 | 40382. Type PNP Sil. Transistors TO-5 can comp. to H65 |

UNMARKED & UNTESTED

- | | | | | | |
|-----|-----|--|-----|-----|---|
| B1 | 50 | Germanium Transistors PNP, AF and RF | B86 | 100 | Sil. Diodes sub. min. IN914 and IN916 types |
| B65 | 150 | Germanium, Diodes Min. glass type | H20 | 20 | BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts |
| B83 | 200 | Transistors, manufacturers' rejects AF, RF, Sil. and Germ. | H34 | 15 | Power Transistors, PNP, Germ. NPN Silicon TO-3 Can |
| B84 | 100 | Silicon Diodes DO-7 Min. glass equivalent to IN4148 | H67 | 10 | 3819N Channel FET's plastic case type |

PLASTIC POWER TRANSISTORS

40 WATT SILICON					
Type	Polarity	Gain	VCE	Price	
40N1	NPN	15	15	20p	
40N2	NPN	40	40	30p	
40P1	PNP	15	15	20p	
40P2	PNP	40	40	30p	
30 WATT SILICON					
Type	Polarity	Gain	VCE	Price	
30N1	NPN	15	15	25p	
30N2	NPN	40	40	35p	
30P1	PNP	15	15	25p	
30P2	PNP	40	40	35p	

NEW X-HATCH GENERATOR Mk. 2



Essential for Colour T.V. alignment of 4 patterns. Featuring plug in IC's and a more sensitive sync-pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3". Operates from 3 U2 type batteries (extra).

Complete kit **£7-93** Ready built unit only **£9-93**

TO CLEAR

Hundreds of various portable transistor radio chassis with FM & AM tuning. Ideal for experimenters. All in going order, but no instructions or tuning drives. A cheap way to make a portable. Each £1.

SUNDRY

Electronic Ignition Kit £7-50. 8 assorted relays £1-00. Rev. counter device (for cars) £1-00. U.H.F./TV Tuner Units £2-50. L.M.380 Audio I.C. £1-00 and technical books of all kinds.

TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. Please add 8% to total value of your order including postage. No. V.A.T. on overseas orders.

POSTAGE Except where stated, add 15p for postage & packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum value—£1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

BI-PRE-PAK LTD

Co. Reg. No. 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 90F.

TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED




challenging values!

Stirling Sound


STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatched and include well printed instructions.

AMPLIFIER MODULES

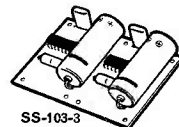- Pre-amplifiers; tone control**
- SS.100 Active tone control unit to provide bass, treble, balance and volume controls **£1-60**
 - SS.101 Pre-amp for ceramic cartridge, tape and radio **£1-60**
 - SS.102 Pre-amp for low output magnetic cartridge, tape and radio. With R.I.A.A. correction $\pm 1\text{dB}$ at 1K **£2-25**




SS-103-3

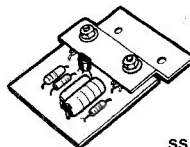


SS.105

POWER AMPLIFIERS

- SS.103 Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6 to 22. Size 3" x 2" **£1-75**
- SS.103-3 Stereo version of above using one I.C. on each channel **£3-25**
- SS.105 A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 2 1/2" x 1 1/2" **£1-95**
- SS.110 Similar in size to SS.103 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 25 to 32V. **£2-40**
- SS.140 Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier, S/N ratio better than 75dB. THD better than 0.2%. Power requirements—45V. d.c. With 0.15" centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms **£3-60**

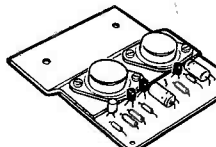


SS.140

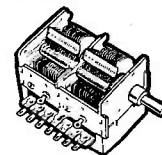

TUNER MODULES


- SS.201 Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-105MHz. With A.F.C. facility. Operates from 6-16V **£6-25**
- SS.202 I.F. stage (with I.C.) Pre-tuned, A.F.C. connection. Operates from 4.5 to 14V **£5-25**
- SS.203 Stereo Decoder. Designed essentially for use with SS.201 and 2, this module can also be used in most mono FM tuners. A LED may be attached. Operating voltage 9-16V. d.c. **£5-62**

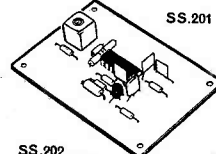

SS.201

POWER SUPPLY STABILIZER

- SS.300 Add this to an unstabilized supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential on your audio and special systems. Money saving and very reliable **£3-25**

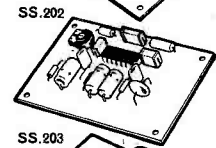


SS.202

● ALL MODULES TESTED AND GUARANTEED WITH INSTRUCTIONS

MAINS TRANSFORMERS FOR ABOVE

- Type A 18V/1A (Suit SS.103) **£1-50**
- Type B 25V/2A (Suit SS.110) **£2-00**
- Type C 30V/2A (Suit SS.140) **£3-25**
- Bridge Rectifiers—Type A 27p. Types B & C 38p

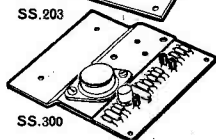

SS.203

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose inc. V.A.T.

Name

Address

PWS

Marshall's

A. Marshall & Son (London) Limited Dept. PW
42 Cricklewood Broadway London NW2 3HD Tel: 01-452 0161
& 85 West Regent Street Glasgow G22 QD Tel: 041-332 4133

Everything you need is in our new 1975 catalogue. Available now price 25p

Trade and export enquiries welcome

Our range covers over 7,000 items. The largest selection in Britain

Top 200 IC's TTL, CMOS & Linears


CA3018A	85p	CD4043	£1.80	NE565	£4.48	SN7448	90p	SN74157	95p
CA3020A	£1.80	CD4044	£1.80	SL414	£1.80	SN7450	16p	SN74160	£1.10
CA3028A	79p	CD4045	£2.85	SL610C	£1.70	SN7451	16p	SN74161	£1.10
CA3035	£1.37	CD4046	£2.84	SL611C	£1.70	SN7453	16p	SN74162	£1.10
CA3046	70p	CD4047	£1.65	SL612C	£1.70	SN7454	16p	SN74163	£1.10
CA3048	£2.11	CD4049	81p	SL620C	£2.60	SN7460	16p	SN74164	£2.01
CA3052	£1.62	CD4050	66p	SL621C	£2.60	SN7470	33p	SN74165	£2.01
CA3089E	£1.96	LM301A	48p	SL623C	£4.59	SN7472	26p	SN74167	£4.10
CA3090Q	£4.23	LM308	£2.50	SL640C	£3.10	SN7473	36p	SN74174	£1.25
CD4000	£1.50	LM005TL	£1.50	SN7400	£1.50	SN7474	36p	SN74175	90p
CD4001	36p	LM380	£1.10	SN7401	16p	SN7475	50p	SN74176	£1.44
CD4002	36p	LM381	£2.20	SN7401AN	38p	SN7476	35p	SN74180	£1.40
CD4006	£1.58	LM702C	75p	SN7402	16p	SN7480	50p	SN74181	£1.95
CD4007	36p	LM709	38p	SN7403	16p	SN7481	£1.25	SN74190	£2.30
CD4008	£1.63	SD1	49p	SN7404	19p	SN7482	75p	SN74191	£2.30
CD4009	£1.18	14D1L	40p	SN7405	19p	SN7483	95p	SN74192	£1.15
CD4010	£1.18	LM710	47p	SN7406	45p	SN7484	95p	SN74193	£1.15
CD4011	36p	LM723C	90p	SN7407	45p	SN7485	£1.25	SN74196	£1.60
CD4012	36p	LM741C	40p	SN7408	19p	SN7486	32p	SN74197	£1.58
CD4013	66p	BD1L	40p	SN7409	22p	SN7490	45p	SN74198	£2.35
CD4014	£1.72	14D1L	38p	SN7410	16p	SN7491	85p	SN74199	£2.25
CD4015	£1.72	LM747	£1.05	SN7411	25p	SN7492	45p	SN76003N	£2.92
CD4016	66p	LM748	60p	SN7412	28p	SN7493	45p	SN76013N	£1.95
CD4017	£1.72	14D1L	73p	SN7413	35p	SN7494	82p	SN76023N	£1.60
CD4018	£2.55	LM3900	70p	SN7416	35p	SN7495	72p	SN76033N	£2.92
CD4019	86p	LM7805	£2.00	SN7417	35p	SN7496	75p	TAA263	£1.10
CD4020	£1.91	LM7812	£2.50	SN7420	16p	SN74100	£1.25	TAA300	£1.80
CD4021	£1.72	LM7815	20.50	SN7421	29p	SN74107	36p	TAA350A	£2.10
CD4022	£1.64	LM7824	£2.50	SN7425	29p	SN74118	£1.00	TAA550	60p
CD4023	36p	MC1303L	£1.50	SN7427	29p	SN74119	£1.92	TAA611C	£2.18
CD4024	£1.24	MC1310P	£2.59	SN7430	16p	SN74121	37p	TAA621A	£2.03
CD4025	32p	MC1330P	90p	SN7432	28p	SN74122	50p	TAA661B	£1.32
CD4027	43p	MC1351P	80p	SN7437	35p	SN74123	60p	TBA641B	£2.25
CD4028	£1.50	MC1352P	80p	SN7438	35p	SN74141	85p	TBA651	£1.69
CD4029	£3.50	MC1466L	£3.50	SN7440	16p	SN74145	90p	TBA800	£1.40
CD4030	87p	MC1469L	£2.75	SN7441AN	85p	SN74150	£1.50	TBA810	£1.40
CD4031	£5.19	NE555V	70p	SN7442	65p	SN74151	85p	TBA820	£1.15
CD4032	£1.93	NE556	£1.30	SN7446	95p	SN74153	85p		
CD4037	£1.86	NE560	£4.48	SN7447	95p	SN74154	£1.50		

PW TELE TENNIS KIT £42.50 + VAT Reprint 75p
TRY OUR GLASGOW SHOP

POPULAR SEMICONDUCTORS

2N696	22p	2N3906	27p	AF139	65p	BD139	71p	MPSA56	31p
2N697	16p	2N4037	42p	AF239	65p	BD140	87p	OC28	76p
2N698	82p	2N4036	67p	AF240	90p	BF115	36p	OC35	60p
2N699	59p	2N4038	18p	AF279	70p	BF117	55p	OC42	50p
2N706	14p	2N4052	74p	AF280	70p	BF154	36p	OC45	32p
2N708	17p	2N4289	34p	AL102	£1.00	BF159	27p	TIP29A	49p
2N916	28p	2N4920	£1.10	BC107	14p	BF180	35p	TIP29C	58p
2N918	32p	2N4921	83p	BC108	14p	BF181	36p	TIP31A	62p
2N1302	18p	2N4923	£1.00	BC109	14p	BF184	30p	TIP32A	74p
2N1304	26p	2N5245	47p	BC147B	14p	BF184	12p	TIP34A	£1.01
2N1306	31p	2N5294	48p	BC148B	15p	BF195	12p	TIP34A	£1.51
2N1308	47p	2N5296	48p	BC149B	15p	BF196	13p	TIP35A	£2.90
2N1711	45p	2N5457	49p	BC157A	16p	BF197	15p	TIP36A	£3.70
2N1702	60p	2N5458	46p	BC158A	16p	BF198	18p	TIP42A	£0.90
2N1747	78p	2N5459	49p	BC167B	15p	BF244	21p	TIP295S	98p
2N1748	94p	2N6077	65p	BC168B	15p	BF257	47p	TIP305S	50p
2N2218A	28p	2N128	73p	BC169B	15p	BF258	53p	TIS43	28p
2N2219A	26p	3N140	£1.00	BC182	12p	BF259	55p	ZTX300	13p
2N2220	25p	3N414	81p	BC182L	12p	BF561	27p	ZTX301	13p
2N2221	18p	3N200	£2.49	BC183	12p	BF598	25p	ZTX500	15p
2N2222	20p	40361	40p	BC183L	12p	BF939	24p	ZTX501	13p
2N2369	20p	40362	45p	BC184	13p	BFR79	24p	ZTX502	18p
2N2646	55p	40406	44p	BC184L	13p	BFX29	30p	IN91	7p
2N2904	22p	40407	35p	BC212A	16p	BFX30	27p	IN3754	15p
2N2905	25p	40408	50p	BC212LA	16p	BFX84	24p	IN4007	10p
2N2906	19p	40409	52p	BC213LA	15p	BFX85	30p	IN4148	7p
2N2907	22p	40410	52p	BC214LB	18p	BFX88	25p	IN5404	22p
2N2924	10p	40411	£2.00	BC237B	16p	BFY50	23p	IN5406	30p
2N2926C	12p	40594	74p	BC238L	15p	BFY51	43p	BA119	8p
2N3053	25p	40595	84p	BC239C	15p	BFY52	20p	BA102	25p
2N3054	60p	40636	£1.10	BC257A	16p	BRY39	48p	BA145	18p
2N3055	75p	40673	73p	BC258B	16p	ME0402	20p	BA154	12p
2N3391	28p	AC126	20p	BC259B	17p	ME0412	18p	BA155	12p
2N3392	15p	AC127	20p	BC301	34p	ME102	11p	BB103B	23p
2N3393	15p	AC128	20p	BC307B	17p	MJ480	95p	BB104B	8p
2N3440	59p	AC151	27p	BC308A	15p	MJ481	£1.20	BY126	12p
2N3442	£1.40	AC152	49p	BC309C	20p	MJ490	£1.05	BY127	15p
2N3638	15p	AC153	35p	BC327	23p	MJ491	1.45	BYZ11	51p
2N3702	12p	AC176	30p	BC328	22p	MJ2955	£1.00	BYZ12	51p
2N3703	13p	AF137K	35p	BCY70	17p	ME340	48p	CA47	18p
2N3704	15p	AC188K	40p	BCY71	22p	MIE370	65p	OA81	18p
2N3706	15p	AD143	68p	BCY72	15p	MJE371	75p	OA90	6p
2N3708	14p	AD161	50p	BD121	£1.00	MJE520	60p	OA91	6p
2N3714	£1.38	AD162	50p	BD123	82p	MJE512	70p	WOZ1A200	
2N3716	£1.80	AF106	40p	BD124	67p	MJE2955	£1.20		
2N3771	£2.20	AF109	40p	BD131	40p	MJE3055	75p	BY164	57p
2N3773	£2.15	AF116	35p	BD132	50p	MJE313	47p	BY165	70p
2N3789	£2.06	AF116	35p	BD135	43p	MPE102	39p	40665	£1.00
2N3819	37p	AF117	35p	BD136	47p	MPSA05	25p	TIC44	29p
2N3820	64p	AF118	35p	BD137	55p	MPSA06	31p	C106D	65p
2N3904	27p	AF124	30p	BD138	63p	MPSA55	31p	ORP12	60p

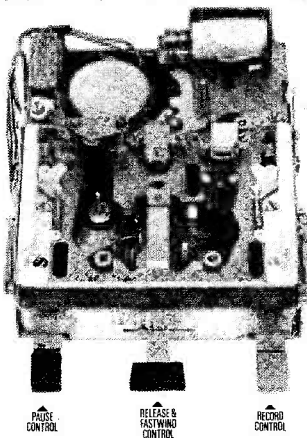Prices correct at April 1975, but all exclusive of VAT. P. & P. 25p.



GARRARD CT4'S MK III STEREO CASSETTE PLAYER & RECORDER

has full facilities for record, playback, pause, erase, rest, fast forward and reverse wind, automatic tape end stop and cassette release.

Robust, precision engineered mechanism based on the "STARR" patented design. Ideal for use in Car stereo cassette players, HI-FI stereo cassette recorders, industrial and many other applications.

Send cheque or Postal Orders for £19.98 (£18.50 + 8% VAT) (includes post and packing) to:

BOTHWELL ELECTRIC SUPPLIES
(Glasgow) LIMITED
431 Sauchiehall Street
GLASGOW G2 3LG Tel: 041-332 6184
Scotland's Leading Electronics Centre

Quality Loudspeaker Systems

Direct from manufacturer as supplied by us to the trade. Finished in natural Teak veneer 15 watt 8 ohm bass reflex speaker system containing Goodman's 8" bass with HF speaker. Frequency response 50 Hz - 19000 Hz. Complete with leads and DIN plug. Cabinet size 17" x 10" x 7" deep.
Price £17.00/pair including VAT plus £1.90 packing, carriage and insurance (U.K. mainland).
*Bulk discounts available for trade enquiries. Please send cash with order direct to:-
Forward Marketing, 30 Ridgeway, Stanground, Peterborough.



Crescent Quality Components

BARGAIN CAPACITOR 2,200MFD at 63v. DC wkg.
Size = 2" x 1 1/2" diameter. Tag ended. All new and unused. Our price 85p.


S. G. BROWN HEADSET
Finest quality British made lightweight headphones. Incorporates ceramic piezo electric transducers.
Specification:—
Frequency—20-17,500 CPS
Impedance—Predominantly capacitive, at 60IMFD per earpiece can be regarded as 150K at l.kcs.
Weight—3-6oz. (98 grams).
A bargain at £1.25 each set

JBL1D STEREO JUNCTION BOX
The most popular stereo junction box. Facility for two pairs of headphones and two speakers. 3 position switch selects headphones, loudspeakers or both.
A bargain at £2.50



LIGHT EMITTING DIODES

TL1 209 (Red) With Clip 22p each
TL1 209 (Green) With Clip 38p each
TL1 209 (Yellow) With Clip 90p each
Med 600 Type Type 16p each
LED READOUTS
Litronix
DL707 3 Character 14 Pin Dtl. £2.00
DL701 as above but ± 1 £2.00
DL747 6 Character £2.62
Mintron
3015 F Segment 16 Pin Dtl £1.18
3016G as above but ± 1 £1.18
Clock Chip
CT7001 MOS/LSI Digital Clock/Calendar Chip Plus full Circuits and Information leaflet £4.95
Circuits and Information Sheet 15p
Lit 704 Led Display for above £1.10
Or 4 for £4.20

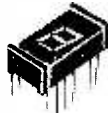

WAFER SWITCHES

1 Pole 12 Way
2 Pole 2 Way
2 Pole 3 Way
2 Pole 4 Way
2 Pole 6 Way
3 Pole 4 Way
4 Pole 3 Way
22p each



POTENTIOMETERS

All types 1" and less diameter
Singles Dual
5K Log or 5K
10K Lin Less 10K
25K Switch 25K Less
50K 15p each 50K Switch 45p each
100K 100K
250K Double 250K
600K Pole 500K
1M Switch 1M
2M 30p each 2M

PRE SETS

Sub Miniature Skeleton Type 0-1 Watt Horizontal Mounting, 10k, 250 and 500 ohm, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, and 1M ohm 8p each

MAINS TRANSFORMERS

Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded flying leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high
Fixing centres: 2 1/2", 3 1/2"
TR1 20-0-20v 100 m/a
TR2 12-0-12 v 100 m/a All
TR3 9-0-9 v 100 m/a 240 Volt
TR4 6-0-6 v 100 m/a Primary
TR5 3-0-3 v 100 m/a
Our Price £1.23 each

800/850v MAINS RELAY

Heavy duty contacts 2-500 ohm coil. All new and unused D.P.D.T. mains relays 50p, Carr. Frce. Special quantity £40 per 100 off.

MINIATURE RELAYS

Brand new range of British made Relays, Size 1 1/2" x 1" x 1/2". All two changeovers with 250v 1.5A contacts and suitable for fitting on 1m Veroboard.
Type Volt Current Ohms
27/A 12v 17M/A 700 All
21/A 12v 28M/A 430 £1.30
12/A 6v 33M/A 185 each

MONO/STEREO MICROPHONE MIXER

9 volt. High impedance input. Gold finish with four black plastic chrome tipped level control knobs. On/Off switch and stereo/mono switch. 4 Input sockets.
SPECIFICATIONS:—
Input Imp For XTAL Mics etc.
Gain Approx 3.0dB
Max Input Sig 1 volt
Max Output Sig 1.3 volt
Noise Ratio — -60dB
Supply = 9 volt
OUR PRICE — £5.25

POWER PACKS

PP1 Switched 3 - 6 - 7 1/2 - 9 volt 400mA Transistor and Zener Stabilised On/Off Switch and Polarity Reversal Switch, in a black metal case £5.25 each.
PP2 Switched 6 - 7 1/2 - 9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders £3.25
PP3 Car converter. From 12v Pos. or Neg. to 6 - 7 1/2 - 9 volt. Easy to fit and transistor regulated £3.00



VEROBOARD

2 1/2 x 3 1/2	1	15	Plain 75
2 1/2 x 5	32p	24p	15p
3 1/2 x 3 1/2	34p	34p	18p
3 1/2 x 5	34p	34p	
3 1/2 x 5	38p	45p	
17 x 2 1/2	1.00p	77p	
17 x 3 1/2	1.45p	1.16p	60p
17 x 5	1.85p		1.10p

Pin insertion tool 72p
Spot face cutter 52p
Pkt. 30 pins (state 1 or 15) 25p

LOUDSPEAKERS

2 1/2" 8 ohm 50p
2 1/2" 40 ohm 50p
2 1/2" 80 ohm 50p
5" 8 ohm ceramic £1.25
6 1/2" 8 ohm dual conc ceramic £2.50
10" 8 ohm dual conc ceramic £3.75
7" x 4" 8 ohm ceramic £1.60
5" x 6" 8 ohm Permanent Magnet £1.60
*EM1 13" x 8" 450 Kit £4.10
3 - 8 - 15 ohm
*EM1 13" x 8" 350 Kit £7.50



10 inch DUAL CONE L/S

Manufactured by "ELAC" to a very high standard these loudspeakers are a real bargain
SPEC:—Size=10" Dual Cone.
Power=10 Watts
Frequency=40-12000Hz
Our Price = £3.75p each



MAINS KEYNECTOR

KeyNECTOR connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage demonstrations, etc. Multi connections can be made (max. load 13A fused).
£3.25p.



ALUMINIUM BOXES

Metal project boxes give your work a professional finish

AB7	L	W	H	54p
AB8	2 1/2	5 1/2	1 1/2	83p
AB9	4	2 1/2	1 1/2	54p
AB10	4	5 1/2	1 1/2	83p
AB11	4	2 1/2	2	54p
AB12	3	2 1/2	1	45p
AB13	6	4	2	69p
AB14	7	5	2 1/2	84p
AB15	8	6	3	99p
AB16	10	7	3	£1.35
AB17	10	4 1/2	3	£1.02
AB18	12	5	3	£1.20
AB19	12	8	3	£1.60

ABS PLASTIC BOXES


Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.
1005 = 105mm x 73mm x 45mm = 51p
1006 = 160mm x 75mm x 47mm = 86p
1007 = 184mm x 124mm x 60mm = 96p
1021 = 106mm x 74mm x 45mm (sloping front) = 50p

BARGAIN BOARDS

Components galore for the experimenter Ex Computer boards with Resistors, Capacitors and useful Transistors— at least 4 transistors per board. Five boards £1.00.

CLEAR PLASTIC PANEL METERS

Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.
ME6 — 0 to 50 micro amp Full Scale
ME7 — 0 to 100 micro amp Full Scale
ME8 — 0 to 500 micro amp Full Scale
ME9 — 0 to 1 m/a Full Scale
ME10 — 0 to 5 m/a Full Scale
ME11 — 0 to 10 m/a Full Scale
ME12 — 0 to 50 m/a Full Scale
ME13 — 0 to 100 m/a Full Scale
ME14 — 0 to 500 m/a Full Scale
ME15 — 0 to 1 amp Full Scale
ME16 — 0 to 50 volts
ME17 — 0 to 300 volts
A.C. Full Scale
ME18 — "S" Meter
ME19 — "VU" Meter

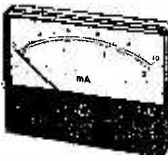

OUR PRICE £3.00

ADD LUXURY TO YOUR CAR

with a motor driven car aerial
SPEC:— ★ 5 section
★ extended length 100cm
★ Length under fender 40cm
★ Cable length 120cm
Supplied complete with fixing bracket and control switch £7.50

DECON DALO 33PC ETCH RESIST PEN
The Decon Dalo 33PC is a unique instrument for the professional and amateur electronics engineer, enabling him to prepare in minutes a perfect printed circuit board
OUR PRICE 80p

WIRE WOUND VOLUME CONTROL
250ohm Only 25P EACH.
Approx 1" Diameter. Long standard spindle.

CABLE LESS SOLDERING IRON

WABL "ISO-TIP"
★ Completely Portable
★ Heats in 5 seconds
★ Solders up to 150 joints or more per charge
★ Recharges automatically in its own stand
★ No AC leakage or induced current to damage delicate components
★ Heats to 700 deg. F
★ Fine Tip for delicate and general purpose soldering
★ Only 8" long and weighs just 6 ozs.
OUR PRICE £9.75 (spare bits are available)

STOP PRESS

BHA0002	15 watt Amp Modul-	£2.50
NE565	Timer I.C.	78p
MC1310P	Stereo Decoder I.C.	£8.00
7805	Regulator	£1.49
TTP 29A		55p
TTP 30A		10p
BC107		10p
BC108		10p
BC109		10p



I.C. SOCKETS

D.I.L.
8 pin 14p
14 pin 14p
16 pin 14p

BARGAIN TRANSFORMERS

12-0-12 volt 500m/a
240 volt primary transformer bargain.
approx size = 60mm x 40mm x 50mm
fixing centres = 75mm
Our Price = £1.20.
18 volt 500m/a
240 volt primary
approx size = 60mm x 40mm x 50mm
fixing centres = 75mm
Our Price = £1.00.

LOW NOISE LOW PRICE CASSETTES
Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C90 - 31p
C90 - 42p
C120 - 53p
10% Discount on ten or more cassettes of one type

U.K. POSTAGE 15p UNLESS OTHERWISE STATED

V.A.T. Please add 8% to all Totals

CRESCENT RADIO LTD. P.W.

All mail to 11 MAYES ROAD, WOOD GREEN, LONDON N22 6TL
Phone: 01-888 3206

Callers Welcome at 15 Mayes Road & 13 South Mall, Edmonton N9.

If you construct You should own one.

CRESCENT CATALOGUE Price 30p.

Practical Wireless Classified Advertisements

Receivers and Components

MULTI-BAND RADIOS. Grundig Satellit, 13 band, £129; Kovo, marine, aircraft, PSB, FM, SW1, SW2, MW, LW, batt/mains, £44; 4-band, MW, FM, aircraft, PSB, £14. SAE lists. Langtons Radio, High Street, Rochester, Staffordshire. 088 923 388.

INFLATION? PRICE INCREASES? SGS.ATES 7 watt IC TBA810AS, only 99p. Send £1.98+20p post for two, data included. PC Boards 55p each, post 10p. 7 watt IC kit, all parts £2.25, post 20p. Ready Built 7 watt IC modules using TBA810AS overload protected size 3 1/4 x 2 1/2 x 3/4, £2.50 each, (stereo) 2 for £4.60, (quad) 4 for £8.50. Post 25p per order. Send mail order to Watson, c/o 131 Buxton Street, London E1.

Precision Polycarbonate Capacitors

All High Stability—Extremely Low Leakage

440V AC (±10%)	63V Range	±1%	±2%	±5%
0.1µF (1" x 1/2")	50p	0.47µF	50p	40p
0.22µF (1" x 1/2")	50p	1.0µF	60p	45p
0.25µF (1" x 1/2")	60p	2.2µF	80p	55p
0.47µF (1" x 1/2")	71p	4.7µF	£1.30	£1.05
0.5µF (1 1/2 x 1/2")	75p	6.8µF	£1.64	£1.29
0.68µF (2" x 1/2")	80p	10.0µF	£2.00	£1.40
1.0µF (2" x 1/2")	81p	15.0µF	£2.75	£2.15
2.0µF (2" x 1/2")	81p	15.0µF	£2.75	£2.15

TANTALUM BEAD CAPACITORS—Values available: 0.1-0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 5V/10V or 15V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 10p each, 10 for 85p, 60 for 24.

TRANSISTORS:	BC188/183L	11p	BFY50	20p
BC107/8/9	8p	BC184/184L	12p	BFY51
BC114	12p	BC212/212L	14p	BFY52
BC147/8/9	10p	BC647/568A	12p	AF178
BC153/7/8	12p	BF194	12p	OC71
BC182/182L	11p	BF197	18p	2N3055

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 80p; 1N916 8p, 6 for 45p, 14 for 80p; 1844 5p, 11 for 50p, 24 for £1.00, 1N4148 5p, 6 for 27p, 12 for 45p; 1N4001 4p, 602 6p, 603 6p, 904 7p, 905 7p, 906 8p, 907 8p. **LOW PRICE ZENER DIODES**—400mW. Tol. ±5%. 34 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.6V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. All at 7p each, 6 for 39p, 14 for 84p. **SPECIAL OFFER:** 100 Zeners for 45.00.

RESISTORS—High stability, low noise carbon film 5%, 1W at 40°C, 1/2W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. **SPECIAL PACK:** 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 45.

SLIDON PLASTIC RECTIFIERS—1.5 amp, brand new wirewound DO27-100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2 1/2 amp; 200V 40p; 350V 45p; 600V 55p.

SUBMINUTE VERTICAL PRESETS—0.1W only: ALL at 5p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 680kΩ, 1MΩ, 2.2MΩ, 5MΩ.

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SFA/AIRMAIL.

PLEASE ADD 8% V.A.T. TO ORDERS. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. W5), The Old School, Edstaston, Nr. Wem, Shropshire. Tel: Whixall 448/445 (829 094 872). (Proprs. Minicost Trading Ltd.)

BRAND NEW COMPONENTS by return. Electrolytics, 15V, 25V, 50V 0.47, 1, 2.2, 4.7, 10 Mfd.—4p, 22, 47—4 1/2p (50V—5p), 100—5 1/2p (50V—7p), 220—6p (50V—9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 22/16V, 47/6V, 100/3V—9p. Mylar Film 100V 0.001, 0.002, 0.005, 0.01, 0.02—2 1/2p, 0.04, 0.05—3p. Mullard Tubular Polyester 400V E6 series, 0.001-0.022—3p, 0.033-0.1—4p. Mullard miniature C333 ceramics E.12 series 2% 1.8pf-47pf.—2 1/2p, 56pf-330pf.—3p. Polystyrene 63V, E12 series 10pf-1,000pf.—2 1/2p, 1,200pf-10,000pf.—3 1/2p. Miniature Highstab Carbon Film Resistors 1/2W E12 series 5% 10-10MΩ (10% over 1 Megohm)—1p. Postage 10p. Prices VAT inclusive. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

MULLARD 10W RMS AMPLIFIER MODULES. Absolutely complete. £2.65 inclusive. LTE, 46 Minehead Road, South Harrow, Middx.

BETA DEVICES FOR BETTER PRICES

TRANSISTORS	DIODES & RECT.	BRIDGE RECT.
AC187/8 PR 0-40	1N914 0-04	1A 100V 0-20
BC107/8/9 0-09	1N4148 0-04	1A 200V 0-22
BC109C 0-11	BY127 0-14	1A 600V 0-30
BC147/8 0-10	1N4001/2 0-05	2BA 200V £2-00
BCY70/1/720-13	1N4003/4/5 0-08	ZENERs
BFX88 0-20	1N4006/7 0-08	BZ788c 3-3-
BFY50 0-18	1N5401 0-11	33V 5% 0-00
BFY61/52 0-12		1 watt 6.8-200V 5% 0-15
2N1132 0-25	7 SEG DISPLAYS	
2N1711 0-25	3015F £1-00	L.E.D.
2N2646 0-30	DL707-LEDE1-70	289-RED 0-17
2N2905A 0-23	DL747-LEDE2-45	LED CLIP 0-02
2N3053 0-14		OP. AMP. IC's
2N3055 0-38	D.I.L. SOCKETS	709C T099 0-30
TIP29A 0-49	8 Pin 0-12	709C D.I.L. 0-30
TIP30A 0-57	14 Pin 0-12	741C T099 0-36
TIP31A 0-61	16 Pin 0-14	741C D.I.L. 0-36
TIP32A 0-74		723C D.I.L. 0-30
TIP4A 0-74	V.A.T. INC.	747C D.I.L. 0-85
TIP42A 0-90		748C D.I.L. 0-36
7400N 0-16	74 SERIES T.T.L.	7474N 0-37
7401N 0-18	7420N 0-18	7490N 0-63
7402N 0-18	7427N 0-28	7492N 0-63
7404N 0-19	7430N 0-18	7498N 0-82
7408N 0-23	7440N 0-18	74123N 0-50
7410N 0-18	7447N £1-00	74123N 0-70
7413N 0-39	7472N 0-32	74141N £1-26

C.W.O. PLUS P.P. 15p TO BETA DEVICES, Abbey Chambers, 4, Highbridge Street, Waltham Abbey, Essex.

PROBLEM GETTING AWKWARD or unusual components? Let us help you find them. Also 'one off' P.C.B.'s by return of Post Service. Yorke Electronics—027-588 (Bitton) 2707.

CLEARING DISTRIBUTOR STOCKS, transistors, diodes, components, etc. Sample pack 65p incl. postage and send stamp for list. Redhawk Sales Ltd., 10 Maple Lodge Close, Rickmansworth, Herts. Mail Order Only.

250mA. Cartridge Fuses 1 1/2" 90p per 100. Unused Carbon Resistors. 100 different 50p. Unused W/W Resistors. 100 assorted £1.10. 100 Capacitor Mixture, 85p. 1/8, 8 to 2BA, Nut & Bolt mixture 28p. Brass 38p. 18 Assorted Potentiometers Unused £4.15 Ex Government Standard Jack Plugs 4 for 50p 6 volt 36 or 18 watt Bulbs. SBC, 70p per doz. Earphones Ex Govt. 85p per pair. New Meter or Cassette Cases, stiff imitation leather 6 1/2" x 3 1/2" 47. Only 55p. Ex T.V. Speakers. Perfect. 3Ω elliptical 55p. 0.300mA Meters New. £1.75p. 7" Tape Spools 16p each. All postage in U.K. included in price

SOUND SYSTEMS OF SUFFOLK 676 Foxhall Rd., Ipswich, Suffolk IP3 8NQ

7-SEGMENT LED's. Red and Green. £1.30 each, 4 for £4.50 inc. p&p & V.A.T. CWO to Industrial Electronic Supplies (Stockport) Ltd., 181a Bramhall Lane, Stockport, SK2 6JA.

For Sale

WOW AND FLUTTER METER (Tecnica WF971). Unused as New £275.00. Telephone Mike Yorke 027-588 (Bitton) 2707 (daytime) or 0249 (Corcham) 713283 (evenings).

RGD 410 Radiogram, mint condition. Perfect working order. Offers. 021 705 5480. Bowen.

MICROPHONES: AKG D109, £12.65; AKG D202EI, £45.45; AKG D190C, £18.70; AKG D190E, £20; AKG D224 £55; Sennheiser MD211N, £49.50; Sennheiser MD413N, £29.70. All brand new and boxed. Send CWO to J. J. Francis, (Wood Green) Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

COPPER CLAD LAMINATE FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1.0p/sq. inch. Single sided 1/16" glass-epoxy—1.5p/sq. inch. Any rectangular size cut to your requirements. Please send cash with order. Price includes postage and packing. From: **SIMTECH ENGINEERING LTD VOLUNTARY PLACE WAINSTEAD LONDON E.11. 01-530-4240.**

SOUNDLIGHT CONVERTORS. 3 channel 1.5 kW £17; 5kW £25; 1 channel 1kW £9. STROBES: from £21. SEQUENCERS (Chasers): £95, etc. Call or catalogue sent. Aarvak Electronics, 98A (P), West Green Road (side door), London N15 5NS. Tel. 01-800 8656.

OSCILLOSCOPE (Cossor CDU 110) T/B Reconditioned as new £255. Telephone Mike Yorke 027 588 (Bitton) 2707 (daytime) or 0249 (Corcham) 713283 (evening).

Wanted

WANTED. Mains transformer, B40C receiver, Warner, 'Tasis', Carbis Bay, St. Ives, Cornwall.

"RADIO & TV SERVICING" books wanted from 1961 onwards. Any quantity. £2.00 paid per copy by return of post.—Bells Television Services, 190 Kings Road, Harrogate, Yorkshire. Tel. (0423) 55885.

TOP PRICES PAID for NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C), 367 Kensington Street, Bradford 8, Yorkshire.

AVO. 7 & 8 any condition. Any quantity. Huggett's, 2 Pawns Road, W. Croydon.

EARLY WIRELESS receivers, components and magazines, details to Johnson Raffles, Haverbreaks, Lancaster.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S,** 55 Worcester Street, Wolverhampton.

WANTED. Old Pye Radio or Radiogram. Condition immaterial.—Collins, 151 Hazleton Way, Horndean, Hants. Horndean 8725. Reverse charge evenings or weekends.

Books and Publications

THE McCOURT T.V. REPAIR MANUALS MAKE REPAIRS SIMPLE AS A.B.C.

Set out in the easiest to follow style, showing symptom, cause and cure for every common fault and virtually every possible one, for every British standard or portable set plus many foreign. Contained in 4 large manuals, only £12 set or send your model, make and £3-35 for the correct manual by return. Colour manuals £3-35 each, full details from:—

T.V. TECHNIC, 76 CHURCH STREET, LARKHALL, LANARKS.

Technical Books — Radio & Electronics

World's Radio & TV Stations (International Edit).....	£0.68
Audio Amplifiers	£0.70
Boys Book of Crystal Sets & Simple Circuits	£0.33
Television Timebase Circuits	£1.15
Radio TV and Industrial Tube & Valve Equiv	£0.68
How to get the best out of your Tape Recorder	£1.67
Modern Electronic Troubleshooting	£1.55
Jack Darr's Service Clinic	£1.55
Transistor Circuits for Modern Test Equipment.....	£0.68
Rad & Electr Colour Codes and Oata Chart.....	£0.20
Handbk of Transistor Equiv.and Substitutes.....	£0.48
Hi Fi, PA & Disco Amplifier Design Hndbk.....	£0.87
Radio Servicing Problems	£0.75
Electronic Circuits for the Amat Photographer.....	£0.68
Handbook of Simple Transistor Circuits	£0.40
TV Fault Finding	£1.10
Sound and Loudspeaker Manual	£0.60
TV Technicians Bench Manual	£2.80
Radio Amateur Operator's Handbook	£0.85
Towers International Transistor Selector.....	£3.30
Television Servicing Vol. No. 2.....	£1.27
Television Servicing Vol. No. 3.....	£0.75
Television Servicing Vol. No. 4.....	£1.00
Radio Technicians Bench Manual	£3.30
Servicing Transistor Radio Receivers.....	£0.90
1st Book of Hi Fi Loudspeaker Enclosures	£0.68
2nd Book of Hi Fi Loudspeaker Enclosures.....	£0.68
Manual of Electronic Circuits for the Home.....	£0.60
Modern Crystal Set Circuits for Beginners.....	£0.40
Electronic Novelities for the Motorist.....	£0.58
2nd Book of Transistor Equiv. & Substitutes.....	£1.07
Handbook of Electronic Musical Novelities.....	£0.58
Transistorised Novelities for Hi Fi Enthusiast.....	£0.40
Fault Location Exercises in Rad. & TV Vol.1.....	£0.95
Fault Location Exercises in Rad. & TV Vol.2.....	£1.55
Colour TV Picture Faults.....	£2.70
Practical Transistor Novelty Circuits	£0.48
Boys Book of Practical Radio & Electronics.....	£0.68
Radio Receiver Construction using ICs & Transis.....	£0.68
ICs & Transistor Gadgets Construction Handb'k.....	£0.68
Integrated Circuits Equiv. & Substitutes Hbk.....	£0.85
Audio Technicians Bench Manual	£3.30
Improving your Hi-Fi	£3.30
Guide to Printed Circuits	£2.80
Receiving Pal Colour Television	£5.35
World Radio TV Handbook 1975	£3.80

All prices include Postage & Packing

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

Agencies



RADIO ROTOR MAILING ORDERS B.V.

Main Office DEN DOLDER Marterin. 10
The Netherlands. Phone 30-762439

We are a Mail Order House and we are interested in hearing from suppliers and manufacturers of HOBBY-ELECTRONIC-EQUIPMENT, such as Electronic kits, Amateur Transceivers, Receivers etc.

Ladders

LADDERS, timber and aluminium.
Tel: Telford 586644 for brochure.

BOOKS

ON ELECTRONICS

Electronics £1-60

—An elementary introduction for beginners (SI Units). The eagerly awaited step by step explanation for those meeting with the subject for the first time.

Towers International

Transistor Selector

Just Published £3-30

Mullard Publications

Data Book 50p

Integrated Circuits 50p

Thyristors 60p

Magnetic Core

Memories 50p

Simple Transistor

Measurements 30p

Simple Valve

Measurements 30p

A Simple Closed Circuit

Television Camera 90p

(Prices include postage & packing)

SELRAY BOOK COMPANY

60, Hayes Hill,
Hayes, Bromley, BR2 7HP

Service Sheets

SERVICE SHEETS for Radio, TV, etc., 50p and SAE. Catalogue 20p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 20p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)
ALL AT 50p EACH

" PLEASE ENCLOSE LARGE S.A.E WITH ALL ENQUIRIES & ORDERS "

Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE
We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

BELL'S TELEVISION SERVICES for Service Sheets, Manuals, Books on Radios, TVs, etc. Service Sheets 50p plus SAE. Free booklists on request. Back issues of PW, PE, EE, TV available 25p plus 9p post. SAE with enquiries.—BTS (Mail Order Dept.), 190 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

Business Opportunities

Run your own hi-fi store

A unique opportunity to run your own hi-fi superstore and become the outright owner of a franchise that's the only one of its kind in Britain

Tandy Corporation (Branch UK), a division of The Tandy Corporation of America, where its 'Radio Shack' operation has over 2,000 retail outlets, arrived in Britain late in 1973 and has already opened 100 audio superstores in England. During 1975, the same fast rate of growth will be maintained and openings will commence in Scotland. Every major town and city will have at least one Tandy Store.

The product range consists of exclusive Tandy brands of radio, audio and communications equipment plus components, accessories and kits offering the highest possible quality at competitive prices.


This ensures high volume sales with substantial profits. Previous trade experience is not necessary. Tandy's 50 years experience assures realistic training of the Franchise and covers everything from your Grand Opening, to everyday routines, plus regular newspaper advertising, full merchandising and promotional support.

A minimum investment of £17,000 is required.

For further information please write in confidence to the Senior Vice President, Mr. Richard N. O'Brien.

TANDY

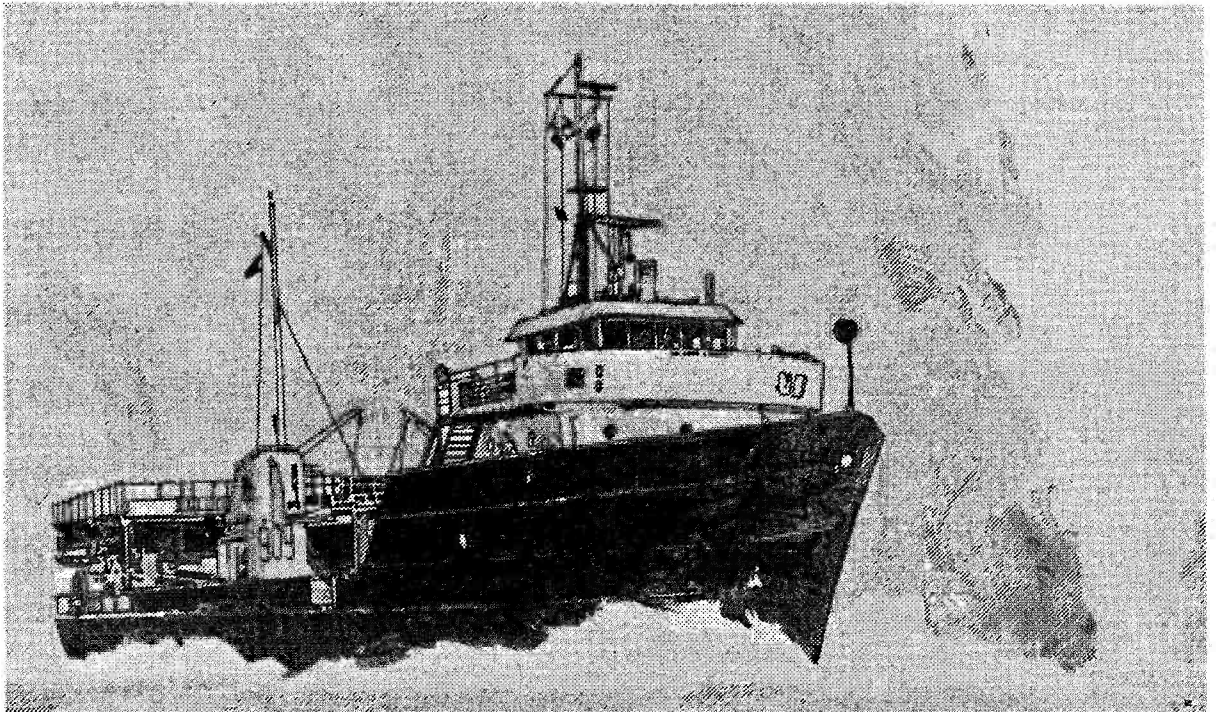Tandy Corporation (Branch UK)
Bilston Road, Wednesbury, WS10 7JN, Staffs.



Oil Exploration

G.S.I. Ltd, a subsidiary of Texas Instruments requires technicians with approximately four years experience in maintenance and repair of digital and analogue electronic equipment and qualified to ONC/HNC or City & Guilds (F.T.C.).

The openings available are in overseas marine seismic operations and are based on a 26 month contract with opportunities for home leave during this period.

The type of people we are looking

for are single men who want a career that involves travel, work on ship-board Texas Instruments navigation and seismic digital recording equipment but will still be prepared to get their hands dirty.

If you feel that you fit the qualifications listed and are looking for a job that is not "9 a.m. to 5 p.m." contact David Kennedy, Personnel Department, G.S.I. Ltd, Canterbury House, Sydenham Road, Croydon, Surrey. Tel: 01-686 6511, ext 257.

Geophysical Service International Ltd.

ELECTRONIC CRAFTSMEN

Is your present job routine and uninteresting ?

We are a research establishment and our craftsmen are engaged on a wide variety of work in the fields of prototype and small batch wiring and assembly, test and inspection, maintenance fault finding and repair. Why not join us and enjoy working in first class conditions in the country.

You can expect gross earnings including overtime of £45 per week, and we can offer good housing at low rental (for applicants who reside outside the radius of our Assisted Travel Area) together with 3 weeks paid holiday with holiday bonus, free pension and excellent sick benefit scheme.

Applicants who should have served a recognised apprenticeship or have had equivalent training together with experience in one of the fields detailed should phone Tadley 4111 (STD 073.56.4111) Ext. 5230, or write to:

**Industrial Recruitment Officer
(PA/78/PW) Procurement Executive
Ministry of Defence
AWRE Aldermaston
Reading, Berks
RG7 4PR**

**MEN!
£70p.w.
can be yours**

Jobs galore? Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay Prospects? £3500 + p.a.

London Computer Operators Training Centre subscribes to the British Government backed National Computing Centre code of practice for Computer Training Schools so you know your training will be second to none.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

**London Computer Operators
Training Centre**
Y23, Oxford Hse.,
9-15 Oxford St. W1. Tel: 01-734 2874

Educational

C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians Radio/TV/Electronics Technicians. Telecomms Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

**INTERNATIONAL
CORRESPONDENCE SCHOOLS,**
Dept 732, Intertext House, London SW8 4UJ.
Or Phone 01-822 9911 (All Hours)

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Miscellaneous

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 4 1/2 p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwicks., CV37 9NF.

PRINTED CIRCUIT manufacturer's offer, ready drilled PCBs for PW and PE projects published after June 1974, at one price 70p. E.g. Orion amp, telephone exchange. Also full sets for: Tele-tennis £3.50; PE CCTV £1.40p. Power slaves £1.35p. Scorpion ignition and Ferret locator 60p. CWO. Please add 15p per 40 sq in P&P. Production space available for PCB production, design, silk-screen printing, electroplating, tinning plus all graphic/art and photographic masters. Estimates by return post or phone. WKF Electronics, Welbeck Street, Whitwell, Worksop, Notts. Tel: Whitwell 695 (Derbys.).

SUPERB INSTRUMENT CASE by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronics and Hi-Fi enthusiasts are choosing the case they require from our range of over 200 models. Largest choice at highly competitive prices, why pay more. Fast despatch. Free literature, (stamp would be appreciated), Bazelli, Department No. 25, St. Wilfrids, Foundry Lane, Halton, Lancaster LA2 6LT.

**SIMPLE TO FORM
NON-MAGNETIC RUST PROOF
MILL FINISH**

ALUMINIUM

10ins. x 14ins. 20 swg (0.90mm.)
6 sheets for £2 incl P&P

OTHER SIZES AVAILABLE
**For general car repairs,
trims, kick plates, etc.**

**BAYKIN
ENGINEERING LTD.**

(Dept. PW)
GREVILLE ROAD, BEDMINSTER,
BRISTOL, BS3 1LL

PCBs, PCBs, PCBSS, PCBs, PCBs. Any PE, PW, EE, WW project PCB from January 1974, 75p each. Only top quality glass fibre boards supplied. Strip or perforated board layouts converted to true PCBs. SAE and sketch or schematic for quotation. Capacity for one-off or quantity production of PCBs. Design, artwork or assembly. Northpoint (Electronics) Ltd., Wellington Trading Estate, Ashton-U-Lyne, Lancashire. 24 hour phone-answering service on 061-339 4917.

12 VOLT 21" 13 Watt Fluorescent Lighting (by Thorn/AEI) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.

£5.50 inc. VAT & Post. List price £7.02 inc. VAT
SALOP ELECTRONICS 23 Wyle Cop,
Shrewsbury, Shropshire
Tel. 53266

LOWEST COST IC SOCKETS. Use Soldercon IC socket pins for 8 to 40 pin DIL's. Make 8 pin sockets for 4p, 14 pin for 7p (at 300 pin price). 70p for strip of 100 pins, £1.50 for 3 x 100. £4 for 1000. 10p p&p for orders under £2. Add 8% VAT. Instructions supplied—send sae for sample. SINTEL, 53a Aston Street, Oxford. Tel: 0865 43203.

Synthesiser "Sounds Supreme"

by Dewtron (VAT extra.)

Famous kits, e.g. waa-waa complete kit £3.50; Fuzz kit £5.50. P & P 25p under £10. Ring Modulator modules £9. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.


FANTASTIC NEW MICROTEST 80

MEASURES ONLY
90x70x18 mm



Amazing Value at **£11.95**
8 fields of measurement and 40 ranges

- Volts D.C. 6 ranges: 100mV - 2V - 10V - 50V - 200V - 1000V. (20k Ω/V)
- Volts A.C. 5 ranges: 1.5V - 10V - 50V - 250V - 1000V. (4k Ω/V)
- Amp. D.C. 6 ranges: 50μA - 500μA - 5mA - 50mA - 500mA - 5A
- Amp. A.C. 5 ranges: 250μA - 2.5mA - 25mA - 250mA - 2.5A
- Ohms 4 ranges: Low Ω - Ω x 10 - Ω x 100 (da 1/10 di Ω fino a 5 Mega Ω)
- V Output 5 ranges: 1.5V - 10V - 50V - 250V - 1000V
- Decibels 5 ranges: + 6dB, + 22dB, + 36dB, + 50dB, + 62dB
- Capacity 4 ranges: 25μF - 250μF - 2500μF - 25,000μF

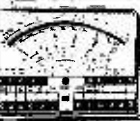

SUPRETESTER 680R I.C.
20,000 Ohm per Volt/sensitivity
Fully screened against external magnetic field
Scale width and small case dimensions (128 x 95 x 32mm)
Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading
Simplicity and ease of use and readability
Full range of accessories - 1000 times overload
Printed circuit board is removable without de-soldering
More ranges than any other tester
Ask for free catalogue **£18.50**

Accessories (extra) available to convert Microtest 80 & Supertester 680R into following: SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLTMETER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR—Send for details.

MORE RANGES FOR LESS MONEY!
AC/DC Multimeter type U4324
A-DC 0-0.05-3A - 6 Ranges.
A-AC 0-3-3A - 5 Ranges.
V-DC 0-6-1200V - 9 Ranges.
V-AC 3-900V - 8 Ranges.
Resistance: 500 Ohm to 5 MΩ
Freq.: In the range of 45 to 20kHz.
Accuracy: ± 2.5% DC, ± 4% AC
Dimensions: 167 x 98 x 63 mm.



ALPHANUMERIC NIXIE TUBES B7971
The Alpha-numeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube
From the standpoint of both readability and electrical characteristics, the Alpha-numeric NIXIE tube provides many unique benefits including ★ 170V-21mA ★ All d.c. operation ★ Uniform, continuous line characters of equal height ★ Memory with simple solid state drive circuits ★ Readability in high ambient light ... 200 footlamberts brightness ★ Long life with no loss of brightness ★ Character height 2 1/2 in.

Price only **99p** each plus 16p P/P.
Bases for above 60p each.

JUST ARRIVED!!
NUMERIC INDICATOR TUBES
Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V D.C. Current 14mA, Pulse duration 100μs. Character height 0-51, overall size 1.4.
Brand new, guaranteed. Surplus to manufacturers requirements. Type B5853st
1-25 £1.00 25+ 90p 100+ 80p
1000+ price on application
Add 8% VAT to all items + 35p P & P

ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

VALVES. New, boxed, and reclaimed types. S.A.E. for lists. Al Radio Components, 14 The Borough, Canterbury, Kent, CT1 2DR.

LOW COST I.C. MOUNTING. Lengths of 100 I.C. pin sockets, 60p (p & p 5p). Quantity rates, SAE details & sample. L.E.D. (MLED500), 20p each. (post paid). P.K.G. Electronics, "Oak Lodge", Tansley, Derbyshire.

BULK OFFERS
All goods full spec. and marked

1N4001	£2.50/100	1N4002	£2.80/100
1N4003	£3.20/100	1N4004	£3.60/100
1N4005	£4.30/100	1N4006	£4.70/100
1N4007	£5.00/100	1N914	£3.00/100
BC116A	£8.00/100	BC267	£6.00/100
741C	£19.00/100	NE555V	£39.00/100

400mW Zeners, most values £5/100
Assorted Computer Panels £25/cwt
Assorted small value caps—mica, ceramic etc. 228/10000
Ferric Chloride £30/100 1lb bags
Miniature Mains transformers, all 100mA Sec: 6-0-6V £5/10; 9-0-9V £5.50/10; 12-0-12 £6/10
1/2" ex-computer tape on 10 1/2" NAB spools £100/100
Veroboard Offcuts 10lb £22
Minimum order £5; Carr. Free.
Add VAT at appropriate rate.

JUNIPER ELECTRONICS (PW1)
PO BOX 61, SOUTHAMPTON

ANTIQUÉ WIRELESS ENTHUSIASTS!
For all your requirements in obsolete radio, contact "Tudor Rees." 1975 Full catalogue now available, 40p post paid. Antique Wireless Service, 64 Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. 0272 565472.

SINTEL
Add 10p P. & P. for orders under £2. Data, and circuits where appropriate supplied with orders, or available separately (send 9in x 4in S.A.E.) **ADD VAT at 8%.**

Economy DL704 0-3in LED 7 segment display
Only 95p
NSN33 0-12in 3 Digit LED readout—only 55p/digit £1.65
MAN 3M type 0-12in 7 segment display 40p
MK50250N Alarm Clock I.C. £5.60
P.C.B.s now available for clocks, drivers, displays (send 9in x 4in S.A.E.)
CT7001 + 4 DL704 only £10.80; CT7001 + 6 DL704 for £12.70
SOLDERCON I.C. Socket Pins 100 pins for 50p 300 pins for £1.50 (Instructions supplied) 1,000 pins for £4.00
Send S.A.E. for sample 3,000 pins for £10.50

SINTEL, 53N ASTON STREET, OXFORD.
Tel. (0865) 43203

P.W. CRATA F.M. TUNER. Set of five P.C. boards £3, p&p 20p. Other components available. S.A.E. for lists. Teleradio, 325 Fore Street, Edmonton, London N9 0PE.

P.W. EASY-BUILD ORGAN
Set of two P.C.B's £7.20
Set of thirteen MOS I.C.s £21.65
Set of all semiconductors £26.70
Set of all semiconductors plus the P.C.B's £32.00

P.W. TELE-TENNIS
SET OF SIX P.C.B's £7.50

All include P & P and V.A.T.
FORESIGHT ELECTRONICS
62 HIGH STREET,
CROYDON, SURREY

DIGITAL CLOCK CHIP, AY-5-1224, with data & circuit diagram, £3.66 + VAT. 'Jumbo' LED digits (16mm high), type DL-747, only £2.04 each + VAT, post free.—Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside. L62 5AG.

TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weights only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Complete £9.80 Built, tested and guaranteed £13.75
1 A.P. 50 33 V.A.T P & P 60p + £1.10 V.A.T

MINIKITS ELECTRONICS
4 CLEVELAND ROAD,
LONDON, E16 2AN (Mail order only)

VALVES, TRANSISTORS. Valves 1930 to 1975, 2,000 types in stock, many obsolete. List 15p. Transistor list 15p. Wanted valves and transistors all types. Dealers, wholesalers, etc. stock cleared. Must be new and boxed. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. West Wittering 2023.

MINI ACCUMULATORS
2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.
Size L450-1.4" x 1.1" x .44", 3 for £1.85 inc. P. & P.
Size A2, 1.7" x 1.3" x .5", 3 for £2.35 inc. P. & P.
GARFIELDS, 289 Rye Lane, London, S.E.15

AERIAL WIRE. High quality PVC covered multi-strand copper, 50ft 60p (10p); 75ft 87p (13p); 100ft £1.20 (15p); 150ft £1.80 (24p); 200ft £2.35 (26p); 250ft £2.96 (28p); 300ft £3.54 (31p). P & P in brackets. Longer lengths available. SAE all enquiries. Al Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

Aerials

GENUINE FULL SIZE 18 element TV aerial as used by leading TV companies

FOR ONLY **£2.20** + 59p carr

Save £5. We supply this genuine U.H.F. aerial for only £2.20, can be fitted outside or inside.
Quality made technically advanced design. Precision grid reflector eliminates ghosting.
Complete with clamp, instructions advice. Money Back Refund
Wall/Caravan Bracket 25p. Best Cable 12p per yard. Plug TOP & FREE with order maps & channel reference of Radio & TV Transmitters.
SEND DIRECT TO DEPT. PW10
219 Mansfield Rd. Nottingham.

IMPERIAL TRADING AERIALS LTD.
The quality aerial specialists

J. & A. TWEEDY (Electronic Supplies) LTD.
79 Chatsworth Road, Chesterfield, S40 2AP
We have in stock a good range of Jumbos TV and FM aerials. As well as these we have a good stock of accessories. A SAE will bring more details.
Multibeam: MBM 28 £5.00. MBM £8.00. MBM 70 £12.50. JBM 18 £4.00. Rotators AR 30 £27.00. AR 40 £32.00. CD 44 £64.00. Stereobeam: SBM2 £3.00. SBM 3 £4.00. SBM 4 £5.00. SBM 6 £8.95. NEW 9 element £19.00.
VAT included on all prices.
Masthead amplifiers £11.00. Setback £5.50. State group required on all aerials and amplifiers. Carriage is paid on all aerial orders but extra on accessories.

VALVE BARGAINS

Any 5 50p, 10 75p, 50 £3.30, 100 £6.40. Your choice from the following list:

ECC82, ECL80, EB91, EF80, EF183, EF184, PC86, PC88, PC97, PC900, PCC84, PCC89, PCC189, PCF80, PCF802, PCF805, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14.

Colour Valves 25p each
PL508 PL509, PY500/A

Press 4 Button UHF
Tuners £2.50.

AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.

B11—For Stereo and Standard VHF Radio

B12—For the older VHF Television, please state BBC1 and ITV Channels.

B45—For mon. or colour this covers the complete UHF band.

All Boosters are complete with Battery and take only minutes to fit.

Price £3.40 each

BARGAIN PACKS

All Components in the Bargain Packs are unused and marked.

Pack 1—Polyester (C280) Axial Leads Capacitors—250V/W & 400V/W, very good mixed selection from 0.01 UF to 2.2 UF. Price 100 £1, 1000 £8 (our choice).

Pack 2—Electrolytic Capacitors—complete mix selection from 1 UF to 1000 UF, and from 10V/W to 63V/W. Price 100 £1.50, 500 £6 (our choice).

Pack 3—Transistors—any 10 80p, any 100 £7 (your choice). AC128 - AC176 - BC113 - BC115 - BC135 - BC153 - BC171 - BC172.


Pack 4.—15 Mixed Plugs, mixed selection of co-ax, din 2-3-5 pins, jack standard—3.5mm-2.5mm. Price £1.

Prices include V.A.T. P. & P. under £1/10p, £1 to £3/15p, above £3/20p. Overseas at cost. Money back guarantee on all orders.

ELECTRONIC MAILORDER LTD., 62 BRIDGE ST., RAMSBOTTOM, BURY, LANCs. Tel. Rams. 3036.

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

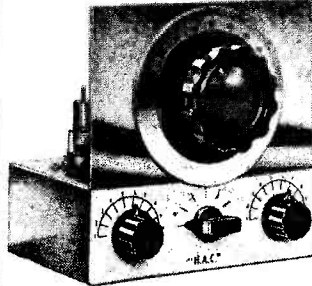

Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

1974 "DX" RECEIVER
Complete kit—Price £4.60 (incl. p. & V.A.T.). Customer writes: "Australia, India and America at loud volume."—"I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valver."

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue of kits and components.

Send stamped envelopes for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX No. 16, EAST GRINSTEAD,
SUSSEX RH19 3SN

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £
149	20	1 8	7.0 x 6.0 x 6.0	2.80 38
150	60	3 12	9.9 x 7.7 x 6.6	4.37 45
151	100	5 8	9.9 x 8.9 x 8.6	4.89 45
152	200	8 0	12.1 x 9.3 x 10.2	8.13 53
153	250	13 12	12.1 x 11.8 x 10.2	9.83 73
154	350	15 0	14.0 x 10.8 x 11.8	11.88 73
155	500	19 8	14.0 x 13.4 x 11.8	13.65 91
156	750	29 0	17.2 x 14.0 x 14.0	20.51 *
157	1000	38 0	17.2 x 16.6 x 14.0	29.15 *
158	1500	46 0	21.6 x 13.4 x 18.1	33.23 *
	2000	60 0	21.6 x 15.3 x 18.1	37.07 *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.67 30
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.90 38
4	150	4 8	8.9 x 7.7 x 7.7	0-115-200-220-240	4.12 45
66	300	6 4	9.9 x 9.6 x 8.6	"	5.82 53
67	500	12 8	12.1 x 11.2 x 10.2	"	8.82 67
84	1000	19 8	14.0 x 13.4 x 14.3	"	13.68 91
93	1500	30 4	14.0 x 15.9 x 14.3	"	18.31 *
95	2000	32 0	17.2 x 16.6 x 14.0	"	24.20 *
73	3000	40 0	17.2 x 13.4 x 18.1	"	35.09 *

CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2-pin outlets. 20VA £3.23 pp 38p
500VA £10.45 pp 80p 1000VA £17.51 via B.R.S.

TRANSFORMERS

Ref. No.	Primary Amps	Weight lb oz	Size cm.	Secondary Windings	P & P £
111	0.5-0.25	1 4	8.8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.47 23
213	1.0-0.5	1 4	6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	1.74 30
71	2 1	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x 2	2.29 38
18	4 2	2 12	8.0 x 7.7 x 7.0	0-12V at 2A x 2	2.86 38
70	6 3	3 8	8.9 x 9.0 x 8.6	0-12V at 3A x 2	4.12 45
108	8 4	5 8	9.9 x 8.9 x 8.6	0-12V at 4A x 2	4.56 45
72	10 5	6 4	9.9 x 9.6 x 8.6	0-12V at 5A x 2	5.14 53
116	12 6	6 12	9.9 x 10.2 x 8.6	0-12V at 5A x 2	5.52 53
17	16 8	8 12	12.1 x 9.9 x 10.2	0-12V at 8A x 2	7.28 60
115	20 10	11 8	14.0 x 9.6 x 11.8	0-12V at 10A x 2	10.39 73
187	30 15	15 8	14.0 x 12.1 x 14.0	0-12V at 15A x 2	13.59 85
226	60 30	32 0	17.2 x 15.3 x 14.0	0-12V at 30A x 2	16.83 *

30 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.81 30
79	1.0	2 4	7.0 x 6.7 x 6.1	"	2.40 38
3	2.0	3 4	8.9 x 7.7 x 7.7	"	3.49 38
20	3.0	4 8	9.9 x 8.3 x 8.6	"	4.53 45
21	4.0	6 4	9.9 x 8.6 x 8.6	"	5.13 53
51	5.0	6 12	12.1 x 8.6 x 10.2	"	6.41 53
117	6.0	8 0	12.1 x 9.3 x 10.2	"	7.16 60
88	8.0	12 0	12.1 x 11.8 x 11.8	"	9.90 67
89	10.0	13 12	14.0 x 10.2 x 10.2	"	9.87 73

50 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.58 30
103	1.0	2 12	8.3 x 7.4 x 7.0	"	3.38 38
104	2.0	5 8	9.9 x 8.9 x 8.6	"	4.68 45
105	3.0	6 12	9.9 x 10.2 x 8.6	"	5.81 53
106	4.0	10 0	12.1 x 10.5 x 10.2	"	7.60 67
107	6.0	12 0	14.0 x 11.8	"	12.10 67
118	8.0	18 0	14.0 x 12.7 x 11.8	"	12.98 85
119	10.0	25 0	17.2 x 12.7 x 14.0	"	16.99 *

60 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60	2.33 38
125	1.0	3 4	8.3 x 7.7 x 7.7	"	3.08 38
127	2.0	6 4	9.9 x 9.6 x 8.6	"	5.08 45
125	3.0	8 12	12.1 x 9.9 x 10.2	"	7.52 60
123	4.0	13 12	12.1 x 11.8 x 10.2	"	8.75 67
40	5.0	12 00	14.0 x 10.2 x 11.8	"	9.75 73
120	6.0	15 8	14.0 x 12.1 x 11.8	"	11.30 85
121	8.0	25 00	14.0 x 14.7 x 11.8	"	15.00 *
122	10.0	25 00	17.2 x 12.7 x 14.0	"	17.52 *
189	12.0	29 00	17.2 x 14.0 x 14.0	"	19.98 *

MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref. No.	MA	Weight lb oz	Size cm	VOLTS	P & P £
238	200	2	2.8x2.6x2.0	3-0-3	1.54 10
212	1A IA	1 4	6.1x5.8x4.8	0-6-0-6	1.84 30
13	100	4	3.9x2.6x2.9	9-0-9	1.41 13
235	330,330	2	4.8x2.9x3.5	0-9-0-9	1.56 19
207	500,500	1 00	6.1x5.4x4.8	0-8-9, 0-8-9	1.92 30
208	1A, 1A	1 12	7.0x6.4x6.1	0-8-9, 0-8-9	3.30 38
236	200,200	4	4.8x2.9x3.5	0-15-0-15	1.43 19
214	300,300	1 4	6.1x5.8x4.8	0-20, 0-20	1.93 30
221	700 (D.C.)	1 8	7.0x6.1x6.1	20-12-0-12-20	2.17 38
206	1A, 1A	2 12	8.3x7.7x7.0	0-15-7, 0-15-20	3.46 38
203	500,500	2 4	8.3x7.7x7.0	0-15-27, 0-15-27	3.00 38
204	1A, 1A	3 4	8.9x7.7x7.7	0-15-27, 0-15-27	3.85 38

* Carriage via BRS

PLEASE ADD 8% FOR V.A.T.
INCLUDING P. & P.

BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS. ALDGATE & LIVERPOOL ST.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER. CALLERS SATURDAYS ONLY

Send 15p postage for our comprehensive catalogue

TRANSISTORS (less 10% for 25+ of one type)			
AC125 13p	BC149C 8p	BF180 33p	OC81 15p
AC126 11p	BC154 18p	BF181 33p	OC82 15p
AC127 11p	BC157 13p	BF184 22p	OC83 20p
AC128 11p	BC158 11p	BF185 22p	OC140 100p
AC176 12p	BC159 13p	BF194 10p	OC202 70p
AC180 12p	BC167 12p	BF195 10p	OC202 70p
AC183 12p	BC168 12p	BF196 12p	OC202 70p
AC197 35p	BC169 12p	BF197 15p	OC202 70p
AC199 25p	BC170 11p	BF257 32p	OC202 70p
AC200 24p	BC171 11p	BF595 18p	OC202 70p
AC201 23p	BC172 11p	BF896 21p	OC202 70p
AC202 16p	BC177 16p	BF898 22p	OC202 70p
AD140 48p	BC178 16p	BFY50 15p	OC202 70p
AD143 48p	BC179 18p	BFY51 15p	OC202 70p
AD161 38p	BC182 16p	BFY52 15p	OC202 70p
AD162 38p	BC183 10p	BFY53 17p	OC202 70p
AF114 33p	BC184 11p	BSX20 16p	OC202 70p
AF115 33p	BC212 12p	BU105 42p	OC202 70p
AF116 18p	BC213 12p	TIS44 17p	OC202 70p
AF117 13p	BC214 17p	MJE371 78p	OC202 70p
AF118 40p	BCY42 28p	MJE520 62p	OC202 70p
AF121 33p	BCY43 25p	MPP102 30p	OC202 70p
AF124 30p	BCY58 18p	MPP103 30p	OC202 70p
AF125 30p	BCY59 18p	MPP104 30p	OC202 70p
AF126 30p	BCY70 15p	MPP105 30p	OC202 70p
AF127 30p	BCY71 15p	OC26 40p	OC202 70p
AF139 33p	BCY72 12p	OC28 48p	OC202 70p
AF181 45p	BD131 40p	OC35 48p	OC202 70p
AF186 48p	BD132 40p	OC36 52p	OC202 70p
AF239 38p	BD137 40p	OC41 15p	OC202 70p
BC107 10p	BD145 58p	MF42 30p	OC202 70p
BC108 10p	BDY60 75p	OC44 11p	OC202 70p
BC108B 12p	BDY61 65p	OC45 11p	OC202 70p
BC109 10p	BF115 22p	OC70 11p	OC202 70p
BC109C 12p	BF177 28p	OC71 11p	OC202 70p
BC147 8p	BF178 28p	OC72 11p	OC202 70p
BC148 8p	BF179 33p	OC74 22p	OC202 70p

DIGITAL ICs			
7400 14p	7428 38p	7473 33p	74121 32p
7401 14p	7430 15p	7474 32p	74123 63p
7402 15p	7432 25p	7475 47p	74141 75p
7403 15p	7433 36p	7476 32p	74151 69p
7404 18p	7437 27p	7480 44p	74153 69p
7405 18p	7438 27p	7481 99p	74155 69p
7406 38p	7440 59p	7482 75p	74156 70p
7407 38p	7441 75p	7483 83p	74160 101p
7408 15p	7442 65p	7484 90p	74166 143p
7409 15p	7443 120p	7485 125p	74167 315p
7410 15p	7444 105p	7489 334p	74170 215p
7411 20p	7445 89p	7490 47p	74172 540p
7412 20p	7446 105p	7491 80p	74176 103p
7413 35p	7447 100p	7492 48p	74180 106p
7414 60p	7448 86p	7493 47p	74184 160p
7416 35p	7450 15p	7495 63p	74185 169p
7417 35p	7451 15p	7496 72p	74190 160p
7420 15p	7453 15p	74100 135p	74191 160p
7422 24p	7454 15p	74104 40p	74192 128p
7423 27p	7460 15p	74105 40p	74193 128p
7425 27p	7470 30p	74107 33p	74198 210p
7426 27p	7472 26p	74110 33p	74199 210p

LINEAR IC'S (less 5% 50+ mixed)	BRIDGE RECTIFIER	SCR (Thyristor)	DIL SOCKETS
709C 28p	LM380 100p	1A 50V 38p	8 pin 14p
723C 55p	LM381 185p	1A 100V 42p	14 pin 14p
741C 28p	MC1303L 130p	1A 600V 21p	16 pin 15p
747C 80p	MC1304P 360p	1A 600V 25p	24 pin 75p
748C 80p	MC1310P 240p	1A 600V 70p	
7805 (T03) 160p	MC1710CG 55p	2A 50V 30p	
AY-1 202 5-50p	MFC4000B 54p	2A 100V 35p	
AY-1 5051 1-15p	MLM309K 158p	2A 200V 40p	
CA3018 72p	MVR12 170p	2A 400V 44p	
CA3035 135p	NE555 55p	2A 600V 45p	
CA3036 90p	NE562 310p	4A 800V 90p	
CA3046 55p	PA263 195p	6A 100V 58p	
CA3048 220p	SL403D 150p		
CA3075 150p	SL414A 250p		
CA3081 150p	SN7603 150p		
CA3089E 210p	SN7615 250p		
CA3090Q 310p	TAD100 140p		
LM300 170p	TB140 130p		
	TBA810 150p		
	ZN414 110p		

FUSES AND HOLDERS	SPEAKERS	ENAMEL COPPER WIRE (2oz reel)	FERRITE RODS: 3/8" diam.
20mm 150mA-5A 4p	8Ω 3" 0-5W 68p	16, 18, 20, 22 SWG 32p P & P	2" - 8p; 3 1/2" - 15p; 6 1/2" - 18p
1" 2A-13A mains 3p		24, 26, 28, 30 SWG 39p 5p per reel	
1 1/2" 250mA-15A 3p		32, 34, 36, 40 SWG 48p	
Panel Holder Single 6p			
Chassis Holder 20mm 16p			
Chassis Holder 1 1/2" 22p			

OPTO ELECTRONICS	EARPHONES	THERMISTORS 15p each
Minitrons 3105F ORP61 46p	With Cord and Jack Plug Magnetic 2-5 mm plug 15p	VA 1034; VA 1040; VA 1055; VA 1066;
7 seg display 110p	3-5 mm plug 28p	VA 1068; VA 1069; VA 1077;
OCPT70 40p	Crystal 15p	VA 1098; VA 1100,
OCPT71 85p	3-5 mm plug 28p	
ORP12 58p		

AIRCRAFT BAND CONVERTOR Mod. VHF 105
Enjoy listening to Aircraft band by merely placing it beside a radio.
Price: £4.75 p & p 15p.

ALL DEVICES BRAND NEW AND FULLY GUARANTEED.
ORDERS DESPATCHED BY RETURN OF POST. TERMS
OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS
DRAFT WITH ORDER. GOVERNMENT AND
EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS
ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME.
P & P ADD 20p TO ORDERS UNDER £5.00. OVERSEAS
ORDERS POSTAGE AT COST, AIR/SURFACE.
PRICES EXCLUSIVE OF VAT.

POLYESTER CAPACITORS: Axial lead type. (Values are in μF).
400V: 0.001, 0.0012, 0.0015, 0.0018, 0.0022, 0.0033, 0.0047, 0.01 3p; 0.015,
0.022, 0.033, 0.047, 0.068, 0.1 4p; 0.15, 0.22, 7p; 0.33, 10p; 0.47, 13p; 180V: 0.1, 0.15,
0.22, 0.33, 0.47, 0.68, 1.0 4p; 0.68 10p; 1.0 13p. 250V: 0.22 6p; 0.33 8p; 0.47 9p; 0.68 12p; 1.0 15p.

RADIAL LEAD P.C. TYPE (Values are in μF).
250V: 0.01, 0.015, 0.022, 3p; 0.033, 0.047, 0.068, 3p; 0.1 4p; 0.15 4p; 0.22, 0.33 5p;
0.47 7p; 0.68 10p; 1.0 11p; 1.5 20p; 2.2 22p.

ELECTROLYTIC CAPACITORS. Axial lead type (Values are in μF)
63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 5.6, 6.8, 10, 15, 20, 22, 47, 68, 6p, 100, 12p, 40V 100, 6p
50V: 1000, 42p, 30V: 3500, 41p, 2.5V: 10, 65, 150, 2p; 220, 11p; 470, 13p; 680, 18p;
1000, 24p; 2200, 34p; 3000, 39p; 4700, 47p. 16V: 1.0, 125, 250, 6p. 16V: 1000, 1500, 16p.
10V: 4, 100, 5p; 540, 10p; 1000, 14p; 2200, 18p.

POTENTIOMETERS (AB) Carbon
Track, 0-25W Log & 0-5W Linear values
1KΩ-2MΩ single gang 14p
5KΩ-2MΩ single gang D/P switch 32p
2KΩ-2MΩ dual gang stereo 45p

TANTALUM BEAD CAPACITORS
25V: 0.1μF, 0.2, 0.47, 1.0, 2.2, 4.7, 6.8
30V: 0.1μF, 0.2, 0.47, 1.0, 2.2, 4.7
35V: 10μF; 16V: 22μF; 10V: 33μF, 22μF.
6V: 33μF, 47μF; 3V: 47μF, 100μF.
Price: 10p each.

SLIDER POTENTIOMETERS
0-25W Log and linear values
5KΩ-500KΩ single gang 35p
10KΩ-500KΩ ohm Dual gang 50p

MYLAR FILM CAPACITORS
0.01μF, 0.002, 0.005, 0.01μF 3p
0.015, 0.02, 0.04, 0.05μF 4p
0.15, 0.250V: 0.47μF 6p

PRESET POTENTIOMETERS
0-1W 50Ω-1MΩ Vertical only 5p
0.25W 10Ω-2MΩ Horizontal 6p
0.25W 1KΩ-2MΩ Vertical 6p

CERAMIC CAPACITORS
50V d.c. Plaquette body 25mm leads.
Range: 5p-10,000pf 2p
0.015μf, 0.022μf, 0.033μf, 0.047μf 3p

QUALITY RESISTORS. ERIE MAKE	PRICE	JACKSONS DIELECTRIC TUNING CAPACITORS
Small Size, High Stability, Low Noise		
Type Pwr Tol. Range Val. 1-99 100-499 500+		
Carbon 1W 5% 2-2Ω-10M E24 1p		100pf 80p
Carbon 1/2W 5% 2-2Ω-10M E12 1p		0.7p 8p
Carbon 1W 5% 2-2Ω-10M E12 2.5p		2p —
WW 4W 10% 2-2Ω-100Ω E12 8p		300pf 80p
Quantity price applies to resistors of each value not mixed.		500pf 95p

JACK PLUGS	SOCKETS	PANEL METERS
2.5mm Screened chrome 10p	Plastic body 8p	60mm x 46mm x 35mm requires 1 1/2" hole
3.5mm 14p	Open metal 8p	FULL SCALE
Standard Mono 17p	Moulded with break contacts 17p	ME 6 0-50μA
Standard Stereo 30p		ME 7 0-100μA
		ME 8 0-500μA
		ME 9 0-1mA
		ME 10 0-5mA
		ME 11 0-10mA
		ME 12 0-50mA
		ME 13 0-100mA
		ME 14 0-500mA
		ME 15 0-1 amp
		ME 16 0-50V AC
		ME 17 0-300V AC
		ME 19 "VU" Meter
		Price £2.65, p & p 10p

DIN 2PIN LOUDSPEAKER	Plugs	Sockets	Couplers
TYPE 3, 4, 5 (180° & 240°) 6PIN	12p	8p	15p

CO-AXIAL (TV)	10p	8p	15p (f.f.)
PHONO assorted colours	8p	7p (sgl.) 5p (dbl.) 10p (trpl.)	9p

BANANA	7p	7p	—
SWITCHES			
TOGGLE: SPST 18p			
DPDT 22p			
PUSH BUTTON: Miniature push to make or break non locking 15p			
ROCKER (white): 10A 250V S P changeover centre off. 25p			
ROCKER: Illuminated (white) incorporates neon, lights when on 3A 240V 45p			
SLIDE: 1A DP 250V 10p			
1A DP 250V C/O 12p			
1A DP 250V 9p			
ROTARY SWITCH: 1 pole/12way 2p/6w, 2p/2w, 2p/4w, 3p/3w 3p/4w, 4p/2w, 4p/3w			

TRANSFORMERS MAINS	LAMP HOLDERS AND LAMPS
Primary 220-240V	L5S HOLDER Dome shaped, Red, Blue, Green, Yellow, White 14p
6-0-6 (miniature) 100mA 90p	LES BULBS 6v and 12v 6p
9-0-9 (miniature) 100mA 90p	MES HOLDERS Chrome cover, Red or Amber, Jewelled top 28p
12-0-12 (miniature) 100mA 90p	MES BULBS 3-5V 6V and 24V 6p
24-0-24V 500mA 220p	NEON: RED round top 250V 21p
30-24-20-15-12-0 2A 340p	NEON: 1/2" square top, red, green, Req. 1/2" hole 21p
Pulse Transformer PT ATA 85p	

VEROBOARD	KNOB (fits 1/4" shaft, with grub screw except K2 and K8)
0-1 (copper clad) 14p	K1 Black or white pointer type 10p
0-15 (plain) 23p	K2 Slim silvered aluminium 10p
2 1/2x3 1/2" 32p	K3 Black 1 1/2" with chrome rim 15p
2 1/2x5" 32p	K4 Black serrated. Metal top with line indicator 33m diam. 18p
3 1/2x3 1/2" 32p	K5 Black fluted metal top and skirt calibrated 0-10. 37mm dia. 20p
3 1/2x5" 38p	K6 PK2 as K5 with pointer on skirt top 20p
2 1/2x1 1/2" 96p	K7 Black, knurled, tapered. Metal top & skirt. Calif. 0-10, 30mm top 20p
3 1/2x1 1/2" 130p	K8 Black or silvered for slider pot 9p
4 1/2x1 1/2" 173p	
Pkt of 36 pins 22p	
Spot face cutter 48p	
Pin insertion tool 59p	

And now the FANE 'SPECIALIST' RANGE

L'SPEAKERS OF OUTSTANDING QUALITY FOR THE DISCRIMINATING PROFESSIONAL

Features include ROBUST CAST ALUMINIUM CHASSIS and 2" EXTRA HIGH POWER VOICE COILS

All models available in impedances of 8 ohm or 15 ohm

Recommended Prices inc. VAT

Guarantee: 2 years



Illust.
12"
'DISCO 60'

12" 'DISCO 60' 60 watts R.M.S.

Linen Cone Surround. Fitted extra large Tweeter Cone. Frequency Range 50-15,000 Hz

£24.75

Rec. Retail Price

12" 'GUITAR 60L' 60 watts R.M.S.

Plastiflex Cone Surround. Aluminium Centre Dome. Frequency Range 50-9,000 Hz.

£23.50

Rec. Retail Price

DESIGNED FOR LEAD GUITAR

12" 'GUITAR 60B' 60 watts R.M.S.

Linen Cone Surround. Frequency Range 45-9,000 Hz.

£23.95

Rec. Retail Price

FOR USE IN MULTIPLES FOR BASS GUITAR

12" 'PA 60' 60 watts R.M.S.

Plastiflex Cone Surround. Fitted Tweeter Cone. Frequency Range 50-15,000 Hz.

£23.50

FOR GENERAL PURPOSE PUBLIC ADDRESS

15" 'BASS 70' 70 watts R.M.S.

Linen Cone Surround. Frequency Range 40-7,000 Hz. Can be used singly but ideally TWO UNITS IN A SINGLE CABINET.

£35.75

Rec. Retail Price

RECOMMENDED FOR ALL BASS INSTRUMENTS

HIGH FREQUENCY HORN UNITS

MODEL 910

Rating 50 watts with recommended filter inc. VAT

£15.95

MODEL 920 Mk II (as illust)

SIGNIFICANTLY INCREASED SENSITIVITY. UNCHANGED PRICE.

Rating with recommended filter 100 watts. Price inc. VAT **£39.95**

HPXI HIGH POWER CROSS-OVER UNIT Suitable for above Horn Units **£2.50** inc. VAT.



OUR FAST SELLING and RELIABLE

'POP' RANGE

IS STILL AVAILABLE AT REC. PRICES from

£6.30

AND for those who can afford the very best there is our range of

'CRESCENDO'

MODELS

12" UNITS

£39.95

from

Rec. Retail

15" UNITS

£46.95

from

Rec. Retail



Please send S.A.E. for leaflets on any of above ranges

Distributors to Wholesale and Retail Traders—**LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS**
Manufacturers enquiries to—**FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS**
Prices shown correct at 3 Mar, 1975

INDEX TO ADVERTISERS

Allard Electronics ... 4
Ambit International ... 47
Amtron Electronics ... 32
A.S.P. Ltd. ... 71
Astro Electronics Ltd. ... 88
A.W.R.E. (Ministry of Defence) ... 83

Barrie Electronics ... 85
Baykin Engineering Ltd. ... 83
Ben Ford Cabinets Ltd. ... 64
Bentley Acoustics Ltd. ... 16
Beta Devices ... 80
B. H. Components Factors Ltd. ... 32
Bi-Pak Semiconductors ... 12-13
Bi-Pre-Pak Ltd. ... 77
Bib Hi-Fi Accessories Ltd. ... 10
Bothwell Electric Supplies ... 78
British Institute of Engineering Technology
68, 76, Cover iii
British National Radio & Electronics
School ... 35, 64, 72
J. Bull (Electrical) Ltd. ... 17
Bush & Meissner ... 16

C. Caranna ... 81
Chromasonic Electronics ... 74-75
C.J.L. Ltd. ... 72
Codar ... 40
Colomor (Electronics) Ltd. ... 64
Crescent Radio Ltd. ... 79

D.E.W. Ltd. ... 83

Electronic Brokers ... 84
Electronic Design Associates ... 59
Electronic Mail Order Ltd. ... 85
Electronic Supplies Co. ... 60
Electroni-Kit ... 71

Electrospares ... 8
Electrovalue Ltd. ... 4
Everest Instruments Ltd. ... 60

Felstead Electronics ... 71
Flairline Supplies ... 59
Foresight Electronics ... 84
Forward Marketing ... 78

Garfields ... 84
Geophysical Service International
Goldring Ltd. ... 82
Greenweld Electronics ... 14

H.A.C. (Shortwave) Products ... 85
Harversons Surplus Co. Ltd. ... 63
Heath (Gloucester) Ltd. ... 68
Henry's Radio Ltd. ... cover iv
Home Radio Ltd. ... 39

Imperial Trading ... 84
Intertext (I.C.S.) ... 83

Jones, J.C. ... 59
Juniper Electronics ... 84

Kensington Supplies ... 80
Keytronics ... 16

Lasky's ... 5-6-7
Lewis Radio ... 76
Light Soldering Developments Ltd. ... 4
Linear Products Ltd. ... 87
London Computer Operators Training
Centre ... 83
Lowe Electronics ... 72

Maplin Electronic Supplies ... 11
Marco Trading ... 80

Marshall, A. & Son ... 78
Minikits Electronics ... 84

Newmart Electronics ... 15
Newnes Butterworth ... 40

Partridge Electronics Ltd. ... 76
Pembroke College of Electronics ... 14

Radio Book Services ... 81
Radio Component Specialists ... 73
Radio Exchange Ltd. ... cover ii
Radio Rotar ... 81
R.S.C. (Hi-Fi) Centre Ltd. ... 2-3
R.S.T. Valve Mail Order Co. ... 9
R & TV Components Ltd. ... 18-19
Riversdale Electronics ... 8

Salop Electronics ... 83
Saxon Entertainments Ltd. ... 67
Selray Book Co. ... 81
Sinclair Radionics Ltd. ... 31
Simtech Engineering Ltd. ... 80
Sintel ... 84
Sound Systems of Suffolk ... 80
Studio Electronics ... 88
Suplectronics ... 60
Surplus Electronic Trading ... 16
Swanley Electronics ... 36

Tandy Corporation ... 81
Technomatic Ltd. ... 88
Trampus Electronics Ltd. ... 14
TV Technic Publications ... 81
Tweedy (J. & A.) ... 84

Watford Electronics ... 86
Web Europa 32 ... 32
West London Direct Supplies ... 60
Wilmslow Audio ... 36

Z & I Aero Services ... 88


Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

AC/DC MULTIMETERS

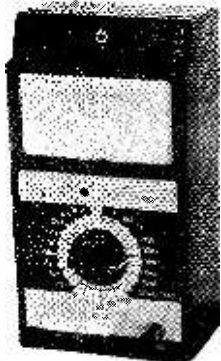

TYPE U4313

39 ranges:
600 μ A to 1.5A A.C.,
60 μ A to 1.5A D.C.,
1.5V to 600V A.C.,
75mV to 600V D.C.,
Resistance up to 1M Ω
Capacity up to 0.5 μ F
Level up to 12db

Accuracy: 1.5% D.C.,
2.5% A.C.

Sensitivity: 20k Ω /V D.C.,
2k Ω /V A.C.

Mirror scale: 86mm long
Dimensions: 115 x 215 x
90mm

PRICE, incl. steel carrying
case, leads and manual
£13.80*

TYPE U4315

42 ranges:
500 μ A to 2.5A A.C.,
50 μ A to 2.5A D.C.,
1V to 1000V A.C.,
75mV to 1000V D.C.,
Resistance up to 1M Ω
Capacity up to 0.03 μ F
Level up to +2db.

Accuracy: 2.5% D.C.,
4% A.C.

Sensitivity: 20k Ω /V D.C.,
2k Ω /V A.C.

Plain scale: 86mm long
Dimensions: 115 x 215 x
90mm.

PRICE, incl. steel carrying
case, leads and manual
£10.00*

LINEAR INTEGRATED CIRCUITS

— Please note reductions in prices —

Mullard TAA263. Direct coupled three stage low level amplifier for use from DC to 600 kc/s. Supply voltage 6-8v. Typical power gain 77 db into 150 Ω load. Output power 10mW. TO72 four-lead encapsulation **£0.65***

Mullard TAA293. Medium frequency amplifier with frequency response of 600kc/s. Nominal supply voltage 6v. Typical power gain 89db. Maximum power dissipation 160 mW. Power output 10 mW. into 150 Ω load. TO74 ten lead-encapsulation **£0.65***

Mullard TAA320. Metal oxide silicon low frequency pre-amplifier consisting of a MOST stage followed by a bi-polar transistor. Gate to source voltage 9-14v. Total power dissipation 200 mW. Drain current 1 μ A. Output conductance 0.65 mho. TO18 3-lead encapsulation **£0.60***

Type 741 Operational Amplifiers, 8-dual-in-line encapsulation **£0.30***

L.E.D. TYPE HP5082/4850

Red Light GASP Light Emitting Diodes giving bright diffused light of 0.8 mcd at forward voltage of 1.6V and DC current of 20 mA. Plastic wide angle lens 0.200; diameter. Ideal for panel lights, etc. Price for 12 pieces **£1.75** incl. VAT and p.&p.

OUR NEW 1975 ILLUSTRATED CATALOGUE/PRICE LIST covering VALVES, TUBES, SEMICONDUCTORS, PASSIVE COMPONENTS AND TEST EQUIPMENT IS NOW READY. PLEASE SEND **£0.20** FOR YOUR COPY.

* ALL PRICES EXCLUSIVE OF V.A.T. WHEN REMITTING CASH WITH ORDER PLEASE ADD **£0.50** PER MULTIMETER AND **£0.15** IN **£** FOR OTHER ITEMS—SUBJECT TO A MINIMUM CHARGE OF **£0.20**—TO COVER HANDLING AND POSTAGE. NO C.O.D. ORDERS ACCEPTED.

TECHNOMATIC LTD. 54 SANDHURST ROAD, LONDON NW9

Tel: 01-204 4333

AC126/7/8 11p	2N8645 36p	DIODES	SCR-THYRISTORS
AC176 11p	2N1226 8p	1N4001 5p	1A/50V 40p
AC187/8 11p	2N3053 18p	1N4007 7p	1A/400V 54p
AD161/2 36p	2N3055 40p	1N4148 4p	3A/400V 75p
AF114/5/7 12p	2N3442 140p	Q.A.202 6p	C106D 31p
BC107/8 11p	2N3702/3/4 11p	AEY11 50p	2N3525 31p
BC109 11p	2N3705/6 19p	TIL209 16p	TRIAC
BC109C 10p	2N3773 220p	ZENERS	3A/400V 95p
BC154 12p	2N3819 20p	400mW 9p	6A/400V 120p
BC182/3 10p	3N128 75p	1.3V 18p	16A/500V 180p
BC184 11p	3N140/1 85p	1.5W 27p	DIAC
BC187 18p	40361 40p	BR. RECT.	1A/50V 22p
BC212/3 11p	40362 45p	1A/600V 29p	2A/100V 35p
BC214 11p	40603 53p	2A/400V 45p	2A/400V 45p
BCY71 18p	40673 53p	6A/100V 60p	DIL SOCKETS (Low Profile Texas)
BFY50/1/2 11p	SCR		8 Pin 12p
MPF103/5 30p	MCR101 25p		14 Pin 13p
TIP41A 63p	12A/50V 122p		16 Pin 14p
TIP42A 70p			

TTL SERIES	Linear IC's	1 AMP REG	MC1314	CMOS LOGIC
7400 13p	7473 34p	5V, 12V, 15V 140p	360p	Gates (CD4001AE, CD4011AE etc) 23p
7401/214p	7474 34p	CA3046 50p	430p	CD4013AE 55p
7404 18p	7475 45p	ICL8038	50p	CD4016AE 70p
7408 16p	7476 34p	LM380 90p	275p	CD4017AE 183p
7410 14p	7486 41p	LM390 70p	80p	CD4027AE 95p
7413 35p	7489 340p	MC1310	100p	CD4029AE 196p
7420 14p	7490 41p	DIL 8 or 14	210p	CD4024AE 136p
7430 14p	7491 82p		210p	CD4030AE 75p
7441 70p	7492 52p		210p	CD4046AE 220p
7442 50p	7493 41p		210p	CD4047AE 154p
7447 85p	74107 45p		210p	CD4018AE 227p
7448 80p	74121 34p		210p	
7472 27p	74141 75p		210p	

SPECIAL OFFERS

555 TIMER 50p
723 Vol. Reg. 45p
741 Op. Amp 23p
TIL209 LED 16p

5001 12 Digit Calculator Chip 485p
5314 Clock chip 650p
Clock chip with Alarm (Similar MMS316) 750p
PC Keyboard 4" x 3" 76" x 0.45" 400p

FOR MORE SELECTION REFER TO OUR ADVERTS IN P.E. OR W.W.

Complete semiconductor kit for PW ASCOT STEREO CASSETTE DECK **£5.70 + VAT.**

MAIL ORDER ONLY
MINIMUM ORDER **£2.**

P & P 15p.
Add 8% VAT on total.

SEND NOW!

YOUR SINGLE SOURCE FOR
THE EASY-BUILD ORGAN
Studio Electronics

LTD

PO BOX 18 HARLOW CM18 6SH ESSEX

Tel: HARLOW (STD 0279) 416771

New catalogue now available on receipt of S.A.E.

INVERTERS

240v—50Hz. from your 12v car battery.
25 watt—£3.90 + 30p p & p.
40 watt—£6.80 + 55p p & p.
75 watt—£9.96 + 75p p & p.
150 watt—£18.30 + 80p p & p.
300 watt (12v)—£28.80 + £1.05 p & p.
300 watt (24v)—£22.70 + £1.05 p & p.
All above inverters are in kit form but may be purchased built up & ready for use. Price list sent on receipt of stamped addressed envelope.

P.W. AUTOMATIC EMERGENCY SUPPLY

250v—50Hz—150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 73 P.W. Complete kit of parts (excluding meter) **£22.50 + £1.10 p & p.**

COMPLETE FLUORESCENT LIGHT INVERTOR KIT

8 watt—12v—Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for, factories, hotels etc. 12" — 3 watt **£2.90 + 25p p & p.** 21" — 13 watt. **£3.30 + 30p p & p.**

TRANSFORMERS & COILS

Both high volume & small order capacity available for Mains, R.F., & I.F. Transformers. Before you buy elsewhere let us quote you and see what you save.
V.A.T. at 8% included.

TRADE & EXPORT ENQUIRIES WELCOMED

ASTRO ELECTRONICS, 10A SPRINGBANK RD., CHESTERFIELD, DERBYSHIRE

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call in on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course". Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects"—Student J.A.O. Dublin.
 "My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to

ALDERMASTON COLLEGE
 Dept. TPW05, Reading RG7 4PF.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> ELECTRICAL ENGINEERING City & Guilds Wiring and Installations	<input type="checkbox"/> Practical Radio & Electronics (with self-build kit) <input type="checkbox"/> Radio Amateurs' Exam	<input type="checkbox"/> Clerk of Works Diploma <input type="checkbox"/> C. & G. Building Quantities <input type="checkbox"/> General Building <input type="checkbox"/> General Civil Eng. Heating, Ventilating & Air Conditioning <input type="checkbox"/> Carpentry & Joinery <input type="checkbox"/> Painting & Decorating <input type="checkbox"/> Plumbing
<input type="checkbox"/> C. G. Electrical Tech-Primary <input type="checkbox"/> Gen. Electrical Eng.	<input type="checkbox"/> ELECTRONIC ENGINEERING Gen. Electronic Eng.	<input type="checkbox"/> C.E.I. (Part 1) <input type="checkbox"/> Inst. Cost & Management <input type="checkbox"/> Accountants <input type="checkbox"/> Works Management etc. etc.
<input type="checkbox"/> AERONAUTICAL ENGINEERING Air Registration Board Certificates <input type="checkbox"/> Gen. Aero Engineering	<input type="checkbox"/> AGRICULTURAL ENGINEERING	
<input type="checkbox"/> AUTO ENGINEERING City & Guilds Auto Engineering <input type="checkbox"/> Practice <input type="checkbox"/> Inst. Motor Industry <input type="checkbox"/> M.A.A./I.M.I. <input type="checkbox"/> Management Diploma <input type="checkbox"/> Gen. Auto Engineering <input type="checkbox"/> Auto Diesel Maintenance <input type="checkbox"/> Motor Mechanics <input type="checkbox"/> Service Station and Garage Management	<input type="checkbox"/> REFRIGERATOR SERVICING	
<input type="checkbox"/> TELECOMMUNICATIONS City & Guilds Telecommunications	<input type="checkbox"/> MECHANICAL ENGINEERING Society of Engineers <input type="checkbox"/> Inst. Engineers and Technicians <input type="checkbox"/> General Mechanical Eng. <input type="checkbox"/> Welding <input type="checkbox"/> Maintenance Eng. <input type="checkbox"/> General Diesel Eng.	
<input type="checkbox"/> RADIO & TV Gen. Radio and TV Eng. <input type="checkbox"/> Radio Servicing, Maintenance and Repairs	<input type="checkbox"/> CONSTRUCTION & BUILDING Institute of Building <input type="checkbox"/> Construction <input type="checkbox"/> Surveyor's Inst.	
<input type="checkbox"/> TELECOMMUNICATIONS City & Guilds Telecommunications	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering <input type="checkbox"/> Draughtsmen & Designers <input type="checkbox"/> General Draughtsmanship <input type="checkbox"/> Technical Drawing	

G.C.E.
 —58 'O' & 'A'
 Level Subjects
 —over 10,000
 Group Passes!

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College,
 Dept. TPW05, Reading RG7 4PF.

NAME.....
 Block capitals please
 ADDRESS.....

POSTCODE.....

OTHER SUBJECTS.....


AGE.....

Accredited by C.A.C.C. Member of A.B.C.C.

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd.; Publisher's subscription rate (including postage): for one year UK £8.95, Overseas £4.95 (\$18.50 USA/Canada) International Giro facilities Account No. 5122097. Please state reason for payment "message to payee". PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Hire where the selling price is subject to V.A.T., and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's Radio

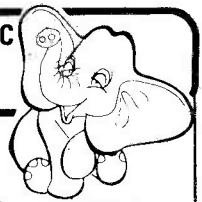LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT. LOW PRICES—MEAN LESS VAT.



You can build the Texan and Stereo FM Tuner TEXAN 20 + 20 WATT IC STEREO AMPLIFIER

Features glass fibre PC board, Gardners low field transformer 6-IC's, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15 1/2" x 23 1/2" x 6 1/2" mains operated. Free teak sleeve with every kit. **£31-00 (Carriage 50p).** (also built and tested **£37-50**)

HENELEC Stereo FM Tuner Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 23" x 6 1/2". Complete kit with teak sleeve **£21-00 (Carriage 50p).** (also built and tested **£24-95**)

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

NEW SPECIAL PURCHASE

Mullard type LP1179 and LP1171

AM/FM tuner modules
These two modules together form a high quality AM/FM tuner covering the long, medium and VHF broadcast bands. Requires only 16 resistors and capacitors and a switch to complete. Supplied with circuits and spec. data **LP1179**
FM Coverage 87-108 MHz
Bandwidth 300 KHz
Selectivity 36 dB
Signal to noise at limiting threshold 40 dB
Audio output 75 mV with built in tuning gang



LP1171

AM Bandwidth 6-5 KHz
Sensitivity 1 pV
Built-in AGCLP1171
Supply 6V negative earth
LP1179 and LP1171 **£4 each or £7-50 pr.**
Suitable Ferrite aerial **£0-75**
£4-00 each or £7-50 pair



Mullard Modules

LP1157 AM/Type 2-50
LP1185 10-71A Unit 11-75
LP1186 10-7 FM Tuner 4-85
Gortler Perm. F/M Tuner 4-20

Amplifiers with controls

E1210 12 volt 2 1/2 + 2 1/2 watts 8 ohms 8-25
SAC14 Mains 7 + 7 watts 8 ohms 11-75
SAC30 Mains 15 + 15 watts 8 ohms 14-95
CAO38 9 volt 1 1/2 + 1 1/2 watts 8 ohms 6-95
CAO68 12 volt 3 + 3 watts 8 ohms 10-50

FM and AM Tuners and Decoders

FM5231 (tu 2) 6 volt fm tuner 7-95
TU3 12 volt version (FM use with Decoder) 7-95
SD4912 Stereo Decoder for Tu 3-12 volt 7-95
SP62H 6 volt stereo FM tuner 14-80
A1007 9 volt MW-AM 4-95
A1016 9 volt FM tuner in cabinet 13-95
A1005M (S) 9-12 volt Stereo decoder FM for above 7-50
1062 12 volt Stereo decoder general purpose 6-50

Power Supplies Mains Input

(*chassis-rest cased)
470C 6 1/2/9V 300 MA with adaptors 2-25
P500 9 volt 500 MA 3-20
HC244R 3/6/7 1/2/9V. 400 MA stabilised 5-50
*P11 2v. 1/2 amp. 3-30
*P15 28V. 1/2 amp 3-30
*P100 12V 1A. 4-70
*P1081 45V 0-9A 7-80
P12 4 1/2-12V. 0-4-1 amp 7-15
SE101S 3/6/9/12V. 1 amp stabilised 12-75
P1076 3/4/6/7 1/2/9/12V. 1/2 amp 4-20
SE800A 1-15 VOLT 0-1A stabilised 17-50

SINCLAIR MODULES & KITS

SINCLAIR PROJECT 80

ST80 Stereo preamplifier 11-95
Audio Filter Unit 6-95
Z40 15 Watt Amplifier 5-45
Z60 25 Watt Amplifier 6-95
PZ5 Power Supplies for 1 or 2 Z40

PZ6 Power Supplies (S Tab) for

1 or 2 Z40 7-98
TRANSFORMER FOR PZ8 4-00
FM TUNER 11-95
STEREO DECODER 7-95
IC20 power amp kit 7-95
PZ20 power supply for 1 or 2 IC20 5-45

PACKAGE DEALS

(carr./packg 35p)
2 x Z40 ST80 PZ5 25-00
2 x Z60 ST80 PZ6 27-75
2 x Z60 ST80 PZ8-trans 34-75
805 Kit 35-95

Sinclair Special Purchases

*Project 60 stereo preamp **£5-75** (post 20p)
*Project 605 Kit **£19-95** (post 25p)

EMI SPEAKERS SPECIAL PURCHASE

13 in. x 8 in. chassis speakers (Carr./packing 30p ea. or 50p pr).
*1150 TC 10 watts 8 ohms twin cone **£2-20**
150A Built in tweeter 8 ohms **£3-85**
EW 15 watt 8 ohms with tweeter **£5-25**
350 20 watt 8, 15 ohm with tweeter **£7-80 each**
*Polished wood cabinet **£4-80** carr., etc. 35p each or 50p pair.



UHF TV TUNERS

625 line receiver UHF transistorised tuners UK operation. Brand new. (Post/packing 25p. each).
TYPE C variable tuning **£2-50**
TYPE B 4-button push-button (adjustable) **£3-50**

PA-DISCOTHEQUE LIGHTING EQUIPMENT



Without doubt U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc.

FREE stock lists (Ref. No. 18) on request CALL IN AND SEE FOR YOURSELF AT

HENRY'S DISCO CENTRE,
309 EDGWARE ROAD,
TEL. 01-723 6963

TEST EQUIPMENT MULTIMETERS

Carr/packing 35p)
U4324 20kΩ/V £ p
with case 9-85
U4313 20kΩ/V with steel case 13-80
U4317 20kΩ/V with case 17-00
U4341 33kΩ/V plus transistor steel case 11-00
U4323 20kΩ/V plus 1kHz OSC with case 8-00
U4311 Laboratory meter **£52-00**
U4312 20kΩ/V with case **£10-75**
U4315 20kΩ/V with case **£10-00**
U4317 20kΩ/V with case **£17-00**
ITL-2 20kΩ/V slim type 5-95
THL33D (L33DX) 2kΩ/V Robust 7-50
TP55N 20kΩ/V (Case £2) 10-75
TP10S 20kΩ/V 8-50
TW20S 20kΩ/V 13-00
TW50K 50kΩ/V 14-50
S100TR 100kΩ/V plus transistor tester 22-50

NEW REVOLUTIONARY SUPERTESTER 680R

£ p
680R Multi-tester 18-50
†TE40 AC Multivoltmeter 19-75
†TE15 Grid dip meter 14-50
†440k Hz-28MHz voltmeter 19-50
†TE120 28 Range valve voltmeter 22-50
†TE20D RF Generator 18-95
†120kHz-500MHz 18-95
†TE22D AF Generator 19-95
†20Hz-200KHz
*HM350 In circuit transistor tester 19-50
*C3025 Deluxe meter 1-300mOhm 6-95
*TT145 Compact transistor tester 14-75
†G3-36 R/C osc. 20Hz-20KHz 19-75
*SE350A De-luxe signal tracer 12-95
*SE400 Mini-lab all in one tester 15-50
CI-5 Scope 500,000KHz (carr. £1-00) 43-00
Radio activity counter 0-10r (carr. £1) 9-97
Mains unit for above (carr. 50p) 3-75

TAPE HEADS

Marriot XRPS/17 1/4 Track High 2-50
Marriot XRPS/18 1/4 Track Med 3-50
Marriot XRPS/36 1/2 Track Med. 5-00
Marriot XRPS/63 1/2 Track High 7-75
Marriot Erase Heads for XRSP 17/18/36 (XES11) 75p
Marriot BXIZE 343 1/2 Track erase 75p
R/RP1 Rec'd/Play 1/2 Track HRP S'gle Trk Rec/Play 45p
Bogen Type UJL90 Erase Miniature Stereo Cassette Rec/Play 1-25

EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load. 30 volt max. DC operation, complete with data. Price **£1-50** each or 2 for **£2-85**.
Printed Circuit Panels 50p.

8 DIGIT POCKET ELECTRONIC CALCULATORS

Sinclair Cambridge Built **£11-00**
Cambridge Kit **£9-00**
Cambridge Memory Built **£17-50**
Scientific Built **£16-00**
Scientific Kit **£13-50**

ALL PRICES SUBJECT TO 8% VAT

FREE:—

SEND NOW FOR OUR FREE LIST NO. 36 FOR OUR COMPLETE RANGE OF OVER 10,000 SEMI-CONDUCTOR DEVICES AT NEW LOW PRICES.



EXTRA DISCOUNTS

Semiconductors—Any one type or mixed SN74 Series IC's, 12—extra 10%; 25—extra 15%; 100—extra 20%.

TRANSISTORS & INTEGRATED IC's

TTL "7400 series" IC's from 16p each
Cosmos "4000 series" IC's from 25p each
Linear Op-Amps from 40p each
Signetics Phase Lock IC's; RCA Linear IC's; TO3 Power Devices in PNP and NPN; BC107 and "BC range" Range of OC Types 18p
Plastic Power Devices, Rectifiers, Zener, Power Regulator IC's and many others.
Diodes up to 10 watts

DIL SOCKETS

8 PIN 14p
14 PIN 15p
16 PIN 17p
24 PIN **£1-15**
28 PIN **£1-25**

NOMBREX TEST EQUIPMENT

Model 35 Stabilised Power Supply

A short circuit proof power supply delivery up to 30 volts at 1 Amp. Built-in Volts and ammeters. **£34-00**

Model 40 Wide Range Audio Signal Generator

A high stability signal generator using the low distortion Wien bridge principle. Covering 10Hz to 100 KHz in 4 ranges. Adjustable output from 1mV to 1V. Sine and Square wave output. **£34-00**

Model 41 RF Signal Generator

Covering 150 KHz to 220 MHz in 8 ranges. Built in AF mod. Output up to 50mV. Crystal calibration facilities. Large linear scale with slow motion drive. **£38-00**

Model 42 Wide Range RF Signal Generator

Covering 150 KHz to 300 MHz in 8 ranges. Highest range n harmonic. Built in AF mod. Output up to 50mV. Circular scale. **£24-50**

Model 43 RC Bridge

Null indicating bridge for resistors and capacitors. Resistance range 10R to 10M ±2% at Centre Scale. Capacity range 10pF to 10μF ±2% Centre Scale except 1pF to 10pF Range ±3%. Power Factor Measurement 0-70% **£23-50**

Model 44 Inductance Bridge

Measures 1μH to 100H in 4 ranges ±5% accuracy. Q measurement from 0-1—1,000 ±10%. **£34-00**

Model 45 Direct Reading Frequency Meter

10Hz to 100 KHz in 4 ranges. Input from 10V to 100V. **£36-00**

All models except Model 35 are internally powered from 9V battery (extra). Carriage and packing all models 3p.

NOW OPEN—SUPERMARKET

Come and browse round the new components supermarket at 404 Edgware Road. Bargains galore. Goodie Bags. Components, etc. WATCH FOR FURTHER DEVELOPMENTS!

Henry's Radio

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW
Prices correct at time of preparation. Subject to change without notice. E.&O.E

Hr Fri and Electronics Centres Open 9 am - 6 pm