

PRACTICAL WIRELESS

JULY
1975

30p

PW **TEXAN II**

UPDATING YOUR
PRESENT TEXAN
AMPLIFIER



Also

PW
TELE-TENNIS
ADD-ON
SOUND EFFECTS


REPORT ON:-
THE HEATHKIT GR 78 RECEIVER

PW

APOLLO SERIES

VARICAP AM/FM STEREO TUNER



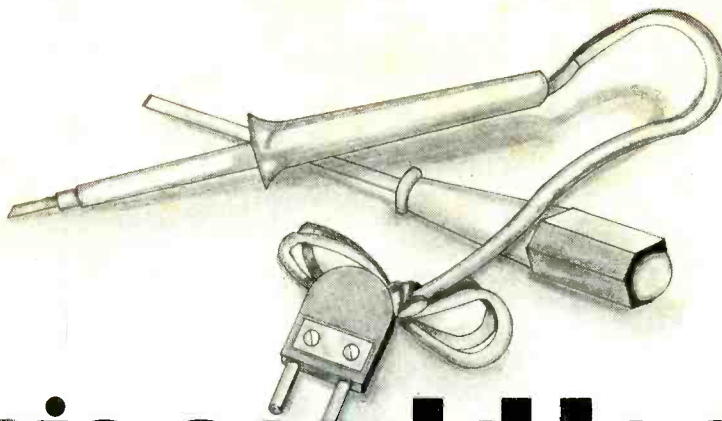

This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

1

Build an oscilloscope.

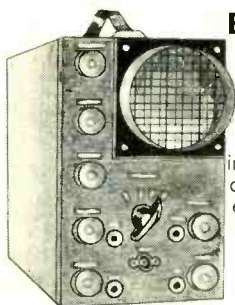

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2

Read, draw and understand circuit diagrams.



In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

Carry out over 40 experiments on basic circuits.



We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS



FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

WAA

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept WL/65
P.O. Box 156, Jersey, Channel Islands.

NAME.....

ADDRESS.....

.....

(Block caps please)

PRACTICAL WIRELESS

VOL. 51 NO. 3

ISSUE 821

JULY 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Sam Lewis B.Sc. (Eng.)

PRODUCTION & NEWS EDITOR

Colin R. Riches

TECHNICAL SUB-EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Jenny Maunder

Susan King

ADVERTS MANAGER

01-634 4293

Roy Smith

CLASSIFIED ADVERTS

01-634 4301

Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £5.00 and to the rest of the world £5.00 (\$13.50 USA/CAN) including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.90) and indexes 30p (inc. VAT) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

196 VAT MUDDLE!—Editor's comment

196 CIRCULATION DETAILS

197 NEWS . . . NEWS . . . NEWS . . .

210 LETTERS—Readers comment

213 HOTLINES on recent developments by *Ginsberg*

219 NEXT MONTH IN PRACTICAL WIRELESS

230 PRODUCTION LINES by *Colin Riches*

242 ON THE AIR

242 Amateur Bands—*Eric Dowdeswell, G4AR*

245 Broadcast Bands—Short Waves—*Derek Bell*

246 Broadcast Bands—Medium Waves—*Charles Molloy*

● CONSTRUCTIONAL

198 THE P.W. TEXAN II—updating our stereo amplifier—
Richard Mann

204 P.W. 'APOLLO' Series—Part 3—Varicap AM/FM Stereo
Tuner—*W. Poel*

220 DIGITAL WAVEFORM GENERATOR—Part 2—*John Smith*

226 TELE-TENNIS Sound Effects Unit—*M. J. Hughes, M.A.,
C.Eng., MIERE*

237 A UHF WAVEMETER—*R. Longden*

● OTHER FEATURES

214 SPECIAL PRODUCT REPORT—Heathkit GR78 General
Coverage Receiver

218 TECHNICROSS—No. 9—Solution

225 GOING BACK—Earlier days of Wireless—*Colin Riches*

229 POINTS ARISING—P.W. 'Easybuild' Organ

233 CALCULATRICKS—*R. Stanwicki*

246 CQ!CQ!CQ!CQ!CQ!

HEATHKIT COMPETITION — RESULTS — Page 196

RSC 100 watt DISCO SYSTEM

50 WATT SPEAKER **50 WATT SPEAKER**

TWIN TURNTABLE WITH PRE-AMP. and POWER AMPLIFIER

AT FANTASTIC LOW PRICES!

Complete with lid **HEADPHONES MICROPHONE**

Units listed below

(a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier

(b) PAIR OF HI-FI HEAD- PHONES

(c) MATCHING DYNAMIC "MIKE" (attached to h'phone)

(d) PAIR 50 WATT SPEAKERS

Black Texene covered Cabinets Size approx. 18" x 18" x 8"

(a) (b) (c) & (d) Carr. £3-00

£169-95

DEP. £19-99 & 18 fortnightly payments of £9-67 (Total £194-05).

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BSR MP60 type turntables and Sonotone or Acoac Cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amp. complete with lid. Or Deposit £12-95 and 18 fortnightly payments £8-81 (Total £128-53)

£79-95

Carr. £1-50

DEP. £8-00 and 18 fortnightly payments £4-61 (Total £91-98)

STEREO VERSION

of Above System

OR DEPOSIT £28-95 and 18 fortnightly pymts. £11-11 (Total £228-93)

£199-95

Carr. £3-50

TDIS STEREO VERSION OF ABOVE

Terms DEPOSIT £15 and 18 fortnightly payments £8-61 (Total £132-18)

£115-00

Carr. £1-60

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £109-95

Garrard SP25 or McDonald MP60 turntables. Sonotone or Acoac cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amp. complete with lid. Or Deposit £12-95 and 18 fortnightly payments £8-81 (Total £128-53)

STEREO VERSION £145 OR DEPOSIT £20 and 18 fortnightly pymts £8-15 (Total £168-70). Carr. £2

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Vynalide & Vynair

TYPE C132 40-50 WATTS £27-95

Incorporating three exceptionally efficient 13" x 8" speaker units. Dep. £3-95 and 8 monthly payments £3-50 (Total £31-95) Carr. 65p

TYPE C8/70 70 WATTS. Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 6 1/2" x 14" x 11". Dep. £3-11 & 8 monthly pymts. £5-11 £39-95 (Total £45-99) Carr. 85p

FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15 Ω	15" 60 Watt 14,000 gauss 8/15 Ω	12" 50 Watt 13,000 gauss 15 Ω
£34-50	£18-95	£13-95
Dep. £6-80 and 8 monthly payments £4-00 (Total £28-80)	Dep. £4-17 and 8 monthly payments £2-17 (Total £21-63)	Terms for pairs Dep £5-90 & 8 mthly pymts £3-16 Total £31-18 PAIR SUITABLE FOR ALL PURPOSES

FOR BASS GUITAR, ELECT. ORGAN, ETC.

ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

SUPER MINSTREL 10 W GUITAR AMP.

Incorporating Tremolo and 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo, Speed Tremolo Intensity.

Terms: DEPOSIT £7-78 and 8 monthly payments £3-40 (Total £24-98) Carr. Free

£30-94

'POP' 25/T 12" 25W. PH50 HIGH POWER TWEETER £6-65

Dual cone. 15 ohm Imp. (Not for Bass Guitar use)

£9-95

'POP' 20/1 10" 20W. £8-50

Gauss 18,000 Imp. 8-15 Ω

Response 3KHz-20KHz with 2 to 4 mfd. Non elect. filter available 55p. Rating 50 Watt Imp 8 Ω

FAL MAESTRO COMBINED 30W AMP. AND 12" SPEAKER £48-60

For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass Instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass, TREMOLO with associated controls. Attractively finished in black with silver-finished fascia. Compact size Fitted carrying handle. Deposit £8-60 and 8 mthly payments £5-75 (Total £24-60)

Rating 50 watts. 3 inputs, 2 vol. controls. Bass, Treble, Presence

Dep. £8-00 & 8 mthly. pymts. £5-78 (Total £22-08).

£55-00 Carr. £1-50

D40 FULL RANGE 40 WATT POWER SPEAKER KIT £21-00

Consisting of 12" 40 watt Bass Unit, HPX1 200w Cross-over and PH50 Tweeter. Rating 40w R.M.S. Imp. 8 ohms. Terms: Deposit £3-00 and 8 mthly payments £2-75. (Total £25-00).

FAL PHASE 50 Mk. III AMPLIFIER 50 WATT

Solid state. 4 Sep. controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protection against serious o/p overloading. O/p for spkrs. 8 to 15 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. O/p 50W Music. Deposit £8-60 & 8 mthly. payments. £5-75. Total £24-60

Carr. Free. **£48-60**

TITAN GROUP/ DISCO SPEAKERS

as advertised elsewhere in this issue

FULL RANGE AT DISCOUNT PRICES

JINGLE MACHINES I.S.E. CA127 £79-95

REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 60w Peak O/P rating. Not for Bass Instruments.

★ Two Fane heavy duty high flux 12in. spkrs.

★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls.

Send S.A.E. for leaflet. Credit Terms: Deposit £9-95. & 18 fortnightly payments of £4-15 (Total £24-65).

Carr. £2-50

£74-95

HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO-TONE VYNALIDE AND VYNAIR FINISH

L12/2 50 WATT Fitted pair of 12" 30 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50

Or deposit £5-11 and 8 monthly pymts. of £5-11. Total £45-99

L12/25G 18" 25 WATT 13,000 lines 15 ohms Terms for Pairs. Dep. £3-28 & 8 mthly pymts £3-28 (Total £29-88)

£39-95

L12/10 10-15 WATT Vaneered cabinet 12" unit 8-15 ohm. Approx. 14" x 14" x 9"

Carr. 65p. Terms for Pairs. Dep. £2-05 & 4 mthly pymts £2-05 (Total £18-45).

£7-95

REGENT 50B for Bass Guitar and general purposes. Or Dep. £9-00 & 18 fortnightly payments £4-61. £79-95

REGENT 50B for Bass Guitar and general purposes. Or Dep. £9-00 & 18 fortnightly payments £4-61. £79-95

(Total £21-98). Carr. £2-50

GP30 AMPLIFIER

For Guitar, Vocal or Instr. Group. Gram, Radio or Tape. 4 inputs. 2 Vol. Controls. Current Valves. Peak o/p rating. Strong Vynalide covered cabinet with carrying handles. Black/Silver Facia. Neon Indicator. For 200-250v A.C. For 3 or 15 Ω

Speakers. Send SAE for leaflet. Terms: Dep. £5-58 & 8 mthly pymts £3-58 (Total £24-22)

Carr. 70p **£29-95**

FAL DISCO PRE-AMPLIFIER

T/Table mixing inputs. Headphone Monitoring. Mic. Jack & Tape inputs. Independent Vol. Control. Std. 200-250v A.C. Mains operation

£18-50

LIQUID WHEEL PROJECTORS £24-75

'SOUND TO LITE' SYSTEM

PULSAR special price complete kit **£99-95**

Dep. £11-48 and 18 fortnightly pymts. £5-74. (Total £114-80). Super SL Unit 1000 watt per channel. Manual override buttons. 2 spotbombs with 6 bulbs (3 sep. colours) 5 yd. and 10 yd. leads, fitted plugs. Units sold sep.

FAL SOUND-TO-LITE UNIT **£21-60**

" 3-WAY SPOTBANK Excluding Bulbs Each **£16-20**

COMPLETE SYSTEM Incl. 2 Spotbombs and bulbs. Carr. £1-50 **£55**

NEW BRANCHES AT BOLTON, DONCASTER, and PRESTON

OPEN ALL DAY SATURDAYS (5 Day Week)

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349

BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512

BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).

COVENTRY 17 Shelton Square, The Precinct. Tel. 25983

DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361

DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

HI-FI CENTRES LTD.

Barclaycard and Access accepted

All items subject to availability. Prices correct at 12.5.75 E. & O.E.

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs). Tel. 63069

EDINBURGH 101 Leithan Rd. (Closed Wed.). Tel. 229 9501

GLASGOW 328 Argyle St. (Closed Tues.). Tel. 248 4158

HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505

LEICESTER 32 High Street (Closed Thurs.). Tel. 58420

LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252

LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573

LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1829

MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778

MIDDLBROUGH 106 Newport Road (Closed Wed.). Tel. 47051

NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469

NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48088

PRESTON 41 Friargate Walk, St. Georges Shoppo Prec. Tel. 51979

SHEFFIELD 13 Exchange Street (Castle Mkt. Blds.) (Closed Thurs.). Tel. 20718

STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777

SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573



TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Pr. 120/240 V Sec. 120/240 V Centre Tapped and Screened

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
149	60	3 12	7.0 x 6.0 x 6.0	2.80 38
150	100	5 8	9.9 x 7.7 x 8.6	4.37 45
151	200	8 0	9.9 x 8.9 x 8.6	4.89 45
152	250	13 12	12.1 x 9.3 x 10.2	8.13 53
153	350	15 0	12.1 x 11.8 x 10.2	9.83 73
154	500	19 8	14.0 x 10.8 x 11.8	11.88 73
155	750	29 0	14.0 x 13.4 x 11.8	13.65 91
156	1000	38 0	17.2 x 14.0 x 14.0	20.51 *
157	1500	46 0	17.2 x 16.6 x 14.0	29.15 *
158	2000	60 0	21.6 x 13.4 x 18.1	33.23 *
			21.6 x 15.3 x 18.1	37.07 *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	0	5.8 x 5.1 x 4.5	0-15-210-240	1.67 30
64	75	2 4	7.4 x 6.7 x 6.1	0-15-210-240	2.90 38
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	4.12 45
66	300	6 4	9.9 x 9.6 x 8.6	"	5.82 53
67	500	12 8	12.1 x 11.2 x 10.2	"	8.82 67
84	1000	19 8	14.0 x 13.4 x 14.3	"	13.68 91
93	1500	30 4	14.0 x 15.9 x 14.3	"	18.38 **
95	2000	32 0	17.2 x 16.6 x 14.0	"	24.20 **
73	3000	40 0	21.6 x 13.4 x 18.1	"	35.09 *

CASED AUTO TRANSFORMERS
240V mains lead input and U.S.A. 2-pin outlets. 20VA £3.23 pp 38
500VA £10.45 pp 80p 1000VA £17.51 via B.R.S.

TRANSFORMERS

PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RANGE

Ref. No.	12V 24V	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5	0.25	1 4	4.8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.35 23
213	1.0	0.5	1 4	6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	1.74 30
71	2	1	1 2	7.0 x 6.4 x 6.1	0-12V at 1A x 2	2.29 38
18	4	2	2 12	8.3 x 7.7 x 7.7	0-10-12V at 2A x 2	2.86 38
70	6	3	3 8	8.9 x 8.0 x 7.0	0-12V at 3A x 2	4.12 45
108	8	4	5 8	9.9 x 8.9 x 8.6	0-12V at 4A x 2	4.56 45
72	10	5	6 4	9.9 x 9.6 x 8.6	0-12V at 5A x 2	5.14 53
116	12	6	6 12	9.9 x 10.2 x 8.6	0-12V at 6A x 2	5.52 53
17	16	8	8 12	12.1 x 9.9 x 10.2	0-12V at 8A x 2	7.28 60
115	20	10	11 8	14.0 x 9.6 x 11.8	0-12V at 10A x 2	10.39 73
187	30	15	15 18	14.0 x 12.1 x 11.8	0-12V at 15A x 2	13.59 85
226	60	30	32 0	17.2 x 15.3 x 14.0	0-12V at 30A x 2	16.83 **

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.81 30
79	1.0	2 4	7.0 x 6.7 x 6.1	"	2.40 38
3	2.0	3 4	8.9 x 7.7 x 7.7	"	3.49 38
20	3.0	4 8	9.9 x 8.3 x 8.6	"	4.53 45
21	4.0	6 4	9.9 x 9.6 x 8.6	"	5.13 53
52	5.0	6 12	12.1 x 9.6 x 10.2	"	6.41 53
117	6.0	8 0	12.1 x 9.3 x 10.2	"	7.16 60
88	8.0	12 0	12.1 x 11.8 x 10.2	"	9.90 67
89	10.0	13 12	14.0 x 10.2 x 11.8	"	9.87 73

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.58 30
103	1.0	2 12	8.3 x 7.4 x 7.0	"	3.38 38
104	2.0	5 8	9.9 x 8.9 x 8.6	"	4.68 45
105	3.0	6 12	9.9 x 10.2 x 8.6	"	5.81 53
106	4.0	10 0	12.1 x 10.5 x 10.2	"	7.60 67
107	6.0	12 0	14.0 x 10.2 x 11.8	"	12.10 67
118	8.0	18 0	14.0 x 12.7 x 11.8	"	12.98 85
119	10.0	25 0	17.2 x 12.7 x 14.0	"	16.99 **

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60	2.33 38
126	1.0	3 4	8.9 x 7.7 x 7.7	"	3.41 38
127	2.0	6 4	9.9 x 9.6 x 8.6	"	5.08 45
128	3.0	6 12	12.1 x 9.9 x 10.2	"	7.53 60
123	4.0	13 12	12.1 x 11.8 x 10.2	"	8.75 67
40	5.0	12 00	14.0 x 10.2 x 11.8	"	9.75 73
120	6.0	15 8	14.0 x 12.1 x 11.8	"	11.30 85
121	8.0	25 00	14.0 x 14.7 x 11.8	"	15.00 **
122	10.0	25 00	17.2 x 12.7 x 14.0	"	17.52 **
189	12.0	25 00	17.2 x 14.0 x 14.0	"	19.98 **

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	MA	Weight lb oz	Size cm.	VOLTS	P & P £ p
238	200	2	2.8x2.6x2.0	3-0-3	1.54 10
212	1A 1A	1	4.6x5.8x4.8	0-6-0-6	1.84 30
13	100	4	3.9x2.6x2.9	9-0-9	1.41 13
235	330,330	4	4.8x2.9x3.5	0-9-0-9	1.56 19
207	500,500	1	6.1x5.4x4.8	0-8-9-0-8-9	1.92 30
208	1A, 1A	12	7.0x6.4x6.1	0-8-9-0-8-9	3.30 38
236	200,200	4	4.8x2.9x3.5	0-15-0-15	1.43 19
214	300,300	4	6.1x5.8x4.8	0-20-0-20	1.93 30
221	700 (D.C.)	1	8.7x6.1x6.1	20-12-0-12-20	2.17 38
206	1A, 1A	2	8.3x7.7x7.0	0-15-20, 0-15-20	3.46 38
203	500,500	2	4.8x3.7x6.7	0-15-27, 0-15-27	3.00 38
204	1A, 1A	3	4.8x3.7x7.7	0-15-27, 0-15-27	3.85 38

PLEASE ADD 25% FOR V.A.T. INCLUDING P. & P.

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

CJL PRICES INCLUDE P&P AND V.A.T.

- AERIAL, telescopic, 15-120cm. £1.20
- AERIAL, telescopic, h and v swivel, 15-80cm. £1.78

BIB HI-FI ACCESSORIES

- CASSETTE TAPE RECORDER CARE KIT £1.95
- CASSETTE SPlicing AND EDITING KIT £1.50
- HI-FI STEREO TEST CASSETTE £2.10
- 1" TAPE EDITING KIT £1.35
- GROOV-KLEEN RECORD CLEANER £1.85
- EARPHONE, stethoscope style, 8 ohm dynamic £1.00
- HAND DRILL, (Laytool), compact precision drill, 5/16" chuck. Gears totally enclosed. S/L bearings. £2.99

INTEGRATED CIRCUITS

- AUDIO POWER AMPLIFIER (National) LM380 £1.00
- A.M. RADIO RECEIVER (RCA) CA3123E £1.40
- F.M. STEREO DECODER (Motorola) MC1310P £2.80
- TIMER (Signetics) NE555V £0.78
- VOLTAGE REGULATOR (Fairchild) uA7805 £1.70
- VOLTAGE REGULATOR (Signetics) NE550A £0.80
- D.I.L. SOCKETS (Pk of 3) 8 or 14 pin £0.50
- KEYNECTOR, rapid connect to mains-single/multiple leads. Built-in piano switches, neon & 13A fuse £3.20
- LOCKFLEX RULE (Rabone Chesterman), 3m/10ft precision pocket rule. Easy to read, 13mm/1/2" wide steel tape. Blade length lockable-power return. A superb rule £0.93
- MICROPHONE, lightweight dynamic, remote start stop, 200 ohms, 100-10kHz, 6mV average output £1.80
- MULTIMETER, attractive design, Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA, R-150k £4.95
- SIGNAL INJECTOR, audio through video signals, excellent for servicing amplifiers, radio & tv £3.92
- SOLDERING IRON, 25 WATT (Antex), X25, 240V, Very low leakage, 1/8" long life bit (interchangeable) £2.05
- U3/32" bit £0.47 3/16" bit £0.47 Element £1.10
- STAND, ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits £1.00
- SPEAKER, miniature, 75mm dia, 8 ohms. £0.80

CJL CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

Train for television

Course commences September 8th 1975

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name _____

Address _____

THE PEMBRIDGE COLLEGE OF ELECTRONICS
(Dept PW5) 34a Hereford Rd., London W2 5AJ

no extras

FREE delivery



ALL ITEMS SUBJECT TO MANUFACTURERS INCREASE AND AVAILABILITY
Personal Callers are Welcome!



High Quality Construction Kits, stocked at all branches. Send for catalogue!

AMPLIFIERS
Rotel RA211 £43.95
RA311 £54.95
RA611 £86.95
Sansui AU101 £48.25
AU505 £74.95
Sinclair 4000 £50.00
Linton Mk. II £59.95

TUNERS & RECEIVERS
Sinclair 4000 Tuner £43.95
Rotel RT222 £42.75
Pioneer SX434 £99.00
Rotel RX150A Tuner/ Amp. £59.95
Rotel 152 £69.95
Sansui
210 AM/FM/MPX £75.50
310 AM/FM/MPX £99.50
441 AM/FM/MPX £91.95

RECORD DECKS (Ins. 50p)
Garrard SP25 MkIV £14.75
BSR MP60 £12.95
Garrard
SP25 MkIV P & C G/800 £25.00
Goldring GL78 P & C/ G800E £59.95
Rank Domus BD 2000/ Rex 999 Cart. £50.00
Connoisseur
BDI Kit £13.50
BD2 Chassis/SAU2 £32.50
SAU Arm £14.25
SCUI Cartridge £5.95
Pioneer PL12D £43.50

TAPE DECKS (Insurance 2-00)
Akai
4000DS Reel to Reel £97.95
4000DB Reel to Reel £149.50
Dolby £85.00
GXC36D £107.95
GXC38D £107.95
CS33D £82.95
Akai CR81D 8-track Rec. player £85.95
GXC82D £95.95
CS30D £66.95

SPEAKERS
Chassis Speakers
EMI (Plain) 13in x 8in, 3 or 8 ohm Bass unit £2.50
with Single Tweeter (only 8 ohm) £2.75
with Tweeter and Cross-over 3, 8 or 15 ohm £4.25
Type 350 Kit 15 watt 8 ohm £8.25
13in x 8in Bass unit 15 watt 8 ohm or 15 ohm £5.45
8in x 5in 5 watt 3, 8 or 15 ohm £1.70
8in x 5in 10 watt Dualcone 8 ohm £2.95
6 1/2" 10 watt 8 ohm £2.45
8in 10 watt 8 ohm £4.50
8in 4 or 15 ohm £2.25
7in x 4in 3 or 8 ohm £1.30
Elac 6 1/2" 8 ohm Dualcone £2.65
Elac 8in 8 ohm Dualcone £2.70
Elac 10in 8 ohm Dualcone £3.75
Baker Group 25 12in 8 or 15 ohm £8.25

Adastra 'Top 20' 12in 25 watt 8 or 15 ohm £8.25
Adastra 'Hi-Ten' 10in 10 watt 8 or 15 ohm £3.70
Also 5in 8 ohm speaker £0.95
2 1/2in 8 or 64 ohm speaker 60p

WHARFEDALE SPEAKER BARGAINS
Denton 1 pr. £26.75
Denton 2 pr. £32.00
Linton 2 pr. £40.75
Glendale 3 pr. £60.95
Kingsdale 3 ea. £64.95
Dovedale 3 ea. £44.95

KITS
Linton 2 pr. £20.95
Glendale 3 pr. £35.95
Dovedale £55.50

SPEAKER CABINETS IN KIT FORM (Teak Veneer) (Ins. 50p. per pair)
12in x 8in x 6in (8 x 5 or 7 x 4 cutout) £3.50
14in x 12in x 9in (10", 8 x 5, 8", 6 1/2" & 3 1/2") £4.25
18in x 11in x 9in (8" x 3" or 13 x 8) £5.50
22in x 14in x 9in (12" x 3" or 13 x 8) £7.25

TWEETERS & CROSSOVERS
Cone Tweeter 10 watt 8 or 15 ohm (K2006) £2.95
Cone Tweeter 3 watt 8 ohm (K2003) £1.55
Horn Tweeter 8 ohm (K2007) £6.50
Dome Tweeter 8 ohm (K2011) £5.75
2-way Crossovers (CN23, CN28, CN216) £1.40
3-way Crossover (CN38) £2.85

CARTRIDGES & STYLII

ACOS	Cart.	D/D Styli	£	£
GP91/2SC or 3CS (ster. comp.)	1.10	1.25		
GP93/1 or 95/1 ster. cryst.	1.35	1.25		
GP94/1 or 96/1 ster. ceram.	1.75	1.25		
GPI01 cryst. comp.	90	—		
GPI04 ster. ceram.	1.95	1.25		
BSR				
X5M or X5H cryst. comp.	1.95	1.25		
SX6M or SX6H cryst. ster.	2.10	1.25		
SC5M ster. ceram.	2.85	1.25		
SONOTONE				
9TAHC or 9TAHC/G (Diam.)	1.95	1.25	5"	1.25
3509 Magnetic	1.95	1.25	5 1/2"	1.25
AUDIO TECNICA AT55	1.95	—	7"	1.25
EMPIRE 999 REX	3.95	—		
GOLDRING G850	3.10	1.95		

G800 4.25 1.95
G800H 4.25 1.95
G800E 7.25 3.95
SHURE
M44G 4.95 3.95
M55E 6.25 4.95
M75ED Type 2 11.75 8.25
MJEJ Type 2 9.75 6.25
V15 Type 3 32.25 —

MICROPHONES
UD130 50K/600 ohm uni-dir. ball metal £6.75
UD147 £9.25
Condenser Mic. 600 ohm uni-dir £9.50
Cassette Stick Mic. with R/Control £1.65
Cass. Stiek Mic. with R. control (Philips type) £2.00
Mic-Mixers Mono/stereo £5.50
TW209 £5.90

HEADPHONES
Rotel
RH430 £4.75
RH 630 £7.75
RH 700 £11.50
Koss
K711 £11.50
KRO711 £10.95
K6 £13.00
K6LC £14.95
KO727B £16.75
KO747 £21.50
HV1 £21.95
PRO4AA £29.25
PRO54 £29.95
K6LCQ £26.00
Sansui SS10 £16.75
*Headphone adaptor (Junction box) £2.75
extension lead 2ft curly £1.50

CASSETTES
C40 C60 C90 C120
Low Noise — 35p 45p 55p
Philips — 55p 75p 110p
Memorex 65p 79p 110p 155p
Ampex (360) 45p 55p 75p 99p
Ampex
(20-20+) 59p 65p 99p 135p
Chromium
Dioxide — 99p 140p —
Cassette Head Cleaner 45p
Ampex Head Cleaner/Damage £1.65
BIB Stereo Test Cassette £2.15
Cassette Racks (hold 6) £0.45
Cassette Rotating Racks (hold 20) £3.50
Cassette Carrying Case (hold 18) £1.95
8-Track Cartridge Blanks C40 C64 C80
80p 95p £1.10
Ampex
8-track H/Cleaner £1.90
Demagnetiser £1.90
8-track Carrying Cases (BIB) £1.65

TAPES

	Std	LP	DP	Cases
5"	55p	65p	1.00	20p
5 1/2"	65p	86p	1.35	25p
7"	80p	110p	1.85	30p
High frequency Ampex				
5"	—	1.40p	1.55p	
7"	—	1.90p	2.95p	
AKAI Metal Reel 7"				£2.10

CALCULATORS
Sinclair Cambridge Build £12.95
Sinclair Cambridge with memory £17.95
Scientific £19.95

SINCLAIR PROJECT 80
Stereo Pre-amp. £12.95
Active Filter Unit £7.25
Z40 15 watt Amp £5.75
Z60 25 watt Amp £7.25
P25 Power Supply for 240 £5.45
P26 Power Supply for 240 £8.45
P28 Power Supply for 260 £8.25
FM Tuner £12.95
Stereo Decoder £8.45
Q16 Speaker £7.75
IC20 Stereo Amp. Kit £7.45
PZ20 Power Kit £5.25

PORTABLE RADIOS
Meridian Mk. II £12.25
Vega Jade £5.95
Vega Sapphire £8.75
Vega VEF206 £15.50
Selena LM/MW/FM/55W £22.50
Murphy
B833 MW/VHF £9.95
BA838 LW/MW/VHF £18.50
M/Batt
MA5003 Head Sec Radio LW £7.95
Bush
VTR165 LW/MW/VHF £22.00
VTR127 LW/MW/VHF £15.50
VTR 175 LW/MW/VHF £13.95
VTR188 LW/MW/VHF/25W M/Batt £31.95
BY5661 LW/MW/VHF £14.95
Selga 2 wave band with leather case £5.50

CLOCK RADIOS
Bush CR128 LW/MW £15.50
Bush CR232 MW/VHF £24.95
Murphy MV5600 MW/VHF £22.95
Vega Signal 2 wave band £9.95

CASSETTE RECORDERS
Bush TP66 M/Batt £25.75
Murphy BA200 M/Batt £22.75
Bush BT8504 (miniature) £25.50
Mains Battery Cass. £15.50

RADIO CASSETTES (Mains/Batt.)
Murphy BA209 MW/VHF £33.50

STEREO RECORD PLAYER & SYSTEM
Bush A1005 £56.50
Hanimec HRC5060 8-track AM/FM/MPX + Speaker £116.95

CAR AUDIO
Hitachi Car Radio WM702R LW/MW £16.50
KM1510 LW/MW/VHF £32.50
Hitachi Car Cassette CS114 £45.00
Hitachi AM/FM & Cassette CSW 217 £57.00

Battery Eliminators 240 in 6, 7.5 or 9 volt output £3.10
(PLEASE ADD VAT)

ALL MERCHANDISE FULLY GUARANTEED

NEWMART ELECTRONICS

Mail Order Dept PW/7
Belmont St, Monton, Eccles, Manchester.
Tel: 061-789 5268

Manchester
30-32 Shudehill. tel 061-832 7710
Leeds
4 New Market St tel 0532 42708
Liverpool
15 Whitechapel tel 051-236 0738



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE CPW07

DEPT. CPW07
READING RG7 4PF

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

Name

Address

POST CODE



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY


QUALITY STEREO SOUND

ALMOST 1/2 PRICE OFFER!

SOLENT AUDIO SYSTEM

£5.95 down

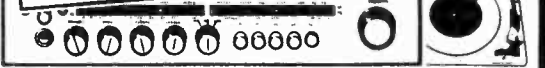MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM
OUR PRICE **£59.95**



*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/2". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £59.95. Credit Sale £5.95 deposit 9 monthly payments of £7.00 (Total Credit price £68.95). P. & P. £3.00. Send £8.95 today.

Chassis only available for cash at £42.00.

Full 12 months Guarantee.

CALLERS WELCOME.

Stereo headphones supplied with every complete order. **LEWIS radio** PW/7/75 100 CHASE SIDE SOUTHGATE LONDON N14 5PL Telephones: 01-882-1644

ALLARD ELECTRONICS

New Branded Components—Full Specification—Guaranteed

Transistors	Price ea.	I.C.'s	Price ea.
AC125/6/7/8	0.13	709C (DIL or TO)	0.27
AD140/149	0.48	723C (DIL or TO)	0.50
AD161/162	0.35	741C DIL	0.38
AF114/6/6/7	0.13	748C TO	0.44
AF118	0.35	748C DIL	0.28
BC107/8/9 0.09		LM309K	2.00
BC147/8/9 0.07		TBA800	0.95
BC157/159	0.13	ZN414	1.05
BC158	0.11	S.C.B.'s	
BC182/3/4 0.10		CR81/06	0.30
BC212/3/4 0.11		CR81/10	0.58
BCY70/1/2	0.12	CR81/20	0.60
BD131/132	0.35	CR81/40	0.45
BF194/5/6 0.10		CR83/40	0.55
BFY50/1/2	0.15	ZENERS	
MJE370	0.82	BZ88 all voltages	0.09
MJE371	0.23	BZX61 series 1-3w	0.17
2N2218	0.19	ALL-BOXES	
2N2906	0.13	2 1/2 x 5 1/2 x 1 1/2	0.44
2N2926 all 0.09		4 x 4 x 1 1/2	0.44
2N3053	0.15	4 x 2 1/2 x 1 1/2	0.44
2N3054	0.42	4 x 2 1/2 x 2"	0.44
2N3055	0.44	3 x 2 x 1"	0.38
2N3702/3/4	0.10	6 x 4 x 2"	0.60
2N3705/6	0.10	7 x 5 x 2 1/2"	0.70
2N3707/8/9	0.08	VEROBOARD	
2N3819	0.24	1 Matrix	Price ea.
TIP29a	0.45	2 1/2 x 3 1/2"	0.30
TIP30a	0.64	2 1/2 x 5"	0.34
TIP31a	0.61	3 1/2 x 3 1/2"	0.32
TIP32a	0.74	3 1/2 x 5"	0.38
TIP41a	0.68	2 1/2" x 17"	0.95
TIP42a	0.74	3 1/2 x 17"	1.26
		Plus 25 pence pack	
			0.15

SPECIAL OFFER continued while stocks last

NESS5
Price each 0.49
POTENTIOMETERS—CARBON TRACK
Lin. or Log. 1" Bush—Spindle 2" F.M.F.
5K to 2 Meg Single with D/P sw. 0.32 ea.
5K to 2 Meg Dual 0.42 ea.
10K to 2 Meg Dual with D/P sw. 0.62 ea.
Log. only

T.T.L.'s	Price ea.	T.T.L.'s	Price ea.
7400/1/2/3	0.14	74154	1.68
7404/5	0.18	74191/2/3	1.28
7406/7	0.38	74196/7	1.20
7408	0.15		
7409	0.15		
7416/7	0.34		
7423/5/7	0.37		
7428	0.38		
7432/3	0.38		
7438	0.27		
7441/2AN	0.75		
7470/72	0.27		
7473/74	0.32		
7475	0.47		
7480	0.44		
7482	0.75		
7483	0.83		
7484	0.90		
7486	0.37		
7490	0.47		
7491AN	0.80		
74119	1.68		
74141	0.90		


I.C. SOCKETS	DIL	QUL	DIODES
8 pin	0.14	14 pin	1N914/
14 pin	0.15	16 pin	1N4148
16 pin	0.17		1N4001/8
			0.05
			0.08

SPEAKERS	Price ea.
7" x 4" FANE	0.80
3-8-16 ohm	1.68
	0.95 each


Send for FREE CATALOGUE. Listing over 2,000 items. S.A.E. please. Quantity Discounts

BRIDGE RECTIFIERS
p.v. 1A 2A 4A 6A
50v 0.20 0.30 0.45 0.55
100v 0.20 0.38 0.48 0.58
200v 0.25 0.40 0.54 0.68
400v 0.43 0.60 0.78
600v 0.25 0.45 0.70 0.87

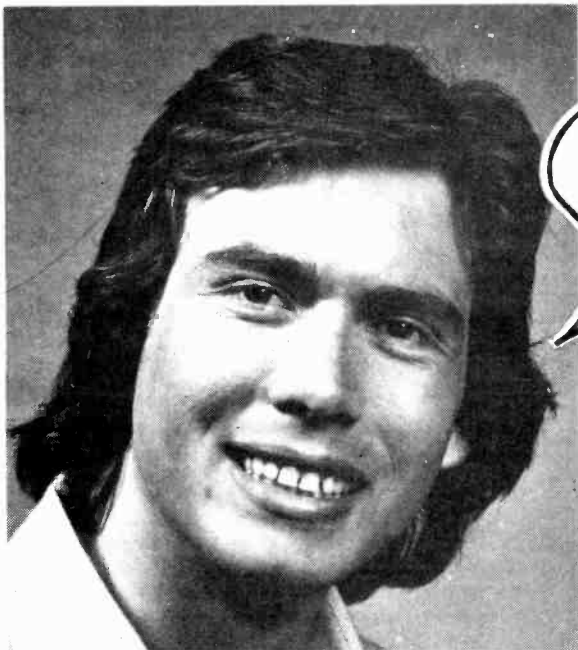DEPT. W.6, 299/301 BALLARDS LANE, LONDON N12 8NP
MAIL ORDER ONLY. Cash with order. Orders under £3 plus 15p. P. & P. Add VAT to total



The world's
DEAREST
Catalogue?

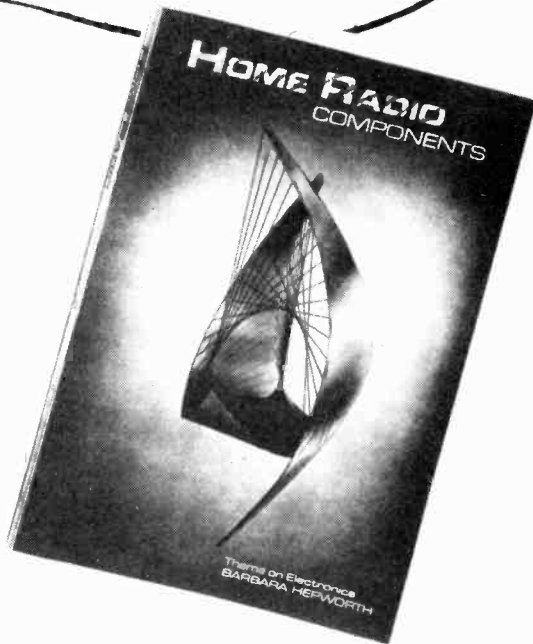

When I told a pal of mine that the Home Radio Components catalogue costs 65 pence plus 33 pence for postage and packing, he whistled through his teeth and exclaimed "It must be the world's most expensive catalogue!"

He changed his tune though when I showed him my copy and he compared it with the lower priced catalogues he'd already bought. He even finished up by admitting "The dearest is the cheapest in the end". Well, that old saying certainly sums it up as far as catalogues are concerned.

With its 240 pages, giving over 6,000 items clearly listed and profusely illustrated, the Home Radio Components catalogue certainly stands out head and shoulders above the rest. And when you remember that the catalogue includes 14 vouchers each worth 5 pence when used as instructed, enabling you to claw back 70 pence of your 98 pence, it's just about the best investment any keen electronics constructor could make. What's more, the catalogue is backed up

by a Mail Order Service that takes all the fuss and frustration out of component buying.

Why not prove it for yourself? Send off the coupon below with your cheque or postal order for 98 pence. Then you'll be able to boast to your friends that you own the world's cheapest dearest catalogue! Then, when they ask to borrow it, just let them have a tantalising glimpse—but make sure they send for their own!

65p. plus 33p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 98p.

The price of 98p applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME

ADDRESS

.....

HOME RADIO (Components) LTD., Dept. PW, (Regn. No. 234-240 London Road, Mitcham, Surrey CR4 3HD London 912966)



HOME RADIO (Components) LTD., Dept. PW, 234-240 London Road, Mitcham, CR4 3HD. Phone 01-648 8422

The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

AC107	0-22	AD161 & AD162(MP) 75	BC151	0-22	BD133	0-72	BF184	0-28	MJE3440	0-65	2G302	0-21	2N1893	0-41	2N3053	0-19	2N4058	0-18
AC113	0-20	AD1140	BC152	0-22	BD135	0-44	BF185	0-33	MPP102	0-48	2G303	0-21	2N2064	0-79	2N3054	0-51	2N4059	0-11
AC115	0-22	AD1140	BC153	0-31	BD136	0-44	BF187	0-30	MPP104	0-41	2G304	0-27	2N2148	0-63	2N3055	0-45	2N4060	0-18
AC117K	0-32	AD174	BC154	0-33	BD137	0-50	BF188	0-44	MPP105	0-41	2G306	0-44	2N2160	0-86	2N3091	0-16	2N4061	0-13
AC122	0-13	AF115	BC167	0-20	BD138	0-55	BF194	0-13	OC19	0-39	2G308	0-39	2N2192	0-39	2N3391A	0-18	2N4062	0-13
AC125	0-19	AF116	BC168	0-13	BD139	0-61	BF195	0-13	OC20	0-70	2G309	0-39	2N2193	0-39	2N3392	0-16	2N4064	0-19
AC126	0-19	AF117	BC169	0-13	BD140	0-66	BF196	0-16	OC22	0-52	2G339	0-22	2N2194	0-39	2N3393	0-16	2N4065	0-19
AC127	0-20	AF118	BC169	0-50	BD155	0-88	BF197	0-16	OC23	0-54	2G339A	0-18	2N2217	0-24	2N3394	0-16	2N4066	0-19
AC128	0-20	AF124	BC181	0-50	BD175	0-66	BF200	0-50	OC24	0-62	2G344	0-20	2N2218	0-22	2N3395	0-19	2N4067	0-19
AC132	0-16	AF125	BC167	0-13	BD176	0-66	BF222	£1.05	OC25	0-42	2G345	0-18	2N2219	0-22	2N3402	0-23	2N4068	0-19
AC134	0-16	AF126	BC168	0-13	BD177	0-72	BF257	0-50	OC26	0-32	2G371	0-18	2N2220	0-24	2N3403	0-23	2N4069	0-19
AC137	0-16	AF127	BC168	0-13	BD178	0-72	BF258	0-66	OC28	0-55	2G371B	0-18	2N2221	0-22	2N3404	0-31	2N4070	0-19
AC141	0-20	AF139	BC170	0-13	BD179	0-77	BF259	0-94	OC29	0-55	2G373	0-19	2N2222	0-22	2N3405	0-46	2N4091	0-19
AC141K	0-32	AF178	BC171	0-18	BD180	0-77	BF262	0-61	OC35	0-46	2G374	0-19	2N2268	0-18	2N3414	0-17	2N4292	0-19
AC142	0-20	AF179	BC172	0-16	BD183	0-72	BF263	0-81	OC36	0-58	2G377	0-19	2N2269	0-18	2N3415	0-17	2N4293	0-19
AC142K	0-28	AF180	BC173	0-18	BD186	0-72	BF270	0-39	OC39	0-39	2G378	0-18	2N2368A	0-18	2N3416	0-31	2N4297	0-13
AC151	0-17	AF181	BC174	0-16	BD187	0-77	BF271	0-33	OC42	0-27	2G381	0-18	2N2411	0-27	2N3417	0-31	2N5294	0-30
AC154	0-22	AF186	BC175	0-24	BD188	0-77	BF272	0-88	OC44	0-42	2G382	0-18	2N2412	0-27	2N3525	0-83	2N5457	0-35
AC155	0-22	AF239	BC177	0-21	BD189	0-83	BF273	0-39	OC45	0-14	2G401	0-33	2N2646	0-52	2N3614	0-74	2N5458	0-35
AC156	0-22	AL102	BC178	0-21	BD190	0-83	BF274	0-39	OC70	0-11	2G414	0-33	2N2711	0-23	2N3615	0-82	2N5459	0-34
AC157	0-27	AL103	BC179	0-21	BD195	0-94	BF270	0-66	OC71	0-11	2G417	0-23	2N2712	0-23	2N3616	0-82	2N6221	0-75
AC165	0-22	ASV26	BC180	0-27	BD196	0-94	BF279	0-30	OC72	0-16	2N388	0-39	2N2717	0-23	2N3701	0-10	2N8301	0-55
AC166	0-22	ASV27	BC181	0-27	BD197	0-99	BF284	0-24	OC74	0-16	2N388A	0-61	2N2904	0-19	2N3702	0-13	2N8302A	0-46
AC167	0-22	ASV28	BC182	0-16	BD198	0-99	BF285	0-33	OC75	0-17	2N404	0-22	2N2904A	0-23	2N3703	0-13	2N8302	0-46
AC168	0-27	ASV29	BC182L	0-18	BD199	£1.05	BF286	0-24	OC76	0-17	2N404A	0-81	2N2905	0-23	2N3704	0-14	2N8303	0-61
AC169	0-16	ASV30	BC183	0-16	BD200	£1.05	BF287	0-27	OC77	0-28	2N524	0-46	2N2905A	0-23	2N3705	0-18	2N8304	0-77
AC176	0-22	ASV51	BC183L	0-16	BD200	0-88	BF288	0-24	OC81	0-17	2N524	0-46	2N2906	0-16	2N3706	0-13	2N8305	0-86
AC177	0-27	ASV52	BC184	0-22	BD206	0-88	BF290	0-22	OC81D	0-17	2N598	0-46	2N2906A	0-20	2N3707	0-14	2N8306	0-86
AC178	0-31	ASV54	BC184L	0-22	BD207	£1.05	BF291	0-22	OC82	0-17	2N599	0-50	2N2907	0-22	2N3708	0-09	2N8307	0-86
AC179	0-31	ASV55	BC188	0-31	BD208	£1.05	BF292	0-22	OC82D	0-17	2N696	0-14	2N2907A	0-24	2N3709	0-10	2N8321	0-62
AC180	0-22	ASV56	BC187	0-31	BDY20	£1.10	BFY53	0-19	OC83	0-22	2N697	0-15	2N2923	0-16	2N3710	0-10	2N8322	0-46
AC180K	0-32	AC140	BC188	0-16	BF115	0-27	BFX19	0-17	OC139	0-22	2N698	0-27	2N2924	0-16	2N3711	0-10	2N8322A	0-48
AC181	0-22	ASV58	BC208	0-12	BF127	0-24	BFY59	0-61	OC140	0-22	2N699	0-39	2N2925	0-17	2N3819	0-11	2N8323	0-62
AC181K	0-32	ASV73	BC209	0-13	BF118	0-77	BFY25	0-17	OC169	0-09	2N706	0-09	2N2926(G)	14	2N3820	0-55	2N8324	0-77
AC187	0-24	ASZ21	BC212L	0-14	BF119	0-77	HSY26	0-17	OC170	0-28	2N706A	0-10	2N2926(Y)	12	2N3821	0-89	2N8325	0-62
AC187K	0-25	BC107	BC213L	0-14	BF121	0-50	HSY27	0-17	OC171	0-28	2N708	0-13	2N2926(O)	11	2N3823	0-81	2N8326	0-77
AC188	0-24	BC107	BC214L	0-18	BF123	0-55	HSY28	0-17	OC200	0-28	2N711	0-33	2N2926(R)	11	2N3823	0-81	2N8327	0-77
AC188K	0-25	BC109	BC205	0-28	BF125	0-50	HSY29	0-17	OC201	0-31	2N717	0-39	2N2926(B)	11	2N3824	0-33	2N8327A	0-46
AC189	0-20	BC113	BC217	0-11	BF126	0-55	HSY30	0-20	OC202	0-31	2N717	0-27	2N2926(C)	11	2N3825	0-77	2N8328	0-62
AC189K	0-20	BC114	BC230	0-30	BF127	0-55	HSY31	0-17	OC203	0-31	2N718	0-27	2N2926(D)	11	2N3826	0-33	2N8329	0-62
AC197	0-28	BC113	BC226	0-29	BF128	0-61	HSY32	0-17	OC204	0-33	2N719	0-27	2N2926(E)	11	2N3827	0-33	2N8330	0-62
AC197K	0-28	BC114	BC230	0-30	BF129	0-61	HSY33	0-17	OC205	0-28	2N726	0-31	2N2926(F)	11	2N3828	0-33	2N8331	0-62
AC199	0-22	BC116	BC202	0-27	BF133	0-50	HSY40	0-31	OC204	0-28	2N726	0-31	2N2926(G)	11	2N3829	0-33	2N8332	0-62
AC199K	0-22	BC116	BC303	0-35	BF154	0-50	HSY41	0-31	OC205	0-39	2N727	0-31	2N2926(H)	11	2N3830	0-33	2N8333	0-62
AC199L	0-22	BC117	BC304	0-40	BF155	0-77	HSY45	0-14	OC309	0-44	2N743	0-22	2N2926(I)	11	2N3831	0-33	2N8334	0-62
AC199M	0-22	BC118	BC340	0-40	BF156	0-53	HSY50A	0-14	OC309	0-44	2N744	0-22	2N2926(J)	11	2N3832	0-33	2N8335	0-62
AC199N	0-22	BC119	BC340	0-40	BF156	0-53	HSY50A	0-14	OC309	0-44	2N744	0-22	2N2926(K)	11	2N3833	0-33	2N8336	0-62
AC199O	0-22	BC120	BCY30	0-27	BF157	0-61	Bu105	£2.20	ORP12	0-48	2N914	0-48	2N2926(L)	11	2N3834	0-33	2N8337	0-62
AC199P	0-22	BC121	BCY31	0-28	BF158	0-61	CI11E	0-55	ORP60	0-44	2M918	0-33	2N2926(M)	11	2N3835	0-33	2N8338	0-62
AC199Q	0-22	BC122	BCY32	0-28	BF159	0-66	C400	0-33	ORP61	0-44	2M919	0-33	2N2926(N)	11	2N3836	0-33	2N8339	0-62
AC199R	0-22	BC123	BCY33	0-33	BF160	0-44	C407	0-28	P20	0-28	2N930	0-23	2N2926(O)	11	2N3837	0-33	2N8340	0-62
AC199S	0-22	BC124	BCY34	0-28	BF162	0-44	C424	0-28	P346A	0-44	2N1131	0-22	2N2926(P)	11	2N3838	0-33	2N8341	0-62
AC199T	0-22	BC125	BCY70	0-18	BF164	0-44	C425	0-55	P997	0-46	2N1132	0-24	2N2926(Q)	11	2N3839	0-33	2N8342	0-62
AC199U	0-22	BC126	BCY71	0-22	BF164	0-44	C426	0-38	ST140	0-14	2N1302	0-16	2N2926(R)	11	2N3840	0-33	2N8343	0-62
AC199V	0-22	BC127	BCY72	0-16	BF165	0-44	C428	0-22	ST141	0-19	2N1303	0-16	2N2926(S)	11	2N3841	0-33	2N8344	0-62
AC199W	0-22	BC128	BCZ10	0-22	BF167	0-24	C441	0-33	TP129	0-48	2N1304	0-19	2N2926(T)	11	2N3842	0-33	2N8345	0-62
AC199X	0-22	BC129	BCZ11	0-28	BF173	0-24	C442	0-20	TP130	0-56	2N1305	0-19	2N2926(U)	11	2N3843	0-33	2N8346	0-62
AC199Y	0-22	BC130	BCZ12	0-28	BF176	0-39	C444	0-39	TP131A	0-60	2N1306	0-23	2N2926(V)	11	2N3844	0-33	2N8347	0-62
AD130	0-42	BC142	BC115	0-88	BF177	0-39	C450	0-24	TIP32A	0-73	2N1307	0-23	2N2926(W)	11	2N3845	0-33	2N8348	0-62
AD140	0-53	BC143	BD116	0-88	BF178	0-33	MAT100	0-21	TIP41A	0-73	2N1308	0-26	2N2926(X)	11	2N3846	0-33	2N8349	0-62
AD142	0-53	BC145	BD121	0-66	BF179	0-33	MAT101	0-22	TIP42A	0-88	2N1309	0-26	2N2926(Y)	11	2N3847	0-33	2N8350	0-62
AD143	0-42	BC146	BD123	0-72	BF180	0-33	MAT102	0-21	TIS43	0-34	2N1613	0-22	2N2926(Z)	11	2N3848	0-33	2N8351	0-62
AD149	0-55	BC147	BF181	0-33	MAT103	0-21	TIS44	0-34	UT46	0-80	2N1711	0-32	2N2926(AA)	11	2N3849	0-33	2N8352	0-62
AD161	0-39	BC149	BF182	0-44	MJE2955	0-85	ZB14	£1.20	2N1859	0-55	2N1859	0-55	2N2926(AB)	11	2N3850	0-33	2N8353	0-62
AD162	0-39	BC150	BF183	0-44	MJE3055	0-82	2G302	0-21	2N1890	0-50	2N1890	0-50	2N2926(AC)	11	2N3851	0-33	2N8354	0-62

DIODES AND RECTIFIERS

AA119	0-09	BY128	0-17	OA10	0-16
AA120	0-09	BY130	0-18	OA17	0-08
AA129	0-09	BY133	0-23	OA70	0-08
AA					

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed
Pak No. EQVT
T1 8 2G3713 OC71
T2 8 D1374 OC75
T3 8 D1216 OC81D
T4 8 2G381T OC81
T5 8 2G382T OC82
T6 8 2G344B OC44
T7 8 2G345B OC45
T8 8 2G378 OC78
T9 8 2G399A 2N1302
T10 8 2G417 AF17
All 54p each pak

ND 120 NIXIE DRIVER TRANSISTOR.
Suitable replacement for BSX 21, C. 407, 2N 1893 120voh.

1 25 100+
0.19 0.17 0.16

Sil. trans. suitable for P.E. organ. Metal to 18 Eqty. ZTX300 6p each. Any Qty.

GP 100 TO3 METAL CASE GERMANIUM
Vbe = 100V. Vceo = 50V. I.C. = 10 amps. Ptot = 30W. hfe = 30-170.
Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1 25 100+
0.47 0.44 0.40

GP 800 TO3 METAL CASE SILICON
Vbe = 100V. Vceo = 60V. I.C. = 15 amps. Ptot = 115W. hfe = 20. 100fT = 1MHz. Suitable replacement for 2N 3055, BDY 11 or BDY 20.

1 25 100+
0.55 0.53 0.51

NEW 9th EDITION
Over 300 pages
TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. £2.30 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

2 Amp. BRIDGE RECTS.
50 v RMS 35p each
100 v RMS 40p ..
200 v RMS 45p ..
400 v RMS 50p ..
1,000 v RMS 55p ..
Size 16 mm x 16 mm.

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N708/8. BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20 For 0.54
50 For 1.08
100 For 1.92
500 For 8.25
1000 For 14.30

SIL. G.P. DIODES 5p
300mW 30 0.55
40PIV(Min.) 100 1.85
Sub-Min. 500 5.50
Fully Tested 1,000 9.90
Ideal for Organ Builders.

AD161/162
M/P COMP GERM. TRANS. OUR LOWEST PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS ADVERTISEMENTS PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-38V. 400mW (DO-7 Case) 9p ea. 11W (Top-Hat) 18p ea. 10W (SO-10 Stud) 35p ea.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Price	
Q1	20 Red spot transistors PNP	0.54
Q2	16 White spot R.F. transistors PNP	0.54
Q3	4 OC 77 type transistors	0.54
Q4	6 Matched transistors OC44/45/81/81D	0.54
Q5	4 OC 75 transistors	0.54
Q6	5 OC 73 transistors	0.54
Q7	4 AC 128 transistors PNP high gain	0.54
Q8	4 AC 126 transistors PNP	0.54
Q9	7 OC 81 type transistors	0.54
Q10	7 LC 71 type transistors	0.54
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0.54
Q12	3 AF 116 type transistors	0.54
Q13	3 AF 117 type transistors	0.54
Q14	3 OC 171 H.F. type transistors	0.54
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0.54
Q16	5 NPN 2x BT. 141 & 3x ST. 140	0.54
Q17	4 MADDTS 2x MAT 100 & 2x MAT 120	0.54
Q19	3 MADDT's 2x MAT 101 & 1x MAT 121	0.54
Q20	4 OC 44 Germanium transistors A.P.	0.54
Q21	4 AC 127 NPN Germanium transistors	0.54
Q22	20 NKT transistors A.F. R.F. coded	0.54
Q23	10 OA 292 Silicon diodes sub-min	0.54
Q24	8 OA 81 diodes	0.54
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0.54
Q26	8 OA95 Germanium diodes sub-min IN 69	0.54
Q27	2 10A PIV Silicon rectifiers IS425R	0.54
Q28	2 Silicon power rectifiers BYZ 13	0.54
Q29	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0.54
Q30	7 Silicon switch transistors 2N706 NPN	0.54
Q31	6 Silicon switch transistors 2N708 NPN	0.54
Q32	3 NPN Silicon transistors 2x 2N1131, 1x 2N1132	0.54
Q33	3 Silicon NPN transistors 2N1171	0.54
Q34	7 Silicon NPN transistors 2N2369, 600MHz (code P997)	0.54
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N905	0.54
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0.54
Q37	3 2N3055 NPN Silicon transistors	0.54
Q38	7 NPN transistors 3x 2N3703, 2x 2N3702	0.54

555 I.C. 65p each

All prices include V.A.T.
MAMMOTH I.C. PACK
APPROXIMATELY 200 PIECES ASSORTED MANUFACTURERS FALL-OUT INTEGRATED CIRCUITS INCLUDING LOGIC 74 SERIES LINEAR and AUDIO AMPLIFIERS MANY CODED ALSO SOME UNKNOWN TYPES - YOU TO IDENTIFY
PAK NO. M.I.C. 200
PRICE £1.25 per PAK including p & p & V.A.T.

1975 CATALOGUE NOW READY 10p

NEW LOW PRICED TESTED S.C.R.'s

P1V	4A	5A	5A	7A	10A	16A	30A
T05	T06	T06	T06	T04	T04	T04	T04
50	0.28	0.28	0.39	0.39	0.52	0.55	0.59
100	0.28	0.37	0.52	0.52	0.62	0.64	0.70
200	0.39	0.41	0.54	0.54	0.63	0.67	0.83
400	0.48	0.52	0.62	0.62	0.74	0.83	1.03
600	0.59	0.63	0.75	0.75	0.85	1.07	1.38
800	0.70	0.77	0.88	0.88	0.99	1.32	1.65

2N3055
115 WATT SIL POWER NPN 45p EACH

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.54
U 2	60 Mixed Germanium Transistors AF/RF	0.54
U 3	75 Germanium Gold Bonded Sub-Min. like OA6, OA47	0.54
U 4	40 Germanium Transistors like OC91, AC128	0.54
U 5	60 200mA Sub-Min. Silicon Diodes	0.54
U 6	30 Sil. Planar Trans. NPN like BSY95A, 2N706	0.54
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000V	0.54
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.54
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.54
U10	20 BAY56 charge storage Diodes DO-7 Glass	0.54
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.54
U13	30 PNP-NPN Sil. Transistors OC200 & 2N 104	0.54
U14	150 Mixed Silicon and Germanium Diodes	0.54
U15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0.54
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.54
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.54
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.54
U19	25 Silicon NPN Transistors like BC108	0.54
U20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.54
U21	30 AF Germanium Alloy Transistors 2G300 Series & OC71	0.54
U23	30 MADDT's like MHz Series PNP Transistors	0.54
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.54
U25	25 300 MHz NPN Silicon Transistors 2N708, BBY27	0.54
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.54
U29	10 1 Amp SCR's TO-6 can, up to 600 PIV CR81/25-600	1.08
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0.54
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.54
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0.54
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.54
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0.54
U37	30 Silicon Alloy Transistors 80-2 PNP OC200, 28322	0.54
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.54
U39	30 R.F. Germ. PNP Transistors 2N1903/5 TO-5	0.54
U40	10 Dual Transistors 6 lead TO-5 2N2060	0.54
U43	25 Sil. Trans. Plastic TO-18 AF. BC113/114	0.54
U44	20 Sil. Trans. Plastic TO-5 BC115/116	0.54
U45	7 3A SCR, TO66 up to 600PIV	1.08
U46	20 Unijunction transistors similar to T1848	0.54
U47	10 TO220AB plastic triacs 50V 6A	£1.08
U48	9 NPN Sil. power transistors like 2N3055	£1.08
U49	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	£1.08

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

FREE
One 55p Pak of your own choice free with orders valued £4 or over

SIL. RECTS. TESTED
PIV 300mA 750mA 1A 1.5A 3A 10A 30A

50	0.05	0.06	1N4001	0.05	0.08	0.15	0.21	0.60
100	0.05	0.07	1N4002	0.06	0.10	0.17	0.23	0.75
200	0.06	0.10	1N4003	0.07	0.12	0.22	0.25	0.80
400	0.08	0.15	1N4004	0.08	0.16	0.30	0.38	1.35
600	0.09	0.17	1N4005	0.10	0.18	0.38	0.45	1.95
800	0.12	0.19	1N4006	0.11	0.20	0.38	0.55	2.10
1000	0.14	0.30	1N4007	0.12	0.25	0.48	0.65	2.50
1200	-	10.35	-	-	0.30	0.58	0.75	3.00

CADIUM CELLS
ORP12 48p

DIACS FOR USE WITH TRIACS. BR100 (D32) 25p each

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each

TRIACS			
VBOM	2A	6A	10A
TO-5	TO-66	TO-104	
100	3p	5p	8p
200	5p	6p	9p
400	7p	8p	12p

Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS
Postage and packing add 20p. Overseas add extra for airmail.
Minimum order 55p. Cash with order please.
Guaranteed Satisfaction or Money Back




TRAMPUS

Electronics Ltd.
WINDSOR, BERKS.
58/60 GROVE RD
SEND C.V.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 80p.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS, LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. GALLERY WELCOME.
CATALOGUE/LIST FREE SEND S&S
BARCLAYCARD & ACCESS N POST.

Digital Displays

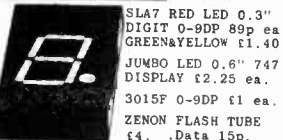

LEDS red 13P

SIAT RED LED 0.3" DIGIT 0-9DP 89p ea
GREENYELLOW £1.40
JUMBO LED 0.6" 747
DISPLAY £2.25 ea.
3015F 0-9DP £1 ea.
ZENON FLASH TUBE
£4. Data 15p.

PHOTO IC 81P

TEC12 PHOTO AMP/SCHMITT/RELAY
DRIVER OF LED TTL INTERFACE 81P



FLUORESCENT LIGHTS 12V MADE IN UK
8 WATT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MMS311/4 6 DIGIT CLOCK £7

CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder
with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 DIL14 29p	LM377 2x2Wf2.87
555 TIMER 54p	LM380 2W AF 89p
703 RF/IF 28p	LM381 2xPre £2
709 T099 29p	LM3900 4xOPA69p
710 DIL 14 28p	MC1303 £1.20
720 DIL 14 34p	MC1308 49p
723 Reg. 54p	MC1310LEdf2.65
741 DIL 8 27p	MC1312 SQ £2.10
741 DIL 14 29p	MC1330 69p
741 T099 29p	MC1339 2xPre £1
747 2x741 70p	MC1350 55p
748 DIL 8 33p	NE536 fetOPA £1
7805 5V £1.40	NE540 Driver £1
7812 & 15 £1.40	NE550 2vRef 79p
78013 6W AF £1	NE555 Timer 55p
8038 SIG GEN £3	NE556 2x £1.20
CA3028 £1	NE560 PLL £3.15
CA3046 55p	NE561 PLL £3.15
CA3048 £2	NE562 PLL £3.19
CA3052 £1.50	NE565 PLL £2.69
CA3054 £1	SN72709 709 28p
LM300 2-20V £2	SN72741 741 26p
LM301 OPA 45p	SN72748 748 33p
LM304 0-40V £3	SN76660 IF £1
LM307 OPA 49p	SN76611 IFF1.25
LM308 HIBO 95p	TAD110 & IF £2
LM309K 5V £1.48	TBA810 7WAF 99p
LM372 IF £1.80	ZN414 RX £1.09

SPECIAL OFFERS
2N3055 FULL HIGH SPEC 115W 37p
741C 8PIN DIL 27p. MFC4000B 33p
NE555 TIMER 55p. ZN414 RX £1.09
BC109 9p. 2N3819e 16p. BFY51 15p

74N TTL

7400 GATES 13p	7473/74/76 29p
7404 INVERT 17p	7475 45p
7401/2/10etc14p	7490 52p
7413 SCHMITT 31p	7491/2/3/4 59p
7440 BUFFER 14p	74100 74175 £1
7447 DRIVER 89p	74121 32p
7470 & 7472 29p	74123 59p
	74141(&7441)73p

TRANSISTORS & DIODES

Price each	
AC127 & 128 16p	
AC187 & 188 19p	
AD149 43p	
AD161 & 162 33p	
BC107 & 108 9p	
BC109 10p	
BC147/8/9 10p	
BC157/8/9 12p	
BC167/8/9 12p	
BC177/8/9 18p	
BC182/3/4A&L10p	
BC212/3/4A&L11p	
BCY70/1/2 17p	
BD131 & 132 39p	
BRF51	
BRF50/51 23p	
BRF50/51 23p	
BRF88 250V 29p	
BFY50/1/2 15p	
BX19/20/21 16p	
MJE2955 90p	
MJE3055 65p	
MPU131 PUT 49p	
OA91 OA81 6p	
OA81 & OA91 6p	
TIP 29 & 30 52p	
TIP 31 & 32 69p	

vero

VERO PINSx36 28p.
COPPER CLAD VEROBOARD 0.1"
2 1/2"x5" 29p 2 1/2"x3 1/2" 26p. 3 1/2"x3 1/2" 31p.
3 1/2"x5" 31p 3 1/2"x 1 7/8" £1.50
DIL IC'S BOARDS 6x4 1" £1.50
24 way edge connector 80p.
36 way edge connector PLAIN 3 1/2"x1 7/8" £1.
FACE CUTTER 45p. FEC ETCH PAK 50p

DALOpen69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK NPW 69p
DECON DESOLDER BRAID REEL 59p

HEATSINKS

5F/T05 & 18F/T018 5p ea. TV4 15p.
TV3/T03 16p. EXTRUDED 4" 4Y1 29p.

TGS308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 uf 1n
10v 5p 25v 6p. 50v 8p. 2uf/10v 5p.
1000 uf/25v 18p. 200/500 25v 9p.

POTENTIOMETERS (POTS) AB or EGIN

LTN or LOG ROTARY 13p. SWITCH 14p
DUAL 45p. SLIDERS 29p. STEREO 57p
KNOBS 7p. PRESETS 6P. RESISTORS 14p

SWITCHES: SPST 18p. DPDT 25p.

DIN PLUGS ALL 12P. SOCKETS 10P.
ALI CASES AB5/AB7 50p. AB13 65p.
TRANSFORMERS 1A 6v6v or 12v12v
Only £1.34. 100mA type CT 75p.


Oil sockets

TEXAS GOLD
LOW PROFILE ea
8, 14, & 16 PIN 13p
SOLDERCON STRIPS:
100 PINS 50p. 1K £3.

NEW TRAMPUS FULL SPEC PAKS

PAK A 10 RED LEDS our choice £1
PAK B 4 741 OP AMP " £1
PAK C 4 2N3055 £1. D 12 BC109 £1
PAK E 10 BC182 £1. F 11 2N3704 £1
PAK G 8 BFY51 £1. H 9 2N3819e £1
PAK J 9 2N3053 £1. K 40 1N914 £1

LOWE ELECTRONICS

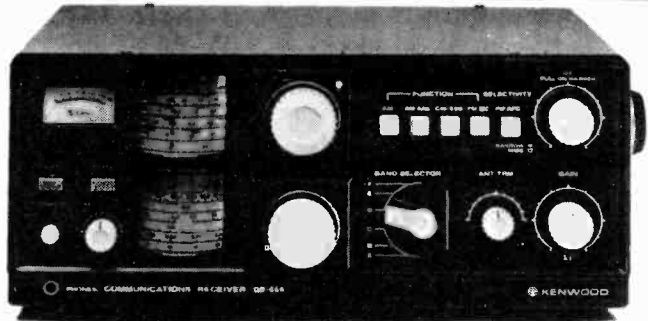

SPECIFICATION 170-410
Frequency coverage 170-410kHz, 525-1250kHz, 1.25-3.0MHz,
3-7.5MHz, 7.5-18MHz, 18-30MHz (Dual conversion)
Bandspread 3-4MHz, 7-7.5MHz, 14-14.6MHz, 21-21.5MHz
(Dual conversion), 28-30MHz (Dual conversion)
Modes AM, USB, LSB, CW
Selectivity 2 position wide/narrow
Antenna 50-100Ω
Sensitivity 1uV for 10dB S/N (SSB/CW)
AF Output More than 1.5W into 8Ω. Internal speaker fitted
Power supply 100/117/220/240V ac 50/60Hz. External 12V dc.
Internal 12V batteries. Automatic changeover to
internal supply in the event of mains failure
Dimensions (mm) 362 wide x 163 high x 322 deep
Weight 7.3kg (16.09 lbs)
Options 500kHz marker QR6MK, FM broadcast tuner
QR6FM

An all new receiver from the TRIO company providing general coverage reception 170kHz to 30MHz with calibrated bandspread for the amateur bands. Dual-gate MOSFETS for RF and mixer stages ensure high gain, good selectivity and first class A.G.C. characteristics.
Dual position selectivity gives two bandwidths to cater for all band conditions.
Use the QR666 at home, in the car or boat or truly portable; all catered for by the exclusive 3-way power supply.
PRICE £130 (VAT excl)

We stock a great many products apart from those advertised month by month—everything in fact for the radio amateur operator. If you need more information, our complete catalogues are available free to callers. If you require them sending by mail, postal charges being what they are today, please send us 20p in stamps because that's what it costs to send them to you!

HEAD OFFICE
BRANCH OFFICES
AGENTS

119 Cavendish Road, Matlock, Derbyshire. Tel. 2817 or 2430 9 a.m. to 9 p.m.
Goring Road, Steyning, Sussex. Tel. Steyning 814466
Soho House, 362-4 Soho Road, Handsworth, Birmingham. Tel. 021-554 0708
Alan GW3YSA, 35 Pen-Y-Waun, Efail Isaf, Nr. Pontypridd. Tel. Newton Llantwit 3809
John G3JYG, 16 Harvard Road, Ringmer, Lewes, Sussex. Tel. Ringmer 812071
Sim GM3SAN, 19 Ellismuir Road, Baillieston, Nr. Glasgow. Tel. 041-771 0364


OPENING HOURS: 9-5.30 TUESDAY TO SATURDAY INCLUSIVE

73 from BILL G3UBO/VEBDP, ALAN G3MME, JOHN G3PCY/5N2AAC, IAN G3ZYC




I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

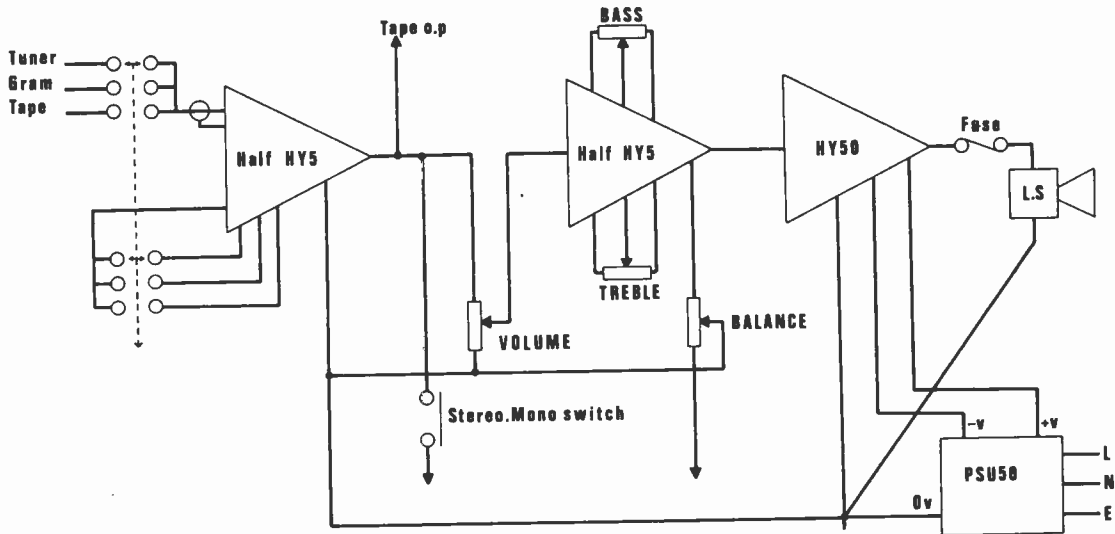

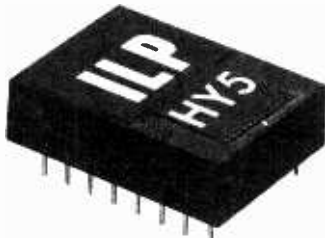MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier. Ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION
Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3-100mV; input/impedance 47kΩ at 1kHz. Outputs: Tape 100mV; Main output 0db (0-775V RMS). Active Tone Controls: Treble ± 12db at 10kHz; Bass ± 12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: ± 10-25V.


PRICE £4.50 + 36p VAT
P. & P free



The HY50 is a complete solid state hybrid HI-FI amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION
Output Power: 25W RMS into 8Ω. Load Impedance: 4-16Ω. Input Sensitivity 0db (0-775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ± 3db. Supply Voltage: ± 25V. Size: 105 x 50 x 25mm.

PRICE £5.98 + 48p VAT
P. & P. free

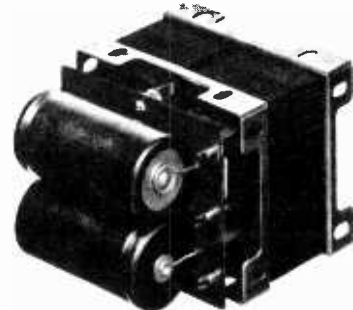

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS
Output voltage: 50V (25-0-25V). Input Voltage: 210-240V.
Size: L.70. D.90. H.60mm.

PRICE £6 + 48p VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD

Tel (0227) 63218

Regd. V.A.T. No. 202141535

Please supply,

Total Purchase price

I Enclose, Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name & Address

Signature



GIRO NO. 331 7056. Access accepted.
C.V.O. only p & p 10p on orders below £5
Discount: £10-10%, £10-15% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT AT 8%

SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.95 net
25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
5E12 1/2W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £3.45 net

Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3µF, 0.068µF
0.1µF, 4µF, 0.15µF, 5p, 0.22µF, 6p, 0.33µF, 8p, 0.47µF, 10p, 0.68µF, 13p 1µF, 16p, 1.5µF, 24p, 2.2µF, 27p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 3p, 0.0068µF, 0.01µF, 4p
0.015µF, 0.022µF, 0.033µF, 5p, 0.047µF, 0.068µF, 0.1µF, 4µF, 0.15µF, 5p
0.22µF, 6p, 0.33µF, 8p, 0.47µF, 10p
160V: 0.01µF, 0.015µF, 0.022µF 3µF, 0.047µF, 0.068µF, 4p, 0.1µF, 4µF, 0.15µF, 5p
0.22µF, 6p, 0.33µF, 7p, 0.47µF, 9p, 0.68µF, 13p, 1µF, 15p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 2µF each. 0.1, 30V, 5p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 4µF.

RESISTORS
CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%
W. Type Range 1-99 100-999 500-999 1000+ Size mm
+ CF 22-1M 1 0.80 0.80 0.60 2.4x7.5
+ CF 22-2M2 1 0.40 0.65 0.60 3.9x10.5
+ CF 22-1M 1 0.80 0.65 0.60 5.5x16
+ MF 10-2M7 2 1.7 1.4 1.2 3x7
+ MF 10-2M2 2 1.6 1.3 1.1 4.2x10.8
+ MF 10-10M 3 1.98 1.81 1.65 6.6x13
2 MF 10-10M 4.5 3.52 3.08 2.75 8x17.5

(Price in pence each)

VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS
MINIATURE 0.25W Vertical or horizontal 7p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 7p each.

B. H. COMPONENT FACTORS LTD. (P.W.) LEIGHTON ELECTRONICS CENTRE, 59 NORTH ST., LEIGHTON BUZZARD, BEDS. Tel.: LEIGHTON BUZZARD 2316 (STD. Code 05253) CATALOGUE No. 4 20p

Miniature Mullard Electrolytics

1.0µF 63V	7p	100µF 25V	7p
1.5µF 63V	7p	100µF 63V	17p
2.2µF 63V	7p	150µF 16V	7p
3.3µF 63V	7p	150µF 63V	17p
4.0µF 40V	7p	220µF 6.4V	7p
4.7µF 63V	7p	220µF 10V	7p
6.8µF 63V	7p	220µF 16V	8p
10µF 25V	7p	220µF 63V	25p
10µF 63V	7p	330µF 16V	14p
15µF 16V	7p	330µF 63V	24p
15µF 63V	7p	470µF 6.4	8p
16µF 40V	7p	470µF 40V	25p
22µF 25V	7p	680µF 16V	17p
22µF 63V	7p	680µF 40V	28p
33µF 10V	7p	1000µF 16V	28p
33µF 16V	7p	1000µF 25V	28p
33µF 40V	7p	1500µF 6.4V	17p
47µF 10V	7p	1500µF 16V	28p
47µF 25V	7p	2200µF 10V	28p
47µF 63V	7p	3300µF 6.4V	28p
68µF 16V	7p		
100µF 10V	7p		

VEROBOARD 0.1 0.15

24 x 5"	36p	36p
24 x 3 1/2"	33p	25p
34 x 5 1/2"	42p	46p
34 x 3 1/2"	36p	36p
24 x 1 1/2"	10p	9p
24 x 5" (Plain)	—	19p
24 x 3 1/2" (Plain)	—	16p
5 x 3 1/2" (Plain)	—	29p
Insertion tool	73p	73p
Track Cutter	56p	56p
Pins, Pkt. 50	22p	22p

TRANSISTORS

AC127	21p	BC212L	13p
AC128	22p	BC213L	13p
BC107	12p	BC214L	18p
BC108	12p	OC44	19p
BC109	13p	OC71	13p
BC148	13p	OC81	17p
BC149	13p	OC170	29p
BC182L	13p	2N2926	13p
BC183L	13p	2N3702	14p
BC184L	14p		

POTENTIOMETERS
Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 17p Dual Gang 48p. Log single with switch 28p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p, 45mm, 47p, 60mm, 55p.

DIODES

IN4001 6p	DIN 2 Pin	12p
IN4002 7p	3 Pin	13p
IN4003 9p	5 Pin 180°	16p
IN4004 9p	Std. Jack	20p
IN4005 12p	2.5mm Jack	13p
IN4006 14p	Phono	7p
IN914 7p	DIN 2 Pin	10p
IN916 7p	3 Pin	10p
EA100 10p	5 Pin 180°	12p
OA47 9p	Std. Jack	18p
OA81 11p	2.5mm Jack	13p
OA200 8p	Phono	7p

PLEASE NOTE OUR NEW ADDRESS
Our new Electronics Centre is now open in Leighton Buzzard and all callers are welcome. As well as our normal stock of over 2000 product lines, we have a large range of surplus equipment, Bargains, Calculators, etc. **OPEN 6 DAYS 9 to 5** (shut 12.30 to 1.30).

ELECTROLYTIC CAPACITORS: Tubular & Large Cans
(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 7p, 50/50, 8p, 100/50, 200/25, 10p, 250/50, 18p, 500/10, 8p, 500/25, 17p, 500/50, 25p, 1000/10, 0.17p, 1000/25, 25p, 1000/50, 40p, 2000/10, 20p, 1000/100, £1.10, 2000/25, 35p, 2000/100, £1.20, 2500/25, 38p, 2500/50, 68p, 5000/25, 69p, 5000/50, £1.20.

HI-VOLT: 4/350, 20p, 8/350, 23p, 100/100 27p, 16/350, 35p, 100/100, 27p, 100/250, 40p.

METALLISED PAPER CAPACITORS
250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7µF, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7µF, 0.5, 9p, 1000V: 0.01, 12p, 0.022, 13p, 0.047, 0.1, 19p, 0.22, 28p, 0.47, 36p.

NEW KIT
5E12 1W Metal Film.
5 each value 10Ω-1M,
total of 305 £3.75 net.

MULTIMETER U4323
22 Ranges plus AF/IF Oscillator 20,000Ω/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Vdc—0.05—500mA in 5 ranges
Resistance—5Ω—1MΩ in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465 KHz (A. M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £8.64 net p & p 50p.

MULTIMETER U4341
27 Ranges plus Transistor Tester. 16,700Ω/Volt. Overload protected.
Vdc—0.3—900V in 8 ranges.
Vac—1.5—750V in 6 ranges.
Idc—0.06—600mA in 5 ranges.
Iac—0.3—300mA in 4 ranges.
Resistance—2KΩ—2MΩ in 4 ranges.
Accuracy—dc—2%, ac—4% of F.S.D.
hfe—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11.88 net p & p 50p.

MULTIMETER U4313
33 ranges. Knife edge with mirror scale. 20,000Ω/Volt. High accuracy. mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2 ldc—0.6—1500mA in 6 ranges.
Iac—0.6—1500mA in 6 ranges.
Resistance—1KΩ—1MΩ in 4 ranges.
db scale—10 to +12db.
Accuracy—dc—1%, ac—2 1/2%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14.90 net p & p 50p.

NEW CAPACITOR KITS

C280 Kit—PC Mounting polyester 250V. 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22µF. 2 of 0.47, 1µF. £1.40 net.

C296 Kit—Tubular polyester, 400V. 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22µF. 2 of 0.47µF. £1.40 net.

Ceramic Kit—square plaquette 50V. 5 each value: 22, 33, 47, 100, 220, 330, 470, 1000pF, 2200, 4700pF, 0.01µF. £1.40 net.

250V Paper kit—Tubular metal case. 3 of each value: 0.05, 0.1, 0.25, 0.5, 1µF. £1.00 net.

500V Paper Kit—Tubular metal case. 3 of each value: 0.025, 0.05, 0.1, 0.25, 0.5µF. £1.00 net.

1000V Paper Kit—Tubular metal case. 3 each value: 0.01, 0.025, 0.05, 0.1µF. £1.20 net.

MULTIMETER U4324
34 Ranges. High sensitivity. 20,000Ω/Volt. Overload protected.
Vdc—0.6—1200V in 9 ranges.
Vdc—3—900V in 8 ranges.
Idc—0.6—3A in 6 ranges.
Iac—0.3—3A in 5 ranges.
Resistance—25Ω—5MΩ in 5 ranges.
Accuracy—dc and R—2% of F.S.D.
ac and db—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE £10.64 net p & p 50p.

MULTIMETER U4313
33 ranges. Knife edge with mirror scale. 20,000Ω/Volt. High accuracy. mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2 ldc—0.6—1500mA in 6 ranges.
Iac—0.6—1500mA in 6 ranges.
Resistance—1KΩ—1MΩ in 4 ranges.
db scale—10 to +12db.
Accuracy—dc—1%, ac—2 1/2%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14.90 net p & p 50p.

MULTIMETER U4325
32 Ranges. High Sensitivity 20,000Ω/Volt
Vdc—75mV—1000V in 8 rgs.
Vac—2.5—1000V in 7 rgs.
Idc—0.001—2.5A in 6 rgs.
Iac—0.005—2.5A in 5 rgs.
Resistance—3—300K in 3 rgs.
Capacitance scale 0.0—5µF Accuracy—
dc and R—2 1/2% of F.S.D.
ac and C—4% of F.S.D.
Size—205 x 116 x 84mm
COMPLETE WITH STEEL CARRYING CASE, TEST LEADS AND BATTERY
PRICE £9.45 net p&p 25p

S-DeC £2.18
T-DeC £4.00
µDeC "A" £4.39
µDeC "B" £7.69
2 DeC £4.72

ANTEX
CCN240 £2.87
CN240 £2.60
X25 £2.44

SEND NOW!
YOUR SINGLE WORKSHEET FOR THE EASY-BUILD ORGAN

We are the only manufacturers supplying the easy-build organ kit in full

Studio Electronics LTD

PO BOX 18 HARLOW CM18 6SH ESSEX
Tel: HARLOW (STD 0279) 416771
New catalogue now available on receipt of S.A.E.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEWEST! MODERN! TRY!

DISCOUNT PRICES

5 SIZES ALL INTERLOCK

Latest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. ID have space dividers. Build up any size cabinet for wall, bench or table top.

SINGLE UNITS (5" x 2 1/2" x 2 1/2") £2.00 Dozen
DOUBLE UNITS £3.50 Dozen. **TREBLE (3D)** £3.50 for 8
DOUBLE TREBLE £4.90 for 8.
EXTRA LARGE SIZE (6D) £4.50 for 8.

Carriage 50p. Orders over £10 please add 10% carr.
QUANTITY DISCOUNTS 5% in £1 for orders over £20
7 1/2% for orders over £60. Quotations for large quantities.
PLEASE ADD 8% VAT TO TOTAL REMITTANCE.
(Dept. PWT), 124 CRICKLEWOOD BROADWAY
LONDON N.W.2 01-450 4844
FLAIDLINE SUPPLIES

ALL OUR PRICES INCLUDE V.A.T.

£6-50 Post 45p.



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop complete with cartridge. Base-plate, Size 11in x 8in. Turntable. Size 7in. diameter. A/C mains. 200/250V motor has a separate winding 14 volt to power a small amplifier. Three speeds. Plays all records.

COMPLETE STEREO HI-FI

Two full size loudspeakers 18 1/2 x 10 x 3 1/2in. Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2 x 8 1/2 x 3 1/2in. 3 watts per channel. plays all records 33 rpm, 45 rpm Separate volumes & tone controls. 240V AC mains.



Attractive Teak Finish Weight 18lbs. Bargain Price **£29** 85p carriage

SPECIAL OFFER

SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES

Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home. Turn on or off at full or intermediate settings. Makers last list price £4-50. Brand new and fully guaranteed. Fully insulated. **OUR PRICE £2-60 Post 25p**



WEYRAD P50—TRANSISTOR COILS

RA2V Ferrite Aerial. 85p
I.F. P50/SCC 470 kc/s. 40p
3rd I.F. P50/SCC. 40p
Spares Cores. 8p
P50/AC. 60p
Ferrite Rod 8 x 1in. 20p 6 x 1in. 20p 3 x 1in. 10p

Printed Circuit. PCA1. 85p
J.B. Tuning Gang. £1-20
Weyrad Booklet. 10p
OPTI. 65p
Driver Trans. LFDT4. 65p

VOLUME CONTROLS

8 K. ohms to 2 Meg. LOG or LIN. L/S 20p. D.P. 85p.
STEREO L/S 65p. D.P. 75p.
Edge 5K.S.P. Transistor 25p

80 Ohm Coax 5p. rd.
BRITISH AERIALITE AERIAL-AIR SPACED 40yd. £2. 60yd. £3.
FRINGE LOW LOSS 10p yd.
Ideal 625 & colour

8in or 10 x 6in ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 c/s. Bass resonance 55 c/s. 8 ohm 10 watt. **£4-35** Each Post 40p



10 inch 12 watt Twin Cone, 8 ohm £5-20

E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With tweeter and crossover. 10 watt. State 3 or 8 or 15 ohm. (As illustrated) **£5-25** Post 35p

With fared tweeter cone and ceramic magnet. 10 watt. Base res. 45-80 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 35p **£3-45**

BOOKSHELF CABINET Size 18 x 10 x 7 in. teak finish **£7-50** Post 45p



E.M.I. 18 x 8 in. BASS WOOFER. 20 WATTS RUBBER CONE SURROUND. 85 50 Post 40p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides 6 x 4in. 45p; 9 x 6in. 55p; 10 x 7in. 65p; 12 x 8in. 85p; 14 x 9in. 90p; 16 x 9in. 90p; 12 x 8in. 65p; 16 x 10in. £1.

ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 15p; 8 x 6in. 18p; 10 x 8in. 20p; 10 x 7in. 24p; 12 x 6in. 25p; 12 x 8in. 24p; 16 x 6in. 24p; 14 x 9in. 40p; 12 x 12in. 47p; 16 x 10in. 60p

SPECIAL OFFER

100 ohm 20W Rheostat 2 1/2in. diam. Ceramic Former, screw terminals, 1in. diam. spindle. 85p, post 25p.

ANOTHER RGS BARGAIN!

ELAC 9 x 8in. HI-FI SPEAKER. TYPE 59RM. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE **£3.45**

4MFD 800V DC PAPER CAPACITOR
Block Capacitor. Ideal as Filter Unit in 100 watt Loudspeaker Systems. 95p each, post 30p.

GOODMANS CONE TWEETER

15'000 cps. 25 watts. 8 ohm. Price **£3 30**

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. A.C. operation. Size 1 1/2 x 1 1/2 x 1. Response 25 c/s to 25 Kc/s. 28 dB gain. For use with valve or transistor equipment. **£1.45** Post 20p
Full instructions supplied. Details S.A.E.

TRAKWOOD LOUDSPEAKER GRILLS. Will easily fit to baffle board. Size 18 1/2 x 10 1/2in.—75p. 10 1/2 x 7 1/2in.—45p.

E.M.I. WOOFER AND TWEETER KIT

Woofer 10 1/2 x 8in. Ceramic Magnet, 440x. 13,000 lines. Tweeter 8 1/2in. square, 10,000 lines. Crossover condenser full instructions supplied. Impedance 8 ohms. Power 12 watts. **£6-75** Post 45p.

BRITISH FM/YHF TUNING HEART

88 to 108 MC/S British made. 2 Transistors ready aligned requires 10-7 MC/S I.F. Complete with tuning fork. Connections supplied, but some technical experience essential. **Our price £3-95** 10-7 MC/S IF Strip £4-95
DECODER = £4-75

MAINS TRANSFORMERS

250-0-250 80 mA. 6-3V 2amp	All post 25p each
250-0-250 80 mA. 6-3V 1A or 5V 2A	£2-60
250-0-250 80 mA. 6-3V 3A, 6-3V 1A or 5V 2A	£4-60
300-0-300V 120mA. 6-3V 4A C.T.; 3-3V 2A	£7-00
MIDGET 220V 45mA. 6-3V 2A	£1-75
HEATER TRANS. 6-3V 1 amp 85p. 3 amp £1-20	

GENERAL PURPOSE LOW VOLTAGE. Trapped outputs at 8 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £4-60
1 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60 £4-60
3 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60 £7-00
5 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60 £8-70
5 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60 £11-25
6-0-6V 500mA 90p. 20V 1A £1-85
9V 1 amp 95p 12V 300mA 75p 12V 100mA 85p 12V 750mA 85p
9V 1.5 amp 30.40V 2 amp £2. 20V 3 amp £2. 40V 3A £2-50.
22-0-22V 1A £2. 16V 1 amp 85p. 16V 2 amp £1-85.
AUTC TRANSFORMERS. 115V to 230V or 230V to 115V 150W £4-60; 500W £8-70; 750W £17-50; 1000W £21.
FULL WAVE BRIDGE CHARGER RECTIFIERS;
6 or 10A outputs. 1 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 780W. Insulated terminals. Varnish impregnated. Fully and used in steel case with fixing feet. OUR PRICE **£13-50** Carr. Famous make. (Value £19)

Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS

2/350V .14p	100/25V .10p	50+50/300V .50p
4/850V .14p	250/25V .14p	350+350/25V .50p
9/350V .22p	500/25V .20p	32+32/350V .40p
16/350V .85p	100+100/275V 65p	32+32/450V 60p
32/450V .85p	150+200/275V 70p	32+32+32/350V 65p
32/500V .85p	8+8/450V .25p	32+32+32/450V 85p
25/25V .10p	8+16/450V .85p	900/850V .95p
50/50V .10p	18+16/450V 40p	4700/83V .95p

LOW VOLTAGE ELECTROLYTICS

1, 2, 3, 4, 5, 6, 8, 25, 30, 50, 100, 200mF. 15V. 10p.
500mF. 15V. 15p; 25V. 20p; 50V. 30p.
1000mF. 12V. 20p; 25V. 35p; 50V. 47p; 100V. 70p.
2000mF. 6V. 25p; 25V. 42p; 50V. 57p.
2500mF. 6V. 65p; 3000mF. 25V. 47p; 50V. 65p.
5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 50V. 85p; 50V. 95p.

MICRO SWITCH. Single Pole Change Over. 20p.
MICRO SWITCH. Sub Min 25p.

CERAMIC 1pF to 0-01mF. 4p. Silver Mica 2 to 5000pF. 4p.
FILIPER 250V-0-1 7p. 0-5 18p; 1mF 15p; 2mF 150V 15p.
500V-0-001 to 0-05 4p. 0-1 10p; 0-25 15p; 0-47 25p.
TWIN GANG. "0-0" 200pF + 175pF. £1-20; 500pF standard 75p; 245+245 with 25+25pF slow motion drive 50p.
TWIN GANG. 150pF 50p. 385pF 50p.
SECT WAVE. SINGLE 150pF 80p; 25pF 55p; 50pF 55p.
NEON PANEL INDICATORS. 250V AC/DC Amber 25p.
RESISTORS. 1W, 1/2W, 1/4W, 20%; 1/2W, 5%; 10 Ohm to 10M Ohm.
HIGH STABILITY. 1/2 W. 2% 10 ohms to 8 meg., 10p.
Ditto 5% Preferred values 10 ohms to 10 meg., 4p.
WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K Ohm 10p.
TAPE OSCILLATOR COIL. Valve Type 35p.

NEW MODEL "BAKER LOUDSPEAKER" 18in. 50 watt GROUP 50/12 8 or 15 ohm high power full range. Professional quality. **£16-00**

BAKER MAJOR 12" £11-50



30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14-50**
Post free
Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
18 inch 25 watt	18 inch 35 watt	15 inch 50 watt
8 or 8 or 15 ohm	8 or 8 or 15 ohm	8 or 15 ohm

TRAK VENEERED HI-FI SPEAKER CABINETS
For 12in. or 10in. dia. speaker 20" x 18" x 12" £12-00 Post 85p
For 13" x 8in. or 8in. speaker 18" x 10" x 7" £7-50 Post 75p
For 8 x 6in. speaker 16" x 8" x 6" £5-80 Post 45p
For 12" x 8" x 6" £4-60 Post 35p

LOUDSPEAKER CABINET WADLING 18in. wide, 20 1/2in. deep


EMI 6 1/2in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Rubber cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Column, HI-FI Excursion System, Suitable cabinet 12 x 6 x 6 1/4 in. Suitable Tweeter £2-00. **£4-60**




ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 15,000 c/s. Size 8 1/2 x 8 1/2 in. Deep. Rating 10 watt, 8 ohm Suitable. Crossover £1-60 **£2-20** Post 20p



SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-18kc/s, 10W 8 ohm or 15 ohm £2-50
CROSSOVERS TWO-WAY 3000cps 3 or 8 or 15 ohm £2-50
CROSSOVERS 3 OHMS. 7 x 4in. £1-25; 6 1/2in. £1-50
SPECIAL OFFER: 8 ohm. 2 1/2in. x 2 1/2in. £1-90; 10in. £2-00.
15 ohm, 3 1/2in. dia. x 4in. 7 x 4in.; 8 x 5in. 7 x 5in. 7 x 6in. 8 x 6in. 8 x 7in. 8 x 8in. 8 x 645in. 8 x 646in.

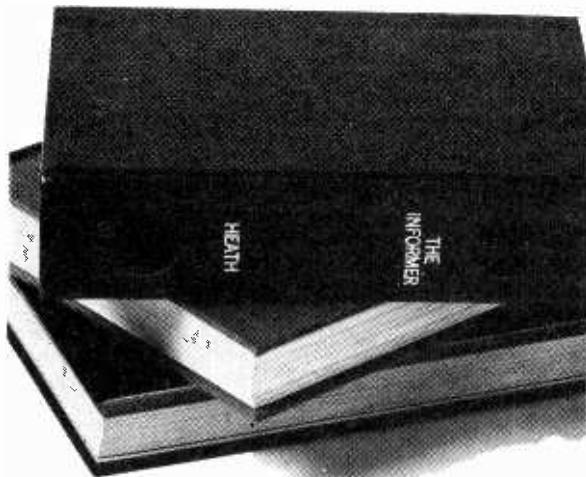Enough books are written about crime, this one stops it.



Outside it's a book. Inside it's an ingenious ultrasonic burglar alarm from Heathkit. The GD-39. A complete kit that can be assembled in only a few enjoyable hours, with the help of a very easy to follow instruction manual.

The GD-39 works by transmitting a silent, ultrasonic signal throughout the room. And continuously monitoring it. Any movement made by an intruder in the room will then automatically produce a change in the signal. Which triggers off a lamp and, thirty seconds later, a remote buzzer, that just you hear, or a loud bell.

Enough to scare the living daylights out of a burglar. For more details, and a bookful of other ideas, just post the coupon now for your free Heathkit catalogue.

Or, if you're in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

Heath (Gloucester) Limited,
Dept. PW-65, Bristol Road,
Gloucester GL2 6EE.
Tel: (0452) 29451.




The GD-39 Ultrasonic Burglar Alarm

To: Heath (Gloucester) Limited, Dept. PW-75, Gloucester GL2 6EE. Please send me a free Heathkit catalogue.



Name _____
Address _____
Postcode _____

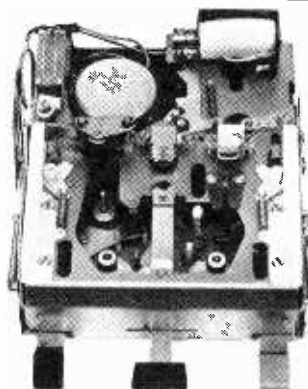Remember easy terms are available with the Heathkit Monthly Budget Plan.



GARRARD CT4S' MK III STEREO CASSETTE PLAYER & RECORDER

has full facilities for record, playback, pause, erase, rest, fast forward and reverse wind, automatic tape end stop and cassette release.

Robust, precision engineered mechanism based on the "STARR" patented design. Ideal for use in Car stereo cassette players, HI-FI stereo cassette recorders, industrial and many other applications.

Send cheque or Postal Orders for £19.98 (£18.50 + 8% VAT) (includes post and packing) to:

BOTHWELL ELECTRIC SUPPLIES
(Glasgow) LIMITED
431 Sauchiehall Street
GLASGOW G2 3LG Tel: 041-332 6184
Scotland's Leading Electronics Centre



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence


free!

Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS
SCHOOL** Dept. WB75, P.O. Box 156, JERSEY


NAME : _____
ADDRESS : _____

— BLOCK CAPS please

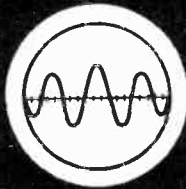


TUAC

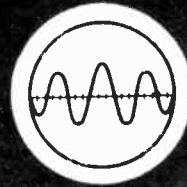TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137 9080



MANUFACTURERS OF
ELECTRONIC &
AMPLIFICATION
EQUIPMENT. ALSO
QUALITY TRANSISTOR
EQUIPMENT.
OPEN MON.-SAT.
9.30 a.m.-6.00 p.m.


NEW TUAC POWER MODULES offering more power and quality than ever before.

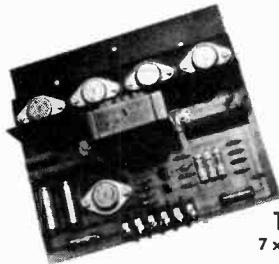

TPI25
7 x 6½ x 3in
£22.50

★ 125 watts RMS continuous sine wave output
★ 4 R.C.A. 150 watt 15 amp output transistors


- Rugged layer wound driver transformer
- Short — Open — and Thermal overload protection
- Only 6 connections

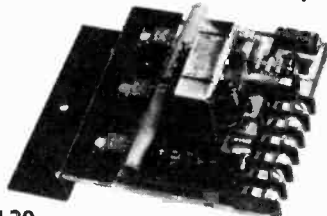

TL30
4 x 5½ x 2½in **£9.00**

★ 30 watts RMS continuous sine wave output
★ 2 R.C.A. 40 watt output transistors

Specification on all power modules: All output power ratings ± 0.5 dB; Output impedance 8-15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10k Ω ; Frequency response 20Hz-20kHz ± 2 dB; Hum and noise better than -70dB.

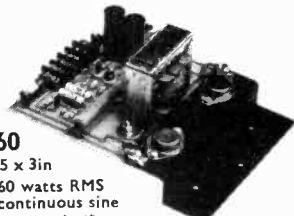

TL60
5 x 5 x 3in
★ 60 watts RMS continuous sine wave output
★ 2 R.C.A. 110 watt 15 amp transistors
£14.50

TL100
5 x 5 x 3in
★ 100 watts R.M.S. continuous sine wave output
★ 2 R.C.A. 150 watt 15 amp transistors

£17.50

TUAC DISCOTHEQUE MIXER WITH AUTO FADE




PANEL SIZE
18 x 4½in.
DEPTH 3in.

£36.50

Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls; Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

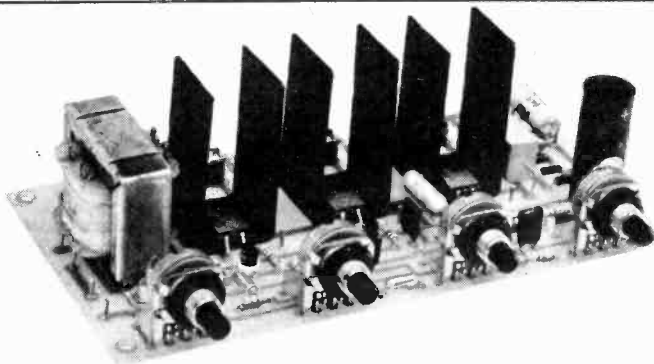Specification: Deck Inputs—50mV into 1m Ω ; Deck Tone Controls—Treble +20-10dB at 12kHz. Bass +22-15dB at 40Hz; Mic input—200 ohms upwards. 2mV into 10k Ω ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape input—30mV into 47k Ω ; Power Requirements—30-45 volts at 100mA.




NEW! 3 CHANNEL LIGHT MODULATOR

● R.C.A. 8 Amp Triacs ● 1000W per channel ● Each channel fully suppressed and fused ● Master control to operate from 1W to 100W ● Full wave control—12 easy connections

£18.00

Single Channel Version 1500 watts £8.50

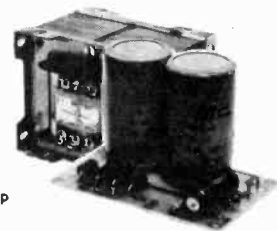

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

PS 125 \pm 50 volts for one TPI25	£14.25
PS100 \pm 45 volts for one TL100	£13.00
PS60 \pm 40 volts for one TL60	£11.50
PS30 + 50 volts for one TL30	£7.00
PSU 2 for supplying disco mixer	£5.50

STOCKISTS—CALLERS ONLY

Arthur Salis Ltd., 28 Gardner Street, Brighton, Sussex. Tel 65806, Bristol Disco Centre, 86 Stokes Croft, Bristol 1. Tel. 41666, Socodi, 9 The Friars, Canterbury. Tel. 60948. Cookies, 132 West Street, Crewe. Tel. 4739 or 581202. Calbarrie Audio, 88 Wellington Street, Luton. Tel. 411733. Al Music Centre, 88 Oxford Street, Manchester. Tel. 061-236 0340. Damon Electronics, 99 Carrington Street, Nottingham. Tel. 53880. Mitchell Electronics, 64 Winchester Street, Salisbury. Tel. 23689. Wec Lighting, 10 Commercial Road, Southampton. Tel. 28102.

HOW TO ORDER BY POST

Make cheques/P.O.'s payable to TUAC LTD. (P.W.4) OR QUOTE ACCESS/BARCLAY CARD NO. and post to TUAC LTD (P.W.4) 163 MITCHAM ROAD, LONDON SW17 9PG

We accept phone orders against ACCESS/BARCLAY CARD Holders Phone 01-672-3137/9080

H.P. arranged through PAYBONDS

ALL PRICES INCLUDE V.A.T. (25%) AND POSTAGE AND PACKING

RTVC*

NEW!

VISCOUNT IV STEREO SYSTEM

System 1a. £69.00

The new 20+20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls — volume, bass, treble, balance, mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear — for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion @ 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. — 3 millivolts @ 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. — 50 millivolts @ 50 K ohms (R.I.A.A.); 3, 4, 6. Tape Tuner/Aux. — 140 millivolts @ 50 K ohms (flat frequency response); 5. Microphone — 3 millivolts @ 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket, Aux. mains output. Frequency response: 25 Hz to 25 KHz @ full rated output. Signal to noise ratio: better than —50 dB on all inputs. Tone control range: Bass +15 dB @ 50 Hz, Treble +12 dB @ 10 KHz. Power requirements: 200-250V A.C. mains @ 60 watts. Approx. size: 15½" x 3" x 10".

Garrard SP 25 deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type 11a matched speakers — Enclosure size approx 19½" x 10½" x 7½" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling, 30 watts peak.

Complete System with these speakers £69.00 + £6.50 p & p.

System 2. £85.00

Viscount IV amplifier (As System 1a)

Garrard SP 25 deck (As System 1a)

Two Duo Type 111 matched speakers

— Enclosure size approx. 27" x 13"

x 11½" Finished in teak simulate.

Drive units 13" x 8" bass driver, and

two 3" (approx.) tweeters. 20 watts

RMS, 8 ohms frequency range —

20 Hz to 18,000 Hz.

Complete System with these

speakers £85.00 + £7.60 p & p.

PRICES: SYSTEM 1a

Viscount IV R103 amplifier £25.00 + £1.90 p & p

2 Duo Type 11a speakers £30.00 + £6.50 p & p

Garrard SP 25 with Mag. cartridge de luxe plinth and cover £24.50 + £3.30 p & p

Total if purchased separately: £79.50

Available complete for only £69.00 + £6.50 p & p.

PRICES: SYSTEM 2

Viscount IV R103 amplifier £25.00 + £1.90 p & p

2 Duo Type 111 speakers £46.00 — £7.50 p & p

Garrard SP 25 with Mag. cartridge de luxe plinth and cover £24.50 + £3.30 p & p

Total if purchased separately: £95.50


Available complete for only £85.00 + £7.60 p & p.



20x20 SYSTEM

Scotland P & P Surcharge System 1a £1.75 System 2 £3.50

EMI SPEAKERS AT FANTASTIC REDUCTIONS

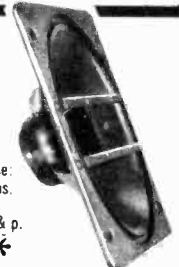

LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.

Specification — Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz—20 KHz.

Our Price £34.00

(normally £66.00) + £5.80 p & p.

EMI 350 KIT

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

Complete with crossover Components and circuit diagram **£6.50 + £1.20 p & p.**

20 WATT SPEAKER SYSTEM*



System consists of a 13" x 8" (approx.) elliptical woofer unit with a 8" x 5" (approx.) mid-range unit incorporating parasitic tweeter and crossover components and circuit diagram

Technical Specification: Bass Unit: Flux density — 100 K, speech coil — 1½". Cone, Triple laminated paper with P.V.C. surround. Mid-Range Unit: Flux density — 33 K, speech coil — 1" with parasitic tweeter. Power handling: 20 watts RMS, impedance — 8 ohms, frequency response — 20 Hz to 18,000 Hz.

Our Price £8.70

Complete + £1.60 p & p.

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3½" tweeter and matching crossover.

Easily put together with just a few basic tools.

Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20—20,000Hz. Size 20" x 11" x 9½" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

£22.00 pair complete

+ £5.20 p & p.

Complete with crossover Components and circuit diagram



DECCA STEREO AMPLIFIER CHASSIS

Specification: 4+4 watts into 8 ohms. Input Sensitivity 4mV into 47K (for magnetic cartridges). AC Mains only 240V. Controls — volume, bass, treble, on/off, mono/stereo switch. Chassis size 11" x 5½" x 3½" approx.

£6.90 + £1.20 p & p.



PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.


TECHNICAL SPECIFICATION: (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF module.

Controls volume manual tuning and five push buttons for station selection. Illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide 2" high and 4 1/2" deep approx. **£9.50 + £1.05 p & p.** Speaker including baffle and fixing strip **£2.00 + 45p p & p.** Car Aerial Recommended — fully retractable **£1.60 + 40p p & p.**

The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20 + £1.05 p & p.**

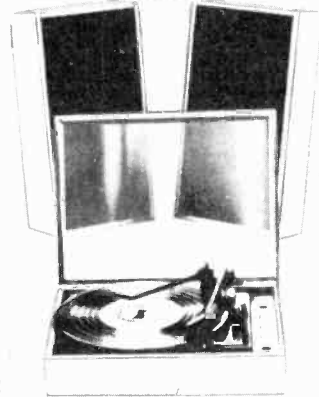*STEREO 21 QUALITY SOUND FOR LESS THAN £24.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth. Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets. Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications — For the technically minded: Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8—15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only £23.20 + £3.00 p & p.

Extras if required. Optional Diamond Stylus **£1.60.** Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80.**

*DISCO AMPLIFIER



Reliant MK IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms). Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES — Input — 1) Crystal mic. guitar or moving coil mic. 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx. 12 1/2" x 6" x 3 1/2".

£20.00 + £1.35 p & p.

*8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at **£24.00** approx. Yours for only

£16.20 + £1.70 p & p.



BUILD YOUR OWN *STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7" x 4") **£10 + £1.75 p & p.** **£8.95 + £1.05 p & p.**

PORTABLE DISCO CONSOLE*



INCORPORATES Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP6D type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:

Pre-amp Output — 200mV.
Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation.
Turntables capacity 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kalee meter).
Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17 1/2" x 13 1/2" x 8 1/2" (app.)
Unit Open — 35 1/2" x 13 1/2" x 4 1/2" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.
The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only

£57.00 + £6.50 p & p.



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st May 1975 and subject to change without notice. All prices include V.A.T. at 25% rate



21C HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2.

Personnal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

VAT MUDDLE!

THE ominous expansion of VAT to 25% has indeed brought forth justifiable protests from many quarters of the electronic components industry.

Customs and Excise Notice 742 states that the 25% rate of VAT is applicable not only to assembled radio receivers, amplifiers, TV's etc. but applies also to all component parts, accessories and service in respect thereof. Notice 742 states that the 25% VAT rate applies to all resistors, capacitors, coils, transistors, etc. if they are of a kind suitable for use as parts of goods for the aforementioned items, even when these goods are supplied for the manufacture or service of other equipment not taxed at 25%.

There is considerable uncertainty within the trade and industry over the new VAT schedule. The industry is quite justifiably up in arms over this punitive rate of tax.

The pursuit of our hobby, and the pursuit of many others, could be severely restricted by the extra cost of components. Research, development and experimentation will be throttled and the widespread implications of this should be obvious to anyone.

LIONEL E. HOWES—Editor

PRACTICAL WIRELESS

**AFTER 43 YEARS—STILL
THE No.1 MAGAZINE IN
THE FIELD!**

Practical Wireless—the favourite magazine of the radio and electronics constructor—extensively read by the trade and many others concerned with modern electronics

108,698

ABC*JULY-DECEMBER 1974

*Average net sales of copies per issue certified by the Audit Bureau of Circulations

NEWS...

Heathkit Competition Result

IN our March issue we invited readers to assess advantages of building one's own electronic equipment over buying ready-made outfits.

Having considered all entries, the judges decided that the best received was that submitted by Mr. Robert Gregory, of Mansfield, Notts, who had listed the featured advantages in the following order: 1st—C; 2nd—A; 3rd—J; 4th—E; 5th—L; 6th—B; 7th—K; 8th—D.

Mr. Gergory wins a £100 voucher to spend on equipment from Heathkit.

The four next best entries were from:—Mr. H. Boland, Armagh; Mr. J. McKeown, Wigtown; Mr. P. Garside, Kings Lynn; Mr. I. Marsden, Nottingham. Each wins a £50 Heathkit voucher.

To complete the prize-list there were a further eight £25 Heathkit vouchers, and these went to Mr. R. Armstrong, Farnborough; Mr. M. Clay, Sevenoaks; Mr. B. Cambray, Croydon; Mr. Pidun, Braintree; Mr. P. Royle, Bristol; Mr. E. Rumble, Haywards Heath; Mr. S. V. Bentall, Buntingford; Mr. P. G. Hazelwood, Brierley Hill.

Advertisers Note

RECENTLY *Practical Wireless* has been able to offer a unique service to its advertisers. On request, advertisers have been given advance information concerning components for P.W. projects.

Advertisers should contact Dennis Brough on 01-634 4116 or Christine Dunn on 01-634 4293.

Essex Repeater Group

THE above group have submitted their application to the Home Office for a 70cm repeater to be sited on Danbury. To assist fund raising a Grand Bring & Buy and Junk Sale will be held at St. John's Hall, Vicarage Road, Chelmsford, on Saturday, June 28th from 11 a.m. to 6 p.m. The Group will be arranging 'talk in' on 433.200 UHF S20/S22 and 4 metres. For further information contact G3VKQ, G3WCO or G3MVV.

Sinclair wins Queen's award



SINCLAIR Radionics has won a Queen's Award to Industry, 1975, in recognition of its outstanding export achievement and for technological innovation in scientific electronic calculators.

During a three-year period ending in April 1974 the company, which is Europe's largest manufacturer of electronic calculators increased its exports tenfold to £2,232,040 p.a. or 56 per cent of turnover.

Award for technological innovation has been made for the development of the low cost, Sinclair 'Scientific' pocket calculator.

Picture shows Clive Sinclair, aged 35, founder and Managing Director of Sinclair Radionics of St. Ives, Cambs.

More awards

THE X-Ray Systems Division of EMI Limited and the Telecommunications Division of EMI Sound & Vision Equipment Limited have both won the 1975 Queen's Award to Industry for export achievement.

EMI contract

THE original £1.25 million contract won by EMI Sound & Vision Equipment Limited to supply the complete antenna system for the CN Tower in Toronto, the world's tallest self-supporting structure, has been boosted by £60,000. This latest contract covers the provision of additional antennas for Ch. 70.

Three Q concept

THE ability to provide quality products in quantity, quickly has always been the strength behind the Mullard company. At the International London Electronic Components Show at Olympia this 'Three Q' concept was adopted as an overall theme aptly illustrating the company's attitude towards trading in the challenging years ahead.

Eleven major displays on a stand of 300 square metres highlighted what is believed to be the broadest range of components ever shown. In addition to the 'Three Q' components available now to meet equipment production needs, the displays included over a hundred new products for tomorrow's designs, many of them on show for the first time.

A team of Mullard engineers was on hand to discuss all aspects of the displays and a data-bar provided visitors with the latest information on every product in the Mullard range.

Following their participation at the London Electronic Components Show, Mullard took their displays to Edinburgh, Manchester and Bristol. At each centre the displays were backed by a series of lectures from Mullard experts.

Books received

Slide-Tape and Dual Projection

By R. Beaumont-Craggs

Covers all aspects of music and 'chat' with slides. Topics covered include essential equipment, taking pictures, preparing the sound track, dual projection, special effects, audio visual in education and the all-important presentation of the show. It would prove invaluable to tape-recording enthusiasts, photographers, photographic and amateur cine clubs, teachers, sales and publicity personnel etc.

Price £3

Focal Press Limited 31 Fitzroy Square, London, W1P 6BH

Plessey Semiconductors Integrated Circuit Data Book

No author

Contains full information on the continually - growing range of standard products manufactured by the Plessey Company.

No price quoted

Plessey Semiconductors, Cheney Manor, Swindon, Wilts, SN2 2QW

Tape Recording from A to Z

By Doug Crawford

Simple language explanation of how tape recording works—a simple step-by-step account of using reel-to-reel machines; what to look for when buying one etc.

Price £1.85

Kaye and Ward Limited, 21 New Street, London, EC2M 4NT

Questions and Answers on HiFi

By Clement Brown

Q and A in very simple language on most things you need to know about HiFi. All sources are covered—discs, tapes, radio. Guidance on costs is given, specifications, planning requirements, etc. etc.

Price: 75p

Butterworth & Company, 88 Kingsway, London, WC2B 6AB

BBC Handbook 1975

No author

Almost everything you need to know or want to know about the BBC.


No price quoted

British Broadcasting Corporation, 35 Marylebone High Street, London, W1M 4AA





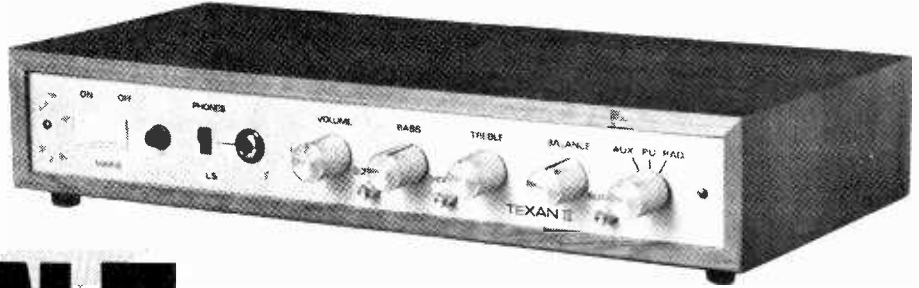TEXAN II (UP-DATING OUR STEREO AMPLIFIER)



RICHARD MANN*

ALTHOUGH this article is headed The Texan II it would probably be more accurate to describe it as the Texan III/II! Since the first design appeared in these pages about three years ago I am told that approximately 45,000 kits have been sold. (Next time, I'm going to make sure that I have a slice of the action!) With all those Texans knocking around it was inevitable that there should be quite a bit of correspondence on the subject. These notes, therefore, are intended to deal with some of the points which have come up most often and aimed at the man who already has a working Texan and who wants to upgrade it slightly. In the not-too-distant future I hope that PW will be able to publish a new design which is currently gestating, but new designs are not much comfort if you have already spent your money.

The three points which have arisen most consistently have been:—

- 1 Susceptibility to RF interference.
- 2 How to increase the power output.
- 3 How to install a Tape Monitor facility.

There have been other comments, of course. Some of them are repeatable, but not really within the scope of the Texan concept. The idea of the Texan was to produce a value-for-money design without a lot of frills but which would be very reproducible and would sound really good under normal domestic conditions.

SUSCEPTIBILITY TO RFI

I think this fault was the one real shortcoming of the original design. Unfortunately it is not a very easy thing to test for under laboratory conditions. It's not until 45,000 fridges have clicked on and off a few times that you know you really have a problem on your hands! The weakness was partly due to the rather skimpy screening of the Texan metalwork and partly to the over-simplification of the design so that there were no filtering components in it from input to output.

Basically, anything which is wired into the amplifier is capable of introducing interference, the mains lead, the pick-up leads and the loudspeaker leads.

I mention the loudspeaker leads last because it appears that these have been the major cause of the trouble. They are usually long for a start, and in the output circuit, which is shown in Fig. 1, it will be noted that there is virtually a short-circuit to RF from the output, through C18 and on to the inverting input of IC3. Now although they are miraculous things, operational amplifiers are not normally noted for the fastness of their slew-rates. Slew-rate being the maximum volts per second that they can deliver. They might give out 100mV at 1MHz or 10V at 10kHz but there is no way they will give 10V at 1MHz! Consequently a fast signal appearing spuriously at an input terminal will tend to be greatly amplified in the early high-gain stages of the op-amp but the later stages will be unable to follow it with the result that there will be distortion and demodulation of the signal and rude noises at the output.


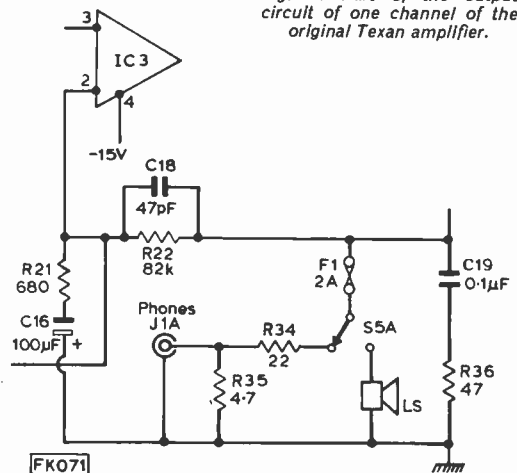


Fig. 1: Part of the output circuit of one channel of the original Texan amplifier.

Two simple high-pass filters have been added, R39/C24 in Fig. 2a and R40/C26 in Fig. 2b. These have a cut-off frequency of 2.2MHz so they do not have any audible effect on the amplifier response. However they filter out most of the spurious RF before it can do any harm. A further capacitor, C25,

* Texas Instruments Limited

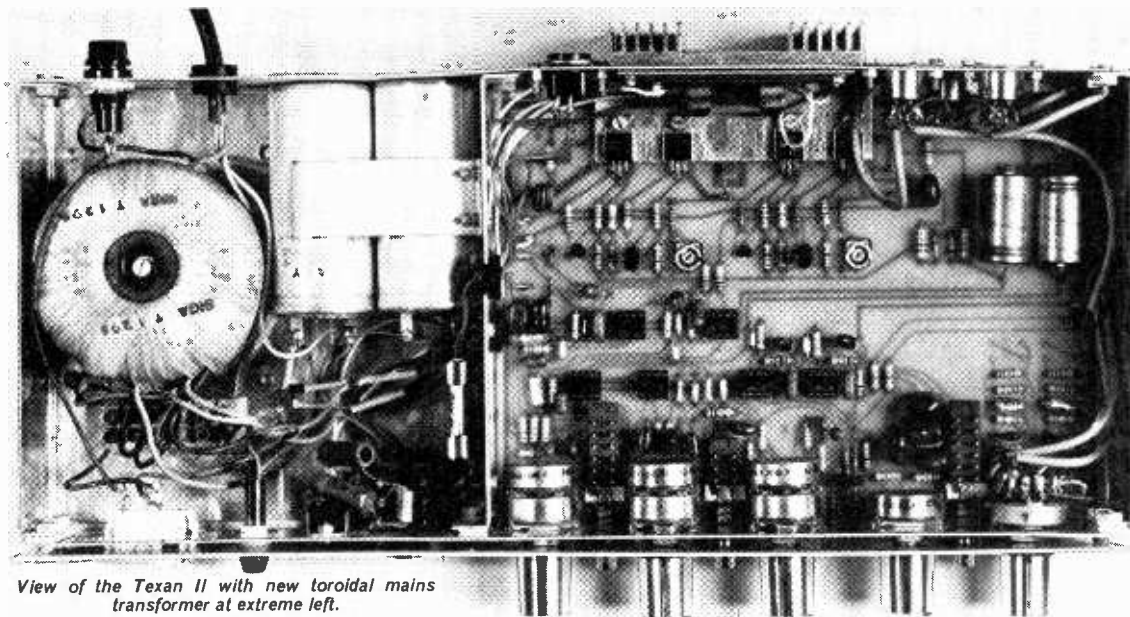

View of the Texan II with new toroidal mains transformer at extreme left.

is added directly across the input terminals of IC3 in order to provide a shunt for any residual noise which appears differentially at this point. This capacitor causes a slight drop in the high-frequency open-loop gain of the op-amp which consequently causes a slight increase in the high-frequency distortion of the Texan but the audible difference is quite undetectable.

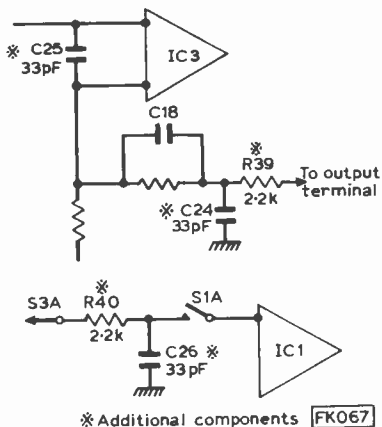


Fig. 2: Circuits of the two high-pass filters added to each channel.


These extra components are very easy to add. Resistor R40, and its complementary resistor in the other channel, R140, are wired in directly between switch S3 and points H and I on the PCB which is shown in Fig. 3. These resistors replace the short wire connections originally there. The PCB can then be drilled to take the remaining filter components. This can be done quite accurately with a sharp drill held in a pin-chuck and twisted in the fingers. If it is a Texan kit with a removable base it is easy to hold the board against a light and drill through from the top. The exact positioning of the holes is not critical but it is obviously important to avoid any damage to existing components. Take care also that

the track is not drilled through as the solder joint, when made, may fail to close the gap in the track. It is better to drill just alongside the track and bend the component wire across.


INCREASING OUTPUT POWER

There are two approaches to increasing output power: one is to increase the peak power obtainable under transient conditions; the other is to increase the continuous output power from both channels simultaneously. The first is a function of the power rail voltage while the second is a function of the power supply regulation. Both of these factors, in turn, are primarily a function of the mains transformer used. The transformer used in the original design was chosen for its combination of economy and good performance. It would not, however, give the regulation obtainable from a rather more expensive toroidal transformer, such as that used here in the Texan II. This has been designed to fit in the same space but it has a 75VA rating and has some extra taps. The primary has a tap for 220V input as well as 240V and the secondary is wound to give 25-20-0-20-25V.

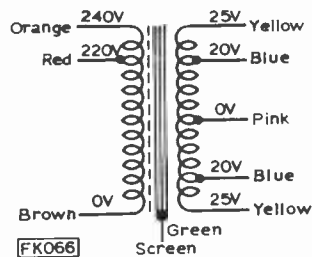The Texan I was capable of delivering 20W + 20W into 8 ohms with an intermittent sine wave input but would give only 16W + 16W with continuous



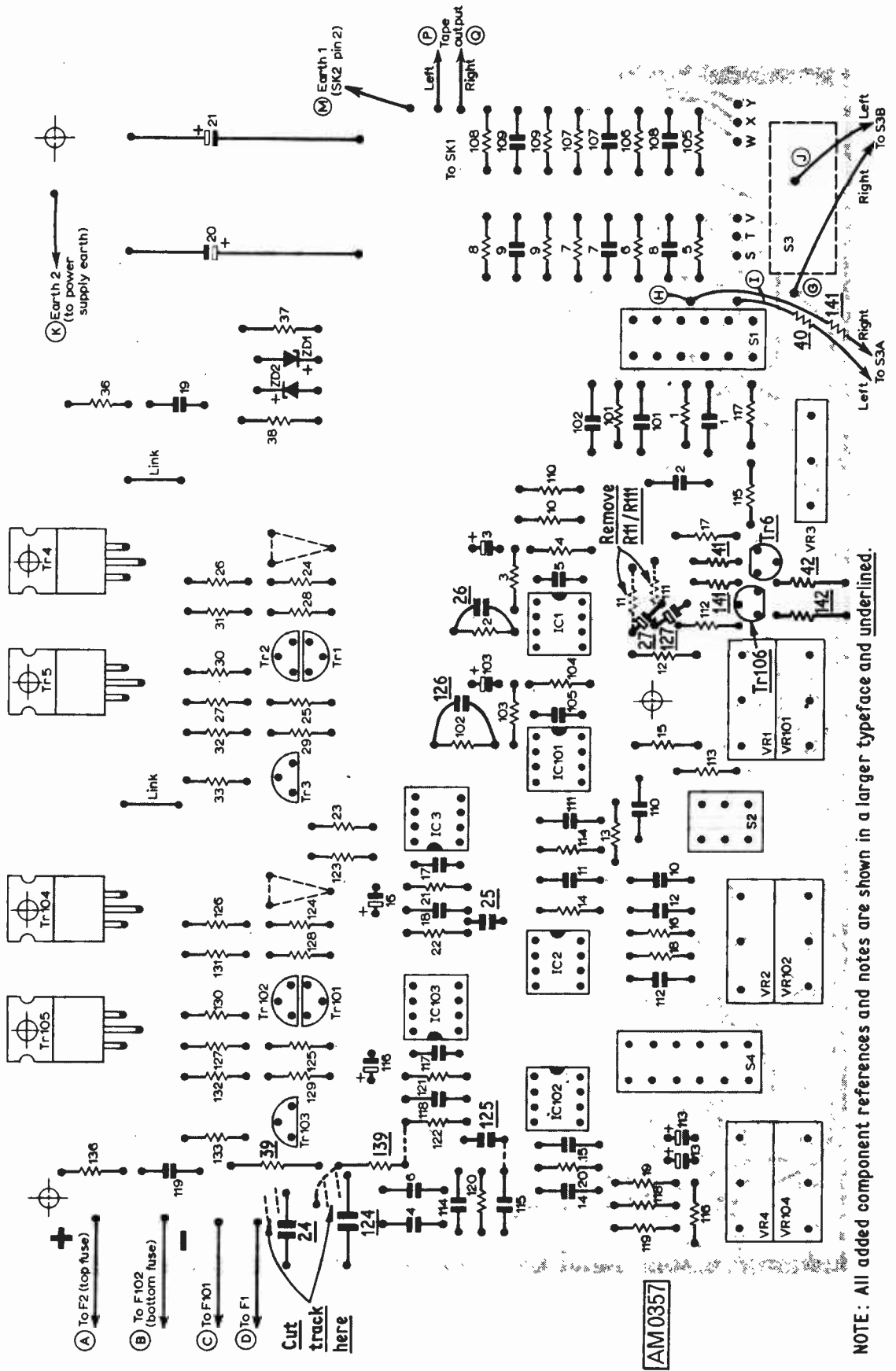Colour coding of the toroidal transformer. A small terminal block is desirable to take extra secondary leads. The block can be seen below the transformer in the photograph above.



- (A) To F2 (top fuse)
 - (B) To F102 (bottom fuse)
 - (C) To F101
 - (D) To F1
- Cut track here**

NOTE: All added component references and notes are shown in a larger typeface and underlined.

Fig. 3: Original Texan PCB with RFI suppression components added. Tape monitor modifications, centre bottom, are shown from foil side in Fig. 11.

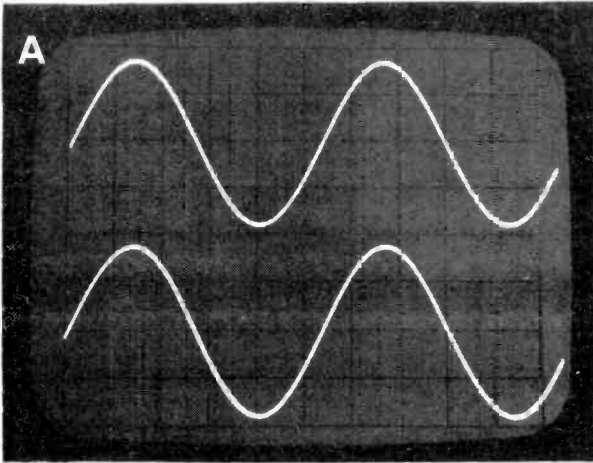


Fig. 4: Sinewave output with amplifier running at $2 \times 20W$ into 8Ω speakers and using 20V taps on transformer.

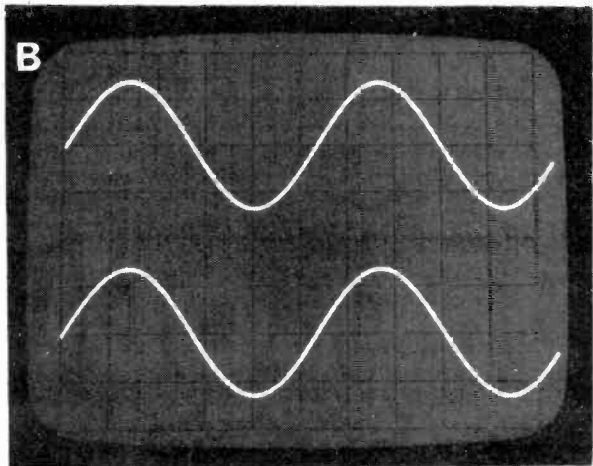


Fig. 5: Output of 22W per channel into 4Ω speakers. Again, 20V taps on transformer.

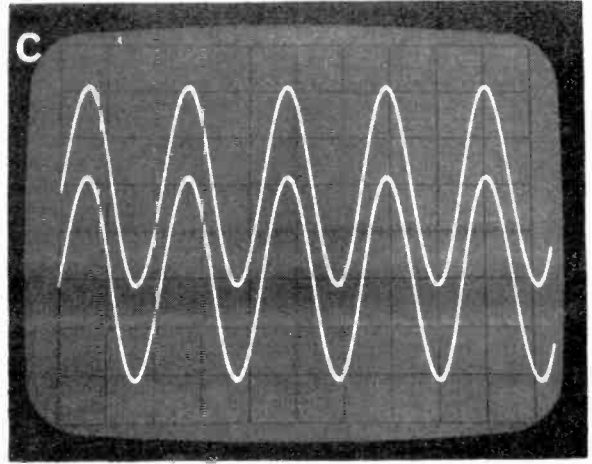


Fig. 6: This time the 25V transformer taps are used, giving $2 \times 28W$ into 8Ω speakers.

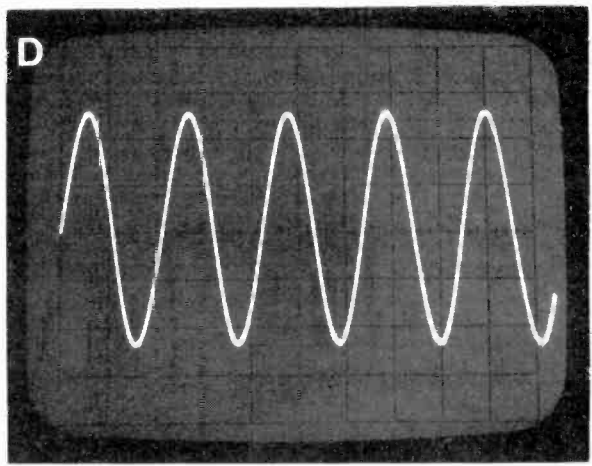


Fig. 7: Output from one channel providing 40W into an 8Ω speaker using 25V taps on mains transformer.

inputs. Simply by replacing the original transformer with a toroidal version, the amplifier will comfortably deliver 20W continuously into 8 ohm loads or 22W+22W into 4 ohm loads. No other circuit changes are necessary except that the two 2A fuses in the supply lines should be increased to 3A rating. The oscillograms in Figs. 4 and 5 show that there is no clipping under these maximum output conditions.

If it is wished to increase the output power substantially then the 25V secondary taps can be used. It then becomes necessary to change the output transistors, Tr4 and Tr5, since the breakdown voltage, V_{CE0} , for the TIP41A and TIP42A is only 60V. The DC rail voltage under quiescent conditions is now $\pm 37V$. It is therefore quite possible that the breakdown voltage of the transistors will be exceeded and although there is a chance that they will stand it, it is far wiser to be on the safe side and replace them with TIP41B and TIP42B respectively. These have a breakdown voltage of 80V. It is not necessary to change any other components.

Oscillogram, Fig. 6, shows the clean output of the amplifier, with the higher voltage rails, delivering a continuous sine wave power of 28W+28W in 8 ohm loads. Probably of more significance is the oscillogram shown in Fig. 7 which shows a con-

tinuous sine wave power of 40W being delivered to an 8 ohm load. The amplifier will, in fact, give an instantaneous power of about 100W on transient inputs. The effect of this, for normal music listening, is that peaks sound extremely clean. My record of Beethoven's Ninth suddenly seemed much better, and all the time I have been blaming it on the recording company!

In order to maintain these higher powers it now becomes highly advisable to add an extra heat sink. For this I have used a short length of Redpoint M-type Powersink. Unfortunately this is just too wide to fit in between the sockets on the back of the Texan without some modification. One fin section has therefore been sawn off each side of heatsink reducing its size to $3\frac{1}{4} \times 1\frac{3}{4}$ in. It can then be drilled and tapped to take the 6BA screws which hold the original heat sink assembly together.

Alternatively it might prove easier to use separate countersunk screws to hold the transistor mounting plate and the heatsink independently on to the back panel of the amplifier. In this case all the screw heads will be "blind" being sandwiched between the parts of the assembly. The screws should therefore be inserted and held in place with a touch of Durofix until they can be tightened up with the nuts, Fig. 8. Although this is rather tricky it does avoid a slight

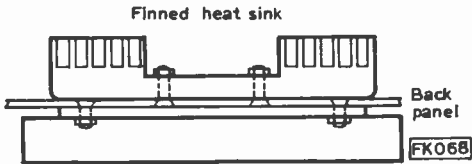


Fig. 8: Suggested method of fixing new heatsink.

“bodge” which is needed to work the screws between the fins of the Redpoint Powersink. Whichever method is used a smear of heat sink compound should be placed on the adjoining surfaces.

TAPE MONITOR

The tape monitor facility is very simple to add from a circuit point of view but it requires rather more care to add mechanically. The function of the tape monitor is to provide a means of breaking the amplifier between the equalization stage and the tone control stage so that a tape recorder with separate record and replay functions can be inserted to “fill the gap”. This allows a recording to be made off a disc, for example, using the correct equalization in the first stage. The remainder of the amplifier can then be used to amplify the tape recorder output so that a direct comparison can be made between input and recorded signals.

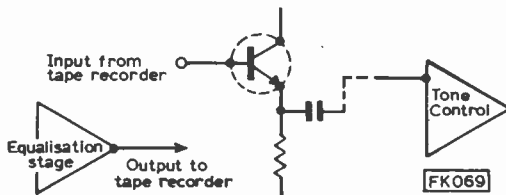


Fig. 9: Emitter-follower buffer stages must be introduced for the tape monitor facility.

The tone control stage in the Texan must be driven from a low impedance source so it is necessary to buffer the tape monitor inputs with a pair of emitter-followers as shown in Fig. 9. This modification can be incorporated by wiring the extra transistors across the back of the Auxiliary Input socket and putting a small switch on the back panel. A neater alternative is to make use of the Mono/Stereo switch. Although it is normal to have this facility on a stereo amplifier I have found that it is very seldom used in practice. Since the switch unit S2 is a 2-pole changeover type it is ideal for its new role.

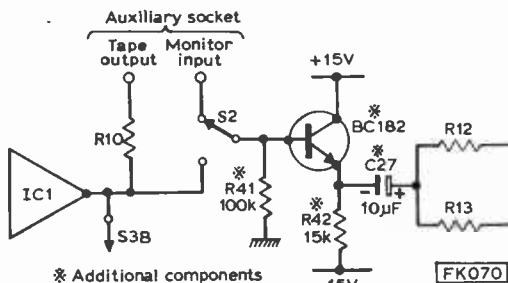


Fig. 10: Circuit of one of the buffer stages.

★ components list

Resistors

R39/139 2.2kΩ R41/141 100kΩ
R40/140 2.2kΩ R42/142 15kΩ
All resistors 10% 1W carbon film

Capacitors

C24/124 33pF polystyrene
C25/125 33pF polystyrene
C26/126 33pF polystyrene
C27/127 10µF tantalum bead

Transistors

BC192 TIP41B TIP42B 2 off each type

Heatsink

Redpoint M type modified, see text, or similar.
83 x 44mm (3¼ x 1¾in.)

Transformer

Toroidal transformer Type T1295 available from SIGA Electronics Ltd., Sunderland Road, Sandy, Bedfordshire SG19 1QY for £8.88 inc. VAT and p/p.

In the high power version the fuses should be 3A rather than 2A.

The actual circuit modifications are shown in Fig. 10. Resistor R111 is no longer necessary and can be removed from the PCB, making room for the new components. The circuit track connecting to S2 is removed. The easiest way to do this is to cut the track with a sharp razor blade at the ends of the unwanted section and then heat the track with a fine soldering iron so that it can be peeled off with a pair of tweezers. The board should then be drilled very carefully as shown in Fig. 11 and the extra components wired in position. It is, unfortunately, necessary to use a few wire links in order to complete the modification but they fit in quite neatly as shown.

The input connection to the Monitor switch can be made using the existing length of twin screened

AM 0358


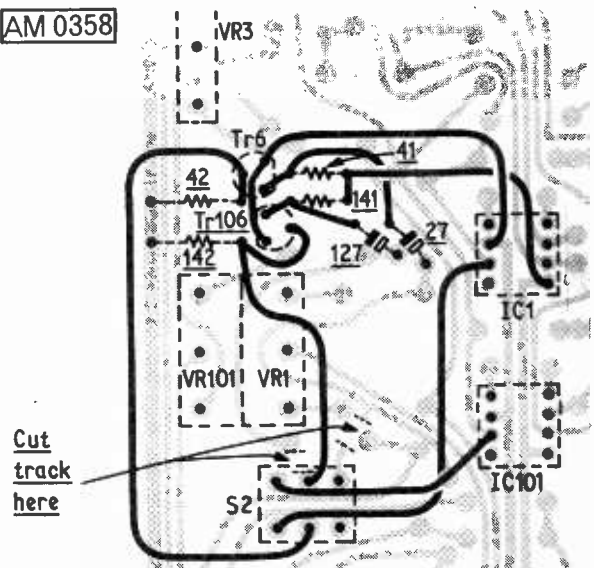


Fig. 11: Area of PCB affected by tape monitor modifications. See also Fig. 3.

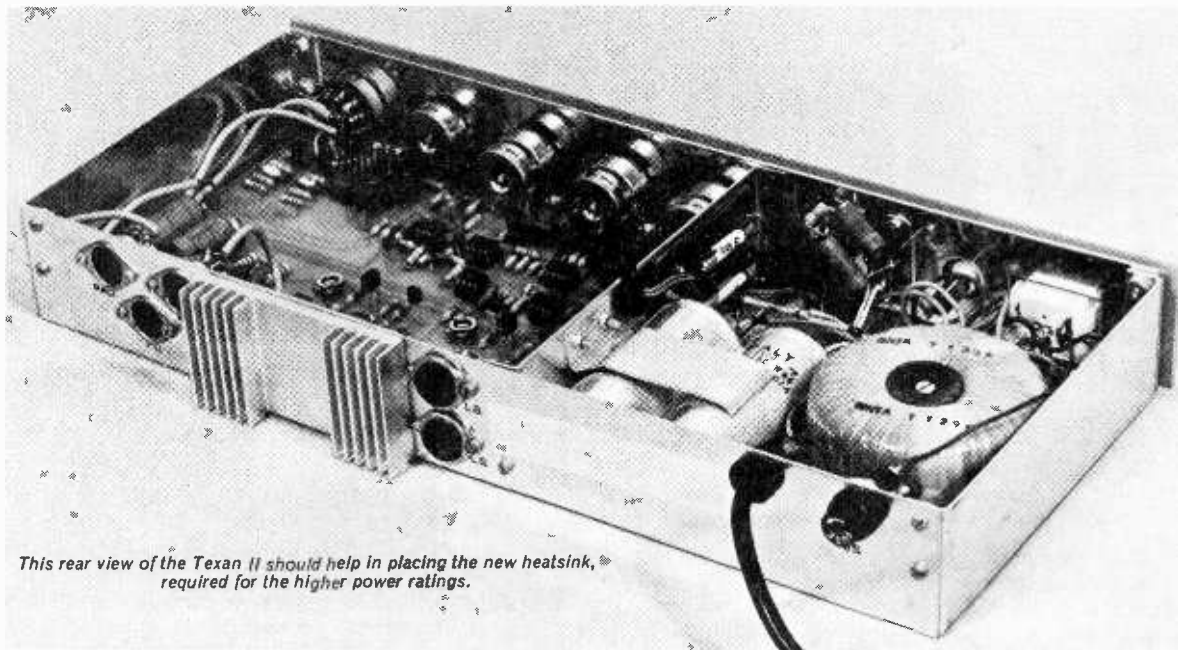

This rear view of the Texan II should help in placing the new heatsink, required for the higher power ratings.

cable which normally runs between the AUXILIARY DIN-socket and the AUX. position of S3. In the photograph this wire is shown running underneath the PCB, however it can just as easily be run over the top with the connections being made to the upper leads on S2. The unused contacts on S3 can be left open or, more usefully, can be shorted across to the RADIO contacts so that two different sensitivities could be selected for one source by switching from RADIO to AUX. at the front panel.

Another rather fortuitous point is that the "O" of "MONO" on the front panel can be removed with a little delicate surgery leaving an appropriate "MON" for "monitor".

Adding this tape monitor modification gives an extra advantage in that it AC couples the equalisation stage to the tone control stage. On reflection I think I was rather over-anxious to reduce the number of capacitors in the Texan to an absolute minimum. The result of DC coupling between these two stages is that the DC gain of the tone control stage becomes dependent on the setting of the bass control. Thus, if there is a small offset voltage at the output of IC1 this will be amplified by the following stage. If the bass control is then moved rapidly there can be a rather disconcerting plop in the loudspeakers. If your Texan suffers from this it is well worth while to insert a 10 μ F capacitor between R11 and the junction of R12 and R13 even if you do not wish to add the tape monitor facility itself.

IN CONCLUSION

I hope that the modifications suggested above will provide the answers to the majority of constructors' problems. They are not very dramatic but, as I said earlier, to do much more would be to change the concept of the Texan's value-for-money design. In spite of the odd bits of "knocking copy" that have since appeared I still think it was quite a good concept. It is clear that the changes can be made

singly or collectively according to how much time and money the constructor wants to spend.

To those people who have blown up several sets of output transistors, there is little I can offer but my sympathy. If the specified devices are used it is extremely unlikely that they will have been faulty themselves. However, they are connected across a beefy power supply with no form of current limiting in series with them. Any circuit fault which causes both transistors to turn on at the same time, even momentarily, will almost certainly cause them to blow. It is therefore **vital** to ensure that the greatest care is taken when soldering the output stage components. There is always a reason why things go wrong no matter how sure the unlucky constructor may be that "it just happened." Furthermore, one disaster may well cause a degradation of another component, so if you have an accident make sure you remove and check all the devices before throwing away another good set of power transistors. All the transistors can be checked adequately with an Avo and ICs can be checked by swapping around. If IC3 or IC10 is removed, protect the output devices by breaking the set-up link in the emitter of Tr4 or Tr104 respectively. Finally, if you do not have a fine soldering iron or do not know how to use it, buy one and practice. I have seen some of the plumbing jobs that have been perpetrated! You don't know whether to laugh or cry!

Editorial Note—The author has also supplied some technical information on disc equalisation. Interested readers can obtain a copy of this by forwarding a self-addressed stamped envelope to PW marking the outside of the covering envelope "Texan II." No other correspondence should be enclosed.

Reprints of the original series of articles on the Texan can still be obtained from PW for 40p inc. p/p. Make out cheques/postal orders to IPC Magazines Ltd. and mark covering envelope "Texan Reprint."

PW

Pw APOLLO series

Part 3

VARICAP AM/FM STEREO TUNER

W. POEL*

IN THIS, the third part of the Apollo series, we will look at the way varicap diodes can be used in an AM/FM system to give simple frequency control using a single long-throw slider potentiometer.

The complete tuner offers a specification compatible with most hi-fi systems, yet it is built from a series of AM/FM modules which are simply interconnected on a base board. This method of construction does away with the uncertainties of various pieces of wire trailing around the chassis and allows the constructor to use ready-built modules for sections such as the FM IF strip which otherwise may be considered beyond one's resources to test and align.

THE COMPLETE SYSTEM

The theme of the Apollo series is the "all-electric wireless" so do not be surprised to find that varicaps abound in all the signal frequency tuned circuits. The tuning is accomplished by means of the long

slider pot and the cursor gives direct scale readout. Fig. 3.1 shows a block diagram of the complete unit.

For the front end of the FM section the new Toko EC3302 varicap tunerhead was chosen since it offers a low-cost combination of performance and varicap tuning together with an a.f.c. system that is directly compatible with the output of the IF detector.

The importance of compatibility should not be overlooked since methods of a.f.c. vary considerably and the system used in the LP1186 for example does not suit a quadrature detection system such as that used by the KB4402 IF IC.

The input stage to the tunerhead is an FET with facilities for either 300 or 75 ohm aerials. The mixer stage then feeds the IF signal at 10.7MHz into the IF amplifier block with the local oscillator functioning at the signal frequency plus 10.7MHz in accordance with usual superhet techniques.

The IF amplifier (Fig. 3.2) is worthy of note since it employs two linear phase filters rather than the popular ceramic filters, giving good selectivity at 10.7MHz.

* Ambit International

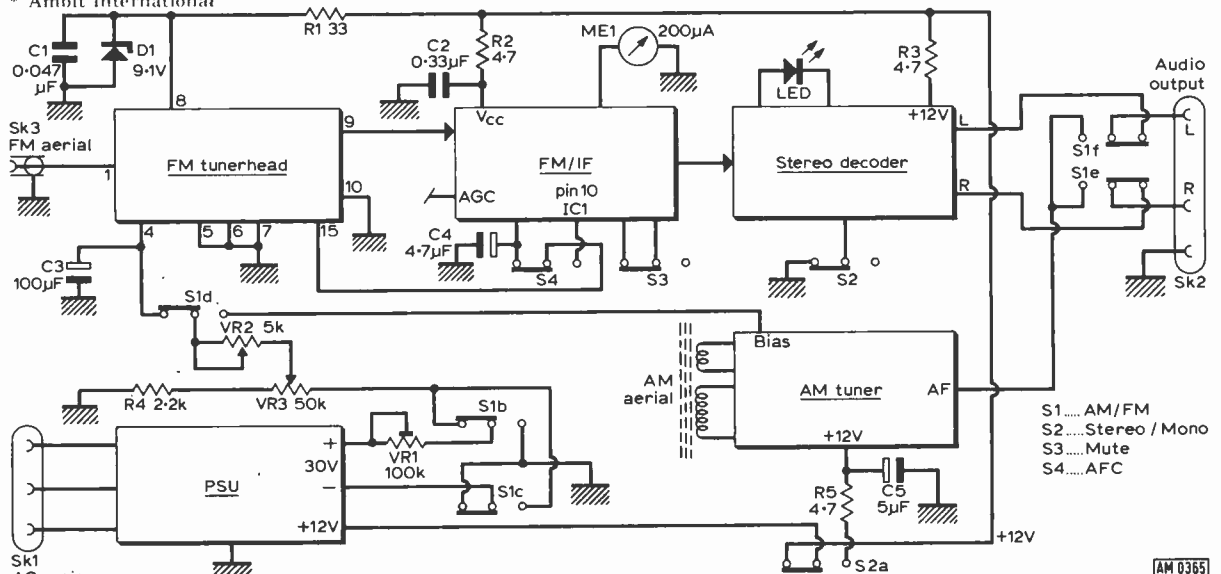


Fig. 3.1: Block diagram of the complete AM/FM Varicap Tuner showing interconnection of units and switching arrangements.

★ components list

FM TUNERHEAD

Toko EC3302U (Ambit)

FM IF MODULE

Resistors

R1 330Ω	R9 10kΩ
R2 470Ω	R10 18kΩ
R3 2.2kΩ	R11 33kΩ
R4 56Ω	R12 4.7kΩ
R5 2.2kΩ	R13 2.7kΩ
R6 120kΩ	R14 4.7kΩ
R7 330Ω	R15 4.7kΩ
R8 470Ω	

All $\frac{1}{2}$ W \pm 5% carbon

VR1 470kΩ skeleton preset

Capacitors

C1 0.01μF	C7 0.01μF
C2 0.01μF	C8 0.01μF
C3 0.022μF	C9 0.01μF
C4 0.01μF	C10 0.01μF
C5 0.022μF	C11 0.01μF
C6 0.22μF	

Inductors

F1, F2 Toko BBR3125N Linear phase filter (2 off)
 L1 Toko TKACS 34342/3 double tuned detector
 L2 22μH choke

Semiconductors

Tr1 BF274
 IC1 CA3089E or TDA1200

STEREO DECODER MODULE

Resistors

R1 18kΩ	R4 3.9kΩ
R2 1kΩ	R5 390Ω
R3 3.9kΩ	

All $\frac{1}{2}$ W \pm 5% carbon

VR1 5kΩ skeleton preset

Capacitors

C1 470pF	C7 0.25μF
C2 0.25μF	C8 2μF 16V
C3 0.5μF	C9 10μF 25V
C4 0.05μF	C10 10μF 25V
C5 0.02μF	C11 0.047μF
C6 0.02μF	

Filter

F1 Toko BLR3107N pilot tone filter

Integrated Circuit and LED

IC1 KB4400 (or MC1310P, CA1310E, SN76115N)
 D1 TIL209 or similar

AM TUNER MODULE

Resistors

R1 47Ω	R5 100kΩ
R2 330Ω	R6 33kΩ
R3 100kΩ	R7 200kΩ
R4 100kΩ	R8 1kΩ
All $\frac{1}{2}$ W \pm 5%	R9 2.2kΩ

Capacitors

C1 1500pF	C10 0.047μF
C2 10μF 25V	C11 10μF 16V
C3 10μF 25V	C12 0.1μF
C4 1500pF	C13 0.1μF
C5 10μF 16V	C14 0.47μF 35V tantalum
C6 0.1μF	C15 4700pF
C7 56pF	C16 4700pF
C8 330pF	C17 4μF 4CV
C9 0.47μF 35V tantalum	
TC1, TC2 5 to 25pF miniature trimmer (2 off)	

Inductors

T1 Toko 6A6371
 T2 Toko 6A6372
 IFT1 Toko YHCS11100AC2
 CF1 Toko CFU050D
 L1 Ferrite rod aerial (see text)

Semiconductors

D1 1N4148
 IC1 LM1820N (or CA3123E, μA720, NE546)
 IC2 MVAM1

POWER SUPPLY

Resistors

R1 100Ω 1W
 R2 4.7Ω $\frac{1}{2}$ W
 VR1 100kΩ skeleton preset
 VR2 5kΩ linear carbon
 VR3 50kΩ linear 150mm slider (Rivlin WS150)

Capacitors

C1, C2 100μF 25V (2 off)
 C3, C5 1000μF 25V
 C4 470μF 40V
 C6-C8 0.1μF (4 off)

Semiconductors

D1, D2 1N4148 (2 off)
 D3-D6 1N4001 (4 off)
 D7 9.1V 400mW Zener
 IC1 78L12
 IC2 MC7818CP

Miscellaneous

T1 Mains primary, 0-20V 0-20V 6VA secondary
 LP1 Mains neon indicator

MISCELLANEOUS

Resistors

R1 33Ω
 R2, R3 4.7Ω
 R4 2.2kΩ
 R5 4.7Ω


Capacitors

C1 0.047μF
 C2 0.33μF
 C3 100μF 10V
 C4 4.7μF 16V
 C5 5μF 16V

Switches, etc

S1-S4 4-way pushbutton unit (6 pole c/o + 2 pole c/o + 2 pole c/o + 2 pole c/o, non-interlocking)
 S5 Mains on/off pushbutton
 ME1 200μA f.s.d. edgewise meter
 Case approximately 400 x 220 x 75mm (16 x 8½ x 3in)
 Escutcheon
 Printed circuit boards, coaxial cable, twin screened cable
 Sk1 Mains input socket
 Sk2 5 pin 180° DIN
 Sk3 Coaxial socket
 D1 7.5V Zener

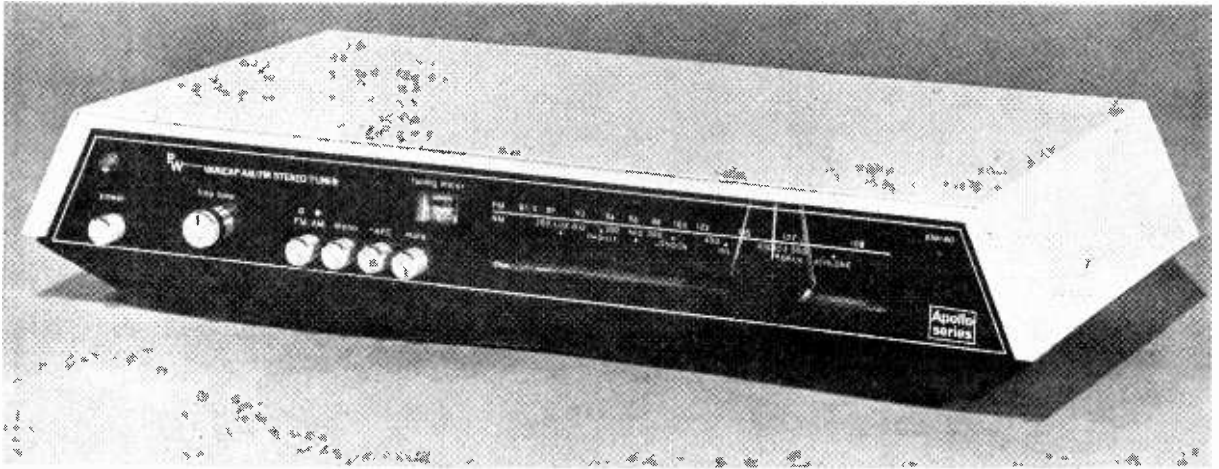Complete kits including case and escutcheon are available from T.T.S. Ltd., 7 West Road, Westcliff-on-Sea, Essex. Kits for FM/IF, stereo decoder and AM modules are available from Ambit International. Order numbers are 91200, 91310 and 9720 respectively.



Linear phase filters have certain advantages over the ceramic types and they may be summarised as follows:

- Lower intermodulation distortion;
- Being LC the temperature stability is better;
- The out-of-band attenuation is superior. This means that whereas some of the signal from the local oscillator may leak through ceramic filters from the front end it will be very much more severely attenuated in this eight-stage filter.

Experience has shown that the susceptibility of the IF amplifier device to local oscillator leakage is unpredictable: some chips may not be affected at all whilst others suffer severe muting as a result of instability induced by this leakage signal.

TRANSISTOR STAGE

The transistor gain stage compensates for the loss caused by the two filters and then feeds the IC with a suitably tailored 10.7MHz signal for amplification, limiting, detection and muting.

Much has already been said about the CA3089E, but the other versions (e.g., Kyodo's KB4402, SGS's TDA1200 and Hitachi's HA1137W) all seem to perform similarly except for the muting function. Although there is a preset on the board to set the threshold of muting, the muting variability of different devices leads to problems in predicting the exact effect that any sample will provide.

Most devices tried to date have offered a quite acceptable level of muting and some are quite faultless.

The meter drive facility is fed to the panel meter to provide a guide to fine tuning. Although a facility exists for centre-zero tuning meters it is not necessary unless one is after a tuner that resembles a Concorde flight deck rather than a means of reproducing euphonic sounds.

QUADRATURE DETECTOR

The quadrature detector of the IC is quite simple but can pose problems in alignment where the double

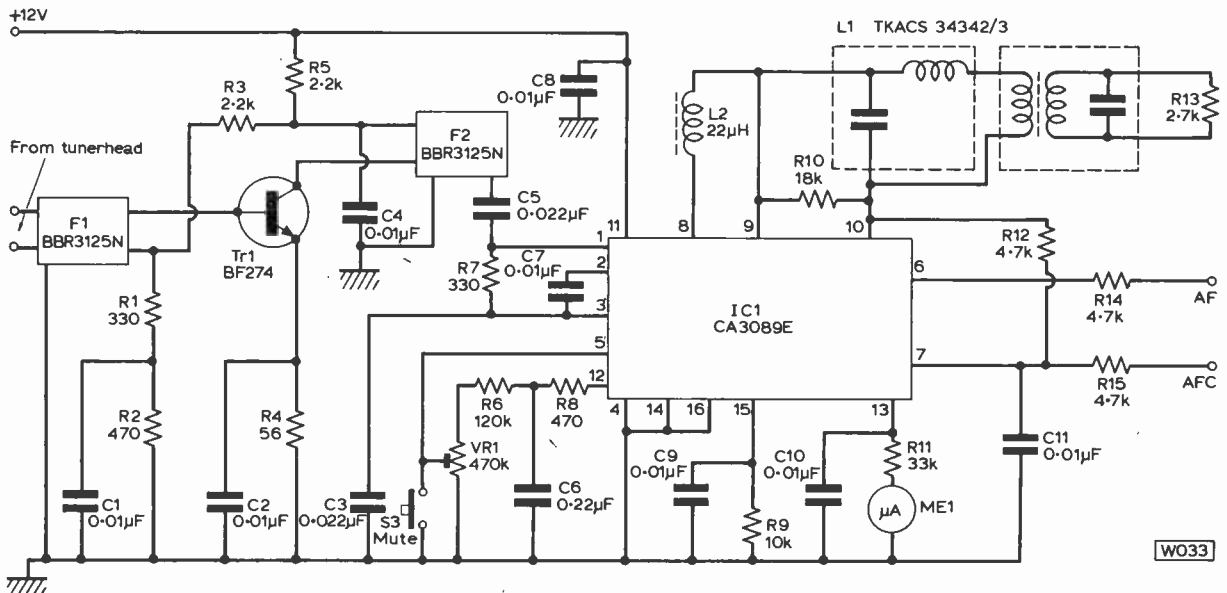


Fig. 3.2: Circuit diagram on the FM/IF section of the tuner. This unit takes its input from the tunerhead.



Now there's Doram, you need never wait for electronic components.

7-day service
Buy the new Doram catalogue and you could have your components within 7 days. If you don't want it back and no questions asked.

No-quibble guarantee
It's just about impossible for a part from us to be wrong. If you do have a problem, we'll replace it for you free of charge. And our guarantee is backed by the fact that we're the largest electronics distributor in Britain.

All included goods
All goods are guaranteed to be first class. We're the only electronics distributor in Britain to offer a 7-day service.

Millions of components
Doram is a brand new service for serious amateurs. It's a catalogue of over 4,000 products available by mail order. You buy the catalogue for 25p (that's a year's worth of savings for the price of a newspaper) and we'll deliver it to your door. We're big enough to order you the best of the best of the best.

And so confident of our service that if we can't get you what you want within 7 days of receiving your order, we'll give you your money back.

Combining the best of service and price, you'll have enjoyed...

So don't delay. Use the first Doram catalogue to make your life a whole lot easier.

For 25p that can't be paid, can it?

ENCLOSE 25p AND ASK FOR THE NEW DORAM CATALOGUE.

Doram Electronics Ltd., PO Box TR8, Wellington Road Industrial Estate, Leeds LS12 2UF

DORAM

Already we know of 22,000 people who like our ideas.

In October of last year we ran several ads announcing a brand-new service for amateur electronics enthusiasts.

The new service was called Doram.

And it promised the first-ever professional electronics service for amateurs.

We said that if you didn't get your order within seven days we'd refund your money. So you'd have no long wait.

We said that we'd only give you top quality, big-name components.

We said that we'd give you a no-quibble guarantee and replace any component which arrived faulty.

And finally we said that we'd offer you a choice of millions of components on over 4,000 product lines.

Buy the Doram catalogue for 25p, we said, and you'll get a fantastic electronic component mail

order service.

We were as good as our word.

And your letters of thanks flooded in. Thousands tried our service. Hundreds went out of their way to write congratulating us.

'Your storeman must be power assisted,' you said.

'I think you are a good firm and live up to your advertisement well,' you said.

'How nice to find a firm which actually stocks all the items in its catalogue,' you said.

And an awful lot more we'd blush to admit.

The Doram catalogue is still available, price 25p.

To encourage you to try us we'll give a £10 voucher to the first catalogue buyer out of the post bag on 30th June. And a £5 voucher to the next 19 new buyers.

Similarly, on 31st July, we'll give a £10 voucher to the first new

catalogue buyer. And a £5 voucher to the next 19 new buyers.

Use the coupon now while the offer lasts. Only these coupons are eligible, and all unsuccessful coupons from the June draw will also be entered for the July draw.

£10 VOUCHERS AND £5 VOUCHERS TO BE WON

I enclose 25p and look forward to receiving my Doram catalogue.

Doram Electronics Ltd., PO Box TR8, Wellington Road Industrial Estate, Leeds LS12 2UF

Name _____

Address _____

DORAM

PW/7/75

POWER UNIT Type A126

Supplying 6, 7.5 or 9 Volt DC at 200 mA.

In moulded case forming a 2 pin 5A mains plug.

2 metre output lead with 4-way multiplex giving 2.1 and 2.5 mm sockets and 3.5 mm plugs.

Price £2.30. Post 10p.



2" and 4" PANEL METERS

2"		4"	
SIZE: 60mm Wide x 45mm High x 40mm Deep.	Movement	SIZE: 110mm Wide x 82mm High x 43mm Deep.	Movement
0-80 micro A.	1250	0-50 micro A.	1400
0-100 micro A.	580	0-100 micro A.	730
0-300 micro A.	170	0-500 micro A.	200
0-1 mA	170	0-1 mA	200
0-5 mA	170	0-5 mA	200
0-10 mA	6	0-10 mA	6
0-80 mA	0.5	0-50 mA	0.5
0-100 mA	0.5	0-100 mA	0.5
0-800 mA	0.5	0-500 mA	0.5
0-1 AMP	0.5	0-1 AMP	0.5
0-2 AMP	0.5	0-2 AMP	0.5
0-25 Volt	15K	0-25 Volt	15K
0-50 Volt	60K	0-50 Volt	50K
0-300 Volt	300K	0-300 Volt	300K
"g" Meter	170	"g" Meter	200
VU Meter	5250	VU Meter	5250

VU Meters are complete with detectors. Modern wide scale. Price 2" £3.20 Post 10p. Price 4" £4.00 Post 10p. Lamps 60p per set.

1/2 watt CARBON FILM RESISTORS

1/2 watt at 70°C E 12 range 10Ω-1MΩ 5% tol above 470 KΩ 10% tol at 95p per 100.

C100 MULTIMETER

Special Offer

Compact General Purpose Mini Multimeter. Input Resistance 1000 ohms per volt

Range:

AC Volts 0-15, 50, 250

1000 V

DC Volts 0-10, 50, 250

1000 V

DC Current 0-1 mA

0-100mA

Resistance 0-150K ohms

Size 60 x 24 x 90 mm

Complete with Batteries, Test Prods, Instructions. Special price £3.20 Post 25p.



C1001 MULTIMETER

Input Resistance 20,000 ohms per volt
Overload protection
150 μA movement, clear scale
Ranges—AC Volts 0-10, 50, 250, 1000V
DC Volts 0-5, 25, 125, 500, 2500V
DC Current 0-50 mA
Resistance 0-60 Kohms, 0-6 Mohms
Decibels -20 to +22 dB.
Carrying Case, Test Prods and Batteries included.
Size: 11.5 x 8.3 x 2.7 cm.
Price £9.85. Post 20p.

TRANSFORMERS

CASED TRANSFORMERS

Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets, and are available with 110 volt or 240 volt output. (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices.

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA	Ref. No.	Price Cased	Price Plugs	Price Open	Post
60	149	8.35	0.88	4.37	0.56
100	150	9.15	0.88	4.90	0.64
200	151	11.45	0.88	8.14	0.80
250	152	12.90	0.88	9.30	0.88
350	153	16.50	0.88	11.88	0.95
500	154	17.25	0.88	18.63	1.13
750	155	27.10	1.10	20.59	O.A.
1000	156	35.40	1.10	29.15	O.A.
1500	157	42.00	1.10	33.37	O.A.
2000	158	49.75	2.64	37.10	O.A.
3000	159	78.15	2.64	58.55	O.A.

12 & 24 Volts Prim. 200-240V.

VA	Ref. No.	Price Cased	Price Plugs	Price Open	Post
12V	24V				
0-3	0-15	242	1.53	0.34	
0-5	0-25	111	1.33	0.34	
1	0-5	213	1.74	0.47	
4	1	71	2.30	0.47	
6	2	18	2.98	0.56	
8	3	70	4.13	0.56	
10	4	108	4.56	0.64	
12	5	72	5.20	0.72	
16	6	116	5.51	0.72	
20	10	115	10.42	0.88	
30	15	187	13.25	1.01	
40	20	232	14.85	O.A.	
60	30	226	16.83	O.A.	

30 Volts

VA	Ref. No.	Price Cased	Price Plugs	Price Open	Post
0-5	112	1.90	0.47		
1	79	2.40	0.56		
2	3	3.50	0.56		
3	20	4.50	0.64		
4	21	5.15	0.72		
5	61	6.40	0.72		
6	117	7.18	0.88		
8	88	9.55	0.95		
10	89	9.67	0.95		

AUTO TRANSFORMERS

VA	Ref. No.	Price Cased	Price Plugs	Price Open	Post
Tapped at 115, 220, 240 Volts		3.85	0.20	1.71	0.47
Tapped at 115, 200, 220, 240 Volts					
150	4	6.38	0.20	4.18	0.56
200	65	7.04	0.20	4.95	0.64
300	66	8.00	0.20	5.81	0.72
500	67	10.99	0.20	8.85	0.88
750	82	13.82	0.85	10.80	0.95
1000	84	17.27	0.85	13.68	1.13
1500	93	21.87	0.85	18.81	O.A.
2000	95	33.11	1.60	24.25	O.A.
3000	73	47.94	2.10	35.10	O.A.

50 Volts

Prim. 200-240V. Sec. 19, 25, 32, 40, 50V.	Amps	Ref. No.	Price £	Post £
0.5	102	2.58	0.47	
1	103	3.48	0.56	
2	104	5.03	0.64	
3	105	5.81	0.72	
4	106	7.88	0.88	
6	107	12.30	0.95	
8	118	13.20	1.13	
10	119	17.02	O.A.	

60 Volts

Prim. 230-240V. Sec. 24, 30, 40, 48, 60V.	Amps	Ref. No.	Price £	Post £
0.5	124	2.30	0.56	
1	126	3.41	0.66	
2	127	5.09	0.72	
3	125	7.53	0.80	
4	123	8.75	0.95	
5	40	9.75	0.95	
6	120	11.20	1.01	
8	121	15.00	1.19	
10	122	18.20	O.A.	
12	189	18.60	O.A.	

MINIATURE AND EQUIPMENT

Prim. 240V with screen.	Sec. 1 Volts	Sec. 2	Milliamps	Ref. No.	Price £	Post £
3-0-3	—	200	—	238	1.50	0.25
0-6	0-6	500	500	234	1.38	0.25
0-6	0-6	1000	1000	212	1.90	0.47
0-9	0-9	100	—	13	1.40	0.25
0-9	0-9	330	330	238	1.50	0.25
0-8-9	0-8-9	500	500	207	1.93	0.34
0-8-9	0-8-9	1000	1000	208	2.75	0.47
0-10-15	—	40	—	240	1.35	0.25
0-15	0-15	200	200	336	1.38	0.25
20-0-20	—	30	—	241	1.35	0.25
0-20	0-20	150	150	237	1.38	0.25
0-15-20	0-15-20	500	500	205	2.73	0.56
0-20	0-20	300	300	214	1.93	0.47
0-20	—	3500	N.O. SCREEN	1110	3.30	0.64
20-12-0-12-20	—	700 (11/C)	—	221	2.20	0.47
0-15-20	0-15-20	1000	1000	206	3.50	0.66
0-15-27	0-15-27	500	500	203	3.00	0.56
0-15-27	0-15-27	1000	1000	204	3.85	0.56

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 20p	50 P.I.V. 35p	100 P.I.V. 65p	50 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 50p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 30p	400 P.I.V. 60p	600 P.I.V. 75p	400 P.I.V. 80p

ADD 10p P & P PER ORDER

PLEASE
ADD 8%
FOR VAT

POWER UNIT Type CC 12-05

Output switched 3, 4.5, 6, 7.5 and 12 volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players etc. Size 7.5 x 5.0 x 14.0cm. Price £3.95. Post 25p.



MINIATURE NEONS

6mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor 150K ohms for 240 Volt operation. Price: Packet of 10 for 60p. Postage 15p.

A.S.P. LTD.

DEPT PW6, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

INVERTORS

240v—50Hz. from your 12v car battery.
25 watt—£3.90 + 30p p & p.
50 watt—£4.80 + 30p p & p.
75 watt—£5.95 + 30p p & p.
150 watt—£11.30 + 80p p & p.
300 watt (12v)—£28.80 + £1.05 p & p.
300 watt (24v)—£22.78 + £1.05 p & p.
All above invertors are in kit form but may be purchased built up & ready for use. Price list sent on receipt of stamped addressed envelope.

P.W. AUTOMATIC EMERGENCY SUPPLY

250v—50Hz—150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 73 P.W. Complete kit of parts (excluding meter) £22.50 + £1.10 p & p.

COMPLETE FLUORESCENT LIGHT INVERTOR KIT

8 watt—12v—Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for, factories, hotels etc. 12"—8 watt £2.95 + 25p p & p. 21"—13 watt. £3.30 + 30p p & p.

TRANSFORMERS & COILS

Both high volume & small order capacity available for Mains, R.F., & I.F. Transformers. Before you buy elsewhere let us quote you and see what you save.

V.A.T. at 8% included.

TRADE & EXPORT ENQUIRIES WELCOMED

ASTRO ELECTRONICS, 10A SPRINGBANK RD., CHESTERFIELD, DERBYSHIRE

poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker
Super-thin construction permits new installation ideas.



Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz. Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 11-3/4" x 14-11/16". Weight: 19 ounces.

£8.50 each Stereo pair £16.50

INCLUSIVE OF VAT AND POSTAGE

web europa

P.O. Box 9, Ruthin Clwyd

tuned detector coil option is chosen. It operates by simply mixing the original FM signal and an out-of-phase portion so that the original AM results. A single tuned coil can be aligned by a meter but a double tuned coil can only be set up accurately with aid of a wobulator to observe the characteristics of the "S" curve while the adjustment is carried out.

A single tuned detector will give 0.5% total harmonic distortion though in practice this is usually only 0.3% with standard broadcast levels. The double tuned circuit gives 0.1% THD when accurately set up. In practice this figure can again be improved to around 0.08% which is rather better than most FM tuners costing over £100 claim in their specification.

Layout is everything with the CA3089E IF amplifier. Deviate from the suggested circuit at your peril since instability can easily be introduced, not easily traced and cured only by revising the track layout until it ceases.

STEREO DECODER

From the detector the audio passes through the mute gate to the stereo decoder (Fig. 3.3). The Kyodo KB4400 (equivalent to the MC1310P) performs the task of decoding a multiplex signal and producing the two discrete channels for power amplification.

Since the various switching signals tend to produce a series of unpleasant waveforms together with the pilot tone at 19kHz and the 38kHz regenerated signal, trouble is removed at source with the Toko pilot tone filter on the module. The block contains two

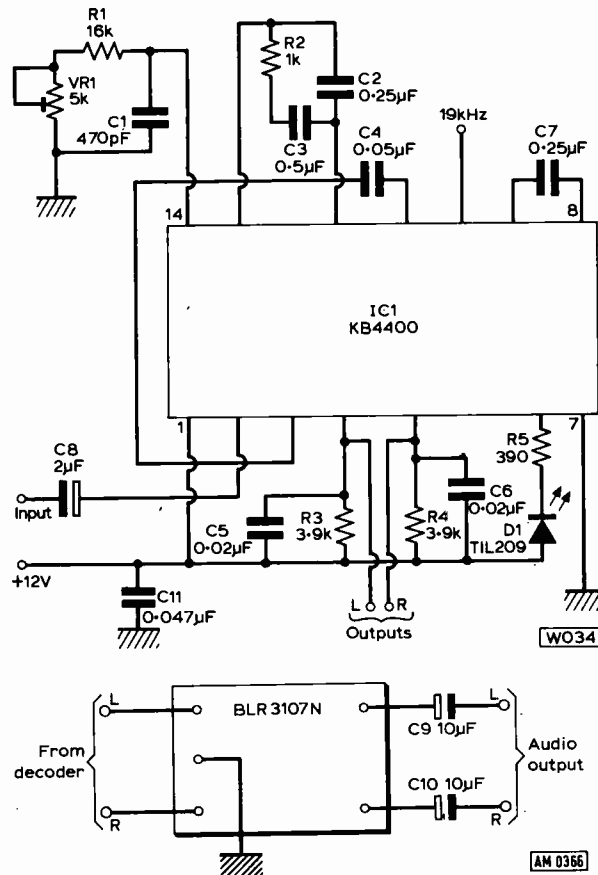


Fig. 3.3: Circuit diagram of the stereo decoder and pilot tone filter.

notches: one at 19kHz and one at 38kHz, plus a low-pass filter with a roll-off commencing at 15kHz which is the upper limit of the multiplex bandwidth. When correctly matched only 1dB will be lost at 15kHz which is not likely to spoil listening enjoyment. If allowed through unattenuated the pilot tone and the residual hash could cause amplifier problems of intermodulation and high frequency instability.

Facilities are provided to switch out the muting and to manually defeat the operation of the stereo decoder. On weak stereo signals intermittent operation of the stereo decoder will cause annoyance if left in the automatic mode.

On switching to AM the same power supply is used for the tuning voltage but it is switched to positive earth system to account for the different orientation of the AM tuning diode block.

The 12V supply is fed to the AM module. Operation of this particular unit has been extensively covered on Part 1 of this series. The quality of the AM section is truly excellent providing a very tolerable partner to the FM section. The purity of the oscillator waveform is good and this results in little interstation noise when tuning the medium wave.

POWER SUPPLY

Two windings are required for the secondary of the transformer to accommodate the different earth requirements for the AM tuning voltage from the rest of the equipment. Rectification is carried out in conventional fashion but the stabilisation and smoothing make use of one of the popular 78 series three terminal regulator ICs. Fig. 3.4 shows the power supply circuit diagram.

The Marconi International Marine Co. Ltd., of Chelmsford, has asked us to point out that there is no connection between the Apollo SSB/General Purposes marine communication receiver manufactured by that company and any receiver described by us in our current Apollo series of articles.

TO BE CONCLUDED

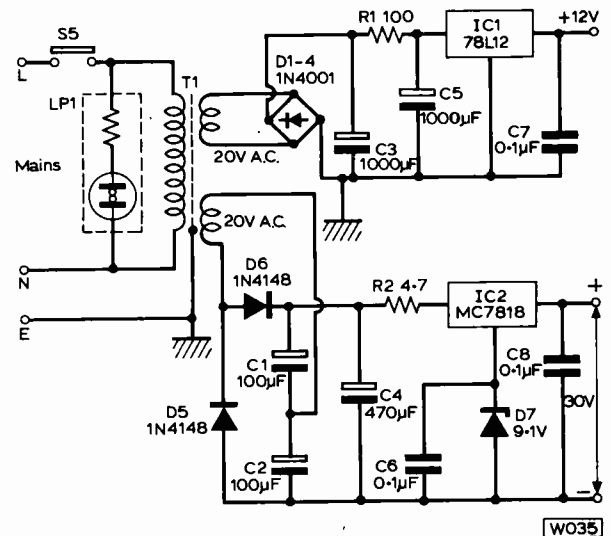


Fig. 3.4: Circuit diagram of the power supply section of the AM/FM Varicap Tuner.

Dear Sir,



Equally tempered or Just natural

In reply to P. G. Quatermain (Letters, P.W. May 1975) may I offer one reason why purists might wince at the idea of an organ tuned to the equally tempered scale?

As Mr. Quatermain points out, notes tuned to the equally tempered scale will sound at a slightly different frequency to those of the Natural or Just scale and he correctly observes that within an octave, these tiny errors will not be noticed. However, the Just scale represents the ratios of frequencies which sound most pleasing to the human ear, so the slight errors which arise through equal temperament are in fact small dissonances; if there were circumstances under which these errors could add, a discordant note might result.

Alan Douglas suggests (Electronic Music Production, Pitman 1973, p 31) that when dealing with pure sine waves, results become dubious after adding waves corresponding to a fundamental and its sixth harmonic. If we are adding complex waves, each with its own harmonic series, the chances of discord are more likely. In the case of the "Easybuild" organ with its limited footages and stop-circuits tending to suppress high harmonics, this problem is likely to be negligible, but when considering a large electronic or pipe-organ, the possibility of discord is very real. Thus intervals are "stretched" away from equal temperament to tune out dissonances the rule being to reconcile purity of the octaves with a concordant

sound. It is in these circumstances that the skill of an experienced organ tuner really counts.

The fact that notes generated by frequency-division cannot be "stretched" has precluded its use in large electronic organs designed for classical or church use. Examination of these instruments reveal that they usually use individually tuned oscillators, for example the Miller Organ, or alternatively pipe organ sounds are somehow recorded, stored and retrieved electronically. The latter system has been brought to a high degree of perfection in the Allen Computer Organ which uses LSI devices to store digitally encoded pipe organ tones.

Nonetheless, now that CMOS frequency dividers and generators are available, construction of a small organ is at last a practical reality even for the beginner in electronics, and Mike Hughes deserves thanks for his clear and thoughtful instructions on the subject.—Thomas Weil (Croydon).

Ouchⁿ!

The letter from Mr. Rix in the May issue has given me the final prod to write a letter. I have wanted to write for quite some time on the subject of the misuse of certain of the symbols used for the metric system multipliers, namely 'k' and 'm'. As we should all know there is no upper case K used at all, only the lower case k meaning $\times 1,000$. With the M both upper and lower case are in use with the upper case M meaning $\times 1,000,000$, and the lower case m meaning $\times 1/1,000$, respective names are mega and milli.

In a single page advertisement appearing in P.W. one regular advertiser used upper case K no less than 21 times in lieu of lower case k.

In addition we were offered the following interesting items:

Grid Dip Meter—to 280 millihertz
A.C. millivoltmeter—to 1.2 millihertz
R.F. Generator—to 500 millihertz
Portable Radio, MW/LW—600 megawatt output (Rather whacks Mr. Rix!)

L.F. Generator—to 1 millihertz
VHF timer—120-160 millihertz
P.S.U. 6-9V—300 megamps.

In the current issue, however,



things have improved somewhat, as we have K in place of k only eight times.

Turning now to Mr. Quatermain's letter (also of the May issue) there are two numerical misprints in the third paragraph. Line five should surely read the ratio is 1:1.0594 while line seven should read $1.0594^{12} = 2$.—James Livie (Heston).

Car wiper delay modification

With reference to the car wiper delay unit as featured in the May issue of *Practical Wireless*, I wish to point out that during the last few years permanent wiper motors have been fitted to many cars. These motors are wired up as shown in Fig. 1.

As there were no details in the article concerning fitting the delay unit to this type of motor, I decided to devise a method of my own. The only extra components needed were a miniature relay (12V 185ohm coil) with two pairs of changeover contacts, wired in parallel, and a DPDT switch in place of the one specified, Fig. 2. I find this arrangement works very well and I hope that it will be helpful to other readers.—Colin Robertson (King's Langley, Herts).

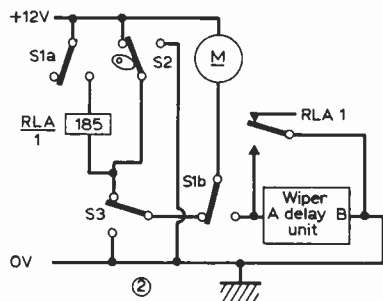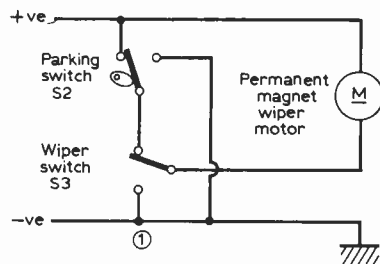

All switches and relay contacts shown in the "off" position.

W032

Fig. 1: above, shows the circuit of a permanent magnet car wiper motor, while Fig. 2 shows the connections necessary for the May PW wiper control to be used with this type of motor.

Sinclair Scientific kit

Britain's most original calculator – now in kit form

The Sinclair Scientific is an amazing calculator.

It offers logs, trig, and true scientific notation over a 200-decade range – features normally found on calculators costing around £50 or more.

Yet even ready-built, it costs a mere £21.55 (including VAT).

And as a kit it costs under £15!

Forget slide rules and four-figure tables

On the Scientific, you can handle *directly*

all three trig functions, their inverses,

\log_{10} , antilog_{10} , giving quick access to x^y (including square and other roots),

plus, of course, the four arithmetic functions and any calculation based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.



**Now only
£14.95
(inc. VAT)**

So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.

All parts are supplied – all you need provide is a soldering iron and pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer – they're still exceptional value. Use the order form.

Features of the Scientific

- 12 functions on a simple keyboard
- Scientific notation
- 200-decade range
- Reverse Polish logic
- 25-hour battery life
- Genuinely pocketable

Features of the Cambridge

- Only 4½" × 2" × 1½". Weight 3½ oz.
- Fully-floating decimal point.
- Algebraic logic.
- Constant on all four functions (+ - × ÷).
- Constant and algebraic logic combine to act as limited memory.
 - Clear, bright 8-digit display.
 - Operates for weeks on 4 AAA batteries.

Sinclair Cambridge kit

**Now only
£9.95
(inc. VAT)**



At its new low price, the Sinclair Cambridge kit remains unbeatable value.

The Cambridge is now Britain's most popular pocket calculator. And it's not surprising. Check the features – then ask yourself what other calculator offers such a powerful package at such a reasonable price.

Take advantage of this money-back no-risk offer today

The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee any correctly-assembled calculator for a year. This guarantee also applies to calculators supplied in built form.

Simply fill in the preferential order form below and post it – today!

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Scientific kit – £14.95 inc. VAT

Scientific built – £21.55 inc. VAT

Cambridge kit – £9.55 inc. VAT

Cambridge built – £13.99 inc. VAT

*I enclose a cheque for..... made out to Sinclair Radionics Ltd, crossed.

*Please debit my *Access/Barclaycard account number: _____

*Delete as required

Signed _____ Name _____

Address _____

Please print. FREEPOST – no stamp required.

Sinclair Radionics Ltd,
London Road, St Ives, Huntingdon, Cambs., PE17 4JH. Tel: St Ives (0480) 64646
Reg. no: 699483 England. VAT Reg. no: 213 8170 88

sinclair

FLEA POWER PROVIDES THE PROOF !!!

THE EXPERTS AGREE—A GOOD TRANSMITTING AERIAL IS A GOOD RECEIVING AERIAL !

A "flea powered" VFA from an average location, operated mainly in the "rush hours" regularly penetrates the "jungle" on 80, 40 and 20 metre bands. The VFA is ONLY 230cm long but by combining LOW ANGLE with a virtual ABSENCE of POWER WASTING HARMONICS the VFA is incredibly efficient.

ANY ANTENNA WILL RADIATE HIGH POWER—WE'RE TALKING ABOUT "FLEA" POWER!!

PARTRIDGE have a complete **VFA SYSTEM**, correctly terminated for your equipment ranging from modern communications gear to a modest solid state radio. Don't be satisfied with anything less than the **PARTRIDGE WORLD RECORD ANTENNA SYSTEM!** Make your selection from the list below:-

(Each **SYSTEM** consists of the elegant gold stove enamelled 7' 6" VFA and a matching finish **JOYMATCH A.T.U.**, despatched direct by parcel post—our risk). (All prices delivered—our risk). Prices subject to alteration without notice.

SYSTEM 'A' for modern Communications Receivers	£32.76
SYSTEM 'D' for other S.W. and M.W. receivers, all types	£24.43
SYSTEM 'J' for TXs and TCVRs up to 500w PEP 160 thru 10m (pa inpt)	£40.72
SUPER SENSITIVE general coverage DX-CRYSTAL SET that REALLY WORKS, not a toy, complete with Aerial and a sensitive matching Earpiece	£4.73
COMMUNICATIONS HEADPHONES , 8 ohms, matches most modern Comm. Rxs.	£4.82
JOYMATCH Artificial Earth (ground) switch tuned	£7.20
A.G.T.U. Artificial Earth D.I.Y. add on unit for your A.T.U.	£0.70
Radials for the A.G.T.U. cut to required band, each	£0.72
"INVISIBLE AERIAL" wire, tough PVC covered tinned copper 22swg per 10m	£0.72
A.G.T.U. supplied fitted to JOYMATCH A.T.U.'s (less radials)	£0.93
FIELD STRENGTH METER , (Japanese)	£2.10
VALVES , complete set for 9R59DS & 9R59DE, including OA2 stabiliser	£6.12

PARTRIDGE SUPER PACKAGE

COMPLETE RADIO STATION FOR ANY LOCATION. Comprising: Trio QR666 Gen. Cov. RX, Headphones VFA., System 'A', all connecting cables, del. (our risk)

£185.18

Send stamp for details and expert advice.



Phone 0843 62535
or 62839
(after office hours)
G3CED G3VFA



And now the FANE 'SPECIALIST' RANGE

LOUDSPEAKERS OF OUTSTANDING QUALITY FOR THE DISCRIMINATING PROFESSIONAL

Features include **ROBUST CAST ALUMINIUM CHASSIS** and **2" EXTRA HIGH POWER VOICE COILS**

All models available in impedances of 8 ohm or 15 ohm Guarantee: 2 years

Recommended Prices inc. VAT

12" 'DISCO 60' 60 watts R.M.S.

Linen Cone Surround. Fitted extra large Tweeter Cone. Frequency Range 50-15,000 Hz

£29.95

Rec. Retail Price

12" 'GUITAR 60L' 60 watts R.M.S.

Plastiflex Cone Surround. Aluminium Centre Dome. Frequency Range 50-9,000 Hz.

£28.95

Rec. Retail Price

DESIGNED FOR LEAD GUITAR

12" 'GUITAR 60B' 60 watts R.M.S.

Linen Cone Surround. Frequency Range 45-9,000 Hz.

£28.50

Rec. Retail Price

FOR USE IN MULTIPLES FOR BASS GUITAR

12" 'PA 60' 60 watts R.M.S.

Plastiflex Cone Surround. Fitted Tweeter Cone. Frequency Range 50-15,000 Hz. Rec. Retail Price

£29.98

FOR GENERAL PURPOSE PUBLIC ADDRESS

15" 'BASS 70' 70 watts R.M.S.

Linen Cone Surround. Frequency Range 40-7,000 Hz. Can be used singly but ideally TWO UNITS IN A SINGLE CABINET.

£42.50

RECOMMENDED FOR ALL BASS INSTRUMENTS



Illust
12"
'DISCO 60'

'POP' RANGE

New prices of these **FAST SELLING** and **RELIABLE UNITS**

POP 15 12" 15w	£7.99
POP 25T 12" 25w	£10.99
POP 50 12" 50w	£15.99
POP 55 12" 60w	£19.99
POP 60 15" 60w	£21.95
POP 70 15" 70w	£23.50
POP 100 18" 100w	£39.95

Available in impedances of either 8Ω or 15Ω

AND for those who can afford the very best there is our range of **'CRESCENDO'**

MODELS

12" UNITS from **£45.95**

Rec. Retail

15" UNITS from **£63.95**

Rec. Retail



Please send S.A.E. for leaflets on any of above ranges

Distributors (Wholesale & Retail Trade): **LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.** Manufacturers enquiries to: **FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS.**

HIGH FREQUENCY HORN UNITS

MODEL 910 Mk II

Rating 50 watts with recommended filter. Rec. Price

£19.62

MODEL 912 with even higher sensitivity

Rec. Price **£22.57**

MODEL 920 Mk II (as illust) Rec. Price

£54.98

significantly increased sensitivity. Rating with recommended filter 100 watts

HPXI HIGH POWER CROSS-OVER UNIT

Suitable for above Horn Units Rec. Price **£2.90**



Prices shown correct at 1 May, 1975

HOTLINES

ON RECENT DEVELOPMENTS

ORGAN CHIP

MUSIC lovers and electronic organ tyros can rejoice at the latest offering from Italian-based SGS-Ates, manufacturer of integrated circuits. One of its latest prodigies bears the innocent title of M251. It is claimed to be the first IC ever to integrate bass lines, chords and arpeggios.

You have to actually hear this tiny chip working to appreciate just what it will do. It plays the correct bass notes, the right chord and the right arpeggio accompaniment (if you want it) all in one go, automatically—and it changes key, too.

Having heard this wonder chip, I feel quite sure that organ players of the future will just whisper the tune into a loudspeaker and the organ will reply, "If you can 'um it mate, I'll play it".

D.I.L. SWITCHES

At the Paris Components Show earlier this year many people were exhibiting dual-in-line switches. These seem to be coming on to the market now and could be of use to the amateur constructor who specialises in miniature and sub-miniature projects.

Eight tiny single pole changeover switches can be accommodated in a single 16-pin DIL package with minute switch actuators brought out on top of the case and operated with a rocker action, or at the sides and operated using a slide action. How about a fixed inductance ferrite rod midget radio where you could just switch in (or out) various values of capacitance to tune the stations in?

CHOOSING 'Cs'

Ah, says you, getting exact values of capacitance isn't quite that simple. I can buy a 100pF capacitor, but what if I want an odd value to tune in some station exactly?

Well, you could try using a Vee Cal TrimChip capacitor. It's an adjustable capacitor but its fixed—if you see what I mean? These tiny chip capacitors have a series of minute adjustment points on their sides. By connecting these points in a variety of

configurations, it is possible to vary the capacitive value of the fixed capacitor. The amount by which you can vary the capacitance of individual units ranges from 1pF to 20pF per increment. The components are manufactured to a nominal value. As an example, a capacitor with a base value of 100pF and with ten incremental adjustments can be set to any value between 100pF and 152pF. It can be done by rubbing the sides with a soft lead pencil—readers are left to draw their own conclusions!

Typical size of a Vee Cal TrimChip is 0.18in. long by 0.005in. wide. Experimental kits are available which consist of a selection of TrimChips, a metallic epoxy (for setting the final capacitance instead of using pencil), dispenser and a book of instructions.

GETTING TOUCHY

Another interesting new approach (in practical terms, the idea's been there for some time) was talk by one manufacturer/supplier to market touch-sensitive keyboards for things like electronic calculators. The keyboards are not, as I understand it, capacitive and they do need a very slight "push", however, the force is so small that they could be fairly described as touch sensitive.

The touch causes the plastic film itself to move less than four thousandths of an inch and this is sufficient to cause a switching effect since the plastic film back is metallised. The open circuit resistance is around the 10M Ω mark and claims have been made that the contact resistance is only 0.1 Ω . A touching story.

ELECTRONIC PATTERNS

When was the last time you bought yourself a decent dress? (So, why shouldn't lady electronics/radio enthusiasts read Ginsberg?). Think of the processes involved in making a double-knit pattern. Sketches through to finished product. A long business.

Not anymore, though. An Israeli company has brought out a machine which seems to do it all in no time. The designer sits comfortably at the console with a colour display. Here, the sketch can be "sketched" and

colour varied and/or altered until they suit. The input of the whole system relies for its nourishment on an input of nice fresh sketches. It promptly converts these into a digital code. Needless to say there's a computer hidden in the system somewhere which assures that everything happens in the right order.

The system takes only one hour to change a sketch into colour separations and that used to take 150-200 hours before. (The system can also be used to do wallpaper patterns).

KNITTING LIBRARY

How does it automate things still further? Well, the output, in the case of a double-knit pattern, is simply fed to the knitting machines. A "library" of 999 colours is held in the system which gives quite a choice. Ah well—Ginsberg's going to miss his old spinning wheel.

MINI HENRYS

Earlier, we looked at some variable chip capacitors. I see that some miniature variable inductors are now on the US market. There's 37 standard values in the range which goes from 0.001 μ H up to 1,000 μ H—but they're variable, too! A minute threaded core allows a 20% variation from nominal value. But there's still more to come—the size. Each unit measures an almost unbelievable 0.15in. x 0.2in. with a height of 0.16in. It looks as though tweezers and a magnifying glass will become a standard part of the constructor's tool box.

NEW OP AMP

I was interested to hear of the new CA3130 op amp which manufacturers RCA put out. It is an interesting beast because it combines MOS/FET, bipolar and COS/MOS. The input resistance is 1.5 x 10¹² Ω or 1.5T Ω , and the signal voltage gain is 110dB.

**SPECIAL
PRODUCT
REPORT**

HEATHKIT GR-78

**GENERAL
COVERAGE
RECEIVER**



THE GR78 is basically a portable receiver for the short wave listener and radio amateur although the medium and part of our long wave band are included. The LW band is particularly useful now that the BBC has taken it into its head to broadcast many sports commentaries on this band only!

One of many interesting features of the set is the provision in the kit of two bandspread scales, one for the amateur bands and the other for the short wave broadcast bands, the constructor using the one of his choice. Since most SWL's eventually turn to the amateur bands in the course of time so the scale could be changed accordingly.

If the idea of a portable receiver conjures up thoughts of piles of dead expensive batteries, forget it! The GR78 has an internal nickel-cadmium battery which is automatically charged from the mains when the set is plugged in but switched OFF, or from an external 12 to 15V DC supply if that is all that is available. The internal battery can be expected to maintain a full charge even if it is used for as much as eight hours daily at average listening levels. No need to worry about overcharging either, since the set can be left plugged into the mains but switched off for as long as a month without the trickle charge facility damaging the battery. A spring-loaded switch on the dial lights helps to reduce the load on the battery.

CIRCUIT DETAILS

The internal telescopic aerial, or external aerial, feeds into a 40673 mosfet RF amplifier stage which has its own gain control. Another 40673 is used in the first mixer which derives its injection voltage from an MPF105 Hartley oscillator operating on signal frequency plus 455kHz on Bands A, B, C and D and minus the IF on Band E. On Band F it operates at 4034kHz higher than the signal frequency when it feeds into a second mixer stage, again using a 40673. The 2N3694 conversion oscillator is crystal controlled on 3579kHz also feeding into the second mixer stage, the output of which is again 455kHz, the IF on the lower frequency bands.

The double IF of 455 and 4034kHz on Band F is designed to reduce the interference from images which can be very troublesome on the higher frequencies when a single IF of 455kHz is used. The change from single to double conversion is achieved automatically with the band switching.

The output of the second mixer IF stage is fed to four 455kHz ceramic filters, eliminating any need for IF alignment. Two 2N3694 IF amplifier stages feed into a 40673 product detector for SSB and CW, another 2N3694 being used in the BFO. On AM a simple diode detector circuit is employed. A portion of the IF signal is fed to an AGC amplifier stage providing two control voltages, for the RF amplifier and the first IF amplifier.


The audio from the PD can be fed direct to the 2N3393 audio pre-amplifier or via a simple automatic noise limiter stage. Another stage of audio precedes the 2N2430/31 complementary pair output stage, feeding either the internal speaker or headphones. The relative signal strength meter is part of the first IF amplifier circuit and is operated by the AGC line voltage.

Instant calibration checks are obtainable from a 500kHz crystal calibrator using a 2N3393, the output being fed into the aerial input circuits.

CONSTRUCTION

Construction is considerably simplified by the use of six boards; one main board for the power supply and certain auxiliary components, a receiver board for the IF stages, etc. and four switch boards for the aerial, RF, mixer and oscillator stages. The only point of criticism is that holes on the switch boards had to be slightly enlarged to take some of the switch tags but this did not take very long to perform.

Installation of the boards and chassis construction proceeds logically with even the smallest nut and bolt being specified as it is used. There is a line sketch of every item used, down to washers, and this is very helpful, even to the experienced constructor, when faced with a shapeless two-lead blob that turns out to be a 300µH inductor! Where possible components are marked with their part number.

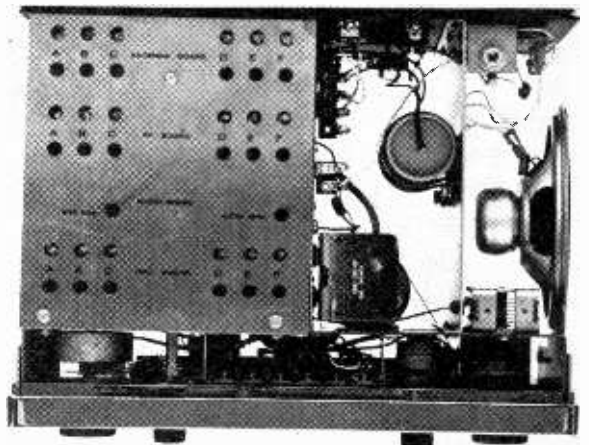

The plate covering the RF and oscillator boards is clearly marked for easy alignment. The capacitor-like object to the left of the speaker is the nickel-cadmium battery.

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 £6-60 Carriage free
35W RMS 25-50V
7 transistors, 7 diodes

SA50 £8-50 Carriage free
50W RMS 25-65V
7 transistors, 7 diodes

SA100 £12-50 Carriage free
100W RMS 45-70V
10 transistors, 7 diodes

- ★ 25Hz-25kHz
- ★ 0-2% distortion
- ★ Noise—80dB
- ★ 500mV into 20K
- ★ 4-16 ohms
- ★ Simple wiring
- ★ Short and open circuit proof
- ★ Continuously rated
- ★ Top-grade components



THE SAI100 MODULE

POWER SUPPLIES

UNSTABILISED—READY WIRED & FUSED

PU45 Suits 2 SA35 or 1 SA50 (4 ohm) £6-50 Carriage 50p

PU70 Suits 2 SA50 (8 ohm) or 2 SA100 £9-50 Carriage 60p

STABILISED

PS45 Suits 2 SA35 or 1 SA50 (4 ohm) £5-50 Carriage free

MT45 Transformer for above £3-90 Carriage 50p

PS70 Suits 2 SA100 £6-50 Carriage free

MT70 Transformer or above £5-50 Carriage 60p

N.B. PS70 is not suitable for the SA50

120 watt module complete with built-in supply—extra heavy duty £24-75 Carr. 60p

Mk II STEREO DISCO MIXER £29-50

Carr. 60p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, base, treble. Left/Right fade, deck volume, bass, treble, h/phone select. vol, Mains. Size 17 1/2 in x 3 in x 4 in deep.



DISCO MODULE £12-50

Carr. 50p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12 1/2 in x 3 in x 2 in deep.



3-CHANNEL SOUND-LITE £24-75

Carr. 50p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12 in x 3 in x 2 1/2 in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7-90 Carr. free
High sensitivity compact handles 1kW. Full wave operation.

ADD 8% VAT TO ALL ORDERS


MULTI-PURPOSE MIXERS

M4HL £25-00 Carr. 60p
M6HL £35-00 Carr. 60p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

VA30 CHANNEL MODULE £3-90 Carr. free

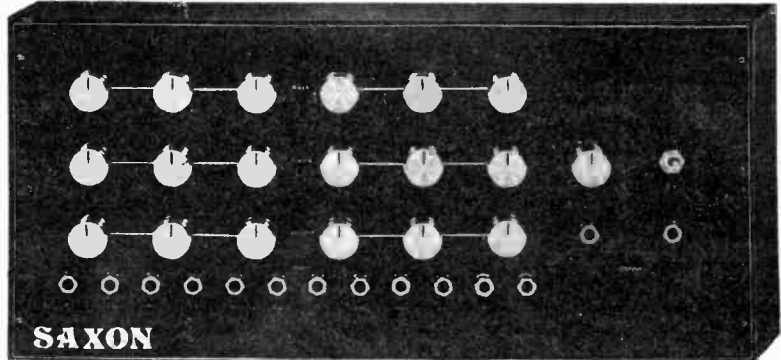This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)



SAXON CSE 100

COMPLETE AMPLIFIER

£39-90 Carr. 60p

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vynide case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE50 £33-00 Carr. 60p

NEW !!

SAXON MULTIMIX 100 £57-00 carr. £1-00

100W rms four inputs slider controls plus master slider. Wide range bass and treble controls. Fantastic value, ideal for complete disco's, groups, clubs etc. SAXON MULTIMIX 50—Exactly as above but 50W rms. £45-00


CALLERS AND MAIL ORDER

SAXON ENTERTAINMENTS LIMITED
327-331 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)
SHOP HOURS: 9 a.m.—5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.—3 p.m.
24-HOUR ANSWER SERVICE. TEL. 01-684 6385. TECHNICAL ENQUIRIES: 01-684 0098.

SEND 0p FOR OUR 26 PAGE MANUAL—full circuits & details.
TERMS OF BUSINESS: C.W.O. C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.
Please send S.A.E. with all enquiries.
VAT @ 8% must be added to all orders including carr. charges.

BIG Discounts

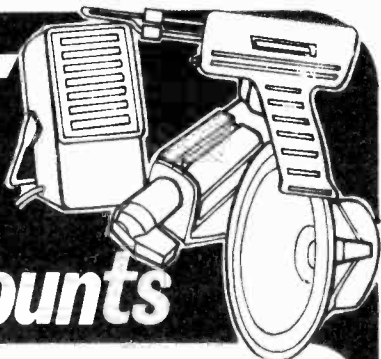

SPEAKER BARGAINS

P. & P. 40p per speaker	£
EMI 13" x 8" 3 or 8 ohm Plain	2-20
With Co-Axial Tweeter	
8 ohms only	2-30
Tweeter & Crossover 3, 8	
or 15 ohm	3-95
Type 350	
8 or 15 ohm,	
20 watt	7-95
6 1/2" 8 ohm, 10 watt	2-60
8" 8 ohm, 10 watt	4-50
8" x 5" C/Mag. 3, 8 or	
15 ohm 5 watt	1-40
8" x 5" Dualcone	
8 ohm, 10 watt	2-55

TWEETER & CROSSOVER

Cone Tweeter 8 or 15 ohm,	
10 watt	2-80
Cone Tweeter 8 ohm, 3 watt	1-45
Horn Tweeter 8 ohm, 20 watt	6-40
Dome Tweeter 8 ohm, 30 watt	5-80

KIT FORM CABINETS TEAK VENEER

12 x 12 x 6 with 8" x 5" or	3-50	18 x 11 x 9 with 8" x 5" or	4-95
8 1/2" and 3 1/2" cut out		13" x 8" cutout for EMI 350	4-95
17 x 10 x 9 with 8" or 13" x 8"	4-50		5-50
cutout			

MICROPHONES

CM70 Planet stick metal,	1-55	switch crystal	
DM150 Dynamic omni-dir.	4-90	ball metal	
UD130 50K/600 ohm, uni-dir	6-40	ball metal	
TW209	5-75	CONDENSER MIKE 600 ohm,	8-35
		uni-dir	
		Cassette Stick/Mike with R.	1-50
		Control on/off switch	
		(2-5 & 3-5mm J/Ply)	3-30

SOLDERING IRONS

ANTEX CN240 15 watt	2-10	X25 25 watt (low	2-10
SK 1 Kit (15 watt iron	3-40	2 spare B/bc etc.)	1-15

CARTRIDGES & STYLII

ACOS GP91/25C or 35C ster.	1-00	SONOTONE	
comp.		9TAHC or 9TAHC/G Diam.	2-00
GP93/1 or 95/1 ster.	1-50	3509 Ster. ceram. Diam.	2-00
cryst.		GOLDRING G850	3-25
GP94/1 or 96/1 ster.	1-85	G800	4-10
ceram.		G800E	4-10
GP101 cryst. comp.	2-80		P. & P. 1-15
GP104 ster. ceram.	1-95		
B5R X5M or X5H cryst. comp.	1-80	D. Diamond Stylil for above	1-25
SX6M or SX6H cryst.	2-00	G800/G850	1-95
comp.	2-00	G800E	4-10
SC5M ster. ceram.	2-75		P. & P. 1-05

CALCULATORS SINCLAIR

Cambridge	12-95	Scientific	19-95
Cambridge with memory	17-95		

BATTERY ELIMINATORS

240v Input 6, 7-5 or 9	2-85	12v Input, 6, 7 1/2, 9 output, 1 amp	4-25
------------------------	------	--------------------------------------	------

TAPES

Std.	LP	DP
5"	85p	1-00p
5 1/2"	85p	1-40p
7"	80p	1-10p

LOW NOISE CASSETTES

C60	1-5	6-10	11-20	Cassette Cases	10p
C90	35p	33p	30p	Cassette Head Cleaner	40p
CI20	45p	43p	40p	C. & P. 1-5, 5p ea. 6-10, 20p lot.	
	55p	52p	50p	C. & P. 1-3, 9p ea. 4 or more, lot 35p	

BIB ACCESSORIES

Tape Editing Kit	Ref. 23	1-35	WHARFEDALE SPEAKER BARGAINS	£	P&P
Recording Tape			Linton 2 Kit (pr)	18-95	2-00
Splicer	Ref. 20	1-15	Glendale 3 Kit (pr)	33-50	2-00
Cassette Tape, editing Ref. 24	1-50		Dovedale 3 Kit (pr)	52-00	2-00
Cassette Salvage Kit Ref. 29	1-45		Denton 2 Speaker (pr)	30-00	2-50
Stylus Balance	Ref. 32A	1-20	Linton 2 Speaker (pr)	39-50	2-50
Spirit Lever	Ref. 46	5-0	Dovedale 3 Speaker	42-00	2-50
Hi-Fi Stereo Test Cassette	2-19		Glendale 3 Speaker (pr)	57-00	3-50
Groove-Kleen Record Cleaner	1-90		Kingsdale 3 Speaker		4-10
P. & P.	1-5p		(each)	58-95	

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED. Subject to manufacturer increase and availability.

PLEASE ADD V.A.T.

Riversdale Electronics

Mail Order Department

P.O. Box 470, Manchester M60 4BU

ULTRON COMPONENTS

35 PARK AVENUE, POTTERS BAR, HERTS. 01-882 4355

MAIL ORDER ONLY

CASH WITH ORDER, OR PHONE US

DISCOUNTS: -15% off for 12 + 20% off for 50 + 25% off for 100 +

COMPARE THESE PRICES— ALL INCLUSIVE OF V.A.T.

Add 15p p & p for orders under £2.00

ALL TOP BRANDED MAKES, AND GUARANTEED

AC126	18p	BCY42	27p	2N087	14p	2N2928	8p	R.C.A.	80p
AC127	18p	BCY43	25p	2N088	25p	2N3053	13p	40809	
AC128	18p	BCY58	18p	2N089	30p	2N3054	42p	40810	48p
AC154	10p	BCY59	18p	2N706A	11p	2N3055	44p	40811	32p
AC187	12p	BF154	18p	2N708	18p	2N3302	36p	40812	60p
AC188	12p	BF177	27p	2N014	16p	2N3526	80p	40814	32p
ACY17	28p	BF182	38p	2N016	24p	2N3614	80p	40815	32p
ACY20	18p	BF183	38p	2N018	30p	2N3615	63p	40816	48p
ACY21	20p	BF185	27p	2N920	45p	2N3707	10p	40817	32p
ACY22	16p	BF195	20p	2N929	18p	2N3702	10p	40819	39p
ACY40	21p	BF200	31p	2N961	50p	2N3703	10p	40820	32p
ACY41	25p	BF274	18p	2N131	20p	2N3704	11p	TIP33C	90p
ACY44	86p	BFW88	10p	2N132	20p	2N3705	10p	TIP35	22-00
AD149	48p	BFW89	18p	2N1302	18p	2N3707	10p	TIP36C	28-80
AD161	80p	BFW91	17p	2N1303	18p	2N3708	8p		
AD162	86p	BFX29	25p	2N1304	18p	2N3709	7p	Stud diodes	
AF114	18p	BFX38	80p	2N1305	28p	2N3710	11p	6 Amp	28p
AF117	13p	BFX87	28p	2N1306	28p	2N3711	11p	15p Atn	45p
AF125	24p	BFX88	21p	2N1307	25p	2N3730	90p		
AF139	38p	BFY11	20p	2N1308	27p	2N3731	22-28	Bridge Rectifiers	
AF178	49p	BFY18	47p	2N1309	27p	2N3733	22-28	1A, 50V	84p
BC107	10p	BFY19	54p	2N1671	90p	2N3819	25p	2A, 500V	48p
BC107B	10p	BFY50	18p	2N1671A	90p	2N3866	70p	4A, 200V	55p
BC108	10p	BFY61	18p	2N2717	21p	2N3893	14p	6A, 100V	65p
BC109	10p	BFY64	39p	2N2218	20p	2N3904	14p	S.C.R.s	
BC109B	10p	BFY90	72p	2N2220	18p	2N3905	15p	1/05	80p
BC113	15p	BFW70	25p	2N2229	27p	2N3906	15p	1/10	36p
BC114	14p	BHX26	22p	2N2287	27p	2N4061	12p	1/20	40p
BC115	13p	BHX67	28p	2N2303	75p	2N4081	27p	1/30	80p
BC116	13p	BY127	11p	2N2369	13p	2N4548	27p	1/40	40p
BC118A	14p	BU105	£1-00	2N2389A	15p	OA81	15p	16/400	80p
BC117	13p	MFP103	85p	2N2411	50p	OC20	£1-00	16/800	£1-20
BC118	10p	MJ480	75p	2N2446	44p	OC28	58p	Triacs	
BC119	22p	MJ481	95p	2N2846	70p	OC29	80p	SC40D	£1-05
BC134	12p	MJ490	80p	2N2894	35p	OC35	45p	SC45D	£1-30
BC136	16p	MJE371	60p	2N2904A	45p	OC36	50p	SC45E	£1-45
BC137	16p	MJE2801	£1-00	2N2905	22p	OC71	30p	SC50D	£1-50
BC138	16p	MJE2803	£1-15	2N2906	14p	OC83	20p	I.C.s	
BC153	17p	MJE2955	£1-00	2N2906A	16p	OCP71	75p	741	25p
BC154	17p	MJE3055	65p	2N2907A	16p	ZTX107	8p	1310	22-00
BC167B	10p	MFP102	30p	2N2925	14p	PL4005	10p		
BC183L	12p								

Mullard Hi-Stab 1/2 watt resistors, 21p each



4 1/2in x 3 1/2in METER. 30µA, 50µA or 100µA, £3.85. P. & P. 13p.

TAPE RECORDER LEVEL METER

500µA, 80p. P. & P. 10p.



CARDIOID DYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000/c/s. Impedance Dual 50K and 600 ohms, £7.40. P. & P. 13p.

42 x 42mm METERS 100µA, 500µA, 1mA, 500mA £2.76, 11p P. & P.

60 x 45mm METERS 50µA, 100µA, 500µA and 1mA VU METER £2.92, 11p P. & P.

EDGEWISE METERS, 90mm x 34mm, 1mA £3.40, 13p P. & P.

MULTI-METER

Model ITI-2 20,000 ohm/volt, £6.90. P. & P. 16p.





3 WATT STEREO AMPLIFIER 1/2W PER CHANNEL £4.30. P. & P. 12p.

All above prices include V.A.T. LARGE S.A.E. for List No. 12. Special prices for quantity quoted on request.

M. DZIUBAS

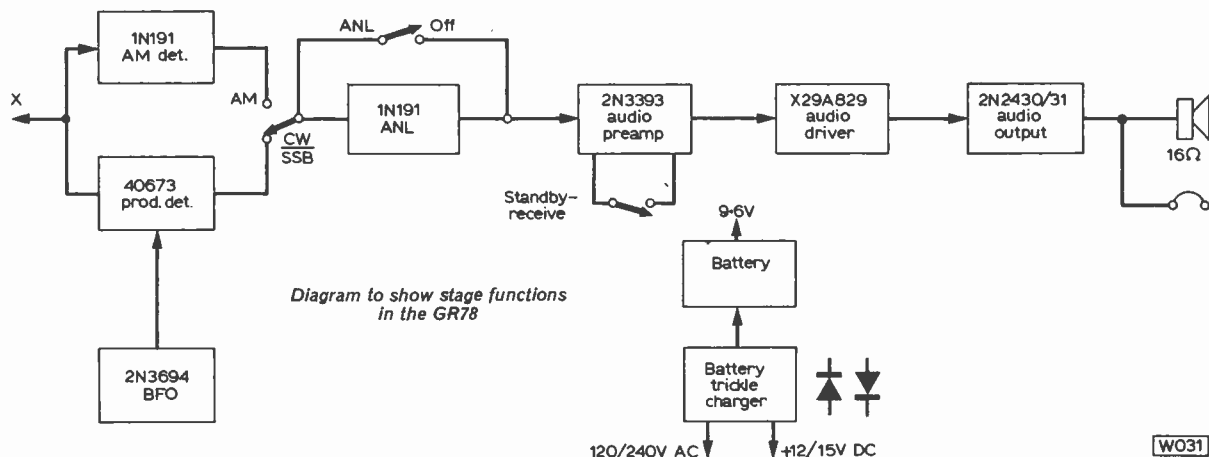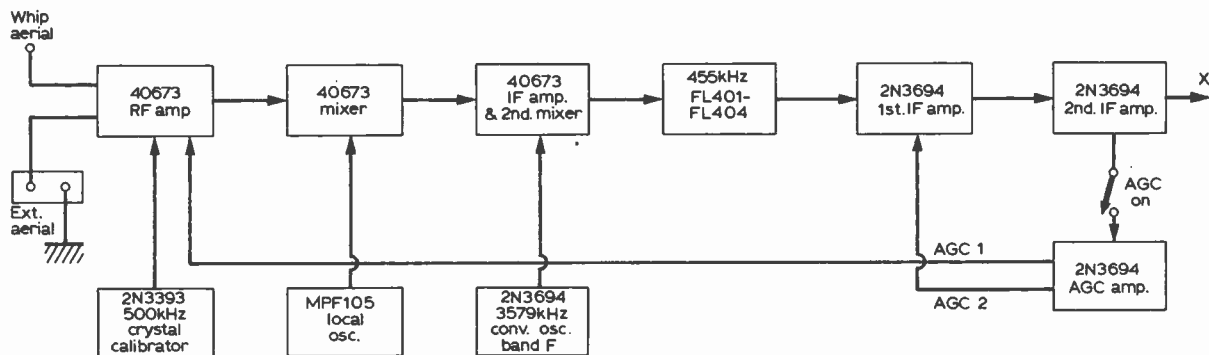158 Bradshawgate · Bolton · Lancs. BL2 1BA



W031

Frequency Coverage				
Band A: 200kHz—400kHz				
Band B: 550kHz—1300kHz				
Band C: 1.3MHz—3.0MHz				
Band D: 3.0MHz—7.5MHz				
Band E: 7.5MHz—18.0MHz				
Band F: 18.0MHz—30MHz				
Sensitivity*	AM		CW/SSB	
	Low	High	Low	High
Band A:	10 μ v	3 μ v	6 μ v	2 μ v
Band B:	3	1	2	0.7
Band C:	3	0.6	1.5	0.4
Band D:	2	0.3	2	0.2
Band E:	3	0.2	3	0.2
Band F:	2	0.3	2	0.2
* Signal level for 10dB signal-plus-noise to noise ratio				
Image Rejection	Band A: 65dB or more			
	Band B: 60dB or more			
	Band C: 48dB or more			
	Band D: 35dB or more			
	Band E: 25dB or more			
	Band F: 35dB or more			
IF's	Band A to E: 455kHz			
	Band F: 455kHz and 4034kHz			
Selectivity	7 \pm 1kHz wide, 6dB down			


Audio Output	300 milliwatts
Crystal Calibrator	500kHz
Meter	Indicates relative signal strength
Panel Controls	Bandspread AM-CW/SSB AF Gain-Off AVC-MVC RF Gain ANL-OFF Panel light Bandswitch RCV-STBY Main Tuning CAL
Rear Panel	Muting External aerial 12 VDC Receptacle 120/240 VAC Receptacle Phone Jack
Battery Drain	65mA at 50mW audio output 40mA at no audio output
Weight	4.5kg (10lbs)
Overall Size	292mm wide, 160mm high, 230mm deep (11 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " x 9")

Transistor identification proved a little difficult with some devices where the marking was completely missing but a few moments with the drawings soon cleared up the identification.

In check lists the colour code is given for each resistor as well as the actual value. The length of every wire that is used is given, cut from the wire provided. Where necessary the length of leads to be left on components is given and even the lead shape where appropriate!

Everything goes together very well, which perhaps is not surprising when one considers the enormous amount of work that has obviously gone into the preparation of the manual. Nevertheless, it is very satisfying when the pile of bits and pieces has dwindled to almost nothing!

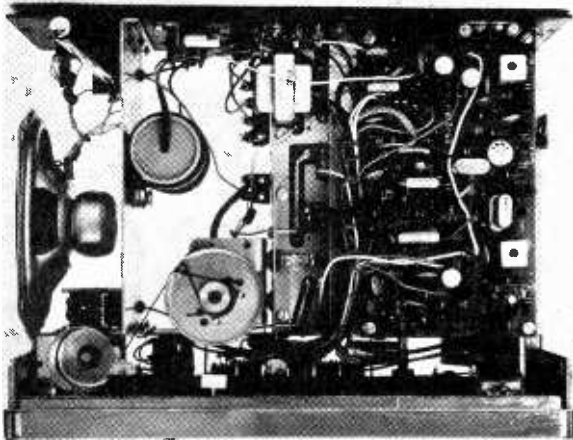The potential builder of this receiver kit needs two things, time, and the ability to wield a small soldering iron successfully. As is usual with Heathkit the accompanying manual gives every step of the construction with many detailed illustrations, some of which are seemingly much too detailed for the step involved. However for the newcomer to kit construction they are invaluable.



In this top view the main circuit board is on the right, main tuning gang just left of centre-bottom linked to the bandspread dial at extreme left.

A frequent worry of the do-it-yourselfer is the subsequent electrical alignment required and the fear that a workshop full of test equipment will be necessary before the fruits of all the labour can be tasted. But no worries need be entertained here. A short list of tests to be carried out with a simple multimeter coupled with a fault-finding chart obviate any serious faults before switching on.

All the coils in the RF and oscillator stages are pre-aligned enabling stations on known frequencies to be quickly located on each band and cross-checked with the integral 500kHz crystal oscillator, in conjunction with the set's relative signal strength meter. If one has access to a signal generator however then advantage can be taken of the full instructions given, enabling the receiver to be aligned to give of its best on all bands.

Having reassured the potential builder of the GR78 kit that he need have no worries about alignment it should be said that he must be prepared to sit down for quite a few evenings, wading through the manual ticking off each step as it is done. Spaces are even provided for the ticks! The biggest mistake is to jump or anticipate any steps and strangely enough, this is more likely to happen with the experienced constructor who thinks he can beat Heathkit to the finish!

Naturally, some previous experience of the construction of electronic equipment is desirable and the GR78 kit is probably best suited to the hobbyist who has had a go at a few simple projects already, and now feels that he is ready for a serious project.

One or two tips as you open the box! Try to find a workspace where the set and tools can be left out as construction progresses and where the many bits and pieces and components can be sorted out and located within easy reach.

Do follow all instructions and check all parts as and when directed, especially at the start, before any attempt is made to begin construction, however great the temptation may be! Tidy up after each session and cover over the set and workspace. In this way even short periods of half an hour can be put to good use, the steps completed to date being clearly shown in the manual.

ALIGNMENT

The set was working after the initial series of simple circuit checks had been carried out and the set had been plugged into the mains and left, with the on-off switch at OFF, for 24 hours while the battery was charged. For peace of mind the set was disconnected from the mains while tests and alignment were carried out, and plugged into the mains again between times.

Alignment is conventional, trimmer capacitors at the HF end of each band and coils at the LF end, but as mentioned before, the coils are prealigned and should need little adjustment. As Radio 2 is on 200kHz it was necessary to cheat a bit on Band A (200 to 400kHz) and alter the oscillator coil to bring 200kHz just inside the end of the scale to ensure that it was possible to tune in Radio 2 properly.

Band B covers part of our MW band, the balance being found on Band C and there are plenty of stations here for calibration purposes. Needless to say, the internal 500kHz calibration oscillator is invaluable during alignment especially on the SW bands. Further adjustments include the BFO, calibration oscillator and 5.5MHz trap circuit.

The kit K/GR78 now costs £125 which includes the new rate of VAT at 25%, from Heath (Gloucester) Ltd., Gloucester, GL2 6EE.

PW TECHNICAL CROSS PUZZLE No. 9

presented last month




THE IN-CAR 'SET'

**IN NEXT MONTH'S
PRACTICAL
WIRELESS**


Pw Car Radio

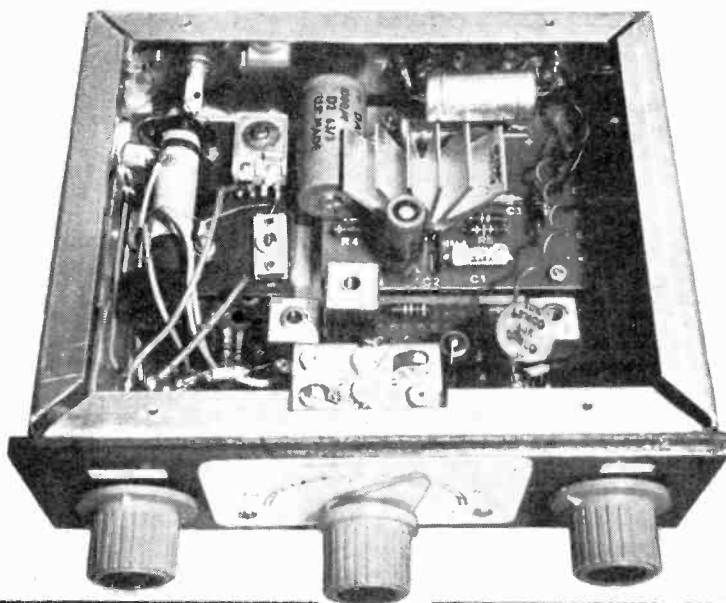This easily built receiver provides switch selected stations or manual tuning. Three transistors plus a cheap audio module rated at 5 watts out. Suitable for positive or negative earth vehicles. Economical consumption allows optional operation from dry batteries.



&

Dual Conversion Receiver

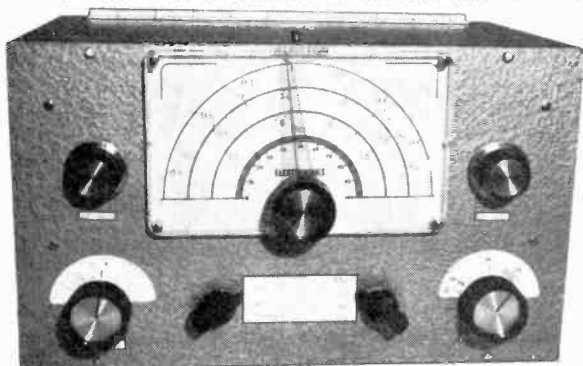

A reliable design for the 20, 40, 80 and 160m bands, CW/SSB/AM. Conversion at 5.5MHz and 465kHz reduces second channel interference especially at the higher frequencies.

plus

'IC of the Month' looks at the versatile

TDA 2020 audio IC

ON SALE IN JULY

DIGITAL WAVEFORM

THE function generator is constructed in a RS instrument case type 4. This case has a very slim front panel, dimensions 432 x 88mm (17 x 3.5in). Whilst this particular case is not essential (any other type would be suitable), it does lend itself to the construction of an instrument having a very modern appearance. This, together with the in-line layout of the switches and the LED indicators make a very functional instrument.

The instrument is constructed in three parts: the front panel; the centre circuit board; and the rear power supply. The front panel accommodates the switches and most of the switched components. The circuit board in the centre contains the 8038 IC, the transistors, and most of the remaining components. The rear panel is utilised for the power supplies, ± 15 volts. An inside view of the general construction was shown last month.

DRILLING

First drill the front and rear panels to take all the necessary components. The front panel is marked with Letraset legends to suit the knobs chosen, then sprayed with a varnish protective.

Fit the four stand-off mountings and screw in the 4BA studding which holds the circuit board.

Some switches may necessitate mounting the circuit board further back. Next, fit all the switches and indicators to the front panel then the circuit board must be drilled with 4BA clearance holes to fit the studding and temporarily fitted.

CAUTION The circuit board is long and thin and cannot be used without adequate support. Therefore it is necessary to fit a metal frame around the board, or two metal strips as fitted to the prototype instrument illustrated in Fig. 6. Any convenient metal bars

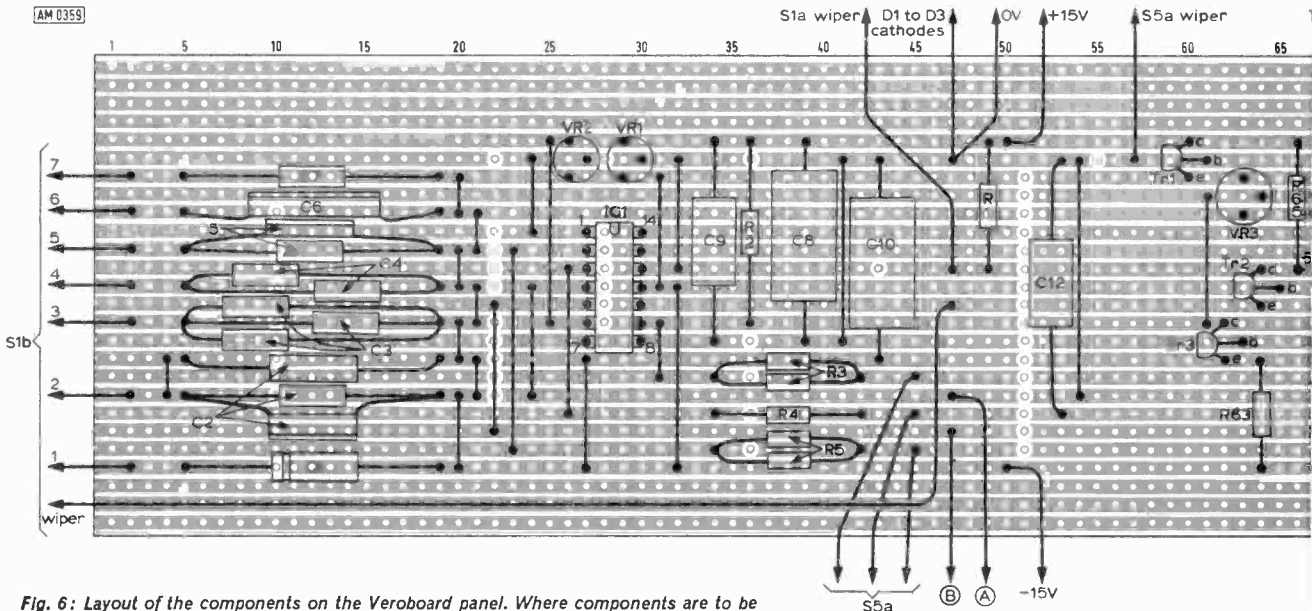


Fig. 6: Layout of the components on the Veroboard panel. Where components are to be trimmed it is advisable to use Veroplus for mounting. Note that the number of components for a trimmed value may vary from that shown. Note also that there are some variations between the board shown here and that shown in the photographs.

GENERATOR

John Smith C. Eng PART TWO

may be used here, with the whole assembly bolted to the 4BA studding. Finally the power supply components are mounted on the rear panel as shown in Fig. 7.

The whole unit is then assembled in the case to ensure that there is adequate clearance for all components. The three parts, front panel, circuit board and rear panel are removed from the case for wiring.

WIRING


The power supply is wired first as shown in the circuit diagram published in Part 1. Connect the unit to the mains supply and (after checking) switch on. The supply should give ± 15 volts. If it does not it will be due either to faulty wiring or to component failure. However, it is essential to check out the power supply before proceeding further, as any

trouble in this area can damage the very expensive 8038 IC.

It is desirable to check the supply on a load of about 50 mA. This can be accomplished by monitoring the output voltage with a voltmeter and then connecting a resistor of about 330 ohms across the supply to see that the voltage does not change appreciably. It is also worth checking the ripple.

The output voltage need not be precisely 15 volts; the instrument will function quite well on 15 ± 1 volt, but it must be stable and have a low ripple voltage.

The front panel is wired next, fitting all the resistors around switches S3, S4, and S6. Fig. 8 shows the positioning of the switches on the front panel. The components on S2 have to be selected, so R6 and R15 only are temporarily wired into circuit. Of course, readers building option 2 will proceed with the wiring of S2 using the design values.

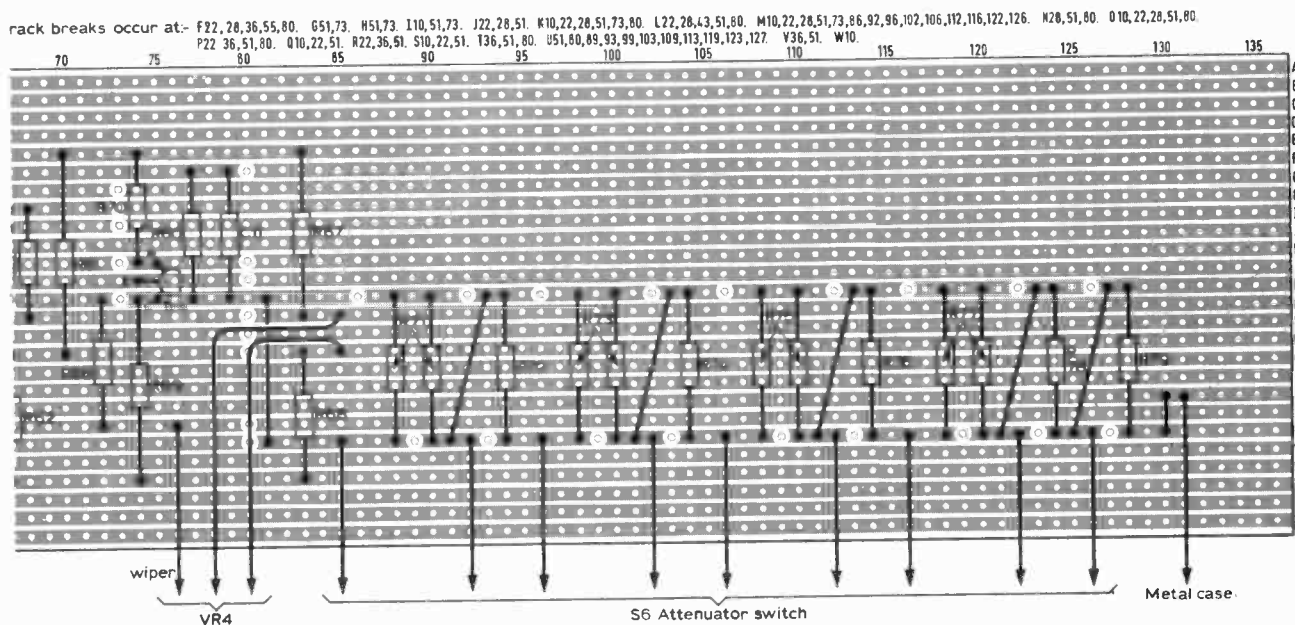

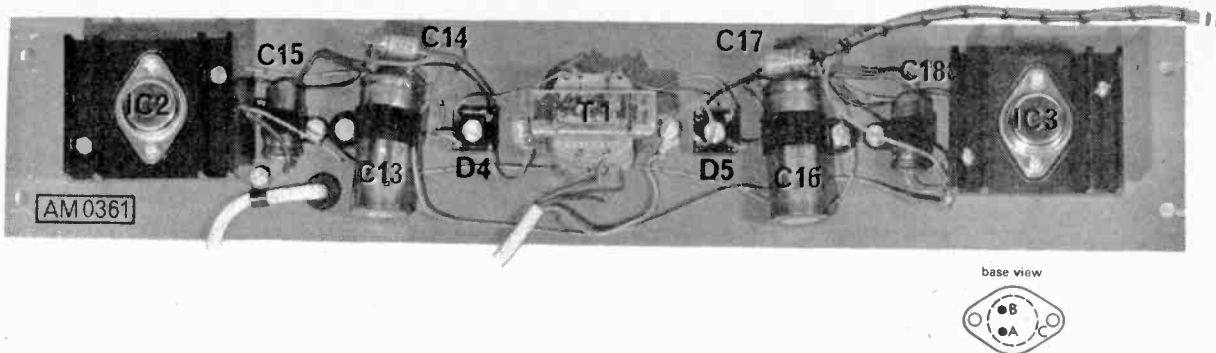


Fig. 7: Layout of the components on the rear panel. The wiring should be completed by referring to the circuit diagram of Fig. 5 in Part 1. Note the polarity of the regulator ICs and the resistor in series with the lead which is hidden behind the heatsink.

CIRCUIT BOARD

The circuit board is wired last. Cut the tracks and fit the components as shown in Fig. 6, with the exception of the components marked "trim" on the circuit diagram. C1 to C7 are not fitted until later, R3 to R5 and R68 are fitted temporarily with the design values. The whole instrument is now wired together with enough spare wire for the component board to lay flat, so that the selected components may be wired to S2 and the capacitors C1 to C7 may be fitted to the component board.

With all the "trim" components it is advantageous to fit a wiring pin onto the circuit board to facilitate removal and rewiring. Carry out a complete and final check of the wiring and the unit is ready to switch on, BUT DO NOT do so until the following instructions have been carried out.

TESTING AND COMPONENT SELECTION

Before starting the test and selection procedures it is necessary to know the function of the selected components. Firstly, frequency is controlled primarily

by capacitors C1 to C7, so a high degree of accuracy and stability is necessary here. Resistors R6 to R23 not only control frequency, or period, but also control waveform symmetry. This means that these components must be selected with considerable care, using an oscilloscope to check symmetry.

VR1 and VR2 control the purity of the sine wave signal and must be carefully adjusted at a low frequency. Resistors R3 to R5 control the output voltage of the signal and are adjusted with the aid of an oscilloscope. VR3 and R68 are concerned with the offset control and are also adjusted with the aid of an oscilloscope.

CAPACITOR SELECTION

Before switching on the instrument VR1 and VR2 must be set to the centre of their range. Then fit either C5 3,000pF or C6 300pF; the value chosen will depend upon the accuracy of the oscilloscope used to calibrate the instrument. Range 5 (3,000pF) gives 100μS to 900μS. Range 6 gives 10μS to 90μS so pick the one most suited to the oscilloscope used and fit that capacitor—1% silver mica or Suflex is recommended.

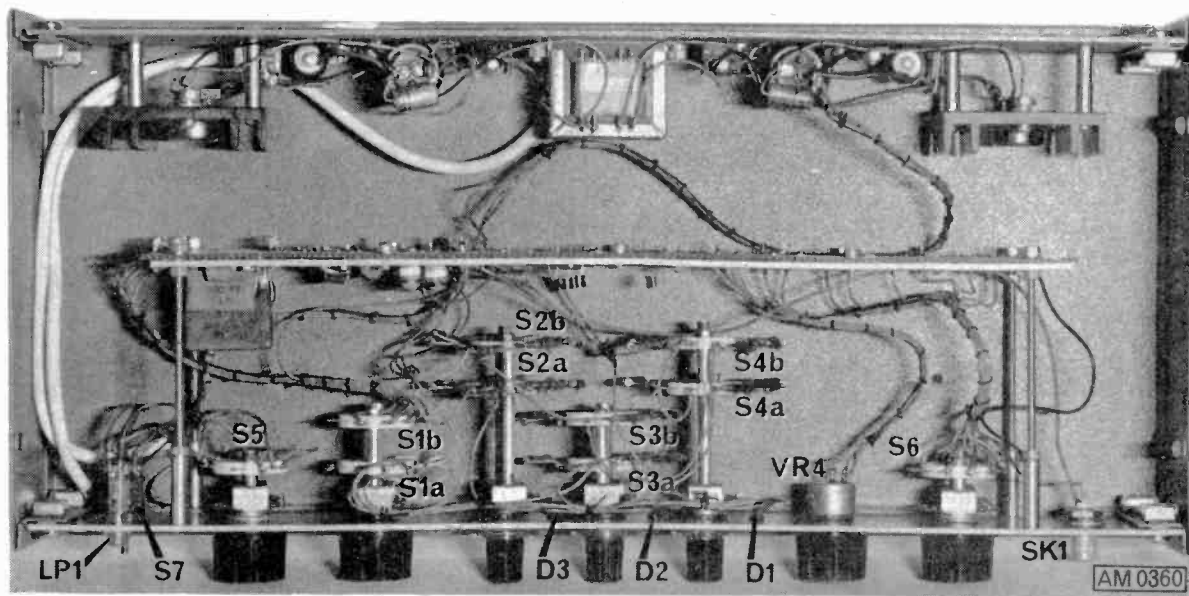


Fig. 8: Layout of the switches and the LEDs on the front panel. Wiring should again be completed by reference to the circuit diagrams in Part 1.

Switch on the instrument, with the range switch set to range 5 or range 6 depending upon which capacitor has been fitted, and set S3 and S4 to zero. Set the DC shift control to the centre of its range, LED B or C should be on. Check that when the range switch is turned from the left (range 7) to the right the LED's go through the sequence (ABCABCA), LED A being the extreme left hand one.

Next, turn the attenuator switch S6 to maximum output and examine the waveform on the coaxial socket. This waveform should be sine, triangle or square as selected by the function switch, ten volts approximately peak amplitude and roughly swinging about zero.

Check that each function gives an output, that the offset control works and the attenuator functions. If any of these facilities do not work there are wiring or component errors or faults which must be corrected before proceeding further.

TRIGGER PULSE

Some oscilloscopes need a trigger pulse to function properly, such a pulse may be obtained from the junction of R2 and R3. This pulse is about 24 volts in amplitude but may be attenuated ($\div 10$ for example), with the aid of a 10k Ω and 1k Ω resistor divider. Some users may consider a trigger output as a useful permanent feature of the function generator, although the prototype shown does not incorporate this feature. Having attended to the trigger pulse, adjusted the oscilloscope and repaired any faults, the calibration procedure may begin.

CALIBRATION

In addition to the oscilloscope a frequency meter is necessary for the highest possible accuracy. If this degree of accuracy is not sought after the instrument may be adjusted to correspond to the oscilloscope time base calibration.

First switch to the triangular waveform and see if the output is asymmetrical as is shown in Fig. 9a. Here the up stroke is shorter than the down stroke. This wave form is made symmetrical by selecting R6 and R15. Shunt each one in turn with a 100k Ω resistor to determine which affects the up and the down stroke.

Symmetry is very important because this form of distortion affects both the sine wave purity and the duty cycle of the square wave, see waveforms b and c Fig. 9. Having adjusted R6 and R15 to give a perfectly symmetrical waveform with an upstroke/downstroke time of 50 μ Sec (100 μ Sec period), the frequency must now be corrected.

FREQUENCY CALIBRATION

Before discussing the frequency calibration a few words about procedure: R6 and R15 are selected by fitting series or shunt resistors to correct their value. It is relatively easy to find out what adjustment is needed if one makes use of the other two decade switches S3 and S4. S3 introduces resistance increases of 1k Ω whilst S4 introduces resistance increases of 100 Ω . By making use of these two switches the increase or decrease in value can be estimated.

Now switch to sine output and measure the frequency. This should be 10kHz (100 μ Sec period) or 100kHz if range 6 is being used. The use of range 5 will be assumed from now on, so readers who have

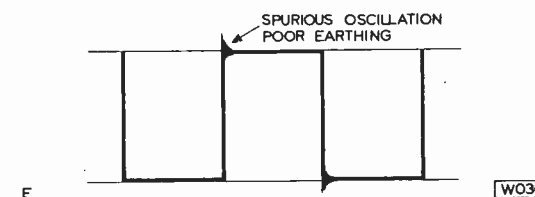
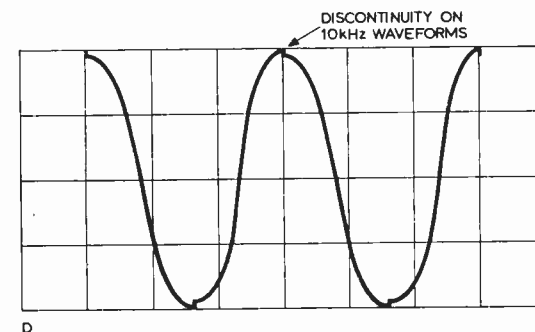
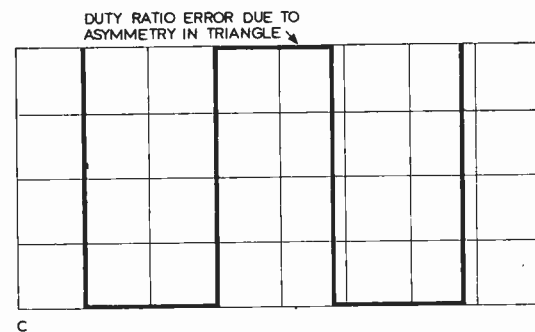
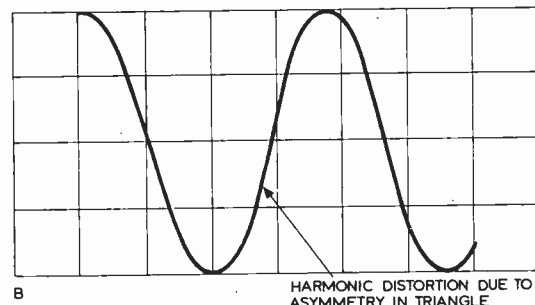
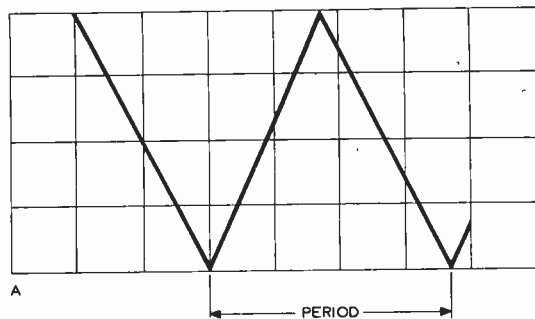


Fig. 9 (a) Asymmetry in the triangular waveform is indicated by a difference in the up and down strokes as shown here (b) Asymmetry in the triangular wave results in a slight flattening of the sine waveform (c) The mark-space ratio of the square wave will also be asymmetrical (d) If the square and triangular outputs are not earthed discontinuities in the sine wave result (e) poor earthing causes ringing on the square wave.

W036

chosen range 6 must divide period by ten and multiply frequency by 10 whenever they are mentioned. However, it is important to carry out all the calibration on one range if at all possible.

If the frequency meter reads high adjust S3 and S4 until the correct reading is obtained. This shows the value of series resistor needed to correct the frequency. Warning, if more than one step of S3 is necessary (e.g. three steps) fitting $3k\Omega$ in series with both R6 and R15 whilst correcting frequency will also distort symmetry.

In this case it is better to fit values proportional to those already in circuit and re-check to find the final value needed. If on the other hand the frequency were too low R6 and R15 have to be shunted. In this case use S3 and S4 to lower frequency by a corresponding amount to arrive at an estimate of the shunt percentages needed.

All this is rather a long-winded procedure especially as each resistor R6 to R23 must be adjusted, but once the correct procedure is understood it becomes easier with practice. It will take at least a weekend to complete an accurate calibration of this instrument.

SYMMETRY AND PERIOD

Next fit temporarily R7 and R16 ($10k\Omega$). Use the same procedure as before to adjust for symmetry and a period of $200\mu\text{Sec}$. Switch to sine output and adjust frequency to 5kHz. Work through each component on switch 2 in sequence; R8 and R17 gives $300\mu\text{Sec}$ (3.3kHz), R9, R18 $400\mu\text{Sec}$ (2.5kHz), R10, R19 $500\mu\text{Sec}$ (2.0kHz), R11, R20, $600\mu\text{Sec}$ (1.66kHz) R12, R21 $700\mu\text{Sec}$ (1.43kHz), R13, R22 $800\mu\text{Sec}$ (1.25kHz) and R14, R23 $900\mu\text{Sec}$ (1.1kHz).

People who have paid the extra for the 8038BC will find that they have a big advantage during calibration due to the higher accuracy of this unit. For those with suitable instrumentation it is well worth spending time on this calibration procedure because the 8038 is a very stable IC. Temperature stability is $50\text{ppm}/^\circ\text{C}$ and as the power supplies are also stabilised the instrument will retain its accuracy. Unfortunately if the 8038 needs replacing at any time the instrument will need recalibration.

RANGE SWITCH

Next the range switch is calibrated. Switch to range 6 and adjust the period switches to $10\mu\text{Sec}$. Switch to sine output and connect the frequency meter. Fit C6 (30pF), switch on, and check frequency. C6 must be adjusted to give 100kHz . Switch to range 5 and adjust C5 ($3,000\text{pF}$) to give 10kHz (this range has of course already been adjusted). Now proceed with each range: Range 4, C4, $30,000\text{pF}$ adjust frequency to 1kHz ; Range 3, C3, $0.3\mu\text{F}$, 100Hz ; Range 2, C2, $3.0\mu\text{F}$, 10Hz ; and Range 1, C1, $30\mu\text{F}$, 1Hz . It may be difficult to find a suitable capacitor for range 1; a 15 volt tantalum is recommended although many electrolytics will perform quite well. Finally fit C7. The 8038 will only oscillate up to 1MHz on the square wave output, the other waveforms being of very poor quality. Fit any value between 5pF and 30pF which is capable of giving a useful range of signals.

ADJUSTING SINE PURITY

If the sine wave output is examined on Range 6 it will be seen that it has a high frequency discontinuity, see Fig. 9. This is caused by breakthrough

from the pulse and triangular waveforms. It can be improved by making use of a three pole switch (S5) arranged to short R4 to earth when switched to sine output. It may also be improved by running the sine lead from R5 to S5 separately, or screened from the other function leads.

Discontinuities are made worse by poor earthing. To investigate the earthing, switch to square wave and examine the edges of the waveform. If the edge of the square wave shows oscillations as indicated in Fig. 9e try earthing various parts of the front panel to the Veroboard. Take care to ensure that it is not the oscilloscope giving rise to spurious oscillations on this test.

In practice these oscillations and discontinuities are at a very high frequency and may be ignored providing one is aware of their presence. The final adjustment of sine purity is carried out by switching to Range 5, period $500\mu\text{Secs}$ (which is a frequency of 2kHz) and adjusting VR1 and VR2 to give the purest sine wave possible.

This may be carried out using an oscilloscope or it may be adjusted by comparing the waveform with another sine wave. Those able to measure harmonic distortion can adjust for minimum second and third harmonic. Those able to hear distortion may be able to pass the signal through an amplifier and adjust by ear.

ADJUSTING OUTPUT VOLTAGE

Adjust the output voltage to give a ten volt swing on each waveform. This is carried out by checking the output with an oscilloscope and adjusting R3 for the correct square wave amplitude, R4 for the triangular wave amplitude and R5 for the sine wave amplitude. The design values should give a voltage quite close to the swing required.

ADJUSTING OFFSET


Switch to the triangular waveform and set the offset potentiometer VR4 to its centre position (calibrated zero). Examine the waveform on the oscilloscope and adjust VR3 so that the excursion is ± 5 volts. If, due to power supply and component tolerances, VR3 is unable to centralise the waveform, select another value for R68 to give a reasonable degree of control on VR3. Increasing R68 will push the waveform down in a negative direction and decreasing it will push the waveform in a positive direction.

This completes the adjustment and calibration of the instrument which is now ready for use. Fit the instrument into its case and run through all the controls to familiarise yourself with their functions. Examine the DC shift control and attenuator carefully.

These are designed so that the signal can be shifted to all positive, symmetrical about earth, or all negative. This is equally true of all settings of the attenuator. Thus at maximum output the DC shift is ± 5 volts, but if the signal is attenuated to 100mV the DC shift is $\pm 50\text{mV}$.

In next month's article we shall discuss how to simplify the instrument and mention some of the uses to which it may be put.

GOING BACK...

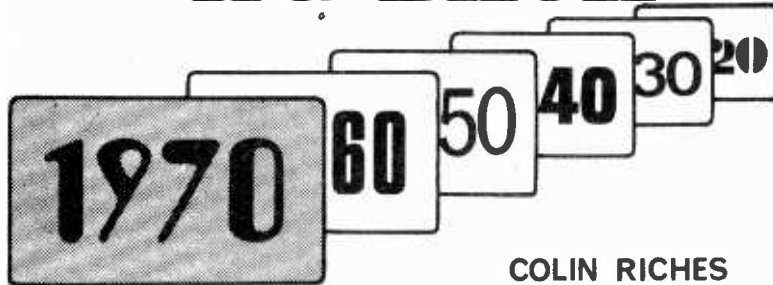

Memories

MR. LESLIE SPENDLA from Hampshire tells us that after 50 years it still thrills him to know that he was an on-the-spot witness of the early lead taken by Britain in the field of wireless, with the formation of the British Broadcasting Company and the opening of its first transmitter on medium waves at Savoy Hill in November 1922. A few months after this date, a local advertisement stated that a public demonstration of wireless reception by the Marconi Co. was to be given at the Station Road Garage, Winslow, seven miles from his home in Buckingham.

Mr. Spendla was a schoolboy at the time and he went there with some friends to listen.

To introduce wireless reception and Marconi sets to the public, the company organised tours of the country districts—often setting up their equipment in garages—these eventually becoming their first trade outlets. These garages had only just progressed from the practice of dispensing petrol (Pratts Motor Spirit) from 2-gallon cans.

Two tall white masts in the adjoining field carried an aerial similar to those seen in pictures of an ocean liner—its parallel wires being separated by spreaders at each end.

The open garage doors revealed the sloping desk type receiver, with its row of glowing bright emitters, feeding two large upright horn speakers, with whistles, crackles and mush, as the engineers tuned up in preparation for the opening of the evening programme from the London transmitter some 50 miles away.

Then, over the ether, came the magic voice—"Hello! Hello! This is 2LO calling." This thrilled the crowd as much as if it had

COLIN RICHES

come all the way from the moon.

In the next few years, Mr. Spendla says he was absorbed by wireless, moving on to one-, two- and three-valve sets.


After burning much midnight oil, the success of a DX session on the medium wave in those days was measured by the ability to receive such items as the nightingale from Milan, the cuckoo call from Ljubljana, the musical box notes from Budapest (Buda-Pest as it was then), the trumpet call from Krakow, the rapid metronome from Vienna or the slow one from Munich.

Over are the days when people used to have to cycle to a garage in the next town to hear the wonders of that array of Marconi equipment and know-how, heralding the birth of a new science. These 50 years of progress enable the schoolboy of today to carry around in his pocket the means to receive "London" and many other broadcasts at will—Tempus fugit!

Attic searcher

MR. M. J. DARBY of 266 Canley Road, Coventry, Warwickshire, happened to be searching the loft of an old house when he discovered a receiver like that shown in our picture.

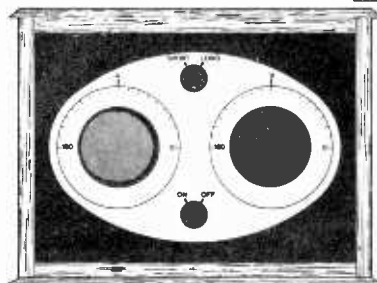The set has two aerial input terminals, one earth, two speaker



terminals and wires for a 2V l.t. battery, h.t. battery with two positive tappings, and a grid bias battery.

The valves are an Osram H2 triode detector coupled to a P220 Osram output triode through a Cossor transformer. Two dials are marked from 0° to 180° and one is marked 'A' for tuning. The other is designated 'B' for reaction. There is no volume control—just a short/long wave switch and an on/off switch.

The receiver's wooden case has a hinged top lid, and the speaker with its associated transformer is in its own wooden case.

The set works quite well when connected to suitable power supplies—radio 2 and 3 being received at good strength.

If any readers could tell Mr. Darby more about this set, could they please contact him direct.

Avo 1923



THE year 1923 marked the Golden Jubilee of Avo Limited, the makers of the well-known Avometer.


In 1923 the Automatic Coil Winder and Electrical Equipment Company (as Avo was then known) was formed to manufacture a range of coil-winding machines. Soon afterwards they introduced the first test meter in the world with multi-range facilities. Its picture is shown above.

On the right track

ALL Austrian trains in 1926 were equipped with wireless. A fee of 50 groschen (3½d. then) was made for a journey of any length.

TELE- TENNIS

SOUND EFFECTS UNIT

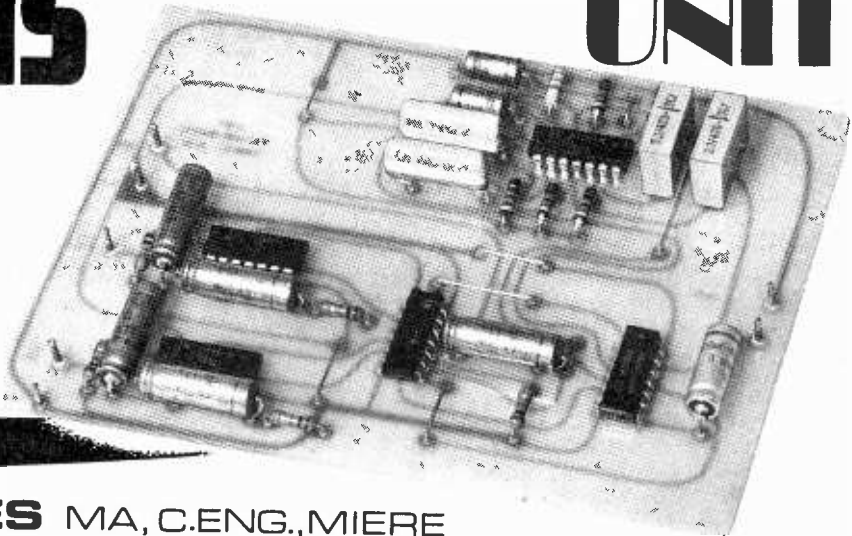

M. J. HUGHES MA, C.ENG., MIERE

Increase your enjoyment of the game!

IN the original articles describing the construction of our Tele-Tennis game (July to November 1974 —reprints of which are still available) reference was made to sound effects, but did not show any circuitry which would provide this function. Since the article first appeared, *PW* has had numerous requests from readers for a sound effects unit which could be a simple attachment to the unit already constructed.

This article describes a simple, and comparatively cheap, sound effects unit which can be wired into the original game without any wiring modifications being made to the constructed unit. All that is required is access to three signal points and the 0V and +5V rails of the Tele-Tennis game. The whole of the attachment is housed on a single PCB which, with care, could be bolted within the existing case. But, as a loudspeaker is required, most readers might prefer to construct a separate enclosure and take off the five lines from the Tele-Tennis game via a multi-pin plug and socket. This can be positioned in the space provided for the "Video" output of the original game.

SUB-CARRIER

Originally a 6MHz sub-carrier suitably frequency modulated and fed to the modulator of the original game was envisaged. This meant that the sound effects would come from the audio channels of the television receiver to which the game was connected. In principle this is quite easy to do, but in practice

there are quite a few problems in maintaining the sub-carrier stability, and there was complexity enough in handling the video signals through the modulator without having sub-carriers to contend with. Consequently it was decided to go for the simple expedient of a separate loudspeaker. In actual fact there is no difference in the overall cost and there should be no problems in getting this system to work.

CIRCUIT

The complete circuit is shown in Fig. 1. Three sounds are generated by the free-running multi-vibrators made from the six inverters of IC5. These tones are continuous at the oscillators, but are gated by the logic to give three different pitches of "bleep" when the ball hits the top or bottom bases, bats, or left and right bases. The frequencies of these bleeps can be set by the values of C7 to C12, and in the prototype a rebound off top or bottom base produces a medium pitch, a successful return off the bats produces a high pitch, and contact of the ball with the left and right bases (which constitutes a "Lose") gives a rather rude low frequency "burp"!

The logic is fairly simple to follow if the production of each audio signal is described in turn. First of all, the rebound from top or bottom bases. As those who have already constructed the original game will know, the ball is in motion around the screen all the time, but is only in play when it is brightened up by the Ball Blanking logic. Consequently the only sounds wanted occur while the Ball

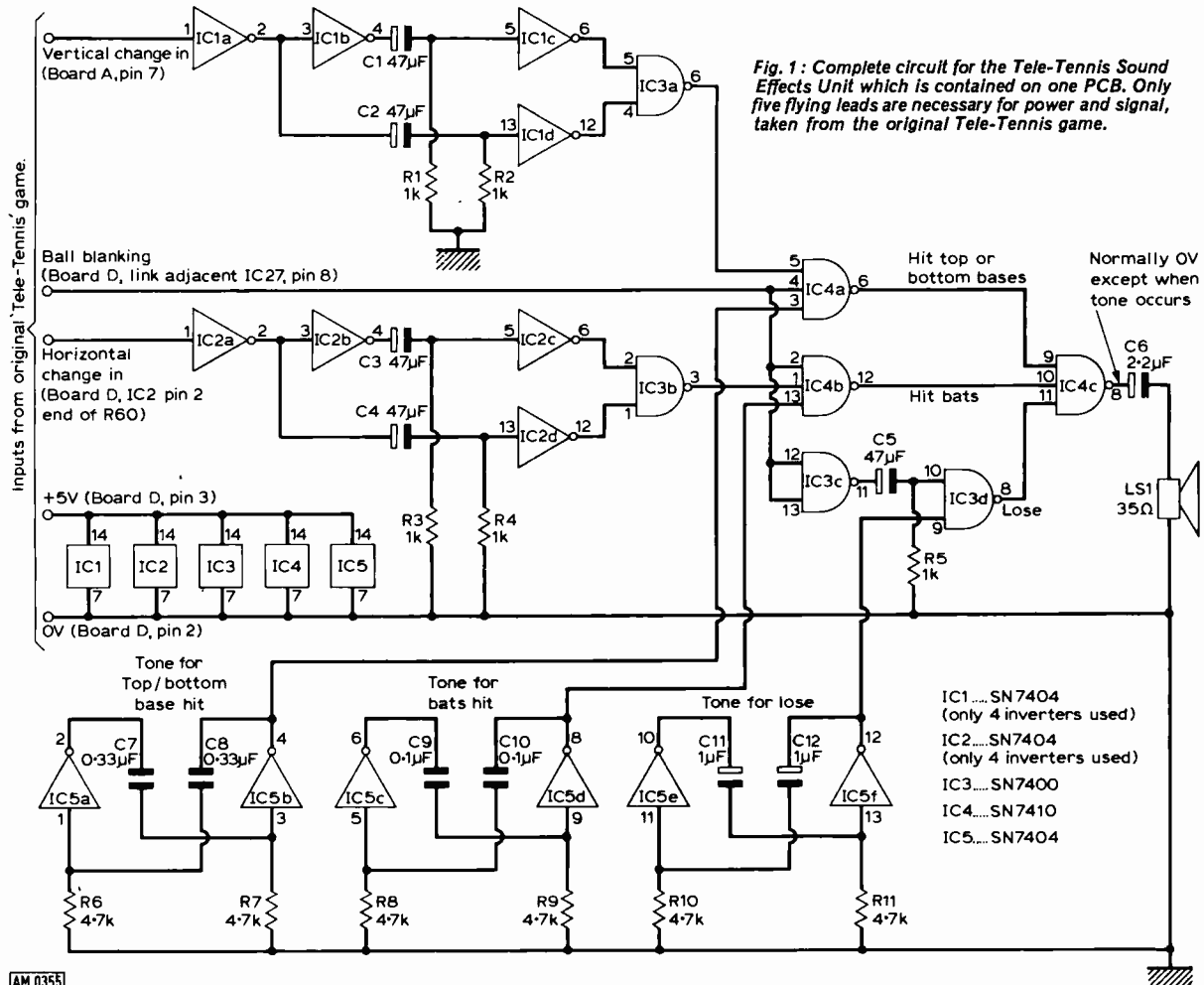


Fig. 1: Complete circuit for the Tele-Tennis Sound Effects Unit which is contained on one PCB. Only five flying leads are necessary for power and signal, taken from the original Tele-Tennis game.

AM 0355

★ components list

Resistors			
R1	1kΩ	R7	4.7kΩ
R2	1kΩ	R8	4.7kΩ
R3	1kΩ	R9	4.7kΩ
R4	1kΩ	R10	4.7kΩ
R5	1kΩ	R11	4.7kΩ
R6	4.7kΩ		1W 10%

Capacitors			
C1	47μF (6V)	C7	0.33μF
C2	47μF (6V)	C8	0.33μF
C3	47μF (8V)	C9	0.1μF
C4	47μF (6V)	C10	0.1μF
C5	47μF (6V)	C11	1.0μF (6V)
C6	2.2μF (6V)	C12	1.0μF (6V)

Integrated circuits			
IC1	SN7404	IC4	SN7410
IC2	SN7404	IC5	SN7404
IC3	SN7400		

Miscellaneous
 LS1, 35Ω loudspeaker. Five, 14 lead DIL sockets., Seven circuit board pins. 5-way panel mounting socket and mating plug. Length of 5-way cable. 140 x 102 mm (5½ x 4in.) fibre glass PCB, available from Crofton Electronics, 124 Colne Road, Twickenham, Middlesex, TW2 6QS. Tel: 01-898 1588. Priced £1.25 including VAT and p & p.

Blanking signal is at Logic Level "1" (i.e. when the ball appears on the screen). When the ball hits top or bottom base the signal, which in the original game was designated "Vertical Change", alternates from a logical "1" to a "0" and vice versa. This signal is therefore ideal to initiate a bleep for a rebound from the top or bottom bases, and can be produced at pin 7 on Board A.

DIFFERENTIATION

IC1a acts as a logic buffer to prevent loading on the original circuitry, so an inverted form of Vertical Change is fed to C2 which differentiates it. Therefore, on the negative going edge of Vertical Change, a positive going pulse (having a width set by the value of C2 and R1) is fed to IC1d. The duration of this pulse is a few hundred milliseconds, long enough to give a useful bleep when used to gate the tone oscillator. A pulse like this must be produced for both the positive and negative edges of Vertical Change so that a bleep is produced by a change in either direction. Therefore the signal from IC1a is inverted by IC1b and is used to carry out the same differentiation operation. IC1c and IC1d together with IC3a, give an OR function so

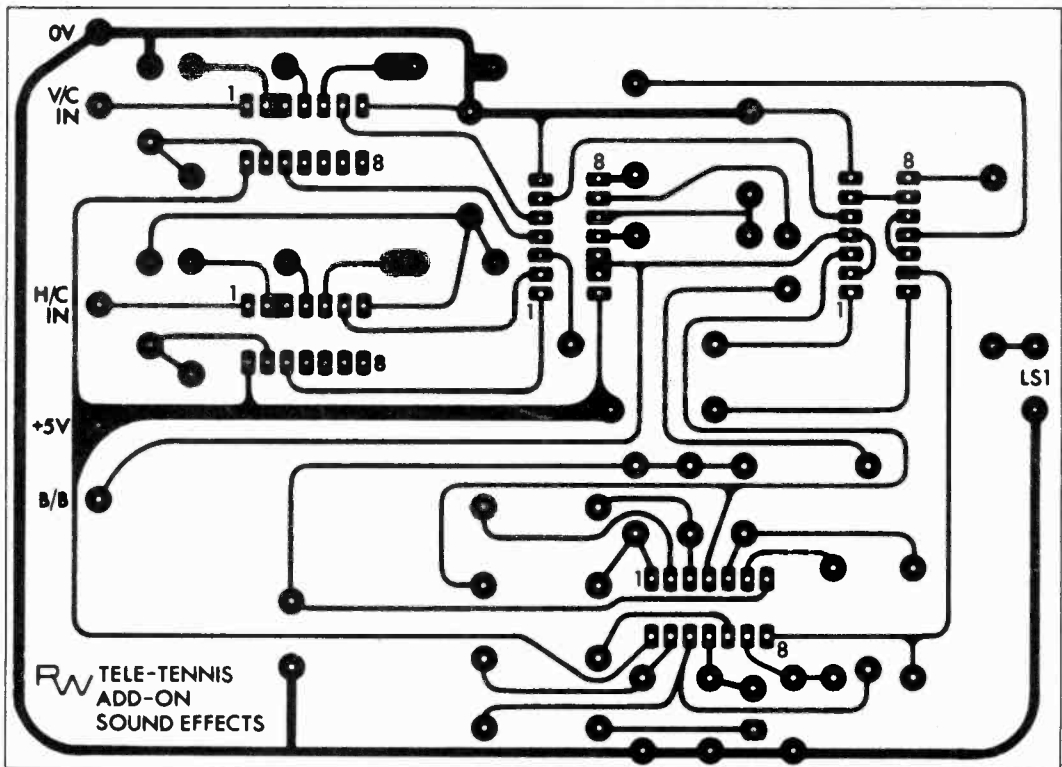
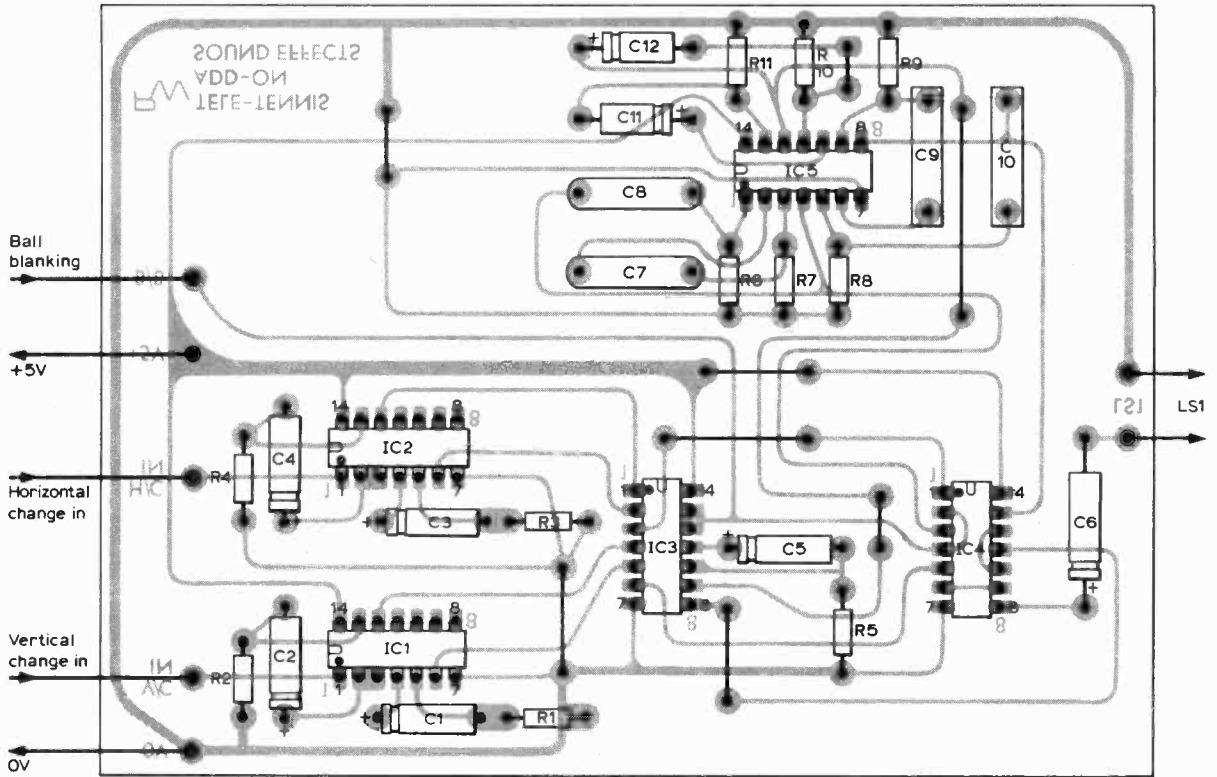


Fig. 2: Top diagram of the PCB gives details of the component layout and flying lead configuration, while the lower drawing shows the foil side only. Both are reproduced full size.

that the output from IC3a will be a positive pulse whenever the ball hits top or bottom base.

This signal is fed to IC4a together with Ball Blanking and the tone from IC5a and IC5b. Provided the ball is bright (i.e. Ball Blanking is "1") the pulse from IC3a will allow the tone to appear at the output of IC4a for the duration of the pulse caused by the contact. This signal is fed to IC4c where it is effectively ORED with the two other signals and fed to the loudspeaker.

A 'GLITCH'


The signal for contact with the bats is produced in exactly the same way except that the Horizontal Change signal is used to initiate it. This signal occurs at pin 2 of IC27 and can be conveniently picked up from the end of R60 going to this pin on board D. A Horizontal Change signal is produced by contact of the ball with either bats or the left and right bases. However, as soon as contact is made with one of the bases, the ball is blanked in a few nanoseconds, and hence the pulse so produced (usually called a "Glitch") is not resolvable as a bleep. The composite stretched pulse, produced by contact of the ball with either bat is fed from IC3b to IC4b, together with Ball Blanking and the tone from IC5c and IC5d. As already mentioned, this signal (the bat hit bleep) is ORED by IC4c before feeding the loudspeaker.

The easiest tone to generate is the rude tone for a lose. It should always occur when the ball is blanked, i.e. on the falling edge of Ball Blanking. Hence Ball Blanking, which is obtained from pin 8 of IC27 on board D, is fed to IC3c which acts as a buffer and an inverter. To gain access to Ball Blanking there is a convenient connection going from pin 8 of IC27 to which a lead can be soldered. The falling edge of Ball Blanking produces a positive-going pulse at the differentiator (C5 and R5) which is used to gate the low frequency from IC5e and IC5f. Some people might like to make the rude tone have a longer duration, in which case the value of C5 can be increased to about 100 μ F.

It is advisable to use a loudspeaker having an impedance not less than 35 Ω , but the prototype has worked on several ranging from 15 to 70 Ω without damage to IC4c. Apart from taking note of this point there are not many critical values in the circuit, although the constructor should stick to the recommended resistor values and be within the quite wide tolerances in capacitance values. The prototype board was mounted with spacers, on the bottom of a metal case made to match the original game, with the loudspeaker bolted to the underside of the lid.

CONCLUSION

The output volume is not great but is ample for a living room. The unit was demonstrated to visitors at the International Audio Fair in Olympia last year and amongst the cacophony of sounds there, it could be heard over quite a long distance.

 Without doubt the addition of this comparatively small extra, livens up the Tele-Tennis game enormously, and those people who have already made the original unit are recommended to try it. 

Points arising . . .

PW EASYBUILD ORGAN

It has come to our notice that the 8ft and 16ft pitch switches were reverse connected. Therefore Figs. 12 (May issue) and 17 (June issue) were incorrectly drawn. The corrected drawings are reproduced, in part, below, with the relevant figure numbers.

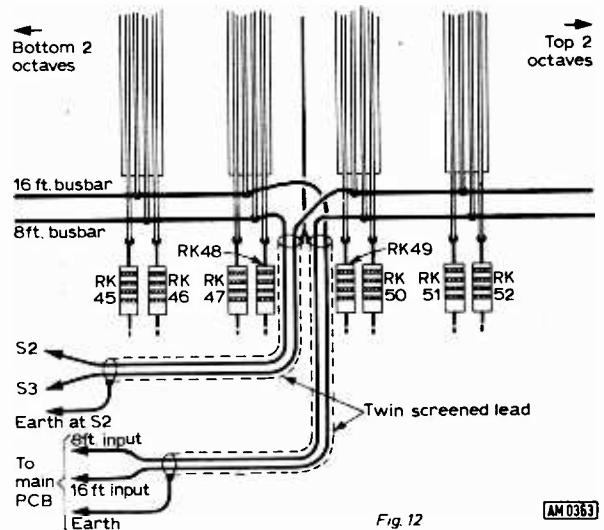


Fig. 12

AM 0363

AM 0364

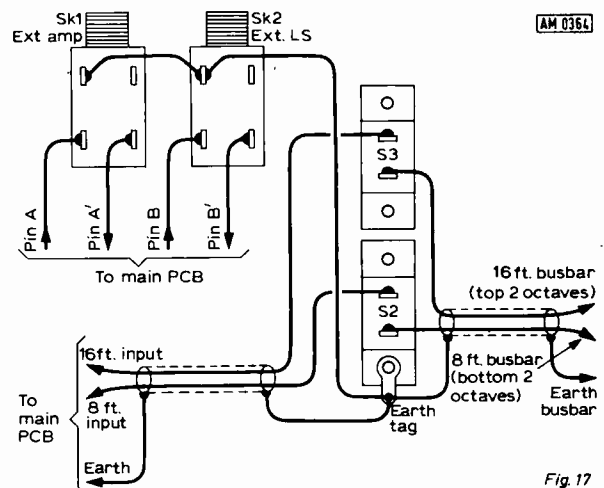


Fig. 17

There has been a number of readers who wanted the base connections of the BCY71's used in the Master osc., Vibrato and Tune circuits. Below is shown the lead configuration of this type viewed from the underside.



Tr1,2 and 3...BCY71
(viewed on connections)

AM 0362

PRODUCTION LINES

colin riches

TEXAS INSTRUMENTS CALCULATOR



A new version of the popular Data-math TI-2500 portable electronic calculator has been announced by Texas Instruments. Model TI-2500 (II) has a percent key and automatic constant in addition to the four basic functions.

Featuring an eight-digit LED display, the TI-2500 (II) weighs less than nine ounces and fits neatly in a pocket, briefcase or purse. With the percent key, problems such as taxes, discounts, and percentage calculations are easily solved.

The automatic constant allows multiplication or division of a series of numbers by one number and addition or subtraction of a constant number to or from a series of numbers.

Operation is either from two "AA" size alkaline batteries or from two nickel-cadmium batteries. Included with the calculator is an AC adapter/charger for use with nickel-cadmium batteries.

The TI-2500(II) electronic calculator is warranted for a period of one year from the original purchase date under normal use and service against defective materials and workmanship. Price is about £30.

Texas Instruments Limited, Manton Lane, Bedford, MK41 7PA

TELE-TENNIS REPRINTS

These are still available from:

Chief Cashier (P.W. Tele-Tennis) IPC Magazines, Tower House, Southampton St., WC2E 9QX. Price is 75p + 7p postage.


12V DRILL

Electroplan Limited, the Royston based distributors of electronic instruments, tools and accessories have introduced a new versatile drill to their range of laboratory bench aids.

Manufactured by EXPO, the 12V operated drill is supplied complete with a full range of accessories which include twist drills, cutting, milling, reaming and grinding tools. Although small, the drill has a high torque with a typical load current between 500mA and 1 Amp.

The chuck rotates at approx. 9000 r.p.m. and has three collets that accommodates the range of accessories.

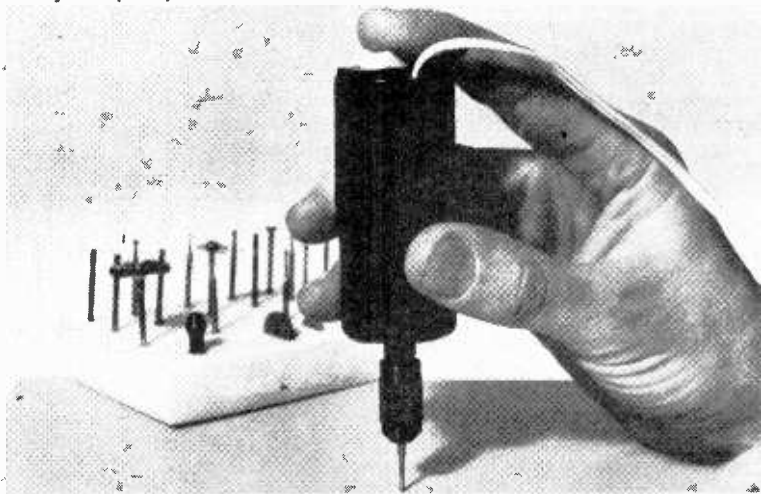The new handy drill will saw, grind, de-burr, brush and polish with the efficiency of drills that are more expensive and larger in size and yet, is sufficiently small to reach places where a conventional drill could not be used. Price is £19.17 plus VAT. Available same day despatch by post. *Electroplan Limited, P.O. Box 19, Orchard Road, Royston SG8 5HH, Herts. Tel: Royston (0763) 41171*



TAKING THE MICKEY?

When I first saw the picture of this new Decimo calculator, I wondered if it was a take-on but I've found it's quite genuine and not such a mickey-taking idea as it at first seems!

Known as the Mickey Math, it is a basic four-function, one-chip calculator with green read-out, powered by four pen-cells and with facilities for an external 6V power supply. It's not pocket-sized (unless you're a poacher) as it's 7½ in. square, but it's robust and ideal for being stuffed into a school satchel without being damaged.

Basically, the Mickey Math is a bit of a gimmick but it's a calculator that should appeal to children and perhaps initiate them into the use of a



calculator—something which will be very useful to them in these days of scientific advancement (rich Dads take note).

At £17.50 plus VAT it's not cheap for what it does but it'll raise a laugh even if people do think you are a bit Goofy using it!

Further gen from *Douglas Dorsett, Managing Director, Decimo Limited, Park House, 2/16 Chobham Street, Luton, Beds.*


WIRE STRIPPER



The Scotchlok TH 213 tool is a pliers type stripper which operates without adjustment on wires from 0.75 to 6 mm² conductor area ($\frac{3}{32}$ to $\frac{1}{4}$ in²). Quick and easy to use, the tool cuts into the insulation and strips it from the core in one simple action, without risk of damage to solid or stranded conductors. The TH 213 has a spring loaded return action so that it is always ready for immediate use, and has an auxiliary side wire cutter. The 213 wire stripper is 183 mm (7 $\frac{1}{4}$ in) long and weighs less than 180 g (approximately 6oz). Further gen from: *3M United Kingdom Limited, 3M House, Wigmore Street, London W1A 1ET.*

NEW CASES

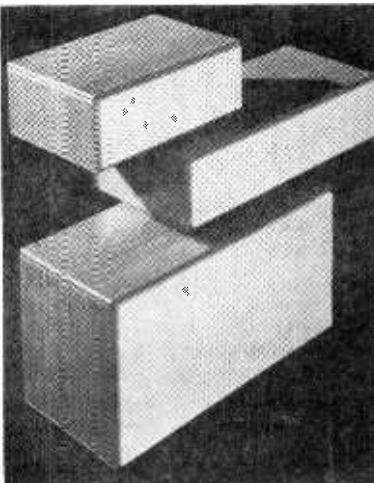West Hyde Developments have announced some useful little cases with a woodgrain finish. They come in 13 sizes and prices range from £4.64 (Mod. 2-A) to £14.63 (Mod 2L), excluding p.p. and VAT. Further information from *West Hyde Developments Limited, Ryefield Crescent, Northwood Hills, Northwood, Middx. HA6 1NN.*



BSR DECK

BSR Limited have introduced a new series of belt drive transcription engineered turntables. First in the series is the BDS80. The belt gives almost silent power transmission between the constant speed high-torque motor and the 4lb machined, diecast turntable thereby reducing 'rumble' to an insignificant level.

The BDS80 has a low-mass aluminium tone-arm with a calibrated stylus pressure control. There is provision for full counter-balance adjustment and bias compensation. A viscous cueing device ensures a

feather-like touchdown of the stylus on a record and the head-shell incorporates a slide-in carrier.

A 'click' suppressor and a muting switch are fitted to eliminate the possibility of unwanted noise through the amplifier while the 'set-down' and 'switch-off' are in operation.

The BDS80 comes complete with an ADC K7E cartridge. Mounted in a plinth with cover, the suggested retail price is £41.00. In chassis form, the price is £25.20. *BSR Limited, Monarch Works, Cradley Heath, Warley, Worcs., B64 5QH.*



BSR BDS80 deck

NEW LIFE FOR WHARFEDALE

Rank Radio International Limited are offering their dealers a new XP range of speakers carrying the well-known names of Denton, Linton and Glendale. All will have greater power handling and better performance than their predecessors.

These new speakers were introduced to the Company's dealers at it's Hi-Fi Dealer Conference at the Skyline Hotel, Heathrow on 6th April.

The previous Denton 2 (launched in 1967) and Linton 2 (launched in 1965) have each narrowly approached the half million mark in production and have been successfully sold throughout the world. Succeeding these will be the Denton 2XP and Linton 3XP.


All the three new loudspeakers have been given a new appearance. They can be used with or without their grille cloth which is held in place with simple snap fastenings.

Further information and prices from:—*Rank Radio International, PO Box 596, Power Road, Chiswick, London W4 5PW. Tel: 01 994 6491.*

VERO HANDLES

Vero (the board makers) are marketing a range of handles which help to give a professional look to items of home-constructed equipment, etc.

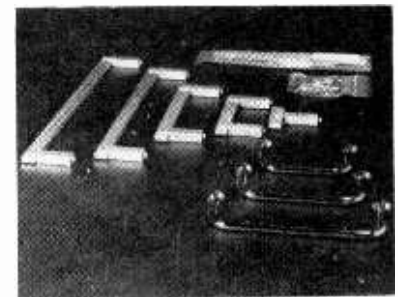In addition to the range of chrome "D" handles, an aluminium panel handle with an attractive anodised finish can now be supplied. Handles are available in various sizes suitable for panels from 1 $\frac{3}{4}$ in to 10 $\frac{1}{2}$ in height. *Vero Electronics Ltd., Industrial Estate, Chandler's Ford, Eastleigh, Hants.*



SPARKRITE MK2

CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and therefore eliminates the possibility of blowing the transistors or the SCR. (Many capacitive discharge ignitions are not completely foolproof in this respect.)


Sparkrite can therefore give you: up to 20% better fuel consumption, instant all weather starting, cleaner plugs—they last up to 5 times longer without attention, faster acceleration, higher top speeds, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

NOTE—FUEL CONSUMPTION. The fitting of a Sparkrite Mk. 2 should reduce fuel consumption although the amount of the reduction will vary. A fair estimate of the savings which could be expected, based on reports by our customers and upon our own experience, are as follows:
 any 4-cylinder vehicle, 10% improvement
 any 6-cylinder vehicle, 15% improvement
 any 8-cylinder vehicle, 20% improvement
 It is worth remembering that while fuel saving is important there are many other advantages to be gained from fitting a Sparkrite ignition system.

Voted best of 8 ignition systems tested by a leading Motoring Magazine



THE KIT COMPRISES EVERYTHING NEEDED: Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink, top quality 5-year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.
WE SAY IT IS THE BEST SYSTEM AT ANY PRICE

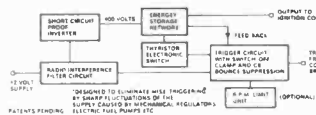

OPTIONAL EXTRAS
Electronic A.P.M. limitation
 This can be included in the unit to prevent over revving, an advantage to most companies, hire firms, high performance drivers, etc.
Electronic/conventional ignition switch.
 Gives instant changeover from Sparkrite ignition to conventional ignition for performance comparisons, static timing, etc. and will also switch the ignition off completely as a security device, includes switch, connectors, mounting bracket and instructions. Cables excluded.

PRICES: D.I.Y. assembly kit £10.93*. Ready built unit £13.88* (both to fit all vehicles with coil/distributor ignition up to 8-cylinders).
 Switch for instant changeover from Sparkrite ignition to conventional ignition £2.78*. R.P.M. limiting control £2.42* (fitted in case on ready built unit, dashboard mounting on kit).
 * Including VAT, post and packing.
 We can supply units for any petrol-engined vehicle (boat, motorcycle, etc.) with coil/contact breaker ignition. Details on request.
CALL IN AND SEE US FOR A DEMONSTRATION.

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES

These project boxes are manufactured from 18-gauge aluminium and come complete with lids and screws.

The prices shown include VAT (at 8%) but 18p should be added to the total order value for postage and packing.

Order No	Length (in)	Width (in)	Height (in)	Price (inc. VAT)
7	5 1/2	2 1/2	1 1/2	47p
8	4	4	1 1/2	48p
9	4	2 1/2	1 1/2	46p
10	5 1/2	4	1 1/2	49p
11	4	2 1/2	2	46p
12	3	2	1	38p
13	6	4	2	56p
14	7	5	2 1/2	75p
15	8	6	3	93p
16	10	7	3	£1.14

Boxes can be made to any size but the minimum order for special sizes is 500. General trade enquiries welcome.

FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12 volt, 8 watt, fluorescent light. Everything needed is supplied: white enamelled drilled metalwork, ready drilled heat-sink, printed circuit board, high quality components and transformer, end caps, cable, the fluorescent tube, nuts, bolts, washers, and simple assembly and operating instructions.

When complete the light has many uses: workshop and workbench illumination, garage lighting, emergency lighting, lighting for camping, caravanning, and boating, as an inspection lamp and many more.

If you can't spare 1 hour to put the light together then we will supply it ready built (FOR A FEW EXTRA PENCE)

PRICES:
 Assembly kit £3.46 inc. VAT post and packing.
 Ready built £4.10 inc. VAT post and packing.
 Diffuser 59p inc. VAT post and packing.

ORDER NOW

To: ELECTRONICS DESIGN ASSOCIATES DEPT PW7
 82 Bath Street, Walsall WS1 3DE Phone 33652

From: Name

Address

Please Supply Quantity

SPARKRITE Mk. 2 DIV assembly kits at £10.93	
SPARKRITE Mk. 2 ready built negative earth at £13.88	
SPARKRITE Mk. 2 ready built positive earth at £13.88	
Ignition changeover switches at £2.78	
R.P.M. Limit systems in the above units at £2.42	
Fluorescent light assembly kits at £3.46	
Fluorescent light built units at £4.10	
Diffusers for the above at 59p	
of number alum boxes at	
of number alum boxes at	
of number alum boxes at	

I enclose cheque P.O. or £ Cash No (Send S.A.E. if brochure only required)

VALVE BARGAINS

Any 5 64p, 10 99p, 50 £4.15,
 Your choice from the following list:

ECC82, ECL80, EB91, EF80, EF183, EF184, PC86, PC88, PC97, PC900, PCC84, PCC89, PCC189, PCF80, PCF802, PCF805, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14

Colour Valves 30p each
 PL508, PL509, PY500/A

Press 4 Button UHF Tuners £2.90.

Prices include V.A.T. P. & P. under £1/15p, £1 to £3/20p over £3/25p.

ELECTRONIC MAILORDER LTD., 62 Bridge Street, Ramsbottom, Bury, Lancs 1.

AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.

B11 — For Stereo and Standard VHF Radio

B12 — For the older VHF Television, please state BBC1 & ITV Channels.

B45 — For mon. or colour this covers the complete UHF band.

All Boosters are complete with Battery and take only minutes to fit.

Price £3.90 each

Semiconductor Specialists (U.K.) LTD.

PREMIER HOUSE, FAIRFIELD ROAD, YIEWSLEY, WEST DRAYTON, MIDDX. UB7 8EX

FOR YOUR P.W. ELECTRONIC ORGAN

AY-5-0212 Master Tone Generator £5-55
 AY-5-5051 4 Stage Divider £1-20

FOR YOUR ELECTRONIC CALCULATOR

C550 G.I. 8 Digit Calculator Circuit £6-50
 MAN 3M Seven Segment 0-127" LED £1-43

FOR YOUR DIGITAL CLOCK

AY-5-1224 12/24 Hour Clock Circuit £4-25
 NEW MAN 4000 Series 0-4" Seven Segment Common Cathode LED Display in Red, Yellow & Green £2-15

ADD 25% VAT TO TOTAL

And 30p Postage Per Order

MAIL ORDER ONLY

CALCULATRICKS

R. STAWICKI

With ever growing numbers of electronic calculators in use the craze of 'calculatricks' just had to come sooner or later! Imagine the scene—there you are, with a calculator in your hand, thinking of a calculation which will put the electronic wizard to a real tough test, at the same time knowing that the answer will come out instantaneously and correct, up to the last decimal point. or will it?

For instance, your calculator will tell you the name of our local barmaid! Try it, as I did. Her phone number 31471, and clearly defined 40, 26, 36 vital statistics were the only data available. Therefore enter $31471 + 40 + 26 + 36$ and the result:—

31573

might not mean much to you at first glance but if you turn the calculator upside down the full impact of its hitherto undiscovered potential strikes you and drives you to further tests, and so calculatricks gains another addict.

Want to know what my job is like now? That's easy to work out. I started 12 years ago at a salary of £1,289, but this is now worth only about half. Therefore enter 1289, divide by 2=644.5 and multiply by 12 to find out what my job is like at present. The answer, right enough, is 7734, upside down.

7734

If you use your car travelling 35.5 miles around for a day for 20 working days every month, what should you check?

710

Do you want to find out what could be in my girl-friend's pockets? No names, no telephone exchange given but all data absolutely genuine! We have four known facts on her vital statistics:— B=35, W=24, H=36 and phone number P=4692. Using the formula:

$(B \times W \times H) + (P \times \text{Workdays/week}) + \text{number of known facts}$.

Therefore: $(35 \times 24 \times 36) + (4692 \times 5) + 4 =$

53704


is the answer to your question.

And a topical one? 14215 investors each buy shares worth £469 to buy 5 tankers. So who owns the tankers?

So start by entering 14215469×5 , turn it upside-down and hey presto! You have the answer!

71017345

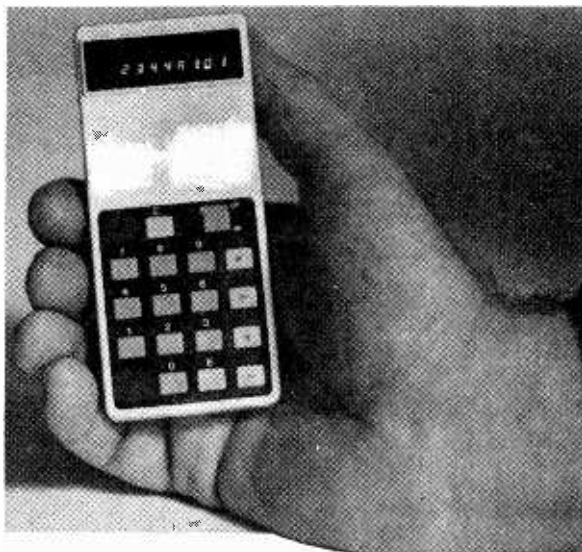There must be countless other calculatricks still to be discovered so try it yourself. All you need



is an electronic calculator with an eight-digit capacity and seven-segment type of display.

You have paid 81p for two drinks. Where? simply divide £0.81 by 2 to find out the answer which is

0405

This one is more complicated and shows the planned maintenance points of my car, calculated as follows:

Engine number	19249
Number of shifts worked	3
Max. number of days in month	31
Max. number of months between service	6
Number of work days per week	5
Therefore	$19249 \times 3 \times 31 \times 6 \times 5 =$

53704710

which indicates the points needing attention.

Sharing the car with your wife? If you drive to work 9 miles and she drives a further 25.5 miles with return journeys that's twice each day for 5 days a week = 10 journeys. The formula is simply $(9 + 25.5) \times 10$ and the answer 345 will tell you who should pay for the petrol.

345

Finally a true calculator addict will not count the people at a party. He will count the legs and divide by two. Much more fun that way and always a chance to prove your calculator wrong if Long John Silver comes along. . . .!

Dw

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

10p for 1 Valve.
Each additional Valve add 2p in UK

DM70	0.61	ECL83	0.66	GY501	1.18	PLR2	0.48	30C1/PCF80	
DY51	0.80	ECL86	0.64	GZ34	0.80	PLR3	1.04	30C15/	0.54
DY86/7	0.41	EP80	0.42	PC86	0.95	PLR4	0.68	PCF800	1.01
DY802	0.48	EP83	0.98	PC88	0.95	PL500	0.90	30C17	1.01
EACB90	1.03	EP85	0.42	PC90	0.57	PL508	1.24	30C18/	
EB91	0.64	EP86	1.16	PC94	0.50	PL509	1.56	PCF805	1.00
EB98	0.79	EP89	1.14	PC98	0.88	PL802	1.40	30F5/PT818	
EBF80	0.58	EP91	1.00	PC99	0.64	PY33	0.65		1.03
EBF83	0.59	EP92	1.37	PC99	0.80	PY81/800	0.49	30FL1/	
EBF89	0.53	EP93	0.63	PCF80	0.54	PY82	0.57	PCF800	1.00
EC86	0.78	EF184	0.63	PCF82	1.22	PY800A	1.00	30FL2	0.80
EC88	0.76	EH90	0.85	PCF86	0.64	PY800	0.49	30FL12	1.13
EC90	0.86	EL34	0.92	PCF200	1.00	PY901	0.49	30FL14	1.00
EC97	0.60	EL36	1.01	PCF201	1.00	U26	0.88	30L1/PC84	
EC98	0.47	EL42	0.85	PCF202	0.84	U191	0.88		0.54
EC99	0.44	EL41	0.85	PCF802	0.70	U193	0.50	PC805	1.03
EC983	0.47	EL81	0.47	PCF806	0.64	U194	0.71	PC805	1.03
EC984	0.58	EL84	0.85	PCG1200	1.15	UBC80	0.90	PC805	1.03
EC985	0.71	EL86	0.85	PCG1200	1.15	UBC81	0.71	PC805	1.03
EC988	0.84	EL86	0.85	PCL82	0.58	UBF89	0.58	30P4MR	1.27
EC989	0.85	EL91	0.00	PCL83	0.64	UC85	0.59		
EC990	0.60	EL91	0.00	PCL84	0.61	UC181	1.12	PC801	1.01
EC991	0.85	EL95	0.72	PCL85	0.64	UC182	0.72	30P19/	
EC992	0.88	ELL80	2.50	PCL86	0.64	UC183	0.72	PC805	0.89
EC998	0.68	EY51	0.79	PCL805/85		UF89	0.80	30PL1/	
ECH181	1.18	EY86/7	0.40	PD500	1.88	UL84	0.92	PC801	1.00
ECH83	0.94	EY88	0.72	PFL200	0.83	UY85	0.54	PC805	1.15
ECH184	1.00	EZ80	0.54	PL36	0.90	ECX804	0.98	30PL14/	
ECL80	0.67	EZ80	0.54	PL81	0.77	6P23/EP812	1.03	FCL88	1.85
ECL82	0.64	EZ81	0.38	PL81A	0.90			30PL15	1.13

NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

AZ1	0.75	EF39	1.25	KTW61	1.50	PY83	0.50	6P28	0.75
AZ31	0.80	EF80	0.35	MU14	1.00	PY86	0.58	6J35M	0.65
CL13	1.40	EF86	0.50	NU78	3.50	PY800	1.10	6J36G	0.65
CL33	0.50	EF86	0.50	OA2	0.45	PY81/800	0.50	6J36	0.35
CY31	0.60	EF89	0.35	OB2	0.45	Y801	0.55	6J7G	0.35
DAF91	0.40	EF91	0.40	PC86	0.65	SP41	3.00	6J7M	0.65
DAF96	0.60	EF92	0.50	PC88	0.65	SP61	0.85	6K6GT	0.80
DOC90	1.35	EP95	0.45	PC97	0.55	T41	1.00	6K7G	0.35
DF91	0.40	EP98	0.60	PC900	0.55	U14	0.75	6K7M	0.45
DF96	0.80	EP183	0.40	PC984	0.45	U25	1.00	6K8G	0.45
DK91	0.50	EF184	0.40	PC988	0.82	U26	0.85	6K8M	0.70
DK92	1.00	EL32	0.60	PC989	0.55	U191	0.75	6K25	1.00
DK96	0.75	EL33	2.50	PCF189	0.65	UABC80	0.40	6L6G	0.55
DL92	0.50	EL34	0.70	PCF80	0.40	UAF42	0.75	6Q7G	0.40
DL94	0.43	EL36	0.60	PCF82	0.42	UBC41	0.80	6Q7M	0.60
DL98	0.55	EL41	0.90	PCF86	0.85	UBC91	0.50	6B17GT	0.55
DY86	0.45	EL42	1.55	PCF88	0.65	UBF80	0.50	6B7GT	0.55
DY87	0.45	EL42	1.55	PCF801	0.60	UBF89	0.50	6B7GT	0.55
DY802	0.47	EL84	0.35	PCF806	0.90	UCB56	0.50	6B7GT	0.55
EACB90	0.38	EL85	0.65	PCF806	0.90	UCB86	0.50	6U6G	1.50
EAF42	0.70	ELL80	2.00	PCF808	1.00	UCB87	0.50	6U6G	1.50
EB91	0.25	EM80	0.55	PCL82	0.45	UCB88	0.50	6V6GT	0.60
EB93	0.40	EM81	0.80	PCL83	0.70	UCB89	0.50	6X4	0.45
EB94	0.40	EM84	1.00	PCL84	0.60	UCB91	0.70	6X5G	0.45
EBF80	0.40	EM87	1.00	PCL85	0.60	UCB92	0.70	6X5GT	0.45
EBF83	0.40	EY51	0.45	PCL805/85		UD1	0.75	6X8GT	0.45
EBF89	0.52	EY86	0.45			UF89	0.50	7B8	0.80
EBC11	2.00	EZ40	0.60	PD500	1.50	UL41	0.85	7B7	0.80
EBC41	0.75	EZ41	0.75	PEN45	0.85	UL84	0.50	7C5	1.80
EBC81	0.40	EZ81	0.30	PL35	0.85	UY41	0.55	7C6	1.00
EBC82	0.40	EZ81	0.30	PL35	0.85	UY85	0.45	7H7	0.80
EBC84	0.35	EZ80	0.30	PL35	0.85	VR105/30	0.40	7R7	0.80
ECC86	0.50	GY501	0.85	PL82	0.50	VR160/30	0.45	787	2.25
ECC88	0.45	GZ32	0.65	PL83	0.50	W4	0.80		0.80
ECC89	0.50	GZ32	0.65	PL84	0.50	6A25	0.80	12A7	0.45
ECH42	0.85	GZ34	0.75	PL500	0.85	6A26	0.80	12A7T	0.45
ECH81	0.35	GZ37	1.25	PL504	0.85	6A27	0.80	12A8	0.50
ECH83	0.50	HN309	1.50	PL508	0.90	6A28	0.80	12A8T	0.45
ECL80	0.60	KT81	2.50	PL509	0.85	6A29	0.80	12A8T	0.45
ECL82	0.40	KT86	2.95	PL802	1.55	6A30	0.80	12A8T	0.45
ECL83	0.75	KT81 (7C5)	0.85	PX25	3.50	6A31	0.80	12A8T	0.45
ECL86	0.55	KT81	1.30	PY33	0.88	6A32	0.80	12A8T	0.45
ECLL800	3.50	KT81	1.75	PY81	0.50	6A33	0.80	12A8T	0.45
EF37A	1.20	KT88	3.25	PY82	0.45	6A34	0.80	12A8T	0.45

TRANSISTORS-INTEGRATED CIRCUITS

All transistors, I.C's offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.

EXPRESS POSTAGE

10p per order in UK

AA119	0.07	BD124	0.65	OA200	0.08	ZTX501	0.15	2N2904A	0.25
AA213	0.12	BD131	0.42	OA202	0.08	ZTX503	0.16	2N2905	0.32
AA218	0.10	BD132	0.50	OC16	1.00	ZTX531	0.16	2N2905A	0.25
AC107	0.51	BF115	0.20	OC20	2.00	ZTX600	0.15	2N2906	0.20
AC126	0.25	BF167	0.25	OC23	1.25	IN914	0.06	2N2926	0.12
AC127	0.25	BF173	0.28	OC25	0.40	IN4001	0.06	2N3053	0.18
AC128	0.15	BF179	0.38	OC28	0.68	IN4002	0.07	2N3055	0.45
AC176	0.25	BF180	0.33	OC35	0.55	IN4003	0.08	2N3225	0.91
AC187	0.21	BF181	0.35	OC36	0.60	IN4004	0.08	2N3614	0.85
AC188	0.20	BF194	0.30	OC42	0.40	IN4005	0.15	2N3615	0.95
ACY21	0.22	BF195	0.13	OC44	0.20	IN4006	0.12	2N3709	0.10
AD140	0.75	BF197	0.15	OC45	0.20	IN4007	0.12	2N3703	0.12
AD149	0.50	BF200	0.32	OC46	0.18	IN4009	0.06	2N3704	0.14
AD149	0.50	BF201	0.25	OC48	0.28	IN4148	0.06	2N3705	0.15
AD161	0.44	BF698	0.25	OC55	0.55	IN4003	0.07	2N3706	0.11
AD162	0.44	BFV10	0.81	OC62	0.60	IN4004	0.08	2N3707	0.13
AF115	0.25	BF194	0.28	OC64	0.40	IN2051A	0.25	2N3708	0.07
AF116	0.25	BF195	0.24	OC69	0.28	IN2051B	0.20	2N3709	0.10
AF117	0.24	BFY51	0.20	OC71	0.18	IN4007	0.12	2N3703	0.12
AF186	0.48	BFY52	0.20	OC72	0.28	IN4148	0.06	2N3705	0.15
AF239	0.48	BY100	0.27	OC76	0.30	18921	0.07	2N3706	0.11
ASV27	0.33	BY126	0.14	OC77	0.55	182033	0.20	2N3707	0.13
BA108	0.25	BY127	0.15	OC81	0.40	182051A	0.25	2N3708	0.07
BA109	0.25	BZK61 series		OC81B	0.28	182100A	0.20	2N3709	0.10
BA115	0.10			OC81Z	0.45	183010	0.25	2N3710	0.11
BC107	0.14	HZY88 series		OC83	0.27	2N695	0.15	2N3711	0.11
BC108	0.13			OC140	1.14	2N697	0.16	2N3819	0.38
BC112	0.12	CR81-05	0.30	OC170	0.30	2N706	0.10	2N3820	0.60
BC113	0.15	CR81-40	0.80	OC171	0.30	2N706A	0.12	2N3823	0.50
BC117	0.21	CR83-06	0.40	OC200	0.55	2N1131	0.25	2N3903	0.14
BC143	0.30	CR83-40	0.85	OC201	1.00	2N1132	0.24	2N3904	0.20
BC147	0.10	MJES40	0.47	OC202	0.90	2N1302	0.18	2N3905	0.25
BC148	0.08	MJES70	0.88	OC203	0.55	2N1303	0.18	2N3906	0.25
BC189C	0.15	MJE520	0.85	OC271	1.20	2N1304	0.22	2N4058	0.15
BC189E	0.12	MJE2855	1.27	ORP12	0.60	2N1305	0.22	2N4059	0.10
BC189F	0.12	MJE3055	0.78	ORP16	0.55	2N1306	0.28	2N4060	0.18
BC184L	0.13	MFP109	0.40	TOC44	0.29	2N1307	0.28	2N4061	0.18
BC338	0.15	MPP103	0.38	TZ226D	1.50	2N1308	0.28	2N4062	0.14
BCY32	0.85	MPP104	0.35	TIL209	0.20	2N1309	0.20	2N4289	0.30
BCY38	0.38	MPP105	0.38	TX1207	0.12	2N1613	0.31	3N125	1.75
BCY34	0.46	NETA04	0.65	ZTX108	0.08	2N1614	0.45	3N141	0.81
BCY70	0.18	OA5	0.72	ZTX300	0.13	2N2147	0.78	40360	0.40
BCY71	0.82	OA19	0.40	ZTX301	0.14	2N2149	0.78	40361	0.45
BCY72	0.18	OA79	0.10	ZTX302	0.18	2N2899A	0.18	40382	0.40
BCV11	0.65	OA81	0.18	ZTX304	0.24	2N2646	0.50	40430	0.88
BD121	1.00	OA91	0.07	ZTX500	0.13	2N2904	0.20		

SN7400	0.18	SN7428	0.40	SN7486	0.47	SN74145	1.26	SN74192	2.00
SN7401	0.18	SN7430	0.18	SN7490	0.55	SN74150	1.75	SN74193	2.00
SN7402	0.18	SN7433	0.37	SN7491A		SN7			

CHROMASONIC electronics

Dept. 1. 56, Fortis Green Road,
Muswell Hill, London. N10 3HN.
telephone: 01-883 3705

C-MOS

74 TTL


LINEAR I.C.'s

C-MOS			74 TTL			LINEAR I.C.'s			
1-24	25-99	100up	1-24	25-99	100+				
CD4000AE	23p	19p	5p	7400	14p	12p	10p	555 (8 pin dip) V	55p
CD4001AE	23p	19p	15p	7401	14p	12p	10p	555 (TO-99) T	81p
CD4002AE	23p	19p	15p	7402	14p	12p	10p	556 (14 pin dip)	£1.29
CD4006AE	£1.59	£1.33	£1.06	7403	15p	12p	10p	703 (RF/IF Amp)	59p
CD4007AE	23p	19p	15p	7404	16p	13p	11p	709 (8 pin dip)	33p
CD4008AE	£1.75	£1.46	£1.17	7405	16p	13p	11p	709 (14 pin dip)	34p
CD4009AE	Use	CD4049		7408	16p	13p	11p	710 (8 pin dip)	34p
CD4010AE	Use	CD4050		7409	16p	13p	11p	710 (TO-99)	39p
CD4011AE	23p	19p	15p	7413	29p	24p	20p	710 (14 pin dip)	38p
CD4012AE	23p	19p	15p	7417	27p	22p	20p	711 (TO-99)	49p
CD4013AE	69p	58p	46p	7420	20p	13p	11p	711 (14 pin dip)	38p
CD4014AE	£1.75	£1.46	£1.17	7427	27p	22p	18p	720 (A.M. Radio)	£1.76
CD4015AE	£1.75	£1.46	£1.17	7430	16p	13p	11p	723 (TO-99)	94p
CD4016AE	69p	58p	46p	7432	27p	22p	18p	723 (14 pin dip)	64p
CD4017AE	£1.75	£1.46	£1.17	7437	27p	22p	18p	741 (8 pin dip)	31p
CD4018AE	£2.51	£2.09	£1.67	7441	75p	62p	50p	741 (TO-99)	37p
CD4019AE	10p	8p	5p	7442	65p	55p	43p	741 (14 pin dip)	31p
CD4020AE	£1.97	£1.64	£1.31	7445	85p	71p	57p	747 (14 pin dip)	90p
CD4021AE	£1.75	£1.46	£1.17	7447	95p	83p	67p	748 (8 pin dip)	36p
CD4022AE	£1.83	£1.53	£1.22	7447A	95p	83p	67p	748 (TO-99)	44p
CD4023AE	23p	19p	15p	7448	85p	71p	57p	748 (14 pin dip)	42p
CD4024AE	£1.26	£1.05	84p	7470	30p	25p	20p	753 (F.M. str. I.F.)	£1.08
CD4025AE	23p	19p	15p	7472	25p	21p	17p	75491	
CD4026AE	£2.79	£2.33	£1.86	7473	30p	25p	20p	75492	£1.10
CD4027AE	98p	82p	65p	7474	30p	25p	20p	Regulators 100mA	
CD4028AE	£1.53	£1.28	£1.02	7475	47p	39p	31p	78105WC (TO-18)	60p
CD4029AE	£1.12	£1.76	£1.41	7476	32p	26p	21p	7812WC (TO-92)	60p
CD4030AE	71p	59p	47p	7482	75p	62p	50p	7815WC (TO-92)	60p
CD4035AE	£1.75	£1.46	£1.17	7485	£1.30	£1.09	87p	Regulators 100mA	
CD4040AE	£2.01	£1.68	£1.34	7486	32p	26p	21p	78105WC (TO-18)	60p
CD4042AE	£1.49	£1.24	99p	7489	£3.56	£2.80	£2.10	7812WC (TO-92)	60p
CD4049AE	69p	58p	46p	7490	49p	40p	32p	7815WC (TO-92)	60p
CD4050AE	69p	58p	46p	7491	65p	55p	45p	Regulators 100mA	
CD4051AE	£2.78	£2.32	£1.85	7492	57p	46p	36p	78105AWC (TBA625A) 90p	
CD4052AE	£2.78	£2.32	£1.85	7493	49p	40p	32p	7812AWC (TBA625B) 90p	
CD4056AE	£2.12	£1.76	£1.41	7495	67p	55p	45p	7815AWC (TBA625C) 90p	
CD4060AE	£2.51	£2.09	£1.67	74100	£1.08	89p	72p	Regulators 500mA	
CD4066AE	£1.13	94p	75p	74107	35p	29p	22p	78M05HC	£1.35
CD4068AE	28p	24p	19p	74121	34p	29p	23p	78M12HC	£1.35
CD4069AE	28p	24p	19p	74122	47p	39p	31p	78M15HC	£1.35
CD4070AE	28p	24p	19p	74141	78p	63p	53p	78M18HC	£1.35
CD4071AE	28p	24p	19p	74145	68p	58p	48p	78M24HC	£1.35
CD4077AE	71p	59p	47p	74154	£1.75	£1.48	80p	Regulators 1A	
CD4081AE	28p	24p	19p	74174	£1.00	83p	67p	7805KC (TO-3)	£2.09
CD4082AE	28p	24p	19p	74180	£1.06	88p	71p	7812KC (TO-3)	£2.09
CD4085AE	£1.28	£1.06	85p	74181	£3.20	£2.50	£1.90	7815KC (TO-3)	£2.09
CD4086AE	£1.28	£1.06	85p	74192	£1.35	£1.14	90p	7818KC (TO-3)	£2.09
CD4092AE	£1.56	£1.20	£1.04	74193	£1.65	£1.14	90p	7824KC (TO-3)	£2.09
CD4099AE	£2.95	£2.46	£1.96	74196	£1.34	99p		Regulators 1A	

SIEMENS LCD's

LINE-O-LIGHT

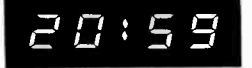LIQUID CRYSTAL DISPLAY complete with socket and removable reflective backing. Ref AN4132K 13mm character height. Can be directly driven by National Semiconductors Alarm Clock chip MM5316. £13.99



NEW LED Linear Cursors emit device contains 10 light emitting diodes in a 20pin dual-in-line package. Ideal for solid state analogue meters or dials. Type 101 RED £2.26

Regulators

Regulators 100mA
78105WC (TO-18) 60p
7812WC (TO-92) 60p
7815WC (TO-92) 60p

Regulators 100mA
78105AWC (TBA625A) 90p
7812AWC (TBA625B) 90p
7815AWC (TBA625C) 90p

Regulators 500mA
78M05HC £1.35
78M12HC £1.35
78M15HC £1.35
78M18HC £1.35
78M24HC £1.35

Regulators 1A
7805KC (TO-3) £2.09
7812KC (TO-3) £2.09
7815KC (TO-3) £2.09
7818KC (TO-3) £2.09
7824KC (TO-3) £2.09

Regulators 1A
7805KC (TO-220) £1.72
7812KC (TO-220) £1.72
7815KC (TO-220) £1.72
7818KC (TO-220) £1.72
7824KC (TO-220) £1.72

Regulators 1A
7805KC (TO-220) £1.72
7812KC (TO-220) £1.72
7815KC (TO-220) £1.72
7818KC (TO-220) £1.72
7824KC (TO-220) £1.72

Regulators 1A
7805KC (TO-220) £1.72
7812KC (TO-220) £1.72
7815KC (TO-220) £1.72
7818KC (TO-220) £1.72
7824KC (TO-220) £1.72

Regulators 1A
7805KC (TO-220) £1.72
7812KC (TO-220) £1.72
7815KC (TO-220) £1.72
7818KC (TO-220) £1.72
7824KC (TO-220) £1.72


PHOTO-DARLINGTON

SPECIAL PURCHASE

SEVEN SEGMENT DISPLAYS

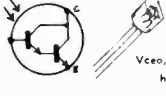

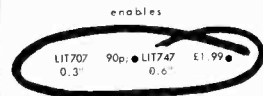
2N5777
Vceo, Vcbo 25v, Vcbo Bv
Vceo, Vcbo 25v, Vcbo Bv
Ifc 2500; Ic 250 mA



enables
L17707 90p, L17747 £1.99



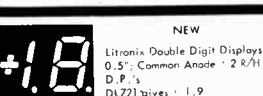I.C. SOCKETS
Dual in-line
TO5
Pins 8 14 16 24 28 36 40 8 10
Price 15p 15p 26p 30p 39p 44p 31p 35p



NEW
Litronix Double Digit Display
0.5" Common Anode - 2 1/2 H
D.P.'s
DL721 gives 0.19
DL722 gives 0.0 to 9.9
Suitable for Clocks, Instruments,
T.V. Channel Indicator
Our Price £4.75 each

L.E.D.'s

Free snap-on plastic retainer

Red	Green	Orange	Yellow
10p	27p	24p	22p
15p	24p	22p	20p
24p	22p	20p	18p
31p	29p	27p	25p

0.125" dia. lens (TL1209)	0.16" dia. lens (MLED 650)	0.2" dia. lens (MLED 650)
1- 10p	1- 10p	1- 10p
10- 10p	10- 10p	10- 10p
100- 10p	100- 10p	100- 10p

Low Cost Red GaAs
Molecular MLED 500
in a TO92 package. 15p

NEW Opto-isolators
ILI (4N25 or TL1116)
6 pin industry standard package
2.5KV isolation £1.00



	COMMON ANODE R/H	COMMON ANODE L/H	COMMON ANODE I	COMMON CATHODE R/H	Our Price
0.3"	RED DL707P	DL707	DL701	DL704	£1.82
	GREEN MAN51	MAN52	MAN53	MAN54	£1.82
	RED MAN71	MAN72	MAN73	MAN74	£1.82
	YELLOW MAN81	MAN82	MAN83	MAN84	£1.82
	ORANGE MAN3610	MAN3620	MAN3630	MAN3640	£1.82
0.4"	GREEN XAN51	XAN52	-	XAN54	£1.49
	RED XAN71	XAN72	-	XAN74	£1.49
	YELLOW XAN81	XAN82	-	XAN84	£1.49
0.5"	GREEN MAN4510	MAN4520	MAN4530	MAN4540	£2.32
	RED MAN4710	MAN4720	MAN4730	MAN4740	£2.32
	YELLOW MAN4810	MAN4820	MAN4830	MAN4840	£2.32
	ORANGE MAN4610	MAN4620	MAN4630	MAN4640	£2.32
0.6"	C.A. L/H Dec. Pr	Ç.A. L/H Dec. Pr	C.C. L/H Dec. Pr	Ç.C. L/H Dec. Pr	
	RED DL747	DL746	DL750	DL749	£2.42

NOTE: MAN4000 series pinouts are 14 pin all the same as MAN50,70 & 80 series.

VAT INCLUDED

Items marked with a • include 8% VAT
Items unmarked include VAT at 25%
ADVERT. No.1. of Series B

CALLERS WELCOME

ELECTROVALUE

Present

STABILIZED PRICE POLICY QUALITY COMPONENTS, KEEN PRICES AND DEPENDABLE SERVICE

112 page catalogue · attractive discounts · free postage & packing (U.K.)

A 100 OF THE BEST out of our latest catalogue

2N1307	47p	AF200U	40p	BD135	37p
2N2546	51p	A7239	60p	BD138	39p
2N3053	30p	B1906	35p	BDY20	83p
2N3054	60p	BA138	31p	BF194	15p
2N3055	70p	BB103	24p	BFR39	23p
2N3702	11p	BB104	48p	BFR79	23p
2N3703	10p	BB105	34p	BFX29	33p
2N3704	11p	BB107	18p	BFX84	27p
2N3705	19p	BC107B	12p	BFY51	23p
2N3794	18p	BC108B	15p	BRY39	50p
2N3819	28p	BC108C	15p	BY164	51p
2N4062	11p	BC109B	18p	C106B1	42p
2N4443	93p	BC109C	18p	C106D1	47p
2N8052	42p	BC147A	12p	C1406	78p
2N5163	20p	BC147B	13p	MJ481	£1.20
2N8459	35p	BC148B	12p	MJ491	£1.35
40361	48p	BC149C	14p	MJ2955	80p
40362	44p	BC158B	15p	MJE371	89p
40602	46p	BC159A	15p	MJES21	81p
40636	£1.36	BC187B	13p	MJE2955	£1.12
40669	£1.10	BC188B	12p	MJE3055	68p
AC128	17p	BC189B	12p	QA91	91p
AC151R	36p	BC189C	13p	SD4	8p
AC153	27p	BC179B	28p	TIP31A	70p
AC153K	37p	BC182L	12p	TIP32A	80p
AC176	24p	BC184L	11p	TIP41A	80p
AC176K	38p	BC212L	12p	TIP42A	£1.00
AC187K	31p	BC214L	14p	W02	30p
AC188K	29p	BC257A	14p	W02	30p
AD133	£1.92	BC259B	14p	ZTX300	14p
AD136	£1.11	BCY58	30p	ZTX304	23p
AD149	52p	BD130	70p	ZTX500	14p
AD181	42p	BD131	48p	ZTX504	45p
AD182	40p	BD132	52p		

all in the E.V. CATALOGUE 7 (issue 3)

112 pages of up-dated information and prices. More valuable than ever now that our price stabilizing has been introduced. Includes a 25p refund voucher for spending on orders for £5 or more list value. So before you even look at a screwdriver, make sure you have your E.V. Catalogue No. 7 issue 3 to hand. Price, post paid **30p**

PRICE STABILIZATION

Instead of changing prices from day to day with all the difficulties that brings, EV prices are held for 3 monthly periods and then reviewed to see if changes are necessary for the next 3 months following. So far, to date, we have made no changes since Jan 1st this year.

DISCOUNTS

apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more.

FREE POSTAGE & PACKING in U.K. for pre-paid mail orders over £2 (except Boxandall cabinets). If under, there is an additional handling charge of 10p.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to makers specifications. No rejects, seconds or sub-standard merchandise.

VAT

—add 25% to total value of order except for items marked * which carry only 8% VAT. Every effort is made to ensure correctness of information at time of preparing and putting this advertisement to press.

CAPACITORS

DALY ELECTROLYTIC In cans, plastic sleeved

1000mF/25V 34p	2200/100 £1.81
5000/100 £3.56	1000/50 50p
5000/25V 75p	2000/50 10p
2000/25 45p	5000/50 £1.44
1000/100 £1.00	

POLYESTER TYPE C.280. Radial leads for P.C.B. mounting. Working voltage 250V d.c.

0-01; 0-015; 0-022; 0-033; 0-047	ea. 3p
0-068; 0-1; 0-15	ea. 4p
0-22 5p; 0-33 7p; 0-47 8p; 0-68 11p; 1-0 14p; 1-5 21p; 2-2 24p	

SILVERED MICA. Working voltage 500V d.c. Tolerance 1% or 0.5pF

Values in PFs—2.2 to 250 in 26, stages	ea. 6p
270-820 in 9 stages, ea. 7p	
1000; 1500; 1800 9p; 2200 10p; 2700; 3600; 4700; 5000 16p;	
6800; 8200; 10,000 25p	

TANTALUM BEAD

0-1; 0-22; 0-47; 1-0 mF/35V, 1-5/20V	ea. 16p
2-2/16V, 2-2/35V, 4-7/16V, 10/6-3V	ea. 16p
4-7/35V, 10/16V, 22/8-3V	ea. 21p
10/25V, 22/16V, 47/8-3V, 100/3V, 6-8/25V, 15/25V	ea. 23p

POLYCARBONATE

Type B.32540 Values in µF:	
0-0047; 0-0068; 0-01; 0-015; 0-022	ea. 4p
0-018; 0-027; 0-033; 0-039; 0-047; 0-068; 0-1;	ea. 5p
0-056; 0-082; 0-12; 0-15	ea. 6p
0-18; 0-22 7p; 0-27; 0-33 9p; 0-39; 0-47 11p; 0-56; 0-68	16p

CERAMIC PLATE

Working voltage 50V. d.c. In 26 values from 22pF to 8800pF, ea. 2p

POTENTIOMETERS

ROTARY, CARBON TRACK.

Double wipers for good contact and long working life. P.20 SINGLE liner 100 ohms to 4.7 meg ohms, each 14p P.20 SINGLE log. 4.7 Kohms to 2.2 megohms, each 14p J.P.20 DUAL GANG lin. 4.7 Kohms to 2.2 megohms, each 48p J.P.20 DUAL GANG log. 4.7 Kohms to 2.2 megohms, each 48p J.P.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only, each 48p J.P.20 DUAL GANG antilog 10K only 48p 2A DP mains switch for any of above 14p extra. Decades of 10, 22 and 47 only available in ranges above. Skeleton Carbon Presets, Type PR, horizontal or vertical 8p each.

SLIDER

Linear or log mono 4-7K to 1 meg. in all popular values each 30p STEREO, matched tracks, lin. or log in all popular values from 4-7K to 1 meg. 80p Eucutcheon plates, mono, black or grey, each 10p Control knobs. blk/wht/red/yel/grn/blue/dk.grey/lt.grey, each 7p

MINITRON DIGITAL INDICATORS

3015F Seven segment filament compatible with standard logic modules. 0-9 and decimal point; 9mm characters in 16 lead DIL £1.20 Suitable BCD decoder driver 7447 £1.15 3015G showing + or - & 1 & dec. pt. £1.20

LEDS (Light Emitting Diodes)

Photo Cells, cadmium sulphide each 25p 40p

ANTEX Soldering Irons

C240	£2.25	Spare bits	32p
CN240	£2.85	Spare bits	42p

ELECTROLYTIC CAPACITORS

Axial Lead	3V	6-3V	10V	16V	25V	40V	63V	100V
0-47	—	—	—	—	—	11p	8p	8p
1-0	—	—	—	—	—	11p	8p	8p
2-2	—	—	—	—	11p	—	8p	8p
4-7	—	—	—	11p	—	—	8p	8p
10	—	11	—	—	—	—	8p	8p
22	—	—	8p	—	—	—	8p	8p
47	8p	—	8p	8p	—	—	8p	10p
100	9p	8p	8p	8p	8p	10p	12p	18p
220	8p	8p	8p	10p	10p	11p	17p	28p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	—	—	26p	37p	41p	—	—
4,700	—	—	—	39p	44p	58p	—	—
10,000	42p	46p	—	—	—	—	—	—

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	1/3	4-7-470K	1-3	1-4	0-9 nett
C	1/2	4-7-10M	1-3	1-1	0-9 nett
C	3/4	4-7-10M	1-5	1-2	0-97 nett
C	1	4-7-10M	3-2	2-5	1-92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-22-0-47 10	16	14	11 nett
WW	1	0-56-3-9 12	10	10	8 nett
WW	3	1-10K	9	8	8 nett
WW	7	1-10K	11	10	8 nett

Codes:

C—carbon film, high stability, low noise.
MO—metal oxide. Electrofil TR5 ultra low noise.
WW—wire wound, Pleesey.
Values: All E12 except C 1/2, C 3/4 and MO 1/2.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:

5% except WW 10% ±0.05Ω below 10Ω and 1/2 MO 25%
Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

WAVECHANGE SWITCHES

1 pole 12 way; 2 pole 8 way; 3 pole 4 way; 4 pole 3 way each 33p TAG STRIP 28 way 11p

NUTS, SCREWS, etc.

In lots of 100 each 4BA NUTS 34p; 6BA NUTS 28p 1/4" 4BA Screws 30p; 1/2" 6BA Screws 24p Threaded pillars 6BA, 1/2" hexagonal £1.40 Plain spacers 1/2" round £1.32 Other sizes available

ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily; Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA Telephone (061) 432 4945 Shop hours 9-5.30 daily; Sat. 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PW 7 S.A.E. with enquiries requiring answers.

A UHF WAVEMETER

R. LONGDEN

A WAVEMETER is an essential item of equipment required to check the order of multiplication obtained in the various tuned circuits of a transmitter. For example, consider a 144MHz transmitter using an 8MHz oscillator. The oscillator is usually followed by a stage tuned to the third harmonic, to obtain 24MHz. This is followed by a 3x harmonic amplifier, then a doubler, giving $24 \times 3 \times 2$, or 144MHz. Wrong tuning could give 2×4 or 4×2 in the early stages, providing 64MHz, doubled to 128MHz. Tuning the PA to this would cause out-of-band operation.


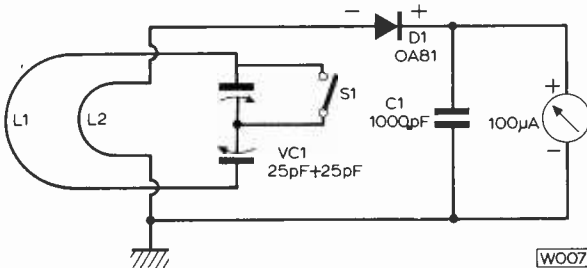


Fig. 1: Simple circuit of the two-range UHF wavemeter.

A calibrated wavemeter will ensure that the output is at 144MHz. It can also be used to check for possible harmonic output on 288MHz, 432MHz, or other related frequencies. A wavemeter is not intended to show the exact frequency, but to indicate that the correct harmonic or band is in use. If a large graph is prepared to show wavemeter dial readings and frequency, good accuracy is obtainable, but a much smaller graph is quite adequate for harmonic and similar checks.

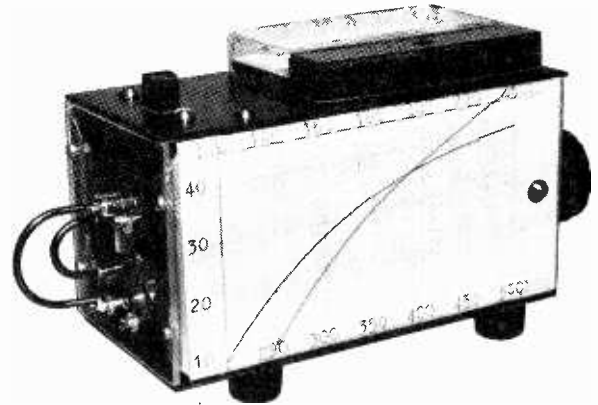For frequencies above about 300MHz, a very low minimum tuning capacitance is necessary and it becomes difficult to use ordinary plug-in coils,



fixed loop L1, but switch S1 allows two ranges to the holder and leads. The circuit in Fig. 1 has a because of the stray capacitance and inductance of be obtained.

For the higher range of approximately 220 to 500MHz, the two sections of the butterfly capacitor VC1 are in series, giving a maximum capacitance of about 12.5pF and a very low minimum. With S1 closed one section of 25pF is in use, and the range is approximately 120-240MHz. VC1 is operated by a small reduction drive. The diode is coupled by the loop L2 to avoid loading L1 and rectification by diode D1 provides current for the 100µA meter. Resonance is indicated by the maximum meter reading.

CONSTRUCTION

The layout is shown in Fig. 2. The sides of the case are 4x2in flanged universal chassis members. A further 4x2in member is cut into two. One part


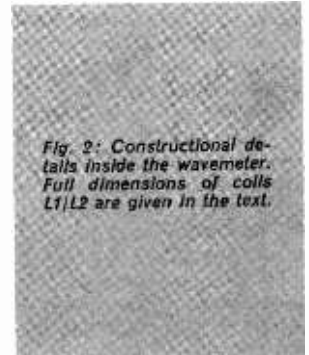
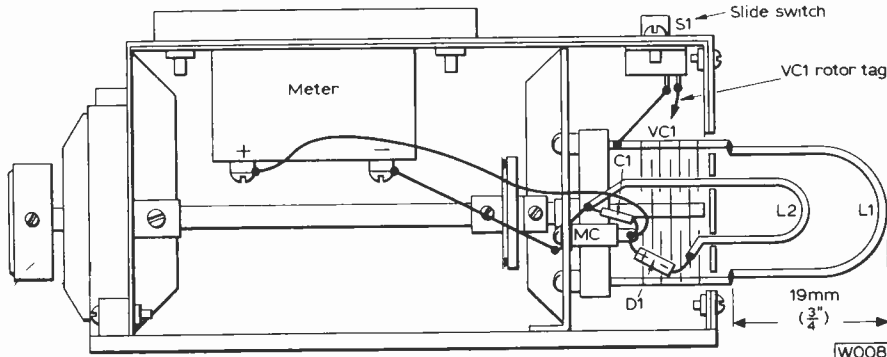


Fig. 2: Constructional details inside the wavemeter. Full dimensions of coils L1/L2 are given in the text.

of this provides the end, on which the ball drive is mounted. The other part is used to mount VC1. The end flanges of the sides are cut off at the ball drive end. The top of the box is paxolin, $4\frac{1}{16} \times 2$ in, and cut to take the meter and S1.

Assembly is most easily carried out by fitting together the top, one side, and parts to take VC1 and the drive. A length of $\frac{1}{4}$ in rod fits between the drive and insulated flexible coupling. The shaft of VC1 occupies a clearance hole, and VC1 is fixed by two short 6BA bolts into the "dead" bushes provided. As VC1 spindle is slightly smaller, a piece of tinplate is cut and bent round it to bring it up to about $\frac{1}{4}$ in diameter. Wiring can then be done as in Fig. 2, except for L1 and L2. C1, D1 and the meter lead are anchored at an insulated tag.

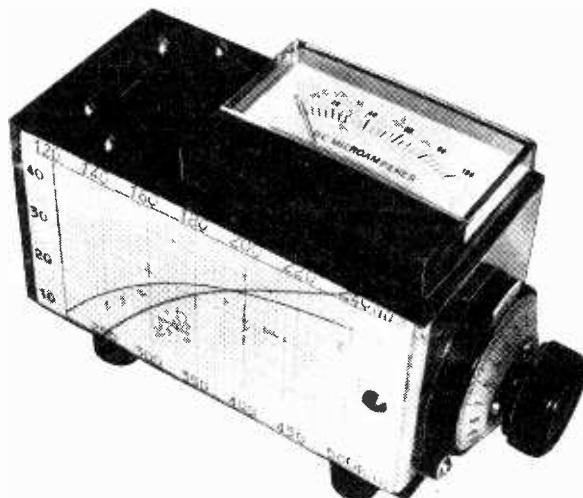

★ components list

C1 1000pF disc ceramic. D1 OA81.
 VC1 25 + 25pF butterfly type (Jackson C713).
 M1 Meter, 100μA. Universal coupling.
 Drive, (Eagle $\frac{1}{16}$ in. dia.) Rod $\frac{1}{16}$ in. dia.
 Universal chassis members 4 x 2 in. (3) (Home Radio).
 S1, miniature slide switch.

The case end was $\frac{1}{16}$ in thick Perspex, so that drilling positions can be seen. Clearance holes are drilled for the four studs of VC1. Two holes are also drilled for the ends of L2. About one-half the width is cut off the end flanges of the metal sides members, and these and the end are drilled for four 8BA bolts. L1 is 16swg or other stout wire and is 22mm ($\frac{7}{8}$ in) across and 19mm ($\frac{3}{4}$ in) long (Fig. 2). It is soldered to the projecting studs of VC1, near the position for L2. L2 is of similar wire, 13mm ($\frac{1}{2}$ in) across and projecting about 13mm ($\frac{1}{2}$ in), with ends long enough to reach the MC tag and D1. When L2 is soldered on, the case bottom can be fixed with self-tapping screws. The dial reads zero with VC1 closed.

USE OF WAVEMETER

The wavemeter loop or coil is positioned so that it can pick up RF energy from the oscillator, amplifier or other coil of the equipment, and the wavemeter is tuned to resonance, as shown by maximum meter indication. The frequency is then found from the wavemeter scale.

Best accuracy is secured when coupling is loose, so that only a small meter indication is obtained. So, as the wavemeter tuning position is found, it is moved away from the RF coil where energy is present. With very low power circuits, close coupling is needed to begin with, inductors or windings in line. Coupling is reduced by moving the wavemeter away, or turning it to place its coil at an angle. Where a few watts of RF may be present, a full-scale reading may be obtained at some inches spacing, so care is needed when first testing any circuit, to avoid possible damage to the meter.

Exactly similar methods are used to couple the wavemeter to a circuit for calibration purposes, except that in this case the frequency will be known already.

CALIBRATION

One or more of several methods can be used. As the final calibration is an important aspect, three methods are described. In each case it is wise to plot a graph showing dial readings against frequency, because this gives intermediate readings, and helps avoid any error as a displaced calibration point is suspect.

As the wavemeter is a passive device, it is always necessary to provide an oscillator or other source of RF energy, even if this is not itself the origin of calibration.

Lecher Line. This can be excited by an oscillator whose frequency is not known, and the frequency found by measurement with a ruler, to calibrate the wavemeter. With care it is usually considered that accuracy can be better than 1%. Fig. 3 shows essential features of the line. It can be made on a board about 130×25 mm (5×1 in) and 1.85m (6ft) long (actual dimensions are not important). X-X can be a strong tag-strip anchoring the wires about 25mm (1 in) to 40mm ($1\frac{1}{2}$ in) apart. An insulated loop about 13mm ($\frac{1}{2}$ in) in diameter with ends some 50mm (2 in) long is soldered on here. The wires can be 20SWG tinned-copper, 25mm (1 in) or more clear of the board. Points Y-Y can be long screws with nuts, so that the wires can be drawn taut. The wires must be parallel, but fixing details at X-X and Y-Y do not influence calibration.


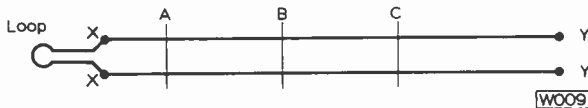


Fig. 3: Arrangement of Lecher line as a means of calibrating wavemeter.

Energy is coupled to the line by positioning the loop near the oscillator inductor. A metal straight-edge, at right-angles to the wires, is then slid along in contact with the wires, from X-X. At some point such as A, resonance causes the line to draw power. This is marked. The straight-edge is moved on, until this is repeated, as at B. The distance A to B is then measured. If measured in cm, $15,000/\text{cm} = \text{MHz}$. E.g., $30\text{cm} = 500\text{MHz}$, or $60\text{cm} = 250\text{MHz}$, and so on.

NEW EDU-KIT MAJOR

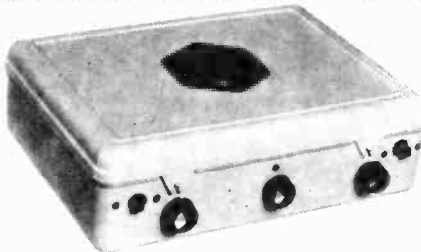

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ 5 Transistor Push Pull Amplifier.
- ★ Batteryless Crystal Radio.
- ★ Signal Tracer.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ One Transistor Radio.
- ★ Signal Injector.
- ★ 5 Transistor Short Wave Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ Transistor Tester NPN-PNP.
- ★ Electronic Metronome.
- ★ 3 Transistor Regenerative Radio.
- ★ 4 Transistor Push Pull Amplifier.
- ★ Electronic Noise Generator.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.

Total Building Costs

£7-23 P P & Ins. 55p.
(Overseas Seamail P & P £3-40)
(+ 8% VAT 57p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/2" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 55p free with parts.

ROAMER TEN Mk 2

WITH VHF INCLUD-
ING AIRCRAFT

Now with free earpiece and switched socket.

10 Transistors. Latest 4 watt Ferrite Magnet Loudspeaker.

9 Tunable Wavebands. MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band

Built in Ferrite Rod Aerial for MW/LW. Chrome plated 6 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p free with parts.

Total building costs
(Overseas Seamail P & P £3-50)

£9-50 P P & Ins. 65p
(+ 8% VAT 76p)

POCKET FIVE

NOW WITH 3" LOUD
SPEAKER

8 Tunable wavebands. M.W. LW. and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List free with parts.

Total Building Costs P P & Ins. 38p
£2-95 (+8% VAT 24p)
(Overseas Seamail P & P £2-30)

ROAMER EIGHT Mk 1

NOW WITH VARIABLE
TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

Total building costs
(Overseas Seamail P & P £3-50)

£6-98

P P & Ins. 65p
(+ 8% VAT 66p)

NEW JIFFY TESTER


Easy to build and operate, fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Also for checking short circuits of capacitors, tuning capacitors and many other uses not listed here. See instruction sheet free with kit. Complete with earpiece, jack plug and socket, resistors, capacitors, components, etc. Parts Price List and Easy Build Plans free with Parts.

Total Building Costs

£2-25

(+ 8% VAT 18p)
P P & Ins. 22p
(Overseas Seamail P & P £1-70)

NEW EVERY-DAY SERIES SIX

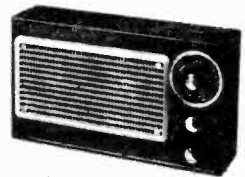

Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output. Parts Price List and Plans free with parts.

Total Building **£3-98** P P & Ins. 50p
(Overseas Seamail P & P £2-30)

(+ 8% VAT 32p)

TRANS EIGHT


8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves 3in. Speaker. Improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

Total building costs **£4-48** P P & Ins. 50p

(+ 8% VAT 36p)
(Overseas Seamail P & P £3-50)

"EDU-KIT"

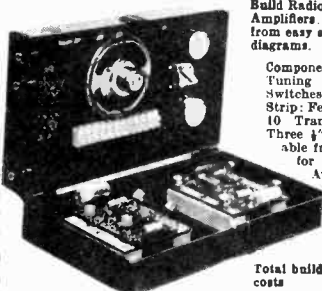

Build Radios, Amplifiers etc. from easy stage diagrams.

Five units including master unit to construct.

Components include:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

Total building costs **£5-50** P P & Ins. 50p
(Overseas Seamail P & P £3-40)
(+ 8% VAT 44p)

Prices are subject to alteration without notice.

★ Callers side entrance "Lavelle's" shop.

★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA

Tel.: 0234 52367. Reg. No. 788372.

I enclose £..... for

- ROAMER TEN
- EV6
- ROAMER EIGHT
- TRANS EIGHT
- JIFFY TESTER
- MAJOR EDU-KIT
- POCKET FIVE
- EDU-KIT

Parts

Name

Address

(Dept. PW6)

IMPROVE PETROL CONSUMPTION

Fit the Brilliant
New P.E. Scorpio Mk II
"Dual Polarity"
Capacitive Discharge
Electronic Ignition
System



- ★ Genuine improvement in overall petrol consumption (independent report claims at least 8%—10%)
 - ★ Much easier cold weather starting, less strain on your battery
 - ★ Less use of choke—increases engine life
 - ★ Smoother running at lower revs—makes your four cylinder car feel like a six cylinder
- Together with the following 'Scorpio Mk II' plus features not previously available with other makes:—
- ★ Only one model used for both positive (+) and negative (—) earth vehicles—if you change your car, you can certainly transfer your 'Scorpio'.
 - ★ Retains your original contact breaker points, which last their mechanical life—no points burn
 - ★ Will drive electronic tachometers.


Send a stamped addressed envelope for our free interesting brochure, "Electronic Ignition—How it Works", containing circuit and itemised price list. Price for complete kit of parts, with easy to follow, comprehensive instructions, connecting wire, etc. ONLY £18-95, including V.A.T. and postage and packing. Ready made unit, fully tested, for immediate installation with easy to follow instructions, all leads, etc., ONLY £13-85, including V.A.T. and postage and packing.

THOUSANDS ALREADY IN USE—FULLY GUARANTEED.

ELECTRO SPARES, 288 ECCLESALL ROAD, SHEFFIELD S11 8PE

Please allow 14 days minimum for delivery, for postal delays, cheque clearance, etc.

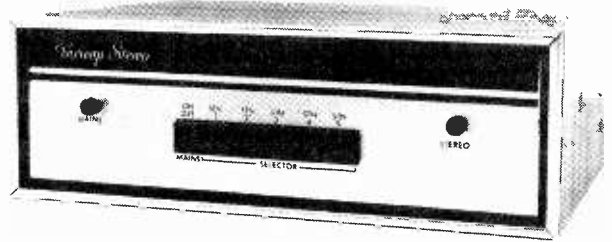P.E. 'VARICAP' STEREO PUSH BUTTON F.M. TUNER



The P.E. 'Varicap' Stereo Tuner uses the latest Mullard modules for R.F. and I.F. circuits—highly sensitive and pre-aligned for ease of construction. This superb kit has everything to enable you to construct this highly sensitive F.M. Stereo Tuner, with instant push button station selection, self contained regulated

power supply, stereo decoder, etc. etc. Easy to construct, highest quality reproduction. Price only £34-50 including V.A.T. and postage and packing. Please send stamped addressed envelope for our free brochure on the Varicap, which gives performance figures, detailed description, etc., etc.

P.E. 'GEMINI' STEREO AMPLIFIER

Output genuine 30W R.M.S. per channel! Distortion 0.01% (Maximum)! Frequency response —3dB, 20Hz to 100 kHz into 8 ohms! Fully comprehensive inputs, disc, tape, MIC etc.1. Yes, we are still supplying all components for this superb Stereo Amplifier, since we have not yet found a better one!

Fully comprehensive constructional booklet available, containing full specification, performance graphs, step-by-step, assembly instructions, photographs, fault finding guide, etc. etc. Price 55 pence plus 9 pence postage and packing.

For itemised price list only please forward stamped addressed envelope.

TOROIDAL TRANSFORMERS FOR THE TEXAN II

Designed by S.I.G.A. ELECTRONICS in conjunction with Texas Instruments for uprating Texan 20+20 Amplifiers. Pri. 220-240V; 50Hz; Screen; Sec. 25-20-0-20-25V, 1-5A. Fully impregnated; flying lead connections. Ref. T1295 Price £8-70 + 25% VAT post 50p.

Ref. T1295/F with resin filled centre, 2BA clear hole. Price £7-10 + 25% VAT post 50p.

Toroidal transformers suitable for Audio Power Supplies Pri. 240V 50Hz; Screen; fully impregnated; flying leads

REF	SECONDARIES	O.D. (cms)	HT.	Price	Post
315	(a) 33-0-33V 2A	12-0	× 4-4	£8-50	£0-69
	(b) 25-0-25V 0-1A				
291	(a) 33-0-33V 4A	13-0	× 5-7	£10-69	£0-78
	(b) 25-0-25V 0-2A				
271	24-0-24V 1A	8-6	× 4-1	£5-07	£0-50
061	20-0-20V 1A	8-5	× 4-0	£4-87	£0-50
285	25-0-25V 2A	10-8	× 5-1	£6-37	£0-60
284	0-45V 1A	9-5	× 4-4	£5-15	£0-60
000	0-45V 2A	12-0	× 4-4	£6-64	£0-69

Terms: Cash with order, please add 25% VAT to goods only. Quantity discounts available on request.

Dept. PW 01
S.I.G.A. (ELECTRONICS) LIMITED
Sunderland Road, Sandy, Beds
SG19 1QY

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB

WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

<input type="checkbox"/> Build-As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit)	<input type="checkbox"/> Electronic Engineering	<input type="checkbox"/> CITY AND GUILDS Installations and Wiring
<input type="checkbox"/> Electrical Engineering	<input type="checkbox"/> Computer Electronics	<input type="checkbox"/> CITY AND GUILDS Electrical Technicians
<input type="checkbox"/> Electrical Installations and wiring	<input type="checkbox"/> Computer Programming	<input type="checkbox"/> CITY AND GUILDS Telecommunications
<input type="checkbox"/> Electrical Draughtsmanship	<input type="checkbox"/> General Radio and TV Engineering	<input type="checkbox"/> Radio Amateurs' Exam etc. etc.
<input type="checkbox"/> Electrical Mathematics	<input type="checkbox"/> Radio Servicing, Maintenance and Repair	<input type="checkbox"/>
<input type="checkbox"/>	<input type="checkbox"/> Transistor Technology	<input type="checkbox"/>

To ALDERMASTON COLLEGE Dept. EPW-05, Reading RG7 4PF **EPW 05**

NAME (Block Capitals Please) _____

ADDRESS _____

POST CODE _____

Other subjects _____ Age _____

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

The measurement can be confirmed, as by moving from B to C.

With low power, resonance with the oscillator is most easily shown by including a meter to show anode or collector current. With the frequency determined, tune the wavemeter to it as described, and mark the graph. The oscillator frequency is then changed, and the procedure repeated for a new point.

Fig. 4 is an oscillator found suitable for up to 500MHz. L1 is three-quarters of a turn 8mm ($\frac{5}{16}$ in) in diameter soldered directly across TC2. TC1 is a miniature tubular pre-set and though this needs to be near minimum capacitance, oscillation was not obtained without it. The whole is assembled in any convenient form, but with very short leads for RF circuits.


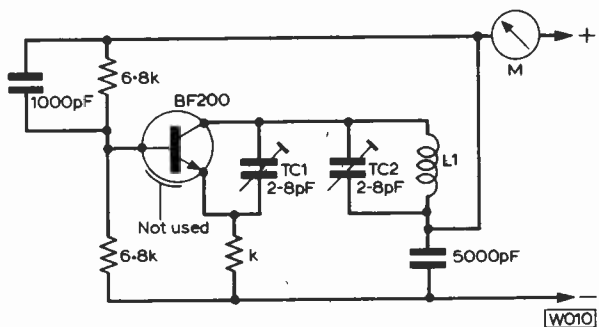


Fig. 4: Circuit of low power oscillator, used as a source of energy at UHF.

Best indication was obtained using a 1mA meter, with the supply voltage reduced for nearly a full-scale reading. Shorting or holding TC2 should cause a drop in current. If not, the circuit is not oscillating.

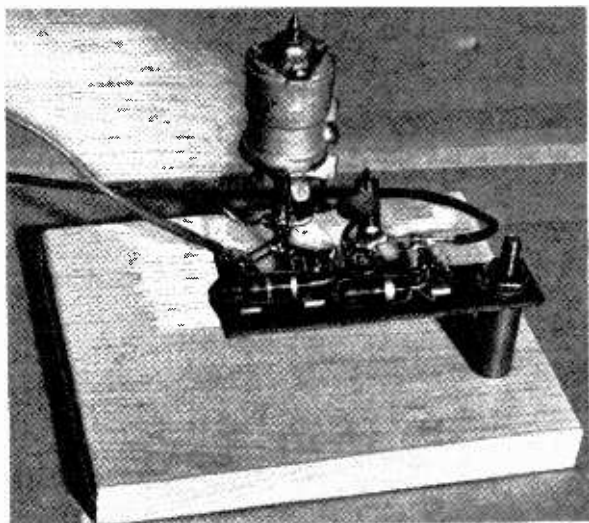The line loop is coupled to L1 so that a dip can be seen on the meter for two positions of the shorting bar. The line is then removed, and the wavemeter is loosely coupled and tuned to produce the same dip, and its chart marked with the frequency determined by the line.



Layout of Fig. 4 on a simple tag strip. A 9V supply should be adequate.

Use of GDO. If a calibrated grid dip oscillator can be used, the wavemeter can be easily calibrated within the range available on the GDO. Keep GDO and wavemeter separated so that only a small wavemeter reading is obtained on resonance.

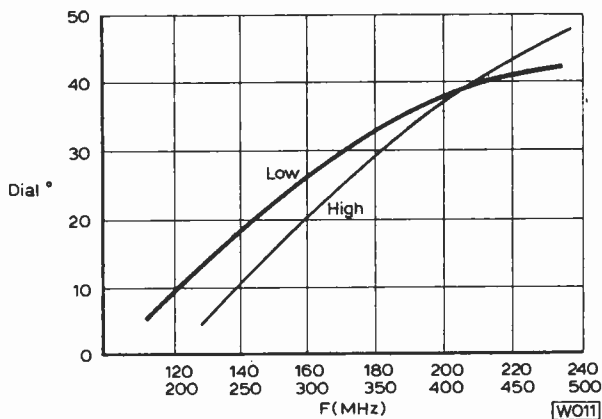


Fig. 5: Typical calibration curves for the two ranges on the wavemeter

Transmitter Harmonics. A 2m transmitter will provide a 144MHz calibration mark. With some circuits, second and other harmonics of this or other frequencies may be found. With a transmitter such as the 10 watt one for 2m (PW, October 1973) where RF is generated at 72MHz and followed by three circuits tuned to 144MHz, it may prove impossible to find any harmonic or spurious frequencies, in normal operation, with the wavemeter. Some calibration marks can be obtained by temporarily changing the doubler anode coil for operation on a higher harmonic. HT is reduced so that doubler current cannot exceed some 30-40mA at 200V or so. The PA is removed or similarly kept within its anode dissipation rating, and can be operated as a doubler for this purpose.

Fig. 5 is a guide on what to expect when calibrating the circuit in Fig. 1. A larger graph on graph paper is recommended. Calibration was done using a tunable oscillator, Lecher line, and harmonics.

Television

from **JULY** issue onwards

bigger pages—more pages

more of your favourite subjects

Look for it—in June

See page 256 for details.



AMATEUR BANDS

by Eric Dowdeswell G4AR

AS this copy is being bashed out there will be many hundreds of likely candidates around the country doing their utmost to put on to paper their answers to a few technical questions which, they hope, will result in a 'pass' slip for the Radio Amateurs Examination coming through the post in a couple of months' time. One of the best articles I have ever seen on the subject appeared in Radio Communication for April, entitled "Taking the Radio Amateurs' Examination", by R. G. Marden G3MWF.

Strangely enough, it wasn't technical but it did show how to approach the examination on strictly commonsense lines thus giving a candidate an edge over those who arrive at the examination centre hot and bothered, without pens or pencils and without the faintest idea of how they are going to tackle the questions. I have invigilated at many of these exams and I can tell you it has broken my heart to see the way that some candidates have gone about their task. I would say that the vast majority had sufficient knowledge to pass but many made a complete hash of the written work, entirely through lack of preparation.

Frankly, the amount of technical knowledge required is pretty small and the papers are so similar every time that it doesn't take a genius to assess just what is wanted and to concentrate on learning the essentials. Like any other examination, find out what the questioner wants to know and give it to him, without any frills. And the most important piece of advice, as underlined by Mr. Marden: regardless of having finished the paper or not spend at least ten minutes at the end reading your answers and making corrections, and there will be some, I assure you, and these could make all the difference between a pass and a fail.

Obviously many of you enjoyed copying lots of nice new prefixes in the CQ WPX Contest, some of which were pretty easy to fix but others like XX for CR(6) were not so obvious. Steve Blake (Aylesbury) logged some, such as CV0Z, CQ7AZ and PW4. Steve is improving his 2m rig by changing his ground-plane for two five-element quads at around 40ft. Mark Corrigan (New Zealand) sent a brief first log but the only ones of possible interest were G8PO and G3WMZ on 80m SSB. Mark has a Heathkit SW717 and ATU with 100ft wire and dipole for

20m. Paul Heath of Wolverhampton did well with his 1155 set to get VQ9M on 80m SSB and the address for QSL's is Box 191 Mahé, Seychelles. Paul also mentioned OA4S/P/4X of the UN contingent on the Golan Heights, which must be a DX'ers dream QTH judging by the TV coverage we have seen of those parts! Mike Green (Northwich, Cheshire) has not been very active but managed to spend some time in the WPX contest when he captured PJ9UA, VP5B, 3B6DW, among many others on 15m which confirms my long-held theory that it's lack of activity rather than bad conditions that turns people against this band and 10m.

Ian Moore (Leeds) turned in a very brief log for 20m that included YN1WB, a prefix not heard all that often. Paul Barker (Sunderland) reports little doing on the SSTV frequencies apart from usual Italians and a few other Europeans. He notes 5L9A, yet another recent prefix, in place of the perfectly respectable EL series! Excuse this time, 10th anniversary of the President!

Stephen Budd A8713 (Worthing) was kind enough to send me a copy of the Geoff Watts DX News Sheet which is the place to get all the gen on these new calls as they come up. The cost is modest and it is posted out every Tuesday. Can't be more up to date than that! Details from Geoff at 62 Belmont Road, Norwich NR7 0PU. On his FRDX400 Stephen has found Asia open from 14 to 1600 and the Pacific from 07 to 0800. Tim Charles (Colchester) thought chess players might be interested in the net on 3798kHz around 1700 every evening. He says G3ZYY claims to have worked ZL3RB on Top Band again, 449 both ways. Tim is one of our few stalwarts who actually enjoys listening to the CW ends of the bands. More should try it as it can be very rewarding.

M. J. Connolly A8796 (Yeovil) stuck to 20m SSB trying out an ATU he has now completed. Paul Heath, again, had to think quick when he lost a vital guy wire from his mast but saved the day by using one if his dipoles in lieu! John Porter (Baslow, Derbys) used his FR50B and two multiband dipoles to drag in stations on 80, 20 and 15m and was pleased to copy VE8RCS of the Polar Amateur Radio Club in the North West Territories, this at 1040 in the morning!

Log extracts

S. Blake:—20m CV0Z VP5B ZY5YZ 15m CQ6LF FH8CY PW4KL ZZ8JO.


M. Green:—80m YB0ABV 40m CR4BC HC2BV HZ1AB 9Y4VU 20m FK8CA PJ9EE YS1JWD ZF1MA 3C1AGD (Expedition to Equat. Guinea by SM0ATD) 15m CW3BH PW4FL 3B6DW.

MAPLIN

ELECTRONIC SUPPLIES

NEW SHOP NOW OPEN, details below

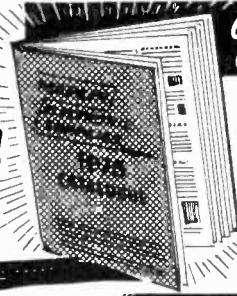SUPERSONIC SAME-DAY-SERVICE-MEANS QUALITY COMPONENTS-FAST!



Get your 1975 CATALOGUE!

132 Big Pages

Includes dozens of useful & interesting circuits you can build; data; hundreds of pictures, transistor equivalents list and hundreds of new lines. Packed with information. Only 40p.

RESISTORS

CARBON FILM

1/2W 1Ω to 1M: 5%, 1M2 to 10M: 10% E12
1/2W 1Ω to 10Ω: 5%, 1M2 to 10M: 10%
E12 11Ω to 910k: 5% E12 & E24 1.6p each

METAL OXIDE

1/2W 10Ω to 1M: 2% E12 & E24 5p each

WIREWOUND

3W 0.22Ω, 0.27Ω, 0.33Ω, 0.47Ω;
10%, 1Ω: 5% 18p each
1-2Ω to 270Ω: 5% E12 14p each
Other ranges stocked. See our catalogue for details.

E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades.
E24: 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades.

POTENTIOMETERS

Rotary miniature carbon track 1/2" spindle
Values available: 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M.

Log. Single-gang 17p
Lin. Single-gang (+ 1k) 17p
Log. Lin. Single-gang with switch 38p
Log. or Lin. Dual-gang without switch 54p

Slider 60mm track. Metal-cased: overall length 86-155mm (knob extra 7p)
Values available: 1k; 5k; 10k; 25k; 50k; 100k; 250k; 500k;

Lin. Single Gang 38p
Log Single Gang 42p
Lin or Log Dual Gang 49p

Presets: 0-1W Vertical or Horizontal.
100Ω, 220Ω, 470Ω, 1K, 2k2, 4k7, 10k, 22k, 47k, 100k, 220k, 470k, 1M 7p each

CAPACITORS

Sub-miniature Axial lead electrolytic

Mid V Price Mid V Price
1 63 6p 63 6p
1.5 63 6p 63 6p
2-2 63 6p 63 6p
3-3 63 6p 100 4 6p

47 63 6p 100 10 6p 470 6.3 8p
68 40 6p 100 25 8p 470 10 18p
68 63 6p 100 40 8p 470 25 20p
10 25 6p 100 63 20p 470 40 32p
10 63 6p 150 6.3 6p 680 6.3 18p
15 16 6p 150 16 6p 680 16 20p
15 40 6p 150 25 8p 680 25 32p
15 63 6p 150 40 18p 680 40 35p
22 10 6p 150 63 20p 1000 4 18p
22 25 6p 220 4 6p 1000 10 20p
22 63 6p 220 10 6p 1000 16 32p
33 6.3 6p 220 16 8p 1000 25 35p
33 16 6p 220 25 18p 1500 6.3 20p
33 40 6p 220 40 20p 1500 10 32p
47 4 6p 220 63 32p 1500 16 35p
47 10 6p 330 4 6p 2200 6.3 32p
47 25 6p 330 10 8p 2200 10 35p
47 0 6p 330 16 18p 3300 6.3 35p
47 63 8p 330 63 35p 4700 4 35p

MAINS CONNECTORS

P360 3-pin 1.5A Chassis Plug with Line Socket 38p
SA2190 3-pin 5A Chassis Plug 29p
SA 11862 Line Socket for SA2190 32p
P437 3-pin 5A Chassis Socket with Line Plug 77p

TRANSISTORS & DIODES

AC127 18p BY126 13p
AC128 18p HY127 13p
AC176 17p HY164 40p
AD161/162 MP HZY88 series 99p

BA100 9p MPF102 38p
BA145 22p GA91 8p
BC107 10p OA200 7p
BA108 10p OC71 20p
BC109 13p SC146D 88p
BC109C 13p T1843 28p
BC142 23p VF005 38p
BC143 25p VF04 38p
BC147 10p 1N914 4p
BC148 10p 1N4001 6p
BC149 12p 1N4002 61p
BC168C 12p 1N4003 7p
BC169C 12p 1N4004 71p
BC175 17p 1N4005 8p
BC182L 12p 1N4006 81p
BC183L 12p 1N4007 8p
BC184L 12p 1N4148 4p
BC212L 14p 2N1302 20p
BC213L 15p 2N1303 20p
BC214L 15p 2N1304 30p
BCY71 22p 2N1711 24p
BD131 45p 2N2919 31p
BD132 54p 2N2646 45p
BD131/BD132 2N2905 33p
MP 1.20 2N2926or 12p

BD135 36p Ye 12p
BD138 46p G1 18p
BD140 68p 2N3053 28p
BF258 35p 2N3055 48p
BF259 25p 2N3819 28p
BFX29 30p 2N5459 51p
BFX30 33p 7400 16p
BFX84 30p 7413 30p
BFX85 30p 7447 11p
BFX87 30p 7473 54p
BFX88 25p 7474 45p
BFY50 20p 7490 98p
BFY61 22p 7493 98p
BFY62 20p 74921 30p

L.E.D. RED
2med 1/2" only 15p
Panel mtg. clip 6p
(Other colours and 7-seg. displays in our catalogue)

INTEGRATED CIRCUITS

CA3046 (14-pin DIL) 68p
LM139 (TO9) 24.25p
MC1310P (14-pin DIL) 42.50p
MC1496 (UA796) (14-pin DIL) 78p
MFC4000B 59p
MFC6040 85p
NE565V (8-pin DIL) 66p
SC1455 (14-pin DIL) 22.70p
SG3402 (14-pin DIL) 11.68p
TBA8108 11.00p
μA741C (8-pin DIL) 36p
μA741C (14-pin DIL) 45p
μA747C (14-pin DIL) 11.05p
μA748C (8-pin DIL) 39p
ZNA4 (TO18) 11.20p

VOLTAGE REGULATORS

μA7805 5V 1.5A (TO9) 11.75p
μA7815 15V 1.5A (TO3) 11.75p
MYR 5V, 12V, 15V, 500mA (TO3) 11.60p
μA78M05 5V 500mA (Plastic power) 11.05p
μA78M15 15 500mA (Plastic power) 11.05p
μA78L05 5V 100mA (TO92) 80p
μA78L15 15V 100mA (TO92) 80p
μA723C Variable 2 to 37V (TO99 or 14-pin DIL) 75p
Our catalogue contains application circuits and data for all the above I.C.s and many more

PRICES

Please note that some prices shown may have changed on June 1st 1975. For latest prices send s.a.c. for our June/July price list/newsletter.

SWITCHES

Rotary adjustable top 1 pole, 2 to 12 way; 2 pole, 2 to 6 way; 3 pole, 2 to 4 way; 4 pole, 2 or 3 way 46p each
Slide Sub-min DPDT 10p
Slide Min. DPDT 14p
Push to make Non-locking 8pST
Push-on, Push-off Locking DPDT 250V 4A 26p
Rocker White DPST 250V 10A 42p
Rotary Mains DPST 250V 2A 26p
Toggle with ON/OFF plate DPDT 250V 1.5A 26p

BLD OUTPUT SLIDE SWITCH
Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue. 13.38

PLUGS & SOCKETS

DIN	PLUG	CHASSIS SOCKET
2-pin	8p	7p
3-pin	9p	8p
4-pin	10p	8p
5-pin A (180°)	12p	8p
5-pin B (240°)	12p	8p
6-pin	12p	8p

JACK PLUGS
1/2 in. Std. Mono Plastic Barrel 13p
1/2 in. Std. Mono Metal Barrel 24p
1/2 in. Std. Stereo Plastic Barrel 18p
1/2 in. Std. Stereo Metal Barrel 33p
2.5mm Plastic Barrel 10p
2.5mm Metal Barrel 15p
3.5mm Plastic Barrel 10p
3.5mm Metal Barrel 15p

JACK CHASSIS SOCKETS
2.5mm Open-type metal 9p
3.5mm Open-type metal 9p
1/2 Std. Mono Open-type metal 14p
1/2 Std. Mono Moulded with 2 break contacts 14p
1/2 Std. Stereo Open-type metal 18p
1/2 Std. Stereo Moulded with 3 break contacts 18p

PHONO
Plastic-topped Plug 7p
Screened Plug 12p
Chassis Socket Single 8p
Chassis Socket Twin 8p

TRANSFORMERS

LT700 min. output. Pri. 1k2; Sec. 5Ω 200mW 56p
Sub-min mains 6.0-6V 100mA 11.03p
12.0-12V 50mA 11.03p
(Size both approx. 30 x 27 x 25mm)
Min. mains
0-6V 500mA, 0-6V 500mA 21.88p
0-12V 250mA, 0-12V 250mA 11.88p
0-20V 150mA, 0-20V 150mA 11.88p
0-24V 125mA, 0-24V 125mA 11.88p
Mains MT3AT: Sec: 12-16-20-24-30V 2A 24.23p
Mains MT208AT: Sec: 0-15-20V 1A, 0-15-20V 1A 23.98p

ORGAN CONSTRUCTION

A Full Scale Electronic Organ that you can Build to Your Own Specification.

FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS

Leaflet MES 51: Price 15p. describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument.
Leaflet MES 52: Price 15p continues the description of the MES 50 keyboard organ and shows you how to add a second keyboard with lots more stops.
Leaflet MES53 "Stage 1 Full-Range Organ" includes a novel solid-state switching system, six new footages and a pedal-board: price 15p



THE AMAZING DMO2

A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4k to 8k (highest) or 2k to 4k or 1k to 2k, etc. right down to 16Hz to 32Hz! And this new compatible design is even smaller!—only 3.5in x 3.7in including gold-plated edge connexion.

DMO2 includes built in variable depth and rate frequency shift tremulant.
DMO2 £12.25 DMO2T £14.25

SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1.80 each or 6 for £9.94 or 12 for £18.18.

Keyboard high quality, fully sprung.
Flat-front 48-note F to E £15.95
Sloping-front 49-note C to C £15.95
Sloping-front 61-note C to C £20.44
*Swing pedal with 10k log. pot £8.33
*Spring Line Unit (Short) £3.05
*Spring Line Unit (Long) £8.29
*Reverberation Driver Module £5.34

* S.A.E. please for full details: leaflet MES 24. Gold-clad phosphor-bronze wire 30p per yd. Palladium earth bar 15p per octave length. Contact Blocks 2-make (GB2) 22p
Stop Tabs rocker type not engraved (white, red, grey or black) with DPDT switch 58p

"ELECTRONICS TODAY INTERNATIONAL"
4600 SYNTHESISER
We stock all parts for this brilliantly designed synthesiser. This includes all the P.C.B.s, metal-work and drilled and printed front panel giving a truly professional finish. Authoritative opinions agree the E.T.I. International Synthesiser is technically superior to most of today's models. Complete constructional details in our booklet, available shortly, price £1.50. S.A.E. please for price list and specification.



P.O. BOX 3, RAYLEIGH, ESSEX. Tel.: Southend-on-Sea (0702)44101
SHOP NOW OPEN: 284 LONDON ROAD, WESTCLIFF-ON-SEA, ESSEX
VAT Please add 25% to the final total. Post and packing included in U.K.
(15p handling charge on orders under £1).
First-class post pre-paid envelope supplied free with every order.



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£8-00
Baker Group 35 3, 8 or 15 ohm	£9-50
Baker Group 50/12 8 or 15 ohm	£13-00
Baker Deluxe 12" d/cone	£11-00
Baker Major	£9-50
Baker Regent	£2-00
Baker Superb	£14-50
Baker Auditorium 12	£13-00
Celestion GH2H 8 or 15 ohm	£10-20
Celestion PS8 for Unilux	£3-00
Celestion G12M 8 or 15 ohm	£11-15
Celestion G12H 8 or 15 ohm	£13-90
Celestion G15C 8 or 15 ohm	£22-25
Celestion G18C 8 or 15 ohm	£30-55
EMI 13 x 8" 3, 8 or 15 ohm	£2-10
EMI 13 x 8" 150 d/c 3, 8 or 15 ohm	£2-35
EMI 13 x 8" type 350 8 or 15 ohm	£7-65
EMI 13 x 8" 20 watt base	£2-15
EMI 6 1/2" 93850 4 or 8 ohm	£2-32
EMI 5" 14A/7030 mid range 8 ohm	£2-80
EMI 2 1/2" tweeter 97492AT	£2
Eagle DT33 30 watt tweeter	£5-05
Eagle HT15 horn tweeter	£3-52
Eagle CT5 cone tweeter	£1-65
Eagle CT10 tweeter 8 or 16 ohm	£2-40
Eagle MHT10 horn tweeter	£3-55
Eagle crossover CN23, CN28, CN216	£1-40
Eagle FR4	£4-90
Eagle FR65	£7-70
Eagle FR8	£9-85
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2-75
Elac 6 1/2" 6RM171 d/c roll surr.	£3-25
Elac 6 1/2" 6RM220 d/cone	£2-50
Elac 4" tweeter TW4	£1-40
Elac 10" d/cone 10RM239 8 ohm	£2-50
Elac 8" 8CS175 3 ohm	£2-50
Fane Pop 15 watt 12"	£4-85
Fane Pop 25T 30 watt 12"	£6-95
Fane Pop 50 watt 12"	£11-15
Fane Pop 55 60 watt 12"	£12-00
Fane Pop 60 watt 15"	£12-75
Fane Pop 100 watt 18"	£24-00
Fane Crescendo 12A 100 watt 12"	£31-95
Fane Crescendo 12B bass	£33-80
Fane Crescendo 100 watt 15"	£43-98
Fane Crescendo 150 watt 18"	£58-33
Fane 801T 8" d/c roll surr.	£5-50
Fane 807T 8" d/c roll surr.	£3-70
Fane 808T 8" d/c	£2-75
Fane 701 twin ribbon horn	£32-40
Fane 910 horn	£13-85
Fane 920 horn	£31-45
Goodmans 8P 8" or 15 ohm	£5-10
Goodmans 10P 8 or 15 ohm	£5-40
Goodmans 12P 8 or 15 ohm	£12-95

Goodmans 12P-D 8 or 15 ohm	£15-75
Goodmans 12P-G 8 or 15 ohm	£14-75
Goodmans Audiomax 12AX 100 watt	£33-75
Goodmans Audiomax 15AX	£37-25
Goodmans 15P 8 or 15 ohm	£19-50
Goodmans 18P 8 or 15 ohm	£33-50
Goodmans Hifax 750	£14-95
Goodmans Axent 100 tweeter	£6-75
Goodmans Audiom 100 12"	£11-12
Goodmans Axiom 401 12"	£16-00
Goodmans Twinaxiom 8	£8-11
Goodmans Twinaxiom 10	£8-60
Kef T27	£4-85
Kef T15	£5-55
Kef B110	£6-70
Kef B200	£7-60
Kef B139	£13-20
Kef DN8	£1-85
Kef DN12	£4-60
Kef DN13	£3-10
STC4001G super tweeter	£5-25
Richard Allan CG8T 8" d/c r/surr.	£5-90
2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm	£2
2 1/2" 75 ohm	£47
7" x 4" 3 or 8 ohm	£1-30
8" x 5" 3 or 8 ohm	£1-40
10" x 6" 3, 8 or 15 ohm	£2-15

SPEAKER KITS

Baker Major Module	each £10-75
Goodmans Mezzo Twinkit	pair £37-75
Goodmans DIN 20	each £10-75
Helme XLK 25	pair £20-35
Helme XLK 30	pair £13-75
Helme XLK 50	pair £37-00
Keffit 1	pair £38-75
Keffit 3	each £34-00
Richard Allan Twinkit	each £8-30
Richard Allan Triple 8	each £12-75
Richard Allan Triple 12	each £18-50
Richard Allan Super Triple	each £22-00
Wharfedale Linton 2 kit	pair £18-30
Wharfedale Glendale 3 kit	pair £32-50
Wharfedale Dovedale 3 kit	pair £50-50

PA/DISCO AMPLIFIERS

(carr. and ins. £1)	
Baker Major 100 watt	£46-00
Linear 30/40	£28-00
Linear 40/50	£32-50
Linear 80/100	£54-50
Linear 100 watt slave	£40-75
Eagle PA range in stock—ask for catalogue.	

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, 12" and up 50p each. Speaker kits 75p each (£1.50 pair) tweeters and crossovers 25p.

PLUS V.A.T. AT 25%.

WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF
Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow
Send stamp for free booklet "Choosing a Speaker"



Agfa Cassettes

The best buy!

Agfa Low Noise Cassettes
AT LESS THAN
HALF PRICE!

AGFA HIGHDYNAMIC SUPER

AGFA STEREO-CHROM CHROMIUM DIOXIDE

C60	1	5	10
C90	40p	£2-00	£3-98
C120	54p	£2-70	£5-38
	75p	£3-70	£7-38
C60+8	1	5	10
C90+8	54p	£2-70	£5-35
C120	70p	£3-50	£6-75
	99p	£4-95	£9-85
C60	1	5	10
C90	90p	£4-50	£8-75
	£1-10	£5-50	£10-90

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO

(DEPT. PW)
10 SWAN STREET, WILMSLOW,
CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back up service to ensure your success. VHF and UHF Modulator kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes and focus/scan coil assemblies. Ready built cameras also available. Complete kits available for P.W. tele-tennis game. Send 5" x 7" S.A.E. for full details, or come along for a demonstration and a chat with our technical staff.

CROFTON ELECTRONICS

124 Colne Road, Twickenham, Middlesex, TW2 6QS

Tele: 01-898 1569

Telex 934642

Cadanac LDN



Greenbank Electronics

FREE!

Data and circuit diagram for Digital Clock Chip AY-5-1224, Digital Alarm Clock Chip MK 50253, also data sheet for Economy DL-747, DL-750 LED displays.

(A stamped addressed envelope with enquiries would be a great help to us, but is not essential).

CLOCK CHIPS

AY-5-1224, 4 digit, 12/24 hr., 50/60 Hz, TTL compatible, zero reset, easy display interface, 16 pin package £3-66
MK 50253, 4/6 digit alarm clock chip, 50 Hz, 12/24 hr., AM/PM and activity indication, 'snooze' feature, intensity control, simple time setting, 28 pin package. £5-50

L.E.D. DISPLAYS

DL-747 15mm (0-6") high, common anode £2-04
DL-750 15mm (0-6") high, common cathode £2-25

Add VAT at the appropriate rate to all prices, post, etc. 10p + VAT per order

GREENBANK ELECTRONICS
(Dept. W7P),
94 New Chester Road, New Ferry,
Wirral, Merseyside L62 5AG
Tel. 051-645 3391



I. Moore:—20m C6ABN FG7AN HV3SJ YN1WB VP8NP.

P. Barker:—80m OE2SCL/YK 20m M1BS 3B8DR 5L9A 8Q6AC.

S. Budd:—80m C31LO (Box 10 Andorra) EA9EL FC2CD JY3ZH 20m DU1DCC VS9MB 9V1QM VP5SL PJ3DO YB0AAG ZF1MA KH6OT 5T5ZR (Box 202 Nouakchott) 3D2AJ (Box 1220 Suva) UA9VH/JT1 (Box 639 Ulan Bator) 15m VQ9HCS 9J2WR.

T. Charles:—160m VO1KE 80m A2CJP A4ANG FL8MF HC2TV HR1AT KG4DS KZ5ZK YN1AZ 40m CO2AM FK8AC VK7GK 20m JT1KAA KX6LP PZ9AA TR8WR YS1MAE 4W1FZ 6O2AP 8P6BU 15m CO2FT CX8DI FH8CY HC2AF PJ9EE VP7RU 5N2GV 5V4DV ZD7BS 2m DK6AB F1BUC from Oscar 7 on 70cm. OK30MDB SP9EGM UR2EQ all via Oscar 7.

M. Connolly:—20m A6XR HR3JJR OA42/P/4X VP2AA YS1GMV 3D6AW 6Y5DA 9M2CX.

P. Heath:—80m EA6CE KZ5BC PJ3HM VQ9M ZL4KF 20m VE8DC VP5B OA4S/P/4X.

J. Porter:—80m FC2CD HZ1AB ZB2A 20m PZ3EVK VE8RCS 8P6CC 15m LU9CV ZD7FT ZP5NP.

All stations are SSB except those in bold which are CW.

BROADCAST BANDS

SHORT WAVE BROADCASTS

by Derek Bell

I HOPPED over to the other side of the fence recently and went to the North Midlands mobile radio rally at Drayton Manor Park. There I chanced upon three youngsters bent on forming a DX club in the Birmingham area. So in response to their plea for help I would ask anyone interested to write to **Tony Fenton**, 124 Wolverhampton Road, Oldbury, Warley, West Midlands B68 0LW and help them get it off the ground.

Another cry for help comes from **Dave Evered** of Cardiff, he is another of these lucky people who has managed to pick up a communications receiver for a few pence. He would like anyone who can supply any literature or gen on an Eddystone S640 to write to him at 13 Daviot Street, Roath, Cardiff. Dave also wants to know the best frequency for the BBC World Service here in the UK. This is on the Medium Waves in Charles Molloy land, on 1088kHz, radiated from Crowborough. SINPO, by the way Dave, stands for Strength, Interference, Noise, Propagation and Overall Readability. These are ways of measuring a radio signal and are scaled from 0 to 5, with 5 as strongest, 0 weakest, and most stations like to have SINPO ratings on QSL requests.

Tony Rowland from Glorious Devon writes with a beef, and that is because he has waited since Novem-

ber for his 1975 World Radio and TV Handbook. Tony, I am afraid that I had to wait almost as long, and in the end the book came by post from Denmark. Can anyone help Tony identify "Radio Carlos" heard on 5050 at 2245, the programme content was news, documentary items and music, so let us know folks if any of you can pinpoint this station. An answer now to a recent "crie de coeur" comes from **Lawrence Bennett** of Bristol. He provides the info that the station RTV Dominicana has an outlet on 9505 and that Radio Messiah comes from Radio Luxembourg transmitters on 6090. Lawrence sends quite a list of Latin American "goodies," heard on an Astrad 17, among them the following:

11700 Radio Clarin Dominica at 2255

11925 Radio Bandierentes at 2200

11805 Radio Globo Brazil at 2230

15135 Radio Record Brazil at 2135.

Andrew Cope of Southport also fills us in on RTV Dominicana and he says it is a 50 kilowatt using the callsign HISD and is best heard around 0215 to 0230. Andrew recommends very highly his ex-army A510 this being fed by an ATU. It also has a unique earthing system in that Andrew has installed in the ground three large dog meat tins and from these a spider's web of 18SWG copper wire, this is all connected to the set by another length of copper wire!

More unusual happenings are reported by **Robert Hill** of Crewe. These come from the sunny Algarve in Portugal where Robert has been on holiday. It seems that while listening to the Portuguese domestic radio which, Robert says, is controlled by the military, the transmitter signed off with, of all things, the march "A life on the ocean wave"! Has any one else a funny story to tell us? From Kettering, QTH of **Peter Bowyer** comes the question "how can I fit a bandspread capacitor." Well, Peter, I cannot of course speak on your Murphy A168 simply because I do not know the set but the basic theory is that you fix a variable capacitor to the chassis in such a position that the capacitor spindle protrudes through the set "box," then connect it to the chassis of the existing tuner and to the fixed vanes of the oscillator tuning capacitor. Vague, I know, but there it is, there is never a way of doing anything that is common to every set except perhaps fitting a valve or making a soldered joint.

Jonathon Marks of Norwich has an item for all those fans of Radio Canada. He writes to say that RCI have changed their QSL policy and now cease to put date time and frequency details on the card, and, as Jonathon says, have made it like the BBC acknowledgement card. I am sure we wish a "get well soon" to our old mate **James Walker** of Milton Keynes. He has been in hospital for a month and has taken the trouble to drop a few lines to the column. James passes on the tip that Radio Bucharest has in its DX show on Thursdays at 1300 on 15250, 11940 and 9690 a short item for radio amateurs. **Robert Gibson** of Wadhurst asks if it is worth while fitting a preselector. This gadget is an RF amplifier, tunable over the SW bands, and has the job of boosting the signal that comes from the aerial and feeding it into the set. Unfortunately it also boosts the noise as well. However despite my saying this they are undoubtedly a very useful tool especially to anyone who is in an area of weak radio signals.

I recently cast an eye over the latest copy of



"Communication" the journal of the newly formed Twickenham DX Club. The editor, namely **Dave Kenny** of 37a Popes Grove, Twickenham gave me permission to quote the fact that one of their members reported Radio Omdurman in the Sudan at 1655 on 11835. This is a 120 kilowatt and is very rarely reported. The service is for Sudanese people abroad and is only on for one hour a day from 1800 to 1900 except Saturday, when it changes to 1900 to 2000, so no wonder it is a rarity.

That, I am afraid, draws the meeting to a close, a very heavy post bag this month for the space allowed so apologies if you were left out and 73s to you and yours.

MEDIUM WAVE DX

by **CHARLES MOLLOY**

STOKE-ON-TRENT listener **Christopher Owens** uses a Bush BP12 receiver when DXing on the medium waves. His transatlantic successes are WNBC in New York City on 660kHz at 0115, CJON St John's Newfoundland on 930kHz at 0145, WBZ in Boston on 1030kHz at 0150, CBA Moncton New Brunswick on 1030kHz at 0205. Other catches are Radio Algiers on 251kHz on the long waves (this station has a daily programme in English at 1900 GMT), Dakar in Senegal, West Africa on 764kHz carrying an international programme at 0130, Agadir in Morocco on 935kHz at 0030 and the Voice of Tangiers on 1232kHz at 0040.

An excellent log of Latin American DX heard between 0200 and 0300 GMT comes from **Alfred Johnson** of London. Among the more notable are HJND Radio Nacional, Bogota in Colombia on 570kHz, HJHJ Radio Libertad, Barranquilla Colombia on 600kHz, YVLH Radio Giradot, Maracay in Venezuela on 650kHz, YVLL Radio Rumbos, Caracas in Venezuela 670kHz, HJCX Radio Sutatenza, Cali on 700kHz, YVKY Radio Capital, Caracas 710kHz, HJDK La Voz de Antioquia, Medellin 750kHz, YVQQ Radio Puerto La Cruz 760kHz, PJB Trans World Radio Bonaire, Netherlands Antilles 800kHz, HJCY Radio Sutatenza Bogota 810kHz, HJKC Emisora Nuevo Mundo, Bogota 850kHz, PRA3 Radio Mundial, Rio de Janeiro Brasil on 860kHz, Radio Jornal do Brasil on 940kHz, HJHN Radio Sutatenza, Magangue 960kHz, YVTB Exitos 980 in Maracaibo 980kHz, Radio Margarita, La Asuncion 1020kHz, PRE3 Radio Globo in Rio de Janeiro on 1180kHz, YVMN Radio Coro 1210kHz and ZYD74 Radio Tupi, Rio de Janeiro on 1280kHz. Latin Americans are usually at their best here in the UK in summer. Listen during the hour before sunrise for Brazilian stations which peak up at this time, such as Radio Jornal on 940kHz, Radio Nacional 980kHz and Radio Globo 1180kHz all in Rio de Janeiro and Radio Record 1000kHz, Radio Tupi 1040kHz and Radio Nacional 1100kHz in Sao Paulo.

Steve Whitt, who is a recent convert to the medium waves, reports again from London. His shack is equipped with an 8 valve Chapman 6BS

communications receiver with the Practical Wireless Audio Processor Unit and his 40ft L shaped aerial strung between three chimneys at 30ft above ground level is connected to the receiver via the PW Aerial Tuning Unit. DX reported includes Sud Radio Andorra on 818kHz, CJON St John's on 930kHz and CBA Moncton on 1070kHz. Steve is building the Practical Wireless medium wave loop aerial including the FET balanced preamplifier.

Dr H. S. Brodribb (St Leonards-on-Sea) asks for information about the ITU LF/MF Conference which was held in Geneva last October. The recommendations made would maintain the 9kHz channel spacing in the European Area but would start at 531kHz instead of 539kHz as at present. This 9kHz spacing is useful to the medium wave DXer since stations in other parts of the world are spaced on multiples of 10kHz and consequently there are parts of the band where DX can be found between European stations. Listen at sunset for Riyadh in Saudi Arabia on 587kHz, Baghdad on 760kHz, Teheran on 1326kHz, Gorgan Iran on 1426kHz, Kuwait 1345kHz, Kirkuk in Iraq on 1360kHz, Ahwaz in Iran on 1390kHz and Dubai in the Persian Gulf on 1480kHz.

An unusual broadcaster can be found on 1095kHz during the evening. This is Radio Bayrak located in the Turkish held part of Cyprus. Heard by the writer at 2030 GMT with Turkish music, on a Marconi Mercury communications receiver and a 90ft outdoor aerial.

BROADCAST BANDS

Short Wave Reports by the 15th of the month to **Derek Bell**, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD. Medium Wave Logs to **Charles Molloy**, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

Logs covering any amateur band/s in band/alphabetical order by the middle of the month to **Eric Dowdeswell G4AR**, Silver Firs, Leatherhead Road, Ashted, Surrey, KT21 2TW.

CQ! CQ! CQ! CQ!

EXCHANGE

...exchange or part-exchange Codar CR70A receiver for other general coverage Rx.—**P. Dupleton**, 37 Mountview Avenue, Dunstable, Beds.
...P.E. March 1972 to Jan. 1974. P.W. June 1973 to Jan. 1974: any five for P.W. Oct. 1971, Jan 1972 or April 1972.—**R. Sylvester**, 8 Poplar Avenue, Johnstone, Renfrewshire Scotland.

ISSUES FOR DISPOSAL

...about 150 back numbers of P.W. from Nov. 52 to Nov. 1973.—**R. Collins**, 35 The Riding, Woking, Surrey.
...back copies of P.W. from 1952 to 1974.—**Harry Reilly**, 76 Dundela Avenue, Belfast, BT4 3BU, N. Ireland.
...copies of P.W. going back to 1946.—**W. C. Brown**, GW8A1B, Pendref, Caersws, Montgomery, Wales.
...complete sets of E.E., odd P.W. and P.E. issues.—**J. Tobin**, 38 Blythwood Road, London, N.4.
...copies of P.W. April 1971 to October 1973 inclusive excepting Aug. 1972, July 1971 and April 1973. Includes all articles by **Hellyer** on Transistor Circuitry for Beginners.—**J. W. Talbot**, 58 Colston Avenue, Carshalton, Surrey.
...numerous issue of P.W. from 1959 to 1973.—**R. A. Miller**, 7 Woodrow Court, Melbourne Road, London, N.17.
...issues from 1958 (P.W.) to 1974.—**J. Choppin**, 9 Kitchin Avenue, Woodhouse Close Estate, Bishop Auckland, Co. Durham, DU4 6RB.
...P.W. October 1968 to October 1973 inclusive minus 4 issues.—**P. Johnson**, 158 Radford Road, Coventry, CV6 3BP.
...P.W. June 1969 to December 1973.—**J. White**, 57 Chandos Ave., Ealing, London, W.5.

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

Bargains from our FREE Catalogue

20 large pages, filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 6p stamp for your FREE copy of 6th Edition by return. Meanwhile, for prompt delivery order from this month's ad. NOW.

TRANSISTOR PACKS ALL AT 50p EACH TESTED & GUARANTEED

B79	4	IN4007 Sil. Rec. diodes, 1,000PIV 1 amp. plastic	H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC945
B81	10	Reed Switches, 1 long 1/2 dia. High-speed P.O. type	H41	2	Complementary Plastic Transistors 40361 Type NPN Sil. Transistors TO-5 can comp. to H66
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	H65	4	40362 Type PNP Sil. Transistors TO-5 can comp. to H65
H38	30	Short lead, NPN Silicon Planar Ex Equipment.	H66	4	

UNMARKED & UNTESTED

B1	50	Germanium Transistors PNP, AF and RF	H6	40	250mV zener diodes. At least 20 good.
B66	150	Germanium Diodes Min. glass type	H15	30	Silicon rectifiers 750mA assorted. Top-hat type.
H68	10	Experimenter's pack of I.C.s, D.T.L. and T.T.L. (some marked)	H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	H67	10	3819N Channel FET's plastic case type

PLASTIC POWER TRANSISTORS

40 WATT SILICON					
Type	Polarity	Gain	VCE	Price	
40N1	NPN	15	15	20p	
40N2	NPN	40	40	30p	
40P1	PNP	15	15	20p	
40P2	PNP	40	40	30p	

90 WATT SILICON					
Type	Polarity	Gain	VCE	Price	
90N1	NPN	15	15	25p	
90N2	NPN	40	40	35p	
90P1	PNP	15	15	25p	
90P2	PNP	40	40	35p	

NEW X-HATCH GENERATOR Mk. 2



Essential for Colour T.V. alignment of 4 patterns. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3". Operates from 3 U.2 type batteries (extra).

P/P add 30p Complete kit **£7.93*** Ready built unit only **£9.93***

TO CLEAR

Hundreds of various portable transistor radio chassis with FM & AM tuning. Ideal for experimenters. All electronic components in good order, but no instructions or tuning drives. A cheap way to make a portable. Each £1

SUNDRY

Capacitor Discharge Ignition Kit £7.50 (8). 8 assorted relays £1.00 (8). Rev counter device (for cars) £1.00, U.H.F./TV Tuner Units £2.50, LM.389 Audio I.C. £1.00. Technical books of all kinds (no VAT).

TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. This must be added to total value of your order including postage at 25%, except for prices marked * or (8%), when only 8% V.A.T. is required. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 20p for postage & packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum order value £1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

BI-PRE-PAK LTD

C. Reg. No. 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED



challenging values!


Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatched and include well printed instructions.


PRE-AMP TONE CONTROLS

Pre-amplifiers; tone control

SS.100	Active tone control unit to provide bass, treble, balance and volume controls	£1.60
SS.101	Pre-amp for ceramic cartridge, tape and radio	£1.60
SS.102	Pre-amp for low output magnetic cartridge, tape and radio. With R.I.A.A. correction $\pm 1\text{dB}$ at 1K	£2.25

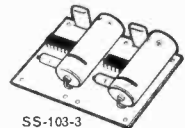


SS-103-3

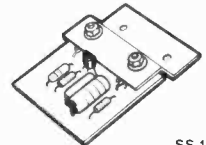

SS.105

POWER AMPLIFIERS


SS.103	Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 10-20v. Size 3 1/2" x 2"	£1.75
SS.103-3	Stereo version of above using one I.C. on each channel	£3.25
SS.105 MK2	New improved all-purpose power amp which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 3 1/2" x 2"	£2.25
SS.110 MK2	Similar in size to SS.103 but with a 10 watt output. Ideal for many domestic and small size P.A. applications. Operates from 26 to 32V	£2.75
SS.140	Excellent designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. THD better than 0.2%. Power requirements—45V. d.c. With 0.15" centre edge connections. Two can be bridged to give 80 watts R.M.S. into 8 ohms	£3.60

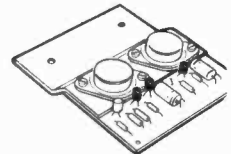


SS.140

BUILD A STEREO FM TUNER!

SS.201	Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6-16V	£6.25
SS.202	I.F. stage (with I.C.) Pre-tuned. A.F.C. connection. Operates from 4.5 to 14V	£5.25
SS.203	Stereo Decoder. Designed essentially for use with SS.201 and 2, this module can also be used in most mono FM tuners. A LED may be attached. Operating voltage 9-16V. d.c.	£5.62

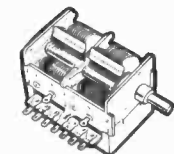

SS.201

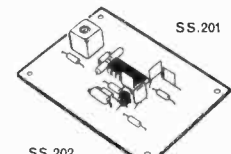


SS.202

SPECIAL £5 MONEY SAVING OFFER

Buy all three modules for building a stereo FM Tuner (Total list £17.21) and you pay only £12.12

POWER SUPPLY STABILIZER

SS.300	Add this to an unbalanced supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential on your audio and special systems as well as test bench. Money saving and very reliable	£3.25
--------	---	--------------

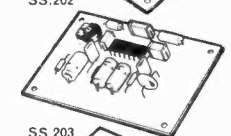


SS.203

MAINS TRANSFORMERS FOR ABOVE

Add 35p per transformer for P/P

Type A 18V/1A (Suit SS.103)	£1.50
Type B 25V/2A (Suit SS.110)	£2.00
Type C 30V/2A (Suit SS.140)	£4.50

Bridge Rectifiers—Type A 27p. Types B & C 38p

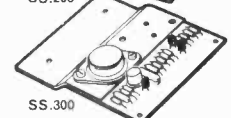

SS.300

Founded 1959

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose inc. V.A.T.

Name

Address


PW7

LISTEN TO

CODAR®

THE WORLD!

★ **CR70A**

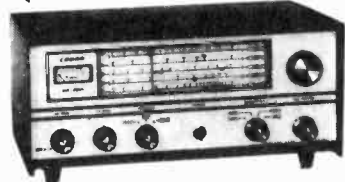

COMMUNICATION RECEIVER

★ **MADE TO ORDER!**
£36 + £9 VAT
CARRIAGE PAID

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ **IMPORTANT NOTE**

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your receipt, sent by return.

* Special discounts for Educational Authorities and Senior Citizens.



ON THE DESIGN STAFF—
G3SZM G3IRE


CODAR®

TO COPE WITH INCREASING DEMAND—PLEASE
NOTE NEW SALES OFFICE TEL No. BRIGHTON 38345
MON-THURS-9.30 a.m.-4.30 p.m.

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX
WORLD-WIDE MAIL ORDER—EXPORT QUOTES FREE. **BN15 - 8TZ**



★ **P.R.40** ★

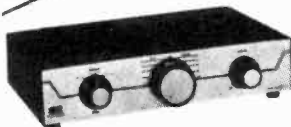

£11 + £2.75 VAT
CARRIAGE PAID

R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by Silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee ...



MULTIBAND-6 ★

SHORT WAVE RECEIVER KIT

£16.56 + £4.14 VAT

CARRIAGE PAID

All transistor T.I.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship / Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

ILLUSTRATED LEAFLETS FREE ON REQUEST (STAMP APPRECIATED)

ESSENTIAL BOOKS FOR RADIO AMATEURS

NEW (16th) EDITION

A GUIDE TO AMATEUR RADIO

by Pat Hawker, G3VA

For over 40 years the many editions of the *Guide* have helped successive generations of amateurs to learn about amateur radio and to obtain transmitting licences.

The new edition has been extensively revised and enlarged. Chapters include: (1) This is amateur radio; (2) Getting started; (3) Communication receivers; (4) Amateur transmitters; (5) Licence examinations; (6) Operating an amateur station; (7) Workshop practice, and (8) Amateur equipment.

An entirely new chapter on popular equipment include facts on over 160 well-known models—receivers, transmitters, transceivers. Full constructional details are given of two simple receivers and a phone/cw transmitter.

This edition reflects current interest in ssb, vhf, transistor and valve equipment, Class A and Class B licences. It describes how licences are obtained and provides guidance on both home-built and factory-made equipment.

Almost 100,000 copies of all editions sold

112 pages, fully illustrated

Price £1.10 post paid

TEST EQUIPMENT

for the radio amateur

by H. L. Gibson, CEng, MIEE, G8CGA

Explains in detail the theory behind modern measurement techniques, and describes many items of equipment of special interest to the home constructor. Topics include signal sources, attenuators, oscilloscopes, swept measurements, aerials and transmission lines. Detailed instructions are given for the construction of many items of test gear.

120 pages

£2.20 post paid

TELEPRINTER HANDBOOK

by D. J. Goacher, G3LLZ, and

J. G. Denny, G3NTT

A renowned book covering all aspects of modern teleprinter techniques. Full descriptions and maintenance data for all widely-used machines, together with design and use of ancillary equipment. Definitely a book for the teleprinter enthusiast's work bench.

376 pages

£5.60 post paid

These are just three of a complete range of technical publications, log books and maps for the radio amateur. Send a large stamped self-addressed envelope for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.



RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688

Europe's Largest Hi-Fi Retailers

LASKYS

give you :-

- GREAT CHOICE
- BIG VALUE
- BIG NAMES
- 27 STORES to give you BIG SERVICE



TMK 200 MULTIMETER KIT

Build yourself a quality 20000 opv multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test prods and instructions. Ranges: 0/0.5 6 30 120 600/1200V AC, 0/1 3 120 600/1200V AC, Current: 0 0.5 6 60/600mA, Resistance: 0/10 100K/1/10 Meg ohms. Decibels: -20 to +63dB. Size: 90x150x35mm.



OUR PRICE £9.67 P&P Ins 30p

AUDIOTRONIC Model ATM1

Top value 1,000 opv pocket multimeter. Ranges: 0/10/50/250/1,000 volt AC and DC, DC current 0.1mA/100mA, Resistance: 0/150K ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.



OUR PRICE £4.25 P&P Ins 25p

AUDIOTRONIC MODEL ATMS

Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0.3/15/150/300/1200V AC, (2500 opv), 0.6/30/300/600V DC, (5000 opv), 0.300 uA/0.300mA DC, Resistance: x10 & x100, -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.



OUR PRICE £4.85 P&P Ins 25p

MODEL C7202EN

20,000 opv DC, 10,000 opv AC, Mirror Scale. Ranges: 5/25/50/250/1000/2500V DC, 10/10 100/500/1000V AC, DC Resistance x 10, x100 (30K centre scale), DC Current 50uA, 2.5mA, 250mA, -20 to +68dB.



OUR PRICE £7.51 P&P Ins 30p

U435 MULTIMETER

20,000 opv. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC, 2.5/10/25/100/250/500/1000V AC, Current: 50uA/1/5/25/100mA/0.5/2.5A DC, 5/25/100mA/0.5/2.5A AC, Resistance: 0/10 100K/1/10 Meg ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.



OUR PRICE £9.45 P&P Ins 30p

MODEL C7208FM

30,000 opv DC, 15,000 opv AC, 6.3/15 60 300 600 1200V DC, 6 30 120 600/1200V AC, DC Resistance x 1, x10, x100, x1000 (50K centre scale), DC Current 30uA, 3.30 600mA, -20 to +63dB.



OUR PRICE £9.67 P&P Ins 30p

U4324 MULTIMETER

High sensitivity, 20,000 opv. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC, 3/6/15/60/150/300/600/900V AC, Current: 0.06/0.6/6/60/600mA/3A DC, 0.3/3/30/300mA/3A AC, Resistance: 25/500 ohms/0.5/5/50/500K ohms/5 Mohms, Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.



OUR PRICE £10.64 P&P Ins 60p

U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC, Current: 10/25/100/250/500A, Accuracy 4%, Size 293 x 24 x 36mm. Complete with carrying case, leads and fuses.



OUR PRICE £15.12 P&P Ins 60p

HIOKI 730X

30,000 opv. Overload protection. Ranges: 6.30/60/300/600/1200V DC, 12/60/120/600/1200V AC, 60/60uA, 30mA/300mA, 2K/200K, 2 Meg Ohm, 10 to 63dB.



OUR PRICE £8.10 P&P Ins 30p

U4323 MULTIMETER

20,000 opv. Simple unit with audio/RF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC, 2.5/10/15/250/500/1000V AC, 0.05/0.5 5 50 500mA DC, Resistance: x10, x100, x1,000, x10,000 (50K, 500K, 5K, 50K centre scale). Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.



OUR PRICE £8.64 P&P Ins 60p

U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 6670 opv. Ranges: 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV, 0/0.3/1.5/7.5/30/60/150/300/600/900V AC, 0/300uA/1.5/6/15/150/60/60/150/300/600/900V AC, 0/300mA/1.5/6/15/150/60/60/150/300mA/1.5/6A AC, 0/200/3K/30K ohms, DC accuracy 1%, AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.



OUR PRICE £11.61 P&P Ins 60p

HIOKI 750X VOLT-OHM MILLIAMMETER


43 ranges, mirror scale. 50K V/DC, 50K V/AC, DC Volts: 0.125/0.25/1.25/2.5/10/25/50/100/500/1000, AC Volts: 1.5/3/15/10/25/50/100/500/1000, DC current: 25/50mA/2.5/5/25/50/250/500mA/5/10A, Resistance: 0-3/300K/3/30Mohms, Decibels: -10 to +17dB, Output: 0.5/1/2/5/10/20/50/120/300V, Accuracy ± 3% DC, ± 4% AC, Sensitivity: 50,000 opv DC, 5,000 opv AC, 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.



OUR PRICE £12.90 P&P Ins 60p

TMK MODEL TW50K

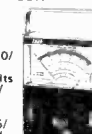48 ranges, mirror scale, 50K V/DC, 50K V/AC, DC Volts: 0.125/0.25/1.25/2.5/10/25/50/100/500/1000, AC Volts: 1.5/3/15/10/25/50/100/500/1000, DC current: 25/50mA/2.5/5/25/50/250/500mA/5/10A, Resistance: 10k/100K/1 Meg/10 Meg ohms, -20 to +81.5dB.



OUR PRICE £13.50 P&P Ins 60p

MODEL C7080EN

Giant 6" mirror scale, 20,000 opv, 0/0.25/1.25/10/50/250/1000/5000V DC, 0/2.5/10/50/250/1000/5000V AC, 0/50uA/1/10/100/500mA/10A DC, 0/2k/200k/20 Meg, -20 to +50dB.



OUR PRICE £21.55 P&P Ins 60p

MODEL 500

30,000 opv with overload protection. Mirror scale. Ranges: 0/0.5/2.5/10/25/100/250/500/1000V DC, 0/2.5/10/25/100/250/500/1000V AC, 0/50uA/5/50/500mA, 12A DC, 0/60K/6 meg/60 megohms p.p.g.



OUR PRICE £15.07 Ins 60p

MODEL AS.1000 VOM

100,000 opv. Mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1200V DC, 0/6/30/120/300/600V AC, 0/10uA/6/60/300mA, 12A DC, 200K/2M, 200 Meg Ohm, -20 to 17dB.



OUR PRICE £18.90 P&P Ins 60p

KAMODEN HM720B FET VOM

Input impedance 10 Megohms. Ranges: 0/0.5/2.5/10/50/250/1000V AC, 0/25uA/2.5/25/250 mA DC, 0/5k/50k/500k/5M 500 Megohms.



OUR PRICE £24.30 P & P Ins 60p

KAMODEN 360 MULTIMETER

High sensitivity, DC 1000uA/100uA/100uA, 5" mirror scale, overload protected. Ranges: 0/0.5/2.5/10/50/250/1000V DC, 5/10/50/250/1000V AC, 0.1mA/0.5/5/50/500mA/10A, Resistance: 0/1/10/100 ohms/1/10/100K ohms/1/10/100M ohms/10/100M ohms, Decibels: -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads etc.



OUR PRICE £18.90 P & P Ins 60p

Model HT10084 MULTIMETER

Overload protected, shock proof circuits, 9.5uA Meter with mirror scale. Sensitivity 20,000 opv. Polarity change switch. Ranges: 0/5/2.5/10/50/250/1000V DC, 2.5/10/50/250/100V AC, DC resistance: 0-20/200k/22 Meg ohms, DC current: -10/250uA/2.5/25/250mA/10A, AC current: -0-10A, -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 186 x 134 x 79mm.



OUR PRICE £21.06 P&P Ins 60p

370WTR MULTIMETER


Features AC current ranges, 20,000 opv, 0/0.2/2.5/10/50/250/500/1000V DC, 0/2.5/10/50/250/500/1000V AC, 0/50uA/1/10/100 mA/1/10A DC, 0/100mA/1/10A AC, 0/5k/10k/500k/5 Meg/50 Meg, Decibels: -20 to +62dB.



OUR PRICE £21.55 P&P Ins 60p

U4317 MULTIMETER

High sensitivity instrument for field and laboratory work. Knife edge pointer, 86mm, mirror scale, overload protection. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC, 0.5/2.5/10/25/50/100/250/500/1000V AC, Current: 50uA/0.5/1/5/10/50/250mA/1.5A DC, 0.25/0.5/1/5/10/50/250mA/1.5A AC, Resistance: 5/15/100/200 ohms/1/3/30/300K ohms, Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.

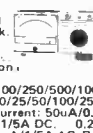

OUR PRICE £18.36 P&P Ins 60p

KAMODEN 72.200 Multitester

High sensitivity tester, 200,000 opv, Overload protected. Mirror scale. Ranges: -0/0.6/3 3/30/120/600/1200V DC, 0/3 12/60/300/11200 V AC, 0/50uA/1mA/5mA/600mA/12A DC, 0/12A AC, -20 to +63dB, 0/2/20k/2 Meg/200 Megohms.



MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter scale, protection. 0/3 3/12/60/120/300 600/1200V DC, 0.6 30 120/300/600/1200V DC, 0/30uA/6/60/300mA, 12 Amp, 0/10K/1m/10m/100 Meg Ohms, -20 to 17dB.



OUR PRICE £13.50 P&P Ins 60p

LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.



OUR PRICE £4.86 P&P Ins 20p

KAMODEN TT35 TRANSISTOR TESTER

High quality instrument to test reverse leak current and DC current. Amplification factor of NPN, PNP, diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions. Leads carrying handle.



OUR PRICE £18.90 P & P Ins 60p

U4341 Multimeter & Transistor Tester

27 ranges, 16,700 Opv. Overload protected. Ranges: 0/0.5/2.5/10/50/250/1000V DC, 1/5/7.5/30/150/300/750V AC, Current: 0.06/0.6/6/60/600mA DC, 0.3/3/30/300mA AC, Resistance: 0/6.6/20/60/200K ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.



OUR PRICE £11.88 P&P Ins 60p

S100TR MULTIMETER TRANSISTOR TESTER

100,000 opv. Mirror scale. Overload protection. Ranges: 0/0.12/0.6/3/12/30/120/600V DC, 0.6/30/120/600V AC, 0/12/30/60/120/600/12A DC, 0/10k/1 Meg/100 Meg, -20 to +50dB, 0.01 - 0.2 MFD. Transistor tester measures Alpha, Beta and Ico. Complete with instructions, batteries and leads.



OUR PRICE £22.68 P&P Ins 60p

SWR METER MODEL SWR3


Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%, impedance 50 Ohm indicator, 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.



OUR PRICE £4.60 P&P Ins 60p

C15 PULSE OSCILLOSCOPE

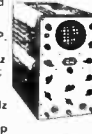For display of pulsed and periodic wave forms in electronic circuits. VERT. Amp. Bandwidth: 10MHz, Sensitivity at 100kHz VRMS/mm: 0.1-25, HORIZ. Amp. Bandwidth: 500kHz, Sensitivity at 100kHz VRMS/mm: 0.3-25. Preset triggered sweep 1-3000uses, Free running 20-200 kHz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V AC.



OUR PRICE £47.52 Ins £1.50

ALL PRICES INCLUDE VAT

Also see following pages

ASK LASKYS
about test equipment

SINCLAIR DM2 DIGITAL MULTIMETER

Will measure AC and DC volts, AC and DC current, and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply.

RANGES:
 DC VOLTS: 1v, 10, 100v, 1000v.
 AC VOLTS: 1v, 10v, 100v, 1000v.
 DC CURRENT: 1mA, 10mA, 100mA, 1000mA.
 AC CURRENT: 1mA, 10mA, 100mA, 1000mA.
 RESISTANCE: 1k, 10k, 100k, 1000k.

OUR PRICE £64.75 P & P Ins. 50p

RUSSIAN C116 Double Beam OSCILLOSCOPE

5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2µs to 100 milli-sec/cm. Free running time base 50Hz-1MHz. Built-in tone base. Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual. P & P

OUR PRICE £93.90 P & P Ins. £2.00

MODEL TE15 GRID DIP METER

Transistorised Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 40kHz-280MHz in six coils. 500µA meter. 9V battery operation. Size: 180 x 80 x 40mm.

OUR PRICE £18.90 P & P Ins. 30p

TRANSISTORISED L.C.R. A.C. BR/B MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-1.1 megohm ± 1% Inductance: 6 ranges: 1 microhenry-111 henries ± 2% Capacity: 6 ranges: 10pF-1110 mfd ± 2% Turns Ratio: 6 ranges: 1:1/1000-1:1/1000 ± 1% Bridge Voltage at 1,000cps. Operates from 8-12V battery. 100 microamp meter indication. Size 71 x 52 x 22mm.

OUR PRICE £29.70 P & P Ins. 60p

TE16A TRANSISTORISED SIGNAL GENERATOR

5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy man. Operates on 9V battery. Wide easy to read scale, 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.

OUR PRICE £9.69 P & P Ins. 30p

TE-200 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.

OUR PRICE £24.30 P & P Ins. 60p

ARF 300 AF/RF SIGNAL GENERATOR

All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Squares. Sine wave 10V. P.P RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.

OUR PRICE £40.50 P & P Ins. 60p

MODEL TE20 RF SIGNAL GENERATOR

Six bands, 120kHz-280MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements: 106-125V, 220-240V AC. Size: 193 x 265 x 150mm. Complete with test leads and manual.

OUR PRICE £20.47 P & P Ins. 60p

TE22 SINE SQUARE WAVE AUDIO GENERATOR

Sine 200cps to 2000Hz on 4 bands. Square 20 cps to 30 kHz. Output impedance 5000 Ohms. 200/250V. AC operation. Supplied brand new guaranteed, with instruction manual and leads.

OUR PRICE £26.95 P & P Ins. 60p

STOP PRESS!!

TODAYS BEST VALUE

WHARFEDALE SPEAKERS at Special LASKYS PRICES

DENTON 2 in Walnut or Rosewood £35.00 per pair Ins. P & P £1.50

LINTON 2 in Walnut £46.23 per pair Ins. P & P £1.50

GLENOALE 3 in Teak £71.88 per pair Ins. P & P £1.50

UNREPEATABLE OFFER - BUY NOW LIMITED STOCKS

NEARLY 25% OFF GARRARD 865B MODULE

This complete unit comes fitted in white with hinged cover. Includes M765M magnetic cartridge. This 2-speed belt drive deck comes with many features. Bias control, low resonance arm. Todays value £62.60.

OUR PRICE £44.94 P & P Ins. £1

BATTERY/LEVEL PANEL INDICATOR

18mm 18mm Panel mounting. **OUR PRICE 94p** P & P Ins. 15p Discounts for quantity.

NEW GOLDRING G102 KIT

Belt-drive 2-speed turntable in kit form complete with pick up arm and head shell. **OUR PRICE £21.20 Ins. £1.00**

VU METER TYPE 3

250 uA Size: 33mm 20mm. **£1.57 P & P Ins. 15p**

T.T.C. SPRITE STEREO HEADPHONES

Feather weight (5oz) Dynamic stereo headphones providing high quality reproduction at a budget price. Soft removable ear pads and adjustable headband. Speaker size: 28mm. Impedance: 8 Ohms. Frequency response: 30-13000 Hz. **OUR PRICE £2.44 P & P Ins. 30p**

SDH8 MONO/STEREO HEADPHONES

Volume control for each channel. 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug. **OUR PRICE £6.22 P & P Ins. 30p**

AUDIOTRONIC HEADPHONES

LSH20 Individual volume controls. Mono/stereo switch. 40-19,000 Hz. 8 ohms. **OUR PRICE £5.63 P & P Ins. 50p**

LSH30 Individual tone and volume controls. Mono/stereo switch. 30-20,000 Hz. 8 ohms. **OUR PRICE £8.75 P & P Ins. 30p**

LSH40 Two-way speaker system. Individual volume controls. 20-20,000 Hz. 8 ohms. **OUR PRICE £10.63 P & P Ins. 30p**

RANK AUDIO RA 210T STEREO AMPLIFIER

7; 7; watts rms. Inputs for magnetic phono, tuner, tape and aux. Separate base, treble, balance and volume controls. Headphone socket. Teak case. Unrepeatable offer. **OUR PRICE £21.88 P & P Ins. £1**

SUPERB QUALITY LOW PRICES

AUDIOTRONIC DIGITAL CLOCK RADIOS

ADC22 24-hour clock radio, covering MW/FM wave bands. 180-minute sleep timer. Choice of Gray or White cabinet. **NOW ONLY £17.44 P & P Ins. £1**

ADC33 Deluxe 24-hour clock radio covering MW/FM wavebands. 180-minute sleep timer. Buzzer alarm. Tone control. **NOW ONLY £19.95 P & P Ins. £1**

ALL PRICES INCLUDE VAT

FM TUNER CHASSIS

6 transistor high quality tuner. Size only 153 x 101 x 63mm. 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-106MHz. Ready built, ready for use. Fantastic value for money. **OUR PRICE £7.44 P & P Ins. 20p** Stereo Multiplex Adaptor £5.95 extra.

WALKIE TALKIES SKYFON NV7

Super low cost transmitter/receivers. 100MW with call buzzer and on/off volume control. 7 transistors. Telescopic rod antenna. **OUR PRICE £9.38 P & P Ins. 50p** NOT LICENSABLE IN THE U.K.

POCKET CALCULATOR 'TECO TE8053'

8 digit, 4 function. List price £11.34. **OUR PRICE £9.67** P & P Ins. 25p

SINCLAIR CALCULATORS LOWEST PRICES EVER!

SINCLAIR CAMBRIDGE 8 digit, Constant, DC only. List Price £13.99. **OUR PRICE £11.88 P & P Ins. 25p**

SINCLAIR CAMBRIDGE MEMORY 8 digit, Automatic Constant, Memory, DC only. List Price £19.40. **OUR PRICE £16.47 P & P Ins. 25p**

SINCLAIR SCIENTIFIC Loga Trig, Arithmetic, Scientific notation, DC only. List Price £21.55. **OUR PRICE £18.31 P & P Ins. 25p**

SINCLAIR EXECUTIVE MEMORY 8 digit, Constant, Memory, DC only. List Price £26.95. **OUR PRICE £22.95 P & P Ins. 25p**

SINCLAIR NEW OXFORD RANGE **OXFORD 100** 4 function (DC). Mains adaptor optional extra. List Price £13.99. **OUR PRICE £11.88 P & P Ins. 25p**

OXFORD 200 4 function plus Memory and Percentage (DC). Mains adaptor optional extra. List Price £21.55. **OUR PRICE £11.83 P & P Ins. 25p**

OXFORD 300 Scientific (Available late March). (DC). Mains adaptor optional extra. List Price £32.36. **OUR PRICE £27.54 P & P Ins. 25p**

OXFORD MAINS ADAPTOR **OUR PRICE £3.19** optional extra

ELECTRONIC CALCULATORS

We carry a tremendous range of both pocket and desk calculators from as little as £9.13. Owing to the demand it is not possible to include them in this advertisement, so send for our latest price list or call into any branch.

MINIATURE ORGAN MUSIC MASTER AM100

Spanning nearly two octaves, including semitones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The Keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V DC socket. **Size 229mm x 127mm x 64mm. OUR PRICE £9.94 P & P Ins. 60p**

HANIMEX HDC 1900 DIGITAL ALARM CLOCK

240V operation with large clear numbers, night light and 'noodle' switch. Attractively finished in white and silver. **OUR PRICE £9.38 P & P Ins. £1.00**

SINCLAIR Project 80 Modules

240 Power Amp £5.63 P & P 15p Ins.
 280 Power Amp £7.00 P & P 15p Ins.
 Stereo 80 Pre-Amp £17.46 P & P 15p Ins.
 Active Filter Unit £9.31 P & P 15p Ins.
 FM Tuning Meter £13.12 P & P 15p Ins.
 Stereo Decoder £8.44 P & P 15p Ins.
 PZ8 Power Supply £4.69 P & P 30p Ins.
 PZ6 Power Supply £8.44 P & P 30p Ins.
 PZ8 Power Supply £7.94 P & P 30p Ins.
 Transformer for PZ8 £5.07 P & P 50p Ins.

AUDIOTRONIC LOW NOISE CASSETTES

TYPE	9	10	25
CS6	£1.70	£3.24	£7.65
CS9	£2.42	£4.69	£10.80
CT20	£2.95	£5.59	£13.22

P & P Ins. 3p each. 10 and over Post Free.

AUDIOTRONIC AH401 Stereo Headphone Amplifier

All silicon transistor amplifier operates with magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel. **OUR PRICE £10.63 P & P Ins. 30p**

HIGH QUALITY CONSTRUCTION KITS

WARE STOCKISTS at Oxford Street, 42 & 257 Tottenham Court Road, 34 Lisle Street, 152, Fleet Street, 311 Edgware Road. CROYDON BIRMINGHAM KINGSTON LEICESTER NOTTINGHAM SOUTHEND TUNBRIDGE WELLS WOLVERHAMPTON branches, or by Mail Order.

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee. Post and Packing Ins. 15p per kit.

- AF20 Mono amplifier..... £7.01
- AF25 Mixer..... £4.11
- AF30 Mono pre amplifier..... £4.00
- AF35 Emitter amplifier..... £2.63
- AF80 0.5W mic. amplifier..... £8.08
- AF305 Intercom..... £9.59
- AF310 2 Mono Amplifier..... £5.44
- M160 Multi-vibrator..... £2.73
- M1302 Transistor tester..... £10.41
- M191 VU Meter..... £6.71
- M192 Stereo balance meter..... £7.41
- L380 Quadraphonic device..... £10.53
- AT5 Automatic light control..... £4.89
- A130 Photo call switch unit..... £8.35
- AT50 400W triac light dimmer/speed control..... £8.48
- AT56 2,200W triac light dimmer/speed control..... £8.44
- AT60 1 Stereo light control..... £13.53
- AT65 3 channel light control..... £20.65
- GU330 Tremolo unit..... £10.13
- HF61 Dige detector..... £4.84
- HF65 FM transmitter..... £4.02
- HF75 FM receiver..... £5.44
- HF310 FM tuner..... £20.40
- HF325 Deluxe FM tuner..... £32.91
- GP304 Circuit board..... £6.88
- GP310 Stereo pre-amplifier for use with 2 x AF310..... £28.73
- AF312 Circuit board..... £12.53
- HF380 UHF aerial amplifier..... £7.53
- HF395 broadband aerial amp..... £2.63
- NT10 Stabilised power supply 100mA 9V..... £7.84
- NT300 Stabilised p. supply..... £16.46
- NT310 Power Supply 240 V A.C. or 2 x 18 V D.C. at 2amps..... £7.05
- NT305 Voltage converter..... £7.05
- NT315 Power supply 240 V A.C. to 4 x 15V D.C. 500mA..... £15.08

Amateur Electronics by Josty-Kit, the professional book! - the amateur covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1 to AE10 listed below. **OUR PRICE £3.30 (No VAT)** P & P Ins. 25p plus VAT

- AE1 100mV output stage..... £1.94
- AE2 Pre-amplifier..... £1.65
- AE3 Radio receiver..... £2.58
- AE4 Flasher..... £1.88
- AE5 Astable multi-vibrator..... £1.43
- AE6 Monostable multi-vibrator..... £1.39
- AE7 RC generator..... £1.35
- AE8 Bass filter..... £1.31
- AE9 Treble filter..... £1.31
- AE10 CCR filter..... £1.31

Also see previous page **ALL PRICES INCLUDE VAT**

SEW PANEL METERS


SEW PANEL METERS ARE STOCKED AT OUR 3 LISLE ST., 311 EDGWARE RD., & 152 FLEET ST., BRANCHES or order by post.

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.
Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£4.21
100uA	£4.16
200uA	£4.10
500uA	£4.05
50-0-500uA	£4.16
100-0-100uA	£4.10
1mA	£4.05
5mA	£4.05
10mA	£4.05
50mA	£4.05
100mA	£4.05
500mA	£4.05
1A DC	£4.05
5A DC	£4.05
10A DC	£4.05
5V DC	£4.05

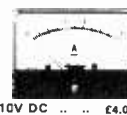

*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

50uA	£4.75
100uA	£4.70
200uA	£4.64
500uA	£4.59
50-0-500uA	£4.70
100-0-100uA	£4.64
1mA	£4.54
5mA	£4.54
10mA	£4.54
50mA	£4.54
100mA	£4.54
500mA	£4.54
1A DC	£4.54
5A DC	£4.54
10A DC	£4.54
5V DC	£4.54



CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£4.37
100uA	£4.27
200uA	£4.21
500uA	£4.18
50-0-500uA	£4.27
100-0-100uA	£4.21
500-0-500uA	£4.10
1mA	£4.10
1-0-1mA	£4.10
5mA	£4.10
10mA	£4.10
50mA	£4.10
100mA	£4.10
500mA	£4.10
1A DC	£4.10
5A DC	£4.10
10A DC	£4.10
5V DC	£4.10



CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£5.08
100uA	£4.97
500uA	£4.75
50-0-500uA	£4.97
100-0-100uA	£4.91
1mA	£4.75
1A DC	£4.75
5A DC	£4.75
10A DC	£4.75
50V DC	£4.75
300V DC	£4.91
300V AC	£4.91
300V AC	£4.91
300V AC	£4.91



CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA	£4.56
100uA	£3.51
200uA	£3.48
500uA	£3.35
50-0-500uA	£3.61
100-0-100uA	£3.46
500-0-500uA	£3.29
1mA	£3.29
10mA	£3.29
50mA	£3.29
100mA	£3.29
500mA	£3.29
1A DC	£3.29
5A DC	£3.29
10V DC	£3.29
20V DC	£3.29
50V DC	£3.29
300V DC	£3.29
15V AC	£3.40
300V AC	£3.40
300V AC	£3.40
300V AC	£3.40



BAKELITE MODEL S80 Enlarged Window

Size: 85 x 80mm

50uA	£4.97
100uA	£4.81
200uA	£4.64
500uA	£4.64
50-0-500uA	£4.81
100-0-100uA	£4.86
500-0-500uA	£4.86
1mA	£4.86
10mA	£4.86
50mA	£4.86
100mA	£4.86
500mA	£4.86
1A DC	£4.86
5A DC	£4.86
10V DC	£4.86
20V DC	£4.86
50V DC	£4.86
300V DC	£4.86
300V AC	£4.86
300V AC	£4.86
300V AC	£4.86
300V AC	£4.86



EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.59
100uA	£4.54
200uA	£4.48
500uA	£4.48
50-0-500uA	£4.53
100-0-100uA	£4.48
1mA	£4.27
5mA	£4.27
10mA	£4.27
50mA	£4.27
100mA	£4.27
500mA	£4.27
1A DC	£4.27
5A DC	£4.27
10A DC	£4.27
5V DC	£4.27



MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.



CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.46
100uA	£3.40
200uA	£3.35
500uA	£3.13
50-0-500uA	£3.40
100-0-100uA	£3.35
500-0-500uA	£3.08
1mA	£3.08
1-0-1mA	£3.08
2mA	£3.08
5mA	£3.08
10mA	£3.08
50mA	£3.08
100mA	£3.08
500mA	£3.08
1A DC	£3.08
5A DC	£3.08
10V DC	£3.08
20V DC	£3.08
50V DC	£3.08
300V DC	£3.08
15V AC	£3.08
300V AC	£3.08
300V AC	£3.08
300V AC	£3.08



CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£4.10
100uA	£3.89
200uA	£3.73
500uA	£3.89
50-0-500uA	£3.73
100-0-100uA	£3.73
500-0-500uA	£3.67
1mA	£3.67
5mA	£3.67
10mA	£3.67
50mA	£3.67
100mA	£3.67
500mA	£3.67
1A DC	£3.67
5A DC	£3.67
10V DC	£3.67
20V DC	£3.67
50V DC	£3.67
300V DC	£3.67
15V AC	£3.67
300V AC	£3.67
300V AC	£3.67
300V AC	£3.67



CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£5.05
100uA	£5.89
200uA	£5.84
500uA	£5.83
50-0-500uA	£5.89
100-0-100uA	£5.84
500-0-500uA	£5.78
1mA	£5.78
1-0-1mA	£5.78
5mA	£5.78
10mA	£5.78
50mA	£5.78
100mA	£5.78
500mA	£5.78
1A DC	£5.78
5A DC	£5.78
10A DC	£5.78
50V DC	£5.78
300V DC	£5.83
300V AC	£5.89
300V AC	£5.89
300V AC	£5.78
300V AC	£5.78



CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.89
100uA	£3.83
200uA	£3.78
500uA	£3.73
50-0-500uA	£3.83
100-0-100uA	£3.78
500-0-500uA	£3.67
1mA	£3.67
5mA	£3.67
10mA	£3.67
50mA	£3.67
100mA	£3.67
500mA	£3.67
1A DC	£3.67
5A DC	£3.67
10V DC	£3.67
20V DC	£3.67
50V DC	£3.67
300V DC	£3.67
15V AC	£3.67
300V AC	£3.67
300V AC	£3.67
300V AC	£3.67



BAKELITE MODEL MR 65

Size: 80 x 80mm

25uA	£5.83
50uA	£4.43
100uA	£4.37
200uA	£4.05
500uA	£4.38
50-0-500uA	£4.32
100-0-100uA	£4.00
500-0-500uA	£4.00
1mA	£4.00
5mA	£4.00
10mA	£4.00
50mA	£4.00
100mA	£4.00
500mA	£4.00
1A DC	£4.00
5A DC	£4.00
10V DC	£4.00
20V DC	£4.00
50V DC	£4.00
300V DC	£4.00
15V AC	£4.21
300V AC	£4.00
300V AC	£4.00
300V AC	£4.00



240° Wide Angle 1mA METERS

MW1-6 60 x 60 mm	
£6.50 P & P 15p	
MW1-8 80 x 80 mm	
£7.02 P & P ins.15p.	



YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

1A	£9.18	£1.00
5A	£18.20	£1.00
8A	£24.30	£1.50
10A	£29.70	£1.50
12A	£32.40	£1.50
20A	£76.80	£1.50
25A	£81.00	£1.50
40A	£91.80	£1.50



TO LASKYS CUSTOMER SERVICES DIVISION
Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me the following items

TOTAL PURCHASE PRICE
Please send me your Free 32-page price list
I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is

Name
Address

Signature

(inc. P & P Ins.)

LASKYS

CALL INTO YOUR NEAREST LASKYS BRANCH OR SEND COUPON BELOW FOR NEW 32 PAGE HI-FI PRICE LIST

CENTRAL LONDON

481 OXFORD ST.	01-493 8641
3 LISLE ST. WC2	01-437 8204
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6111
207 EDGWARE RD. W2	01-723 3271
311 EDGWARE RD. W2	01-262 0387
346 EDGWARE RD. W2	01-723 4453
382 EDGWARE RD. W2	01-723 4184
109 FLEET ST. EC4	01-353 5812
152/3 FLEET ST. EC4	01-353 2833
10 TOTTENHAM CT. RD.	01-437 2332
33 TOTTENHAM CT. RD.	01-634 2605
42/45 TOTTENHAM CT. RD.	01-634 0845
257/8 TOTTENHAM CT. RD.	01-580 0670

ESSEX

84 SOUTH ST. ROMFORD	20218
205/206 CHURCH LANE, WEST	8702 612241
VICTORIA CIRCUS, SOUTHEND	

AVONSHIRE

16/20, PENN ST. BRISTOL	0272-20421
-------------------------	------------

KENT

53/57 CAMDEN RD., TUNBRIDGE WELLS	0872-23242
-----------------------------------	------------

LEICESTERSHIRE

45 MARKET PLACE, LEICESTER	0533-537678
----------------------------	-------------

NORTHAMPTONSHIRE

73 ARLINGTON STREET, NORTHAMPTON	0604-35753
----------------------------------	------------

NOTTINGHAMSHIRE

5-7 LOWER PARLIAMENT STREET, NOTTINGHAM	060248987
---	-----------

OXFORDSHIRE

14 WESTGATE SHOPPING CENTRE, OXFORD	0845-722870
-------------------------------------	-------------

STAFFORDSHIRE

30 WULFURIM WAY, WOLVESHAMPTON	0902-23384
--------------------------------	------------

SURREY

1046 WHITGIFT CENTRE, CROYDON	01-481 3027
38/40 EDEN ST., KINGSTON	01-546 1271
32 HILL ST. RICHMOND	01-948 1441

WARWICKSHIRE

116 CORPORATION ST., BIRMINGHAM	021-236 3503
---------------------------------	--------------

ALL BRANCHES OPEN FROM 9am to 6pm MON TO SAT

OUR CUSTOMER SERVICES DIVISION at head office will answer all your enquiries - just ring 01-200 1321

EXPORT Personal exports arranged for overseas visitors. Goods specially packed insured and despatched to all parts of the world at minimum cost & delivery in 24 Hrs. Payment by bank transfer, certified cheque, postal note or money order in any currency.

BARCLAYCARD & ACCESS

Phone your order to 01-200 1321 or call into any branch

NO DEPOSIT TERMS available on most goods for personal callers

CHEQUES TO THE VALUE OF £30. ACCEPTED FROM PERSONAL SHOPPERS WITH BARBERS CARD. IN OTHER CASES AND FOR AMOUNTS IN EXCESS OF £30. PLEASE ALLOW TIME FOR CLEARANCE. BANKERS DRAFTS ACCEPTED.

All prices correct at 2/8/75 but subject to change without notice E.&O.E.

A member of the Audiotronic Group of Companies

12 inch MODELS

T12/35 Rated Power 35 WATTS

Centre Pole Diam. 1 1/2" Imp. 8-15Ω
Twin Cone. Range: 50-17000Hz
Ceramic Magnet
Weight: 600 Gms


Rec. Price **£13.00**



T12/60 Rated Power 60 WATTS

Centre Pole Diam. 2" Imp. 8-15Ω
Range: 60-9000Hz
Ceramic Magnet
Weight 1150 Gms.


Rec. Price **£20.00**

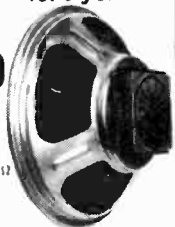

T12/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp 8-15Ω
Range: 40-5000Hz
Ceramic Magnet
Weight: 1250 Gms

Rec. Price **£39.00**

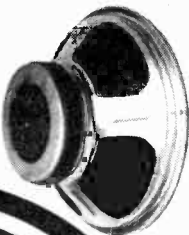

Power Ratings
R.M.S.
Continuous

All Rec. Prices inc. VAT

15 inch MODELS

T15/70 Rated Power 70 WATTS

Centre Pole Diam. 2" Imp 8-15Ω
Ceramic Magnet
Weight: 1150 Gms
Range: 50-4000Hz

Rec. Price **£27.00**



T15/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp. 8-15Ω
Ceramic Magnet
Weight: 1250 Gms.
Range: 50-4000Hz

Rec. Price **£44.00**




18 inch MODEL

T18/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp. 8-15Ω
Ceramic Magnet
Weight: 1250 Gms.
Range: 35-4000Hz

Rec. Price **£49.00**

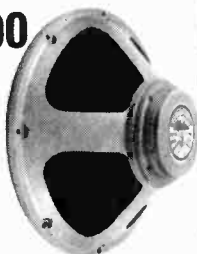

Wholesale, Retail and Export enquiries to Sole Distributors:-

AUDIO EQUIPMENT LTD.
102 Henconner Lane, Leeds 13

S.A.E. please for trade terms or leaflet

Guaranteed for 5 years

Guaranteed for 5 years

PC ETCHING KIT MKII

Contains 1lb Ferric Chloride, 100 sq ins copper clad board, D.A.L.O. etch resist pen, abrasive cleaner, etching dish and instructions. Also included are 2 small drills £3.50.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb 99p, 3lb £1.80, 10lb £4.65, 100lb £35.

COMPUTER PANELS

Large quantity always available. 3lb assorted £1.60, 7lb £2.45, 58lb £15. Pack with about 500 components Inc at least 50 transistors 1c, Pack with 10 200V 1A SCR's + 120 other parts £1.10, Pack with 18 2N2369 etc 80p.

71b BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, pots, switches, PC boards with transistors & diodes, also loads of odds and ends. Contents always changing £3.00.

POWER SUPPLY UNIT

G101: Mains transformer, 2A thermal cut-out, bridge rect, will give 1.7 to 10.5V output with 2 extra capacitors (provided). With data £1.30.

8 PIN DIL 741's

10+ 30p; 25+ 26p; 100+ 24p; 250+ 23p

555 TIMERS

3+ 89p; 10+ 57p; 25+ 53p; 100+ 49p

2N3055's—FULL SPEC

10+ 40p; 25+ 37p; 100+ 35p

All prices quoted include UK post and VAT at 8% or 25% as appropriate. SAE list.

GREENWELD (PW7)

51 Shirley Park Road
Southampton, SO1 4FX.
Tel: (0703) 772501.
Also callers at 21 Deptford Bdy SE8
01-692 2009, & 38 Lower Addiscombe Rd, Croydon 01-688 2950.

BARGAIN PACKS

12 BC107	£1.20	25 1N4001	£1.20
14 BC108	£1.20	22 1N4002	£1.20
12 BC109	£1.20	20 1N4003	£1.20
15 BC148	£1.20	18 1N4004	£1.20
13 BC149	£1.20	16 1N4005	£1.20
12 BC157	£1.20	14 1N4006	£1.20
12 BC158	£1.20	12 1N4007	£1.20
12 BC159	£1.20	40 1N4148	£1.20
2 2N2646	£1.20	3 2N3055	£1.20
10 BC328	£1.20	12 BC548	£1.20
12 BF194	£1.20	12 BF195	£1.20
7 BF173	£1.20	5 BF181	£1.20

TRANSFORMERS

All Mains Primary, 6.0-6V @ 100mA
85p; 9.0-9V 90p; 12.0-12V 95p; 6.5-0-6.5 @ 500mA £1.50; 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V @ 1A. also 12.0-12 or 15.0-15V £2.70; 2A version £3.90.

RESISTORS & CAPACITORS

400 asstd carbon resistors £1.50
250 Hi-stabs, 1, 2 & 5% £1.40; 100 wirewounds, 2-15W £2.00 200 poly, 0.25 ceramic etc caps £1.15; 100 C280 polyesters, -01-47µF £1.30; 200 miniature electrolytics, but mostly unmarked, so only £1.50.

7 SEGMENT LEDS

standard DIL package, 0-33 4 for £3.40, 6 for £5.20

VEROBOARD

100 sq ins, about 8 pieces asstd sizes and pitches. £1.15

MISCELLANEOUS

9 pole 6 way Yaxley switches 50p; SPCO 5A microswitch 12p; 15 asstd pots 75p; 15 asstd trimmers £1; Plug In relay, 2500Ω 4c/o 25p; Crystal mic Insert 40p; 4 x 80V 10A rects on heat sink, ideal batt. charger £1.20; SN76680N 80p. Good range of close tolerance resistors—SAE List.

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Tag Strips, Coil Formers, Wire, Grommets, Magnets, Transistor Panels, etc. Save yourself £'s on these well selected parcels, 6lb net weight £1.00, p.p. 70p.

Brand New Wire-wound Resistors 1-7 watts, mostly Plessey GWS-1.3-5-7. Good selection. 100 for £1.00, p.p. 35p.

Mullard Ferrite Cores LA3 50p, LA4 75p, LA2100 50p.

SPECIAL OFFER. Metallised Polyester Capacitors by Erie, Mullard, etc. Values include -01/160V, -01/250V, -015/160V, -022/160, -033/160, -047/160V, -068/160V, -1/160-250V, -22/160V, etc. This is a bargain not to be missed. 100 for £1.50, p.p. 35p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene, Tremendously good selection. 300 for £1, p.p. 35p.

Please add 25% V.A.T. to total amount

Mail Order Only.


XEROZA RADIO,

1, EAST STREET, BISHOPS TAWTON, DEVON.

Hi-Fi SPEAKER OFFER

BOOKSHELF SPEAKERS HALF PRICE AT ALMOST

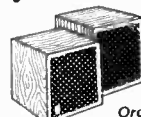- Neat, compact size - 6 1/2" cube
- Ideal for stereo or quadrophonic systems
- Big performance over 10 watts RMS
- Frequency response from 50 Hz to 18 kHz
- Real teak or walnut finish



LIMITED NUMBER ONLY


£17.50
per pair inc. p&p

Order now while stocks last - Send P.O. or cheque to:

C.A.P.A. Group Ltd, Dept pw1, 9c High St, Bramley, Guildford, Surrey.



PRINTED CIRCUIT BOARD TRANSFER SYSTEMS

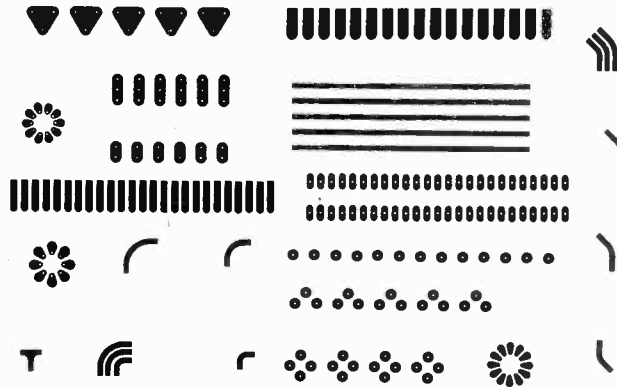

Acid resistant transfers for direct application to P.C. Board. This is a new approach to printed circuit board manufacture, giving a professional finish with all details that an electronics engineer would require, including all drilling positions automatically marked.

Ideal for single unit boards or small quantities. All at a very low cost—for example an average 6" x 4" layout would cost less than 30p, and the time taken under one hour, including etching to complete.

The system is simple, briefly it consists of 10 sheets of self adhesive acid resistant transfers made in required shapes—i.e. edge connectors, lines, pads, dual in line I.C.'s, 8-10-12, T.O.5 Cans, 3-4 lead transistors, etc., etc., which only require pressing into the required positions on the printed circuit board before etching.

The printed circuit transfer system is a genuine offer to the public and industry. A full money back guarantee is sent with each order, trade prices on application.

List of Prices

Complete system including post and VAT	£2.50
Sample sheet	25p

Printed circuit board PCB transfer systems patent applied for.

P.M.S. NAMEPLATES, BROOK STREET, HIGHER HILLGATE, STOCKPORT, CHESHIRE

TELEPHONE NUMBER : 061-480-0959

Don't miss your copy of

HENRY'S NEW 1975 CATALOGUE

only
50p
Plus 15p
P&P



- ★ OVER 5,000 ITEMS — largest UK range of electronic components for home constructors.
- ★ 200 PAGES — every aspect of electronics and components for amateurs and hobbyists — kits, projects, test gear.
- ★ DOZENS of new lines and new ranges.
- ★ MANY price reductions throughout the new Catalogue.
- ★ A Discount Voucher with every copy, worth 50p.

FREE TO EDUCATIONAL ESTABLISHMENTS when ordered on official notepaper.

Write now for your copy, enclosing 65p remittance.

Now Open Supermarket,
Browse Round The New
Supermarket at 404 Edgware
Road.
ALL PRICES INCLUSIVE OF VAT

HENRY'S

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA Discoo-lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW
Prices correct at time of preparation. Subject to change without notice. © G O E

Hi-Fi and
Electronics
Centres Open
9 am - 6 pm

ELECTRONIC FOOTBALL & TENNIS WITH THE FABULOUS VIDEO SPORT

Play three exciting electronic ball games FOOTBALL, TENNIS, HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.

OUR INCREDIBLE PRICE £35.00 DEMONSTRATIONS NOW IN ALL HI FI CENTRES!

NEW SPECIAL PURCHASE

Mullard type LP1179 and LP1171 AM/FM tuner modules
These two modules together form a high quality AM/FM tuner covering the long, medium and VHF broadcast bands. Requires only 16 resistors and capacitors and a switch to complete. Supplied with circuits and spec. data.
LP1179
FM Coverage 87-108 MHz
Bandwidth 300 KHz
Audio output 75mV with built in tuning gang
LP1171
UK Coverage mW-1W
Supply 6V negative earth
LP1179 and LP1171 £4.60 each or £8.63 pr. Suitable Ferrite aerial £4.60 ea. or £8.63 pr.

UHF TV TUNERS

625 line receiver UHF transistorised tuners UK operation.
Brand new. (Post/packing 25p each).
TYPE A var. tun. slow motion drive £3.50.
TYPE C variable tuning £2.90.
TYPE B 4-button push button (adj.) £4.60.
TYPE D 6-button UHF/VHF tuner £5.15.

You can build the Texan and Stereo FM Tuner
TEXAN 20 — 20 WATT IC STEREO AMPLIFIERS

Features glass fibre P.C. board, Gardners low field transformer 6-11 2's, 10-transistors plus diodes etc. Designed by Texas instruments engineers for Henry's and P.W.1972. Overall size 15 1/2" x 2 1/2" x 6 1/2" mains operated. Free teak sleeve with every kit.
£38.75 (CARRIAGE 50p.).
(also built and tested £46.87).

HENELEC STEREO FM TUNER
Features capacity diode tuning, head and tuning meter indicators, mains operated. High performance and sensitivity.
Overall size in teak sleeve 11" x 2 1/2" x 6 1/2".
Complete kit with teak sleeve.
£26.25 (Carriage 50p.).
(also built and tested £31.20).

JOIN THE LARGE BAND OF CONSTRUCTORS!

FREE: SEND NOW FOR OUR FREE LIST NO. 36 FOR OUR COMPLETE RANGE OF OVER 10,000 SEMI-CONDUCTOR DEVICES AT NEW LOW PRICES.

EXTRA DISCOUNTS
Semiconductors—Any one type or mixed
SN74 Series 'IC' 12-extra 10%; 25-extra 15%; 100-extra 20%.

TRANSISTORS & INTEGRATE D/I/C's
TTL "7400 series" IC's from 18p each
Cosmos "4000 series" IC's from 2 1/2p each
Linear Op-Amps from 43p each
Signetics Phase Lock IC's; RCA Linear IC's; TO3 Power Devices in PNP and NPN; BC107 and "BC range" from 13p ea each
Range of OC Types 20p
Plastic Power Devices, Rectifiers, Zener, Power Regulator IC's and many others.
Diodes up to 10 watts.

Wire Wound Resistors. Our selection of mixed values. 30 for £1.40, 100 for £3.50.

Audio Amplifier Module. Mullard LPI 73, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2.30 + post.

Ferguson Stereogram chassis Model 3357, all transistor, medium long, VHF/FM, 3 watts per channel S/M, with connection data, less tuning scale, £18.00. Post paid.

Crystals HC6U: 52.03333 MHz: 52.02500: 52.01667: 51.58667: 51.58330: 37.78250: 37.75000: 12.895.8: 12.891.8: 12.700.0: 9.456.25: 9.455.55: 9.533.33: 9.531.94: 9.530.55: 9.090.62: 9.087.5 50p each.

Electrolytics. 32/32/32µF, 325v. 2" x 1 1/2" 35p: 80µF 150v 1 1/2" x 1" 20p: 2000µF 30v, 2 1/2" x 1" 25p: 2000µF 35v 3" x 1" 30p: 470µF 100v 3" x 1 1/2" 25p: 2000µF 25v 2" x 1 1/2" 35p: 700µF 200v 3 1/2" x 1 1/2" 30p: 16/16µF 275v 1 1/2" x 1" 20p: 40/40/20µF 275v 3" x 1" 20p: 4500/900/900µF 30v 2 1/2" x 1 1/2" 50p: 2500µF 40v 2 1/2" x 1 1/2" 40p: 470µF 25v 1 1/2" x 1 1/2" 15p: 4,000µF 25v 3" x 1 1/2" 40p. 32µF 450v 1 1/2" x 1" 30p: 8µF/16µF 450v 1 1/2" x 1 1/2" 30p: 1000µF 12v 1 1/2" x 1 1/2" 15p.

Try our parcel of small capacitors 20 mixed valves £1.50 + post.

Matched pair of bookshelf speakers. Teak finish, size 12" x 8" x 5". 8 x 5 ohms ceramic, 5 watts RMS. Complete with tin leads. £10.00 pair + post.

Thorn TV IF chassis, 950 series (less valves). £1.00 + post.

UHF 625 transistor push button tuner (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, circuit diagram supplied £3.00 + post.

P-C Boards (not computer panels) 1 off 6 transistor single wave band. 1 off 4 transistor audio. 1 off 3 transistor £1.40 + post, three boards.

Repanco Transformers AF1, AF2, TT45, 46, 47, 49, 53. 20p each + post.

L/M, M/W, VHF Tuner 5 transistor in kit form, complete with full assembly instructions. 9v supply, positive earth. O/p out 100mw. Built-in A.M. aerial. 88-108 Mcs. £5.25 + post.

Stereo Decoder using MC1310. Fully assembled, can be used with our tuner kit. With data. £3.90 + post.

Mains Droppers, 10 mixed values, £1.00 + post.

Edgewise Level meters, 200µA, size 3" over all. 50p + post.

Chrome Plastic knobs, 3 types, 4 off each with spring clip. £1.25 + post.

Aluminium Chassis, 7 1/2" x 5 1/2" x 2 1/2" 85p + post; 10" x 7 1/2" x 2 1/2" 75p + post. 11" x 7 1/2" x 2 1/2" 85p + post.

BSR P12n, similar to HT70 single play, with heavy die cast turntable, less cartridge, £10.00 + post.

Ferguson Stereogram Chassis, MW/LW/VHF with tuning scale (5+5 watts sine wave) 15 ohms £26.25. Post paid 15 ASSORTED SWITCHES £1.90 + post. 50-3 way to 7 way TAG STRIPS, £1.15 + post, ALMA REED RELAY TYPE DRH. 3 VOLTS 50p + post.

REPANCO & DENCO COILS, NEW/BOXED OUR SELECTION—5 FOR £1.15 + post. Please add 10% post and packing. Add 25% VAT to total order. Gram Chassis free postage. No goods despatched outside U.K.

SURPLECTRONICS
216 LEAGRAVE ROAD,
LUTON, LU3 1JD, BEDS.

4-STATION INTERCOM



£16.15

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/Off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. 65p.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £25.91 + VAT £5.74 per pair P. & P. 75p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £11.95 + VAT 9p

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £12.95 + VAT £1.04 P. & P. 85p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (EE6)
189 KENSINGTON HIGH STREET, LONDON, W8

RECHARGEABLE BATTERIES

CAN SAVE YOU A FORTUNE!
Bush & Meissner's two purpose-built battery chargers for economy minded enthusiasts:

The "KESTREL-DOWN" Charger .. £11.31 for Alkaline rechargeable batteries, no-load voltage of 1.5-volts per cell, for the following sizes ALKALINE (All prices ex-VAT)

Equivalent to	Type	Capacity	PRICE
U2 size	SA-13D	2Ah	£1.73
U11 size	SA-14C	1Ah	£1.13
U7 size (pencil)	SA-15AA	0.3Ah	£0.56p

NICKEL-CADMIUM (All prices ex-VAT)
The "DAIMON" Charger .. £9.76 for Nickel-Cadmium batteries, no-load voltage of 1.25 volts per cell, for the following sizes:

Type	Capacity	PRICE
NCC400	4Ah	£3.64
NCC200	2Ah	£2.48
NCC50	0.5Ah	£1.45

Charger designed to give optimum results with a specific type of cell. Never be without power, day or night.

*Note, under no circumstances must Alkaline batteries be used with the Daimon charger.

S.A.E. brings full details

Bush & Meissner

Importers & Distributors
Dept LS260
275 West End Lane,
London NW6 1QS
01-794-9611

NEW SINCLAIR IC20
10+10 Watt stereo amplifier kit with free 16 page booklet and printed circuit £6.99 (82p)
PZ20 power supply kit for above £4.45 (66p)
VP20 stereo volume, tone control and preamp kit £4.95 (72p)

AMPLIFIER KITS
SEND SAE FOR FREE DATA BOOKLET

SINCLAIR CALCULATORS AND MULTIMETERS

Sinclair Digital Multimeter DM2 £58.95 (£26)
Scientific calculator assembled £15.63 (£1.57)
Cambridge Calculator assembled £10.07 (£1.13)
Cambridge Memory Assembled £13.96 (£1.44)
Oxford £100 £10.50 (£1.20). Oxford 200 £15.95 (£1.70). Oxford 300 £23.95 (£2.40)

CALCULATOR POWER SUPPLIES
Mains adaptor for the Oxford series £2.65 (54p)
Mains power supply unit for the Sinclair Cambridge, Cambridge Memory and Scientific Calculators £3.30 (65p).

FERRANTI ZN414
IC radio chip with data £1.20 (25p). Also available kit of extra parts to complete a radio £2.55 (47p)
Send sae for free leaflet

SINCLAIR PROJECT 80
Stereo 80/2 Z40/PZ £24.48 (£2.40)
Stereo 80/2 Z40/PZ £26.70 (£2.67)
Stereo 80/2 Z60/PZ £28.66 (£2.87)
AFU £6.38 (78p)
Z40 £4.87 (68p)
Z60 £6.38 (78p)
Q16 £6.70 (95p)
PZ5 £4.42 (73p)
PZ6 £7.41 (94p)
PZ8 £7.25 (90p)
Decoder £7.46 (89p). Trans for PZ8 £3.75 (70p).
Tuner £11.43 (£1.42). Stereo 80 £11.43 (£1.42).
Project 805 £29.95 (£3). Project 805SQ £33.95 (£3.30) Project 80 SQ Quad Decoder £15.95 (£1.25)

SINCLAIR SUPER IC12
6 Watt IC power amp and preamp. With 44 page booklet and printed circuit £2.30 (43p)

DELUXE KIT FOR THE IC12
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.80 (31p). Stereo model with balance control £3.90 (49p)

IC12 POWER KIT
Supplies 28V 0.5 Amps £3.27 (62p)

PREAMP KITS FOR THE IC12
Type 1 for magnetic pickups, mics and tuners. Mono model £1.50 (30p). Stereo model £2.70 (35p). Type 2 for ceramic or crystal pickups. Mono 80p (23p). Stereo £1.60 (30p)

SEND SAE FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAINS
The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7, 9 and 12V at 500 mA £3.90 (80p).
Other eliminators stocked—
250mA:—3 way switched model giving 6, 7 1/2 and 9V £2.50 (65p).
50mA:— 4 1/2V £2.40 (40p). 6V £2.40 (40p). 9V £2.40 (40p). 7 1/2V cassette type £2.80 (50p). Double 4 1/2V + 4 1/2V £2.95 (50p). 6V + 6V £2.95 (50p). 9V + 9V £2.95 (50p).
500mA:— Heavy duty deluxe models 6V £3.30 (65p). 7 1/2V £3.30 (65p). 9V £3.30 (65p)

S-DECS AND T-DECS
S-DeC £1.98 (36p)
T-DeC £3.63 (52p)
µ-DeC A £3.99 (56p)
µ-DeC B £6.99 (86p)
IC carriers:—
16 pin: plain 81p (18p).
With socket £1.77 (28p).
10 TO5: plain 76p (18p). With socket £1.68 (27p)

SWANLEY ELECTRONICS
PO BOX 68, SWANLEY, KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover post and 8% VAT., then multiply total by 1.16 (except for calculators and S and T-DeC range) to allow for luxury VAT rate.

MAINS TRANSFORMERS

All models 230-250 volt primaries	amps	price
1V	1 amp (special)	1.75
2-4v	5 amp	85
6-3v	2 amp	1.00
6-3v	3 amp	1.50
9v	1 amp	95
9v	3.5 amp	1.95
12v	1 amp	1.00
12v	2 amp	1.50
6.5v-0-6.5v	1 amp	1.35
18v	1 amp	1.25
20v	1 amp	1.00
24v	1 amp	1.50
24v	3 amp	3.50
12-0-12v	50mA	1.20
6-0-6v	50mA	1.20
8-0-8v	1/2 amp	1.25
18-0-18v	2 amp	3.50
25v	1 1/2 amp	1.95
50v 2 amp & 6.3v 1 amp		5.50
60v 5 amp & 5v 1 amp		7.50
27v	8 amp	4.50
30v	37 amp	22.00
80v tapped 75v & 70v	4 amp	5.50
230v-60mA & 6.3v	1.5 amps	1.75
275-0-275v at 90mA & 6.4v	3 amps	2.25

Charger Transformers	amps	price
6v and 12v	2 amps	1.25
6v and 12v	3 amps	2.25
6v and 12v	5 amps	3.50
EHT Transformer 5Kv at 23mA (intermittent)		5.50

NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac NX11 Price 99¢ each, 10 for \$9

OIL PUMP

Driven by Redmond Motor of approx. 1/20th horse power, pump originally intended for oil-fired boilers etc, with normal inlet and outlet pipes and unions. \$2.15 plus 30p post and insurance.

LIGHT DIMMER KIT

For dimming up to 250w without heat sink or 750w with heat sink. This comprises quadric variable control potentiometer, condenser, resistors, tag strip for mounting and data. Price \$1.50.

RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable for closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and rectifier. \$2p each.

AM/FM TUNER

Unit made by the American GEC company, 8 transistor, all-wired ready to work. Complete with tuner condenser, needs only scale and pointer. Tunes AM range 540 to 1620 KHz. FM range 88 to 108 MHz. Switches for on-off and AFC. Output for MXP or direct. Special slip price \$5 plus 30p post. Three or more post free.

7 WATT STEREO AMPLIFIER

Again by the American GEC company. This has exceptionally good tone quality. Is complete with pre-amp and treble base volume and balance controls. Also has mains smoothing circuit and rectifiers so requires only mains transformer. Output for 15 ohm speakers. Inputs for tuner, pick-up, mike, etc. Special slip price \$6 plus 30p post. Three or more post free.

WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to home. \$2.75.

PORTABLE CABINET OFFER

A nicely made portable cabinet, soft padded black finish intended for portable stereo system. Dimensions as sketch. With motor board cut out for Garrard SP 25. This was obviously a very costly cabinet originally made for a de-luxe record player. Offered at \$1.95 plus \$1 carriage free if bought with the Garrard or BSR record decks.

CAR CASSETTE POWER SUPPLY

To give stabilized output of 6 or 9v, complete kit contains 2 transistors—zener diode—zero board panel resistors and plastic case to house it with constructional data. \$2.50.

PLAY YOUR 8-TRACK CASSETTE FROM MAINS

12v, 700mA unit all assembled and in neat plastic case with mains lead and terminals, full wave rectifier and transformer has overload protection and is double insulated. One of today's best buys at \$2.80 + 35p VAT.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated to equal divisions for switch-setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips, thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. None of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting, animated and signs, Signalling, etc. Price from makers probably over £20 each. Special slip price \$2.50 plus 25p post and insurance. Don't miss this terrific bargain.

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in x 18in \$1.80 18in x 0in \$1.50

HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:

Programme	Hot Water	Central Heating
	Off	Off
1	Twice Daily	Twice Daily
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously

Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact, there is no limit to the versatility of this Programmer. Mains operated. Size 3in x 3in x 2in deep. Price \$4.35 as illustrated but less case.

TAPE DECK

In metal case with carrying handle, heavy fly wheel and capstan drive. Tape speed 31. Mains operated on metal platform with tape head and guide. Not new but in good order. Price \$1.95 plus \$1 post and insurance.

SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19.25-31.39 metre bands—Kit contains chassis front panel and all the parts. \$1.25—crystal earphone 50p.

SPIT MOTOR

200-250V induction motor, driving a Carter gearbox with a 1 1/2" output drive shaft running at 5 revs per min. Intended for roasting chickens, also for driving models—windmills, coloured disc lighting effects, etc. \$2.50 plus 20p post and ins.

INFRA-RED BINOCULARS

Made for military purposes during and immediately after last war to enable snipers, vehicle drivers, etc. to see in the dark. The binoculars have to be fed from a high voltage source (5KV approx.) and providing the objects are in the rays of an infra-red beam, then the binoculars will enable these objects to be seen. Each binocular eye tube contains a complete optical lens system as well as the infra-red cell, technical data on which is available. The binoculars are unused, believed to be in good working order. In fact they were never issued and are still in original cases, but since they were made a long time ago, they can hardly be called new. Sold without guarantee. Price \$16.50 per set + \$1 carriage.

12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price \$2.50 plus 30p post & packing.

HEAVY DUTY MAINS POWER PACK

Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 8 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price \$8.75 plus \$1.00 post.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. \$2.75 plus 25p P. & P.

RADIO STETHOSCOPE

Easiest way to find traces-signal from aerial to speaker, when signal stops—where found the fault. Use it on Radio, TV, amplifier, anything. Complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. \$2.80 twin stetho-set instead of earpiece \$3p extra post and ins. 20p.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quick running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering, etc. etc. A real bargain at \$2.50p.

TERMS:—ADD 8% V.A.T. Except where noted
Send postage where quoted—other items, post free
If order for these items is £6.00, otherwise add 30p.

J. BULL (ELECTRICAL) LTD.
(Dept. P.W.), 102/3 TAMWORTH RD.,
CROYDON CRO IX.

NEW ITEMS THIS MONTH

The bargains in this column are just some of the items which appeared in the April supplement of our catalogue. You can receive this catalogue and the next 12 supplements by sending \$1.

Pre-recorded tapes. Those of you who had our selection of ten tapes last month may wish to order selection 50 which is 50 more reel to reel pre-recorded tapes, new in perspex type storage box, different titles, classical and light music. Our assortment £28 the lot post paid.

50v amplifier transformer made by Parmeko so obviously very well-made, 2 amp, upright mounting with shrouds, a transformer that will enhance the performance of any amplifier. Offered at only \$4.50 + 75p post—less than current cost.

3 core waterproof flux, standard pvc, circular, new colour code, 100 metre drums, 25 per drum + 50p post.

Tachometer motor/generator made by the famous Mullhead Co., when driven at 1,000 revs, the voltage generated is exactly 3. At higher or lower revs, proportionately higher or lower voltages result. The motor therefore is the basis of a very useful general purpose revolution counter. Price \$1.50 each.

DC high current panel meters, 3 1/2" wound wide angle 240° movement meters, with mounting lips for flush mounting fitted with external shunts, made by Crompton Parkinson or similar high quality inaker for the GPO but brand new, still in maker's cartons. These are a real bargain at \$5.50 each. Reasonable quantities available in the following ranges:
0-10 amps 0-20 amps 0-30 amps 0-40 amps 0-50
0-100 amps 0-100 amps 0-200 amps.

50 amp fuses, cartridge type, mounted in plug-in fuse carrier with panel mounting fuse holder. Price 50p each. 100 amp ditto, price 85p each. Post 25p each.

100 amp 50 volt silicon rectifier on heat sink for panel mounting. \$3.50.

Miniature plug-in uni-selector switches made for the GPO, unused, perfect condition. 50v coil 360° rotation 4 pole 25 watt. \$2.50.

Edge mounting moving coil meter, size 3" x 2 1/2" scaled dB made for the GPO, unused still in original maker's cartons. \$2.50 each.

Frequency changing unit. This is another ex GPO item. We do not quite know for what purpose it could be used, but it is designed to change the frequency from 50 cps to 100 cps, output being 75v at 15mA 100 cps. A well-made piece of equipment fitted with mains transformers and rectifiers. A few only at \$5 each plus \$1 post.

GPO switchboard. We have an assortment of these, the old fashioned type with the winking eyes and lever switches, all mounted in wooden box. Price depends on number of lines, for instance the 8 line 40 extension model is \$25.

Highly sensitive moving coil relay, panel mounting with glass window, this needed approx 6 1/2" x 4" x 5" the actual triggering current can be varied from a fraction of a milliamp to 5 milliamperes by removing the front and adjusting the setting level. Few only of these, price \$5 each.

100 amp contactors, with auxiliary microswitch, coil voltage 50 volts DC. Price \$3.50 each.

Ditto, mounted in a pair with optional selector bar which prevents both contactors closing together; enclosed in perspex cover. Price \$7 each.

Figure of eight twin flex wire, 14 strands, suitable for lighting or loadspeaker extension etc. Price \$3 per 100 metre coil + post 50p.

Miniature multi-core wire, colour coded cores, 15 core screened overall, then pvc covered. 30p per metre. \$26 per 100 metre coil, post 50p.

Mains motor 1 1/2" stack induction type, 1 1/2" spindle of 1 1/2" length, special quiet bearings made by Smiths for fans and blowers etc. \$1.25 each, post 20p.

13" x 8" Speakers, E.M.F. good performance 5 watt, mid range unit, very suitable for columns etc., these are 8 ohm coil. We can offer at approx. half price—only \$1.95 each plus 50p each post.

Klaxon hooper mains operated, makes loud, shrill noise, ideal as fire alarm. Well-made unit. \$2.50 + 50p post.

7 watt amplifier, made in Ireland to American GEC specification, exceptionally good tone, on one panel with all controls and complete with rectifiers and smoothing condenser so requires only mains transformer. Price \$5 + 40p post.

AM/FM tuning unit 8 transistor, made by the previous named company complete with tuning condenser but needs scale and pointer. \$5, no extra for postage if ordered with amplifier, otherwise add 50p.


White ex GPO telephones, last standard desk model with internal bell and dial. \$2.3 + 75p post.

Black, ditto, \$1.50 + 75p.

Black, ditto, less internal bell. \$1 + 50p.

Wall mounting with switched hook but not dial or bell. \$1.40 + 50p.

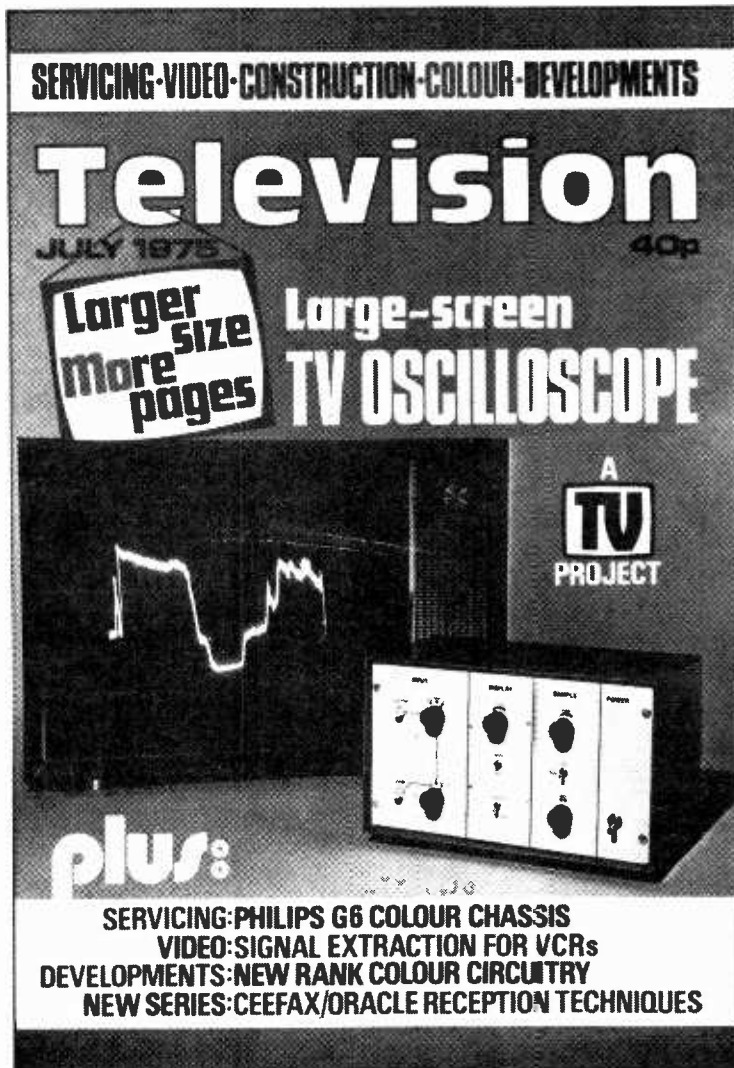WATCH OUR Television NOW IT'S BIGGER & BETTER More pages! Larger size! Extra features!



Special Features this month:

LARGE SCREEN TV OSCILLOSCOPE

How a large-screen monochrome receiver can be converted for displaying television waveforms.

CEEFAX/ORACLE RECEPTION

Start of a new series explaining the principles and the practical techniques used for teletext news displays.

LATEST COLOUR RECEIVER CIRCUITRY

An account of the many novel circuit techniques used in the latest Rank colour chassis.

VIDEO SIGNAL EXTRACTION

Many VCRs require a v.f. input. K. Cummins presents a suitable circuit for extracting the video signal from a domestic TV set.

COLOUR RECEIVER SERVICING

Les Lawry-Johns deals with faults experienced on the Philips G6 colour chassis

PLUS ALL THE REGULAR FEATURES

JULY ISSUE OUT MONDAY 16th JUNE, PRICE 40p

Marshall's

A. Marshall & Son (London) Limited Dept. PW
42 Cr. Churchwood Broadway London NW3 3JD Tel: 01-432 0161
& 85 West Regent Street Glasgow G2 2QD Tel: 041-332 4133

Everything you need is in our new 1975 catalogue. Available now price 25p

Trade and export enquiries welcome

Our range covers over 7,000 items. The largest selection in Britain

Top 200 IC's TTL, CMOS & Linear

CA3018A 85p	CD4043 £1-80	NE565 £4-48	SN7448 90p	SN74157 95p
CA3020A £1-80	CD4044 £1-80	SNL414 £1-80	SN7450 60p	SN74160 £1-10
CA3028A 79p	CD4045 £2-65	SL610C £1-70	SN7451 16p	SN74161 £1-10
CA3035 £1-37	CD4046 £2-84	SL611C £1-70	SN7453 16p	SN74162 £1-10
CA3046 70p	CD4047 £1-65	SL612C £1-70	SN7454 16p	SN74163 £1-10
CA3048 £2-11	CD4049 81p	SK620C £2-60	SN7460 16p	SN74164 £2-01
CA3052 £1-62	CD4050 66p	SL621C £2-60	SN7470 33p	SN74165 £2-01
CA3089E £1-96	LM301A 48p	SL623C £4-59	SN7472 26p	SN74167 £4-10
CA3090Q £4-23	LM308 £2-50	SL640C £3-10	SN7473 36p	SN74174 £1-25
CD4000 36p	L005TL £1-50	SN7400 16p	SN7474 36p	SN74175 90p
CD4001 36p	LM380 £1-10	SN7401 16p	SN7475 50p	SN74176 £1-44
CD4002 36p	LM381 £2-20	SN7401AN 38p	SN7476 35p	SN74180 £1-40
CD4006 £1-58	LM702C 75p	SN7402 16p	SN7480 50p	SN74181 £1-95
CD4007 36p	LM709 38p	SN7403 16p	SN7481 £1-25	SN74192 £1-15
CD4008 £1-63	8DILL 45p	SN7404 19p	SN7482 75p	SN74199 £2-30
CD4009 £1-18	14DILL 40p	SN7405 19p	SN7483 95p	SN74191 £2-30
CD4010 £1-18	LM710 47p	SN7406 45p	SN7484 95p	SN74192 £1-15
CD4011 36p	LM723C 90p	SN7407 45p	SN7485 £1-25	SN74193 £1-15
CD4012 36p	LM741C 40p	SN7408 19p	SN7486 32p	SN74196 £1-60
CD4013 66p	LM749 40p	SN7409 35p	SN7489 45p	SN74197 £1-58
CD4014 £1-72	14DILL £1-72	SN7410 16p	SN7491 85p	SN74198 £2-25
CD4015 £1-72	LM747 £1-05	SN7411 25p	SN7492 45p	SN74199 £2-25
CD4016 66p	LM748 60p	SN7412 25p	SN7493 45p	SN76033NE £2.92
CD4017 £1-72	14DILL 73p	SN7413 35p	SN7494 82p	SN76033NE £1.95
CD4018 £2-55	LM3900 70p	SN7416 35p	SN7495 73p	SN760233N £1.60
CD4019 86p	LM7805 £2-00	SN7417 35p	SN7496 75p	SN76033NE £2.92
CD4020 £1-91	LM7812 £2-50	SN7420 29p	SN74100 £1-25	TAA363 £1-70
CD4021 £1-72	LM7815 £2-50	SN7423 29p	SN74107 36p	TAA363 £1-70
CD4022 £1-66	LM7824 £2-50	SN7425 29p	SN74118 £1-00	TAA300 £1-80
CD4023 36p	MC1303L £1-50	SN7427 29p	SN74119 £1-91	TAA350A £2-10
CD4024 £1-24	MC1318P £2-59	SN7430 16p	SN74121 37p	TAA611C £2-18
CD4025 32p	MC1330P 90p	SN7432 28p	SN74122 50p	TA A621 £2-03
CD4027 43p	MC1351P 80p	SN7437 35p	SN74123 60p	TA A661B £1-32
CD4028 £1-50	MC1352P 80p	SN7438 35p	SN74141 85p	TA B641B £2-25
CD4029 £3-50	MC1466L £3-50	SN7440 16p	SN74145 90p	TBA651 £1-69
CD4030 87p	MC1469L £2-75	SN7441AN 85p	SN74150 £1-30	TBA800 £1-40
CD4031 £5-19	NE555V 70p	SN7442 65p	SN74151 85p	TBA810 £1-40
CD4037 £1-89	NE566 £1-30	SN7446 95p	SN84152 85p	TBA820 £1-40
CD4041 £1-86	NE560 £4-48	SN7447 95p	SN84154 £1-30	TBA820 £1-15

PW TELENNIS KIT £42.50 + VAT Reprint 75p
TRY OUR GLASGOW SHOP

POPULAR SEMICONDUCTORS

2N696 22p	2N3906 27p	AF139 65p	BD139 71p	MPSA56 31p
2N697 16p	2N4037 42p	AF239 65p	BD140 87p	OC28 76p
2N698 82p	2N4036 67p	AF240 90p	BF115 36p	OC35 60p
2N699 94p	2N4058 18p	AF279 70p	BF117 55p	OC42 50p
2N706 19p	2N4062 15p	AF380 79p	BF154 20p	OC45 32p
2N708 17p	2N4259 15p	BF102 £1-00	BF159 27p	TIP29A 49p
2N916 28p	2N4920 £1-10	BC107 14p	BF180 35p	TIP29C 58p
2N918 32p	2N4921 83p	BC108 14p	BF181 36p	TIP31A 62p
2N1302 18p	2N4923 £1-00	BC109 14p	BF184 30p	TIP32A 74p
2N1304 26p	2N5245 47p	BC147B 14p	BF194 12p	TIP33A £1-01
2N1306 31p	2N5294 48p	BC148B 15p	BF195 12p	TIP34A £1-51
2N1308 17p	2N5329 48p	BC194 15p	BF196 12p	TIP35A 49p
2N1711 45p	2N5457 49p	BC157A 16p	BF197 15p	TIP36A £3-70
2N2102 60p	2N5458 46p	BC158A 16p	BF198 18p	TIP42A £0-90
2N2147 78p	2N5459 49p	BC167B 15p	BF244 21p	TIP295S 98p
2N2148 94p	2N6027 45p	BC168B 15p	BF257 47p	TIP305S 50p
2N218A 23p	3N128 73p	BC169B 15p	BF258 53p	TIS43 28p
2N219A 26p	3N140 £1-00	BC182 12p	BF259 55p	ZTX300 13p
2N2220 25p	3N141 81p	BC182L 12p	BF561 27p	ZTX301 13p
2N2221 18p	3N200 £2-49	BC183 12p	BF598 25p	ZTX500 15p
2N2222 20p	40361 40p	BC183L 12p	BFR39 24p	ZTX501 13p
2N2369 20p	40362 45p	BC184 13p	BFR79 24p	ZTX502 18p
2N2646 55p	40406 44p	BC184L 13p	BFX79 20p	IN914 7p
2N2904 22p	40407 35p	BC212A 16p	BFX30 27p	IN375A 7p
2N2905 25p	40408 50p	BC212LA 16p	BFX84 24p	IN4007 10p
2N2906 19p	40409 52p	BC213LA 15p	BFX85 30p	IN4148 7p
2N2907 22p	40410 52p	BC214LB 18p	BFX88 25p	IN5404 22p
2N2924 20p	40411 £2-00	BC237B 16p	BFY30 23p	IN5408 30p
2N2966 12p	40594 74p	BC238C 16p	BFY51 25p	IRS115 5p
2N3033 25p	40595 80p	BC239C 15p	BFY52 20p	BA102 35p
2N3054 60p	40636 £1-10	BC257A 16p	BRY39 46p	BA145 18p
2N3055 75p	40673 73p	BC258B 16p	ME0402 20p	BA154 12p
2N3391 28p	AC162 20p	BC259B 17p	ME0412 18p	BA155 12p
2N3392 15p	AC127 20p	BC301 34p	ME4102 11p	BB103B 23p
2N3393 15p	AC128 20p	BC307B 17p	ME480 95p	BB104B 45p
2N3440 59p	AC151 27p	BC308A 15p	MJ481 £1-20	BY126 12p
2N3442 £1-40	AC152 49p	BC309C 20p	MJ490 £1-05	BY127 15p
2N3638 15p	AC153 35p	BC327 23p	MJ491 1-45	BYZ11 51p
2N3702 12p	AC176 30p	BC328 22p	MJ295S £1-00	BYZ12 51p
2N3703 13p	AC187A 35p	BCY70 17p	MJE340 48p	OAA47 6p
2N3704 15p	AD188K 68p	BCY71 22p	MJE370 47p	OAA81 16p
2N3706 15p	AD143 35p	BCY72 15p	MJE371 75p	OA90 6p
2N3708 14p	AD161 50p	BD121 £1-00	MJE520 60p	OA91 6p
2N3714 £1-38	AD162 50p	BD123 82p	MJE521 70p	WO21A 20p
2N3716 £1-80	AF106 40p	BD124 67p	MJE295S £1-20	BY164 32p
2N3771 £2-20	AF109 40p	BD131 40p	ME305S 75p	STZdiac 26p
2N3773 £2-65	AF115 35p	BD132 50p	MPB113 47p	40669 £1-00
2N3789 £2-06	AF116 35p	BD135 43p	MPF102 39p	TIC44 29p
2N3819 37p	AF117 35p	BD136 47p	MPSA05 25p	TIC44 29p
2N3820 64p	AF118 35p	BD137 55p	MPSA06 31p	CI06D 65p
2N3904 27p	AF124 30p	BD138 63p	MPSA55 31p	ORP12 60p

Prices correct at June 1975, but all exclusive of VAT. P. & P. 25p.

AIRCRAFT H.F. Rx type R4187 & Control Box these are a crystal controlled Rx intended for remote control and will provide up to 24 channels in the range 2.8 to 18 Mc/s the Rx is a dual conversion type with 2 RF stages, N.B.W I.F. filter, BFO, N.L., O/P stage etc uses 16 B7g type valves, 1st IF 2.15Mc/s 2nd IF 100Kc. Normal power I/P 24 & 19v DC (or 200v HT & 19v DC) crystals required are Hc6/u type not supplied. The Rx is supplied complete with remote control box, circuits notes etc. **£16-20.**
ROLLER COASTER coil 5 x 1 3/4" dia 36 turns silver plated fittings & carbon brush **£3-30.** **CONTAMINATION METER** Geiger counter meter ind. 1 to 10 Mill/R per hour with probe head & G.M. tube complete with mains P.U. in carrying case new **£8** or S/H tested **£6-50.**

U.H.F. WAVEMETER absorption type direct cal 410 to 470 Mc/s with detector needs HT LT & phones **£3-50.**
METER UNIT dual scale as 270 deg 1 Ma & 100-0-100 Ua meter in same case size 3 1/2" sq ex aircraft **£4.** **SONAR INDICATOR UNITS** these are a aircraft unit with 5" sq flat face tube that as dual beam, Blue/Yell trace approx 40 miniature valves, 3 counter dials linked to CRT cursors these req ext H.T. supplies some details available new boxed **£13-50** S/H **£11-50.** **AERIAL SYSTEM** 103 single dipole type Ae for use on 100/150 Mc/s band complete with 36ft of UR67 H.D. 50 ohm coax, mast head fixing etc new in wood case **£5-40.** **INDICATOR UNIT** 266 6" tube unit with VCR97 tube green screen okay

scope use, 18 valves, slow motion dial, tuning conds etc **£9.** **RADIO TELEMETRY UNITS** for use on 200/250 50c/s these are a L.F. Rx on 120Kc will convert to 200Kc, contain 6 valves, Speaker, Tape unit, Coin Box Unit, 2 low speed motors, all in neat case size 14 x 7 x 6" in new cond with circ & mods **£6-50.** **T.V. FILTER UNITS** made to fit in Ae lead fully screened Ali box 4 1/2 x 1 1/2 x 1 1/2" fitted standard coax plug & sk okay for Ae pre amp new.

3 for £1 HEADPHONE MATCHING TRANS & LEAD as high to low res trans with 5ft lead & standard jack plug new **£1.** **CRYSTALS** FT 243 type in range 5.6 to 8.3 Mc/s 5 different for **£1-20.** **A. F. WATTMETERS.** type CT44 by Marconi read up to 6 watts on 2.5 to 5000 ohm loads, large meter, wattage range can be increased with ext load res, tested **£12.** **HEAD & MIKE SETS** for use with 19 set low res mike & phones new **£2-50.** **CRED TYPE 85R** Printing Reporators with 110/220 DC motor good condition **£14.** **DIODES** 800 PIV 750 Ma 12 for **£1**, 100 PIV 3 amps wire ends 4 for **60p** both new.

ROTARY SWTS INST Type 8p 12w 8b & 2p 23w 2b **£1-40** ea, 7p 23w 7b **£1-70** all new. **PHOTOSTAT COPIES OF MANUALS.** R1155A to N,19 set, 62 set, CT38, 13A, R1475, AR88D or LF, all **£2-50.** R107, HRO **£2-70.** TF144G, 88 set **£1-30.** CT316 (CD518) **£2-30**, 31 set **£1-65**, 52 set **£1-20.** CT52/84 **£1-40**, R1392 **£1-50**, CR100 (B28) **£4**, R209 Mk 1, 2 **£1-75**, 1049 Mk 1 **£2-50**, S640 **£1-20**, 730/4 **£2-30**, other available list on request.

Above prices inc. carriage & VAT, SAE for list No. 12 or enquiry. Goods ex equipment unless stated otherwise.

A. H. SUPPLIES

57, MAIN RD., SHEFFIELD. S9 5HL.
Telephone: 444278 (0742)

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 12p per word (minimum 12 words), box number 30p extra. Semi-displayed setting £10.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

Receivers and Components

BRAND NEW COMPONENTS BY RETURN: Electrolytics—16V, 25V, 50V—0.47, 1.0, 2.2, 4.7, 10 mfd.—5p, 22, 47—5 $\frac{1}{2}$ p. (50V—6p) 100—7p. (50V—8p), 220—8p. (50V—10p), 500—11p. (50V—16p), 1000/25V—18p. Subminiature bead-type tantalums—0.1/35V, 0.2/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/6V, 100/3V—11p. Mylar Film 100V.—0.001, 0.002, 0.005, 0.01, 0.02.—3p. 0.04, 0.05—3 $\frac{1}{2}$ p. Mullard tubular polyester 400V E6 series 0.001-0.022—3 $\frac{1}{2}$ p. 0.033-0.1—4 $\frac{1}{2}$ p. Mullard miniature C333 ceramics 63V E12 series 2%, 1.8 pf. 47 pf. 5p. 56 pf. 330 pf.—3 $\frac{1}{2}$ p. Polystyrene 63V E12 series 10 pf. 1.000 pf.—3p. 1200 pf. 10,000 pf.—4p. Miniature Highstab. carbon film resistors $\frac{1}{3}$ W E12 series 5% 1 Ω -10M Ω . (10% over 1M Ω) 1.2p. Postage 10p. Prices VAT Inclusive. The C.R. Supply Co., 127, Chesterfield Road, Sheffield S8.

BULK OFFERS

ALL GOODS FULL SPEC AND MARKED

1N4001 £2.50	BC148 £5.00	BSY95A £8.00
1N4002 £2.30	BC149 £8.00	2N2646 £24.00
1N4003 £3.20	BC157 £6.00	2N3055 £28.00
1N4004 £3.00	BC158 £5.00	NE55V238 £8.00
1N4005 £4.30	BC159 £8.00	709C £18.00
1N4006 £4.70	BC161 £10.00	741C £19.00
1N4007 £5.00	BC267 £8.00	SN76660 £22.00
1N4148 £2.20	BC328 £10.00	
BC107 £7.00	BC548 £8.00	
BC108 £7.00	BF178 £14.00	
BC109 £7.00	BF181 £20.00	
BC116A £8.00	BF194 £8.00	
BC147 £8.00	BF195 £8.00	

All prices per minimum quantity of 100. Out of spec mainly unmarked transistors 2500 £10 Ferric Chloride £30 per 100 lb bags (8% VAT). Miniature mains transformers 100mA sec: 6-6V £5/10; 9-9V £5/10; 12-6V £6/10; subminiature 6-6V 100mA £6/10 400mV Zeners, most voltages, £5/10 Assorted small value capacitors—ceramic, mica, poly, etc., £26/10,000. Assorted C280 polyesters £28/10,000. **MINIMUM ORDER 5% CARR. FREE: Add VAT at the appropriate rate (25%). SAE enquiries.**

JUNIPER ELECTRONICS (PW3)
PO BOX 61, SOUTHAMPTON, SO9 7EE

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

ELECTROLYTICS 5% P DESPATCH BY RETURN

2.2uF, 4.7uF - 63v. 10 uF, 22uF, 47uF, 100uF - 25v.
ALL 8.5p (inc. Vat) + 10p p&p
Discount: 10% on totals over £3, 15% over £8. C.W.O.
SUB SOUND ELECTRONICS, THE SHOP BLACKMORE END, BRAINTREE, ESSEX

MULTI-BAND RADIOS. Grundig Satellit, 13 band, £129; Koyo, marine, aircraft, PSB, FM, SW1, SW2, MW, LW, batt/mains, £44; 4-band, MW, FM, aircraft, PSB, £14. SAE lists. Langtons Radio, High Street, Rochester, Staffordshire. 088 925 388.

CLEARING DISTRIBUTOR STOCKS, transistors, diodes, components, etc. Sample pack 65p incl. postage or send stamp for list. Redhawk Sales Ltd., 10 Maple Lodge Close, Rickmansworth, Herts. Mail Order Only.

Precision Polycarbonate Capacitors

All High Stability - Extremely Low Leakage

440V AC ($\pm 10\%$)	53V Range	1%	±2%	±5%	
0.1uF (11" x 1")	60p	0.47uF	50p	48p	38p
0.25uF (11" x 1")	60p	1.0uF	60p	60p	48p
0.47uF (11" x 1")	71p	2.2uF	80p	85p	65p
0.9uF (11" x 1")	75p	4.7uF	110p	115p	85p
0.98uF (2" x 1")	75p	8.0uF	110p	115p	110p
1.0uF (2" x 1")	81p	10.0uF	120p	120p	110p
2.0uF (2" x 1")	11.22	10.0uF	120p	125p	110p

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 8.0uF at 16V/25V or 35V; 10.0uF at 18V/20V or 25V; 22.0uF at 6V/10V or 16V; 33.0uF at 6V or 10V; 47.0uF at 3V or 6V; 100.0uF at 3V. ALL at 10p each, 10 for 95p, 50 for £4.

TRANSISTORS: BC188/183L 11p BFY60 80p
BC107/8/9 9p BC184/184L 12p BFY61 80p
BC114 15p BC212/212L 14p BFY63 80p
BC147/8/9 10p BC547/568A 18p AF178 80p
BC183/7/8 12p BF194 18p OC71 80p
BC182/182L 11p BF197 18p 2N3055 60p

POPULAR DIODES—1N914 5p, 8 for 45p, 18 for 90p; 1N918 8p, 6 for 45p, 14 for 90p; 1844 5p, 11 for 60p, 24 for 11.00; 1N4148 5p, 8 for 27p, 12 for 45p; 1N4001 6p, 100 for 50p, 1000 for 500p; 0047p; 005 8p; 007 8p; 008 8p; 009 8p; 010 8p.

LOW PRICE ZENER DIODES—400mW, Tol. $\pm 5\%$ at 5mA. Values available: 8V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 15V, 18.5V, 18V, 18V, 18V, 20V, 23V, 24V, 27V, 30V, 33V. All at 7p each, 6 for 39p, 14 for 86p. **SPECIAL OFFER:** 100 Zeners for 45.00p.

RESISTORS—High stability, low noise carbon film 5%, $\frac{1}{4}$ W at 40°C, $\frac{1}{4}$ W at 70°C. E12 series only—from 2.2 Ω to 3.2M Ω . ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. **SPECIAL PACK:** 10 of each value 2.2 Ω to 3.2M Ω (730 resistors) 85p.

SILICON PLASTIC RECTIFIERS—1.0 amp, brand new wirewound D027: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2 $\frac{1}{2}$ amp: 200V 40p; 350V 45p; 500V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: AL at 6p each; 50 Ω , 100 Ω , 220 Ω , 470 Ω , 680 Ω , 1k Ω , 2.2k Ω , 4.7k Ω , 6.8k Ω , 10k Ω , 15k Ω , 22k Ω , 47k Ω , 100k Ω , 250k Ω , 680k Ω , 1M Ω , 2.5M Ω , 5M Ω .

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW 50p. ALL EXPORT ORDERS ADD COST OF SEA/FREIGHT.

PLEASE ADD 25% V.A.T. TO ORDERS.

MARCO TRADING (Dept. W7).
The Old School, Edstaston, Nr. Wem, Shropshire.
Tel: Whixall 464/465 (STD 094 872)
(Propr. Minicost Trading Ltd.)

NEW COMPONENTS. Polystyrene 10pF-8200pF 2p; mylar 0.001, 0.002, 0.005 2p; polyester 250V 0.01-0.068 3p; 0.1, 0.15 4p; 0.22, 0.33 5p; 0.47 7p; electrolytic 0.47, 1, 2.2, 4.7, 10uF 50V 4p; 22, 47uF 25/50V 5p; 100uF 25/50V 7p; tantalum 9p; zeners 9p; resistors $\frac{1}{4}$ W 1p; 1W 2p. Inclusive prices. P&P 10p. List SAE. D. Coulam, Thimbleby, Horncastle, Lincs.

250mA. Cartridge Fuses $\frac{1}{4}$ " 90p per 100. Unused Carbon Resistors. 100 different 55p. Unused W/W Resistors. 100 assorted £1.10. 100 Capacitor Mixture, 85p. $\frac{1}{4}$ in. 8 to 2BA. Nut & Bolt mixture 30p. Brass 40p. 15 Toggle Switches, assorted £1.18. Ex Government Standard Jack Plugs 4 for 50p 6 volt 38 or 18 watt Bulbs. SBC, 70p per doz. Earphones Ex Govt. 85p per pair. New Meter or Cassette Cases, stiff imitation leather 6 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " x 4". Only 55p. Ex T.V. Speakers, Perfect, 3 Ω elliptical 60p. 300mA Meters New, £1.75p. 7" Tape Spools 18p each. All postage in U.K. included in price.

SOUND SYSTEMS OF SUFFOLK
676 Foxhall Rd., Ipswich, Suffolk IP3 8NQ

BETA DEVICES

MANUFACTURERS BRANDED PRODUCTS

TRANSISTORS	DIODES & RECT	BRIDGE RECT
AC187/8 FR 0-40	1N914 0-04	1A 100V W01 0-20
BC107/8/9 0-09	1N4148 0-04	1A 200V W06 0-23
BC109C 0-11	BY127 0-14	1A 600V W08 0-30
BC147/8 0-10	IN4001/2 0-05	2EA 200V 0-30
BCY70/71/720-18	IN4003/4/5 0-08	ZENERS
BFY88 0-20	IN4006/7 0-08	BZ788c 3-3.
BFY50 0-18	IN6401 0-11	33v 5% 0.09
BFY51/52 0-18		1 watt 6.8.
2N1132 0-25	555 Timer 0-50	200V 5% 0.16
2N1711 0-25	566 Dual Tr 1.00	L.E.D.
2N2646 0-20	TBA800 1.50	209-RED 0.17
2N2905A 0-21	TBA810 1.60	LED CLIP 0.08
2N3055 0.14		OP. AMP. 10p
30055 0-23	D.I.L. SOCKETS	709C T099 0.30
OC28 0-45	8 Pin 0.12	709C D.I.L. 0.30
OC35 0-35	14 Pin 0.18	741C T099 0.30
TIP29A 0-49	16 Pin 0.14	741C D.I.L. 0.30
TIP31A 0-61		729C D.I.L. 0.86
TIP41A 0.74		747C D.I.L. 0.38
TIP42A 0.90	V.A.T. INC.	748C D.I.L. 0.38

7400N	0-16	74 SERIES TTL	74121N	0-50
7404N	0-18	7447N	1.00	74123N 1.25
7410N	0-18	7474N	0.87	74141N 1.13

ALUMINIUM ELECTROLYTIC CAPACITORS
10uF 22uF 47uF 100uF 220uF 470uF 1,000uF
18v 0.07 0.07 0.07 0.10 0.12 0.14 0.22
25v 0.07 0.07 0.08 0.10 0.13 0.16 0.26

C.W.O. PLUS Pp 15p TO BETA DEVICES,
4, Highbridge Street,
Waltham Abbey, Essex.

UNBELIEVABLE SPEAKER BARGAINS! 8 Ω Acoustic Suspension, teak/sculptured foam front, 6 watt £5.30; 12 watt £6.50; 16 watt (8in woofer, 3in tweeter) £7.90. (Lists 20p.) Satisfaction guaranteed (10% p&p). Gregg Electronics, 105 Grange Road, London SE25.

Wanted

VALVES. 6HR6, 6BE6, 6AK6 or 6AR5 for "Star Roamer". Mason, Fort View, Eastcombe, Stroud, Glos.

PRACTICAL WIRELESS 1932-1940. Continuous runs, rather than single copies, preferred. Box 126.

TOP PRICES PAID FOR NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8, Yorkshire.

TELEPHONES WANTED, candlestick type or older (foreign and English). 01-722 4151.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S, 55 Worcester Street, Wolverhampton.**

Ladders

LADDERS, timber and aluminium. Tel: Telford 586644 for brochure.

For Sale

MICROPHONES: AKG D109, £12-65; AKG D202E1, £43-45; AKG D190C, £18-70; AKG D190E, £20; AKG D224 £55; Sennheiser MD211N, £49-50; Sennheiser MD413N, £29-70. All brand new and boxed. Send CWO to J. J. Francis, (Wood Green) Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

VALVES AND COMPONENTS. 1922-1975. Wireless, television, cine. 3000 types. Television and radio service sheets 1932-70. Order from GEM, Wireless and Television Services Ltd., by return. 210 Gordon Avenue, Camberley, Surrey. Or telephone 0276 29460.

COPPER CLAD LAMINATE

FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1.0p/sq. inch. Single sided 1/16" glass-epoxy—1.5p/sq. inch. Any rectangular sizes cut to your requirements. Please send cash with order. Price includes postage and packing. From: **SIMTECH ENGINEERING LTD** Station Works, Station Approach BRAINTREE, ESSEX CM7 6QJ Braintree 20911

FOR SALE 'Practical Wireless' from May 1966 to September 1971 inclusive. Offers to include postage and packing cost. Replies to Box No. 124.

BLAUPUNKT short wave car radio, 9 bands, £15-00 from Dodds, 75 East Street, Bridport, Dorset. Tel: 2831.

SOUNDLIGHT CONVERTERS. 3-channel: 1-5kw £19-50; 3kw £28-75; STROBES 1-joule £21; 4J £27; 15J £45. Chasers from £27. Rainbows, Projectors. Bumper catalogue: **AARVAK ELECTRONICS.** 98a (P), West Green Road, N15 5NS. 01-800 8656.

Service Sheets

SERVICE SHEETS for Radio, TV, etc., 50p and SAE. Catalogue 20p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS) ALL AT 50p EACH

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882
NO OVERSEAS MAIL PLEASE

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telay, 154 Brook Street, Preston PR1 7HP.

Aerials

GENUINE FULL SIZE 18 element TV aerial

as used by leading TV companies

FOR ONLY **£2.55** incl. VAT +59p post

ITV BBC1 & 2B/W & Colour Guaranteed Perfect Pictures. Save £15. We supply this genuine U.H.F. aerial for only £2.55, can be fitted outside or inside. Quality made technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions, advice. Money Back Refund. Wall/Caravan Bracket 25p. Best Cable 12P per yard. Plug 10P & FREE with order maps & channel reference of Radio & TV Transmitters! Send direct to Dept. PW 10 219 Mansfield Rd, Nottingham

IMPERIAL TRADING (AERIALS) LTD.
the quality Aerial Specialists.

STOCKISTS of Jaybeam Stereobeams, Antiference Mush Killers, Rotars, coax cable, masts and fittings. Send stamp for full lists competitive prices. Alan Turner Services, 26 Chapel Garth, Skipsea, Driffield.

J. & A. TWEEDY (Electronic Supplies) LTD.

79 Chataworth Road, Chesterfield, S40 2AP. We have in stock a good range of Jaybeam TV and FM aerials. As well as these we have a good stock of accessories. A SAE will bring more details. Multibeam: MBM 28 £5-00, MBM £8-00, MBM 70 £12-50, JBM 18 £4-00, Rotators AR 30 £27-00, AR 40 £32-00, CD 44 £64-00, Stereobeam: SBM2 £3-00, SBM 3 £4-00, SBM 4 £5-00, SBM 6 £8-95. NEW 6 element £19-00. VAT included on all prices. Masthead amplifiers £11-00. Setback £5-50. State group required on all aerials and amplifiers. Carriage is paid on all aerial orders but extra on accessories.

NEW HIGH GAIN 4 ELEMENT VHF/FM RADIO AERIAL

Stereo or mono!

Increase volume, quantity and sensitivity

of any VHF/FM

Radio or Hi-Fi, stereo or mono with this genuine aerial it's a necessity if you want the best out of your equipment, whether a small radio or expensive stereo. Don't put up with poor reception any longer. Send now hear for yourself. Ideal for the do it yourself enthusiast. Supplied with clamp, instructions and advice. Use inside or out FREE with order maps and channel reference of all Radio and TV Transmitters! Money Back Refund. Send Direct to Dept. NS10 219 Mansfield Rd., Nottingham

ONLY £4.49 incl. VAT +65p P&P

Best Cable 12p per yard

IMPERIAL TRADING (AERIALS) LTD.
the quality Aerial Specialists.

Hi-Fi Equipment

FELSTEAD ELECTRONICS (PW93)

LONGLEY LANE, GATLEY
CHEADLE, CHESHIRE SK8 4EE

For Low Price

Styli, Cartridges, Leads, Cassettes, Tape, Plugs, Sockets, Components and Accessories, &c. (by post only). Send S.A.E. for list incl. Illus. Stylus Chart

All items also available to callers in Manchester, at **TRIONIX, 177 SCHOOL LANE,** (Kingsway Corner), EAST DIDSBUURY 19

Books and Publications

Technical Books - Radio & Electronics

World's Radio & TV Stations (International Edit).....	£0.88
Audio Amplifiers.....	£0.70
Boys Book of Crystal Sets & Simple Circuits.....	£0.33
Television Timebase Circuits.....	£1.15
Radio TV and Industrial Tube & Valve Equip.....	£0.68
How to get the best out of your Tape Recorder.....	£1.67
Practical Electronic Science Projects.....	£0-85
Jack Darr's Service Clinic.....	£1.55
Transistor Circuits for Modern Test Equipment.....	£0.68
Rad & Electr Colour Codes and Data Chart.....	£0.20
Handbk of Transistor Equiv. and Substitutes.....	£0.48
Hi Fi, PA & Disco Amplifier Design Hndbk.....	£0.87
Radio Servicing Problems.....	£0.75
Electronic Circuits for the Amateur Photographer.....	£0.40
Handbook of Simple Transistor Circuits.....	£0.40
TV Fault Finding.....	£1.10
Sound and Loudspeaker Manual.....	£0.60
Practical Stereo & Quadrophony Handbook.....	£0-85
Radio Amateur Operator's Handbook.....	£0.85
Towers International Transistor Selector.....	£3.30
Television Servicing Vol. No. 2.....	£1.27
Television Servicing Vol. No. 3.....	£0.75
Receiving Pal Colour Television.....	£5-35
Radio Technicians Bench Manual.....	£3.30
Servicing Transistor Radio Receivers.....	£0.90
1st Book of Hi Fi Loudspeaker Enclosures.....	£0.68
2nd Book of Hi Fi Loudspeaker Enclosures.....	£0.60
Manual of Electronic Circuits for the Home.....	£0.40
Modern Crystal Set Circuits for Beginners.....	£0.40
Electronic Novelties for the Motorist.....	£0.58
2nd Book of Transistor Equiv. & Substitutes.....	£1.07
Handbook of Electronic Musical Novelties.....	£0.58
Transistorised Novelties for Hi Fi Enthusiast.....	£0.40
Fault Location Exercises in Rad. & TV Vol.1.....	£0.95
Fault Location Exercises in Rad. & TV Vol.2.....	£1.55
Colour TV Picture Faults.....	£2.70
Practical Transistor Novelty Circuits.....	£0.48
Boys Book of Practical Radio & Electronics.....	£0.68
Radio Receiver Construction using ICs & Transis.....	£0.68
ICs & Transistor Gadgets Construction Handbk.....	£0.68
Integrated Circuits Equiv. & Substitutes Hbk.....	£0.85
Audio Technicians Bench Manual.....	£3.30
Improving your Hi-Fi.....	£3.30
Guide to Printed Circuits.....	£2.80
HOW TO LISTEN TO THE WORLD, 9th EDIT.....	£2-65
WORLD RADIO TV HANDBOOK 1975.....	£3-80

All prices include Postage & Packing

RADIO BOOK SERVICE
40 Elwil Way, Beckenham BR3 2RZ

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

C AND G EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms Technicians' Electrical Installations, Radio, TV & Electronics Technicians' Radio Amateurs'. Full details from ICS School of Electronics, Dept. 320, Intertext House, London, SW8 4UJ. Tel: 01-622 9911 (all hours).

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from ICS School of Electronics, Dept. 321, Intertext House, London, SW8 4UJ. Tel: 01-622 9911 (all hours).

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new home study course approved by leading manufacturer. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from ICS School of Electronics, Dept. 322, Intertext House, London SW8 4UJ. Tel: 01-622 9911 (all hours).

Situations Vacant

MEN!
£90 p.w.
can be yours

Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

It can pay around £35 p.w. as a starter and can reach over £90 p.w.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

**London Computer Operators
Training Centre**

Y25, Oxford Hse.,
9-15 Oxford St. W1. Tel: 01-734 2874

Miscellaneous

PRINTED CIRCUIT manufacturer's offer, ready drilled PCBs for PW and PE projects published after June 1974, at one price 70p. E.g. Orion amp, telephone exchange. Also full sets for: Tele-tennis £3.50; PE CCTV £1.40p. Power slaves £1.35p. Scorpion ignition and Ferret locator 60p. CWO. Please add 15p per 40 sq in P&P. Production space available for PCB production, design, silk-screen printing, electroplating, tinning plus all graphic/art and photographic masters. Estimates by return post or phone. WKF Electronics, Welbeck Street, Whitwell, Worksop, Notts. Tel: Whitwell 695 (Derbys.).

INFLATION? 7 watts—200 watts. 7 watt IC TBA810AS+PCB+Data £1.45, post 15p. 7 watt complete kit £2.25 (25p). 7-7 watt with mains kit £5.80 (35p). 7 watt ready built IC modules £2.50 each, two+£2.30 each (25p). Sound system mono/stereo or hi-fi RMS power amp transistor and component kits with Juicy 1.3° heatsinks 50/70 watts £5.50 (50p). 75/100 watts £6.50 (50p). 150/200 watts £8.50 (50p). Power supply kits also available. SAE for list. Post in brackets. Send mail order, Watson, c/o 131 Buxton Street, London E1.

BUDGET MINI AUDIO MIXERS

With Professional Facilities

Slider faders ★ Tone controls ★ Monitoring VU Meter ★ Mono or Stereo ★ Ready to use or kits

Details ref. PW

**PARTRIDGE
ELECTRONICS**

21-25 Hart Road,
Benfleet, Essex.

AERIAL WIRE. High quality PVC covered multi-strand copper, 50ft 60p (10p); 75ft 87p (13p); 100ft £1.20 (15p); 150ft £1.80 (24p); 200ft £2.39 (26p); 250ft £2.96 (28p); 300ft £3.54 (31p). P & P in brackets. Longer lengths available. SAE all enquiries. Al Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 4½p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwicks., CV37 9NF.

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters'!

★ Pocket-sized **MAXI-VOLT** Big ¼ inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send **£1.90** for your Maxi-Volt now!

★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send **£6.90** for yours now!

★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send **£2.90** now! (all prices include V.A.T., packing & postage.)

Send remittance to:

**BOFFIN PROJECTS,
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY**
(Mail order U.K. only)

Or for more details, send 20p for lists

VALVES. Radio, TV, transmitting, industrial. 1930 to 1975. Many obsolete. 2,000 types stocked. List 20p. We wish to purchase new and boxed valves. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. West Wittering 2023.

GLASS FIBRE PCBs for all projects. Drilled and tinned. Send master print and 30p per board plus 5p per square inch. Electro Circuits, 4 Highcliff Way, Wickford, Essex.

SIMPLE TO FORM
NON-MAGNETIC RUST PROOF
MILL FINISH

ALUMINIUM

FLAT MINI SHEETS

10ins. x 14ins. 20 swg (0.90mm.)
6 sheets for **£2 plus 30p P&P**

OTHER SIZES AVAILABLE

For general car repairs,
trims, kick plates, etc.

**BAYKIN
ENGINEERING LTD.**

(Dept. PW)

GREVILLE ROAD, BEDMINSTER,
BRISTOL, BS3 1LL

LOW COST IC MOUNTING. 100 IC pin sockets, 50p. Quantity rates. SAE details and sample. 7 and 8 hole plastic supports 5p/pair (P&P 8p/order). LED (MLED500), 20p each, post free (quantity rates). PKG Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

VALVES: 1920 to 1955, large stocks at realistic prices, send SAE for free list, or 40p for our full "Antique Wireless Catalogue". Tudor Rees, 64 Broad Street, Staple Hill, Bristol. Tel: 0272-565472.

H.M. ELECTRONICS

275a, Fulwood Road, Broomhill,
SHEFFIELD S10 3BD Tel: 0742-600670

SEC CABINETS (Book End Chassis)



Standard cabinet
GB1 14" x 6" x 2"
GB1A 9" x 6" x 2"
GB2 14" x 7" x 3"
GB3 14" x 9" x 4"
GB4 14" x 9" x 6"

Send 15p for wallet of leaflets (Refundable on 1st purchase)

A beautifully designed modern cabinet with simulated black leatherette top (PVC bonded to metal) solid wooden end cheeks, with room at the back for Output Sockets etc.. Feet pads are fitted on bottom of cheeks for non-scratch.

DIGITAL CLOCK CHIP, AY-5-1224, with data & circuit diagram, £3.66 + VAT, 'Jumbo' LED digits (16mm high) economy type DL-747, only £2.04 each + VAT, post free.—Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

SINTEL

Add 10p P. & P. for orders under £2. Data, and circuits where appropriate supplied with orders, or available separately (send 8in x 4in S.A.E.) **ADD VAT at 8%.**

DL707 Red 0-3in LED 7 seg display C. Anode £1.35
DL747 Red 0-8in LED Jumbo display C. Anode £2.45
Economy DL704 Red 0-3in 7 seg LED C. Cath. 85p
NBS33 Type 0-12in 3 digit LED C.C. Red £1.05
MK50250N Alarm Clock IC £5.00
CT7001 Clock/Calendar/Timer IC £5.00
MK/704-6 MK50250N 6 digit Alarm Clock Kit £16.85
(complete less case, transformer, switches, LS)
SOLDERCOM I.C. Socket Pins 100 pins for 50p
(Nylon supports available) 300 pins for £1.50
Send s.a.e. for pin sample 1000 pins for £4.00
ADD VAT at 8%—new 25% rate does not apply to any of these goods.

Phone (9.30 to 7) or send s.a.e. for lists.

SINTEL, 53N ASTON STREET OXFORD
Tel. (0865) 43203

TRIACS (plastic) 10A/400V, 64p (60p for 3+); Diac 19p; NE555V 58p (55p for 3+); LEDs 0.2in dia. Red 20p, Amber Green Yellow 25p. P&P 10p. Add VAT. CWO. TK Electronics, 106 Studley Grange Road, London W7 2LX.

BLUE PCB INK

(ETCH-RESIST)
USE WITH ANY
£1.75 PEN!
(175cc)

VAT & Post FREE
CWO Please to:
JFH SUPPLIES, 30 BAKER ST. LONDON W1M

12 VOLT 21" 13 Watt Fluorescent Lighting (by Thorn/AEI) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 inc. VAT
SALOP ELECTRONICS 23 Wyle Cop,
Shrewsbury, Shropshire Tel. 33206

UFO CHARTS: Wave Prediction, 54p; Daily Flight Pattern, 50p; TV Doppler Detection, 63p; Propulsion Theory, 65p; "Anti-Gravity", 55p. Map 50p. Circuits: Transistor Optical Detector, 60p; Radiation/Optical, 44p; Crystal Radiation Counter/Timer/Stopclock, 85p. R. & E. Highlands, Needham Market, Suffolk.

KIT OF PARTS for car wiper delay unit (PW, May 1975), £3.45, less case, postage, etc., free. SAE for lists. G. Newman, 12 Francis Avenue, St. Albans AL3 6BX. (Mail order only.)

Synthesiser "Sounds Supreme"

by Dewtron (25% VAT extra.)

Famous kits, e.g. waa-waa complete kit £3.50; Fuzz kit £5.50. P & P 25p under £10. Ring Modulator modules £9. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 20p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

LOWEST COST IC SOCKETS. Use Soldercon IC socket pins for 8 to 40 pin DIL's. Make 8 pin sockets for 4p, 14 pin for 7p (at 300 pin price). 70p per strip of 100 pins, £1.50 for 3 x 100 £4 for 1000. 10p p&p for orders under £2. Add 8% VAT. Instructions supplied—send see for sample. SINTEL, 53n Aston Street, Oxford. Tel: 0865 43203.

PRINTED CIRCUIT COPPER CLAD. Single Sided. Quality material. Flame retardant to N.E.M.A. Spec. Paper Base (FR2) 1/4 x 7 x 5, 3 for £1. Epoxy Glass (FR4) 1/4 x 7 x 5, 2 for £1 Also panels cut to your requirements, quotation by return.

Prices include P. & P. Cash with Order.

P. G. OLIVER & CO.

4 Hearsall Lane,
COVENTRY CV5 6HH.

P.W. CRATA F.M. TUNER. Set of five P.C. boards £3, p&p 20p. Other components available. S.A.E. for lists. Teleradio, 325 Fore Street, Edmonton, London N9 0PE.

BUILT TO TASTE

TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 11in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete Kit £10.90 Post 60p + 92p VAT(8%)
Built & tested £15.25 Post 60p + £1.27 VAT(8%)

MINIKITS ELECTRONICS,

6a CLEVELAND ROAD,

LONDON, E18 2AN (Mail order only)

SUPERB INSTRUMENT CASE by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronic, Hi-Fi enthusiasts, and Industrial users are choosing the cases they require from our range. Make your VAT go further with our competitive prices which begin at a low 75p. Examples: Width, Depth, Height 7" X 7" X 5" £2.65, 8" X 10" X 6" £3.60, 12" X 8" X 7" £4, 12" X 12" X 7" £4.40. Over 200 Models to choose from, Prompt despatch, Free literature (Stamp would be appreciated) Bazelli Dept No 25, St. Wilfrids, Foundry Lane, Halton, Lancaster LA2 6LT.

FANTASTIC NEW MICROTEST 80

MEASURES ONLY

90×70×18 mm
ELECTRONIC ZERO Ω

Amazing Value at £11.95

8 fields of measurement
and 40 ranges

PRINTED CIRCUIT BOARD IS
REMOVABLE WITHOUT SOLDERING

Volts D.C. 6 ranges: 100mV - 2V - 10V - 50V - 200V - 1000V. (20kΩ/V) (2% precision on DC and A.C.)

Volts A.C. 5 ranges: 1.5V - 10V - 50V - 250V - 1000V. (4kΩ/V)

Amp. D.C. 6 ranges: 50μA - 500μA - 5mA - 50mA - 500mA - 5A

Amp. A.C. 3 ranges: 250μA - 2.5mA - 25mA - 250mA - 2.5A

Ohms 4 ranges: LowΩ - Ω x 1 - Ω x 10 - Ω x 100 from 1/10dΩ to 11.5 Mega Ω

V Output 5 ranges: 1.5V - 10V - 50V - 250V - 1000V

Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +62dB

Capacity 4 ranges: 25μF - 250μF - 2500μF - 25,000μF



SUPERTESTER 680R ICE


20,000 Ohm per Volt/sensitivity • Fully screened against external magnetic fields • Scale width and small case dimensions (128 x 95 x 32mm) • Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading • Simplicity and ease of use and readability • Full ranges of accessories • 1000 times overload • Printed circuit board is removable without desoldering • More ranges than any other meter. Ask for free catalogue £18.50

Accessories (extra) available to convert Microtest 80 & Supertester 680R into following: LIGHT-METER GAUSS METER, ELECTRONIC VOLT-METER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100K Multiplier SIGNAL INJECTOR—Send for details.

Accessories (extra) available to convert Microtest 80 & Supertester 680R into following: LIGHT-METER GAUSS METER, ELECTRONIC VOLT-METER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100K Multiplier SIGNAL INJECTOR—Send for details.

MORE RANGES FOR LESS MONEY!

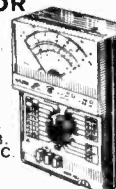
AC/DC Multimeter type U4324
A-DC 0.08-3A - 6 Ranges.
A-AC 0.3-3A - 5 Ranges.
V-DC 0.6-1200V - 9 Ranges.
V-AC 3-900V - 8 Ranges.
Freq.: In the range of 45 to 20kHz.
Resistances: 500 Ohm to 5 MΩ Ohm-5 Ranges, Decibel: -10 to +12dB.
Accuracy: ± 2.5% DC, ± 4% AC.
Dimensions: 167 x 98 x 63 mm.



Only £9.25

ALPHANUMERIC NIXIE TUBES B7971

The Alpha-numeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including: • 170v-210v A.C. • All d.c. operation • Uniform, continuous line characters of equal height • Memory with simple solid state drive circuits • Readability in high ambient light... 200 footcandle brightness • Long life with no loss of brightness • Character height 2 1/2 in.

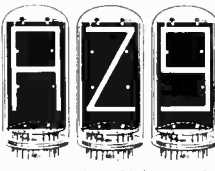

Price only 99p each plus 16p P/P. Bases for above 60p each.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V D.C. Current 14mA. Pulse duration 100μs. Character height 0.51, overall size 1.4. Brand new, guaranteed. Surplus to manufacturers requirements. Type B5853st
1-25 £1 25+ 90p 100+ 80p

1000+ price on application
8% VAT to all items + 35p P & P
ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

Everest Instruments Ltd.

34, Shakespeare St., Nottingham.
Tel. (0602) 45466

All prices quoted include p. & p., & VAT, min. order £1, CWO only. 12 x 10 SAE for full lists.

Transformers		P.C. Board	
Volts	Amps	Single sided s.r.b.p.	
All 240V 50hz primaries		sq ft	
6-3	1-5	1	0.55
6-3	3-0	1	0.70
9-0	1-0	1	1.00
12-0	0-5	1	1.83
12-0	1-5	2	2.09
12-0	3-0	3	3.02
12-0	3-0	3	3.02
6-0-6	0-5	1	1.96
9-0-9	0-5	1	1.96
9-0-9	1-0	2	2.23
10-0-10	2-0	3	3.00
12-0-12	1-0	2	2.13
12-0-12	2-0	3	2.93
12-0-12	3-0	4	4.12
15-0-15	1-0	2	2.88
18-0-18	2-0	4	0.1
20-0-20	2-0	4	0.33
30-0-30	1-0	4	1.32
0-10-12-14			2.2
16-18	4-0	4	4.58
0-12-15-20			
24-30	2-0	4	4.45
0-5-20-30			
40-60	2-0	6	6.54
Battery charger transformers 6 & 12V			
1-0	2-35		
2-0	3-27		
4-0	4-32		
240/110	30 watts	2.88	
autos	50 watts	3.66	
	100 watts	5.23	
	150 watts	6.33	
	200 watts	8.36	
	400 watts	13.14	
	600 watts	15.54	
	1000 watts	23.67	
Bulk tape eraser			
15-8-3 ohm 12 watt		3.53	
matching		1.71	
Transistor driver			
4:1+1		0.27	
Speakers			
3" Goodman tweeter		£ p	
8 ohm 51CD4	1.47		
3" Audax tweeter			
8 ohm 6-5TWB18	1.60		
5" Audax 8 ohm bass			
HIF13E8	3.23		
6 1/2" EMI d/cone 8 ohm			
10 watt	4.7		
6 1/2" Audax 8 ohm	2.95		
6 1/2" Celestion 8 ohm			
d/cone PS8 9858	2.76		
10 x 6 EMI 8 ohm			
mldrance	4.18		
10 x 6 EMI 8 ohm			
20 watt	7.36		
13 x 8 EMI 8 ohm			
20 watt	6.75		
13 x 8 EMI 8 ohm			
25 watt	7.84		
Electrolytics. Tubular with axial leads except where stated.			
Mfd.	Volts	Pence	
47	4	7	
330	4	7	
68	6.3	7	
470	6.3	9	
1000	6	11	single end p/c fitting
25	10	7	
47	10	7	
220	10	7	
330	10	9	
15	15	7	
33	16	7	
68	16	7	
220	16	9	single end p/c fitting
330	16	12	
1000	16	20	single end can
10	25	7	
22	25	7	
47	25	7	
100	25	7	
150	25	9	
200	25	11	
1250	25	24	single end can
5000	25	55	single end can
1000+1000	30	32	single end can
2500	30	40	single end can
6.8	40	7	
16	40	7	
100	40	9	
1000	50	35	single end can
1	63	7	
4.7	63	7	
10	63	7	
80	63	32	single end can
200	63	32	single end can
4700	63	140	single end can
Oddments to clear			
50mfd @ 50V tubes		6	
250mfd @ 60V cans		10	
300mfd @ 10V p/c		5	
60+250mfd @ 350V cans		30	
0.03mfd @ 200V tantalum		5	

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS SATURDAYS ONLY

Send 15p postage for our comprehensive catalogue

ALL DEVICES BRAND NEW AND FULLY GUARANTEED.
ORDERS DESPATCHED BY RETURN OF POST. TERMS OF
BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT
WITH ORDER. GOVERNMENT AND EDUCATIONAL
INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE
AND EXPORT INQUIRY WELCOME. P & P ADD 20p TO
ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE
AT COST, AIR/SURFACE.

PRICES EXCLUSIVE OF VAT

OUR NEW LOW PRICES MEAN YOU PAY LESS VAT.

TRANSISTORS (less 10% for 25+ of one type)

AC125 13p	BC149 9p	BF179 33p	OC72 11p	1S920 7p	2N2826Y 8p
AC126 13p	BC154 18p	BF180 33p	OC74 28p	1S921 7p	2N3053 18p
AC127 11p	BC157 13p	BF181 33p	OC81 12p	1S922 8p	2N3054 42p
AC128 11p	BC158 12p	BF184 22p	OC82 12p	1S923 10p	2N3055 45p
AC176 11p	BC159 13p	BF185 22p	OC83 28p	2N696 15p	2N3614 59p
AC187 12p	BC187 12p	BF194 10p	OC140 100p	2N697 13p	2N3615 65p
AC188 13p	BC189 12p	BF196 12p	OC201 70p	2N698 30p	2N3702 12p
ACY17 35p	BC169 12p	BF196 12p	OC202 80p	2N708 11p	2N3703 12p
ACY19 25p	BC170 11p	BF197 12p	TIC44 30p	2N708 16p	2N3704 12p
ACY20 24p	BC171 11p	BF257 32p	TIP29 43p	2N918 40p	2N3705 12p
ACY21 29p	BC172 11p	BF595 18p	TIP29A 45p	2N930 18p	2N3706 10p
ACY22 18p	BC177 16p	BFX86 21p	TIP30 48p	2N131 20p	2N3707 10p
AD140 48p	BC178 16p	BFX88 22p	TIP30A 54p	2N132 20p	2N3708 8p
AD149 45p	BC179 11p	BFY50 15p	TIP31 54p	2N1301 20p	2N3709 8p
AD181 34p	BC182 10p	BFY51 15p	TIP32 64p	2N1302 17p	2N3710 9p
AD182 34p	BC183 10p	BFY52 15p	TIP33 95p	2N1303 20p	2N3711 140p
AF114 13p	BC184 11p	BFY53 17p	TIP34 130p	2N1304 24p	2N3712 160p
AF115 13p	BC212 12p	BSX20 16p	TIP41A 68p	2N1305 24p	2N3713 240p
AF116 13p	BC213 10p	BUE10 62p	TIP42A 74p	2N1306 24p	2N3721 10p
AF117 13p	BCY14 18p	MJ310 63p	TIS43 26p	2N1307 24p	2N3820 57p
AF118 13p	BCY42 28p	MUE37 75p	TIS44 17p	2N1893 30p	2N3823 60p
AF121 33p	BCY43 25p	MUES20 62p	ZTX107 10p	2N1990 45p	2N3824 50p
AF124 30p	BCY58 18p	MFP102 30p	ZTX108 8p	2N2217 23p	2N3904 15p
AF125 30p	BCY59 18p	MFP103 30p	ZTX119 12p	2N2219 20p	2N3905 17p
AF126 30p	BCY70 15p	MFP104 30p	ZTX300 12p	2N2221 20p	2N3906 17p
AF127 30p	BD191 15p	MJ105 30p	ZTX301 14p	2N2222 20p	2N4037 35p
AF139 33p	BDY32 12p	OC23 144p	ZTX302 18p	2N2303 25p	2N4058 15p
AF181 45p	BC131 40p	OC26 40p	ZTX304 22p	2N2369A	2N4061 13p
AF186 48p	BD124 75p	OC28 48p	ZTX311 10p	14p	2N4062 14p
AF239 39p	BD132 40p	OC35 48p	ZTX341 19p	2N2483 30p	2N4871 31p
BC107 9p	BD137 45p	OC36 30p	ZTX500 15p	2N2646 30p	2N5457 30p
BC108 9p	7440 15p	OC15 15p	ZTX501 13p	2N2904 10p	2N5458 30p
BC108B 12p	BDY60 75p	OC42 15p	ZTX502 18p	2N2906 25p	2N5459 30p
BC109 9p	BDY61 65p	OC44 12p	ZTX504 42p	2N2907 17p	3N140 85p
BC109C 12p	BF115 22p	OC45 12p	ZTX505 23p	2N2926G10p	3N141 85p
BC147 7p	BF177 28p	OC70 11p	ZTX550 18p	2N2926G 8p	40361 40p
BC148 7p	BF178 28p	OC71 11p	1S44 5p	2N2926R 8p	40362 40p

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F).

0.001, 0.0012, 0.0015, 0.0018, 0.0022, 0.0033, 0.0047 3p; 0.0068, 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1 4p; 0.15, 0.22, 6p; 0.33, 10p; 0.47, 13p; 160V: 0.1, 0.15, 4p; 0.22 5p; 0.33 6p; 0.47 9p; 0.68 10p; 1.0 13p. 250V: 0.22 6p; 0.33 8p; 0.68 12p; 0.47 9p; 2.2 18p.

POLYESTER RADIAL LEAD P.C. TYPE (Values are in μ F).

0.25V: 0.01, 0.015, 0.022, 0.033, 0.047 3p; 0.068, 0.1 4p; 0.15 4p; 0.22 6p; 0.33 8p; 0.47 9p; 0.68 10p; 1.0 13p; 1.5 20p; 1.5 20p; 2.2 22p; 1000pF/350V 8p

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F).

63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 20, 22, 47, 68, 100, 12p; 40V 10p, 6p; 50V: 1000, 42p, 30V: 3500, 41p, 25V: 40, 68, 150, 6p; 220, 11p; 470, 13p; 680, 18p; 1000, 24p; 2200, 34p, 3000, 39p; 4700, 47p, 16V: 4, 10, 125, 250, 6p, 16V: 1000, 1500, 16p. 10V: 4, 100, 5p; 640, 10p; 1000, 14p; 2200, 18p.

POTENTIOMETERS (AB) Carbon

Track, 0-25W Log & 0.5W Linear values
1K Ω -2M Ω single gang 14p
5K Ω -2M Ω single gang D/P switch 32p
2K Ω -2M Ω dual gang stereo 45p

TANTALUM BEAD CAPACITORS

25V: 0.1 μ F, 0.2, 0.47, 1.0, 2.2, 4.7, 6.8
35V: 0.1 μ F, 0.2, 0.47, 1.0, 2.2, 4.7
60V: 10 μ F, 16V: 22 μ F, 10V: 33 μ F, 22 μ F.
2V: 33 μ F, 47 μ F, 3V: 47 μ F, 100 μ F.
Price: 10p each.

SLIDER POTENTIOMETERS

0-25W log and linear values
5K Ω -500K Ω single gang 35p
10K Ω -500K Ω Dual gang 50p
KNOBS for above Black or Silvered 8p

PRESET POTENTIOMETERS

0.1W 50 Ω -1M Ω Vertical only 5p
0.25W 100 Ω -2.2M Ω Horizontal 6p
0.25W 1K Ω -2 M Ω Vertical 6p

Mylar film capacitors

100V: 0.001, 0.002, 0.005, 0.01 μ F 3p
0.015, 0.02, 0.04, 0.05 μ F, 0.1 μ F 4p
0.15, 0.25 μ F: 0.47 μ F 6p

CERAMIC CAPACITORS

50V d.c. Plaqueette body 25mm leads.
Range: 5pF-10,000pF 2p
0.015 μ F, 0.022 μ F, 0.033 μ F, 0.047 μ F 3p

TTL 74 DIGITAL ICs

7400 14p	7428 38p	7473 33p	AA120 10p	SPECIAL OFFER
7401 14p	7430 15p	7474 32p	BY100 18p	Beat the VAT Man.
7402 15p	7432 25p	7475 32p	BY127 11p	LED TIL209 type
7403 15p	7433 36p	7476 32p	BY211 25p	Red
7404 18p	7437 27p	7480 44p	OA5 38p	Green, Yellow,
7405 18p	7438 27p	7481 39p	OA10 36p	Amber & White
7406 30p	7440 15p	7482 75p	OA9 9p	7 Seg Display
7407 38p	7441 65p	7483 83p	DL707	£1.25
7408 15p	7442 65p	7484 90p	DL747	£1.85
7409 15p	7443 120p	7485 125p	741C	25p
7410 15p	7444 105p	7489 275p	748C	25p
7411 20p	7445 86p	7490 40p	7447TTL	70p
7412 20p	7446 105p	7491 80p	NE555	42p
7413 35p	7447 100p	7492 48p	TBA800	88p
7414 60p	7448 70p	7493 39p	ZN414	88p
7415 35p	7450 15p	7495 63p	EARPHONES	
7416 35p	7451 15p	7496 72p	With Cord and Jack	
7420 15p	7453 15p	7497 40p	Plug Magnetic	
7422 24p	7454 15p	7421 21p	2 1/2 mm plug	15p
7423 27p	7460 15p	74141 65p	3.5 mm plug	15p
7425 27p	7470 30p	74190 160p	Crystal	28p
7426 27p	4772 26p	74191 160p	3.5 mm plug	28p

DIODES

AA120 10p	NE555 304p	SCR (Thyristors)
BY100 18p	NE562 315p	1A 50V 38p
BY127 11p	NE567 315p	1A 100V 42p
BY211 25p	SL403D 150p	1A 200V 47p
OA5 38p	SL414A 150p	1A 400V 52p
OA10 36p	SN7603Z 250p	1A 600V 70p
OA9 9p	SN76115 20p	3A 50V 38p
DL707	TAD100 130p	3A 100V 43p
DL747	TBA800 110p	3A 200V 55p
741C	TBA810 130p	3A 400V 74p
748C	TBA812 110p	3A 600V 91p
7447TTL	ZN414 110p	5A 400V 90p
NE555	TRISACs	7A 400V 95p
TBA800	3A200V 90p	7A 600V 108p
ZN414	3A400V 90p	3A 600V 91p
BRIDGE RECTIFIERS	3A600V 122p	2A100V 35p
(plastic case)	6A400V 122p	2A200V 40p
1A50V 20p	6A500V 147p	2A400V 44p
1A500V 21p	10A400V 158p	2A600V 45p
1A200V 24p	10A500V 184p	3A600V 91p
1A600V 30p	15A400V 178p	4A100V 48p
3A 50V 38p	15A500V 198p	4A400V 60p
3A 100V 43p		4A800V 90p
3A 200V 55p		DIAC
3A 400V 74p		ST2 20p
3A 600V 91p		
5A 400V 90p		
7A 400V 95p		
7A 600V 108p		
3A 600V 91p		
2A100V 35p		
2A200V 40p		
2A400V 44p		
2A600V 45p		
3A600V 91p		
4A100V 48p		
4A400V 60p		
4A800V 90p		

QUALITY RESISTORS. ERIE MAKE

Type	Pwr Tol.	Range	Val.	1-99	100-499	500+
Carbon 1/2W	5%	2.2 Ω -10M	E24	1p	0.8p	0.7p
Carbon 1/4W	5%	2.2 Ω -10M	E12	1p	0.8p	0.7p
Carbon 1W	5%	2.2 Ω -10M	E12	2.5p	2p	-

Quantity price applies to resistors of each value not mixed.

LINEAR IC'S

709C 14 pin 29p	LM300H	170p	LM301	45p
723C	LM301	42p	LM304H	26p
741C	LM304H	170p	LM305	170p
747C	LM305	170p	LM309K	28p
748C	LM309K	185p	LM380	90p
7805	150p		LM381	160p
7815 (T03)	175p		LH3900	75p
AY1-0212 5-50p	MC724P	60p	MC1303L	130p
AY1-5051 1.15p	MC1303L	130p	MC1304P	72p
CA3018 14p	MC1304P	360p	MC1310P	220p
CA3020 14p	MC1310P	220p	MC1710CG	55p
CA3036 90p	MC1710CG	55p	MFC4000B	54p
CA3046 55p	MFC4000B	54p	MFC6040	90p
CA3048 22p	MFC6040	90p	MLM309K	158p
CA3075 150p	MLM309K	158p	MVR12	170p
CA3081 150p	MVR12	170p	NE555	55p
CA3089E 195p	NE555	55p	NE556	99p
CA3090AQ 250p	NE556	99p		

APOLLO-MW TUNER/RECEIVER

(all parts available)	
5-25 pF Miniature	
DAU Trimmers	20p
LM 1820N	£1.40
MVA1M	£2.70
6-Way Tuner	£1.40
IM1 9932	
Slider 5K Ω Lin	35p
Slider 50K Ω Lin	150mm
Rivlin VS 150	£3.00

INDUCTORS

TOKO 6A6408	30p
TOKO Y18576AQ	30p
TOKO YHCS11100AC2	30p
	55p
TOKO CFU050D	30p
P.C. Board	75p
(5% discount for complete kit)	

ENAMEL COPPER WIRE (2oz reel)

16, 18, 20, 22 SWG	32p
24, 26, 28, 30 SWG	38p
32, 34, 36, 40 SWG	48p
	5p per reel

OPTO ELECTRONICS

LED TIL 209 (red) with socket	16p
MINI TRON 3015F 7 seg display	100p
OCR 70	40p
OCR 71	85p
ORP 12	58p
ORP 61	41p
2N 5777	

The Shop Window for the Very Best...

IPC



**COMBINED
PRECISION
COMPONENTS
(PRESTON) LTD**

Department PW
194-200 North Rd.
Preston PR1 1YP
Tel: 55034
Telex: 677122

TOSHIBA VALVES

Type	Price (p)	Type	Price Each (p)	Type	Price Each (p)
DY87	30.0	AD149	40	BD124	75
DY80	30.0	AD161	38	BD131	45
ICCB2	28.0	AD162	38	BD132	39
EF80	29.5	AF114	24	BD160	£1.38
EF183	34.5	AF115	27	BD235	48
EF184	34.5	AF116	27	BD237	57
EH90	35.5	AF117	29	BDX32	£2.40
PC900	24.5	AF118	50	BF115	20
PCCB1	40.0	AF133	35	BF180	18
PCCB9	41.0	AF178	45	BF187	20
PCFB0	31.5	AF180	45	BF171	20
PCFB6	39.0	AF181	45	BF178	35
PCFB01	42.0	AF239	40	BF179	40
PCF902	40.0	AF240	60	BF180	31
PCL82	39.0	BC107	11	BF181	32
PCL84	39.0	BC108	10	BF18A	26
PCL85	44.5	BC109	14	BF185	25
PCL86	41.0	BC109C	14	BF189	8
PLC209	59.5	BC113	13	BF190	11
PL35	55.5	BC116A	19	BF191	12
PL84	25.0	BC128	15	BF198	23
PL504	84.5	BC132	25	BF200	25
PL508	67.0	BC135	15	BF218	30
PL519	£1.50	BC137	18	BF224	23
PV88	35.5	BC141	24	BF258	34
PV800	33.0	BC142	22	BF336	38
PV500A	85.0	BC143	25	BF337	35
		BC147	11	BF355	34
		BC177A	14	BF386	28
		BC148	10	BFY50	28
		BC149	10	BFY52	20
		BC153	15	BSY52	39
		BC154	15	BT106	£1.20
		BC157	14	BU105/02	£1.65
		BC158	10	BU108	£2.10
		BC159	11	BU208	£2.95
		BC173	18	E1222	30
		BC178A	20	MJ340	45
		BC176	22	OC71	15
		BC182L	12	OC72	16
		BC183L	12	R20088	£2.00
		BC187	25	R20108	£2.80
		BC188	17	RCA16334	80
		BC188K	24	RCA16335	80
		BC328	28		
		BC337	19		
		AD142	45		

SEMI CONDUCTORS

Type	Price Each (p)
AC127	17
AC128	13
AC141K	25
AC142K	25
AC151	20
AC154	18
AC155	18
AC156	20
AC176	22
AC187	19
AC187K	24
AC188	17
AC188K	24
AD142	45

DIODES

Type	Each (p)	INTEGRATED CIRCUITS	Price Each
BA115	7	TAA550	49p
BA145	14	TAA700	£2.86
BA148	13	TBA120AS	£1.00
BA154/201	11	TBA120SQ	£1.00
BY126	11	TBA4800	£1.40
BY127	12	TBA5200	£2.35
BY199	27	TBA5300	£1.75
BY206	31	TBA5400	£1.75
BY238	25	TBA5600C	£2.40
DA90	7	TBA800	£1.50
DA202	5	TBA9200	£2.90
IN60/DA91	5	TCA2700	£2.90
NEW TOSHIBA TUBES			
19" A49/191X	£48.95	ETR6016	£2.00
20" 510DJ82	£50.75	SN76013ND	£1.50
22" A56/120X	£54.25		
EHT MULTIPLIERS MONOCHROME (BRC)			
Price Each			
2HD 950MK1 960			£1.20
2T0 950MK2, 1400			£1.85
2DAK 1500 (17" & 19")			£1.85
2TAK 1500 (23" & 24")			£2.00
EHT MULTIPLIERS - COLOUR			
11TA0 ITT CVCI, 2 & 3			£4.50
11T1 GIC Sobell			£4.50
11TAZ GIC 2110			£4.95
11TAM Philips GB			£4.50
11TBD Philips 550			£4.50
3TCW Pye 691/693			£3.50
11T4 Decca 30 Series			£4.50
11TA0 Decca - Bradford			£4.50
3TCU Thorn 3000/3500			£5.00
11HAA Thorn 8000			£1.90
11HAB Thorn 8500			£4.25

PRICES SUBJECT TO 8% V.A.T
All goods subject to settlement
discount of 5% 7 days and 2%
monthly
No postage charges or minimum
order values
Write or phone for full details now.

...In Prices, Quality and Service.

INDEX TO ADVERTISERS

A.H. Supplies	257	Felstead Electronics...	259	Partridge Electronics Ltd.	212-260
Allard Electronics	184	Flairline Supplies	190	Pembroke College of Electronics...	180
Ambit International	cover iv			P.M.S. Nameplates	253
A.S.P. Ltd.	208	Greenbank Electronics	244	Radio Book Services	259
Astro Electronics Ltd.	208	Greenweld Electronics	252	Radio Component Specialists	...
Audio Equipment	252			Radio Exchange Ltd.	239
		H.A.C. (Shortwave) Products	182	Radio Society of Great Britain	248
Barrie Electronics	180	Harversons Surplus Co. Ltd.	181	R.S.C. (Hi-Fi) Centre Ltd.	178-179
Baykin Engineering Ltd.	260	Heath (Gloucester) Ltd.	181	R.S.T. Valve Mail Order Co.	234
Beta Devices	258	Henry's Radio Ltd.	253	R & TV Components Ltd.	194-195
B.H. Component Factors Ltd.	190	H.M. Electronics	260	Riversdale Electronics	216
Bi-Pak Semiconductors	186-187	Home Radio (Components) Ltd.	185		
Bi-Pre-Pak Ltd.	247			Salop Electronics	260
Boffin Projects	260	I.L.P. Electronics Ltd.	189	Saxon Entertainments Ltd.	215
Bothwell	192	Imperial Trading	259	Semiconductor Specialists	232
British Institute of Engineering Technology	184, 240, cover iii	Intertext (I.C.S.)	259	S.I.G.A. Electronics Ltd.	240
British National Radio & Electronics School	cover ii, 192			Simtech Engineering Ltd.	259
Bush & Meissner	254	J.F.H. Supplies	260	Sinclair Radionics Ltd.	211
J. Bull (Electrical) Ltd.	255	Juniper Electronics	258	Sintel	260
Bug Sound Electronics	258			Sound Systems of Suffolk	258
		Kensington Supplies	258	Studio Electronics	190
C.A.P.A. Group Ltd.	252	Keytonics	182	Surpletronics	254
C. Caranna	259			Surplus Electronic Trading	182
Chromasonic Electronics	235	Lasky's	249-250-251	Swanley Electronics	254
C.J.L. Ltd.	180	Lewis Radio	184		
Codar	248	Linear Products Ltd.	212	Technomatic Ltd.	264
Colomor (Electronics) Ltd.	182	London Computer Operators Training Centre	260	Trampus Electronics Ltd.	188
Combined Precision Equipment	263	Low Electronics	188	T.U.A.C. Ltd.	193
Crofton Electronics	244			Tweedy (J. & A.)	259
		Maplin Electronic Supplies	243		
D.E.W. Ltd.	261	Marco Trading	258	Ultron Components	216
Doram Electronics Ltd.	207	Marshall, A. & Son	257		
Dziubas, M.	216	Minikits Electronics	261	Watford Electronics	262
				Web Europa	208
Electronic Brokers	261	Newmart Electronics	183	West London Direct Supplies	254
Electronic Design Associates	232			Wilmshold Audio	244
Electronic Mail Order Ltd.	232	Oliver (P. G.)	261		
Electrospares	240			Xeroza Radio	252
Electrovalue Ltd.	236				
Everest	261			Z & I Aero Services	264

Head Office and Warehouse
 44A WESTBOURNE GROVE
 LONDON W2 5SF
 Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
 85 TOTTENHAM COURT ROAD
 LONDON W1
 Tel: 580 8403
 Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

MULTIMETERS

AC/DC MULTIMETER TYPE U4324
 33 ranges covering
 D.C. current
 60 μ A to 3A;
 AC current
 300 μ A-3A;
 DC voltage: 0-6-
 1200V
 AC voltage: 3-
 900V
 Resistance:
 500 Ω -500k Ω
 Level: -10 to
 +12db
 Sensitivity:
 20,000 o.p.v. DC.
 4,000 o.p.v. A.C.



AC/DC MULTIMETER TYPE U4323
 Apart from usual multimeter facilities the instrument incorporates fixed frequency Audio (1kHz) and I.F. (465kHz) Oscillators. 22 ranges covering AC Voltage 2.5-1000V; D.C. Voltage 0.5-1000V; D.C. current 50 μ A to 500 μ A and resistance 0 to 1M Ω . Sensitivity 20,000 o.p.v. Oscillator output voltage-1V minimum.
PRICE: £8.00

Instrument is powered by re-chargeable nickel cadmium batteries.
PRICE £9.85*

LINEAR INTEGRATED CIRCUITS

— Please note reductions in prices —

Mullard TAA263. Direct coupled three stage low level amplifier for use from DC to 600 kc/s. Supply voltage 6-8V. Typical power gain 77 db into 150 Ω load. Output power 10mW. TO72 four-lead encapsulation **£0.65***

Mullard TAA293. Medium frequency amplifier with frequency response of 600kc/s. Nominal supply voltage 6v. Typical power gain 89db. Maximum power dissipation 160 mW. Power output 10 mW. Into 150 Ω load. TO74 ten lead-encapsulation **£0.65***

Mullard TAA320. Metal oxide silicon low frequency pre-amplifier consisting of a MOST stage followed by a bi-polar transistor. Gate to source voltage 9-14v. Total power dissipation 200 mW. Drain current 1 μ A. Output conductance 0.65 mmho. TO18 3-lead encapsulation **£0.60***

Type 741 Operational Amplifiers, 8-dual-line type encapsulation **£0.30***

L.E.D. TYPE HP5082/4850

Red Light GASP Light Emitting Diodes giving bright diffused light of 0.8 mcd at forward voltage of 1.6V and DC current of 20 mA. Plastic wide angle lens 0.200in. diameter. Ideal for panel lights, etc.
 Price for 12 pieces £1.75 incl. VAT and p.&p

OUR NEW 1975 ILLUSTRATED CATALOGUE/PRICE LIST covering VALVES, TUBES, SEMICONDUCTORS, PASSIVE COMPONENTS AND TEST EQUIPMENT IS NOW READY. PLEASE SEND £0.20 FOR YOUR COPY.

*** ALL PRICES EXCLUSIVE OF V.A.T. WHEN REMITTING CASH WITH ORDER PLEASE ADD £0.50 PER MULTIMETER AND £0.15 IN £ FOR OTHER ITEMS—SUBJECT TO A MINIMUM CHARGE OF £0.20—TO COVER HANDLING AND POSTAGE. NO C.O.D. ORDERS ACCEPTED.**

TTL 74 L.C's.

400	13p	7441	85p	7485	140p
7401	14p	7442	85p	7486	34p
7402	14p	7447	75p	7489	270p
7403	16p	7448	76p	7490	48p
7404	16p	7450	15p	7491	80p
7405	14p	7451	16p	7492	56p
7408	16p	7453	18p	7493	40p
7410	13p	7454	22p	7494	75p
7413	32p	7470	30p	7495	78p
7414	60p	7472	25p	7496	78p
7416	30p	7473	32p	74107	35p
7420	14p	7474	32p	74121	34p
7422	25p	7475	45p	74141	85p
7425	30p	7476	32p	74142	250p
7427	37p	7480	95p	74154	150p
7430	14p	7481	95p	74164	120p
7432	25p	7482	76p	74192	120p
7437	27p	7483	95p	74193	120p
7440	16p	7484	95p		

DIL Sockets by Texas

8 pin 12p, 14 pin 13p, 16 pin 14p
 Mica + 2 bushes for TQ3 & TO86 5p

LINEAR I.C.'s

CA3046	Transistor Array	50p
CA3048	4 Independent Amplifiers	230p
ICL8038	VCO Fun. Gen. 14 pin DIL	275p
LM301A	Op. Amp. with ext. comp.	36p
LM380	Audio Amplifier	90p
LM381	Stereo Pre Amp.	150p
LM3900	Quad Op. Amp.	76p
MC1310	Colless FM Stereo Dec.	225p
MC1312	SO Quadrasonic Dec.	220p
MC1314	SO Quadrasonic Dec.	400p
MC1315	SO Quadrasonic Dec.	400p
MFC4000	4W Audio Amp.	90p
MFC6040	Electronic Attenuator	90p
MFC8070	Zero Voltage Switch	250p
NE336	FET Op. Amp.	250p
NE555	Timer 8 pin DIL	45p

VOLTAGE REGULATORS (PLASTIC)

723 14 pin DIL	1amp +V _e	-V _e
	5v 7805 140p	7905 250p
10p	12v 7812 140p	7912 250p
	15v 7815 140p	7915 250p
Vol. Regs.	18v 7818 140p	—
	24v 7824 140p	7924 250p

Data Sheets on

10p each

NE556	Dual 555 14 Pin DIL	100p
NE560	PLL 16 Pin DIL	325p
NE581	PLL with AM Demod. 16 Pin	325p
NE562	PLL with VCO 16 Pin	325p
NE563	PLL FM/IF Demod. 16 Pin DIL	325p
NE565	PLL 14 Pin DIL	325p
NE566	Function Generator 8 Pin DIL	200p
NE567	PLL Tone Decoder 8 Pin DIL	250p
TBA570	AM/FM Radio receiver	180p
TBA800	5 Watt Audio Amp.	90p
TBA810	7 Watt Audio Amp.	100p
TBA820	2 Watt Audio Amp.	80p
ZN414	TRF Radio Receiver	119p

SCR-THYRISTORS

1A	50v 100v 400v 600v	2N3525	81p
1A	40p 42p 50p 70p	2N4444	185p
3A	43p 49p 75p 100p	2N5060	40p
7A	80p 84p	2N5082	45p
16A	250p 450p	2N5064	50p
Other			
BT106	140p	C106D 45p	MCR101 25p
BT100	BI-DIRECTIONAL TRIGGER FOR SCRs and TRIACS		21p

Popular Op Amps

709	OPA with ext. comp.	8/14 pin DIL	30p
710	Diff. Comparator	14 pin DIL	35p
741	OPA with int. comp.	8 pin DIL	25p
747	Dual 741	14 pin DIL	70p
748	OPA with ext. comp.	8 pin DIL	30p
5001	12 Digit Calculator Chip	28 pin DIL	480p
PC	Keyboard 0-9, decimal, 4 function, C, K, keys. Size: 2.38" x 3.75" x 0.43"		400p

TRIACS

100V	400V	500V
3A	85p	95p
6A	88p	120p
10A	109p	154p
16A	145p	180p
Other		
40430	90p	40486 95p, 40669 95p

I.C. MOS LOGIC

CD4000AE	18p
CD4001AE	18p
CD4002AE	18p
CD4009AE	67p
CD4011AE	21p
CD4013AE	63p
CD4018AE	63p
CD4017AE	163p
CD4022AE	160p
CD4023AE	21p
CD4024AE	116p
CD4027AE	91p
CD4028AE	140p
CD4029AE	106p
CD4046AE	202p
CD4047AE	137p
CD4054AE	190p
CD4080AE	228p
CD4071AE	26p
CD4061AE	28p
CD4510AE	120p
CD4511AE	250p
CD4528AE	128p

DIODES

BY100	15p
BY126	12p
BY127	12p
CA47	7p
CA70	7p
OA79	7p
OA81	7p
OA85	9p
OA90	6p
OA91	6p
OA95	7p
OA200	6p
OA202	7p
IN914	4p
IN4001	3p
IN4004	6p
IN4007	7p
IN4148	4p

LED

TIL209 16p

ZENERS

3-3V to 33V	9p
400mW	18p
1-3W	18p

A Tunnel

AEY11 50p

Varicap

BB105 30p

Noise

ZIJ 75p

BRIDGE RECTIFIERS

0.25A - 20V	100V	400V	600V
1A 22p	24p	27p	29p
2A 30p	35p	45p	48p
4A - 55p			
6A 35p	60p		

OPTO-ELECTRONICS

ORP12	50p	
ORP60	60p	
ORP61	90p	
ORP61	90p	
2N5777	40p	
TIL209	with clip	16p
Green/Yell.	with clip	35p
LIT700 0-33 in	DIL	130p
LIT707 0-33 in	DIL	135p
LIT747 0-63 in	DIL	210p
MAN-3M	0-127 in PCB	120p
MAN-4	0-19 in DIL	180p

NEW VAT RATES

25% on TRANSISTORS, DIODES, BRIDGES, OP. AMPS and RADIO, AUDIO and TV I.C.s.
 8% all others (TTLs, C.MOS, V.Rs, SCRs, TRIACS, OPTO. and many LINEAR I.C.s)

54 SANDHURST ROAD, LONDON, NW9
 Tel. 01-204 4333

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call in on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course". Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects"—Student J.A.O. Dublin.

"My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to

ALDERMASTON COLLEGE

Dept. TPW07, Reading RG7 4PF.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> ELECTRICAL ENGINEERING City & Guilds Wiring and Installations C. G. Electrical Tech-Primary Gen. Electrical Eng.	<input type="checkbox"/> Practical Radio & Electronics (with self-build kit) Radio Amateurs' Exam	<input type="checkbox"/> Construction Surveyor's Inst. Clerk of Works Diploma <input type="checkbox"/> C. & G. Building Quantities <input type="checkbox"/> General Building <input type="checkbox"/> General Civil Eng. Heating, Ventilating & Air Conditioning <input type="checkbox"/> Carpentry & Joinery <input type="checkbox"/> Painting & Decorating <input type="checkbox"/> Plumbing
<input type="checkbox"/> AERONAUTICAL ENGINEERING Air Registration Board Certificates Gen. Aero Engineering	<input type="checkbox"/> ELECTRONIC ENGINEERING Gen. Electronic Eng. Practical Electronics (with kit)	<input type="checkbox"/> C.E.I. (Part 1) Inst. Cost & Management <input type="checkbox"/> Accountants <input type="checkbox"/> Works Management etc. etc.
<input type="checkbox"/> AUTO ENGINEERING City & Guilds Auto Engineering Practice Inst. Motor Industry M.A.A./L.M.I. Management Diploma Gen. Auto Engineering Auto Diesel Maintenance Motor Mechanics Service Station and Garage Management	<input type="checkbox"/> AGRICULTURAL ENGINEERING	<input type="checkbox"/> REFRIGERATOR SERVICING
<input type="checkbox"/> TELECOMMUNICATIONS City & Guilds Telecommunications	<input type="checkbox"/> MECHANICAL ENGINEERING Society of Engineers Inst. Engineers and Technicians General Mechanical Eng. Welding Maintenance Eng. General Diesel Eng.	<input type="checkbox"/> draughtsman-ship Institute of Engineering Draughtsmen & Designers General Draughtsmanship Architectural Draughtsmanship Technical Drawing
<input type="checkbox"/> RADIO & TV Gen. Radio and TV Eng. Radio Servicing, Maintenance and Repairs	<input type="checkbox"/> CONSTRUCTION & BUILDING Institute of Building	

G.C.E.
—58 'O' & 'A'
Level Subjects
—over 10,000
Group Passes!

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College,
Dept. TPW07, Reading RG7 4PF.

NAME

Block capital please

ADDRESS

POSTCODE

OTHER SUBJECTS

AGE

Accredited by C.A.C.C. Member of A.B.C.C.

the wireless tecknowledgedgy page

Pure Wireless has been the Cinderella of electronic component supplies for some time now. Things like coils, ceramic and mechanical filters, linear phase arrays, complete IF systems and tuners haven't been available from a single source until now. We call it the Ambit 'One stop Wireless Service'.

The All Electric Wireless

One of the most significant developments in radio for years - available from AMBIT.

PW Apollo AM varicap tuner module:

MVAM1, CA3123E, 1N4148.....£4.00

Coils/filter pack for MW.....£1.40

PCB.....£0.75; All components and PCB.....£8.00

6 Button preset bank by IMI £3.40

150 mm WW slider potentiometer £3.00

MVAM 1 : £2.75 (inc.data) MVAM 2 : £1.05

Linear and radio ICs:

CA3089E+det.coil £1.94, CA3090AQ+coil £3.75.

CA3123E £1.40, MC1310P £2.20, SN76660N £1.00

ICL8038CC £3.10 μ A7805UC £1.55,

TBA651 £1.81, LM380N £1.00, LM381N £1.85

NE560/1/2/3 £3.19, NE566 £2.55, NE567 £2.75

μ A78L12 45p, μ A78M20 £1.40, μ A7818 £1.55

TBA810 S + heatsink £1.30 μ A753 £0.99

Sundry:

IC sockets: 8 pin DIL 15p

14 DIL 16p

16 DIL 16p

AM coils 27p each, FM coils 30p each, 10.7 MHz linear phase IF filters £1.35 each, ceramic filters 40p, 19 & 38 kHz pilot tone notch filters for MPX £1.60.

Ambit modules for Wireless:

91200: New double linear phase WBFM IF amplifier with double tuned detector stage, mute, meter op, AFC Built £9.00; kit £6.20.

FM1185: Low cost FM IF with ceramic IF filter, CA3089E, muting, meter op, AFC. Built and tested £4.35.

AM/FM 3042: A new FM/AM radio board. FM section contains two ceramic filters, IC IF gain block, IC limiter and ratio detector. AM section uses an IC with ceramic IF filter and Ferrite rod. Can be used with various of our tunerheads to provide a truly high specification low cost AM/FM tuner. There is provision on the board for the CA3090AQ stereo decoder IC for FM.

kit for Mono FM/ AM £14.00

stereo FM/ AM £19.00

Tunerhead extra: AM section may be tuned electronically by the MVAM2, or by a mechanical gang capacitor .

LARSHOLT 7252 Tunerset £20.00 - the complete antenna to audio FM varicap radio system.

All Radio Components have 25% VAT as from May 1st.

Please note that we cannot deal with any enquiries unless accompanied with a stamped addressed envelope of adequate dimensions. Thankyou.

EF5603 £8.40



A major aspect of our 'one stop' wireless facility revolves around Ambit's association with TOKO - the world's largest coil and filter manufacturer.

As the major source of TOKO information and products in the UK and European consumer electronics market: AMBIT is also pleased to supply and advise professional and OEM buyers. Please ensure that your enquiry is directed to the 'OEM Division'.


RET TOKO.

Illustrated here are various TOKO items, ranging from delay lines, through the famous MFH mechanical filters to the varicap tuner-heads, EF5603, EC3302.

CFT AM ceramic filter 45p (455 or 470 kHz)



EC3302 £5.00

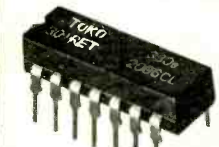

RET delay line POA



7BA choke
1 μ H to 1mH 15p



Variable capacitors



MFH £1.45



S 18

ambit international

CWO please. Prices Exclude VAT. P&P now 20p. Min.order £1.00. Min Invoice £7.50. Catalogue 40p shortform price list free with SAE

37 High Street, Brentwood, Essex. CM14 4RH. tel. 216029 tlx. 995194