

PRACTICAL WIRELESS

MARCH
1977

40p

FREE INSIDE!

PRACTICAL WIRELESS MAR 1977

RESISTORS & CAPACITORS

INFO-CARDS

5

HERE'S THE FIRST!

Pw

fm

stereo

touch tuner

PART 1



also:

Easytune MW-LW Receiver
Practical Audio Amplifiers

RADIO EXCHANGE LTD.

**ALL PRICES
INCLUDE VAT**

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit. Build these projects without soldering iron or solder



Total Building Costs **£9.00**
P & P + Ins. 85p.

- ★ 4 Transistor Earpiece Radio
- ★ Signal Tracer
- ★ Signal Injector
- ★ Transistor Tester
- ★ 4 Transistor Push Pull Amplifier
- ★ 5 Transistor Push Pull Amplifier
- ★ 7 Transistor Loud-speaker Radio MW/LW
- ★ 5 Transistor Short Wave Radio
- ★ Electronic Metronome
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Regenerative Radio
- ★ Audible Continuity Tester
- ★ Sensitive Pre-Amplifier

Components include: 24 Resistors ★ 21 Capacitors ★ 10 Transistors
 ★ 5" x 3" Loudspeaker ★ Earpiece ★ Mica Baseboard ★ 3 12-watt connectors
 ★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ 3 Knobs
 ★ Ready Wound MW/LW/SW Coils ★ Ferrite Rod ★ 6½ yards of wire
 ★ 1 Yard of sleeving, etc. Complete kit of parts including construction plans.

VHF AIR CONVERTER KIT

Build this Converter Kit and receive the Aircraft Band by placing it by the side of a radio tuned to Medium Wave or the Long Wave Band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome plated telescopic aerial, Gain Control, V.H.F. Tuning Capacitor, Transistor, etc.




All Parts including Case and Plans. **£3.95**
P & P and Ins. 45p.

NEW ROAMER TEN MODEL R.K.3.

MULTIBAND V.H.F. AND A.M. RECEIVER
13 TRANSISTORS AND FIVE DIODES
QUALITY 5" x 3" LOUDSPEAKER

WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Slow Motion Drive Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W., Three Short Wave Bands, S.W.1, S.W.2, S.W.3, and Trawler Band. Built in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc. Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push Pull output using 600mw Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Negative Feedback circuit and SPECIAL POWER BOOSTER SOCKET AND RESISTOR, to virtually double gain if required. Powered by P.P.9 9 volt battery.

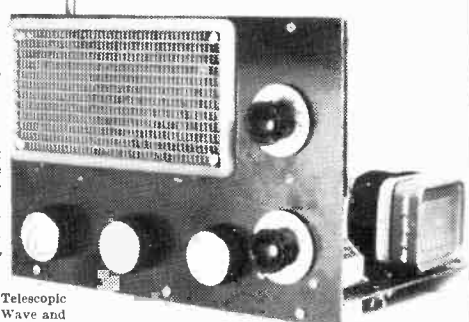

Complete kit of parts including carrying strap. Building instructions and Operating Manuals. **£13.99** Including Post and Packing
 Case Enclosure Kit (if required) £1.80 inc. P & P.


POCKET FIVE

NOW WITH 3" LOUDSPEAKER
3 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3½" approx. All Parts including Case and Plans. **£3.60**
P & P + Ins. 60p.



NEW Everyday Series

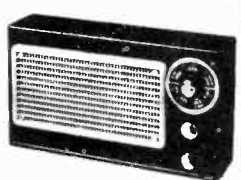Build this exciting new series of designs.




E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 6½" x 2½" approx. All parts including Case and Plans. Total Building costs **£4.30** P & P + Ins. 60p.

E.V. 6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. All parts including Case and Plans. Total Building costs **£4.95** P & P + Ins. 65p.


E.V. 7. Case and looks as above, 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. All parts including Case and Plans. Total Building costs **£6.95** P & P + Ins. 70p.

ELECTRONIC CONSTRUCTION KITS

ECK2 Self Contained Multi-Band V.H.F. Receiver Kit. 8 Transistors and 3 Diodes. Push/Pull output. 3" Loudspeaker, Gain Control. Superb 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. Tuning Capacitor, Resistors, Capacitors, Transistors, etc. Will receive T.V. Sound, Public Service Band, Aircraft, V.H.F. Local Stations, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans. **£7.95** P & P and Ins. 70p.

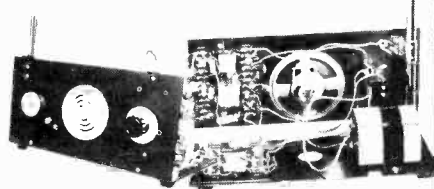


ECK4 7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands. Receiver Kit. With 5" x 3" Loudspeaker. Push/Pull output stage, Gain Control, and Rotary Switch. 7 Transistors and 4 Diodes. 6 section chrome-plated telescopic aerial. 8" Sensitive Ready Wound Ferrite Rod Aerial. Tuning Capacitor, Resistors, Capacitors, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans. **£7.25** P & P and Ins. 70p.

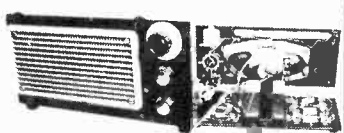

EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage — No Battery necessary.
 - ★ One Transistor Radio.
 - ★ 2 Transistor Regenerative Radio
 - ★ 3 Transistor Earpiece Radio Medium Wave Coverage
 - ★ 4 Transistor Medium Wave Loudspeaker Radio.
 - ★ Electronic Noise Generator
 - ★ Electronic Metronome.
 - ★ 4 Transistor Push/Pull Amplifier.
- All parts including Loudspeaker, Earpiece, MW Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans. **£6.55** P & P + Ins. 60p.

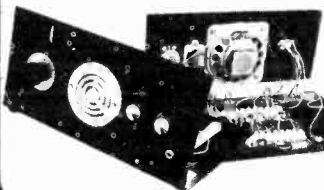

To RADIO EXCHANGE LTD
61A HIGH STREET, BEDFORD MK40 1SA
Tel: 0234 52367

ALL PRICES INCLUDE VAT Reg. No. 788372
 ★ Callers side entrance "Lavelis" Shop.
 ★ Open 10-1, 2.30-4.30. Mon-Fri. 9-12 Sat.

I enclose £
 for
 Name
 Address

PRACTICAL WIRELESS

VOL. 52 NO. 11

ISSUE 841

MARCH 1977

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Terry Carter

PRODUCTION & NEWS EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Linda Walji

Jill Austin

ADVERTISING MANAGER

01-634 4383

Roy Smith

CLASSIFIED ADVERTISING

01-261 5762

Colin R. Brown

PLEASE NOTE: We do not operate a Technical Query Service except on matters concerning constructional articles published in PW. We do not supply service sheets or information on commercial radios, TV's or electronic equipment.

All queries must be accompanied by a stamped, self-addressed envelope otherwise a reply cannot be guaranteed. Send letters concerning advertising matters to the Advertising Manager, Roy Smith.

Send letters concerning editorial matters to the Editor, Lionel Howes.

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. Tel. 01-634 4444

BINDERS

Binders £2-10 and indexes 45p (inc. VAT) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1977. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

920 LEADER ARTICLE—Lend A Hand

920 NEWS . . . NEWS . . . NEWS . . .

934 LETTERS—Comments from PW Readers

937 PRODUCTION LINES—Bill Tull

939 NEXT MONTH IN PRACTICAL WIRELESS

948 HOTLINES—Recent Developments—Ginsberg

949 TELEVISION—What's in the March issue

955 KINDLY NOTE—Chromachase parts 1 & 2 (Dec. '76/ Jan '77), Oscilloscope calibrator Jan. '77

956 PW READERS PCB SERVICE

961 ON THE AIR—Amateur Bands—Eric Dowdeswell G4AR

Broadcast Bands SW—Derek Bell

Broadcast Bands MW—Charles Molloy

● CONSTRUCTIONAL

922 CIRCUITS FOR AUDIO AMPLIFIERS part 1—

F. G. Rayer G30GR

928 VIDEO-WRITER part 8—M. J. Hughes, MA, C.Eng., MIERE

Note:—The UHF Modulator, mentioned in Part VII of the Video-Writer has had to be held over till April due to pressure of space.

940 FM STEREO TUNER part 1—Francis How (BA Cantab.)

950 EASYTUNE MW-LW RECEIVER—F. G. Rayer

957 S-DeC PROJECTS No. 4—'Passionometer'—David Gibson

● OTHER FEATURES

925 SPECIAL PRODUCT REPORT—Heathkit HW8 QRP

Transceiver

938 TECHNICROSS—Puzzle No. 18

FREE THIS MONTH!
YOUR FIRST DOUBLE SIDED INFO-CARD
—See page 938 for full details

Can YOUR Antenna do all this?

A SMALL SELECTION FROM OUR HUGE FILE OF TESTIMONIAL LETTERS ON THE JOYSTICK VARIABLE FREQUENCY ANTENNA (.5-30MHz)

G4DJY's COPY LOG shows 68 North Americans worked in the ARRL W/VE contest.

W6TYP worked WA6JPR over hundreds of miles on 40m. using the JOYSTICK VFA and MICRO-WATTS "equivalent to 1,000,000 MILES PER WATT"—A WORLD RECORD—we can supply conclusive evidence!

"I have used Rhombics, 4 x 1/2 waves in phase, centre fed dipoles, etc., but the success I have had with the V.F.A. has been AMAZING . . . only 20ft high . . . in front of my mobile home, I NEVER RECEIVE LESS THAN R7 AND MOSTLY R9 ON CWDX WORKING—Bob Green, SUIKG/G3APH. W.B.E. W.A.C. Phone & C.W.

W7OE U.S.A. Government Electronics Engr. (ret'd.), claims "VFA 5ft below ground, same as dipole, elevated 15ft, one "S" point UP on dipole".

SYSTEM 'A' £32.40
250 w.p.e.p. OR for the SWL.

SYSTEM 'J' £38.60
500 w.p.e.p. (improved 'Q' on receive).

PARTRIDGE SUPER PACKAGES

COMPLETE RADIO STATIONS FOR ANY LOCATION

All Packages feature the World Record Joystick Aerial (System 'A'), with 8' feeder, all necessary cables, matching communication headphones. Deliv. Securicor our risk. Assembled in seconds! BIG CASH SAVINGS!

PACKAGE No. 1 As above with R.300RX £210.55
SAVE £13.87!

PACKAGE No. 2 Is offered with the FRG7 RX. £193.11
SAVE £13.87!

FLASH!

PACKAGE No. 3 New—low priced package. £154.86
The all solid state SMC73 RX with all the Partridge extras. SAVE £26.05 plus!

RECEIVERS ONLY, inclusive delivery, etc.

R.300 £184.50 FRG7 £167.06 SMC73 £128.81

All prices are correct at time of going to press and carry VAT current at the time and carriage.



Just telephone
your
card number



Phone 0843 62535 (or 62839 after office hours)



Box 5, Partridge House, Prospect Road, Broadstairs, CT10-1LD. (Callers by appointment).

YES SIR 1st class post TONIGHT!
The service is available to anyone
that opens an account.



HIGH SPEC components FAST!

Agents for VERO - ANTEX -
BIB MULTICORE SOLDER

- Open 9am-5pm, 5 days—Phone orders 9am-4pm.
- S.A.E. for stock list including pots, presets, I.C.'s 7400 & CMOS.
- capacitors, plugs, sockets, switches, cable, etc.
- Post free envelope included for your next order.
- SUPER EXPRESS phone service—ask for details.
- Shop at keen prices 6 days per week. Late night—Fri. 7-10pm.

TRANSISTORS + 200 OTHER TYPES IN STOCK

AC125 20p	BC109 12p	BC262A 19p	BFX29 20p	TIP41A 67p
126 20p	109B 13p	287 28p	84 22p	42A 80p
127 28p	109C 13p	300 35p	88 22p	TIS43 35p
128 20p	117 18p*	301 34p	BFY50 25p	ZTX300 13p*
151 35p	142 24p	303 35p	51 25p	302 18p*
153 35p	143 24p	338 18p*	52 25p	500 15p*
176 22p	147A 9p*	557 15p*	BY164 40p	502 18p*
187 22p	147B 10p*	BCY71 18p	ME0401 18p*	1N914 5p
188 20p	148 9p*	72 14p	0411 18p*	1N4001 5p
AD149 60p	148B 10p*	BD123 90p	ME4001 10p*	4002 6p
161 52p	149B 11p*	124 90p	4101 11p*	4005 8p
162 52p	149C 11p*	131 42p	MPF102 48p*	4006 10p
MCH/PR 1-24	154 18p*	132 42p	OA47 14p	4148 5p
AF116 24p	157B 12p*	139 54p*	90 7p	2N2219 30p
117 24p	177 17p	155 75p*	91 8p	2646 45p
124 30p	178B 18p	BF158 20p*	200 10p	2920 13p*
239 48p	179B 19p	184 25p	OC28 1-20	2928G 15p*
AU113 1-72*	184B 12p*	185 28p	29 1-20	3053 25p
BC107 11p	184L 11p*	194 18p*	35 1-20	3055 60p
107A 12p	187 26p	196 12p*	44 45p	3702 11p*
108 10p	212A 13p*	197 12p*	71 35p	3703 14p
CI108 9p	212L 15p*	199 15p*	ORP12 68p	3704 13p*
BC108B 11p	213B 12p*	200 30p	TIP29A 47p*	3705 14p
108C 12p	214 15p*	338 34p	30A 58p*	3707 12p
	214L 17p*	BFW11 60p	31A 37p	3819E 25p*

DIODES	BRIDGES	RESISTORS 1/2p each	LINEAR I/C's
50V 3A 13p	100V 1A 28p	1/2 WATT E12 (5%)	741
100V 3A 15p	200V 1A 30p	1 ohm - 10m ohm	LM380 SL607451-28*
200V 3A 18p	400V 1A 32p	ZENERS (400mw) BZX 83	LM3900N
400V 3A 21p		3V, 3V3, 5V1, 5V6, 7V5,	NE555
THYRISTORS		9V1, 10V, 12V, 18V, 22V,	SN76013ND 1-60*
60V 1A 20p		30V. All at 12p* each.	SN76013N 1-75*
600V 1A 60p TAG 1 600		LED T11 209/0-125 0-2"	TBA800 1-35*
700V 1A 1-20 BT106		Red 20p	TBA810S 1-49*
400V 4A 50p C106D1		Grn 29p	TA820 1-28*
500V 6A 1-25 BT109		Clips for above 2p.	ZN414 1-60*

Post & Packing 25p per order. VAT please add to total + 1 1/2%, rest 8%

ORCHARD ELECTRONICS


FLINT HOUSE, HIGH STREET, WALLINGFORD, OXON, OX10 0DE
Telephone 0491 35529.

Doram kits

DORAM KITS CONTAIN
EVERYTHING DOWN TO
THE LAST NUT!

ELECTRONIC CAR IGNITION

£9.95
+ S

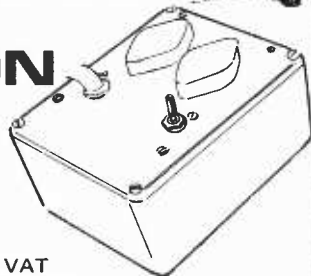

£9.95 + S VAT

(Order code 997-005)

Subject to availability

Avoid difficulty in starting your car on cold mornings with the Doram C.D. Ignition Unit. The complete kit incorporates features such as single switch reversion to the standard ignition system for servicing etc. and also an immobilisation facility. Improved performance and fuel consumption, along with reduced points erosion and longer plug life makes this unit a must for any 12V neg. earth car.

O'seas orders—add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2x25p vouchers, each one usable on any order placed to the value of £5 00 or more (ex. VAT).

DORAM ELECTRONICS LTD

P O BOX TR8 WELLINGTON RD IND. EST LEEDS LS12 2UF

An Electrocomponents Group Company

RSC 100 WATT DISCO SYSTEM

50 WATT SPEAKER

AT FANTASTIC LOW PRICES!

50 WATT SPEAKER

HEADPHONES MICROPHONE

TWIN TURNTABLE WITH PRE-AMP and POWER AMPLIFIER Complete with lid

40 WATT SYSTEM £99-95. 200 WATT SYSTEM £209-95
OTHERS UP TO 300 WATTS AT UNBEATABLE PRICES

DISCOMAJOR TWIN TURNTABLE POWER CONSOLE £129-95

Twin Full size BSR turntables. Sonotone or Acoas Cartridges with Diamond Stylis. Facilities as TD1 Console but with built-in 100 watt Power Amplifier complete with lid. Terms: Deposit £19-95 and 18 fortnightly payments. 27-08 (Total £148-49)

Stereo Version £179-95 Carr. £3 or Deposit £28-95 and 18 fortnightly payments 29-79 (Total £201-55)

RSC PHANTOM 50 COMBO AMP. £69-95

Rating 50 watts. 3 inputs, 2 vol. controls—Bass, Treble Presence. Carr. £1-50 Suitable for Lead or Rhythm Guitar, mic., Radio, Tape etc. Inc. High Flux 12" 50w Speaker. Dep. £10-95 & 8 monthly payments £8-71 (Total £50-63)

POWER (SLAVE) AMP 100 WATT

Suitable for use with DISCO-Consoles. Also for increasing output of lower-powered AMP. Dep. £9-00 and 8 monthly payments £6-05 (Total £57-40) Carr. £1

TITAN TA/50A 50W AMPLIFIER

Solid state, 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynide covered cab. Dep. £9 & 8 monthly payments £6-05 (Total £57-40) Carr. £1

TITAN TA/100A TWIN CHANNEL AMP. 100 WATT R.M.S. OUTPUT

De-luxe Professional unit with many facilities. Dep. £14-00 & 12 monthly payments £5-80 (Total £81-20)

TITAN TA/50A WITH 70W TWIN SPEAKER UNIT

Vynide covered. Fitted protective corner pieces. Dep. £14-95 & 18 fortnightly payments £5-15 (Total £107-65)

TITAN TA/100A WITH 100 WATT TWIN SPEAKER UNIT

For all purposes Inc. Bass Guitar. Terms: Dep. £17-95 & 18 fortnightly payments £6-69 (Total £139-37)

RSC TRANSFORMERS, L.F. CHOKES

MIDGET CLAMPED TYPE 900-950V 50 Hz
250V. (Or 250-0-250V) 60mA 6-3v. 2a. £1-75
STD. UPRIGHT MOUNTING OR DROP-THERO
250-0-250V. 100mA 6-3v. 4a. 0-5-6-3v. 3a. £4-35
300-0-300V. 150mA 6-3v. 4a. C.T. 6-3v. £5-30
1a. for Mullard 610 Amplifier £5-30
350-0-350V. 100mA 6-3v. 4a. 0-5-6-3v. 3a. £4-35
350-0-350V. 150mA 6-3v. 4a. 0-5-6-3v. 3a. £5-30
425-0-425V. 200mA 6-3v. 4a. C.T. 5v. 3a. £9-85
" 200mA 6-3v. 4a. 6-3v. 4a. 5v. 3a. £10-00
450-0-450V. 250mA 6-3v. 4a. O.T. 5v. 3a. £10-45
500-0-500V. 70mA 6-3v. 2a. 0-5-6-3v. 3a. £2-90
250-0-250V. 100mA 6-3v. 3a. £2-90
250-0-250V. 100mA 6-3v. 2a. 6-3v. 1a. £3-30
350-0-350V. 80mA 6-3v. 2a. 0-5-6-3v. 2a. £3-30
300-0-300V. 100mA 6-3v. 4a. 0-5-6-3v. 3a. £4-35

FILAMENT OR TRANSFORMER POWER PAOK
13v. 1a. £1-10; 6-3v. 1.5a. £1-05; 6-3v. 2a. £1-10.
6-3v. 3a. £1-70; 6-3v. 5a. £2-60; 12v. 3a. or 24v. 1.5a. £2-60
0-1-18v. 1.5a. £2-25; 0-12-25-42v. 2a. £3-19
CHARGER TRANS 0-9-15v. 1.5a. £2-03; 2.5a. £2-26; 3a. £2-32; 5a. £2-84; 6a. £2-19; 8a. £2-48.

FULLY GUARANTEED. Improv. and Interlocked where necessary. AUTO (STEP UP/STEP DOWN) TRANSFORMERS 0-110/120V 200-230-250V. 80w. £2-90; 150w. £5-20; 250w. £6-37; 500w. £9-84.

OUTPUT TRANSFORMERS
Pentode 5000 or 7000 to 3Ω £1-18;
Push Pull 8w EL84 to 3 or 15Ω £1-61;
£1-68; 12w 6V6 to 3 or 15Ω £2-61;
12w 6V6 to 3, 8 or 15Ω £2-72;
EL84 to 3 or 15Ω 12w £2-61; Ultra Linear for Mullard 810 etc. £4-35;
18w. sect. wound 6L6, KT66 etc. to 3 to 15Ω £3-71; 20w. sect. wound EL34, 6L6, KT66 etc. to 3 or 15Ω £6-37.

L.F. CHOKES 150mA, 7-10H, 250Ω £1-28; 100mA, 10H, 200Ω £1-10; 60mA, 10H, 400Ω £1p.

ALL RSC PRICES INCLUDE VAT

DISCOMAJOR POWER DISCO CONSOLE

with Integral Power Amplifier. Twin Jack output sockets.

TWIN FULL SIZE B.S.R. TURNTABLES

with cueing device. Cartridges with Diamond Stylis. Separate volume controls each turntable. Full Headphone Monitoring Facilities.

PAIR OF 50 WATT L'SPEAKERS

Black Vynide covered cabinets. Approximate size 15" x 18" x 8".

COMPLETE WITH MICROPHONE PACKAGE PRICE £169-95

(Including VAT) Headphones extra. Carr. £4. Deposit £30.00 & 18 fortnightly payments. £9-18 (Total £195-24)

STEREO VERSION £219-95

of above system. Dep. £45-95 & 18 fortnightly payments £11-50 (Total £282-95). Carr. £5.

TD1M DISCO CONSOLE

Incorporating twin BSR MP00 type turntables and Sonotone or Acoas Cartridges with diamond stylis. Separate Vol. controls for each turntable. Also MONITORING FACILITIES plus Treble and Bass Controls. Separate input for 'mike' with vol. control. Black Vynide covered Cabinet with lid. Or DEP. £17-95 and 18 fortnightly payments £8-52 (Total £135-31) Carr. £1-50

TD2S STEREO VERSION OF ABOVE £125-00

Terms DEPOSIT £20 and 18 fortnightly payments £6-89 (Total £144-02) Carr. £2-00

TITAN 100W BASS BINS £99-95

High quality 16" high type Bass Unit and J104 Horn Tweeter in folded horn type enclosure to provide amazing level of sound output. List price £144 Terms Dep. £14-95 and 18 fortnightly payments £5-88 (Total £115-39) Carr. £3.

FANE HIGH POWER SPEAKERS

Power ratings R.M.S. Cont. 2 YRS GUARANTEE *Gauss 14000 Imp 8-15 ohms. CARR FREE.

*POP 33T 12" 33w £13-95 Dual cone. Full range

*POP 50/12" 50w £15-99 Dep for Pair £8-00 and 8 monthly payments £3-54 (Total £36-32)

*POP 60 15" 60w £25-95 Dep £7-00 & 8 monthly payments £2-87 (Total £29-96)

*POP 100 18" 100w £44-95 Dep £10-00 & 8 monthly payments £5-17 (Total £51-36)

TITAN GROUP/DISCO SPEAKERS GUARANTEED FOR 5 YEARS

Rating R.M.S.	List Price	RSC Price
T12/35 12" 45w	£21-00	£10-95
T12/60A 12" 60w	£26-00	£13-95
T12/100 12" 100w	£36-00	£24-95
T15/60 15" 60w	£28-00	£18-99
T15/70 15" 70w	£28-00	£19-95
T15/100 15" 100w	£41-00	£28-95
T18/100 18" 100w	£47-00	£32-95

Impedance 8-16 ohms

MODEL	MONTHLY DEPOSIT	PAYMENTS	TOTAL
Model T12/35 (Pair)	£5-50	& 8 at £2-56	£25-98
Model T12/60A (Pair)	£7-50	& 8 at £3-01	£31-58
Model T12/100 (Each)	£5-50	& 8 at £2-94	£29-02
Model T15/60 (Each)	£4-50	& 8 at £2-32	£25-06
Model T15/70 (Each)	£4-50	& 8 at £2-37	£25-06
Model T15/100 (Each)	£7-00	& 8 at £3-39	£34-12
Model T18/100 (Each)	£7-95	& 8 at £3-69	£37-47

CABINETS FOR ABOVE SPKRS £10-95

Heavy duty. Beautifully finished FROM black Vynide with Vynair fronts fitted protective corner pieces. Various sizes and cut-outs.

50W H.F. HORNS

Imp. 8Ω. Range 3-15 KHz. Very sensitive. Complete with Fane H.F.3 'X-over' Pair for series wiring plus single 'X-over'. £17-95

FANE J104 50-70w

Imp. 8Ω. 3-15 KHz. Super sensitive 10" x 4" approx. Complete with 'X-over' Use with twin 12" 15Ω or single 15" or 18" 8Ω speakers. £15-50

TITAN H.F. UNITS

Inc. pair of Highly Sensitive Horns. Range 3-15 KHz. Rating 70/100 watt. Use with 2 x 12" 8Ω speakers in series, or single 15" or 18" 15Ω Dep. £6-95 & 8 monthly payments £3-12. (Total £31-91). Carr. 75p.

FAL SOUND-TO-LITE UNIT £21-60 COMPLETE SYSTEM £58-95

Incl. 2 Spotbanks and bulbs

JINGLE MACHINES from £37-95

ECHO CHAMBERS from £49-95

COLUMN SPEAKERS from £29-95

GROUP/DISCO SPKRS in CABS from £11-95

New Branches at YORK, HANLEY, CARLISLE, LIVERPOOL, PRESTON

Barclaycard and Access accepted

All items subject to availability. Prices correct at 12.1.77 E. & O.E.

GLASGOW 326 Argyle St. (Cl'd Tues.). Tel. 248 4158

HANLEY, Stoke-on-Trent, 44 Piccadilly

HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505

LEICESTER 32 High Street (Closed Thurs.). Tel. 56420

LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252

LIVERPOOL 35 Dawson's Way, St. John's Shopping Centre, Tel. 708 9380 (Cl. Wed.). (Closed Thurs.).

LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2776

MIDDLESBROUGH 103 Linthorpe Rd. Tel. 210585 (Closed Wed.)

NEWCASTLE UPON TYNE 59 Grainger St. (Closed Wed.) Tel. 21469

NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 46868

PRESTON 41 Friargate Walk, St. George's Shopping Prec. Tel. 81978

SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20716

STOCKPORT a Little Underbank (Closed Thurs.). Tel. 480-9777


SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70873

YORK, 5 CHURCH ST. (Closed Wed.) Tel. 34355

MAIL ORDERS & EXPORT ENQUIRIES TO:-
AUDIO HOUSE, HENRIKHOORN LANE, LEEDS, 19. Tel: 0512 577631.
MAIL ORDERS MUST NOT BE SENT TO SHOPS
TERMS C.O.D. or G.O.D. or O.O.D. under £1.
POSTAGE 40p PER ORDER OR AS QUOTED.
PLEASE SEND STAMP FOR FREE CATALOGUE.

OPEN ALL DAY SATURDAYS (5 Day Week)
BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
BOLTON 23 Deansgate (Closed Wed.). Tel. 33512
BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.)
CARLISLE 8 English Street. (Closed Thurs.). Tel. 38744
COVENTRY 17 Shelton Sq., The Precinct. Tel. 25683
DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361
DARLINGTON 19 Northgate (Cl. Wed.). Tel. 88043
DEWSBURY 9/11 Kingsway (Closed Tues.). Tel. 468058
DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069
EDINBURGH 101 Lothian Rd. (Cl. Wed.). Tel. 226 9501

INVERTORS

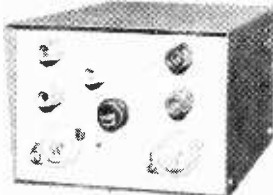

240v-50Hz from your 12v car battery

25 watt-£4-75 300 watt (12v)-£33-08
40 watt-£8-27 400 watt (24v)-£39-05
75 watt-£12-03 500 watt (24v)-£48-18
150 watt-£21-27 1 Kw (50v)-£127-00
300 watt (24v)-£26-45 1.5 Kw (110v)-£140-00

All above invertors are in kit form but may be purchased built up in metal case and ready for use. Price list sent on receipt of s.a.e. Prices include p. and p.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt Inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £24-50 plus £1-70p.p.


DIGITAL WATCH

FOUR FUNCTION DIGITAL WATCH FOR ONLY £16 with 1 Year Guarantee HOURS . MINS. . SECONDS . DATE American Design, UK Manufacture.

TRANSFORMERS AND COILS

Both high volume and small order capacity available. Special offer. Miniature mains transformer 6-0-6v-6vA. 85p + 10p p. & p.

P.E. ORION STEREO AMPLIFIER & TUNER

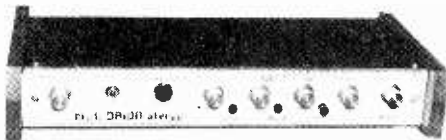

20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response ± 1 dB 20 Hz to 20kHz. Hum level virtually nil with volume full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.

Complete kit of parts including slim line bookend case, silk screened front panel and knobs £48-60 inc. VAT and p. & p.

The bookend case, I.C.'s and semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information.

P.E. ORION TUNER UNIT

PARTS MAY BE PURCHASED AS FULL KIT OR SEPARATE ITEMS. SEND S.A.E. FOR DETAILS.

N.B.—DELIVERIES ON ALL ITEMS MAY TAKE UP TO 28 DAYS, DEPENDING ON AVAILABILITY AND DEMAND. CASH IN REGISTERED ENVELOPE OR POSTAL ORDERS CAN REDUCE TIME by NOT HAVING TO CLEAR CHEQUES

ASTRO IGNITION



ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £10-45 inc. VAT Ready built with only two connections to alter £13-75 inc. VAT. Thousands have used this system both home and abroad. Consider these advantages—more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth.

TRADE and EXPORT ENQUIRIES WELCOMED ON ALL PRODUCTS

ASTRO ELECTRONICS
Springbank Road, West Park
CHESTERFIELD. 31475

VALVE BARGAINS

Any 5-64p, 10-£1-20, 50-£5-00. Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL86, PCL805, PL504, PY81/800, PY88, 30PL-14, 6F28.

Colour Valves—PL508, PL509, PL519, PY500/A. All tested. 35p each.

Aerial Splitters—2 way, 75 OHMS, Inside Type, £1-50

Press Button UHF Tuners—4 Button Transistor—British made—£2-50 each.

60p BARGAIN PACKS

All Packs Un-used Parts—PK1-40-C280 (Mullard) Axial Lead Capacitor mixed values from .01 μ F to .47 μ F (250V/W). PK2-30-C281 (Mullard) Radial Lead Capacitors mixed values from .015 μ F to 1.5 μ F (250V/W). PK3-6 Co-ax. plugs. PK4-6 Co-ax connectors. PK5-8-5m/m formers with slugs, PK6-25-AC128 Transistors. PK7-3 BF200 (VHF) Transistors. PK8-2 BF182 (UHF) Transistors. PK9 Any 6 Transistors BC108, BC113, BC135, BC153, BC171, BC172, BF194, BF195, BF196, BF197. PK10 8-1 amp 400 volts rectifiers. PK11 4-5 pin din plugs (180°). PK12-5 PP3 Battery Connectors.

All prices include VAT. P&P 20p per order. Please send uncrossed P.O. or Cheques for returning if we are out of stock of Bargain Packs or older types of new valves.

ELECTRONIC MAILORDER LTD.

62 BRIDGE ST., RAMSBOTTOM, BURY, LANCs. TEL. RAMS. 070 682) 3036

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11 For TH stereo and standard VHF/FM radio.

B12—For the older VHF television—Please state channel numbers.

B45—For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. £3-80


Doram kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!



£5.70
+ S

Dwell Meter

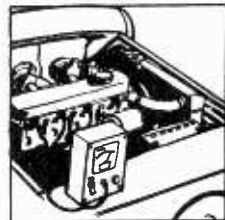

IDEAL FOR THE D-I-Y MOTORIST!


£5.70 + S VAT Subject to availability
(Order code 991-568)

The Dwell Meter permits easy adjustment of worn or pitted contact breakers, based on the electrical contact time and not on the mechanical distance between the points. The improved accuracy obtainable by using this self contained unit, ensures greater precision than may be obtained using Feeler Gauges.

O'seas orders—add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2x25p vouchers, each one usable on any order placed to the value of £5.00 or more (ex. VAT).

DORAM ELECTRONICS LTD
P.O. BOX TR8, WELLINGTON RD IND. EST., LEEDS LS12 2UF

An Electrocomponents Group Company

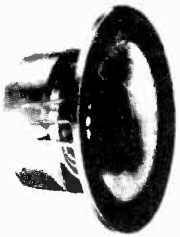

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

- Baker Group 25, 3, 8 or 15 ohms
- Baker Group 35, 3, 8 or 15 ohms
- Baker Group 50/15, 8 or 15 ohms
- Baker Group 50/15, 8 or 15 ohms
- Baker Deluxe 12" 8 or 15 ohms
- Baker Major 3, 8 or 15 ohms
- Baker Major 3, 8 or 15 ohms
- Baker Superb 8 or 15 ohms
- Baker Regent 12" 8 or 15 ohms
- Baker Auditorium 12" 8 or 15 ohms
- Baker Auditorium 15" 8 or 15 ohms
- Celestion G12M 8 or 15 ohms
- Celestion G12H 8 or 15 ohms
- Celestion G12/80 8 or 15 ohms
- Celestion G12/50TC 8 or 15 ohms
- Celestion G15C 8 or 15 ohms
- Celestion G19C 8 or 15 ohms
- Celestion HF1300 8 or 15 ohms
- Celestion HF2000 8 ohms
- Celestion MH1000 8 or 15 ohms
- Celestion CO3K
- Decca London ribbon horn
- Decca London CO/1000/8 Xover
- Decca CO ribbon horn
- Decca CO/1/8 Xover (DK30)
- EMI 14 x 9 Bass 8 ohms 14A 770
- EMI 8 x 5, 10 watt, d/cone, roll surr.
- EMI 8" d/cone, roll surr. 8 ohms
- EMI 8" roll surr. bass
- EMI 5" mid range
- Elac 59RM109 (15) 59RM114 (8)
- Elac 4" d/cone, roll surr. 8 ohms
- Elac 10" 10RM239 8 ohms
- Eagle Crossover 3000hz 3, 8 or 15 ohm
- Eagle FR4
- Eagle FR65
- Eagle FR8
- Eagle FR10
- Eagle HT15
- Eagle HT21
- Eagle MHT10
- Eagle FF28 multicell. horn
- Fane Pop 15, 8 or 16 ohm
- Fane Pop 33T, 8 or 16 ohm
- Fane Pop 50, 8 or 16 ohm
- Fane Pop 55, 8 or 16 ohm
- Fane Pop 60, 8 or 16 ohm
- Fane Pop 70, 8 or 16 ohm
- Fane Pop 100, 8 or 16 ohm
- Fane Crescendo 12A, 8 or 16 ohms
- Fane Crescendo 12BL, 8 or 16 ohms
- Fane Crescendo 15/100A, 8 or 16 ohms
- Fane Crescendo 15/125, 8 or 16 ohms
- Fane Crescendo 18, 8 or 16 ohms
- Fane 910 Mk II horn
- Fane 920 Mk II horn
- Fane HPX1 crossover 200 watt
- Fane 13 x 8, 15 watt dual cone
- Fane 801T 8" d/c, roll surr.
- Goodmans Axent 100
- Goodmans Audiom 200 8 ohm
- Goodmans Axiom 402 8 or 15 ohm
- Goodmans Twinaxiom 8, 8 or 15 ohm
- Goodmans 8P 8 or 15 ohm
- Goodmans 10P 8 or 15 ohm
- Goodmans 12P 8 or 15 ohm
- Goodmans 12PG 8 or 15 ohm
- Goodmans 12PD 8 or 15 ohm
- Goodmans 12AX 8 or 15 ohm
- Goodmans 15AX 8 or 15 ohm
- Goodmans 15P 8 or 15 ohm

SPEAKERS

- £13-00 Goodmans 18P 8 or 15 ohm
- £14-50 Goodmans Hifax 750P
- £14-00 Goodmans 5" midrange 8 ohm
- £18-62 Gauss 12"
- £17-50 Gauss 15"
- £15-00 Gauss 18"
- £22-50 Jordan Watts Module 4, 8 or 15 ohm
- £12-50 Kef T27
- £14-65 Kef T15
- £10-41 Kef B110
- £12-95 Kef B200
- £15-95 Kef B139
- £18-00 Kef DN8
- £20-00 Kef DN12
- £28-95 Kef DMI3 SP1015 or SP1017
- £39-95 Lowther PM6
- £7-50 Lowther PM6 Mk 1
- £8-55 Lowther PM7
- £13-50 Peerless KO10DT 4 or 8 ohms
- £4-46 Peerless DT10HFC 8 ohms
- £29-95 Peerless KO40MRF 8 ohms
- £8-95 Peerless MT225HFC 8 ohms
- £19-95 Richard Allan CA12 12" bass
- £4-75 Richard Allan HP8B
- £11-92 Richard Allan LP8B
- £3-75 Richard Allan DT20
- £3-93 Richard Allan CN8280
- £5-73 Richard Allan CN820
- £3-15 Richard Allan Super disc 60W 12"
- £3-38 Richard Allan CG15 15" bass
- £3-95 Richard Allan Super Disco 10" 50 watt
- £3-95 Richard Allan Super Disco 8" 50 watt
- £1-57 Radford MD9
- £5-51 Radford MD6 dome mid range
- £8-95 Radford TD 3
- £11-95 Radford Crossover network
- £14-06 BD25 Mk II
- £3-96 Soles 4001 G & K
- £4-95 Tannoy 10" HPD
- £4-00 Tannoy 12" HPD
- £5-95 Tannoy 15" HPD
- £3-50 Wharfedale Super 10 RS/DD 8 ohms
- £9-75 Castle 8 RS/DD

SPEAKER KITS

- £39-95 Fane Mode One Mk2 each £10-35
- £18-00 Wharfedale Denton 2XP Kit pair £23-25
- £4-05 Wharfedale Linton 3 x P Kit pair £34-25
- £95-00 Wharfedale Glendale 3XP kit pair £49-50

HI-FI

**ON DEMONSTRATION
in our showrooms**

Akal, Armstrong, Bowers and Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc. Ask for our Hi-Fi Discount Price List.

THIS MONTH'S SPECIALS! Carr. £2-50
 Rotel RA 412 £77-95. Rotel RX 202 Mk II £97-50. Videotone Minimax II £43-00. Videotone Saphir II £49-00. Pioneer SX 450 £116-00. Sansui SC 2000/2002 £149-70.

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners, etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter, etc.

SPEAKER KITS

- £44-95 Baker Major Module 3, 8 or 15 ohms each £13-50
- £54-95 Goodmans DIN 20 4 or 8 ohms each £15-75
- £84-95 Goodmans Mezzo Twin Kit pair £51-95
- £75-95 Helme XLK 20 pair £17-50
- £45-95 Helme XLK 30 pair £21-95
- £45-95 Helme XLK 35 pair £26-75
- £2-50 Helme XLK 40 pair £38-50
- £5-50 KEF kit I pair £53-50
- £8-96 KEF kit III pair £49-00
- £8-50 Peerless 1060 pair £54-00
- £14-95 Peerless 1070 each £46-50
- £32-00 Peerless 1120 each £54-00
- £10-60 Peerless 2050 pair £39-50
- £6-50 Peerless 2060 pair £53-00
- £8-95 Richard Allan Twin assembly each £13-95
- £16-50 Richard Allan Triple 8 each £20-75
- £17-75 Richard Allan Triple 12 each £25-95
- £18-75 Richard Allan Super Triple each £29-50
- £44-00 Richard Allan RA8 Kit pair £37-80
- £49-00 Richard Allan RA82 Kit pair £59-40
- £24-00 Richard Allan RA82L Kit pair £85-70

All Prices include VAT
(Prices correct at 31.12.78)

Send stamp for Free 38 page booklet
'Choosing a Speaker'.

All units guaranteed New and Perfect.
Carriage and Insurance:

- Speakers up to 12" 60p
- 12" £1-00
- 15" £1-75
- 18" £2-50

Kits £1-00 each (£2-00 per pair)

Tweeters & Crossovers 33p each

Complete kits in stock for Radford Studio 90, Radford Monitor 180, Radford Studio 270, Radford Studio 360, HiFi Answers Monitor (Rogers), HiFi News No Compromise (Frisby), HiFi News State of the Art, Wireless World Transmission Line (Bailey), Practical HiFi and Audio Monitor (Giles), Practical HiFi and Audio Triangle (Giles), Popular HiFi (Colloms), etc.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, Hi-Fi On dem. Answers Monitor, State of Art, Free on Request.

P.A. Amplifiers, microphones etc. by Shure, Linear, Eagle, Beyer, AKG etc.

FREE with orders over £10—"HiFi Loudspeaker Enclosures" Book

WILMSLOW AUDIO

Dept. PW

Loudspeakers, Mail Order and Export:
Swan Works, Bank Square, Wilmslow.
Hi-Fi, Radio & TV: Swift of Wilmslow
5 Swan Street, Wilmslow, Cheshire.
PA, Hi-Fi & Accessories: Wilmslow
Audio, 10 Swan Street, Wilmslow,
Cheshire.

Telephone:
Loudspeakers, Mail Order and Export
Wilmslow 29599

Hi-Fi, Radio, etc., Wilmslow 26213
(Access and Barclay Card orders
accepted by phone).

CRESCENT RADIO LTD.

164-166 HIGH ROAD, LONDON N22 6EJ
(also) 13 SOUTH MALL, EDMONTON, N.9
MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN,
LONDON N22 4SJ Phone 888 4474

ALUMINIUM BOXES +8%

Metal project boxes give your work a professional finish

L	W	H		
AB7	2½	5½	1½	54p
AB8	4	4	1½	63p
AB9	4	2½	1½	54p
AB10	4	5½	1½	63p
AB11	4	2½	2	45p
AB12	3	2	2	89p
AB13	6	4	2½	84p
AB14	7	5	2½	84p
AB15	8	6	3	£1.02
AB16	10	7	3	£1.25
AB17	10	4½	3	£1.02
AB18	12	5	3	£1.20
AB19	12	8	3	£1.60

"C100" 100 WATT AMPLIFIER

All built and tested, mounted on a plain aluminium chassis which measures 18" x 9½" x 4" and which you can mount into a cabinet of your choice. Four controlled inputs, master volume, treble, middle and bass controls. S/c protected output. 100 watts clean into 8ohm L/S. Ideal for disco, music groups, P.A. and clubs. A bargain at £42 + £1 carr. + 8% VAT.

P.C. ETCHING KIT

This kit contains all that the constructor will need to etch the circuits of his own design.
Contents—Plastic etching dish. Sample copper clad board. Laminated Cutter. 1 lb Ferric Chloride. Large Plastic Spoon. Etch Resist Pen. Full Etching Instructions.

Complete and Big Kit Value at £4.25 + 8% VAT.

POWER SUPPLY UNITS +8%



PPI switched 3, 4½, 6, 7½, 9 and 12 volts at 500 mA, with on/off switch and pilot light. Size: 130mm x 55mm x 75mm.
Only £25.50



M3 CONDENSER MICROPHONE
Cardioid and omni-directional 600 ohm and 50K ohm impedance. 20-18,000 Hz. On/off switch and wind shield. Complete with stand adaptor. Packed in presentation box.
Price £12.50 + 12½% VAT.



3 WAY MULTIPLE AC ADAPTOR
This compact adaptor enables a large range of battery powered radios, and calculators to be more economically operated off the mains (220-240V A.C.) Instantly switchable for 6, 7.5 or 9 Volts, current rating is 250mA. A polarity reversing coupler is incorporated into the 2 metre lead which is terminated by a unique 4 way plug offering connections by 2.1 and 2.5mm sockets, 2.5 and 3.0mm plug. The sealed moulded unit is fitted with a 2 pin 5 amp mains plug and measures 47 x 25 x 63mm. Nominal weight: 0.22 kg.
Only £2.50 + 8%.


TI-CMIP CONDENSER MICROPHONE
Omni-Directional 600 ohm 40-15,000Hz. Extra long lead. Ideal for stage work, conferences, etc. Price £9.50 + 12½% VAT.

LOW NOISE LOW PRICE CASSETTES +8%
Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C60 = 83p C90 = 48p C120 = 60p
10% Discount on ten or more cassettes of one type

LOUDSPEAKERS +12½%

2½" 8 ohm	90p
2½" 40 ohm	90p
2½" 80 ohm	90p
5" 8 ohm ceramic	£1.25

MULTI-METER MM12 50,000 o.p.v.

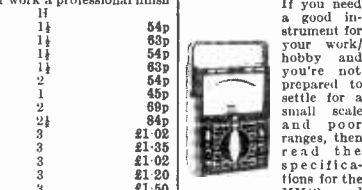

If you need a good instrument for your work/hobby and you're not prepared to settle for a small scale and poor ranges, then read the specifications for the MM12, and send for one!

AC volts: 0 to 1.5, to 0/500 in 10 ranges. DC volts: 0 to 0.5, to 0/500 in 12 ranges. DC current: 0 to 25 µA, to 0/10 amps 10 ranges. Resistance: 0 to 100 ohms, to 0/10 meg ohms in 4 ranges. Decibels: -20 to +62 db in 10 ranges. Size: 6½ x 4½ x 2½ inch.
Price £19.50 + 8% VAT.

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).
OUR PRICE 50p. + 8%

TI MULTI-METER

Ideal tester for everybody interested in electronics. Weighing less than 100 grammes and only 60 x 24 x 90 mm. Ranges: A.c. volts: 0-10V, 50V, 250V, 1,000V. D.c. volts: 0-10V, 50V, 250V, 1,000V. D.c. current: 0-1mA, 0-100mA. Resistance: 0-150 kohm.
Price £5.50 + 8% VAT.

FERRIC CHLORIDE

Anhydrous ferric chloride in double sealed one pound poly packs. Our Price 65p + P/P + VAT @ 8% per lb.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18.50 plus 75p P. & P. + 8%

BARGAIN TRANSFORMERS 12-0-12 volt 500mA

240 volt primary transformer bargain. approx size 60mm x 40mm x 50mm fixing centres 75mm
Our Price £1.20 + 8%

EFFECTS PROJECTOR "150"

No Disco should be without our new effects projector, we believe that this is the most versatile machine for projecting coloured images to supplement your music. Spec:—Volts = 220/240 AC 50Hz. Lamp = A1167 150 watts. Standard Lens = 60 mm.
A sturdy metal construction and takes a range of lenses and accessories. Comes complete with 6" liquid wheel and ready to use. A bargain at £27 + VAT 8%.

A19 STEREO PRE-AMPLIFIER

Using standard phone plug connections. Input impedance: 50,000 ohms. Maximum input: 30 mV. Maximum output: 1.8v (at 1% distortion). Gain: 10mv input, 0.5v output. Frequency response: 30-20,000 Hz. S/N ratio: over 60 db. Power supply: 240V A.C. Dimensions: 101 x 63 x 40mm.
Our Price £5.50 + 12½% VAT.

U.K. CARRIAGE 60p UNLESS OTHERWISE STATED
VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

LOW, LOW PRICES ON BRANDED COMPONENTS.

These are the same components we supply in millions to industrial users. That's your guarantee of quality and service. It's also how we can maintain these sensationally low prices.

- All 'big name' manufacturers
- Same day service
- Money back guarantee

COS/MOS	CD 4063BE	CA 3015	1.35	6.5 1411	3.62	20 3483	0.57
4000AE	0.19	CD 4094BE	1.07	CA 3080	1.54	20 3484	1.54
4001AE	0.19	CD 4095BE	1.21	CD 3081	1.82	20 3485	1.11
4002AE	0.19	CD 4096BE	1.21	CD 3082	1.84	20 3486	1.11
4003AE	1.08	CD 4097BE	1.07	CA 3083E	0.1	20 3487	1.11
4004AE	0.19	CD 4098BE	1.00	CA 3090E	0.92	20 3488	0.30
4005AE	0.88	CD 4099AE	1.57	CD 3091E	0.92	20 3489	0.35
4006AE	0.52	CD 4100BE	1.42	CD 3092E	1.31	20 3490	0.35
4007AE	0.52	CD 4101BE	1.72	CD 3093E	0.91	20 3491	0.35
4008AE	1.19	CD 4102BE	0.75	CD 3094E	0.75	20 3492	0.35
4009AE	1.19	CD 4103BE	0.75	CD 3095E	0.75	20 3493	0.35
4010AE	1.52	CD 4104BE	0.75	CD 3096E	0.75	20 3494	0.35
4011AE	0.92	CD 4105BE	0.75	CD 3097E	0.75	20 3495	0.35
4012AE	0.92	CD 4106BE	0.75	CD 3098E	0.75	20 3496	0.35
4013AE	0.92	CD 4107BE	0.75	CD 3099E	0.75	20 3497	0.35
4014AE	0.92	CD 4108BE	0.75	CD 3100E	0.75	20 3498	0.35
4015AE	0.92	CD 4109BE	0.75	CD 3101E	0.75	20 3499	0.35
4016AE	0.92	CD 4110BE	0.75	CD 3102E	0.75	20 3500	0.35
4017AE	0.92	CD 4111BE	0.75	CD 3103E	0.75	20 3501	0.35
4018AE	0.92	CD 4112BE	0.75	CD 3104E	0.75	20 3502	0.35
4019AE	0.92	CD 4113BE	0.75	CD 3105E	0.75	20 3503	0.35
4020AE	0.92	CD 4114BE	0.75	CD 3106E	0.75	20 3504	0.35
4021AE	0.92	CD 4115BE	0.75	CD 3107E	0.75	20 3505	0.35
4022AE	0.92	CD 4116BE	0.75	CD 3108E	0.75	20 3506	0.35
4023AE	0.92	CD 4117BE	0.75	CD 3109E	0.75	20 3507	0.35
4024AE	0.92	CD 4118BE	0.75	CD 3110E	0.75	20 3508	0.35
4025AE	0.92	CD 4119BE	0.75	CD 3111E	0.75	20 3509	0.35
4026AE	0.92	CD 4120BE	0.75	CD 3112E	0.75	20 3510	0.35
4027AE	0.92	CD 4121BE	0.75	CD 3113E	0.75	20 3511	0.35
4028AE	0.92	CD 4122BE	0.75	CD 3114E	0.75	20 3512	0.35
4029AE	0.92	CD 4123BE	0.75	CD 3115E	0.75	20 3513	0.35
4030AE	0.92	CD 4124BE	0.75	CD 3116E	0.75	20 3514	0.35
4031AE	0.92	CD 4125BE	0.75	CD 3117E	0.75	20 3515	0.35
4032AE	0.92	CD 4126BE	0.75	CD 3118E	0.75	20 3516	0.35
4033AE	0.92	CD 4127BE	0.75	CD 3119E	0.75	20 3517	0.35
4034AE	0.92	CD 4128BE	0.75	CD 3120E	0.75	20 3518	0.35
4035AE	0.92	CD 4129BE	0.75	CD 3121E	0.75	20 3519	0.35
4036AE	0.92	CD 4130BE	0.75	CD 3122E	0.75	20 3520	0.35
4037AE	0.92	CD 4131BE	0.75	CD 3123E	0.75	20 3521	0.35
4038AE	0.92	CD 4132BE	0.75	CD 3124E	0.75	20 3522	0.35
4039AE	0.92	CD 4133BE	0.75	CD 3125E	0.75	20 3523	0.35
4040AE	0.92	CD 4134BE	0.75	CD 3126E	0.75	20 3524	0.35
4041AE	0.92	CD 4135BE	0.75	CD 3127E	0.75	20 3525	0.35
4042AE	0.92	CD 4136BE	0.75	CD 3128E	0.75	20 3526	0.35
4043AE	0.92	CD 4137BE	0.75	CD 3129E	0.75	20 3527	0.35
4044AE	0.92	CD 4138BE	0.75	CD 3130E	0.75	20 3528	0.35
4045AE	0.92	CD 4139BE	0.75	CD 3131E	0.75	20 3529	0.35
4046AE	0.92	CD 4140BE	0.75	CD 3132E	0.75	20 3530	0.35
4047AE	0.92	CD 4141BE	0.75	CD 3133E	0.75	20 3531	0.35
4048AE	0.92	CD 4142BE	0.75	CD 3134E	0.75	20 3532	0.35
4049AE	0.92	CD 4143BE	0.75	CD 3135E	0.75	20 3533	0.35
4050AE	0.92	CD 4144BE	0.75	CD 3136E	0.75	20 3534	0.35
4051AE	0.92	CD 4145BE	0.75	CD 3137E	0.75	20 3535	0.35
4052AE	0.92	CD 4146BE	0.75	CD 3138E	0.75	20 3536	0.35

Terms - c/wo, add 8% VAT on Cos/Mos and 12½% VAT on Transistors, Diodes etc. plus 15p postage and packing.
Rosebank Parade, Plough Road, Yateley, Camberley, Surrey. Tel: 0252 871388.


ROWNSGEM LTD.

Doram kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

POWER SUPPLY

£19.95 + S

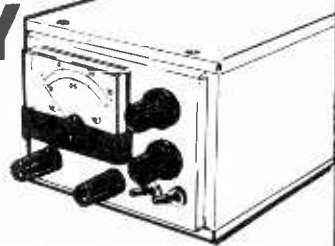

An invaluable piece of equipment for the enthusiasts workshop. This 3-30V d.c. power supply fulfills virtually all experimentation requirements. Avoid frustration and circuit damage with the variable current limit (0-1A max). Regulation typically better than 0.5% (max 3%). Ripple voltage typically better than 20mV (max 120mV).

£19.95 + S VAT (Order code 997-027) Subject to availability

O'seas orders—add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2x25p vouchers, each one usable on any order below the value of £5.00 or more (ex. VAT)
DORAM ELECTRONICS LTD.
P.O. BOX TR8, WELLINGTON RD. IND. EST., LEEDS LS12 2UF


An Electrocomponents Group Company

Stirling Sound

Q.V. MODULES FOR COST CONSCIOUS CONSTRUCTORS

SS.1100

Power and quality cost less!
Special introductory offer
to save you **£1.95**

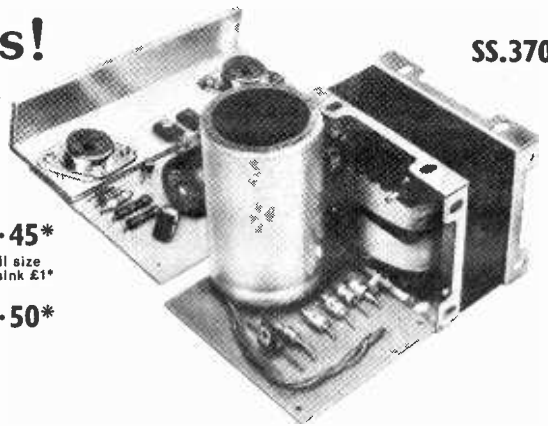

SS.370

POWER AMP.

SS.1100

Delivers 100 watts R.M.S. into 4 ohms using a 70 volt/2A supply. Input sensitivity 500mV for full output. Response—10Hz to 50KHz ± 1 dB. S/N ratio better than 75dB. Distortion at half power typically 0.1%. With heat sink mounting bracket. 5" x 3 1/2" x 1 1/2" (SS.1100H with full size heatsink).

£9.45*

Full size heatsink £1*

SS.370


A new heavy duty power supply unit to deliver 70 volts/2 amps. Complete with mains transformer and low-volt outlet P/p—£1.00

£12.50*

YOU PAY ONLY £21.00* FOR THE TWO TOGETHER

There is real power and reliability in this assembly. By buying them together you save nearly £2.00 on these already competitively priced units. IDEAL FOR DISCO, P.A. and such like applications. Send only £21.00* (+ £1.00 p/p) for SS.1100H with full size heatsink and Power Unit SS.370.

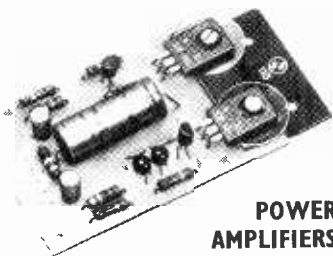MORE STIRLING SOUND Q.V. MODULES TO SAVE YOU MONEY



POWER AMPLIFIERS

3 TO 40 WATTS R.M.S.

SS.103 5 watt r.m.s. mono. I.C. short £1.75
SS.103-3 Stereo version of above using two I.C.s £3.25

SS.105 5 watts r.m.s. into 4 ohms, using 12V £2.25

SS.110 10 watts r.m.s. using 24V and 4 ohm load £2.75

SS.120 20 watts r.m.s. into 4 ohms, using 34V £3.25

SS.104 Delivers 40 watts R.M.S. into 4 ohms using 45 volts supply unit such as SS.345. Ideal for small disco, P.A. etc. £3.95*


If ordering Stirling Sound power supply units with Modules SS.103 to SS.120, V.A.T. becomes 12 1/2%.

TONE CONTROLS/PRE-AMPS

SS.100 Active tone control, stereo. ± 15 dB on bass and on treble £1.60

SS.101 Pre-amp for ceramic cartridges, etc. Stereo. Passive tone control details supplied. £1.60

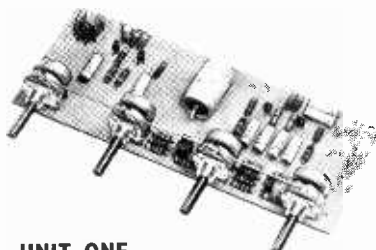SS.102 Stereo pre-amp for low output magnetic P.U.s. R.I.A.A. corrected. £2.65



UNIT ONE

A real money saver this. Compatible with all relevant Stirling Sound modules as well as other makes.

Combined pre-amp with active tone-control circuits. ± 15 dB at 10KHz treble and 30Hz bass. Stereo. Vol./balance/treble/bass. 200mV out for 50mV in. Operates from 10 to 16V supply. £7.80

F.M. TUNING MODULES

SS.201 Front end tuner, slow geared drive, two gang. A.F.C. facility. Tunes 88-108 MHz. £5.00

SS.202 I.F. amplifier. Metering and A.F.C. facilities. £2.65

SS.203 Stereo Decoder for use with the above or other FM mono tuners. A LED may be fitted. £3.85


WHAT Q.V. MEANS TO YOU

It means Stirling Sound QUALITY and VALUE from modules made in our own Essex factory. They are all tested and guaranteed and offer unbeatable value. Designed by highly specialist electronic engineers with wide experience of constructors' and experimenters' needs. WATCH HOW THE STIRLING SOUND RANGE GROWS!

POWER SUPPLY UNITS

WITH 13-15V TAKE-OFF POINTS

Except SS.312

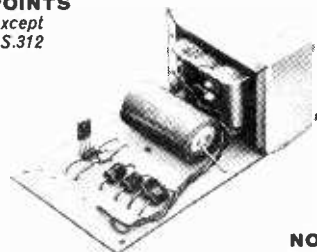

NOW 8 MODELS TO CHOOSE FROM

Complete with mains transformers and low volt take-off points (not SS.300). All at 8% V.A.T. rate. Add 50p for p/p any model with transformer included.

SS.312 12V/1A £3.75*

SS.318 18V/1A £4.15*

SS.324 24V/1A £4.60*


SS.334 34V/2A £5.20*

SS.345 45V/2A £6.25*

SS.350 50V/2A £6.75*

SS.300 Power stabilising unit 10-50V adjustable for adding to unstabilised supplies. Built in protection against shorting (p/p 35p) £3.26*

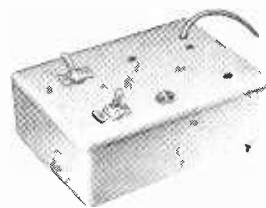SS.310/50 Stabilised power supply with variable output from 10V to 50V/2A. Built-in protection against shorting £11.95*



A GOOD START FOR MOTORISTS

with a STIRLING SOUND "SUPER SPARK" Mk.5 Electronic Ignition Unit. Over 10,000 Super Spark Units have been sold by us. Adjustable for + or - earth; simple rev. limiting control; on-off immobilising switch; switch for instant revert to car's own ignition; neon, indicator; in strong enclosed metal box 6 1/2 x 4 1/2 x 4 1/2 ins. Inc. transformr. (P/P + 50p either model + 8% V.A.T.).

KIT £8.95* READY BUILT £10.95*

WHEN ORDERING add 35p for p/p unless stated otherwise V.A.T. add 12 1/2% to total value of order unless price is shown* when the rate is 8%. Make cheques, etc. payable to Bi-Pre-Pak Ltd. Every effort is made to ensure correctness of information at time of going to press. Prices subject to alteration without notice.

Stirling Sound

A member of the Bi-Pre-Pak group (Southend on Sea)

Dept. PE/3, 220-224 West Road, Westcliffe-on-Sea, Essex SS0 9DF
Tel: Southend (0702) 46344. Personal callers welcome.



TRAMPUS ELECTRONICS LTD

58-60 GROVE RD.
WINDSOR, BERKS.
SL4 1HS.
TEL. 54525

ADD 8% VAT TO PRICES MARKED *
ADD 12% TO ALL OTHER PRICES.
OR AS CURRENT VAT LEGISLATION
SEND C.W.O. (EXCEPT GOV'T DEPT)
POST & PACKING 20P FOR THE U.K.
BARCLAYCARD & ACCESS BY POST
OR 15 MIN ON TELEPHONE ORDERS.
NEW CATALOGUE LIST FREE S.A.S.
MONEY BACK IF NOT SATISFIED.

FAST SERVICE

ON EX STOCK ITEMS
NORMALLY 24 HOURS



SEVEN SEGMENT LED DISPLAYS
BRIGHT DL707 COM ANODE &
DL704 COM CATH. 0.3" 1"
DL747 0.6" JUMBO CA £1.25*

RED LEDS 10P.

RED LEDS 209 STYLE 0.125"
OR 0.2" DIA. NO CLIP 10p*

TIL209 RED LED & CLIP 12p*
BIG 0.2" RED LED & CLIP 14p*
GREEN OR ORANGE LEDS 29p*
ORP12 54p* 2N5777/0CP71 34p*

TRAMPUS
THE GREAT
BRITISH
DISTRIBUTOR



INDUSTRIAL, EDUCATIONAL, TRADE
& EXPORT SUPPLIED. SEND FOR
OUR FREE CATALOGUE LIST SAE
MANUFACTURERS EXCESS STOCKS
PURCHASED. DISCOUNTS 10% OFF
100 up. 15% OFF 1000 up....

TOP DISCOUNTS.

INTEGRATED CIRCUITS

555 TIMER 34p*	LM380(60745) £1
556 2 x 555 90p*	LM381 Preamp £2
703 RF/IF AMP 29p	LM3900 4xOPA 53p*
709 TO99 or DIL28p*	MC1303 2xPre £2
710 DIL14 35p*	MC1310 stereo£2
723 Regulator 44p*	MC1312P SQ £1.70
741 DIL 8pin 21p*	MC1330 IFT 75p
741 DIL 14pin 31p*	MC1333 Preamp£2
741 TO99 33p*	MFC4000 1W 72p
747 DUAL 741 89p*	MFC6030 £1
748 DIL 8 pin 32p*	NE536 FETOPA £2*
7805 5V1A+reg£1.35*	NE540 or 550 £2*
7812 & 7815ea£1.40*	NE555 TIMER 34p*
78013 8W AF £1.50	NE556 2x555 90p*
AY5124 CLOCK £4*	NE560/1/2/5/6/7/3
CA304A 54p*	SN72741 as 741
ICL8038 Sigen £4*	SN76660 IF 74p
LM300H £1*	SN76611 IF £1
LM301A D11 8 33p*	TBA800 5W AF 84p
LM309K 5V reg £2*	TBA810 7W AF 94p
LM309H TOS can £1.4*	ZM414 Radio £1.19
LM318 70uVsOPA £3*	NEW 1468/89 £4

CMOS TTL

4000 14p*	7400 12p*	7490 39p*
4001 15p*	7401 13p*	7491 75p*
4002 16p*	7402 15p*	7492/93 45p*
4007 16p*	7404 19p*	7495/96 72p*
4009 50p*	7408/10 18p*	74100 11.25p*
4011 16p*	7413 29p*	74107 32p*
4012 17p*	7440 16p*	74121 29p*
4049 50p*	7441 71p*	74123 69p*
4069 20p*	7442 72p*	74141 74p*
4501 26p*	7447 79p*	74145 85p*
4511 1.65*	7470/72 27p*	74147 £2.50*
4528 £1*	7473/74 31p*	74151 75p*
4543 £2*	7475/36 35p*	74154 £1.40*
4553 £5*	7486 35p*	74196 £1.50*

DIL SOCKETS PROFESSIONAL QUALITY
8pin, 14pin & 16pin ALL 12p ea*
SOLDERCONS 100 49p* 1000 £3.95*

NEW LOW PRICES.

TRANSISTORS AND DIODES

IBS BUSH SET 5p ea*	TIP31/32 50p*
MATCHING 20p Pr*	TIP31c32c68p*
AC127/8 176 15p*	TIP41/42ea 66p*
AD161/162 ea36p*	TIP41c42c"1.50*
BC107 8p*	TIP2955 68p*
BC107B 13p*	TIP3055 68p*
BC108 5p*	TIS43 UJT 26p
BC108B or C 13p*	1N911/414R 4p
BC109 9p*	1N911/12 4p*
BC109B or C 12p*	1N1004 5p*
BC147/8/9 8p	1N1007 7p*
BC157/8/9 11p	2N706/8 14p*
BC167/8/9 12p	2N2846 UJT 40p*
BC177/8/9 16p	2N2904/5/6/7 9p*
BC182/3/4a/110p	2N2926 ory 7p
BC212/3/4a/112p	2N3053 17p*
BCY70/1/2 15p*	2N3055 90W 33p*
BD131/132ea 16p*	2N3055 115W45p*
BFY50/51 16p*	2N3614 703 £1*
BFY52/53 16p*	2N3702/3 41p*
BSX 18/20/21/10p*	2N3705/6/7 9p*
BZ88 ZENER 10p	2N3708/9 9p
CI08D SCR 54p*	2N3710/11 15p
MJ2855 T03 99p*	2N3819 & 23e17p
MJ2955 99p*	2N3820 PPT40P
MJE3055 65p*	2N3904/5/6 15p
OA81/92 31p*	2N5457 FET 32p
TIP29 & 30 40p*	BRIDGE1A50 20p*

BARGAIN PAKS FULL SPEC FIELA,
PAK A: 11 RED LEDS full spec 11a*
PAK B: 5 741C 8 PIN OP AMP £1*
PAK C: 4 2N3055 £1* D 12 BC109 £1*
PAK E: 11 BC182 £1 F 11 2N3704 £1*
PAK G: 7 BZY51 £1* H 8 2N3819 £1*
PAK J: 6 2N3053 £1* K 40x1N914 £1*
PAK M: 3 TO99 3055 £1N 25 OA911 £1*
PAK P: 20 PLASTIC C109 TYPENP11

10-365PF TUNER SINGLE GANG FOR
MED/SHORT WAVE, XTAL SET etc £1*
SET3/1F CANS 455/470KHZ TOKO £1*

Full spec devices

DALO pen 75p

PCB ETCH KIT 3 ITEMS £2*
ETCH RESIST PEN 2TIPS 75p*
ETCH ETCH PAX TR 600mm £1*
64" SMD 45" NYLON F/60"

SCR AND TRIACS BR100 25p*
TAG 14A00V 50p* 1A600V 69p*
1A50V 37p, C108D 4A400 60p*
TRIACS: SC146D 10A400V £1*
DISCO TRIAC 15A400V £2*

AUDIBLE METERING AB etc 20p
PRESETS 6p PRESTORIS 2p
HEATSINKS T05 or 18 7p
T03 16p T03 4" FINNED 50p

DIN-PLUGS all 15p. Sock 10p
SWITCHES SPST 20p DPST 29p
GAS DETECTOR TGS 308etc£4*

vero

VERO 0.1" PITCH COPPERCLAD
24"x5" 40p* 31"x5" 45p*
31"x3" 36p* 31"x3" 40p*
31"x17" £2 FACE CUTTER 65p*
DIL BREADBOARD 2"x4" £1 or
6"x4" £2. VERO PINS 36 30p*

BLACK PLASTIC CASES 42mmx.
80x60 50p* 100x75 60p* 99x
120 70p, DESOLDER BRAID 50p

NEWMART ELECTRONICS for all your hi-fi needs.

Stockists of: Amstrad · Teleton · Akai · Sansui · Wharfedale · Pioneer · Rotel · Garrard · Connoisseur

BATTERY ELIMINATORS P&P 25p
240v Input 6, 7.5 or 9v
output at 300mA ... £3-25
12v d.c. input (specify output 6, 7.5
or 9 d.c.) at 300mA ... £5-20

CARTRIDGES & STYLII D-D & RPL
P&P 25p Cart. Styli

Acos GP91/25C or 3CS (ster. comb)	£1-60	£1-20
GP93/1 or 95/1 ster. cryst	£2-00	£1-20
GP94/1 or 96/1 ster. ceram.	£2-00	£1-20
GP101 cryst. comp.	£1-00	—
GP104 ster. ceram	£2-15	£1-20
BSR X5M or X5H cryst. comp.	£1-65	£1-20
SX6M or SX6H cryst. ster.	£2-25	£1-20
SC6M ster. ceram.	£2-75	£1-20
Sonotone 9TAHC or 9TAHC/G (Diam.) 3509	£2-60	£1-20
Audio Technica AT55	£2-25	—
Goldring G850	£3-50	£1-75
G800	£5-25	£1-75
G800H	£5-25	£1-75
G800E	£9-96	£3-50
Shure Cartridges & Styli		
M44G/M44C	£7-70	£6-20
M55E	£9-20	£7-15
M75E Type 2	£17-15	£12-65
M75E Type 2	£14-30	£8-78

SPEAKERS P&P 70p

EMI 13" x 8", 3, 8 ohm Plain	£3-40
8" x 5" C.Mag. 5 watt, 3, 8 or 15 ohm.	£2-35
8" x 5" Dualcone	£3-70
8 ohm, 10 watt	£3-70
ELAC C 8 ohm Dualcone	£3-45
8" 8 ohm Dualcone	£3-45
10" Dualcone	£4-10

MICROPHONES P&P 45p

UD 130 50K/600 ohm uni-dir. ball metal	£7-45
Condenser Mic. 600 ohm ECM77 omni-dir	£8-90
Cassette Stick Mic. with R/Control	£1-56
Cass. Stick Mic. with R. Control (Phillips type)	£1-93

CASSETTES P&P 25p

	C60	C90	C120
Low Noise	£0-37	£0-48	£0-59
Phillips	£0-66	£0-90	£1-27
Memorex	£0-81	£1-18	£1-67
Cassette Head Cleaner			£0-48
Bib Head Cleaner			£1-99
magnetiser			£1-99

RECORD DECKS P&P £1-35

GARRARD SP25 Mk IV	£20-70
GARRARD SP25 Mk IV/G800 with Plinth & Cover	£33-20
BSR MP60 (P128R)	£17-35
Plinth & Cover for Garrard, BSR	£4-77

These Prices Apply to Mail Order Only. V.A.T. INCLUSIVE. All items subject to availability & manufacturers increase
Barclay Card and Access welcome
Callers Welcome at Manchester 30-32 Shudehill Tel. 061-832 7710. Leeds 4 New Market St. Tel. 0532 42708. Liverpool 15 Whitechapel. Tel. 051-236 0738

NEWMART ELECTRONICS

Mail Order Dept PW/3
Belmont St, Monton,
Eccles, Manchester.
Tel 061-789 5268

DORAM kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

FM TUNER £64.95 + H VAT
(Order code 991-940)

Modern styling, ease of construction and modular assembly go to make this kit extremely good value for money. Features push-button varicap station selector with manual tuning over-ride, stereo decoder, with mono over-ride + 'mix' facility for reduced separation on weak stations.

Sensitivity: 1.2µV for 26dB quieting
Signal to noise ratio: 67dB typ. (400µV input)
Frequency range: 87.5 - 104MHz
Stereo separation: 40dB at 1KHz
Distortion: 0.5% Subject to availability

O'ceas orders—add 15% for P+P All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2x25p vouchers, each one usable on any order placed to the value of £5.00 or more (ex. VAT).
DORAM ELECTRONICS LTD.
P.O. BOX TR8, WELLINGTON RD. IND. EST., LEEDS LS1 2UF.
An Electrocomponents Group Company

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

THE GREENWELD DRAGON—GUARDIAN OF GOOD VALUE



TAPE DECKS

Real to real chassis, take 7" spools. Single motor operation. Made by Telefunken. No heads or electronics, mechanics only. Diecast alloy frame 13 1/2 x 9 1/2 x 6 1/2" overall depth. Free head (no data) supplied with every order. Only £25.95.

CALCULATORS -£2.75 !!!

There has to be a catch—these Rapidman 1208 machines are a mains powered desk top calculator with 0-9 and dec point, and 7 function keys inc % but the liquid crystal display is missing. However, apart from this they are complete with PSU, 3 IC's + discrete components. Overall size 11 1/2 x 7 x 3". Only £2.75. Free complete working and boxed, as new £18.

KEYBOARDS

Front half of calculator, really. Case 130 x 75mm, has display window, 2 slide switches, and 25 keys. Only £1.

DISPLAYS

Brand new 7-segment LED's, 9 MAN3M on PCB with multiplexed output. £1.35.

1 WATT AMPLIFIER

PCB 100 x 80mm with LM380 and associated components to make 1W amp operating from 9V. (Can be increased to 3W output by raising supply voltage and fitting heat sink). Complete with volume control. Connexion sheet included. Also on the board is a speed control circuit comprising 10 transistors, 2 presets, 4 pole 3 way switch, etc., but no data on this. Only £1.

POT PACKS

An overwhelming abundance of pots of all shapes and sizes, including duals, switched, sliders, etc., prompts us to make this offer: 20 assd for £2.29, 100 for £8.59.

PO 4 DIGIT METERS

Ex-equip, 500R coil, operates on 18V only 49p, 10 for £3, 100 for £29.

RELAY UNITS

Units vary slightly, but a guaranteed minimum 20 relays, PO 3000 type, various coil resistances and contact arrangements. May be a few bent contacts, but excellent value at only £4.99.

BUMPER BARGAIN PARCEL

25 kilos—yes, jcwct. Clearing several stores to make room for more goodies, mountains of miscellaneous items too time consuming to list, so we're disposing of it in this manner. You'll get a great variety of components and made-up units, contents too varied to describe, but excellent value at only £8.99.

SWITCHES

Water switches, 6p3w 30p. Water switch mechanism, 12 way. Room for 2 waters. 15p. Waters to fit, 7p2w 29p, 1p 12w 40p. Bank of 5 push button switches, 4 are 6 pole c/o. Interlocking, 5th is independent dpco. No knobs 70p. Sub-min dpco slide 15p; push to make 15p; push to break 29p. 10A 250V rocker 18p; DPCCO rocker 40p. Sub-min toggles spco 62p; dpco 74p; dpco centre off 86p.

TRIMMERS

2-7pf, 4-15pf, 6-25pf, 8-30pf ceramic. All 15p each. Compression types, 3-40pf 18p; 100-500pf 34p; 500-1250pf 46p.

NEON BANKS

Bank of 40 sub-min neons £1.80p
Bank of 20 std neons £1.80p
Recording heads, 1 1/2" track, type X/RPS/18 £1.90p

HIGH POWER POTS

Berco preset rheostat, type SEF 29.5 ohms 3.3A, with metal cover £2.39, 11 ohm 3.4A without cover £1.59. Rotary types: 25W, 6R, 25R, 114R £1.17 each; 50W, 50R, 100R 1k5 £1.44 each; 100W, 70R £1.88. Mounted Carbon High Voltage Pots, ideal for scope built for audio control, etc. Rated 3W, 2k5, 3k, 5k, 10k, 50k, 100k, 250k, 500, 1M, 2M5, all p82 each.

71b BARGAIN PARCEL

Hundreds of new components—pots, switches, resistors, capacitors, PC Boards with semiconductors, loads of odds and ends. Amazing value at only £2.99.

COMPUTER PANELS

Large quantity always available: 31b asstd. £1.75; 71bs £3.65; 581b £16. Pack with about 500 components inc. at least 50 transistors £1.99. Pack with 12 1/2" quality panels, incl. IC's, power transistors, multitrans trim pots, hundreds of small signal transistors, resistors, zeners, capacitors, etc. Only £2.75. 7400 IC pack—20 74 series IC's on panels £1.20.

PC ETCHING KIT

Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO Quick Dri Etch resist pen, abrasive cleaner, 2 miniature drill bits, etching dish and instructions. £3.65.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb £1.99; 3lbs £2.18; 10lbs £5.99; 100lbs £39.99.

FIBREGLASS PCB

Large quantity of offcuts, all usable pieces. 200 sq ins, single sided, double sided or mixed £1.49.

DEVELOPMENT PACKS

50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF, total 210 caps. £2.79.

CR25 carbon film 1/3rd watt resistors, 5%, 10 of each value 10 ohms to 1M. Total 610 resistors £5.99. Electrolytics, wire ended 25V working 10 each of: 1, 2, 2, 4, 7, 10, 22, 47 and 100mfd. 70 capacitors for £3.29. 400mW zeners 5% 10 each 3V to 30V, 200 in all. Only £14.99.

COMPONENT PACKS

400 assd. carbon resistors £1.35
100 Wirewounds 2-15W £1.99
200 Miniature resistors, 1/2, 1 and 1 1/2W, mostly carbon film £1.29
200 poly, mica, ceramic caps £1.19
100 Polyester, .01-2.2uF £1.99
200 miniature electrolytics, but many unmarked so only £1.99

RELAYS

Miniature Plug-in types: 1250 ohm 4c/o 46p; 700 ohm 4c/o 50p. PO 3000 type 650 ohm with 6 heavy duty c/o contacts (Ex-equip) 75p; 10 for £4.99. 6 1/2" easily removable reeds in 3550 ohm coil 50p. Plug in relay, BTG Base 17mm dia x 42mm long 10k coil 1 c/o contact 46p. Omron MK3P plug in relay. 230V AC coil, 3 sets 10A/c/o contacts. £1.29. Bases 39p. Ex-equip on PCB board, min sealed type, 22 x 20 x 10mm 200R coil (ops on 6-12V) 2 c/o contacts 46p. Ex equip 34 x 30 x 15mm, 250R coil, ops on 6-12V 4 c/o contacts, 60p. Delay relay, 115V 20 sec coil, mains contact 60p; 230V coil 30 sec delay £1.

CRYSTAL FILTER UNIT

Chassis 210 x 115 x 80mm containing 24 way switch, 24 HC6U stal holders, 24 beehive trimmers, + board with 4 BF115, R's C's, etc. £3.59.

5MHz FREQUENCY SOURCE

High stability, better than 1 x 10⁻³ short term, better than 1 x 10 per month. 12.6V drive voltage, output 5MHz into 50R £12. 4-438619MHz colour sub-carrier crystals 69p.

BOOKS

All by R. M. Marston, these titles use readily available components.
20 Solid State Projects for the Home £2.20
Solid State Projects for the Car & Garage £2.10
Semiconductor Projects for the Home Constructor £2.76
110 Thyristor Projects for the Home Constructor £2.70
110 Integrated Circuit Projects for the Home Constructor £2.70
110 Op Amp Projects for the Home Constructor (uses 741) £2.70
110 CosMos Digital IC Projects for the Home Constructor £2.85
110 Electronic Alarm Projects for the Home Constructor £3.15.

VERO BOXES, CASES & BOARD

VEROBOARD

Size	0-1"	0-15"	0-1"	plain
3 1/2 x 3 1/2"	44p	48p	N/A	
5 x 3 1/2"	58p	55p	46p	
17 x 3 1/2"	£1.99	£1.60	£1.39	

Full or half pins, 0-1 or 0-15 35p 100. Spot face cutter for 0-1 or 0-15" 75p.

DIP BREADBOARD

Accommodates 20 x 14 way or 16 x 18 way IC's £2.99.

OFFCUTS

Pack A, All 0-1"
Pack B, All 0-15"
Pack C, Mixed
Pack D, All 0-1" plain

Each pack contains 7 or 8 pieces with a total area of 100 sq ins. Each pack is £1.39. Also available by weight, 1lb £3.45, 10lbs £29.

We are also VERO wholesalers—Trade price list on request from Bone Fide Companies.



VEROCASES


Plastic top and bottom, ally panels front and back.

Type 1410	205 x 140 x 40mm	£3.39
1411	205 x 140 x 75mm	£3.79
1412	205 x 140 x 110mm	£4.69
1237	154 x 85 x 40mm	£2.39
1238	154 x 85 x 50mm	£2.89
1239	154 x 85 x 80mm	£3.69

PLASTIC BOXES

Professional quality, two tone grey polystyrene with threaded inserts for mounting PC Boards.

Type 2518	120 x 65 x 40mm	£2.25
2520	150 x 80 x 50mm	£2.69
2522	188 x 110 x 60mm	£3.59

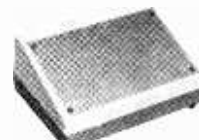

Sloping front version, Type 2523 220 x 174 x 100/52mm £4.00
Type 1798 171 x 121 x 75/37 5mm £4.59
Gen Purpose plastic potting box 71 x 49 x 24. In black or white 49p
Hand Controller box, shaped for ease of use in the hand, 94 x 61 x 23mm 62p

S-DECS & T-DECS

S-DEC Breadboard £2.10
T-DEC Breadboard £3.75

SOLDERING IRONS

Antex 15W Model C £2.79
Antex 15W Model CCN £2.99
DeeGee 25W Model 3612 £2.99
Litesold 10W £2.49
EK400 40W £2.49
Instant Heat Soldering Gun with built in lighting unit and 5 spare tips £4.59.

SOLDER

Multicore small reels, size 10 22g £1.45; Size 12 18g £1.45; 500gm reels 18g £8.59; Small packs of 18 or 22g 30p.

Our retail shops at 21 Deptford Broadway, London, SE8 (01-892 2999) and 38 Lower Addiscombe Road, Croydon (01-888 2359) stock some of the advertised goods for personal callers only. Ring them for details.

SEE PRACTICAL ELECTRONICS FOR INDIVIDUAL COMPONENT PRICES All prices quoted include VAT and UK/BFPO postage. Goods despatched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1 Send 10p for Multimeter catalogue—free on request on orders over £3. Official Orders accepted from Schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Surplus components always wanted.

OUR 44 page CATALOGUE FREE with orders over £2. (Send 10p if under, or 20p stamps for just catalogue).

SURPLUS CAPACITORS

15,000uF 6V 35mm dia x 55mm PC 19p
1,250uF 18V 20 x 50mm, tags 10p
1,250uF 40V 25 x 80mm, tags 20p
800uF 40V 25 x 50mm, tags 16p
10,000uF 10V 35 x 80mm, tags 18p
6,400uF 16V 35 x 80mm, tags 20p
4,000uF 25V 35 x 80mm, tags 25p
10,000uF 16V 40 x 80mm, tags 30p
50uF 350V 25 x 50mm tags 12p
1500uF 18V 18 x 34mm PC 6p
18,000uF 25V 50 x 105mm, screws 60p
NB: Add 30p postage for any quantity. Miniature resistors, carbon film 5% 1p each, £1.99 per 100 of one value 1R to 10M. 1W metal film 2 1/2p each.

BULK OFFERS

3mm wander plugs, black only at special price of £2.29/100. 63mA 20mm quick-blow fuses, £2/100 24V 1W LES lamps £3.99/100 50uF 350V 25 x 50mm tags £4/100

SPECIAL OFFER OF PLUG-IN MODULES

Large quantity just arrived, several diff types. Case size 77 x 50 x 50mm, either octal or 11 pin base. Send SAE for full list of types and circuits. Type R: Contains 6A 200V SCR, 4 x 5A 300V diodes, 24V read relay, C, R, etc. Octal base. With circuit. Only £1.99 each, 10 for £18.00. Type M: 5 BC184, C426, min. R's and C's 65p. Panel with 2 6A 400V triacs, 709C, 2N1711, 100V 1A bridge, 2 pots, 1 preset, zeners, R's, C's, etc. Only £1.59.

MULTIMETER MODEL LT22

WHAT A BARGAIN



Probably one of the lowest priced meters featuring a mirror scale, overload protection and 2000 ohms per volt sensitivity. Modern styled meter with unusually clear scale markings. Ranges: DC Volts 0-0.5-2.5-10-50-250-1000 AC Volts 0-10-50-250-1000 DC Current 0-50uA-25mA-250mA Resistance 0-50k-500k-5M (Mid Scale 300k-30k) db's 4 ranges —20db to +42db. Size 130 x 90 x 42mm. £12.70.

5V 12A REGULATED POWER SUPPLY

Brand new boxed fully stabilized PSU, complete with instruction manual. Load regulation 0.15%. Thermal & Electronic overload protection. Only £24.99.

TRANSFORMERS

All have mains primaries, secondaries as follows: 6-0-6V 100mA 65p; 9-0-9V 75mA £1.00; 12-0-12V 50mA 95p; 12-0-12V 100mA £1.18; 6.3V 1 1/2A £1.95; 6-0-6V 1 1/2A £2.39; 9-0-9V 1A £2.55; 12-0-12V 1A £2.85; 12V 5A £3.65; 12V 8A £4.35; 20V 55MA 90p; 22V 100mA £1.99; 25V 50mA 88p; Multi-tapped types, 0-12-15-20-24-30V 1A £3.50; 2A £5.00; 20-0-20V 2A £4.48; 55-0-55V 5A £8.30; 24-0-24V 2A £1.65.



£35.00 complete with circuit diagram
p & p

PYE STEREO GRAM CHASSIS

Complete ready to install—Wave bands L.M., VHF STEREO, VHF MONO. Controls for tuning, volume, balance, bass and treble. Power output 7 watts R.M.S. per channel 14 watts peak into 8 ohms. 2 x 8" approx chassis speakers and BSR C141 auto record player deck.

Personal shoppers only

NEW! **Sinclair** I.C. 20, 20 WATTS STEREO AMPLIFIER KIT WITH PZ 20 POWER UNIT **FANTASTIC SAVING**

A build-it-yourself stereo power amplifier with latest integrated circuitry 10W RMS per channel output, full short-circuit and overheat protection. **LIST £14.50** **DUM PRICE £4.95** p & p 11

Complete with PZ20 Power Supply

DIY SPEAKER KITS

EASY-TO-BUILD WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching cross-overs. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms. 30 watts peak, each unit. **£25.50** PER PAIR + p & p £5.50

Cabinet size 20" x 11" x 9 1/2" (approx.)



'COMPACT' FOR TOP VALUE

How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £7.50 — just what you need for low-power amplifiers. These infinite baffle enclosures come to you ready mitred and professionally finished. Each cabinet measures 12" x 9" x 5" (approx.) deep, and is in wood simulate. Complete with two 8" (approx.) speakers for max. power handling of 7 watts. **£7.50** per pair + p & p £1.70

15-WATT KIT IN CHASSIS FORM

When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the above enclosures. Size 13" x 8" (approx.) woofer (EMI), tweeter, and matching crossover. Power handling capacity 15 watts rms. 30 watts peak. **£8.50** PER SET + p & p £1.70

DECCA 20 WATTS STEREO SPEAKER

This matching loudspeaker system is hand-made, as only Decca know how, built to a specification, not down to a price.

The kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled PVC surrounds. Two 3 1/2" diameter approx. domed tweeters complete with crossover networks. **Our price per stereo pair £30.00** + p & p £4.00



20 x 20 WATT STEREO AMPLIFIER

£29.90
p & p £2.10



Superb Viscount IV unit in teak-finished cabinet Silver fascia with aluminum rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary. Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak.

HOW YOU CAN SAVE

SYSTEM 1B For only £80, you get the 20+20 watt Viscount IV amplifier, a pair of our 12-watt-rms Duo Type IIB matched speakers; a BSR MP 60 type deck complete with magnetic cartridge, de luxe plinth **£80.00** + p & p £6.50

SYSTEM 2 Comprising our 20+20 watt Viscount IV amplifier; a pair of our large Duo Type III matching speakers which handle 20watts rms each, and a BSR MP 60 type deck with magnetic cartridge, **£92.00** de luxe plinth and cover. + p & p £7.60

Carnegie surcharge to Scotland System 1B + 2.50 System 2 + 5.00

SPEAKERS Two models—Duo IIB, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/4" approx. **£34** PER PAIR + p & p £5.50

Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" approx. **£48** PER PAIR + p & p £7.50

TURNTABLE Popular BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover **£24.00** + p & p £3.50



30 x 30 WATT AMPLIFIER KIT

Specially designed by RT-VC for the experienced constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched; drilled and formed Cabinet is finished in teak veneer. Black fascia and easy-to-handle aluminium knobs. **£29.00** Output 30+30 watts rms, 60+60 peak. + p & p £2.10



BSR T145 8-TRACK CARTRIDGE PLAYER MECHANISM

Requires some attention. Complete with built in pre-amp, A.C. 240V **£6.95** + p & p £1.50

SPECIAL OFFER



TOURIST IV PUSH BUTTON CAR RADIO KIT



MOTOR TOP 10 AWARD

Complete with speaker, baffle and fixing strip. The Tourist IV for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs are used for manual tuning and volume control.

The modern style fascia has been designed to blend with most car interiors and the finished radio will slot into a standard car radio aperture. Size approx 7" x 2" x 4". Power Supply Nominal 12 volts positive or negative earth (altered internally) Power Output 4 watts into 4 ohms **£10.50** + p & p £1.50



35-WATT DISCO AMP

Here's the mono unit you need to start off with. Gives you a good solid 35 watts rms, 70 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble **£27.50** controls and master volume. + p & p £1.50



PORTABLE DISCO CONSOLE with built-in pre-amplifiers

Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single-play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simply connects into your existing slave or external amplifier. **£55.00** + p & p £6.50




70 & 100 WATT DISCO AMPS

Brilliantly styled for easy disco performance! Sloping fascia, so that you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth-acting, vertically mounted slide controls — master volume, tape level, mic level, deck level, PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level 70 watts rms, 140 watts peak output. All the big features as on the 70-watt disco amplifier, but with a massive 100 watts rms, 200 watts peak output power.

70 WATT £49.00 + p & p £3.00
100 WATT £65.00 + p & p £4

STEREO CASSETTE DECK KIT

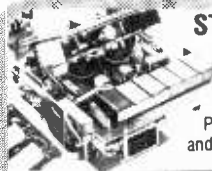Again, this kit is specially designed for the experienced constructor—for mounting into his own cabinet. Features include solenoid-assisted AUTO-STOP, 3-digit counter, record/replay PC board, mains transformer and input and output controls. AC BIAS AND ERASE. **£32.50** + p & p £1.50



DELUXE ACCESSORY KIT Comprises of a matched pair of dynamic mics. and two replacement slider level controls. **£3.95** + p & p £1.00
This item post FREE when purchased with Cassette Deck kit

ALL PRICES INC. VAT. AT 12 1/2%
GOODS NOT DESPATCHED OUTSIDE UK
All items subject to availability. Price correct at 1/11/77 and subject to change without notice

We are unable to show all our products, so please Send stamped addressed envelope for our fully descriptive catalogue and any further information



21c HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2
Personal Shoppers EDGWARE RD. 9.30a.m. - 5.30p.m. Half day Thurs
ACTON - Mail Order only no callers.

Minimum order on Access and Barclaycards £15
DO NOT SEND CARD
Just show your order giving your credit card number

AMBIT international (dept 85)

The Dynamic Twosome: Signalmaster/Audiomaster

After long and thorough deliberation, we are proud to announce a new unit from Larsholt - the Audiomaster. As ever, the instructions are designed to lead the unwary and the inexperienced- through point-to-point steps that culminate in a professionally styled and finished amplifier to complement the Signalmaster FM tuner. Price £79.00




Power: 25+25W RMS
THD: Less than 0.3%
Dynamic range: an exceptional 80dB
(Signalmaster shown on top of the Audiomaster)

The Signalmaster Mk.8 is equally simple to assemble, and results reflect the superb Scandinavian styling and careful electronic engineering. £85.00.



International Mk.2:
A choice of tuners for the more experienced constructors.

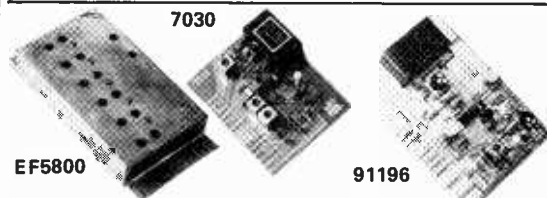A chassis, cabinet and front panel designed to be used with a variety of electronics inside. The standard set, with the Larsholt 7253 varicap FM tuner set, plus all necessary parts to complete costs £65.00. Alternative modules for the signal processing stages are available for the more advanced F.M. radio enthusiast/constructor. (EF5800/7030/91196)



From left to right, the EF5800 6 circuit varicap FM tunerhead. Two MOS RF stages, both with AGC control, and an ultra stable oscillator. Next the 7030 Linear Phase 10.7MHz IF. Distortion 0.08%, muting, AGC, meter, auto stereo switch outputs. Finally the new 91196 mpX decoder and combined birdy filter. Mono THD 0.05%, stereo sep. 55dB at 1kHz, 42dB at 10kHz - the best decoder module yet. EF5800.....£14.50 7030.....£10.95 91196.....£12.99 (Built).

Overall performance of the three modules when correctly assembled:- 30dB S/N at 0.85uV input. 60dB at 5uV. THD 0.09%. AFC holds THD below 0.2% over 400kHz if required. AGC effective over a 90dB range. Image rejection -90dB. Noise floor -73dB.

Components: Coils, ICs Filters, etc.

Radio ICs: (and modules)	Coils and filters:-
CA3089E/HA1137W FM 1.94	AM IFTs TOKO
CA3090AQ mpX 3.75	YRCS/YHCS types(10mm) 0.30
MC1310/KB4400 mpX 2.20	7MCS types (7mm) 0.30
HA1196 mpX 4.20	FM IFTs:
HA1197 AM radio 1.40	KACS/KALS types(10mm) 0.33
TBA120AS FM IF 1.00	94A types (10mm) 0.30
TBA651 AM radio 1.81	AM filters:-
UA720/CA3123E AM rad 1.40	CFT types ceramic (455) 0.55
LM380N 2W Audio 1.00	CFU type ceramic (470) 0.60
TBA810AS 7W Audio 1.09	SFD470 types (470) 0.75
TCA940 10W Audio 1.80	FM filters:-
TDA2020 20W Audio 2.99	CFS/SFE ceramic (10.7) 0.50
LM381N stereo preamp 1.81	SFE6MA (TV sound) 0.80
LM3900 Quad amp 0.68	3132 linear phase 2.25
78M12-20-24 volt reg ea:1.20*	MPX 19 & 38kHz notch 1.75
NE550A variable reg 0.50*	BLR3107 (4k7 imp) 1.75
TAA550B varicap reg 32v 0.50*	BLR2007 (3k3 imp) 1.75
NE560/2B PLL IC ea:2.50	23 or 36mH chokes 0.33
NE561B PLL IC 3.50	Tunerheads: (& tunersets)
NE565A/567V PLL ea:2.50	EF5600 5 gang varicap 12.80
810k kit for TBA810 amp 2.75	EC3302 3 gang varicap 5.50
2020k kit for 2020 amp 9.35	8319 (Larsholt) 12.00
92310 kit for mpX decoder 5.35	7252 tuner set complete 26.00
7020 kit for 3089 FM IF 6.65	7253 stereo tuner set 26.00
971197 kit for varicap AM radio tuner 9.65	Standard transistors also kept in stock - see lists for further detail and price information.
7700 built TV sound tuner 27.00	


Terms: Vat extra, 12.5% unless marked *, which is 8%, all complete tuners require £3.00 for packing and carriage. The standard P&P rate remains at 22p per order. Catalogue 40p. Phone (0277) 216029 (After 3pm please). SAE for free price lists.

Write to: 37a High Street
Brentwood, Essex: CM14 4RH

Still the *simplest, fastest* way of constructing your electronic circuits. Vero Electronics Ltd manufacture boards to suit most of your requirements, including, Verostrip, Dual in line I.C. boards, Plain Boards, etc. A new catalogue is available (price 10p + S.A.E. at least 7" x 9")

VERO

VERO BOARD

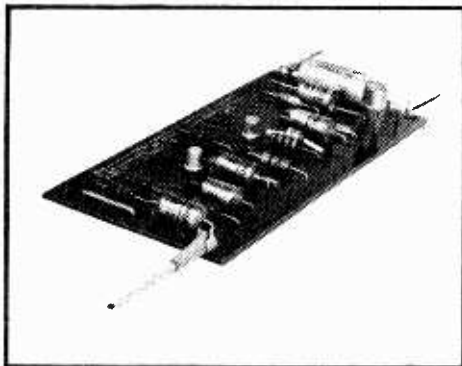

Vero Electronics Limited, Retail Dept., Industrial Estate, Chandler's Ford, Hants., SO5 3ZR Telephone: Chandler's Ford 7956 (STD 04215)

Teach yourself the latest techniques of digital electronics

Elementary course:

Digital Computer Logic & Electronics

1 Basic Computer Logic

2 Logical Circuit Elements

3 Designing Circuits to carry out

Logical Functions

4 Flip-flops and Registers

£4.20 + 80 pence P & P

Advanced course:

Design of Digital Systems

1 Computer Arithmetic

2 Boolean Logic

3 Arithmetic Circuits

4 Memories and Counters

5 Calculator Design

6 Computer Architecture

£6.20 + 80 pence P & P

Order both books at the same time for the bargain price of

£9.70 + 80 pence P & P

To: Cambridge Learning Enterprises (Dept. CIR) FREEPOST, Rivermill House, St. Ives, Huntingdon, Cambs. PE17 4BR

*Please send me set(s) of Design of Digital Systems at £7.00 each, p & p included.

*for set(s) of Digital Computer Logic and Electronics at £5.00 each, p & p included.

*for combined set(s) at £10.50 each, p & p included.

Name

Address

*delete as applicable. No need to use a stamp—just print FREEPOST on the envelope.

PW3

CASIO

fx-201P (illus.)
127 step
programmable
10 digit or 8 digit, 2 Exp.
127 Steps, 10 Inde.
mems, cos, sin, tan.
All log functions
Degree Rad. Un-
conditional jump
and manual jump
as well as indirect
address, subroutine
etc. The programme
function allows you
to handle any type
of calc. under any
condition.



*£49.95

fx-102. The world's first fractional
calculator. 10 digits or 8
plus 2 Exp. sin, cos, tan, Deg. rad. (exp.
10±2). Trig. Inverse common & Natural
logs. Reciprocals. Sexagesimal. Pi
entry. Statistical calcs. incl. 2 kinds of
Standard deviation and other applica-
tions. *£19.95

fx-19. 8 digits or 6 plus 2 Exp. as
102. Trig. inverse Trig. All log
functions. Sqr roots, Reciprocals.
Sexagesimal/Decimal conversions.
Fractions. 2 kinds of Standard Deviation
and other applications. *£16.95

fx-21. 8 digits 2 exponents. 21
Scientific functions. *£15.95

AL8 8-dig. Fractional Calcs.
standard deviations
remainder from division. Time
calcs. 2 mem. facs. *£13.95

AL10. As AL8 but with 10 digits!
*£15.95

TEXAS

SR56. (illus.)
100 Step
programmable
10 digit, 2 Exp.
10 inde memories,
all log trig
and Stat functions.
Can be programmed
for maths, elec-
tronic engineering,
statistical, financial
and navigation.
*£57.95(R)



SR52. 224 programme steps. 20
level parentheses. Card programmable.
Supplied with 20 blank magnetic cards
and prog. manual. (R)£199.00

Any of the following pre-programme
manuals: 1. Statistics. 2. Electrical
Engineering. 3. Mathematics. 4. Finance.
ONLY £25 each

SR51 II. 10 digit, 2 Exp Recharge-
able. All log and trig.
Hyperbolic x to the root of y. Rad & Deg.
Factorial. Mem. 3 Inde. mems. Linear
regression. Mean, variance, standard
deviation. Generation + 7 basic con-
verts., and their Inverse Engineering
Notation. (R)£47.95

T130. 48 functions plus Algebraic
operating system. 15 seats
parenthesis. Constant, roots, powers,
reciprocals. Sci notation. Log, trig, deg
rad, mem, step function.
*£15.95. Nickel Charger Kit £7.95

The ZYCON range of Quality Electronic Watches

L.C.D.

KLC3

L.C.D. Constant display
Shows Hrs, Mins &
pulsating secs. Chrome
finish with Stainless
Steel back and FREE
Adjustable S/Steel
bracelet. *£22.50



Gold Plate £24.50

KLC Stop Watch
Constantly shows hrs, mins
& Pulsating secs. Press
command button for mth
& date, press again for
mins & secs. May be set
to alternate hr & mins to
mth & date every 2 secs.
resets to time. 4 yr cal.
Nite Lite. PLUS STOP
WATCH FACILITIES *£45.90



Gold Plate £49.90.
FREE matching bracelets
with each.

KLC9

Continuous hrs, mins &
pulsating secs. Press
command button for mth
& date. Press again for
secs readout. Setting for
alternating hrs & mins to
mth & date every 2 secs.
Auto-time reset. 4 yr
calendar. *Nite-Lite*.
FREE matching S/Steel
bracelet *£39.95



LADIES DIGITAL THE IDEAL PRESENT!

An elegant 6-function
watch. Shows Hrs,
Mins, Secs, Mth,
Date, Day! She'll love
this piece of
miniaturised elec-
tronic wizardry! Gold
Plate or with stylised
Chrome Bezel, each
with matching
bracelet.



GOLD PLATE *£39.95
S/Steel *£36.95

L.E.D.

KED1

Ideal present! This stylish
5-function L.E.D. shows
Hours, Minutes, Seconds,
Month and Date. 4 year
calendar. Beautifully
finished with S/steel back
& FREE stylised
leatherette strap
Matching S/steel Bracelet *£15.95



KED5

6-Functs. Shows Hrs, Mins,
Secs, Mth & Date and Day.
4-Yr calendar. Beautifully
finished with S/steel back
& FREE Matching Stainless
Steel Bracelet
*£19.95



Gold Plate *£22.95

KED6

A fantastic 6-Functions—
window display shows
Hrs, Mins, Secs, Mth &
Date. Day of week in
letters. Single button.
Auto-hold & Fade-out.
4-Yr calendar. Case in
Heavy Rhodium on Brass
& S/steel back. FREE
matching S/steel
adjustable bracelet.
*£29.95 Gold Plate *£33.90




KED6 PLUS

Month & Day of the Week
in Letters! Shows Hrs,
Mins, Secs, Date, Mth &
Date, Day of Week, Auto
4-Yr calendar, A.M./P.M.
Set/indicate. One of the
most sophisticated
watches at this price.
Accurate to within a few
secs a year. Finished in
Satin Stainless Steel with
FREE matching Steel
bracelet. Trimest watch in the world.
*£37.50 ONLY Gold Plate *£40.50



CBM

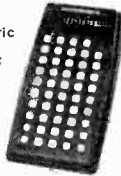4190R (illus.)
10-digit.
2 Exp. 90 function
pre-programmed. Metric
conversions. Extra
functions to the 4148R:
Perms and combina-
tions. Gamma. Pol-
son and Binomial
distributions. fac-
torial, complex num-
bers, hyperbolic
functions, linear
regression and In-
tegration of Y = f(x).



(R)£36.95

7919D. 8-digit or 5-digit + 2 Exp.
Full trig and log functions.
Sqr root. Reciprocals, Y^x, X^y, Pi. Register
exchange. Memory plus. Store recall.
Sign change. Algebraic logic.

£10.95

4148. 10-digit + 2 Exp. Full log and
trig funct. X^y, Reciprocal, π,
x root of y. Polar rectangular co-ordi-
nates. 2-store mem. Mean and Standard
deviation. (R)£26.95

1800. As 4148 but Green display and
Bat operation. *£20.95*

ROCKWELL

64RD (illus.)
12-digit
or 8-digit + 2 Exp.
Additional to the
44RD. Polar rec.,
co-ordinates. Log
Trig, rad or grad.
£24.50



44RD. 9-digit or
5-digit and 2 Exp.
Green Display. Store.
Similar to the 63R
less factorial. *£19.50*

24K. Stainless Steel Slimline. Green
display. In beautiful leatherette wallet
to hold pen, note pad and credit cards
(all included). Full memory. Click
buttons. Rechargeable.
Including recharger. (R)£21.95

DECIMO DIGITAL CLOCK RADIO



**LARGE
DIGITAL
READOUT**

This is the most unique clock/radio in
the country today having a soft, 1 1/2" high
orange-glow digital readout which is
completely silent and non-pulsating.
In a beautifully styled enclosure with
up-to-date VHF/MW radio. You can
awake to soft music or alarm. Auto-
matic 90 minute 'sleep' button in case
you drop off while the radio is on!

OUR PRICE £33.95
Plus £1 P&P

NEW ZYTRONIC TELE-GAMES



Tennis, Football, Squash. Score marker.
Ball sound effects—2 pings. Player
identification. Red light point winner
indicator. *£39.90

DE LUXE



THIS DELUXE MODEL
HAS Tennis, Football
Squash, Solo. 2 bat sizes
2 Ball speeds. 3 distinct
pings—one for point score, one for bat
strike ball, one for ball strike boundary
and automatic scoring. *£48.90

These games are easy to play and a joy for all the family!
ALL ITEMS CARRY 1 YR GUAR. PRICES INCLUDE VAT
* FREE B.S.I. adaptor. (R) FREE Charger

NOVUS

4640 (illus.)
10 digit, 2 Exp. 54 functions.
4-level roll stack. 3 Fully addressable
memories. Logs, Trigs, Stat and Metric
conversions etc. (R)£42.95



4650. 8 digit, 2 Exp. Algebraic logic
Addressable. Trig, sin, cos, tan and
Inverse trig functions. Deg rad. Reci-
procal. Sqr root. Powers and Pi entry.
Mem Ex and Register Ex (R)£27.50

4525. 8 + 2 Exp. 100 step prog. R.P.N.
Full log and trig. XY Exchange.
Mem. 4 roll stack, skip, delete. Ad-
ditional progs within the 100 step
(R)£34.95

4515. 100 step prog
version (R)£31.95

6010. Metric. *£15.95*

6035. 100-step programmable Statis-
tician. Rechargeable. (R)£34.95

6025. Rechargeable. Financier 100-
step programmable. (R)£34.95

4510. 8 digits. 3 level stack. All trig &
log functions. √. π. Reci-
procal Memory, etc. *£12.95*

6030. Statistician. *£15.95*

SINCLAIR

CAMBRIDGE SCIENTIFIC all trig, log &
deg. rad. etc. *£8.95
OXFORD SCIENTIFIC larger version of
above. Green display
PARENTHESIS *£13.90*

ORDER FORM

PHONE CALLS AND PERSONAL CALLERS WELCOME MONS TO
THURS BETWEEN 2 & 5 p.m. 01-458 4755. SUNDAYS 10 a.m. to 1 p.m.
To: BARCLAY ELECTRONICS Dept. 13PW,
1115 FINCHLEY ROAD, TEMPLE FORTUNE, LONDON N.W.11

Please send me.....
with/without optional mains adaptor. I enclose cheque/money order total
value £..... Please add 55p to all items to cover p. & p.
NAME.....
ADDRESS.....

PHONE BARCLAYCARD OR
ACCESS ORDERS.

barclay

BOOKS for Electronics Enthusiasts



COMING SOON—Radio, TV & Audio Technical Reference Book - S.W. Amos. The complete reference book compiled by 31 experts in all aspects of radio, TV & audio.
Spring 77. 1,200 pages

COMING SOON—Beginner's Guide to Radio—8th Edition - Gordon J. King. Completely updated and rewritten it surveys the whole field of radio.
Summer 77. 260 pages

SPECIAL SERIES FEATURE

Master Books

Authoritative yet easily understood by those with no technical knowledge whatsoever, the texts are supplemented by many highly informative illustrations. Each book is written by an expert in his own special field.

MASTER ELECTRONICS IN MUSIC

T.D. Towers

Contents: Creating Musical Sounds by Electricity. Making Musical Instruments Louder. Musical Special Effects by Electronics. Electronic Keyboard Instruments. Electric Guitars. Magnetic Tape Music. The Robot Drummer. Music Synthesisers. Music by Computer. Index.
130 pages. £2.50

MASTER HI-FI INSTALLATION

Gordon J. King

Contents: How it Works. The Amplifier. Programme Signal Sources. Importance of a Good F.M. Signal. The Loudspeaker. Mono, Stereo & Quadrophonic Sound. Four-channel Techniques. Room Effects. Best Use of Controls. Terminology. Index.
150 pages. £2.50

MASTER STEREO CASSETTE RECORDING

I.R. Sinclair

Contents: Stereo Systems. Signal Sources. Controls and Facilities. Making the Recording. Replaying and Monitoring. Essential Maintenance. Aids to Better Recording. Noise Reduction Systems. Cassette Recorder and Hi-Fi.
140 pages. £2.50

STANDARD WORKS

FOUNDATIONS OF WIRELESS AND ELECTRONICS

9th Edition. M.G. Scroggie. 552 pages. £3.75

RADIO VALVE AND SEMICONDUCTOR DATA

10th Edition. A.M. Ball. 240 pages. £2.00



Newnes Technical Books

Borough Green, Sevenoaks, Kent TN15 8PH

FREE!

STEREO HEADPHONES
SUPPLIED WITH
EVERY COMPLETE ORDER

SOLENT MARK II STEREO AUDIO SYSTEM

£5 down

Solent Mark II Stereo Tuner Amplifier chassis with AM/FM radio covering long, medium, short and stereo FM wave bands.

Separate Bass and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) AFC Switching Tape record and playback facilities. Dimensions 18½" x 9" x 3½". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units. **Order early limited stocks available cash price £69.95. Credit Sale £5.00 deposit 9 monthly payments of £8.70 (Total Credit price £83.30). P. & P. £4.00. Send £9.00 today.**

Chassis only available for cash at £49.00 + p. & p. £3.00 Full 12 months Guarantee.

Access and Barclaycard Orders Accepted by Telephone
CALLERS WELCOME

LEWIS radio PW/3/77, 100 CHASE SIDE SOUTHGATE
LONDON N14 5PL Telephone: 01-882-1644

Wire Wound Resistors. Our selection of mixed values. 30 for £1.40. 100 for £3.50.

Audio Amplifier Module. Mullard LP1173. Output nominal 10 watt. Supply voltage +24vt. With data and circuit £2.30.

Varicap Control Selector. 4 way 25K. £1.50. 6 way 14.5K. £2.00.

Mains Croppers. 10 mixed values £1.00.

Edgewise Level Meters. 200µA. Size 1" overall 50p.

15 Assorted Switches. Micro, push button, etc. £1.90.

Tag Strips. 3 way to 7 way. 50 for £1.15.

Chrome Plastic Knobs. 3 Types 4 of each with spring clip. £1.25.

Copper Clad Laminate. 8" x 7"—3 boards £1.00 + 8%.

Ferric Chloride. 1lb 65p + 8%.

Crystals HC6U. (MHz) 12700; 12891.6; 9455.55; 9530.55; 9087.5; 9456.25; 52.01667; 52.02500; 37.7625; 51.56667; 52.03333; 9090.62; 9531.94; 9533.33, 50p each.

Electrolytics. 32/32/32µF, 325v. 2" x 1½" 35p; 80µF 150v 1½" x 1" 20p; 2000µF 30v, 2½" x 1" 25p; 2000µF 35v 3" x 1" 30p; 470µF 100v 3" x 1½" 25p; 2000/2000µF 25v 2" x 1½" 35p; 700µF 200v 3½" x 1½" 30p; 16/16µF 275v 1½" x 1" 20p; 4500/900/900µF 30v 2½" x 1½" 50p; 2500µF 40v 3" x 1½" 40p; 470µF 25v 1½" x ½" 15p; 4,000µF 25v 3" x 1½" 40p; 32µF 450v 1½" x 1" 30p; 8µF 16µF 450v 1½" x 1" 30p; 1000µF 12v 1½" x ½" 15p; 5000µF 50v 2" x 1½" 50p; 150/200/200µF 300v 3" x 1½" 50p; 16/16/16µF 350v 2" x 1" 30p; 50/50µF 500v 3½" x 1½" 50p.

Miniature Presets—Selection of various values 10 for 65p.

Coil Formers. 50 mixed. £1.25.

Slider Volume Controls. 1K Lin; 100K Log; 1 Meg Log; 25K Lin, 25K Log; 10K/100K Log; 100K/100K Log; 50K Log, 35p each.

Aluminium Chassis. 7½" x 5½" x 2½" 65p. 10" x 7½" x 2½" 75p. 11" x 7½" x 2½" 85p + 8%.

Thorn TA/28. Slide synchroniser for 4 track reel to reel recorders. 6 pin DIN socket models. £4.50.

BSR Single Play Decks with Cue. Fitted stereo cartridge. P146 £11.00. P153 £12.00.

Low Voltage Transformers—Prim. 200/240 VT. A.C. (17VT 17VT 34VT 2 amp £2.00) 7½VT 20VT £1.25 (28 VT. 750 MA) (10 VT-10 VT-20 VT 500 MA) (7 VT-12 VT-19 VT 750 MA) £1.50 each. 8% VAT.

4 Phono Sockets on Paxolin Panel. 5 for 75p.

E.H.T. Cable 13/0-2, 10 metres 75p, VAT 8%.

TUNING CAPACITORS—(380 PF 11-5 PF; 320 PF 11-5 PF); (388 PF 10-5 PF; 324 PF 10-5 PF) 95p each; (500 PF 500 PF) 95p (3 Gang Slow Motion Drive 380 PF 380 PF) £1.25.

Please add 20% P.P. Unless stated free P/P. VAT 12½% to be added to total order unless stated 8%. No goods despatched outside U.K.

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON LU3 1JD, BEDS.




NEW! For home constructor

FREE BLOB BOARD!

NOW STOCKED BY ALL GOOD COMPONENT STOCKISTS.

worth 30p

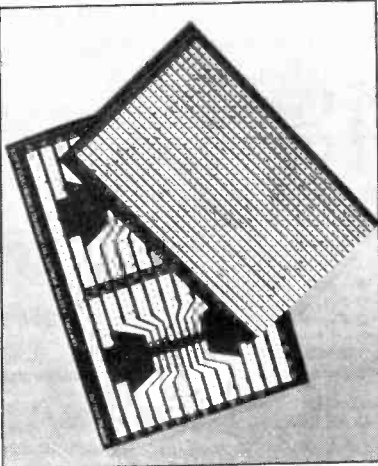

BLOB BOARDS

Circuit diagram to circuit board in minutes. Layout circuit plan on .1" graph paper. Select Blob Board, lay components out with leads on copper strip. Blob of solder onto lead and your circuit is complete. Blob Boards normally half price of competitive boards. Roller tinned to solder components directly. No drilling or mounting. Modifications in seconds. Blob Board is re-usable.


Blob Boards are circuit boards designed exclusively for the home constructor and prototype engineer and are normally half the price of competitive boards. Blob Boards are roller tinned for ease of soldering, most require no cutting or breaking of contact rails. HALF PRICE AND RE-USABLE. That is NEW!

Blob Board .1" or .15" All approx. inch sizes	1 off	3 off	Dip Blob Boards	1 off	3 off
ZB1V 2.5 x 5	£0.30	£0.75	ZB11C 4.5. x 3	£0.36	£0.90
ZB2V 2.5 x 3.75	£0.23	£0.57	ZB21C 4.8. x 3.2	£0.40	£0.96
ZB3V 3.75 x 5	£0.46	£1.14	ZB41C 4.75 x 7.5	£0.85	£2.13
ZB4V 10 x 6	£1.51	£3.78	ZB81C 9.5 x 7.5	£1.70	£4.26
Discrete Blob Board	1 off	3 off	Sample pack: 1 off ZB1V + 1 off ZB8D + 1 off ZB21C normally £2.32 only	£2.00 + free Blob Board.	
ZB5D 3.6 x 2.4	£0.20	£0.51	Many other sizes and patterns available add 30p post + 8% VAT to all orders.		
ZB6D 2.4. x 7.3	£0.42	£1.05			
ZB7D 4.9 x 7.3	£0.69	£1.75			
ZB8D 9 x 7.5	£1.62	£4.05			



S-DeC

Take an S-DeC, take a small stock of components. Plug components into S-DeC, no soldering, make a radio receiver, light operated switch, 3 stage amplifier. When circuit is made unplug components and use them again to make a morse practice oscillator, LC oscillator, binary counter and any other discrete circuitry. See Practical Wireless for new series of S-DeC projects. S-DeC + step by step instructions to build above projects and 3 more + which components to use + free control panel for mounting switches, lamps etc. + free Blob Board. S-DeC only £1.98 + 37p (VAT + post) send only £2.35.

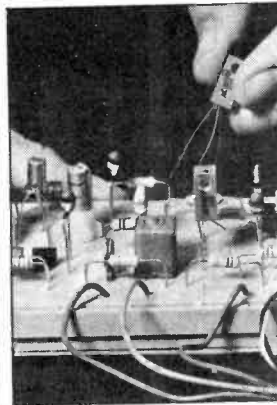

T-DeC

If you are using IC's to build circuits use T-DeC for 1 chip circuits and U-DeC A for 2 chip circuits. Draw circuit on graph paper, plug IC into Adaptor and plug into DeC. No soldering, no bent leads, no wasted IC chip. Lines on DeC show contact rails, plug discrete components in. Cross overs, connections are made using different coloured leads. Circuit completed and working unplug components and use for next circuit. No soldering, no damage to components. Use your DeC and small stock of components over and over again. T-DeC send £4.30. U-DeC "A" send £4.60. Adaptor send £2.30.



DRILL·SAW GRIND·BURR BRUSH·POLISH

PB announce a precision British built drill for the home constructor. Works better than most bigger drills and can be used for fine detailed work. Drills through any circuit board, need to break copper strip simply grind it off.
9000 RPM Drill + 20 Assorted tools £11.20 (+VAT + post) Send £13.00.
9000 RPM Drill only £5.22 + post + VAT send £6.00.
Multi-purpose Drill stand £10.60 + Post + VAT send £12.00.

POT LUCK

Off cuts of fibre glass circuit board 5 sq. ft.	£1.50.
Double sided fibre glass p.c.b. 5 sq. ft.	£2.00.
Ferric chloride 5 litre mix	£2.00.
Negative developer 1 litre	£1.50.

Add £0.75p. to all above for Post + VAT.

PB Electronics Scotland Ltd.
57 High Street, Saffron Walden, Essex, CB10 1AA.
For leaflets and further information please send stamped addressed envelope.

Trade please exchange for Blob Board ZB1V worth 30p when purchasing any of the above items.
Trade enquiries please contact Bambridge, London.
Mr. John Evans Tel: 01-228 9227

30p


SAXON ENTERTAINMENTS LTD

A FULL RANGE OF PRINTED CIRCUIT
MODULES FOR ALL P.A. & DISCO &
GROUP APPLICATIONS

SYSTEM 7000 HAS IT!

A COMPLETE SELECTION OF READY
TO USE PROFESSIONAL QUALITY
AUDIO & LIGHTING EQUIPMENT

POWER AMPLIFIER MODULES 30—240 WATTS

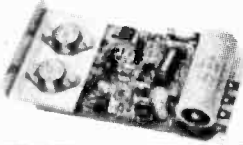

- Fully tested & guaranteed.
- Full RMS Sine Wave output.
- Distortion typically 0-2%
- 10 Transistors, 4 Diodes.
- Response 30HZ-30KHZ
- Fully short & open circuit proof
- Sensitivity suits most mixers.
- Built-in surge suppression & compensation
- Twin D.C. & output fuses.
- Top-grade components throughout.

30 Watts rms	60 Watts rms		120 Watts rms		240W rms
SA308 30W rms/ 8 ohms £8-50	SA604 60W rms/ 4 ohms £12-50	SA608 60W rms/ 8 ohms £12-50	SA1204 120W rms/ 4 ohms £13-50	SA1208 120W rms/ 18 ohms £14-50	SA2404 240W rms/ 4 ohms £25-50

POWER SUPPLIES FOR THE ABOVE MODULES—READY WIRED & FUSED ON
GLASS FIBRE PCB

PM301 For 1/2 SA308 £8-90	PM601/4 For 1/2 SA604 £12-50	PM601/8 For 1/2 SA608 £12-50	PM1201/4 For 1 SA1204 £12-50	PM1201/8 For 1 SA1208 £12-50	PM1202/4 For 2 SA1204 £19-50	PM1202/8 For 2 SA1208 £19-50	PM2404/1 For 1 SA2404 £19-50
------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------

DISCO MIXER MODULES Mono or Stereo (with Auto Fade)



Printed circuit module assembled &
tested with all components ready
mounted.

Mono £19-50 Stereo £29-50

* Front panel to suit £3-50

- Mixes two decks, tape and mic.
- Wide-range bass & treble controls on mic. & music channels.
- Variable autofade (mic. override)
- Ample headphone power.
- Needs only front panel* knobs and selector switch.
- Push-pull monitor circuit.
- 20HZ-20KHZ—Noise — 77dB
- Comprehensive wiring details provided
- Perfect for Incorporation in your system

ALL PURPOSE CUSTOM—MIXER MODULES (Mono or Stereo)



- Using these modules, mixers may be built to your specification up to 20 Channels, mono or stereo, or a combination of both. System 7000 custom-mixer modules have monitoring facilities too!

INPUT MODULES

- Accept low/high 2 mics, ceramic & magnetic cartridges, all musical instruments & line signals
- Low-noise circuitry—high grade components
- Wide-range bass & treble controls (23dB)
- 20HZ-30KHZ Noise — 80dB
- Echo sound/return etc easily fitted
- Mono—IM7001M £5-50
- Stereo—IM7001S

Power supply for up to 20 modules—PPM18 £8-50

MIXING MODULES

- Only one required per mixer track whether mono or stereo
- Feeds up to ten power modules
- Complete with 1/2W monitor amplifier
- Accepts up to 20 input modules
- Will match any other make of amplifier
- Mono—IM7002M £9-00
- Stereo—IM7002S

QUADRAFACT FOUR CHANNEL 4KW SEQUENCER WITH DIMMERS

A COMPLETE
LIGHT
SHOW!!



£29-50

* PANEL £2-50

THE ONLY MODULAR
SOUND TO LIGHT UNIT WITH:

- * Four integral dimmers.
- * Two + Two sequencer
- * Automatic audio level

- RCA 8A Triacs
- Sequence 0-5-20HZ
- I.C. circuitry
- Needs only front panel*
- Audio trigger 1-240W
- Fully suppressed
- Individual fuses
- Complete with speed Slider control

THREE CHANNEL 3KW SOUND/LITE—Low Cost— Superb Value




£16-50

* Panel £2-50

- Long-established Saxon design
- Individual level controls + master
- RCA 8A Triacs
- 1W-240W Input
- Individual channel fuses
- Needs only front panel*

SYSTEM 7000

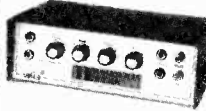MINOTAUR 100—All Purpose Wide Range Amplifier



- 100W rms — 1dB
 - Standard 8 ohm output
 - Twin mixed inputs accept a wide range of signals
 - 30HZ-30KHZ ±2dB
 - 23dB bass/treble
- A four input, high power amplifier which will deliver up to 150 watts output. An absolute must where multiple mixing & power are required
- Four individually mixed inputs
 - Wide range bass/treble+master

An extremely compact and versatile amplifier with full protection and a clean, attractive appearance. Ideal for all groups, disco's & clubs

£49-50

- Vinylde covered case
- Fully short proof
- Superb value for money



SAXON 150 HEAVY DUTY AMPLIFIER £59-00

SYSTEM 7000

COMPLETE DISCO MIXERS (with Auto Fade)

*Ready to plug in & use
* Mono or Stereo



- Automatic mic. override
- Mixes two decks, tape & mic
- Facilities as for modular version opposite
- Mute positions on headphone selector for ease of monitoring
- Two tone stainless steel panel
- Sockets on front & rear panels
- Left/right deck fader
- May be operated from any power supply or from mains

The choice of the professional D.J.

Controls: Mic. volume, bass, treble, A/fade depth, tape, L/deck r/deck vols., treble, bass, master, headphones vol., selector, left/right fader.

Stereo 18V £33-50
Stereo Mains £59-50

MONO 18V £37-50 MONO MAINS £43-50

SYSTEM 7000 COMPLETE CUSTOM MIXERS (Mono or Stereo)

- Similar to the modules opposite these mixing modules are complete with front panels, sockets, monitor switch etc. Up to 20 channels (mono or stereo) may be incorporated in one system with any number of output tracks.

Ideal for the economical & quick assembly of a purpose built mixer with individual channel monitoring, and optional extra facilities—consult our technical dept. to discuss your needs.

- Stainless steel panels
 - Built-in monitoring
 - Will feed all amplifiers
 - Professional appearance
 - Accepts all types or signals
 - Infinitely adaptable
- | | |
|----------------------|--------|
| Mono Input module | £8-50 |
| Stereo Input module | £12-00 |
| Mono mixing module | £8-50 |
| Stereo mixing module | £12-00 |
| Power supply | £8-50 |

SYSTEM 7000 LIGHTING CONTROL MK II



HAS YOUR SOUND TO
LIGHT CONVERTER GOT:

- 4000W Handling
- Integral individual dimmers
- Automatic audio level control
- Two + Two sequence facility

OURS HAS! — PLUS:

- Sophisticated I.C. circuitry
- Heavy duty terminations
- Bondene case
- Matches System 7000 mixers

ALL YOUR ELECTRONIC LIGHTING NEEDS IN ONE SUPERBLY DESIGNED UNIT. £42-50

SAXON SOUND-LITE—An old design with improved appearance

- Scintillating performance
 - Similar to Mk II lighting control in appearance
 - 3KW power handling
 - Individual bass, treble, middle & master controls
 - 1-240W input
 - Fully fused & isolated
- Complete with heavy duty terminations

£24-75

EXPORTERS TO 17 COUNTRIES — ENQUIRIES WELCOMED — NATIONWIDE DISTRIBUTION BY NORMAN

BRANCHES AT CROYDON & WALLINGFORD

CUSTOMERS INCLUDE BBC, LONDON WEEKEND TV,
SCOTTISH TELEVISION, NATIONAL TYRES,
POST OFFICE, GOVT. DEPTS.

**A READY-TO-USE 100W STEREO DISCO WITH
BUILT-IN SOUND/LITE SEQUENCER AND LIGHTS
FOR ONLY £199**

CENTAUR

(Carr £5 in U.K.)

- 100W rms stereo output
- Twin heavy duty loudspeaker
- Four channel fully automatic sound-lite with variable speed sequence
- I.C. pre-amp with tape input & X fade
- Separate mic. & music treble and bass controls
- Attractive Vynide cabinets
- Twin BSR decks with autostop & lift arm



Incredible value for money—2/3 cost of separate parts!

- All connecting leads supplied—ready to plug in
- Loudspeakers have kick-proof grills
- Four colour built-in light display gives ever changing pattern with or without music

**A READY-TO-USE 50W MONO DISCO COMPLETE WITH
TWIN HEAVY DUTY LOUDSPEAKERS FOR ONLY**

- 50W rms output
- Twin heavy duty loudspeakers
- Separate mic. input
- Wide range bass & treble controls
- Smart Vynide cases—clip together to form one neat package
- Twin BSR decks with lift & autostop



£89.90
(carr UK £3)

- Tremendous value—price includes leads just plug in & go!

Accessories for complete discos & other systems

- Dual Impedance Electret Condenser MIC C/W Lead/Cup **£13.95**
- Crown Stereo Headphones **only £6.75**
- Heavy Duty Boom Stand **£12.50**

CUSTOM BUILT DISCOS

A full range of custom consoles are available using System 7000, from 50W mono to 500W stereo. Ask for our price list.




LOUDSPEAKER CABINETS

- Kick proof grills.
- Jointed construction
- Protective corners finished.
- Smart & professional

Single Twelve: Empty £14
With 60W unit **£33.00**
Twin Twelve: Empty **£24**
With units from **£59.00**
Folded Horn—Full range P.A. Bin 100W RMS **£120.00**

This cabinet is 3-4 times as loud as conventional systems for a given input power—thus there is a saving in overall size & cost.

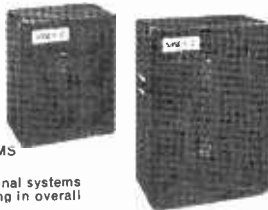- Many other cabinets available—ask for details.



EMPTY DISCO CONSOLES

- £19 with plain motorboard. **£21** with cutouts.
- Black Vynide finish
- Protective corners
- With your choice of cutouts

STROBES & PROJECTORS (We stock the full Pluto range) Send for details

SUPERSTROBE £19.75

- 2-3 Joules
- 80W Tube for long life
- Compact 4" x 4" x 4"

PRO-STROBE £32.50

- 6-8 Joules
- External trigger
- Long Life tube timer circuit



150 WATT LIQUID WHEEL PROJECTOR

- Accepts all accessories
 - C/w with wheel & motor plate
 - Sturdy steel construction
- Remarkable value—
Sold elsewhere at £39.50. Our price is only: **£31.50**

Please add 8% VAT to all orders (12½% for SA308/PM301)
We accept Access & Barclaycard—simply telephone or send your card number—Do not send your card.

You may pay by cheque, crossed postal orders, cash (registered) or bank draft

To order—or for advice phone (01) 684 6385 or (01) 684 0098
Mail orders to: 327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS
Shop open 9am-5pm Mon.-Sat. Mail order desk 10am-3pm Mon.-Fri.

Wallingford Branch: Flint House, High St., Wallingford, Oxon
(Callers only)
9am-5pm Mon.-Sat. Telephone (0491) 35529

ROSE ELECTRICAL TO BONA FIDE TRADE CUSTOMERS

Sparkrite mk2

Capacitive discharge electronic ignition kit

VOTED BEST
OF 2 SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE
OCT 74



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions

OPTIONAL EXTRAS

Electronic/conventional ignition switch.
Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device. Includes switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service — phone (0922) 33008

**PRICES INCLUDE VAT, POST AND PACKING.
IMPROVE PERFORMANCE & ECONOMY NOW**

Note—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £33.95 inc. V.A.T. post & packing.

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, Dept., PW/3
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name
Address

Mk. 2 Diy Ass. Kit @ £11.80

Mk. 2 Ready Built Negative Earth @ £14.97

Mk. 2 Ready Built Positive Earth @ £14.97

Ignition Changeover switches @ £4.30

R.P.M. Limit systems in above units @ £2.42


I enclose cheque/PO's
for **£**

Cheque No.

Send SAE if brochure
only required.

LATEST EDITION
**RADIO
 COMMUNICATION
 HANDBOOK**

Fifth edition
VOLUME I

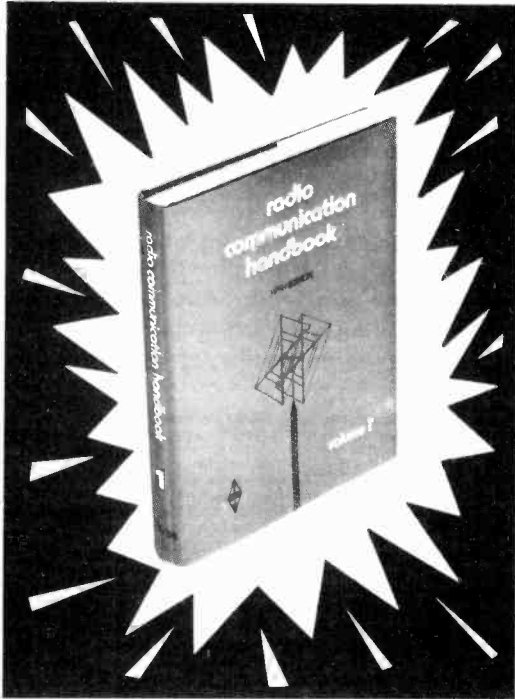

First published in 1938, the *Radio Communication Handbook* has long been a standard textbook on the theory and practice of amateur radio. Its almost encyclopedic coverage of this fascinating subject draws on the practical experience, gained over many years, of a multitude of radio amateurs in this country and abroad. The text, which has been completely revised and reset for this edition, is supplemented by hundreds of line diagrams, together with many photographs, charts and tables, making this probably the most valuable all-round reference book a radio amateur can possess.

- Volume I chapter titles**
1. Principles
 2. Electronic tubes and valves
 3. Semiconductors
 4. HF receivers
 5. VHF and uhf receivers
 6. HF transmitters
 7. VHF and uhf transmitters
 8. Keying and break-in
 9. Modulation systems
 10. RTTY

464 + xvi pages £9.15 including P and P

- Volume 2** (in preparation for publication early 1977) chapter titles:
11. Propagation
 12. HF aerials
 13. VHF and uhf aerials
 14. Mobile and portable equipment
 15. Noise
 16. Power supplies
 17. Interference
 18. Measurements
 19. Operating technique and station layout
 20. Amateur satellite communication
 21. Image communication
 22. The RSGB and the radio amateur
 23. General data

Size and price to be advised.

Obtainable from
RSGB PUBLICATIONS (Sales)
 35 Doughty Street, London WC1N 2AE

CMOS WITH DISCOUNTS!

Any mix: Discount 10% 25+, 25% 100+, 33% 1000+



**CU
 4 CMOS!**

4000	0.20	4039	3.09	4081	0.24	14505	4.38	'E' LED Displays	
4001	0.20	4040	1.19	4082	0.24	14506	0.57	DL-704E 0.3"	70p
4002	0.20	4041	0.93	4085	0.30	14507	0.80	DL-707E 0.3"	70p
4006	1.31	4042	0.93	4086	0.80	14508	3.08	DL-728E 2 x 0.5"	1.80
4007	0.20	4043	1.12	4089	1.74	14510	1.51	DL-727E 2 x 0.5"	1.80
4008	1.07	4044	1.04	4093	0.89	14511	1.74	DL-750E 0.6"	1.50
4008	0.60	4045	1.56	4094	2.08	14512	1.03	DL-747E 0.6"	1.50
4010	0.60	4046	1.48	4095	1.16	14514	3.47	Red Leds	
4011	0.20	4047	1.01	4096	1.16	14515	3.47	0.1"	15p
4012	0.20	4048	0.60	4097	4.13	14516	1.51	0.2"	15p
4013	0.60	4049	0.50	4098	1.22	14517	4.02	Clock Chips	
4014	1.12	4050	0.60	4099	2.03	14518	1.39	AY-5-1224A	3.50
4015	1.12	4051	1.04	40101	1.76	14519	0.57	MK50253	5.50
4016	0.60	4052	1.04	40102	2.18	14520	1.39	Soldercon Pins	
4017	1.12	4053	1.04	40103	2.16	14521	2.77	100	60p
4018	1.12	4054	1.29	40104	2.26	14522	2.15	1000	4.00
4019	0.80	4055	1.46	40107	0.86	14526	2.15	2500	8.75
4020	1.24	4056	1.46	40108	6.18	14527	1.76	DIL Sockets	
4021	1.12	4057	29.81	40109	2.21	14528	1.22	8 Pin	12p
4022	1.07	4059	6.20	40161	4.30	14529	1.72	14/16 Pin	15p
4023	0.20	4060	1.24	40182	7.73	14530	0.85	Red Acrylic Filter	
4024	0.87	4061	25.60	40194	2.26	14531	1.74	For LED displays	
4025	0.20	4062	10.10	40257	2.26	14532	1.39	157 x 92 x 3mm 70p	
4026	1.92	4063	1.22	4700	1.75	14534	8.15	Push Switches	
4027	0.60	4066	0.69	7083	4.25	14536	4.00	Type SW9	15p
4028	1.00	4067	4.13	14160	1.18	14537	13.17	Op-Amps	
4029	1.27	4068	0.24	14161	1.18	14539	1.24	CA3130	
4030	0.60	4069	0.24	14162	1.18	14541	1.62	(COS/MOS) 1.00	
4031	2.46	4070	0.65	14163	1.18	14543	1.82	CA3140	
4032	1.19	4071	0.24	14174	1.08	14549	4.10	(BI/MOS) 95p	
4033	1.55	4072	0.24	14175	1.04	14552	10.50	25p	
4034	2.11	4073	0.24	14194	1.17	14553	4.88		
4035	1.31	4075	0.24	14490	6.51	14554	1.67		
4036	3.09	4076	1.71	14501	0.20	14555	1.01		
4037	1.06	4077	0.65	14502	1.38	14556	1.01		
4038	1.20	4078	0.24	14503	0.75	14557	4.85		

Terms: C.W.O. Add VAT to all prices at 8%. Post etc. U.K. 25p + 2p - 27p per order. All orders processed same day. Official Govt. 'Varsity, Poly etc. orders (written or telephoned) welcome.

GREENBANK ELECTRONICS (Dept. WIP)

94 New Chester Road, New Ferry, Wirral, Merseyside
 L62 5AG Tel: 051-645 3391

**TECHNICAL TRAINING IN
 ELECTRONICS TELEVISION
 AND RADIO SERVICING**

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

- City & Guilds Certificates:**
- Telecommunications Technicians
 - Radio, TV, Electronics Technicians
 - Technical Communications
 - Radio Servicing Theory
 - Radio Amateurs
 - Electrical Installation Work
 - MPT Radio Communications Certificate

- Diploma Courses:**
- Colour TV Servicing
 - Electronic Engineering and Maintenance
 - Computer Engineering and Programming
 - Radio, TV, Audio Engineering and Servicing
 - Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

ICS To: International Correspondence Schools

Dept. No. 777C, Intertext House, LONDON
 SW8 4UJ or telephone 622 9911

Subject of Interest.....

Name.....

Address.....

Tel:.....

RETURN OF POST MAIL-ORDER SERVICE

R.C.S. 100 watt MIXER/AMPLIFIER ALL VALVE CHASSIS



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for details Suitable carrying cabinet £14. Price **£85** carr. £2-50

ANOTHER R.C.S. BARGAIN!

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM
This famous unit now available, 10 watts, 8 ohm.
Price **£3.25** Post 40p



8" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance, 10 watts.
Post 40p **£4.45**

10in round **£5.50**.

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12in.
For 12 in. dia. or **£13.50** 95p
10in. speaker. Illustrated

MODEL "B".
For 13 x 5in. or **£7.50** Post 75p
8 in. speaker

R.C.S. ROSEWOOD
SPEAKERS
Size 12in. x 9in. x 5in.
Response 50 to 14,000 cps
8 watts rms 3 or 8 or 16 ohms.
£12 pair Post 75p

LOUDSPEAKER CABINET
WADDING 18in. wide, 20p ft.



GOODMANS CONE TWEETER

3 1/2 in. diam. 18,000 C.P.S. 25 WATTS 8Ω **£3.25**
8 inch woofer 15 watts 28 75.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£5.75**



STEREO VERSION OF ABOVE 27-50.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply 22-95. **£3.95**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leaflet S.A.E. **£4.25** Post 40p



WAFER HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment. Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convectector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p** EACH (FOUR FOR £1.50)
ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £14.95



Post £1
30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£18.95**

Please state 3 or 8 or 15 ohms. Post £1-60

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "25" **£11.95**
12in 30 watt
3, 8 or 15 ohms. Post £1

GROUP "35" **£13.95**
12in 40 watt
3, 8 or 15 ohms. Post £1

GROUP "50/12" **£20.95**

12in 60 watt professional model. 8 ohms or 15 ohms. Post £1-60
With aluminium presence dome.

GROUP "50/15" **£24.95**
15in 75 watt
8 or 15 ohms. Post £1-60



BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER



Professional amplifier using advanced circuit design. Ideal for disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing. Master treble, bass and volume controls. 3 speaker output sockets to suit various combinations of speakers. 4 to 16 ohm. Slave output. A/C mains. Guaranteed. Details S.A.E. 160w SLAVE £60
Latest 50 watt Model **£49** **£68** Carr. £1-00

100 WATT DISCO AMPLIFIER CHASSIS
MADE BY JENNINGS MUSICAL INSTRUMENTS **£52**
4 speaker outputs, vol., treble, bass controls
CANE USED AS 100WATT SLAVE Carr. £1

B.S.R. SINGLE PLAYER DECK
3 speed. Plays all size records. Stereo Cartridge. **£13.50**
Cneing. Ideal Disco Deck Post 75p

QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered fin thick wood cabinet. Size 12 1/2 in x 18 1/2 in x 8 1/2 in. Weight 23lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 8in. Woofer £8-95. Rosewood Version 22 95. Carr. £1 60. Baffle could be cut for larger speaker.

P.W. SOUND TO LIGHT DISPLAY
Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watts each. As featured in Practical Wireless. Price **£12.50**
Cabinet extra £3.

8 inch PHILIPS LOUDSPEAKER
4 ohm. 4 watt. ceramic magnet **£1.95**
General purpose replacement unit.

MAINS TRANSFORMERS Post 50p
6 VOLT 1 AMP. £1.00 3 AMP. £1.40
12 VOLT 300 MA. £1.00 750 MA. £1.30
30 VOLT 5 AMP. AND 54 VOLT 2 AMP C.T. £3.45
20 VOLT 1 AMP. £1.75 1 AMP. £2.00 3 AMP. £2.20
20-0-20 VOLT 1 AMP. £2 30 VOLT 1 1/2 AMP. £1.75
40 VOLT 2 AMP. £2.95. 0-20-40-80 VOLT 1 AMP. £3.60

E.M.I. TAPE MOTOR **£1.85**
4 pole, 240 v. Size 3 1/2 x 2 1/2 in.
1200 rpm. Spindle 1/4 in. dia. motor. 75v version £1.
Post 40p

E.M.I. GRAM MOTOR **£1.25**
240V a.c. 2,400 rpm
2-pole. Size 2 1/2 x 2 1/2 in.
Collaro gram motor 120v. 75p. Post 35p



BAKER DISCO SPEAKERS HIGH QUALITY—BRITISH MADE


2 x 12" CABINETS

for Disco or PA all fitted with carrying handles and corners. Black finish. Other cabinets in stock. SAE For leaflet

**50
WATT
R.M.S.
£50**
Carr. £8

**70
WATT
R.M.S.
£55**
Carr. £8

**100
WATT
R.M.S.
£69**
Carr. £4

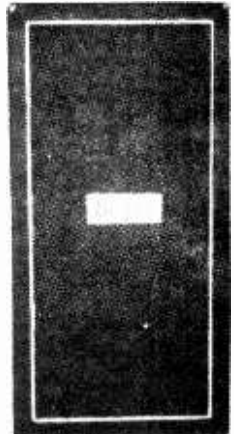

1 x 15" + 1 x 12" 100 WATT CABINET
Size 36" x 24" x 15" **£75.00**. Carr. **£5**
Ideal for Disco, Ogran or PA work.
High quality. Full range.

"SUPERB HI-FI"

12in 25 watts

A high quality loudspeaker. Its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. 25cps
Bass Resonance 16,500 gauss
Flux Density 20-17,000cps
Useful response 8 or 15 ohms models.



£21.95 Post 21-80

"AUDITORIUM"

12in. 35 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques. 35cps
Bass Resonance 15,000 gauss
Flux Density 25-16,000cps
Useful response 8 or 15 ohms models.



£20.95 Post 21-60

"AUDITORIUM"

15in. 45 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi. 35cps
Bass Resonance 15,000 gauss
Useful response 20-14,000cps
8 or 15 ohms models.



£24.95 Post 21-80

Loudspeaker Cabinet Wadding 18in wide. 20p per ft.
Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables, 68p

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON
Open 9—6 Wed. 9—1 Sat. 9—5 (Closed for lunch 1.15—2.30)
Access & Barclay cards welcome. Rail Selhurst. Tel. 01-484 1665

AIRCRAFT H.F. Rx type R4187 & Control box these are a crystal controlled Rx covering 2.8 to 18Mc/s in 3 bands with provision for 24 channels normally remotely controlled the Rx is a dual conversion type using 16 min valves also as BFO, CW & RT IF filters etc. normal O/P for phones. The Rx reqs ext supplies of 24/19v DC or 19/200v DC uses Hc6/u type crystals not supplied, we can now furnish modification details to enable these Rx to tune the 80, 40 & 20 meter bands (or any frequency in range of Rx) also details of power supplies, supplied with copy of mods inc. some parts, handbook for Rx & control box. **£18.30.**

V.H.F. Rx A.M. type R1392 crystal controlled for use in the 100 to 150Mc/s band normally used as ground station Rx, uses 13 valves as BFO, AVC, Tuning meter etc. contained in 19" rack case reqs ext supplies of 250v HT & 6.3v supplied with copy of handbook & mods to make Rx tune over band, supplied complete but store soiled. **£13.**

SLOW MOTION DIALS 3" dia ratio 40:1 scale 0 to 180 with cursor for $\frac{1}{4}$ " shaft **£2.**

TUNING CONDS 3 gang 78pf per section $\frac{1}{4}$ " shaft **£1.30.**

CRYSTALS types 10X & 10XJ in frequency range 2 to 15Mc/s 20 different for **£2.20.**

BLOWER single ended for 240v 50c/s 2,600 RPM.50 CFM, outlet size 2 x $1\frac{1}{2}$ " approx overall size $4\frac{1}{2}$ x $4\frac{1}{2}$ " inc. mtr. very quiet running brushless motor new boxed by Woods **£6.40.**

V.H.F. Power Transis type 2N3375 stud mt 28v 7.5w at 100 Mc/s 3w at 400Mc/s new **£1.80.**

ROTARY SWTS yaxley ceramic 6p 5w 3b or 3p 11w 3b new **£1 ea.** also HD type 6p c/o rated 250v AC 25 amp or 600v 10 amp new **£4.**

POTS high value 10 meg metal case, lin, $2\frac{1}{2}$ x $\frac{1}{4}$ " shaft new **65p.**

AERIAL RODS copper plated $\frac{1}{4}$ " dia 12" long will fit together 10 for **£1.30.**

MIKES stick mike imp 10K dynamic with lead new **£2.30.**

HELIPOTS 50K 10 tr $\frac{1}{4}$ " shaft **£1.30.**

MISC min parts, coils with scr can former 5 x 7mm 10 for **50p.**

RF coupling trans 20 for **60p,** RF chokes 10 x 15mm wire ends 10 for **60p** rotary swts 2p 5w $\frac{1}{4}$ " shaft 2 for **65p.**

TAPE AMP boards with 3 transis & c/o relay single chan with circ **£1.20.**

I.F. trans min type 455/465Kc double wound with sec tap, transistor 3 for **85p.**

TRIMMERS 20pf air spaced 10 for **80p.** 3/10pf min ceramic 5 for **60p** Mullard film trim 18pf 5 for **60p** all new.

SPEAKER unit small horn type for use with m/c RT set new 3 ohm with mt brk **£3.50.**

FILTER UNITS to fit TV set aerial circ fitted coax plug & sk in scr case size $4\frac{1}{2}$ x $1\frac{1}{2}$ x $1\frac{1}{2}$ " new 4 for **£1.40.**

TAPE UNITS with BSR TD.2 deck two chan unit with single O/P complete with valves & circ reqs ext HT & L.T. on base 17 x 13" **£7.50.**

ISOLATING TRANS 230v pria Sec 26v at 13.5 amps with c.t. in carrying case 10 x 7 x 7" fitted ammeter, C core trans new boxed **£17.80.**

TRANSFORMER 230v pria Sec 1200-0-1200 at 700Ma DC or 900v DC 800Ma choke I/P filter size 7 x 7 x 5" new boxed **£10.80.**

METER UNIT X pointer as dual 100Ua meters for use with R1155 Rx **£2.80.**

HEADPHONE LEAD with high to low res matching trans 5ft with $\frac{1}{4}$ " jack plug new **£1.40.**

Above prices include carr/postage & V.A.T. Goods ex equipment unless stated otherwise, S.A.E. for list 17 or enquiry. Shop open Tues to Sat.

A. H. SUPPLIES

122 HANDSWORTH ROAD
SHEFFIELD. S9 4AE. Phone 444278 (0742).



THE

"Manta"

CAPACITIVE DISCHARGE ELECTRONIC IGNITION UNIT

THE NEW, HIGHER RELIABILITY VERSION OF THE P.E. "SCORPIO MK II" IS NOW AVAILABLE IN KIT FORM!!

Our thousands of satisfied customers say:-

More miles per gallon (customers reports give 10%-25% saving—letters available).

An increase in overall performance—your 4 cylinder car feels like a 6 cylinder.

No more cold morning splutters—saves you even more petrol through less use of choke.

The price—a snip at only **£16.50**, fully inclusive of all parts, instructions, postage/packing, and V.A.T. (ready built unit available—**£19.85** fully inclusive).

All parts to high specification, first quality and brand new. Construct this invaluable accessory, following our easy step by step instructions (also available separately, price **30p** post paid). Send for our free interesting six page brochure—"Electronic Ignition—How it Works" (S.A.E. please) to:-

ELECTRO SPARES, DEPT. P.W., 187A SHEFFIELD ROAD, CHESTERFIELD, DERBYSHIRE S41 7JQ—Phone Chesterfield (0246) 36638

WELBROOK STEREO

This new hi-fi amplifier from Welbrook is the result of painstaking design incorporating 5 I.C.'s 22 transistors plus 10 diodes and offers outstanding value for money to the discerning enthusiast.

30W RMS per channel into 8 ohms load. Total harmonic distortion less than 0.1% at all power levels.

Hum/Noise —80db Tape/Tuner
—65db Disc (Magnetic Input)

Complete unit comprising power supply, pre-amplifier with filter networks, two power amplifiers and loudness control all in teak finished cabinet only **£88.00** plus VAT. As above but without filters and loudness control only **£79.00** plus VAT. Also available in module form complete with front panel but without cabinet—easily assembled by the average enthusiast.

Send for details and full price list to:-

Welbrook Engineering & Electronics Ltd., Brooks Street, Hillgate, STOCKPORT SK1 3HT.

Unique full-function 8-digit wrist calculator... available only as a kit.

A wrist calculator is the ultimate in common-sense portable calculating power. Even a pocket calculator goes where your pocket goes – take your jacket off, and you're lost!


But a wrist-calculator is only worth having if it offers a genuinely comprehensive range of functions, with a full-size 8-digit display.

This one does. What's more, because it *is* a kit, supplied *direct* from the manufacturer, it costs only a very reasonable £9.95 (plus 8% VAT, P&P). And for that, you get not only a high-calibre calculator, but the fascination of building it yourself.


How to make 10 keys do the work of 27

The Sinclair Instrument wrist calculator offers the full range of arithmetic functions. It uses normal algebraic logic ('enter it as you write it'). But in addition, it offers a % key; plus the convenience functions \sqrt{x} , $1/x$, x^2 ; plus a full 5-function memory.

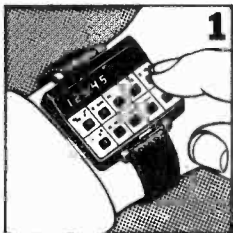All this, from just 10 keys! The secret? An ingenious, simple three-position switch. It works like this.



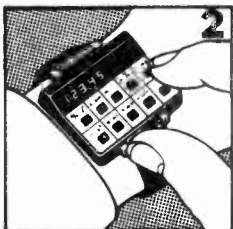
1. The switch in its normal, central position. With the switch centred, numbers – which make up the vast majority of key-strokes – are tapped in the normal way



2. Hold the switch to the left to use the functions to the left above the keys...

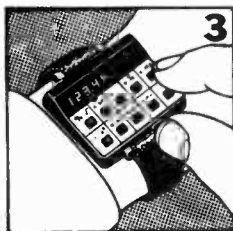3. and hold it to the right to use the functions to the right above the keys.

The display uses 8 full-size red LED digits, and the calculator runs on readily-available hearing-aid batteries to give weeks of normal use.



Assembling the Sinclair Instrument wrist calculator

The wrist calculator kit comes to you complete and ready for assembly. All you need is a reasonable degree of skill with a fine-point soldering iron.

It takes about three hours to assemble. If anything goes wrong, Sinclair Instrument will replace any damaged components *free*: we want you to enjoy assembling the kit, and to end up with a valuable and useful calculator.

Contents

- Case and display window.
- Strap.
- Printed circuit board.
- Switches.
- Special direct-drive chip (no interface chip needed).
- Display.
- Batteries.

Everything is packaged in a neat plastic box, and is accompanied by full instructions.

The only thing you need is a fine-point soldering iron.

All components are fully guaranteed, and any which are damaged during assembly will be replaced free.

The wrist-calculator kit is available only direct from Sinclair Instrument. Take advantage of this 10-day money-back undertaking.

Send the coupon today.

KIT ONLY
£9.95
PLUS VAT, P&P

Sinclair Instrument Ltd,
6 Kings Parade, Cambridge,
Cambs., CB2 1SN.
Tel: Cambridge (0223) 311488.

To: Sinclair Instrument Ltd,
6 Kings Parade, Cambridge, Cambs., CB2 1SN.

* Please send me ... (qty) Sinclair Instrument wrist-calculator kits at £9.95 plus 80p VAT plus 25p P&P (Total £11).

* I enclose cheque/PO/money order for £.....

* Complete as applicable.

Name _____

Address _____

(Please print)

I understand that you will refund my money in full if I return the kit undamaged within 10 days of receipt.

PW/3

SEMI-CONDUCTORS—COMPONENTS

PANEL METERS

4" RANGE

Size 4 1/2" x 3 1/2" x 1 1/2"	
Value No.	Price
0-50UA	1302 £4.50
0-100UA	1303 £4.50
0-500UA	1304 £4.50
0-1MA	1305 £6.00
0-50V	1306 £6.00

2" RANGE

Size 2 1/2" x 1 1/2" x 1 1/2"	
Value No.	Price
0-50UA	1307 £3.50
0-100UA	1308 £3.50
0-500UA	1309 £3.50
0-1MA	1310 £3.50
0-50V	1311 £3.50

MR2P TYPE

Size 4 1/2" x 4 1/2" x 30mm	
Value No.	Price
0-50UA	1313 £4.80
0-1MA	1315 £3.20

EDGEWISE

Size 3 1/2" x 1 1/2" x 2 1/2"	
Cut out 2 1/2" x 1 1/2"	
Value No.	Price
0-1MA	1316 £4.05
0-500UA	1317 £4.05

NEWNES TECHNICAL BOOKS

No. 229 BEGINNERS GUIDE TO ELECTRONICS PRICE £2.25†

No. 230 BEGINNERS GUIDE TO TELEVISION PRICE £2.25†

No. 231 BEGINNERS GUIDE TO TRANSISTORS PRICE £2.25†

No. 233 BEGINNERS GUIDE TO RADIO PRICE £2.25†

No. 234 BEGINNERS GUIDE TO COLOUR TELEVISION PRICE £2.25†

No. 235 ELECTRONIC DIAGRAMS PRICE £1.80†

No. 236 ELECTRONIC COMPONENTS PRICE £1.80†

No. 237 PRINTED CIRCUIT ASSEMBLY PRICE £1.80†

MINIATURE BALANCE/TUNING METER

Size 23 x 22 x 26mm	
Sensitivity 100/0/100MA	
No.	Price
1318	£1.95

BALANCE/TUNING

Size 45 x 22 x 34mm	
Sensitivity 100/0/100UA	
No.	Price
1319	£2.90

MIN. LEVEL METER

Size 23 x 22 x 26mm	
Sensitivity 200UA	
No.	Price
1320	£1.95

VU METER

Size 40 x 40 x 29mm	
Sensitivity 130UA	
No.	Price
1321	£2.90

SUPER UNTESTED PAKS

Pack No.	Qty.	Description	Order No.	Price
U50	100	Germ. Gold bonded OA47 diode	16130	£0.60
U51	150	Germ. OA70/81 diode	16131	£0.60
U52	100	Silicon Diodes 200mA OA200	16132	£0.60
U53	150	diodes 75mA 1M448	16133	£0.60
U54	50	Sil Rect Top Hat 750mA	16134	£0.60
U55	20	Sil Rect Stud Type 3 Amp	16135	£0.60
U56	50	400mV Zeners D07 Case	16136	£0.60
U57	30	NPN Trans BC107/8 Plastic	16137	£0.60
U58	30	PNP Trans BC177/178 Plastic	16138	£0.60
U59	25	NPN T039 2N927/2N1711 sil	16139	£0.60
U60	25	PNP T059 2N2905 silicon	16140	£0.60
U61	30	NPN T018 2N706 silicon	16141	£0.60
U62	25	NPN BFY50/51	16142	£0.60
U63	30	NPN Plastic 2N3906 silicon	16143	£0.60
U64	30	PNP Plastic 2N3905 silicon	16144	£0.60
U65	30	Germ. 0071 PNP	16145	£0.60
U66	15	Plastic Power 2N3055 NPN	16146	£1.20
U67	10	T03 Metal 2N3055 NPN	16147	£1.20
U68	20	Unijunction trans 1L543	16148	£0.60
U69	10	1 amp SCR T039	16149	£1.20
U70	8	3 amp SCR T066 case	16150	£1.20

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

COMPONENT PAKS

C1	200	Resistor mixed value approx. (Count by weight)	16164	*0.60
C2	150	Capacitors mixed value approx. (Count by weight)	16165	*0.60
C3	50	Precision resistors. Mixed values.	16166	0.60
C4	80	1/4W resistors mixed preferred values.	16167	*0.60
C5	5	Pieces assorted ferrite rods.	16168	*0.60
C6	2	Tuning gangs. MW/1W VHF.	16169	*0.60
C7	1	Pack wire 50 meters assorted colours single strand.	16170	0.60
C8	10	Reed switches.	16171	*0.60
C9	3	Micro switches.	16172	*0.60
C10	15	Assorted pots.	16173	*0.60
C11	5	Metal jack sockets 3 x 3.5mm. 2 x standard switch types.	16174	*0.60
C12	30	Paper condensers preferred types mixed values.	16175	*0.60
C13	20	Electrolytics trans. types.	16176	*0.60
C14	1	Pack assorted hardware—Nuts/bolts, gromets etc.	16177	0.60
C15	5	Mains slide switches ass.	16178	*0.60
C16	20	Assorted tag strips and panels.	16179	0.60
C17	15	Assorted control knobs.	16180	*0.60
C18	4	Rotary wave change switches.	16181	*0.60
C19	2	Relays 6-24V operating.	16182	*0.60
C20	1	Pak, copper laminate approx. 200 sq. ins.	16183	0.60
C21	15	Assorted fuses 100mA-5amp.	16184	0.60
C22	50	Metres PVC sleeving assorted size and colour	16185	0.60
C23	60	1/4 watt resistors mixed preferred values.	16188	*0.60
C24	25	Presets assorted type and value.	16186	*0.60
C25	30	Mejres stranded wire assorted colours.	16187	0.60

SLIDER PAKS

S1	6	Slider potentiometers, mixed values.	16190	*0.60
S2	6	Slider potentiometers, all 470	16191	*0.60
S3	6	Slider potentiometers, all 10k 11n.	16192	*0.60
S4	6	Slider potentiometers, all 22k 11n.	16193	*0.60
S5	6	Slider potentiometers, all 47k	16194	*0.60
S6	6	Slider potentiometers, all 47k log.	16195	*0.60

CASSETTES

BI-PAK LOW COST

Order No.	Price
C60	301 £0.36
C90	302 £0.45
C120	303 £0.84

AGFA COLOUR COMPACT

C60	304 £0.68
C90	305 £0.95
C120	306 £1.29

AGFA STEREOCHROME

C60	307 £1.29
C90	308 £1.56
C120	309 £2.22

AGFA S.F.D

C60	310 £0.96
C90	311 £1.23
C120	312 £1.80

T.D.K. S.D.

C60	321 £0.95
C90	322 £1.44
C120	323 £2.04

T.D.K. E.D.

C60	324 £1.48
C90	325 £2.05

T.D.K. SUPER AVILYN

C60	326 £1.53
C90	327 £2.20

Complete in mailing—Box—15 mins. each slide.
Order No. 3193. Price £0.35

MAMMOTH

I.C. PAK

APPROX. 200 PICES

Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices but some unmarked—you to identify. Order No. 16223

OUR SPECIAL PRICE

£1.20*

LINEAR PAKS

Manufacturers "Fall Outs" which include Functional and part Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

U721 30 Assorted Linear Types. 709-741-747-748-750 etc.

ORDER No. 16227 PRICE *£1.50

U765D FM STEREO DECODER

5 I.C.'s 76110 Equ. to MC1310P-MA767.

Data supplied with pak.

ORDER No. 16229 PRICE *£1.50

U76A AUDIO POWER OUTPUT

AMPLIFIERS.

8 Assorted types SL403 76013 76003 etc

Data supplied with pak.

ORDER No. 16228 PRICE *£1.00

74 SERIES PAKS

Manufacturers "Fall Outs" which include Functional and part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

74G 100 Gates assorted 7400-01-04-10-50-60 etc.

ORDER No. 16224 £1.20

74F 50 Flip-Flops assorted 7470-72-73-74-76-104-109 etc.

ORDER No. 16225 £1.20

74M 30 MSI Assorted Types. 7441-47-90-154 etc.

ORDER No. 16226 £1.20

VEROBOARD PAKS

VB1 Approx 30 sq. ins. various sizes, all 1" matrix.

ORDER No. 16199 £0.60

VB2 Approx 30 sq. ins. various sizes, .15" matrix.

ORDER No. 16200 £0.60

BIG VALUE

JUMBO COMPONENT PAKS

Mixed Electronic Components

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs. in weight.

ORDER No. 16221 £1.50 + 85p P&P

C280 CAPACITOR PAKS

75 Mullard C280 capacitors, mixed values ranging from .01uF to 2.2uF complete with identification sheet.

ORDER No. 16204 *£1.20

CABLES

Description	Order No.	Price Per Meter
CP1 Single Microphone	3126	0.07
CP2 Twin Microphone	3127	0.13
CP3 Stereo Screened	3128	0.14
CP4 4 core Screened	3129	0.25
CP5 4 core Individual Screened	3130	0.26
CP6 Single Microphone H/Duty	3131	0.12
CP7 3 core Mains (5 amp)	3132	0.09
CP8 2 core Oval (2.5 amp)	3133	0.08
CP9 2 core Speaker	3134	0.07
CP10 Low-Loss U.H.F.	3135	0.14
CP11 Multicore 8 way	3146	0.25
	15 way	0.40
CP12 Standard VHF Coax	3232	0.10

Just a selection from our huge stocks!

SEE OUR

1977 CATALOGUE

126 pages packed with

valuable information

ORDER NOW ONLY 50p

plus 15p p&p.

WORLD SCOOP!

JUMBO

SEMICONDUCTOR PAK

Transistors—Germ and Silicon Rectifiers - Diodes - Triacs - Thyristors - I.C.'s and Zeners. ALL NEW & CODED. Approx. 100 Pieces. Offering the amateur a fantastic bargain PAK and an enormous saving Identification and data sheet in every pak. Order No. 16222 £2.25

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER

V.A.T.

ADD 12% TO PRICES MARKED*

ADD 8% TO OTHERS EXCEPTING THOSE MARKED†. THESE ARE ZERO

BI-PAK

P.O. BOX 6, WARE, HERTS

SHOP AT 18, BALDOCK ST, WARE, HERTS. OPEN 9 to 5.30 Mon/Sat. Tel: 61593

BI-PAK

PO BOX 6
WARE HERTS

63A HIGH ST., WARE, HERTS

SEMICONDUCTORS

POSTAGE & PACKING
Please add 25p. Overseas
add extra for airmail
Minimum order
£1

2nd

GREAT WINTER SALE!

74 SERIES TTL IC's

Type	Quantity	Type	Quantity	Type	Quantity
1	100	1	100	1	100
£ p	£ p	£ p	£ p	£ p	£ p
7400	0 09 0 08	7448	0 70 0 68	74122	0 45 0 42
7401	0 11 0 10	7450	0 12 0 10	74123	0 65 0 62
7402	0 11 0 10	7451	0 12 0 10	74141	0 68 0 65
7403	0 11 0 10	7453	0 12 0 10	74145	0 75 0 72
7404	0 11 0 10	7454	0 12 0 10	74150	1 10 1 05
7405	0 11 0 10	7460	0 12 0 10	74151	0 65 0 60
7406	0 28 0 25	7470	0 24 0 23	74155	0 70 0 68
7407	0 28 0 25	7472	0 20 0 19	74154	1 20 1 10
7408	0 12 0 11	7473	0 26 0 22	74155	0 70 0 68
7409	0 12 0 11	7474	0 24 0 23	74156	0 70 0 68
7410	0 09 0 08	7475	0 44 0 40	74157	0 70 0 68
7411	0 22 0 20	7476	0 26 0 25	74160	0 95 0 85
7412	0 22 0 20	7480	0 45 0 42	74161	0 95 0 85
7413	0 26 0 25	7481	0 90 0 88	74162	0 95 0 85
7416	0 28 0 25	7482	0 75 0 73	74163	0 95 0 85
7417	0 26 0 25	7483	0 88 0 82	74164	1 20 1 10
7420	0 11 0 10	7484	0 85 0 80	74165	1 20 1 10
7422	0 19 0 18	7485	1 10 1 00	74166	1 20 1 10
7423	0 21 0 20	7486	0 28 0 26	74174	1 10 1 00
7425	0 25 0 23	7489	2 70 2 50	74175	0 85 0 82
7426	0 25 0 23	7490	0 38 0 32	74176	1 10 1 00
7427	0 25 0 23	7491	0 65 0 62	74177	1 10 1 00
7428	0 36 0 34	7492	0 43 0 35	74180	1 10 1 00
7430	0 12 0 10	7493	0 38 0 35	74181	1 90 1 80
7432	0 20 0 19	7494	0 70 0 68	74182	0 80 0 78
7433	0 38 0 36	7495	0 60 0 58	74184	1 50 1 40
7437	0 26 0 25	7496	0 70 0 68	74190	1 40 1 30
7438	0 26 0 25	74100	0 95 0 90	74191	1 40 1 30
7440	0 12 0 10	74104	0 40 0 35	74192	1 10 1 00
7441	0 60 0 57	74105	0 30 0 25	74193	1 05 1 00
7442	0 60 0 52	74107	0 30 0 25	74194	1 05 1 00
7443	0 95 0 90	74110	0 48 0 45	74195	0 80 0 75
7444	0 95 0 90	74111	0 75 0 72	74198	0 90 0 85
7445	0 80 0 75	74118	0 85 0 82	74197	0 90 0 85
7446	0 80 0 75	74119	1 30 1 20	74198	1 90 1 80
7447	0 70 0 68	74121	0 28 0 26	74199	1 80 1 70

Devices may be mixed to qualify for quantity price. Data is available for the above series of I.C.'s in booklet form price 35p.

LINEAR IC'S

TBA 800	*75p
72709 14 pin DIL	*20p
741P 8 pin DIL	*18p
72747 14 pin DIL	*36p
748P 8 pin DIL	*25p
NE 555 Timer	38p
NE 555 Dual Timer	78p

IC SOCKETS

Order No.	Price
BPS8 8 pin	1611 9p
BPS14 14 pin	1612 10p
BPS16 16 pin	1613 11p

TRIACS

Order No.	Price
2A/400 TOS	TR12A/400 50p
10A/400P Plastic	TR110A/400P 80p

ZENER PAKS

400mW PAK No.	
1	Containing 20 3V-10V
2	Containing 20 11V-33V
£1 per PAK*	

DIACS

DR100 15p	D32 15p
-----------	---------

CAPACITOR PAKS

16201 18 Electrolytics	47 µF-10µF
16202 18 Electrolytics	10 µF-100µF
16203 18 Electrolytics	100µF-680µF

BUY ONE OF EACH
Special Price £1.20* the 3

16160 24 Ceramic Caps	22 pf-82pf
16161 24 Ceramic Caps	100pf-390pf
16162 24 Ceramic Caps	470pf-3300pf
16163 21 Ceramic Caps	4700pf-0.047µF

BUY ONE OF EACH
Special Price £1.60* the 4

RESISTOR PAKS


16213 1/8th	100ohm-820ohm
16214 1/8th	1K-8.2K
16215 1/8th	10K-8.2K
16216 1/8th	100K-1M

BUY ONE OF EACH
Special Price £1.60* the 4

AC 128	10p	OC 44	12p
AC 153K	18p	OC 45	12p
AC 176	19p	OC 71	9p
AC 176K	22p	OC 72	14p
AC 187K	22p	OC 81	14p
AC 188	12p	ZTX 107	*6p
AC 188K	22p	ZTX 108	*6p
BC 107	6p	ZTX 109	*6p
BC 108	6p	ZTX 300	*7p
BC 109	6p	ZTX 301	*7p
BC 118	*10p	ZTX 302	*9p
BC 154	*16p	ZTX 500	*8p
BC 147	*8p	ZTX 501	*10p
BC 148	*8p	ZTX 502	*12p
BC 149	*8p	2N 896	10p
BC 157	*10p	2N 697	11p
BC 158	*10p	2N 706	8p
BC 159	*10p	2N 706A	8p
BC 169C	*10p	2N 708	8p
BC 170	*6p	2N 1613	15p
BC 171	*6p	2N 1711	15p
BC 172	*6p	2N 1893	18p
BC 177	12p	2N 2217	18p
BC 178	12p	2N 2218	15p
BC 179	12p	2N 2218A	18p
BC 182L & K	*9p	2N 2219	15p
BC 183	*9p	2N 2219A	18p
BC 184	*9p	2N 2221	16p
BC 212L & K	*10p	2N 2221A	16p
BC 213	*10p	2N 2222	15p
BC 214	*10p	2N 2222A	16p
BC 251	*6p	2N 2369	12p
BC 327	*12p	2N 2369A	12p
BC 328	*12p	2N 2904	14p
BC 337	*11p	2N 2904A	15p
BC 338	*11p	2N 2905	14p
BF 115	10p	2N 2905A	15p
BF 167	10p	2N 2906	12p
BF 173	10p	2N 2906A	14p
BF 194	*9p	2N 2907	12p
BF 195	*9p	2N 2907A	13p
BF 196	*12p	2N 2926G	*8p
BF 197	*12p	2N 2926Y	*7p
BF 198	*12p	2N 3053	14p
BF 199	*12p	2N 3055	38p
BF 257	26p	2N 3702	*7p
BF 258	29p	2N 3703	*7p
BF 259	34p	2N 3704	*6p
BFX 29	18p	2N 3705	*6p
BFX 84	15p	2N 3706	*7p
BFX 85	20p	2N 3903	*11p
BFX 86	20p	2N 3904	*11p
BFY 50	12p	2N 3905	*11p
BFY 51	12p	2N 3906	*11p
BFY 52	12p	2N 5172	*9p
BFY 53	12p		

D.I.Y. PRINTED CIRCUIT KIT

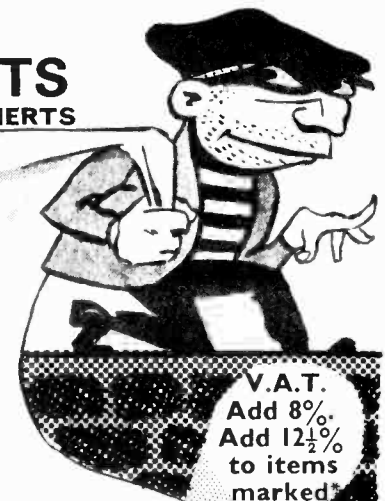NORMAL PRICE £7.80
CONTAINS 6 Pieces copper laminate, box of etchant powder and measure, tweezers, marker pen, high quality pump drill, Stanley knife & blades, 6 inch metal rule. FULL Easy to follow instructions.
SALE PRICE £5.50



V.A.T.
Add 8%
Add 12½%
to items marked

DIODES

OA 47	5p	IN4005	6p
OA 81	5p	IN4006	7p
OA 85	6p	IN4007	8p
OA 91	5p	IN5400	11p
OA 200/BAX 13	5p	IN5401	12p
OA 202/BAX 16	5p	IN5402	13p
IN914	4p	IN5403	14p
IN4148	4p	IN5404	15p
ZTX 501	3p	IN5405	16p
IN4002	4p	IN5406	17p
IN4003	5p	IN5407	18p
IN4004	6p	IN5408	20p

VOLTAGE REGS

MVR 7805	85p
MVR 7812	85p
MVR 7815	85p

OPTOELECTRONICS

L.E.D. Displays	Order No.	Price
DL 707 0-3"	1510	70p
DL 747 0-6"	1511	1 50

L.E.D.'s	Order No.	Price
TIL 209 Red .125"	1501	1501
FLV 117 Red .2"	1504	1504

Photo Devices	Order No.	Price
ORP 12	1515	38p
OCF 71	1520	5 for £1.00

THYRISTORS

TOS	Order No.	Price
IA/50 PIV	THY 1A/50	18p
1A/400 PIV	THY 1A/400	32p
1A/600 PIV	THY 1A/600	38p
TO66		
5A/50 PIV	THY 5A/50	25p
5A/400 PIV	THY 5A/400	40p
5A/600 PIV	THY 5A/600	50p
TO48		
16A/50 PIV	THY 16A/50	40p
16A/400 PIV	THY 16A/400	60p

UNIUNION

UT46/TIS 43	18p
-------------	-----

F.E.T.

2N3819	15p
--------	-----

ORDERING

Please word your orders exactly as printed not forgetting to include our part number.



LEND A HAND

It may be supposed that the great majority of our readers are reasonably sound in wind and limb and able to move around, more or less freely, under their own steam. They can look at a project in the magazine, decide to make it and then jump into their car, or take a bus, and go and get the parts that they need. If they are very lucky and don't live in London or one of the other big cities then they can pop down to the local postbox and send off their order to one of our advertisers.

Having just received the latest copy of *Radial*, the magazine of the Radio Amateur Invalid and Bedfast Club, I am reminded that there are those among us who are not quite so fortunate. Some who are very enthusiastic licensed radio amateurs or listeners but who are handicapped in one way or another and must rely upon others to set up and maintain their gear and aeriels. But can you imagine the joy that these people derive from being able to communicate with or listen to other amateurs from all over the world?

The Club is very active and prospering under the Presidency of Bill Browning G2AOX and his committee but it must be remembered that it is the ordinary healthy member who is so important and on whom so much depends. One such recent recruit was Ken Alford G2DX (what a fabulous call!) who at 83 feels he ought to be helping the youngsters, no doubt!

How many of our readers have bits of equipment or, in particular, short wave receivers, knocking about in the attic or garden shed that could be put into good working order and handed over to the RAIBC without a great deal of trouble? Many, for sure. So even if you don't want to join the Club you can still help in a very practical way those who are generally unable to help themselves.

If you do help you will certainly feel a little glow of satisfaction after having done your bit and may even be tempted to carry on the good work. It might even mean a couple of hours less spent working the DX from your own rig but it will be worth while. After all, conditions aren't so good all the time! If you feel that you want to become involved write in the first instance to RAIBC Secretary Harry Boutle G2CLP of 14 Queen's Drive, Bedford and he'll put you on to the right track. Now, where's that loft ladder?

If you'd like to hear the RAIBC boys on the air try 3750kHz SSB at 1000 on Tuesdays or 1400 on Wednesdays when the Net controller is G3WJT or perhaps the Cheshire Homes Net around 3650 to 3700kHz SSB at 1330 on Thursdays when the MC is G3OPY.

Member Tony G4BPX summed it up very well, in an article in *Radial*, when he said 'In thinking with and for less able friends for over twenty years I have become less handicapped myself' Think about it!

Eric Dowdeswell—Assistant Editor

This issue contains the first of the free PW Info-Cards, on Resistors and Capacitors, see page 938. The second Info-Card will be given away with the May issue of PW and will deal with Semiconductors.

DON'T MISS IT!

NEWS...

Polling time

THE International Short-Wave Club is now holding the tenth in its series of official polls which have been held every three years since 1950 to determine, in the listeners opinion the most popular short-wave Broadcasting stations. The poll began on November 1st, 1976 and will continue until February 28th, 1977. In order to enter, write on a postcard your five favourite Short-Wave stations, in order of preference, and add in not more than 30 words, the reasons for your first choice.

Results will be published in the April issue of the ISWC and announced by many stations. Further information from Mr G. C. Gibbs, 118 Bournemouth Park Road, Southend-on-Sea, Essex, SS2 5LS. Please enclose an SAE with all correspondence.

New licence explained

FROM January 1, 1977, the Home Office has been issuing four new types of radio amateur licence which have replaced all existing amateur licences when they become due for renewal.

The new Amateur Licence A (full facilities) and B (having certain limitations) will include all those facilities available to holders of the existing Amateur (Sound) Licences A or B, and will also include operation from a vehicle, or vessel other than at sea, or as a pedestrian. Fascimile, amateur television, slow scan television, data on amateur bands 144-146 MHz and above, as well as double sideband suppressed carrier operation will also be included. Emergency County Planning Officers will also be added to the categories able to call upon Raynet (emergency communications).

The purposes of the new-style licences are:

- (1) to give more flexibility to

NEWS...

NEWS...

NEWS...

British radio amateurs, so that they may pursue their hobby without having to make special application for several of the above facilities at present needing separate licences or authorities.

(2) to enable the Home Office to deal with the increase in applications for amateur licences and regulatory work over the next few years with the minimum delay.

Existing facilities authorised by a total of 20 licences and special authorities will thus be contained (with a few exceptions) in the new Amateur Licence A or B; and for Aliens combined fixed and mobile facilities in the Amateur Licence C or D. The new fee for all UK amateur licences will be £5.50.

Catkin, Red E, Trigratrons . . . !

AT a recent meeting of the University College of North Wales ARS John Lawrence, GW3JGA, gave a talk on the "Development of the Radio Valve" and showed part of his collection of historic radio valves. On display were over 200 valves covering the 60 year period from 1915 to 1975.



Practical Wireless, March 1977

The pre-war range included an "R" triode, AOR triodes, early indirectly-heated valves, screen grid types, "Catkin", Mullard "Red E" and Mazda octal versions. The wartime range included klystrons, trigatrons, magnetrons (including a MAG1) and a range of unusual disc-seal triodes which were used in early radio-location equipment. The wartime and post-war types included many transmitting valves, one of the latest vapour cooled triodes on show being rated at 60kW CW output.

Smaller types such as acorns, deaf-aid valves and Nuvisitors were also included. In addition to valves a number of opto-electrical devices, photo-cells, camera and convertor tubes were on display. To give a cheery atmosphere to the meeting, two large VT31 tetrodes were set up with their directly-heated filaments glowing brightly (filament rating 10V 10A).

Navy days

ACTIVITY period from HMS *Belfast*, in the Pool of London, 8th to 17th April. Call sign will be GB3RN.

Mobile Rally at HMS *Mercury*, nr. Petersfield, Hants. Sunday, 19th June.

Navy Days at Portsmouth and

Plymouth dockyards, 27th, 28th and 29th August. GB3RN and GB3GUZ.

Jamboree-on-the-Air Camp and Radio Teach-In at HMS *Mercury*, 15th and 16th October.

Annual General Meeting at HMS *Mercury*, nr. Petersfield, Hants, 22nd October.

For further details or membership details of the RNARS write to M. J. Matthews, G3JFF, Hon. Secretary, HMS *Mercury*, East Meon, Petersfield, Hants.

Spring show

A SHORT note here for those readers who attend, or would like to attend the All-Electronics Show which is held annually. This year's show promises to be as successful as those in the past, and will be held at Grosvenor House, Park Lane, London W1 on the 19th-21st April. Watch this page in the coming months for more news on this exhibition.

Teach-in

THE Department of Electrical Engineering Science at Essex University will be holding its annual Electronics Summer School for teachers during the week July 11-15, 1977. Two courses will be run simultaneously. The Linear Circuit Design course is concerned with the use of transistors and operational amplifiers in analogue applications and the basic circuits of a HiFi amplifier will be investigated in detail. The Digital Circuit Design course concentrates on the use of the transistor as a switch and develops design using integrated logic circuits.

Further information from: R J. Mack, Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester CO4 3SQ, telephone Colchester (0206) 44144, extension 2408 or 2299.

Circuits for AUDIO AMPLIFIERS

PART 1

F.G.RAYER G30GR

THE circuits in this series are intended to give practical essential information for the construction of pre-amplifiers, mixers, tone-controls, low-level and Class A output stages as well as various types of push-pull output stages and IC audio amplifiers. Some circuits can be added to existing equipment, or require few components and can be constructed as separate units. Others are more ambitious.



The simpler circuits can be assembled on tag-board but for the larger circuits Veroboard can be used, or printed circuit boards can be prepared. Copper-clad board and the other necessary materials for this purpose are readily obtainable. Numerous cases and cabinets suitable for housing the finished equipment are available and they can include space to accommodate the battery or AC power pack, as appropriate. Input and output sockets and controls can be mounted on the case panel, as well as brackets to carry the circuit board.

The circuits here employ both negative and positive "earth" or chassis line. This will prove to be convenient when new equipment has to suit existing units. Some circuits are readily adapted for either negative or positive earth though, in general, the positive earth is more likely to be found with older amplifiers employing PNP transistors.


LOW-LEVEL "CLASS A" STAGE

A Class A stage is one which is required to amplify the whole audio cycle. The output from the stage should be as faithful a copy of the input as possible, unless some deliberate frequency correction has been made. A pre-amplifier or early audio stage should introduce as little noise as possible, as this would be amplified by later stages. Typical Class A low-level stages include pre-amplifiers and the early stages of an amplifier.

Fig. 1 is a simple low-level Class A stage. Resistor R1 furnishes base bias and the NPN transistor is

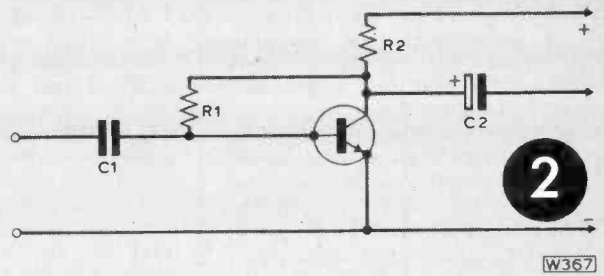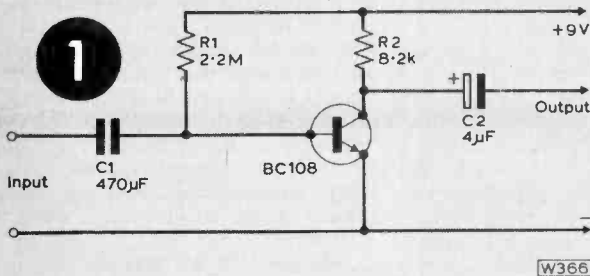


used as a grounded emitter amplifier. This particular circuit can be used by itself or in simple equipment, but lacks any form of stabilisation. As a result, collector current and operating conditions could vary considerably due to spreads in transistor characteristics, changes in temperature or variations in voltages. It is thus necessary with this circuit to limit base and collector currents to low levels. This circuit can be modified by taking R1 to the collector, Fig. 2. This provides a useful degree of stabilisation since base current through R1 depends on collector voltage, as well as on the value of R1. Component values may be as in Fig. 1.

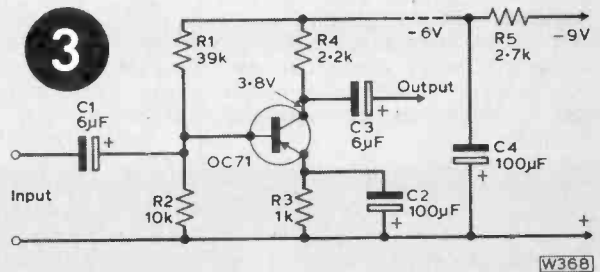

The circuit of Fig. 3, which has a positive earth line, is stabilised. Resistors R1 and R2 form a potential divider setting the base operating point. R3 is the emitter bias resistor and R4 the collector load. With the PNP transistor, the base will be slightly negative, relative to the emitter. Should transistor spread, supply voltage or a rise in temperature cause collector current to be unusually high, the voltage drop across R3 rises due to the increased emitter current. The emitter moves negative, so that the base is relatively less negative with respect to the emitter than before, thus reducing collector current.

Should conditions result in an unusually low collector current, the reverse happens. The voltage

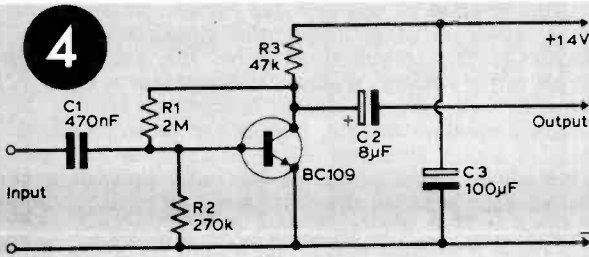drop across R3 is reduced. The emitter thus moves positive, so that the base is relatively more positive and this tends to maintain collector current. In this way stable, satisfactory working conditions are maintained.




W369

Fig. 4 is another low-level amplifier, using a low-noise NPN transistor and it may be used to boost low-level inputs. The 14V supply line is not essential and R3 may be reduced in value with lower voltages, good results being obtained with 6V or less if necessary.

TONE CONTROLS

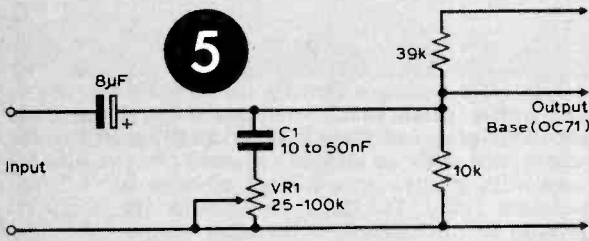
Tone controls may curtail or emphasise treble or bass, according to the circuits used, and are employed to obtain more satisfactory tonal balance or to compensate for recording characteristics, speaker deficiencies or other factors.




W370

Fig. 5 is a simple top-cut control, treble response being curtailed as the value of VR1 is reduced. The values shown are not critical. Such tone controls should not be added to a stage over which negative feedback takes place but to an early stage outside the feedback loop.

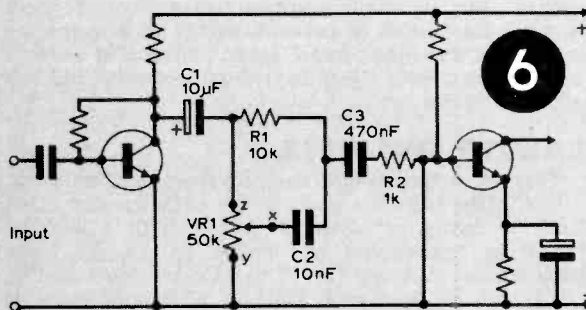The reactance of a capacitor falls as frequency rises. In Fig. 5 C1 has a lower reactance to high frequencies, so that their amplitude is reduced at the transistor base. This change of capacitor reactance



W371

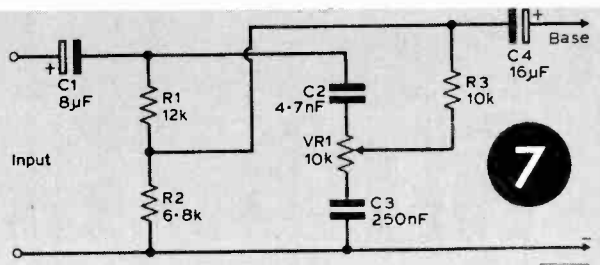


W372

with frequency is generally used in tone control circuits. Cutting treble and turning up the amplifier gain effectively increases the bass frequencies.

Fig. 6 is a circuit in which the potentiometer VR1 allows top frequencies to be cut when slider X is moved towards Y (similar to Fig. 5). However, when X is moved towards Z, C2 is increasingly effective across R1, to lift treble response. These and similar circuits can often be placed in existing equipment. Base, emitter and collector resistors are as for the stage without tone control.

Fig. 7 is another tone control for an early stage. R1 and R2 form an audio potential divider for C4 and the base of the following stage. VR1 provides best bass reproduction when adjusted towards C3 and best treble response when towards C2. Fig. 8 also controls bass and treble but has individual potentiometers. It can be fitted before the first stage if required. VR1 is the bass control and VR2 is for treble. VR3 is the volume control. This is a purely

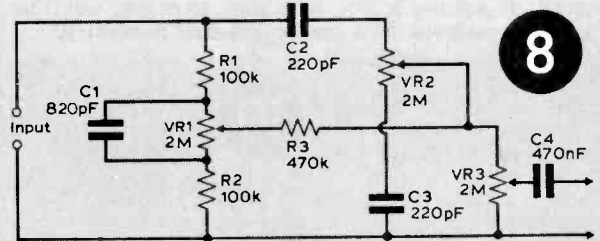

W373


passive circuit which may be assembled in a metal screening box and requires no battery.

Circuits such as these can often be added to existing amplifiers without difficulty as they do not upset the DC working conditions. Some extra gain may be needed to compensate for losses in the tone control circuit when this does not incorporate a transistor. All values can be considerably modified, though there is no point in providing extremes of bass or treble which will never be wanted.

PRE-AMP WITH TONE CONTROL

Fig. 9 is a circuit of a pre-amplifier which incorporates two variable tone controls, VR1 is for treble cut and VR2 for bass cut. A volume control may be incorporated between VR1 and the input circuit, if required. Such a stage is useful when the main amplifier lacks sufficient gain for some particular purpose. This circuit also allows tone controls to be provided as well, with no changes to the main amplifier. If a pre-amplifier is operated from its own battery, no difficulties of hum or coupling through the power supply can arise.

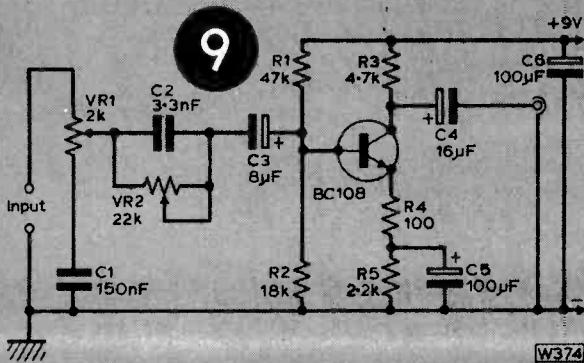When operation is required from the same supply as the main amplifier, a decoupling resistor is added



in the positive supply line, between C6 and the supply circuit. As most amplifiers will be operated from the mains these components (resistor and C6) also help to assure a smooth, hum-free supply for this stage.

A pre-amplifier can have circuits designed for various inputs such as for radio, or for moving-coil or crystal microphones. These may be selected by switching.

INPUT IMPEDANCE

Tuners, crystal pick-ups and other inputs are best operated into loads of a particular impedance. This is not too critical for general purposes but becomes important for improved fidelity. A suitable impedance is frequently obtained with a resistor network. It causes a loss in signal strength, but this is easily restored by a pre-amplifier, if necessary.

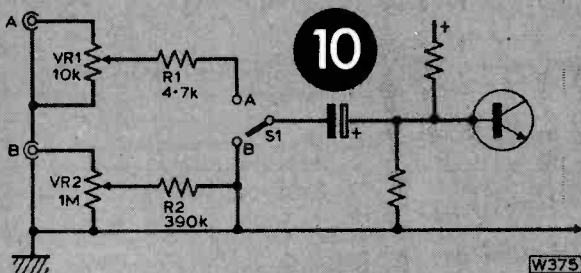


Fig. 10 is a circuit having two inputs, "A" is of relatively low impedance for a radio tuner, pre-amplifier and other inputs of around 10kΩ impedance. Input "B" is more suitable for a crystal pick-up and other high impedance inputs, where a low impedance would reduce frequency response. Individual volume controls VR1 and VR2 can be set to suit the signal levels provided.

INPUT LEADS

The microphone, pick-up or other input leads to the pre-amplifier and amplifier must be screened. So must the inter-connecting audio circuit leads from pre-amplifier, tuner or other units to the main amplifier. The purpose of such screening is to avoid pick-up of hum or other currents induced from adjacent circuits, which, if introduced into the input circuit would be amplified and accompany the signal or cause instability.

The screened leads are fitted with jack plugs or other audio-type connectors to match the equipment.

The outer conductors of the leads form the earthed or chassis return, but should not be used to carry power between units.

"CLASS A" OUTPUT

The addition of one or more further stages to the first, low-level stage raises the signal level, eventually to that required to drive the loudspeaker. With a dry battery, a single transistor as a Class A amplifier can provide ample headphone volume, or modest speaker volume, mainly for personal listening. A single transistor Class A amplifier can give very much higher power in car radio equipment or in mains-operated circuits where current is not limited to that available from dry batteries. Powerful Class A circuits require an output transistor able to handle a high current and the current drain is greater than with an equivalent power Class B output stage (described later). For this reason large Class A stages are not used in battery operated receivers or amplifiers.

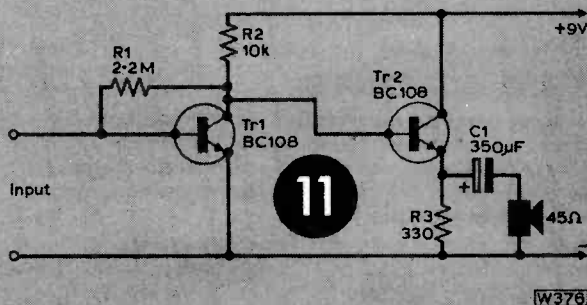


Fig. 11 is a simple directly coupled 2-stage amplifier with a small Class A output stage. It provides excellent gain and gives a surprisingly good volume when used with an efficient speaker. It can also be used with phones or a midget speaker for a small personal radio. The input is suitable for a crystal pick-up or microphone. With other inputs, an isolating capacitor will be necessary in the input circuit so that bias conditions (via R1) for Tr1 are not upset.

Tr2 is an emitter follower, with grounded collector. The collector is earthed as far as audio signals are concerned, as the battery supply is considered to have zero impedance. DC operating conditions for Tr2 are not upset by the speaker resistance as C1 isolates the speaker, but results are best if the speaker is of moderately high impedance.

When a Class A stage is operating properly, a milliammeter placed in the supply circuit should show no significant change of current with varying signals. But in small amplifiers like Fig. 11 there is some fluctuation of current, except at low volume levels. On the other hand, large changes in current are expected with Class B push-pull circuits and are quite in order.

LARGER OUTPUTS


Class A output stages running from accumulators, about 12 to 14V, are popular for vehicles and often have a rating of about 2 to 5W with a current drain in the region of 400mA to 1A. A large power Class A stage for 12 to 14V is shown in Fig. 12. It can be used with PNP or NPN transistors of the OC26 or BD121 type with appropriate polarity

continued on page 927

**SPECIAL
PRODUCT
REPORT**

HEATHKIT

**HW8
QRP**

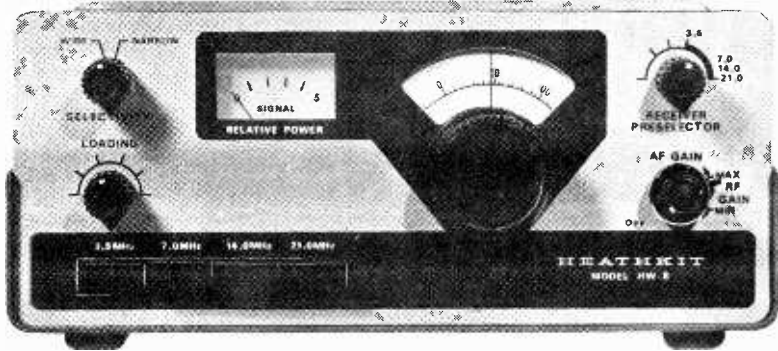

TRANSCEIVER

Many thousands of radio amateurs were introduced to the thrills of operating with low power CW when Heathkit thought up the earlier HW7 transceiver. However that did not have the 80 metre band available, a sad omission in these days of low sunspot activity. There was no gain control on the RF side and there was separate dial calibration for each of the three bands. On the credit side, it was possible to plug in a crystal for fixed frequency operation, a facility lacking on the HW8.

But what is 'low power'? In the USA, 100W or so is spoken of as low power, which it probably is when one considers their maximum licensed power. I prefer to go along with our ideas over here, which is something below 10W input, although there are many enthusiasts who use, and get good results from, a few hundred milliwatts.

DESCRIPTION


The HW8 transceiver is designed to work from a nominal 12VDC supply, in practice from a car battery if in the field or from a mains unit if at home or in a hotel on vacation. In

either case the actual input voltage will be nearer to 13-14V. On transmit the HW8 provides an input of around 3W on CW on the bottom 250kHz portion of the 3.5, 7, 14 and 21MHz bands. The output impedance is fixed at 50Ω with an output loading control on the front panel, coupled with a relative output meter. The receiver uses the direct conversion technique, as did the HW7, and as well as having an RF stage it has a switchable two-stage active filter giving audio bandwidths of 375 and 750Hz (6dB) at 750Hz. In use this means that SSB is just about uncopiable which is rather a pity, although only CW can be transmitted. The two modes are far from incompatible.

THE CIRCUIT

On both receive and transmit the VFO output (8-645 to 8-895MHz) is mixed with the output of an RF oscillator which provides four crystal controlled frequencies, 12-395, 15-895,

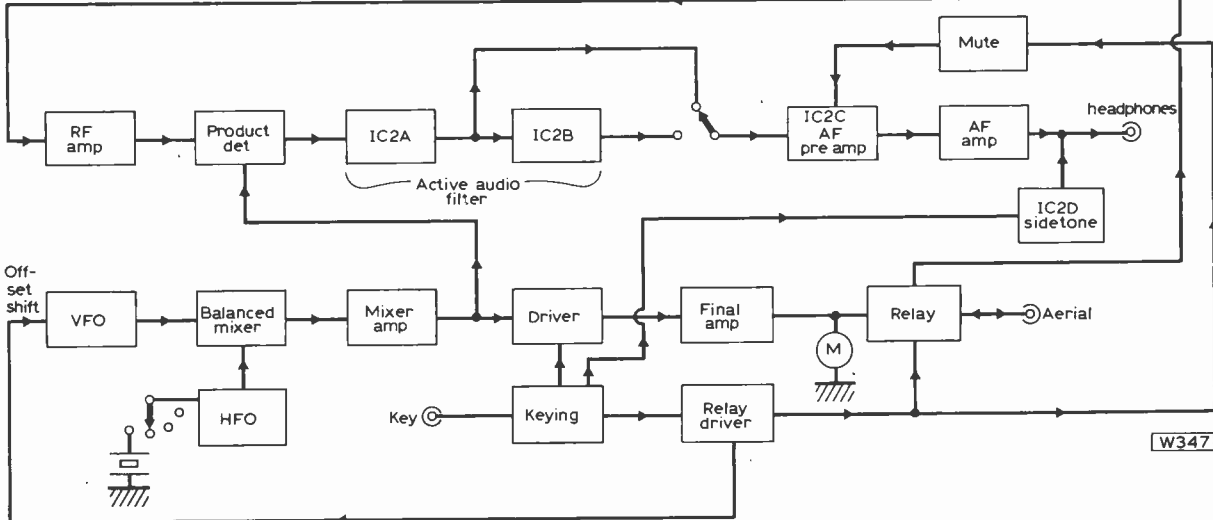This block diagram shows how several of the stages of the HW8 are used on both transmit and receive.



abridged specification

TRANSMITTER	RECEIVER
DC Input 80m 3·5W 40m 3·0W 20m 3·0W 15m 2·5W	Direct conversion, CW only Sensitivity 1 μ V with 0·2 μ V providing readable signal Selectivity Wide:—750Hz @ 6dB down. Narrow:—375Hz @ 6dB down. Passband Freq. 750Hz
Output Impedance 50 Ω unbalanced	Output Imp. 1k Ω
Transmit Offset 750Hz lower	
GENERAL	
Frequency Range MHz 3·5 to 3·750, 7·0 to 7·250 14·0 to 14·250, 21·0 to 21·250	
Frequency Stability	Less than 150Hz/hour after 1 hour
Power Required	13·4VDC nominal 90mA/ receive 430mA/transmit
Dimensions	9 $\frac{1}{2}$ x 4 $\frac{1}{2}$ x 8 $\frac{1}{2}$ in. deep overall. (235 x 108 x 216mm)
Weight	4lbs. (1·8kg)

22·895 and 29·895MHz. The difference frequency is selected for each band by tuned circuits, thus giving 3·5 to 3·750, 7·0 to 7·250, 14·0 to 14·250 and 21·0 to 21·250MHz. The dial calibration of 0 to 250 is thus constant for each band. These frequencies are also used as the heterodyne frequencies for the direct conversion receiver.

This is a good point at which to say that there are 20 tuned circuits plus the four crystals all of which are diode switched! The band switch thus operates at DC rather than at RF, except for the PA tuned circuits. It is not surprising then that the main PCB carries some 300 or so components!

There are 32 coils, 37 diodes, 92 resistors, 120 capacitors and 16 transistors/IC's. Whether all this sophistication is justified to provide a couple of watts of CW on four bands is a matter of opinion!

On transmit the output of the mixer is amplified and fed to a tuned driver stage into the 2N4427 power amplifier. This stage is protected against excessive SWR conditions or accidental no-load dangers. Keying takes place in the driver stage, also activating the transmit/receive relay, the keying sidetone and the receiver muting circuits. There is an adjustable drop-out time control on the T/R relay.


The receiver has an RF stage with the simplest of gain controls, which many amateurs, who complain of cross-modulation on their sets, would do well to copy. Namely, a potentiometer across the input terminals! An MC1496G IC forms the balanced product detector, also fed with a signal from the mixer stage, as previously mentioned. The active audio filter stages have also been covered earlier. Because of the 750Hz peaking effect of the audio filters the carrier has to be offset 750Hz on transmit. This is done automatically when the key is down. In practice this means tuning down from the HF end of a band and tuning a signal right 'on the nose' of the filter giving a 750Hz beat note. The transmitted signal will then be spot on the frequency of the incoming signal.

Two further stages of audio amplification feed a head-phone socket at high impedance, nominally 1k Ω , but in practice a stereo low impedance headset performed quite well! But an old pair of Browns diaphragm type of 4k Ω really got the signals pumping out when peaked on the filter frequency!

CONSTRUCTION

As with any kit the components supplied must be checked against the parts list. Every part, down to the nuts and bolts, is illustrated in the Heathkit manual which is an education in itself and even before construction begins a good knowledge of the HW8 is obtained. Personally, I always read the manual right through anyway, before ever lifting the soldering iron! It is time well spent, often explaining points that might otherwise prove mystifying during construction.

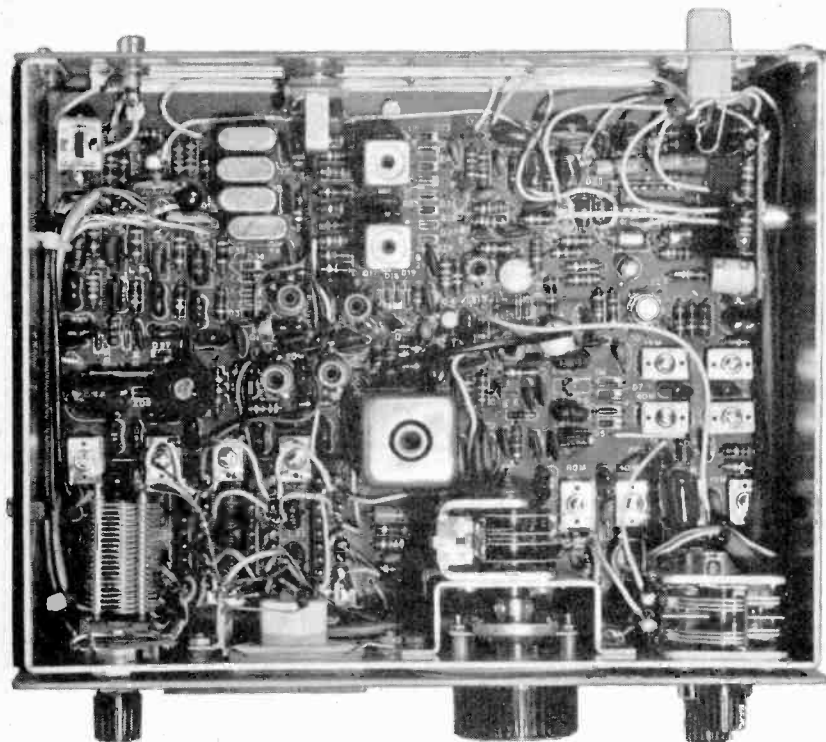The bulk of the work is on the main PCB which carries no



Top view of the finished transceiver. All the cabling round the inside of the cabinet is fitted to the PCB before the cabinet is assembled round the board. The T/R relay is in the top left hand corner close to the aerial socket, with the four HF crystals further to the right. The large screened can in the centre is the VFO unit with the VFO tuning immediately in front on the panel. While the PCB may appear rather cluttered up, the wiring in of the components presented no difficulty at all. There are no components under the PCB which is in the bottom of the cabinet.

less than 308 components! Actually the job of wiring so many resistors and diodes etc. gets boring so give it a break now and again to avoid making errors. The PCB and the associated cabling took nine hours to complete. It is an excellent board on which to work and need not be any cause for apprehension for potential constructors. The PCB was carefully checked for solder 'bridges' with the aid of a watchmaker's eyeglass and all was well.

The simple cabinet, front and rear panels are fitted round the PCB and the wiring completed to the various controls on the front and sockets on the rear panel. The aerial socket is a 'phono' type easily changed to Belling-Lee type or to suit the rest of the station's RF cabling. After completing the PCB a further 5½ hours work saw the transceiver completed. A further check on the PCB underneath and the general wiring was made before tests began.

TESTING

Although the manual did not mention it, it was thought advisable to check the resistance across the 12V input terminals just in case there was a short there! The multimeter red prod (neg polarity) was connected to negative input, giving a reading of 550Ω with the transceiver switched on and on receive. The power unit used for testing was the Heathkit HWA-7-1 giving approx. 13.2V. The initial tests laid down in the manual all proved satisfactory. The relay worked on keying, the sidetone was present and the receiver controls worked but little RF output was present at this stage.

The test equipment required is a receiver, preferably of the communication type, capable of providing accurate checks at 7 and 7.250kHz for checking the VFO, and a high input impedance voltmeter preferably with an RF probe. The alignment is quite clearly described and it is a matter of logical progression which can be completed easily in half an hour.

If one runs into trouble there is plenty of advice in the manual including PCB layout drawings with the voltages to be expected at various points. With a stabilised input voltage of 13VDC the current on receive was 93mA and on transmit 450mA, remaining fairly constant over the four bands. The RF output was measured at the dummy aerial load with the dial set at mid position and the loading control peaked and was found to be 2W on 80m and 40m, 1.8W on 20m and 1.6W on 15m.

Since the accepted segments of the bands on CW are a lot less than the 250kHz coverage available on the HW8 it would seem feasible to align the circuits at, say, 50kHz from the band edge and improve the general performance on both transmit and receive. In practice with the recommended alignment the RF output is remarkably constant over the whole 250kHz.

GENERAL COMMENTS

The transmitted signal was monitored externally on all four bands and found to be clean with excellent keying characteristics. In fact it was possible to get the relay to follow keying up to about 25wpm although some may prefer to increase the relay drop-out time to a second or so. Plenty of DX has been heard on all four bands and the two position audio filter can really sort out the weak ones among the QRM. The RF gain control was most effective especially with some of the powerful signals on 80m.

AERIALS


Nothing spectacular has been worked on any band yet due to lack of suitable aerials. It is a problem to get a four band aerial which provides a low impedance feed on all bands, without using a tuning unit. Anything introduced between the aerial and the set is going to absorb some of the precious power. A trapped dipole is the quick answer but it is a compromise and rather 'lossy'. It is hoped to erect a four band ground plane with a coax feeder when a further report on results obtained will be published.

AED
Heathkit k/HW8 Price £108.19 inc. VAT and post and packing from Heath (Gloucester) Ltd., Gloucester GL2 6EE.

CIRCUITS FOR AUDIO AMPS.—contd. from page 924

of supply, that is positive earth for PNP and negative earth for NPN devices. It can be driven by an AC128 (PNP), BC108 (NPN) or similar stage. The transformer ratios are typical and need not be exactly as shown.

Collector current is set by VR1 and this can be the lowest which gives satisfactory performance. Begin with VR1 at maximum value, corresponding to a low collector current. Actual collector current depends on the transistor and performance and should be around 350mA to 900mA. As the DC operating conditions of this stage are isolated from other stages it is useful for experimental circuits and can actually be employed with about 9V to 24V. With the higher voltages, check carefully that the transistor is not over-run.

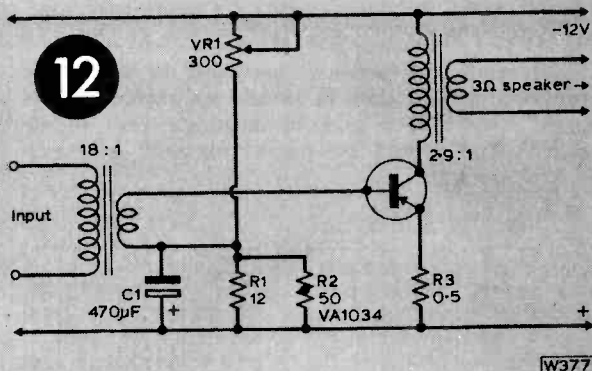

The load impedance can be around 25Ω but it is not too critical, depending somewhat on the supply voltage. Note that with a Class A stage a loudspeaker can only be connected directly to the collector circuit when it is able to carry the required collector current. This is why a transformer is necessary in Fig. 12.

Thermistor R2 is for stabilisation, as described later, whilst R3 also assists in this direction and can be about 1Ω if the volume is sufficient. Resistor R2 may be omitted for low voltages, or providing a check is kept that the current is not too high.

TO BE CONTINUED

AVAILABLE NOW!

REPRINT OF PW'S

TELE-TENNIS SERIES

July-November 74

Send 75p + 10p (post & packing) to: Chief Cashier
(PW Tele-Tennis), IPC Magazines, King's Reach
Tower, Stamford St., London, SE1 9LS

PW 'Easybuild'

WIDE-WRITER

PART 8

M. J. HUGHES M.A., C. Eng. MIERE

NON-KEYBOARD KEYING

Early on in the series we promised an alternative means of entering data to obviate an expensive keyboard. This is done with seven single pole toggle switches and a push-to-make button with an "anti-bounce" circuit.

The code for the character or control function is set up on the switches in binary form and the button depressed to produce a strobe. If this method is used it is suggested that a table of the codes be prepared to tally with the switch positions. The suggested front panel layout and circuit are shown in Figs. 38 and 39. These codes might come in use-

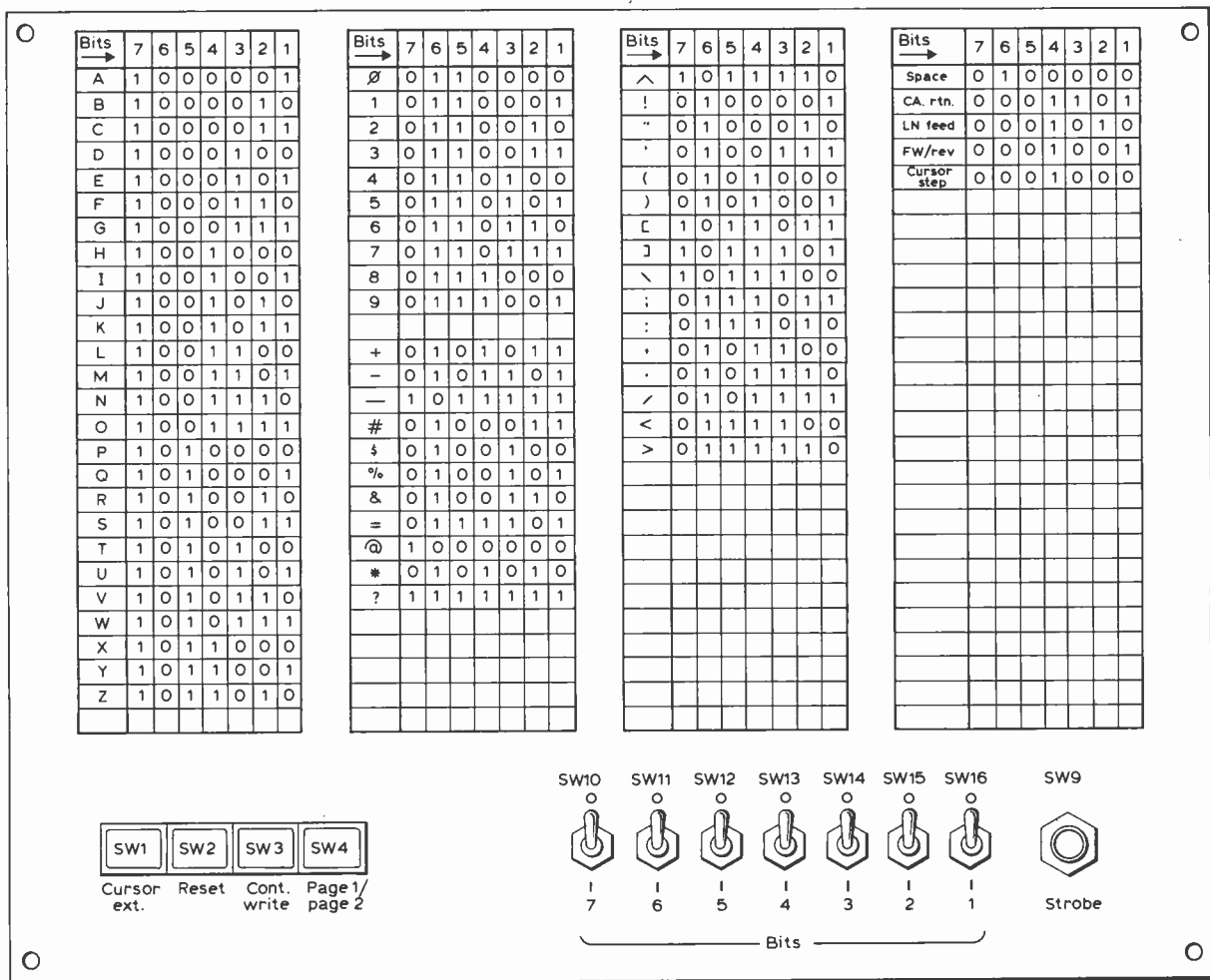


Fig. 38. A suggested layout of the front panel when toggle switches are used for data entry.

W400

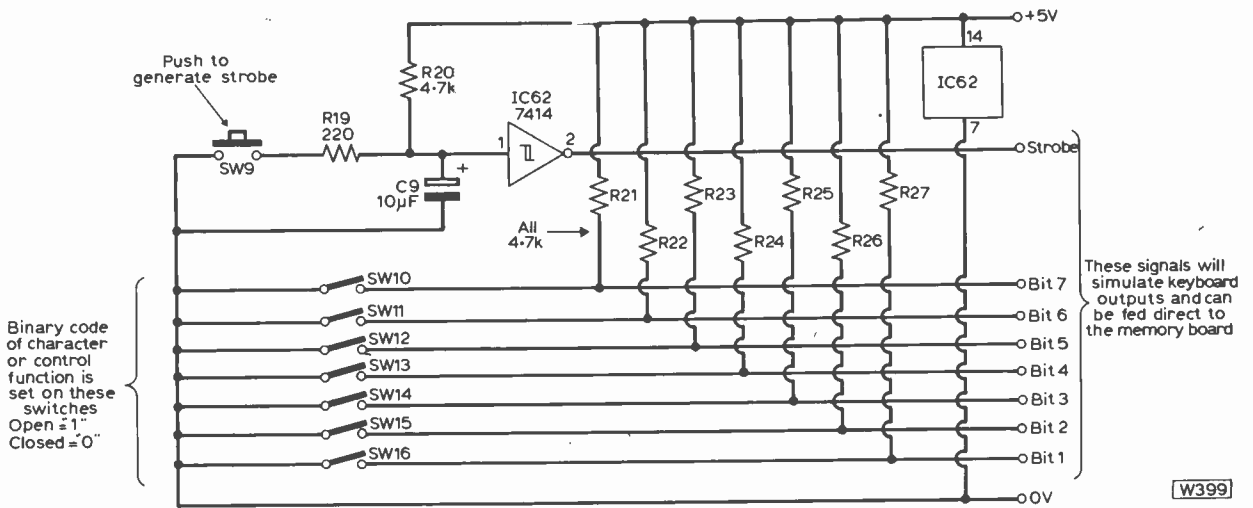


Fig. 39. The circuit diagram of the switching required to set data manually. A closed switch gives a logic "0", an open switch a logic "1".

ful for anyone carrying out the trouble shooting procedure mentioned earlier.

Although this method of entering data will be very tedious for normal use it is ideal for setting up permanent or semi-permanent displays.


PAGE SEQUENCER

A page is selected by applying a logic level "1" or "0" to the most significant address bit of the random access memory. For page 1 this bit is held at logic "1" by R9 on the memory board. To change to page 2 the junction of R9 and the address input is shorted to ground (thus applying a logic level "0"). This is carried out by closing switch SW4 (page 1/2 select). This function could be carried out electronically by an oscillator and would give automatic page sequencing.

A variable-speed page-sequencing circuit can be added to the basic video-writer without any modifications to the original layout. The requirements are a small extra circuit board and a number of flying leads connecting it to the existing pinned "leadouts" on the main boards.

The circuit for such a sequencer is shown in Fig. 40 where IC62, a 555 operating in astable mode, is the oscillator and the frequency is set by VR1 and one of the three capacitors C9-C11. The range is set by selecting one of these capacitors via the auxiliary bank of switches (already embodied in the prototype).

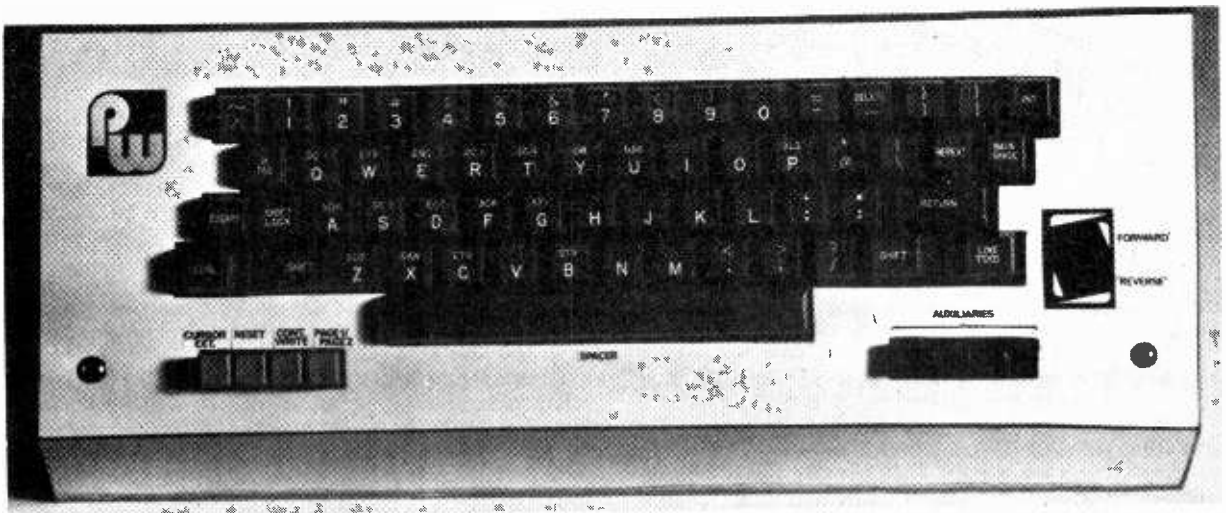VR1 gives fine control within the range selected and, in the prototype, is a preset but could be front panel mounted if desired. IC62 produces negative going pulses at the page sequencing rate and these are fed to the first part of IC63 which is a D-type



A photograph of the original keyboard. Note that the auxiliary switches are retained on the proposed layout for Non-Keyboard Keying.


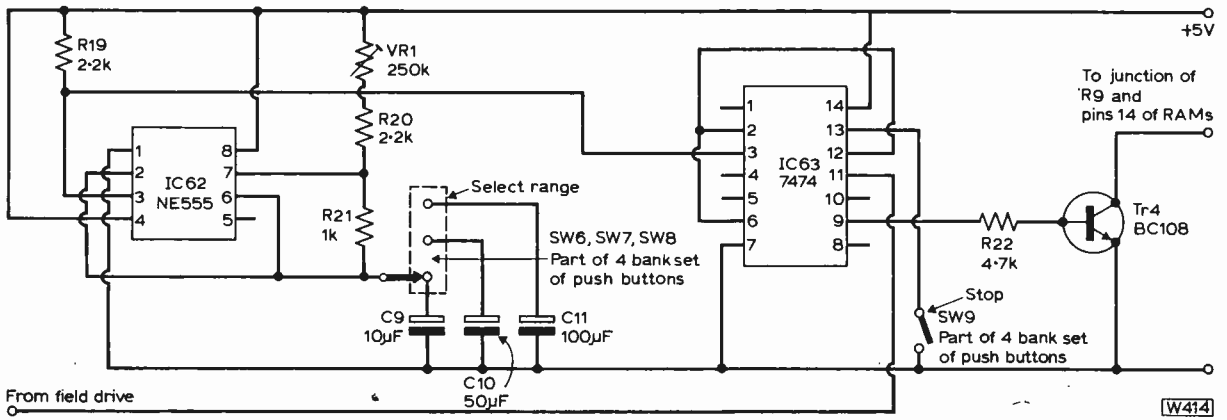


Fig. 40. The circuit diagram for the automatic page sequencer. SW4 must be open (i.e. switched to page 1) for this circuit to operate. C9, 10 and 11 can be selected for any range of speed required.

Fig. 41. The waveform appearing in the Page Sequencer.

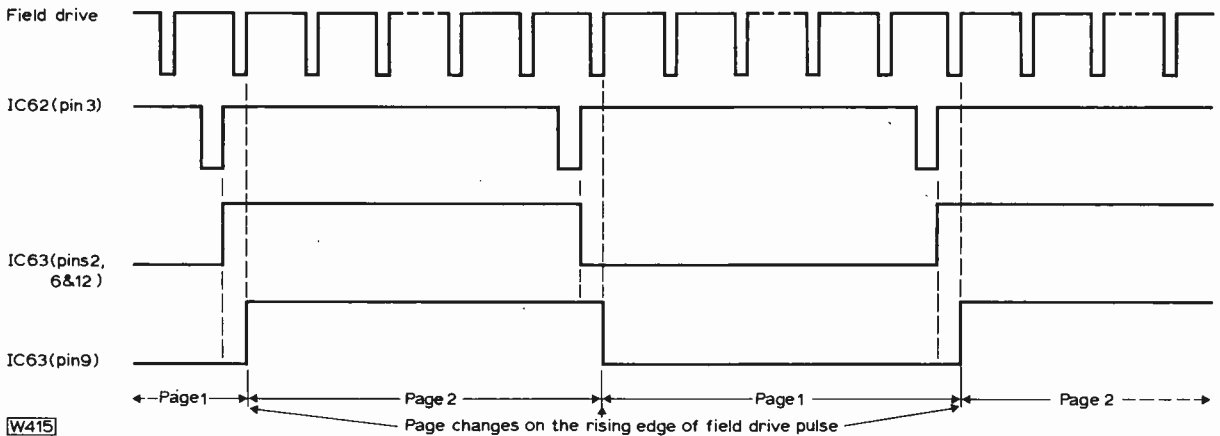

flip-flop giving unity mark space output waveform. It is desirable for the page to change during the field sync period. This prevents the displayed information changing while the scan is in the middle of a raster.

To do this it is necessary to synchronise the output at pins 2 and 6 of IC63 with the field drive pulse (obtained from the Sync Generator Board). This is done by applying the output of the first D type flip-flop in IC63 to the "D" input of its twin and using the Field Drive Pulse as a clock signal. The Clear input of this second half is connected to the fourth push-button of the auxiliary bank which serves as a "disable" to the page sequencer, (i.e. switches it off), and holds the output on pin 9 at logic level "0". The associated waveforms are shown in Fig. 41.

This signal has to be applied to the junction of R9 and the paralleled connections to pins 14 of the random access memories. This is most easily accomplished by the open collector transistor (TR4) which will pull the junction to ground when the output from the page sequencer is at logic level "1". Pro-


vided the manual page select switch SW4 is in an open circuit condition, TR4, in conjunction with R9, will allow the address to alternate from "1" to "0", according to the instruction from the sequencer unit.

If the disable button SW5 is pressed there is no base drive into TR4 and SW4 is free to give manual control of page selection. Note that for automatic page sequencing to occur, SW4 must be in an open circuit state otherwise the address will be permanently grounded (displaying "Page 2").


Using the values of capacitors and variable resistor in the parts list the duration of the page display can be varied from approximately 20 seconds a page to a fraction of a second a page.

High speed page strobing can produce interesting effects for advertising but should be used with discretion due to the hypnotic effects that can be induced. It is possible to strobe at the "Bio" Beta Frequency and under certain circumstances this can produce unpleasant side effects in a viewer.

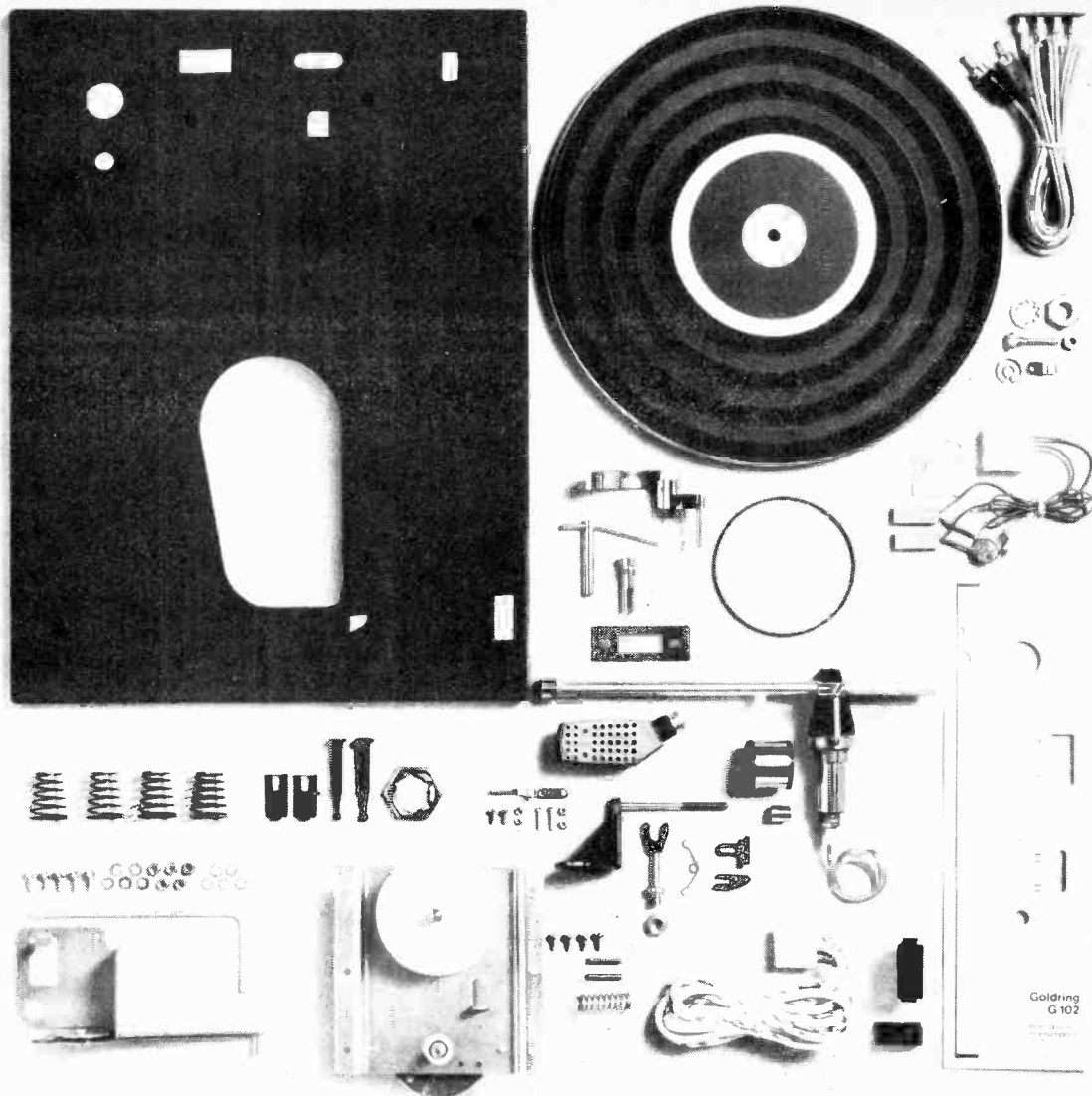The wiring pattern of the printed circuit board is shown as Fig. 42 and the component layout as Fig.



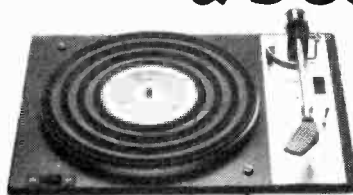You couldn't build a better start to hi-fi.



The Goldring CK2 is a top-quality deck with a difference - you build it yourself.

It's a difference that's amply reflected in the very attractive price.

And for sheer sound craftsmanship, you'd be hard put to better it.

Like more expensive decks it's belt-driven, which means less wow and flutter. And the lightweight pick-up arm has an easily-adjustable playing weight covering a wide range of cartridges. (The Goldring G800 is particularly recommended.) And built-in anti-skating device, too. A viscous damped cueing arm makes contact as light as a feather, protecting both records and stylus.

All you need to achieve the quality and sound of Goldring at an equally remarkable price? Just a soldering iron, long-nosed pliers and a screwdriver.

It's not much to ask for the best start in hi-fi you can buy.

Please send me free brochure on the CK2 turntable kit.

Goldring Manufacturing Co., Anglian Lane,
Bury St. Edmunds, IP32 6SS.

Tel: Bury St. Edmunds (0284) 64011.

Name _____

Address _____



VAT INCLUSIVE PRICES

Fully branded devices from
RCA, TEXAS, MOTOROLA,
MULLARD, etc.

Add 20p P & P—No other extras

TTLs by TEXAS

7400	16p	7492	55p
74H00	30p	7493	43p
7401	18p	7494	90p
7402	18p	7495	70p
7403	18p	7496	90p
7404	25p	7497	60p
74H04	30p	74100	116p
7405	24p	74101	116p
7406	43p	74105	60p
7407	43p	74107	36p
7408	22p	74109	70p
7409	22p	74110	55p
7410	22p	74111	80p
74H10	40p	74118	90p
7411	26p	74121	32p
7412	27p	74122	52p
7413	40p	74123	73p
7414	85p	74125	70p
7416	40p	74126	65p
7417	40p	74132	75p
7420	18p	74136	81p
7421	43p	74141	85p
7422	28p	74142	300p
7423	38p	74145	95p
7425	33p	74146	173p
7427	40p	74150	120p
7428	39p	74151	72p
7430	18p	74153	92p
7432	37p	74154	164p
7437	37p	74155	97p
7440	18p	74156	97p
7441	85p	74157	96p
7441	85p	74159	220p
7442	75p	74160	107p
7443	116p	74161	107p
7444	116p	74162	107p
7445	120p	74163	107p
7446	95p	74164	130p
7447	90p	74165	150p
7448	80p	74166	140p
7450	18p	74167	340p
7451	18p	74170	300p
7453	18p	74173	60p
7454	18p	74174	28p
7460	18p	74175	145p
7470	36p	74176	131p
7472	32p	74177	100p
7473	36p	74180	108p
7474	37p	74181	322p
7475	45p	74182	45p
7476	37p	74185	146p
7480	54p	74190	155p
7481	103p	74191	155p
7482	85p	74192	130p
7483	99p	74193	76p
7484	99p	74194	76p
7485	120p	74195	102p
7486	36p	74196	108p
7489	340p	74197	108p
7490	43p	74198	270p
7491	90p	74199	270p

C-MOS ICs

4000	21p	4029	120p
4001	21p	4030	59p
4002	21p	4042	60p
4008	104p	4043	100p
4007	21p	4046	150p
4009	67p	4047	100p
4011	21p	4049	68p
4012	22p	4050	50p
4013	55p	4055	120p
4015	90p	4056	120p
4016	54p	4056	145p
4017	100p	4060	120p
4018	120p	4069	40p
4019	50p	4071	29p
4020	120p	4072	29p
4022	103p	4084	19p
4023	21p	4082	29p
4024	75p	4510	142p
4025	21p	4511	160p
4026	200p	4516	140p
4027	81p	4518	140p
4028	152p	4528	130p

LOW PROFILE DIL SOCKETS by TEXAS

8 pin 12p, 14 pin 13p, 16 pin 14p, 24 pin 40p

VOL. REGS.

FIXED—Plastic 3 Terminals	1 Amp	Positive
5V	7805	130p
12V	7812	130p
15V	7815	130p
18V	7818	150p
24V	7824	150p
1 Amp	Negative	150p
5V	7905	215p
12V	7912	215p
15V	7915	215p
18V	7918	215p
24V	7924	215p

LM309K (TO3) 5V 1 Amp 150p
LM332K (TO3) 5V 3 Amp 150p
TDA625B (TO5) 12V 0.5A 99p
7805 (TO3) 5V 1 Amp 150p

VARIABLE VOL. REG.

723 14 Pin DIL 45p

TRANSISTORS

AC125	20p
AC126	20p
AC127	20p
AC128	20p
AC178	20p
AC187	20p
AC188	20p
AD149	54p
AD161	39p
AD162	39p
AF114	22p
AF115	22p
AF116	22p
AF117	22p
AF139	40p
AF239	48p
BC107B	10p
BC108B	10p
BC109	10p
BC109C	11p
BC147	9p
BC148	8p
BC157	11p
BC158	13p
BC159	13p
BC169C	15p
BC171	12p
BC172	11p
BC177	20p
BC178	17p
BC179	20p
BC182	12p
BC183	12p

OP. AMPS

301A	Ext. Comp. 8 pin DIL	40p
536T	FET. Comp. AMP TO 99	300p
709	Ext. Comp. 8/14 pin DIL	30p
710	Diff. Comp. 14 pin DIL	45p
747	Int. Comp. 8/14 pin DIL	25p
748	Diff. 7/14 pin DIL	25p
748	Ext. Comp. 8 pin DIL	40p
749	Prog. Op. Amp TO 99	153p
1458	Dual Op. Amp. 8 pin DIL	70p
3130	CMOS/Bipolar Mosfet	108p
3140	BIMOS/FET Input 8 pin DIL	108p
3900	Quad. Op. Amp. 14 pin DIL	78p

LINEAR I.C.s.

AY-1-0212	Tone Gen. 16pin DIL	650p
CA 3028A	Diff. Cascade Amp. To 99	112p
CA 3046	5 Transistor Array 14 pin DIL	85p
CA 3048	Quad. Low Noise Amp.	250p
CA 3053	Diff. Cascade Amp. TO5/DIL	75p
CA 3080	Op Transconduct. Amp. 8 DIL	97p
CA 3089E	FM IF System 16 pin DIL	250p
CA 3090AQ	FM Stereo Decoder QIL	500p
ICL8038CC	VCO Fun. Ken 14 pin DIL	370p
LM380N	2W Audio Amp 14 pin DIL	112p
LM381N	Stereo Pre Amp 14 pin DIL	190p
LM389N	Aud Amp + 3 Trs. Arr. 18 DIL	175p
M252	Rhythm Ken 16 pin DIL	850p
MC1310	FM Stereo Decoder 14 pin DIL	180p
MC1351P	Lim/Det. Audio Preamp	104p
MC1495	Multiplier 14 pin DIL	370p
MC1496	Bal. Mod/Demod 14 DIL	115p
MC3340P	Elec. Attenuator 8pin DIL	180p
MFC4000B	1W Audio Amplifier PCB	90p
NE540L	Audio Pwr. Driver TO99	140p
NE555V	Timer 8 pin DIL	48p
NE556	Dual 555 14 pin DIL	75p
NE61B	PLL with AM Demod	420p
NE562B	PLL with VCO 16 pin DIL	425p
NE565	PLL 14 pin DIL	200p
NE566V	PLL Function Gen 8 pin DIL	200p
NE567V	PLL Tone Decoder 8 pin DIL	200p
SN7514	Dual 555 14 pin DIL	400p
SN72733	Video Amplifier 14 pin DIL	150p
SN76003N	Audio Pwr. Amp with HS	275p
SN76008	10W in 4 ohms 5pin Plas.	280p
SN76013N	Audio Pwr Amp with HS	175p
SN76023N	Audio Pwr Amp with HS	175p
SN76033N	Audio Pwr. Amp with HS	275p
TAA621A	Aud. Amp. for TV QIL	310p
TAA661B	FM IF Amp Lim/Detector QIL	150p
TBA641B	Audio Amp QIL	300p
TBA800	5W Audio Amp QIL	100p
TBA810	7W Audio Amp QIL	125p
TBA920	2W Audio Amp QIL	100p
TDA2020	20W Audio Amp QIL	405p
XR2240	Prog Timer/Counter 16 pin DIL	400p
ZN414	TRF Radio Receiver TO18	140p

OPTO-ELECTRONICS

PHOTO-TRANSISTORS

OCp70	50p	
OCp71	50p	
OCp72	18p	
2N5777	18p	
2N5778	58p	
LDRs	0.2"	
ORP12	70p Red + clip	18p
ORP60	75p Green	38p
ORP61	75p Yellow	32p

SEVEN SEGMENT DISPLAYS

3015F	Minitron 0.3"	160p
DL704	Com. Cathode 0.3"	160p
DL707	Com. Anode 0.3"	160p
DL747	Com. Anode 0.6"	250p

SCR THYRISTORS

BF258	39p
BFR39	34p
BFR40	34p
BFR79	34p
BFR80	34p
BFR88	37p
BFX30	32p
BFX84	30p
BFX85	30p
BFX86	30p
BFX87	30p
BFX88	30p
BFY50	17p
BFY51	16p
BFY52	17p
BRV39	48p
BSX19	20p
BSX20	20p
BU105	175p
BU108	312p
MJE340	48p
MJE2955	130p
MJE3055	130p
MJSA06	37p
MPSA12	62p
MPSU06	78p
MPSU08	88p
OC28	90p
OC35	90p
OC41	19p
OC42	19p
OC45	19p
OC71	25p
TIP29A	50p
TIP29C	62p

DIACs

2N1133	22p
2N1134	22p
2N1135	22p
2N1136	22p
2N1137	22p
2N1138	22p
2N1139	22p
2N1140	22p
2N1141	22p
2N1142	22p
2N1143	22p
2N1144	22p
2N1145	22p
2N1146	22p
2N1147	22p
2N1148	22p
2N1149	22p
2N1150	22p
2N1151	22p
2N1152	22p
2N1153	22p
2N1154	22p
2N1155	22p
2N1156	22p
2N1157	22p
2N1158	22p
2N1159	22p
2N1160	22p
2N1161	22p
2N1162	22p
2N1163	22p
2N1164	22p
2N1165	22p
2N1166	22p
2N1167	22p
2N1168	22p
2N1169	22p
2N1170	22p
2N1171	22p
2N1172	22p
2N1173	22p
2N1174	22p
2N1175	22p
2N1176	22p
2N1177	22p
2N1178	22p
2N1179	22p
2N1180	22p
2N1181	22p
2N1182	22p
2N1183	22p
2N1184	22p
2N1185	22p
2N1186	22p
2N1187	22p
2N1188	22p
2N1189	22p
2N1190	22p

DIACs

2N1133	22p
2N1134	22p
2N1135	22p
2N1136	22p
2N1137	22p
2N1138	22p
2N1139	22p
2N1140	22p
2N1141	22p
2N1142	22p
2N1143	22p
2N1144	22p
2N1145	22p
2N1146	22p
2N1147	22p
2N1148	22p
2N1149	22p
2N1150	22p
2N1151	22p
2N1152	22p
2N1153	22p
2N1154	22p
2N1155	22p
2N1156	22p
2N1157	22p
2N1158	22p
2N1159	22p
2N1160	22p
2N1161	22p
2N1162	22p
2N1163	22p
2N1164	22p
2N1165	22p
2N1166	22p
2N1167	22p
2N1168	22p
2N1169	22p
2N1170	22p
2N1171	22p
2N1172	22p
2N1173	22p
2N1174	22p
2N1175	22p
2N1176	22p
2N1177	22p
2N1178	22p
2N1179	22p
2N1180	22p
2N1181	22p
2N1182	22p
2N1183	22p
2N1184	22p
2N1185	22p
2N1186	22p
2N1187	22p
2N1188	22p
2N1189	22p
2N1190	22p

DIACs

2N1133	22p
2N1134	22p
2N1135	22p
2N1136	22p
2N1137	22p
2N1138	22p
2N1139	22p
2N1140	22p
2N1141	22p
2N1142	22p
2N1143	22p
2N1144	22p
2N1145	22p
2N1146	22p
2N1147	22p
2N1148	22p
2N1149	22p
2N1150	

Fig. 42. The etched wiring pattern of the Page Sequencer board drawn full size.


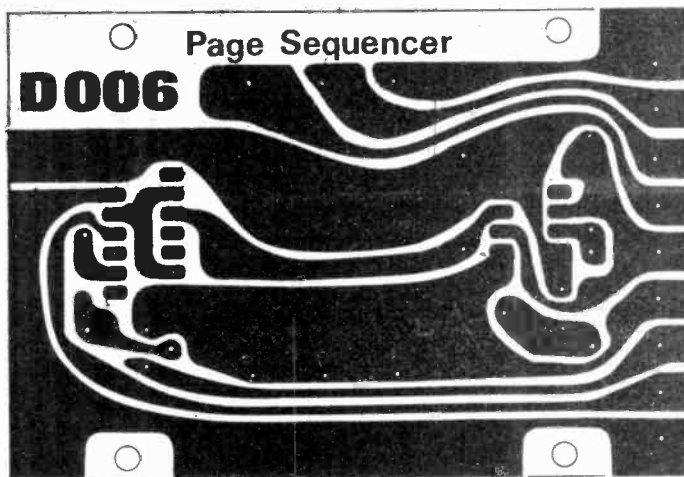


Fig. 43. The component overlay information. Observe the +ve marking when using polarised capacitors. VR1 is shown as a miniature preset but could be externally mounted.

AM 0514A

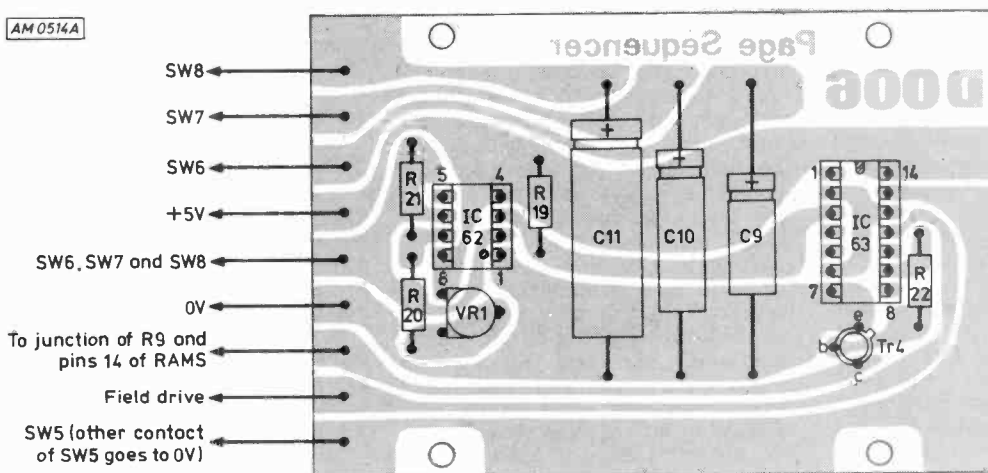

★ components list

NON-KEYBOARD KEYING

- R19 220Ω 10% 1/4W
- R20 4.7kΩ 10% 1/4W
- R21 4.7kΩ 10% 1/4W
- R22 4.7kΩ 10% 1/4W
- R23 4.7kΩ 10% 1/4W
- R24 4.7kΩ 10% 1/4W
- R25 4.7kΩ 10% 1/4W
- R26 4.7kΩ 10% 1/4W
- R27 4.7kΩ 10% 1/4W
- C9 10μF 12V 10% 1/4W
- SW9 Push-to-make button switch
- SW10-SW16 Single pole toggle switches
- IC62 7414
- Small piece of Veroboard.


★ components list

PAGE SEQUENCER

- R19 2.2kΩ, 10%, 1/4W
- R20 2.2kΩ, 10%, 1/4W
- R21 1kΩ, 10%, 1/4W
- R22 4.7kΩ, 10%, 1/4W
- VR1 250kΩ (sub-min horizontal pre-set)
- C9 10μF (10V)
- C10 50μF (10V)
- C11 100μF (10V)
- TR4 BC 108
- IC6 NE 555
- IC6 7474
- One off 8 pin DIL socket
- One off 14 pin DIL socket
- SW5-SW8 Interlocking bank of 4 push switches
- Printed Circuit Board
- Printed Circuit Board Pins

43. The +5V and 0V supply lines are taken off the respective pins of the memory board; the output from the page sequencer goes to the Page 1/Page 2 input of the memory board; the Field Drive is taken from its associated pin on the Sync Generator Board and the page sequencer disable and range select inputs are taken to the respective contacts on SW5, 6, 7 and 8.

This extra board can be mounted inside the Videowriter in any convenient position.

These two modifications complete the original article. Other add-on and interface units are under consideration and, subject to there being sufficient demand, will be published at a later date. 

Dear Sir,



Thermionic passion

Being a long-standing reader, and not too old to remember valves, I really must protest about the dismissal of the Good Old Valve. December issue letters raised my passion. I rarely write protest letters but Mr. Harcourt must surely remember the Coherer, this being one of the earliest forms of detector and non-semiconductor.

Mr. Hill should live surrounded by transmitters as I am. Radio 4 appears as 150mV of RF at the aerial and can be measured using a 20,000 Ω voltmeter in a tuned circuit. The poor transistor, be it unipolar or bipolar, just cannot stand the strain unlike the good old valve, which can be abused to a great degree before it gives up the ghost. Transistors and I.C.s die at the first spike or serious overload, but they still have their uses.

My final comments are that the valve will not be replaced for many years, and to this day there are jobs where the valve remains supreme master. Two examples are front-end stages of communications receivers and high power transmitters. Ask the Radio Amateurs! G. Sims (Derbyshire).

Powerful argument

With reference to Mr. Nuttall's comments in the November issue on your August Editorial, he complains of ignorance on your part, but what hypocrisy!

I refer Mr. Nuttall in the following to "Hi-Fi in the Home", by John Crabbe. (Never heard of it, Mr. Nuttall?)

The amount of power required by an amplifier in excess of 30W RMS has got very little to do with

headroom. It is a question of relating power to loudspeaker efficiency, equated to the volume of the listening environment. Up to 30W power should give plenty of headroom. If it doesn't, then turning down the volume on any amp will assist, and if the result is then lack of loudness and realism in the music, this is a sign that the amp—to speaker—to room conversion efficiency, is unbalanced. High power amps have uses, such as filling halls and auditoriums, but the myth that they are necessary to smooth reproduction all the time is a half-baked truth. Certainly they can help, but only when considering numerous other factors, such as the power supply, pre-amp overload, and speakers.

For the sound powers needed in all but the most exceptional domestic surroundings, the electrical power required from the amp depends mainly on speaker efficiency:- "The quantities of acoustic energy transmitted into the air in a normal sized room when reproducing orchestral music at a realistic loudness, are absolutely minute; a power level of about half of one acoustic watt representing the very maximum needed during peaks of the most enormous climaxes. But most loudspeakers are so inefficient that production of this $\frac{1}{2}$ W of sound output requires about 10W of electrical input. An electro-acoustic efficiency of 5 per cent".

I can assure Mr. Nuttall that low power amps are quite capable of Hi-Fi. If they are not, then it is not the power output availability which is failing, but rather pre-amp overload, transistor junction storage capability, rise-time and slow rate related to negative feedback. A 20W RMS amp with the correct degree of engineering will probably knock up 80W music power, which covers transient peaks quite effectively, other factors allowing. How the loudspeaker interprets this is another story again, depending on the thermal energy and general elasticity of the system amongst other factors.

The newer loudspeaker enclosures on the market are rarely above 2-3 per cent efficient throughout the whole audio bandwidth, so higher power amps are required. But not because they give more headroom, but because the speakers need on average a slightly higher drive level on

music content, all the time. Check the difference between old and new speakers.

So, Mr. Nuttall, although at certain peaks, muddiness does set in on Hi-Fi systems (in this you are right). You are not strictly correct in interpreting its cause. Lets face it Mr. Nuttall, any amp (even your Naim 160) of any power description, will cause its output transistor to bang its head against the power rail and say, "that's enough, no more" if driven hard enough. It's only good pre-amp engineering, transistor stage design and your hand on the volume pot which prevents this—and here we reach the crux, which was partly the point made in the August Editorial. Power transistors cost many pence, signal transistors (even low-noise ones) are comparatively cheap. This is why it is possible for a well designed amp of £30 to be well up in Hi-Fi quality.

My point is made Mr. Nuttall. Your view on power reminds me of the gentleman in the sports car who once said to me, he believed he went a lot, lot faster with the hood down!

Wake-up Mr. Nuttall, and when you do, try appraising what you read or hear a little, before criticising.—E. Hoskins, (Technical Director, CEH Audio-Visual Enterprises, Tonbridge).

Any ideas?

Being an "old timer" I have been a reader of Practical Wireless for many years and am particularly interested in the "Going Back" series. A hobby (or rather a hobby within a hobby) of mine is the rebuilding of pre-war and pre-1930 radio designs and I have accumulated a large amount of gear of this date. One snag is that loudspeaker and headphone magnets have nearly always seriously deteriorated in strength and despite the most thorough reading of technical books available, no worth while information is available on the remagnetisation of these components (I think mostly of balanced armature speakers). Do any PW readers know of literature that deals with this, or can supply any info. on this subject.—T. Howells, (Radio Officer, m/v Geestcrest, c/o Geest Industries, Barry Dock, Glamorgan).

T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD Etc

7400	17p	7413	40p	7432	30p	7454	20p	7490	45p	74120	115p	74138	135p	74154	170p	74170	200p	74188	370p
7401	17p	7414	80p	7437	33p	7460	20p	7491	82p	74121	35p	74139	135p	74155	90p	74171	180p	74189	350p
7402	18p	7416	35p	7438	33p	7470	30p	7492	55p	74122	35p	74141	80p	74156	100p	74174	100p	74190	260p
7403	18p	7417	40p	7440	30p	7471	30p	7493	45p	74123	75p	74142	32p	74157	100p	74175	100p	74191	160p
7404	25p	7420	18p	7441	70p	7472	70p	7494	35p	74125	70p	74143	32p	74158	120p	74176	130p	74192	130p
7405	45p	7422	25p	7442	70p	7473	35p	7495	75p	74126	75p	74144	32p	74159	120p	74177	130p	74193	130p
7406	45p	7423	40p	7443	95p	7474	35p	7496	85p	74127	75p	74145	90p	74160	120p	74178	100p	74194	130p
7407	45p	7424	50p	7444	110p	7475	55p	7497	100p	74128	150p	74146	245p	74161	120p	74179	120p	74195	100p
7408	25p	7425	35p	7445	85p	7476	35p	7498	100p	74129	77p	74147	180p	74162	130p	74180	120p	74196	125p
7409	25p	7426	38p	7446	85p	7477	85p	7499	130p	74130	100p	74148	150p	74163	130p	74181	90p	74197	125p
7410	18p	7427	40p	7447	18p	7478	100p	7500	35p	74131	60p	74149	80p	74164	150p	74182	185p	74198	250p
7411	25p	7428	45p	7448	20p	7479	285p			74132	85p	74150	90p	74165	370p	74183	150p	74199	250p
7412	25p	7430	18p	7449	20p	7480	285p			74133	125p	74151	80p	74166	370p	74184	150p		

SEMICONDUCTORS

by MULLARD, TEXAS, MOTOROLA, SIEMENS, I.T.T., R.C.A.

AA113	10p	BA121	9p	BC159	10p	BC338	12p	BF167	25p	BFW58	20p	C1164	20p	TIP29	45p	TIP41B	75p	2N1308	50p
AA144	10p	BA138	16p	BC167A	12p	BC547	12p	BF173	25p	BFX29	30p	MJE340	45p	TIP29A	47p	TIP41C	90p	2N1711	22p
AAZ17	30p	BA148	16p	BC188B	14p	BC548	12p	BF179	35p	BFX81	130p	MP5A06	25p	TIP29C	75p	TIP42A	80p	2N2194	25p
AC121	30p	BA154	12p	BC188C	15p	BC549B	13p	BF180	30p	BFX82	30p	OA10	40p	TIP30	55p	TIP42B	85p	2N2483	30p
AC126	19p	BA157	15p	BC190C	15p	BC549C	14p	BF181	35p	BFX85	30p	OA90	6p	TIP30A	58p	TIP295F	70p	2N2906	18p
AC127	19p	BA173	15p	BC171	12p	BC557	13p	BF182	30p	BFX87	25p	OA91	6p	TIP30B	65p	TIP3055	55p	2N2907	20p
AC127/01	25p	BA216	16p	BC172C	12p	BC574	80p	BF183	30p	BFX88	25p	OA202	8p	TIP30C	80p	TIS90	25p	2N3053	20p
AC128	18p	BA316	16p	BC178A	16p	BCV70	15p	BF184	25p	BFY50	20p	OC23	200p	TIP31	55p	TIS91	25p	2N3055	60p
AC151	25p	BA313	5p	BC182	10p	BCV71	20p	BF185	25p	BFY51	20p	OC25	100p	TIP31B	65p	IN914	5p	2N3439	50p
AC176	20p	BA318	5p	BC182L	12p	BCV72	15p	BF191	10p	BFY52	20p	OC28	75p	TIP31C	75p	IN3754	10p	2N3702	11p
ACV17	35p	BA305A	35p	BC183L	12p	BD123	100p	BF192	10p	BR101	35p	OC35	75p	TIP32	60p	IN4001	5p	2N3703	12p
AD127	30p	BB110	45p	BC183L	12p	BD131	36p	BF197	10p	BRY36	35p	OC42	75p	TIP32A	65p	IN4002	5p	2N3704	11p
AD149	80p	BC107	10p	BC184	10p	BD132	36p	BF199	25p	BRY56	35p	OC43	35p	TIP32B	85p	IN4003	5p	2N3705	11p
AD161	40p	BC108	10p	BC184L	12p	BD133	36p	BF199	25p	BSX20	20p	OC45	35p	TIP32B	85p	IN4004	5p	2N3706	11p
AD162	40p	BC108C	10p	BC186	24p	BD135	45p	BF200	30p	BSY40	25p	OC71	25p	TIP32C	90p	IN4005	5p	2N3711	12p
AD161/2M	90p	BC109	10p	BC205	14p	BD137	40p	BF201	30p	BSY45	20p	OC72	30p	TIP33A	105p	IN4006	6p	2N3715	12p
AF114	22p	BC109C	14p	BC212	11p	BD139	38p	BF202	20p	BT100A	80p	OC73	30p	TIP33B	115p	IN4007	7p	2N3722	175p
AF115	22p	BC117	19p	BC213L	12p	BD140	40p	BF244B	35p	BU133	75p	OC81	30p	TIP33C	130p	IN4148	4p	2N3819	25p
AF116	22p	BC125	20p	BC214	13p	BD181	80p	BF257	25p	BU208	220p	OC81D	25p	TIP34	115p	2N456A	90p	2N3866	95p
AF117	22p	BC126	15p	BC214L	14p	BD182	80p	BF258	28p	BY100	20p	OC83	30p	TIP34A	118p	2N697	15p	2N4062	14p
AF118	50p	BC146	12p	BC258	13p	BD207	70p	BF259	30p	BY129	15p	OC10	150p	TIP35	225p	2N929	20p	2N4126	20p
AF125	25p	BC147	10p	BC294	35p	BDY10	100p	BF274	15p	BY127	15p	OC171	40p	TIP35A	230p	2N930	20p	2N5061	35p
AF139	35p	BC148	10p	BC303	55p	BDY10	100p	BF274	15p	BY164	50p	OC200	80p	TIP35C	280p	2N1302	25p	2N5163	35p
AF238	45p	BC149	10p	BC317	15p	BDY62/01	30p	BF337	35p	BY164	50p	ORP12	70p	TIP36A	350p	2N1305	30p	2N6207	50p
ASV26	40p	BC157	10p	BC323	60p	BF120	50p	BF363	60p	BYX94	8p	R1039	150p	TIP41A	70p	2N1306	38p	25D234	50p
BA114	9p	BC158	10p	BC328	13p	BF166	30p	BF594	30p	CI120	30p								

SPECIAL QUANTITY PRICES TO MANUFACTURERS AND GOOD OLD FASHIONED SERVICE i.e. GOODS DELIVERED TO YOUR PREMISES WITHIN 150 MILES OF LONDON AREA


BZX61 Zeners 1-3W 12V 10p 15V 10p 18V 20p 15p 20p 11V 15p 13V 15p 15V 15p 22V 15p 30V 15p 100 Mixed Zeners 850p 39V 15p 43V 15p 47V 15p 51V 15p 56V 15p 68V 15p 72V 15p 160V 15p	BZY88 400M.W. Zeners OV7 10p 2V4 10p 2V7 10p 3V0 10p 3V3 10p 3V6 10p 3V9 10p 4V7 10p 5V1 10p 5V6 10p 6V2 10p 6V8 10p 7V5 10p 8V2 10p 9V1 10p 10V 10p 11V 10p	ERIE CARBON RESISTORS Type 7AD £4 1000 Type 10AD £8 1000	ELECTROLYTIC CAPACITORS µF/V 330/25 15p 330/35 16p 330/50 18p 470/10 12p 470/25 18p 470/35 18p 470/50 22p 680/25 25p 1000/15 25p 1000/35 30p 4-7/16 5p 4-7/16 5p 2200/16 35p 2200/63 60p 2200/100 60p 10/10 5p 10/16 5p 10/25 5p 10/35 5p 10/50 5p 4700/25 45p 4700/40 50p 4700/63 120p 22/16 5p 22/25 5p 22/35 5p 22/50 5p 33/63 5p 33/16 6p 33/25 6p 33/40 6p 33/50 7p 33/70 7p 33/100 7p 47/10 7p 47/16 8p 47/25 8p 47/35 8p 47/50 8p 100/10 10p 100/16 10p 100/25 10p 100/35 10p 100/50 10p 100/75 10p 100/100 10p 100/150 10p 100/200 10p 100/300 10p 100/400 10p 100/500 10p 100/630 10p 100/800 10p 100/1000 10p 100/1500 10p 100/2000 10p 100/3000 10p 100/4000 10p 100/5000 10p 100/7500 10p 100/10000 10p	SPECIAL OFFERS BC147 BC148 BC149 BC157 BC158 BC159 BF195 BF197 IN4148 100 for 150p 741 OP AMPS 100 for £25 555 TIMERS 100 for £37 RELAYS 24V 3 C.O. H.D. 11 Pin Plug 1N £1.00 Each ASSORTED POLYESTER CAPACITORS 100 for £3.00 BYX94 DIODES 1250 PIV 1 Amp. 100 for £8.00 MULLARD 4500/84V C.432 Screw Terminal 75p	RESISTORS CARBON FILM 5% -25 W 2-2 Ω-4-7M 2p -5 W 2-2 Ω-4-7M 2-5p 1 W 2-2 Ω 10 MEG 3-5p	POTENTIAL METERS 1K Lin 30p 5K Lin 30p 10K Lin 30p 25K Lin 30p 50K Lin 30p 100K Lin 30p 1 Meg Lin 30p 2 Meg Lin 30p 5K Log 30p 10K Log 30p 25K Log 30p 50K Log 30p 100K Log 30p 1 Meg Log 30p 2 Meg Log 30p	MULLARD POT CORES LA3 10-30 KHz LA4 10-30 KHz LA5 30-100KHz LA7 < 10KHz LA13 FOR W.W. OSCILLOSCOPE 200p	VDR'S RESISTORS 75p E2202/13 E2252/21 E2272/04 E2272/05 E2282/102 E2282D/258 E2282D/A260 E2282D/A265 E229D/P118 E229D/P224 E229D/P226 E229D/P236 E229D/A238 E229D/P342 E229D/P350 E229D/P354 VA1008 VA1011 VA1063 VA1067 VA1072 VA1077 VA1099 VA1106 VA1107 VA1110 VA1111 VA1112 VA1549 VA1550
---	--	---	--	---	--	---	---	--

Incredible Value in Precision Test Meters

AVAILABLE FROM SELECTED STOCKISTS. WRITE OR PHONE FOR LIST

MICROTEST 80—I.C.E. 20,000 Ohms/Volt 40 RANGES

20,000 Ohms/Volt, (d.c.) 4,000 Ohms/Volt (a.c.) 2% accuracy. V d.c. 100mV to 1kV (6 Ranges). I d.c. 50 μ A to 5A (6 Ranges). V a.c. 1.5V to 1kV (5 Ranges) I a.c. 250 μ A to 2.5A (5 Ranges). Resistance, Low Ohms, Ohms \times 1, Ohms \times 10, Ohms \times 100. Output Level Measurements 1.5V to 1000V (5 Ranges) + 6dB to + 62dB (5 Ranges). Capacitance 25 μ F to 25,000 μ F (4 Ranges). 1000 times overload protection (on Resistance ranges). Meter movement diode protection. Size (without case) 90 \times 70 \times 18mm. Automatic zero, non-parallax mirror scale. Unbreakable carrying case and probes supplied. Full After Sales Service available. **Price £15.66 inc. VAT**

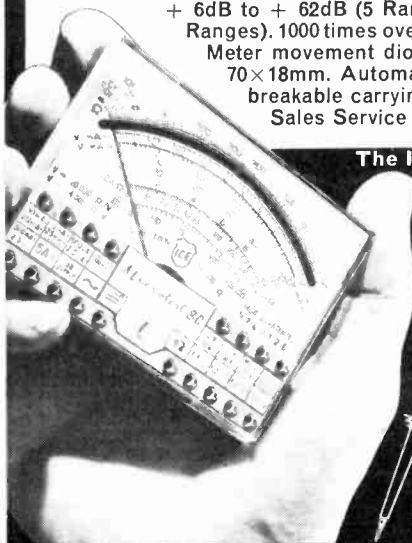


The I.C.E. Measurement System includes a comprehensive range of accessories: shunts, transformers, specialised probes, transistor-tester etc. I.C.E. High-Voltage d.c. Probe, Model 18. Input Impedance: 500M Ohm, nominal (Other values available to order). The Model 18 d.c. Probe consists of a highly insulated moulded plastic body, fitted with a hand guard-ring, containing a stable, precision 500M Ohm resistor, which may be used to extend the d.c. voltage measuring capability of analogue multi-meters or electronic voltmeters, to a maximum value of 25kV. The probe is fitted with a prod-tip for connection to the voltage source to be measured and a connecting lead terminating in a 2mm plug for insertion into the measuring instrument's d.c. voltage input socket. (4mm plug available to order). **£6.42 inc. VAT**



SUPER TESTER 680R—I.C.E.

20,000 Ohms/Volt 80 RANGES

20,000 Ohms/Volt 1% d.c. 4,000 Ohms/Volt a.c. 2% V d.c. 100mV to 2kV (13 ranges). V a.c. 2V to 2kV (11 Ranges). I d.c. 50 μ A to 10A (12 Ranges). I a.c. 250 μ A to 5A (10 Ranges). Resistance Ohms \times 1, \times 100, \times 1000, \times 10,000 and Low Ohms. Reactance Detector 0-10M Ohms. Freq. Measurement 0-5000 Hz (2 Ranges). Output Level 10-2000V (9 Ranges). Decibels -24 to +70dB (10 Ranges). Capacitance 0-500,000 pF (2 Ranges using mains supply) 0-20,000 μ F (4 Ranges using Internal 3 Volt battery). 1000 times overload protection on Resistance ranges and meter movement diode protection. 10 Measurement Functions and 80 Ranges. Size 128 \times 95 \times 32mm. Non-parallax mirror scale. Unbreakable carrying case supplied which contains probes, mains lead, crocodile clips and shorting link. **Price £24.30 inc. VAT**

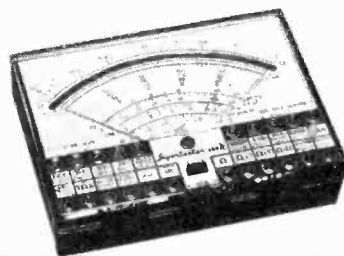


Sole Importers and Distributors

Electronic Brokers Ltd

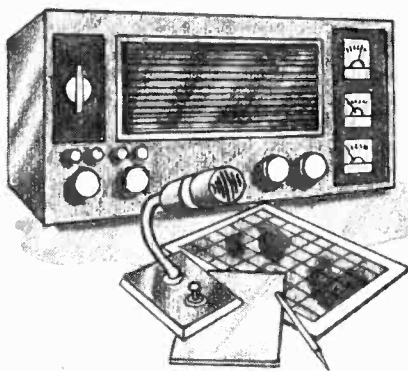49-53 Pancras Rd., London NW1 2QB. Tel: 01-837 7781

Careers and Hobbies in Electronics.

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.



Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.


FREE! Brochure without obligation to
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, WL 3/7
 P.O. BOX 156, JERSEY, CHANNEL ISLANDS.

NAME _____
 ADDRESS _____

 BLOCK CAPS PLEASE

PRODUCTION LINES

bill tull

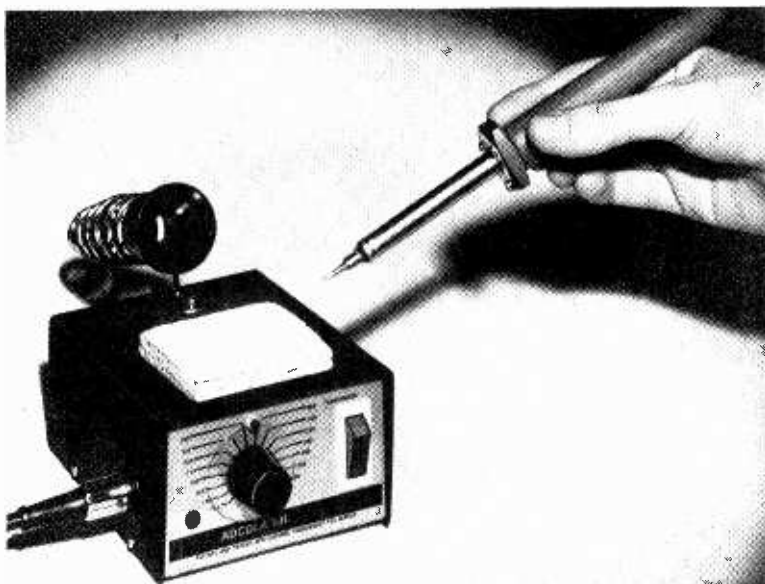

Spot-on iron

I suppose there must be literally hundreds of soldering irons of one kind or another available in the UK at this very moment. Of course the cheap iron that is thrust upon an unsuspecting constructor, accompanied with the words 'psst—wanna buy a cheap iron guv' is little better than useless. A good maxim when looking for an iron is the one that says 'you pays yer money and takes yer choice', and although the latest iron from Adcola is a little on the expensive side, it could be argued that it is simply one of the best irons available to the general public.

Incorporating a thermocouple at the rear of the soldering bit, which then feeds an Op. amp and other circuitry, the temperature can be kept within $\pm 2\%$ of the indicated dial temperature which is 120°C to 420°C . Heating time from a cool 24°C up to a blistering 420°C is claimed to be less than 2 minutes, while at any temperature the handle stays cool and comfortable for the user.

Operating from a 24V toroidal transformer, this 50W, Unit 101 soldering station carries a price tag of £36.75.

Further information from Adcola Products Ltd., Adcola House, Gauden Road, London, SW4.

Space age tape

'Enough to go to the Moon and back 24 times' is the claim put forward by AMSA Magnetics, who further claim to be the largest manufacturer of cassette tape in the world. Realising the enormous potential of the UK market, they have launched a new range of cassettes which are said to be of a very high quality and feature a specially developed jam-proof mechanism—Paraflo guides.

The range of cassettes available are Standard—a quality low noise tape with a permanent head cleaner

leader. Extra—available in C66 or C99 lengths and featuring the new Paraflo guides and head cleaner Leader. Super—Ferric Oxide tape, and XHE—the top of the range tape containing Magnalinc™ Ferric Oxide which is claimed to give a superior S/N ratio and good frequency response. The XHE cassette also features instant-start recording and a jamfree mechanism. Prices range from 89p for a standard C-60 to £2.65 for a C-120 XHE.

AMSA Magnetics, 121 Loverock Road, Reading, Berks.

implies, a lightweight carrier fitted with a velvet pad and cleaning brush, automatically tracks parallel across the record, silently, at the same speed as the pick-up arm.

The Groov-Kleen is supplied with



cleaning brush, a spare tracking brush plus velvet pad, together with spare self-adhesive base pads.

Price of this new Bib accessory is £3.97 and can be obtained from all good audio shops. Bib HiFi Accessories, PO Box 78, Hemel Hempstead, Herts. Tel: 0442 61291.




Keep-it-kleen

Record cleaners tend to follow much the same lines these days, with the designs based loosely on the pick-up arm. In an endeavour to get away from this standard design, Bib have introduced a new parallel tracking record cleaner, called the Groov-Kleen 101.

As the name of this new cleaner

PW TECHNICAL CROSS PUZZLE No. 18

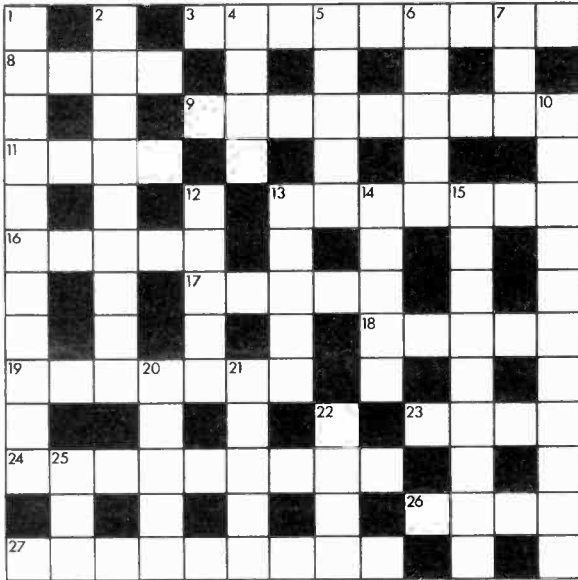

ACROSS

- 3 Only one part of the set (9)
- 8 A circuit-breaker misses a turn on it? (4)
- 9 Type of receiver for dance or brass enthusiasts? (9)
- 11 Answer distortion pique out east? (4)
- 13 Repro blemish that needs solving inside? (7)
- 16 Choose to add Ron to the energetic unit? (5)
- 17 Turn in on cell starter for lightweight set? (5)
- 18 Does without a diode use to say goodbye? (5)
- 19 Lacking outside interference in pastoral areas (7)
- 23 Neat oscillator with a heat generator? (4)
- 24 Microphone with an illegal bar? (9)
- 26 Only a saint understands this circuit! (4)
- 27 It gives you a measure of power (9)

DOWN

- 1 How often are they very high? (11)
- 2 Harshness in the reception area? (9)
- 4 The load we are carrying? (4)
- 5 Oriental in part assembly for Dad? (5)
- 6 Not a shilling Scottish audio for an Indian? (5)
- 7 Two-way system for a dedicated lady? (3)
- 10 Equipment said to make you old-fashioned anon? (11)
- 12 Tax for a broken coral circuit? (5)
- 13 Fear copper casing of Ian's rectifier? (5)
- 14 A lot of water from one A.C. vibrator? (5)
- 15 Live modulator at hand endlessly in a big vessel (9)
- 20 Swapped tales of miniaturization? (5)
- 21 Mrs Forsyte in the wire network? (5)
- 22 Coast-to-coast hook-up excludes it? (4)
- 25 He's no ham! (3)

**FOR AMUSEMENT ONLY
ANSWERS NEXT MONTH**

HERE IT IS!

● Your first Info-Card, presented free this month, is designed to be used flat, or folded as shown here.




● When folded it fits into almost any pocket thus providing a readily accessible source of information when buying resistors and capacitors. Check the wattage rating of resistors by comparing them with the full size drawings.



● Do you wonder what nanofarad or nF means? It's all explained on the PW Info-Card for Capacitors and Resistors.

Our **PW** 
'SPRING COLLECTION'

**IN NEXT MONTH'S
 PRACTICAL
 WIRELESS**

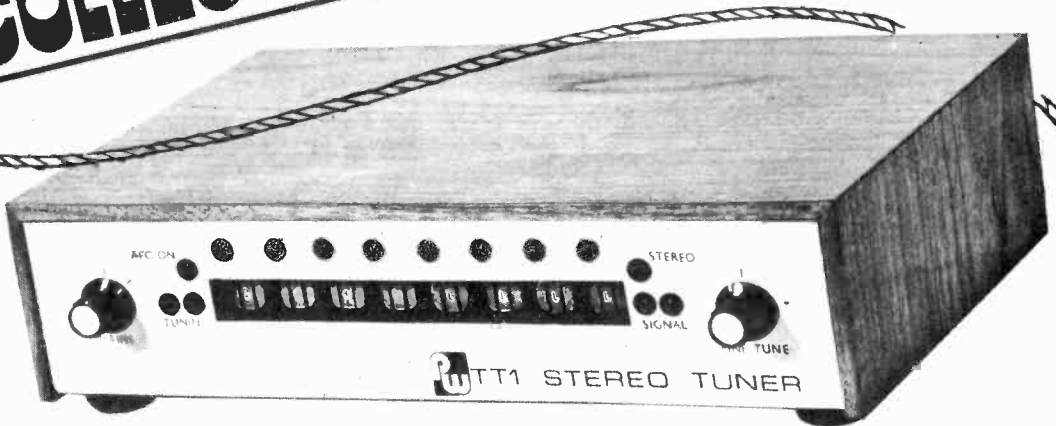

**FM
 STEREO TOUCH TUNER
 (PART 2)**

If Part 1 of this project on page 940 has excited your interest then make sure that you order the April issue which will contain details of the remaining PCB's plus assembly and alignment information.



**SMOKE
 SENSOR
 ALARM**

TUG-O-WAR




It's usually a game reserved solely for those muscular, hairy he-men, but now you ordinary mortals have a chance to take part in PW's latest electronic game—Tug 'O' War.

This project incorporates a sensor unit sensitive to many different gases and to smoke. A sensitivity control sets the level at which the audio alarm is triggered. Can be run from a 12 volt battery or the mains.

**PLUS ALL THE
 REGULAR FEATURES**

**ON SALE IN
 MARCH**

WHILST touch selection of preset stations is not uncommon on modern TV sets, such a method of tuning has yet to make an impact in the FM tuner market. The tuner to be described is therefore unusual in that it possesses just this feature. Any one of eight pre-tuned stations may be selected simply by touching the appropriate "button" on the front panel. The tuner also has stereo defeat, mute and automatic frequency control functions and the required combination of these is set up for each station by a pre-arrangement of diodes inserted in two dual-in-line sockets. Thus when a station is

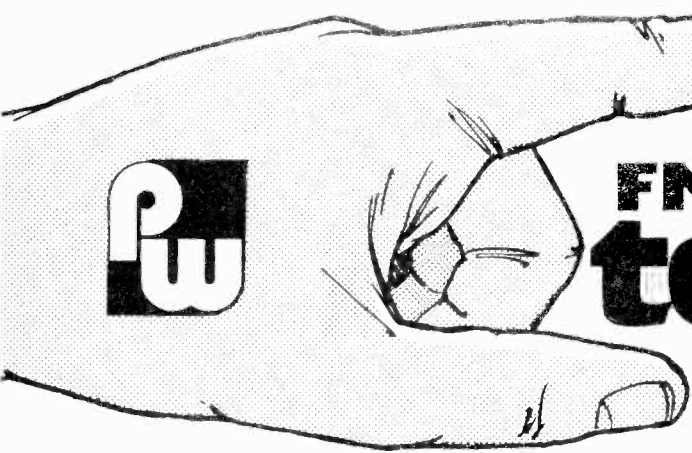

FM STEREO touch tuner

selected, the desired associated set of functions is also switched in.

The tuner itself makes use of fairly orthodox circuitry, using for the most part readily available integrated circuits and a Mullard tunerhead. Light emitting diodes are used to give indications of the station selected, tuning accuracy and signal strength, the presence of a stereo transmission and whether the AFC circuitry is operative or not.

Fig. 1 shows the power supply, which uses two 723 IC regulators. The main power supply rail should be set to about 12V. The tuner will work with anything between about 9 and 14V, but for a variety of reasons, the figure quoted is the most suitable. When a strong signal is being received, and consequently several LEDs are on, current consumption rises to about 200mA; under no-signal conditions it is only 70mA. The tuning voltage is obtained from a separate regulator, IC2. The touch selection ICs require a tuning supply at least 2V higher than the main voltage, and a value of about 17.5V is chosen. Both supplies include current limiting protection and the main power supply uses a power transistor, Tr1,

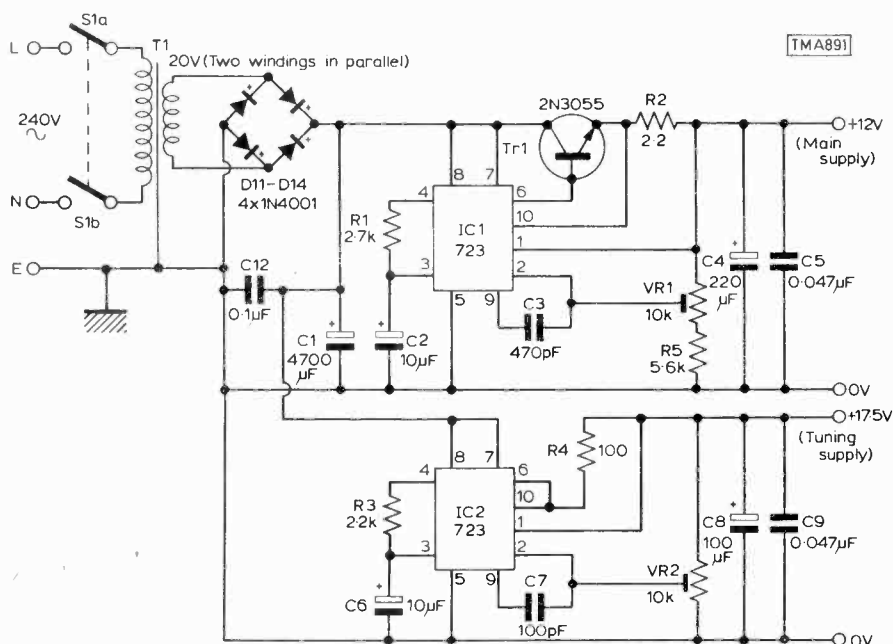


Fig. 1: The power supply section of the tuner provides two regulated voltages, one for the tuning circuitry only and the other for the remainder of the tuner requirements.

Fig. 2: Circuit of the tuner proper comprising the tunerhead, IF amplifier IC3, demodulator IC4, stereo decoder IC5 and the audio output filter.



er

Part 1 FRANCIS HOW (B.A. Cantab)

to dissipate the heat generated in dropping the voltage.


TUNER-IF-AFC

The circuitry for the radio part of the tuner is shown in Fig. 2. The tunerhead is a Mullard LP1186 module which is prealigned and provides a partially filtered IF output of 10.7MHz. This avoids one of the

most difficult problems of FM tuner construction, namely that of designing a good, trouble-free RF amplifier and frequency changer. IC3 is an IF amplifier designed particularly for use with ceramic filters (CF1 and CF2) in the configuration shown, having suitable matching impedances of 330Ω. It has two outputs of differing levels, and here it is quite sufficient to use the lower one (pin 7). The device has a useful additional feature in that pin 6 provides a stabilised DC voltage of 7.8V suitable for driving the tunerhead.

In the prototype CFSA10.7 ceramic filters were used; if however it is intended to use the tuner for long range reception where it may be rather trying to separate stations less than about 300kHz apart it may be worthwhile paying a little more for Vernitron FM4 filters. These have a better out-of-band performance and will make the receiver less susceptible to heterodyning of adjacent station signals (which have leaked through the system) with any stereo pilot tones present, producing annoying chirping in the output.

The well-known CA3089E (IC4) is employed to demodulate the filtered IF signal and a single-tuned detector coil (L2) simplifies alignment of this stage. The IC provides an AFC voltage on pin 7. When the AFC is switched on this voltage is fed via reed relay contact RL1 to the local oscillator in the tunerhead. When off, the oscillator is left tied only to the reference voltage on pin 10 via R52. The tuning indication voltage is also obtained from pin 7, and a signal strength indication from pin 13. The IC also includes a muting circuit which cuts off the audio output in the absence of a signal of sufficient strength. In this instance it is not possible to drive the mute logic (input on pin 5) from the internal

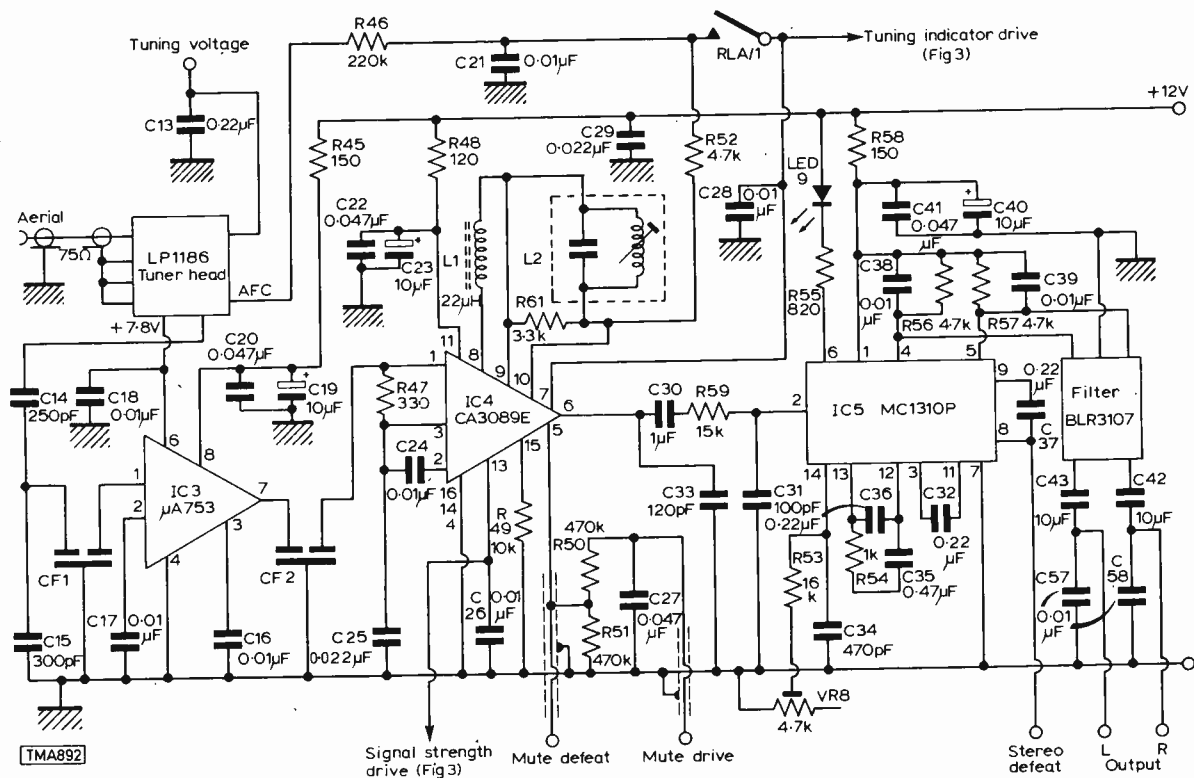

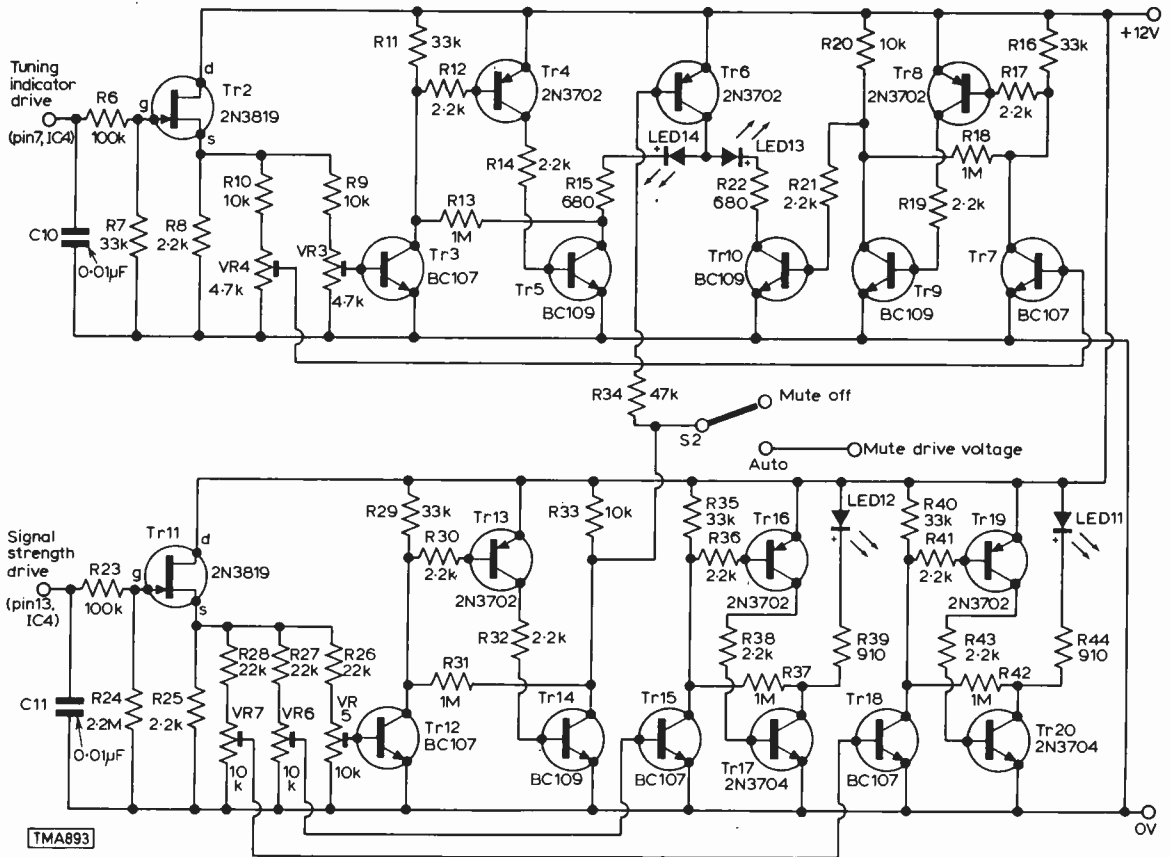


Fig. 3: Tuning indicator circuit including the LED tuning indicators is at the top with the signal strength and associated LEDs at the bottom.

mute drive voltage (pin 12) because the stability of this voltage is upset by the use of a high gain IF stage preceding IC4. Pin 5 is therefore driven by an externally derived voltage.

STEREO DECODER

The stereo output from IC4 (in its multiplexed form) is fed to the stereo decoder MC1310P (IC5) via C33, C30, R59 and C31 which produce a high frequency roll-off to help prevent leakage of adjacent station signals to the decoder (as mentioned before). This filter is not chosen for a -3dB point at 55kHz (the ideal situation) as this tends to diminish the stereo separation. More complicated circuitry would be needed to prevent the leakage and still maintain the full 53kHz bandwidth occupied by the two channels.

The decoder is a phase-locked loop system and the only adjustment required is alteration of the internal oscillator by VR8 until the device captures and demultiplexes the incoming signal. The decoding action can be defeated by earthing pin 8, and the means of doing this will be shown later. The output is fed to a DIN socket via the filter module BLR3107. This unit severely attenuates the 19kHz and 38kHz pilot and multiplex frequencies in the output. If this were not done the frequencies might cause disastrous whistling and howling when recording from the tuner by mixing with the tape head bias frequency. The presence of a stereo signal is indicated by the illumination of the beacon, LED9. Capacitors C57 and C58 are inserted to balance to audio output. The filter

should be terminated with $4.7\text{k}\Omega$ resistors but a better tonal quality was obtained with the arrangement shown. The reader may wish to alter this to suit himself or his amplifier!

TUNING INDICATORS

A pair of LEDs is used to indicate the tuning accuracy. When properly adjusted both lights will come on, and as the receiver is de-tuned one way or the other, will be extinguished depending upon the direction of de-tuning. Similarly the signal strength is indicated by a pair of LEDs. Under good signal conditions both will be on, but only one or neither for weaker signals. With zero or extremely weak signal reception the tuning LEDs will also be extinguished. Most LED tuning indicators of the type described use a long-tailed pair, but the switching of the lamps by this circuitry is not particularly sharp.

The author preferred indicators with a sharp on/off action, and to this end a voltage level detector circuit was designed with low hysteresis but a sharp transition. The basic unit is used five times in the indicator circuitry, Fig. 3. Each is fed by one of two FET buffers via a preset potentiometer (VR3-VR7) which determines the switching level of the circuit. Circuit action is fairly straightforward, the $1\text{M}\Omega$ resistors introducing a small amount of positive feedback to sharpen the switching action.

The top half of the circuit shows the tuning indicator drive. It will be seen that the second level detector contains an extra transistor, Tr10. This

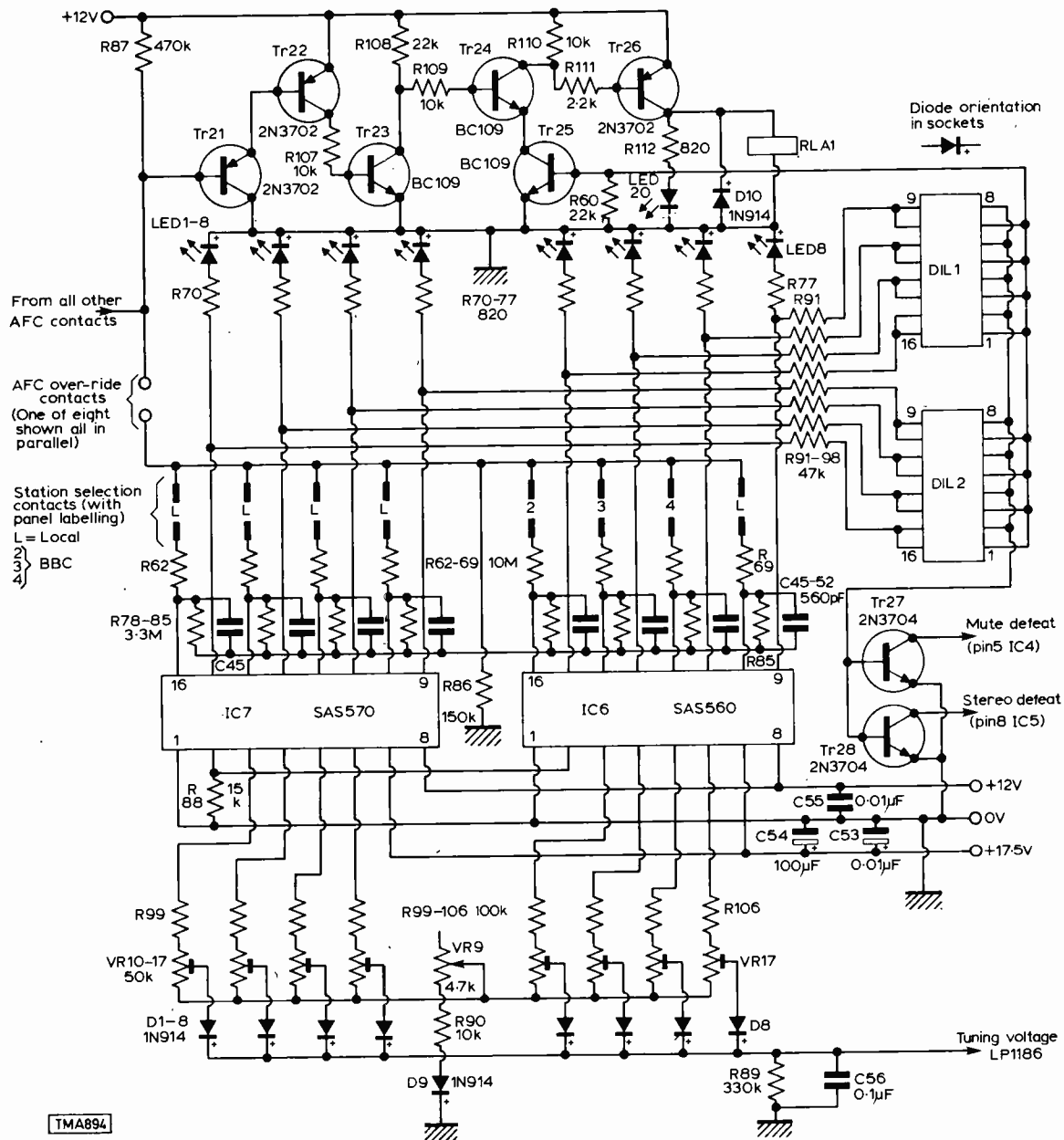


Fig. 4: All the circuits of Figs. 1, 2 and 3 are mounted on the main PCB. The eight touch buttons and the touch selection circuit shown above are mounted on two smaller boards mounted behind the front panel.

inverts the action of that circuit so that the system as a whole acts as a window voltage detector, providing indications as to whether the tuning indicator drive voltage from pin 7 on IC4 is above, below, or in the window. Only in the latter state is the tuner correctly tuned to a station. Tr6 is driven by a signal strength level detector from the bottom half of the circuit so that when that detector is switched off, Tr6 is off and both tuning LEDs are extinguished. This circuit also provides the mute drive voltage mentioned earlier. When Tr14 is on the mute drive falls to about 1V and the audio is not attenuated. S2 is fitted to the rear of the tuner chassis and may be switched either to auto (when the mute action is as described) or to "mute off" when the audio output is never attenuated, regardless of the signal

conditions. The other two level detectors in the bottom half of Fig. 3 provide the signal strength drive to LEDs 11 and 12.

TOUCH SELECTION

All the circuitry so far described is mounted on PCB1 (Figs. 5a and 5b) which lies flat in the bottom of the chassis. Two more PCBs house the touch selection circuitry and they are mounted vertically, just behind the front panel and about 1/4 in. apart. PCB3 is nearer the panel and on this are etched the eight touch "buttons", PCB2, behind PCB3, houses all the circuitry shown in Fig. 4, namely the touch selection ICs, the tuning presets and the AFC over-ride circuitry.


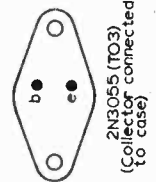
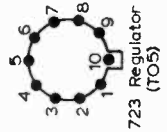
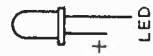
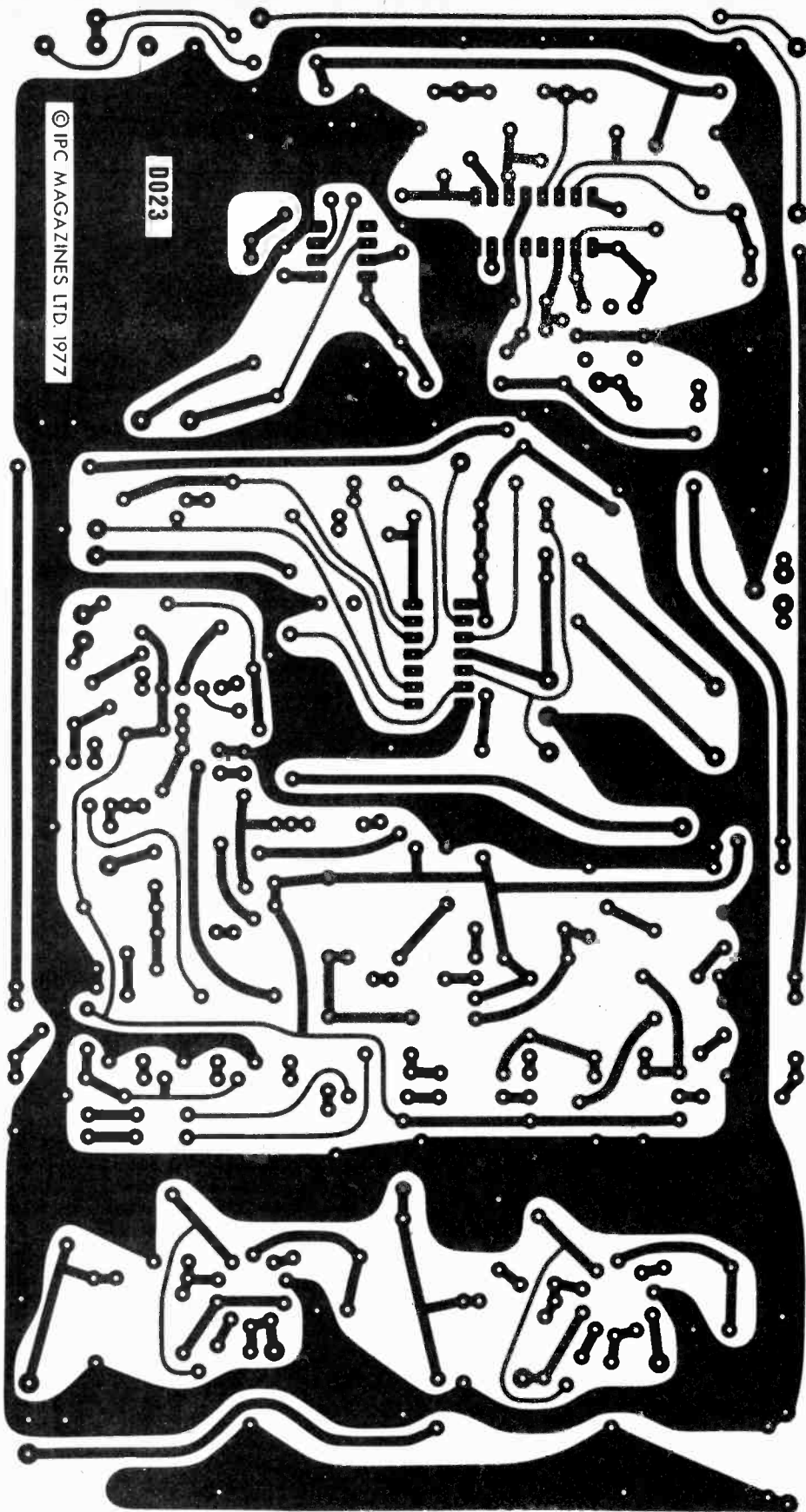


Fig. 5a: The foil layout for the main board PCB1 is shown here full size together with the leadout identification for the transistors, voltage regulators and LEDs.

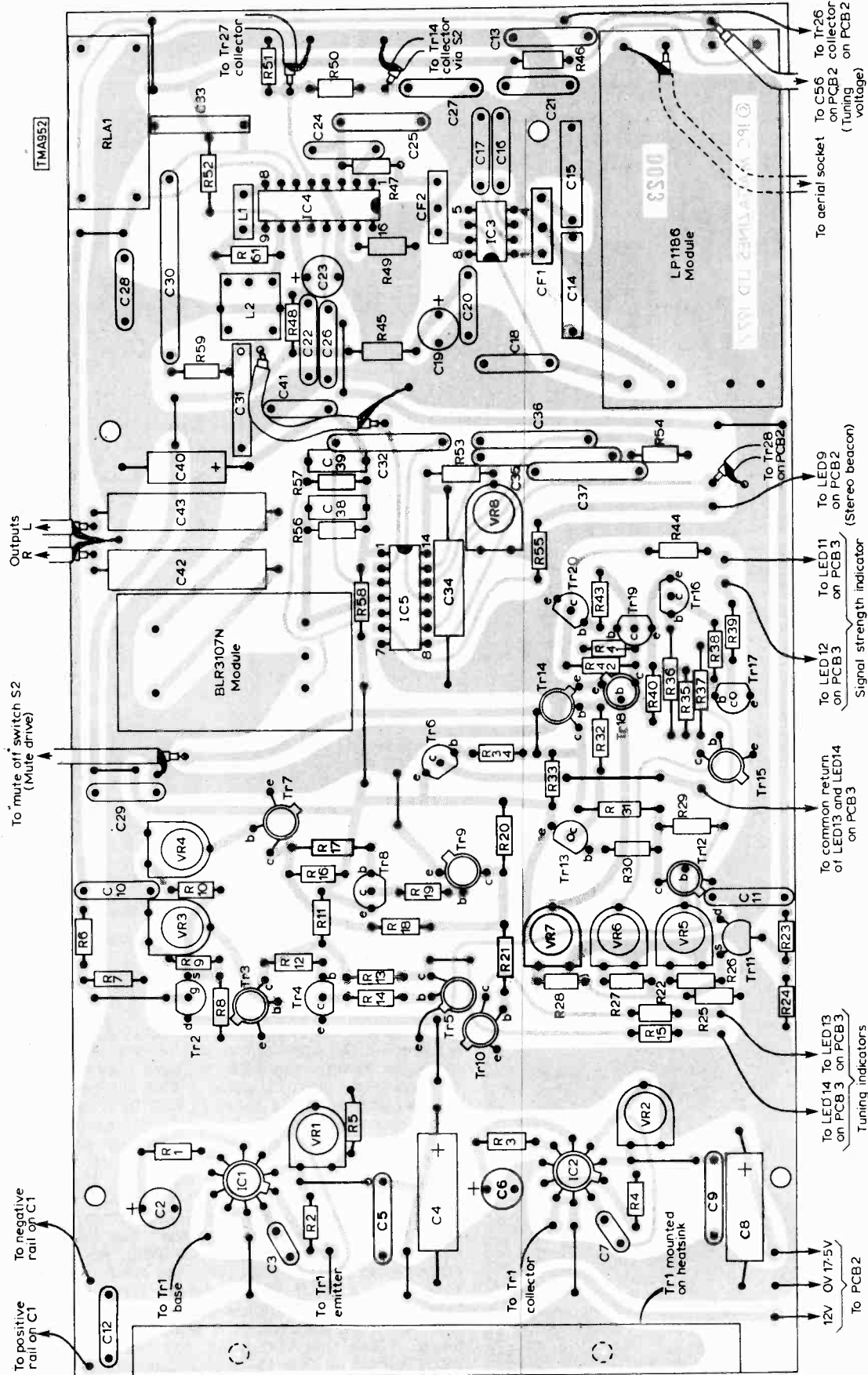

ling this PCB. Care must be taken if using a reed relay other than the one shown to ensure that the contacts of the relay and the operating coil connections go to the correct points on the PCB.

Fig. 5b: Component layout on top of the main PCB. Details of the Tr1 heatsink and reed relay assembly will be shown next month. The IF filters CF1 and CF2 may be mounted either way round. Reference to the photograph of the tuner on page 947 may be helpful when assembling this PCB.

★ components list

Resistors

R1 2.7kΩ	R27 22kΩ	R53 16kΩ
R2 2.2Ω(½W)	R28 22kΩ	R54 1kΩ
R3 2.2kΩ	R29 33kΩ	R55 820Ω
R4 100Ω	R30 2.2kΩ	R56 4.7kΩ
R5 5.6kΩ	R31 1MΩ	R57 4.7kΩ
R6 100kΩ	R32 2.2kΩ	R58 150Ω
R7 33kΩ	R33 10kΩ	R59 15kΩ
R8 2.2kΩ	R34 47kΩ	R60 22kΩ
R9 10kΩ	R35 33kΩ	R61 3.3kΩ
R10 10kΩ	R36 2.2kΩ	R62—R69 10MΩ
R11 33kΩ	R37 1MΩ	R70—R77 820Ω
R12 2.2kΩ	R38 2.2kΩ	R78—R85 3.3MΩ
R13 1MΩ	R39 910Ω	R86 150kΩ
R14 2.2kΩ	R40 33kΩ	R87 470kΩ
R15 680Ω	R41 2.2kΩ	R88 15kΩ
R16 33kΩ	R42 1MΩ	R89 330kΩ
R17 2.2kΩ	R43 2.2kΩ	R90 10kΩ
R18 1MΩ	R44 910Ω	R91—R98 47kΩ
R19 2.2kΩ	R45 150Ω	R99—R106 100kΩ
R20 10kΩ	R46 220kΩ	(2%)
R21 2.2kΩ	R47 330Ω	R107 10kΩ
R22 680Ω	R48 120Ω	R108 22kΩ
R23 100kΩ	R49 10kΩ	R109 10kΩ
R24 2.2MΩ	R50 470kΩ	R110 10kΩ
R25 2.2kΩ	R51 470kΩ	R111 2.2kΩ
R26 22kΩ	R52 4.7kΩ	R112 820Ω

All resistors ½W 5% carbon except where indicated otherwise.

VR1, VR2 10kΩ pre-set	VR9 4.7kΩ lin. carbon pot.
VR3, VR4 4.7kΩ pre-set	VR10—VR17 20-turn cermet trimpots all 50kΩ.
VR5—VR7 10kΩ pre-set	
VR8 4.7kΩ pre-set	Presets are miniature type, horizontal mounting.

Capacitors

C1 4700μF 40V	C27 0.047μF*
C2 10μF 25V	C28 0.01μF*
C3 470pF ceramic plate	C29 0.022μF*
C4 220μF 25V	C30 1μF*
C5 0.047μF*	C31 100pF mica
C6 10μF 25V	C32 0.22μF*
C7 100pF ceramic plate	C33 120pF mica
C8 100μF 25V	C34 470pF polystyrene
C9 0.047μF*	C35 0.47μF*
C10 0.01μF*	C36 0.22μF*
C11 0.01μF*	C37 0.22μF*
C12 0.1μF*	C38 0.01μF*
C13 0.22μF*	C39 0.01μF*
C14 250pF mica	C40 10μF 25V (axial leads)
C15 300pF mica	C41 0.047μF*
C16 0.01μF*	C42 10μF non-polarised 25V
C17 0.01μF*	C43 10μF non-polarised 25V
C18 0.01μF*	C45—C52 560pF ceramic plate
C19 10μF 25V	C53 0.01μF*
C20 0.047μF*	C54 100μF 25V
C21 0.01μF*	C55 0.01μF*
C22 0.047μF*	C56 0.1μF*
C23 10μF 25V	C57 0.01μF*
C24 0.01μF*	C58 0.01F*
C25 0.022μF*	
C26 0.01μF*	

* C280 polyester. C44 is omitted

A set of three PCB's can be obtained from the PW Readers PCB Service, see ad. on page 956. Semiconductors are available from Chromasonic Electronics, A Marshall Ltd., Watford Electronics, etc.


Semiconductors

IC1 } 723 regulators	Tr15 BC107
IC2 } (TO5 can)	Tr16 2N3702
IC3 μA753	Tr17 2N3704
IC4 CA3089E	Tr18 BC107
IC5 MC1310P	Tr19 2N3702
IC6 SAS560	Tr20 2N3704
IC7 SAS570	Tr21 2N3702
	Tr22 2N3702
Tr1 2N3055	Tr23 BC109
Tr2 2N3819	Tr24 BC109
Tr3 BC107	Tr25 BC109
Tr4 2N3702	Tr26 2N3702
Tr5 BC109	Tr27 2N3704
Tr6 2N3702	Tr28 2N3704
Tr7 BC107	
Tr8 2N3702	
Tr9 BC109	D1 to D10 1N914
Tr10 BC109	D11 to D14 1N4001
Tr11 2N3819	
Tr12 BC107	LED1 to LED14 (GP, 0.2" red, with clips)
Tr13 2N3702	Diodes for D1L
Tr14 BC109	Sockets:—1N914's

Miscellaneous

Tunerhead, (Mullard LP1186).	S2, Switch, SP on-off, miniature slide.
L1, 22μH choke (Ambit)	Coaxial socket.
L2, 10.7MHz tuned circuit type KACSK-586HM (Ambit)	DIN socket, 5-pin 180°.
RLA Relay, reed type miniature, 12V 1kΩ, normally open.	Aluminium sheet, 18SWG
Pilot filter, type BLR-3107 (Ambit).	300 x 180mm (11½ x 7¼in.)
CF1, CF2, IF Filters CFSA10.7 (Ambit) specify colour code as 'blank', or Vernitron FM4 (Home Radio).	300 x 90mm (11½ x 3½in.)
T1, mains transformer 240V/0.20V + 0.20V 150mA (6VA). (Doram 980-704).	Mounting clip, vertical, for C1.
S1, Switch, DP mains on-off, rotary.	Mains cable and grommet.
	Plywood and veneer for sleeve.
	Rubber feet, 4 off.
	Panel knobs, 2 off.
	Angle brackets for sleeve, 6 off.
	D1L1, D1L2 16-pin IC sockets.

Construction of the touch selection unit is simplified by the use of two ICs, SAS560 and SAS570, Fig. 4, which are purpose-built for this type of application. They have four high impedance inputs and provide the same number of tuning voltage and LED drive outputs. Any one station is selected by placing a finger on the appropriate pair of contacts, whereupon the tuning and LED voltages appear at the corresponding pins. By using a high tuning voltage (17.5V) and dropping resistors R99 to R106, a fine tune control VR9 on the front panel can be incorporated so that it gives approximately the same range of adjustment at the extremes of the FM broadcast band. Diodes D1 to D8 ensure that those tuning presets (VR10 to VR17) not being fed with the tuning supply voltage are isolated from the one which is. Each electronic "button" has three contacts; one is an earth link (via R86), one is connected to an input on IC6 or IC7 and one is connected to the base of Tr21. This transistor forms the input to a circuit which switches out the AFC (assuming it is on) when the contact is bridged to earth by a finger. When the AFC is on, the tuning indicator LEDs remain on over the whole range for which the

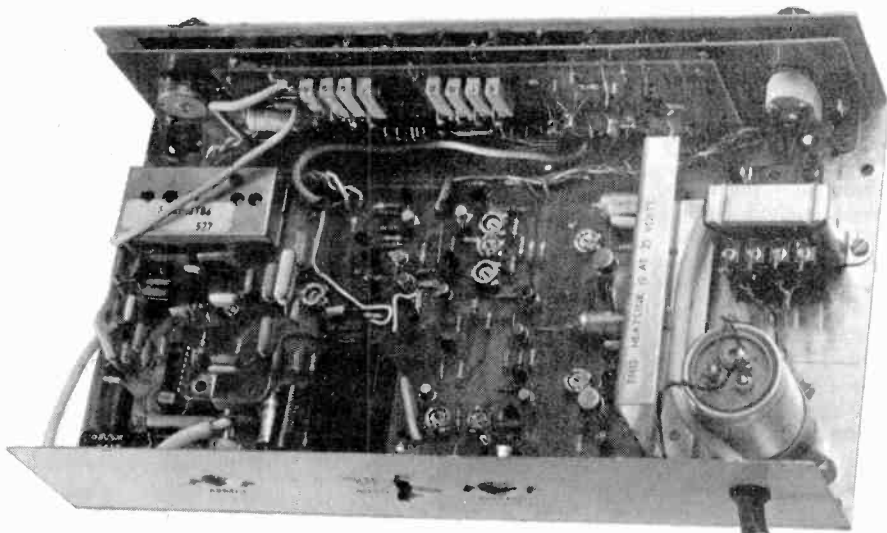

General view inside the finished Touch Tuner. The two PCBs behind the panel carry the touch buttons and selection circuits. The tunerhead is at top left with the audio output filter at bottom centre. At the right is the Tr1 heatsink, mains transformer and smoothing capacitor.

COLLATED COMPONENTS LIST

Resistors $\frac{1}{4}$ W 5% carbon, ex 2-2 Ω

2-2 Ω $\frac{1}{4}$ W	1	2-7k Ω	1	100k Ω 2%	8
100 Ω	1	3-3k Ω	1	100k Ω	2
120 Ω	1	4-7k Ω	3	150k Ω	1
150 Ω	2	5-6k Ω	1	220k Ω	1
330 Ω	1	10k Ω	9	330k Ω	1
680 Ω	2	15k Ω	2	470k Ω	3
820 Ω	10	16k Ω	1	1M Ω	5
910 Ω	2	22k Ω	5	2-2M Ω	1
1k Ω	1	33k Ω	6	3-3M Ω	8
2-2k Ω	15	47k Ω	9	10M Ω	8

Pre-set pots, miniature, horiz.

4-7k Ω	3	10k Ω	5
---------------	---	--------------	---

Pot. linear carbon

4-7k Ω	1
---------------	---

Trimpot, 20 turn Cermet

50k Ω	8
--------------	---

Capacitors

Mica					
100pF	1	0-1 μ F	2		
120pF	1	0-22 μ F	4		
250pF	1	0-47 μ F	1		
300pF	1	1 μ F	1		
P'sty		Elec			
470pF	1	10 μ F 25V	5		
Ceramic		10 μ F 25V			
100pF	1	NP	2		
470pF	1	100 μ F 25V	2		
560pF	8	220 μ F 25V	1		
C280		4700 μ F 40V	1		
0-01 μ F	15				
0-022 μ F	2				
0-047 μ F	6				

Semiconductors

IC's					
723 (T05)	2	2N3819	2		
μ A753	1	BC107	5		
CA3089E	1	BC109	7		
MC1310P		LED GP 0-2" Red			
SAS560	1	wlth clip	14		
SAS570	1				
Tr's		Diodes			
2N3055	1	1N914	10+		
2N3702	9	1N4001	4		
2N3704	4				

station is pulled into tune. Thus to tune the station accurately the AFC must be temporarily defeated, and this is a convenient way of achieving it.

We now come to the two DIL sockets, Fig. 4. Conventional tuners have a row of switches on the front panel, controlling the action of such functions as the stereo defeat, the mute circuitry and the AFC. This tuner is exceptional in that the desired combination of these functions is preset for each station by the insertion of diodes in DIL1 and DIL2. Thus the desired arrangement is automatically switched in when the station is selected. So for Radio 2 (the station labelling is located between electrodes on Fig. 4) LED5 is illuminated; by connecting a diode across pins 1 and 16 on DIL 1 the AFC may be switched in for that station, providing base drive to Tr25 and to defeat the stereo and mute action a diode would be inserted across pins 2 and 15. Similarly diodes may be connected for other stations.

The mute and stereo defeat circuitry always act together since it is rare to require one without the other. Tr27 shorts pin 5 on IC4 to earth when turned on thus switching the mute circuit off, and likewise Tr28 shorts pin 8 on IC5 to earth which inhibits the decoding action of the stereo de-multiplexer IC.

It might be suggested that if tuning is all preset, there is no need for a mute circuit. However, when actually tuning, the interstation noise is very loud and best removed, in this case by the mute action. Secondly, when a station goes off the air that channel then is silent instead of producing 200mV of noise (unless of course the station is so weak that the mute had to be defeated to hear it).

IN PART 2, NEXT MONTH, WE DESCRIBE THE 'BUILD AND TEST AS-YOU-GO' PROCEDURE FOR CONSTRUCTING AND ALIGNING THE TOUCH TUNER. PLUS DETAILS OF THE BOARDS PCB2 AND PCB3 AND GENERAL ASSEMBLY INFORMATION

HOTLINES

ON RECENT DEVELOPMENTS

The melting pot

Things are hotting up in the solar energy field. Latest method is the subject of patents and looks quite ingenious. With a solar cell, sunlight is converted direct into electrical energy. In this newer approach, the sunlight is converted into electricity by chemical means.

First step is to take a solar furnace (a suitable container with a dirty great lens focussing the sun's rays into the centre of it). Into this furnace is pumped some stuff called Sulphur Trioxide—chemically educated associates tell me that it's also known as SO_3 .

The Sulphur Trioxide gets hot and absorbs heat, and as it does so it separates by a process called dissociation. By persuading the separated parts to pass through another chamber, they recombine to form Sulphur Trioxide again but in the process they give up the heat. The Sulphur Trioxide, now recombined and happy with life, is simply pumped back into the solar furnace for the next round of heat absorption and transfer.

Boom boom boom boom— SO_3 .

Ion bullets

Remember Jan's story about I²L, well I see that this new process involves a thing called ion implantation. To achieve this, the semiconductor substrate is prepared and set up inside a chamber. Then ions, tiny particles of the desired impurity, are 'fired' by an electronic machine gun at the substrate. If you were to look at the whole shooting match under a "times umpteen million" microscope, you'd see the lattice structure of the atoms in the substrate surface. And along, at great speed, would come these ions. Depending upon how you angle the substrate and thereby the lattice, will depend on whether the ions go straight into the lattice without striking any of the individual member atoms which make up this lattice, or whether the ions will collide with lattice atoms. If they do they will be slowed down and will not penetrate so far into the substrate. Thus

ion implantation is a very precise method of doping semiconductors and this process is used in the manufacture of this new I²L. Incidentally, the manufacturers are calling it "Substrate-fed logic" or Schottky I²L.

Probing power

New products are launched onto the market by their hundreds every month (some people argue that it's hundreds every week in electronics). Two which caught my eye last month might interest readers. One was a logic probe which allows one to prod round a logic circuit and find out what's happening. It's called the Catch-a-Pulse and will inform on six states; positive-going pulses, negative-going pulses, square waves, a logic one, logic nought, and no signal. Fountain-pen shaped it looked a useful device but most impressive was the price in the U.S.—just \$32.

The second device is a transistor: and what a transistor. It has the impressive name of STC9160 and the even more impressive power handling capability of 500W. This transistor is housed in a TO-3 package and is described by its manufacturer as a 50A device. It's quick, too. It will turn on in just 3.5 millionths of a second.

We've come a long way from those little "red-spot" transistors.

Small talk

If there ever was such a word as "Littlerer" it would surely apply to a new development at the research labs of a British manufacturer. Previously, I've mentioned a semiconductor technology called injection logic or I²L. What the British company has done is to adopt a significant variation of I²L with the result that the packing density—how many transistors can be got in a given size—has been increased some three times. At the latest head count they had managed to squeeze some 800 semiconductor gates into an area of 1mm x 1mm. Just get a ruler and look at one lone millimetre. Better still draw a 1mm square on a

piece of paper and then imagine 800 transistors inside that. See what I mean about "littlerer"?

Spot-on

Yet another interesting device mentioned at the Washington conference was a stable reference voltage source. This one is the brainchild of an American company and is still at the laboratory stage but it looks extremely promising. It employs a short channel MOSFET in what's called the punchthrough mode (don't even ask!) What is important is that when persuaded to supply a reference voltage at just over 3.8V, this device held the voltage stable to within $\pm 0.0005V$. Even more important, it held the voltage to within that 0.0005V over the temperature range of 25°C to 50°C.

Perhaps the government could have a whip round and purchase one for the British economy?

4-layer switch

What about getting a Thermosensor for Easter? I didn't believe it either but it cropped up at the International Electron Devices Meeting in Washington recently. It's basically a temperature-sensitive switching device and it's the handwork of a Japanese company who gave a paper on it at the conference. The theory of it is quite horrendous (I reckon a degree in Venesian physics is required to understand it) but in simple terms it is a pnpn semiconductor, a four-layer device. If it is forward biased it can then switch on at a predetermined temperature. The precise turn-on temperature is decided by the value of a solitary resistor which is wired in parallel with the emitter of the Thermosensor. The temperature switching range extends from 50°C up to 150°C.


Ginsberg

in next month's issue

TELEVISION

MARCH issue, on sale February 21st.

The "TV" TELETEXT DECODER

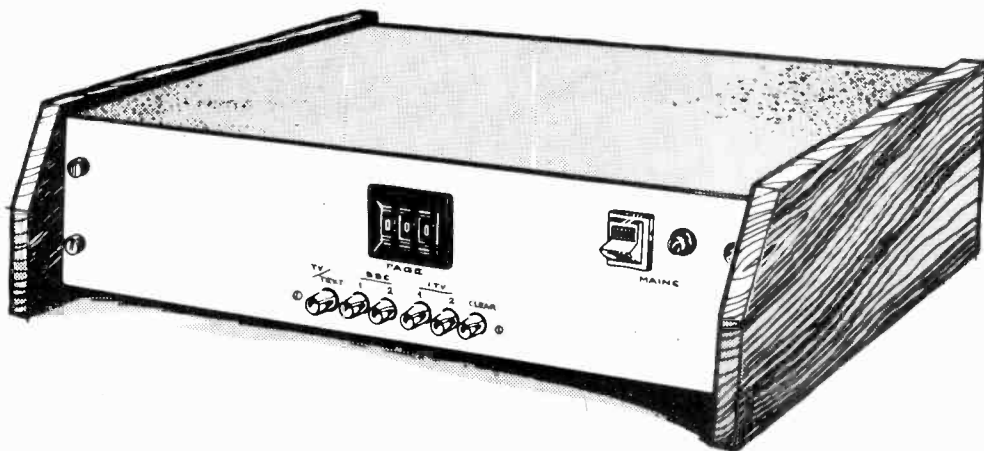


Have you seen Ceefax/Oracle yet? By building the *Television* Teletext decoder you could soon be watching these services in your own home. It's designed to work with any 625-line receiver, either monochrome or colour, and has the advantage that you don't need to modify your domestic TV set in any way – just plug the decoder's output into the aerial socket. A Teletext decoder is complex, but to make assembly easy this design uses plug-in printed boards and a mother board, while the very latest receiver techniques are used in order to simplify alignment. The unit has its own mains power supply.

**Also: SERVICING THE BEOVISION 2600/3000/3200 SERIES
FIELD TIMEBASE FAULTS ON THE RANK A823 CHASSIS
PLUS ALL THE REGULAR FEATURES**

EASYTUNE MW-LW Receiver

F.G.RAYER

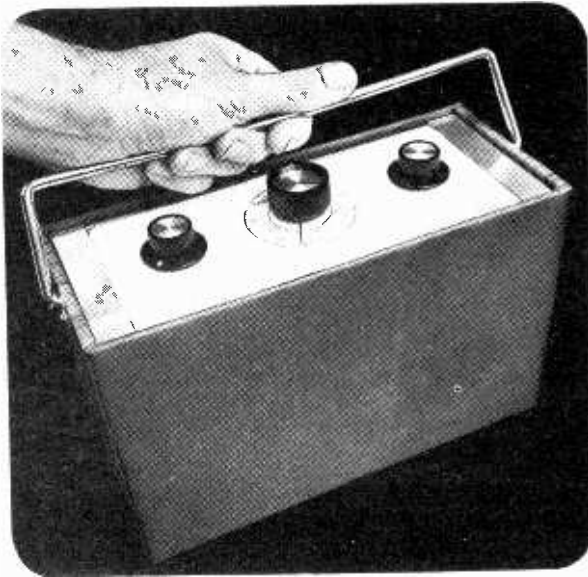

THIS receiver uses three transistors and an audio IC in a circuit which is capable of very good results. With the usual form of receiver tuning, signals at the high frequency end of the medium wave band are crowded together and tuning is critical. As an aid to operation on these frequencies high-frequency bandspread is fitted, in addition to long wave and medium wave coverage. This provides three bands, approximately as follows:

- Long Wave: 165 to 270kHz.
- Medium Wave: 550 to 1525kHz.
- Bandspread: 1475 to 1850kHz.

The receiver is not a miniaturised design which simplifies wiring and construction to some extent.

Receiver Circuit

The circuit is shown in Fig. 1 where L1 and L2 are the medium wave and long wave sections of the internal ferrite rod aerial. Base coupling to Tr1 is via L3 and a tapping on L2. Coil L4 is the oscillator coil, common to long and medium waves. For LW coverage L1 and L2 are in series, VC1 with integral trimmer TC1 being for aerial tuning. Switch S2 introduces C3 and TC4, loading the oscillator coil

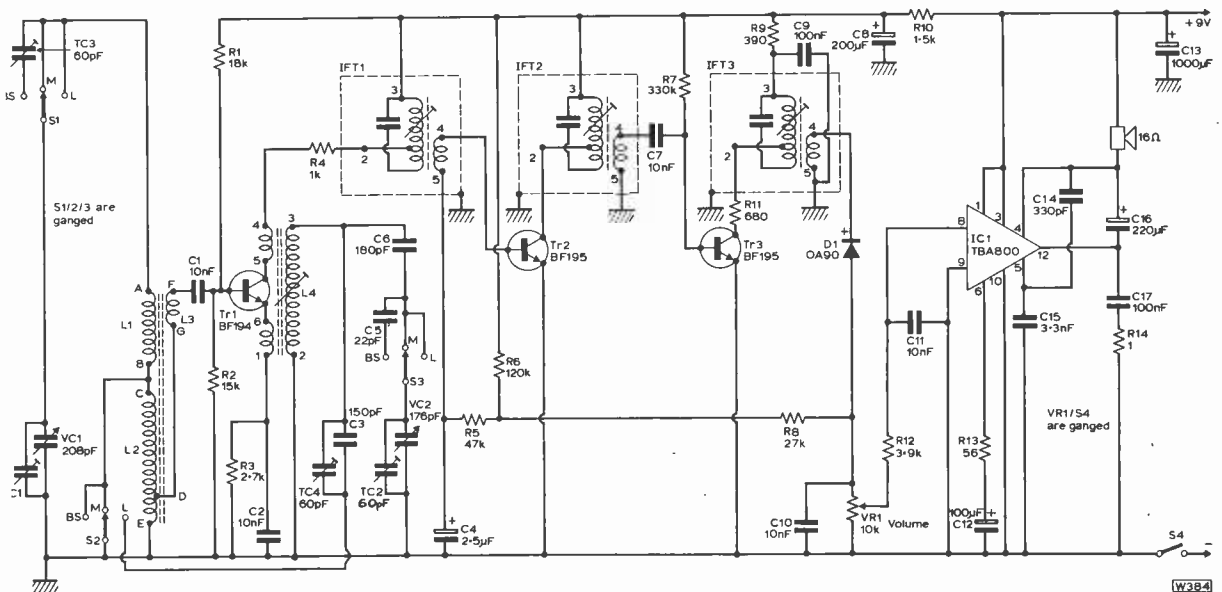


Fig. 1. Complete circuit diagram for the Easytune medium and long wave receiver. The third waveband spreads out the high frequency end of the medium wave band where congestion of stations is prevalent.

★ components list

Resistors	
R1 18k Ω	R8 27k Ω
R2 15k Ω	R9 390 Ω
R3 2.7k Ω	R10 1.5k Ω
R4 1k Ω	R11 680 Ω
R5 47k Ω	R12 3.9k Ω
R6 120k Ω	R13 56 Ω
R7 330k Ω	R14 1 Ω
All $\frac{1}{2}$ or $\frac{1}{4}$ W 5%	
VR1/S4 10k Ω log pot with switch	
Capacitors	
C1 10nF	C10 10nF
C2 10nF	C11 10nF
C3 180pF	C12 100 μ F 6V
C4 2.5 μ F	C13 100 μ F 10V
C5 22pF	C14 330pF
C6 180pF 5%	C15 3.3nF
C7 10nF	C16 220 μ F 10V
C8 200 μ F 10V	C17 100nF
C9 100nF	TC3/4 60pF trimmers
VC1/2 208/178pF, slow motion, with trimmers (Jackson 00)	
Semiconductors	
Tr1 BF194	D1 OA90
Tr2/3 BF195	IC1 TBA800
Inductances	
L1/2/3 MW/LW ferrite rod aerial (Denco FR5)	
L4 Oscillator coil (Denco TOC1)	
IFT1/2 IF transformer (Denco IFT13) IFT3 (Denco IFT14)	
Miscellaneous	
Speaker 16 Ω 3 $\frac{1}{2}$ in. dia., impedance not critical.	
Battery 9V and terminal clips. Knobs. Material for cabinet and covering. 10 x 4in. flanged plate (Home Radio, universal chassis member). Handle. Plastic feet. Two brackets, home made. S1/2/3 3-pole 3-way single waver switch	

Circuit Board

The board is approximately 127 x 70mm (5 x 2 $\frac{3}{4}$ in), Fig. 2. The first step is to drill holes for TC4, L4 and the three IFTs. Position them so that the tags will come as shown in Fig. 3. A coloured spot marks pin 4 of L4. A $\frac{3}{32}$ in drill is suitable here, with a $\frac{1}{16}$ in drill for the can tags of L4 and the IFTs. No force should be used to fit these items and if necessary holes may be adjusted to give an easy fit by employing a small file.

It is as well to leave the transistors and IC1 off until later. Underneath wiring is shown in Fig. 3. Probably the simplest way is to begin by wiring the earth line to the can tags, using 24SWG tinned copper wire. Follow by placing resistors and capacitors as in Fig. 2, then turn the board over and shape and solder the wire ends, cutting off any excess leads. Sleeving is put on leads which cross or run near each other or near joints and tags. There is plenty of space for components but reasonable care is necessary to make a sound job here.

If necessary check resistor values as they are inserted. The electrolytic capacitors must be placed with the polarity shown. If each connection and component is marked in coloured pencil as completed it is unlikely that anything will be omitted.

Semiconductors

The pins of the transistors are placed as in Fig. 3 and leads are soldered to them. Avoid lengthy heating of these joints in particular. The iron should be at its full temperature and should be applied to the cored radio grade solder, which is held on the joint. The solder should flow in a second or so, and the iron is then removed at once.

Shape the ends of D1 to reach pin 4 and R8. Be sure this component is fitted with the polarity correct. Positive on the diode is indicated by a coloured band. If this diode is reversed the AGC action is upset.

The pins of IC1 are located as in Fig. 2 and spaced to fit the 0.15in matrix of holes. Bend the heat sink fins up slightly to clear the board and C14. Only pin 1 is marked on the actual IC. These pins come close together and they are small so a little care is needed when soldering them to connections, as in Fig. 3. Unused tags must not touch other connections or joints.

Wiring

Leads can be provided by fitting lengths of thin coloured flex or by inserting Veropins, which will take leads running to the appropriate points. A lead will run from C1 to F on L3, another from C3 and C6 to sections S2 and S3 of the bandswitch and a wire will run from 2 on the oscillator coil to the frame tag of VC1/2. In the audio section, D1 negative and an earthing lead from pin 5 of IFT2 run to VR1. Resistor R12 is soldered to the rotor tag of VR1 and is wired to C11 and pin 8 of IC1. Twin leads are provided from pins 3 and 4 of IC1 to go to the loudspeaker.

All these leads can be several inches long and arranged to come from the board as in Fig. 2 so that they can be readily identified later.

for suitable coverage. This coil is tuned by VC2, TC2 being part of the ganged capacitor.


For MW reception S2 shorts out L2 and C3/TC4 are out of circuit. C6 is the oscillator coil padder. For bandspread reception, S1 places TC3 in series with VC1 and S3 places C5 in series with VC2. This results in a narrow frequency coverage for the full rotation of VC1/2. Switch S2 shorts out L2 as for ordinary MW tuning.

Silicon transistors are used for the self-oscillating mixer Tr1, and the two IF amplifiers Tr2 and Tr3. Diode D1 is the detector also providing an automatic gain control voltage for Tr2 through R8 and R5.


The required audio level is provided by the volume control VR1. The IC provides audio, driver and push-pull output stages, with diode compensation, and operates the loudspeaker directly. This audio IC has a low standing current and is economical while giving excellent volume from a 9V supply. S4 is the on/off switch incorporated in the audio gain control.

The three IF transformers are pre-tuned and there should be no particular difficulty in aligning the receiver even if no signal generator or other instrument is available.

127 x 70mm (5 x 2 3/4")

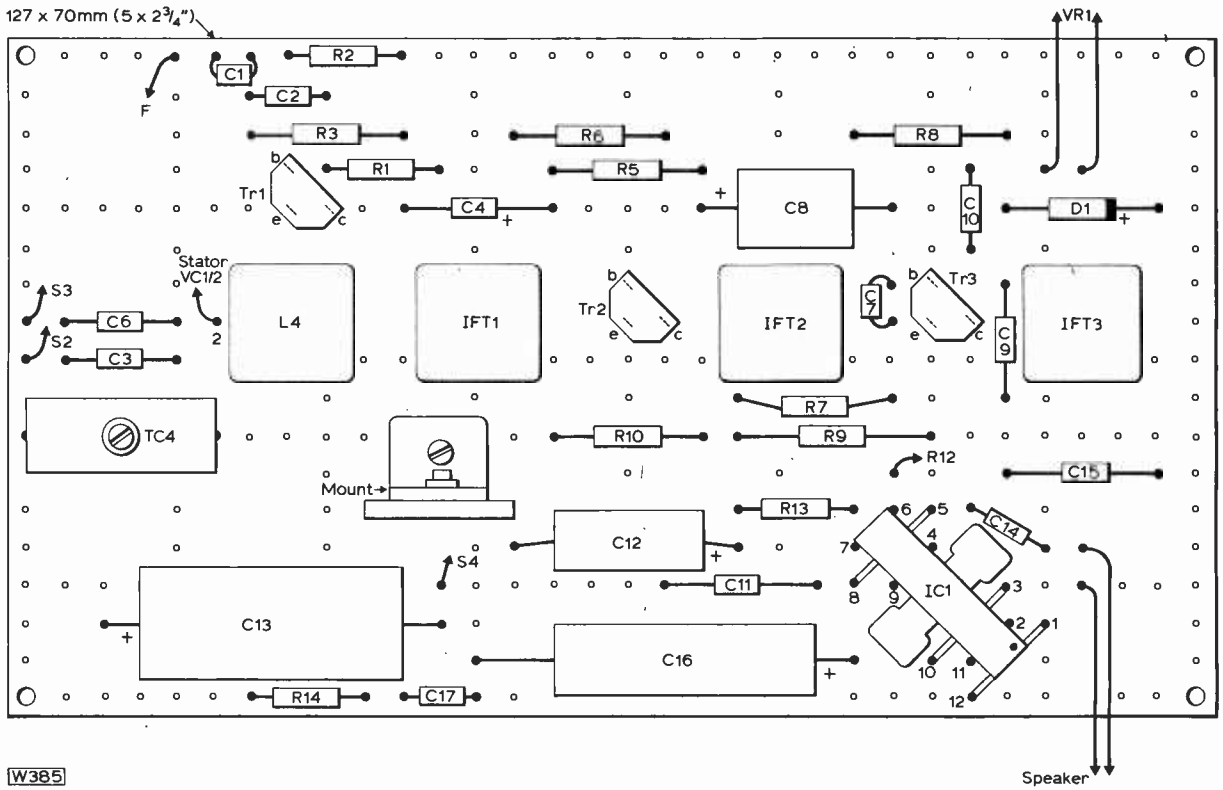


W385

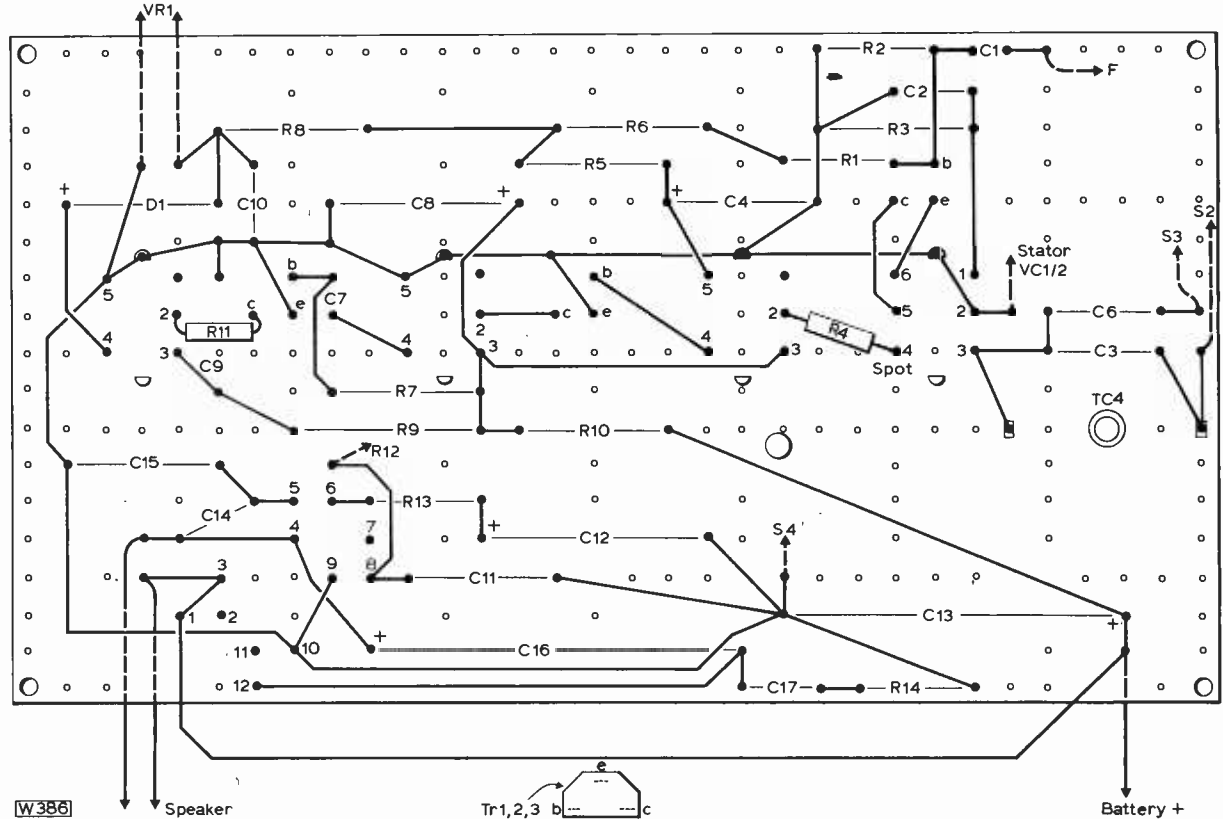

W386

Fig. 2: at the top, shows the top of the veroboard and layout of components. The board size is 127 x 70mm (5 x 2 3/4 in.). Fig. 3: at the bottom, illustrates the wiring necessary under the board. In many cases the component lead is sufficiently long to make a connection.

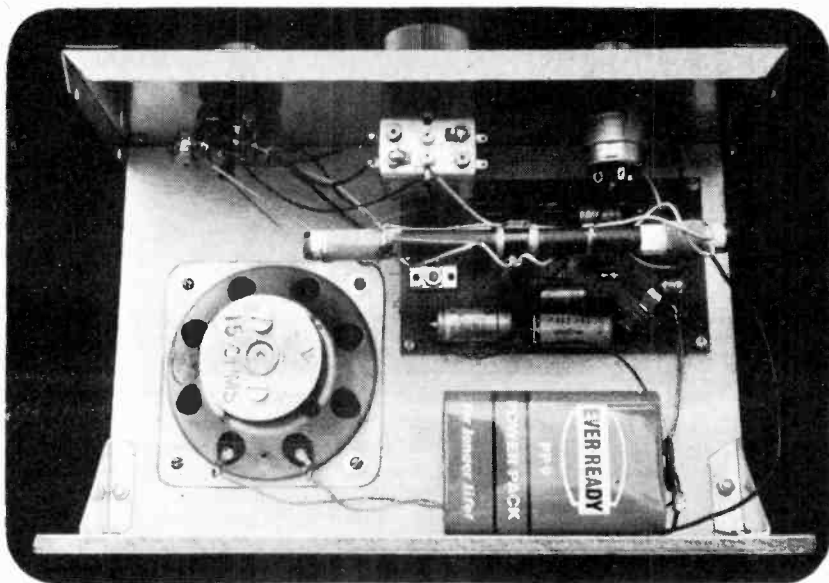

General view of the finished receiver. The details of the bracket holding the ferrite rod aerial can be seen in Fig. 2.

Sub-assembly

This assembly allows the receiver to be made up as a complete working unit while all connections and the underside of the circuit board are easily reached. Cut a piece of 6mm plywood 250 x 160mm ($9\frac{7}{8}$ x $6\frac{1}{4}$ in). At the right, 63mm ($2\frac{1}{2}$ in) from the right edge and 63mm ($2\frac{1}{2}$ in) from the bottom, mark a centre, and draw a 75mm (3in) diameter circle. Cut out this part to take the speaker. If a speaker of different size is used, cut this aperture to suit the dimensions of its cone.

Position the circuit board approximately 12mm ($\frac{1}{2}$ in) from the left edge and a similar distance from the top of the plywood. Mark round the circuit board with a pencil. This part is now cut out, but corners approximately 16mm ($\frac{5}{8}$ x $\frac{5}{8}$ in) and of tri-

angled brackets. This acts as a shelf for the battery and allows the receiver to stand upright when out of its case, or to rest on its back or either end. The top panel is a 254 x 100mm (10 x 4in) flanged "universal chassis member." Using a centre-line, punch a 16mm ($\frac{5}{8}$ in) hole in the middle for VC1/2. At 73mm ($2\frac{7}{8}$ in) distance from this centre, punch holes for the bandswitch and VR1.

Place the top of the plywood inside the front flange and drill flange and wood for three counter-sunk 6BA bolts which will secure these parts together. VC1/2 is fitted by means of three counter-sunk 4BA bolts. This component is set back about 10mm ($\frac{3}{8}$ in) from the panel to bring the tuning knob lower (the spindle cannot be cut short due to the integral reduction drive). This requires spacers, or

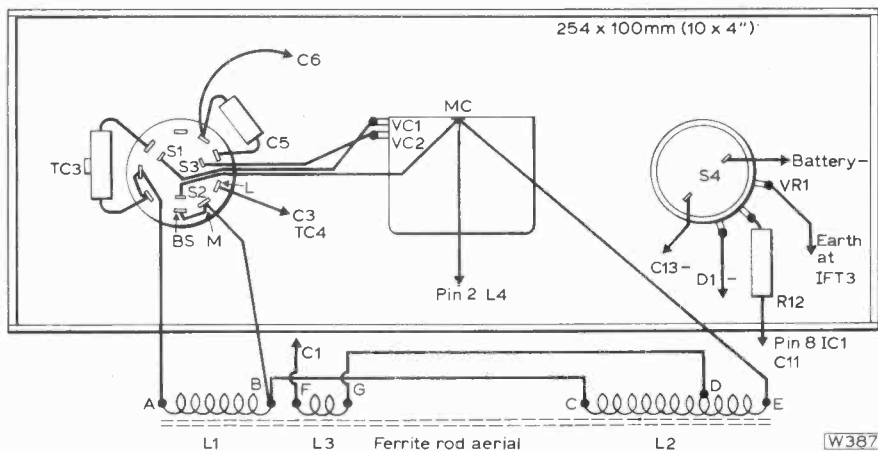


Fig. 4: Arrangement of the components on the front panel and wiring between the range switch and the ferrite rod aerial, and between the volume control and the board.

angular shape are left so that the circuit board can be secured by four woodscrews driven through the holes in Fig. 2, and into the wood. The circuit board is fitted with the IFTs towards the top and IFT3 at the edge. It is then possible to reach all connections, etc. under the board if this should prove to be necessary.

A piece of 6mm plywood 250 x 95mm ($9\frac{7}{8}$ x $3\frac{3}{4}$ in) is fitted to the bottom of the assembly by two right-

extra nuts, locked against the panel and capacitor. The ends of the bolts must on no account project beyond the thickness of the front capacitor plate.

Fig. 4 shows the panel and connections to the circuit board can now be fitted. The trimmers TC1 and TC2 are provided on the ganged capacitor, so are not shown separately. TC3 is soldered directly to the tags of S1 as shown. Capacitor C5 is mounted on S3.

Ferrite Aerial

The aerial can be mounted by cutting a strip of paxolin about 75mm (3in) long and securing it by a small bracket, Fig. 2. The rod is then bound to the top of the paxolin. An alternative method is to cut a piece of hardwood or insulating material about 63mm (2½in) long from material about 12mm (½in) wide and 9mm (⅜in) thick. This can be tapped for a bolt to secure it to the board or drilled for a self-tapping screw. At the top, a 'V' is filed to take the rod which is held with adhesive and thread passed round the rod and through a hole in the mount.

Coils L1 and L3 are supplied wound on one former. Place this so that L3 is towards the middle of the rod, Fig. 4. Connect the beginning of L1, lead A, to S1 and wire F of L3 to C1. L2 is the largest winding, on a separate former. The tapping D is electrically near the end E. This can be seen by examination. Place L2 on the rod in such a way that the direction of rotation of the winding A to B is followed on by C to E. If this is not done LW alignment is impossible and L2 must be taken off the rod and placed the other way.

Point G of L3 is then wired to tapping D. Points B and C are connected together and to S2. Point E of L2 goes to the frame, MC, of VC1/2. These leads should be long enough to allow a little movement of the coils on the rod. Connections are best made with quite thin wire and sleeving is put on all the leads.

IF Alignment

The IFTs are aligned by the maker and it is better not to touch these until proper results are obtained. They may then be adjusted a little as necessary, using a proper trimming tool, such as that available from the maker. A wedge-shaped blade is likely to break the cores.

To adjust the IFTs tune in a weak signal, with VR1 turned up near maximum, and rotate each core for best results. Only a small movement should be necessary. If equipment is available a signal generator may be used, and output observed with an output meter. This allows more precise adjustment than does aligning the IFTs by ear. But despite this, perfectly satisfactory results should be obtainable without instruments. Once the IFTs are aligned, leave them alone, as they do not need touching when trimming the aerial and oscillator circuits.

RF Alignment

Trimmers TC1 and TC2 should be very slightly unscrewed. Switch to MW. Check that the medium wave coverage is from approximately 550kHz to 1525kHz. If there is much error at the LF end of the band rotate the core of L4 to correct this. Should there be considerable error at the high frequency end of the band, adjust TC2 as necessary. Subsequent adjustments depends on the positions of L4 core and trimmer TC2. This means that if any change is made to the settings of these, later adjustments will be upset. So the correct positions for L4 core and TC2 must be found first, as shown by correct MW coverage, with the bandswitch in its central position.

Tune in a weak transmission near the LF end of



the MW band and move L1 on the rod for best volume. Then tune to a signal around 1500kHz and adjust TC1 for best volume. As these adjustments influence each other, repeat them a few times.

Switch to LW, set VC1/2 half closed and rotate TC4 until the 200kHz BBC Radio 2 is heard. Then tune to a signal near the LF end of this band, one or more foreign stations should be audible and move L2 on the rod for best results.

If these adjustments are difficult to achieve check wiring to L2 and its "sense" upon the rod, and also, if necessary, the setting of the core of L4.

Bandspread Adjustment

A signal should be tuned in around 1500kHz, VC1/2 nearly two-thirds closed, and TC3 should be rotated for best results. All the trimming adjustments can, of course, be made with the aid of a signal generator. When using actual transmissions for this purpose, avoid very strong signals. These will operate the ACG system and its action will mask adjustments so that a critical setting is not found easily. Distant signals will be subjected to

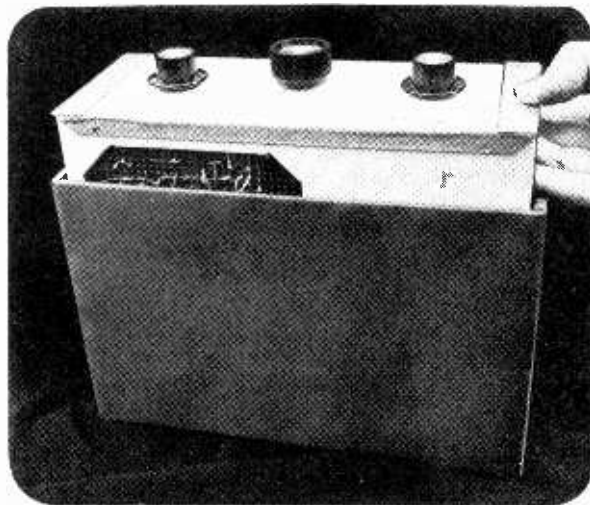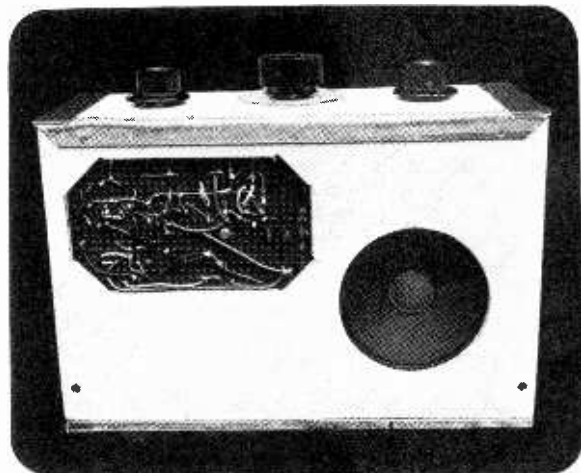

The top photograph shows the cutout in the base which enables the circuit to be worked on by merely pulling the set out of the cabinet. In the view at the bottom the set is lowered into its cabinet, when the speaker should align with the hole in the cabinet, shown in Fig. 5.

fading, especially on the higher frequencies, and this may make adjustment difficult. So choose a local transmission and carefully orientate the receiver for a low level of signal. Check again through each band to get best results.


Cabinet

Construction of the cabinet is shown in Fig. 5. The receiver panel or top is assumed to be 254 x 100mm (10 x 4in) so it is essential that the cabinet will clear this inside. Bearing this in mind the dimensions given are correct. The sides are of plywood while the front and back are hardboard. Glass-paper all meeting surfaces smooth and wipe away all dust. The sides are then secured to the bottom, using adhesive and a few panel pins. A 100mm (4in) diameter opening is cut in the front matching the

to cover the sides and bottom. This is 100mm (4in) wide and overlaps into the top of the case. Four small feet are screwed on the bottom. The handle was pivoted in two small flat plates, screwed to the sides of the case. A flexible handle could be made from a length of material, folded and sewn, to match the case.

The receiver panel can be provided with a card scale, calibrated in frequencies with the aid of a signal generator, or with station names marked. A straight wire can be soldered to the spindle of VC1/2 or a dial can be cut from Perspex and fitted to the spindle.

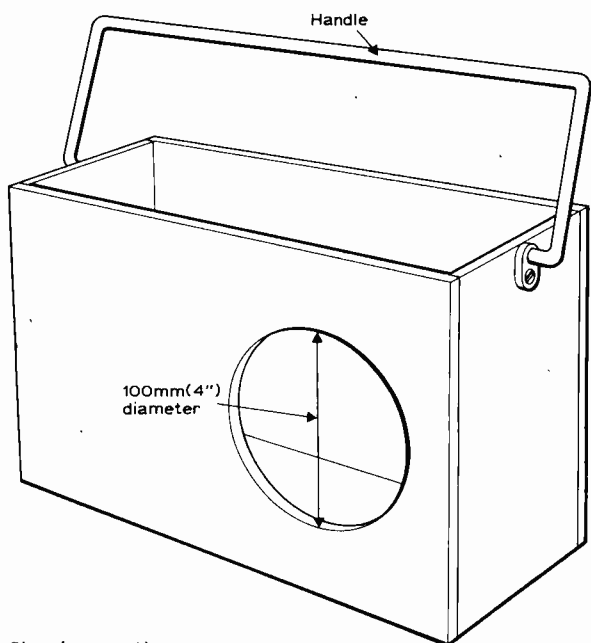The bare aluminium was covered with self-adhesive material and contrasting strips cemented on at each end. There is a great deal of latitude, here, for individual finishes to be used.



Sides (plywood)
178 x 105mm (7 x 4 1/8")

Front and back (hardboard)
270 x 178mm (10 5/8 x 7")

Bottom (hardboard)
257 x 105mm (10 1/8 x 4 1/8")

W388

Fig. 5: Dimensions of the cabinet and material required for its construction.

position of the speaker. The sides and bottom edges and front are smeared with adhesive, placed together and fixed with pins. The case is then turned over and the back similarly fitted. When the adhesive is dry, the exterior can be sanded.

The back and front are covered with fabric secured with adhesive along the bottom of the case, at each end, and inside at the top, drawing the material taut. Any adhesive on the front of the case may penetrate the fabric and spoil the appearance.

Wood-grained self-adhesive material is then cut

KINDLY NOTE!

CHROMACHASE 4

December 76/January 77

Several readers have commented on the fact that the diode matrix in this project is unsatisfactory and many of them have suggested solutions. Although each solution appears to solve the problem each varies from the others.

However, common to all is the correction to D8. As it is used in the article it prevents any operation except Clock Reverse. The removal of this diode will enable the unit to function in all modes except Auto.

We are trying all the readers' recommendations as well as some of our own and will publish our findings as soon as they are clear.

OSCILLOSCOPE CALIBRATOR

January 77

In the components list R12 should be 100kΩ and not 100Ω.

PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING TO
ADVERTISEMENTS

PCB SERVICE FOR READERS

AM D3

All boards, except SRBP, are glassfibre, drilled and roller-tinned

To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es



Issue	Project	Ref	Price P/P	
Sep 75	Electronic Clock (set of three)	DN0795/6/7	2·40+15	<input type="checkbox"/>
Dec 75	Random Number Selector	DN0793A	0·98+12	<input type="checkbox"/>
Dec 75	Sound-To-Light Display	DN0798	1·15+12	<input type="checkbox"/>
Dec 75	12V PA System	DN2/JM	0·98+12	<input type="checkbox"/>
Dec 75	Disco System, Amplifier (2 required)	each AM0421	4·40+22	<input type="checkbox"/>
Dec 75	Disco System, Light Modulator	AM0423	3·50+22	<input type="checkbox"/>
Jan 76	Music Box	SRBP DN1/JM	2·25+18	<input type="checkbox"/>
		glassfibre DN1/JM	3·00+18	<input type="checkbox"/>
Mar 76	CMOS Crystal Calibrator	AM0438	1·19+12	<input type="checkbox"/>
Apr 76	DF Receiver (set of two)	DN4/JM DN5/JM	1·92+15	<input type="checkbox"/>
Apr 76	Wobblator	AM0443	1·08+12	<input type="checkbox"/>
Apr 76	Auto. Slide Synchroniser	AM0441	2·33+15	<input type="checkbox"/>
June 76	Dig. Freq. Meter (set of 4)	4X A004	3·17+15	<input type="checkbox"/>
July 76	Transistor Tester	A002	3·08+18	<input type="checkbox"/>
July 76	Disco Preamplifier	A003	0·65+12	<input type="checkbox"/>
Aug 76	Cassette Player Power Supply	A001	0·65+12	<input type="checkbox"/>
Sep 76	Jingle Machine	A005	2·30+12	<input type="checkbox"/>
Sep 76	Capacitance Meter	A009	2·59+14	<input type="checkbox"/>
Sep 76	Octavia AF Source	A010	1·30+12	<input type="checkbox"/>
Oct 76	Jingle Machine, Mains Unit	A006	2·08+12	<input type="checkbox"/>
Oct 76	Digital Car Clock (set)	A001/2/3	2·58+12	<input type="checkbox"/>
Oct 76	Interwipe	DN8JM	0·80+12	<input type="checkbox"/>
Oct 76	Video-Writer (set)	D002/3/4/5 A007	21·44+50	<input type="checkbox"/>
Oct 76	Hazard Flasher	D005	0·76+12	<input type="checkbox"/>
Nov 76	Low Level Battery Indicator	A016	0·40+12	<input type="checkbox"/>
Nov 76	Electronic Thermostat	A017	1·30+12	<input type="checkbox"/>
Nov 76	Cirtest Probe	A018	0·48+12	<input type="checkbox"/>
Nov 76	Burglar Alarm	A019	0·50+12	<input type="checkbox"/>
Nov 76	DFM Pre-scaler PCB A015 will be added to set of four DFM boards at no extra cost.			
Dec 76	Chromachase	A021	5·70+22	<input type="checkbox"/>
Jan 77	Oscilloscope Calibrator	A023	1·25+12	<input type="checkbox"/>
Jan 77	Icelert	A020	1·45+12	<input type="checkbox"/>
Jan 77	Polyphon, motor and main boards	A025/4	7·90+20	<input type="checkbox"/>
Jan 77	Polyphon, tune disc, blank, SRBP	A008*	0·90+15	<input type="checkbox"/>
Feb 77	Transistor Checker	A026	1·18+12	<input type="checkbox"/>
Feb 77	FM Stereo Touch Tuner	D023/4/5	7·50+20	<input type="checkbox"/>

Post and packing is for one board or set of boards. Prices include VAT
Remittances with overseas orders must be sufficient to cover despatch
by sea or air mail as required.

I enclose Postal Order/Cheque ACCESS welcome.
No..... Send card number only.
for £..... made payable to READERS PCB SERVICES LTD.

NAME.....
ADDRESS.....
.....
..... Post Code

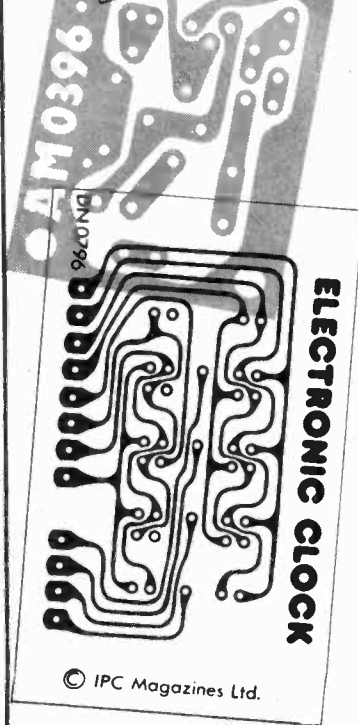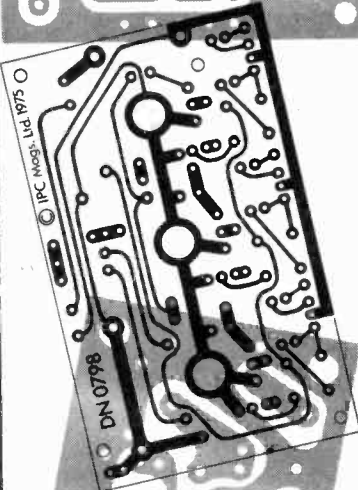
Any correspondence concerning this service must be addressed to READERS
PCB SERVICES and not to the Editorial offices.



S-DeC holes 36 and 41 will complete the base to positive rail circuit via the resistance of the bodies.

With fairly dry hands the bulb will probably not light at all. But if one waits for a few moments the fingers will perspire slightly and this "wetness" will

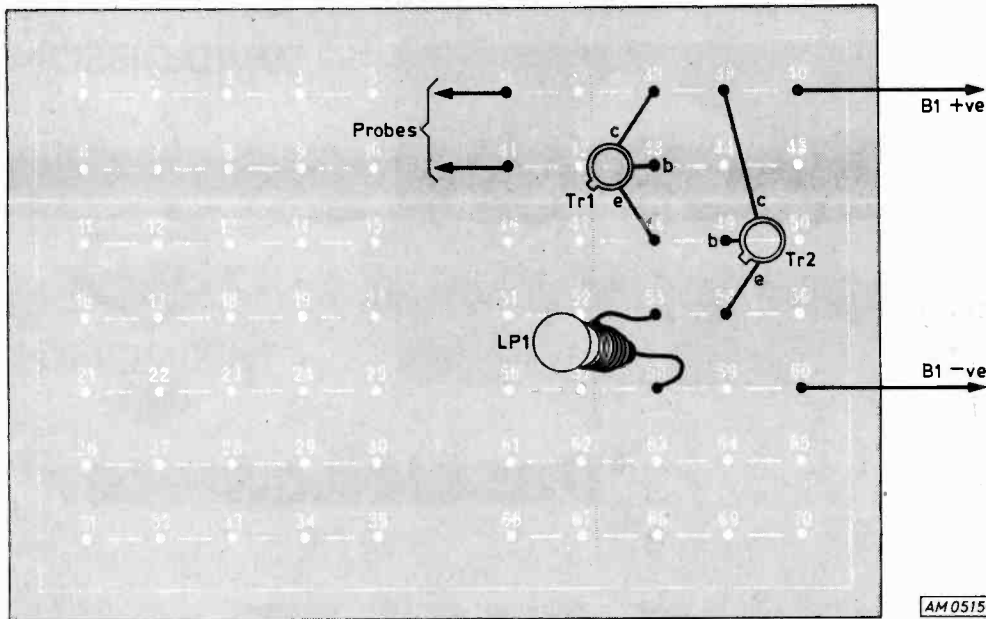vincing version then you might consider purchasing a meter. It would be necessary to remove the dial and recalibrate it with segments labelled "Cold, Cool, Warm, Hot, Passionate and Danger". By simply connecting the meter in series with the bulb LP1



Drawing of the S-DeC shown full size. If a meter is used as well as a lamp, it should be connected to holes 59 and 64.

AM0515


improve the conducting properties of the skin by lowering its resistance thus causing the bulb to start glowing.

Metered

As described, the "Passionometer" is very simple, cheap and will cause a lot of fun at any party. If you wish to make a more sophisticated and con-

it would read the current drawn by the bulb. Thus as the bulb started to glow brighter so the meter would read a higher "passion" score. A 6V 100mA bulb together with a 6V battery was found to be optimum, trading acceptable brilliance against reasonable circuit action.

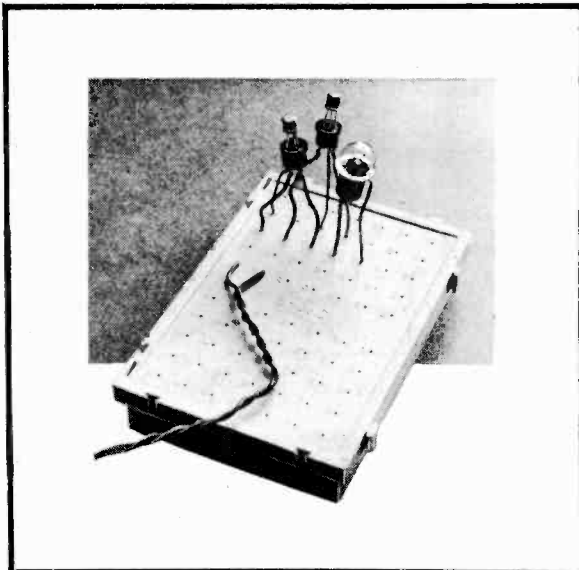For those considering making the "meter version", the meter must be capable of reading 100mA FSD (full scale deflection). On test, simply plug the meter into S-DeC holes 59 (positive side of the meter) and 64, and transfer the battery negative lead from S-DeC hole 60 to hole 65. The probes were simply the free ends of two wires which were plugged into holes 41 and 36 on the S-DeC.




Photograph showing the actual 'Passionometer'. As can be seen only three components are needed to complete this simple circuit.

No guarantee

That's all there is to this month's circuit. Of course, I cannot guarantee that the device will indicate passion with any accuracy nor will it measure emotion—but you can have an awful lot of fun trying to prove me wrong!

Next month's S-DeC circuit again uses many of the components already employed in earlier projects. It can also be used at a party, or for more serious applications. Basically a miniature pocket stroboscope, it is simple and easy to build. It can be employed to give the stroboscopic motion-freezing effect commonly found at Disco's these days. It can also be used for more serious things such as splitting an apparently continuous stream of water from your tap into thousands of tiny crystal droplets.

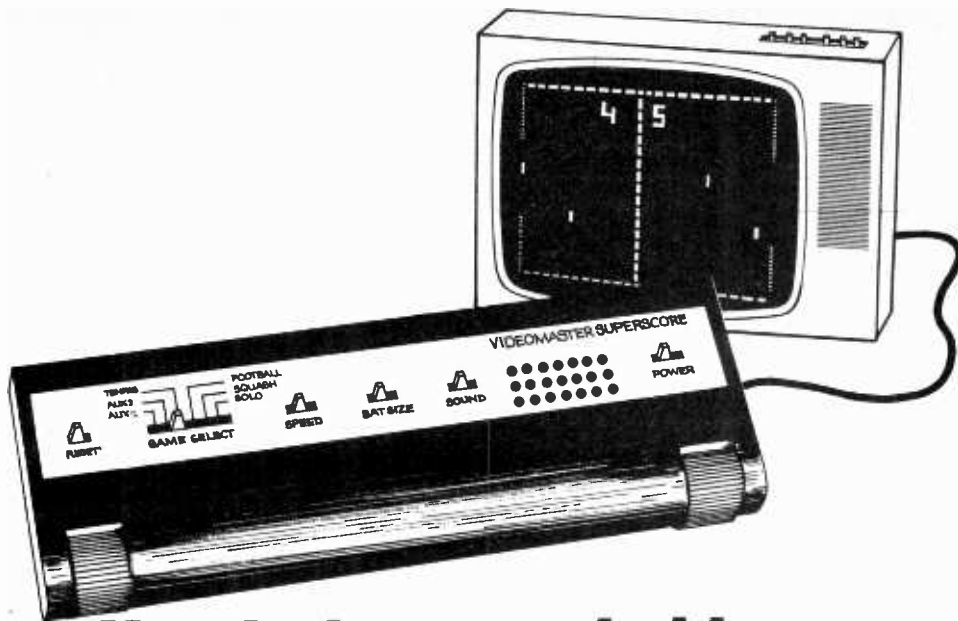The S-DeC project after that is even more fascinating . . . but I'll tell you about that in next month's Practical Wireless.



Here's the remarkable new **VIDEOMASTERTM** Superscore Home TV Game Get it together for only £24.95

Available to you in kit form at the same moment as its national launch, the brilliant new Videomaster Superscore contains the latest product of MOS technology: a TV game chip.

The logic contained in it had previously to be generated by 100 TTL devices. Now it is condensed into one 28-pin chip.

This all-new Videomaster plugs into your 625-line UHF TV set (for overseas customers having VHF sets we can supply the necessary VHF modulator) to give you four exciting games (including tennis and football) and two future game options. It features on-screen digital scoring, realistic hit sounds, two bat sizes, two

ball speeds, automatic serving and much more. It runs on six 1½ volt SP11 type batteries (not supplied).

The Videomaster Superscore kit costs only £24.95 including VAT (recommended retail price of the ready built model is over £40.00) and comes complete with ready-tuned UHF or VHF modulator, circuit board with printed legend, all resistors, transistors and diodes, built-in loudspeaker, socket for mains adaptor, and, of course, the TV game chip itself.

Easy to put together the Superscore has full assembly instructions, circuit diagram and circuit description. Don't miss this chance to own the newest electronic game at such low cost.

POST TODAY TO:

Videomaster Ltd 14/20 Headfort Place, London SW1X 7HN



Please send me (insert No. requ'd).....Videomaster Superscore Kits at £24.95 (inc. VAT & P&P in UK) or £23.10+£4.00 for P&P overseas)

I enclose my cheque/money order* for £.....

VHF modulator required YES/NO*

PW93

NAME _____

ADDRESS _____

ALLOW 21 DAYS FOR DELIVERY

* delete as necessary


TAMBA ELECTRONICS

AMPLIFIER AND MIXER MODULES

25 WATTS — 100 WATTS RMS

QUALITY PRODUCTS
FOR HI-FI, DISCO,
P.A. GROUP AND CLUB USE

TAM1000 100W 4 OHMS 65V	£9.80
TAM500 50W 4 OHMS 45V	£7.50
TAM250 25W 8 OHMS 45V	£4.75
POWER SUPPLIES	
For 1 or 2 TAM250/500	£7.50
For 1 or 2 TAM1000	£9.80
(Carr. 50p on supplies)	

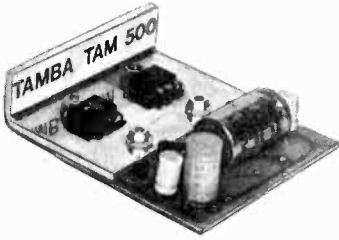

ALL PURPOSE MIXER/PREAMP

(WITH 60 mm SLIDER VOLUME)

- Suits loads 4-16 ohms
- 20-20,000 hz ±1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)
- Low distortion (0-1%)
- Low profile (1" High 3½" x 3")
- 75% efficient
- Accepts most mixer/preamps
- Four simple connections

- Anodised & printed fascia
 - Suitable for multiple input systems
 - High & low impedance inputs
 - High sensitivity
 - Built in supply smoothing
 - 20-20,000 hz ±1dB
 - 80dB Noise level
 - Accepts a wide variety of inputs
 - Wide range bass & treble controls
- Use up to 10 preamps with 1 power!

COMPLETE & TESTED assembly with Treble & Bass controls plus slider Volume Control. **£6.50**

High Grade Components used throughout: Texas, Mullard, R.C.A., Plessey, etc.

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s, etc.) C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50-100W units and at 12½% for 25W units

Hours, 9.30 a.m.—5 p.m.
Monday—Saturday.
Callers welcome.
Tel: (01) 684 0098

TAMBA ELECTRONICS

BENSHAM MANOR ROAD PASSAGE, BENSHAM MANOR ROAD, THORNTON HEATH, SURREY

Random FLASHER UNIT

Wired ready for use
Complete with three
100 watt coloured lamps
that flash independently
at random

£18.95

TWIN BANK 6 LIGHT UNIT

(less lamps) LENGTH 14 1/2 inches

B.C. Fitting **£9.55** EACH
E.S. Fitting **£10.35** EACH

Sound to Light MASTER UNIT

600 WATTS PER CHANNEL

£30.95

INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET

TYPE A SPOT

(less lamp)

B.C. Fitting **£1.95** EACH | E.S. Fitting **£2.12** EACH

TYPE B 3 BANK UNIT

(Less Lamps)

B.C. Fitting **£6.90** EACH | E.S. Fitting **£7.26** EACH

TWIN BANK 12 LIGHT UNIT

(less lamps) Length 31 1/2

B.C. Fitting **£15.60** EACH | E.S. Fitting **£17.00** EACH

100 WATT SPOT LAMPS

RED, YELLOW, GREEN, BLUE, CLEAR

3 lamps **£3.54**

B.C. or E.S. Fitting

ALBEN ENGINEERING CO. LTD.,
DEPT. PW THE CRESCENT, WORSTHORNE,
BURNLEY, LANCs. Tel: Burnley 20940.

FANE SPECIALIST RANGE SPEAKERS



Each designed to produce the individual sound requirement for its purpose. Robust Cast Aluminium Chassis

DISCO/80 **£25.95**
Linen Cone Surround

GUITAR/80L **£24.75**
For Lead Guitar

GUITAR/80B **£24.95**
For use in multiples for Bass Guitar.

PA/80 **£24.75**
For general purpose P.A.

15" BASS/85 85w **£37.95**
15" BASS/100 **£39.95**
For Bass Guitar

FANE 'POP' RANGE SPEAKERS

12" POP 33T 33w **£13.95** | **15" POP 60 60w** **£25.95**
12" POP 50/2 50w **£15.99** | **15" POP 70 70w** **£28.95**
12" POP 55 60w **£22.95** | **18" POP 100 100w** **£44.95**

HIGH FREQUENCY HORNS

J44 Range: 2.5KHz-15KHz Power: 50w with HPX2 Imp: 8 ohms Size approx 10 1/4" x 3 1/4" x 7 1/2" **£7.95**

910/2 Range: 2KHz-15KHz Power: 50w with HPX1 Imp: 8-16 ohms Size approx 6 1/2" x 3 1/4" x 6 1/2" Rec. Price **£17.75**

J104 Range: 2KHz-15KHz Power: 50w with HPX1 Power: 70w with HPX2 Imp: 8 ohms Size approx 10 1/4" x 3 1/4" x 7 1/2" Rec Price **£16.95**

920/2 Range: 1KHz-18KHz Power: 100w with HPX1 Imp: 8 ohms Size approx 14" x 9" x 15" Rec Price **£59.95**

Rec Prices INCLUDE VAT. 2 years guarantee on above speaker models

Distributors (Wholesale & Retail)
LINEAR PRODUCTS LTD, ELECTRON WORKS, ARMLEY, LEEDS.
Manufacturers & Export enquiries to—
FANE ACOUSTICS LTD, 286 BRADFORD ROAD, BATLEY, YORKS.



AMATEUR BANDS

by Eric Dowdeswell G4AR

ALTHOUGH I haven't seen one yet I gather that we radio amateurs in the UK are to get a nice, new, shiny, and more expensive, licence from the Home Office as we renew our 'tickets'. Seems all the odd bits of paper separately authorising one to operate /T, /M and various odd modes not in the normal licence have all been abolished, and high time too. It is opportune to mention that the RSGB was fully consulted on the new licence at all stages and no doubt they have obtained every advantage for us that they could.

The three world regional organisations that make up the International Amateur Radio Union have reached agreement on the radio frequency allocations to be sought for the Amateur Service at the World Administrative Radio Conference to be held in 1979. Such early agreement augurs well for our cause but whether we amateurs get all that's being asked for will largely depend upon how well each national society presents its case to its own administration.

We should count ourselves as being very lucky to have the RSGB behind us considering the very high esteem in which it is held by our authorities but, regrettably, the opposite is the case in many other countries where commercial interests and politics decide such matters. Whatever happens at the WARC at least we shall know that the RSGB did its best on our behalf.

I wish it were possible for me to check back and see how long it takes someone writing in as a 'first timer' to go on and get his amateur radio licence. **Jim Oram**, just moved to a new QTH in Basingstoke, has been a SWL for about a year now and has joined the Basingstoke ARS. He hopes to take the RAE next May and while I am sure that we all wish him all the best I feel that he is being a trifle optimistic. However, have a go, Jim! The experience of taking the exam is worth its weight in gold, pass or fail. Jim has a Heathkit GR64 and expects to really get into the DX when he gets his new aerial up.

Alan Doherty BRS34968 is now in the peace and calm of Rotorua in New Zealand, at least until March next year when he is due to return to Northern Ireland. He has managed to listen around the bands

using two old valved radios, one as a BFO, so that he can copy SSB. Alan visits local ZL1QC who runs an FT401 and uses a Zepp aerial system, so he doesn't feel too home sick!

In Holyhead **John Higginbotham** now has a nice new FR100B which puts his old receiver to shame. He is also talking about an FL200 Tx and a linear, so obviously John is not too far off getting his RAE. Don't forget the Morse exam OM, you'll need it if you are going to use all that gear! The only QRM being suffered by John at the moment is that caused by exam worries! Newcomer **Bob Harvey** of Oxford is 15 and has got under way on the SW bands with a Codar Mini-Clipper but feels he could do with something more ambitious. Perhaps Father Christmas came up trumps OM? Anyway, Bob added an audio amplifier and a large dial which he calibrated himself, and with a 32ft. aerial he started to hear things. Bob, too, has made contact with his local ARS and looks forward to starting an RAE course soon.

Anent the misfortunes of **Robin Bayley** of All-ripton whose local RAE course collapsed, he heard from G4FGR who put him on to another course so let's hope it all proves worthwhile for Robin. He now has an Eddystone EC10 which enables him to copy CW and SSB from 15 to 80m, using a long wire. Readers often refer to a 'long wire' aerial but I wonder if that is really what they mean. In this sense it should mean that the aerial is long in terms of the wavelength which would mean 275 odd feet to be a couple of wavelengths on the 40m band! I don't think that many readers can go to that sort of garden! Most aerials are much shorter which is why it is so essential to employ an aerial tuning unit to make up the length electrically.

In Harrogate **Steve Cottis** A8961 reports new countries with VP5, 5W1, VQ9 (Chagos Is) and FR7 all on 80m. He finds 20m closing down around dusk although the DX is still there after the Europeans have gone. **Brian Harrison** found something for the log on most bands down in Hastings, including rare KX6MU on 20m SSB. FO8EB is another that is quite rare and a worthwhile at any time on any band. **Arnold Silverwood** won't mind if I call him a 'first timer'. He lives in Nottingham and has built himself an HAC receiver and is starting to understand some of the amateur 'language'. While his set can be made to give quite good results I have pointed out to Arnold that there are more sophisticated sets around, and that he shouldn't write off our hobby too soon, if he feels he is not getting results!

A very interesting club magazine that comes my way each month is TARS TALK, the 'voice' of the Torbay ARS, edited by F. Bolton G3VTQ. Besides



all the usual club chatter there are a couple of small but interesting articles in the November issue on Roof Space Aerials and Receiver Drift. At present, meetings are held at Bath Lane, Torquay (rear of 94 Belgrave Road) but more suitable accommodation is being investigated. Anyone interested in joining the TARS is recommended to contact the Secretary, M. Yates G3UIQ at 23 Waverley Road, Newton Abbott, Devon.

In Hastings, Jesse Luxton G8GMI is not bothering too much about VHF but concentrating on getting his code up for the examination. Unfortunately Jesse had a stroke in 73 which he feels has not helped at all. He recommends PA0AA for slow morse as they run a course over the air and suggests getting their booklet from PO Box 2083, Eindhoven, Holland for 6 IRC's.

Andy Grendon of Dun Laoghaire, Co. Dublin has really got going since I wrote to him recently. He joined the IRTS and is now EI508 and attending Morse classes while a Heathkit SW717 helps him to cover the HF bands. He is in a built-up area and has little space for aerials. A 30ft end-fed suffices for the moment.

Log Extracts


R. Bayley:— 80m CW VS6DO ZL2BFU ZS2PR 40m CW CT2BP EA9FD K8CCV VE1AF 20m CR6LF FP8DH HK0COP TG9TI VP8AA 15m AP2AD DU1DBT VK3XI ZP5CD

A. Doherty:— In New Zealand 20m DL8NU EA3AEA EA6CK SV1BR

S. Cottis:— 80m A4XGB FP8DX (QSL K9OTB) JA6YDG WA6EGL/VQ9 (Chagos Is) 20m CX7BV FP8ZZ FR7BI HK1CMX VP2GMB 5W1AB 15m A9XBD JY9CR VP5A YV2AMM 10m ZS1EZ

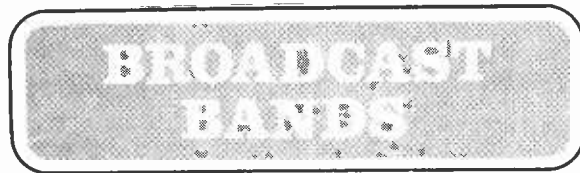B. Harrison:— 80m ZC4FS HP1YV 7X2HM 20m DU2EL KX6MU 9D5A (Iran) 15m PY0ZAE (Trinidad Is)

All SSB except where indicated otherwise.



MEDIUM WAVE DX

by Charles Molloy

TRANSATLANTIC DX dominates the scene this month, reception on this path being better than it has been for several years. Reader's logs show stations not normally heard while others, trying this path for the first time, are able to report success. Laurence Bennett writes from Bristol "at long last, mainly through help from your column, I have heard and verified my first transatlantic DX catches. Here is my complete North American log to date". Many thanks for the bouquet, Laurence. The


receiver is a Trio 9R59DS connected via an aerial tuning unit to a 68ft longwire aerial and the log consists of three stations from Newfoundland, CBN on 640 kHz, CKVO on 710, CJON on 930 plus four in New York City, WOR on 710, WCBS on 880, WINS on 1010 and WNEA on 1130. DXers who have still to hear North America should try after midnight for one of these stations, and if the path is open then at least one should be heard.

Laurence raises an interesting point when he says "I managed to hear both WOR and CKVO on 710 at the same time which resulted in a jumble which was difficult to resolve". DX signals on the MWs are usually subject to slow fading, the cycle often lasting a minute or two. This is typical of E layer reception which is quite different from the fast fading experienced on the short waves and, occasionally, at the high frequency end of the medium waves, where the F layer is the part of the ionosphere responsible for propagation. The technique on the medium waves is to stay tuned to a channel for several minutes when hopefully DX will appear out of the noise or, in the case of WOR and CKVO, either one will become dominant long enough for an identification to be heard.

Simon Knott who lives in Cambridge reports two instances of DX on a channel normally occupied by a North American "local". Using a Trio 9R59 and a 48in loop he heard CFRB in Toronto as well as WINS on 1010kHz and on 930kHz which is normally the domain of CJON he logged CFBC Saint John City in New Brunswick. CFBC sent a QSL after a month and Simon asks if this station has been logged by anyone else recently. CFBC is something of a rarity in the UK because of the directional aerial used at the transmitter. This produces a null towards the north east which protects CJON from interference within its service area but, unfortunately, DXers in Europe as well are prevented from receiving its signal. Simon refers to CBM Montreal on 940kHz which he hears occasionally. CBM has an omnidirectional aerial which presents a rather weak signal to any European DXer who is patient enough to sit on the channel when the path to North America is open.

Derek Taylor (Preston) is still trying to identify a US station on 1390kHz. Although he taped the identification it sounds different every time he plays it! WCSC in Charleston, South Carolina, is a likely candidate here, the writer having heard it several times and the other possibility is WEGP Presque Isle in Maine. Derek who uses a Realistic DX160 and loop also reports hearing WJR Detroit on 760 at 0109, WHAS Louisville Kentucky on 840 together with All India Radio outlets in Bikaner on 1330 (at sign-on at 0100) and Gwalior on 1390 at 0125, Radio Antilles, Montserrat on 930 at midnight, Radio Victoria in Aruba NWI on 960 at 0040 and WMDD in Puerto Rico on 1480 at 0310. Puerto Rico, although in the Caribbean, is one of the states of the USA and consequently US call signs are used. Surprisingly, there are 52 medium wave stations operating in Puerto Rico and since the language can be Spanish or English it is very confusing for the DXer. Other Puerto Ricans heard in the UK are WKAQ Radio on 550, WKVM in San Juan on 810, WHOA Radio Capital in Hato Rey on 870 and WUNO (Radio Uno) on 1320.

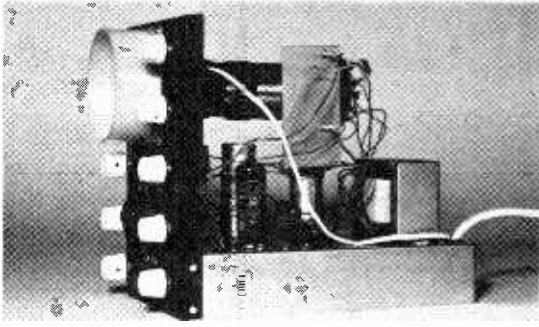
Steve Whitt (G8KDL) who DXes in London with a Chapman S6BS communications receiver, PW loop and differential amplifier (*Practical Wireless*, April 1973) has been experimenting. He replaced the



'There's only one way to master electronics... to see what is going on and learn by doing.'


1 Build an oscilloscope.

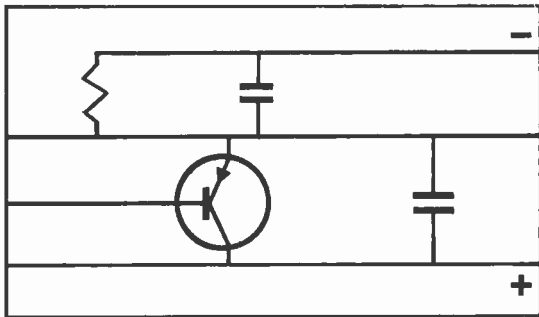As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



2 Read, draw and understand circuit diagrams.

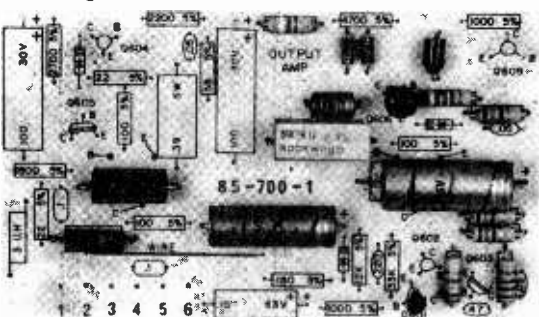In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Write to:- British National Radio & Electronic School
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

WB 37

B. BAMBER ELECTRONICS

Dept. PW, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

GARRARD 9V DC MINIATURE MOTORS, Type 318M, 3200 RPM governed, size approx. 1 1/2 in. dia. x 1 1/2 in. high, with 2mm spindle. Brand New. 60p each or 2 for £1.

SILICON HIGH VOLTAGE RECTIFIER STICKS, BY185 (new) 35kV 2.5mA £1 each, BY140 (ex-equip) 12kV 2.5mA 48p each.

VARIABLE STABILISED POWER SUPPLY, mains input, 0-24V output, stabilised and current limiting at 500mA, ±32V at 50mA. Brand new by British manufacturer. Size approx. 7 1/2 x 2 1/2 x 4 in. complete with external 6kΩ 3-turn pot for voltage control. Connection data supplied. £7.

14 DI LED RELAYS, 5 to 12V DC, 450 ohm coil. Designed to work directly from TTL Logic. Single Pole Change Over. Contact ratings 28V 1A 3W £1.75 each.

PLASTIC BOXES 3 1/2" square, 1 1/2" deep (wall-mounting type) with 5-pin din plug on front panel. 60p each.

MAINS ISOLATION TRANSFORMERS. Tapped mains input. 240V at 3A + 12V at 500mA output. New, boxed, made by Gedrars, £12.

BOLDER BUCKERS (Plunger Type). Standard Model, £4.50. Skirted Model, £4.95. Spare Nozzles 60p each.

2N3055 type Transistors O.K., but unmarked, 5 for £1.

110V NEODONS, SCREW-IN-TYPE, 4 for 50p.

SLOW MOTION MOTORS (suitable for programmers, displays, etc.) 230-240V a.c. Input, rotation, 1 rev. every two to three minutes. Scry, sold out.

MINIATURE PLIERS. High quality "Crescent". Made in USA. £4.35 + VAT (35p).

SIDE CUTTERS. High quality. £3.70 + VAT 30p.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

4MHz XTAL PACKS (10 assorted xtal between 4MHz and 5MHz), our selection only. £1 Pack.

PROGRAMMERS (magnetic devices). Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable. Ideal for switching disco lights, displays, etc. or industrial machine programming. (Need slow motion motor to drive cams, not supplied.) 9 switch version £1.80.

HEAVY DUTY HEATSHINK BLOCKS, un drilled, base area 2 1/2 in. x 2 in. with 6 fins. total height 2 1/2 in. 60p each.

SPERRY 7-SEGMENT P.G.D. DISPLAYS, digit height 0.3in. red, with decimal points. 150V to 200V (nominal 180V) operation. These are high-volt industrial type and therefore brighter than normal displays. All brand new. AT THE BARGAIN PRICE OF 50p PER DIGIT. TYPE 332 (two digits in one module) £1 each. (Sorry, no single digit available) £0.50.

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 80p.
PBC108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 80p.
BCY22 Transistors, 4 for 80p.
PNP audio type T05 Transistors, 12 for 25p.
AF182 (JHF amp/mixer), 3 for 60p.
2N3819 Fet, 3 for 60p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BA131 Signal Diodes, 10 for 35p.
BA121 Varicap Diodes, 4 for 60p.
1N914 Diodes, 10 for 25p.

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio, Hi-Fi inputs, etc.), approx. 1/2 in. x 1 1/2 in., 3 for 80p.

PERSEX TUNER PANELS (for FM Band 2 tuners) marked 88-108MHz and Channels 0-70, clear numbers, red backed out, smart modern appearance, size approx. 8 1/2 in. x 1 1/2 in., 3 for 25p.

Lead suppressors (10kohm) for mobile plug leads, 4 for 50p.

HEAVY DUTY RELAYS, 24V d.c. operated (will work on 18V) 3 heavy duty make contacts (around 10A rating) + 4 change over contacts + 1 break contact. New, complete with mounting bracket. (Ideal for switching HT on Liners.) Many uses for this high quality unit. £1-80 each.

T03 transistor/insulator sets, 10 for 50p.

ALU-SOL ALUMINIUM SOLDER (made by Muller-core). Solders aluminium to itself or copper, brass, steel, nickel or tinplate. 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 40p pack. Large reel £2.75.

VARICAP TUNERS Mullard Type ELC1043/05. Brand New. £4.40 + 12 1/2% VAT.

I.C.'s some coded, 14 DIL type, untested, mixed, 20 for 25p.

Mobile Converters. 24V DC input 13.8V at approx. 3.4A DC output, fully stabilised. £3.50 each (ideal for running 12V car radio from 24V lorry battery).

We now stock Spirax Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

Miniature earphones with min. jack plug, 2 for 50p + 12 1/2% VAT.

I.F. Cans, 1/2 in. square, suitable for rewind, 6 for 30p + 12 1/2% VAT.

TWIN I.F. CANS, approx. 1 in. x 1/2 in. x 1 in. high, offers 3 5-5MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 12 1/2% VAT.

Dubilier Electrolytics, 50µF, 150V, 2 for 50p.
Dubilier Electrolytics, 100µF, 275V, 2 for 50p.
Plessey Electrolytics, 470µF, 63V, 3 for 60p.
TCC Electrolytics, 1000µF, 30V, 3 for 60p.
Plessey Electrolytics, 1000µF, 180V, 40p each (3 for £1).

Dubilier Electrolytics, 5000µF, 35V, 50p each.
Dubilier Electrolytics, 5000µF, 50V, 60p each.
ITT Electrolytics, 800µF, 25V, high grade, screw terminals, with mounting clips, 60p each.
Plessey Electrolytics, 10,000µF at 63V, 75p each.
Plessey Cathodray Capacitors, 0-0.4µF at 12.5kV DC. Screw terminals. £1.50 each.

PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.

TV PLUGS AND SOCKETS

TV Plug (metal type), 5 for 80p.
TV Sockets (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p. Please add 12 1/2% VAT.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

PLUGS AND SOCKETS

N-Type Plugs 50 ohm, 60p each, 3 for £1.50.
P259 Plugs (PTE), brand new, packed with reducers, 85p or 5 for £3.
SO239 Sockets (PTE), brand new (4-hole fixing type), 80p each or 5 for £2.25.
25-way ISEP Plugs and Sockets, 40p set (1 plug + 1 skt).
Plugs and sockets sold separately at 25p each.

BNC PLUGS (ex-equip.) 5 for £1.50.

WELLER SOLDERING IRONS

EXPERT, Built-in-spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN, £8.80 + VAT (54p).
EXPERT SOLDER GUN KIT (apart bits case, etc.), £9.80 + VAT (78p).

SPARE BITS, PAIR, 30p + VAT (2p).
MARKSMAN SOLDERING IRONS
SP15D 15W £3 + VAT (24p).
SP25D 25W £3 + VAT (24p).
SP25DK 25W + bits, etc., kit £3.85 + VAT (31p).
SP40D 40W £3.44 + VAT (28p).
BENCH STAND with spring Marksmen Irons, £2.22 + VAT (18p).

SPARE BITS
MT8 for 150V 46w + VAT (4p).
MT4 for 25W, 36p + VAT (3p).
MT10 for 40W, 42p + VAT (3p).
TCPI TEMPERATURE CONTROLLED IRON, Temperature controlled iron and PSU. £20 + VAT (£1.60).

SPARE TIPS, Type CC single tip, Type K double flat fine tip. Type P, spare fine tip. £1 each + VAT (8p).

MOST VARIETY AVAILABLE.

MULTICORE SOLDER

Size 5 Savbit 18 s.w.g. in alloy dispenser, 32p + VAT (3p).
Size C15AV18 Savbit 18 s.w.g., 56p + VAT (4p).
Size 12, Savbit 18 s.w.g. on plastic reel £1.80 + VAT (15p).
1/2 Kg. (1-1lb) 60 x 40, 20 s.w.g. on plastic reel £3.

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS SATURDAYS ONLY 9.30-12.00. 1.30. 5.00



A. Marshall (London) Ltd Dept: PW
40-42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2 Telex: 21492
& 85- West Regent St Glasgow G2 2QU Tel: 041-332 4133
& 1 Straits Parade Fishponds Bristol BS16 2LX Tel: 0272-654201/2

Catalogue price 55p post paid
(40p to callers) Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Our range covers over 7,000 items. The largest selection in Britain.

TOP 200 IC's, TTL, CMOS & LINEARS

CA3020A	2.29LM380A	98pMCI1350	1.75p76650N	1-10TBA700Q	1-61
CA3028A	1-01LM381A	2-45MCI1351	20076660N	60pTBA720Q	2-31
CA3028B	1-29LM381A	1-60MCI1352	97p766660N	92pTBA750	1-98
CA3030	1-24LM382A	1-25MCI4357	1-45TAA310A	1-50TBA750Q	2-07
CA3030A	1-89LM384A	1-45MCI4558	91pTAA320B	1-15TBA800	1-20
CA3045	1-40LM386A	80pNE555	53pTAA350A	2-48TBA810	1-16
CA3046	89pLM387A	1-05NE556	1-05TAA521	1-00TBA820	1-03
CA3048	1-23LM388A	1-00NE565	1-30TAA522	1-90TBA920	1-79
CA3049	1-66LM389A	1-00NE566	1-65TAA550	60pTBA920Q	2-99
CA3052	1-63LM702C	75pNE567	1-80TAA560	1-60TBA940	1-62
CA3053	60pLM709C	65pSA5560	1-00TAA570	2-30TCA160C	1-85
CA3080	68pLM709N	45pSA5570	1-00TAA61B	1-85TCA160B	1-61
CA3080A	1-88LM710C	60pSO42P	1-00TAA62I	2-15TCA270	2-25
CA3086	51pLM710N	60p76001N	1-57TAA661B	1-32TCA280A	1-30
CA3088	1-59LM723C	85p76003N	2-35TAA700	3-91TCA290Q	3-13
CA3089	2-32LM723N	75p76006N	2-50TAA930A	1-00TCA420A	1-84
CA3090	3-80LM741C	65p76013N	1-70TAA930B	1-09TCA730	3-22
CA3130	94pLM741N	50p76013ND	1-57TAD100	1-95TCA740	4-76
LM301A	65pLM741-8	40p76018K	2-50TBA120	65pTCA750	1-30
LM301N	44pLM747N	90p76023N	1-70TBA400	1-50TCA760	1-38
LM304	2-45LM748-8	50p76023ND	1-75TBA500	2-21TCA800	3-13
LM307N	65pLM748N	90p76033N	2-35TBA500Q	2-30UAA170	2-00
LM308A	1-17LM1800	1-7676110N	1-87TBA510	2-21UAA180	2-00
LM309K	1-9276118N	1-9276115N	2-06TBA510Q	2-30CD4000	20p
LM317K	3-00LM1828	1-7576116N	1-30TBA520	2-30CD4001	20p
LM318N	2-25LM3301N	1-30TBA520	1-94TBA520Q	2-30CD4002	20p
LM323K	6-40LM3302N	1-4076221N	1-91TBA530	1-90CD4006	1-10
LM339N	1-75LM3401N	75p76227N	1-54TBA530Q	2-07CD4007	20p
LM348N	1-91LM1800	75p76228N	1-90TBA540	2-21CD4008	97p
LM368N	2-75LM3905	1-67765310N	91pTBA540Q	2-32CD4009	57p
LM370N	3-00LM3909	68p76532N	1-30TBA550	3-13CD4010	57p
LM371N	2-25MCI303	1-7576533N	1-44TBA550Q	3-22CD4011	20p
LM372N	2-25MCI305	1-4776544N	2-09TBA560Q	3-22CD4012	20p
LM378N	2-25MCI305	1-8576545N	1-44TBA570	1-29CD4013	57p
LM374N	2-25MCI306	1-0076546N	41pTBA570Q	1-38CD4014	1-01
LM377N	1-75MCI310	1-9176550N	61pTBA641Q	2-50CD4015	1-01
LM378N	2-35MCI312	1-9876552N	2-15TBA651	1-80CD4016	56p
LM379S	3-95MCI327	1-5476537N	2-10TBA700	1-52CD4017	1-01
LM380-8	90pMCI330	92p76620N			

SEND FOR OUR NEW CATALOGUE WITH 500 NEW LINES—55p post paid. Call in or send S.A.E. for details.

POPULAR SEMICONDUCTORS

2N696	35p	2N2907	21p	2N3791	3-10	2N6121	38p	BC107	15p
2N697	30p	2N2907A	22p	2N3792	3-50	2N6122	41p	BC108	15p
2N698	62p	2N2924	25p	2N3794	40p	2N6123	43p	BC109	15p
2N699	55p	2N2926	12p	2N3819	36p	2N6126	45p	BC113	17p
2N706	14p	2N3019	55p	2N3820	38p	40361	45p	BC115	19p
2N706A	12p	2N3053	30p	2N3823	75p	40362	48p	BC116	19p
2N708	21p	2N3054	60p	2N3904	21p	40363	1-20	BC116A	20p
2N709	50p	2N3055	70p	2N3908	22p	40366	58p	BC117	22p
2N718	27p	2N3190	25p	2N4036	67p	40407	45p	BC118	16p
2N718A	50p	2N3391	25p	2N4037	55p	40408	65p	BC119	30p
2N720A	80p	2N3391A	25p	2N4058	20p	40409	65p	BC121	45p
2N914	35p	2N3392	16p	2N4060	20p	40410	65p	BC132	30p
2N916	30p	2N3393	15p	2N4061	17p	40411	1-25	BC134	15p
2N918	38p	2N3394	15p	2N4062	18p	40594	75p	BC135	15p
2N929	25p	2N3439	88p	2N4126	17p	40595	86p	BC136	19p
2N930	28p	2N3440	64p	2N4289	20p	40573	73p	BC137	14p
2N1131	60p	2N3441	85p	2N4919	65p	AC126	37p	BC140	40p
2N1132	60p	2N3442	1-35	2N4920	70p	AC127	44p	BC141	45p
2N1613	35p	2N3638	16p	2N4921	50p	AC128	37p	BC142	30p
2N1711	37p	2N3638A	16p	2N4922	55p	AC151V	35p	BC143	30p
2N1893	30p	2N3639	30p	2N4923	70p	AC152V	50p	BC147	12p
2N2102	60p	2N3641	20p	2N5190	60p	AC153	49p	BC148	12p
2N2112	30p	2N3702	17p	2N5191	90p	AC153K	35p	BC149	13p
2N2218A	37p	2N3703	16p	2N5192	75p	AC176	40p	BC153	27p
2N2219	50p	2N3704	15p	2N5195	90p	AC176K	60p	BC157	12p
2N2219A	32p	2N3705	15p	2N5245	35p	AC187K	55p	BC158	12p
2N2220	35p	2N3706	16p	2N5294	40p	AC188X	55p	BC159	14p
2N2221	22p	2N3707	18p	2N5295	40p	AD161	85p	BC160	50p
2N2221A	14p	2N3708	17p	2N5296	40p	AF127	69p	BC172	12p
2N2222	25p	2N3709	18p	2N5298	40p	AF106	55p	BC175	12p
2N2222A	25p	2N3710	16p	2N5447	15p	AF109	75p	BC168	12p
2N2223	25p	2N3711	18p	2N5448	15p	AF124	65p	BC169	12p
2N2369	25p	2N3712	1-20	2N5449	19p	AF125	65p	BC170	16p
2N2369A	25p	2N3713	2-30	2N5457	22p	AF126	65p	BC171	14p
2N2646	75p	2N3714	2-45	2N5458	33p	AF127	65p	BC172	12p
2N2647	1-40	2N3715	2-35	2N5459	33p	AF139	69p	BC177	




2N3819 FETs in the differential amp with 2N4416s and the resistors with metal oxide types and obtained greater gain and less cross modulation. He says that conditions have been excellent and on some days (nights!) WINS on 1010 has been roaring in as early as 2230 causing interference to the Dutch station (Lopik) on 1007kHz. Steve finds North American stations excellent verifiers, he sends an International Reply Coupon with every report, and quotes from a letter from WBZ Boston (on 1030) which suggests that since they beam their signal on 270° he may have received them after their signal had circled the world! Unlikely, as propagation on the medium waves requires a path of darkness between transmitter and receiver.

More DX from Michael Illingworth of Christchurch who reports hearing KMOX in St Louis on 1120 with his Trio 9R59DS receiver. This is a really good catch which is only logged when reception is really good. Incidentally, US stations use one of two prefixes in their call signs. Those beginning with the letter K are with one exception, KDKA, to the west of the Mississippi while those with the letter W are to the east. A call sign beginning with K means real DX from the UK.

An unusual request for identification comes from Nick Hall-Patch of Victoria, British Columbia, who, with a friend, heard an unidentified broadcast, in a transatlantic direction on 566kHz. It was at 0725 and consisted of a single short pip every 15 seconds. The station according to a law well known to medium wave DXers, faded out just before 0730 when of course Radio Eireann would have signed-on for the day. The writer had never noticed these pips before which only shows that one man's DX is another's QRM. (BBC Radio 4 also uses them—AED.)

Bob Bonsall of Buxton wants to buy a good radio that will pick up North American stations on the medium waves. Reports this month come from users of the Trio 9R59D/E, Realistic DX160 and Chapman S6BS. It would be a great help to readers starting the hobby if all logs were accompanied by full details of the receiver, aerials and any other gear in use. The time, in GMT, of any outstanding logging would also be invaluable.

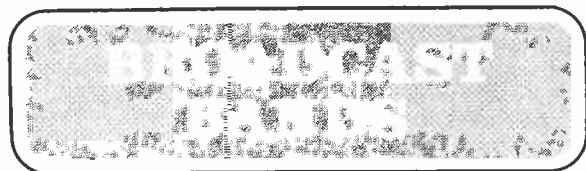

SHORT WAVE BROADCASTS

by Derek Bell

THE Christmas season has slipped into history and one can collect together not only one's thoughts but the paperwork that floods in at this time! From Radio Havana there is the usual

collection of those awful calendars, the size of a matchbox, printed with the dates, unrelentingly, in Spanish! Radio Havana is now asking for letters to be sent to Apartado 7026, Havana, Cuba, and is sending out a schedule which advises that broadcasts for northern Europe will be on 17885 between 2010 and 2140, a very sparse service, with more time devoted to English language broadcasts to north, central and south America on 17750, 11865, 11760, 11725, 9685 and 9525. Nearly 16 hours, in fact!

Alongside this there is the usual crop of "Happy New Year" cards from other similar countries who seem to ignore the fact that the countries they send them to also celebrate Christmas!

Tony Cook, at present living in Gibraltar, logs a few of the signals that whizz around the ether over the Rock. These are as follows: Radio Togo on 5048 at 2100, Morocco on 4650 at 1930, Radio Prague (African Service) on 5760 and 5350 at 1900. Tony asks for information on the HAC Mk 2 set. I must confess I do not know a lot about this set but perhaps other HAC users can answer Tony on the problem of why the reception goes "up the spout" when he connects the bandsread! Finally, Tony would like to know of any books on the subject of DXing and here I can help. Radio Nederland has a very wide range of pamphlets on all aspects of the hobby and their address is PO Box 222, Hilversum, Holland. These publications are all free.


Lawrence Bennett, from Bristol, takes me to task for the lack of Latin American and African stations in the column. Regular readers will remember that a few months ago, with the aid of a Latin American reader resident in London, we looked at the LA scene. However I can only report on the logs that I receive and if no one logs LA then I can't print it! It must be said that it is a long time since anyone sent in such a comprehensive list as Lawrence has and here are a handful of the "DXotics" that his Trio 9R59DS has pulled in via a longwire:—

Radio Difusoras, Venezuela	on 4890 at 2355
Radio Timbira, Brazil	on 4975 at 0430
Radio Sutatenza	on 5095 at 0045
Sierra Leone	on 3316 at 2153
Radio Banqui	on 5038 at 2200

Perhaps it's the thought of the very late nights that puts off the majority of DXers but it is a fact that Latin Americans are strictly for the birds, night owls that is.

M. G. Hayman has also a pet peeve and that is the fact that he waited for the arrival of his Codar Multiband 6 only to find that the firm had sent the order in two lots, and one parcel had got lost in the post! This must be a situation that drives the home-brew enthusiast right up the wall! Meanwhile he has to make do with his HAC Mk 2.

The final letter this month is from V. Marland who resides in Connahs Quay, Clwyd, who requests information on the way that a station report should be laid out. This is very simple, the station name first, then the frequency plus the time in GMT. It is not worth logging signal strength since this can vary enormously. Add some notes on the programme heard and any identification signal heard. Notes on interference to the station are sometimes helpful. If you enclose a couple of IRCs this will expedite a confirmation but don't be too impatient! For now I will wish you best 73s to you and yours.

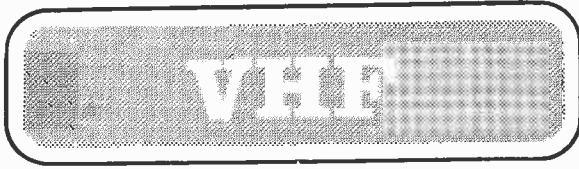

by Ron Ham

THE sun has been very quiet during December; in fact the writer recorded only one burst of solar radio noise (midday December 8th) and that was the first since November 21st. **Alan Taylor**, G3DME, Crowborough, Sx, heard the "seashore sound," normally associated with solar noise, on the 10m band at 1747 on the 15th. Although the sun was set there could have been a large solar burst and Alan detected the radio signals as they came above the horizon. These reports are valuable and since Alan collects the International Beacon Project reports for the RSGB, any that you send to me will eventually end up with him.

At 0947 on Dec. 15th the writer heard the signal from the IBP Beacon in Cyprus (5B4CY 28·180MHz) and that was the first time for a month. An interesting observation came from **Walter Butt** GC2FZC, St Peter Port, Guernsey, who noticed that when he can hear DL0IGI and 5B4CY on 10m, conditions on the 2m band are above normal. What about it readers? The writer would like to hear a lot more about this.

Very soon the number of sunspots will increase as the new cycle gets underway, and **Derek Poulter** G3WHK, Morden, Surrey, a keen all-band DXer, wants to know how to observe these with a telescope. First of all Derek, **NEVER** look at the sun directly through a telescope or any other optical aid, it is **dangerous** to the eyes, in fact it is unwise to look at the sun at all. The technique is to point your telescope toward the sun and project its image on to a white card (shaded from the main sunlight) and pencil in the spots that you can see. Most basic astronomical books will show this.

Of course, you can always direct your 2m beam toward the setting or rising sun and listen around 143MHz (Quiet spot outside amateur band) for the "seashore sound" or "whooshing" which is the radio noise from a sunspot.

Although the atmospheric pressure was below 30·0" for most of December it did rise sharply from 29·5" at noon on the 8th to 30·0" by noon on the 9th and continued to rise slowly reaching 30·4" by noon on the 12th, and true to form, as this high pressure system moved southward, and the AP began to fall, there was a tropospheric opening.

During the late afternoon of the 14th, **Roy Bannister**, G8LXR, Lancing, Sussex, worked several French stations on 2m SSB and on the 15th Roy heard a PA0 and an ON come up on two. From his QTH at Newhaven, Sussex, **Alan Baker** G8LGQ, worked into the Midlands during the evening of the 14th and also noticed patterns on his TV screen, another sure sign that an opening is in progress. From midday until late evening on the 15th the

writer was receiving a strong picture from Lichfield on Chan. 8 (189MHz) and around 2000 a 559 signal from the Sutton Coldfield beacon (GB3SC) on 70cm.

At 0930 on Dec. 5th, **Joost Berden** G3RND, Cowes, IOW, was taking his usual weather picture from the NOAA5 satellite as it passed over and was surprised to find that it's 137·50MHz signal was weak and fluttery for about five minutes, a long time in a pass. The satellite came in at 20°E for an overhead pass, but the signal did not become strong and steady until it was 65°N. At that time, Joost noted that conditions on 70cm were reasonable, he could hear GB3SC and during the previous evening he worked G3OSS in London for the first time, using SSB. There was definitely movement in the troposphere throughout both days, therefore it is possible that this region absorbed the satellite's VHF signal for a short time. The writer has known times when conditions were "up" on 70cm and flat on 2m.

Derek Poulter, G3WHK, has worked a lot of 2m DX by keeping an eye on the barometer and he makes a point of watching the late night weather map on BBC TV to see if there are any "highs" building up. Derek has moved QTH and just received planning permission for his new aerial array:—HQ1 mini-beam for 10/15/20, 4 element yagi for 70MHz, 2 x 6 element arrays for 2m, and something for 70cm, and all supported by a 40ft Versatower! Our readers will be looking for some good reports, Derek!

Another barometer watcher is that experienced VHF DXer, GC2FZC, who monitors the 2m beacons GB3CTC and GB3VHF daily and relates their signal strengths to the prevailing atmospheric pressure. He also has a regular Sunday morning sked with G3IEA and G8DOJ, both in Torquay, and they seldom miss out. In fact the sked with G3IEA has been going on for some 15 years!

Don't forget, if anything unusual occurs on the VHF's the writer will be pleased to have the details. After all, it is your observations that help to put a particular propagation event into its proper perspective.

Late Note: A slight change in the prevailing high pressure during the evening of 23rd December caused a predominantly N/S opening which upset UHF TV and provided some good DX on both 2m and 70cm. Between 1900 and 2200 the writer received 599 signals from beacons GB3SC (432·890MHz) and GB3EM (432·910MHz). At 2117 a 59 signal from G3DY in Northants, while on Ch. 8 (189MHz) a strong picture was received from the IBA transmitter at Lichfield. For most of the evening the 2m band was open from France through to northern-G.

BROADCAST BANDS

Short Wave Reports by the 15th of the month to **Derek Bell**, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.
Medium Wave Logs to **Charles Molloy**, 132 Segars Lane, Southport, PR8 3JG.


AMATEUR BANDS

Logs covering any amateur band/s in band/alphabetical order by the 25th of the month to **Eric Dowdeswell** G4AR, **Silver Firs**, Leatherhead Road, Ashted, Surrey, KT21 2TW.

VHF

Reports on VHF matters to **Ron Ham**, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

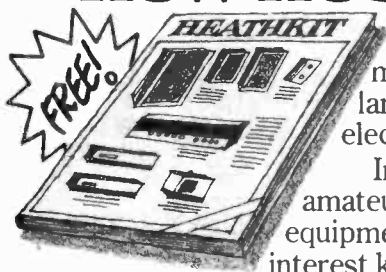Your free start to a rewarding new hobby.



Heathkit make the world's largest range of electronic kits.

Including hi-fi, amateur radio, test equipment and general interest kits.


Every one of which comes to you absolutely complete—right down to the last nut and bolt.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

So, besides making an attractive, useful piece of equipment, you'll also have the makings of a satisfying, rewarding hobby.

To find out more, post the coupon we'll send you our latest catalogue.

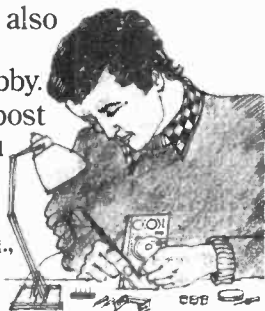Heath (Gloucester) Ltd., Dept. PW-37, Bristol Rd., Gloucester, GL2 6EE. Tel: Glos (0452) 29451.



HEATHKIT

BETTER BUILT BECAUSE YOU BUILD IT YOURSELF

The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Ltd., Dept. PW-37, Gloucester, GL2 6EE. Please send me my Heathkit catalogue. I enclose an 11p stamp for postage.



Name _____


Address _____

Postcode _____

EASY TERMS AVAILABLE WITH HEATHKIT MONTHLY BUDGET PLAN

Showrooms at 233 Tottenham Court Road, London and Bristol Road, Gloucester.

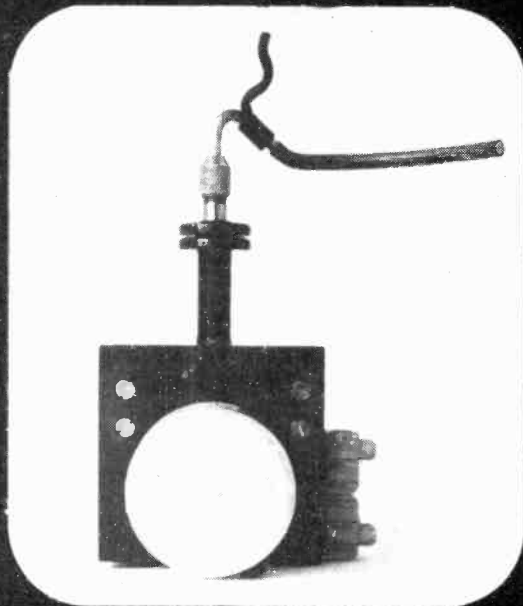The DECCALIFT for armchair control of the orchestra



The higher the price you have paid for your high fidelity equipment the lower the chance you have of obtaining the maximum enjoyment from it.

If you have the very best high fidelity equipment you will have to lower the pick-up arm manually—probably using one of the various mechanical aids available, since in the past any automatic method of raising or lowering the arm might lead to a deterioration in the high performance of your equipment.

The Deccalift is a motorised raising and lowering device which can be controlled from the comfort of your armchair. Just press to lower and press again to raise; allowing you to start and stop the music whilst sitting in your favourite listening position.

The Deccalift makes it possible for you to enjoy to the utmost the pleasure of high fidelity sound reproduction. It has been designed for the hi-fi enthusiast who aims for the highest standard of equipment.



For full details write to:

Decca Special Products, Ingale Place, Queenstown Road, London SW8 3NT

15-240 Watts!

HY5 Preamplifier


The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:

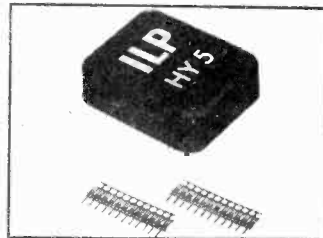INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input Impedance 4.7k Ω at 1kHz.
OUTPUTS: Tape 100mV; Main output 500mV R.M.S.
ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.
DISTORTION: 0.1% at 1kHz. Signal/Noise Ratio 68dB.
OVERLOAD: 38dB on Magnetic Pick-up. SUPPLY VOLTAGE \pm 16-50V.
Price £4.75 + 59p P&P free.



HY30 15 Watts into 8 Ω

The HY30 is an exciting New Kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:

OUTPUT POWER: 15W R.M.S. into 8 Ω ; **DISTORTION:** 0.1% at 1-5W.
INPUT SENSITIVITY: 500mV. **FREQUENCY RESPONSE:** 10Hz-16kHz—3dB.
SUPPLY VOLTAGE: \pm 18V.
Price £4.75 + 59p VAT P&P free.

Available
June '76

HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier

SPECIFICATIONS:

INPUT SENSITIVITY: 500mV
OUTPUT POWER: 25W RMS into 8 Ω **LOAD IMPEDANCE:** 4-16 Ω **DISTORTION:** 0.04% at 25W at 1kHz
SIGNAL/NOISE RATIO: 75dB **FREQUENCY RESPONSE:** 10Hz-45kHz—3dB
SUPPLY VOLTAGE: \pm 25V **SIZE:** 105 50 25mm
Price £6.20 + 77p VAT P&P free.



HY120 60 Watts into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS:

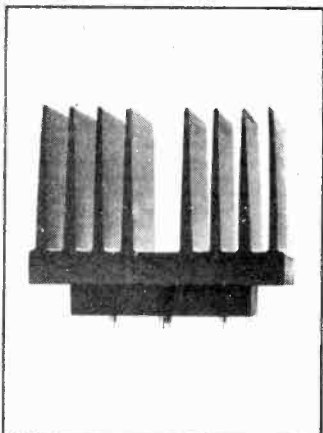INPUT SENSITIVITY: 500mV.
OUTPUT POWER: 60W RMS into 8 Ω **LOAD IMPEDANCE:** 4-16 Ω **DISTORTION:** 0.04% at 60W at 1kHz
SIGNAL/NOISE RATIO: 90dB **FREQUENCY RESPONSE:** 10Hz-45kHz—3dB **SUPPLY VOLTAGE:** \pm 35V
SIZE: 114 50 85mm
Price £14.40 + £1.15 VAT P&P free.



HY200 120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS:

INPUT SENSITIVITY: 500mV
OUTPUT POWER: 120W RMS into 8 Ω **LOAD IMPEDANCE:** 4-16 Ω **DISTORTION:** 0.05% at 100W at 1kHz
SIGNAL/NOISE RATIO: 96 dB **FREQUENCY RESPONSE:** 10Hz-45kHz—3dB **SUPPLY VOLTAGE:** \pm 45V
SIZE: 114 100 85mm
Price £21.20 + £1.70 VAT P&P free.

HY400 240 Watts into 4 Ω


The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco address applications, if the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS:

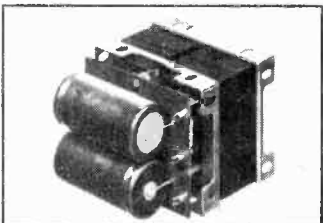OUTPUT POWER: 240W RMS into 4 Ω **LOAD IMPEDANCE:** 4-16 Ω **DISTORTION:** 0.1% at 240W at 1kHz
SIGNAL NOISE RATIO: 94dB **FREQUENCY RESPONSE:** 10Hz-45kHz—3dB **SUPPLY VOLTAGE:** \pm 45V
INPUT SENSITIVITY: 500mV **SIZE:** 114 x 100 x 85mm
Price £29.25 + £2.34 VAT P&P free.



POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus 59p VAT. P/P free.
PSU50 suitable for two HY50's £6.20 plus 77p VAT. P/P free.
PSU70 suitable for two HY120's £12.50 plus £1.00 VAT. P/P free.
PSU90 suitable for one HY200 £11.50 plus £0.92 VAT. P/P free.

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House
Nackington, Canterbury
Kent CT4 7AD
Tel. (0227) 63218

Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number _____
Name and Address _____
Signature _____



PLASTIC BOXES IN 5 SIZES

Easily drilled or punched, grey ABS boxes incorporate slots for 1.5mm pcb's with lid fixing screws running into integral brass bushes


100x50x25mm	51p	(1-9)	49p	(10+)
112x62x31mm	59p	(1-9)	52p	(10+)
120x65x40mm	68p	(1-9)	62p	(10+)
150x80x50mm	77p	(1-9)	74p	(10+)
190x110x60mm	£1.33	(1-9)	£1.30	(10+)

Polystyrene version

Plain inside, no integral bushes
112x61x31mm 35p (1-9) 32p (10+)
Add 25p per £1 order value for Post & Packing

TYPE A NEON INDICATORS

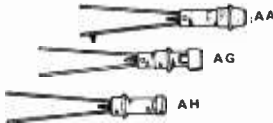Held in 8mm hole by plastic bezel
150mm wire leads



Red, Amber, Clear, Opal 19p each
Green 28p each

TYPE MP NEON INDICATOR

150mm leads, held in 6.4mm hole by nut




Red, Amber, Clear, Opal 20p each

On all orders quote reference PW/3/77.

Stop wasting time soldering

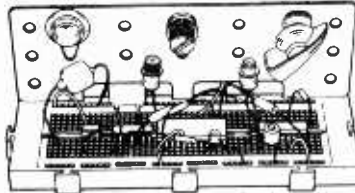
The NEW MW BREADBOARD accepts
Transistors, LED's, Diodes, Resistors, Capacitors
and all DIL packages with 6 to 40 pins



Includes slot-in Component Support Bracket and has over 400 individual sockets, plus Vcc & Ground Bus Strips
Price £9.72 (includes VAT & P.P.)

POWERFUL 12 VOLTS MINI HAND DRILL

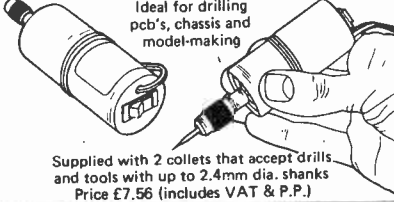Ideal for drilling
pcb's, chassis and
model-making



Supplied with 2 collets that accept drills and tools with up to 2.4mm dia. shanks
Price £7.56 (includes VAT & P.P.)

SEVEN SEGMENT DISPLAYS


Economy Quality - Only 66p
0.3" - Red
Common Anode - Left Decimal



Full specification displays also available
Red, Green and Yellow
£1.35 each inc. data

P.P. Note. Unless included in price add 25p post & packing for orders totalling under £10. Prices include VAT and are valid in UK only for 2 months from journal issue date.

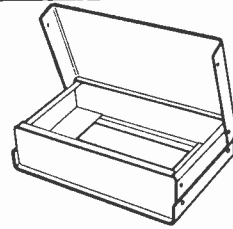Michael Williams Electronics
47 Vicarage Av., Cheadle Hulme, Cheshire SK8 6JP




EYE CATCHING INSTRUMENT CASE

Removable Red, Orange or Grey covers
Black chassis with support brackets
Overall size 250x167x68mm
Price £11.86 (includes VAT & P.P.)

ECONOMY QUALITY LED's

50 for only £5
100 for only £9

Mixed bags, all sizes, various colours

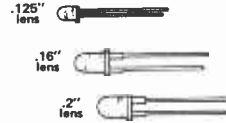

FULL SPEC. INDIVIDUAL LED's

Red (any size) £0.75/package
Green, Yellow, Orange (any size) £1.20/package
Packs contain 5 LED's, clips and data



DH LAMPHOLOER

For LS or Midget flange lamps
13mm hole fixing, lamp not included
Red, Blue, Green, Amber, Clear, Opal, Orange
Price 25p each (See P.P. Note below)

Quantity quotations on request.

SOUTHERN VALVE COMPANY


Upper Floor, 3 Potters Road,
New Barnet, Herts. Tel: 01-440 2641

"QUALITY" Valves—90 day guarantee. ALL
NEW & BOXED VALVES (Incl. tax)—many makes.
Radio Societies, trade etc. welcome.

AZ31 80p	POC85 44p	PY801 41p
DY86/7 36p	POC88 62p	UBF89 47p
DY802 42p	POC89 50p	UOC85 46p
EB91 18p	POC189 53p	UCH42 75p
EOC81 36p	POC80 40p	UCB81 43p
EOC82 35p	POF82 50p	UCL82 42p
EOC83 34p	POF86 58p	UCL83 58p
EOC85 40p	POF200 95p	UF41 68p
EOC88 48p	POF801 50p	VP89 42p
EOC81 36p	POF802 55p	UL41 78p
EOC82 35p	POF805 £1.40	UL84 44p
EOC84 52p	POF806 50p	UY85 38p
EOC85 40p	POF808 £1.40	UZ5 72p
EOC88 48p	PCH200 77p	UZ6 60p
EOC81 36p	PCL82 37p	U191 60p
EOC82 35p	PCL83 50p	8/30L2 70p
EOC83 34p	PCL84 47p	8BW7 65p
EOC84 52p	PCL85 } 62p	8P28 60p
EOC85 40p	PCL86 } 62p	8V6 47p
EOC88 48p	PCL200 £1.30	8L6 (near 99p
EF85 37p	PD500 £2.25	equiv KT66)
EF86 36p	PFL200 78p	20L1 80p
EF88 38p	PL56 70p	20P4 85p
EF89 38p	PL51 50p	30C1 40p
EF90 38p	PL51A 54p	30C15 78p
EL41 58p	PL82 38p	30C17 80p
EL42 58p	PL83 46p	30C18 £1.40
EL43 58p	PL84 46p	30F6 60p
EL44 58p	PL85 } 85p	30FL1 } 97p
EL45 58p	PL86 } 85p	30FL2 } 97p
EL46 58p	PL87 } 85p	30L1 40p
EL47 58p	PL88 } 85p	30L15 78p
EL48 58p	PL89 } 85p	30L17 72p
EL49 58p	PL90 } 85p	30P12 78p
EL50 58p	PL91 } 85p	30P19 70p
EM84 50p	PL92 } 85p	30PL1 £1.40
EY81 47p	PL93 } 85p	30PL13 75p
EY82/7 38p	PL94 } 85p	30PL14 85p
EZ40/1 53p	PL95 } 85p	30PL15 85p
EZ80 85p	PL96 } 85p	30P4MR 80p
EZ81 30p	PL97 } 85p	
GY501 41-10	PL98 } 85p	
QZ30 45p	PY83 82p	
PC88 85p	PY81/3 41p	
PC89 85p	PY88 41p	
PC87 40p	PY600 110p	
PC800 40p	PY500A 110p	
PC84 40p	PY800 41p	

We offer return of post service. Post free over £15.00. Postage: 1st valve 9p, extra valves 6p. Max. 75p. Most types available, send see for lists. Discount Prices. All prices subject to alteration without notice due to market fluctuations etc. Telephone enquiries welcomed, see with enquiries PLEASE! C.W.O. ONLY. No C.O.D. Export enquiries welcomed. VAT invoices on request. Mail order only. (LARGE valves 2p extra).

INTER-LOCKING PLASTIC STORAGE DRAWERS

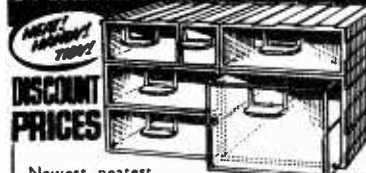

NEW! Improved 1980's
DISCOUNT PRICES
Newest, neatest system ever devised for storing small parts and components; resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

AS SUPPLIED TO POST OFFICE, INDUSTRY & GOVERNMENT DEPTS.

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins). £2.50 DOZEN.
DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins). £4.40 DOZEN.
TREBLE (3D) £4.20 for 8.
DOUBLE TREBLE 2 drawers, in one outer case (6D2), £6.50 for 8.
EXTRA LARGE SIZE (6D1) £5.50 for 8.

PLUS QUANTITY DISCOUNTS!
Orders over £20, less 5%.
Orders over £60, less 7%.

PACKING/POSTAGE/CARRIAGE: Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance

All prices correct at time of going to press
FLAIRLINE SUPPLIES
(Dept. PW3)
124 Cricklewood Broadway, London NW2
Tel. 01-450 4844

Camera Kits and Ready Built Modules



Please send 10 x 12 15p stamp addressed envelope

Whether professional student, teacher or amateur a CROFTON module is the answer

CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

Apart from our popular C.C.T.V. Camera Kits we are launching a range of ready built, tested, and guaranteed electronic modules both for trade and end user. The ultimate range will be extensive. Some of the existing modules available are:-

- E.T.I. Master Mixer
- E.T.I. Electronic Ignition
- Wide range R.F. Wobulator
- E.T.I. Digital Voltmeter
- E.T.I. Frequency Meter
- Video Amplifier
- Video Mixer
- Sound/Video Modulator
- Guitar Amplifier
- As well as all E.T.I. P.C.B.'s
- V.L.F. Transmitters & Receivers
- Send S.A.E. for information.

Secondhand cameras and monitors always available.

NOTE PCBs for most published projects available to order
CROFTON ELECTRONICS LTD
Depl. B, 35 Grosvenor Road, Twickenham, Middx. Tele. 01-891 1923

CONTROL DRILL SPEEDS

DRILL CONTROLLER

Electrically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3.45 including post & VAT. Made up model £1.00 extra.

MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 8v., 12 volts for up to 500mA (class B working). Taken the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: main transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1.50 VAT & Postage 50p.

RADIO STETHOSCOPE

Easiest way to find fault. Traces signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Complete kit comprises two special transistors and all parts including probe tube and crystal ear-piece. £2.95, twin stetho-est instead of ear-piece. £1.00 VAT and postage incl.

MICRO SWITCH BARGAINS

Rated at 5 amp, 250 v., ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 for £1.00, VAT and post paid.

MOTORIZED DISCO SWITCHES

With six 10 amp changeover switches. Multi adjustable switches are rated at 10 amp each so a total of 2000w's can be controlled and this would provide a magnificent display. For mains operating £4.95 post & VAT Paid. Ditto 9 switch £4.95 Post & VAT Paid. DITTO BUT 12 SWITCH £5.75 Post & VAT Paid.

MAINS OPERATED SOLENOIDS

Model TT2—small but powerful 1in. pull—approx. size 1 1/2 x 1 1/2 x 1 1/2in., £1.00
Model 4001—1in. pull. Size 2 1/2 x 2 1/2 x 1 1/2in., £1.50
Model TT1—1 1/2in. pull. Size 3 x 2 1/2 x 2 1/2in., £1.50
Price include VAT & postage.

SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Units in box all ready to work. £7.95 plus 95p VAT & Postage

RELAY BARGAIN

Type 600 relay with twin 500 ohm coils which may be joined in series or parallel thus relay will operate off voltages between 5 and 30 volts DC. Price 44p each, 10 for £4 post and VAT paid.

BATTERY CHARGER

Famous Atlas in metal case with meter, output lead terminated by crocodile clips. For 6 or 12V charging simply by changing plug on front by changing plug on front by changing plug on front. Ready built, new and still £2.95 plus £1 Post & VAT

MULTISPEED MOTORS

Six speeds are available 500, 850 and 1,100 r.p.m. and 7,000, 9,000 and 11,000 r.p.m. Shaft is 1/2 in. diameter and approximately 1 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia x 5 in. long. Price £2.00 including Post & VAT.

SWITCH TRIGGER MATS

So this is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in x 18in £2.35. Post & VAT 60p.
18in x 10in £1.85. Post & VAT 50p.

ROTARY PUMP

Self priming, portable, fits drill or electric motor, pumps up to 200 gallons per hour depending upon revs. Virtually uncorrodible, use to suck water, oil, petrol, fertilizer, chemicals, anything like liquid. Hose connectors each end. £2.00 Post Paid.

SPIT MOTOR WITH CARTER GEAR BOX

Probably one of the best spit motors made. Originally intended to be used in very high priced cookers however this can be put to plenty of other uses, for instance your garden barbecue or to drive a tumbler for stone polishing; in fact, there are no ends to its uses. Normal mains operation. £3.25 including Post & VAT.

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Goodmans speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14.00 including VAT and postage.



TANGENTIAL HEATER UNIT

This heater unit is most efficient, and quiet running. It is fitted in Hoover and blower heaters costing £15 and more. Comprises motor, impeller. 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £5.83 plus VAT & post £1. 2kW Model as above except 2kW £4.25 plus VAT & post 75p. Don't miss this. Control Switch 44p. P. & P. 40p.

ISA ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you wake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.95, VAT & Postage 60p, or with glass front, chrome bezel, £1.50 extra.

ROOM THERMOSTAT

Famous Satchwell, elegant design, intended for wall mounting. Will switch up to 20 amps at mains voltage, covers the range 0-30°C. Special snip this month £2.50, post and VAT paid.

SMITHS CENTRAL HEATING CONTROLLER

Price £7.50 including VAT and postage.

RANDALL CENTRAL HEATING CONTROLLER

Price £6.50 including VAT and postage.

THIS MONTH'S SNIP

250 WATT TRANSFORMER

Heavy duty power transformer which can be used for many purposes. Rated at 250 watts it is very well built with frames for upright mounting and is varnish impregnated. Its primary is for 230/240 volts 50 cycles, it has four secondaries each 10v very high current windings. Just a few of the circuits it can power are 10-0-10v at up to 12 amps, 20-0-20v at up to 6 amps; single 10v at 25 amps; single 20v at 12 1/2 amps; single 30v at 9 amps, single 40v at 8.5 amps. The transformer can be used for power circuits (charging, etc.) or for amplifiers, there being an input screen between primary and secondaries. A transformer like this today would cost at least £15 from the makers, however, we are making a special offer at £5.95 Post & VAT Paid. Grab some while you can, our stock may not last long.

AEROSOL RELEASE LUBRICANT

Dry Film Lubricant. In aerosol can for easy application and for putting lubricant in places where the normal oil can't reach. Home and everyday uses. We have purchased a large quantity of these from the Liquigrator and are able to offer them to you for about half of the original list price. 85p per 8oz can or 12 cans for £5 Post & VAT Paid. The lubricant is I.C.I. fluon LI69.

MAINS RELAYS

With triple 10 amp changeover contacts—operating coil wound for 230 volts AC, chassis mounting, one screw fixing, ex unused equipment 60p each, 10 for £5 post and VAT paid.

HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously

Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact, there is no limit to the versatility of this Programmer. Mains operated, Size 3in x 3in x 2in deep. Price £5.50. 80p Post and VAT, as illustrated but less case

SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 31, 29 metre bands. Kit contains chassis front panel and all the parts £1.90—crystal ear-phone 55p including VAT and postage.

PAPST MOTOR

West German make, these fine motors are noted for their performance and reliability. Special features are the rotating heavy outer which acts as a flywheel to eliminate wow and flutter and switchable reversing. We have four types in stock, all 1350 revs., including starting capacitor.

- (1) Reference No. KLZ 20.50-4, 230 volts 50HZ, price £5.50
- (2) Reference No. KLZ 32.50-4, 230 volts 50HZ, price £5.50
- (3) Reference same as above, 115 volts 50HZ, price £2.50
- (4) Reference same as above, 110 volts 60HZ, price £2.50

Post and VAT 80p each extra.

ITS FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—its an interesting list and its free—just send S.A.E. Below are a few of the Bargains still available from a recent list.

Remember 7.029? Electricians of the old school most certainly will, and will agree it has greater current capacity (20 amps against 13 amps) and being stranded it will not break so easily and being larger it is easier to use. A fortunate buy enables us to offer 3 core 7.029 cheaper than we could offer 3 core 2.6mm. If you are contemplating installing a ring main, an immersion heater, storage heaters or fires, then you should definitely buy some of this cable. It is p.v.c. covered, correctly colour coded and up to all British standards; in fact, was made by one of our most famous cable companies. Price £3.50p + 75p per 100 metre coil. Carriage £2.50 + 20p.

For lighting we offer 3 core 1.8mm only £5.50p + 44p per 100 metres. Post £1.50 + 12p.

Isolation Transformer. Very high current 415 amps, primary 0-260 volts, last 60 volts in 10 volt steps so this transformer can be used to step up voltages for instance at the end of a long cable run. Secondary, 0-20v. -0.130v so this transformer will isolate and step down voltage will isolate at normal mains in and normal mains out or finally it will isolate and step up. A big transformer completely enclosed in sheet steel box weighing about 300 lbs. Price £100 + 32. Carriage as cost but we would prefer you to collect this.

5 Bank Switch Panel. A simple and convenient Burpium item so it is very well made and contains switches which will break 15 amps DC. The 5 switches are completely separate so may be used to control separate circuits or they may be ganged together to bring in 5 heaters in parallel suitable for mains or battery work. Size of the switch is approximately 5 1/2 x 1 1/2 in. An operation is by nickle plated toggles. Price 75p each + 6p. Post 20p + 2p.

Cooling Thermostat. The normal thermostat switches off as the temperature in the room rises. It is, therefore, suitable for controlling electric room heating. We have a simple thermostat but with contacts which switch on as the temperature rises. These are for air conditioning or cooling circuits. Contacts again rated at 20 amps and these have changeover contacts so they can be used for cooling or heating or both but as their original function was intended for cooling they are set and calibrated for 12-40°F. Price £3.50p + 25p.

Flash Ernie is the name we have given to our latest disco light display because it is a random flasher and is very effective especially with coloured bulbs. Kit consists of motorised stud switch, master control switch, anti spark caps, 9 lamp holders, connecting wire and wiring diagram. Price £5 + 40p. Post 50p.

Neon Novelties. One of the most versatile of electronic devices is the neon, you can make it do all sorts of things to regulate voltage, imitate "Ernie" by lighting numbers at random. We have miniature neons at 20p each also just come in neon values 4 pin type, 10 for £1 + 5p. Post 50p + 4p.

Emergency Lighting. We are coming up to the darkest and coldest days so most of us will have memories of power cuts during the previous similar periods. If you are thinking of installing temporary emergency lighting at all you might be interested to know that we have just received some Philips invertors for working 12" fluorescent tubes from 12v car batteries. We are able to offer these invertors at half the proper price, namely £1.50p + 12p. Post 40p + 3p.

Miniature Tubes also available 12" 75p + 6p., no extra post if ordered with invertors, bi pin holders for these miniature tubes 10p + 1p each.

Central Heating; Regulating, Mixing, Pumping System. In addition to circulating the water through the system, this can be used to regulate the supply to upstairs radiators or to domestic water or central heating as in addition to normal pumping (which is itself adjustable 4 ways) the output of the pump passes first through a valve system, this valve system is motorized (or can be hand operated) and can be made to share the output evenly between two sets of pipes or can be made to give an increase in amount to one at the expense of the other. In the Spring for instance, you may not want much heat going through to your radiators but you still want maximum for baths etc. During the daytime you do not want to heat the bedrooms so you can send all the heat through the downstairs rooms etc. The pump is for normal mains operation and comes complete with 4 pipe unions. Summary of the special features of this system is as follows:—Inductive pump drive (without shaft). Self cleaning pump construction, continuous water lubricated rotor, pump output adjustable in 4 stages. Switch to gravity circulation possible. Accurate automatic temperature regulation ± 1°C. We understand that the regular price of this pump is around £40. Our price is £20 + £1.60p. Post £3.24p.

Panel Meters mainly G.P.O.
(1) 3" x 2 1/2" flush mounting, 25UA f.s.d., scale calibrated 0-1000 meg ohms ideal if you are thinking of making a portable insulation tester. Price £3.24p. Post 40p + 4p.
(2) Edgemounting, size 3" x 1 1/2" scaled meg ohms, specification same as above.
(3) 3" x 2 1/2" centre zero 25-0-25 mA special purpose scale, price £2.50p + 20p. Post 40p + 4p.
(4) 3" circular scaled 0db-0mius 15 plus with current transformer. 0db 1 mW 600 ohms. Price £4 each + 32p. Post 40p + 4p.

TERMS: Where order is under £6 please add 50p surcharge to offset packing expenses

J. BULL (ELECTRICAL) LTD.

(Dept. P.W.), 103 TAMWORTH ROAD,
CROYDON CR9 1SG.

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE



CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

- | | | |
|--|--|---|
| <input type="checkbox"/> ELECTRICAL & ELECTRONICS | <input type="checkbox"/> Radio, Servicing & Repairs | <input type="checkbox"/> Painting & Decorating |
| <input type="checkbox"/> Practical Radio & Electronics (with KIT) | <input type="checkbox"/> Radio Amateur's Exam. | <input type="checkbox"/> MECHANICAL |
| <input type="checkbox"/> Electronic Engineering Certificate | <input type="checkbox"/> AUTO & AERO | <input type="checkbox"/> A.M.S.E. (Mech.) |
| <input type="checkbox"/> General Elect. Eng. Certificate | <input type="checkbox"/> Motor Mechanics | <input type="checkbox"/> General Mech. Eng. |
| <input type="checkbox"/> C. & G. Elect. Installations | <input type="checkbox"/> C. & G. Motor V. Mechanics | <input type="checkbox"/> Inst. Engineers & Technicians |
| <input type="checkbox"/> Elect. Install. & Work | <input type="checkbox"/> General Auto Engineering | <input type="checkbox"/> Maintenance Engineering |
| <input type="checkbox"/> C. & G. Elect. Technicians | <input type="checkbox"/> A.M.I.M.I. | <input type="checkbox"/> Welding |
| <input type="checkbox"/> RADIO & TELECOM. MUNICIPALITIES | <input type="checkbox"/> Air Registration Board Certs. | <input type="checkbox"/> MANAGEMENT & PRODUCTION |
| <input type="checkbox"/> Colour TV Servicing | <input type="checkbox"/> M.A.A./I.M.I. Dip. | <input type="checkbox"/> Computer Programming |
| <input type="checkbox"/> C. & G. Telecoms. Technician's Cert. | <input type="checkbox"/> CONSTRUCTIONAL | <input type="checkbox"/> Inst. of Cost & Managements Accts. |
| <input type="checkbox"/> C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> Heating, Ventilating & Air Conditioning | <input type="checkbox"/> DRAUGHTS-MANSHIP & DESIGN |
| <input type="checkbox"/> Radio & TV Engineering Course | <input type="checkbox"/> Architectural Draughtsmanship & Design | <input type="checkbox"/> General Draughtsmanship |
| | <input type="checkbox"/> L.I.O.B. | <input type="checkbox"/> A.M.I.E.D. |
| | <input type="checkbox"/> Carpentry & Joinery | <input type="checkbox"/> Electrical Draughtsmanship |
| | <input type="checkbox"/> Plumbing Technology | |
| | <input type="checkbox"/> General Building | |



G.C.E.
—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPW 21, Reading RG7 4PF.
also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 628 2721.

NAME (Block Capitals)

ADDRESS

..... Postcode.....

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

complete DIGITAL CLOCK KITS TEAK CASES



prompt order despatch
NON-ALARM £10.65
+ VAT £0.85
ALARM £13.43
+ VAT £1.07
including P & P

"DELTA"

GENUINE TEAK OR PERSPEX CASE
DELTA DATA: 4 Radiant Red 1/4 inch high LEDs. 12hr display with AM/PM indication. Beautiful Burma Teak Case or Pretty Perspex in White, Black, Blue, Red, Green. Power failure is indicated by flashing display.
MODULES: Kits can be bought without case: Non Alarm £9.00 Alarm £12.50 inclusive.
READY BUILT: Buy a working tested module and fit your own case. Non Alarm £9.50, Alarm £13.00, Complete Clock ready built. 2 yr guarantee. Non Alarm £13.50 Alarm £16.50.
ALARM FEATURES: Pulsed tone. Tilt operated 10 minute 'Snooze' period. Single switch setting Optional extra mercury switch (45p) allows Alarm reset by tilting clock. Digit brightness is automatically controlled to suit lighting level.

"ALPHA"

4 Glowing Green 1/4" high digits 12 or 24 hour. Non Alarm. **£11.00 inc.**
Built & Tested module plus perspex case.
Clock chip AY5-1202 only £2.50. Discount on orders for 6 or more kits/clocks
Send payment with order. S.A.E. for complete range. Overseas: Add £2.50 Airmail.

PULSE ELECTRONICS LTD
DEPT. PW4, 202 SHEFFORD ROAD,
CLIFTON, SHEFFORD, BEDS.
Telephone Hitchin (0462) 814477

SOLDERLESS BREADBOARDING—DECS

The famous DEC System of Solderless Breadboarding is ideal for both the young and more mature students of Electronic Engineering as it enables circuits to be tried and tested without the use of soldering and because of the specially designed contacts allows components to be used over and over again. It is also extremely useful for the Circuit Designer who wishes to experiment with and perfect his circuit quickly yet economically.

- S-DEC (Model PB11)**
This, the most popular Board, is designed solely for the use of discrete components and is particularly useful for basic educational purposes.
(No. of Contacts: 70) 1 off £1.98
5 off £1.76
- T-DEC (Model PB21)**
This Board allows 2 TO5 or 1 DIL IC Station to be used and so is primarily intended for discrete work or for linear IC application where considerable numbers of discrete components may be required.
(No. of Contacts: 208) 1 off £3.82
5 off £3.21

- μ-DEC 'A' (Model PB31)**
The μ-DEC 'A' is specially designed for ease of use with IC's and allows 2 DIL or 4 TO5 stations to be used but will accommodate discrete components with equal facility.
(No. of Contacts: 208) 1 off £3.97
5 off £3.53

- μ-DEC 'B' (Model PB41)**
The μ-DEC 'B' is for similar uses as μ-DEC 'A', but has two 16 lead IC sockets as part of the Board.
(No. of Contacts: 208) 1 off £6.97
5 off £6.19

DEC ACCESSORIES

- | | |
|---------------------------------------|-------|
| 16 DIL adaptor (with socket) PB062 | £1.92 |
| 10 TO5 adaptor (with socket) PB072 | £1.80 |
| Single ended leads (set of ten) PB101 | £0.90 |
| Double ended leads (set of ten) PB102 | £0.95 |
| 1mm plugs (set of ten) PB103 | £0.45 |

All prices include 8% VAT. P. & P. 25p.
Our retail counter is now open, stocking a large variety of audio and electronic parts and accessories, branded and surplus.

WE ARE SITUATED 2 MIN. WATFORD JUNCTION STATION
THE COMPONENTS CENTRE
7 Langley Road, Watford, Herts., WD1 3PS.
Tel.: Watford 45335

NEW MULLARD & MAZDA VALVES

All individually boxed.
Full trade discounts to
bona fide companies.
Prices on application.

**EXPRESS
POSTAGE**

15p for 1 Valve.
Each additional Valve
add 2p in UK.

DM70	0.69	EF80	0.62	PCC84	0.84	PL504	1.40	30C15/	
DY86/7	0.70	EF83	1.10	PCC85	1.02	PL508	1.73	PCF8001	22
DY802	0.53	EF85	0.70	PCC88	0.98	PL509	2.33	30C17	1.28
EB91	0.97	EF86	1.73	PCC89	0.97	PL802	2.33	30C18/	
EBF81	0.89	EF89	1.73	PCC189	1.22	PY33	0.73	PCF8051	29
EBF80	0.63	EF92	1.51	PCF80	0.34	PY81/800	0.72	30F5/PF818	
EBF83	0.66	EF95	1.63	PCF86	0.97	PY92	0.70	30FL1/	1.35
EBF89	0.50	EF184	0.93	PCF200	1.50	PY88	0.84	PCF8000	98
EC85	0.82	EF183	0.93	PCF201	1.50	PY500A	1.50	30FL2	1.02
EC88	0.86	EH90	1.22	PCF801	0.97	PY800	0.72	30FL12	1.44
EC90	0.94	EL34	1.40	PCF802	1.02	PY801	0.72	30FL14	1.20
EC97	0.69	EL36	1.50	PCF806	0.97	U26	1.22	30L1/PCC84	
ECC81	0.70	EL84	0.70	PCF200	1.50	U191	1.17	30L15/	0.63
ECC82	0.70	EL86	1.40	PCL82	0.84	U193	0.56	PCC8051	35
ECC83	0.70	EL95	1.02	PCL83	0.97	UBF81	0.80	30L17	1.12
ECC84	0.63	EM81	1.24	PCL84	0.93	UBF89	0.65	30L17	1.12
ECC85	1.02	EY51	0.89	PCL85	0.72	UCF85	0.66	30P4MR	1.63
ECC88	1.22	EY86	0.50	PCL86	0.97	UJ181	1.73	30P12/	
ECC189	0.77	EF95/87	0.70	PCL805/		UJ182	1.02	PC801	1.22
ECF80	0.63	EY85	0.70	PCF80	0.34	UL82	0.62	PC802	1.06
ECF82	0.90	EZ80	0.84	PD500	2.92	UL84	1.23	PC801	1.06
ECF86	0.78	EZ81	0.70	PLF200	1.23	U191	0.73	PCL801	1.35
ECF81	1.73	GY501	1.73	PL36	1.40	U85	0.73	30P11/	
ECF93	1.06	GZ34	1.22	PL81	1.23	6/30L2/		PCL801	1.35
ECF94	1.50	OC83	0.60	PL81A	1.40	6/23/EF812		PCL800	1.47
ECF90	1.02	OC86	1.40	PL82	0.48	30C1/PCF80		PCL88	1.72
ECL82	0.69	PC86	1.40	PL83	0.73	30C1/PCF80		30P14/	
ECL83	0.63	PC87	0.70	PL84	0.02	30C1/PCF80		30P15	1.44
ECL83	0.63	PC87	0.70	PL84	0.02				
ECL86	0.82	PC900	6.84	PL500	1.40				

NEW VALVES

Individually boxed and
guaranteed but of Euro-
pean or other origin at
greatly reduced prices.
Quotations for any
valve not listed.

AZ1	1.00	EF39	1.25	OB2	0.45	PY801	0.55	6J5G	0.45
AZ31	1.00	EF80	0.35	PC86	0.65	SP41	0.00	6J8	0.35
CL33	1.50	EF88	0.45	PC87	0.55	SP81	0.35	6V7G	0.80
CBL31	1.40	EF85	0.45	PC86	0.65	T41	1.50	6J7M	0.85
CCY31	1.00	EF89	0.35	PC900	0.55	U14	0.75	6K6GT	0.60
DAF81	0.40	EF91	0.40	PCC84	0.45	U26	1.00	6K7G	0.85
DAF98	0.80	EF92	0.50	PCC88	0.62	U26	0.85	6K8G	0.45
DCY90	1.85	EF95	0.45	PCC89	0.62	U191	0.75	6K8C	0.45
DF81	0.40	EF98	0.80	PCC189	0.65	UAF42	0.75	6K25	1.00
DF95	0.60	EF183	0.40	PCF80	0.40	UBC41	0.60	6L8G	2.50
DK91	0.50	EF184	0.40	PCF82	0.42	UBC81	0.50	6L6GC	0.80
DK92	1.00	EL32	0.60	PCF86	0.65	UBF80	0.50	6Q7G	0.40
DK96	0.75	EL33	0.80	PCF801	0.60	UBF89	0.50	6Q7M	0.80
DL92	0.80	EL34	0.70	PCF802	0.55	UCC385	0.50	6SL7GT	0.55
DL84	0.85	EL36	0.60	PCF805	0.90	UCF85	0.50	6SN7GT	0.55
DY96	0.55	EL37	3.40	PCF906	0.80	UCL82	0.40	6SU7GY	0.40
DY86	0.45	EL41	0.90	PCF808	1.00	UCL83	0.70	6U5G	0.80
DY87	0.45	EL42	1.65	PCL82	0.45	UL41	0.85	6V6GT	0.60
DY802	0.47	EL95	0.60	PCL83	0.70	U41	0.85	6X5G	0.45
EABC80	0.38	EM80	0.55	PCL84	0.50	U41	0.85	6X5GT	0.55
EAF42	0.70	EM81	0.60	PCL85	0.60	U41	0.85	6Y86	0.80
EB91	0.30	EM84	0.40	PCL86	0.50	U41	0.85	7B7	0.50
EB33	1.00	EM85	1.00	PCL805/85	0.50	VR105/30	0.45	7C5	2.00
EB41	0.75	EY51	0.45	PD500	2.92	VR105/30	0.45	7C6	1.00
EBF80	0.40	EY85	0.50	PEN45	0.85	1R5	0.50	7H7	0.80
EBF83	0.40	EZ40	0.50	PL36	0.63	1S5	0.40	7R7	1.30
EBF89	0.32	EZ41	0.75	PL81	1.23	1R5	0.40	7S7	2.25
EEL31	2.00	EZ80	0.30	PL82	0.50	1R5	0.40	7Y4	0.30
ECC81	0.45	EZ81	0.81	PL83	0.50	3V4	0.85	12A7	0.45
ECC82	0.38	GY501	0.90	PL84	0.50	3R4G	1.20	12A7	0.45
ECC83	0.38	GZ30	0.65	PL85	0.85	5U4G	1.25	12A8	0.50
ECC84	0.35	GZ32	0.65	PL86	0.85	5U4GB	0.70	12A8	0.50
ECC85	0.45	GZ34	0.65	PL504	0.88	5Y3GT	0.65	12A7	0.38
ECC88	0.50	HN309	1.50	PL508	0.90	5Z4G	0.95	12BA6	0.50
ECC93	1.50	KT61	3.40	PL509	1.60	6/30C2	0.60	12BE6	0.60
ECH42	0.85	KT66	3.40	PL802	2.00	6A85	0.45	30C1	0.60
ECH81	0.35	KT81	1.00	PY33	0.83	6AM5	2.00	30C15	1.00
ECH83	0.50	(7C5)	2.00	PY81	0.50	6AQ5	0.50	30C17	1.00
ECL80	0.60	KT88	4.00	PY82	0.45	6AS7G	1.00	30C18	0.90
ECL82	0.42	KTW61	1.50	PY83	0.50	6AT8	0.60	30F5	1.00
ECL83	0.75	MU14	1.00	PY88	0.63	6A06	0.40	30FL1	1.00
ECL86	0.55	N78	7.50	PY90	1.10	6B86	0.75	30L15	0.95
EF37A	1.50	OA2	0.45	PY81/800	0.50	6B87	3.00	30L17	0.95

TRANSISTORS-INTEGRATED CIRCUITS

All transistors, I.C's
offered are new and
branded. Manufactured
by Mullard, Texas, RCA,
Ferranti, Motorola, ITT,
Fairchild, Lucas, etc.
Quantity discounts on
application.

**EXPRESS
POSTAGE**

15p per order in UK.

AA119	0.07	BD131	0.40	OA200	0.10	ZTX501	0.13	2N2005A	0.25
AA213	0.18	BD132	0.45	OA202	0.10	ZTX503	0.16	2N2906	0.22
AA215	0.12	BF115	0.20	OC16	1.25	ZTX531	0.25	2N2926	0.15
AC107	0.75	BF167	0.20	OC20	2.00	ZTX550	1.18	2N3053	0.20
AC126	0.25	BF173	0.25	OC23	2.25	IN914	0.08	2N3055	0.60
AC127	0.25	BF179	0.30	OC25	0.65	IN4001	0.07	2N3525	0.90
AC128	0.22	BF180	0.30	OC28	0.75	IN4002	0.07	2N3614	1.00
AC176	0.27	BF181	0.30	OC35	0.75	IN4003	0.08	2N3615	1.50
AC187	0.25	BF194	0.10	OC36	0.75	IN4004	0.08	2N3702	0.13
AC188	0.25	BF195	0.10	OC44	0.45	IN4005	0.09	2N3703	0.13
AC191	0.55	BF197	0.12	OC45	0.45	IN4006	0.11	2N3704	0.15
AC193	1.00	BF200	0.32	OC45	0.45	IN4007	0.11	2N3705	0.13
AD140	0.65	BFS61	0.25	OC72	0.45	IN4008	0.08	2N3706	0.13
AD149	0.65	BFS93	0.25	OC76	0.45	IS921	0.08	2N3708	0.09
AD161	0.45	BFW10	0.61	OC77	0.75	IS2033	0.20	2N3709	0.12
AD162	0.45	BFX29	0.28	OC77	0.75	IS2051A	0.20	2N3710	0.13
AD165	0.45	BFX88	0.25	OC81	0.28	IS2100A	0.20	2N3711	0.13
AF115	0.25	BFY50	0.21	OC81Z	1.00	IS3010	0.25	2N3819	0.37
AF117	0.25	BFY51	0.21	OC83	0.55	2N696	0.20	2N3820	0.55
AF186	1.60	BFY52	0.23	OC140	1.50	2N697	0.17	2N3823	0.60
AF239	0.45	BR100	0.40	OC170	0.50	2N706	0.12	2N3903	0.15
AFY27	0.45	BY100	0.45	OC171	0.50	2N706A	0.12	2N3904	0.15
AGY28	0.25	BY126	0.12	OC201	1.00	2N1131	0.23	2N3905	0.17
BA102	0.25	BY127	0.12	OC202	1.50	2N1302	0.30	2N3906	0.17
BA115	0.15	BFX61 series		OC202	1.50	2N1302	0.30	2N4058	0.16
BC107	0.14			OC203	1.50	2N1303	0.40	2N4059	0.12
BC108	0.14	BZY88 series		OC211	1.25	2N1304	0.45	2N4060	0.13
BC109	0.15			ORP12	0.60	2N1305	0.45	2N4061	0.13
BC113	0.15	CRS1-05	0.45	ORP20	0.65	2N1306	0.50	2N4062	0.14
BC114	0.22	CRS1-40	0.75	ORP50	0.65	2N1307	0.50	2N4289	0.30
BC143	0.25	CRS3-05	0.45	TIC44	0.30	2N1307	0.50	2N4289	0.30
BC147	0.10	CRS3-40	0.75	TIC226D	0.40	2N1308	0.50	3N125	0.75
BC148	0.08	MJE340	0.42	TIL209	0.22	2N1309	0.50	3N141	0.80
BC169C	0.15	MJE370	0.65	TIP24A	0.70	2N1613	0.21	40360	0.40
BC182	0.12	MJE520	0.60	TX107	1.00	2N1217	1.20	40361	0.45
BC182L	0.12	MJE2955	1.25	TX108	1.00	2N1218	0.75	40362	0.40
BC184L	0.12	MJE3055	0.75	TX300	1.12	2N2369A	0.25	40430	0.85
BC338	0.15	MPF102	0.40	TX301	0.13	2N2846	0.50		
BCY32	1.00	MPF103	0.40	TX301	0.13	2N2846	0.50		
BCY33	0.70	MPF104	0.40	TX302	0.17	2N2904	0.25		
BCY34	0.75	MPF105	0.40	TX304	0.22	2N2904A	0.25		
BCY70	0.13	NKT404	1.25	TX500	0.12	2N2905	0.30		
BCY71	0.22	OA5	0.75						
BCY72	0.17	OA10	0.85						
BCZ11	1.25	OA79	0.12						
BD121	1.55	OA81	0.15						
BD124	0.75	OA91	0.07						

XN7400	0.16	SN7428	0.40	SN7486	0.47	SN74145	1.26	XN74192	2.00
SN7401	0.16	SN7430	0.16	SN7490	0.55	SN74150	1.75	SN74193	2.00
SN7402	0.16	SN7433	0.37	SN7491A	1.00	SN74151	1.00	SN74194	1.30
SN7403	0.16	SN7437	0.37	SN7492	0.70	SN74152	2.00	SN74195	1.10
SN7404	0.26	SN7438	0.37						

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

NO HIDDEN EXTRAS

(Prices correct at 14th Dec. 1976)

† WHERE CARRIAGE WILL BE ACCORDING TO WEIGHT & DISTANCE—BR5.

Electrosil Resistors, Semiconductors, Multi-Meters

Wide Range of Panel Meters

MAINS ISOLATING

Prim. 220-240V
Sec. 120/240V
Centre tap with screen
Ref. VA (Watts) £

07*	20	4.57
149	60	6.97
150	100	7.65
151	200	11.95
152	250	14.47
153	350	17.14
154	500	19.73
155	750	27.25†
156	1000	37.97†
157	1500	43.33†
158	2000	48.34†
159	3000	76.36†

*115V or 240V Sec. only.

12 and or 24 Volt

Prim. 220-240 Volts
Amps

Ref.	12v	24v	£
111	0.5	0.25	3.01
213	1.0	0.5	3.69
71	2	1	5.10
68	3	1.5	5.61
18	4	2	4.56
85	5	2.5	5.61
70	6	3	6.36
108	8	4	7.34
72	10	5	7.86
116	12	6	8.39
17	16	8	10.48
115	20	10	15.42
187	30	15	19.50
226	60	30	21.94†

50 VOLT RANGE

Prim. 220-240V
Sec. 0.19-25-33-40-50V

Ref.	Amps	£
102	0.5	4.07
103	1.0	5.27
104	2.0	7.17
105	3.0	8.77
106	4.0	11.26
107	6.0	17.29
118	8.0	18.67
119	10.0	22.04†

TI MINI-MULTIMETER

DC-1000V AC-1000V 1000Ω/V
DCI-100mA RES-150kΩ
BARGAIN AT £6.21

ANTEX SOLDERING IRONS
15W £4.08 18W £4.08 25W £3.80
SOLDERING IRON KIT
£5.66 STAND FOR ABOVE £1.84

MAGNETIC TO CERAMIC CARTRIDGE CONVERTOR
OPERATING VOLTAGE 20-45V ONLY £3.59

SCREENED MINIATURES

Ref	mA	Volts	£
238	200	3-0.3	2.50
212	1A, 1A	0.6-0.6	2.97
13	100	9-0.9	2.28
235	330, 330	0.9-0.9	2.39
207	500, 500	0.8-0.8	3.14
208	1A, 1A	0.8-0.8	4.51
236	200, 200	0.15-0.15	2.28
214	300, 300	0.20-0.20	3.22
221	700 (DC)	20-12.0-12-20	3.66
206	1A, 1A	0.15-20, 0.15-20	5.37
203	500, 500	0.15-27, 0.15-27	4.77
204	1A, 1A	0.15-27, 0.15-27	6.00
5112	500	12, 15, 20, 24, 30	3.15

HIGH QUALITY MODULES

5 Watt RMS AMPLIFIER	£3.59
10 Watt RMS AMPLIFIER	£4.94
25 Watt RMS AMPLIFIER	£4.94
125W RMS AMPLIFIER	£17.61
PRE-AMP for 3-5-10W	£8.07
PRE-AMP for 25W	£15.57
POWER SUPPLIES 3-5-10W	£1.72
POWER SUPPLIES 25W	£4.43
TRANSFORMER 5-10W	£3.89
TRANSFORMER 25W	£5.74

AUDIO KIT 25W

2 - 25W Amplifiers
1 - Pre-Amp
1 - Power supply
1 - Transformer
1 - Front Panel
1 - Kit of parts to include on off switch, neon ind. Stereo headphone socket. Plus Instructions book £32.18.

TEAK AUDIO KIT 25W

Teak veneered cabinet aluminium chassis, heat sink and front panel brackets plus back panel and sockets etc. £11.21

CARTRIDGES

Magnetic Sonotone 100	£5.31
Ceramic E.E.I.CS 2000	£2.72
ACOS GP93-1	£2.38
AT-55	£4.42

POWER UNIT plugs

Direct into 13A 3 pin socket 6-75-9V 300mA £3.59

NEW STEREO 30

Complete Stereo Chassis inc.:
747W RMS, Amp, Pre-amp, Power Supply, Front Panel, Knobs (only needs Mains Trans.), Stereo 30 £18.89. Mains Trans £3.89. Teak veneered cab. £4.54.

STEREO FM TUNER fitted with Phase-lock Loop

4 Pre-selected stations supply 20-35V. 90mA Max. £24.21

HIGH VOLTAGE

Mains Isolating
Prim. 200/220 or 400/440
Sec. 100/120 or 200/240 VA

Ref.	£
60	243
60	247
1000	250
2000	252

AUTO TRANSFORMERS

VA Auto Tops

Ref	£
113	20
64	75
4	150
66	300
67	500
84	1000
93	1500
95	2000
73	3000

CASED AUTO TRANSFORMERS

240V cable in and USA 2 pin out.

Ref	£
20VA	£ 4.95
150VA	£ 8.94
500VA	£15.11
1000VA	£22.84
2000VA	£35.66

Electronic Construction Kit

10-Project (including electronic organ) ideal gift at £8.63. "No soldering"

DECS

Solderless Breadboarding
S Dec 70 contacts £2.41
T Dec 208 contacts £3.92
U Dec 'A' for IC's £4.58
U Dec 'B' for IC's etc. £7.82

BRIDGE RECTIFIERS

200V	2A	£ 0.67
400V	2A	0.72
200V	4A	0.89
500V	10A	2.70

TEST METERS

AVO 8 MK5	£67.33
AVO 72	£26.86
AVO MMS	£23.48
AVO TT 169	£22.94
U415	£16.52

POWER UNIT

3 - 4.5 - 6 - 7.5 - 9 - 12V at 500mA. £5.18.
Stab. 3-6-7.5-9V 400mA £6.98

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST



The Pictorial Method

BASIC ELECTRICITY (5vols) ELECTRONICS (6vols) TELEVISION (3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

My manuals are so easy to digest. I am delighted.
L.P., Huddersfield

The information is presented in such a self-explanatory way. I am truly indebted.
W.H., Highgate

I have a good job thanks to your excellent publications.
H.T. Enfield

I have struggled with other manuals, but yours read like an open book.
S.J. Addington

My qualification as a Training Instructor in Electronics is the result of possessing your manuals. Sincerely indebted.
W.P., Reading

Everything is described so simply. They are truly excellent.
J.P., Crystal Palace

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

- BASIC ELECTRICITY 5 parts £8.00
- BASIC ELECTRONICS 6 parts £9.50
- BASIC TELEVISION 3 parts £5.00

Tick Set(s) required. Prices include Postage
YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS
FULL POSTAL.....
ADDRESS

POST NOW FOR THIS OFFER!

PRINTED CIRCUIT KIT £4.25*
Make your own printed circuits. Contains etching dish, 100 sq ins of pc board, 1lb ferric chloride, daco pen, drill bit, laminate cutter.

JC12 AMPLIFIER

6W IC audio amp with free data and printed circuit £2.25*



DELUXE KIT FOR JC12

Contains extra parts except JC12 needed to complete the amp including balance, volume, bass and treble controls. Mono £2.39. Stereo £5.25

JC12 POWER KIT

Supplies 25V 1 Amp £3.85.

JC12 PREAMP KITS

Type 1 for magnetic pickups, mics and tuners. Mono £1.50. Stereo £3.90. Type 2 for ceramic or crystal pickups. Mono 88p. Stereo £1.76.

SINCLAIR IC20

10W+10W stereo integrated circuit amplifier kit with free printed circuit + data £4.95.

P220 Power supply kit for above £3.95.

VP20 Volume, tone-control and preamp kit £8.55.

JC49 AMPLIFIER

New integrated circuit 20W amplifier kit complete with chip, printed circuit and data £4.45.

FERRANTI ZN414

IC radio chip £1.44. Extra parts and pcb for radio £3.85. Case £1. Send see for free data.

BATTERY ELIMINATOR BARGAINS MILLERIA KITS*

5 Transistor highly stabilized power units. Switched 1 to 30V in 0.1V steps. Send see for free leaflet. 1 Amp kit £12.45. 2 Amp kit £14.95. Case £2.95 extra.

RADIO MODELS

50mA with press-stud battery connectors. 9V £3.75. 6V £3.75. 9V+9V £5.45. 6V+6V £5.45. 4½V-4½V £5.25.

CASSETTE MAINS UNITS

7½V with 5 pin din plug. 150mA £3.95

3-WAY MODELS*

With switched output and 4-way multi-jack connector. Type 1: 3/4½/6V at 100mA £3.20. Type 2: 6/7½/9V at 150mA £3.30.

FULLY STABILIZED MODEL £5.45*

Switched output of 3/6/7½/9V stabilized at 400mA. CAR CONVERTERS £5.10*

Input 12V DC. Output 6/7½/9V DC 1 Amp stabilized.

BATTERY ELIMINATOR KITS

Send see for free leaflet on range. 100mA radio types with press-stud battery terminals. 4½V £2.10. 6V £2.10. 9V £2.10. 4½V+4½V £2.80. 6V+6V £2.80. 9V+9V £2.80.

100mA cassette type 7½V with 5 pin din plug £2.10.

Transistor stabilized 8-way type for low hum. 3/4½/6/7½/9/12/15/18V. 100mA £3.50. 1 Amp £8.50.

Heavy duty 12-way types 4½/6/7½/9/11/13/14/17/21/25/28/34/42V. 1 Amp model £4.95. 2 Amp model £7.95.

Car converter kit Input 12V DC. Output 6/7½/9V DC 1A transistor stabilized £1.95.

MAINS TRANSFORMERS

6-0-6V 100mA £1. 9-0-9V 75mA £1. 18V 1A £1.95. 0/12/15/20/24/30V 1A £4.30. 12/0/12V 50mA £1. 0/12/15/20/24/30V 2A £5.95. 20V 2½A £2.95. 0-0-6V 1½A £2.85. 0-0-9V 1A £2.55. 12-0-12V 1A £2.95. 15-0-15V 1A £3.20. 30-0-30V 1A £4.10.

S-DECS AND T-DECS*

16 dill £2.24. T-DeC £4.85.

u-DeCa £4.45. u-DeCb £7.85.

IC carriers with sockets

16 dill £2.95. 10T05 £1.95.



SINCLAIR CALCULATORS & WATCHES-

Cambridge Universal £6.60. Cambridge Scientific £8.95. Oxford Sci £13.30. Programmable Scientific with free mains unit £19.95. Mains adaptors for other models (state type) £3.20. Assembled Grey Watch with free stainless steel bracelet £16.45. WhiteWatch £13.95.

SINCLAIR PROJECT 88 AUDIO MODULES

PZ5 £4.95. PZ6 £8.70. Z40 £5.75. Project 80SQ £18.95.

ELPAK AUDIO MODULES

S450 tuner £20.95. AL80 £4.80. PA100 £14.95. MK80 audio kit £31.95. Teak 60 £12.95. Stereo 30 £16.95. SPM80 £3.95. BMT80 £3.82. Send see for free data.

SAXON ENTERTAINMENTS MODULES

SA1208 £20.50. SA1204 £14. SA608 £13. SA604 £12. PM1201/8 £12. PM1202/8 £19. PM1201/4 £12. PM1202/4 £19. PM601/8 £12. PM601/4 £12.

SWANLEY ELECTRONICS

DEPT. PW, PO BOX 68,

32 GOLDSSEL RD., SWANLEY, KENT.

NO CALLERS—MAIL ORDER ONLY

Send see for free leaflets on all kits. Post 30p on orders under £2.25 otherwise free. Prices include VAT. Overseas customers deduct 7% on items marked*, otherwise 11%. Official orders welcome.

FM TOUCH TUNER

P.W. MARCH '77

SEMICONDUCTOR PACK £14.65 RESISTOR PACK £2-15
CAPACITOR PACK £4.75

Above Prices include V.A.T. and P. & P.

THYRISTORS

PIV	8A	1A	3A	4A	6A	8A	10A	15A
(TO92)	(TO5)	(C106)	(TO220)	(TO220)	(TO220)	(TO220)	(TO220)	(TO84)
50	0-20*	0-25	0-35	0-32	0-41	0-42	0-47	0-96
100	0-25*	0-25	0-40	0-37	0-47	0-48	0-54	1-02
200	0-27*	0-35	0-45	0-40	0-58	0-60	0-68	1-14
400	0-30*	0-40	0-50	0-45	0-87	0-88	0-98	1-40
600	—	0-65	0-70	—	1-09	1-19	1-26	1-80

TRIACS (PLASTIC TO-220 PKGE ISOLATED TAB)

	4A	(a)	(b)	6-5A	(a)	(b)	8-5A	(a)	(b)	10A	(a)	(b)	15A	(a)	(b)
100V	0-60	0-60	0-70	0-70	0-78	0-78	0-83	0-83	0-83	1-01	1-01	1-01	1-01	1-01	1-01
200V	0-64	0-64	0-75	0-75	0-87	0-87	0-87	0-87	0-87	1-17	1-17	1-17	1-17	1-17	1-17
400V	0-77	0-78	0-80	0-83	0-97	1-01	1-13	1-19	1-19	1-70	1-70	1-70	1-70	1-70	1-70
600V	0-96	0-99	0-87	1-01	1-21	1-26	1-42	1-50	2-11	2-17	2-17	2-17	2-17	2-17	2-17

N.B. Triacs without internal trigger diac are priced under column (a). Triacs with internal trigger diac are priced under column (b). When ordering please indicate clearly the type required.

OPTOELECTRONICS

Displays	Discretes		
704	0-95	0-2 Red	0-13
707	0-95	0-2 Green	0-20
727	1-95	0-2 Clear	0-14
728	1-95	OCPT1	0-90
747	1-95		
750	1-85		

Special Offer
Red Led
TIL209
10p



TTL

74 Series

Plastic

7400 0-16

7401 0-16

7402 0-16

7403 0-16

7404 0-16

7405 0-18

7406 0-51

7407 0-18

7408 0-18

7409 0-18

7410 0-16

7412 0-25

7413 0-25

7414 0-26

7416 0-43

7417 0-43

7420 0-18

7422 0-38

7423 0-40

7425 0-30

7427 0-48

7428 0-53

7430 0-16

7432 0-37

7433 0-49

7437 0-35

7438 0-35

7440 0-16

7441 0-78

7442 0-65

7445 1-50

7448 2-58

7447 0-81

7448 0-81

7450 0-85

7451 0-16

7453 0-18

7454 0-18

7460 0-18

7470 0-32

7472 0-26

7473 0-30

7474 0-32

7475 0-47

7476 0-36

7480 0-55

7481 1-26

7482 0-75

7483 1-12

7484 0-85

7485 1-25

7486 0-82

7489 2-92

7490 0-45

7491 0-68

7492 0-57

7493 0-45

7494 0-85

7495 0-67

ITT BRANDED TRANSISTORS

Type B5Y85. Med Voltage High gain NPN. To-18. Similar to BC107/8/9.

5 pcs for 0-35.

25 pcs for 1-20.

100 pcs 3-50.

LINEAR ICs

LINEAR	ICS		
307		0-55*	
380	14 Pin DII	0-90*	
555	8 Pin DII	0-45	
565	14 Pin DII	2-00*	
568	8 Pin DII	1-50*	
57	8 Pin DII	2-00*	LM340-5 1-35
8/14 Pin DII	0-35		LM340-12 1-35
8/14 Pin DII	0-28		LM340-15 1-35
8 Pin DII	0-35		LM340-18 1-35
3900	14 Pin DII	0-70*	
CA3045		0-85*	
CA3046		0-50*	
CA3130		1-69	
MC1304		1-56	
MC1307P		1-17*	
MC1458P		0-77	
MC1498L		1-10*	
SN75324		2-55	
SN75451		0-89*	
SN75452		0-89*	
TAA300		1-61	
TAA310A		1-38	
TAA350		0-45*	
TAA611B12		1-25*	
TBA530		1-85*	

CARBON FILM RESISTORS

1W E24SER 0-015

1W E24SER 0-02

TO-3 NPN POWER TRANSISTORS

FULLY TESTED BUT UNMARKED. SIMILAR TO 2N3055 EXCEPT V_{CEO} > 50V HFE > 20 @ 3 Amps.

5 pcs for £1-00

10 pcs for £1-80

20 pcs for £3-40

50 pcs for £7-50

100 pcs for £13-00

REGULATORS

723 0-45

1 amp Plastic

7805 1-50

7812 1-50

7815 1-50

7818 1-50

LM340-5 1-35

LM340-12 1-35

LM340-15 1-35

LM340-18 1-35

LM340-24 1-35

LM340-30 1-35

LM340-36 1-35

LM340-42 1-35

LM340-48 1-35

LM340-54 1-35

LM340-60 1-35

LM340-66 1-35

LM340-72 1-35

LM340-78 1-35

LM340-84 1-35

LM340-90 1-35

LM340-96 1-35

LM340-102 1-35

LM340-108 1-35

LM340-114 1-35

LM340-120 1-35

LM340-126 1-35

LM340-1



Yeah - it's electronic.
I built it with components
from HOME RADIO!

The Home Radio Components catalogue has 200 pages filled with over 5,000 items, well over a thousand of them illustrated. With every catalogue comes a free bargain list showing many items at such give-away prices that the savings can pay for the catalogue several times over. The catalogue costs just £1 plus 40p for post and packing. Send for one today!

Please write your Name and Address in block capitals

NAME.....
ADDRESS.....
.....
.....



HOME RADIO (Components) LTD., Dept. PW
234-240 London Road, Mitcham, Surrey CR4 3HD (Regn. No London 912966)


HOME RADIO (Components) LTD. Dept. P.W., 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

J. BIRKETT

Radio Component Suppliers
25 The Strait, Lincoln LN2 1JF
Telephone: 20767

- SUB-MINIATURE 1 1/2" Dia. LOUDSPEAKERS 8 Ohm @ 75p each.
 - 10,000uf 16v.w. ELECTROLYTICS size 3 1/2 x 1 1/2" @ 15p each 4 for 50p.
 - 6 ASSORTED 80 METRE 10X CRYSTALS for £2.16.
 - 30 AF 117-OC 170 TRANSISTORS Untested @ 57p.
 - 50 BC 107-8-9 TRANSISTORS Untested @ 57p.
 - 8D 187 NPN 4 Amp PLASTIC POWER TRANSISTORS @ 5 for £1.
 - SILICON SOLAR CELLS .5 Volt 5 mA @ 35p.
 - 2 AMP R.F. CHOKES Wire Ended 6 for 50p.
 - 50 AC 128 TRANSISTORS Branded but Untested for 57p.
 - 10 MULTI-TURN TRIM-POTS Assorted Values for 60p.
 - .0005uf 75 Kv.w. VISCONEL CAPACITORS at 50p each.
 - 60 ASSORTED WIRE WOUND RESISTORS 1 To 10 Watt at 57p.
 - RADIO I.C. ZN 414 with circuit @ £1.
 - SILICON PHOTO-SWITCHES with data @ 50p each.
 - CRYSTALS 5 MHz 10X Type @ 50p, 7MHz, 8 MHz 10XA) @ 60p each.
 - BYX94 1250 PIV 1 Amp SILICON DIODES @ 12 for £1.
 - FET's like 2N 3819 at 6 for 75p.
 - MINIATURE 8uf 300v.w. ELECTROLYTICS at 10 for 57p.
 - EMI HUGHES or TRANSITRON GERMANIUM GOLD BONDED DIODES 50 for 40p.
 - TEXAS R.F. TRANSISTORS 2G106 PNP 60 MHz at 20 for 57p.
 - 100 ASSORTED MULLARD C280 Polyester Capacitors @ 57p.
 - BRANDED PLASTIC TRANSISTORS T092 BC 108 or BC 212 Types at 10 for 60p.
 - R.F. TRANSISTORS BF 194 or BF 332 Both at 12 for 50p.
 - PT 243 CRYSTALS 8040, 8100 KHz at 75p each, 7620, 7720, 7966-7, 8166-7, 8233-3, 8300, 8366-7, 8483-3, 8583-3, 8650, 8716-7 KHz. All at 40p each.
 - TEXAS BF 177 100 Volt NPN TRANSISTORS 10p each 6 for 50p.
 - VHF TUBULAR TRIMMERS 3pf @ 5p, 8pf @ 8p, 12pf @ 5p.
 - 30 ASSORTED 10XAJ CRYSTALS Between 5100 To 7900 MHz for £1.10.
 - PLASTIC TRIACS 50 PIV 6 Amp @ 15p, 400 PIV 6 Amp @ 60p.
 - PLASTIC S.C.R.'s 50 PIV 6 Amp @ 15p, 400 PIV 6 Amp @ 40p.
 - TEXAS 800 Volt NPN 2 Amp TRANSISTORS 50p each. 3 for £1.10.
 - TEXAS TIP 117 PNP DARLINGTON POWER TRANSISTOR @ 35p each.
 - DUAL GATE MOS FET's like 40673 at 33p each or 4 for £1.10.
 - T8A 1205 14 PIN DIL LIMITING I.F. AMPLIFIER FM DETECTOR Untested with data 6 for 60p.
 - 2.5 GHz TRANSISTOR PAIR Untested with data at 4 for 57p.
- Please add 20p post and packing on orders under £2.
Overseas orders at cost.

New from OLSON

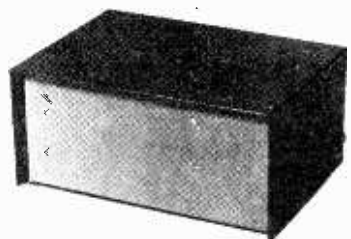


New range of cases attractively designed of robust construction made in two parts. Available from stock in 8 different sizes. Cases made in 20g steel. Top cover sprayed in blue. Hammer bottom part in light grey semi-gloss enamel.

Type	W	H	D	Price
201	5"	2 1/2"	4"	£2.45
202	6"	3"	4"	£2.85
203	7"	3 1/2"	5 1/2"	£3.45
204	8"	3 1/2"	5 1/2"	£3.85
205	9"	3 1/2"	6"	£4.25
206	9 1/2"	4"	6"	£4.80
207	10"	4 1/2"	6"	£4.85
208	11"	5 1/2"	6"	£5.35

Plus Post and Packing 75p and 8% VAT.
OLSON ELECTRONICS LTD.
5-7 LONG ST., LONDON E2 8HJ
TEL: 01-739-2343

A MINIATURE POWER TOOL to speed your building

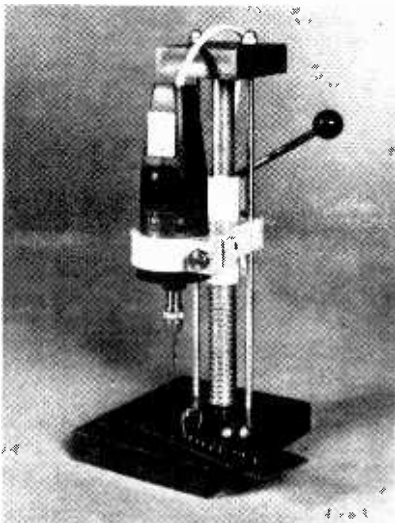- Super 30 Kit (30 Tools) (incl. drill without stand)
£17.62 plus P. & P. 85p
- Mk. II Drill Stand
£4.40 plus P. & P. 35p
- Mk. II Drill only
£8.79 plus P. & P. 35p
- Flexible Drive Shaft
£5.46 plus P. & P. 25p
- Transformer 240V a.c./12V d.c.
£6 plus P. & P. 70p
- Variable Speed Transformer
£8.25 plus P. & P. 70p



Replacement drills, stones, burrs, etc. 40p each. Circular saw blades 50p each. £2 per set of 4 sizes. P. & P. any quantity 20p.

All VAT inclusive

PRECISION PETITE LTD.

119a High Street, Teddington, Middlesex TW11 8HG

Tel. 01-977 0878 (24 hour answering service)

9" x 4" S.A.E. please for leaflet and order form

TORIN ELECTRONICS

24 DARTFORD ROAD, DARTFORD, KENT. Tel. (0322) 73133/25864

All prices inclusive of V.A.T. Below are but a few of the types available. Please phone for quotation of unlisted types. S.A.E. for written replies, please. All goods brand new, boxed and guaranteed for 12 months. Postage: 12p one valve, 3p each subsequent valve. Orders over £10 free. Trade enquiries welcome. Try us first for all obsolete types.

0A2	-42	6F14	-80	20P3	1-10	DM70	-75	EF39	1-40	GZ33	1-75	PY82	-40
0B2	-38	6F15	-70	20P4	-30	DM71	1-85	EF40	-75	GZ34	-75	PY83	-20
IB3	-50	6F18	-50	20P5	1-40	DY86/7	-30	EF41	-75	GZ37	1-10	PY88	-40
1R5	-45	6F23	-60	25L6	-65	DY802	-40	EF42	1-00	KT66	3-10	PY500A	1-00
1S4	-30	6F24	-75	25Z4	-50	EB0CC	2-40	EF80	-25	KT88	1-75	PY800	-40
1T4	-38	6F25	-95	25Z5	-80	EB0CF	5-40	EF83	1-20	KTW61	1-75	PY801	-40
2D21	-50	6F28	-70	25Z6	-80	EB0F	2-40	EF85	-35	N78	4-75	QQV03/101-95	
3A4	-50	6G6	-55	30A5	-80	EB8C	1-40	EF86	-40	PABC80	-40	QQV03/20A	
3O4	-72	6H6	-50	30C15	-75	E180F	-1-10	EF89	-30	PC86	-40	PC86	15-00
3Q5	-65	6J5	-50	30C17	-75	E182CC	3-10	EF91	-50	PC88	-60	QQV06/40	
3S4	-42	6J7	-30	30C18	1-00	E188CC	2-40	EF92	-50	PC95	-65		18-00
5R4	-90	6K7	-35	30F5	-65	EABC80	-40	EF97	-85	PC97	-35	QS95/10	-95
5U4	-55	6K8	-50	30FL1	1-00	EAC91	-50	EF98	-85	PC900	-40	QV06/20	3-40
5V4	-55	6L6	-75	30FL2	1-00	EAF42	-65	EF183	-35	PC884	-35	UABC80	-40
5Y3	-50	6N7	-65	30L15	-70	EB91	-15	EF184	-35	PC885	-45	UAF42	-85
5Z3	-90	6Q7	-45	30L17	-70	EBCA1	-75	EF184	1-60	PC888	-60	UBC41	-45
5Z4	-45	6R7	-60	30P12	-70	EBCC1	-40	EF804	1-60	PC889	-45	UBC81	-50
63/0L2	-75	6SA7	-50	30P19	-85	EBFC8	-40	EL32	-55	PC189	-50	UBF80	-50
6AC7	-50	6SJ7	-55	30PL1	1-00	EBF83	-40	EL34	-85	PCF80	-40	UBF89	-35
6AG5	-35	6SK7	-50	30PL13	1-00	EBF89	-40	EL35	3-20	PCF82	-40	UBC84	-85
6AH6	-68	6SL7	-50	30PL14	1-25	EC86	-80	EL37	3-20	PCF84	-65	UBC85	-40
6AK5	-45	6SN7	-50	30PL15	1-00	EC88	-80	EL41	55	PCF86	-55	UCF80	-75
6AK6	-65	6SQ7	-55	35C5	-75	EC92	-50	EL43	-80	PCF90	1-00	UCH42	-70
6AM8	-65	6V6	-40	35L6	-75	ECC40	-85	EL81	-60	PCF201	1-00	UCB81	-45
6AN8	-65	6X4	-40	35W4	-50	ECC81	-32	EL84	-35	PCF801	-45	UL42	-85
6AQ5	-45	6X5	-40	35Z4	-70	ECC82	-32	EL86	-55	PCF802	-50	ULC83	-55
6AR5	-70	10C2	-65	35Z5	-75	ECC83	-32	EL95	-85	PCF805	-50	UF41	-85
6AS7	-90	10F1	-65	30C25	-70	ECC84	-35	EL360	1-60	PCF808	1-00	UF42	-75
6AT6	-50	10F9	-85	50CD6	1-10	ECC85	-35	EL506	1-10	PCH200	1-00	UF80	-40
6AU6	-40	10F18	-85	50L6	1-10	ECC86	-50	EM80	-50	PCL82	-35	UF85	-40
6AV6	-45	10LD11	-70	85A2	-70	ECC88	-50	EM81	-55	PCL83	-45	UF89	-40
6BA6	-40	10P13	-75	90AG	2-85	ECC89	-50	EM82	-55	PCL84	-45	UL41	-85
6BE6	-40	10P14	2-35	90C1	-80	ECC189	-70	EM84	-40	PCL86	-45	UL84	-45
6BH6	-65	12A05	-75	90C2	2-85	ECF80	1-20	EM85	1-10	PCL805/85	-55	UM80	-55
6BU6	-60	12AE8	-75	807	1-00	ECF80	1-20	EM87	1-10	PL200	-85	UY41	-45
6BQ7	-55	12AT6	-50	5763	1-50	ECF86	-75	EY31	1-40	PL33	-45	UY85	-35
6BR7	1-10	12AU6	-50	6057	1-00	ECF87	-75	EY81	1-40	PL36	-55	U10	-90
6BR8	1-20	12AV6	-50	6060	1-00	ECF804	5-20	EY81	-40	PL38	-55	U12	1-00
6BS7	1-50	12BA8	-50	6067	1-00	ECF82	-70	EY83	-35	PL41	-45	U17	1-00
6BW6	1-00	12BE6	-50	7193	-55	ECF84	-70	EY84	1-10	PL81A	-50	U14	1-00
6BW7	-60	12BH7	-50	CL33	1-85	ECH83	-50	EY86/7	-35	PL82	-35	U19	3-90
6C4	-35	12BY7	-80	CY31	-65	ECH84	-50	EY88	-50	PL83	-40	U25	-70
6C5	-55	12E1	3-00	DAF91	-30	ECL80	-40	EY40	-50	PL84	-45	U26	-55
6CB6	-50	19AQ5	-60	DAF96	-30	ECL82	-40	EZ40	-50	PL500	-80	U191	-50
6CD6	1-50	19G6	-55	DF91	-30	ECL83	-70	EZ41	-50	PL504	-80	VR105/30	-50
6CL6	-65	20D1	-65	DF96	-50	ECL84	-60	EZ80	-30	PL509	1-50	VR150/30	-45
6EW6	-80	20F2	-80	DK92	1-00	ECL85	-70	EZ81	-30	PY33	-50	W729	1-15
6F6	-54	20L1	1-10	DK96	-65	ECL86	-40	GZ501	-80	PY80	-50	X41	1-00
6F7	-80	20P1	1-10	DL96	-55	EF37A	1-40	GZ32	-55	PY81	-40	Z750	5-70

Sonic

HI-FI DISCOUNT CENTRES

DISCOUNT SPEAKERS

Imp 8 or 15Ω as app.

Guarantees:
TITAN 3 years
FANE 2 years
OTHERS 1 year

ALL PRICES INC. VAT

	List	Sonic Price
5" FANE 501 Mid or Full range	Sp. Price	£4.95
8" x 5" 10w Various makes	Sp. Price	£3.95
8" A.F. Model 80	Sp. Price	£5.95
8" A.F. Model 83	Sp. Price	£6.95
FANE 8" 808T	Sp. Price	£3.95
FANE 8" 807TP	Sp. Price	£4.75
8" WHARFEDALE LINTON KIT	Sp. Price Pair	£23.95
8" FANE MODE ONE KIT	Sp. Price Pair	£19.75
10" WHARFEDALE GLENDALE XP KIT	Sp. Price Pair	£33.95
10" ELAC Model 10RM	Sp. Price	£3.85
12" FANE 121/15LR 20w	Sp. Price	£7.95
12" FANE 122/10 25w	Sp. Price	£7.95
12" POP 25T	Sp. Price	£9.95
12" TITAN 12/35 35w	£15.80	£10.50
12" TITAN T12/60A 60w	£22.50	£12.50
12" TITAN T12/100A 100w	£36.00	£22.95
CELESTION G12M	Sp. Price	£12.99
12" CELESTION G12H 30w	Sp. Price	£15.95
12" CELESTION G12/50 50w	Sp. Price	£16.50
G12/50TC	Sp. Price	£17.95
12" GOODMANS 12 PD	Sp. Price	£17.95
12" GOODMANS 12 PG	Sp. Price	£17.95
12" FANE 'SPECIALIST' P.A. 80	£24.75	£16.50
12" " " DISCO 80	£25.95	£17.50
12" " " GUITAR 80L	£24.75	£16.50
12" " " GUITAR 80B	£24.95	£17.95
12" FANE CRESCENDO 12A	£57.35	£37.95
12" FANE " 12L	£59.95	£39.95
12" FANE " 12B	£56.70	£39.95
15" TITAN T15/60 60w	£28.00	£18.95
15" TITAN T15/70 70w	£28.00	£19.95
15" TITAN T15/100 100w	£41.00	£27.95
15" FANE 'SPECIALIST' BASS 85	£37.75	£28.95
15" " " BASS 100	£39.95	£29.95
15" GOODMANS 15P	Sp. Price	£22.50
15" CELESTION G15C	Sp. Price	£26.95
15" FANE CRESCENDO 15/100A	£72.95	£49.95
15" FANE CRESCENDO BASS 15/100LT	£76.00	£49.95
15" " " COLOSSUS 200w	£108.00	£69.95
18" TITAN T18/100 100w	£47.00	£29.95
18" GOODMANS 18P	Sp. Price	£38.95
18" CELESTION G18C	Sp. Price	£34.50
18" FANE CRESCENDO 18A	£101.95	£66.95
18" FANE CRESCENDO BASS 18	£89.95	£59.95
18" " " COLOSSUS' 200w	£115.00	£69.95
HORN UNITS		
CELESTION MH1000	Sp. Price	£13.75
FANE 910 MK II	Sp. Price	£17.75
FANE 920	Sp. Price	£19.50
FANE 925	Sp. Price	£39.95
FANE 144	Sp. Price	£7.95
FANE 1104	Sp. Price	£16.95
HIGH POWER		
FANE HPX1	Sp. Price	£1.75
'CROSS OVERS'		
FANE HPX2	Sp. Price	£1.75
'ADD-ON' H.F. UNITS		
F.A.L. 'Add-on'	Sp. Price	£35.95
TITAN T11 70w	Sp. Price	£25.95
TITAN T2H 100w	Sp. Price	£25.95
CABINETS (Vynide & Vynair covered)		
Fitted Protective Corner Pieces, Heavy duty	Sp. Price	£9.95
For Twin 12" Spkrs	Sp. Price	£29.95
For Single 12" Spkrs	Sp. Price	£14.95
Many other types available.		
Extra Special prices for quantities.		
MANY OTHER DISCOUNT LINES		
(for personal callers only)		
AMPS, T'ABLES, JINGLE MACHINES, DISCO CONSOLES, LIGHTING CABINETS,		
CREDIT TERMS AVAILABLE orders £20 over		
Please enclose stamp for leaflets or with enquiries. Prices correct at 8.12.76.		
Branches at		
403 SAUCHIEHALL STREET	GLASGOW	
Tel: 141 332 0700		
24 NEWGATE SHOPPING CENTRE, Tel: 0632 21469	NEWCASTLE	
106 NEWPORT ROAD	MIDDLESBROUGH	
Cleveland TS1 5JF. Tel: 0642 217402		
Mail Orders & Export to Middlesbrough Branch Add 75p per spkr. (or Pair Spkrs under £5 ea) for carr. Cabinets for personal shoppers only.		



SMALL ADS

The prepaid rate for classified advertisements is 17 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £14.00 per single column inch (2.5cm). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

300W TOUCH SWITCH KITS

TS300K Contains Triac, IC, Diodes, Resistors, P.C.B. Frontplate, etc. Replaces conventional light switch with NO REWIRING. TOUCH one insulated plate for ON, another for OFF. Complete with Instructions—ONLY £3.67. ALSO TSA300K AUTOMATIC as above but with only ONE TOUCHPLATE. TOUCH for ON and light stays on for a preset time. Ideal for stairs and hall. Complete with Instructions—ONLY £3.67. 300W LIGHT DIMMER KIT replaces conventional Light Switch—£2.45.

CMOS Motorola	TRIACS 400V TO220 CASE ISOLATED TAB	BC148 9p*	BC158 11p*
4000 20p	6-5A 80p	2N3055 36p	
4001 20p	8-5A 85p	2N6027 (Dut) 34p	
4007 20p	Diac 20p	1N4004 6p	
4011 20p	NE555 8 pin DIL 44p	1N4148 4p*	
4013 57p	741 8 pin DIL 24p		
4015 105p			
4016 57p	RESISTORS 1/4W 5% E12 22Ω*		
4017 105p	—10M Mullard 2p*		
4040 105p	LDR 1/2" Dia. 400Ω to 1MΩ light to dark 7p		
4049 57p	NEON wire-ended 7p		
4501 20p	—10M Mullard 2p*		
4510 135p	Ferrite rod 1 1/2" x 3/4" diameter 12p		
4516 135p	MINI MAINS TRANSFORMERS		
4566 155p	100mA 6-0-6V 85p		
	12-0-12V 85p		

ADD 8% VAT (*121%) PLUS 25p P&P. Mail Order Only to:—

T.K. ELECTRONICS

106 Studley Grange Road, London, W7 2LX

NOSTALGIA VINTAGE RADIO 1920 to 1950 COLLECTING

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet. Full 1976 catalogue, 50p post paid.

TUDOR REES (Vintage Services), 64, Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. Bristol 565472.

COMMUNICATIONS RECEIVER modules, Small superhet circuit boards requiring only controls and tuned circuits. 9 volt. Mosfet mixer, IC IF, BFO, PROD. Det. Excellent AM/CW/SSB results reported by delighted users. SAE details. PR Golledge Electronics, Millend, Stonehouse, Glos.

Precision Polycarbonate Capacitors

All High Stability—extremely Low Leakage			440V AC RANGE			Value Range		
Value (μF)	Dimensions (mm)	Price/each	Value (μF)	±1%	±2%	Value (μF)	±1%	±5%
0.01-0.2	L D	£1.28	0.01-0.2	£1.28	75p	50p		
0.22-0.47	L D	£1.32	0.22-0.47	£1.32	77p	51p		
0.1μF	27 12.7	68p	0.68μF	£1.44	84p	55p		
0.15μF	27 12.7	80p	1.0μF	£1.66	91p	60p		
0.22μF	33 16	95p	1.5μF	£1.74	1.18	67p		
0.25μF	33 16	92p	2.2μF	£1.95	1.32	75p		
0.33μF	33 16	99p	3.3μF	£2.40	1.60	99p		
0.47μF	33 19	£1.10	4.7μF	£2.82	1.88	1.23		
0.5μF	33 19	£1.16	6.8μF	£3.48	2.32	1.47		
0.68μF	50.8 19	£1.25	10μF	£4.98	3.32	2.01		
1.0μF	50.8 19	£1.37	15μF	£7.14	4.76	2.88		
1.5μF	50.8 25.4	£1.64	22μF	£9.66	6.44	3.90		
2.0μF	50.8 25.4	£1.95						

TANTALUM BEAD CAPACITORS—Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8μF at 16V/25V or 35V; 10.0μF at 16V/20V or 25V; 22.0μF at 4V/10V or 16V; 33.0μF at 6V or 10V; 47.0μF at 3V or 6V; 100.0μF at 3V. All at 12p/each, 10 for £1.10*, 50 for 45*, 100 for 48*.

TRANSISTORS & I.C.'s

BC107/8/9 8p	*BC212/212L 8p	2N3055 60p
*BC114 18p	*BC213/213L 11p	OC44/45 30p
*BC147/8/9 10p	*BC214/214L 11p	OC71/2 20p
*BC153 18p	*BF194/5 12p	NE555 Timer 81p
*BC164/7/8/9 12p	BFY60/1/2 20p	741C 8 pin DIL 82p
BC182/182L 11p	AF178 40p	ZN414 11.15
*BC183/183L 11p	AP239 35p	8N76013ND 11.50
*BC184/184L 12p	2N3702/4 11p	

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p; 1N916 8p, 6 for 45p, 14 for 90p; 1844 6p, 11 for 50p; 26 for £1.00, 1N4148 6p, 6 for 27p, 12 for 48p; 1N4001 6p; 002 8p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p.

LOW PRICE ZENER DIODES—400mW. Tol. ±5% at 5mA. 3V; 3V3; 3V6; 4V7; 5V; 5V6; 6V2; 6V8; 7V5; 8V2; 9V1; 10V; 11V; 12V; 13V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V; 33V. All at 7p each, 5 for 33p, 10 for 65p, 50 for £3.12. SPECIAL OFFER: 100 Zeners may be mixed) for 28.00.

RESISTORS—High stability, low noise carbon film 5% 1/4W at 40°C. 1/4W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p* each. 8p/10 for 10 of any one value, 70p* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 65*.

SILICON PLASTIC RECTIFIERS—1-5 amp, wire-ended DO27: 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p). **BRIDGE RECTIFIERS**—24 amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: All at 6p* each; 50; 100; 220; 470; 680 ohm; 1k; 2k2; 4k7; 6k8; 10k; 15k; 22k; 47k; 100k; 320k; 680k; 1M; 2M5; 5M.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with * which are 121%.

Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. P4), The Old School, Edgaston, Wem, Shropshire. Tel: Whixall 464/465 (STD 094 8728) (Proprs. Minicost Trading Ltd.)

ZN1040E 4 digit count/display IC	£7.00
300W Illuminated Torch Switch with Instructions Built and Tested	£3.90
7489 64 bit read/write memory fully functional/speed failure	0.65
DL707 Litronics CA 7 SEG display	£1.35
7447 BCD-7 SEG decoder driver	0.95
Soldercon Pins /100	0.60
P. & P. 20p free on orders over £5.00	
Data Sheets 10p each S.A.E. (Mail Order only)	
GJD Electronics, 105 Harper Field Road, Radcliffe, Manchester, M26 0RQ	

RESISTORS: Type AEL II Carbon Film 5% E24 (1E to 10M) Sold in units of 10. 1/4w 7p, 1/2w 8p per 10. Min. Order £2 P & P 15p +12% VAT (High rate) SAE for more details to C W ELECTRONICS Dept PW, 10 Kingsley Path Britwell Slough Berkshire. WE CAN ALSO SUPPLY TO THE TRADE, COLLEGES & EXPORT.

VALVES

Radio - T.V. - Industrial - Transmitting We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 2700 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves.

COX RADIO (SUSSEX) LTD.
Dept. P.W. The Parade, East Wittering, Sussex PO20 8BN West Wittering 2023 (STD Code 024366)

DIODES 1N914E 2p ea £1.30/100, £10/1,000 5% Zeniers 2.7-36v 5p ea £4/100, 800V 1 amp Low VF 5p ea £4/100 20p p & p Bale Electronics, 'Nanock' Dalton, Dumfrireshire.

BRAND NEW COMPONENTS BY RETURN.

Electrolytic capacitors 16V, 25V, 50V.—0.47, 1.0, 2.2, 4.7 & 10mfd.—5p, 22, 47—3p. (50V—6p). 100—7p (50V—8p) 220—8p. (50V—10p) 470—11p. (50V—16p) 1000/16V—15p, 1000/25V—18p. 1000/50V—22p.

Subminiature bead tantalum electrolytics—0.1, 0.22, 0.47, 1.0, 2.2 @ 35V, 4.7/25V—11p. 10/25V—13p. 22/18V, 47/6V, & 100/3V—15p.

Mullard miniature ceramic E12 series 2% 63V. 10p. to 47p—3p. 56p. to 330p.—4p. Vertical mounting ceramic plate 58V. E12 series 22pf-1000pf. E6 series 1500pf-4700pf.—2p.

Polystyrene E12 series 63V horizontal mounting. 10pf to 1000pf—3p 1200pf. to 10000pf.—4p

Mullard polyester 250V vertical mounting E6 series. 0.01 to 0.1—4p. 0.15, 0.22—5p. 0.33, 0.47—8p. 0.68—11p. 1.0—13p. 1.5—20p. 2.2—22p.

Mylar (Polyester) Film 100V vertical mounting. 0.001, 0.002, 0.005—3p. 0.01, 0.02—4p. 0.04, 0.05—4p.

Miniature resistors Highstab E12 series 5% tolerance. Mullard C. Film .33W 1Ω to 10MΩ. (10% over 1MΩ)—1p. 0.125W, 0.25W & 0.5W. 10Ω to 2MΩ.—1p. Metal Film 1W.27Ω to 10MΩ.—2p ea.

1N4148—3p. 1N4002—5p. 1N4005—7p. 1N4007—8p. BC107/3/9, BC147/8/9, BF157/8/9 & BF194 & 197—8p. Fuses 20mm. glass, 1 1/2" glass & 4" ceramic. 21p; Post 10p. (Free over £4.00) Prices inclusive of VAT.

THE C. R. SUPPLY CO., 127, Chesterfield Rd., Sheffield S8.

ITT 5870ST N1x1+Data, 50p. Sperry SP-425-09 (9 digit display)+data, £1. SKT. 50p. 747 (Class II), £1.35. MM5314 +data, £3.35. SKT. 45p. TTL209, 10p. BC108, 10p. 1N4148, 3p. EX7001 (CT7001), £5.50. 741 DIL, 18p. TO99, 20p miniature 5 position toggle, £1. P/P 10p. LB, 43 Westcott, Hayes, Middx UB4 8AH.

Service Sheets

SERVICE SHEETS — COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p.
Please send large Stamped Addressed Envelope.
We can supply manuals for most makes of Colour Television Receivers by return of post.
**B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVITA
FERGUSON H.M.V. MARCONI AND MANY MORE**
Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply.
Also comprehensive T.V. repair manuals by J. M. Court, S.A.E. for details.
G. T. TECHNICAL INFORMATION SERVICE
10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA
MAIL ORDER ONLY

SERVICE SHEETS, Radio, TV, etc., 50p and s.a.e. Catalogue 20p and s.a.e. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

ALL AT 75p EACH (Except colour) & CAR RADIOS
Please state if Circuit will do if Service Sheet not in stock.

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to
(Uncrossed P.O.s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882
Large Stocks of Colour Manuals
NO OVERSEAS MAIL PLEASE

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater Fleetwood FY78JZ.

For Sale

NEW ISSUES OF "PRACTICAL WIRELESS" available from April 1974 up to date. Cover price plus 17p postage per copy—Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

CREED 7E TELEPRINTER, excellent condition with Telex unit, £35. Or exchange for S.W. receiver. Dalley, 40 Park Grange View, Sheffield.

Electrical

STYL, CARTRIDGES & AUDIO LEADS etc. For the best at keenest prices send S.A.E. for free illustrated list to: Felstead Electronics (PW), Longley Lane, Gatley, Cheadle, Cheshire. SK8 4EE.

Practical Wireless, March 1977

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders. enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

BELL'S TELEVISION SERVICES For Service Sheets on Radio, TV, etc., 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

Books and Publications

START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS

This unique instruction manual shows step by step how to rewind motors, working part or full time, without previous experience. Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc. A goldmine of information and knowledge.

Only £3.90 plus 26p P&P.

Magnum Publications Dept PWS

Brinkway Trading Estate, Brinksway, Stockport SK3 0BZ.

Overseas Distributors wanted.

FREE T.V. CIRCUIT DIAGRAMS

All main British T.V. sets (plus many foreign) comprehensively covered in our easy-to-follow T.V. Repair Manuals—4 mono and 3 colour. Just send model no., if colour (mfra, chassis type helps) with £4.50 and receive the manual covering your set—plus your set's circuit diagram on request free. Set of 7 only £27 post free. British T.V. Circuit Diagram Manuals—the main mono (over 37 series) for £9.90 and virtually every colour for £17.50.

Full details of these and other publications from:

T.V. TECHNIC

76 CHURCH ST., LARKHALL, LANARKS
Tel. (0690) 883334. MLD 1HE

Situations Vacant

TEST TECHNICIAN to carry out all aspects of testing on a wide range of electrical/electronic apparatus and components used in the manufacture of modern X-ray equipment. General testing experience is essential, although not necessarily in this particular field. Write in the first instance to the Personnel Officer, G.E.C. Medical Equipment Ltd., 14 Progress Way, Waddon, Croydon, Surrey. Tel: 01-688 7495.

Wanted

WANTED—NEW VALVES, TRANSISTORS. TOP PRICES, popular types. Kensington Supplies (C), 367 Kensington Street, Bradford 8, Yorkshire.

Aerials

G2DYM SWL AERIALS

All aerials custom built by G2DYM, Ex-B.B.C. Transmitter and Aerial Engineer. CONSULT US for DESIGN & ADVISORY SERVICE, send large S.A.E., 3, 64 stamps. We will quote you for Custom building aerials to your individual requirements, and space available.
LAMBDA ANTENNA STUD FARM
WHITEBALL, WELLINGTON, SOMERSET

Ladders

LADDERS. Varnished. 20ft 9in extd. £23.03. Carr. £1.90. Leaflet. Also alloy ext. up to 62½ft. The Ladder Centre (WLS) Halesfield (1) Telford, Salop. Tel: 586644. Callers welcome.

Miscellaneous

100 RESISTORS 75p
1w 5% C/Film 2.2Ω—2.2MΩ (E12)
10 each of any value

C60 CASSETTES 32p All Cassettes in Plastic Case with Index and
C90 CASSETTES 45p Screwed Assembly.

All prices include VAT Add Postage 10p in £1.
Quantity Discounts. SALOP ELECTRONICS
10 Units 5% 23 WYLE COP
50 Units 7% SHREWSBURY
100 Units 10% Tel. 53206

SUPERB INSTRUMENTS CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 82p. Examples: width, depth, height, 8in x 5in x 3in, £1.70, 10in x 6in x 3in £2.42, 10in x 8in x 3in £3.02, 12in x 10in x 3in £3.96, 8in x 4in x 4in £1.98, 10in x 6in x 4in £2.97, 12in x 8in x 4in £3.96, 7in x 7in x 5in £2.91, 8in x 10in x 6in £3.96, 12in x 8in x 7in £4.40, 12in x 12in x 7in £4.84. Plus 85p carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). Bazelli, Dept No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

ENAMELLED COPPER WIRE

S.W.G.	1 lb reel	½ lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All the above prices are inclusive of postage and packing in U.K.

COPPER SUPPLIES

102 Parrswood Road, Withington, Manchester 20 Tel: 061-445 8753

RECHARGEABLE NICAD BATTERIES 'AA' (HP7), £1.26; Sub 'C', £1.29; 'C' (HP11), £2.38; 'D' (HP2), £2.92. PP3, £4.98. Matching chargers, respectively, £4.48, £4.48, £5.24, £5.24, £3.98. All packages include VAT. Add 10% post and packing. SAE for full list, plus, if wanted, 50p for 'Nickel Cadmium Power' booklet. Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands B73 6PP. Tel: 021-354 9764.

H. M. ELECTRONICS

275a FULWOOD ROAD, BROOMHILL, SHEFFIELD S10, 3BD.

BEC CABINETS (illus'd)

METAL CASES
DRY TRANSFER LETTERING
Send 15p for leaflets (Refundable)
Trade enquiries invited



Miscellaneous (continued)

SNOOPING LOW?

NOW you can uncover the EXCITING 100-600KHz band—with YOUR receiver. CONVERTER has 20dB gain, antenna matching and 3.5-4MHz output. ALL parts, coils, printed circuit, case, etc., instructions, money back assurance, send £2.99 NOW.

CAMBRIDGE KITS

45(PQ) Old School Lane, Milton, Cambridge

**GORSE'S
MAIN STOCKISTS FOR
GRUNDIG**

Satellit 2100, 21 Wave Band Radio, TK545 and TK745 Stereo Tape Recorders, Radios, Radio/Cassette Recorders, Cassette Recorders, Microphones, etc., etc.

Please write, (send S.A.E.) phone or call for full details and prices.
42-44 CHURCH ST., 77 THE MALL
BLACKBURN BURNLEY
Tel: 51682 Tel: 35229

**LOW COST — HIGH EFFICIENCY
AUDIO TEST
OSCILLATOR £22**



RANGE: 10Hz to 100kHz. OUTPUT: 1V, sine/sq. DISTORTION: less than 0.02%. 9V battery. Also available in Kit form at £17. Add 8% VAT. P. & P. and ins. 75p. Leaflet available, also F.M. Signal Generator, Millivoltmeter, freq. meter, THD analyzer, P.S. Units. S.A.E. please for literature.

TALERADIO ELECTRONICS

325 Fore Street, London, N9 0PE
Tel. 01-807 3719

**MAGNETIC MICROPHONE
SPEAKERS**

4T inserts, ideal for all sound speaking and listening applications. Very rugged—d.c. resistance 20 ohms. Size: 1 1/2" dia, 3/8" deep, 40p each + 10p P. & P. 6 for £2.20 + 20p P. & P. 12 for £4.50 P. & P. free. S.A.E. for list of many other items. Trade enquiries welcome.

B.B. SUPPLIES, 141 Sharnford Street
Nr. Canterbury, Kent. CT4 7QZ.

LOW-COST I.C. MOUNTING for any size DIL package. 100 Soldercon sockets 65p. 7 and 8 hole plastic supports 5p/pair. Quantity rates. SAE details and sample. Trial pack 65p. (P & P 10p/order). P.K.G. Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

**Musical
Miracles!**

by Dewtron®

Build your own synthesiser or musical effects using some of the huge range of DEWTRON modules. Or build fuzz or waa-waa at budget prices using special kits.

Send 25p for Catalogue from—

D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset BH22 9AR.

AERIAL WIRE. High quality p.v.c. covered multi-strand copper. 50ft. 85p (15p); 75ft. £1.28 (17p); 100ft. £1.67 (23p); 150ft. £2.51 (34p); 200ft. £3.36 (39p); 250ft. £4.19 (46p); 300ft. £4.97 (48p); P&P in brackets. A.1 Radio Components, 19 The Borough, Canterbury, Kent CT1 2DR.

MORSE CODE

MORSE CODE TUITION AIDS

Cassette 3 1-12 WPM for Amateur Radio Examination.

Cassette 5 12-24 WPM for Professional Examination Preparation.

Morse by Light System available.

Morse Key and Buzzer Unit for Sending Practice.

Prices: Cassettes including Booklets £4. Morse Key and Buzzer £4. Prices include VAT, Postage, etc. Overseas £1 extra.

MHEL ELECTRONICS

12 LONGSHORE WAY, MILTON
PORTSMOUTH PO4 8LS

BUILD THE TREASURE TRACER

MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit: 4,000 sold
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete Kit £14.75 Built & tested £19.75
Post £1.00 + £1.18 VAT Post £1.90 + £1.58 VAT

MINIKITS ELECTRONICS,
44 CLEVELAND ROAD,
LONDON, E18 2AN (Mail order only)

ENAMELLED COPPER WIRE

swg	1 lb	8oz	4oz	2oz
14-19	2.40	1.20	.80	.50
20-29	2.45	1.00	.82	.50
30-34	2.60	1.70	.89	.64
35-40	2.85	1.90	1.04	.75

Inclusive of p&p and VAT.
SAE brings Catalogue of copper and resistance wires in all coverings.

THE SCIENTIFIC WIRE COMPANY
PO Box 30, London E4 9BW
Reg. Office: 22 Coningsby Gardens,

P.C. BOARD containing over 50 new, unused, C Moss i/cs 4001-2-11-12. ECT 5V i/c 6 14-pin sockets, £3. T. Cooper, 25 Larkwood Road, Chingford, London E4 9DS. Tel: 01-529 8255.

**PRINTED CIRCUITS
and HARDWARE**

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual designs. Prompt service. Send 15p for catalogue.

Ramar Constructor Services,
Masons Road, Stratford on Avon,
Warwicks. Tel. 4879

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions. I enclose Cheque/P.O. for £.....
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME

ADDRESS

Send to: Classified Advertisement Manager
PRACTICAL WIRELESS,
OMG, Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS Telephone 01-261 5448
Rate
17p per word, minimum 12 words. Box No. 40p extra.

Company registered in England. Registered No. 53628. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

ELECTRONIC BROKERS



Computer parts for hobby,
experimental, educational
and professional use.

FRESH STOCKS OF THE POPULAR CLARE-PENDAR ASC11 KEYBOARD TYPE KB6 NOW TO HAND

ASCII-Coded TTL-compatible 4-bank alphanumeric reed-switch keyboard with ROM encoder chip, strobed output, two-key rollover and debounce. Standard 7-pit ASCII code (no parity). Supplied complete with circuit diagrams and code chart.

SPECIFICATIONS Power Supply: + 5VDC $\pm 5\%$ 150mA; -12VDC $\pm 10\%$ 10mA
Output Logic Levels: Data Bits 1 through 7-0v $\pm 10\%$ 45V; 2-6v $\pm 10\%$ 5-25V Fan Out: One
standard TTL load. Strobe: 2-6v $\pm 10\%$ 5-25V; 0v $\pm 10\%$ 45V Fan Out: 10 standard TTL loads.
Strobe signal delay 10 milliseconds nominal to allow data to stabilise.

KB6: 56-station standard Teletype layout. AS RECOMMENDED FOR PRACTICAL
WIRELESS VIDEO-WRITER PROJECT. Price £38.50 plus £1 P&P + 8% VAT (send
£43.74).

ALSO AVAILABLE SPECIAL LOW COST KEYBOARDS
KB5: 3-bank alphanumeric Baudot-coded 38-station keyboard. TTL compatible, strobed
output. Price £29.00 plus £1 P&P + 8% VAT (send £22.68).

NEW ARRIVALS

FABULOUS NEW 96-STATION CRT DISPLAY KEYBOARDS 8-bit ASCII code, upper
and lower case output PLUS separate numeric pad. TTL logic. Delayed strobe signal
and two-key rollover feature. Mounted in attractive box, overall dimensions 20½ x 7½ x
3½". Price £85.00 + £3 carriage + 8% VAT (Send £73.44).

**BCD-coded keyboard, upper and lower case outputs. 54 Key-stations PLUS 5 indicator
lamps and on/off switch. Set in attractive mounting panel, dimensions 15½ x 5 x 2½".
Price £38.50 + £2 P&P + 8% VAT (send £44.82).**

Also available a few only of above model WITHOUT ENCODING, Price £25.00 + £1.50
P&P + 8% VAT (Send £28.82).

FOR THE EXPERIMENTER

Single plane core memory ideal for experimental and instructional applications.
42 x 52 cores storage capacity with 230 0A10 diode-loaded buffer.
£2.00 plus 40p P&P + 8% VAT (Send £2.59).



Ferrite core memory plane mounted on plastic frame
5 x 8" consisting of matrix 40 x 52 x 4 cores, divided
into four individually addressable planes with separate
sense and inhibit wires per plane giving 1000 bits capacity,
comprising of a grid of wires passing through
ferrite cores at a 90 angle. £2.50 plus 40p + 8% VAT
(Send £3.13).

ELECTRONIC BROKERS LTD
49/53 Pancras Road
London NW1 2QB
Tel: 01-837 7781

Please
mention

Practical
Wireless

when
replying
to

Advertisements

MAIL ORDER PROTECTION SCHEME

The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:—

'Direct response advertisements, displays or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

AC/DC TAUT SUSPENSION MULTIMETERS (Made in USSR)



TYPE	U4312	U4313	U4315
Sensitivity D.C.	667 o.p.v.	20,000 o.p.v.	20,000 o.p.v.
Sensitivity A.C.	667 o.p.v.	2,000 o.p.v.	2,000 o.p.v.
D.C. Current	300 μ A-6A	60 μ A-1.5A	50 μ A-2.5A
A.C. Current	1.5mA-6A	0.6mA-1.5A	0.5mA-2.5A
D.C. Volts	75mV-900V	75mV-600V	75mV-1000V
A.C. Volts	300mV-900V	15V-600V	1V-1000V
Resistance	0.02-3k Ω	1K-1M	300 Ω -500k Ω
Capacity	—	0.5 μ F	0.5 μ F
Accuracy	1% D.C., 1.5% A.C.	1.5% D.C., 2.5% A.C.	2.5% D.C., 4% A.C.

Price complete with pressed steel carrying case and test leads.


£14.50 £17.50 £14.95

TYPES U4313 AND U4315 ARE PROVIDED WITH ANTI-PARALLAX MIRROR SCALES



TYPE	U4324
D.C. Current:	0.06-0.6-60-600mA-3A
A.C. Current	0.3-3-30-300mA-3A
D.C. Voltage:	0.6-1.2-3-12-30-60-120-600-1200V
A.C. Voltage:	3-6-15-60-150-300-600-900V
Resistance:	500 Ω -5-50-500k Ω
Accuracy:	D.C. 2.5%; A.C. 4% (of F.S.D.)

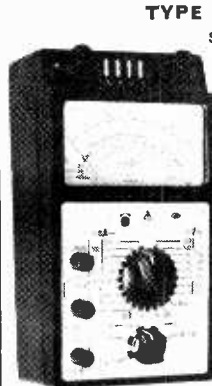PRICE complete with test leads and fibreboard storage case £14.50



TYPE U4341

Sensitivity:
16700 Ω /V D.C.,
330 Ω /V A.C.
Ranges:
D.C. current: 0.06-
0.6-6-60-600mA
A.C. current 0.3-3-30-
300mA
D.C. Voltage: 0.3-1.5
-6-30-60-150-300-
900V
A.C. Voltage: 1.5-7.5-
30-150-300-750V
Resistance: 2-20-
200 Ω -2M Ω
Transistor collector
cut-off current 60 μ A
Transistor D.C. current
gain in two
ranges 10-350
Accuracy: 2.5% D.C.,
4.0% A.C.,
5% D.C. current gain
Power supplies: 4.5V
battery
(Eveready 1289)

Complete with steel carrying case, test lead, battery and instruction manual £14.50

NO OVERLOAD PROTECTION IS INCORPORATED IN THESE INSTRUMENTS

THE ABOVE PRICES ARE EXCLUSIVE OF VAT (at present 8%) HANDLING AND POSTAGE CHARGES £1.25 PER INSTRUMENT

OUR NEW 1976/1977 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0.30

PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Alnsle)

IF Sub-Assembly (G8) £6.80. P & P 75p.
Mullard ELC1043 Varicap UHF Tuner £4.00. P & P 30p.
3-way Station Control Unit £1.20. P & P 25p.
6-way Station Control Unit (Special Offer) £1.00.
Resistors, Caps, Semiconds etc. £5.22. P & P 55p.
Printed Circuit Board £1.00. P & P 30p.
Mains Transformer £2.50. P & P 30p.

Add 12½% VAT to price of goods. P & P all items 75p.

Copy of original article supplied on request

Callers welcome at shop premises.

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6
(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

IT'S EASY WHEN YOU KNOW!

To avoid missing your copy of PRACTICAL WIRELESS—simply complete this order form and hand it to your newsgagent.

ORDER FORM

To: (name of newsgagent)

Address

.....

.....

Please reserve/deliver every month one copy of PRACTICAL WIRELESS until further notice.

My Name

Address

.....

.....

.....

THE OPEN DOOR TO QUALITY



This 144 page catalogue—Electrovalue Catalogue No. 8 (Issue 2, up-dated) offers items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The Company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts are allowed on many purchases; Access and Barclaycard orders are accepted.

40p

POST PAID
inc. 40p Refund
Voucher

+ FREE POSTAGE on all C.W.O. mail orders in U.K. over £2.00 list value (excluding V.A.T.) If under, add 15p handling charge.

All communications to Dept. PW/10
28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
TW20 0HB. Tel Egham 3603. Telex 264475 Shop 9-5.30, 9-1 pm Sat
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester
M19 1NA. Tel: (061) 432 4945. Shop 9-5.30pm, 1 pm Sat.

ELECTROVALUE LTD

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz \pm 5db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 4" deep. AC 200/250V. PRICE £13.75. P. & P. £1.00.

LATEST AGOS GP91/18C mono compatible cartridge with 1/2 stylus for LP/EP/78. Universal mounting bracket. £1.60. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal mounting brackets and Turnover stylus. 70mV per channel output. ONLY £1.90. P. & P. 15p.

SOMATONE STAHG COMPATIBLE STEREO CARTRIDGE 1/0 stylus Diamond Stereo LP and Sapphire 78. ONLY £2.36 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.86. P. & P. 15p.

LATEST CRYSTAL T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/78 Stereo. £1.80. P. & P. 15p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for 1/2 stylus EP/LP/78 mono or stereo records on mono equipment. Only £1.58. P. & P. 15p.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din sockets & 5 pin dm tape rec./play socket are mounted on the printed circuit panel size output. 9 1/2" x 3 1/2" x 1 1/2" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £20.00 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at £1.50 + 40p P. & P. if required. Full connection details supplied.

VYNAIR & REMINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £1.50 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-40-50-60 half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30, at 2 amps full wave. Size 3in. long x 3 1/4in. wide x 3in. deep. Price £2.90 P. & P. 90p.

MAINS TRANSFORMER. For power supplies. Pri. 200/240V. Sec. 9-0-9 at 500 mA. £1.50. P. & P. 60p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.65. P. & P. 60p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2.35. P. & P. 90p. Pri. 200/240V Sec. 23V at 1.5amp, 6V at .6 amp, 8V at 50mA. £2.00 + 65p P. & P.

ALL-PURPOSE POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7.5v, and 9v, and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 4" Ready built and tested Price £2.75 P. & P. 85p.

STEREO-DECODER SIZE 2" x 3" ready built. Pre-aligned and tested. Sec. 20-50V for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £2.40 plus 20p. P. & P. Stereo beacon light if required 40p extra.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 8 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £7.00. P. & P. 90p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £8.00. P. & P. £1.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200/240V Mains operated Solid State F/M A/M Stereo Tuner. Covering M.W. A.M. 540-1805KHz VHF/FM 88-108MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" x 4 1/4" x 9 1/4" deep.

LIMITED NUMBER ONLY at £28.00 + £1.30 P. & P.

SPECIAL OFFERS

Mullard LP1159 R.F.-I.F. Double Tuned Amplifier Module for nominal 470 KHz. Size approx. 2 1/2" x 1 1/2" x 1 1/2" 7-8 Volt + earth. Brand new pre-aligned. Full specification and connection details supplied. £2.25. P. & P. 12p

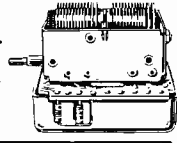Fye VHF/FM Tuner Head covering 88-108 M/HZ. 10-7 M/HZ I.F. output. 7-8 Volt + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-gear FM gang and 323P1 + 323P1 A.M. Tuning gang only £3.15 + P. & P. 35p.



PRECISION MADE Push Button Switch bank. 8 Buttons giving 16 S/P C/O Interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" x 2 1/4" x 1". Supplied complete with chrome finished switch buttons. £ for £1.50 + 20p P. & P.

HI-FI LOUDSPEAKER SYSTEM MK II

Beautifully made, simulated teak finish enclosure with attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm Impedance (state which). Handling power 10 watts R.M.S. OUR PRICE £12.80 each. Carr. £1.90 ea. Cabinet Available Separately £7.60. Carr. £1.40 each. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £11.10. Carr. £1.90 ea.

LOUDSPEAKER BARGAINS 5in. 3 ohm £1.45. P. & P. 35p. 7 x 4in. 8 ohm £1.60. P. & P. 45p. 10 x 6in. 3 or 15 ohm £2.50. P. & P. 75p. E.M.I. 8 x 5in. 8 ohm with high flux magnet £2.06. P. & P. 50p. E.M.I. tweeter. Approx. 3". Available 3 or 8 or 16 ohms, £2.00 + 25p. P. & P.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER Size 11" x 14" x 1 1/4" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8.40 each + p. & p. (one 75p, two 90p).

Now also available 8" - 8 ohm 10 watts, r.m.s. 20 watt peak 40 Hz-20,000 Hz. Overall depth 1". Ideal for HI-FI or for use in cars £2.10 + p. & p. (one 35p, two 65p).

SPECIAL LINES OFFERED SUBJECT TO STOCK AVAILABILITY


Limited number of British manufacturer's surplus professional 100 watt RMS slave amplifiers. Special features, 2 separate power modules, 1 for Bass response and 1 for mid-range/tweeter, 5 stage LED display for power o/p indication. A/C mains i/p switchable for 110 or 230V. Can easily be converted to Stereo. AVAILABLE TO PERSONAL CALLERS ONLY, PLEASE PHONE TO CONFIRM AVAILABILITY. Brand new & tested only £23.75.

25 watt RMS Solid state power amplifier module. Fre. Resp. 35 Hz-20 KHz. Power requirements 40 volts @ 1.5 amps. Full c/d & connection details supplied. £2.20 + 30p P/P.

New but very slightly marked 'GLRNBURN' BSR automatic record changer decks fitted with cueing lever, lightweight arm and ceramic HI-FI stereo/compatible cartridge. Can be used for automatic or manual play. PRICE £2.56 + £1.20 P. & P.

Limited number of the latest BSR C149 auto manual changer de-luxe. Lightweight tubular arm with adjustable counterweight cueing lever, bias compensator. PRICE £13.00-£1.00 P. & P.

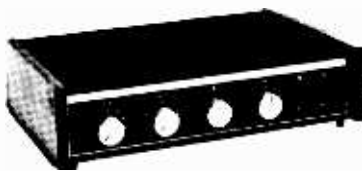HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response \pm 3db 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3db 12-15,000 Hz. Bass boost approx. to \pm 12db. Treble cut approx. to -16db. Negative feedback 18db over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT £13.50 P. & P. 65p (Magnetic input components 33p extra)
POWER PACK KIT £5.50 P. & P. 85p
CABINET £5.50 P. & P. 85p

SPECIAL OFFER—only £23.75 if all 3 items ordered at one time plus £1 p. & p.
Full after sales service

Also available ready built and tested £31.25. P. & P. £1.




8-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for HI-FI reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4 1/4" x 4 1/4". Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 8 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £20.20. P. & P. £1.00.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £7.60 P. & P. £1.00.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + SAE (Free with parts) All parts sold separately. ONLY £12.00 P. & P. £1.35. Also available ready built and tested £16.50 P. & P. £1.35.

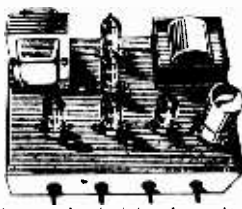

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 1Hz-20KHz. Gain 26db. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price £1.80 P. & P. 15p.

Prices include VAT at Current Rate

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday.

All prices and specifications correct at time of press and subject to alteration without notice.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station. SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

The new Maplin Catalogue is no ordinary catalogue...




Hundreds of fascinating new lines

Several major new projects to build



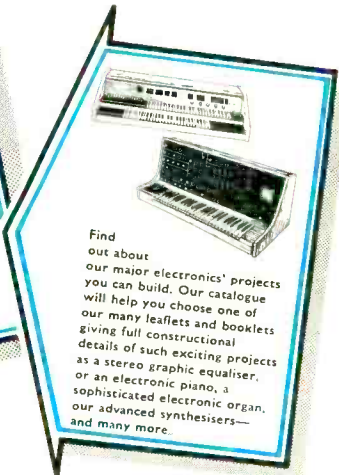
The new tools section includes a range of soldering irons and equipment whilst the test gear section includes a selection of multimeters from 1000 Ω/V to 100,000 Ω/V to suit your requirements.



Find out about our major electronics' projects you can build. Our catalogue will help you choose one of our many leaflets and booklets giving full constructional details of such exciting projects as a stereo graphic equaliser, or an electronic piano, a sophisticated electronic organ, our advanced synthesisers—and many more.

Super Discount Scheme - saves you pounds!

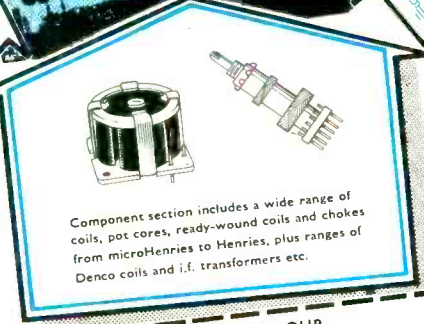Hundreds of photo-graphs and illustrations



Component section includes a wide range of coils, pot cores, ready-wound coils and chokes from microHenries to Henries, plus ranges of Denco coils and i.f. transformers etc.

Catalogue includes a very wide range of components: hundreds of different capacitors; resistors; transistors; I.C.'s; diodes; wires and cables; discotheque equipment; organ components; musical effects units; microphones; turntables; cartridges; styli; test equipment; boxes and instrument cases; knobs, plugs and sockets; audio leads; switches; loudspeakers; books; tools - AND MANY MANY MDRE.



* Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers (they save you pounds) - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

SEND THIS COUPON FOR YOUR COPY OF OUR CATALOGUE ON APPROVAL! Price 50p—SEND NO MONEY NOW.

Please rush me a copy of your brand new 1977/78 catalogue by return of post. Only if I am completely satisfied that it is worth every penny, will I send 50p within 14 days of receipt. If I am not satisfied, I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME _____

ADDRESS _____

PW3

Maplin Electronic Supplies P.O. Box 3, Rayleigh, Essex, SS6 8LR

MAPLIN

ELECTRONIC SUPPLIES
P.O. BOX 3, RAYLEIGH, ESSEX SS6 8LR

DON'T DELAY
POST COUPON NOW
IT COULD BE THE BEST 50p
YOU'VE EVER SPENT.

Telephone: Southend (0702) 715155
Call at our shop: 284 London Road, Westcliff-on-Sea, Essex.
(Closed all day Monday) Telephone: Southend (0702) 47379

69 Rayleigh Defad