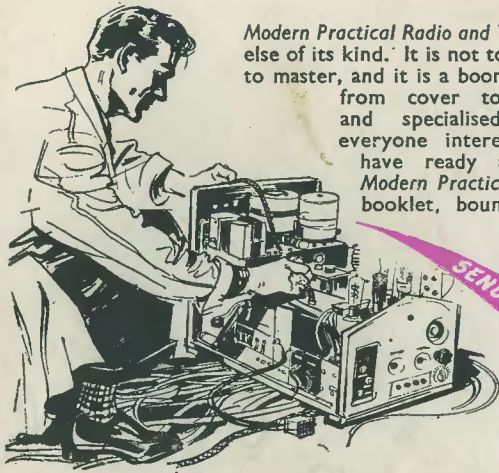


MODERN PRACTICAL RADIO AND TELEVISION



Modern Practical Radio and Television is quite different from anything else of its kind. It is not too advanced for the enthusiastic amateur to master, and it is a boon for any expert. It is, in fact, crammed from cover to cover with a wealth of general and specialised knowledge — knowledge that everyone interested in Radio and Television should have ready at their finger-tips. Supplied with *Modern Practical Radio and Television* there is a separate booklet, bound to match, which gives details of 48 circuits and models, and a mass of useful formulae and data.



THE CONTENTS

Sound, Capacity, Reactance and Impedance, Tuned Circuits, Principles of the Thermionic Valve, Detection, H.F. of Tetrode and Pentode, High-frequency Amplification, Frequency - changing Valves, Design of the Superheterodyne, Low-frequency Amplification, The Output Stage, Automatic Controls, Frequency Modulation, Five Circuits Analysed, High Vacuum Cathode-ray Tube and its Application to Television, Television - receiver Design, Adjustments and Faults of a Television Receiver, Valve Testing Fault-Finding Procedure, etc. etc.

THE ILLUSTRATIONS

"Modern Practical Radio and Television" is profusely illustrated. It contains 16 full-page plates, over 400 diagrams in the text and 7 large folding insets. Each illustration has been specially selected for its practical utility.

FREE PARTICULARS

To THE CAXTON PUBLISHING COMPANY LIMITED,

73 MORLEY HALL, ST. GEORGE STREET, HANOVER SQUARE, LONDON, W.1.

Please send me, free of charge, particulars of "Modern Practical Radio & Television" together with your terms of easy payment.

Name.....

(Send this form in unsealed envelope 1½d. stamp)

Address.....

RT16.....


The

RADIO CONSTRUCTOR

Volume 8
Number 2
SEPTEMBER
1954

incorporating *The Radio Amateur*
for the *Radio and Television Enthusiast*

THE EASI-BUILD

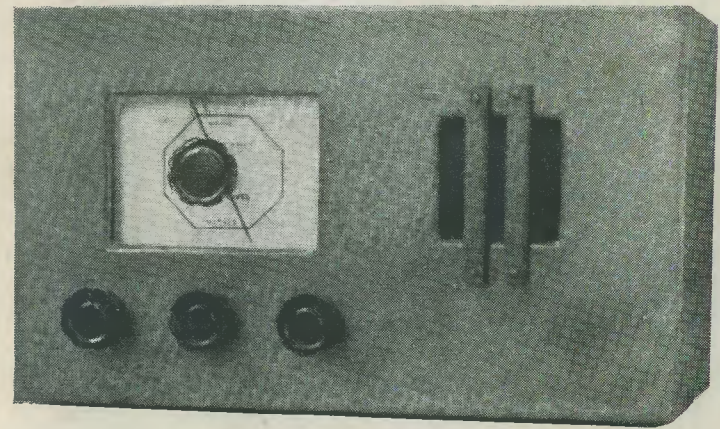

A design for the Beginner

ALSO IN THIS ISSUE

DESIGN, CONSTRUCTION, CALIBRATION AND USE OF SIGNAL GENERATORS, PT. I

FM TUNER UNIT MODIFICATIONS


REPAIR & MAINTENANCE OF LINE OUTPUT TRANSFORMERS

INEXPENSIVE RECORD PLAYER

KNUPPLE SYSTEM OF RADIO CONTROL

BEGINNERS THREE-VALVE BATTERY RECEIVER · Matching · Using

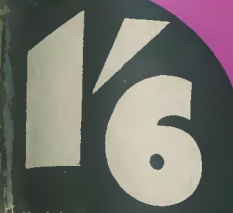the New Panel-Signs · Query Corner · Radio Miscellany, etc



Printed in Great Britain for the Proprietors and Publishers Data Publications Ltd., 57 Maida Vale, London, W9, by A. Quick & Co. Ltd., Oxford House, Clacton-on-Sea, Essex. Is obtainable abroad through the following: Collects Subscription Service, Continental Publishers & Distributors, Ltd., William Dawson & Sons Ltd. Australia and New Zealand: Gordon & Gotch Ltd. South Africa: Central News Agency. U.S.A.: Gilfer Associates. Holland: "Radio Electronica." Scandinavia: Intrapress. Registered for transmission by Magazine Post to Canada (including Newfoundland).



THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS OF ENGLISH & AMERICAN TECHNICAL BOOKS

'VADE-MECUM' Television and Special Tubes, 11th edition. By P. H. Brans. 22s. 6d. Postage 1s.

Radio Valve Data. By Wireless World. New edition. 3s. 6d. Postage 3d.

Radio Control for Model Ships, Boats and Aircraft. By F. C. Judd, G2BcX. 8s. 6d. Postage 4d.

The Electronic Musical Instrument Manual. By Alan Douglas. 30s. Postage 1s.

Tape and Wire Recording. 2s. 6d. Postage 2d.

Electronic Gadgets for the Constructor. By E. N. Bradley. 3s. 6d. Postage 3d.

The Oscilloscope and its Applications. Philips Electrical Co. 5s. Postage 3d.

Sound Recording and Reproduction. By Godfrey & Amos. 30s. Postage 1s.

Oscilloscope at Work. By Haas and Hallows. 15s. Postage 9d.

Practical Television Circuits. By Camm. 15s. Postage 9d.

TV Fault Finding. 5s. Postage 3d.

The Radio Amateur's Handbook. By A.R.R.L. 30s. Postage 1s.

Practical Wireless Circuits. By Camm. 10s. 6d. Postage 6d.

Basic Electronic Test Instruments. By Turner. 32s. Postage 1s.

Write or call for our catalogue

19-23 PRAED STREET (Dept. RC) LONDON W2

PADDington 4185

SCOTTISH INSURANCE CORPORATION LTD.



62-63 CHEAPSIDE LONDON, E.C.2.

TELEVISION SETS AND SHORT WAVE TRANSMITTERS

Television Sets and Short Wave Transmitters/Receivers are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets and Short Wave Transmitters/Receivers provides the following cover:—

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) (i) and (ii) costs only 2/6 a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's Office at the above address, a proposal will be submitted for completion.

NAME (Block Letters).....

(If lady, state Mrs. or Miss)

ADDRESS (Block Letters).....

/JB

ALL-ROUND DEPENDABILITY

VALVE CHARACTERISTIC METER
UNIVERSAL BRIDGE
ELECTRONIC TESTMETER
ELECTRONIC TEST UNIT
WIDE RANGE SIGNAL GENERATOR
HEAVY DUTY METER
THE D.C. MINOR
UNIVERSAL METER

AVO Precision ELECTRICAL MEASURING INSTRUMENTS

Dependability is an essential quality in any good electrical testing instrument. Absolute dependability is the outcome of good design, suitability for purpose, and a high standard of accuracy. These indispensable factors are exemplified in all "AVO" instruments, which are also noteworthy for their compact portability and robust construction.


You can depend on "AVO." When choosing instruments, consult our complete catalogue, a copy of which may be had free on application.

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
WINDER HOUSE • DOUGLAS STREET • LONDON S.W.1. Telephone: V1Ctor10 3404-2

MAXI-Q

REGD.

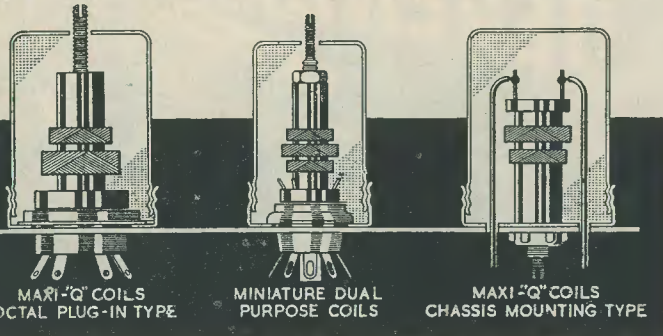CONTAINER the size of which has been mathematically arrived at to enable you to use it as a SCREENING CAN for the ACTUAL COIL itself.



MAXI-Q COILS
OCTAL PLUG-IN TYPE

MINIATURE DUAL
PURPOSE COILS

MAXI-Q COILS
CHASSIS MOUNTING TYPE

Range covers from 3.8 to 2,000 metres—Litz Windings—Neosid Iron Cores—Full information on Plug-in and Chassis Mounting Maxi-Q Coils is given in Technical Bulletin DTB.1—Price 1/6. Miniature Dual Purpose Coil information given in DTB.4—Price 1/6—No change in prices, see General Catalogue Price 9d. Cans available separately at 6d. each.

DENCO (CLACTON) LTD., 357/9 OLD ROAD, CLACTON-ON-SEA

We are sure you will agree

that our company has and still continues to give you the finest possible service and value in coil design. We were one of the first to introduce Polystyrene Insulated Formers, then came the Octal Plug-in type, then B9A Plug-in or Chassis Mounting Miniature Dual Purpose Coils and the last to be introduced was the all moulded Former single hole fixing with a Polystyrene Nut giving you crackle and corrosion free inductors. Now we think we have reached our last possible improvement. EVERY COIL IS PROVIDED IN AN AIRTIGHT ALUMINIUM



POST TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE & INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications: A.M.Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training

★ The teaching methods are planned to meet modern industrial requirements. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY COURSES WITH EQUIPMENT

With many of our courses we supply actual equipment which is sent upon enrolment and remains your property. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Courses from £1 per month

POST THIS COUPON TODAY


Please send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 179K, 43 Grove Park Road, Chiswick, London, W.4.

NAME _____
ADDRESS _____
SUBJECT(S) _____

EMI INSTITUTES

The only postal College which is part of a world-wide Industrial Organisation.

Announcing an Entirely New TAPE UNIT

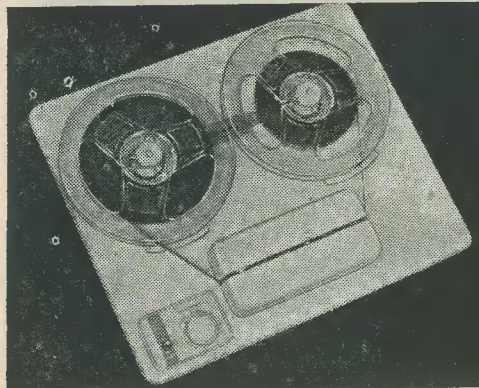

2 SPEED, Mk. VI


- ★ Three high grade motors
- ★ Single knob control electrically and mechanically interlocked
- ★ Drop in tape loading
- ★ Automatic brakes
- ★ 2 speed, 7½"/sec. 3¾"/sec.
- ★ Automatic speed change

£18 10 0

Attractive discounts to quantity buyers. Beautifully finished and engineered, this new model offers unequalled value. Write for full details to

VERDIK SALES LIMITED

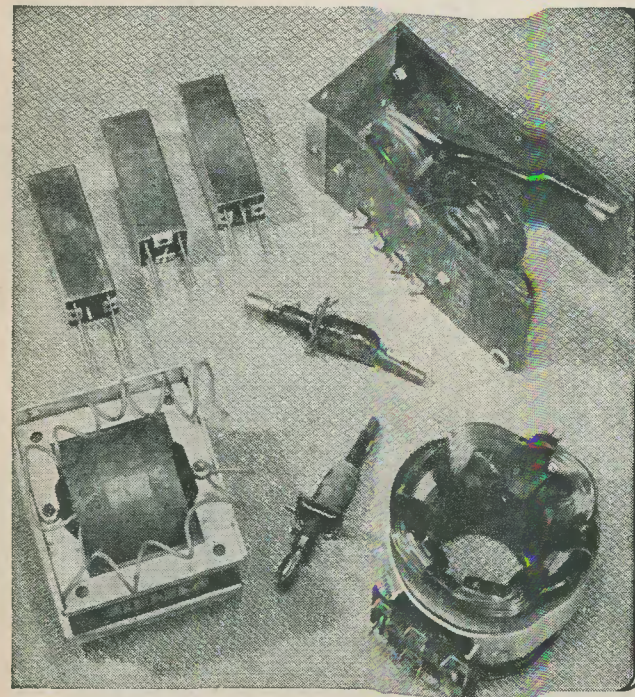8 RUPERT COURT, WARDOUR STREET, LONDON W.1. GERard 8266



THESE STANDARD WIDE ANGLE COMPONENTS ARE USED IN THE "TELEKING" AND "SUPERVISOR"

Also for the conversion to 14" or 17" C/R Tube of all popular home-built televisions.

From all leading stockists.

ALLEN COMPONENTS LIMITED

Crown Works
Lower Richmond Road
Richmond Surrey

Telephone Prospect 9013

Send 9d. and stamped addressed envelope for Circuit Diagram.

Smith's of EDGWARE ROAD

Component Specialists Since Broadcasting Started

Can now supply a full range of 4-sided Blank Chassis of 16 Gauge half-hard aluminium.

Size (inches)	Price	Size (inches)	Price
6 x 4 x 2	4/6	11 x 8 x 2½	8/-
7 x 5 x 2	5/-	10 x 8 x 3	8/6
8½ x 5½ x 2	5/6	13 x 8 x 2½	8/9
10 x 4 x 2½	6/-	12 x 9 x 2½	8/11
9 x 7 x 2	6/6	13 x 10 x 2½	9/9
12 x 4 x 2½	6/6	14 x 10 x 2½	10/-
9 x 8 x 2½	7/3	12 x 10 x 3	10/3
10 x 8 x 2½	7/6	15 x 10 x 2½	10/6
12 x 5 x 3	7/9	17 x 10 x 2½	11/3
12 x 7 x 2½	7/11	17 x 9 x 3	11/9
		17 x 10 x 3	12/6

Keep this List for reference.

H. L. SMITH & CO. LTD
287/9 Edgware Road London W2
Telephone Paddington 5891
Hours 9 till 6 (Thursday 1 o'clock)
Nr. Edgware Road Stations, Metropolitan & Bakerloo

Frequency Modulation Tuner

described in the July and Sept. 1954 issues.

JACKSON BROS. dial and condenser
£1 5 3

Completely drilled chassis 8 0

All coils with S.M. Condensers and Cans £1 0 6

Complete Set of Parts, including valves, pair of matched Germanium crystals and small items such as nuts and screws £7 2 6

Complete Tuner, assembled and aligned £10 0 0

G. BLUNDELL
7 SUNNYSIDE HOUSE
CHILDS' HILL LONDON NW2

ARTHURS HAVE IT!

LONDON'S OLDEST RADIO DEALERS
LARGE VALVE STOCKS

AVOMETERS IN STOCK
Avo Test Meters and Signal Generators and Taylor Meters
Leak Point One Amplifiers and Tuning Units.

Chapman Tuning Units.
Crystal and Moving Coil Mics.
Decca Replacement Heads and Pickups.
Goodman's Axiom 150 Speakers.
Partridge Output Transformers for Williamson Amplifier.

All Components for the Radio Constructor's 16" Telesvisor.

Wears & Wright Tape Deck £35.

LATEST VALVE MANUALS
Mullard, Osram & Brimar No. 4 5/- each
Mazda 2/- each Postage 6d extra

TELEVISION SETS, WIRE AND TAPE RECORDERS ALWAYS IN STOCK
Goods offered subject to price alterations and being unsold.

Arthurs first
Est 1919

Proprietors: ARTHUR GRAY LTD.
OUR ONLY ADDRESS Gray House
150-52 Charing Cross Road
London, W.C.2.
TEMPle Bar 5833/4 and 4765 WRITE FOR LISTS

Have Your Copies Bound

VOLUMES OF
RADIO CONSTRUCTOR

FULLY BOUND IN IMITATION LEATHER WITH GOLD LETTERING. 8s. 6d.
POST FREE. PRICES FOR OTHER PUBLICATIONS ON APPLICATION

If not required to be bound in remove covers before sending

A. QUICK & CO LTD
OXFORD HOUSE
CLACTON-ON-SEA · ESSEX

Bring your equipment up-to-date with ACOS REPLACEMENT PICK-UP HEADS

If you already own a fine radiogram or record-player you now have the opportunity of rejuvenating it—of bringing it right up-to-date for a quite modest sum. Acos Hi-g crystal pick-ups are now available in a range of specially designed "plug-in" models to suit most famous makes of record reproducing equipment.

These Acos "Hi-g" Pick-ups, you will find, represent a truly phenomenal advance in pick-up design—with regard to both reproduction and tracking characteristics (so important with many of the new micro-groove recordings).

Ask your dealer!

MODEL HGP 33-I & HGP 37-I Collaro		HGP 33-I Collaro. Hi-g head incorporating HGP 33-I turnover cartridge for standard and micro-groove records. HGP 37-I Collaro. As above with HGP 37-I turnover cartridge (cantilever styli). Both models available in cream or walnut and will fit Collaro units RC 532; AC 534; AC3/534; 3/RC 532; and Studio pick-up. Ask for Data Sheets No. 4700 and 4800.
HGP 33-I & HGP 37-I Garrard		HGP 33-I Garrard. Hi-g head incorporating HGP 33-I turnover cartridge for standard and micro-groove records. HGP 37-I Garrard. As above with HGP 37-I cartridge (cantilever styli). Both models will fit Garrard units RC 75M; RC 80M; RC 90; RC 111; Model TA. Ask for Data Sheets No. 4700 and 4800.
HGP 39-I		Hi-g pick-up heads incorporating cantilever sapphire styli. Separate heads for standard and microgroove records. Will fit the Acos GP 20 pick-up arm and the Garrard C type adaptor. Used on the following Garrard units: RC 72A; RC 75A; RC 80; and the Model M unit. Can be used on any units which at present use the GP 19 heads. Ask for Data Sheet No. 4400.
HGP 35-I		Separate plug-in type Hi-g heads for standard and microgroove records; fitted with cantilever sapphire styli. The crystal unit is identical to that of the HGP 39-I above. Can be used on Garrard units RC 75M; RC 80M; RC 90; RC 111 and the TA player. Ask for Data Sheet No. 4000.
HGP 41-I		Separate Hi-g plug-in type heads for standard and microgroove records incorporating the crystal unit as used in the HGP 39 pick-up head. Will fit Collaro units RC 532; AC 534; AC3/534; 3RC 532. Available in cream or walnut. Ask for Data Sheet No. 4500.
HGP 45		Separate Hi-g pick-up heads for either standard or microgroove records. The crystal unit is identical to that used in the HGP 39-I head. Will fit Garrard units RC 80; RC 72A; RC 75A; and the Model M player. Can be used on any unit which at present uses the Garrard C adaptor with GP 19 heads. Ask for Data Sheet No. 4600.



Price 32/6 (Plus 10/5 P.T.) for all types except the HGP 39 which are 32/- (PLUS 10/3 P.T.)

...always well ahead

ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.
GOSMOCORD LIMITED ENFIELD MIDDLESEX

THE **Osram**

'NINE-ONE-TWO'
A book you simply must get!



PRICE

3'6

On sale at the G.E.C. Demonstration Room D8 (where the Amplifier will be demonstrated), The National Radio and Television Exhibition, Earls Court, or 3/9 post free from The General Electric Co. Limited.

NOTE THESE POINTS:—

Full power output (12 watts) within 1db from 30 to 20,000 cycles/sec. (9 octaves).
Provision for 4 controls of frequency response (in addition to volume control), to achieve the requirements of "Art" in listening.
Uses the famous Osram Z729 low noise pentode—acknowledged the lowest measured microphony and hum level of any comparable valve in the world.
Uses NEW Osram power pentodes type N709 in push-pull "ultra-linear" output stage, with selective feedback.
Sets a startlingly new standard (combined with G.E.C. speaker in octagonal loaded port cabinet) in the realism possible from listening to modern L.P. records.
Variable "slope" control allows for reduction of surface noise in older cherished records, with minimum reduction in higher frequency response.

As the "Williamson" KT66 Amplifier—designed around Osram Valves—set the standard in its class throughout the world, so now the Osram 912 sets the standard in high quality sound for everyman.

- * Complete circuit data
- * Easily followed wiring diagram
- * Specified components of highest quality only

Much other valuable information for the Home Constructor is in the book—"The Osram 912"—a practical sequel to "Art and Science in Sound Reproduction."

THE GENERAL ELECTRIC COMPANY LTD., MAGNET HOUSE, KINGSWAY, W.C.2

The Radio Constructor

INCORPORATING *The Radio Amateur*



CONTENTS FOR SEPTEMBER

- 72 Suggested Circuits: An Inexpensive Record Player, by G. A. French
- 74 In Your Workshop, by J. R. D.
- 78 Club News
- 79 Repair and Maintenance of Line Output Transformers, Part 1, by S. Welburn
- 83 The Easi-Build Receiver, Part 1, by M. Harvey
- 90 Frequency Modulation Tuner Unit Modifications, by W. Gordon
- 94 The Design, Construction, Calibration and Use of Signal Generators, Part 1, by R. J. Stephenson
- 98 Using the New Panel Signs
- 101 Building the RCS Battery Receiver, Part 3, by James Sinclair
- 105 Query Corner—A Service for Readers
- 107 Can Anyone Help?
- 108 Radio Miscellany, by Centre Tap
- 109 Walton Amateur Radio Exhibition
- 110 Knipple System of Radio Control, by A. C. Gee, G2UK
- 114 Let's Get Started: Matching, by A. Blackburn
- 118 Some Observations on the 1954 National Radio Show

VOL. 8 NO. 2
ANNUAL SUBSCRIPTION 18/-
SEPTEMBER 1954

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9

Telephone
CUNNINGHAM 6518

Editor
C. W. C. OVERLAND, G2ATV

Advertising Manager
F. A. BALDWIN, A.M.I.P.R.E.

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor. Opinions expressed by contributors are not necessarily those of the Editor or proprietors


NOTICES

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

All Mss must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc. are invited to submit samples or information of new produce for review in this section.

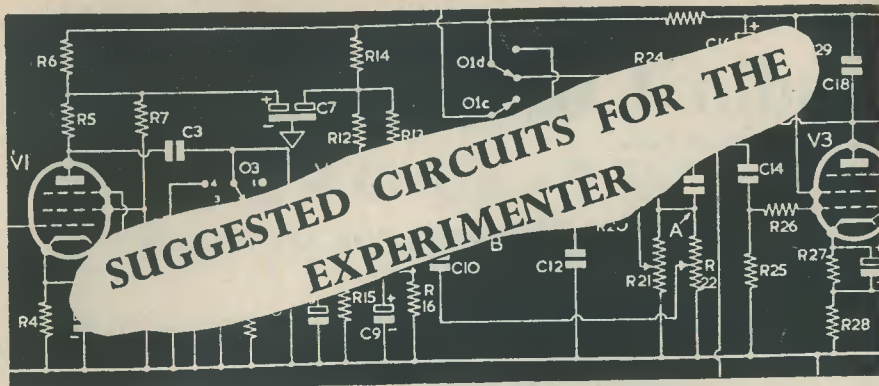ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR, 57 Maida Vale, London W.9 Telephone CUN. 6518



The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data

No. 46. AN INEXPENSIVE RECORD PLAYER

THERE APPEARS TO BE, AT THE PRESENT time, a large number of gramophone record players of various manufacture offered for sale to the public. These players range from the inexpensive popular types to the more costly "quality" models. Several readers have requested details of a simple and reliable record player, stating that, although much space is devoted in the technical press to high-fidelity equipment, little attention is given to the design of cheap and less pretentious gear.

This month's circuit, therefore, illustrates a very simple amplifier which may be used with most modern crystal pick-ups, and which is capable of being built into a compact carrying case together with the attendant gramophone motor and loudspeaker.

The Circuit

As will at once be apparent, the circuit is very simple and straightforward. The amplifier proper employs one valve only, and this may consist of any high-gain output pentode. The crystal pick-up is taken direct to the grid of this valve, via the volume control R1. The anode then feeds into the speaker transformer, and thence to the speaker.

A simple tone control is provided by R3, R4 and C4. This control is of the top-cut variety. (For smooth operation, incidentally, R3 should be logarithmic). The resistor R4 is included to prevent heavy AF current flow through the track and slider of the tone control when it is set to the full-cut

position. If this resistor were not fitted it is possible that the heavy AF current would burn the track and cause subsequent sparking when the speaker transformer primary had high AF voltages built up across it.

The power supply arrangement is of interest. This utilises a normal heater transformer to supply the heaters of the valves. The primary has three taps at the conventional voltages (210, 230 and 250); and the rectifier anode is fed from the 250 volt tap to ensure that a reasonably high HT voltage is available whatever the mains supply voltage may be. If the record player is to be built as a "portable," it would be worth-while having a mains adjustment panel fitted in an accessible position.

The half-wave rectifier, V2, is supplied via a 120Ω limiter resistor, and its cathode is connected to a 32μF reservoir condenser, C6. The HT voltage appearing across this condenser is applied to the anode of V1 directly. The screen-grid of V1 is fed from C5, however, the resistor R5 providing additional smoothing. Suitable rectifiers are the 6X4 or EZ41.

The bias resistor, R2, has been chosen for use with the Mullard EL41 output pentode. It may be necessary to alter its value when other output valves are employed.

Performance

The performance to be obtained from this record player will, with most crystal

pick-ups, be found to be surprisingly good. The amplifier is, of course, by no means intended to be in the high fidelity class, but its quality of reproduction will be at least as good as that given by the conventional domestic type of receiver.


Although only one stage of amplification is used, volume should be more than adequate for normal purposes. As mentioned above, a crystal pick-up is needed. The voltage of a magnetic pick-up would not be sufficiently high for the limited amplification available. The writer has checked the circuit by building a working model; and

with most of the more inexpensive loudspeakers which are at present available.

The Chassis

The record player has two chassis; that of the amplifier, and that of the motor-board and pick-up assembly.

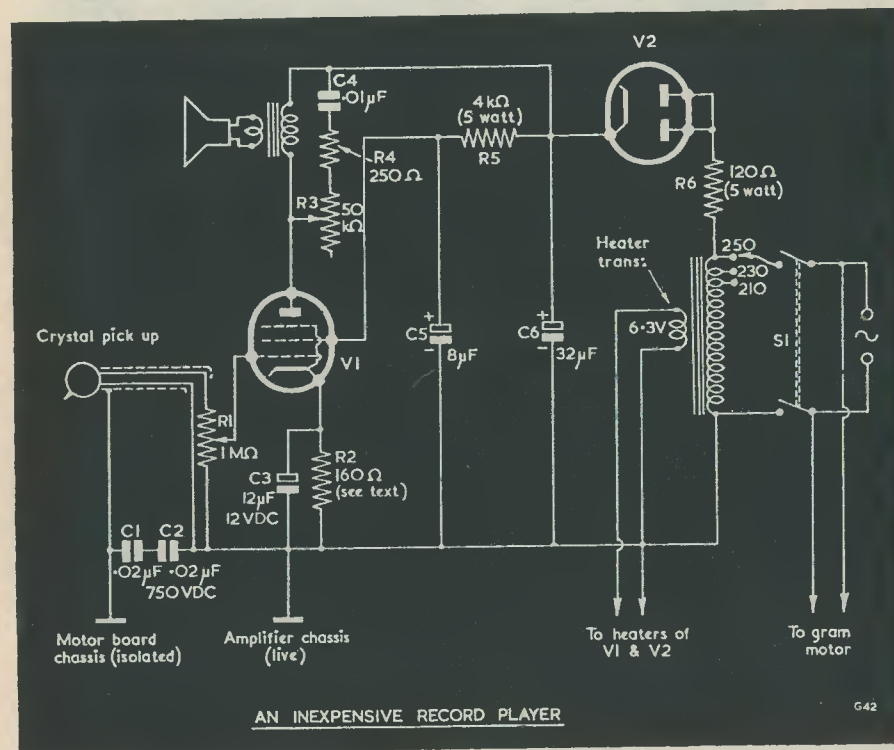The amplifier chassis is "live," and must be mounted, accordingly, in the body of the record player cabinet where it cannot inadvertently be touched. As the motor-board chassis will most probably consist of a large surface of metal, part of which must inevitably be handled when the player is




he obtained very good results with a modern turn-over crystal cartridge playing both 78 rpm and microgroove records.

Despite the extremely simple HT arrangements, no trace of hum was discernible in the working model. If a large, high fidelity reproducer were used, however, slight hum might be apparent. Nevertheless, it is doubtful if hum would be at all noticeable

operated, this is isolated from the mains. Although it is customary to use a single isolating condenser at this part of the circuit, two condensers connected in series (C1 and C2), are shown here. This course is recommended as it lessens the chances of accidental shock due to breakdown or leakage.

[continued on page 78]

IN YOUR WORKSHOP

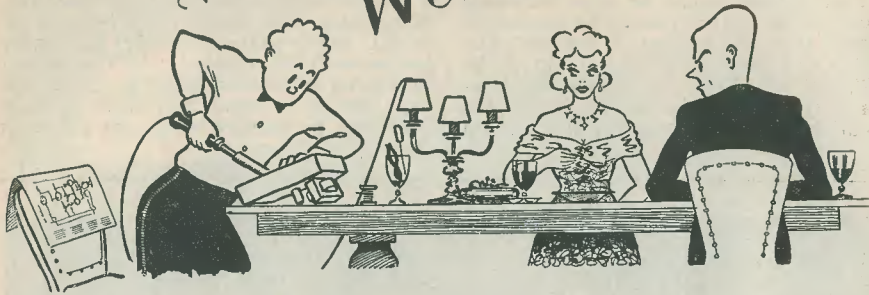

In which J. R. D. discusses Problems and Points of Interest based on Letters from Readers and his own experience

POTTERING AROUND WITH SURPLUS EQUIPMENT is liable, at times, to bring back many recollections of the war. The other day, for instance, I was rather urgently in need of some temporary test-gear for a special job. I didn't have the time to make up a proper chassis and case for the gear, and so I dug out an old store-soiled R1132 which I had bought some years ago at a knock-down price.

Looking Back

This set had never done anything since I bought it; apart, that is, from collecting dust and yielding the odd resistor or condenser every now and again. It had become, therefore, thoroughly "Christmas-treed," and I decided to strip it down for the chassis.

On examining the receiver more carefully I found that someone in the past had been writing in pencil on the chassis at the side of the RF strip. The legend ran something like the following.

"IF's re-aligned to 180 kc/s bandwidth. V5 replaced. C12 (leaky) replaced. RF Volume pot slightly scratchy, no spares." It carried on like this for a few more lines, then ended with the date: 22/3/44. There was no signature.

In 1944, I was doing my inconspicuous bit to help win the war on an RAF Maintenance Unit near Naples. And in our Radio Workshop we used to have a very keen type repairing R1132's who was in the habit of putting an unofficial report of this nature on the sets he passed through in just this very manner. It was quite a good idea, too.

The repair system working at that time was that all the unserviceable radio gear from the nearby RAF units went into the Maintenance Units' Stores and was issued to the Radio Workshop for repair. The sets were put out, usually in dozens, on Job Cards; and were sent to the Serviceable Stores, for re-issue to units, on the same Job Card number after they had been made serviceable. It was quite a good system since the Job Cards kept a reasonable tally on what went in and what came out, and it didn't give the office staff the excuse to waste too much paper.

However, it suffered from some disadvantages, the worst of these being that it didn't allow for shortages of spare components. If some of the Powers-that-be at that time had had their way, they would have been quite happy to see two receivers sitting side-by-side on the shelf awaiting spares, one with a burnt-out output transformer, the other with a broken tuning condenser. The technical types, who wanted to get the war over and go home, were not too keen on this scheme and so, in practice, one set was often "cannibalised" to repair another.

The result of this was that from a Job Card of a dozen sets there occasionally emerged an output of eleven shining and serviceable receivers and one which, like Jacques' old man, was "sans eyes, sans teeth, sans taste, sans everything!"

Of course, the work was not really carried out quite as irresponsibly as the above may suggest, and it was usually found possible to keep a set which was very bad on receipt

hidden away in the Stores, and use this for spares.

"That Old Junk!"

Another disadvantage with the Job Card idea was that a record of faults and repairs was never attached to the set itself. A set was either "Serviceable" or it was "U/S." Therefore it was never possible to know whether a set had been aligned recently, what components had been replaced in it, and, most important of all, whether it had ever suffered from an intermittent fault.

The airman who was servicing the R1132's at the time I am talking about felt rather keenly about this, and so he started making his own unofficial and unsigned maintenance records on the chassis. It was quite possible, therefore, that the 1132 I was stripping down a few weeks ago was one of those that passed through his hands in 1944. I couldn't help reflecting on the journey it must have undergone: from Italy to England; thence to the MOS dump; to the job-lot buyer; and, finally, to the shop in London where I purchased it.

At about that moment, a young chap who has just completed his National Service marched into my workshop and watched me working away on the dusty old receiver.

"This," I remarked impressively, "is one of the sets which helped to win the war."

"What!" he said scornfully, "that old junk!"

VHF

That young man was quite right, in a way, because the R1132, with its VR65's and VR53's, is definitely somewhat venerable these days. But it was never junk. One has only to examine an 1132 to appreciate the care with which it was designed and, despite the fact that these receivers were built during the war, the workmanship which went into its construction.

The 1132 was the first ground station VHF receiver used in the RAF, and it carried on all the way through the war with hardly a modification at all. It was one of those receivers which one fitted into a rack, switched on, and forgot about until it was due for its next workshop checkover.

So far as I can remember it suffered from one snag only, that being frequency drift. The drift was not excessive, especially after the set had been switched on for several hours, but it was enough to make it worthwhile checking the tuning every thirty minutes or so. Bad cases of drift could usually be cleared by changing the oscillator valve.

Apart from that small trouble the 1132 was a very fine receiver, and was well to

the fore-front of contemporary design at the date of its inception. So I think I wasn't so far wrong, either, when I described it as a set "which helped to win the war."

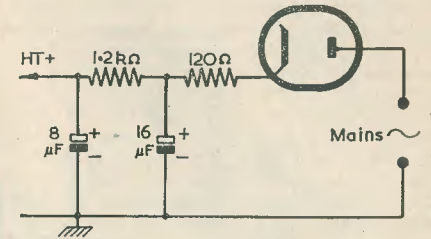


Fig. 1a

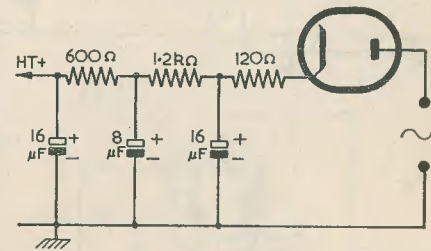


Fig. 1b

E60

Fig. 1. "Before and After" diagrams showing how hum was cleared in a midget receiver when it was connected to a larger loudspeaker. The original circuit is shown at (a); whilst (b) shows how an additional resistor and condenser improved smoothing. The two extra components need take very little space on the chassis.

Improving a Midget

An acquaintance, working on a small broadcast receiver, encountered one or two interesting little points recently which should be of interest to readers.

He had obtained a set in the semi-midget class and had decided to improve its performance. Examining its circuit, he soon realised that it was just a normal four-plus-one in miniature, with most of the trimmings. He considered therefore that his first step should be to try it out with a bigger loudspeaker. His ultimate aim was to keep the little set on the mantelpiece and to have the speaker, in a large cabinet, in a corner of the room.

The set, working into the larger speaker, gave a much improved performance; and was marred only by a slight, but noticeable, hum. He decided, quite rightly, that the

8 μ F condenser. My friend considered that this was not adequate when the larger speaker was being used. He would have liked to have fitted a choke instead of the

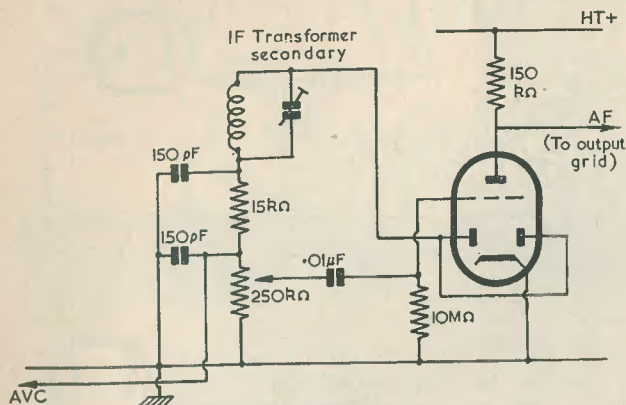


Fig. 2a

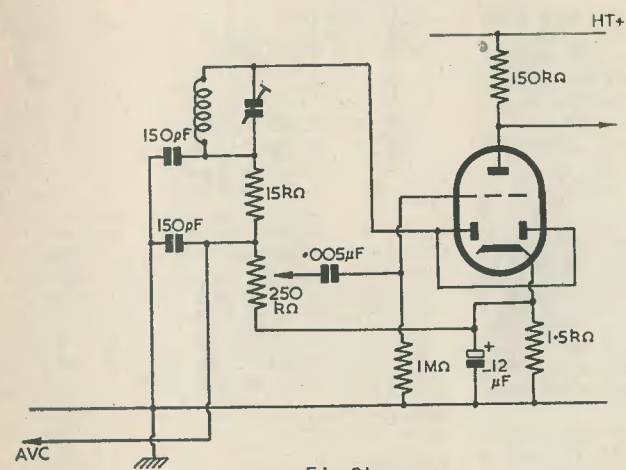


Fig. 2b

Fig. 2. Another improvement to the miniature receiver. In (a) an economic circuit, which provides bias for the triode by leaky-grid rectification, is employed. This was changed to that of (b), in which conventional cathode bias is used.

hum had been present in the output of the set all the time, and that the miniature speaker used originally simply hadn't been capable of reproducing the lower audio frequencies at their full volume. What was needed was extra smoothing.

The original HT circuit is shown in Fig. 1 (a). The arrangement used is perfectly conventional, a half-wave rectifier feeding into a 16 μ F reservoir condenser and being finally smoothed by a 1.2k Ω resistor and an

1.2k Ω resistor but there wasn't sufficient room on the chassis for the component he had in mind. He finally used an additional resistor and condenser, as shown in Fig. 1 (b), and this cleared up the hum completely. The extra condenser, incidentally, was a miniaturised component; a condenser of this type being quite permissible as it had to pass very little ripple current.

My acquaintance was still not quite satisfied with the reproduction, however, and he next

attacked the double-diode-triode stage. This, originally, used the arrangement shown in Fig. 2 (a), in which the triode grid is biased by reason of the negative voltage developed across the relatively high value of grid leak. He altered this to the circuit of Fig. 2 (b), in which conventional cathode bias is used. He was careful, as may be seen from this diagram, to return the diode load to the cathode as well, instead of leaving it connected to chassis. As the AVC line now had a standing positive bias equal to the cathode bias at the detector it was necessary to increase the cathode resistors of the frequency-changer and IF amplifier to allow for this. After having completed all these alterations he tried the set once more; and he claims that the altered circuit gave noticeably improved reproduction.

Speaker Transformers

Nevertheless, he felt that he could improve the quality still further, and so he next directed his attentions to the speaker transformer. This component was rather small in physical size. My friend suddenly noticed also that the laminations were not interleaved, but were butt-jointed. That is to say, all the "E's" had been put in together on one side of the bobbin and all the "I's" on the other. (The same would apply, of course, if "U" and "T" shaped laminations had been used).


Breathing curses on the machinations of "tight-fisted manufacturers who wouldn't spend an extra penny on their products if they could get away with it," (his own words!), he then proceeded to remove the transformer from the chassis, strip out the laminations, and refit them carefully interleaved. He connected the transformer to the set and switched on, expecting the reproduction to be as good now as it ever could be. His disappointment was intense when he found that it was worse than it had been in the first place with the miniature loud-speaker! Thinking that he had possibly damaged the transformer, he dropped in to see me in order to borrow a spare component to check the circuit.

This series of events is rather like last month's "glowing fuse" fault, because I am certain that the more experienced reader will know immediately what was wrong. The trouble, of course, was that the output transformer was intended to be butt-jointed, and should never have been altered.

The reason for this is that speaker transformers intended for single-ended output stages have to carry the continual standing anode current of the output valve. Thus, if the laminations were interleaved, they would be relatively heavily magnetised due to the completed magnetic circuit. In the case of

miniature output transformers the iron could, indeed, be well on the way to complete saturation. To prevent this trouble single-ended speaker transformers are always butt-jointed; the slight gap between the laminations preventing the completion of the magnetic circuit. In better-class transformers this gapping is maintained accurately within close tolerances during manufacture.

On the other hand, push-pull transformers are always interleaved. This is due to the fact, of course, that the opposing standing anode currents in the primary cancel out each other's magnetic field, and there is then no risk of core saturation. It is possible, therefore, for a push-pull speaker transformer to work more efficiently than a single-ended transformer even when both types employ laminations of the same size.

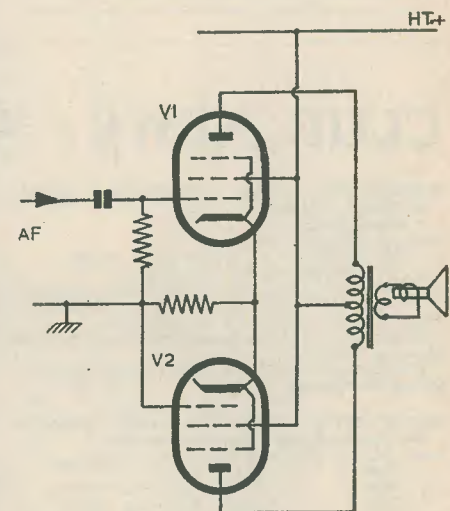

E62

Fig. 3. A "Mystery Circuit," dating from the earlier days of radio. It was claimed that this circuit gave push-pull performance merely by adding V2, as shown.

Whilst on this subject, Fig. 3 shows a "Mystery Circuit" which used to cause a certain amount of heated discussion in the earlier days of radio. With this circuit one converted an ordinary single-ended output valve (V1) to "push-pull" working simply by omitting its cathode by-pass condenser and adding V2, with a push-pull output transformer, as shown. The results, so it was

claimed, were those of a push-pull output stage.

This is quite untrue, of course, because V2, although driven in anti-phase to V1 via the common cathode resistor, receives only a small proportion of the drive applied to V1. The only "advantage" of the circuit, therefore, is that the two standing anode currents passing through the transformer primary cancel out each other's magnetic field, and

slightly improved reproduction with small output transformers is quite feasible. But the circuit is not push-pull.

To revert once more to my friend and his midget receiver, he solved the problem finally by obtaining a larger single-ended (and butt-jointed!) output transformer which could just be squeezed onto his chassis; and he is now quite satisfied with the performance he obtains.

SUGGESTED CIRCUITS

continued from page 73]

Particular attention should be paid to the method of connecting the leads from the pick-up to the amplifier. The two central leads are connected to the volume control, R1, and are consequently at amplifier chassis potential. The *screening*, however, is connected to the motor-board chassis and is isolated, therefore, from the mains.

Switching

It will be noted, finally, that the mains input to the gram motor is taken direct from the mains supply, and not through the amplifier on-off switch, S1. This method of connection is advisable, since the loading on the contacts of S1 is thereby reduced. The gram motor can, of course, be switched on or off by the switch contacts fitted on the motor-board itself.

CLUB NEWS

WARRINGTON AND DISTRICT RADIO SOCIETY, G3CKR

Future Events:
 Aug. 3 Mystery evening.
 " 15 Shack Visit to G2FCV—G. S. Leigh.
 " 17 Business and any questions.
 " 29 Field Day. Site: "Davyhulme Cottage," Dark Lane, Higher Whitley, Cheshire.
 Sept. 7 Radio Drive for Model Planes.
 Meetings are held in the King's Head Hotel, Winwick Street, at 7.30 p.m.
 Hon. Secretary: G. H. Flood, 32 Capesthorpe Road, Orford, Warrington.

THE CLIFTON AMATEUR RADIO SOCIETY

The proposed programme for September is:
 Sept. 3rd and 17th Constructional evenings.
 " 5th 3rd D.F. Contest.
 " 10th 8th Annual General Meeting.
 " 24th "Radio Receiving Valves and their Manufacture," Mr. G. P. Thwaites (Standard Telephones & Cables Ltd.).
 Meetings are held every Friday at 7.30 p.m. at the clubrooms 225, New Cross Road, London, S.E.14.
 Secretary: C. H. Bullivant, G3DIC, 25 St. Fillans Road, London, S.E.6.

NORWOOD AND DISTRICT GROUP—RSGB

The next meeting of the above group will be held as usual on the third Saturday in September (i.e. September 18th) at Windmere House, Westow Street, Crystal Palace. The meeting will commence at 7.30 p.m. and all local members and interested persons are invited to attend.
 Further particulars may be obtained from W. G. Mott, B.R.S. 18308, of 199 Tilson House, Tilson Gardens, S.W.2.

SOUTH MANCHESTER RADIO CLUB, G3FVA

Our future programme of lectures will be as follows:
 Sept. 10 Design of Mains Transformers and Chokes, N. Ashton, G3DQU.

Details for insertion in this section should reach us not later than the 8th of the month before insertion.

Sept. 24 Power Pack Design, M. Barnsley G3HZM.

Oct. 8 ANNUAL GENERAL MEETING.
 Our scheme of simple lectures for beginners has been a great success and new members are continually coming along to join us. Anyone who desires to come along and see what we have to offer in the way of membership of our club can do so without any obligation.

Hon. Secretary:
 M. Barnsley G3HZM
 17 Cross Street,
 Bradford,
 Manchester 11.

SLADE RADIO SOCIETY

Headquarters: The Church House, High Street, Erdington, Birmingham 23.
 FUTURE PROGRAMME—THIRD QUARTER, 1954.
 1954
 Sept. 3 "The Balancing of Rotors," by Mr. A. B. Cape, M.B.E.
 " 17 "The Possibilities of Inter-Planetary Travel," by Mr. W. E. Merrill (Member).

D. F. Events

Sept. 12 R.S.G.B. National D.F. Contest Final.
 " 26 Double Midnight D.F. Test.

Aug. 25—
 Sept. 4 NATIONAL RADIO SHOW.
 Oct. 23 ANNUAL DINNER.

Visitors to the Society's meetings, which commence at 7.45 p.m. prompt, are cordially welcome.
 Full particulars of the Society and its activities may be obtained from the Honorary Secretary: Mr. C. N. Smart, 110 Woolmore Road, Erdington, Birmingham 23.

The Society's clubroom at the Church House is now available, and is open every day of the week for the use of members.


Transmitting and receiving equipment is being installed, constructional facilities are available, and Morse and theory classes are being arranged.

REPAIR and MAINTENANCE of Line Output Transformers

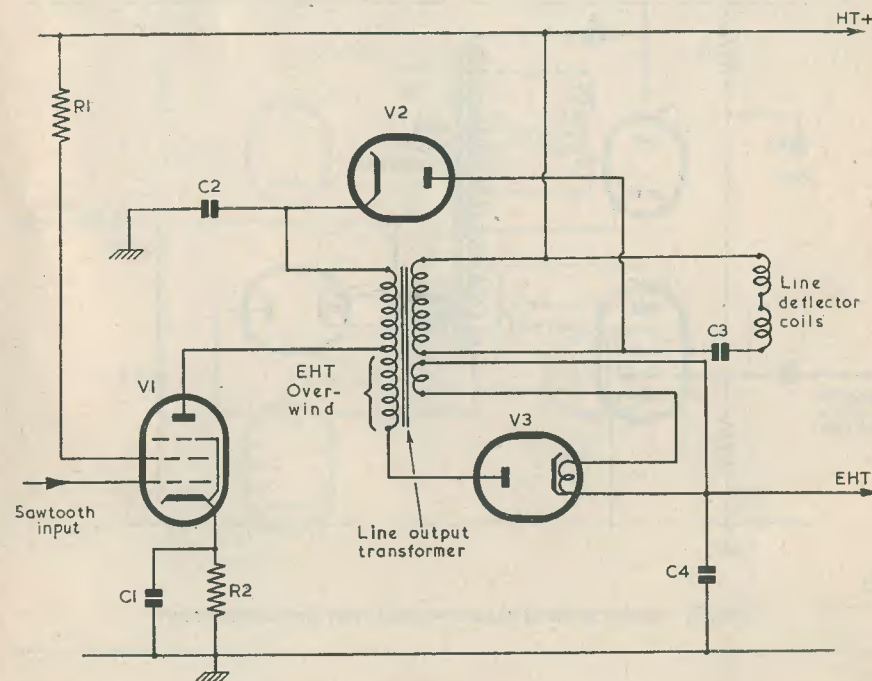Part 1. By S. WELBURN

AS MANY PROFESSIONAL RADIO ENGINEERS will agree, one of the most troublesome and difficult-to-service components in the modern television receiver is the line

vision set is rather fortunate in this respect because, if he chooses a branded transformer of reliable manufacture, he can avoid many of the line output snags which are relatively



E54

Fig. 1. A typical line output stage using a transformer with a separate secondary winding

output transformer. This is due mainly to the fact that this component has to perform several functions simultaneously whilst handling comparatively high power, and because it needs considerable care in its manufacture. The amateur who constructs his own tele-


vision set is rather fortunate in this respect because, if he chooses a branded transformer of reliable manufacture, he can avoid many of the line output snags which are relatively

Basic Theory

Modern line output transformers and their associated circuits can nowadays be said to

flyback, with the result that the bottom terminal (see Fig. 3) of the EHT over-wind swings violently positive and provides an EHT charging pulse.

It is usually conceded that the main purpose of the line transformer in the direct-drive arrangement is merely that of providing

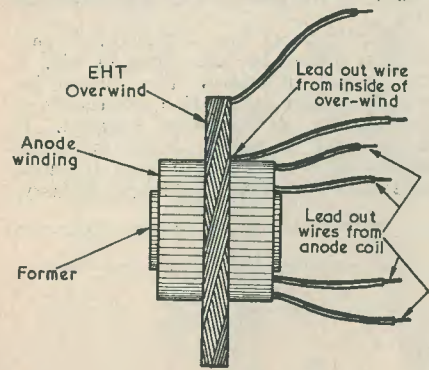

ES7

Fig. 4. Side view, showing the construction of the windings of a conventional line output transformer

the EHT voltage, together with a heating voltage for the EHT rectifier. Since the power handled by the transformer is comparatively light it need only be small in physical size, and it can consequently be manufactured at low cost. Whereas a conventional line output transformer usually requires a closed magnetic circuit of core material, the windings of a direct-drive transformer need be mounted only on a small rod or cylinder.

The great disadvantage with direct-drive circuits is given by the fact that very high flyback voltages now appear across the deflector coils, instead of across the windings of the line output transformer. In cases of breakdown, they are consequently more difficult to deal with.

Width and Linearity

No width and linearity controls have been shown in the circuits of Figs. 1, 2 and 3.

INDEXES FOR VOLUME SEVEN

Readers desiring a copy should forward a stamped self-addressed envelope (preferably 9in. x 6in.) marked RC INDEX in top left-hand corner to

The Radio Constructor • 57 Maida Vale • London W9

They have been omitted because the types of control most commonly used, and their position in the line output circuit, vary considerably for different manufacturers and designers. It is fairly safe to say, however, that when inductive width controls are used they are usually connected either across part of the anode winding of the output transformer or, suitably damped, in series with the deflector coils. In the first case they then offer a variable load across the transformer winding; whilst in the second case, they give a variable impedance between the scanning coils and the transformer. Linearity controls may appear almost anywhere in the line output circuit. They are sometimes omitted in commercial designs.

Construction

The construction of most line output transformers is nowadays fairly standard. So far as the windings are concerned, they consist usually of the anode winding, on top of which is wound the EHT over-wind. The general arrangement is shown in Fig. 4. (This diagram does not show the "corona ring" fitted around the outside of the over-wind).


A very important feature of line output transformer design is given by the low number of turns-per-volt which occur during the flyback period. Indeed, it is usually the other way round - volts-per-turn! Figures as high as ten volts-per-turn are quite feasible.

Because of the high voltages appearing between consecutive turns, great care has to be taken in design and during manufacture. The anode coil is almost always interleaved with paper; and the EHT over-wind, which uses thinner wire, is given its characteristic narrow dimension to ensure that too high a potential cannot exist between any two adjacent turns in the winding.

Line output transformer cores consist mainly of one of the specially-developed magnetic materials; notably Ferroxcube (Mullard) and Caslam (Plessey). These materials have now ousted laminations, which are rarely encountered in modern televisions.

(To be continued)

THE EASI-BUILD RECEIVER

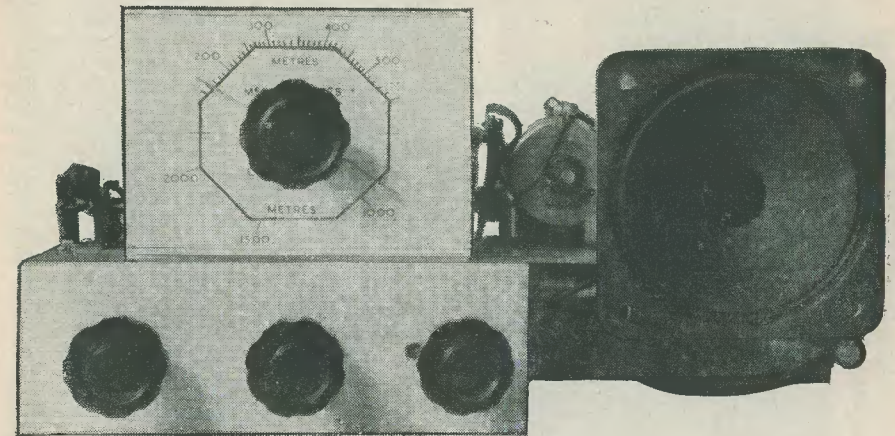

Part 1. By M. HARVEY

Introducing a simple local station receiver designed especially for the beginner and for those with limited workshop facilities

ALTHOUGH THE "RADIO CONSTRUCTOR" has been a pioneer in the field of television for the amateur, and has published many constructional articles on advanced equipment and test gear, a considerable number of letters arriving at the Editorial offices still ask that such material be balanced by articles intended for the beginner. These letters convey most forcefully the fact that there is a strong demand for a simple receiver which may be constructed by the tyro who has little experience and few facilities.

It is for this reason that we now introduce the Easi-Build, a receiver in which everything, including the chassis-work and the wiring itself, has been designed to make construction as simple as it possibly can be without detracting from the final performance obtained. The set has no trimmers and, apart from the adjustable iron-dust cores, which are used only to finally make the dial calibration correspond to the frequencies received, the set is ready for use as soon as it

has been completed. Indeed, the iron cores themselves need not be adjusted at all if this is not desired; as their setting at the factory is sufficiently accurate to enable dial readings to be reasonably correct for normal purposes. No loss of sensitivity is incurred if the cores are left un-adjusted.

The Easi-Build is a mains-operated medium and long wave receiver capable of working from any aerial longer than four feet. It will adequately load any normal loudspeaker, and its quality of reproduction compares very well with any normal domestic broadcast set. It is, however, intended strictly as a local-station receiver. Whilst its sensitivity is sufficient to bring in almost as many Continental and remote Home stations as the average superhet, the simple tuning arrangements employed are obviously not in the class needed to separate weak stations in the present crowded broadcast bands. In many districts it will, admittedly, be capable of selecting a large number of stations with excellent selectivity, but such a

Resistors	R1 1M Ω , $\frac{1}{2}$ W.	Rectifier	MR1 Metal rectifier; 250V, 60mA; DRM1B Brimar.
R2 50k Ω , $\frac{1}{2}$ W.	R3 22k Ω , $\frac{1}{2}$ W.	Valves	V1 ECC40 Mullard.
R4 220k Ω , $\frac{1}{2}$ W.	R5 100k Ω , $\frac{1}{2}$ W.	V2 EL42 Mullard.	
R6 2.2k Ω , $\frac{1}{2}$ W.	R7 250k Ω , volume control, with DP switch, Dubilier.	Valveholders	BM8/E McMurdo.
R8 470 Ω , $\frac{1}{2}$ W.	R9 2.7k Ω , 5W.	XM8/EC1 McMurdo.	8/85 (Screening Can) McMurdo.
R10 120 Ω , 1W.		Transformers	
Condensers	C1 0.0025 μ F, 600VDC, type 648, TCC.	Output transformer, type OPI320, Allen Components, Ltd.	
C2 800pF, 350 VDC, type 601 SMP, TCC.	C3 0.0025 μ F, 600 VDC, type 648, TCC.	Heater transformer, type MT1209, Allen Components, Ltd.	
C4 300pF Variable, reaction, Jackson Bros.	C5 500pF Variable, tuning, Jackson Bros.	Loudspeaker	3 $\frac{1}{2}$ " 3 Ω coil, Whiteley Electrical type S.3.57.
C6 50pF, 350 VDC, type 101 SMP, TCC.	C7 4 μ F, 350 VDC, type CE88LE, TCC.	Epicyclic Drive	$\frac{1}{4}$ " spindle, Jackson Bros.
C8 400pF, 350 VDC, type 501 SMP, TCC.	C9 0.02 μ F, 350 VDC, type 346, TCC.	Switches	S1, S2, S3, S4 Miniature 4-pole, 2-way, H. L. Smith & Co.
C10 25 μ F, 25 VDC, type CE77C, TCC.	C11 0.02 μ F, 350 VDC, type 346, TCC.	Tag Strips	5-way, centre earthed, 5 required.
C12 0.005 μ F, 400 VDC, type 545, TCC.	C13 25 μ F, 25 VDC, type CE77C, TCC.	Grommets	$\frac{3}{8}$ " inside diameter, 5 required.
C14 8 μ F, 350 VDC, type CE99LE, TCC.	C15 16 μ F, 350 VDC, type CE91LE, TCC.		
C16 0.005 μ F, 600 VDC, type 648, TCC.			
Inductors	L1, L2, L3 Medium Wave Coil, type DM/2 Teletron.		
L4, L5, L6 Long Wave Coil, type DM/1 Teletron.	L7 Reaction Choke, type SP/1 Teletron.		

performance cannot be guaranteed for every locality. In one or two instances where the receiver is used in the close proximity of a powerful station it may be necessary to employ a rejector wave-trap in the aerial circuit; but this course will probably only be necessary in isolated cases.

The Circuit

The circuit of the receiver is shown in Fig. 1, and it will be seen at once that this is very simple and straightforward.

Starting at the power supply, it will be noted that the mains input is applied directly to the primary of the heater transformer, and to chassis and a metal rectifier for the HT supply. The rectified HT is smoothed by the two condensers, C14 and C15, and the resistor, R9. The smoothed HT supply is then directly available for the screen-grid

and anode supplies of the output valve, V2. A tone-correction condenser, C12, is connected across the primary of the output transformer, and one side of the speaker voice coil is connected to the speaker chassis to prevent static discharge.

The AF input to the grid of V2 is taken via the volume control, R7. The volume control is fitted at this point rather than in an earlier part of the circuit in order to simplify wiring and to obviate the necessity of using screened cable. It has the further advantage that it is completely isolated from the reaction circuits and that there is consequently no possibility of interaction between the two controls. During tests on the prototype, very heavy signals were fed to the receiver, but there was no evidence of overloading of V1 (b), despite the fact that this valve receives the full AF output of V1 (a).



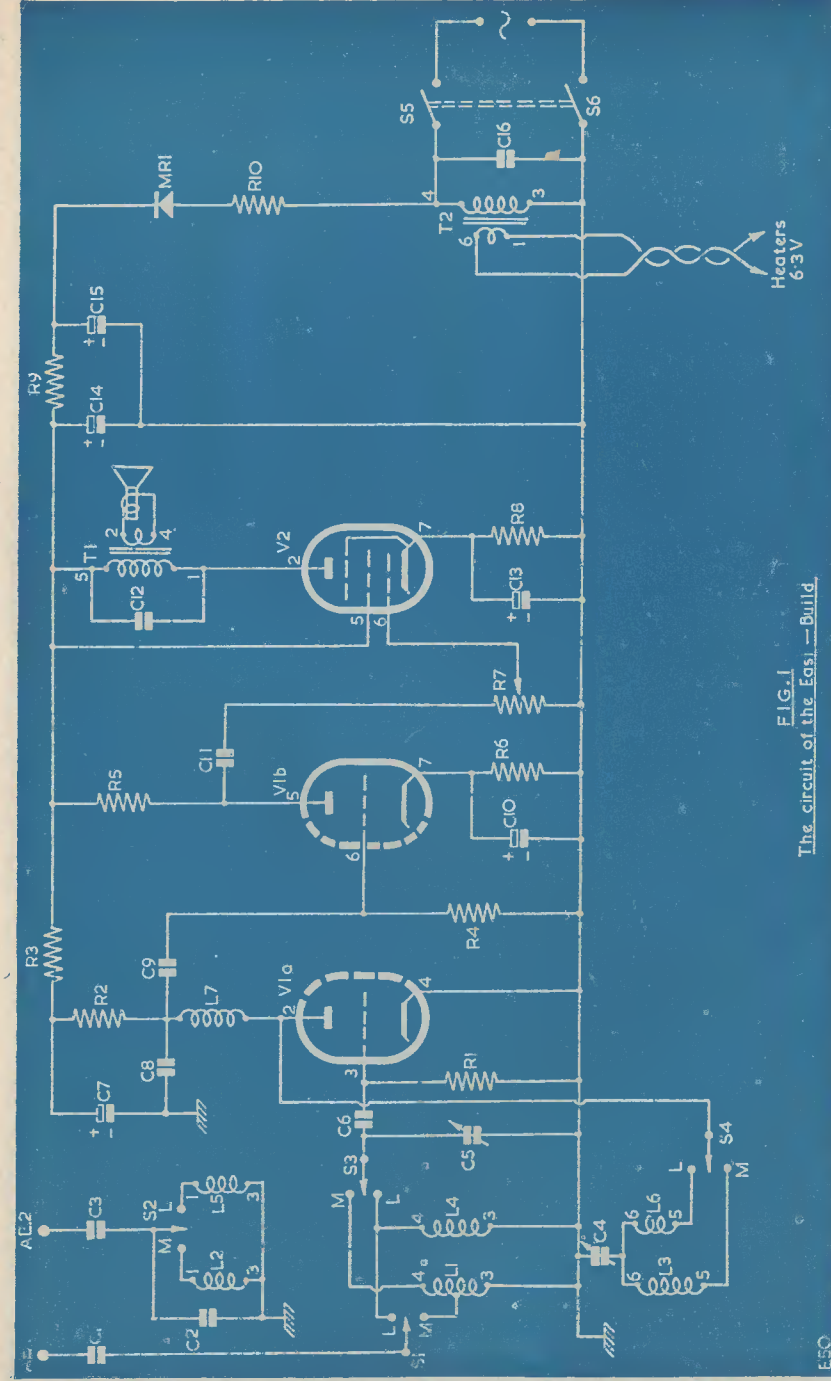


FIG. 1
The circuit of the Eqs. — Build.

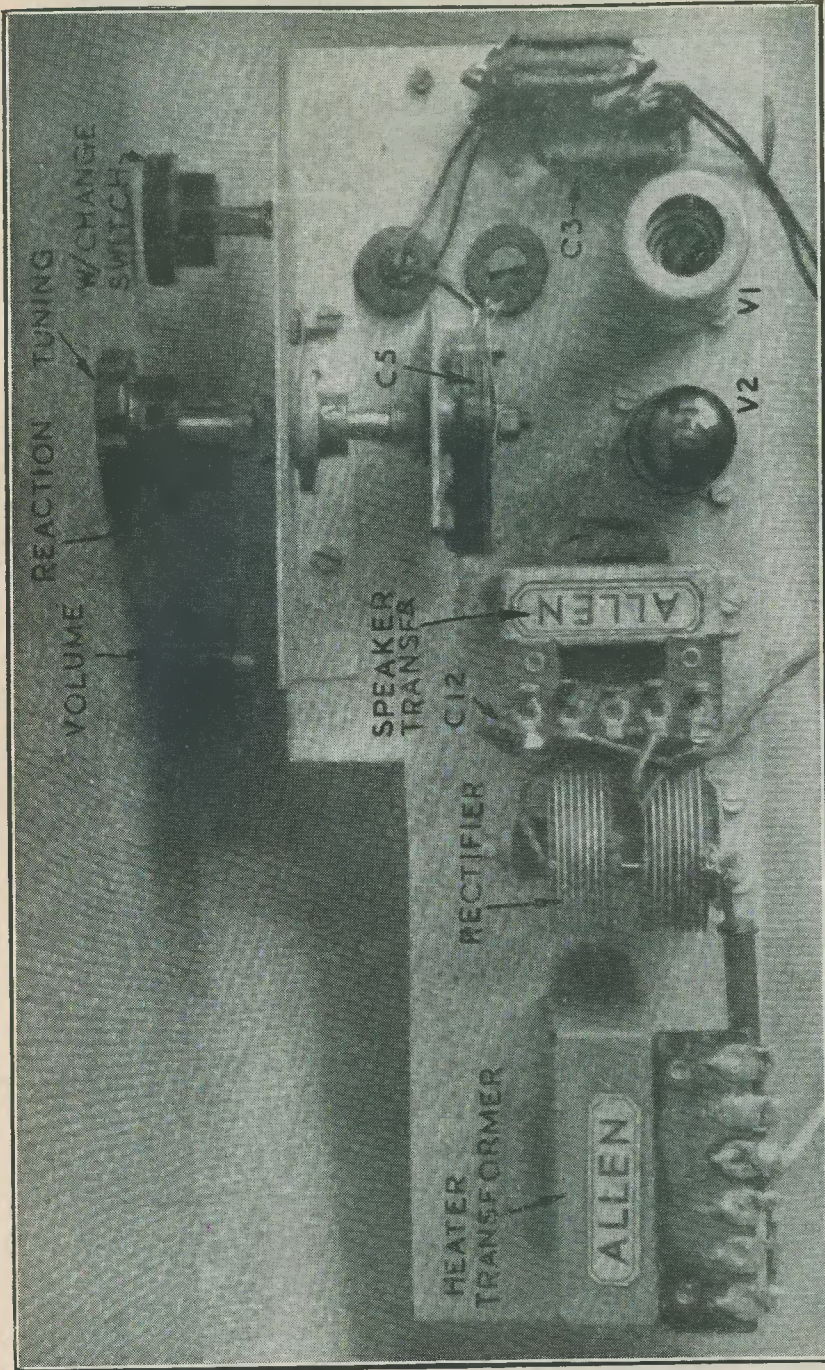Note. In the above circuit one side of the heater wiring should be connected to chassis. The tap on L1 is brought out to tag No. 2 on the coil former.




The Easi-Build—above chassis layout

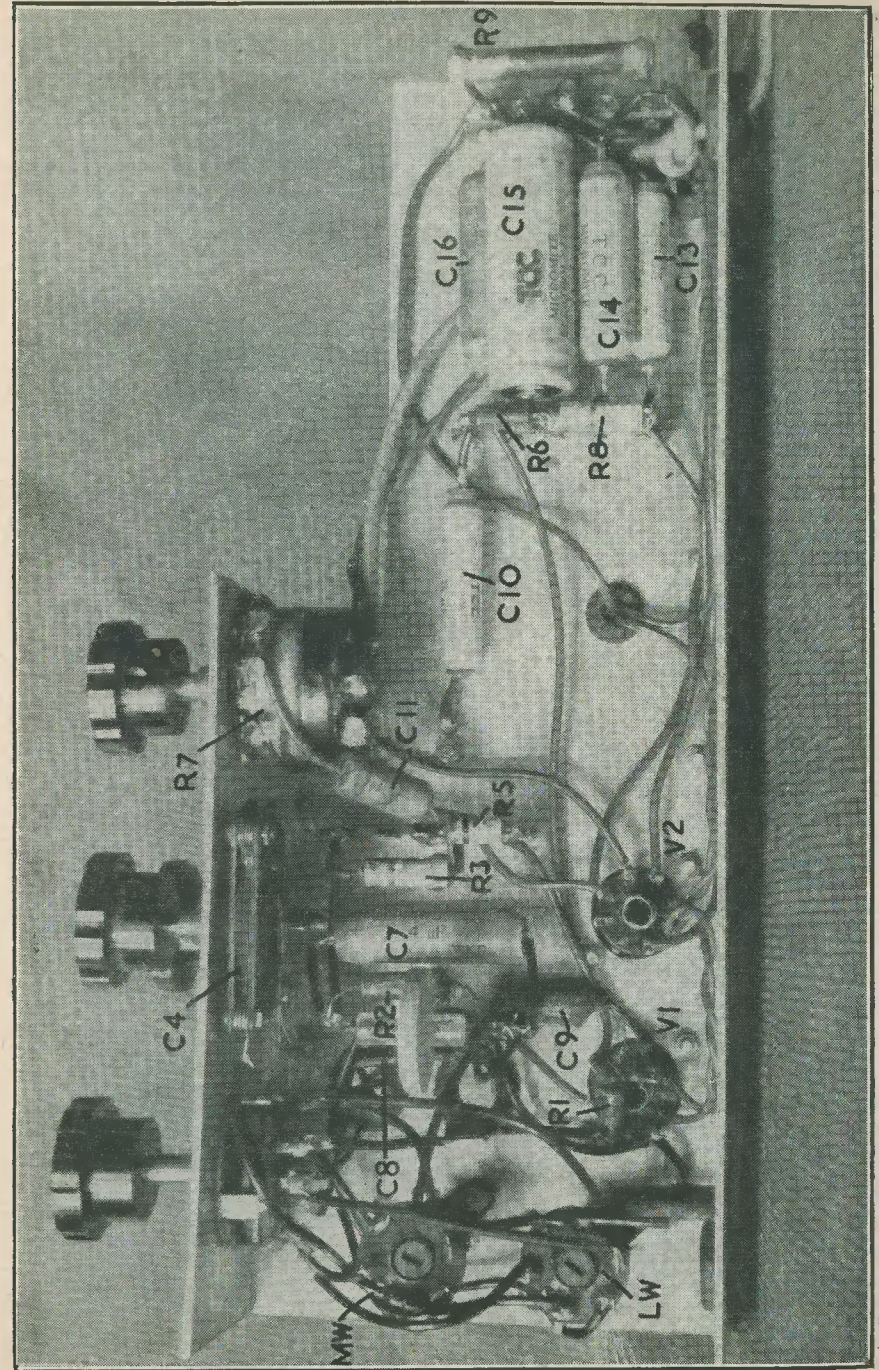

The Easi-Build—layout underneath

The volume control is fed from the anode of V1 (b), this being half of the double-triode, V1. V1 (b) acts solely as an AF amplifier, AF input to its grid being applied via C9. V1 (a) is a leaky-grid detector, and has the additional refinement of being fitted with a reaction circuit. Whilst reaction is not usually needed with the receiver when listen-

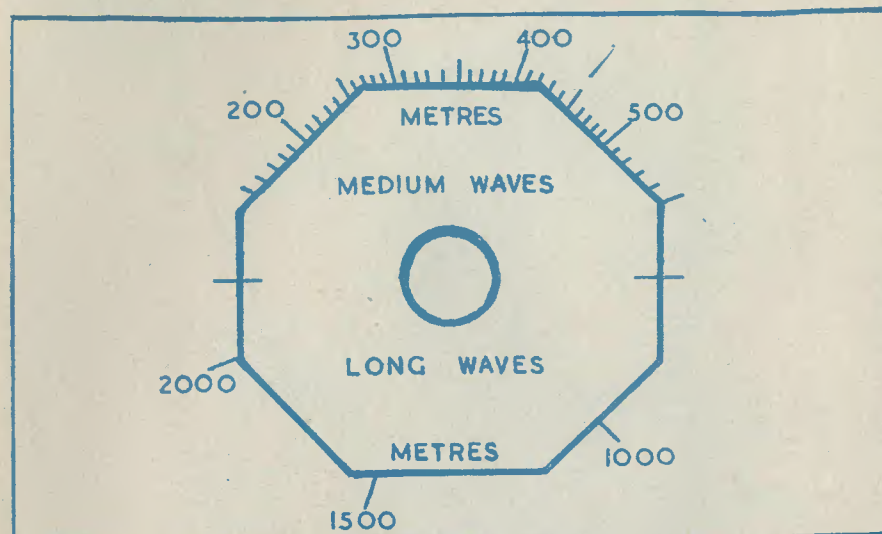nection, an aera of four or five feet will give full loudspeaker volume in most localities from the local medium-wave Home station and from the Light programme on 1,500 metres. This facility is particularly attractive since it allows the receiver to be treated as a portable. The looser coupling (Ac2), is intended for a larger and more



This dial should be cut out and pasted on thin card which may then be fastened on to the Metal Backing Plate

ing to local stations, its availability has the considerable advantage of improving selectivity when it is desired to pull out a weak signal from an interfering background. A simple RF decoupling circuit consisting of the RF choke, L7, and the condenser, C8, assists in providing smooth reaction and in preventing RF from being passed to later stages in the set. A simple AF decoupling circuit (C7, R3), is also provided.

A conventional leaky-grid arrangement is provided at the grid of V1 (a), the values of C6 and R1 being specially chosen to ensure smooth reaction.

Two aerial input circuits are provided, one being a tight coupling which connects to the grid winding itself of each coil, the other being a loose coupling which is taken to a separate aerial coupling winding. The tight coupling connects to the point marked "Ae 1" in the diagram and is intended for use with very short aerials. Using this con-

ventional type of aerial. In many cases, excellent results will be given with this terminal using an aerial of the "bed-springs" variety. No earth connection is needed, and none should be used unless conditions of heavy interference necessitate it. This point is dealt with later on in these articles.

It will be noted that a relatively large value of capacity, C2, is connected across the aerial coupling coils. This condenser is fitted to ensure that the resonant point of the coupling coils lies well outside the band to which the receiver is switched. The coupling achieved is then almost entirely aperiodic. The fitting of this condenser has the further advantage of lowering the effective input aerial impedance of the receiver, with the result that highly differing aerials result in hardly any variation in reaction or tuning adjustments.

Live Chassis

It will be appreciated from Fig. 1 that

the chassis of the Easi-Build is "live" to one side of the mains. Although live chassis are not at all new to the home-constructor, emphasis is placed once more upon the fact that the appropriate precautions should always be observed when the chassis is handled. The only safe method of ensuring that the chassis is disconnected from the mains when it is desired to work upon it is to remove the mains plug from its socket. Professional engineers observe this precaution, and it is a very wise measure.

Components List

This month's article is intended to serve as an introduction to the Easi-Build. It also includes a list of the components needed for building the receiver. All the more important components are specified by the manufacturer's name and reference number; these being the types which will fit into the chassis layout to be described in the succeeding article. The resistors have not been specified under manufacturer's names as, so long as the wattage ratings recommended are followed, standard components will

fit comfortably into the chassis. If they are difficult to obtain, however, the two eighth-watt resistors, R1 and R4, may be replaced by quarter-watt components; although this will make their mounting slightly more difficult. The condenser C2 has rather an "awkward" value, and it may be replaced, if desired, by two 400pF condensers in parallel.

The loudspeaker used with the receiver is not mounted on the chassis, although a cut-away is provided for it. The type finally chosen depends mainly upon the cabinet employed; an easily built cabinet will be described later. The impedance of the voice coil should, however, be 3 ohms. The speaker used with the prototype and illustrated in the photographs is the W.B. Stentorian 3½" model, reference S3.57, and this component may be relied upon to give good results with this receiver.

Next Month's Article

The next article in this series will describe the chassis-work and wiring procedure needed for building this simple receiver.

DATA BOOK SERIES, NO. 9

Radio Control

FOR MODEL SHIPS, BOATS AND AIRCRAFT

BY F. C. JUDD, G2BCX



To operate a model ship or aircraft is a most interesting hobby. But how much more fascinating it would be if one could emulate the skipper or pilot and remain in control after the model has been set off on its course. This, thanks to radio control, can now be done, and enthusiasm for it is steadily mounting. With the publication of this book, we really believe that we have produced what will become a recognised handbook in this field.

Standard Edition, art board cover . . . 8s. 6d.

Cloth bound, with gold lettering . . . 11s. 6d.

Postage 3d.

A really comprehensive work on this fascinating subject

144 pages

135 diagrams and illustrations


TRADE ENQUIRIES INVITED

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telephone CUNningham 6513

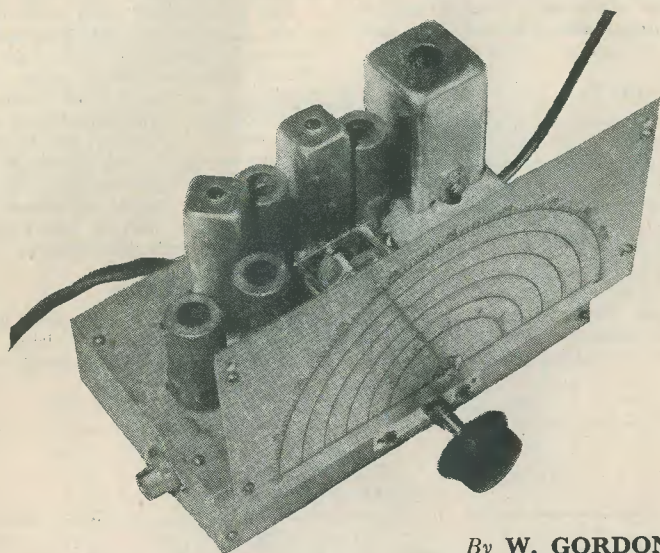FREQUENCY MODULATION TUNER UNIT MODIFICATIONS



By **W. GORDON**

MANY READERS HAVE BUILT THE FM TUNER Unit described in the July issue of this magazine, with good results. Since then, various improvements have been effected which will be discussed in this article.

The Frequency Changer circuit has been altered because it was found that, in the old circuit, some valves were prone to spurious harmonic oscillation. The new circuit, given here, is easier to align and is very stable. It is, in effect, a tuned-anode tuned-grid oscillator, and therefore no critical coupling is required between L2 and L3, and these windings should be spaced $\frac{1}{4}$ " apart. L3 has now only 4 turns instead of the original 5, and this coil is tuned by parting the turns to give a maximum limiter grid voltage reading. L2 is the main frequency controlling circuit and, as this has no grid capacity connected across it, the oscillator is inherently very stable.


When measuring the limiter grid voltage, a $100k\Omega$ resistor should be soldered to the junction of C15 and R10. If a long lead is connected to this point, the tuning of L5 secondary is altered. The $100k\Omega$ isolation resistor prevents this. It has also been found that a $47k\Omega$ $\frac{1}{4}W$ resistor across the anode

circuit of L5 improves the balance of the response curve in most cases.

If the audio output is low, check carefully that C24 is connected the right way round. The positive of the condenser should be connected to the red end of the crystal. Low output may also be caused by poor crystals. Some cheap crystals of a well-known make have been found quite effective. Others provide a heavy damping on the ratio detector coil, and spoil the linearity. G.E.C. crystals type GEX34 are very suitable, or alternatively make sure that the crystal has been tested for this application before purchasing.

A diode in the ratio detector is not recommended because IF harmonic feedback occurs along the heater line. This becomes more prevalent when a floating heater supply is used. For the same reason, when using a floating heater supply, chokes are required between V3 and V4. The specification of the chokes is as follows: Using $\frac{1}{8}$ " diam. former, wind on as many turns as possible of 26 swg enamelled to make a coil length of $1\frac{3}{4}$ ". This harmonic trouble can easily be recognised by the fact that dead spots occur at harmonics of the IF—85.6, 96.3 and 107 Mc/s.

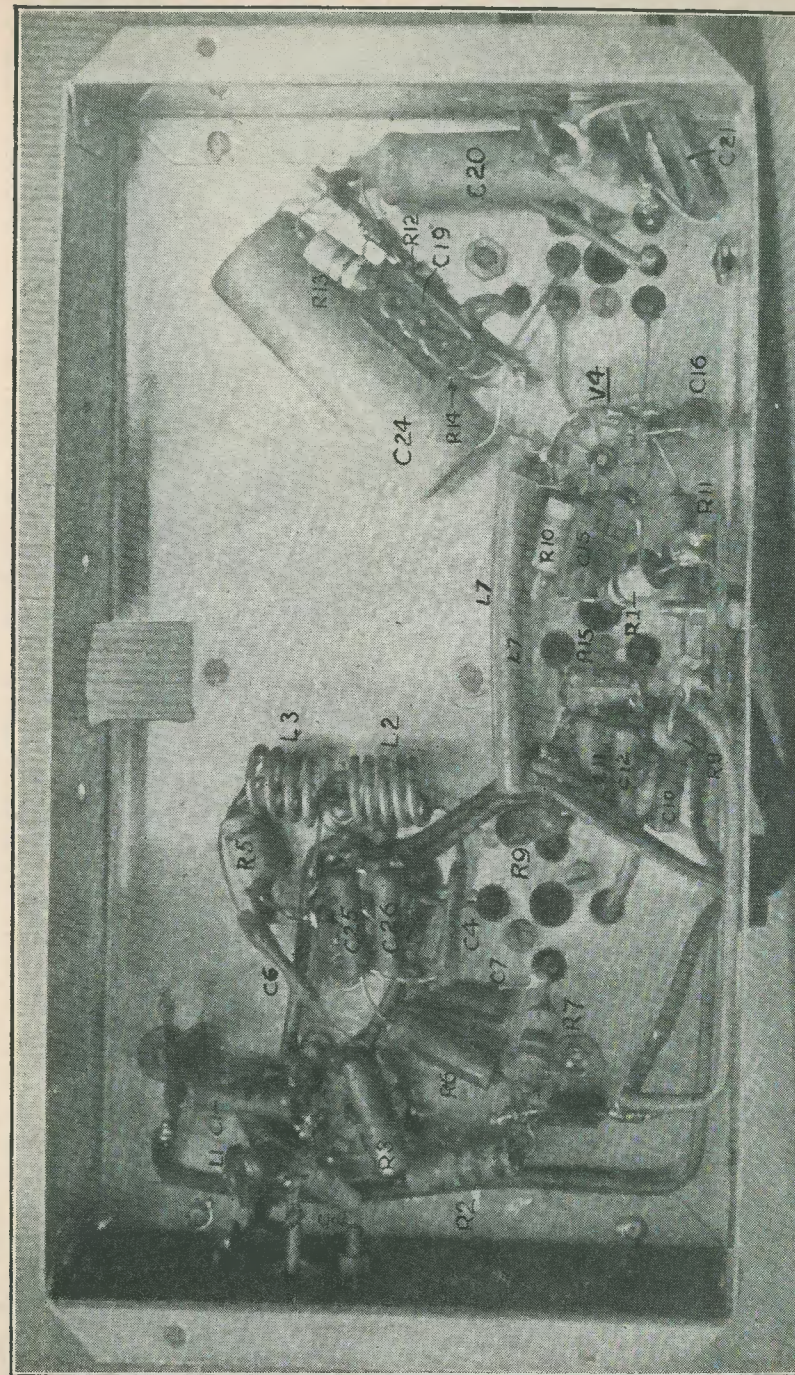Without the aerial connected, there should



New layout when using floating heater supply—compare with photograph in July issue, page 717

be a quiet rushing noise which does not change as the tuning is altered. Whistles may be heard; these will be caused by the old cathode tap oscillator, and the employment of the new circuit will overcome this.

From the photograph it may be seen that the layout has been altered to leave room for the heater chokes L7 between V3 and V4.

If one side of the heater is earthed, as in the original circuit, then no heater chokes are necessary and only one condenser, C25, is required, connected from the heater of V2 to chassis.

There was also one circuit error in the ratio detector. The bypass condensers C22 and C23 are no longer connected to chassis. As previously drawn, a very slight loss of top response may have experienced.

The aerial coil slug is of the same type as used in the other coils, but may need cutting shorter. The diameter of the slug is $\frac{3}{16}$ ", and it has a 2-BA thread moulded on it. The length should be cut to $\frac{1}{4}$ ", and the wire wound in the thread.

RADIO AMATEURS EXAMINATION COURSE

Dear Sir,

I am pleased to inform you that once again we have made arrangements with the Islington L.C.C. Mens' Evening Institutes for an official course of instruction for the RADIO AMATEURS EXAMINATION to be held at the Grafton School, Eburne Road, Holloway, N.7 (one minute from the "Nags Head") during the coming winter months in conjunction with the society.

Classes, with Morse instruction to the required speed, will be held on Monday evenings at 7.0 p.m. - 10 p.m., commencing Monday, September 27th (enrolment week Sept. 20/24th) - instructor: Mr. A. Perry (G3DKX) - fee 10/-.

Application, in the first instance, should be made to the GRAFTON RADIO SOCIETY Hon. Secretary - Mr. A. W. H. Wennell (G2CJN), 145 Uxendon Hill, Wembley Park, Middlesex.

COMPONENT LIST

Resistors

R1	100k Ω
R2	4.7k Ω $\frac{1}{2}$ W
R3	6.8k Ω $\frac{1}{2}$ W
R4	150 Ω
R5	470k Ω
R6	47k Ω $\frac{1}{2}$ W
R7	4.7k Ω
R8	4.7k Ω $\frac{1}{2}$ W
R9	150 Ω
R10	47k Ω
R11	47k Ω $\frac{1}{2}$ W
R12	100k Ω
R13	10k Ω
R14	10k Ω
R15	47k Ω


Resistors all $\frac{1}{2}$ W unless otherwise stated.

Condensers

C1	5,000pF ceramic
C2	1,000pF ceramic
C3	5,000pF ceramic
C4	33pF silver mica
C5	33pF silver mica
C6	47pF silver mica
C7	5,000pF ceramic
C8	15pF silver mica
C9	15pF silver mica
C10	5,000pF ceramic
C11	5,000pF ceramic
C12	5,000pF ceramic
C13	15pF silver mica
C14	15pF silver mica
C15	47pF silver mica
C16	5,000pF ceramic
C17	15pF silver mica
C18	47pF silver mica
C19	300pF mica or ceramic
C20	0.05 μ F paper
C21	500pF mica or ceramic
C22	300pF mica or ceramic
C23	300pF mica or ceramic
C24	8 μ F 150V electrolytic
C25	2,000pF ceramic
C26	2,000pF ceramic
VC1-2	Split stator 25pF+25pF, Jackson Bros. type U101.

Miscellaneous

Tag Strips	
Dial	Jackson Bros., full vision drive type 2154 fitted with scale type 4838
Valves	V1, Osram Z77 V2, Osram Z77 V3, Osram Z77 V4, Osram Z77 V5, G.E.C. GEX34 germanium diodes.
Chassis	Coils, complete with condensers. G. Blundell, 7 Sunnyside House, Child's Hill, London, N.W.2.

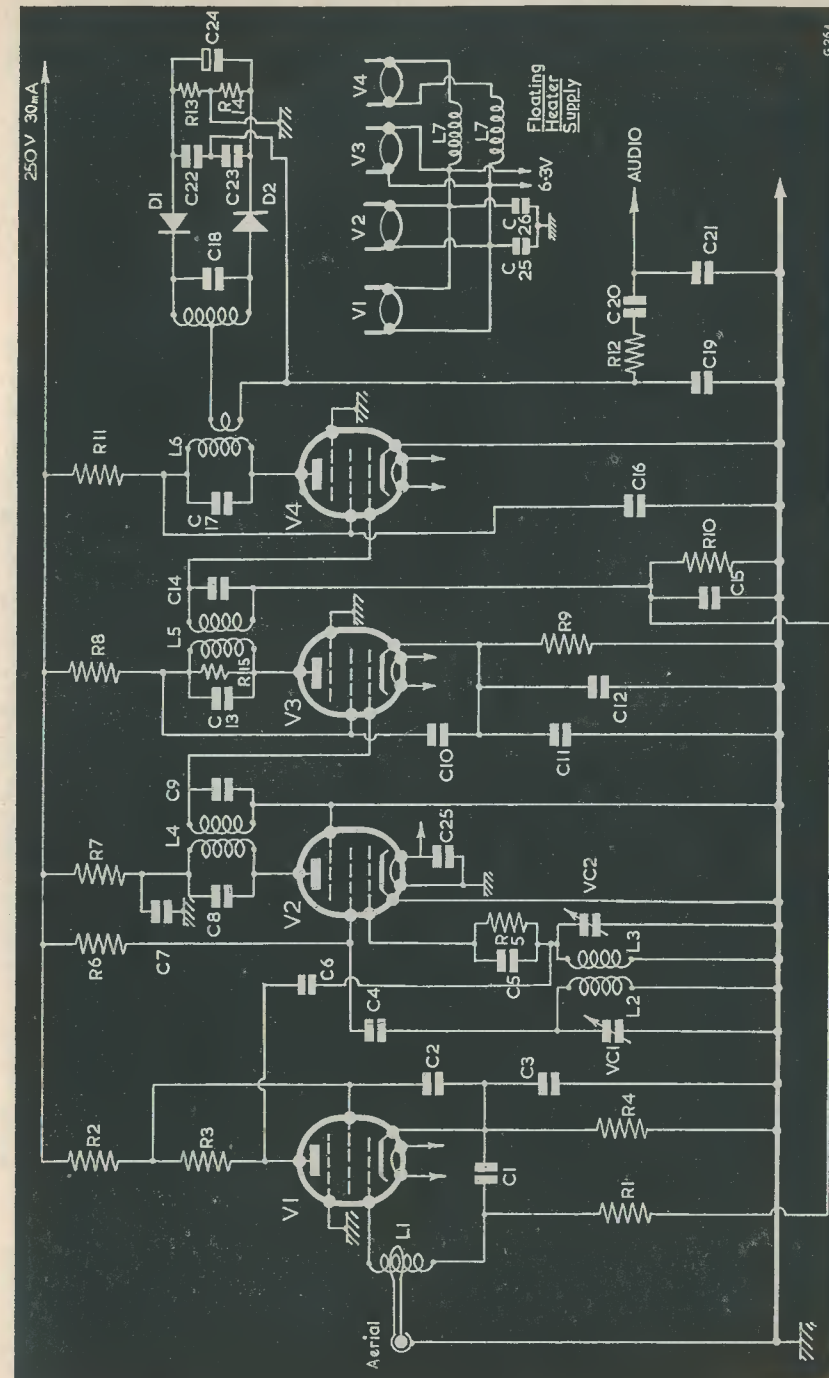

Modified circuit of the FM tuner unit

THE DESIGN, CONSTRUCTION CALIBRATION and use of SIGNAL GENERATORS

Part 1. By R. J. STEPHENSON

IN THE HOME CONSTRUCTOR'S WORKSHOP, one of the most important items of test equipment is usually noticeable by its absence.

I refer to a good signal generator. A good commercially made signal generator is an expensive item. Most enthusiasts who build one are usually disappointed with the performance, but it is hoped to show that a good signal generator can be made and calibrated in the home workshop, once the basic principles have been understood.

In the course of these articles, a circuit that the author has used satisfactorily for some time will be given, the purpose being to give the average reader some ideas on which to base his own individual design.

First, let us examine the requirements of a signal generator. These are:—

- (1) Freedom from Frequency drift of the RF oscillator.
- (2) An AF oscillator capable of modulating the RF oscillator up to about 30%.
- (3) The AF oscillator should operate on about 400 c/s and be of good waveform.
- (4) The frequency of the RF oscillator should be unaffected by the audio modulation.
- (5) The complete instrument must be carefully screened to prevent unwanted direct radiation.
- (6) The range of frequencies must cover all the usual ones (including TV), but not necessarily on fundamentals.
- (7) If mains operated, the hum must be negligible.
- (8) The output need only be of the order of a few volts, but an attenuator should be fitted.

(9) For convenience, a switch should select the type of output required, i.e., RF, Modulated RF, or AF.

Many single-valve signal generators have been described in the past, but a glance at the requirements will show that it is

rather a lot to expect one valve to do. It is my experience that such circuits usually fail in requirements 2, 3 and 4.

The most important requirement for the RF oscillator is its frequency stability (i.e., its freedom from drift). The following points must be observed:—

- (1) The internally generated heat must be kept down to a minimum.
- (2) The components forming the tuned circuit must be of a high "Q".
- (3) The Ra of the oscillator must be high.
- (4) The loading of the tuned circuit must be light.
- (5) Some oscillators are more prone to frequency drift than are others.

Let us examine these points in more detail.

(1) *Internally Generated Heat.* If the tuned circuit is subjected to changes of temperature, its resonant frequency will change. A change in temperature will cause both the coil and condenser to expand or to contract, thus altering their values. Whilst compensating condensers with a negative temperature co-efficient can be used, it is better to reduce the heat to a minimum by placing resistors and valves (e.g., rectifiers) as far away as possible from the tuned circuit. I prefer to use a separate power pack, kept well away from the signal generator proper.

(2) *The "Q" of the Tuned Circuit.* Without going too deeply into mathematics, the expression for the resonant frequency of a tuned circuit is usually given as

$$f = \frac{1}{2\pi\sqrt{LC}}$$

This formula is only approximate, since it takes no account of the resistance of the coil or the condenser leakage resistance, or the Ra of the valve (if used as an oscillator). The full equation contains an expression taking these resistances into consideration.


From this it can be shown (a favourite phrase with mathematicians!) that the higher the "Q" of the components in the tuned circuit, the better the frequency stability. It is beyond the scope of the modest workshop to wind coils to exact specifications, especially the lower (RF) frequency ones, but several manufacturers produce suitable inductors. (The Teletron Co. will supply coils to individual specifications - Ed.). The tuning condenser should be of the best type available, preferably with ceramic insulation.

(5) *The Oscillator Valve Circuit.* The type of circuit used must be given careful thought. Some of the more common types of oscillator are listed below, with a few notes on their characteristics.

Tuned Grid. This circuit is easy to build and works well, it is reliable in operation, and suitable coils are readily available - but it is difficult to load. It can be series- or parallel-fed.

Tuned Anode. Very similar to tuned grid.

Meissner Oscillator. Very stable, but

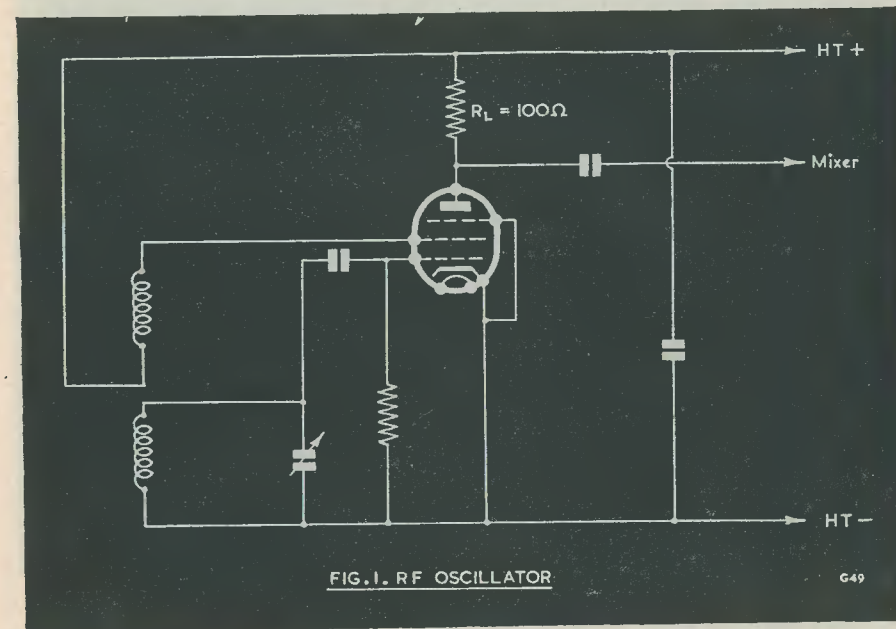

(3) *The Ra of the Valve.* The Ra of the oscillator valve also has some effect upon the frequency stability. Briefly, the higher the Ra of the oscillator valve the better the stability will be. For this reason, a pentode with an anode resistance of about 1MΩ is preferred to, say, a triode whose anode resistance is much lower.

(4) *The Loading of the Tuned Circuit.* If the output of the signal generator is taken from the oscillatory circuit, either via a separate winding on the coil former or a tapping on the grid coil, the load will effectively lower the "Q" of the tuned circuit - which is what we are trying to avoid (see section (2)). The loading must be taken from some point other than the tuned circuit.

difficult to load. Suitable coils are not readily available commercially.

Hartley Oscillator. The performance of this circuit is good, but it is not easily loaded. Commercial coils are not readily available with a suitable tapping point (see note re The Teletron Co. above - Ed), and there is the practical difficulty that neither the rotors nor the stators of the tuning condenser can be earthed. It can be series or parallel-fed, or can have a cathode tap.

Colpitts Oscillator. This is very stable in operation, but again is not easily loaded. Furthermore, the tuning condenser consists of two units in series, which reduces the tuning range unless high value condensers are used. The output is practically free

from harmonics, which is a decided disadvantage from our point of view.

Tuned Anode Tuned Grid (TPTG) Oscillator. This circuit is not suitable for continuous tuning.

circuit by the writer, he has not seen it described before. It has been used for some time now in a signal generator, with excellent results. Using coils which can be readily obtained, it is stable in operation, and the

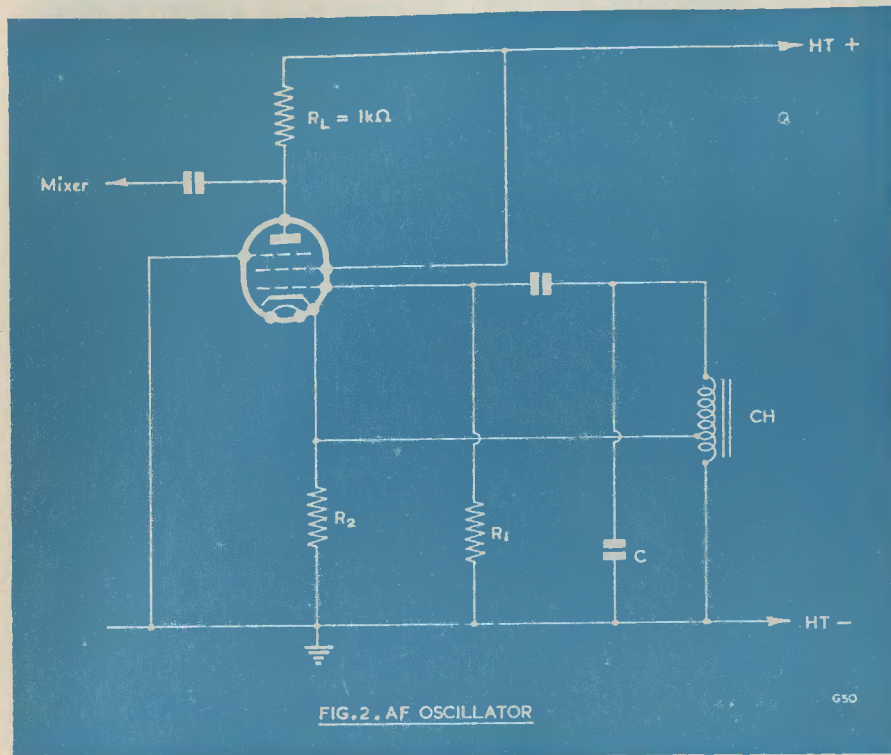


FIG. 2. AF OSCILLATOR

Common Anode Oscillator. As the TPTG. **Common Grid Oscillator.** As the TPTG. **Franklin Constant Frequency Oscillator.** As its name implies, this circuit is very stable in operation, but it is not easily loaded and the value of the coupling condensers is rather critical for any particular frequency. This last makes it difficult to achieve satisfactory operation with continuous tuning.

Electron Coupled Oscillator (ECO). This is a very stable oscillator, and if the load is taken from the anode it has little or no effect upon the oscillatory circuit. Its second and third harmonics are strong - indeed its fourth and fifth harmonics are of useable strength - and the ECO is capable of being continuously tuned.

The Screen Coupled Oscillator. Although no personal originality is claimed for this

load, if taken from the anode, has no appreciable effect upon the tuned circuit, since it is screened from this by the suppressor grid. Also, the load resistor of a pentode has very little effect upon the anode current (a pentode can be used as a constant current device - hence its high R_a).

The circuit is given in Fig. 1. It will be noticed that the anode load is unusually low, but if a larger output is required the value of the resistor may be increased. The reason for the low value of 100Ω will be explained later.

Let us now consider one or two points about the audio oscillator for the modulation of the RF voltage. First, and most important, it must approach as nearly as possible a pure sinusoidal waveform, i.e., it must be substantially free from any harmonic content. An audio oscillator of poor waveform

working on, say, 400 c/s can have harmonics as high as 200 kc/s. If this were used to modulate the RF it would produce "whiskers" extending to 200 kc/s on either side of the carrier frequency. This is most undesirable, hence the need for a pure modulating waveform. The actual frequency (fundamental) of the oscillator is usually between 100 c/s and 1 kc/s, but it is in no way critical. A value of about 400 c/s is usually employed, since this is a standard test frequency ($\omega=2,500$) and also a pleasant note to which to listen.

Also, the output must be capable of being adjusted to give the necessary modulation depth. The circuit given in Fig. 2 is most useful. The condenser C is of such a value (found by trial and error) as to cause the tapped choke (Ch) to resonate at about 400 c/s. A variable resistor of low value (say $5k\Omega$) is connected in place of R2, and reduced in value until the circuit just oscillates, when the waveform will be very nearly sinusoidal. The variable resistor is then removed, its resistance measured, and replaced by a single fixed resistor of like value (or combination of resistors to this value). Incidentally, it is interesting to observe the output on an oscilloscope as R2 is varied.

The load resistor R1 is chosen to give the required output; in the instrument to be described it was $1k\Omega$, as will be later explained.

ed. The tapped choke Ch can very well be an interval transformer connected as in Fig. 3.

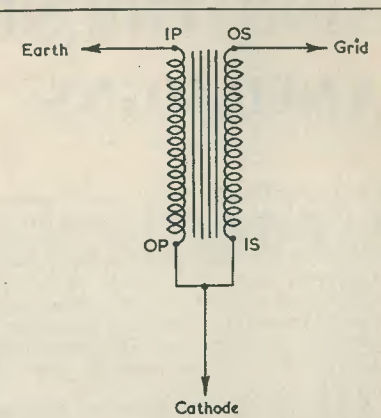


FIG. 3. AF TRANSFORMER CONNECTIONS

Many other types of audio oscillator can be used, but this one - it is an ECO - is very flexible.

(To be continued)

COURSES OF INSTRUCTION

EAST LONDON R.S.G.B. GROUP

THE FOLLOWING CLASSES ORGANISED BY THE EAST LONDON R.S.G.B. GROUP in conjunction with the Essex County Council are available for all those interested in Amateur Radio irrespective of whether they are members of any Society or of the general public.

1. RADIO AMATEUR EXAMINATION COURSE

Wednesday, 7.30 p.m. to 9.30 p.m.

Eight months course for those intending to take the examination.

2. MORSE AND CODES OF PRACTICE

Monday, 7.30 p.m. to 9.30 p.m.

Six months course for those who wish to learn Morse up to the G.P.O. requirements for an Amateur Licence. Arrangements have been made with the G.P.O. for those who, in the opinion of the Masters, have reached the required speed, to be tested at the College by a representative of the Post Office.

The venue for the above classes is the Ilford Literary Institute (High School for Girls) Cranbrook Road, Ilford, Essex. It is adjacent to Gants Hill Station on the Central London Tube, and buses pass the door. The fee for any one course for those living in the Essex County Council area will be 10/-. For those attempting both courses, the fee will be 17/6. Students from other parts of London will be admitted as out-County Students provided the local authority is notified.

ENROLMENT NIGHTS

September 6th, 7th and 8th.

CLASSES COMMENCE

September 20th.

These classes have now been running for seven years, during which period over 100 students have passed the R.A.E. examination. Those interested should drop a line to C. H. Edwards, G8TL, 10 Chepstow Crescent, Ilford, for reservations.

USING THE NEW PANEL-SIGNS

WITH THE INTRODUCTION OF "PANEL-SIGNS," designers and constructors of home-built equipment may now purchase cheaply, for a few shillings only, panel fixtures which previously would have cost considerably more. Moreover, these may easily be adapted to the particular purchaser's requirements and are not, in themselves, difficult to affix to any panel or piece of equipment.

It is not the writer's intention here to present a list of the packet contents, or indeed to state the method of mounting; details are given in the advertisement on page 113 of this issue, and in the case of panel fixing, instructions are clearly given, on the reverse of every package, for water-slide or varnish fixing, whichever is preferred. Within the scope of this article, it is the many uses and methods of adaptation which will be discussed in order to give readers some ideas on how best to utilise these transfers - which are, in themselves, a new departure for the home constructor.

Receivers and Amplifiers - Set No. 1

First to note here is the large full vision dial, measuring some 6 inches across and 4 inches deep. This has a provision for five ranges, and each range is clearly numbered along the bottom. Once having been affixed correctly to the panel, it may be calibrated with a signal generator; a note being taken of the outer scale reading (which is accurately marked with 100 divisions), this considerably assisting with the accurate calibration of the receiver. The dial itself may either be marked in "Block" form, i.e., the various broadcast bands being filled in solid line, or it may be marked in kc/s and/or Mc/s and/or metres - your choice entirely and not that of the manufacturer, as is the case with most commercial scales. Whether the coils are home-wound or commercial items does not matter one iota - the difficulty of matching frequency coverage of the former type of coil with a standard commercial scale does not now apply.

Dial marking is simple - and this applies to the whole range of these transfers - it merely requires a little patience and a supply

of ordinary indian ink together with a mapping pen.

The transfer, once in position, should first be allowed to dry thoroughly. This having been done, calibration and dial marking may be safely commenced. The tuning condenser knob, or spindle, should have affixed to it a length of thin perspex sheet some 2½ inches in length (measuring from the spindle centre), and this should be scored along the centre, afterwards filling in with indian ink. The outer scale readings may now be read against known signal generator readings, or those of a frequency sub-standard. Having noted these readings, it is a simple matter to mark the dial on the chosen scale line, e.g., band 4, with the correct frequency. The whole full vision dial may be easily and accurately calibrated in this manner within a very short period of time. Note that it is not essential to use direct drive; reduction gearing or a cord drive may be employed - the only proviso is that the condenser spindle should project through the panel.

Should the dial prove to be too large physically for any particular panel, it may, of course, be cut to a smaller size, within reason, with a sharp pair of scissors prior to mounting on the panel. The decorative top portion and some of the lower part may be omitted in this manner if so desired.

It should also not be overlooked by the user that various colours of indian ink, say one colour for each band, or perhaps red for broadcast and blue for amateur bands, etc., may be utilised. The possibilities and variety of markings are many and varied indeed.

The control panels, i.e., those used with potentiometers, switches and condensers, are self explanatory, but a few words on their possible uses will not come amiss here - especially for those who are beginners in radio construction.

Those with 180° rotation are for use with small variable condensers such as, in a TRF, *Reaction*, *RF Trim*, *Aerial Coupler*, or even *Bandset*; in a superhet - in addition to the aforementioned, *BFO*, *Crystal Phasing*, *Oscillator Shift*, etc. For potentiometers, in a TRF - *Reaction* (where screen HT is


varied), *Tone*, *AF Gain*, *RF Gain*, *Audio Filter*, etc. For Superhet, apart from those previously mentioned, *IF Gain*, *Noise Limiter*, *Variable Selectivity*, etc.

Appropriate transfers for Yaxley type switches are also included, and these may be marked in accordance with the constructor's wishes from the wording included. Mentioning only a few uses to which these may be put, there are *Bandswitch* (marked with the

Finally, as a point worth noting, it should be borne in mind that these "Panel-Signs" may be used with any existing transfer wording which the constructor may have on hand.

Test Instruments - Set No. 2

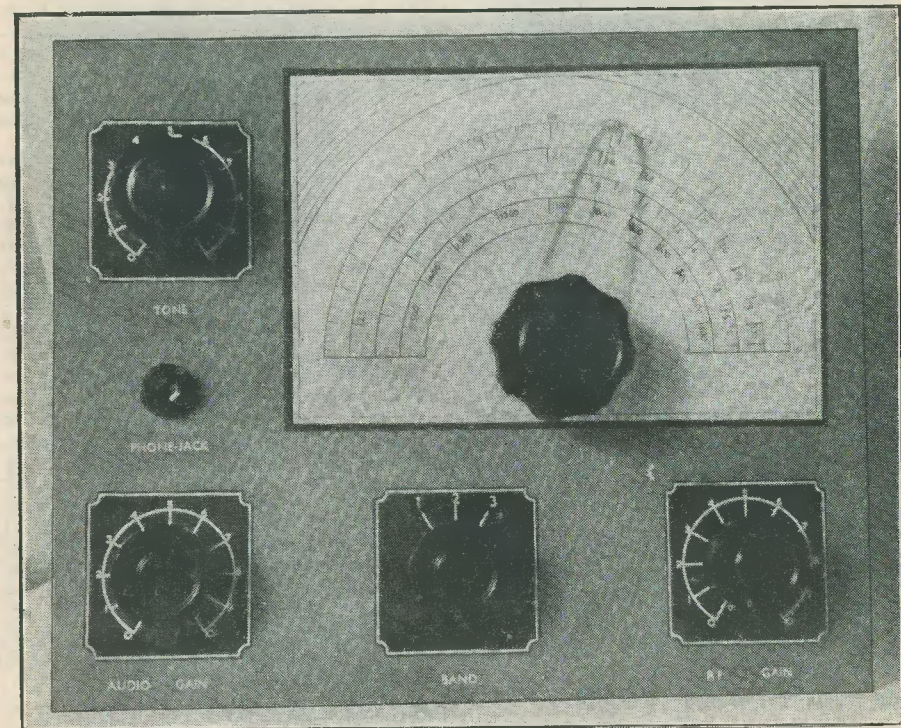This set contains, in addition to the wording, lettering and figuring commonly used on test equipment, a useful set of



Panel for an all-wave receiver, showing the workmanlike and professional appearance obtainable with "Panel-Signs"

selected frequency coverage from the figures provided), a switched *Tone Control*, *AVC* or *BFO On/Off* control, switched *Selectivity*, etc. As before, these may be cut into any desired size, within certain limits, by means of scissors. Any particular white markings not required may be omitted by the simple expedient of blacking them out with indian ink - a most useful point to remember. The name of the control may be placed either above, at the side of, or below the panel, whichever is the more convenient or best suits the panel layout.

electronic symbols such as μ , Ω , +, -, %, and various other markings. Potentiometer, Yaxley type switch and variable condenser control panels are included. The uses to which these may be applied are almost too numerous to mention here. Almost every unit of test equipment contains a varied selection of these controls. As in Set No. 1, these transfers may be altered either by blacking out with indian ink, should erasures be required, or by the addition of wording and/or symbols should these be considered necessary.

Two dials are included in this set, and these measure 4 inches long by 2½ inches deep. They are both marked from 0 to 100 and provision is made to accommodate four separate ranges.



Whilst "Panel-Signs" are self-fixing as supplied, the use of fixing varnish is recommended for best results on crackle and other rough surfaces.

These dials are of the full vision type, and an interesting feature here is that two may

HAMFEST IN HOLLAND

The V.R.Z.A., the Radio Society of Transmitting Amateurs in Holland, will celebrate its annual hamfest this year in a beautiful camp site in Voorthuizen, half-way between Apeldoorn and Amersfoort, on the week-end of the 25th and 26th of September.

Accommodation will be in bungalows, and all licensed amateurs, S.W.L.'s and their families will be very welcome.

There is an extensive programme of entertainment with dances, films and cabaret, together with all kinds of radio lectures, a D.F. competition, an exhibition of modern equipment, and demonstrations.

The cost for the whole week-end, including all meals and sleeping accommodation, is only 10 guilders, or one pound.

Further information will be gladly given by

PAOXE, Claes de Vrieselaan 153 a Rotterdam, Holland, who will also be pleased to accept bookings.

This is an ideal occasion to see the other end of your contact, and as an extra attraction we may add that besides door prizes to every 25th visitor, the visitor who came farthest will get an extra prize.


be "married" to form a complete circular dial calibrated to a total of 200 divisions, i.e., 100 to the left and 100 to the right. This is especially useful for those about to construct a bridge and no doubt other uses will suggest themselves to readers.

General

The new "Panel-Signs" are, of course, permanent paint transfers, and it is a good point to remember that added protection may be imparted by treating these, when once dry, with a coat of varnish (Panel-Signs Transfer Fixing Varnish is recommended), which may be obtained from your local radio supplier. The use of clear nail varnish is not recommended, as this soon becomes brittle and easily chips.

Set No. 1, previously referred to, is also equally applicable to amplifiers, suitable wording and control panels being provided. "Panel-Signs" are an indispensable aid to the home constructor; nothing like them have ever before, to the best of the writer's knowledge, been offered to enthusiasts in this country. They most certainly fill a long-awaited need, and, regarded in the same manner as most constructors view their components, they are very good value for money indeed. When one considers the cost of dials and other panel fixtures of the type to be found currently on the market, these new components, for that is what they are, represent a great saving. And as for adaptability - if they prove to be too large for the scheme of things, then cut them down; calibrate and mark them as you will; erase such markings as are not required; add the chosen wording or the figures, juggle with the symbols and even choose your own pet colour scheme for the tuning dials - what more could the discerning radio enthusiast desire of any component?

BUILDING THE RCS BATTERY RECEIVER*

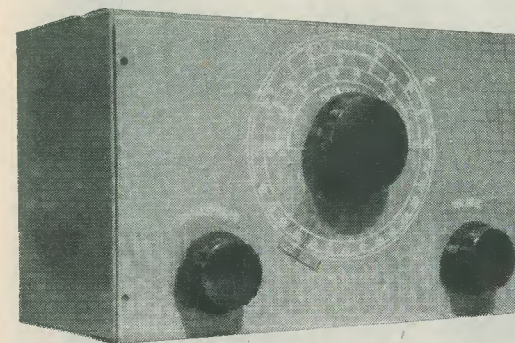

Part 3

A THREE-VALVER

By JAMES SINCLAIR

IN THIS ARTICLE IS DESCRIBED HOW TO add the third and last valve, together with the associated components required, to make this little set into a three-valve receiver. As such, it is capable of a very good performance indeed. Being a battery set, the background noise is very small, almost unnoticeable in fact, and this means that many stations are audible which might otherwise go unnoticed.

With a set of this nature, it is advisable for the beginner to spend some time getting thoroughly used to the receiver and to develop some skill at operating, particularly on the Short Waves. Here, with the world at one's fingertips, many happy hours may be spent listening to the various transmissions put out by the many powerful international broadcasting stations. For the guidance of those interested, Table 1 should be consulted. (*World Radio Handbook*, obtainable from us, gives a complete list of these stations, together with times of transmission, call signs, interval signals, station addresses etc., - Ed.). The Amateur Bands should also be "watched" for interesting transmissions between Amateurs (See Table 2).


The simple and comparatively cheap receiver described places within the reach of every beginner the delight and thrills of these bands, i.e., the Amateur and Broadcast

Short Wave frequencies. These, together with the Medium Waves, provide most of the broadcasts likely to be of interest.


Wiring Instructions

- STEP No. 1. Disconnect one end of R2 which goes to Yellow on phone socket, and solder a length of Green flex to this end of R2, and then push Green flex through rubber grommet on rear of chassis.
- „ No. 2. Disconnect wire that goes to Red on phone socket, and then connect this wire to one end of C6 and one end of R5.
- „ No. 3. The other end of R5 goes to Yellow on phone socket.
- „ No. 4. The other end of C6 goes to one end of R4. The other end of R4 is soldered to earthing tag fitted under nut which holds valveholder No. 3 in place.
- „ No. 5. To the junction of C6 and R4, fit a short length of wire and push through chassis. At the other end of this wire solder one of the valve clips provided and fasten this to the

* See advertisement on page 123.

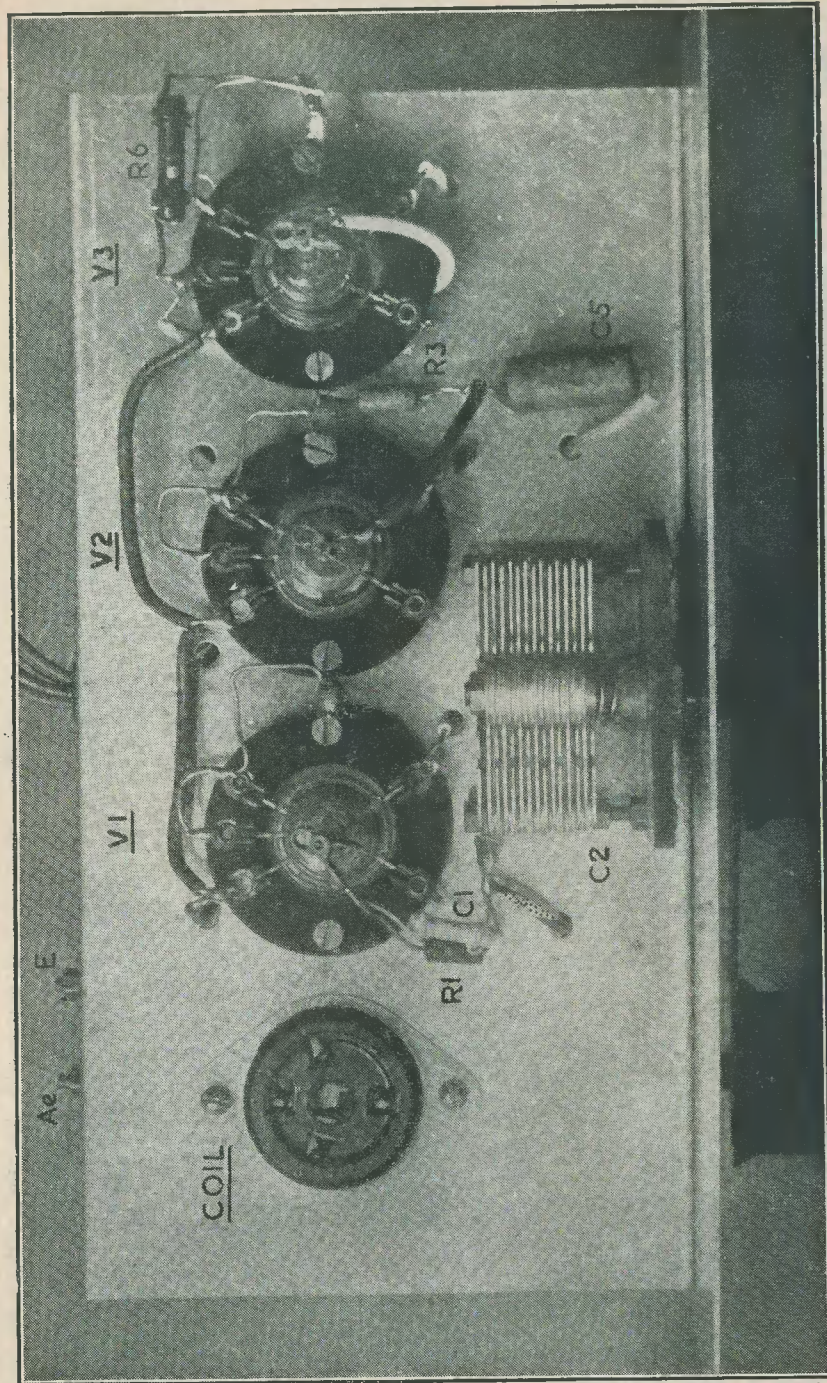

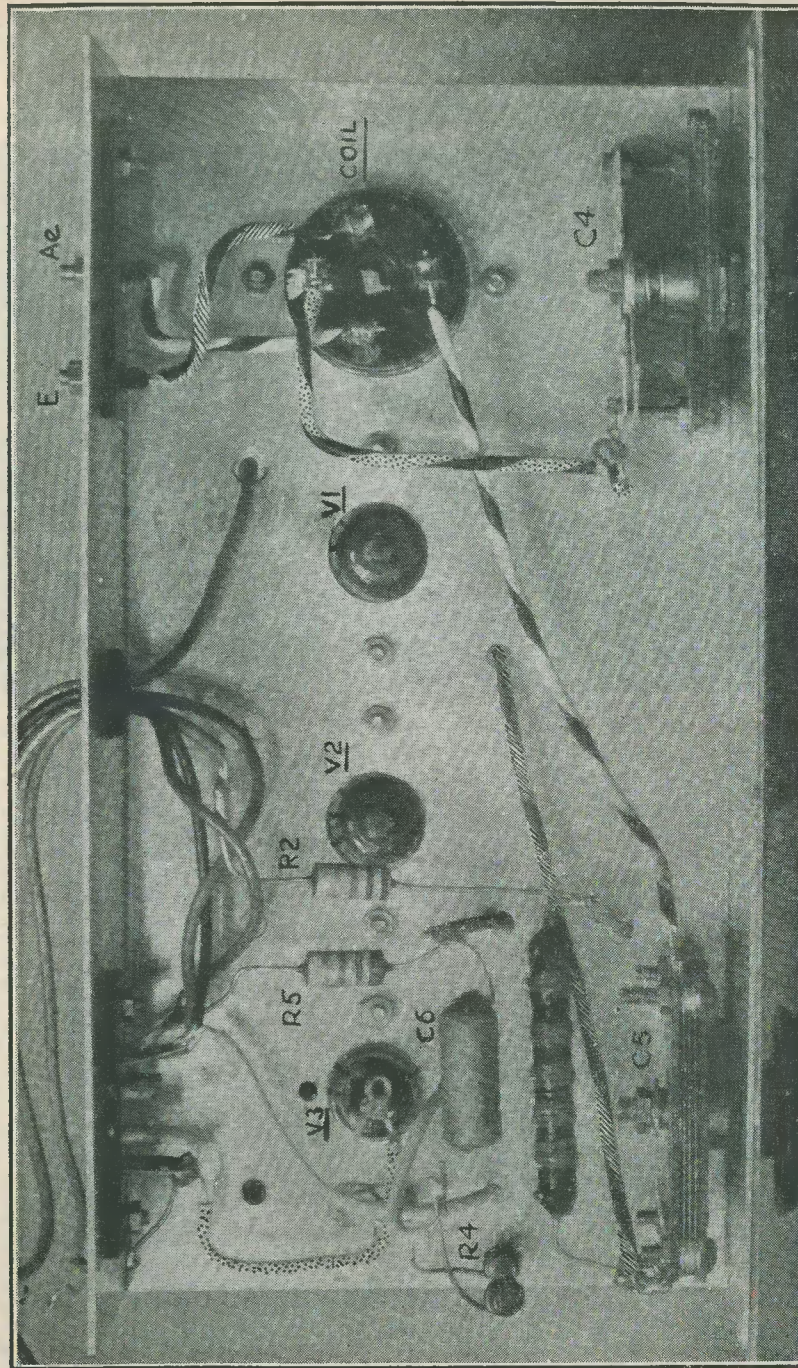
Above chassis view of the RCS three-valver



Below chassis. Identification of components

STEP No. 5. grid connection which protrudes from the valve. (This is opposite to the Red end of the valve).

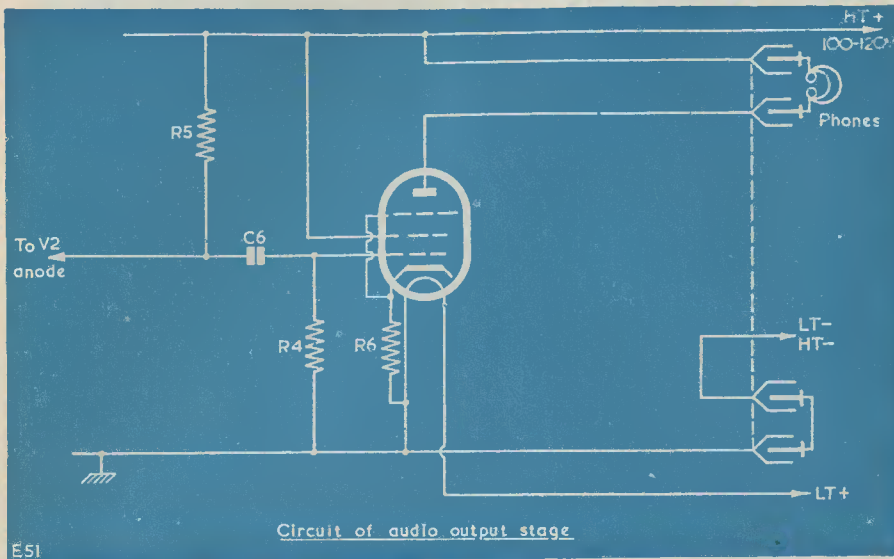STEP No. 8. Solder one end of R6 to Red on valveholder No. 3 and other end to earthing tag fitted on valveholder.



NOTE: In the August issue there was an error in the circuit of the AF stage—R2 should have been connected to the other side of the phone sockets. The text and photographs were correct

STEP No. 6. Join White on valveholder No. 2 to White on valveholder No. 3.
 „ No. 7. With a short length of flex, join Gold and Red on valveholder No. 3.

STEP No. 9. Join Blue on valveholder No. 2 to White on valveholder No. 3.
 „ No. 10. Solder length of flex to Yellow on phone socket and push through hole in chassis. Connect other end of this flex to Yellow on valveholder.
 „ No. 11. To Red on phone socket, solder short length of flex at the other end of which is fitted the other valve clip provided. Secure this clip to anode connection which protrudes from valve (End of valve coloured Red).

This completes the actual construction of the three-valve receiver, but a change in the voltage supply is now required in order to get the best performance out of this set. The LT, of course, remains the same, but the HT+ should be increased and connected as follows:—Black to HT-, Green to HT+ 30-50 volts and Red to HT+ 100-120 volts. For the small outlay both in cash and time, this little set is the ideal medium for the budding radio enthusiast to gain both experience and some knowledge.

TABLE 1
SW BROADCAST BANDS

Metre Band	6,000 kc/s to 6,500 kc/s	Metres
49	6,000 kc/s to 6,500 kc/s	50 to 45.88
41	7,000 kc/s to 7,500 kc/s	49.85 to 40
31	9,370 kc/s to 10,000 kc/s	32.01 to 30
25	11,560 kc/s to 11,996 kc/s	25.92 to 25.01
19	15,000 kc/s to 15,640 kc/s	20.00 to 19.18
16	17,677 kc/s to 18,025 kc/s	16.97 to 16.64
13	21,460 kc/s to 21,750 kc/s	13.98 to 13.79

NOTE: Most of the short wave stations are to be found within these frequency limits. Many stations, however, work on lower frequencies, the most notable being the South American stations below 6,000 kc/s. These extend right down to as low as 2,340 kc/s or 128.2 metres.

TABLE 2
LF AMATEUR BANDS

Metre Band	1,800 kc/s to 2,000 kc/s	"Top Band"
160	1,800 kc/s to 2,000 kc/s	"80 Metres"
80	3,500 kc/s to 3,800 kc/s	"40 Metres"
40	7,000 kc/s to 7,300 kc/s	"20 Metres"
20	14,000 kc/s to 14,350 kc/s	"15 Metres"
15	21,000 kc/s to 21,450 kc/s	"10 Metres"
10	28,000 kc/s to 30,000 kc/s	

Query Corner

A Radio Constructor Service for Readers

Earthed Ion Traps

I have noticed that in a number of the more modern television receivers the ion trap magnet assembly is earthed to the receiver chassis by a short length of wire. What is the purpose of this connection?

F. Hamer, Cardiff

The use of higher EHT voltages for the picture tubes in television receivers is now standard practice, with most receiver manufacturers. Potentials in the region of 14-16kV are quite common, and are used to provide pictures of the best possible brightness and definition. The use of these high voltages introduce added complications to the receiver - one of these complications, although small but nevertheless significant, is that isolated parts in the vicinity of the tube can collect an appreciable electrostatic charge. This may in time build up to the point where it can flash over to some nearby component causing a burst of interference on the picture. The ion trap magnet assembly can collect such a charge either because of stray fields from points of high potential, or because of a small amount of leakage along the glass walls of the tube. This charge can be most unpleasant if the magnet is touched; and it may cause the operator to remove his hand very quickly, introducing the possibility of damage to a component. It is to prevent an occurrence such as this that many set manufacturers now earth the ion trap assembly, a procedure which can be recommended to the constructor.

Anti-Static Polish

There are a number of anti-static polishes at present on the market. Do you recommend the use of these on the screens of CR tubes to prevent the collection of dust on the glass?

E. Browne, Ilford

In order that it may be effective in preventing the formation of static charges, this type of polish must be a semi-conductor

of electricity. By this means it prevents the building up of isolated electrostatic charges. It is particularly suitable for treating gramophone records and the plastic masks through which many television tubes are viewed. In preventing the formation of these electric charges, the polish also reduces the tendency for dust to be attracted to the treated object, which therefore requires much less frequent cleaning.

It is not, however, advisable to use an anti-static polish on the screens of television tubes because, whilst it may prevent

Query Corner

RULES

- (1) A nominal fee of 2/6 will be made for each query.
- (2) Queries on any subject relating to technical radio matters will be accepted, though it will not be possible to provide complete circuit diagrams for the more complex receivers, transmitters and the like. Queries relating to ex-W.D. surplus or commercial equipment cannot be accepted.
- (3) Complete circuits of equipment may be submitted to us before construction is commenced. This will ensure that component values are correct and that the circuit is theoretically sound.
- (4) All queries will receive critical scrutiny and replies will be as comprehensive as possible.
- (5) Correspondence to be addressed to "Query Corner," Radio Constructor, 57 Maida Vale, Paddington, London, W.9.
- (6) A selection of those queries with a more general interest will be reproduced in these pages each month.

the collection of dust, it will lead to a tendency for screen blocking. This effect is noticeable on many tubes when the receiver

is first switched on, the raster often appearing very distorted and not completely filling the whole screen area. The distortion

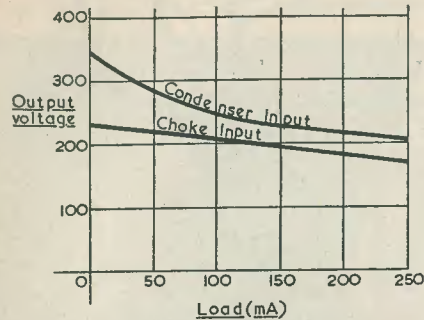


Fig. 1
Comparative graphs for a 250V AC
input to rectifier

E58

disappears after a minute or so, its disappearance being hastened if the picture brightness is turned up. This form of screen blocking is attributed to the formation of isolated charges on the screen phosphor, a trouble which may be aggravated if the outer glass of the tube is covered by a semi-conducting layer of polish.

If any readers have tubes which are giving trouble with screen blocking, the cure lies in wiping the screen and the clear glass around the sides of the screen with a cloth damped with methylated spirits. Care should be taken not to wipe over the cone of the tube if it is coated with graphite as this coating can easily be washed off.

Choke Input Filter


I have a power pack in an amplifier which is giving an output voltage too high for the valves in the output stage. Is it permissible to reduce the voltage by the use of a choke input filter in the HT smoothing circuit to avoid the use of large dropping resistors?

H. Lennox, Brighton


The choke input HT smoothing filter is indeed capable of providing a lower output voltage than the condenser input filter. To many designers this point may be a disadvantage; so to present the case fairly, the other properties of this type of filter must be considered. The choke input system has two main advantages. First, the inductance restricts the condenser charging current so that the peak current drawn from the rectifier is substantially reduced; this results in a much improved

rectifier life. Secondly, the regulation of the power supply is very much better, a feature which is of particular importance if the power pack is required to supply a fluctuating load current. The regulation characteristics of the two types of filter are shown in Fig. 1, whilst in Fig. 2 the circuits of the three main variations of smoothing filters are shown. However, as with all circuits, optimum performance can only be obtained if the correct values of inductance and capacitance are chosen for the filter components.

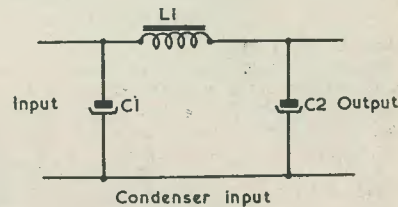
The function of the choke is to raise the ratio of average to peak current, and in so



Condenser input

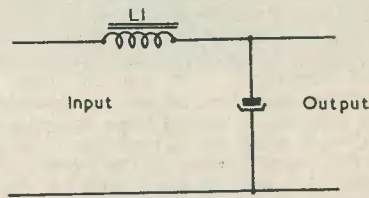

Single-stage choke input

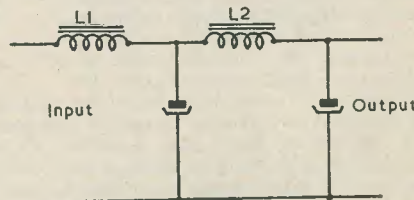

Two-stage choke input

Fig. 2

Basic types of smoothing filters

E59

doing it prevents the DC output voltage rising above the average value of the AC voltage fed to the rectifier. The choke can only perform this function properly if its value equals or exceeds the critical induct-

ance which is given approximately by the formula:

$$L (\text{Crit}) = \frac{\text{Load Res. (ohms)}}{830}$$

assuming a full-wave rectifier circuit operating on a 50 c/s supply. The optimum value of inductance is twice the critical value, and represents the point at which further increase in inductance gives a disproportionately small improvement in operating characteristics. The load resistance is calculated from Ohm's law by knowing the HT voltage and load current. The above formula clearly indicates that the optimum filter inductance varies with the load resistance, the inductance being highest under conditions of light load. Now the inductance of a choke tends to fall as the current through it increases, so it is possible to design a choke having a "swinging" characteristic. A swinging choke is designed to have the critical inductance at very low loads and optimum inductance at full load. By fulfilling these requirements, optimum performance is achieved with a choke of minimum size.

The value of capacitor is chosen to give the required degree of smoothing. The degree of ripple is given for a single section choke input filter by the approximate formula:

$$\% \text{ ripple} = \frac{70}{LC}$$

If a ripple better than 5% is required, it is usually most economical to employ a two stage filter. In this case the ripple is given by:

$$\% \text{ ripple} = \frac{380}{L_1 L_2 (C_1 + C_2)^2}$$

The above formula applies to a full-wave circuit operating from a 50 c/s supply.

It is most important to avoid resonance in the first stage of the filter. Resonance will occur when the product of the choke inductance in henrys and the condenser capacitance in microfarads equals 2.53. The product should equal at least twice this figure to guard against resonance effects.

Finally, the output voltage of a correctly designed power pack using a choke input filter is given very closely by the formula:

$$V_{\text{out}} = 0.9 V_E - \frac{I(R_c + R_r)}{1,000}$$

where V_E = RMS voltage applied to one anode of the rectifier,

I = Load current (mA)

R_c = Resistance of choke(s)

R_r = Resistance of rectifier valve between anode and cathode. (About 100Ω for a high vacuum valve).

[END

Can Anyone Help?

DEAR SIR,—Can any of your readers help me in converting a 1/50th horsepower 50V 50c/s 3-phase induction motor to 230V single phase operation?—G. Truscott, 2 Granville Street, Monton, Eccles, Manchester.

DEAR SIR,—I wonder if any of your readers would lend, sell or give me the circuit and details of the Eddystone 358X receiver. The makers cannot now supply me with the required information.—K. Gray, 60 Braithwell Street, Denaby Main, Nr. Doncaster.

DEAR SIR,—I would like to take advantage of your offer under *Can Anyone Help* to ask for circuit diagram and conversion data for 144 Mc/s of the R1137A.—A. R. A. Love, 18 Coy. R.A.S.C. (W.T.), H.M. Gun Wharf, Sheerness, Kent.

DEAR SIR,—I would be glad of any books, circuit diagrams, etc., on all-purpose super-selective IF amplifiers, better IF selectivity, and double-conversion 35 kc/s, 50 kc/s, 85 kc/s or 100 kc/s second IF's. All literature, etc., will be returned if required.—B. N. Gregory, G3DNT, "Savesbury," Jackson Tor Road, Matlock, Derbyshire.

SIR,—I am constructing a double superhet, some details of which appeared in the Jan. '53 issue of *The Radio Amateur*. The author, C. R. Greenland, G4HD, gives the second IF's as Ferrocart 110 kc/s with variable mica coupling condensers between the windings. I understand these IF transformers are no longer obtainable; perhaps one of your readers has three in his "junk-box" which he will supply to me.—A. Nash, 3 Swiss Cottage, Tadworth, Surrey.

SIR,—Can anyone furnish me with details, such as crystal frequencies, valve line-up, HT line voltage, and where a circuit diagram could be obtained, of the R.A.F. Transmitter A.M. type T1043, Ref. 10/D 3330.—H. G. Chieseman, "Malvalla," 265 Cliffe Road, Strood, Nr. Rochester, Kent.

DEAR SIR,—May I be allowed to crave a space to appeal for help in getting a home-built 6H6 ratio discriminator for FM to work—signal going in but no audio output.—J. A. Cusdin, 99 Cavalry Crescent, Eastbourne, Sussex.

DEAR SIR,—Can anyone possibly sell, lend or otherwise supply me with any information on the 358X communications receiver?—R. O. Streek, Cawood Road, Wistow, Selby, Yorks.

Radio Miscellany

Portable

A CORRESPONDENT, REFERRING TO MY recent comments on telephone gadgets etc., writes to say that perhaps the G.P.O. are not so unenterprising after all. He tells me that at an Acton Hospital there is a roving telephone, fitted on a trolley which is wheeled around the Wards. The trolley is complete with Directories—and coin box! It is designed to enable bed-ridden patients to call up relatives and friends, and occasionally join in the old English pastime of getting wrong numbers.

No, there is no VHF link or anything like that. Simply a plug-in socket beside each bed.

Of Mice and Men

The latest edition of TV's Inventors' Club contained one item which interested me greatly. As usual the programme was spoiled by its breakneck speed. It is impossible to treat fourteen or fifteen ideas adequately in what is left of thirty minutes after the introduction, announcements, lists, and farewells are deducted. True, such ideas as new coathangers, or an indicator to stick on a reel to show where the cotton ends, can be demonstrated in half-a-minute, but mechanical devices need more than just showing. Most people I have discussed this with agree with me that they are not content to merely see that the inventions submitted DO work; they want to see HOW they work.

Many TV programmes, especially the documentaries, are padded out with lots of tedious detail about the obvious or the unnecessary. This makes the high pressure speed of Inventors' Club doubly exasperating. I can only imagine the BBC fix programme times by the clock instead of allowing each item to run its natural length. To the admin. staff the time-table has always been more important than the broadcast itself. Perhaps that is why the plays are usually successful. The time has to be made to fit the play, not the play to fit the time.

However, the invention which so excited my especial interest was a "contour accommodating vice" which, in contrast to the rigid jawed type, shapes itself so as to securely hold irregularly-shaped objects.

Hot-Point

Don't ask me how it works. Either the commentators didn't know or weren't telling. They did, however, vouchsafe that it was the most beautiful model submitted. A vague reference was made to some little stops in the jaws and we were shown how a piston engine con-rod could be held in it.

Even if this invention had not been so useful and of obvious interest to radio-men, it would have captured my attention as it was quite a coincidence that a vice should be in the programme. Earlier in the evening I had been at a friend's workshop and seen an idea I intended to mention in Miscellany. Many will have already heard of, or practised, the idea of using a spring-clip clothes peg for holding wires and small objects when soldering. They don't absorb the heat and, more to the point, they obviate scorching one's fingers. The friend I visited had gone one better. He uses a break-back mouse trap, screwed to the bench, for soldering jobs of this nature. It not only gives a firmer grip than clothes pegs, but being screwed to the bench there is no danger of it moving just as you take the iron away.

TV Marches on

Recently when washing down my ancient roadster I had an interviewer call from the BBC Audience Research. I dutifully answered all the questions—even the politely worded nose ones about my age group, occupation etc.

Perhaps I wasn't a lot of help. I neither listened or looked-in the previous evening or on the Sunday, the nights in which he seemed most interested. Experience teaches us to be cautious of the results of such "surveys" even when it is possible for a decisive answer to be given. Frequently,

"polls" are several-per-cent out on clear cut issues. With questions to which it is impossible to give an unqualified answer the results are often widely wrong. It is indisputable that two separate interviewers will get quite different answers simply on account of differences in the way in which the questions are phrased. How simple it will be when we have an alternative programme. All one will have to answer will be, which programme one's family preferred to watch last night and the night before.

something specially edited for semi-literates. Since my interview, the April/June Audience Research figures have come to hand. Once again it seems that TV expansion is gaining ground by stealing the customers from "sound" radio. Does this mean that the regular viewing public is chiefly made up of people who don't know what else to do with their spare time?

All in a Row

I suppose most readers solved last month's

CENTRE TAP

talks about

G.P.O. — B.B.C. Programmes
Inventor's Club—B.B.C. Polls

I am still convinced there are too many hours of both sound radio and TV. Less hours and better programmes is still the slogan for discriminating audiences, and in "off-peak" hours there could well be a number of specialised programmes for minority groups. While there are many programmes of the entertainment or amusement type the BBC do well—really well—serious programmes can rarely be included under this heading. Why must it always be assumed that listeners have never given time or thought to any subject of a serious nature? Many a programme which, on paper, has promised well has turned out like

problem without difficulty but, as promised, here is the answer. The following ten resistors will enable any value to the nearest ohm between 1 and 1,023 to be selected at will.

1	2	4	8
16	32	64	128
256	512		

By simply adding another five resistors to the collection one could get any value up to well over thirty thousand ohms and it wouldn't require many more to go over the million mark. Yet quite why anyone should want a 469,999 ohm resistor instead of the conventional 470,000 would be a still harder problem to solve.

WALTON AMATEUR RADIO EXHIBITION

Organised by the QRP Society

On Saturday, October 30th, 1954, there will be staged for the first time in Walton-on-Thames an exhibition covering all aspects of Amateur Radio.

The purpose of the Exhibition is: (a) to convey to the visitor a comprehensive idea of the varied and often valuable work which Radio amateurs are carrying out, (b) to lay special emphasis on the efficiency of low power for amateur transmissions, particularly as regards local communications, and (c) to provide a review of contemporary equipment, both amateur built and commercially manufactured, in all branches of radio and allied spheres.

The Exhibition, to be held in the St. Mary's Parish Church Hall, will be opened by a well-known public personality at 2.30 p.m. Admittance will be by ticket, price 1/- (children half), obtainable at the entrance. Blocks of six or more tickets at 8d. each are obtainable from the Secretary of the QRP Society not later than 23rd October.

Refreshments will be available, and there will be approved parking facilities for motorists.

All proceeds will be given to the Chorister's Parents Guild of St. Mary's, whose funds are devoted to the requirements of the Parish choir.

Among the exhibits there will be displays of amateur equipment, commercial sound and vision receivers and components; demonstrations of radio-controlled models, high fidelity reproduction, amateur television and "walkie-talkie" communication. There will be an amateur station "on the air" from the exhibition hall, exhibits from the popular National radio journals and a stand devoted to the sale of surplus equipment.

It is hoped that many of the amateurs from the Home Counties will visit the Exhibition and to aid those who have no knowledge of the district, there has been prepared a guide leaflet obtainable from the Secretary, QRP Society, "The Retreat," Rydens Avenue, Walton-on-Thames, Surrey.

KNUPPLE SYSTEM OF RADIO CONTROL

By A. C. GEE G2UK

THE WRITER RECENTLY DESCRIBED, in this journal, a steering unit for use in radio controlled models, which would give proportional control, i.e. it could be 'inched' up, back and forth, so that a fine degree of control can be obtained.

The conventional type of circuitry needed for this mechanism requires two channels, which are usually provided by a receiver using the tuned reed system.

There is a method available, however, which will permit this proportional control mechanism to be used with a single channel receiver and transmitter. It is known as the 'Knupple' system, after that used in the German glide bombs of wartime fame. It consists essentially of a space-marker pulse system, the position of the proportional control depending on the ratio between the signal beats and the spaces between them.


A normal single channel, unmodulated transmitter is keyed in such a way that it will send either a continuous signal, or no signal at all, and all stages of interrupted signals between these two extremes. That is, if the control is set halfway, a signal consisting of equal spaces and impulses is sent; if it is set a quarter way, the spaces are a quarter of the impulses and so on. This signal is picked up on a normal single channel radio control receiver and it will be found, of course, that the relay arm follows the time-space ratio of the transmitted signal. When a continuous note is sent, the relay stays over on one stop. When no signal is being transmitted, it stays over on the other stop; and when intermediate pulses are sent, the arm oscillates between the two stops at a time-ratio in keeping with that of the transmitted signal.

If the relay is connected up as shown in Fig. 1, the motor of the proportional control unit will 'oscillate' in keeping with the relay. It will turn a few revolutions in one direction, and then back again a few turns in the other direction. At the midway point of the transmitter control, the back and


forth revolutions will cancel out and the proportional control unit arm will remain stationary or almost stationary, depending on the amount of backlash in the gearing. When a continuous note is sent, the motor will rotate continuously in one direction until the limiting switches cut it out. When no signal is sent, it will turn in the opposite direction, until again the other limiting switch will cut it out. Similarly, intermediate stages of the transmitter control will produce corresponding positions in the proportional control unit.

The unit described herewith consists of the transmitter control unit by means of which the space-marker pulses can be produced. It can be used either with the proportional control unit described previously - as it was in the writer's case - or, of course, with similar home constructed or commercial units. The variation in space-marker ratio is provided by a rotating roller of insulating material on which is fixed a long V-shaped piece of copper foil. A contact arm slides over this V-shaped piece of foil, the arm being actuated by the control rod on the outside of the box. The roller is turned rapidly by a small miniature electric motor mounted as shown in the illustrations. The gearing mechanism shown in the writer's model came from the dial mechanism of a disused telephone, and gives a reduction of about twenty to one. If similar gears cannot be obtained, little ingenuity is needed to devise a satisfactory gear train from the gears usually to be found in the junk box of most radio control enthusiasts.

The roller is made from $\frac{1}{4}$ " dowel rod and the foil is stuck on with Bostik Adhesive. Little further comment is necessary as the construction is self-evident from the photographs. The unit is built into one of Eddy-stone's $4\frac{1}{2} \times 3\frac{1}{2} \times 2$ " die-cast boxes. The wiper arm carrying the contact which slides over the foil is attached to a short length of rod which passes through a bush to the outside of the box, a short length of rod

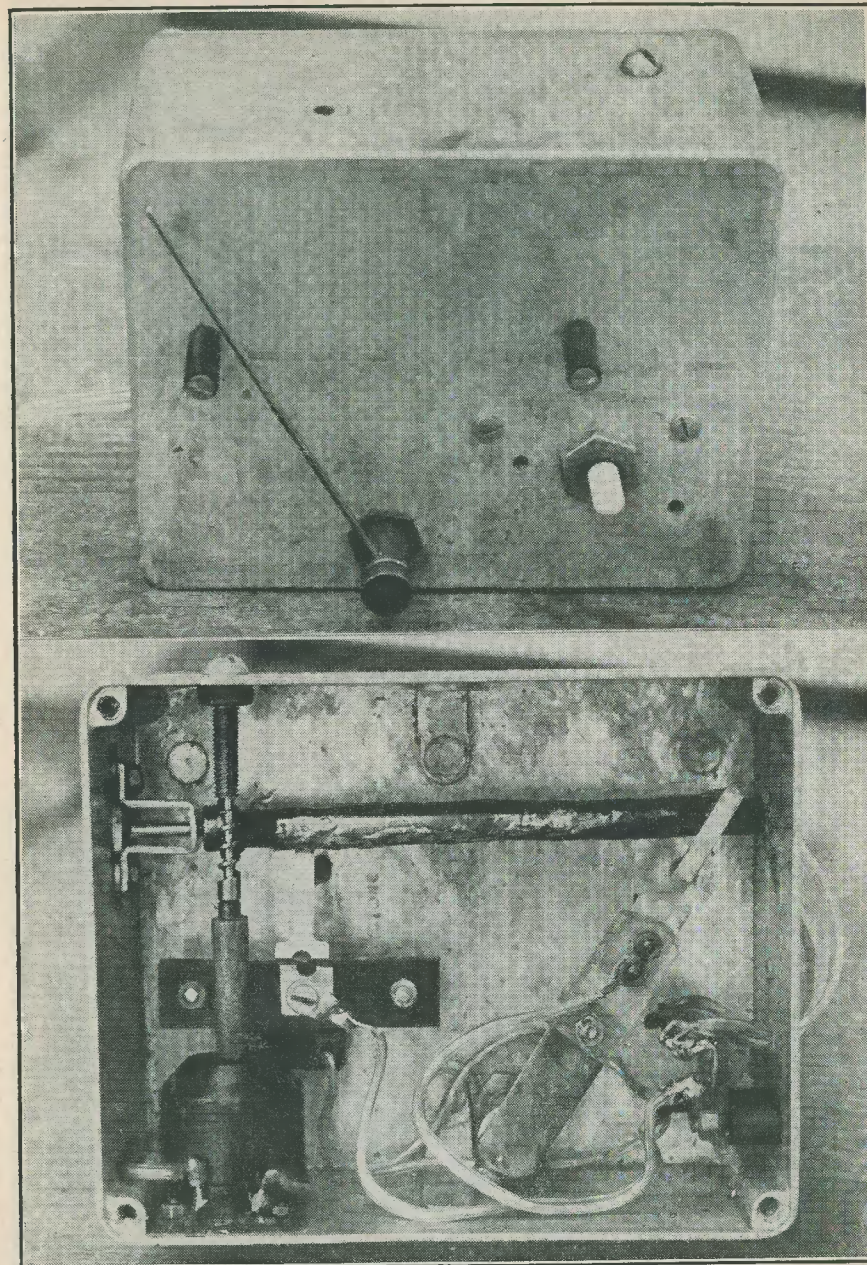

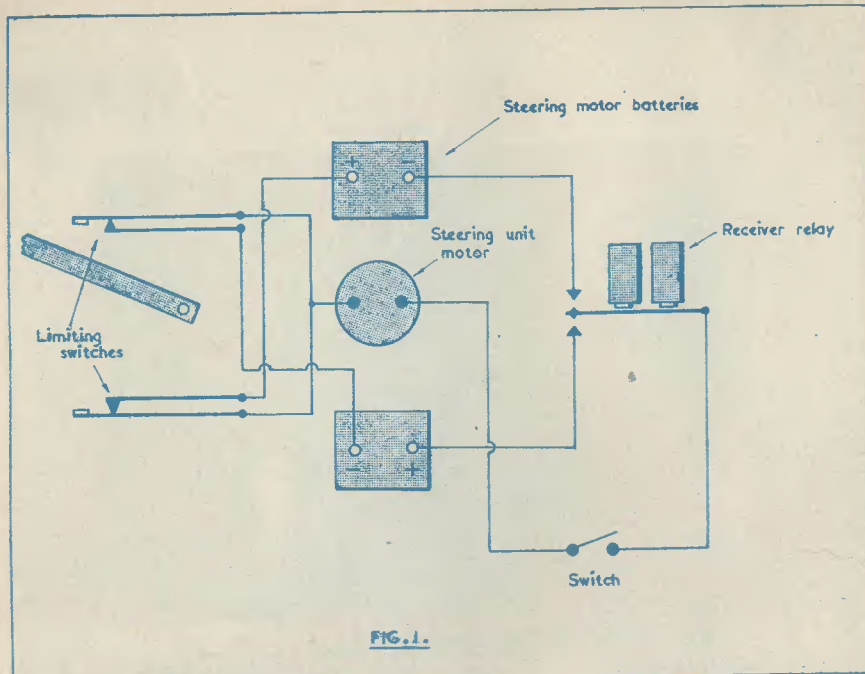Inside and outside views of Knupple type radio control transmitter control unit



being fixed to it as shown to form the control lever. Two stops are fitted as shown to limit the travel of the arm. A small switch should also be fitted to switch off the motor when required. A second wiping contact is needed to make the second contact with the foil. This contact has to be insulated from the box. Two leads are needed from the box; one to carry the current for the motor and the other to connect the rotating foil etc. to the keying terminals of the transmitter.

Once completed, it can be tested out without the radio circuit in the first place, by connecting up to a relay and battery; the contacts of the relay being wired up to the proportional control unit as shown in Fig. 1. In this way final adjustments can be made to ensure that the roller runs smoothly

and proper contact between the foil and the wiper arm is taking place. Once everything is going nicely, the radio circuit can be set up and the unit used to key the transmitter in place of the normal transmitter keying arrangements.



The only alteration which is needed to the receiver is that, whereas in the 'sequence' type of operation only one of the contacts on the receiver relay is used, in this circuit both contacts are needed. In most radio control receivers however, the relay is provided with two contacts, so that all that is needed is for a second lead to be soldered to the relay. Some adjustment of the relay itself may be needed to ensure that it travels equally between both stops, but normally little adjustment should be necessary.

Announcing . . .

PANEL-SIGNS

Permanent Paint Transfers for a Professional Finish

A real boon to the Serious Constructor

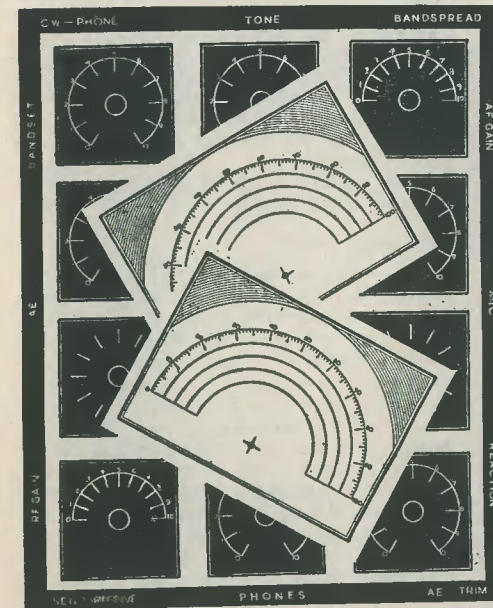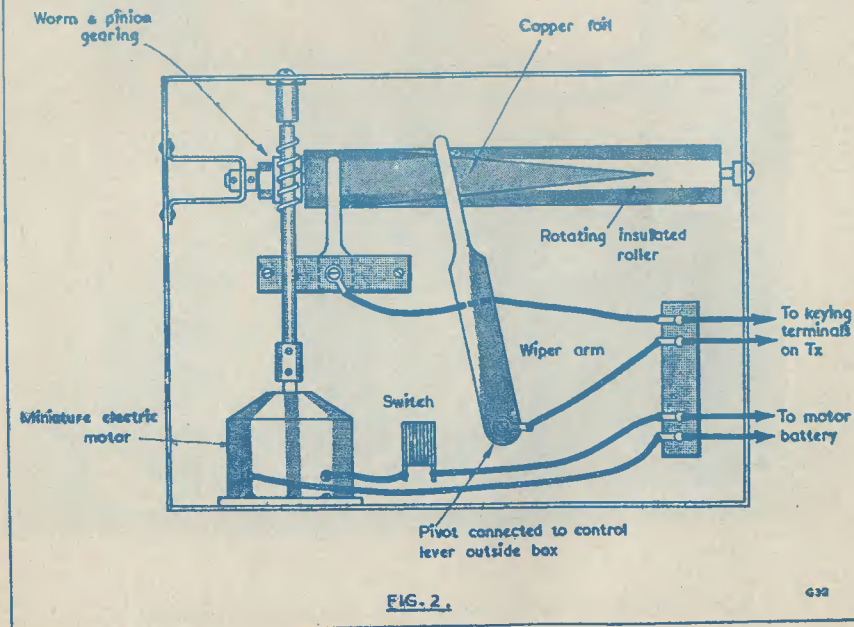

SET No. 1: RECEIVERS AND AMPLIFIERS—

Five sheets $8\frac{1}{4}'' \times 5\frac{1}{4}''$ containing one Large scale, twelve control panels and wording.

SET No. 2: TEST INSTRUMENTS—

Five sheets $8\frac{1}{4}'' \times 5\frac{1}{4}''$ containing two Medium scales, twelve control panels and wording.

WILL FIX TO ANY SURFACE AS SUPPLIED
Fixing Varnish is recommended for best results, particularly on uneven surfaces.

Price 3s. 6d. per Set

Panel-Signs Transfer Fixing Varnish
1s. per bottle.

Trade enquiries invited

Published by
DATA PUBLICATIONS
57 Maida Vale London W9
Telephone: CUN 6518

14: MATCHING

By A. BLACKBURN

IT MAY SEEM A BIG JUMP FROM SHORT waves—the subject of last month's article—to audio frequencies, but these apparently diverse topics have one problem in common, regardless of frequency.

Matching the power generator to the load, so that the maximum amount of generated power is efficiently used, can be a headache for any radio engineer until the snags involved have been cleared up.

Unfortunately, despite the fact that this basic requirement has to be met at all frequencies, the conditions may vary considerably from one frequency to another.

Internal Resistance

The simplest type of circuit, for the purpose of illustrating the meaning of the process known as matching, is the battery and resistor.

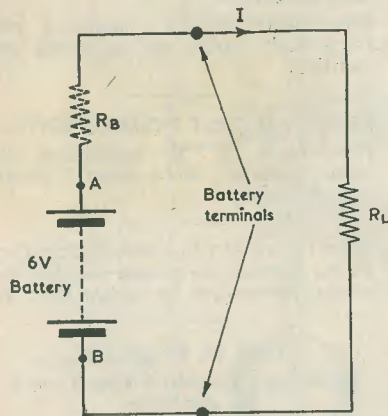


FIG. 1.

G43

Fig. 1 shows a 6V battery connected to a load resistor, R_L . The other resistor, R_B , is the internal resistance of the battery, and

is another of those invisible components which are always cropping up. We can show, however, that it does exist.

Say a short circuit is connected across the battery. For good measure we will make it a 12" x 12" bar of silver, just to show it really is a short circuit. If the resistance of this bar were 0.0001 ohms, and the battery were 6 volts, the current in the circuit should be $6/0.0001=60,000$ amps!

But it is most likely that, on measuring this current, we should find it far less than the expected figure. The reason can only be that an additional resistance has found its way into the circuit and limited the current. Suppose the value we find is 100 amps, then the total resistance in circuit is $6/100=0.06$ ohms. We know that our short circuit is 0.0001 ohms resistance, which is negligible compared to 0.06 ohms; so the internal resistance of the battery is 0.06 ohms.

One further obstacle must be overcome before going on to power considerations. We cannot get at points A and B in Fig. 1 to measure the battery voltage, because R_B is 'in the box'. If our voltmeter has a very large resistance compared to R_B , then only a tiny current will be drawn from the battery, and the voltage drop across R_B will be negligible.

This voltage is called the 'open circuit voltage' of the battery.

Maximum Power

Now suppose that R_L in Fig. 1 were a heating coil and we wished to get a maximum amount of heat from it with the 6V battery, of internal resistance 0.06 ohms. By application of Ohm's Law:

$$I = \frac{E}{R_B + R_L} \text{ amps,}$$

where E is the open circuit voltage of the battery.

The power in R_L is $I^2 R_L$; by substituting the value of I in the former expression for I in the latter, we get:

$$\text{Power } P = \left(\frac{E}{R_B + R_L} \right)^2 R_L \text{ watts.}$$

A graph should help us here. In the expression for power that we have just derived, we can substitute values for R_L , and plot the power in R_L against R_L .

The graph Fig. 2 shows clearly that the power reaches a maximum at $R_L=0.06$ ohms, which is the internal resistance of the battery. We can conclude, then, that to achieve a maximum transfer of power from a source to a load, the load resistance must equal the internal resistance of the source.

However, since our problems are primarily concerned with AC applications, the obvious query now arises—what happens at AC? The first step is to replace the battery by an AC generator. Instead of heating a wire, we will use the power of the generator to drive air about, via a loudspeaker.

Even so, it is not plain sailing yet. The first snag we come up against is the resistance of the loudspeaker. We have no say in this at all. Its resistance has been determined by the manufacturer, as has the internal impedance of the generator. But we know that if the two are very different, we shall not get maximum power into the speaker coil.

The solution to this difficulty is to be found in the transformer. There is no need to go so far as to prove the mechanics of matching with a transformer, but the expression

$$\text{Ratio } n = \sqrt{\frac{R_B}{R_L}}$$

is important to remember. Some figures will illustrate its use.

A common value for R_L is 2 ohms, and R_B may be 50 ohms. The transformer ratio will then be

$$n = \sqrt{\frac{50}{2}} = 5:1.$$

With an AC generator, therefore, the source and load resistors need not be equal, providing that a transformer is used to match them. In this way, a maximum power transfer is obtained. Of course, some losses occur in the transformer, but these need not be large and we needn't worry about them.

The Equivalent Circuit

Fig 3 is worth closer inspection from one standpoint a little removed from matching. Obviously, the loudspeaker has no way of knowing what the source of the driving voltage is. It may be an AC rotary generator, or a valve. It would be reasonable to assume, therefore, that as far as load is concerned, a valve may be represented by a generator.

However, every generator has an internal resistance. So when a valve is represented by a generator, how are we to find its internal

resistance? The answer lies in one of the basic parameters of valves. When a signal is applied at the grid of the valve, the anode voltage, as we already know, fluctuates with the grid signal.

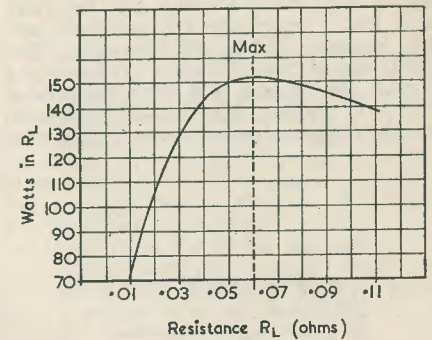


FIG. 2.

G44

To any load that may be connected between anode and cathode, this has the effect of likening the behaviour of the valve to a generator. The anode resistance,

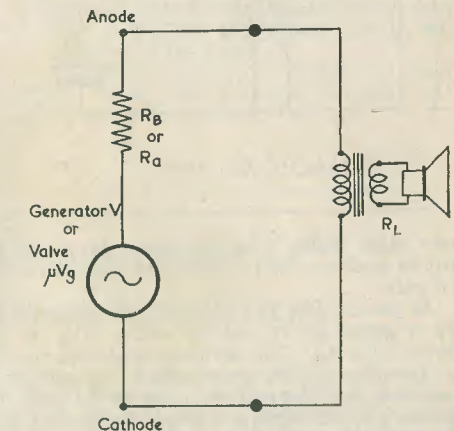


FIG. 3. ILLUSTRATING EQUIVALENCE BETWEEN VALVE & GENERATOR

G45

R_a , of the valve appears to be in series with this generator—virtually, inside the valve. The value of the alternating anode voltage is expressed as 'the amplification factor μ of the valve times the grid signal voltage'.

We have already defined μ as the change in anode voltage for a given change in grid voltage, when the anode current is held constant. R_a is the change in anode voltage for a given change in anode current when the grid potential is held constant.

In the case of a loudspeaker being driven by a valve, then, the circuit may be drawn as in Fig. 3, except that V becomes μV_g and R_p becomes the R_a of the valve. The advantage of this method of showing valve circuits can be seen if a more complicated circuit is studied. Fig. 4a shows the well-known resistance capacity coupling between

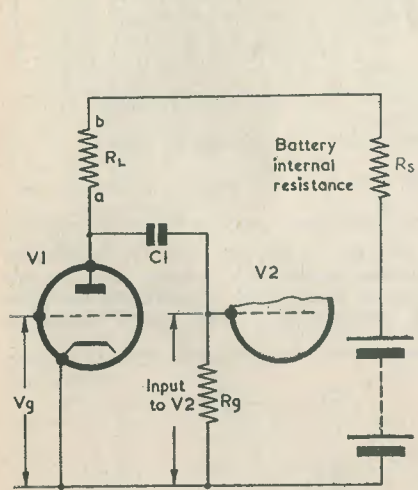


FIG. 4A. RC COUPLING

G46

R_L is of the order of many thousands of ohms, and R_s is probably not greater than 10 ohms. We can safely ignore R_s in relation to R_L , because the signal voltages developed across it will also be negligible compared to those developed across R_L . If R_s is ignored, the HT may be regarded as connected to earth so far as the signal current is affected. Which is just what has been done in Fig. 4b. The point marked b in 4a is connected to earth in 4b.

Other Cases

The valve amplifier is not the only circuit

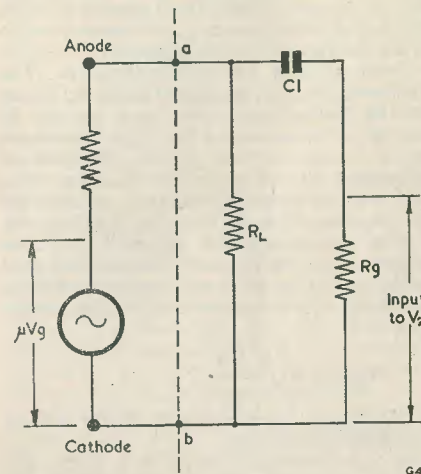


FIG. 4B. EQUIVALENT CIRCUIT OF FIG. 4A

G47

two valve stages. Fig. 4b shows the same circuit re-drawn, and is called the equivalent circuit.

As you can see, the valve has been replaced by a generator, of output voltage μV_g in series with R_a . The network connected to it consists of the anode load, coupling capacitor, and the grid resistance of the next valve. The DC supplies may now be ignored, because the equivalent circuit deals with signal voltages only.

The idea is useful to demonstrate why the DC supplies do not appear. In Fig. 4a the HT supply is a battery of internal resistance R_s , and the current flows around the circuit as shown by the arrows. The battery has no resistance because we have taken it out of the battery box and represented it by R_s . This resistance is therefore added to the anode load R_L . Normally, however,

that can be represented by an equivalent. An interesting case is that of the oscillator.

An oscillator is often required to provide power to a load. The most obvious case is that of the audio oscillator which operates a loudspeaker. The equivalent circuit may be drawn in exactly the same way as in Fig. 3. The oscillator and all its constituent parts are collectively contained in the generator. As we have seen, however, every source of power must have an internal impedance which, once again, is represented by R_p .

The same thing applies with an RF oscillator feeding an aerial. The impedances of both aerial and oscillator must be known and a suitable transformer used to achieve a match. Admittedly, these two factors are difficult to estimate and the match is effected by trial and error. The importance of this

circuit representation is that it enables one to see more clearly how the circuit works, and therefore helps toward a better understanding of the underlying principles.

The equivalent circuit may be used in any case where a source of voltage or power is feeding a network - however complex.

So much for equivalent circuits which, although not strictly relevant to the subject of matching, will later prove a useful reference.

Currents and Voltages

Changing from high to low impedance or vice versa requires a change in the voltages and currents involved, and this is necessary if we wish to have the same power available on either side of the matching circuit as, for example, when using a transformer.

Suppose we wish to transform 1 watt from a $10k\Omega$ source to a 10Ω load. The voltage on the $10k\Omega$ side will be 100V and the current 10mA. On the 10Ω side they will be 3.2V and 320mA. The transformer ratio will be approximately 32 to 1.

The essential thing to notice is that the current increases in the stepped down secondary. So low impedances imply high current and low voltages, and high impedances high voltages and low currents. This is important to remember when wiring a low impedance loudspeaker extension from one room to another. If the gauge of wire used is too small, there will be a voltage drop along the line, and a loss of volume will result.

It is interesting to note that the electrical supply grid is designed to take advantage of the effect of decreased current in high voltage transmission lines.

For example, power is generated at, say, 11kV. For transmission over great distances the voltage is stepped up to 132 kV. The current is stepped down, however, by the same ratio, and the losses in the lines are accordingly reduced.

Receivers

In receivers, matching is important only at one or two points. The aerial may be represented as before by an equivalent circuit of generator and resistance. The generator voltage is the signal voltage developed in the aerial. In this case, however, the series resistance is not quite correct. In actual fact, an aerial has an 'internal' impedance consisting of inductance, capacity and resistance. This has to be matched to the input circuit (normally a tuned circuit) of the receiver. The problem of aerial to input stage matching is a little too difficult and extensive to tackle here and now.

IF transformers are adjusted, not for matching as we have dealt with it, but bearing in mind voltage output and bandwidth. The only IF transformer that feeds a load is the one connected to the rectifier. Due to the fact that the diode takes current when conducting, the IF transformer coupling must be designed to ensure maximum energy transfer from primary to secondary.

In the audio stages, voltage is the important thing and impedances are normally kept as high as possible, so power matching does not enter into the design.

The final match is, of course, between output stage and loudspeaker, which we discussed earlier in this article.

[END

RADIO CONTROLLED MODELS AT THE MODEL ENGINEER EXHIBITION

BOTH IN THE COMPETITION SECTION AND ON THE WATER TANK, radio-controlled models were again one of the most interesting features of "The Model Engineer" Exhibition, held at the New Horticultural Hall, Westminster, which H.R.H. Prince Bernhard of The Netherlands graciously consented to open.

The International Radio-Controlled Models Society were represented on the water tank and had a stand, in the Club centre, where experts were available to discuss problems.

The radio-controlled boats manoeuvring on the tank provided one of the more spectacular exhibits in the Exhibition. Among the models taking part this year was Norman Ough's H.M.S. *Curacao* - this well-known model has been modified so that its guns fire and a smoke screen can be laid.

Entries in the competition section included a radio-controlled Metropolitan Police Launch, *Geebaa III*, a radio-controlled cabin cruiser and transmitter, and a steam-driven fishing trawler which has already had over 100 hours afloat and under radio control. An unusual prototype, *The Royal Barge*, had been chosen for a 40in long model, which has radio-controlled steering; a model which is to have radio control installed later is the *Zwerke Zee*, a Dutch ocean going Salvage Tug. A luxury cabin cruiser model had radio control of clutch and throttle in addition to steering.

Some Observations on 1954 National RADIO SHOW

ALTHOUGH THESE LINES ARE WRITTEN, of necessity, several weeks before the commencement of the Radio Show at Earls Court, they will appear just after its opening, on August 25th. Sufficient advance information has been promulgated by the exhibitors and by the Radio Industry Council to enable a preview to be prepared; and it is considered that this should be of interest and of value both to readers who are able to visit the Show personally and to those who are not.

Twenty-First

This is the twenty-first National Radio Show, and will occupy more space than ever before. There are over a hundred exhibitors, about forty of which are manufacturers of radio and television receivers. The remainder are, mainly, manufacturers of components, sound reproducing equipment, aeriels and valves. The R.I.C. is exhibiting special equipment for industry and commerce, together with radio-controlled models.

The BBC is expected to supply many items of interest; these including the "roving eye" camera - a portable camera and transmitter designed on "walkie-talkie" lines. Other cameras exhibited will be of the commercial closed-circuit class, together with miniaturised models. An arena, intended especially for demonstrations by the BBC of outside broadcast technique, will be a new feature; and particular prominence is being given at the Show to camera and studio equipment suitable for export.

One of the most interesting features of the Show is invariably given by the central control room. This is the glass-walled room which handles and routes all programme material used during the ten-day period over which the Show remains open. The control room this year is situated on the first floor above the Warwick Road entrance, and may be reached by means of the escalator behind the turnstiles at this point. It will handle TV signals emanating in the Show, passing these on for outside transmission over the BBC television network; and it will receive TV signals from Alexandra

Palace in the reverse direction, piping these around the exhibition. It will also deal with productions intended purely for the Show itself, such as interviews at the Celebrity Dais, films, and continuity by the staff of three announcers. The control room will also look after the usual PA and sound receiver channels.

As always, this room is on full view to the visitor, affording a fascinating glimpse of what occurs behind the scenes during an actual telecast. It cannot be denied that a certain amount of the fascination given is provided by the sudden "panics" which occur when something goes wrong at the last minute! However, the fact that the control room, with its complicated equipment and wiring, has been set up successfully in the short time available is always an achievement worthy of praise.

The TV outlets to the stands inside the Show will be working on the Birmingham frequency (Channel 4), this being done to prevent any interference occurring from Alexandra Palace transmissions. The signal level at each outlet will be 1mV at 70 ohms unbalanced. Superimposed along the cable network carrying the Band I programme will be a Band III signal. This will have approximately the same strength as the Band I programme but it will only carry a fixed picture; the picture taking the form of a caption with a suitable background. The provision of a Band III carrier will, of course, allow receivers with "commercial" channels to be examined and demonstrated.

Frequency Modulation

VHF FM receivers and adaptors will also be on show, but, at the time of writing, there is no evidence as to whether they will be in operation. It is to be hoped, for the good of the trade itself, that FM demonstrations will be given, since the public demand for these receivers is bound to be lethargic until convincing evidence of the advantages of FM is made available.

The Television Society has its own stand (No. 205) and will exhibit equipment which has been the subject of lectures in the

Society's programme. These exhibits will illustrate industrial and broadcast techniques, together with circuit developments. Also on this stand will be reprints of important papers read during the Society's recent session, books written by members, and the newly-published Bibliography of Colour Television. Non-members are welcomed to the stand.

Training

Technicians and engineers are always required in the electronic industry. To emphasise the importance of present training for the filling of future establishment, the RIC Technical Training Committee, with the help of the Ministry of Education and representatives from the colleges participating, are staging a special Technical Training Display. This will feature the use and working of test gear, together with information on machine-shop practice, components, circuitry, and glass manipulation (including build-up of valves and CRT's).

The Services will, as usual, be putting on their own exhibits (with recruiting staff at the ready!) "To be especially commended this year is the Royal Navy. The Navy stand will feature, amongst other things, a ship's wireless cabin and part of a shore station, working models of a 3 cm high definition warning radar set, a Decca Navigator, and typical examples of what is most recent in teleprinter and facsimile equipment. An imaginative demonstration of under-water television cameras operated by remote control will be presented, the public having full view of the equipment used since the camera is immersed in a glass-sided tank. Of especial interest will be an electronic clock displayed on a cathode ray tube. Although operated entirely by waveform generators, this gives a picture of the hands and markings found on a normal clock-face.

Manufacturers

As is to be expected, many manufacturers do not give details of their exhibits until after the opening of the Show. However, some advance information has been received and is recorded here.

Mullard have passed on, for instance, preview details of their main exhibits. Of particular interest to readers of the *Radio Constructor* will be a demonstration of the 5-valve, 10-watt, high-quality amplifier described recently in these pages. The amplifier may be heard in Demonstration Room D3A (admission by tickets obtainable from Mullard stand No. 59). Readers whose visits to the Show are inspired by business as well as by interest should also visit Demonstration

Room D29 ("Dealers' Rendezvous"), where Mullard aids to dealers are exhibited.

The Telegraph Condenser Co. will also be to the fore on stands 101 and D17. TCC developments shown here will include six new ceramic condensers designed especially for Band III, Band IV, and other tuners.

TCC have, in addition, produced a new electrolytic condenser - the "Superlytic". This condenser is primarily intended for grid coupling in AF amplifiers, its exceptionally low leakage current allowing this application to be made feasible. A working exhibit illustrating the use of condensers for Power Factor Correction will also be on show.

GEC have also released advance news of their exhibits, one of the more intriguing of which is a mains portable receiver, the BC4644, which is housed in a plastic cabinet. The plastic used is polystyrene; and colour is applied to the inside surface of the cabinet, thus allowing a lustrous appearance to be attained and obviating wear on the colouring material.

The General Electric Co. Ltd. has developed a circuit for a new high quality Amplifier to give realistic reproduction of gramophone records in the home. This Amplifier, designed for home construction, is intended to operate in conjunction with the G.E.C. Metal Cone loudspeaker, for which a special cabinet has been designed, and the two units operating together give a quality of reproduction, of both speech and music, of startling realism and clarity.

The Amplifier, known as the "Osram 912," has been introduced as a practical sequel to F. H. Brittain's *Art and Science in Sound Reproduction*, and a comprehensive booklet describing the wiring in full detail is available from the Osram Valve Department of the G.E.C.

This Amplifier with its accompanying loudspeaker is being shown on the Osram Valve Stand and demonstrated in the G.E.C. Demonstration Room at the show, where the descriptive book "Osram 912" will be on sale, price 3s. 6d.

We hope to publish a report, from the constructor's point of view, in our next issue. [END]

A LIMITED NUMBER of bound volumes of the *Radio Constructor*, Volume 7 only, are available at the special price of £1 1s. 0d. Orders should be sent without delay to the Subscription Manager, Radio Constructor, 57 Maida Vale, W.9.

EDDYSTONE

MODEL '840' AC/DC COMMUNICATIONS RECEIVER



The New Model "840", illustrated above, possesses full Communication facilities and operates from either A.C. or D.C. mains 100/110 and 220/250 volts.


- Seven valve superheterodyne with R.F. stage.
- Frequency coverage 30 Mc/s. to 480 kc/s.
- Gear driven tuning with 140/1 reduction.
- Mechanical bandspread. Accurate re-setting.
- B.F.O. and noise limiter.
- Internal loud-speaker. Headphones jack.
- Robust diecast construction. Rustproofed steel case.
- Suitable for tropical service.
- Weight 30 lbs. Size 16½" x 10½" x 8½" high.

List Price (in U.K.) £45

Exempt from Purchase Tax

PLEASE WRITE FOR FULL SPECIFICATION TO THE MANUFACTURERS:

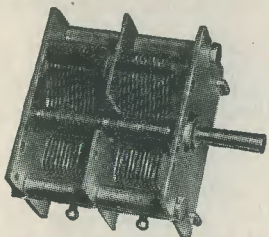STRATTON & CO. LTD., EDDYSTONE WORKS, BIRMINGHAM, 31



M.G. GANG CONDENSER

M.G. Gang Condenser available as 1, 2 or 3 gang, 490 p.F. nominal capacity with Cadmium plated steel frame, aluminium vanes; matched and standardised to close limits. Low loss non-hygroscopic insulation. Supplied with trimmers if required. Other capacities available. Write for further details. Prices 9/3, 14/-, 18/3. Please write for our list of condensers and drives

JACKSON BROS

(London) LTD

KINGSWAY, WADDON CROYDON Surrey
Telephone CROYDON 2754-5
Telegrams WALFILCO, SOUPHONE, LONDON

IKOPATENTS

LTD.

Managing Director

E. G. O. ANDERSON

Consultants

- RADIO
- TELEVISION
- ELECTRONICS

17 CRISP ROAD W6
RIVERSIDE 2678

NEW!


RADIO & T.V. OUTFITS

LEARN THE PRACTICAL WAY

Specially prepared sets of radio parts from which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at very moderate cost.

EASY TERMS FROM £1 A MONTH

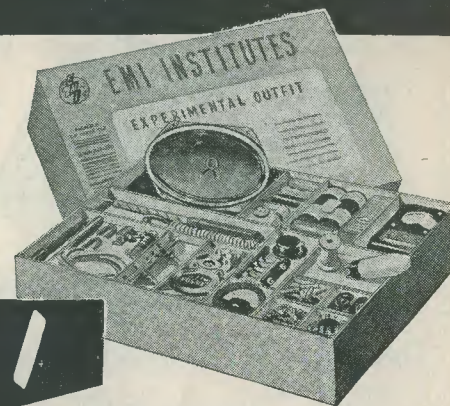With these outfits, which you receive upon enrolment, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to complete Radio and Television Receiver Testing and Servicing.




BEGINNER'S RADIO OUTFIT

— For carrying out basic practical work in Radio and Electronics, from first principles and leading to the design and building of simple Receivers.

ALL EQUIPMENT SUPPLIED IMMEDIATELY AND REMAINS YOUR PROPERTY

ADVANCED RADIO OUTFIT

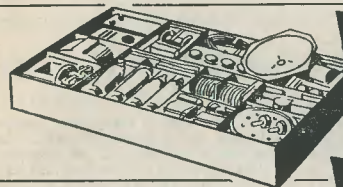
— With this equipment, you are instructed in the design, construction, testing and servicing of a complete modern T.R.F. Superhet Radio Receiver.



2

TELEVISION — With this equipment you are instructed in the design, construction, servicing and testing of a modern high quality Television Receiver.

3

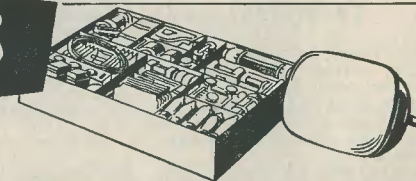

OTHER COURSES WITH EQUIPMENT INCLUDE:

MECHANICS • ELECTRICITY
CHEMISTRY • PHOTOGRAPHY
CARPENTRY

ALSO

DRAUGHTSMANSHIP • COMMERCIAL ART
AMATEUR S.W. RADIO • LANGUAGES • ETC.

POST THIS COUPON TODAY

FREE PROSPECTUS

Please send me your FREE book on Practical Courses.

Subject(s) of interest.....
To: E.M.I. INSTITUTES, Dept. 179x, 43, Grove Park Road, Chiswick, London, W.4.

NAME.....


ADDRESS.....

1/9.....

E.M.I. INSTITUTES

The only Postal College which is part of a world-wide industrial Organisation

SPECIAL . . . Radio Show OFFER

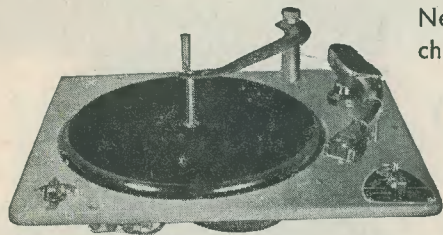

New Collaro 3RC/531 3-speed auto-changers with the famous Studio 'O' high fidelity turn-over crystal pick-up head. New and complete in makers original cartons, very limited number and cannot be repeated

OUR SPECIAL PRICE £10 : 10 : 0

USUALLY £15 3 10

CARRIAGE 5/-

START BUILDING THAT SUPER RADIOGRAM TODAY WITH ONE OF THESE UNITS

HOME RADIO OF MITCHAM

187 LONDON ROAD, MITCHAM, SURREY Telephone MIT. 3282
Open every day including Saturday until 6.30 p.m. (Wednesdays 1.0 p.m.)

MONEY BACK GUARANTEE **DUKE & Co** Tel: GRA 6677 CWO OR COD
621 ROMFORD RD. LONDON, E.12.

TV TUBES GUARANTEED

TV TUBES. £5 12". Most types from stock. Insured carriage, 15/6. 3 months guarantee. Your enquiries invited.

SPOTLIGHTS, 8/9. Butlers, Ex-W.D. Pre-focus fitting, easily adapted. 7½" diam., 6½" deep. Post 1/3.

BULBS for above, 6 volt 36 watt. 12 volt 48 watt, 4/6 each.

SIDLIGHTS, 1/9, infra-red glass. Ideal tail lamps (orange glass). New. Ex-W.D. Post 9d.

AMPLIFIERS, 9/6. Ex-W.D. Contain E.F.36 valve, 2 trans., 400 ohm relay, v/control, various conds., resistors, etc. Case measures 5" x 5". FREE drawings. Post 1/6.

METAL RECTIFIERS, 8/9. TV Type. Salvage. Guaranteed, 250 volt at 250 mA, 8/9. Also 250 volt at 60 mA, 8/9. New 250 volt 250 mA, 12/9. All wave. Post 1/-.

DUNLOPILLO. Ex-Coach seats, 37/6. 34" x 16" x 4" thick. Complete with back. Carriage 4/6.

H.T. BATTERIES, 3/9. 60v., 90v., portable, 7/9. 90v x 1½v, 5/9. Post 1/9 each.

L.T., 4½v, 1/- Post 6d.

ACCUMULATORS. 2v, 45 ampere, 7/9. Post 2/3.

BURGLAR ALARMS, 3/9. To clear. Brand new. Self-contained unit. Made by Truvox. Consists of bell and trip device mounted in metal cover. Works off 4½ volt battery. Post 1/3.

SEND STAMP ONLY FOR 1954 CATALOGUE

Still the best TV Kit

"VIEW MASTER" TELEVISOR

A sound design backed by leading component manufacturers. All instructions and diagrams can easily be followed. Chassis are ready punched and all tiresome and difficult work eliminated. Send 7/6 now for the Constructional Envelope with 34-page fully illustrated manual and large scale plans. Please state for which station. Revised price list of View Master components post free. View Master "Big Picture Conversion" Constructional Envelope, 3/6.

Another Winner

"SOUND MASTER" TAPE RECORDER

Constructional Envelope with manual, by W. I. Flack (designer of the famous "View Master") and full-scale diagrams for building in easy stages with ready-drilled chassis a first-rate tape recorder which will faithfully record the voices of your family, friends and radio. The recordings can be kept or erased at any time when required and the tape used again. Price 6/6. Complete list of parts post free.

Illustrated Catalogue free on request
We stock Thousands of Radio & TV Components
WE HAVE BEEN ESTABLISHED 20 YEARS AND ARE ONE OF THE ORIGINAL PRE-WAR MAIL ORDER BUSINESSES

SOUTHERN RADIO & ELECTRICAL SUPPLIES

SORAD WORKS
REDLYNCH, SALISBURY
Telephone: Downton 207

CHASSIS AND COVER. Steel chassis 7" x 10" front panel with handles 9" x 8", suitable for mounting new front panel as existing one is over-drilled. Cover 8" x 7½" x 10½" deep. In very clean condition. Price 3/-, post 2/1.

SMALL D.C. MOTORS. Size 2½" long x 1½" wide x 1½" high, frey fitted ⅜" shaft, operates from 6-12 volt, weight 11 oz. As new 15/6, post 1/3. 12-24 volt 9/6. We have sold many of this 12 volt type to model boat builders for use in boats up to 3" 6" long.

GYRO ANGLING UNITS. This unit contains a 24 volt reversible motor, worm and spur reduction gearing to a shaft dog which rotates approximately 7 r.p.m., also fitted with pulsing device for operating electrically a repeater compass. This unit is suitable for rotating aerial arrays, etc., since by using this unit in conjunction with the repeater compass, exact direction of the aerial can be ascertained by reading from the remote indicator. Price 20/-, post 2/-.


PILOT'S REPEATER COMPASS (suitable for working with above unit—Gyro Angling Unit). Pilot's repeater compasses or observer's repeater compasses, containing 24 volt repeater motor. Ref. number 6B/742. Brand new, price 12/6, post 1/6.

UNISELECTORS. Siemens miniature 3 banks of 10 contacts. 3 sets of wipers set at 120 degrees. Coil resistance 10 ohms. Stripped from new equipment. Price 27/6, post 1/6.

ARTHUR T. SALLIS (RC)
93 NORTH ROAD, BRIGHTON
SUSSEX
Telephone Brighton 25806

Enjoy the Thrills of ALL Wave Radio at a Down-to-Earth Price

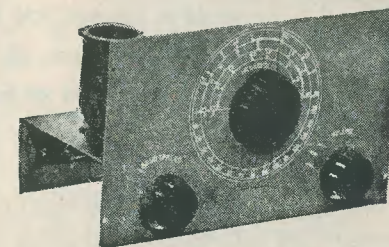Build this Set for 30/- from our Components.



- ★ Covers 10-100 metres.
- ★ Picture diagram and instruction for beginners.
- ★ World-wide reception.
- ★ Assembling time 1 hr.
- ★ Low drain valve.
- ★ This 1 valve S.W. receiver can be built from our list of components for 30/-, including valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list to:-

R.C.S. PRODUCTS (RADIO) LTD
11 OLIVER ROAD, LONDON, E17. Mail order only

YOU CAN RELY ON US

Radio and TV Component Bargains

VALVES

6V6G 7/6, 6X5G 7/6, 6X5gt 7/6, 6SN7 9/6, EM34 7/6, 6U5G 7/-, ECC40 9/-, EL42 8/-, ECC81 9/6, 6K7G 7/6, 6K7(metal) 8/-, KT63 7/6, EF54 6/-, EF50 7/-, EL32 7/6, 12A6 7/-, 12SC7 6/6, 6J7G 7/6, 76 6/6, 12J5 4/6, EB34 3/6, EF36 6/6, 6B4 7/6, 6B8 7/-, 6K8G 8/6, 12K8gt 8/6, 1T4 7/6, 1S5 7/6, 1R5 8/6, 3A4 7/6, R3 9/-, 35Z4 7/6.

TRANSFORMERS TV

WB107 Line 32/6, WB106 Frame 25/6, WB103 Heater 42/-, WB103A Heater 52/6, Denco WA/LOT Line 42/-, WA/FMAI Frame 21/-, WA/FBT1 F/Blocking 16/-, Allen LO308 Line 40/-, F0305 21/-, BT314 15/-, and Haynes (when available) TV Mains Trans. 350-0-350v 250mA, 5v 3a, 6.3v 8a, 6.3v Tapped 2v at 2a 67/6 Fully Shrouded.

VOLUME CONTROLS

5K, 10K, 25K, 50K, 100K, 250K, 500K, 1mg, with Switch 4/-, Less S/W 2/6, DP Switch 5/6, Wirewound Preset from 100Ω to 30K 3/2 each. Standard 3w Colvern 6/4.

Next Door South Ealing Tube Station. 6 o'clock, 1 p.m. Wed.

82 SOUTH EALING ROAD
LONDON W5 Telephone EAL 5737

TRANSFORMERS

Speaker Trans. Pentode O/P 4/6. Midget Mains 3/9, Battery Standard 4/-, Super-Midget for P/Portables 5/-, Charging Transformers 2v, 6v and 12v charging at 2a 19/6, 1v, 2v, 4v, 6v, 10v, 15v, 20v, 30v, up to 15v at 4a 30v at 2a 22/6. Midget Mains Transformer 60mA 250-0-250v 6.3v at 3a, 4v 2a 21/6. Elstone SR/250 or SR350 28/6.

SOLDERING IRONS

Tyana Pencil Bit 14/11, Adcola Pencil Bit 25/6, Detachable Bit 33/6, Henley Small Pencil Bit 19/8, Solon Standard Pencil 25/4, Oval Bit 23/8, Elements for Henley, Solon, Tyana in stock. Adcola Iron Shield 10/6. Multi-core Solder 18swg 5/- cartons. Flux 1/6.

COILS

Osmor Full Range 4/- each, Weymouth 'H' Type 3/9, 'K' Type 5/-, CS3W3 12/3 per pair, CT2W2 10/- per pair, Denco Maxi-Q Midget Chassis or Plug-in Type 3/11 each. Full Range of Osmor and Weymouth Coilpacks.

IF TRANSFORMERS

Denco 1FT11 12/- pair, P4(Weymouth), 15/- pair, Wearite M800 21/- pair, 501/502 20/- pair.

Q MAX CHASSIS

PUNCHES
½", ¾", 1", 1¼", 1½", 1¾", 2", 2½", 3", 3½", 4", 4½", 98", 98½", 99", 99½, 100". (All inclusive of keys).

RESISTORS

¼w ¼w 4d., 1w 8d., Midget Type 'T' ¼w max 6d., Type 'R' 1watt max 8d. Full Range. 2% High Stab. 1/6 each (Range 100 ohms to 2mg). Wirewound max 7 watts 2/3, 10 watts 2/9 (33 ohms to 10K only).

A BARGAIN

New Tubular 8mfd 500v Wire-End Electrolytics 1/11 each. 2 for 3/6.

Orders Despatched Promptly, C.O.D. by Return (over £1). Please add P/Pkg. fee up to £1-1/- £2-1/6. Over £2 Free.

Catalogue of Surplus Ready soon 6d. each. Catalogue of New Proprietary Components (250 Illustrations, 70 Pages) 3/- Returnable on Order over 30/-

RADIO SERVICING CO

HENRY'S

RADIO LIMITED

CRYSTAL MICROPHONE INSERTS

8/6
POST FREE
Ideal for tape recording and amplifiers. No matching transformer required.

F.M. FEEDER UNIT

Denco's last word in Audio. Complete kit £6 7/6
Fully assembled and aligned at £8 10 0
Alignment service 7/6

PYE 45 Mc/s STRIP
Type 3583 Units. Size 15" x 8" x 2". Complete with 45 mc/s Pye Strip, 12 valves 10 EF50, EB34 and EA50. Sound and vision can be incorporated on this chassis with minimum space. New condition. Modification data supplied. Price £5 carriage paid

INDICATOR UNIT TYPE 182A. This unit contains VCR517C Cathode Ray 6" Tube complete with Mu-Metal Screen, 3 EF50, 4 SP61 and 1 5U4G valves. Offered Brand NEW (less relay) in original packing case at 67/6, plus 7/6 carriage. Demonstration Model now on view, completely modified as per the article now being featured in this issue. All components for conversion can be supplied. Kit of modification parts and "182A" Unit £8 18 6 carriage paid

CATHODE RAY TUBES

VCR97 40/- car. 2/-
VCR517C 35/- car. 2/-
VCR139A 35/- car. 2/-
Guaranteed for TV 3BP1 30/- car. 2/-

T.C.C.—1 5/7000 v. wkg. Type CP58QO. Bakelite Case, 7/6 each

We have 20,000 American & B.V.A. valves in stock

ALL VALVES NEW AND GUARANTEED

1R5 7/6	6SK7GT 7/6	EY51 12/-	VR105/30
1S4 7/6	6SL7GT 9/-	EK32 6/6	8/6
1S5 7/6	6SN7GT 9/-	EF91 9/-	VR150/30
1T4 7/6	6SC7 10/-	EL33 10/-	8/6
1C5 8/-	6V6GT 7/6	EL32 7/6	CK510AX
3A4 9/-	6AG7 12/6	EF50 Red	5/-
3V4 7/6	12A6 7/6	Syl. 10/-	DI 2/-
354 7/6	12K7GT 8/6	EF50 5/-	AC6PEN
5Z3G 8/6	12K8GT 8/6	SP2 8/6	6/6
5U4G 8/6	12Q7GT 8/6	VP2 8/6	AC5/PEND
5Z4G 8/6	12SA7GT	TDD2A 8/6	D 12/6
6A7G 8/6	8/6	DK40 9/-	PEN25 6/6
6AC7 6/6	12SQ7GT	UL41 9/-	PEN46 7/6
6A8G 8/6	8/6	UY41 9/-	QP25 6/6
6AM6 9/-	12SJ7 8/6	4D1 4/-	SP61 4/-
6B8 7/6	12SK7 8/6	8D2 4/-	SP41 4/-
6C5GT 5/-	12SR7 7/6	9D2 4/-	HL23/DD
6C6 6/6	25Z6GT 8/6	D41 5/-	VP23 6/6
6D6 6/6	25Z5 8/6	KT2 5/-	VP41 7/6
6F6G 8/6	35Z4GT 8/6	U52 8/6	U22 8/6
6G6G 6/6	35Z5GT 8/6	U19 10/-	ATP4 4/-
6H6GT 5/-	25A6 8/6	Y63 8/6	TP22 8/6
6I5GT 5/-	35L6GT 8/6	MU14 8/6	TH233 10/-
6J6 9/-	50L6GT 8/6	PL81 11/-	41MP 7/6
6AK5 9/-	42 8/6	PL82 10/-	42SPT 6/-
6K7G 6/6	43 8/6	PX25 12/6	215SG 4/-
6K7G 6/6	75 8/6	PY81 10/-	MS/PEN 7/6
6K8G 9/-	80 8/6	PY82 8/6	MS/PENB
6L6G 10/-	866A 15/-	KT33C 10/-	7/6
6U5 7/6	TZ40 37/6	KT66 12/6	VT501 7/6
6U5G 7/6	931A 50/-	GU50 12/6	AC/PEN
6N7GT 7/6	EA50 2/-	XP2V 4/-	(7) 10/-
6Q7GT 8/6	ECH35 12/-	XH (1.5) 4/-	PENDD 10/-
6SJ7GT 8/6	EF54 6/-	VU111 4/-	4020 12/6
6X5G 8/6	EB34 3/6	VU133 4/-	FC13C 10/-
6SA7GT 8/6	EBC33 8/6	VU120A 4/-	VP4(7) 8/6
6SQ7GT 8/6	EF36 6/6	QP230 8/-	ID5 8/6
6SG7 7/6	EF39 6/6		

MORSE PRACTICE BUZZER

Complete with tapper and 4 volt buzzer on baseboard, 6/-, brand new. Post paid

200 kc/s, 2-pin (U.S.A.)	... 10/-
465 kc/s, 2-pin (U.S.A.)	... 10/-
500 kc/s, 2-pin (British)	... 15/-

Send postage for new '54 comprehensive 23-page catalogue
Open Monday to Sat. 9 a.m. to 6 p.m. Thursday 1 p.m.

5 Harrow Road, Paddington, W.2

Telephone Paddington 1008/9, 0401

SMALL ADVERTISEMENTS

Reader's small advertisements will be accepted at 3d per word, minimum charge 2/- . Trade advertisements will be accepted at 8d. per word, minimum charge 6/- . If a Box Number is required, an additional charge of 1/- will be made. Terms: Cash with order. All copy must be in hand by the 10th of the month for insertion in the following month's issue.

PRIVATE

THREE BARGAINS. Goodmans 12" Axiom twin-cone speaker, baffle mounted on 3' x 2'6" Oak 1 1/2" thick, with stand, £6 10s 0d. Portable Oscilloscope, black crackle finish with fly back suppression, home built but engraved as professional job, £8 10s 0d. Portable AC/DC Amplifier, in Rexine case with 10" speaker. Mic and Gram inputs, isolated chassis, push-pull, 6-8 watts output, £4 10s 0d. Jepson, 65 Rutilth Avenue, Bedford Park, London W.4.

FOR SALE Cossor Signal Generator, Model 3343, £5. Homelab Signal Generator, £4. Buyers collect. 18 Derwent Avenue, Edmonton, London, N.18.

UNUSED Marconi 15" console TV cabinet with doors, for sale, £12 10s 0d. Also Ferranti 9" table model, used, £1 10s 0d. 86 Cumberland Road, Hanwell, London, W.7.

NEW VALVES All Guaranteed. PEN383, EY51, 9/-; ECL80, EF80, PY81, 8/6; PY82, 10F1, 6Q7, 12K8, 7/6; 6U7, 6J5GT, VR91, 6AG5, 6SK7, 5/6; 6H6, VR54, VR65, 2/6. Also used but guaranteed, Z77, U404, B36, 4/- . W. Fewell, 308 Nisbet House, Homerton, London, E.9.

FOR SALE 1224 Receiver, un-modified, perfect condition, £4. Kitching, 47 Woodland Drive, Mansfield, Notts.

TAPE DECK Wearite Model A, latest type, brand new and boxed, complete with reel of unused tape, £30. Box No. D132.

AMATEUR SELLING UP. Everything must go. SAE for details of bargains—Resistors, Condensers, Valve Bases, Transformers, Relays, Oddments, Valves of most types. For the VHF enthusiast, a remote controlled 8 channel selector for Transmitter and Receiver. Please state which list. Golding, Sandyend, St. Ives, Ringwood, Hants.

MAGAZINES 120 Practical Wireless, 1943 and on; 70 Wireless World, 1948 on; 39 Practical Television, recent. Offers to Berry, 6 Arbory Avenue, Moston, Manchester.

FOR SALE Television components including main Viewmaster components, also table cabinet, value £26, accept £10. Candish, 17 Peel Drive, Hendon, London, N.W.9.

FOR SALE Technical Instruction for Marine Radio Officers by Dowsett and Walker, 9th Edition, as new, £1 12s 6d. Fry, 11 City Walls, Chester.


VALVES Selection of new miniature types, 6/- each. Box No. D130.

SERVICE SHEETS for hire or sale, over 2,000 models Radio and Television. SAE enquiries. W. Gilbert, 24 Friethville Gardens, London, W.12.

PREMIER (HM) long range S & V Chassis. E.E. Sync and time bases. Two power packs and E.H.T. Trans. New unused Brimar C12D, mask, glass, focus, L and F coils. Lined up, power packs require completion. 4 chassis, 20 valves (new), data. First £29 10s 0d carriage paid. 3 S motor, ACOS GP20/ plus LP head. Motor rumbles slightly. £4. Box No. D131.

[continued on page 127]

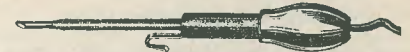ADCOLA (Regd. Trade Mark) SOLDERING INSTRUMENTS



Reg. Design No. 860302 (British, U.S. and Foreign Patents)
Designed for wireless assembly and Maintenance
Supplied for all volt ranges from 6/7v to 230/250v 3/16" Dia. Bit Standard Model 25/6
Sole Manufacturers **ADCOLA PRODUCTS LTD.**
Sales Office and Works Cranmer Court, Clapham High St. London SW4 (MAC 4272)

ALL ITEMS POST PAID UNLESS OTHERWISE STATED
VALVE BARGAINS. 1R5, 1S5, 1S4, 3V4, 354, 3Q4 6/- 1T4 5/-, 6V6 6/-, ECL80 7/- .
SPEAKERS. All P/M all 3 OHM, 5 inch 11/6. 6 1/2 inch 12/6. 7 inch elip. 13/6.

CABINET BARGAIN. Ideal for that set to make up and sell or for a spare. Brand new polished walnut veneer finish 16/6. With TRF or S/het chassis, dial, back plate and 3 knobs 19/-, post 1/-.

COMPLETELY ASSEMBLED ready to work 4 valve + recs/het L/M wave, 200-240 volt A/C chassis. To fit our 16/6 cabinet with valves and 5-inch SPEAKER £5 17 6 3 valve plus rec TRF for the 16/6 Cabinet L/M wave 200-240 volt A/C £4 7 6.

MISC. BARGAINS. GERMANIUM DIODES 1/3. 11b. reels resin cored solder 6/9. Morse Key 3/-.

A. BLACKBURN, CENTRAL HOUSE, BURY WHARF, BURY ST., RUISLIP, MIDDLESEX

WORLD RADIO HANDBOOK

1954 Edition

now available

8s. 9d. post paid

DATA PUBLICATIONS LTD
57 MAIDA VALE LONDON W9

TELETRON SUPER INDUCTOR COILS

MINIATURE DUST CORE TYPES

TRANSISTOR coils of high Q. Triple wound for max. selectivity. HMX. 200/550M., 3/- . HLX. 1000/2000, 3/6. HAX. used with Xtal diodes, as "Radio Head" in Recording Amplifiers, 3/- . TRF. A/HF. Matched pairs, 7/- (as illustrated).



Hartley coils for "R.C." Mod. Osc.

Stamp for complete list and circuits.

THE TELETRON CO.
266 NIGHTINGALE RD., LONDON, N.9. HOW 2527

Prices slashed at Clydesdale

TI154B TRANSMITTER UNIT
Medium/high powered for C.W.-M.C.W. R/T 3 ranges
10-5.5 mc/s. 5.5-3 mc/s, 500-200 kc/s. Complete with
4 valves, etc., in metal case 14" x 16 1/2" x 8 1/2". External
power supply required.

ASK FOR **39/6** each CARRIAGE
B/E5A 7/6 EXTRA

VISUAL INDICATOR TYPE I (Ref. 10Q/2)
Dual reading left/right. D.F. Meter for R1155, 2 3/8" scale
overall. Dim. 3 1/2" x 2 1/2". In used condition.

ASK FOR **12/6** each POST
B/H862A 7/6 PAID

BC-456 SPEECH MODULATOR UNITS
Part of SCR-274-N "Command Equipment" (U.S.A.
made). Complete with valves 1625 and VR150/30,
transformers, relays, etc., less dynamotor. Overall dim.
10 1/2" x 7 1/2" x 4 1/2". Loose stored.

ASK FOR **17/6** each CARRIAGE
B/E42 7/6 PAID

Available, BC-456, as above, in original carton.
ASK FOR **27/6** each CARRIAGE
B/E42A 7/6 PAID

STAINLESS STEEL AERIAL WIRE
7/015 in reels of approx. 1,600 ft., made by Temco.

ASK FOR **25/-** per reel CARRIAGE
B/E143 7/6 PAID

PLEASE NOTE. Carriage and Postal Charges refer to the
U.K. only. Overseas freight, etc., extra.

Order direct from: Telephone SOUTH 2706/9
CLYDESDALE SUPPLY
2 BRIDGE STREET GLASGOW C.5. CO. LTD.

RADIOVISION

4 PRAED STREET
LONDON W2
Telephone AMB 4670

We have a very large selection of
Valves and Spares at the Lowest
Possible Prices

We have a Large Selection of used but
perfect C.R. Tubes. Every Tube carries
a 6 week guarantee. Callers can see picture
on premises.

9"	£4 0 0
12"	£6 0 0
15"	£8 10 0

Post, Packing and Insurance, 10/-

URGENTLY WANTED

COMMUNICATION RECEIVERS TEST
EQUIPMENT. RADIOS—and TELE-
VISION SETS, TAPE RECORDERS.

Best Prices Given

Phone or Call

SMALL ADVERTISEMENTS

continued from page 125]

SALE. Transformers: 350-0-350 at 500mA, multitap
heater winding, 30/-, 200-0-200 at 50mA, two
2v heater windings, 15/-, Headphones: 2000 ohm
Sterling, 12/6. Ex-W.D. moving coil, 10/-, Meters:
50mA M/C, 2" sq., 5/-, I.F. Transformers: 465
midget, per pair, 7/6. 465 standard, per pair, 5/6.
Variable Capacitors: Eddystone Type 832, 2,500v,
50-50 transmitting, new, 20/-, 30pF, 5/6, .0005, 7/6.
Interstage Transformers: Heavy duty, 5/-, Minia-
ture, 3/6. Output Transformers: 7000 ohm, 48-1
ratio miniature, 3/6. For personal receivers, 3/6.
Crystals: 3,500 kc/s (band edge marker) octal base,
15/-, 7097 kc/s GEC 3" spaced pins, 12/-, Speakers:
Extension, in polished cabinets 12" x 12" x 6", 40/-,
Vitavox "A" M/C Mike, with desk stand, oxy,
black, 90/-, Black crackle carrying case 12" x 9" x 6 1/2"
leather handle, cover over panel end, Ideal portable
gear, 15/6. Capacitors: TCC plug-in elect. 16 x 16,
new, 7/6. Hunts 32uF 500 v.d.c. at 3/6. Charging
transformer and metal rectifier 6v, 2 amp at £1.
Vibrator unit Type 244; 130v 30mA, 6.3v 2 amp,
6v input, £1. G.E.C. Crystal and holder 7097 kc/s,
10/-; Q.C.C. Crystal and holder 7171 kc/s, 10/-,
"East Keal," Romany Road, Oulton Broad, Suffolk.

NEW RADIO COMPONENTS for sale at half price.
Send SAE for lists.—Box No. D133.

TRADE

CABINETS five glossy sides, black or brown, stand
any position. For Crystal sets, Test Meters, etc.
5 1/2" x 4" x 3", 3/6. 5 1/2" x 6" x 3", 5/6. 5 1/2" x 8" x 4",
7/6. Postage 1/-. Wilkinson, 42 Frances Road,
Windsor, Berks.

FOR F.M. TUNER UNIT (July issue), Wound Coil
Sets, 15/-; Fully Punched Chassis, 8/6. C. O.
Preston, Healey Lane, Batley, Yorks.

OSCILLOSCOPE TRANSFORMERS 10/-, 12/24v.
AC/DC Motors 15/-, Hand Microphones 5/-.
Valves from 1/6, 1155 receivers £6. Aircraft Com-
passes £1. List 2 1/2 stamp. Pimble, 66 Liverpool
Road, Newcastle, Staffs.

"**GLOBE KING**" (Regd.) Miniature Single Valve
Receiver gets real DX. Amateur Radio enthusiasts
should send for free copy of interesting literature
and catalogue (enclose stamp for postage). Write
to maker: Johnsons (Radio), 46 Friar Street,
Worcester.

BLUEPRINTS. High Gain 10 Metre Converter,
with a de-luxe circuit comprising EF91 RF stage,
ECC91 double triode mixer and oscillator, EF92
IF amplifier, with stabilised voltage supply via a
7475, 1s 8d post free with full instructions, Data
Publications, 57 Maida Vale, London, W.9.

KENDALL AND MOUSLEY. Manufacturers of
Laboratory Equipment, chassis and instrument
cases, also suppliers of B.V.A. valves, Radio and
T.V. components, 99 Dudley Port, Tipton, Staffs.

COILS, COILS, COILS. We can supply coils for
all frequencies, RF Chokes, Filters, etc. Coils
wound to specification—send details for estimate.
Send SAE for circuits and Data. The Teletron
Co., 266 Nightingale Road, London, N.9.

I.P.R.E. PUBLICATIONS, 5,500 Alignment Peaks for
superhets 5/9. Sample copy *The Practical Radio
Engineer* 2/-. Membership examination particulars
1/-, Syllabus of TV and Radio Courses free and
post free. Secretary, I.P.R.E., 20 Fairfield Road,
London, N.8.

METALWORK. All types cabinets, chassis, racks,
etc. to your own specification. Philpott's Metal-
works Ltd. (Dept. R.C.), Chapman, Street, Lough-
borough.

[continued on page 128

VALVES—OVER 3,000 IN STOCK

6AM6, EF91, 8D3, Z77, W77, EF92, 9D6, 6AL5, D77,
EB91, EAC91, 5/-

12AT7, 6BR7, 6CH6, 6BW6, 6F33, 85A1, 85A2, EC91,
12AX7, 7/6.

SKILLMAN FRANCHISE STREET, WEYMOUTH

NEW! RADIO AND TELEVISION COMPONENT CATALOGUE

available on request to

J. T. FILMER

MAYPOLE ESTATE, BEXLEY, KENT
Telephone: Bexleyheath 7267

REP HIGH GAIN COILS

Dual Range Miniature Crystal
Set Coil with Circuit. Type
DRX1 ... 2/6


Dual Range Coil with Reaction
with 2 mains and 2 battery
Circuits. Type **DRR2** ... 4/-

Matched Pair Dual Range
T.R.F. Coils with Reaction;
with battery and mains circuits.

Type **DRM3** ... Pair 8/-

All Coils wound on Low-loss Formers
* Individually Tested and Guaranteed

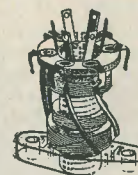* Post 3d. on all Orders * Trade Supplied
RADIO EXPERIMENTAL PRODUCTS LTD
33 MUCH PARK STREET COVENTRY



VALVES NEW TESTED AND GUARANTEED

1A4	8/6	6BS7	8/6	8D3	7/6	EBC33	8/6
1A7GT	12/6	6F8G	8/6	12AH7	7/6	ECH35	11/6
1B4	8/-	6G6G	5/9	12AT6	8/6	ECL80	12/6
1C5GT	11/6	6J5G	5/-	12A7	8/6	EF22	7/6
1E7	9/6	6I7G	8/6	12AU7	8/6	EF37A	15/-
1H5GT	10/6	6K6	8/6	12AX7	6/9	EF36	7/6
1N5GT	10/6	6K7G	5/6	12Q7GT	8/6	EF39	6/6
1R5	7/9	6K8G	8/6	25A6	7/6	EF80	10/6
1S5	7/9	6K8GT	8/6	57	8/6	EF91	7/6
1T4	7/9	6L6G	9/6	58	7/6	EF92	8/6
354	7/9	6N7	6/9	5763	8/6	EL32	7/6
3V4	7/9	6Q7G	8/6	807	8/6	EL91	10/6
5Y3GT	9/6	6Q7GT	8/6	954	2/6	EZ35	8/-
5Z4G	8/6	6S17	8/6	1625	10/6	EZ40	9/6
6AG5	6/9	6SK7	8/6	9006	5/6	GZ32	15/-
6AM6	7/6	6SL7	9/9	AZ31	10/6	KT32	8/6
6AT6	8/6	6SN7	8/6	DAF91	7/9	KT33C	8/6
6BE6	8/6	6SS7	6/9	DF91	7/9	ML4	7/-
6BVY6	8/6	6U7G	8/6	DL92	7/9	PL82	10/6
6B7G	8/6	6V6GT	8/6	DL94	7/9	PL82	10/6
6B8	7/6	6V6G	8/6	EA50	2/-	PY82	10/6
6BB6	7/6	6X4	8/6	EAC91	6/-	VR91	8/6
688G	8/6	6X5GT	8/6	EAF42	9/6	U50	9/6
6BR7	8/6	7H7	8/6	EB91	6/6	6FG6	8/6

MATCHED PAIRS 6V6G and gt, 17/-; 6F6G, 17/-;
KT66, 25/-; 6G6, 12/-; 6J5G and gt, 9/6 per pair.
6K8G, 6V6G, 6Q7G, 6K7G, 5Z4G, 34/6 per set.
1R5, 1T4, 1S5, 354, 30/- per set.

ELECTROLYTIC CONDENSERS
2 mfd, 350vw T.C.C., 1/3; 8 mfd, 350vw, T.C.C., 1/6;
8 mfd, 450vw B.E.C., 1/9; 32 mfd, 450vw, B.E.C., 4/6;
8+8 mfd, 450vw B.E.C., 3/9; 8+16 mfd, 500vw, Dub.,
4/9; 8+8 mfd, 500vw, Deb., 4/-; 32+32 mfd, 275vw,
B.E.C., 4/-; 12 mfd, 50vw, T.C.C., 1/3; 20 mfd, 12vw,
T.C.C., 1/-; 25 mfd, 25vw, T.C.C., 1/3.

R. COOPER

32 SOUTH END CROYDON SURREY
Telephone CROYDON 9186

OSMOR radio products limited

418 BRIGHTON RD. SOUTH CROYDON, SURREY
Dept. R.C.16 Telephone CROYDON 5148/9

COILPACKS. A full range
available for Superhet and T.R.F.
Mains or Battery. Size only 1 1/2"
x 3 1/2" x 2 1/2". Ideal for the reliable
construction of new sets, also
for conversion of the 21 RECEI-
VER, TR 1196, TYPE 18, WAR-
TIME UTILITY and others.


SEPARATE COILS 4/- each
A full range available for all popular
wavebands and purposes.

*Only lin. high. *Packed in
damp-proof containers. *Vari-
able iron-dust cores. *Fitted
tags for easy connection. *Low
loss Polystyrene formers.

I.F.s Standard 465 kc. Permeability-tuned with
flying leads. Size 1 1/2" x 1 1/2" x 3 1/2". For use with OSMOR
coilpacks and others, 14/6 pair. **MIDGET I.F.s** 465
kc. 1 1/2" x 1 1/2" x 2 1/2", 21/- pair. **PREALIGNED** 1/6 extra.

FREE Send 5d. (stamps) for fully descrip-
tive literature, including The really
efficient 5 valve Superhet Circuit and
practical Drawings. 6-valve ditto, 3-valve (plus recti-
fier) T.R.F. circuit, Battery portable superhet circuit,
Chassis Cutter, Coil & Coilpack leaflets and full radio &
component lists and interesting Miniature circuits etc.

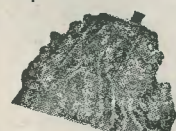Our Technical Dept. will be pleased to answer
(by letter only) any enquiry relating to circuits
in which Osmor Coils or Coil Packs are used
or are intended to be used.



Frequency Modulation Feeder Units

for studio quality, noise free reception of B.B.C.'s experimental transmissions from Wrotham. Tunable 88-100 Mc/s. Latest type valves used. Line up:—I-R.F. Frequency Changer. 2-IF. Ratio Discriminator. A.F. output to existing equipment. Power supply needed: 250v at 50mA, 6.3v heaters.

Kit less valves	£5 17 0
Kit with B.V.A. valves	£10 8 0
Kit with surplus valves	£8 3 8
Assembled and air tested	£12 0 0
Assembled with surplus valves	£9 15 0

These units use well-known manufacturers I.F.'s and R.D. transformer and are built to their specification. Within 30 miles of transmitter good results are obtainable with I-IF stage. Prices then reduced to:

Kit less valves	£5 6 6
Kit with B.V.A. valves	£9 0 6
Kit with surplus valves	£7 4 6
Assembled and air tested	£10 12 6
Assembled with surplus valves	£8 16 6

All with circuit, point to point wiring diagram and constructional details. Circuit only 1/8 post free, refundable if kits or units are purchased.

Components for above units supplied separately. Completely drilled chassis with screens, 7/6; IF Transformers, 6/- each; Ratio Discriminator Transformers, 12/6 each; Aerial, R.F. & Osc. Coils, 3/11 each; Tuning Condenser, 6/6. Small calibrated dial and pointer knob 1/6. Valve Holders with screening cans, B7G & B9A, 1/3 each. All orders over £1 post free. Demonstrations given Monday to Friday, day and evening. Saturday, evenings only.

Cash with Order please

Radio & Electrical Service

7 Plender Street
Camden Town • London N.W.1.
Telephone EUSton 3155

REPORT PADS

REPORT/REPLY RATIO LOW ?

Then send a report which contains all the information a station requires. Each pad contains 50 printed forms detailing the headings under which reports should be made. Your QSL returns will be much higher if you use these properly prepared reports. Printed on a high quality paper suitable for airmail transit they cost only 3/9 post paid.

Orders with remittance to

DATA PUBLICATIONS LTD
57 MAIDA VALE LONDON W9

SMALL ADVERTISEMENTS

continued from page 1271

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M.Brit.I.R.E. City and Guilds Telecommunications R.T.E.B. and other professional examinations. Train with the College operated by Britain's largest Electronic Organisation, Moderate fees. Write to E.M.I. INSTITUTES, Postal Division. Dept. RC28, E.M.I. Institutes, London, W.4

OSMOR—for efficient coils, coilpacks, etc. Send 5d stamp for FREE circuits and lists. Dept. RCC, Osmor Radio Products, Ltd., 418 Brighton Road, South Croydon, Surrey. Telephone Croydon 5148/9.

JOIN THE ISWL. Free services to members including QSL Bureau, Translation, Technical and Identification depts. Dx certificates, contests, and activities for the SWL. Monthly magazine 'MONITOR' duplicated, containing articles of general interest to the SWL and League members, 10/6 per annum, post free. ISWL HQ, 86 Barringer Road, London, N.10.

ANNOUNCEMENT A. Jerome Alcock, Cheadle, Stoke-on-Trent, regrets that he is unable to accept orders for bookbinding until further notice, which will be published in this Journal.

PANL, the air-drying crackle finish. In black, green and brown at 3/6 per 1/8th pint can, post paid, from—G. A. Miller, 8 Kenton Park Crescent, Kenton, Middx.

WORTHING AND DISTRICT AMATEUR RADIO SUPPLIES. Maxi-Q (Denco), Osmor, T.C.C. Dubilier, LAB, AVO, Bulgin, Radio Books, F.M. components, Tuner Units, Amplifiers, etc., etc. Available from A. E. Cray, 59b High Street, Worthing Sussex.

BARGAINS in Test Gear, Ex-Govt. Sets, Valves, Components, 800 Items on list. Stamp to 506 Loughborough Road, Birstall, Leicester.

FREE, PERFORMANCE DATA of a new hi-fi direct coupled amplifier of exceptionally simple design. SAE please or circuit and full details 2/6, post free. White, 25 Abbey Park Road, Grimsby.

RADIO MODEL CONTROL—Unlimited advice, Handbook 3/6. Carter, 101 High Street, Harlesden, London, N.W.10.

TELETRON SUPER INDUCTOR COILS

as specified for the EASI-BUILD

DM/1 Long wave coil	3/9
DM/2 Medium wave coil	3/9
SP/1 Reaction choke	2/6

Obtainable from your local stockist, or, in case of difficulty write to:

THE TELETRON CO

266 NIGHTINGALE ROAD . LONDON N9
Telephone HOW 2527


THE JASON 3-SPEED GRAMOPHONE MOTOR

A motor designed to suit the most critical taste at a reasonable cost. The cast aluminium turntable is accurately machined and is fitted to a hardened steel shaft turning on a steel thrust ball in a well bearing. The weight of the turntable ensures freedom from rumble and wow.

The speed selector for 78, 45 and 33 1/3 consists of an accurate rubber tyred idler wheel which engages a three-step motor pulley. When the motor is out of use the idler wheel is withdrawn from the motor pulley and turntable to prevent deformation of the rubber, thus preventing the appearance of "flats."

A small variation allows the motor to be set to exact speed irrespective of mains voltage or frequency fluctuations.

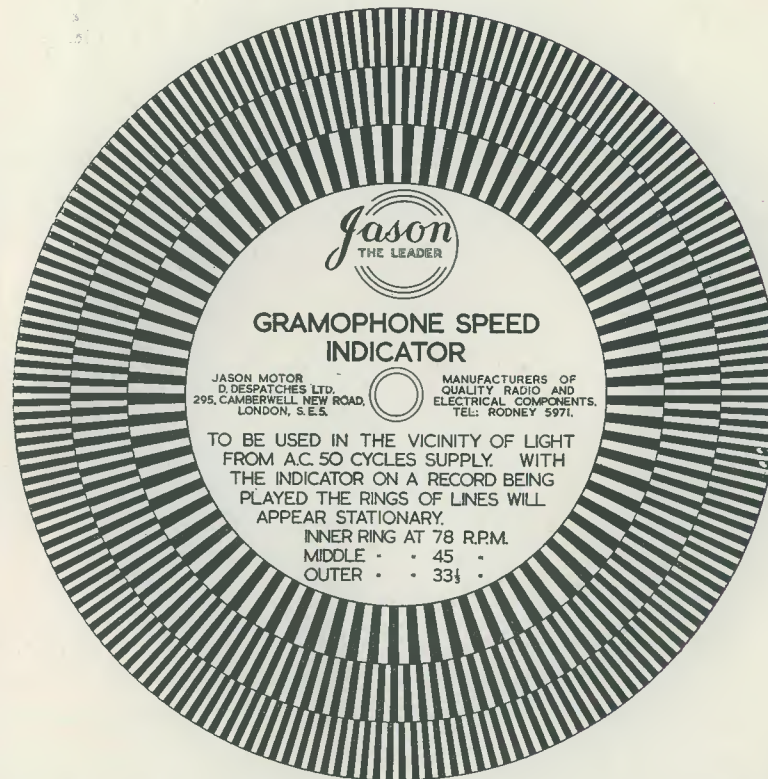The whole unit is mounted on a sturdy cast base and is finished in a stove enamel.



Price of complete unit £14 18s. 2d. This includes the cast aluminium base, turntable and drive unit and special motor.

All parts available separately.

JASON MOTOR COMPANY

295 CAMBERWELL NEW ROAD
Telephone RODney 5971

LONDON SE5