

RADIO



BOOKS

- Tape and Wire Recording.** A selection of articles reprinted from the pages of *The Radio Constructor*, covering both the theory and practical applications. A really useful book on this latest development of the hobby. 4th Edition, 3/-. Postage 3d
- Receivers, Preselctors and Converters.** Practical articles, again reprinted from past issues of *The Radio Constructor*, which will prove of interest to many radio enthusiasts. 2/6. Postage 3d
- TV Fault Finding.** Profusely illustrated with photographs taken from a televisior screen depicting the faults under discussion, and containing a wealth of technical information, with circuits, enabling those faults to be eradicated. 5/-. Postage 4d
- F.M. Tuner Units for Fringe and Local Area Reception.** Including optional Tuning Indicator and circuit of Osram 912 Amplifier. 2/-. Postage 2d
- The Argonaut AM/FM MW/VHF Tuner Receiver.** Describing the construction, alignment, and other details of a high quality tuner (or complete receiver), together with map of present and projected coverage areas. 2/-. Postage 3d
- Radio Amateur Operator's Handbook.** An indispensable aid to the amateur transmitter and listener, containing all details of information which are constantly required. Prefix Lists, Zone Boundaries, Call Areas, Codes, and Mileage Tables, together with Maps and much other useful operating data. 1957/8 edition, 3/-. Postage 3d
- Inexpensive Car Radio.** In which two versions, one constructed from surplus and one from new components, are described. 1/6. Postage 2d
- Radio Control for Model Ships, Boats and Aircraft,** by F. C. JUDD, G2BCX. A comprehensive work on this fascinating subject. Standard edition 8/6. Postage 5d
Cloth bound edition 11/6. Postage 7d
- The "Eavesdropper."** A miniature transistor local station receiver. Complete constructional details of this pocket portable. 1/6. Postage 2d
- Radio Control Mechanisms,** by RAYMOND F. STOCK. The only book dealing solely with this important part of radio control. 4/6. Postage 4d

All available from your local bookseller, or from

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141 (2 lines)

Published in Great Britain by the Proprietors and Publishers

Data Publications Ltd 57 Maida Vale London W9

Printed by A Quick & Co Ltd Oxford House Clacton on Sea England

Obtainable abroad through the following Collects Subscription Service Continental Publishers & Distributors Ltd William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency Holland "Radio Electronica"

Registered for transmission by Magazine Post to Canada (including Newfoundland)

Further Notes on the "Companion"

The RADIO Constructor



VOLUME 11
NUMBER 2
SEPTEMBER
1957

RADIO · TELEVISION · AUDIO · ELECTRONICS

The
MAYFAIR
Turret Tuned
Band 1-Band 3
Home
Constructor
TELEVISOR



Included in this issue

EASILY SET-UP & CALIBRATED VALVE VOLTMETER

A SENSITIVE SIGNAL TRACER

"THREE-DEE" 3 TRANSISTOR RECEIVER

SIMPLIFIED LOW DISTORTION DETECTOR

A CIGAR BOX RADIO

ADD-ON A.F. AMPLITUDE LIMITER

DATA
Publications 1/9

THE MODERN BOOK CO

Hi-Fi Year Book 1957. 10s. 6d.
Postage 9d.

Rapid TV Repair. By G. Warren
Heath. 23s. Postage 1s.

The Radio Amateur's Handbook.
By A.R.R.L. 1957 edition. 32s. 6d.
Postage 1s. 6d.

Radio Control Mechanisms. By R. F.
Stock. 4s. 6d. Postage 4d.

Frequency-Modulated Radio. By
K. R. Sturley. 15s. Postage 6d.

TV—It's a Cinch. By E. Aisberg.
23s. Postage 1s.

The New High Fidelity Handbook.
By I. Greene and J. Radcliffe. 36s.
Postage 1s.

TV Fault Finding. A Data Publica-
tion. 5s. Postage 4d.

Transistors: Circuits and Servicing.
By B. R. A. Bettridge. 2s. 6d. Postage
3d.

**Radio Servicing: Supplementary
Volume: Fault Finding.** By G. N.
Patchett. 5s. Postage 4d.

Transistor Techniques. Gernsback
Publications. 12s. Postage 8d.

**Electronic Gadgets for the Con-
structor.** By E. N. Bradley. 3s. 6d.
Postage 3d.

Radio Valve Data. Compiled by
"W.W." 5s. Postage 6d.

**Guide to Broadcasting Stations
1956-7.** Compiled by "W.W."
2s. 6d. Postage 3d.


We have the Finest Selection of British and American Radio Books in the country

Complete list on application

19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185

MAXI-Q

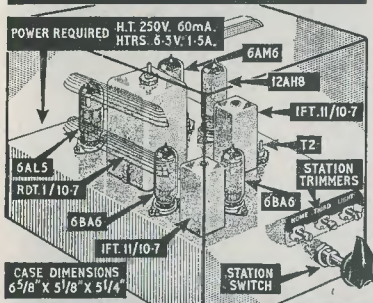

PRE-SET F.M. TUNER

VHF/FM HOME, LIGHT AND THIRD PROGRAMMES—Instantly selected at the turn of a switch

Full constructional details, point-to-point wiring diagrams and alignment instructions for building the "MAXI-Q" PRE-SET FM TUNER and also the VARIABLE TUNED version are given in Technical Bulletin DTB.8, 1/6

Completely punched Chassis, Screens and Bronze finished Cover, 19/-. Station Indicator Plate, 1/1. 3-position Switch 4/3. Station Condenser Trimmers, 3-9pF, 2/- each. Complete set of RESISTORS and CONDENSERS for either version, 48/-

RATIO DISCRIMINATOR TRANSFORMER, RDT, 1/10.7 Mc/s. Secondary winding of bifilar construction, iron dust core tuning, polystyrene former, silver mica condensers Can size: 1" sq. x 2 3/8" high

I.F. TRANSFORMER, IFT. 11/10.7 Mc/s. Miniature I.F. Transformer of nominal frequency 10.7 Mc/s. The 'Q' of each winding is 90 and the coupling critical. Can size 1 1/8" square x 1 1/2" high, 6/6

COILS TYPE L1, T1 and T2. Specially designed for use in this unit, are wound on polystyrene formers complete with iron dust core tuning, 3/11 each

THE "MAXI-Q" PRE-SET FM TUNER is available completely wired, assembled, valved and housed in a sturdy made bronze finished cover at £8.11.5, plus £3.8.7 P.T. = £12

VARIABLE FM TUNER completely assembled, £11.0.0 including P.T. (carriage 3/-, terms c.w.o.)

GENERAL CATALOGUE covering technical information on full range of components, 1/- post free

DENCO (CLACTON) LTD (DEPT. R.C.) 357/9 OLD ROAD
CLACTON-ON-SEA ESSEX

STOP PRESS: "MAXI-Q" 60 kc/s TAPE DECK OSCILLATOR COILS, TDO.1—for high impedance Erase Heads (Truvox, etc.), 5/- TDO.2—for low impedance Erase Heads (Brenell and Collaro), 5/-
Trading Terms for direct Postal Orders, C.W.O. plus appropriate postal charge



See AVO Instruments at the


**RADIO Stand No.
SHOW 62**

EARLS COURT, LONDON
Aug. 28th. — Sept. 7th.



Designed for

Dependability

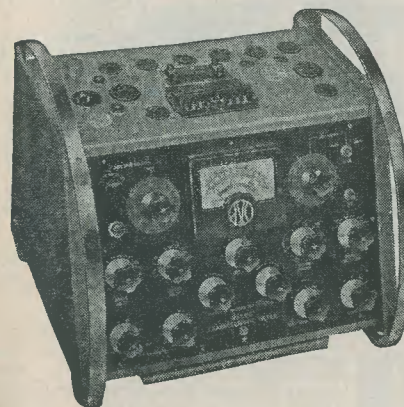

The "AVO" Valve Characteristic Meter, Mk. III is typical of the ingenuity of design and high standard of workmanship that exemplify all of the multi-range instruments in the wide "Avo" range.

It is a compact and comprehensive meter that will test quickly any standard receiving valve or small transmitting valve on any of its normal characteristics under conditions corresponding to a wide range of D.C. electrode voltages. The method of measuring mutual conductance ensures that the meter can deal adequately with modern T.V. receiver valves. It does many useful jobs too numerous to mention here, but a completely descriptive pamphlet is available on application.

List Price **£75** complete with Instruction Book and Valve Data Manual.

AVO LTD.

Victoria 3404
(9 lines)

AVOCET HOUSE • 92-96 VAUXHALL BRIDGE ROAD • LONDON • S.W.1.

PREMIER RADIO COMPANY

B. H. MORRIS & CO. (RADIO) LTD.
(Dept. R.C.9) 207 EDGWARE ROAD LONDON W2

Telephone
AMB 4033
RAD 3271

Open till
6 p.m. Saturday

Build the New "MAYFAIR" Televisor

which gives complete SAFETY
to the constructor!

These Televisors use a double wound mains transformer which gives you complete safety from contact with the mains supply when handling the chassis or controls.

* B.B.C. & I.T.A. DESIGN

WITH NEW TURRET TUNER
MAY BE BUILT FOR **£33.7.11** PLUS COST OF C.R.T.


Build in 5 easy stages. Full Construction details available. Instruction Book 3/6 post free.

Console Cabinets with full-length doors for 14in., 16in. and 17in. tubes. Price £14.14.0.

H.P. Terms: Deposit £7.7.6 and 9 monthly payments of 18/6.

Console Cabinets. Half-door £12.12.0. H.P. Terms: Deposit £6.6.0 and 8 monthly payments of 18/3.

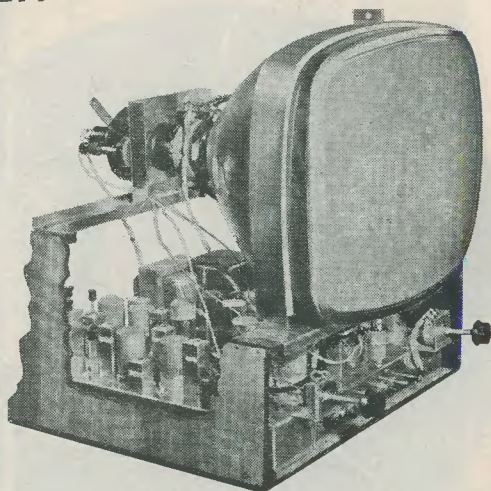On above cabinets add 21/- for pkg. and carr.



Introducing the "PETITE" Portable

A completely new design with the all star feature from the firm with 45 years of experience in the supply of designs for the home constructor.


MAY BE BUILT FOR **£7.7.0** Plus p. & p. 3/-

- ★ Size only 8" x 8" x 4 1/2"
- ★ Weight including batteries, 5 1/2 lb.
- ★ 4 Valves of the economy type
- ★ Medium and long wave superhet circuit
- ★ High Q frame aerials
- ★ High sensitivity on both wavebands
- ★ Prealigned I.F. transformers
- ★ 5" Speaker of the latest type
- ★ Automatic on/off switch operated by lid.
- ★ Simple to construct using normal soldering methods.
- ★ Mains Unit will be available later. Instruct. Book 1/6

The Teletron "COMPANION"


3 Transistor Pocket Receiver
Plastic Cabinet complete with drilled chassis 8/6. Ferrite Inductor FX25 15/-, Ardente Transformers D240 & D239 10/- each. Wavechange switch 1/3. Transistor R. F. 21/-, Transistor Audio 10/- each. Construction Book 6d.

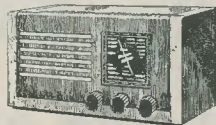This receiver may be built for **89/6** Complete p. & p. 1/6




The new Premier WIDE ANGLE TELEVISOR "The Mayfair." Construction Book 3/6 post free.

BUILD YOUR OWN RECORD PLAYER

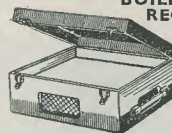

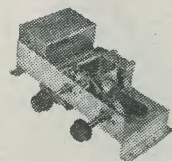Compact Amplifier, A.C. mains only ... **£2.19.6** p. & c. 2/6



3-speed Single Player, B.S.R. TU8 ... **£4.12.6** p. & c. 2/6

PC2 De Luxe Cabinet, **£2.15.6** p. & c. 3/-

7" x 4" Elliptical Speaker **£1.1.0** p. & c. 1/6

2-BAND T.R.F. RECEIVER

MAY BE BUILT FOR **£5.15.0** Plus 3/- Pkg. & Post

3-Band Superhet Receiver may be built for **£7.19.6** plus pkg. and carr. 3/-, These two receivers use the latest type circuitry and are fitted into attractive cabinets 12" x 6 1/2" x 5 1/2" in either walnut or ivory bakelite or wood. Individual instruction books 1/- each, post free.

CONDENSERS. Mica or S. Mica. All pref. values. 3pF to 1000pF, 6d. each. Ceramic types, 2.2pF to 5,000pF, 9d. each. Tubulars, 450V, Hunts and T.C.C., 0.0005, 0.001, 0.005, 0.01 and 0.1, 350V, 9d.; 0.02, 0.05, 0.1, 500V Hunts, T.C.C., 1/-; 0.25 Hunts, 1/6; 0.5 Hunts, 1/9; 0.001 6kV T.C.C., 5/6; 0.001 20kV T.C.C., 9/6.
8" P.M. SPEAKER. Ex mfrs. units: Rola, Elac, Celestion, etc. All reconditioned and guaranteed. Ideal ext. unit. Bargain 7/6. Carriage 1/6
TRANSISTORS. Mfrs. surplus PNP Junction type. Audio Type, 800 kc/s, 250mW, 9/6; R.F. and L.O. Mixer Type, 2.5 Mc/s, 19/6. All tested and guaranteed.
TRANSISTOR COMPONENTS. Midget i.f. transf., 315 kc/s, 5/-; Ferrite Slab Aerial (dual range), 13/6; M. and L.W. Osc. and 1st I.F., 11/6; Push pull interstage transf., 8/6; Push pull output transf., 8/-; M/coil phone inserts dia. 2", 4/6; M/iron dynamic inserts dia. 1 1/8", 3/9
RESISTORS. Pref. values 10 ohms 10 megohms, 20% tol., 1/6, 3d.; 1W, 5d.; 1W, 6d.; 2W, 9d.; 10% tol., 1/6, 9d.; 5% tol., 1/6, 1/-; 1% hi-stab., 1/6, 2/-
PRE-SET W/W POTS. T.V. knurled, slotted knob type, 25 ohms to 30,000 ohms, 3/-; 50,000 ohms, 4/-; 50,000 ohms to 2 Megohms (carbon), 3/-
S.T.C. RECTIFIERS. E.H.T. types, K3/25 2kV, 5/-; K3/40 3.2kV, 6/9; K3/45 3.6kV, 7/3; K3/50 4kV, 7/9; K3/100 8kV, 13/6, etc. Mains types: RM1 125V 60mA, 4/9; RM2 125V 100mA, 5/6; RM3 125V 120mA, 7/6; RM4 250V 250mA, 16/-; RM4B type 250V 275mA, 17/6
LOUDSPEAKERS. P.M. 3 ohm, 2 1/2" Elac, 16/6; 3 1/2" Goodmans, 18/6; 5" Celes., 17/6; 6" Celes., 18/6; 7" x 4" Goodmans, 18/6; 8" Elac, 20/-; 10" R. and A., 25/-
SPEAKER FRET. Expanded bronze anodised metal: 8" x 8", 2/3; 12" x 8", 3/-; 12" x 12", 4/3; 12" x 16", 6/-; 24" x 12", 8/6, etc. **TYGAN FRET** (Murphy pattern): 12" x 12", 2/-; 12" x 18", 3/-; 12" x 24", 4/-, etc.
VOL. CONTROLS. Log ratios 10kΩ-2MΩ, long spindles, 1 year guar. Midget Edison type, no switch 3/-, s.p. switch 4/-, d.p. switch 4/9. Lin. ratios less sw. 3/-
MAINS TRANSFORMERS. Made in our own workshops to top grade spec. Fully interleaved and impregnated. We shall be glad to quote for your specials.

80 OHM CABLE, CO-AXIAL. Special. Semi-air spaced polythene standard 1/4" dia. Stranded core. Feeder losses cut 50%, 9d. yd. Standard Grade A Coax. Polythene insulated 1/4" dia., 8d. yd.
ELECTROLYTICS—ALL TYPES—NEW STOCK
Tubular Wire Ends Can Types, Clips 3d. each
25/25V, 50/12V 1/9 8+8/450V T.C.C. 4/6
50/50V, 4/500V 2/- 8+16/450V Hunts 5/-
100/25V, 2/450V 2/- 16+16/450V T.C.C. 5/6
8/450V B.E.C. 2/3 32/350V 4/-
8/500V Dub. 2/9 32+32/275V Hunts 4/6
8+8/500V Dub. 4/6 32+32/450V T.C.C. 6/6
8+16/450V T.C.C. 5/- 250/350V B.E.C. 8/6
16/450V B.E.C. 3/6 100+200/275V 12/6
MIDGET TRANSISTOR TYPES. 2μF, 4μF, 8μF 6V, 3/9; 6μF, 10μF, 16μF 3V, 3/9; 32μF 1 1/2V, 3/9
I.F. TRANSFORMER, 465 kc/s. Brand new ex-manufacturer's midget i.f.t., size 2 1/2" x 3" x 3", dust core tuning. Litz wound coils, high-Q. Bargain offer 7/6 pair
VALVES—NEW BOXED—ALL GUARANTEED
1R5, 1T4, 7/6; 1S5, 1S4, 7/6; 3S4, 3V4, 8/-; 5Z4, 9/6; 6AT6, 8/6; 6K7, 6/6; 6K8, 8/6; 6Q7, 8/6; 6SN7, 8/6; 6V6, 7/6; 6X4, 7/6; 6X5, 7/6; 7C5, 9/-; 7Y4, 8/6; DAF96, 9/-; DF96, 9/-; DK96, 9/-; DL96, 9/-; 35L6, 10/6; EABC80, 9/6; EB91, 6/6; EBC41, 10/6; EBC33, 8/6; ECC84, 12/6; ECH42, 10/6; ECH81, 10/6; ECL80, 10/6; EF41, 10/6; EF80, 10/6; EF86, 12/6; EF91, 8/6; EY51, 10/6; EZ40, 8/6; EZ80, 8/6; MU14, 9/6; PCC84, 10/6; PCF80, 10/6; PCF82, 10/6; PCL83, 12/6; PL81, 11/6; PL82, 10/-; PL83, 11/6; PY80, 9/6; PY81, 9/6; PY82, 8/6; U22, 8/6; U25, 11/6; UY41, 8/6
TRS RADIO COMPONENT SPECIALISTS
70 Brigstock Road
Thornton Heath Surrey
THO 2188. Hours 9 a.m.-6 p.m., 1 p.m. Wed. Terms: C.W.O. or C.O.D. Post and packing up to 1lb 7d., 1lb 1/1, 3lb 1/6, 5lb 2/-, 10lb 2/9. Bargain lists 3d.

RADIO SOCIETY OF GREAT BRITAIN



RADIO HOBBIES EXHIBITION

Royal Horticultural Old Hall • Vincent Square • London SW1

WEDNESDAY to SATURDAY — OCTOBER 23rd to 26th — 11 a.m. to 9 p.m.

ADMISSION 2/-


HOME CONSTRUCTION
DO - IT - YOURSELF
FEATURES

Kits of Parts to BUILD . . .
Receivers, Transmitters, Televisors,
Hi-Fi Amplifiers, Test Gear, Tape
Recorders, and Transistor Equipment

HOME-BUILT Live Television Station and Studio. Live Radio Station talking to the World.

Win an Eddystone Communications Receiver (See next month's issue)

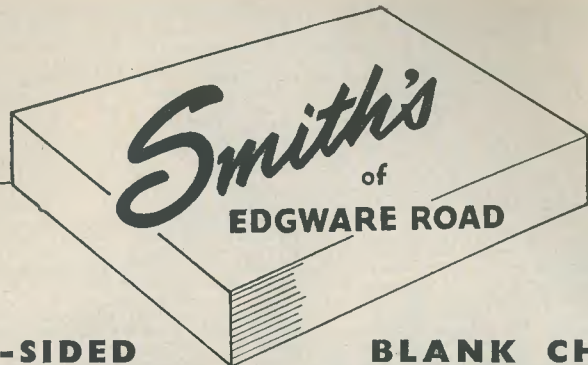FURTHER DETAILS FROM P. A. THOROGOOD, G4KD, 35 GIBBS GREEN, EDGWARE, MIDD.



FOUR-SIDED

BLANK CHASSIS

Made in our own works from commercial quality half-hard aluminium of 16 s.w.g. thickness, these chassis will carry components of considerable weight and normally require no corner strengthening. Standard stock sizes (in inches) are as follows:—

6 x 4 x 2	5/-	9 x 8 x 2½	7/6	10 x 8 x 3	8/6	14 x 10 x 2½	10/-
7 x 5 x 2	5/6	10 x 8 x 2½	7/10	13 x 8 x 2½	8/10	12 x 10 x 3	10/3
10 x 4 x 2½	6/4	12 x 5 x 3	7/11	12 x 9 x 2½	8/11	15 x 10 x 2½	10/6
9 x 7 x 2	6/6	12 x 7 x 2½	8/-	14 x 7 x 3	9/6	17 x 10 x 2½	11/3
12 x 4 x 2½	6/10	11 x 8 x 2½	8/3	13 x 10 x 2½	9/9	17 x 9 x 3	11/6
						17 x 10 x 3	12/3

The above are sizes for which we have most demand, but we can also make other sizes to order (at a small extra charge) within the following limits: Depths 1", 1½", 2", 2½" and 3" only. Maximum length 17". Minimum width for 3" depth is 5". Minimum width for 2½" depth is 4". Minimum width for 2" depth is 3½". Minimum width for 1½" depth is 3". Minimum width for 1" depth is 2". We cannot undertake to make odd shapes, extra bends, lips, etc. To arrive at the approximate cost of a special size of chassis take the nearest standard size above and add 2/6. **PANELS**—We can also supply the aluminium for use as panels, screens, etc., cut to any size up to 3' x 3' at 4/- per square foot. **NOTE**—A panel cannot be sent through the post if the length plus twice the width exceeds 6'. Keep this list for reference.

H. L. SMITH & CO. LTD. 287/9 Edgware Road London W2 Telephone Paddington 5891

G2AK THIS MONTH'S BARGAINS G2AK

SPECIAL OFFER!

DI04 CRYSTAL HAND MIKES

List £6.0.0 complete with 6ft of cord and plug

VERY LIMITED QUANTITY AVAILABLE. ONLY £3.10.0 each. DON'T BE TOO LATE

ABSORPTION WAVEMETERS. 3.00 to 35.00 Mc/s in 3 switched bands, 3.5, 7, 14, 21 and 28 Mc/s. Ham bands marked on scale. Complete with indicator bulb. A must for any Ham Shack. Only 17/6 each post free

Full range of Denco, Repanco and Eddystone coils and components available. Also most comprehensive range of Hi-Fi equipment in the Midlands including Quad, R.C.A., W.B. Leak, Rogers, etc.

HEADPHONES, H.R. type. 4,000 ohms. Very sensitive, only 12/6 pair, post 1/6. **C.L.R. type** (low res.) 8/6, post 1/6

AMERICAN BREAST MIKES. Swivel head, push-to-talk and lock-on switch; excellent job, only 12/6, post 1/6

BRITISH BREAST MIKES, complete with pair h.r. 4,000 ohm phones in wooden carrying case. New W.D. stock, unrepeatable at 17/6, post 2/-

SEMI-MIDGET I.F. TRANSFORMERS. 10.7 Mc/s and 465 kc/s (can be used as 10.7 Mc/s and 465 kc/s only), 9/11 per pair, postage 9d.

HEAVY DUTY SHROUDED CHOKES. 10H, 150mA, 80 ohms. Only 10/-, p and p 2/6

COLLINS MODULATION TRANSFORMERS. P.P. 807s 20V audio to parr. 807s. Beautiful job. 12/6 each carr. paid

RACK MOUNTING PANELS. 19" x 5½", 7", 8½" or 10½" black crackle finish, 5/9, 6/6, 7/6, 9/- respectively, postage and packing 2/-

Special Offers

CONDENSERS

8µF, 600V trop, 750V normal. New ex-W.D. stock, 5/6 each, p. and p. 2/-

T.C.C. TYPE 111, 8µF 1,000V d.c. (list over £3). Our price 10/6, plus 1/9 p. and p.

AERIAL EQUIPMENT

COPPER WIRE 14g. h.d.; 140' 17/-, 70' 8/6; 7/25 stranded: 140' 10/-, 70' 5/-, Plus 2/- p & p

RIBBED GLASS INSULATORS, 3" 1/6 each or 6 for 7/6. 12 or more post free.

TWIN FEEDER 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K35B Telcon (round), 1/6 per yard. Post on above feeder and cable, 1/6 any length.


PANL HOME CRACKLE. Black, 3/- tin, postage and packing 8d.

PLEASE PRINT YOUR NAME AND ADDRESS

CHAS. H. YOUNG LTD

Dept. 'R' 110 DALE END BIRMINGHAM
Telephone Central 1635

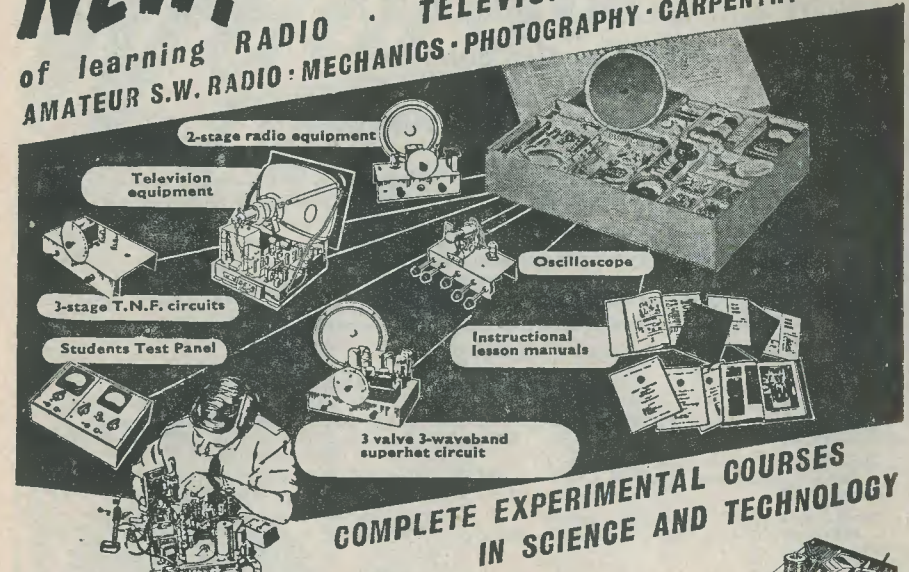NEW! — THE PRACTICAL WAY
of learning RADIO · TELEVISION · ELECTRONICS
AMATEUR S.W. RADIO · MECHANICS · PHOTOGRAPHY · CARPENTRY etc. etc.



COMPLETE EXPERIMENTAL COURSES
IN SCIENCE AND TECHNOLOGY

NEW—completely up-to-date methods of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teaching staff.


NEW—experimental outfits and lesson manuals are despatched on enrolment and remain the student's property. A tutor is allotted to each student for personal and individual tuition throughout the course. In the case of radio and television, specially prepared components are supplied which teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern commercial radio and television receivers.

If you are studying for an examination, wanting a new hobby or interest, commencing a career in industry or running your own full-time or part-time business, these practical courses are ideal and may be yours for moderate cost. Send off the coupon to-day for a free Brochure giving full details. There is no obligation whatsoever.

SUBJECTS

INCLUDE:—

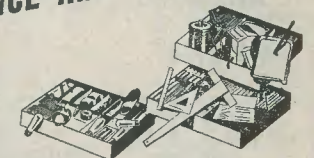- RADIO
- SHORT WAVE RADIO
- TELEVISION · MECHANICS
- CHEMISTRY · PHOTOGRAPHY
- ELECTRICITY · WOODWORK
- ELECTRICAL WIRING · DRAUGHTSMANSHIP · ART, ETC.



COURSES FROM 15/- PER MONTH



Send without obligation your FREE book.
E.M.I. INSTITUTES, Dept. 179X, London, W.4

NAME _____ Age _____
(If under 21) BLOCK CAPS PLEASE

ADDRESS _____

I am interested in the following subject(s) with/without equipment

(We shall not worry you with personal visits) Sept./57

The only Home Study College
run by a world-wide Industrial organisation.

E.M.I. Factories at Hayes.

EMI INSTITUTES

—Part of "His Masters Voice", Marconiphone, etc. etc.

◆ ◆ ◆ ◆ REPANCO ◆ ◆ ◆ ◆

HIGH GAIN COILS and QUALITY COMPONENTS for the constructor

TRANSISTOR COMPONENTS

- FERRITE SLAB AERIAL TYPE FS2.** A new super-sensitive aerial, Long and Medium Wave, specially designed for transistor portable receivers. Complete with fixing brackets. Length 5½" 13/6
- COMBINED OSCILLATOR AND 1st I.F. TRANSFORMER TYPE OT1** (315 kc/s), fully screened, 1½" x 1½" x 1½" ... 11/6
- 2nd I.F. TRANSFORMER TYPE TT2** (315 kc/s), 1" x ⅝" dia. ... 5/-
- 3rd I.F. TRANSFORMER TYPE TT3** (315 kc/s), 1" x ⅝" dia. ... 5/-
- PUSH-PULL INTER-STAGE TRANSFORMER TYPE TT4.** Ratio 1:1 ct. Stack 1⅜" x 1⅞" x 7/16" 8/6
- PUSH-PULL OUTPUT TRANSFORMER TYPE TT5.** Ratio 15:1 ct. Stack 1⅜" x 1⅞" x 7/16" 8/-
- All components complete with theoretical circuit and layout diagram of Transistor Portable*

HIGH GAIN COILS

- | | |
|---|--|
| Dual-range Miniature Crystal Set Coil with circuit, type DRX1 ... 2/6 | } Matched pair TRF Dual-range Coils with Reaction. With mains, battery and feeder unit circuits, type DRM3 pr. 8/- |
| Dual-range Coil with Reaction. With 2 mains, 2 battery and Transistor Circuit type DRR2 ... 4/- | |
| Ferrite Rod Aerial, Long and Medium Wave. With fixing brackets, type FR1 12/6 | } Miniature I.F. Transformers, pre-aligned, 465 kc/s 1⅜" x 1⅞" x 1½", type MSE ... 12/6 |
| | |

'R' COILS

	Range	Aerial	H.F.	Osc.
Miniature Iron Dust Cored Superhet Coils 465 i.f., 0.0005µF Tuning	800-2,000 metres	RA1	RHF1	RO1
	190-550 metres	RA2	RHF2	RO2
	70-230 metres	RA3	RHF3	RO3
	15-50 metres	RA4	RHF4	RO4

REPANCO FM COIL SET 29/6 Complete

REPANCO EASY-TO-BUILD RECEIVERS

Constructors' Envelopes of easy wiring plans, instructions and detailed price lists of components

- THE HIWAYMAN** ... Four-valve superhet Dual-range Portable using Ferrite Rod Aerial ... Envelope 1/6 (post 3d.)
- REPANCO ONE-VALVE** ... Beginner's Dual-range Radio Set for use with headphones ... Envelope 9d. (post 3d.)
- REPANCO FM TUNER UNIT** ... Using 4 EF91, 1 EB91, 1 EM80 Valves, Ratio Detector ... Envelope 1/6 (post 3d.)
- REPANCO "THREE DEE"** ... Dual-range Transistor Radio using 3 Transistors and Crystal Diode. Amazing loud-speaker reception from 7½ volt battery supply ... Envelope 9d. (post 3d.)
- REPANCO "TRANSEVEN"** ... A new 7 Transistor superhet Portable with preset station tuning using Repanco transistor components ... Envelope 1/6 (post 3d.)

MAIL ORDER and TRADE—

RADIO EXPERIMENTAL PRODUCTS
LIMITED
33 MUCH PARK STREET COVENTRY
Telephone 62572

WHOLESALE and EXPORT—

REPANCO LTD
O'BRIENS BUILDINGS
203-269 FOLESHILL ROAD COVENTRY
Telephone 40594

Wanted!


QUALIFIED MEN AND WOMEN

Industry and Commerce offer their best posts to those with the qualifications — appointments that will bring personal satisfaction, good money, status and security. As part of a modern industrial organisation, we have skilled knowledge of what is required and the best means of training personnel for its present day and future requirements. We specialise also in teaching for hobbies, new interests or part-time occupations in any of the subjects listed below. Write to us to-day for further information. There is no obligation of any kind.

PERSONAL & INDIVIDUAL TRAINING IN —

Accountancy	Electronics	Production
Advertising	Electronic	Planning
Aeronautical Eng.	Draughtsmanship	Radar
A.R.B. Licences	Eng. Drawing	Radio Amateurs
Art (Fashion, Illustrating, Humorous)	Export	(C&G) Licence
Automobile Eng.	General Certificate of Education	Radio & Television Servicing
Banking	Heating & Ventilation Eng.	Refrigeration
Book-keeping	High Speed	Sales Management
Building	Oil Engines	Sanitary Eng.
Business	Industrial Admin.	Salesmanship
Management	Jig & Tool Design	Secretaryship
Carpentry	Journalism	Shorthand & Typing
Chemistry	Languages	Short Story Writing
City & Guilds	Management	Short Wave Radio
Exams	Maintenance Eng.	Sound Recording
Civil Service	Mathematics	& Reproduction
Commercial	M.C.A. Licences	Telecommunications
Subjects	Mechanical Eng.	Television
Commercial	Metallurgy	Time & Motion
Art & Drawing	Motor Eng.	Study
Customs Officer	Painting & Decorating	Tracing
Draughtsmanship	Photography	Welding
Economics	P.M.G. Cert.	Workshop Practice
Electrical Eng.	Police	Works M'gement
Electrical	Production Eng.	and many others
Installations		

OUR BACKGROUND!

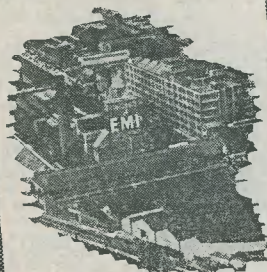

The E.M.I. Factories at Hayes, England.

Also courses for GENERAL CERTIFICATE OF EDUCATION, A.M.I.H.&V.E., A.M.S.E., A.M.Brit.I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.Ae.S., A.M.I.P.E., A.M.I.I.A., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Examinations, R.T.E.B.Serv. Cert., R.S.A. Certificates, etc.

The only Home Study College
operated by a world-wide
manufacturing organisation

NEW! Courses with PRACTICAL EQUIPMENT

IN RADIO · TELEVISION · MECHANICS · CHEMISTRY
ELECTRICITY · DRAUGHTSMANSHIP
PHOTOGRAPHY, ETC., ETC.

COURSES FROM 15/- PER MONTH



EMI

INSTITUTES

POST THIS TODAY

E.M.I. INSTITUTES, Dept. 179K, London, W.4

NAME _____ AGE _____
(if under 21)

ADDRESS _____

I am interested in the following subject(s) with/without equipment _____

_____ Sept./57

(We shall not worry you with personal visits).

FREE

BLOCK
CAPS
PLEASE

IC92

— Part of "His Master's Voice", Marconiphone, etc. etc.

Build for Quality

WITH THE FAMOUS JASON ARGONAUT KIT (AM-FM TUNER OR RECEIVER)


The "Argonaut" is a super-sensitive unit to receive medium-wave AM and FM transmission. It can be built either as a tuner for feeding to amplifier, or a complete receiver. Switching and wiring are reduced to complete simplicity without sacrificing performance and efficiency, and since its introduction the "Argonaut" is creating more and more enthusiasts for its all-round excellence.

Full building instructions are available as a Data Publications reprint, price 2/-

Send S.A.E. for complete list of components and prices

JASON MOTOR AND ELECTRONIC CO

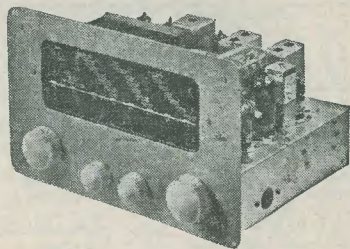328 CRICKLEWOOD LANE LONDON NW2
Telephone SPEedwell 7050



- **DIAL ASSEMBLY**
With chassis, flywheel tuning, Jackson Bros. 4-gang condenser, 500pF+500pF, and 15pF+15pF, glass scale. Station-name calibrated on both bands. Hammer finish front panel **£4.4.0**
 - **SET OF COILS**
All coils, including ratio detector, M.W. coils and 2 twin-i.f.t.'s (472 kc/s and 10.7 Mc/s) **£2.17.9**
- Approximate cost to build as a self-powered receiver **£16.0.0**

Home Radio of Mitcham

187 LONDON ROAD MITCHAM SURREY Telephone MIT 3282

Official Stockists for **EDDYSTONE** components and receivers and **PANDA** transmitters

The HIWAYMAN



All-dry battery portable. 4 valves and high efficiency Ferrite rod aerial. Medium and Long Waves. Full constructional details and price list. PRICE 1/6. Total building cost approx **£7.10.0**


Elliptical Speakers. 7" x 4" brand new units. Price 15/-, plus 1/6 post.

BEGINNERS 1 VALVE SHORT WAVE RECEIVER
All specified parts in stock and detailed price list free. S.A.E.

HI-FI SPEAKERS FULL RANGE W.B. STENTORIAN, GOODMAN'S & WHARFEDALE

TSL HIGH STABILITY FM/VHF TUNER

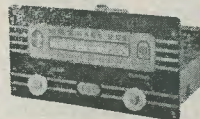With visual tuning indicator pre-set audio level and self-contained power supplies. 6 valves and 10 tuned circuits combining high sensitivity and best signal-to-noise ratio. Send s.a.e for full technical specification. **PRICE £17.10.0**



Also TSL high stability amplifier to suit above. Full details and specification on request. **PRICE £11.10.0**

THE COMPANION

Pocket Portable. Complete kit price **£4.5.0**. Detailed price list free.

The Radio Constructor

incorporating THE RADIO AMATEUR



CONTENTS FOR SEPTEMBER

VOL. 11. NO. 2

SEPTEMBER 1957
ANNUAL SUBSCRIPTION 25/-
including postage

Editorial and Advertising Offices

57 MAIDA VALE LONDON W9

Telephone
CUNningham 6141
(2 lines)

Telegrams
DATABUX, LONDON

Editor
C. W. C. OVERLAND, G2ATV

Advertising Manager
F. A. BALDWIN, AMIPRE

- 84 Suggested Circuits: An Add-On A.F. Amplitude Limiter, *by G. A. French*
- 87 In Your Workshop
- 95 An Easily Set-Up and Calibrated Valve Voltmeter, *by A. A. Tucker*
- 97 Radio Miscellany, *by Centre Tap*
- 99 The "Three-Dee" 3 Transistor Receiver, *described by James S. Kent*
- 103 Can Anyone Help?
- 104 Simplified Low-Distortion Detector, *by D. E. Pasfield, Ass. Brit. I.R.E.*
- 106 The "Mayfair" Turret-Tuned Home-Constructor Televisor, Part 1, *by S. Welburn*
- 113 Technical Forum
- 116 Further Notes on the "Companion" Regenerative Transistor "3" Pocket Receiver *by R. A. Langis*
- 118 A Sensitive Signal Tracer, *by P. Yates*
- 123 Right—from the Start: Part 18, Gains and Losses, *by A. P. Blackburn*
- 126 Design Charts for Constructors: No. 17, Triode Stage Gain, *by Hugh Guy*
- 130 A Cigar Box Radio, *by E. C. Harris*
- 132 Vibrator Basing Data, Part 3, *compiled by E. G. Bulley*

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

NOTICES


THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

All MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

QUERIES. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

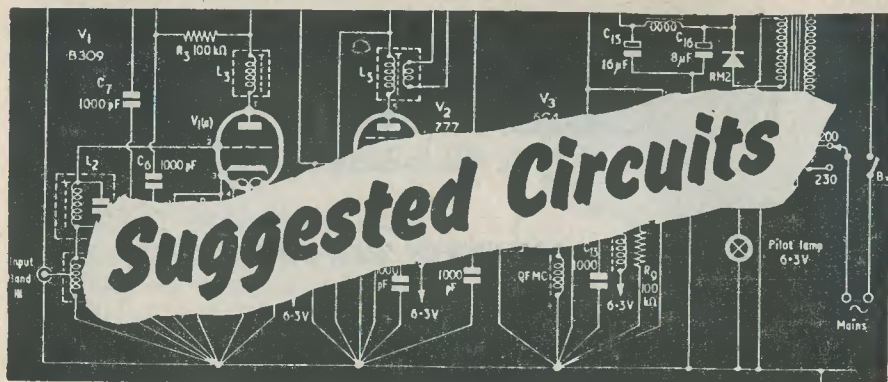ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 Maida Vale London W9



The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data

No. 82. AN ADD-ON A.F. AMPLITUDE LIMITER

AN INTERESTING REQUEST RECENTLY reached the writer via the Editor of *The Radio Constructor*. The correspondent making the request stated that he had fitted up a circuit by means of which the output of a sound receiver could be applied to a pair of headphones for the benefit of a friend who was rather hard of hearing. The headphones were of high-impedance type, and were coupled to the extension loudspeaker sockets of the receiver via an output transformer connected in such a manner that what was originally its primary now fed the headphones. The arrangement worked quite well so far as speech was concerned, but music, due to the B.B.C.'s frequent habit of broadcasting this at considerably higher levels than speech, was at times so loud as to be almost unbearable for the person wearing the headphones. The worst cases of discomfort occurred whenever an introductory loud burst of music followed a period of relatively quiet speech. The correspondent asked for details of a simple limiter circuit which could overcome this trouble.

Although the above instance does not represent a widespread requirement, the

writer feels that the solution which was passed on to the correspondent would also make a suitable subject for inclusion in this series of articles. Quite a number of radio enthusiasts are interested in short wave work, etc., and many employ headphones in conjunction with mains receivers having, so far as this application is concerned, an unnecessarily high degree of a.f. output power. Long periods of listening under such conditions can at times be fatiguing, and especially so when reception is subject to interference from static and unwanted powerful transmitters. A noise limiter of the type to be described in this article should prove to have quite a definite value for the short wave listener, in addition to the advantages conferred in the previous case.

The Circuit


This month's Suggested Circuit is depicted in the diagram which accompanies this article, and, as may be seen, represents a very simple and inexpensive design. The limiter unit proper is contained between the "Input" and "Output" terminals illustrated; and the diagram also shows how an additional

speaker transformer may be connected up when the associated headphones are intended to be run from the extension loudspeaker sockets of a conventional domestic receiver. When the transformer is connected in the manner illustrated it converts the low impedance output at the extension loudspeaker sockets to the high impedance needed by the phones and the limiter unit. For the limiter unit to function correctly it is necessary for the headphones to be of "high-resistance" type (preferably 2,000 ohms per phone), and for the a.f. output of the receiver to have power in reserve. This last requirement is due to the fact that a loss in output level occurs in the noise limiter circuit.

Setting-Up

The setting-up of the unit should not raise any difficulties provided that it is borne in mind that the a.f. voltage at which limiting occurs is fixed, and that the purpose of the adjustments is to enable individual requirements to conform to this fixed level.

After the unit has been assembled, it should be connected to the receiver with which it is to be used and checked for correct operation. Initial testing should be carried out with both R_1 and R_3 set to maximum, i.e., with their sliders at the top ends of their tracks. Using, preferably, a source of programme having a fairly constant level, the receiver volume control should then be turned up until the

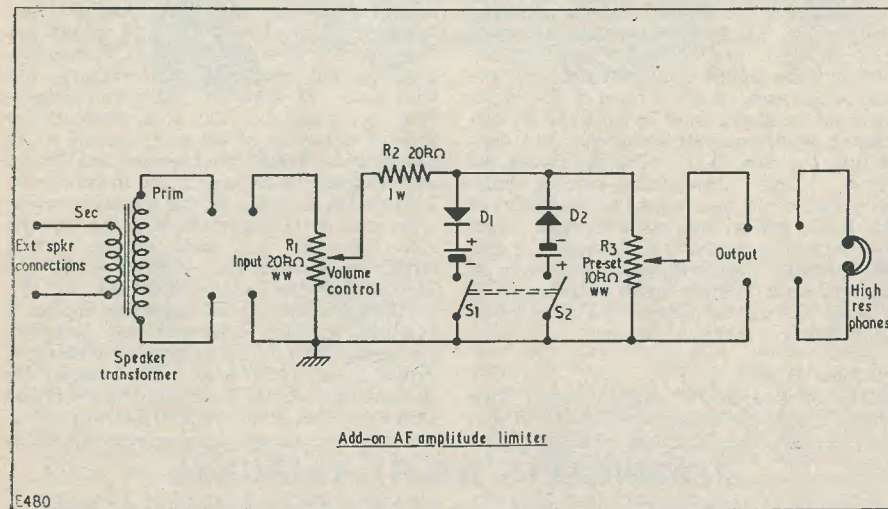

The operation of the unit is extremely simple. The a.f. appearing at the slider of the volume control R_1 is applied to the two crystal diodes, D_1 and D_2 , via resistor R_2 . Both D_1 and D_2 work with voltage delays, these being provided by the 1.4 volt cells with which they are connected in series. When the level of a.f. tapped off by R_1 exceeds a value of 2.8 volts peak to peak, both diodes conduct, thereby applying an effective resistance across the circuit which is equal to their forward resistances in series with the internal resistances of the delay cells. The resistance applied when the diodes conduct is much lower than that of R_2 (plus any resistance between the top end of the track of R_1 and its slider) with the result that a.f. voltages above the delay level are heavily attenuated. The amplitude-limited a.f. is then fed to the pre-set potentiometer R_3 , this being adjusted, as described below, to provide a comfortable level in the headphones.

level at which limiting takes place is found. R_3 is next adjusted at this limiting level, its final setting being that which provides a volume level in the phones which is equivalent to the maximum tolerable. The unit is then ready for use, future alterations to volume being made either by adjusting the receiver volume control or R_1 .

When the limiter is used in conjunction with a domestic receiver, it may be found advisable to site the unit such that the person wearing the headphones may adjust R_1 himself. Changes in the setting of R_1 will not, of course, alter the output level available from the receiver loudspeaker. It must be stated that some distortion will occur when the a.f. applied to the unit reaches limiting level, but this should not be too unpleasant in character and is, in any case, far more tolerable than excessive headphone volume. If desired, the listener using the headphones can, of course, adjust R_1 such that the volume falls below the

limiting level during the time in which loud music is being broadcast.

Due to its inherent simplicity, the circuit can be altered in one or two ways to meet particular circumstances without detracting from its performance. For instance, if it is found that limiting occurs at too low a level, all that is required is to raise the delay voltages by employing 3, or 4.5, volt batteries in place of the single cells shown in the diagram. When the unit is used with short wave receivers, it may become possible to delete the volume control, R_1 , as this component might then merely be duplicating the function of the volume control in the receiver itself. When R_1 is deleted, the upper input terminal connects directly to R_2 .

Attempts at altering the circuit to make it limit at a.f. voltages lower than 2.8 volts peak to peak are liable to prove rather difficult if the simple circuitry employed here is to be retained. A crude form of limiting at lower a.f. voltages could be obtained by dispensing with the cells altogether and connecting the two diodes directly across the circuit. This arrangement would take advantage of the non-linear characteristics of the diodes insofar that their forward resistances would be greater at lower than at higher a.f. voltages. However, an arrangement of this type does not have much to commend it, because a certain amount of distortion would be evident at all volume levels.

Practical Points

One or two minor points need a little further discussion before concluding. It will,

PERFORMING RIGHT TRIBUNAL

The Performing Right Tribunal, which was set up under Section 23 of the Copyright Act, 1956, has now taken occupation of the premises allotted to it at Someries House, Regents Park, London, N.W.1. The telephone number is Welbeck 1358-9.

The function of the Tribunal is to determine disputes arising between licensing

LITERATURE RECEIVED

From Messrs. M. Foy, 6 Wykebeck Gardens, Leeds 9, a General Catalogue of Radio and Television Service Components, comprising 60 pages containing a most comprehensive selection of components, some of them special replacements, tools and servicing accessories. Available from the above address, price 1s. post free.

An illustrated booklet describing some of the main applications of Styron polystyrene recently published by British Resin Products Ltd.

for instance, be noted that R_2 is given what may at first sight appear to be the rather large power rating of 1 watt. This rating is necessary due to the fact that the resistor may be called upon to dissipate quite high a.f. powers during loud passages of music. The two diodes, D_1 and D_2 , may consist of any reliable type. There is no necessity to employ diodes having high turnover voltages as one diode protects the other in this respect. A good choice of diode would be the OA70, or an equivalent.

Since the internal resistances of the delay cells form part of the limiting network, it is important to use cells in the unit which are fairly large in physical size. Cells intended for normal flash-lamp service should prove adequate for the purposes desired here. Although their terminal voltages should not drop by any noticeable amount during use, their internal resistances may gradually rise with time. It would be worthwhile, therefore, to replace the delay cells whenever the limiting efficiency of the unit appears to be decreasing. It will have been noticed that an on-off switch, S_1-S_2 , is provided in the circuit. This switch can be a simple miniature wafer type, and its sole purpose is to protect the cells from the very small reverse current which may otherwise flow through the diodes when the unit is not in use.

Although the circuit diagram depicts a "chassis" connection, it is not really necessary to mount the unit on a metal chassis or to provide any screening. If desired, for instance, the whole circuit could be assembled into a wooden case or similar housing.

bodies and persons requiring licences to perform in public or to broadcast copyright works. It also has jurisdiction in the case of the public performance and broadcasting of records and the public performance of television broadcasts.


Communications for the Tribunal should be addressed to the Secretary.

This booklet describes a wide range of Stryron polystyrene products in a simple, non-technical way which will interest moulders and manufacturers in a number of industries.

The refrigeration, packaging, housewares, toys and fancy goods and the electrical industries are discussed, and attractively illustrated.

Copies of the booklet may be obtained free of charge on application to the Information Department, British Resin Products Ltd., Devonshire House, Piccadilly, W.1.

IN YOUR WORKSHOP

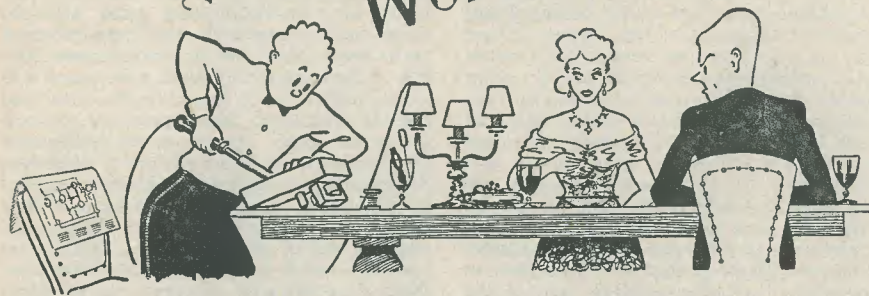

Aided by his able assistant Dick, Smythy the Serviceman continues to run the Workshop

JUST FOR ONCE IN A WHILE, THE WORKSHOP was passing through a quiet period. Both Smythy and Dick welcomed the break, and they had spent much of the morning in tidying up their benches and cleaning out the cupboards. They had now settled down for an unhurried cup of tea. They were both quiet, each being occupied with his own thoughts.

"You know, Smythy," Dick said, breaking the silence, "I've been fairly busy in my spare time over the last week or so knocking up a little transistor set for myself. It's going quite nicely now, incidentally, but while I was building it I kept saying to myself that I wasn't really quite certain how the transistors I was putting into it worked. In my mind's eye I can just about visualise the idea of electrons and holes moving around in a slab of germanium, and I know from what I've picked up on the subject that a hole merely means the absence of an electron; but, even so, I am still very vague about what exactly does go on in a working transistor. Could you tell me, in a few short sentences, exactly how a transistor amplifies?"

Smythy put down his cup of tea and stared at it for some moments.

"There's a very good film on at the local cinema," he volunteered, at length.

"Come off it, Smythy," protested Dick. "You've never shied away from any of my questions yet!"

"Well, I'm not really trying to avoid answering it," chuckled Smythy. "Only, to

my mind, what you want is well-nigh impossible. There aren't many difficulties in explaining how a thermionic valve amplifies, because it is easy to imagine the flow of electrons through a grid which applies a deterrent force when it holds a negative potential relative to cathode. However, the internal processes of a transistor are rather more complicated than are those of a valve, and I just couldn't give you a short explanation without leaving out something important. Perhaps it is the comparative newness of transistors which makes me think that way; and it is possible that, as time goes by, we will find no more difficulty in visualising transistor action than we do when considering the valve. Unfortunately, that state of affairs doesn't appear to exist at the present time. I might add that quite a few supposedly simplified descriptions of transistor operation have been published over the last few years, but I can't say that I very much like the explanations offered in some of these. Anyway, if you're prepared to accept the fact that the rather long description I am about to give you represents the basic facts with very few trimmings, it should, at any rate, help you to get the 'feel' of transistor operation and enable you to work intelligently with these devices."

Dick leaned back comfortably in his chair and prepared to listen.

Germanium

"To start at the beginning," said Smythy, "I have to remind you that the transistors most frequently encountered these days

employ germanium made up in crystalline form. An alternative to germanium is silicon (which functions in more or less the same manner), but I shall confine myself here to germanium only. When germanium is in crystalline form, its atoms combine together in a lattice or framework wherein the outer electrons which exist around the nuclei of their parent atoms are nicely balanced out throughout the body of the crystal. These electrons are, of course, held to their nuclei by the ordinary forces which hold an atom together; but, in this case, they are also kept in position by the bonds which hold the crystal lattice together. Normally, the outer electrons of a germanium atom are not held very securely to their nuclei; and they are quite liable to wander away from their parent atoms and join other germanium atoms, thereby causing electrons from these second atoms to similarly wander off. This random movement of electrons occurs even in the crystalline form, but it is usually quite small and insignificant. It is caused by the thermal agitation given at the normal temperatures in which the germanium finds itself. So, if we have a germanium crystal at room temperature, we can safely assume that there is a very small continuous random movement of electrons throughout its structure.

"When one of these wandering electrons travels away from its atom it leaves behind a 'hole,' and this hole will very probably soon be filled in by another wandering electron. This second electron leaves behind a hole in its own atom, which then becomes filled in by a third electron, and so on. As a result, therefore, thermal agitation causes a small movement both of electrons and of holes inside the germanium crystal structure. The holes do not actually move, of course, but since they appear to travel in the reverse direction to the electrons which fill them in, we assume that they *do* move. Also, since the existence of a hole means that a negative electron has departed therefrom, we say that a hole possesses a positive charge.

"As I have just said, the random movement of electrons and holes through a crystal of germanium is not very great. It certainly is not large enough, for instance, to allow us to put pure germanium amongst the ranks of good conductors of electricity. If we so desire, however, we can increase random movement in a crystal of germanium fairly easily; and this we do, not by raising its temperature and thereby the thermal agitation it suffers, but by adding very tiny quantities of impurities to the crystal. One of the impurities we can add is arsenic. Arsenic atoms are very similar to germanium atoms so far as the particular crystal structure we are considering here is concerned, and they enter into the germanium crystal quite readily.

However, the arsenic atom has one more electron in its outer ring of electrons than has the germanium atom; with the result that one electron from each arsenic atom remains outside the crystalline structure whilst still being held to its nucleus by the normal forces which hold the arsenic atom together. The attraction given by the arsenic nucleus to this 'spare' electron is not very great, with the result that it is extremely liable to wander off on its own. Since, on its travels, it may join one of the germanium atoms with which it is surrounded, an electron from the latter will become dislodged and repeat the process somewhere else. Because of the addition of the arsenic atoms, with their 'spare' electrons, therefore, the adulterated germanium crystal is now liable to have far more electrons wandering through its structure than it had when it was in the pure state. If they are made to travel in one particular direction, these electrons will, of course, constitute a flow of electric current, in just the same manner as a single-direction movement of electrons in any other material constitutes a flow of electric current. Since electrons are negative particles of electricity, germanium which has been adulterated by arsenic—or by any other impurity which causes a similar release of wandering electrons—is described as N-type germanium.

"A very important point to remember is that, although an arsenic electron which wanders away from its parent atom does so because it doesn't fit into the *germanium* crystalline structure, it still leaves behind an *arsenic* atom having an overall positive charge due to the negative charge it has just lost. I hope you can see that point."

"I think I've got the idea," said Dick. "Electrons which fit into the germanium crystalline structure are held in position not only by the attraction of their nuclei but also by the bonds of the structure itself. The 'odd' arsenic electrons are not held by the bonds of the crystalline structure and are more liable to wander through the crystal in consequence."

"That sums it up fairly well," said Smithy, "and the statement is true enough for the very shallow depth to which we want to delve into the subject just now. The arsenic atoms which provide the crystal with these spare electrons are, incidentally, called 'donor' atoms—an easy name to remember since they 'give' an electron to the structure. I should add that there are other impurities, such as antimony, which have the same effect on germanium as has arsenic.

"Now, it is also possible to find impurities, for addition to the germanium crystal, which have not one more, but one fewer electron than the crystalline structure calls for. Indium, or boron, have atomic make-ups

which fall into this class. Impurities of this type enter the crystalline structure of the germanium quite readily, but there is, once again, a certain amount of unbalance. Since the impurity atom is, in this case, one electron short of what is required by the structure, an electron from a nearby germanium atom is very liable to take up its position at the impurity atom, leaving behind a hole. A second electron may then travel to fill up this hole, leaving behind another hole, and so on. The nett result is that, by the use of this second class of impurity, we now have a crystal which has a number of *holes* moving throughout its structure. Since holes are equivalent to positive charges of electricity, insofar that they represent the absence of electrons, we call germanium adulterated in this manner P-type. The situation in P-type germanium is almost exactly opposite to that in N-type germanium, and the impurity atoms which attract the extra electrons to them-

*Electrons moving without stricture
Give an N-type style of mixture
When it's holes which travel free,
Then we call the mixture P!"*

Smithy, who had grown used to Dick's ability to produce doggerel almost at will, chuckled at this latest attempt.

"O.K.," he said at length, "I'll agree that that effort is a bit above average. Anyway, it makes a fairly useful mnemonic."


"Fair enough," commented Dick, modestly. "Incidentally, what type is germanium if it is absolutely pure and unadulterated?"

"Well, it hasn't a letter," replied Smithy, "but if it had, I suppose it would be U-type!"

P.N. Barrier

"Anyway," resumed Smithy, "let's get a little closer to the transistor itself. I think I should say at this stage that I'm not going to bother about point contact transistors in this explanation, because they are rather more

Fig. 1. A block of P-type and N-type germanium joined together. Despite the apparent attraction between them, the free holes in the P-section and the free electrons in the N-section remain on their own sides of the junction barrier. Fig. 2. If a potential having the polarity shown here is connected to the two blocks of germanium, the electrons and holes are assisted in overcoming the barrier at the junction

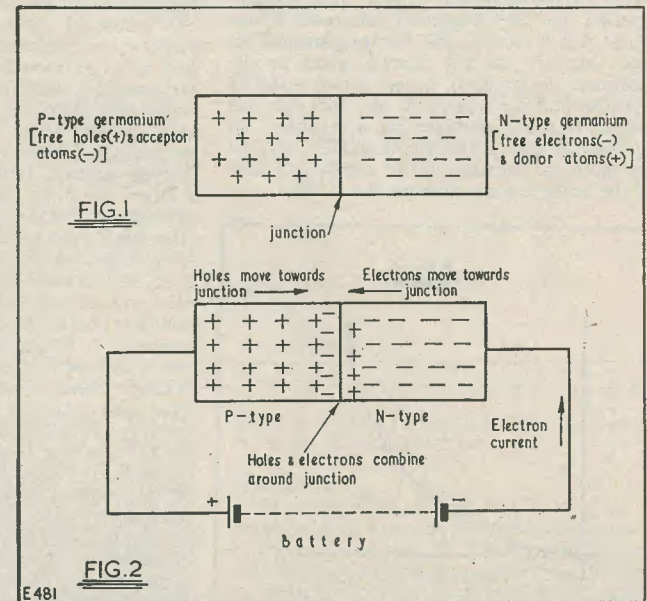

selves are called 'acceptor' atoms—another easy and obvious name to remember. Since acceptor atoms are forced by the crystalline structure to take to themselves one electron more than they would normally have, they acquire a negative charge."

"In fact," said Dick, who had been scribbling on a piece of paper at his side, "you could say:

complicated than junction transistors, and because they are not in any case encountered so often nowadays.

"However, before we tackle the working of a complete junction transistor, we must first of all look at what happens when we join together a block of N-type germanium and a block of P-type germanium (Fig. 1). Now, in this sketch I have shown the wandering

electrons in the N-type germanium as a number of 'minus' signs, and the wandering holes in the P-type germanium as a number of 'plus' signs. After looking at the diagram, I daresay you might imagine that the first thing that should happen is that the electrons in the N-type germanium would want to cross over to and cancel out the holes in the P-type germanium, and that the holes in the P-type germanium would want to cross over to the N-type block to cancel out the electrons there. But the interesting thing is that this doesn't happen at all. Indeed, we get quite an opposite effect, and what amounts to nothing short of a barrier to both the holes and the electrons appears at the junction of the two types of germanium. The reason for this barrier effect is quite simple to understand if we remember what I was talking about a few minutes ago. What occurs is that electrons attempting to cross over to the P-type germanium are repelled at the junction by the negatively charged acceptor atoms in that germanium. Similarly, holes trying to travel in the reverse direction are repelled by the positively charged donor atoms which exist in the N-type germanium. And thus we get the barrier effect at the junction. In practice, a very small quantity of holes and electrons may get through this barrier, but their numbers are negligible. To all intents and purposes, therefore, all the free electrons remain over on the N side, and all the holes remain over on the P side.

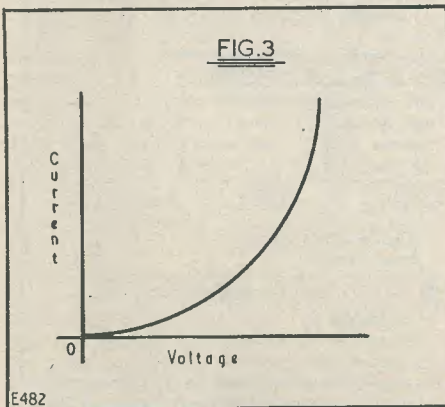


Fig. 3. A curve showing the relationship between current and voltage given by the arrangement of Fig. 2

"Another way of explaining the barrier effect at the junction might be given by saying that, whilst both the N and P blocks have free electrons and holes, both blocks are,

overall, electrically neutral. It is only the crystalline structure, plus its impurity, which causes the large number of wandering electrons and holes in either block. Considered in its entirety, either block has the correct quantity of electrons required by its atoms—even if they do not remain in their proper positions—so that it is completely neutral when considered as a whole. Thus, there is really no reason why the electrons or the holes should want to leave one electrically neutral block to enter another electrically neutral block.

"Next, let's see what happens if we apply a potential, given by a battery, to the two blocks of germanium such that its negative terminal connects to the N block and its positive terminal to the P block (Fig. 2). We now get quite a different state of affairs. This is because the negative terminal of the battery repels the free electrons in the N block, causing them to travel towards the junction; whilst the positive terminal repels the free holes in the P block, causing these also to travel towards the junction. If it is sufficient, the potential difference between the two battery terminals then causes the electrons and holes to overcome the repulsion effect at the junction, with the consequence that both holes and electrons cross over to the other side where they combine and become neutralised. However, electrons leaving the N-type section have to be replaced, and further supplies are provided from the negative terminal of the battery. At the same time the P-type germanium near the junction loses holes, which is the same thing as saying that it acquires extra electrons. These electrons attract holes from the germanium which is nearer the connection to the positive terminal of the battery, with the result that the excess of electrons now appears at this point. These excess electrons finally find their way into the positive terminal of the battery. In other words, we have a flow of electric current through the two blocks of germanium which is caused by the potential of the applied battery. To keep ourselves thinking transistor-wise, we can say that the current in the N block consists of a movement of electrons, whilst the current in the P block consists of a movement of holes in the opposite direction. At the same time the current at the junction itself consists half of electrons and half of holes.

"I would like to emphasise the fact that it is the potential of the battery which initiates the current, because it enables the holes and electrons to overcome the barrier at the junction of the two blocks of germanium. If the battery potential is low, this barrier is only partially overcome, and the current flowing is small. If the voltage of the battery is high, the barrier may be almost completely

overcome, and a disproportionately heavy current may flow. In other words, the resistance offered by the two blocks of germanium is non-linear and, if drawn as a curve, would look something like this (Fig. 3).

"Let's next see what occurs when we connect our battery to the two blocks of germanium the other way round (Fig. 4). If we were to do this we would find that the positive terminal of the battery would merely attract the electrons in the N-type germanium away from the junction, and that the negative terminal would similarly attract the holes in the P-type germanium. The result would be that negligible current would flow, since all the battery does is to assist the barrier at the junction in keeping the holes and electrons apart."

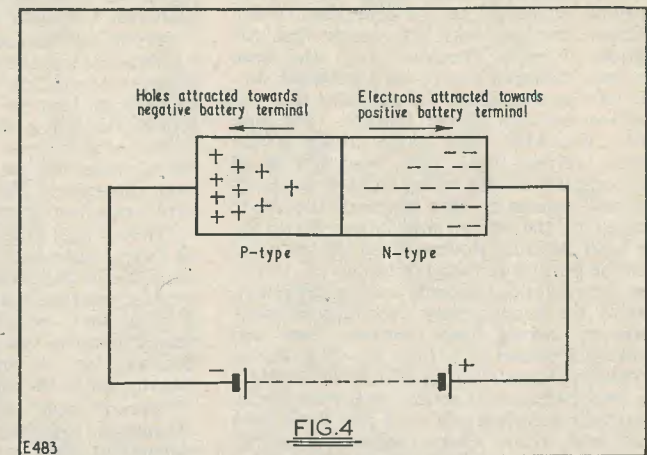


Fig. 4. When the applied potential has the polarity illustrated in this diagram it assists the barrier in keeping holes and electrons apart. No current flows

"To sum it up," commented Dick, breaking in at this point, "when we join a piece of P-type germanium to a piece of N-type germanium we have a device which passes current when a battery is connected to it one way round; and which passes no current—or proportionately very little current—when it is connected the other way round."

"That's exactly right," replied Smyth, "and because of this effect the device becomes nothing more nor less than a rectifier. We would, in fact, be perfectly truthful if we called it a junction germanium diode. Just so that we may continue to keep our terms correct I must now say that, when the applied polarity is such that the diode exhibits low resistance—or that it conducts—we refer to the forward current and to the forward resistance. If the applied polarity is changed round so that the diode offers very high resistance and negligible current flows, then

we have the reverse current and the reverse resistance.

"Before finishing on this particular part of the discussion I should also add that it is possible to apply too high a potential to the diode either way. If too high a potential is applied when the diode is conducting the junction may burn up, simply because the forward current is too great. At the same time, if we apply too high a potential when the diode is connected up in the non-conducting manner we may strain the crystalline structure of the germanium so much that it breaks down, and both electrons and holes become released to cause a heavy reverse current to flow. The reverse potential which is just large enough to cause this effect is called the 'turnover' potential. When either

of the two cases I have just described occurs, the diode is usually ruined.

Transistors

"We can now at long last commence to consider what happens in the transistor itself. To start ourselves off, I have sketched an N-P-N junction transistor here (Fig. 5), with no external circuit connected to it at all. The 'minus' signs in the emitter and collectors parts indicate that these are made of N-type germanium and that they have a number of wandering electrons inside them; whilst the 'plus' signs in the P-type base indicate the presence of wandering holes. As you can see, the transistor consists, in reality, of two germanium junction diodes with a common P-type block shared between them.

"The next step consists of connecting a battery, which I shall call 'battery A,' to the transistor like this (Fig. 6). As you will note,

all I have done here is to apply to the diode formed by the base and collector a potential whose polarity is such that the diode is non-conducting. The result is that, as before, negligible current flows. If, however, I add a second battery, 'battery B,' between emitter and base (Fig. 7), so that a forward current flows in the particular diode formed by these two sections, quite a different thing happens throughout the transistor. As occurred with the conducting diode we considered earlier on, battery B causes holes from the base to pass through the junction barrier into the emitter section, and electrons from the emitter to pass through the barrier into the base section. If the base section is very thin, quite a number of the electrons from the emitter will continue on through it, passing right into the collector section. We already have a positive potential from the battery terminal connected to the other end of the collector section, with the result that the ingress of extra electrons from the base becomes balanced out by an equivalent outflux of electrons from the collector into the positive terminal of the battery. We now have, therefore, two paths along which electric current flows. We have first of all the complete circuit where battery B causes forward current to flow through the diode formed by the emitter and base. Secondly, we have electrons flowing from the collector into the positive terminal of battery A. Since this second lot of electrons are, in actual fact, lost by the emitter, their deficiency is made good by having fresh electrons leave the negative terminal of battery B. The second circuit we are considering, then, is supplied by the two batteries in series—you may notice that their polarities are such that their voltages add—from whose negative terminal electrons flow to the emitter, and into whose positive terminal a similar number of electrons flows from the collector.

"Just to make the idea of the two separate circuits more clear, let's have a look at another possible set-up (Fig. 8). In this arrangement we have battery B connected, as before, between emitter and base, and polarised such that a forward current flows in the diode which these two sections form. As occurred previously, some of the electrons entering the base pass right on through to the collector. Because of this influx of electrons into the collector, a similar quantity of electrons flows into the positive terminal of battery A. At the same time electrons flow from the negative terminal of battery A into the emitter to make good those it has lost to the collector. And that's the second circuit, with its associated current, in its entirety. We have one current flowing through battery B; and we have a second current flowing through battery A. The overall effect of this

arrangement is pretty well the same as that given by the previous set-up (Fig. 7), but I think you may find it easier to visualise.

"And so we finally come to the amplifying action of the transistor. I told you it couldn't be done in a few sentences! You don't need much imagination to realise that, if the potential of battery B is increased, the flow of electrons and holes through the barrier between the emitter and base sections is going to increase also. Since the electrons entering the base from the emitter increases, the number passing through into the collector section must also become greater. The current flowing through the circuit energised by battery A will then also increase in consequence. In other words, an increase in emitter-base current causes an increase in collector current. If, similarly, we decrease the emitter-base current, the collector current decreases in sympathy.

"When the base section is made very thin it is possible for a very high proportion of the electrons leaving the emitter to carry straight on through into the collector, only a small proportion being needed to maintain the emitter-base current. Small changes in the emitter-base current may thereupon cause large changes in the collector current. We have, therefore, a basic amplifier."

"Phew," said Dick, as Smithy paused. "It all seems quite clear now. As you say, the operation of the transistor is quite a lot more complicated than that of the valve; although, as you also mentioned, this is probably mainly because you have to spend so long 'building up the background' before you actually get to the meat of the subject."

"You're right there," agreed Smithy. "Transistor operation is easy enough to understand once you've grasped the basic ideas of donor and acceptor atoms, and of wandering electrons and holes. Even in the description I've just given you, I'm afraid that the information about the structure of N and P type germanium is rather skimpy. Still, you've got to start somewhere, and what I've told you may perhaps be sufficiently intriguing to make you work backwards, as it were, by studying the atomic and crystalline structure of germanium in greater detail. At the same time I hope I've given you enough to enable you to visualise what goes on inside the transistor, and thereby more readily understand transistor circuits and design. By the way, the two types of transistor operation I've already shown you are typical of two standard modes of amplification. The first one (Fig. 7) is the basic circuit used for an earthed-base transistor amplifier, whilst the second (Fig. 8) is that for an earthed-emitter transistor amplifier. In both cases battery B represents a source of bias potential, and battery A a source of h.t.

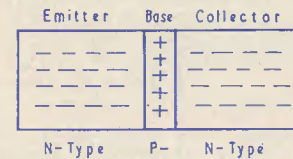


FIG. 5

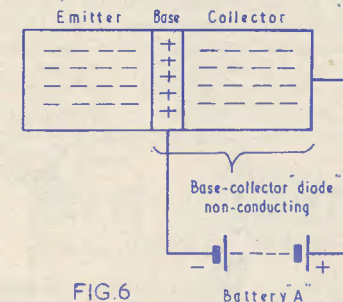


FIG. 6

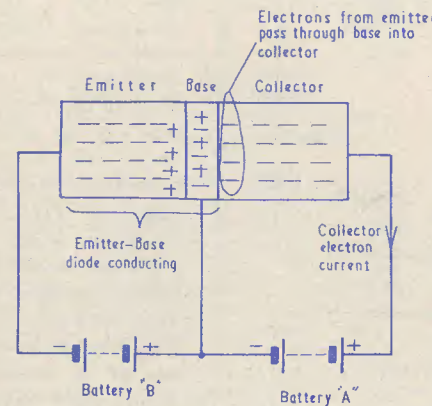


FIG. 7

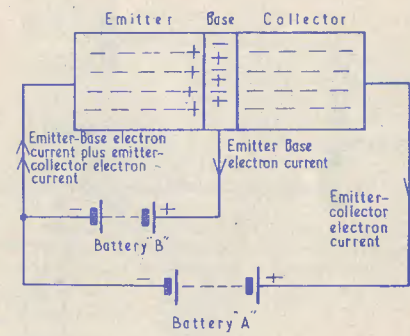


FIG. 8

E484

Fig. 5. An elementary N-P-N junction transistor. Fig. 6. Applying a potential between base and collector in the manner shown here, results in no (or negligible) current flow. Fig. 7. If a second battery, "B," is applied to base and emitter as shown, some of the electrons entering the base will pass on through into the collector. Fig. 8. A re-arrangement of Fig. 7 which may assist in visualising emitter-collector current as a separate entity

potential. If I redraw the circuits like this (Figs. 9 (a) and (b)) you will see the resemblance at once. You may note that I've also inserted an impedance, 'Z,' in series with the collector supply to form a 'load' and make the transistor fall in line with standard amplifying practice. Since, in the earthed-

emitter amplifier (Fig. 9 (b)), the negative terminals of both batteries connect to the emitter we can dispense with one, if we wish, by using a circuit arrangement like this (Fig. 9 (c)) wherein a series resistor controls the emitter-base, or bias, current which flows."

"So far as I can see," commented Dick, "a useful statement would be given by saying that, to get a transistor to work, you have to apply a potential to emitter and base such that forward current flows through the diode given by these two sections. The h.t. supply is then applied in such a manner that

N-P-N junction transistors. However, this does not raise any difficulties, as the action in a P-N-P transistor is the same as that in an N-P-N type, with the exception that all the applied battery potentials are reversed in polarity, and that the roles of holes and electrons are reversed. In the P-N-P tran-

he had already left several stubs there during the time that he had been speaking.

"I see," he remarked, "that I have once again let the time roll by whilst I have been nattering away to you. Anyway, it doesn't matter so much today, when things are quiet."

"No, I suppose not," agreed Dick, just a shade too solemnly, "and I must thank you for having also made me understand how a cathode ray tube works."

"How a cathode ray tube works?"

"Why, yes," said Dick. "I've never quite understood how the picture builds up on the screen. Now I can see that what happens is that holes leave the screen and travel back towards the negatively charged cathode. When holes pass through an aluminium backing they cause intense heat; which is why aluminised tubes give brighter pictures!"

Dick waited expectantly for a response from Smithy, but he was disappointed. For once, the Serviceman's feelings were rather too intense to be safely expressed in words.

AN EASILY SET-UP AND CALIBRATED

VALVE VOLTMETER

by A. A. TUCKER

ALTHOUGH THERE ARE EXCELLENT VALVE voltmeters on the market, the writer decided that it would be interesting to design one which would be relatively cheap to make, be easy to set up and to calibrate, and at the same time have a useful range and degree of sensitivity. A high degree of accuracy was not aimed at, but it is thought that the accuracy obtained should be sufficient for most amateur purposes.

Fig. 1 shows the basic design features of what is, in effect, a form of peak valve voltmeter.

The valve is an indirectly heated a.f. power amplifier, which is biased by the potential developed across R_4 to operate at the point of cut-off, indicated by a sensitive meter in the anode circuit. A resistor, R_2 , is also included in the anode circuit, primarily to form an a.c. filter in conjunction with C_1 , but also to act as a guard for the meter. Here it may be noted that an ordinary good grade voltmeter set to a suitable range may be inserted between the terminals shown, thus avoiding the expense of another meter. The resistor R_1 completes the bias circuit whilst maintaining a high input resistance.

The h.t. supply must be smooth, quiet, constant and isolated—in a d.c. sense—from earth and the mains.

When a steady voltage is applied to the test terminals, the meter will indicate a flow of anode current. The purpose of R_5 is to enable a variable and known voltage to be applied in opposition to the measured voltage. When both are equal, the anode current will have been restored to zero. By providing a linear scale around the potentiometer spindle, the unknown voltage may be read off directly. In the case of alternating voltage measurement, peak values are indicated and, to correct to r.m.s. values in the case of sinusoidal waveforms, the scale reading must be divided by $\sqrt{2}$. The resistor R_5 determines the range of the instrument. In the

diagram (Fig. 1), R_5 is shown as $2k\Omega$, and when 10mA passes through it 20V will be developed across it, therefore giving a range of 0-20V. Other values for R_5 and the current through it may be chosen to obtain a desired range.

Setting Up and Calibration

Turn R_5 to "Zero Volts" and R_4 to maximum resistance. Switch on h.t., when the meter should show zero anode current. Reduce the resistance of R_4 until current begins to flow, then increase again until current reaches zero—the valve is now at the cut-off point. Next adjust R_3 until 10mA flows through R_5 —a suitable meter will have to be inserted in series at the h.t.—end to indicate this. Then re-set R_4 to restore the cut-off point.

Repeat this procedure until both adjustments are simultaneously correct. Hereafter, it will only be necessary to set the cut-off bias before use by a slight adjustment of R_4 , whilst R_5 is at "Zero."

Increasing the Range

Fig. 2 shows how the instrument may be given a more comprehensive range on four scales, i.e. 0-200V by means of switch S_1 in the $\times 10$ position and S_2 in the $\times 1$ position; 0-20V, S_1 at $\times 1$ and S_2 at $\times 1$; 0-4V, S_1 at $\times 1$ and S_2 at $\div 5$; 0-1V, S_1 at $\times 1$ and S_2 at $\div 20$.

Sensitivity and Accuracy

The sensitivity of the voltmeter is influenced by the sensitivity of the meter movement and the g_m of the valve.

Assuming that the current through R_5 has been truly measured, the accuracy of the meter depends only on the accuracy of the resistors used and upon the accurate division of the potentiometer scale—this only applies except when high radio frequencies are involved. At these frequencies it is the practice to employ a diode rectifying probe in front of the test terminals.

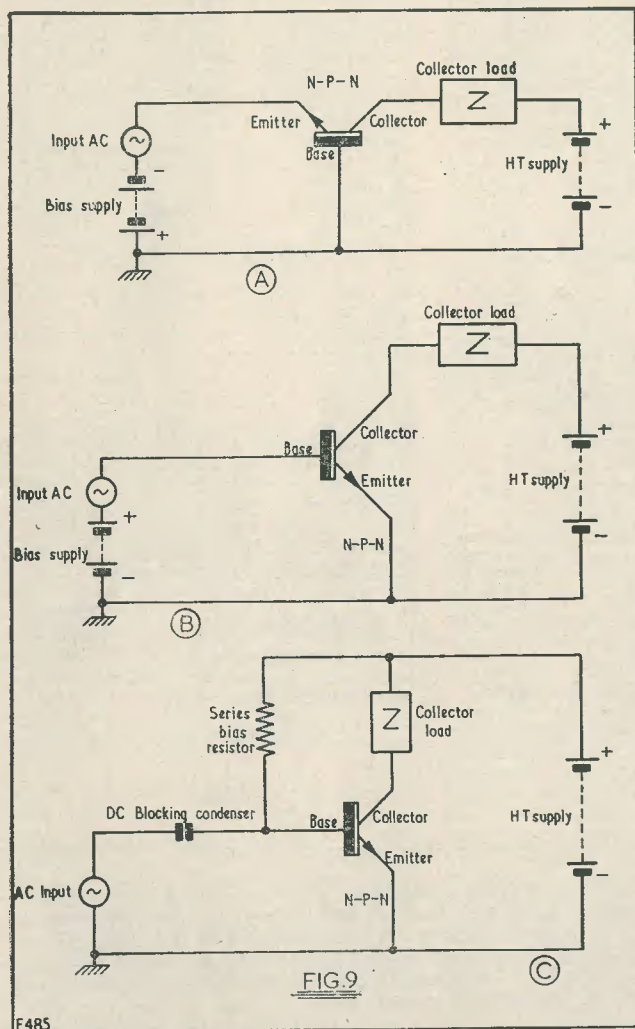


Fig. 9 (a). An earthed-base transistor amplifier. This is the same as Fig. 7, with the exception that a "generator," to represent signal input, and a collector load have been added. Fig. 9 (b). An earthed emitter transistor amplifier. Apart from the addition of the "generator" in the input circuit and the collector load this is the same as Fig. 8. Fig. 9 (c). An alternative version of (b), wherein we may dispense with the bias supply battery by the use of a suitably valued series resistor. The blocking condenser prevents the input generator from altering the d.c. potential existing between base and emitter

the diode formed by the collector and base would normally be in the non-conducting state."

"That seems to tie it up fairly neatly," agreed Smithy. "And there is just one final point. Up to now I have only mentioned

sistor it is holes which travel through the thin base section and, thence, into the collector."

A Further Explanation


Smithy put his cigarette out in the ashtray at his side, and seemed surprised to note that

Construction

Details of construction are hardly necessary for such a simple circuit, but the following points should be borne in mind.

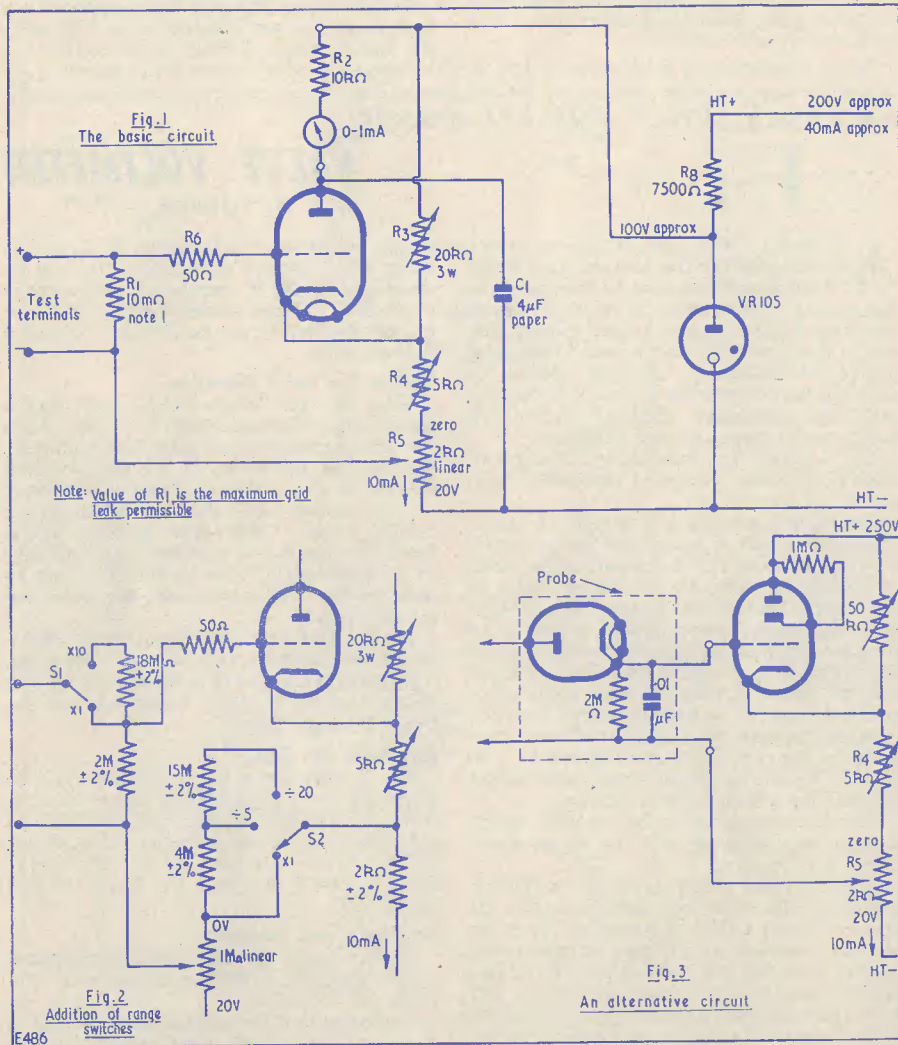1. Avoid unwanted pick up by making use of adequate screening.
2. Keep grid wiring short.

bine the function of the valve and the meter by using a magic eye indicator, as shown in Fig. 3. The bias developed across R_4 in this circuit is adjusted to close the angle of target illumination to 0° under zero input conditions. When a voltage is applied to the input, the screen illumination will open. R_5 is



3. If an external power supply is used, screen the supply leads connecting the two units.

Another Suggested Circuit


A variation on the same theme is to com-

then adjusted to close the shadow to zero angle again, and the voltage is read off the scale in the same way as in the previous circuit. A rectifying probe is again necessary for alternating voltage measurements.

Radio Miscellany

THE RECENT DISCUSSION IN THIS COLUMN regarding the unimaginative sameness of most modern receivers brings a letter from Mr. J. E. Fogg of Whitburn, Co. Durham. His individual ideas have found expression in an interesting composite receiver allowing scope for immediate experiment and, at the same time, providing for easy modification to bring it into line with his subsequent needs. His receiver comprises six main parts, each of which can be easily handled and brought to the stage of maximum efficiency.

The detector stage is from the circuit of the *Quality Tuner* (June 1955), but instead of a magic eye an 0-10 millimeter is inserted in the second i.f. anode lead. The i.f. amplifier itself is an exact duplicate in valves and design of the *Clipper* (April 1955). The coils are Osborn, which J.E.F. praises highly for neatness and efficiency, and the tuning circuit is again from the *Quality Tuner*, and is made mostly from components culled from an R.F.26 Unit. The i.f. circuitry is that of the "Micro-amp" (September 1955), and the power supply is from the *Globemaster* (December 1954).

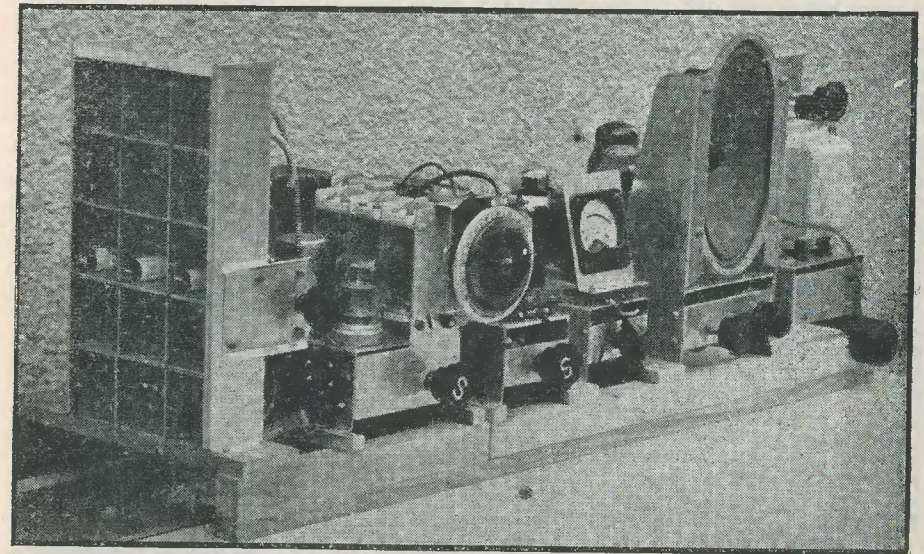

Reader J. E. Fogg's Receiver

A photograph illustrating how he has put his ideas into practical form appears on this page. Sections of various receivers taken from *The Radio Constructor* descriptions have been adapted or modified to suit both the gear in hand or to conform to his personal conception.

Additions already on schedule are the noise limiter from the *Voyager* (January 1954), the *Electronic Selectivity Filter* (April 1954), and a b.f.o. using an acorn valve.

J.E.F.'s approach to his individualist set serves as an excellent pattern for the keen constructor with a taste for experiment. Each

stage of the receiver can be brought to perfection, while at the same time a lot of practical knowledge is acquired. Nor need it be expensive. In his particular case only the coils, mains transformer and speaker were new—virtually everything else is ex-W.D. To my mind this is amateur radio at its best. Every receiver consists of a number of minor circuits each doing its separate job. There is no surer way of learning to evaluate each stage when it is met in the multi-stage receiver design to which a keen interest in radio inevitably leads.

Mr. L. Sergeant (Newton-Le-Willows—no small town this, you southerners: pop. just under 22,000), although no old-timer himself, is greatly interested in the types of gear used in the early days of the century. He also sent along Part 16 of *Harmsworth Wireless Encyclopaedia*, which he recently acquired. This came out in 1923 in about 30 fortnightly parts. Here we find apparatus of the period in all its glory, with a four R-type valve set appearing on the cover, which with 'phones, horn-type loudspeaker, and rotating table aerial looks for all the world like a

CENTRE TAP

talks about

Items of General Interest

The Golden West

Many of the readers who appeal for assistance in the way of data or special components through the medium of "Can Anyone Help" later write of their gratitude and pleasure at finding so much good fellowship among constructors. It has been noticeable recently that quite a goodly proportion of these letters especially mention the West of England as the most fruitful source of response. I recall, only a few months back, Mr. Gilbert Davey (of Kenton) mentioning that all the best specimens of early type valves came from that part of the world. He jokingly asked whether people down there hang on to their sets much longer, or are they more cautious in dumping their former "good servants" in the dustbin?

The fact that help in other directions also appears to be readily forthcoming from enthusiasts in the western counties seems to suggest that they are generally more friendly and have a stronger sense of the fellow-hobbyist spirit than elsewhere. It would be interesting to know if this is general, or whether it has just happened in the few particular cases that have come to my notice.

Days of Yore

My recent paragraphs about long-service hobbyists brought in quite a number of interesting letters. No new records are claimed, so it appears that the veterans already mentioned must be considered the most senior. A few readers found themselves reminded of early apparatus built by fathers and uncles. Perhaps it is well now and again to ponder on things that are fast becoming forgotten. Our up-to-the-minute sets will look just as laughably absurd to coming generations.

section of a small power station. Unit construction was the thing in those days. Tuning unit, detector unit and each amplifying stage were built in their own separate wooden boxes, each fitted with a row of lacquered brass terminals. These were connected to the corresponding terminals of the next unit, and all the best constructors used stout brass strips with slotted holes to connect their many units together.

Stand-by


This particular part also contains an article on how to build a "3-valve Neutrodyne Receiver on Prof. Hazeltine's Principle," complete with a three-fold photogravure plate. I remember such receivers well. One didn't operate them—one manipulated them. After a few minutes of adjusting everything with the most delicate care (remember, too, each valve had its own rheostat), a signal of reasonably satisfactory level could be obtained. Holding one's breath one tried cautiously to move back, but before one got a full pace, something happened. While standing over it, it behaved itself (more or less), but however cautiously the attempt to withdraw was made, it immediately "spilled over." This meant the most horrible shrieks emanated from the loudspeaker trumpet, and all the young children within a radius of 100 yards ran screaming to their mothers. Wise-aces told us it was due to the capacity of our bodies in proximity to the set. Hence we "earthed" ourselves with a flexible wire, but it made no difference. We knew better. It wasn't body capacity. It was sheer temperament!

(continued on page 117)

the 'THREE-DEE' 3 transistor receiver

Described by

JAMES S. KENT

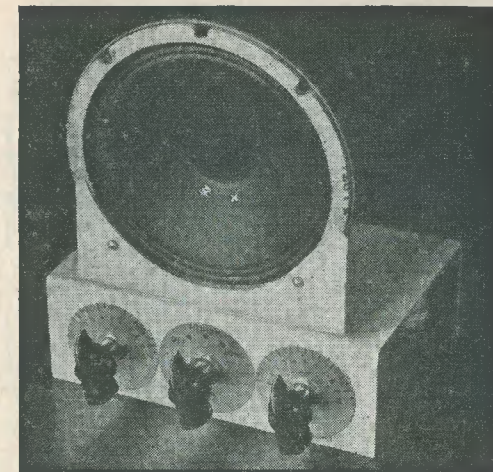

THE DEMAND AMONG THE HOME constructor fraternity for transistor receiver designs continues unabated, with the result that numerous prototypes are being built and the resultant end products placed on the market for purchase by the hobbyist. The present design, about to be described, is available in complete kit form from Radio Experimental Products Ltd. and other advertisers.

The "Three-Dee" transistor receiver has been primarily designed to meet the need for an economical local station set. It is ideal for caravan installation, as a bedside receiver, the workshop or as a second domestic radio. In the prototype shown herewith, the speaker is mounted on the chassis by means of a small piece of aluminium cut and shaped to suit the speaker—an Elac 5in type. Normally, the kit is not supplied with this type of speaker mounting, it being a very simple matter for the average constructor to make this mounting. The speaker output is taken to a socket panel on the rear of the chassis, thus allowing the speaker to be mounted in the required position according to the cabinet, or other enclosure, chosen by the individual constructor.


Whilst surplus transistors were used throughout in the original model, the quality of output may be somewhat improved by fitting a Mullard type OC72 transistor in the output stage.

With the "Three-Dee," an aerial and earth system is necessary; the length of aerial

largely depends on local station reception. Where signals are inclined to overload the receiver, a series aerial condenser of between 100 and 500pF may be fitted. Where a short aerial is used, a similar value condenser may be fitted between the two green tags of the respective aerial coils.

Component List


R ₁	220kΩ ¼ watt
R ₂	100kΩ ¼ watt
R ₃	6.8kΩ ¼ watt
R ₄	10kΩ ¼ watt
R ₅	47kΩ ¼ watt
C ₁	500pF variable, mica dielectric
C ₂	500pF variable, mica dielectric
C ₃	2μF, electrolytic, 150V wkg.
C ₄	2μF, electrolytic, 150V wkg.
C ₅	2μF, electrolytic, 150V wkg.
C ₆	100μF, electrolytic, 25V wkg.
	Speaker, Elac 5in, 3Ω
	Transistors, Red Spot type
	Type DRR2 coils, Repanco Ltd.
	Socket Panels (2)
	Crystal Diode
	7½V battery
	Chassis, Repanco Ltd.
	Yaxley switch, 3-pole, 3-way
	Tag Board, 8-way
	Output Transformer, type TT5, Repanco Ltd.
	3 Dial plates, Repanco Ltd.
	Battery plug

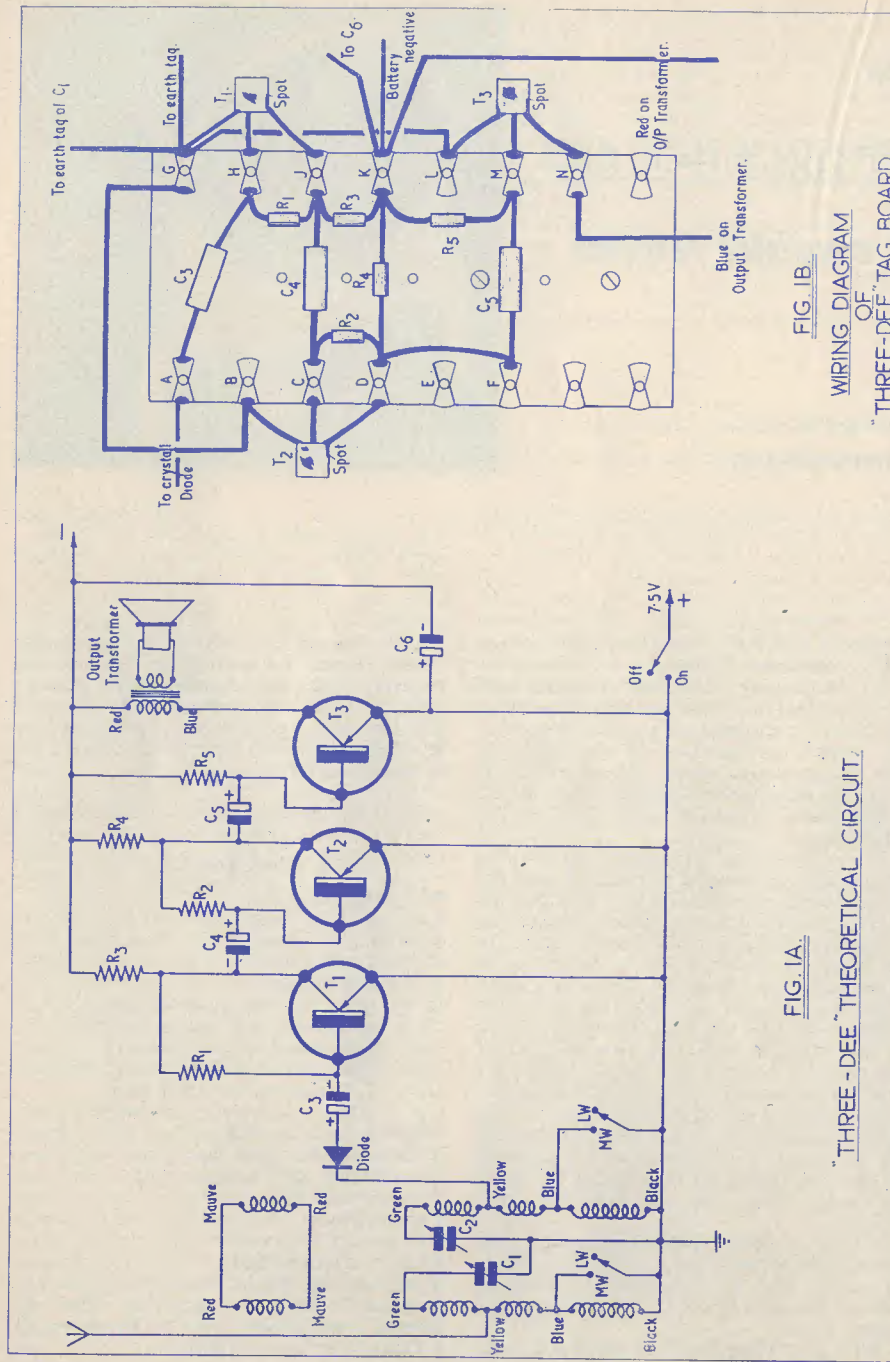

C 444

FIG. IB.
WIRING DIAGRAM
OF
'THREE-DEE' TAG BOARD.

FIG. IA.
'THREE-DEE' THEORETICAL CIRCUIT.

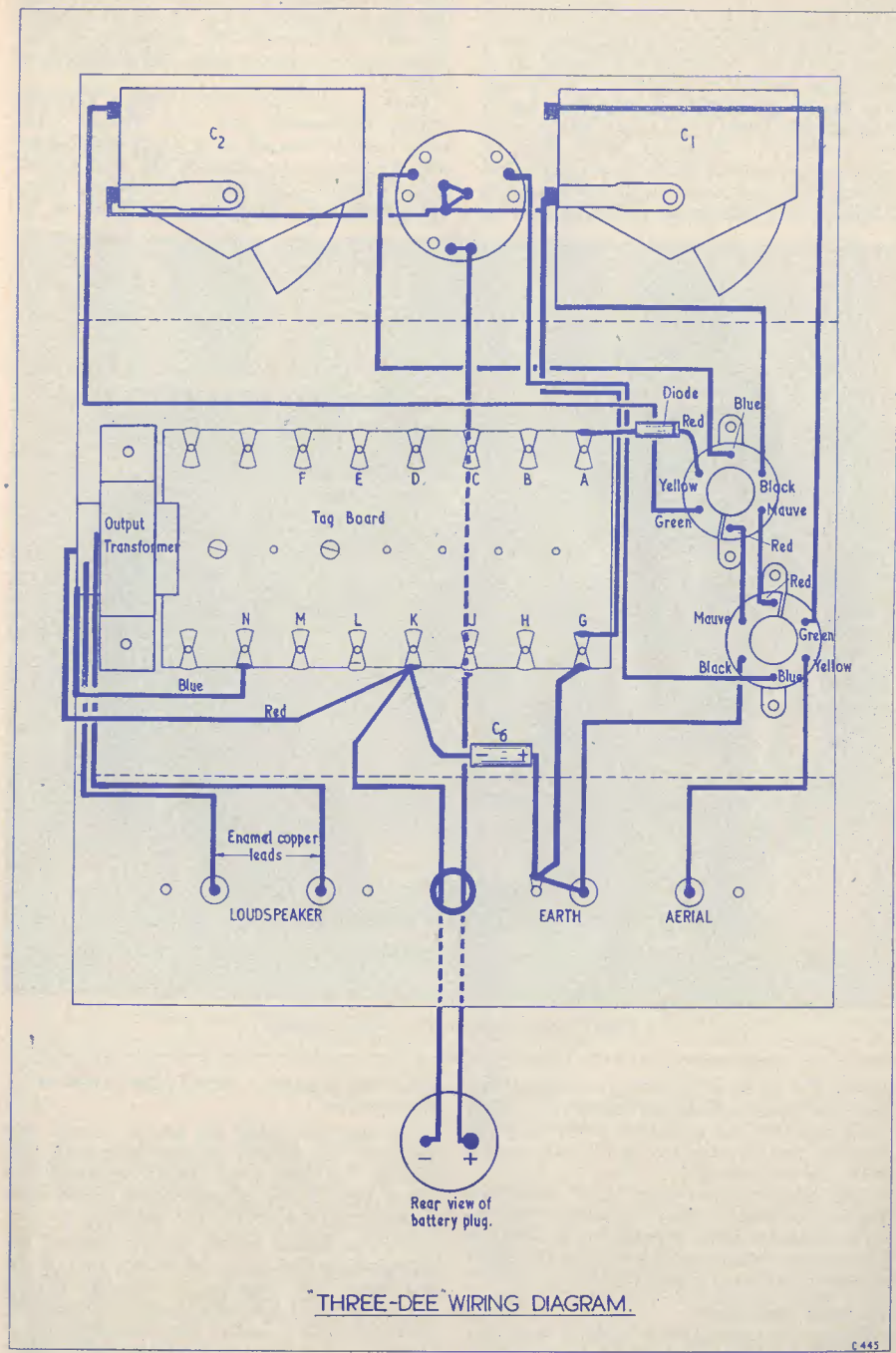

C 445


'THREE-DEE' WIRING DIAGRAM.

Circuit

This is shown in Fig. 1(a), from which it will be seen that it comprises a bandpass tuned crystal diode as the detector followed by a three stage transistor amplifier. It will be noted that each coil of the bandpass circuit is independently tuned by a single 500pF variable condenser. This has been done in preference to the more conventional method of utilizing a two-gang component, both in order to achieve the maximum sensitivity and to

even by the beginner. It should be noted here that the tag board is wired up before mounting into position on the underside of the chassis—the wiring process being described later.

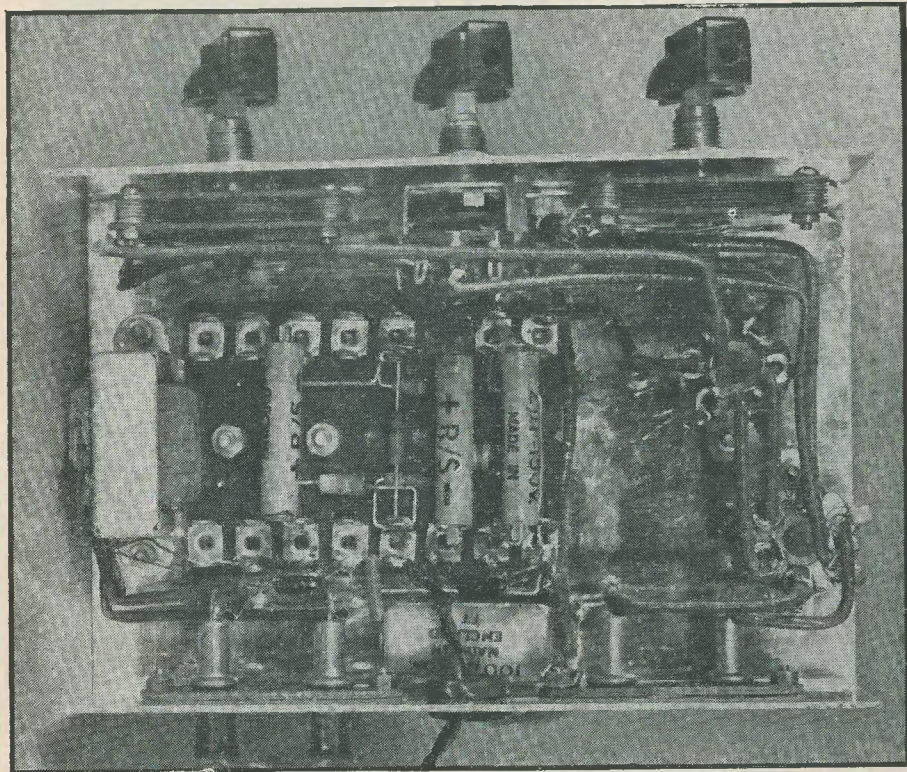First, mount both of the 500pF variable tuning condensers and the Yaxley type switch on the chassis front drop, not forgetting to place into position the dial plates before finally tightening the fixing nuts. Note from the photograph the positions of



Under chassis view—see wiring diagram

obtain the greatest selectivity without the need for using additional trimmers. Both Long and Medium waves are covered by the receiver, the wavechange switch also acting as the on/off control.

The output from the three transistor cascade amplifier, each working in the earthed emitter mode, is sufficient to effectively drive the 3 ohm speaker via the transistor output transformer type TT5.

Assembly Instructions

These are quite simple and, if carefully followed, no difficulty should be encountered

these components. Next fit the knobs on to the spindles.

Having completed the above, mount into position, by means of the 6BA nuts and screws, the two type DRR2 coils—noting from Fig. 2 the alignment of these with reference to the slots in the tag rings.

Fit the socket panels on the rear of the chassis with 6BA nuts and screws; that on the left-hand side, looking at the rear of the receiver, being the aerial/earth connections, and the other being the speaker output sockets. A solder tag should be fitted under

the nut nearest the external earth connection (see Fig. 2). Place into position the $\frac{1}{16}$ in rubber grommet in the hole between the socket panels.

This completes the assembly instructions—the output transformer being fitted later with the tag board.

Wiring the Receiver

Carry out the wiring as shown in Fig. 2 to those components which have already been fitted. It is best here to commence with the wavechange switch and follow with the variable condenser wiring. Leave the leads to A, K, G and N to be fitted later, when the tag board is mounted. Having done this, solder into position the crystal diode—the red end of which should be soldered to the yellow tag of the coil. Careful attention to Fig. 2 will ensure that no errors are made with reference to the above.

Having carried out the wiring so far, continue by wiring up the tag board as shown in Fig. 1. This is self-explanatory and no further instructions are, therefore, required. Great care must be observed when soldering the transistors; the wire ends should be held with pliers between the actual transistor body and the point of soldering—the pliers thereby forming a heat shunt and thus avoiding damage to the transistors themselves.

Fit the tag board to the chassis with the four 4BA nuts and the 2 screws, using the extra 2 nuts to space the tag board away from the underside of the chassis deck. Fit these

screws into the last and the third holes from the unused tags on the tag board (see Fig. 1).

With the above completed, next wire in the previously missed leads A, K, and G to the appropriate tags on the tag board. Solder into position C₆ from point K on the tag board to the earthed solder tag, taking care that the positive end of this condenser is connected to the earth side.

The next step is to fit the output transformer to the chassis by means of two 6BA nuts and screws; note from Fig. 2 the orientation of this component. Solder the red lead of the transformer to point K of the tag board and the blue lead to point N. Next solder the output leads of the transformer to the speaker output strip terminals. The black lead of the output transformer is not used in this circuit, and it should, therefore, be left disconnected and preferably be taped in order to avoid contact with the chassis, etc.

This completes the wiring of the receiver circuit. The next step is to connect the speaker, aerial and earth and the battery, and to try out the receiver on either the Medium or Long wave bands.

It will be found that this receiver will work very well with an external "throw-out" aerial, but the addition of a good earth connection will result in greatly increased signal strength. The length of the aerial will largely depend on the actual location of the individual constructor but, generally speaking, some six to eight feet should suffice in the majority of cases.

Can Anyone Help?

Requests for information are inserted in this section free of charge; subject to space being available

M. KEOGH, Willowbeck, Planetree Road, Hale, Cheshire, asks if any reader can supply data concerning the ex-Govt. Wireless Set No. 17, Mk. 2, in particular relating to its operation on the Amateur bands.

C. E. REES, 83 Mirador Crescent, Upton Lea, Slough, Bucks., would like to obtain data or circuits for the Wayfarer "Major" and the American Wards Airline Radio No. 14BR-684A.

W. A. COLLIN, 42 Pellatt Road, East Dulwich, London, S.E.22, wishes to obtain circuits and details of conversion of the U.S.A. Command Receiver type BC.455B to make it suitable for use as a car radio on MW.

J. SANGWOOD, 187 Brettell Lane, Stourbridge, Staffs, would like to borrow, if possible, the circuit and data on the BC.624A Receiver.

A. R. HAGGARTY, 55 Finsbury Park Road, London, N.4, would like particulars of the Service type Signal Generator/Wavemeter G.73, and would like to purchase any service data regarding this equipment.

WAYNE WHEELER, KL7DR, Box 903, Anchorage, Alaska, wishes to obtain details of the "ZL Special" 135° Beam Antenna. These were given in the *Short Wave Magazine*, July 1950 issue, but this is now unobtainable from the publishers.

L. C. LUCAS, 36 Lindfield Road, Ealing, London, W.5, would like to borrow or purchase data and circuits relating to the R.A.P. "Transatlantic" 5-valve LW, MW, 2-SW receiver and the Ferguson 372A LW, MW, SW and FM receiver. He can lend full data for the Philco A537 and the Regentone Multi 99.

(continued on page 115)

SIMPLIFIED LOW-DISTORTION DETECTOR

by D. E. PASFIELD, Ass. Brit. I.R.E.

THIS CIRCUIT MAY BE OF INTEREST TO readers who are in a reasonably good service area for medium and long wave reception, as it can be built cheaply and is an excellent introduction to hi-fi. The circuit to be described is simplicity itself and uses the minimum of components.

It is basically an r.f. stage followed by a diode detector directly coupled to a cathode follower. The qualities of the diode and infinite impedance detectors are well known, both with their advantages and disadvantages, and will not be enlarged on here. Let it be said that this circuit combines both the advantages and considerably less of the disadvantages.

The excellent performance is due primarily to two facts:

1. The diode load for normal a.m. carrier frequencies is essentially resistive, and the effects of excessive shunting capacity is eliminated.
2. As coupling to the cathode follower is direct, there are no biasing current effects as developed in a normal diode circuit using condensers.

The distortion figures, which can be seen from the graph, are 0.3% at 400 cycles and 0.8% at 4 kc/s at 100% modulation.

The r.f. stage for preference is a 6BW7. This valve was designed originally for t.v. circuits and has a very high input impedance, and considerable damping can be used with still useful gain. A 12AT7 is used for the next two stages, one half strapped as a diode, the other half as a cathode follower. Obviously, these are not critical and any similar type of diode and triode can be used.

It must be stressed that in all circuits of this type strict attention must be paid to adequate screening, otherwise the circuit will not be stable.

As to the performance of the circuit, this can be assessed from the following comments.

The writer lives in Daventry within one mile of 11 high power short-wave transmitters, one radar station, one aircraft beacon (within the medium-wave band) and several national grid systems!

The aerial used is 70ft long, 36ft high at one end and 8ft at the other, and the Home, Light and Third programmes are received even during darkness with quality and absence of noise which could even be the envy of f.m.

In spite of the strong local r.f. field, no cross modulation or other effects have been noticed; in fact, any short-wave signals tend to favour the feedback circuits of the l.f. amplifiers.

This is a thing which the writer also has to contend with, and l.f. screening has to be of a very high order also.

All listening has been done on a Williamson amplifier with a Wharfedale three-speaker system, and the absence of background noise between items is quite remarkable for a.m. signals.

It must be remembered that the writer is about 40 miles from Droitwich for Light and Home programmes.

The unit is also used for high quality tape recordings and the results are such that the writer no longer feels he ought to buy commercial records.

Component List

R₁, R₂ Between 50kΩ and 100kΩ according to available signal strength. Adjustment made under operating conditions

R ₃	15kΩ ½ watt
R ₄	250Ω ½ watt
R ₅	4.7kΩ ½ watt
R ₆	250kΩ ½ watt
R ₇	15kΩ ½ watt
R ₈	10kΩ ½ watt
R ₉	1.0MΩ ½ watt
C ₁	500pF, 2-gang
C ₂	0.1μF, 350V
C ₃	0.1μF, 350V
C ₄	0.1μF, 350V
C ₅	8μF, 450V
C ₆	100pF
C ₇	0.1μF, 350V

Coils: Weymouth iron cored

Switch: 4-pole 2-way

Valves: Brimar 6BW7, 12AT7

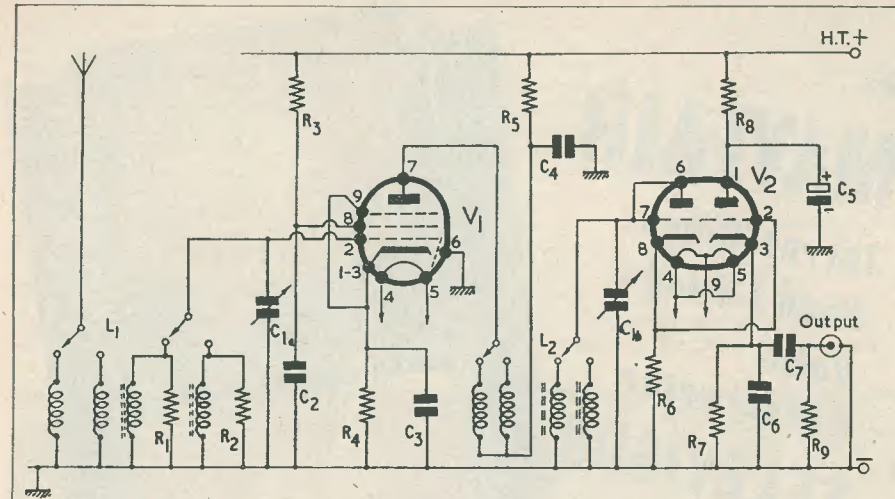


FIG. 1

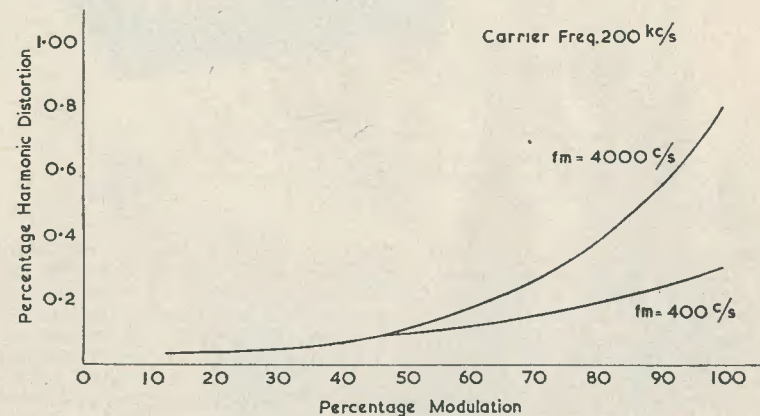


FIG. 2

M.451

BOUND VOLUMES

A limited number of bound volumes (Vol. 10 only) are available,

price £1.5.0. post 1/9

DATA PUBLICATIONS LTD

INDEXES

for Volume 10, August 1956—July 1957 are now available, price 6d. post free.

READERS' OWN COPIES

can be bound by us for 10s. 6d. postage and packing 1s. 9d. extra (index supplied free).


This offer does not apply where readers wish to remove pages.

57 MAIDA VALE LONDON W9
Telephone CUN 6141 (2 lines)

The

MAYFAIR

Turret Tuned Band 1-Band 3 Home Constructor TELEVISOR

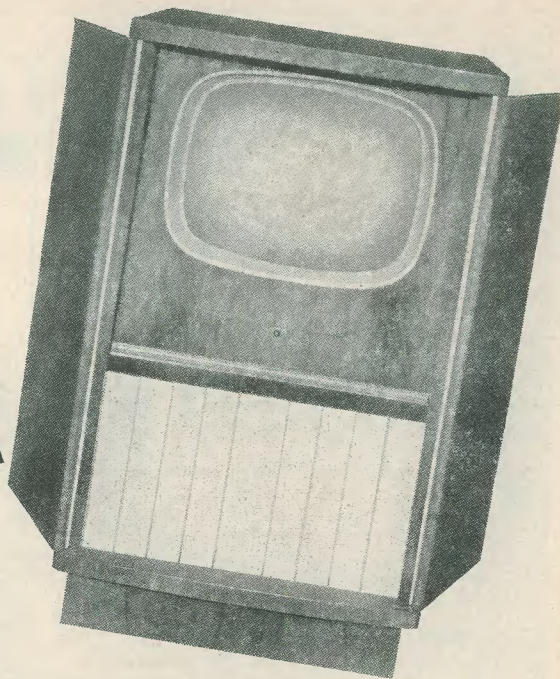

PART I

by S. WELBURN

Our popular contributor on television topics, S. Welburn, returns to introduce a receiver designed expressly for the home-constructor

READERS MAY RECALL THAT, JUST BEFORE the writer finished his previous series of articles on the subject of television, he stated on several occasions that there was a dearth in television receivers designed for the home-constructor. Since the time when his comments appeared in this magazine, he has had much evidence to show that there is, nevertheless, a very considerable demand for an amateur-built television, and he has adjusted his line of thinking in consequence.

Unfortunately, the business of presenting a home-constructor television is not so easy as it may at first sight appear. A large number of difficulties have to be overcome, and it is symptomatic of the present television scene that the question of circuit design constitutes one of the lesser obstacles.

Home-Constructor Receivers


Before proceeding further it might be worth-while studying, from a basic common-sense angle, the several factors which affect home-constructor t.v. receivers. First of all, it is obviously very desirable that a home-constructor design must be capable of being

built at a cost which is not excessive. Although much pleasure and pride may be obtained from the efficient working of a piece of equipment which has been built completely at home, it would be uneconomic for the amateur to embark on the construction of such equipment if its overall price were markedly higher than that of a commercially produced equivalent. The days of relatively expensive commercial televisions are now over, and complete sets are being offered at prices which are extremely competitive when compared with home-built receivers. Some of the amateur designs which appeared a number of years ago, although capable of good results from a technical point of view, are unattractive these days purely from financial considerations. It is true that these receivers can still be built without too great an outlay by those constructors who have many of the parts, such as resistors, condensers, valve-holders, etc., already on hand, but this state of affairs is not general. It follows from the above that, for an amateur design to be successful and worthwhile, it *must* be economic from the cost point of view.

A second point, and one which is equally important, is concerned with the availability of components. As the television trade stands at present, commercial receiver manufacture is proceeding at a considerable rate, and many makers of television components are fully occupied in feeding their output to the assured market which this manufacture entails. Some of the component makers who supply to home-constructor markets may not be fully prepared to embark on the manufacture of television components, where they have not done this before. A safe statement would be given in this context by saying that the manufacture of television components normally involves working to very tight specifications, and that it requires a con-

siderable amount of know-how, plus expenditure on factory and test equipment, if it is to be fully satisfactory. We therefore have the case where the supply of television components designed specifically for a particular home-constructor application may be limited to the rather small number of firms who have established themselves in this field, and who have not dropped out in the last five years or so.

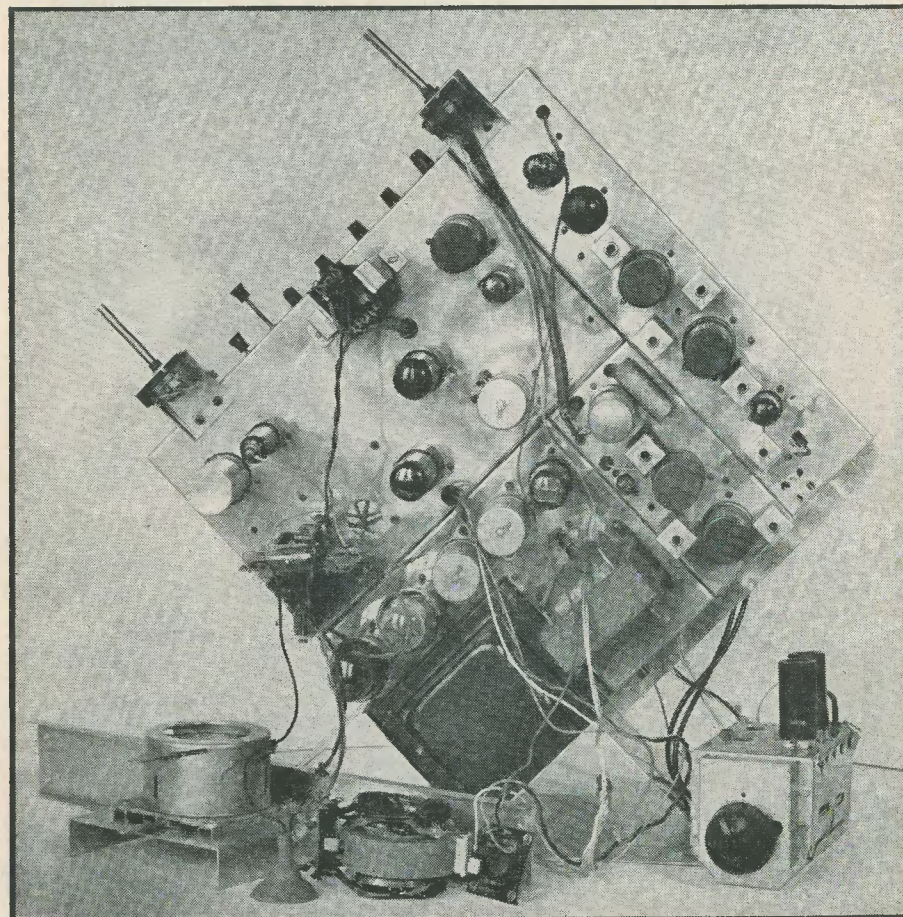Also under the heading of availability of components comes the question of component distribution to retailers. As will be apparent from the paragraphs which follow, not only this but the preceding points have been taken up with regard to the "Mayfair" television.



Top view of the Mayfair Television, showing the various chassis assembled together in one easily serviced unit

The Mayfair

The Mayfair receiver is a televisor which, as well as providing efficient reception and a picture of excellent definition, also meets the requirements just dealt with. As can be gathered from the advertisers' announcements in this issue, the cost of construction is very competitive when compared with commercial receivers. The design of the set is based very largely on the Premier "Design I" televisor, and Premier components are specified in the parts lists where these are particularly applicable to the Mayfair circuitry. *It must be emphasised that all components for the Mayfair are available to the general trade and may accordingly be pur-*

chased where advertised. An innovation is a turret tuner, this being available as a complete item fitted with coils for whatever channels in Band I and Band III are required by the purchaser. Normally, one Band I and three Band III channels are supplied according to locality. The turret tuner is *not* made up by the constructor. Instead, it is obtained as a completely built and aligned unit which has been set up on factory test equipment to the appropriate frequencies. It is worth pointing out that the turret tuner is, basically, exactly the same model as is used in many commercial receivers, and that worries about oscillator drift and frequency response can, in consequence, be forgotten.

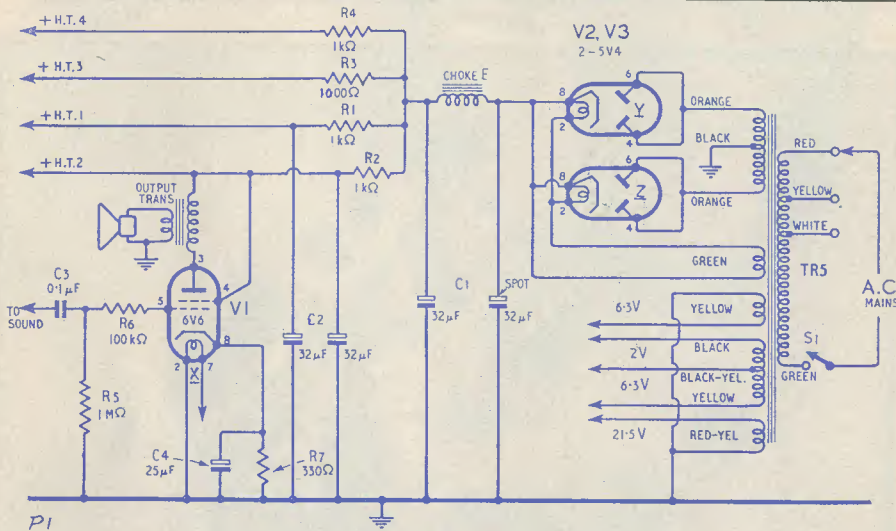


Fig. 1. The circuit of the power pack and sound output stage

Resistors

R₁, R₂ 1kΩ, 4 watt, wirewound
 R₃ 1kΩ, 12 watt, wirewound
 R₄ 1kΩ, 1 watt
 R₅ 1MΩ, ½ watt
 R₆ 100kΩ, ½ watt
 R₇ 330Ω, 1 watt

Condensers

C₁, C₂ 32 + 32μF, 350V wkg., electrolytic. With clips for vertical mounting
 C₃ 0.1μF, 350V wkg., paper
 C₄ 25μF, 25V wkg.

Valves

V₁ 6V6
 V₂, V₃ 5V4

Transformers and Choke

1 mains transformer type TV5 (Premier Radio)
 1 sound output transformer (Mayfair type) (Premier Radio)

1 smoothing choke (Mayfair type) (Premier Radio)

Chassis and Chassis Components

1 power unit chassis, fully punched (Premier Radio)

3 valveholders, international octal
 1 voltage selector panel (Premier Radio)
 3 5-way tag-strips (end tag earthed)
 1 3-way tag-strip (end tag earthed)
 1 2-way tag-strip

Miscellaneous

2 grommets
 1 yd 2mm sleeving
 1 yd tinned copper connecting wire (22 s.w.g.)
 Mains lead and inter-chassis P.V.C. covered wire.*

Nuts, bolts, solder tags, etc.

* The mains lead and P.V.C. covered wire are employed at a later stage.

The Mayfair receiver is, itself, a superhet and employs comprehensive vision and sound i.f. circuits. The coils for these are pre-aligned, with the result that, so long as reasonable care is employed in following the specified layout, no test equipment is needed to bring the receiver into working order after completion. The vision i.f. is 16 Mc/s, and the sound i.f. is 19.5 Mc/s.

The timebase section employs blocking oscillators both in frame and line circuits.

the circuitry to obviate cross-talk between line and frame coils.

The power pack is generously designed and employs components which are more than adequate for the job they have to carry out. Of particular importance is the fact that a mains transformer with isolated h.t. and l.t. secondaries is included. This component ensures that the chassis is completely isolated from the mains supply, and that the risks of shock associated with the con-

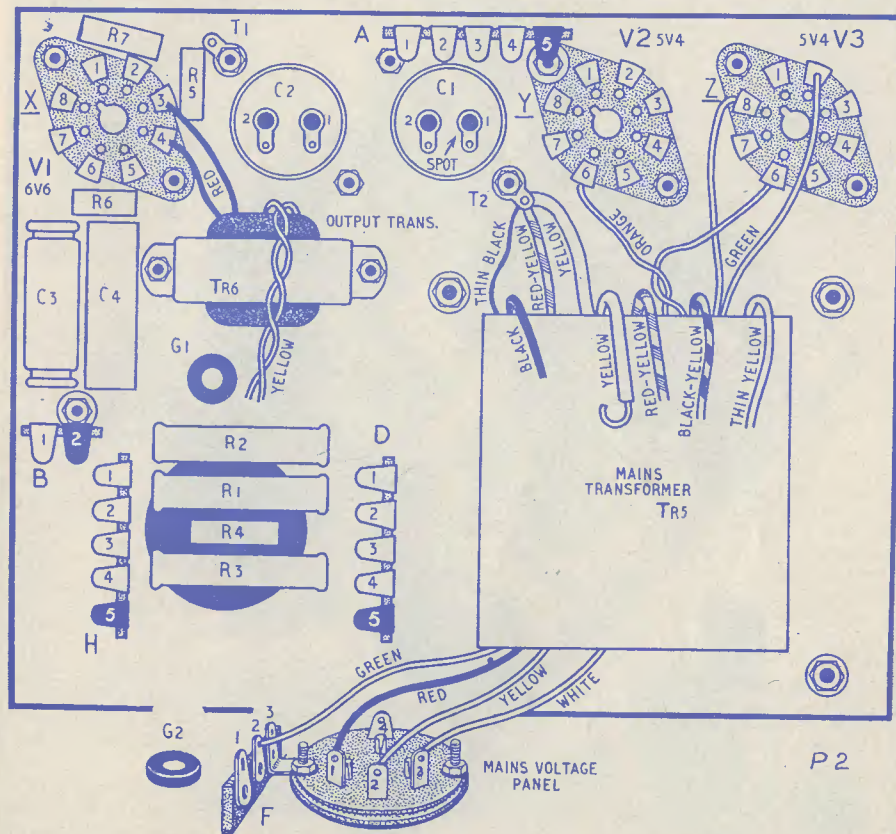


Fig. 2. Layout of the power pack unit below the chassis


Linearity controls are provided for both these circuits, in addition to the requisite height and width controls. A reliable and well-proven line output transformer is employed in the timebase unit, and this provides an e.h.t. voltage suitable for any modern 14 or 17in 70 degree cathode ray tube. The deflector yoke is similarly reliable in design and performance, and care has been taken in

ventional a.c./d.c. type of receiver are entirely eliminated.

The complete receiver is built up in units, these being comprised of the following: the power pack chassis, including the audio output stage; the vision i.f. strip with the video output stage; the sound i.f. strip; the timebase chassis; and the turret tuner. Apart from the turret tuner all these sections bolt

together to form the complete chassis shown in the photographs which accompany this article. The turret tuner is connected to the main chassis by flexible leads and is intended for mounting in the televisior cabinet. The various items of metalwork which make up the receiver are, incidentally, available in

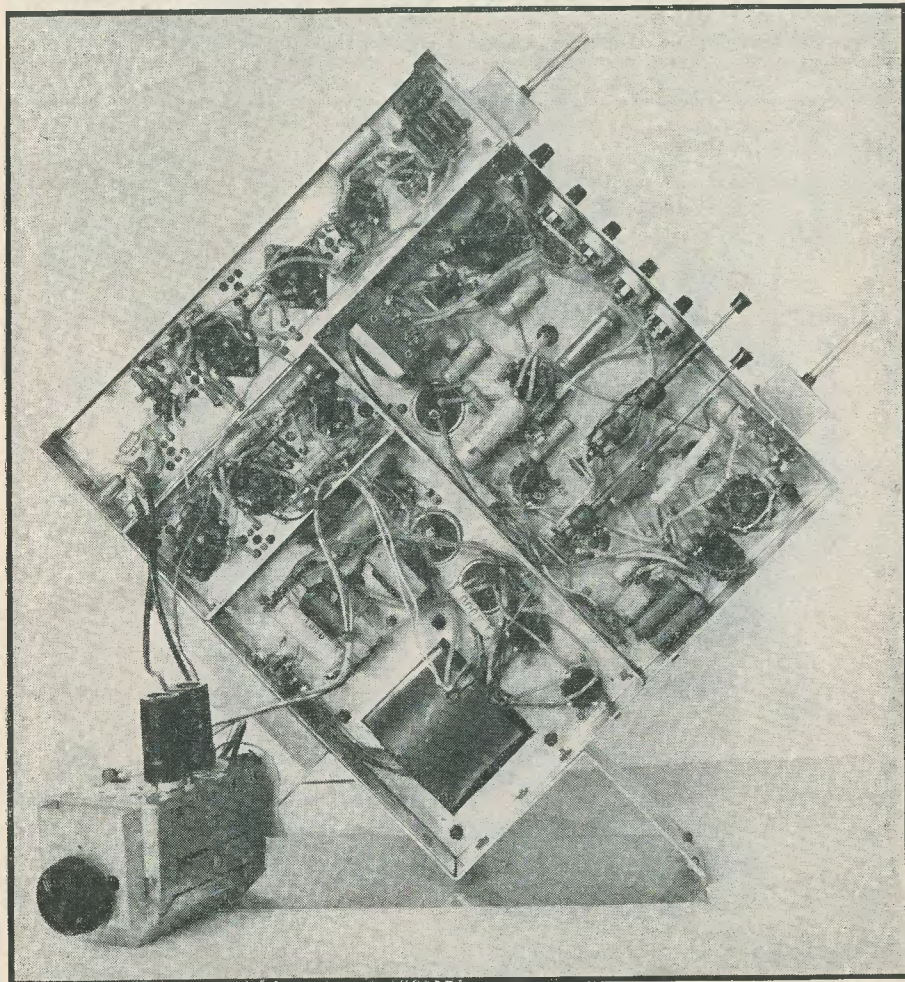turers' lists, are also available via ex-Government sources. Thus, EF50's are employed in both the sound and vision i.f. strips where no advantage would be gained, performance-wise, from the use of B7G or B9A equivalents. In the same manner, octal-based valves are used elsewhere in



Another view of the Mayfair Televisior assembly, showing the "bottom" or reverse side

finished form ready for immediate assembly.

As has just been mentioned, the Mayfair design ensures that the requirements of low building cost and adequate component availability are met. Further economies within the design itself are effected by the use of valves which, whilst still current in manufac-

positions where they provide just as good results as would be given by smaller types. For a number of circuit applications the use of B7G and B9A affords almost the only advantage of saving of space, this being more applicable to commercial costing than to that of home-constructor equipment. It is very

interesting to note, incidentally, that in current American television design octal-based valves, such as the 6SN7, are in very frequent use, despite the availability of B7G or B9A equivalents.

Constructional Articles

Due to the large amount of space needed, it would be impracticable to attempt to describe the construction of the complete Mayfair receiver in one single article. Each section of the set will, therefore, be described separately in succeeding issues; this procedure commencing this month with the power pack chassis. Individual articles will include the parts lists applicable to the section being described. It is possible that special prices will be available to readers who purchase the complete Mayfair kit, in which case it might be advisable to order this in advance of the articles. Also, arrangements may be made with advertisers where some of the components required are already on hand.

The Power Pack

The first part of the receiver which is to be described is the unit containing the power pack and sound output stage. The circuit of the power pack unit is given in Fig. 1 and, as may be seen, this diagram clearly demonstrates the fact that complete isolation from the mains is provided by the power transformer. This transformer has several heater secondaries, as well as a centre-tapped h.t. secondary. Rectification is provided by two 5V4's, these feeding into a filter circuit employing a heavy choke and large-value filter condensers. A number of separate h.t. lines are taken from the main h.t. supply, these feeding the various parts of the receiver circuit.

Also included in the power pack unit is the sound output stage. This consists of a single 6V6 output valve with its associated circuitry, and there is little here which requires further comment.

The layout of the power pack unit is illustrated in Figs. 2 and 3, these showing the positions taken up by the various components employed. It will be noted that some of the tags on the tag-strips are shown black. These tags are those which support the associated tag-strip and which are in consequence at chassis potential. For obvious reasons it is most important to ensure that only those tags are bolted to the chassis. It may also be noted that all the components shown in Figs. 2 and 3 are designated either with their circuit reference or with a separate letter or number reference. Thus, the two grommets on the chassis are marked G₁ and G₂, whilst the tag-strips are identified by different letters. This method of indication enables full

wiring instructions to be given without any risk of ambiguity.

Step-by-Step Instructions

The assembly of the power pack and output stage should be carried out in the following manner.

Mount the three valveholders and tag-strip A, one fixing bolt securing one end of this tag-strip and one end of valveholder Y. The valveholders are bolted to the underside of the chassis. Next mount the mains voltage panel and tag-strip F, both these components sharing a common mounting bolt. Fit the two grommets G₁ and G₂, these being followed by the output transformer TR₆ and the 2-way tag-strip E. Tag-strip E is above the chassis and is secured by one of the bolts mounting the output transformer.

Choke E, above the chassis, comes next, and three of its mounting bolts also secure 5-way tag-strips D and H, and 2-way tag-strip B, below the chassis. Fit, with the aid of their clips, the two electrolytic condensers C₁ and C₂ mounting at the same time the two earth tags T₁ and T₂. T₁ is mounted under one of the bolts securing C₂, and T₂ under one of the bolts securing C₁. Make certain that the "spot" tag of C₁ takes up the position shown in Fig. 2. Finally, mount the mains transformer.

Wiring up may now be started. Care should be taken during wiring to ensure that all joints are well made and reliable. The first component to be connected up is the mains transformer. One of the thick yellow leads from this transformer should be taken to chassis tag T₂, the second thick yellow lead being bent back across the transformer as shown in Fig. 2. Also taken from the transformer to chassis tag T₂ are one thin black flexible (as opposed to solid) lead, and one red/yellow lead. All three leads should now be soldered at T₂. It may be found that the two thick yellow leads just mentioned need to be cleaned before soldering, and it may be found advisable to initially tin their ends. The yellow lead bent back over the transformer acts as an anchor for heater leads which will be added later.

We have already connected one red/yellow lead to chassis tag T₂. The second red/yellow lead is now connected to tag 1 of tag-strip A. Next, connect one green lead from the transformer to pin 8 of valveholder Z, and the second green lead to pin 2 of the same valveholder. Connect one orange lead to pin 6 of valveholder Y and the other orange lead to pin 6 of valveholder Z. Connect the black solid lead from the transformer to tag 4 of tag-strip A, the black/yellow lead to tag 3 of tag-strip A, and the thin yellow lead to tag 2 of tag-strip A.


Next make the following transformer primary connections. The green lead from the transformer connects to tag 2 of tag-strip F. Proceeding to the mains voltage panel, the red lead from the transformer connects to tag 1 of this panel, the yellow lead to tag 2, and the white lead to tag 3.

The mains transformer is now wired up, and the next component to tackle is the output transformer. One red lead from this component connects to tag 3, and the other to tag 4, of valveholder X. The two yellow leads from the output transformer travel above the chassis through grommet G₁ to tag-strip E, where one lead connects to tag 1 and the other to tag 2.

The output transformer is followed by the smoothing choke. Both leads from the tags

negative end to tag 2 of tag-strip B. Connect resistor R₁ between tag 2 of tag-strip H and tag 2 of tag-strip D; R₂ between tag 1 of tag-strip H and tag 1 of tag-strip D; R₃ between tag 4 of tag-strip H and tag 4 of tag-strip D; and R₄ between tag 3 of tag-strip H and tag 3 of tag-strip D. This clears up the larger resistors. Next fit R₅ between pins 2 and 6 of valveholder X; R₆ between pins 6 and 5 of valveholder X; and R₇ between pins 8 and 2 of valveholder X. All the components are now fitted and all that remains is the wiring between tags.

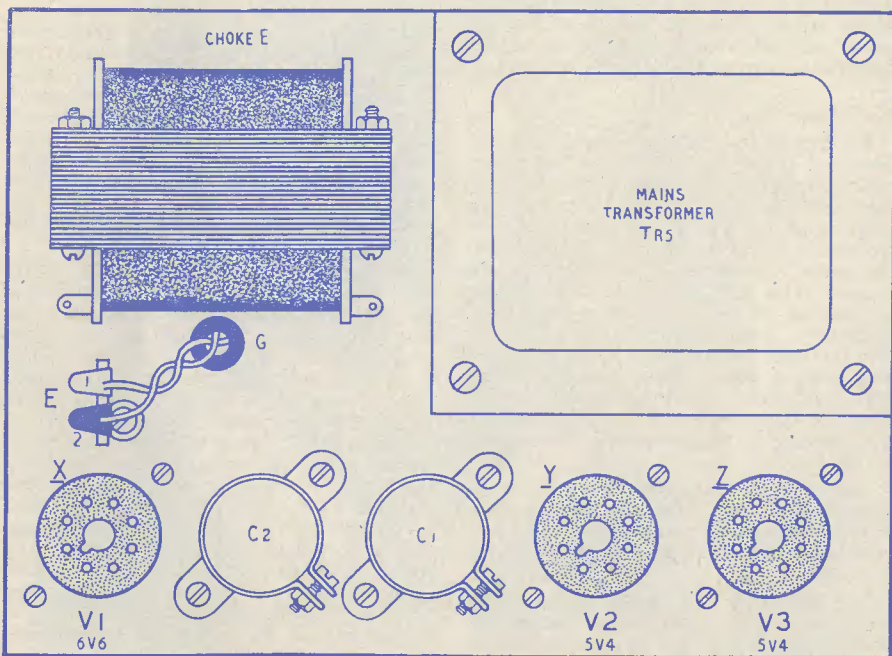Wiring should be carried out in the following manner. Connect together pins 1 and 2 of valveholder X and the chassis tag T₁. Connect together pins 6 and 4 of valveholder Y. Connect together pins 6 and 4 of



P3

Fig. 3. Above-chassis layout of the power pack

of this choke travel through grommet G₁, one lead connecting to tag 1, and the other to tag 2, of condenser C₁.

The smaller components come next. When wired, these should take up the positions shown in Fig. 2. First of all, connect condenser C₃ between tag 1 of tag-strip B and pin 6 of valveholder X. Connect the positive end of C₄ to pin 8 of valveholder X, and its

valveholder Z. Connect pin 2 of valveholder Z to pin 2 of valveholder Y. Connect together pin 8 of valveholder Z, pin 8 of valveholder Y, and tag 1 (spot) of condenser C₁. Connect tag 2 of condenser C₁ to tags 1, 2, 3 and 4 of tag-strip D. Connect tag 1 of condenser C₂ to tag 2 of tag-strip H. Connect together tag 2 of condenser C₂, pin 4 of valveholder X, and tag 1 of tag-strip H.


Finally, connect pin 7 of valveholder X to the thick yellow wire from the mains transformer which was bent back earlier.

Apart from one extra resistor, which will be added when the turret tuner is wired in, the power pack unit is now complete.

Next Month

In next month's issue the assembly of the Mayfair television receiver will be taken one stage further. The writer will continue to

employ the same wiring instruction technique as he has used this month, since he feels that step-by-step instructions of this type are of especial value to the beginner, insofar that each stage in the wiring may be ticked off as it is completed. He might add that such a description may also be of assistance to the more experienced constructor who does not want to waste his time mentally transferring every connection from the theoretical circuit to the actual model he is building.

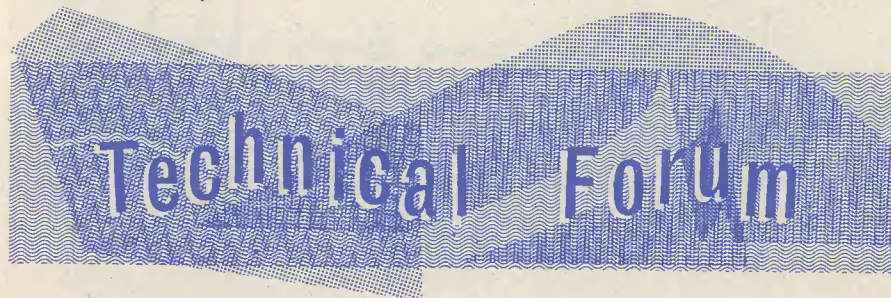

Safety with AC/DC Grams

IN THE JULY ISSUE WE DISCUSSED CERTAIN of the major safety precautions which are necessary in domestic radio and television equipment to protect the user against accidental shock. It was seen that, if a receiver should have a "live" chassis—that is, one which is connected to one side of the mains supply—it is necessary to ensure that no part of it is accessible to the user. There are two reasons for this; firstly, it is possible to connect the mains plug in the socket in such a direction that the chassis is at the full mains voltage with respect to earth; and secondly, even if the plug should be reversed there may still exist a small voltage to earth which is capable of providing quite large current. Thus whichever way the mains plug is connected, it is not really safe to allow the chassis to be accessible. It should also be noted that even if the very desirable precaution is taken to ensure that the chassis is joined to the earthy side of the mains, it is not necessarily at earth potential, and can, in no circumstances, be connected directly to earth.

These features of a.c./d.c. technique raise certain difficulties when a universal radiogram is being designed. The reason for this will be apparent when it is remembered that in the standard a.c.-only model in which the chassis is isolated from the mains, the metal motor board carrying the turntable assembly is connected directly to the amplifier chassis, which is in turn often joined to an earth line.

This renders the unit completely safe to touch and at the same time eliminates any possibility of hum. Now with the live chassis equipment no direct connection is permissible between record player and amplifier, and this can easily lead to a most prolific source of hum. One solution lies in the use of a record player in which the motor board and often also the turntable are made of a rigid plastic material. In this case a crystal pick-up is most desirable, and often essential if induction hum such as might occur with a magnetic unit is to be avoided. The pick-up is connected to the amplifier through two capacitors, one in each lead, each having a maximum d.c. working voltage in excess of 750V. There are players available in which the p.u. arm is entirely of plastic and the screened connecting cable completely inaccessible from the outside; with such units the use of isolating capacitors may be avoided in a permanent installation.


Should the player have a metallic motor board, ascertain whether or not it is connected either directly or indirectly to the outer screening of the pick-up lead. If there is no connection, the lowest hum level should be obtained by using the arrangement shown in Fig. 1. Here a separate earth return path is provided via C₁ for any interference signal induced on to the motor assembly. If the motor board were connected to the cable screen, capacitor C₂ would act as a common return impedance in the signal path and might easily lead to hum or excessive motor

interference. These notes are not intended to deter the reader from making a.c./d.c. types of amplifiers, but to be forewarned of the possible causes of input hum is half the battle in either eliminating or avoiding it.

the dummy load line. This alternative is shown as a dotted lead in the diagram.

Hum on Recorders

Whilst on the subjects of mains hum and

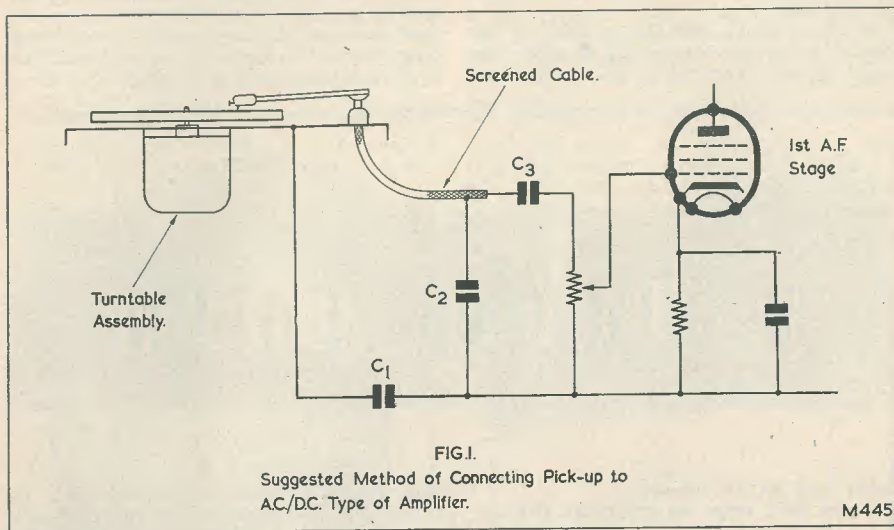

Tape Deck Switching

In the June issue we published a suggested method of connecting up the switch assembly on the Collaro tape deck. As readers will know, the occasional error does occur—and the writer has to apologise for one in the diagram Fig. 1, p. 754 of the June issue. A lead is missing between the top right-hand contact on the switch assembly and the line marked L.S. (S_{1A}). Also, the two leads shown connected to the lower pair of contacts on the sixth set top row should be reversed. Several constructors have also suggested an improvement to the circuit, and we are passing this on as it may well interest other readers. When the deck is in the stand-by condition with all Record and Replay buttons up, there is no load on the amplifier. This may be simply avoided by connecting the bottom contact of the second set in the top row to the line marked "Dummy Load." To clarify these instructions we are reproducing the connections to the top row of switch contacts as they should be (Fig. 2). As an alternative, some constructors may wish to have the speaker connected in circuit when the stop bar is operated; this will enable the amplifier to function normally in this condition. This may be achieved by joining the lower contact of the second set to the L.S. line and not to

tape recorders, it is opportune to mention one or two points which are worth bearing in mind when contemplating the construction of a portable recorder. It is inadvisable to consider a live chassis type of amplifier for use in a recorder, so in employing an isolated chassis it is permissible to connect the main assembly of the deck to the amplifier chassis. Hum bucking coils are often included in series with the Record/Replay heads to balance out any voltage induced into the heads by stray fields from the motors. These bucking coils are included in the decks, if necessary, by the makers. It will be realised from this that the heads are very sensitive to hum from stray a.c. fields, and certain precautions are necessary in the design and positioning of the power pack components. These points may be listed as follows:


(a) It is usually of advantage to construct the power pack on a separate sub-chassis and mount it as far from the tape heads as is possible. A little experimental work to find the best orientation of the mains transformer with respect to the heads normally makes possible some further reduction of hum.

(b) The stray field of a mains transformer is dependent partly on the size and type of core. In general, the smaller the core, the nearer it will be to magnetic saturation and

the greater will be the stray field. Hence, it is advisable to use a good quality product, having a core of reasonable dimensions.

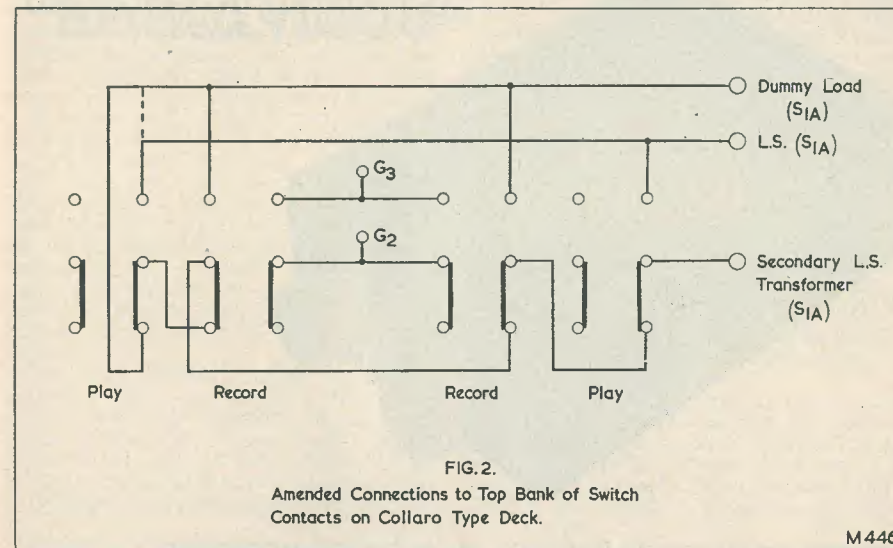(c) The h.t. supply must be adequately smoothed, but in a portable equipment this is

gap can produce a very high extraneous field. If the choke is following a full wave rectifier, this field will have a large 100 c/s fundamental component which can be particularly troublesome to eliminate. It is usually easier



best achieved by means of a resistance-capacity smoothing filter. Chokes normally are fitted with a gapped core to prevent magnetic saturation, and the presence of a

to avoid setting up a magnetic field in an equipment rather than attempt to screen sensitive components from a field which already exists.

Can Anyone Help?

(continued from page 103)

A. BURROWS, 132 North Road, Bellshill, Lanarkshire, Scotland, wishes to obtain the service sheets for, or any data on, the Vidor model CN.247 5-valve receiver and the Alba model 462 5-valve receiver.

L. KEAST, Royal Oak Cottage, Chainhurst, Marden, Kent, wonders if any reader can supply any information on the Signal Generator type W.1268, 30-86 Mc/s, ref. No. 10T67, XW530V/179.

E. NORTHCOTT, 60 Harwell Street, Plymouth, Devon, wishes to obtain information on the Service receiver type P.104, and will pay for any circuits or return if required.

A. J. B. CUTLER, 22 Cox Lane, Chessington, Surrey, would like to buy or borrow any details, and especially the circuit, of the surplus C.R. Unit "Wavemonitor G87" design "H."

P. A. RUSSELL, 133 Monks Park, Wembley, Middx., wishes to buy or borrow a service sheet for the Ultra 9in console televisor W.470 (London transmissions).

J. S. BELL, 7 Wascana Close, Anlaby Park Road South, Hull, Yorks., requires the circuit or service data for the True Vue televisor model A.33.


J. U. CULL, 6 Rising Brook, Stafford, wishes to obtain details of the linking connections for the Parmeko Universal Output Transformer, believed purchased just prior to the last war. The manufacturers are unable to help.

ERRATA—On p. 40, August issue, it was stated: "From the right-hand tag of the head-phone strip . . . solder one end of both R_2 and R_3 . . ." This is incorrect; R_2 should be connected to the outer tag, and R_3 to the inner tag, to which the h.t.+ lead is also connected.

Further Notes on

THE

"COMPANION"

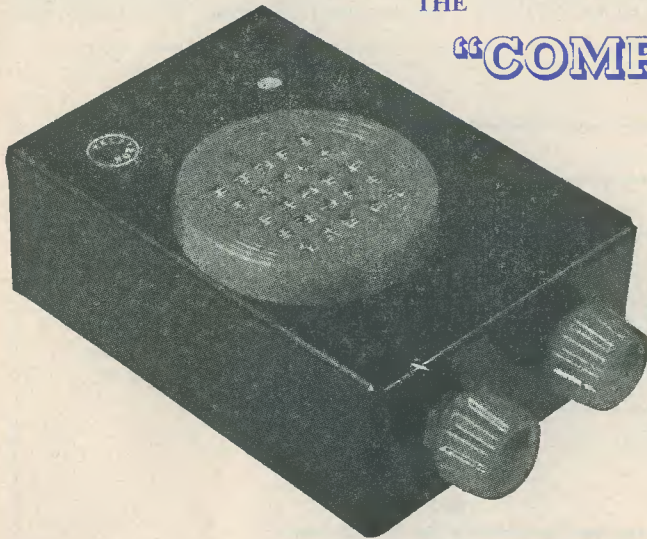

REGENERATIVE TRANSISTOR '3' POCKET RECEIVER

by R. A. LANGIS

SINCE THE PUBLICATION OF CONSTRUCTIONAL and other information on the above receiver in our July issue, many enquiries have been received from intending constructors. Of these enquiries, some asked for further information on the final cabinet design, and others required details and additional information on the various allied uses of the receiver.

Dealing with the cabinet first, this is shown in the illustration, from which it will be seen that it largely follows the prototype design but differs in certain respects. Of these, the most striking is the attractive two-colour scheme, the cabinet itself being black with the speaker fret in a contrasting shade of red. The whole assembly itself is a very sturdy affair, the lid being fixed to the case by two strong metal hinges—these being moulded into the strengthened wall of the cabinet.

Regarding the allied uses, two of the most frequently asked questions were: "Can the receiver be used as a car radio," and "Can larger speakers be incorporated into the design?". The following endeavours to

answer these queries, and deals with some additional points concerning the actual construction of the receiver.

The balanced armature reproducer is essentially a low impedance earphone which provides audio output similar to a small speaker. Where portability is of secondary importance, a larger moving coil speaker with a suitable matching transformer will provide improved performance. Class B push-pull output may be added, using TR₃ as a driver stage, but of course a larger cabinet and chassis would be required to house the resultant receiver.

The "Companion" receiver is not suitable for use as a car radio, although in some cases it will operate within a car, but with much reduced volume due to the shielding effect of the metal car body. Similar results will prevail when the receiver is used within a reinforced concrete building. Results achieved with the receiver will vary greatly depending on the actual location of the user with respect to the local transmitting station. Judicious use and careful adjustment of the feedback control R₂ will also greatly affect

the results obtained at any given location. This control must be maintained just below the point of oscillation for best results and the loudest signal strength.

The layout of components, as shown in the drawing (Fig. 2) should be strictly adhered to, with neat and tidy wiring, angled and kept close to the chassis in order to both minimise r.f. instability and acoustic feedback. Haphazard "point to point" wiring will usually produce disappointing results.

Blue Spot or r.f. junction type transistors were specified for TR₁ in the original design, but either Red/Yellow Spot or the White Spot types are satisfactory as substitutes. Where either of these two latter types are used, however, L₂ may be omitted and C₃ should be reduced from 50pF to 20pF. In the case of TR₂, a Green/Yellow Spot type may be substituted for the specified Red Spot; for TR₃, a Green/Yellow Spot type may be used in place of the Brimar TS3 transistor.

The stated values for both R₅ (8.2kΩ) and R₆ (4.7kΩ) are optimum values but, due to the wide variation of transistor characteristics, these values should be adjusted so that the collector current of TR₂ is 0.5 to 1mA, and that of TR₃ some 3mA. A milliammeter connected in series with the

collector of each transistor, and a 10kΩ variable wired temporarily in place of R₅ or R₆ will enable the correct value of resistor to be ascertained.

The three 1.5V cells are connected in series, with the "plus" end connected to the "earth" line. When correctly wired into circuit, with suitable values for both R₅ and R₆ having been chosen and fitted, a low level hiss from the reproducer will be heard upon switching on the receiver.

Where the hiss level is excessive, this would indicate a faulty junction in TR₁ which may have been caused through the application of excessive heat during the soldering operation.

In the absence of suitable test equipment, rough functional tests may be carried out by momentarily connecting a 1 or 2μF condenser across R₅, then across R₆. These connections should produce a loud "click" in the reproducer. Similar results should occur when R₄, C₄ are momentarily short circuited.

Dealing with the wiring of R₂ (see Fig. 2), care should be observed that the correct tags are wired into circuit as follows: Tag A (top tag) should be connected to R₃; Tag B (centre) to 2 of the FX25 tag ring and Tag C (nearest to chassis) to positive end of C₁.

Radio Miscellany (continued from page 98)

Help!

Also described is a Mercury Jet Interrupter, a Microphonic Amplifier and an Omnigraph. In case you have no idea what the latter might be, it was a device with a hand-driven notched wooden drum for practising Morse. The notches on the revolving disc operated a contact breaker to give the necessary dots and dashes. The faster you wound, the faster the Morse; all perfect copy, of course, at umpteen words per minute provided the notches had been carefully cut.

Our old friends the Oojah coils also appear. These are simply basket coils wound in and out of nails driven into a wooden core. Then the lot was steeped in boiling paraffin wax to hold the wiring together, as after cooling the nails and wooden core were removed. Their self-capacity was terrific, but they looked nice, had a pleasant smell, and it was good fun making them.

The *pièce de résistance* which really intrigued me was in the cover advertisement for Part 17. The Polar Blok System of building sets was to be described. That has got me completely foxed. I cannot remember the name, let alone how it was done. It is described as "an extremely ingenious patented

method of building up receiving sets with ease and simplicity," etc.

That makes it my turn to appeal to "Can Anyone Help." WANTED URGENTLY by puzzled Radio Magazine Columnist. Full details of the Polar Blok System of Set Building—from friendly western county readers who don't want their postage money refunded.

Quid Pro Quo

An idea which may be of interest to many readers, at least those who also happen to be photographers, was recently noted whilst on holiday. The bottom of the carrying-case of a home constructed battery portable had been fitted with a bush to fit a camera telescopic tripod. When out picnicking, etc., the portable was kept clear of the ground (preserving the finish of the leatherette case), could be rotated to use the frame aerial to the best advantage, and could be set for any height to make for easy tuning adjustment or volume level, according to whether the user was seated on the grass or a camp stool.

There are many instances of electronics lending ideas to the photographer—here, at last, we borrow one in return!

A SENSITIVE

SIGNAL TRACER

by P. YATES

THE TECHNIQUE OF SIGNAL TRACING, AS A means of swiftly diagnosing faults in t.v. and radio equipment, has always greatly interested the writer. Even the simplest form of tracer—a pair of 'phones with a $0.1\mu\text{F}$ capacitor in series with one lead—can be put to a large variety of uses, e.g. distortion tracing, checking pick-ups, hum location, etc.

A less obvious use is the tracing of faults in the sync separator and timebase circuits of t.v. receivers. In the absence of an oscilloscope the 'phones are invaluable. The frame sync is recognised as a 50 cycle hum, and the line-sync as a high-pitched whistle (10,125 c/s). Care must be taken to ensure that it really is the sync voltages being traced, and not the output due to the respective timebase oscillators themselves. To check this, the contrast-control should be turned to the minimum gain position, which means that there is no output from the sync separator, and the audible indications due to the sync voltages will disappear.

The addition of a crystal-diode in series with the capacitor and 'phones enables the tracer to be used for radio-frequency tracing as well. Here the need for greater sensitivity is quickly felt, as these voltages in the early stages of a receiver are usually of the order of millivolts only. To provide this increased sensitivity the more advanced tracer about to be described was constructed, and has proved very successful in actual use. It can be used for r.f. and a.f. tracing, and provides both visual and aural indications of the signal.

Referring to the block schematic diagram Fig. 1, it will be seen that the signals from the r.f. probe feed into the first r.f. amplifier stage, which uses a 6SJ7 type pentode valve. This stage is resistance-capacity coupled into the second r.f. amplifier, which uses a similar valve. The r.f. gain is controlled by means of a $25k\Omega$ wire-wound potentiometer in the cathode circuit of these valves.

The amplified r.f. signal is then passed to the detector stage, which uses a 6U5G "magic-eye" valve. The triode section of this valve acts as a leaky-grid detector, demodulating the r.f. signal and passing it on as a.f. to the a.f. gain-control. A leaky-grid detec-

tor can be considered as a diode-detector followed by a stage of Class A amplification, thus this stage also provides useful amplification.

The "magic-eye" section of this valve is used as the Visual Indicator, and the "eye" will close progressively as the signal strength increases.

Following the path of the signal, it has now arrived at the a.f. gain-control, and from here it feeds into the grid of the 6V6 beam-tetrode type output valve, which operates the loudspeaker to give aural indication.

A full-wave rectifier type 5Z4 is used in the power unit, followed by a two-section smoothing circuit, thus ensuring a very low hum-level.

Each stage is decoupled from the h.t. + line by a large capacitor, to ensure good stability.

Components

In general all component values are shown on the circuit diagram, and any special features are referred to below.

Valves

These should preferably be of the metal type, as these provide their own screening. If the glass type are used, however, external screens must be used on the r.f. amplifiers.


Resistors

The wattage rating shown on the circuit diagram are important, and should be adhered to; of course, there is no objection to using a $\frac{1}{2}$ watt in a $\frac{1}{4}$ watt position if this is more convenient!

All resistors can be 20% tolerance, except R_4 and R_9 , which should be 5%. RV_1 , the $25k\Omega$ r.f. gain control, must be wire-wound, as it has to carry the combined cathode currents of V_1 and V_2 . The a.f. gain-control RV_2 should preferably have a logarithmic law, but a linear one would be acceptable.

Capacitors

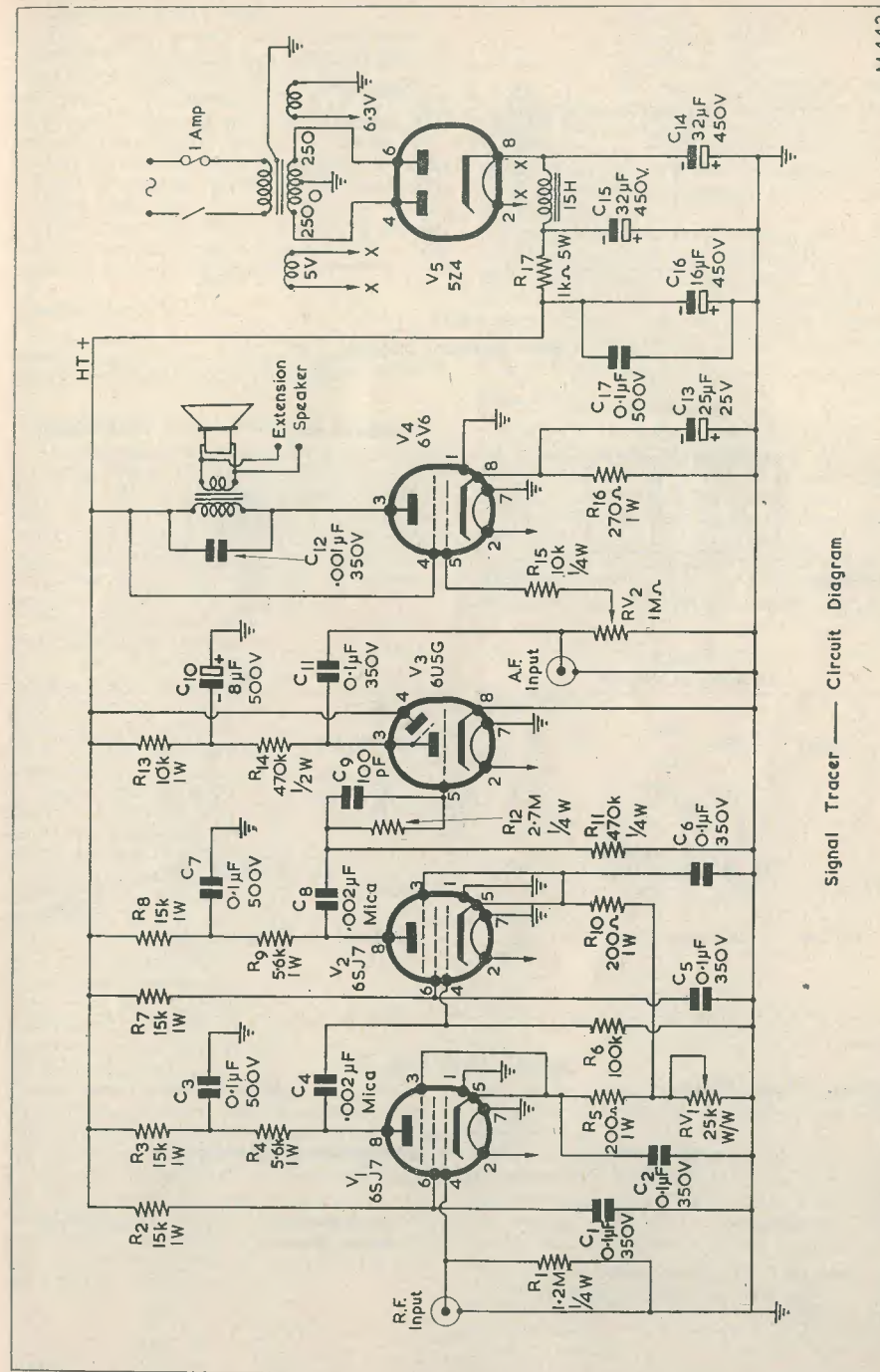C_4 and C_8 must be of the mica type (or non-inductive paper). The working voltages are shown on the circuit diagram and are specified to give a good safety factor.



Signal Tracer — Circuit Diagram

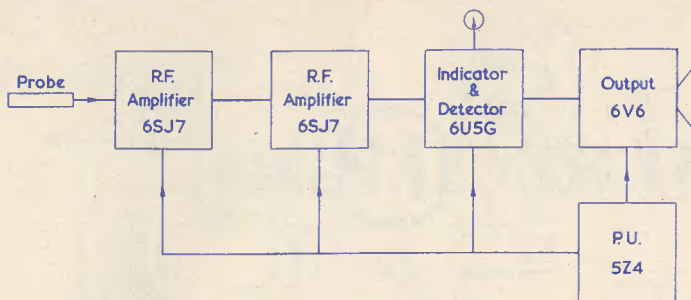


FIG. 1
Block Schematic Diagram.

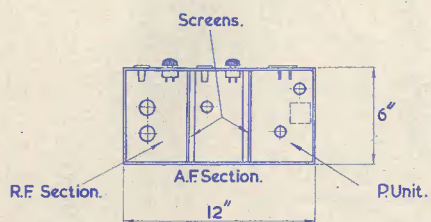


FIG. 2
Underside of Chassis.

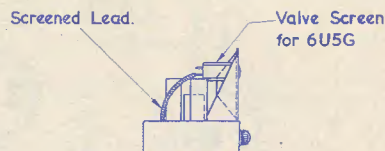


FIG. 3.

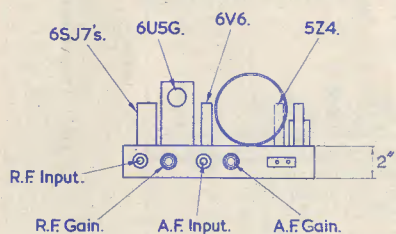


FIG. 4.


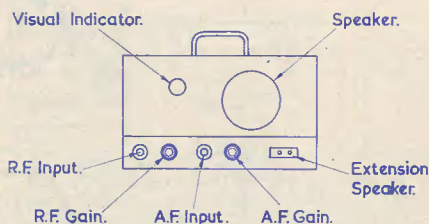


FIG. 5.

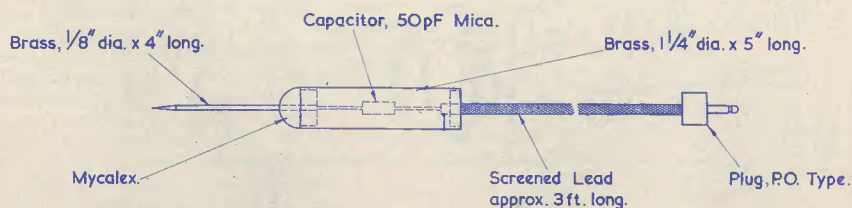

Note. A.F. Probe is similar to R.F. Probe but with Capacitor increased to 0.05 μ F.

FIG. 6.
R.F. Probe.

M443

Transformers and Chokes

The mains transformer should have a 250-0-250 volt secondary winding, and be capable of delivering at least 60mA d.c. The secondary windings are 5V at 1 amp and 6.3V at 3 amps. It should preferably also have an electrostatic screen.

The smoothing choke should be between 10 and 20 henrys, and be capable of carrying at least 60mA d.c.

The output transformer should, of course, be of a suitable ratio to match a 6V6 to the speaker, and is a standard type.

Loudspeaker

This is a 5in p.m. Elac unit, with a 3-ohm speech coil; however, any good quality speaker of similar type can be used.

Constructional Details—Chassis Layout

The chassis used was one which happened to be at hand, the dimensions being 12in \times 6in \times 2in, and this appears to be the smallest size on which the components can be conveniently arranged. It is housed in a metal case—again conveniently available—which measures 12 $\frac{1}{2}$ in \times 8in \times 7in and so makes a compact portable unit (Fig. 5).

The wiring layout is not particularly critical and any convenient chassis could be used, provided the following precautions in the interests of stability are undertaken.

The underside of the chassis is divided into three compartments by metal screens (Fig. 2). The r.f. components are contained in the first section, the a.f. in the middle, and the power unit parts in the third. The connections to the base of the 6U5G "magic-eye," which is mounted horizontally on a bracket above the chassis, are made via a screened lead (Fig. 3). This general layout should be adhered to as it prevents pick-up between stages working at different frequencies.

Individual leads in the r.f. sections should be kept as short as possible, especially grid leads, and a colour code for wiring facilitates the tracing of any particular lead in the event of a fault developing. The particular code used by the writer is as follows:

- Anode: Blue
- Grids: Green
- H.T.+: Red
- Earth: Black

- Heaters: Brown
- Cathodes: Yellow
- Screens: Orange
- Misc.: White, Grey, Violet

The valve connections are shown numbered on the circuit diagram, and resistors and capacitors were wired directly across them; however, a perhaps neater construction could be made by using tagboards, provided leads are kept short.

The speaker is fixed to the chassis by means of a 16-gauge mild-steel right-angled bracket attached by one of the magnet retaining bolts at the rear. The front circumference is recessed into the chassis by $\frac{1}{4}$ in and secured through the bottom-fixing hole to the chassis by a 4-BA bolt.

Probe Construction (Fig. 6)

The physical construction of both r.f. and a.f. probes is identical, the only difference being in the size of the capacitor used; 50pF for the r.f. and 0.05 μ F for the a.f. one.

The bodies are made from 1 $\frac{1}{2}$ in diam. brass tube, with Mycalex plugs at either end. The front plug is drilled to give a tight push fit to the needle itself, a 4in piece of tapered $\frac{1}{16}$ in brass rod. The rear plug is drilled to accom-

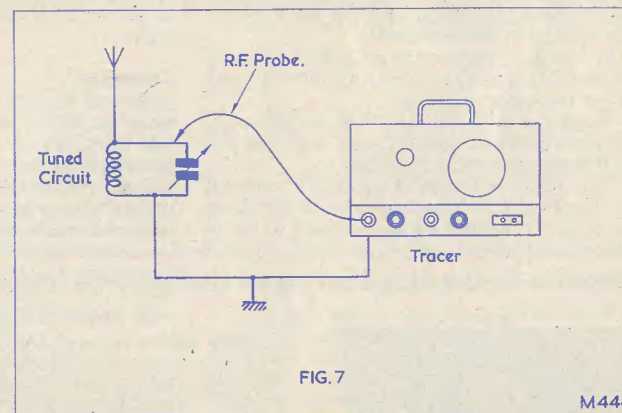


FIG. 7

M444

modate the insulated screened lead, the screening of which is bonded to the brass housing.

The screened-lead need not be more than approximately 3ft long or shorter if required, and terminates at the other end in a P.O. type two-contact plug. P.O. type jacks are used in the chassis to receive them, labelled R.F. Input and A.F. Input on Fig. 4.

The brass housings effectively screen the pick-up capacitors from hand-capacity and external fields, and it is only when the needle itself is touched that a healthy "burp" is heard from the loudspeaker!

Operation of Tracer

A general view of the unit is shown in Fig. 4. Some notes on the operational use might be useful.

The technique of signal tracing is rapidly mastered and soon becomes second nature, and in many cases cuts servicing time considerably.

The sensitivity of the tracer is such that the signal can be traced from aerial input right through to the speaker—this with an input from a picture-rail aerial. So in the case of a "dead" receiver—after a visual check has ascertained that all heaters are O.K. and a meter check has indicated the presence of h.t.—tune the receiver to a strong local signal; or inject a signal (modulated r.f.) if a signal-generator is available.

Then with r.f. jack plugged in, and r.f. and a.f. gain controls at maximum, place the tip of the probe on the Ae socket; the signal will be heard, and the "eye" will partially close. Next, place the probe on the frequency-changer grid, and if the signal is again indicated, proceed to the frequency-changer anode. Here the signal should be louder, and the "eye" should close more. In this way, working backwards to the speaker, all r.f. and i.f. stages can be checked; if the signal ceases at a certain point, then the fault obviously lies between that point and the point where the signal was last indicated.

For tracing faults in the a.f. section, the a.f. probe is used, and the r.f. gain control turned to the minimum position.

In general it is best to work with the a.f. gain at maximum always, and with the r.f. gain at the minimum possible.

The visual indicator is particularly useful in checking the local-oscillator stage in a superhet. Frequently it is necessary to know

if the oscillator is, in fact, oscillating. This can be checked by placing the r.f. probe tip on the anode of the local-oscillator when, if all is O.K., the "eye" should close or partially close. There will be no audible indication, as, of course, the oscillator is generating unmodulated c.w.

Distortion Tracing

The point of entry of distortion can be swiftly located by working back from the detector anode, a task which can be very tedious by any other means.

Checking Bypass Capacitors

If, when the respective probe is placed on a bypass condenser, a signal is heard, then obviously the condenser is no longer bypassing, and should be replaced! Cases of instability due to this cause are quickly located.

Pick-ups may be checked by placing the a.f. probe tip on the live lead, with the a.f. gain at maximum; in the case of a low-impedance type, connection must be made to the secondary of the matching transformer.

Many more uses will soon present themselves to the user, and when the unit is not in use as a tracer, it can be used as a Monitor receiver. To do this, connect a tuned circuit as shown in Fig. 7 and tune to the desired signal.

Conclusion

Several further facilities have been envisaged but not yet incorporated. These include the bringing-out of the power-unit supply potentials to pins on the front-panel; and the use of a multi-match output transformer with connections also brought out. This would further increase the versatility of the unit.

Sixpence-in-the-Slot Shaving at the National Radio and Television Show

28 August–7 September, 1957



There will be no need for either visitors or exhibitors' staff to suffer a "five o'clock shadow" at the forthcoming National Radio and Television Exhibition at Earls Court. The Management's consideration of this problem has prompted them to instal slot machine shavers in a number of their cloakrooms. For sixpence these will give five minutes' use, and they are automatically disinfected at the end of each shave.

On a hectic day-trip to London, many an out-of-town radio dealer, fitting a session at the Exhibition into a tightly packed schedule, will appreciate this opportunity of a quick shave before leaving Earls Court for other engagements. Radio enthusiasts, rushing straight from business to the exhibition in the evening, will also enjoy this chance of grooming before making their tour of inspection.

Such are the facilities afforded by the "Auto Shaver" produced by Partwest Ltd., of 50 Mount Street, London, W.1. The "Auto Shaver" is now available to an infinite variety of industrial, commercial and social organisations.

RIGHT—From the Start

Part 18

GAINS AND LOSSES

by A. P. BLACKBURN

EVERY ART, SCIENCE OR WHAT-HAVE-YOU has its technical language and its jargon. Radio, not the least of these, is liberally peppered with terms, many of them having no existence whatever in everyday speech.

Many become "household words," like frequency modulation, for example, or television. Others, however, remain elusive, usually because they are not directly connected with improvement in sales. Such a one is "decibel." The hi-fi enthusiasts will need no help in this matter, I am sure, as their life revolves around such things as "db's of bass lift" and "the response is 3 db down at 20 kc/s," and so on. Indeed, the decibel (db) is particularly useful when dealing with changes from one state to another as, I hope, we shall see later.

Levels

We will start by postulating a system of circuits, get in a tangle with them, and then see if there is an easy way out. Fig. 1 shows three attenuators connected in cascade. The first reduces the input power by half, the next reduces the output of the first by 10 times, and the last reduces the remaining power by half again. Now the output power may be calculated as follows. At the points BB the power will be $\frac{1}{2}P_i$. The next attenuator reduces this 10 times, so at CC the power will be $\frac{1}{2} \times 1/10 P_i$ and, therefore, the output power after attenuator No. 3 will be

$$\frac{1}{2} \times 1/10 \times \frac{1}{2} P_i = 1/40 P_i.$$

In other words, the attenuations have merely been multiplied together and the input power multiplied by the result to give the output power. This admittedly is not particularly difficult, but as systems become more complicated, it becomes clumsy.

Now another way of multiplying numbers together is to take the logarithm of these numbers and merely add them together. Say, for example, our attenuators had reduced the powers by 1/2.37, 1/10.4 and 1/3.21 instead of the easy numbers we assumed, multiplying these numbers would be a little clumsier than before, and to resort to logs would be one way out. We could say, then, that the powers may be expressed as follows:


$$\log \frac{1}{2} + \log 1/10 + \log \frac{1}{2} = \log A,$$

where A is the total attenuation from input to output. If we now multiply all these terms by 10 we get

$$10 \log \frac{1}{2} + 10 \log 1/10 + 10 \log \frac{1}{2} = 10 \log A \quad (1)$$

Now call each of these terms A_1 , A_2 , A_3 and A_4 , and we may write $A_1 + A_2 + A_3 = A_4$ (2)

In simple language we may add the attenuations of each attenuator providing we take their logs and are satisfied with the total attenuation being given as the log of the true attenuation, i.e. $\log A = A_4$. You will probably say at this point, "this seems to be just complicating the issue. After all, multiplication is simple enough." That is certainly true of this simple case, but if you will bear with it a little longer I hope to show that it is justified generally.

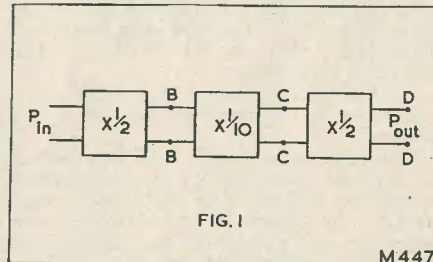

You will notice that the quantity behind the log is always a ratio, 1 : 2, 1 : 10, etc., and it represents the ratio of power into the attenuator to power out. We can say, therefore, that A_1 , A_2 , etc., can be written

$$10 \log \frac{P_1}{P_2} \dots \dots \dots (3),$$

where P_1 and P_2 are the output and input powers respectively. At last we have arrived at the db. It is defined by (3) above.


$$\text{i.e. db} = 10 \log \frac{P_1}{P_2} \dots \dots \dots (4)$$

So reverting again to (2) we see that all the A's are actually attenuation in these new units, decibels.

In other words, the decibel may be defined as "10 times the logarithm of the ratio of two

power levels." Applying this to Fig. 1 we get $\log 0.5 = -0.3$; $\log 1/10 = -1$.

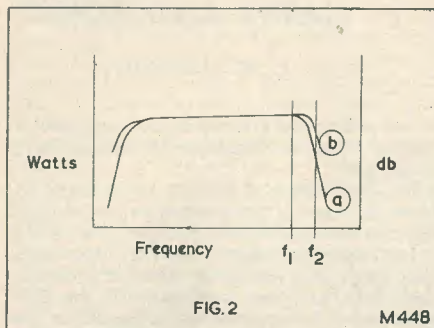Therefore, $10 \log \frac{1}{2} = -3\text{db}$ and $10 \log 1/10 = -10\text{db}$. The total attenuation of the three attenuators is therefore $(-3)+(-10)+(-3) = -16\text{db}$.



Signs

There is one feature in the above answer, the negative sign, that has not been explained. The simple answer is that negative signs mean attenuation (or losses) and positive signs gains.

To illustrate this we will work out a case for an amplifier. If the input were 1 watt and the output 10 watts, the ratio is 10 to 1. The gain in db is therefore

$$\text{Gain db} = 10 \log 10/1 = 10\text{db}$$

The sign is positive, showing that it is a gain.

Input and output power is all very well in its way, but very often we are interested in voltage or current. An ordinary voltage amplifier, for example, does not involve us in power at all. How may the gain of the amplifier be expressed in db?

We know that power = E^2/R . If we put this into the definition of the db as in (4) we get

$$\text{db} = 10 \log \frac{E_1^2/R}{E_2^2/R}$$

where E_1 and E_2 are the input and output voltages.

A theorem of logarithms enables us to write this as

$$\text{db} = 20 \log \frac{E_1}{E_2} \dots \dots (5)$$

Therefore an amplifier which has an input of 0.001 volt and an output of 1 volt has a gain of 1,000 times, and in db,

$$\text{Gain} = 20 \log 1,000 = 60\text{db}$$

Here is one of the advantages of the db. The numbers involved are smaller. A gain of a million times is merely 120 db.

There is one thing to notice about expression (5), and that is that it was derived from (4), which involves powers. The derivation of (5) assumed that the input and output resistances were equal, of value R in that case.

This must be strictly observed; an amplifier with an input resistance of $1M\Omega$ and an output resistance of $1k\Omega$ cannot have its voltage gain stated in db.

Cause and Effect

So far only two justifications have been given for the use of the decibel, and these are that smaller numbers may be used and gains and losses in a system may be added rather than multiplied. Another and far more important reason is that in some cases the db gives a more truthful representation of the state of affairs than any other method.

Most human perceptions are logarithmic in their effect. This means that the effect observed does not appear to vary in the same way as the cause. For example, a loudspeaker producing 1 watt will not sound twice as loud when the volume is increased to 2 watts.

But if, say, 5 watts produced an apparent loudness of twice that at 1 watt, then changing the level to 25 watts would only sound twice as loud again, and 125 watts twice as loud again. Now this is particularly awkward when plotting frequency response curves. A typical curve is shown in Fig. 2. This is plotted directly in watts and frequency. But it has already been said that a change in power of n watts does not produce an effect in our ear of n times the loudness, so the curve of Fig. 2 will not tell us what the change in loudness is between f_1 and f_2 . If, however, we plot decibels against frequency, we will obtain curve b, which will give a more accurate idea of the change in loudness from frequency f_1 to f_2 .


Another more striking example of the same thing is shown in Fig. 3. An amplifier has been tested at two gain settings, shown by curves 1 and 2. When plotted gain against frequency, as in 3(a), the shapes of the curves look quite different—the lower gain curve looks as though it might have a better frequency response than the higher gain one. In fact, the 3 db "down" points, i.e. those frequencies where the gain has dropped to -3 db relative to the middle frequency gain, are the same for both curves.

Plotting the same curves on a db-against-frequency basis produces Fig. 3(b). The curves are exactly the same shape for both gain settings. This is certainly far less misleading than Fig. 3(a).

Relative Levels

You will notice that the db has always referred to a condition of change. The ratio

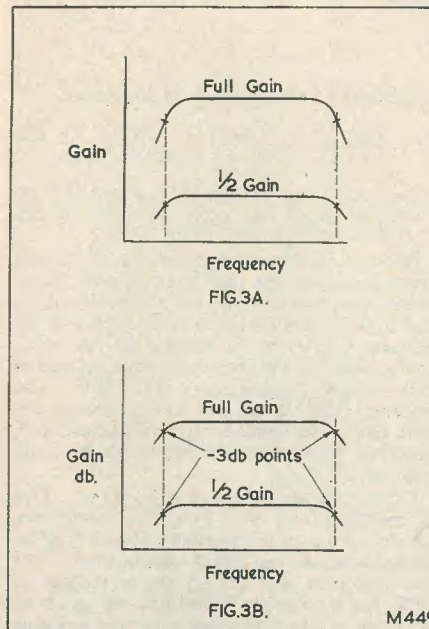between two levels at input and output of an amplifier or attenuator, or the two levels of output at two frequencies, etc. The db is a measure of change. It would be meaningless to say: "My radio has an output of 50 db." One could only ask, "20 db more (or less) than what?"



Such a statement can only be made if it is understood what level is taken as standard. If 50mW were taken, quite arbitrarily, as a standard of power output, then it could be said that the output of a receiver were 20 db, relative to 50mW. There have been a number of standard levels, one, for example, at 1mW in Europe and another of 6mW in America.

An expression that is always cropping up is, "the response is 3 db down at 10 kc/s." The reason for picking 3 db is that this number represents half power.

$$\text{i.e. db} = 10 \log \frac{1}{2} = -3\text{db (power)}$$

(Note the minus sign representing a loss.)

This is a power ratio, however. As a voltage ratio 3 db is $1 : \sqrt{2}$.

$$\text{i.e. db} = 20 \log \frac{1}{\sqrt{2}} = -3\text{db (voltage)}$$

In other words, the power will have dropped to half its normal value at 10 kc/s, the voltage to $\frac{1}{\sqrt{2}} = 0.707$ of its normal value at 10 kc/s.

This 3 db criterion is used when talking of tuned circuits. The Q of the circuit is often defined as (see Fig. 4):

$$Q = \frac{f_0}{f_2 - f_1}$$


Now f_2 and f_1 are the frequencies where the voltage across the circuit has dropped to 0.707 of its peak value (i.e. dead on tune) at f_0 . These points, as may be seen, are also the points where the available power across the circuit has dropped to half its peak value, and are often called the "half power points." Either way, these points are the -3 db points.

The -6 db points are also shown in Fig. 4. These are of no particular significance in relation to tuned circuits, but it is worth remembering that -6 db represents half voltage and quarter power.

Historical

Early on in this article, in expression (1) to be precise, a mysterious 10 appeared, and was not explained at the time.

It appears that in telephone work at the beginning of the century, a "transmission unit" was evolved for expressing the performance of a telephone line in terms of a standard line. Later the "bel" appeared, and was subsequently divided by ten to become the decibel. The name "bel" is derived from Alexander Graham Bell, the inventor. It should be remembered that the decibel uses logarithms to the base 10. Another unit is the "Neper." This uses "natural" logarithms to the base 2.718, or e as it is usually designated.

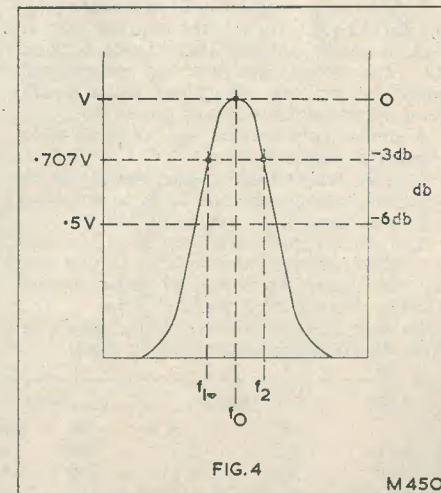

DESIGN CHARTS FOR CONSTRUCTORS

No. 17 TRIODE STAGE GAIN

by HUGH GUY

WHEN THE TRIODE VALVE IS USED AS AN amplifier the voltage gain provided by the stage, defined as the output a.c. voltage per input a.c. volt, is given by the well-known formula:

$$G = \frac{\mu R_L}{R_a + R_L}$$

where μ is the amplification factor of the valve R_a is the anode impedance of the valve in $k\Omega$ and R_L is the value of the anode load in $k\Omega$.

Now for any given triode, working under specified conditions, the two valve parameters are constants and can usually be found quoted in valve data. The problem of determining stage gain then reduces to one of selecting the correct value of anode load R_L to give the correct gain. To do this the formula must be rearranged to give

$$R_L = \frac{G R_a}{\mu - G}$$

Although this method yields a mathematically correct value for R_L , the required gain, if high, is rarely obtained in practice because the valve parameters are not maintained under the working conditions which result from the calculated value of anode load.

A deliberately chosen bad example soon brings this defect to light.

A resistance-coupled triode stage is to be designed to give a gain of 12 in an amplifier working from an h.t. supply of 350V.

The constructor's first step is to examine the contents of his valve boxes. In this case we will assume he finds two rather similar triodes—namely the 6J5 and a 6L5.

He then turns to his valve data, where he finds the following characteristics listed.

Type	Heater		Anode		Bias	R_a $k\Omega$	μ	Base
	V	A	V	mA				
6J5	6.3	0.3	250	9	-8	7.7	20	10
6L5	6.0	0.15	250	8	-9	9.0	17	10

Trying each valve in turn he calculates the value of R_L from formula.

For the 6J5 this would be solved as follows:

$$R_L = \frac{12 \times 7.7}{20 - 12} = 11.55k\Omega \text{ or } 12k\Omega \text{ to the nearest available value.}$$

For the 6L5 the anode load would be:

$$R_L = \frac{12 \times 9}{17 - 12} = 21.6k\Omega \text{ or } 22k\Omega \text{ to the nearest available value.}$$

The conditions of operation must now be considered from the point of view of the effect they have on the circuit values.


Taking first the calculated value of the 6J5 anode load, we see that the required 9mA, which must flow through the valve and anode load to achieve an amplification factor of 20, produces a drop in the resistor of 108 volts, which, added to the specified anode voltage of 250V, makes the necessary h.t. 358V. The proposed 350V is not too low to change the valve parameters sufficiently in this case, and, therefore, the choice of a 6J5 would be quite satisfactory.

This is not true of the 6L5, however. This valve should draw 8mA for correct operation, but were it to do so, then 176 volts would be dropped across the 22k Ω anode load. For this condition, and for an anode voltage of 250V, the h.t. supply would have to be about 425 volts. In fact, to specify the true working conditions for the valve, the characteristic curves would have to be consulted for an accurate assessment of the performance of the stage.

Now this process of compromise is one that cannot be avoided in the design of an amplifier, and, in fact, it is only after quite a number of design attempts that the engineer becomes sufficiently experienced to know the limitations of his valves, and on this basis, which type to select for a particular application. The purpose of conducting the above exercise was twofold; both to demonstrate


the steps involved, and to show that a certain amount of inevitable and tedious arithmetic arises.

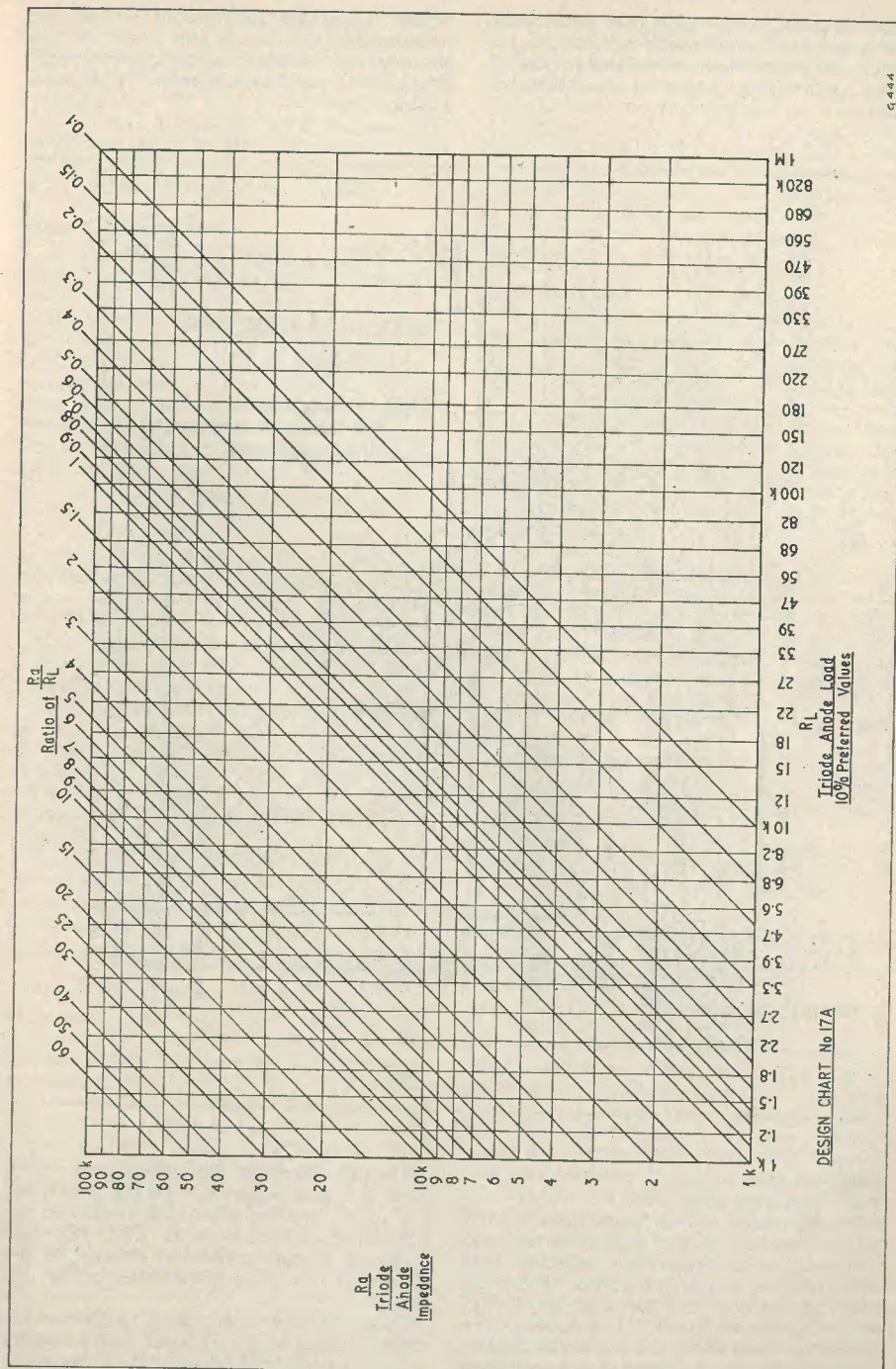The charts are, of course, designed to eliminate the latter process, and may be used



both to calculate the gain that a particular valve and load combination will give, and to determine the anode load required for known valve parameters to give a predetermined gain.

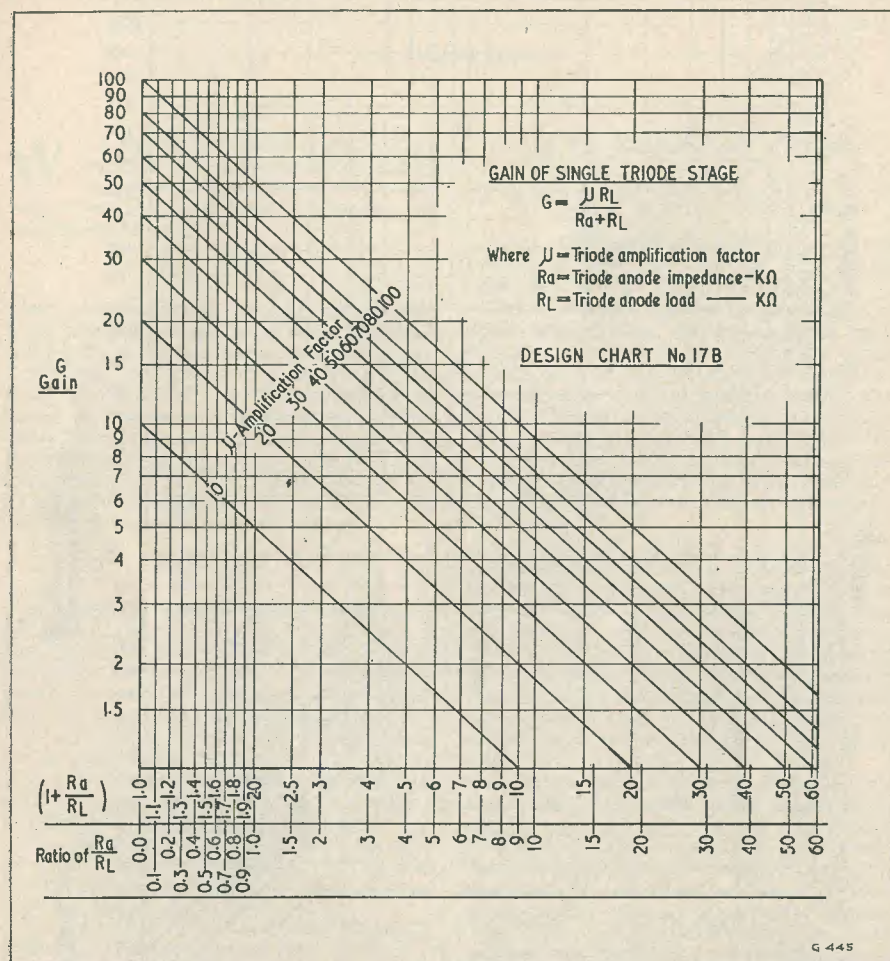noted. Diagonal lines indicate the principal intersections, and where two values do not actually cross on one of the existing diagonals, the ratio value can be interpolated from those already there.



Using the Charts

A. To Calculate Stage Gain.

The R_a and R_L of the stage under review are first required. Chart A gives vertical and horizontal scales respectively covering most values likely to be met in practice. This chart must be used to find the ratio of R_a/R_L , which is accomplished as follows. The respective values of R_a and R_L are located on their scales on the chart and their intersection

Having obtained the appropriate ratio, chart B is now consulted. To the ratio value 1 is added, and this new value located on the horizontal scale of chart B. (For reference purposes a scale calibrated directly in the ratio R_a/R_L is given immediately below this scale.)

Diagonal lines on this chart are marked for various values of amplification factor ranging from 10 to 100, and selecting the appropriate

" μ " line for the chosen valve, the point of intersection of the " $(1+R_a/R_L)$ " value and the " μ " value is referred back to the vertical "Gain" scale to give the value of stage gain resulting from the known parameters.

Like most detailed technical explanations, the process reads far more formidably than it appears in practice, and to clarify the procedure a design example is now detailed.

Stage Gain Example

What gain can be obtained using a 6J5 triode under the operating conditions specified previously, but with a 3.9k Ω anode load?

The previous operating conditions gave an anode impedance of 7.7k Ω , and hence using chart A the ratio R_a/R_L is approximately 2.

Referring now to chart B we add 1 to the ratio 2 to give 3 on the horizontal scale. Locating the diagonal " μ " line of 20 we see that horizontal and diagonal lines intersect at 6.6. The gain, therefore, of such a stage is 6.6, to an accuracy of better than 2%.

B. To Calculate Anode Load Values

In most practical cases the designer wishes to evaluate the anode load required for a specified gain, and to do this the above procedure is reversed. Again, an example is most helpful here.

What value of anode load must be used for a 6P5 triode (μ of 100, R_a 91k Ω) to give a gain of approximately 60?

Referring to chart B we see that a gain of 60 is obtained when the " μ " line of 100 intersects the horizontal scale reading $(1+R_a/R_L)$ of 1.65. This latter reading results from the ratio R_a/R_L of 0.65, which is promptly located among the diagonal lines of Chart A.

At the intersection of this ratio value and the value of R_a of 91k Ω , the required value of anode load will be found. Since no visible

values exist for any of these quantities, the nearest obtainable anode load resistance to the interpolated values would be chosen. In this case it is a toss-up between 120k Ω and 150k Ω , the former giving a gain of 57 and the latter a gain of 62. The h.t. potential would have to be quite high to achieve such a gain in practice, and the constructor should verify that the typical operating conditions specified in the valve data are maintained in the practical circuit in the manner already indicated.

Point to Watch

The true gain of a triode under a.c. conditions should take into account the effect of the grid leak of the stage following the circuit under consideration. This grid leak effectively appears in parallel with the anode load, tending to reduce the real anode load, and hence lowering the gain. Though this effect does not modify the d.c. working conditions of the circuit, the reduction in the load to a.c. signals should be offset by an appropriate increase in the calculated value of anode load.

In the example considered above, for instance, if the following grid leak were 1M Ω , then the effective a.c. load with a 150k Ω anode load would be the resultant parallel value of 130k Ω approximately. Under this condition the gain becomes 59 instead of 62. If the following grid leak had been only 250k Ω , then the gain would have been reduced to 51.

As a rough general rule, the effect of the following grid leak can be ignored if the leak can be made ten times (or greater) the value of the anode load.

But take note of the manufacturer's ruling on the maximum grid leak for any given valve, particularly if the latter is an output stage.

RADIO COURSES

"The GRAFTON RADIO SOCIETY announce that they have again made arrangements with the Islington L.C.C. Men's Evening Institutes for official courses in the RADIO AMATEURS EXAMINATION and MORSE (both for beginners) to be held this winter at the Isledon School, Upper Hornsey Road, Holloway, London, N.7. The classes will meet on Mondays, commencing September 23rd, for the R.A.E. 7-9 p.m., followed by the Morse at 9-10 p.m., under the instruction of Messrs. S. H. Iles (G3BWQ) and L. Barber respectively. The fee is 20s. for one course, with an additional 2s. 6d. for the second. Application in the first instance should be made to the Hon. Secretary of the Grafton Radio Society, A. W. H. Wennell (G2CJN), 145 Uxendon

Hill, Wembley Park, Middlesex, at once so that a place may be assured."

A course is being held during the coming autumn-winter Evening Classes at Doncaster Technical College, the instructor being Mr. J. B. Willmott, A.I.P.R.E. The course is purely an "interest" one, not being designed with any trade or professional examination in view, and it is mainly of a practical nature. Students are encouraged to bring along their own receivers, etc., home-built or otherwise, for alignment, servicing, etc.

Classes are held on Monday evenings. Full details and application form can be obtained on request from Mr. S. Edwards, Electrical Engineering Section, Doncaster Technical College.

A CIGAR BOX RADIO

by E. C. HARRIS

THE WHOLE RECEIVER, COMPLETE WITH batteries, was contained in a cigar box which previously held twenty Mannikin cigars. This box fits into most jacket pockets and is, therefore, very suitable for its purpose.

External controls have been selected so that they do not protrude more than is necessary for easy operation. The volume and on-off control are operated by one finger, and so is the sliding wavechange switch. The tuning trimmer has a knob which is only slightly larger in diameter than the depth of the box.

The circuit consists of a tuned crystal detector followed by a high-gain, three-valve amplifier. The signals are tuned by a Repanco Crystal Set Coil in parallel with a 250pF trimmer. Any reliable crystal can be used for rectification. The amplifier is built round three CK507AX deaf-aid pentodes, requiring 1.25 volts l.t. and 30 volts h.t. Control of filament current and volume is provided by a miniature 1MΩ pot. The output transformer is also of the miniature type, providing correct matching for the valve and earpiece.

The circuit is shown below; all resistors are 1/4 watt type. A minimum of components is used and the circuit is quite stable.

Construction

The main components, i.e. trimmer, coil, batteries and their clips, wavechange switch and volume control are mounted. The battery clips can be made from any springy metal, the writer using brass plates from a tuning condenser. The low tension positive terminal was made from the contact from a mains lamp-holder. The volume control is mounted by two woodscrews on the edge of the box, a suitable gap having been cut (see diagram).

The wavechange switch is mounted near the tuning components, to keep wiring short and direct.

The amplifier is built in a U-shape, curving round at the bottom so that all leads can be taken through the top of the box. The valves need not be mounted, but can be just held down at earthing points, etc., by their wires. They can be protected from microphony and damage by rolls of cotton wool contained in cello tape. The output transformer also needs no mounting, being held down by its wiring.

The valves have wire ends, and the electrodes are identified by numbering the wires from a red spot at one end, numbering 1 to 5, as shown in diagram.

After great trouble in identifying these leads, the writer found their connections stamped on the manufacturer's labels.

Results

For indoor use the set needed an earth and its 3ft rod aerial. An external aerial greatly improved volume to loudspeaker strength, the loudspeaker being five times as large as the receiver.

Outdoors, away from buildings, volume was quite adequate with the rod aerial and no earth. Volume increased slightly by connecting the earth clip to the framework of the writer's bicycle.

For listening on the bicycle, the writer devised a stethoscope arrangement with the miniature earpiece. A piece of rubber tubing from heavy cable was cut and a small hole made in its centre. This fitted the flange of the earpiece. Into both ends of this were fitted two lengths of tubing taken from the outer sheath of a length of co-axial cable. These were cut so that, when in the ears, the earpiece hung about two inches under the chin. The ends were covered by a single layer of soft foam rubber to make an airtight cavity and a comfortable fit. If the tubes tend to pull outwards they can be folded, tied and left in that position for a while.






The writer's aerial was one of the elements of an indoor t.v. aerial. It had another rod inside it, and its extension increased volume and range considerably.

The knob for the trimmer was made from a large accumulator terminal. The screw was removed from the trimmer and replaced by one of the same thread, but selected so that when the trimmer was fully open the "spindle" extended for 1/4 in out of the box. The knob was fixed by a lock-nut and solder.

The set is easy to build and very inexpensive. Its musical qualities can be improved by the addition of a 0.001μF condenser across the primary of the output transformer.

Components

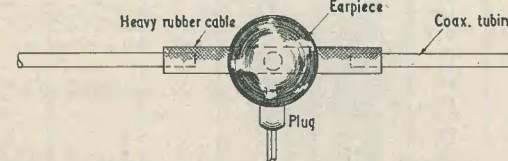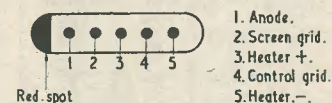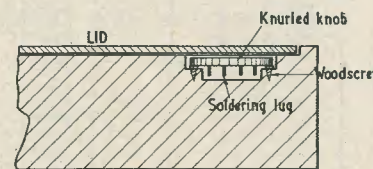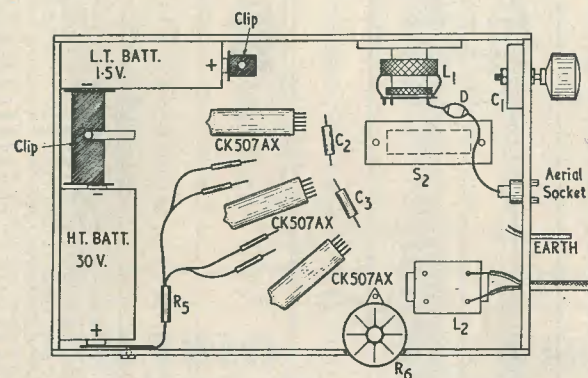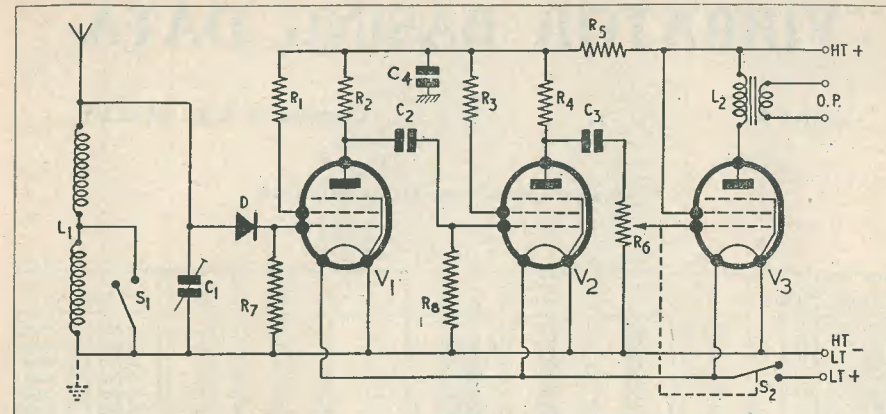- C₁ 250pF (trimmer)
- C₂ 0.002μF
- C₃ 0.002μF
- C₄ 0.1μF
- R₁ 10kΩ
- R₂ 500kΩ
- R₃ 10kΩ
- R₄ 500kΩ
- R₅ 10kΩ
- R₆ 1MΩ pot with switch.
- R₇, R₈ 2MΩ
- S₁ Sliding switch
- S₂ Filament switch on pot
- D Any reliable diode
- L₁ Repanco Crystal Set Coil
- L₂ Output transformer to match 30Ω
- V₁, V₂, V₃ CK507 AX



VIBRATOR BASING DATA

PART 3

Compiled by E. G. BULLEY

For base connections and key see July issue

Type	Base	1	2	3	4	5	6	7	Remarks
V5770	1	Blank	P1	P2	R	---	---	---	4 pin UX base
5310	1	R	P1	P2	Blank	---	---	---	4 pin UX base
T15S	1	R	P1	P2	Blank	---	---	---	4 pin UX base
7239124	1	R	P1	P2	Blank	---	---	---	4 pin UX base
903M	1	R	P1	P2	Blank	---	---	---	4 pin UX base
454	1	R	P1	P2	Blank	---	---	---	4 pin UX base
V5641	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5312	2	R	P1	Blank	Blank	P2	Blank	---	6 pin UX base
5052374	2	R	P1	Blank	Blank	P2	Blank	---	6 pin UX base
PJ14S	2	R	P1	Blank	Blank	P2	Blank	---	6 pin UX base
2991	2	R	P1	Blank	Blank	P2	Blank	---	6 pin UX base
5313	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5052378	1	R	P1	P2	Blank	---	---	---	4 pin UX base
T12	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5314	1	R	P1	P2	Blank	---	---	---	4 pin UX base
350	1	R	P1	P2	Blank	---	---	---	4 pin UX base
8543	1	R	P1	P2	Blank	---	---	---	4 pin UX base
2041	1	R	P1	P2	Blank	---	---	---	4 pin UX base
1100	1	R	P1	P2	Blank	---	---	---	4 pin UX base
400	1	R	P1	P2	Blank	---	---	---	4 pin UX base
NP490	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5320	1	R	P1	P2	Blank	---	---	---	4 pin UX base
324B	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5042703	1	R	P1	P2	Blank	---	---	---	4 pin UX base
2685	1	R	P1	P2	Blank	---	---	---	4 pin UX base
J15ST	1	R	P1	P2	Blank	---	---	---	4 pin UX base
505P	1	R	P1	P2	Blank	---	---	---	4 pin UX base
464	1	R	P1	P2	Blank	---	---	---	4 pin UX base
NP64	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5321	1	R	P1	P2	Blank	---	---	---	4 pin UX base
902M	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5323	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5324P	2	P1	P1	Blank	P2	P2	R	---	6 pin UX base
337	2	P1	P1	Blank	P2	P2	R	---	6 pin UX base
J16	2	P1	P1	Blank	P2	P2	R	---	6 pin UX base
506P	2	P1	P1	Blank	P2	P2	R	---	6 pin UX base
5325P	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5326P	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5327P	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5330	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5331	1	Blank	P1	P2	R	---	---	---	4 pin UX base
2945W	1	Blank	P1	P2	R	---	---	---	4 pin UX base
ZW37216	1	Blank	P1	P2	R	---	---	---	4 pin UX base
5333	1	R	P1	Blank	P2	---	---	---	4 pin UX base
338	1	R	P1	Blank	P2	---	---	---	4 pin UX base
7237666	1	R	P1	Blank	P2	---	---	---	4 pin UX base
2689	1	R	P1	Blank	P2	---	---	---	4 pin UX base
J9S	1	R	P1	Blank	P2	---	---	---	4 pin UX base
860	1	R	P1	Blank	P2	---	---	---	4 pin UX base
5334	1	R	P1	Blank	P2	---	---	---	4 pin UX base
345	1	R	P1	Blank	P2	---	---	---	4 pin UX base
T9S	1	R	P1	Blank	P2	---	---	---	4 pin UX base
7238685	1	R	P1	Blank	P2	---	---	---	4 pin UX base
2088	1	R	P1	Blank	P2	---	---	---	4 pin UX base
PJ7	1	R	P1	Blank	P2	---	---	---	4 pin UX base
870	1	R	P1	Blank	P2	---	---	---	4 pin UX base
436	1	R	P1	Blank	P2	---	---	---	4 pin UX base
402	1	R	P1	Blank	P2	---	---	---	4 pin UX base
NP487	1	R	P1	Blank	P2	---	---	---	4 pin UX base
5335	1	R	P1	Blank	P2	---	---	---	4 pin UX base
5339	1	R	P1	Blank	P2	---	---	---	4 pin UX base
5340M	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5341M	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5342	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5343M	1	R	P1	P2	Blank	---	---	---	4 pin UX base
TU3S	1	R	P1	P2	Blank	---	---	---	4 pin UX base

Type	Base	1	2	3	4	5	6	7	Remarks
5052378	1	R	P1	P2	Blank	---	---	---	4 pin UX base
5365	2	R	P1	internally connected to pin 2	internally connected to pin 5	P2	internally connected to pin 1	---	6 pin UX base
5052374	2	R	P1	internally connected to pin 2	internally connected to pin 5	P2	internally connected to pin 1	---	6 pin UX base
PJ14S	2	R	P1	internally connected to pin 2	internally connected to pin 5	P2	internally connected to pin 1	---	6 pin UX base
452	2	R	P1	internally connected to pin 2	internally connected to pin 5	P2	internally connected to pin 1	---	6 pin UX base
5400	2	P1	S1	Blank	Blank	S2	P2	---	6 pin UX base
5404	2	P1	S1	R	Blank	S2	P2	---	6 pin UX base
540	2	P1	S1	R	Blank	S2	P2	---	6 pin UX base
T69	2	P1	S1	R	Blank	S2	P2	---	6 pin UX base
8637	2	P1	S1	R	Blank	S2	P2	---	6 pin UX base
PJ69	2	P1	S1	R	Blank	S2	P2	---	6 pin UX base
954	2	P1	S1	R	Blank	S2	P2	---	6 pin UX base
734	2	P1	S1	R	Blank	S2	P2	---	6 pin UX base
SP633	2	P1	S1	R	Blank	S2	P2	---	6 pin UX base
5406	3	P2	S1	R	S2	P1	---	---	5 pin UX base
525	3	P2	S1	R	S2	P1	---	---	5 pin UX base
T63	3	P2	S1	R	S2	P1	---	---	5 pin UX base
5053183	3	P2	S1	R	S2	P1	---	---	5 pin UX base
2687	3	P2	S1	R	S2	P1	---	---	5 pin UX base
P157	3	P2	S1	R	S2	P1	---	---	5 pin UX base
289Y	3	P2	S1	R	S2	P1	---	---	5 pin UX base
781	3	P2	S1	R	S2	P1	---	---	5 pin UX base
SP72	3	P2	S1	R	S2	P1	---	---	5 pin UX base
QD6	3	P2	S1	R	S2	P1	---	---	5 pin UX base
5409	3	P2	S1	R	S2	P1	---	---	5 pin UX base
S20	3	S1	P1	R	P2	S2	---	---	5 pin UX base
T61	3	S1	P1	R	P2	S2	---	---	5 pin UX base
5053185	3	S1	P1	R	P2	S2	---	---	5 pin UX base

(to be continued)

RADIO CONTROL

FOR MODEL SHIPS, BOATS AND AIRCRAFT

by F. C. JUDD, G2BCX

To operate a model ship or aircraft is a most interesting hobby. But how much more fascinating it would be if one could emulate the skipper or pilot and remain in control after the model has been set off on its course. This, thanks to radio control, can now be done, and enthusiasm for it is steadily mounting. Radio Control for Model Ships, Boats and Aircraft has become a recognised handbook in this field.

144 pages 135 diagrams and illustrations

Standard Edition, art board cover, 8s. 6d. postage 5d.

Cloth bound, with gold lettering, 11s. 6d. postage 7d.

DATA PUBLICATIONS LTD
57 MAIDA VALE LONDON W9

THREE DEE

Build this amazing new transistor radio featured in this issue

SIMPLE TO BUILD

FULL SPEAKER VOLUME

LOW RUNNING COST

Components as specified by the designers

Repenco drilled chassis	3/-
Repenco coils type DRR2	4/-
Repenco transformer type TT5	8/-
Variable 500pF condensers	each 3/10
Red Spot transistors	each 10/-
Resistor kit	2/6
Condenser kit	7/3
3-pole 3-way switch	3/9
8-way tag board	1/6
Socket panels	each 6d.
Set of dial plates	2/3
Set of pointer knobs	2/3
Battery plug	8d.
Loudspeaker	22/6
7½ volt battery	2/-
Crystal diode	2/6
Hardware kit (nuts, bolts and wire)	1/6

RADIO EXPERIMENTAL PRODUCTS LIMITED
33 MUCH PARK STREET COVENTRY

TELETRON Type FX.25

Self-tuned, dual wave
Ferrite rod aerial. 15/- each



Specified for the "Companion" 3 Transistor regenerative pocket receiver.
Type 24 Inductor 3/6 each



TRANSISTOR I.F. TRANSFORMERS

High Q "potted" construction, with Ferrite screw cores. Mounted in screening cans 1" x 3/4" dia. 6/6 each. Oscillator coil, 6/6. Transistor type Ferrite rod aerial for MW band, 10/-. Selective crystal diode coil type HAX, 3/- each. Type HAX.L (for LW band), 3/6. Dual wave TRF coils, type A/HF, matched pair, 7/-, with adjustable iron dust cores.

FERRITE ROD AERIALS



Wound on high permeability Ferro-cube rod. No external aerial required. Full sensitivity. Ideal for battery portable receivers. Medium wave, type FRM 4" x 1/8", 8/9. Dual wave type FRD, 8" x 1/8", 12/9. Miniature R.F. Chokes, wound on iron dust cores, with wire end terminations. 2.5 and 5mH, 3/- each; 10mH, 3/6. 200mH top lift Inductors, 6/6 each. Bias rejector coils, 4/6 each. Tape oscillator coils for push-pull operation, 8/6 each.

Send 5d. in stamps for complete data and circuits. All types available from advertisers in this Magazine and local component stockists.

THE TELETRON COMPANY LIMITED

266 Nightingale Road . London N9

Telephone HOW 2527

Trade enquiries to sole distributor

S. Mozer Ltd 288 Hedge Lane N13 Telephone PAL 1748 or EDM 7707

DATA BOOK No. 8

PRICE 3/- postage 3d.

"Tape and Wire Recording"

(Revised Edition)

DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9 CUN 6141 (2 lines)

NEW CATALOGUE

"60 Pages of Spares"

Price 1/- Post Free

It includes 118 exact replacement Potentiometers and Mains Droppers, Line Output Transformers, Tools, etc., etc. For example:

MAINS DROPPERS. For Ultra Twin. SMD.6 1,690 ohms+1,450 ohms 5/3; SMD.7 175 ohms+340 ohms+410 ohms 5/3, etc., etc.

OUTPUT TRANSFORMERS. For Ultra Twin 11/9; Philips 290U 12/9, etc., etc.

ELSTONE TRANSFORMER RANGE. CRT Isolation, Mains Primary, 2V, 4V, 6.3V, 10.8V, 13.3V, optional 20% boost, 22/-, etc., etc. State CRT voltage required.

TOOLS. Stead wire cutters 5/6; Solon Instrument Iron 24/-, etc., etc.

SERVICE AIDS. Switch cleaner 4/6; Ersin solder 5/- and 2/6, etc., etc.

Air Spaced Coaxial Cable, 9d. per yd. Minimum postage 6d.

M. FOY

6 WYKEBECK GARDENS LEEDS 9

The Walk-around Shop

for THE MOST SIGNIFICANT
RELEASE THIS YEAR

--- the **TS184 A/AP** ---

Real 70 cm Test Gear,
brand new in carrying case for only **£5.10.0**
plus 10/- packing & carriage


Portable precision for mobile hams, amateur TV telearchics (with acknowledgments to Free Grid) and those Monitoring the latest U.H.F. allocations.

Resonant Cavity Wavemeter, calibrated 400-430 Mc/s. Tuning stops adjustable to any 30 Mc/s band within 400-470 Mc/s coverage. Calibrated scale rack and pinion drive piston input attenuator—and alternative fixed coupling loop input provide facilities for use as signal generator.

Plug-in "Telescopic Probe Antenna," 616 detector and monitor amplifier, 2-600 ohm 'phone jacks for modulated signals. Panel output terminals for metering 616 output current. Power required: 6V at 300mA and 30V at 1/2 mA.

Circuit diagram and instructions for adjusting tuning stops supplied. Details of suggested free running oscillator to plug in front panel. Socket for signal generator operation (or built-in oscillator for those who prefer) and comprehensive circuit description available shortly; automatically sent to every purchaser as soon as ready.

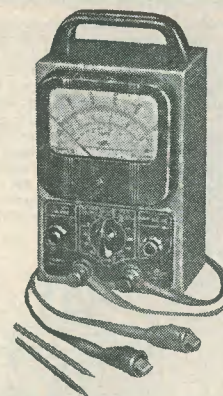PROOPS BROS. LTD Open all day Saturday
Dept. R, 52 Tottenham Court Rd. W1
Hours 9-6 p.m. Thursday to 1 p.m. LAngham 0141



**Yours
by
return
for
only
£2.10.0
deposit**

(CASH PRICE £12.7.6)

PULLIN SERIES 100 MULTI-RANGE TEST SET


21 ranges AC/DC from 100 microamps to 1,000 volts, sensitivity 10,000 ohms/volt. This is the famous Pullin Series 100, now available brand new on the easiest of terms. Send 50/- deposit, balance to be paid in nine monthly payments of 24/6.

Descriptive literature available on request

HOME RADIO (Mitcam) LTD
(Dept. RC) 187 London Road
MITCHAM, SURREY

Telephone MITcham 3282

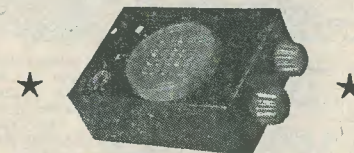The Teletron "COMPANION" COMPLETE KIT (as spec.) **£4.15.0** (Postage 1/6)



COMPONENT PRICE LIST

Cabinet and chassis, ready drilled	8/6
C1 2µF 6V condenser	2/6
C2 & C3 500pF & 50pF condensers each	9d.
C4 0.01µF condenser	10d.
L1 Teletron FX25	15/-
T1 & T2 Ardent D239 & D240 trans. each	10/-
R2 25kΩ Egan switched volume control	7/-
R1, R3 to R6 miniature resistors ... each	4d.
Tag strip	7½d.
Balanced armature reproducer	5/6
TR1 R.F. transistor	21/-
TR2 & TR3 audio transistors ... each	10/-
Wave change switch	1/3
Knobs	each 9d.
Circuit diagram with full instructions	9d.
*Blue Spot transistor	15/-
*L2 type 24 coil	3/6

*Not required when using TR1 R.F. transistor

ELEC-RADIO

172a BLACKSTOCK ROAD Highbury
LONDON N5 Telephone CANonbury 1672
Callers Welcome

BARGAINS TO CLEAR

A.C. Superhet 5-Valve Chassis. Medium and two short, unused, but less valves and mains transformer. Uses standard Octal range. 27/6. (Again, coil pack worth much more.) Non-callers add 6/6.

A.C. Superhet 7v. 5-Waveband Chassis. H.F. stage. Unused. Less valves and power pack. Slightly soiled. Coil pack worth twice as much, circuit diagram supplied. £2.15.0, carriage and insurance 7/6.

A.C. 4-Valve Superhet, complete with valves, but less scale and pointer, unused. Circuit diagram supplied. 39/6 plus.

Note that the above three chassis, although unused, will need checking. On account of low price, no guarantee is given. Nor, we regret, can technical assistance be given.

0.1 mfd. 350 v. Small Tubular Metal cased Condensers. Made by Dubilier. 2/6 per dozen. **Germanium Diodes.** B.T.H. with wire ends. 10d. each or 9/- dozen.

Midget I.F. Coils. Dust cored, size 1 1/2" x 1", 465 kc/s. 4/6 pair **Standard Size. I.F. Coil.** Dust cored, 465 Mc/s. 4/6 pair.

Coil Pack for Superhet. 465 kc/s, I.F. Medium and 2 short waves. 9/6.

Cathode-Ray Tube. VCR97. Instrument type. New 7/6 each, carriage 3/6.

Bakelite 5 Amp. Electric Wall Switch. "Hicraic," 9d. each, or 8/- per dozen.

Series, parallel and off-electric wall switch made by Crabtree. Price 1/3 each, or 13/6 per doz. NOTE: Additional Technical Data is not available on these bargain items.

Amplifier, ex-Government unit 1134 contains one double triode and one triode. 6/6, post and ins. 2/6.

Connecting Wire, P.V.C. covered 24 s.w.g. copper. 2/6 per 100ft., or 5 coils, different colours, for 10/-.

Scanning Coils by very good maker. New and unused. 4/6 complete.

10 v. Superhet, 1 1/2 metre. Ex-Govt., but unused. Complete with valves. Easily converted for Band III. 39/6, carriage and packing 7/6.

Cathode-Ray Tube, VCR517. 8/6 each, carriage 2/6.


Mains Lead. Metal screened to stop interference, 9d. yard.

Midget Push-pull Input Transformer and push-pull output transformer to match. 8/- pair.

NOTE: Orders for small components over £2 are post free, otherwise please add sufficient.

DO-IT-YOURSELF

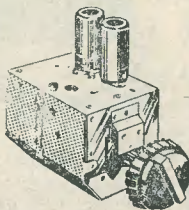Hundreds of people have already fitted our T.V. converter and now enjoy BBC and ITA programmes—you can do the same. Our outfit contains: ITA Converter—ITA Aerial—36ft. Co-ax Down Lead—Interference Suppressor—Illustrated detailed instructions—nothing else to buy, all for £8.10.0, carriage and insurance 4/6 or 10/- deposit and 9 monthly payments of £1.




TURRET TUNER


Brand new stock, not surplus, with coils for Bands I and III, complete with valves—PCC84 and PCF80—I.F. Output 33/38 Mc/s with circuit diagram 79/6. With knobs 3/6 extra, post and ins. 2/6.

14" T.V. CABINET

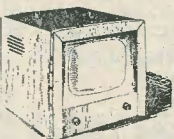14" T.V. cabinet of the latest styling made for one of our most famous firms—beautifully veneered and polished—limited quantity—19/6 each. Carriage and packing 3/6 extra.



THIS MONTH'S SNIP

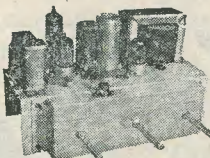

THE OCTAVIAN


HIGH FIDELITY AMPLIFIER

3 valve 4 watt with frequency response better than 40-15,000

c.p.s. Control panel size 8" x 2 1/2" comes fixed to chassis but is intended for independent mounting. Separate bass and treble controls giving fullest variation of cut and lift. Separate switch, absolutely no mains hum. Remarkable value at £4.19.6. plus 3/6 post and insurance.

TWIN FEEDER

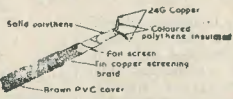
Ideal for f.m. down lead, as a twin microphone lead, etc. Sale price 6d. per yd. 80 ohm co-ax. low loss for Band III, 8d. per yd.



TELETRON COILS

Customers please note that all our branches carry good stocks of Teletron components


BAND III PRE-AMP

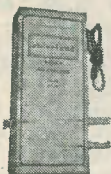

Price £4. post and packing 3/6.


In difficult areas it will be necessary to increase the signal level and this is the ideal unit for this purpose. It is A.C. mains operated and is fitted with input and output coax. plugs.

THE ELPREQ E.H.T. GENERATOR

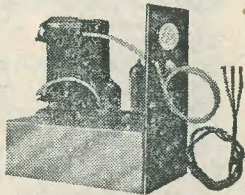

This unit contains three BVA valves. Output from 6kV to 9kV rectified with normal H.T. rail input but somewhat higher outputs can be obtained with higher H.T. supply. Dimensions are 6 1/2" x 4 1/2" x 7". Price 69/6, post., packing, etc., 5/-.

The "ESTRONIC" Band III Converter

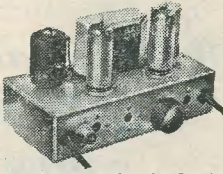

To-day's best value in Band III converters suitable for your T.V. or money refunded. Complete ready to operate. 49/6 non-mains, or 79/6 mains, post and insurance 3/6.

MORGANITE POTENTIOMETERS

Single and 2 gang types available standard size with good length spindle, all new and boxed.

Gang type 3/- each—values available: 5K + 5K, 100K + 100K, 1/2 meg. + 1/2 meg. Single types 1/- each, values available: 10K, 25K, 50K, 100K, 250K, 1 meg., 2 meg.



High "Q" Coils

4/- EACH
Iron dust cores. Clip in fixing.
EXTREMELY SMALL
AMAZING EFFICIENCY for Superhet T.R.F. or Transistor operation.

OSMOR (Frequency Controlled) F.M.

Switch-tuned Feeder With special quick-build chassis

A completely stable drift-free unit for adding to existing radio or Hi-Fi amplifier
EASY TO BUILD Size 4 1/2 in x 5 1/2 in
Wiring diagram and circuit on request.

OSMOR COILS AND COMPONENTS AVAILABLE FOR THE FOLLOWING PUBLISHED CIRCUITS

Wireless World
F.M. Tuner (Amos)
Economic Rx.
Reflex Push-pull Rx.
2-v Superhet
Car Radio
Transistor Portable (Amos)
Bedside Rx.
Sensitive TRF Rx.

Practical Wireless
High Quality B'cast Rx.
Alternative Superhet
Modern Battery Superhet
7-5 Push-pull Superhet
Car Radio
Crystal Tuner
Autoradiogram

The Radio Constructor
TRF Tuner
3 plus 1 Superhet
Hi Q Pre-set push-pull Transistor
Progressive Rx.
Whistle Filter
S.W. Rx.
Band III Converter

WE HAVE A FULL RANGE OF COILS FOR TRANSISTOR CIRCUITS

OSMOR COILS FOR HIGH "Q" SELECTIVITY & PERFORMANCE



FREE! Send 10d. (stamps) for fully descriptive literature including OSMOR DESIGNS—5-Valve Superhet, Miniature ditto, Battery and Battery/Mains Receiver, Mains T.R.F. Superhet and T.R.F. Feeders. Band 3 Converters, Wiring Diagrams, Chassis Templates, Coil and Coilpack information and price lists and information on circuits in *Wireless World*, *Practical Wireless*, *The Radio Constructor*

(Dept. RC14) 418 BRIGHTON ROAD Telephone SOUTH CROYDON · SURREY CROYDON 5148/9

SPECIAL OFFER I.T.A. CONVERTERS

70/- to clear

Post 2/6 C.O.D. 1/6



Only a few dozen. London and Winter Hill areas I.T.A. converter in chassis form. Made by famous manufacturer. Valves PCC84 and ECC81; with power supply. Working and ready for use. Direct switching I.T.A. to B.B.C.; cabinet (walnut) to fit, 10/-

DROP-THROUGH MAINS TRANSFORMERS. Brand new, 250-0-250V at 60 mA; 6.3V at 2 1/2 A and 6.3V at 1/2 A. Price 12/6 plus 2/6 post; 1/6 C.O.D.

BAND 3 CONVERTER available for Philips' receivers; complete with power pack. Bakelite case, 8 1/2" x 4 1/2" x 6" high. PCC84 and PCF80. Post 2/6, C.O.D. 1/6. Price £5.5.0

Posted orders to Camberley please

Gladstone Radio

3 CHURCH ROAD REDFIELD BRISTOL
(next door to Lawrence Hill station) and
82B HIGH STREET CAMBERLEY SURREY

ARTHURS HAVE IT!

Large Stocks of Valves and C.R.T.s
Full Range of Meters available
Avo, Taylor, Cossor, Advance, etc.
Particulars on Request

FM Kit of Parts £5, less valves

(Ref. *Radio Constructor* July 1954)

Amplifier Tape Recorders and Loudspeakers

Jason FM Tuner Unit £15 17 0
Jason Power Pack £3 10 0

Radios and Television always in stock

VALVE MANUALS

Mullard, 10/6; Brimar No. 6, Osram, Part 1

5/-; Osram, Part II, 10/-

Postage 9d. each extra

Publications "Lodestar" Tape Recorder 3/6

Goods offered subject to price alteration and being unsold

Arthurs first

Est. 1919

Proprietors ARTHUR GRAY LTD

OUR ONLY ADDRESS Gray House
150-52 Charing Cross Road
London WC2

TEmple Bar 5833/34 and 4765

ELECTRONIC PRECISION EQUIPMENT LTD

Post Orders should be addressed to Dept. 34 66 Grove Road Eastbourne

Personal shoppers, however, can call at:

266 London Road Croydon Telephone CROYdon 6558. Half-day Wednesday

42/46 Windmill Hill Ruislip Middlesex Telephone RUISlip 5780. Half-day Wednesday

152-3 Fleet Street EC4 Telephone FLEet 2833. Half-day Saturday.

29 Stroud Green Road Finsbury Park N4 Telephone ARChway 1049. Half-day Thursday

HENRY'S

(RADIO) LTD

5 Harrow Road Edgware Road
Paddington London W2

Opposite Edgware Road Station

PADdington 1008/9

OPEN MONDAY to SAT. 9-6 THURS. 1 o'clock

SEND 3d. FOR 28-PAGE CATALOGUE

TRANSISTORS

JUNCTION TYPE P-N-P
(British Manufacture)

RED-SPOT 800 kc/s Audio Frequency	10/-
BLUE SPOT 1.6 Mc/s Mixer and Frequency Changer	15/-
WHITE-SPOT 2.5 Mc/s R.F. and I.F. Amp.	20/-

All Transistors are Tested and Guaranteed

N.B.—The Red-Spot is similar to Mullard OC71 Transistor Bases 9d. each

TRANSISTOR PUSH-PULL AUDIO AMPLIFIER

(200 Milliwatts Output)

Build this Push-Pull Amplifier which is ideal for Crystal or Magnetic Pick-up Amplification, Baby Alarm, Microphone Amplifier, etc. Powered by 6-volt Dry Battery lasting for months. Complete Kit of Parts including 4 Transistors and all Components with Circuit (less Speaker), £4.10.0

COLLARO RC456

4 speed auto-changer. Latest type with crystal turnover pick-up £9.15.0

TRANSISTOR SIGNAL TRACER

Complete Kit with 2 Transistors, components, phones, with circuit and plastic case 42/6

TRANSISTOR SQUARE WAVE GENERATOR

Complete Kit with 2 Transistors, Components, Circuit and plastic case 25/-

DIODES

B.T.H. Germanium	1/6
Mullard OA74	2/6
1N21	3/6
1N22, 1N23, 1N21A	5/-

MODEL-MAKERS' MOTORS

Two types available, 12 or 24V with 1/4" spindle, 10/- each

6V VIBRATOR PACKS

Output 120V 30mA. Brand new


12/6

Valves — Valves — Valves

We have over 300 different types of British and American valves in stock. We give below new types that are available. Send for 28-page Catalogue for further details of valves, components, etc.

DK40 10/-	EF42 14/-	PL81 12/6	6AL5 9/-
DK92 9/-	EF80 9/-	PL82 10/-	6AM6 9/-
DAF96 10/-	EF85 10/-	PL83 12/6	6AQ5 10/-
DF96 10/-	EF86 12/6	PY81 10/-	6AU6 8/6
DK96 10/-	EF89 10/-	PY82 10/-	6BA6 8/6
DL96 10/-	EF92 9/-	PY83 12/6	6BE6 10/-
DM70 9/-	EL41 10/-	U25 14/-	6BV6 10/-
EABC8010/-	EL42 10/-	UABC8011/-	6C4 6/6
EAF42 12/-	EL84 11/-	UAF42 11/-	6U4 12/6
EBF80 11/-	EM34 10/-	UBC41 10/-	6X4 7/6
EBF89 11/-	EM80 10/-	UBF89 11/-	7C6 10/-
EBC41 10/-	EM81 11/-	UCC85 11/-	7Y4 9/-
ECF80 14/-	EM85 11/-	UCL82 15/-	12AH8 12/6
ECF82 12/6	EY51 10/-	UCH42 12/6	12AT6 8/-
ECC40 14/-	EY86 12/6	UCH81 12/6	12AT7 9/-
ECC81 9/-	EY91 10/-	UF41 10/-	12AU6 9/-
ECC82 9/-	EZ40 8/-	UF80 12/-	12AU7 9/-
ECC83 9/-	EZ80 10/-	UF85 12/-	12AX7 9/-
ECC84 11/6	EZ81 10/-	UF89 11/-	12BA6 9/-
ECC85 10/-	PABC8015/-	UL41 10/-	12BE6 10/-
ECH42 11/-	N78 12/6	UL84 11/-	14S7 14/-
ECH81 11/-	PCF80 12/6	UY41 9/-	19AQ5 11/-
ECL80 10/6	PCC84 11/-	UY85 9/6	20L1 14/-
ECL82 14/-	PCF82 11/-	3A5 10/-	35W4 8/-
EF40 12/6	PCL82 12/6	3Q4 9/-	50B5 10/-
EF41 10/-	PCL83 15/-	6L18 12/6	117Z3 8/6

All Valves Tested and Guaranteed

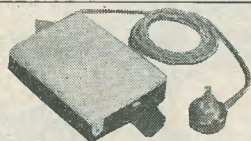

MINI-TWO

2-TRANSISTOR MINIATURE POCKET RADIO
(No Aerial or Earth)

The smallest transistor set offered on the market. Variable tuning. Drilled chassis, plastic case size 3" x 2" x 3/4", miniature hearing aid, 2 transistors and all components including 1 1/2 volt battery, circuits and full practical layout diagrams.

Total cost 55/- complete

"HOMELIGHT"

2-TRANSISTOR PERSONAL PORTABLE
No Aerial or Earth required

Variable Tuning

We can supply all components including 2 transistors, diode, resistors, condensers and miniature hearing aid and plastic case, size 4 1/2" x 2 7/8" x 1 1/2", and 1 1/2V battery, for 55/-. All items sold separately


COLLARO RC/3/554

3-speed single player with crystal turnover pick-up type "T." £6.19.6, carr. 3/6. Brand new in original carton

The NEW "TRANSISTOR - 8"

Push-Pull Portable Superhet

Can be built for £11/10/-

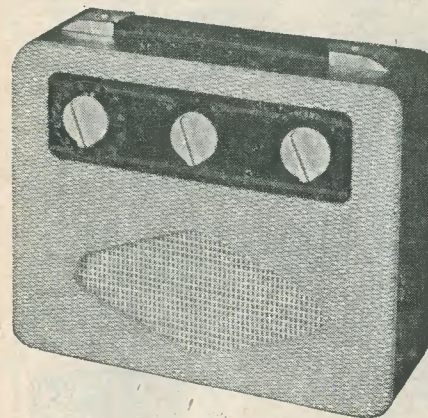

TEN STAR FEATURES

- ★ 8 specially selected Transistors
- ★ 250 Milliwatts output push-pull
- ★ Medium and Long Waves
- ★ Internal Ferrite Rod Aerial
- ★ 7" x 4" elliptical High Resistance Speaker
- ★ Drilled plastic Chassis 8 1/2" x 2 1/2"
- ★ Point to point wiring and practical layout
- ★ Economical. Powered by 7 1/2V battery
- ★ Highly sensitive
- ★ Attractive lightweight contemporary case

We can supply all these items including cabinet for £11.10.0 All parts sold separately

Send for circuit diagrams, assembly data illustrations and instructions, and full shopping list 1/6

N.B.—Pair of OC72's supplied at additional cost of 40/- Call and hear demonstration model

As featured in August issue and described on page 28

"EAVESDROPPER"

THREE-TRANSISTOR POCKET RADIO

(No Aerial or Earth required)

Variable tuning—medium wave. Total cost, as specified including Transistors, Transformers, Coils, Condensers and Battery, etc., with circuit, plastic case and battery.

All items sold separately 77/6 POST FREE

With miniature hearing aid 90/-


With balanced armature 82/6

THE TELETRON 'COMPANION'

THREE-TRANSISTOR POCKET RECEIVER

Medium and Long Waves No Aerial or Earth

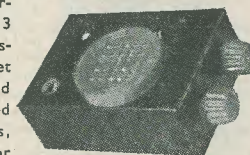Tuned R.F. Circuit. Ardenite transformers. 3 transistors. Drilled plastic chassis and cabinet size 4 1/2" x 3" x 1" and all components. Balanced armature, batteries, knobs and transistor holders.



Total cost 89/6

ALL PARTS SOLD SEPARATELY


N.B.—Transistor Holders are supplied free with all kits and we would respectfully suggest you use same, both in order to protect the Transistors and to simplify testing, and only those sets using these Holders will be accepted for inspection and testing.

HENRY'S RADIO LTD • 5 HARROW ROAD • LONDON W2

CASH or TERMS

12 MONTHS GUARANTEE TV TUBES
17" £7.10.0 14" £5.10.0

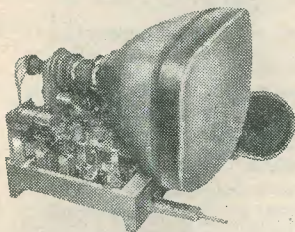
As supplied to the trade for the last 7 years. 6 months full replacement, 6 months progressive. Made possible by the high quality of our tubes. Ins. carr. 15/6
Special offer of 14", 15", 16" TV Tubes ... £5
Convert your 9", 10", 12" to above sizes. Information on how to "Do it Yourself" in our FREE catalogue. Ins., carr. 15/6
12" TV Tubes, with guarantee, £6. Ins., carr. 15/6



CO-AX. CABLE 6d. yd. Good quality. Cut to any length. P. & P. 1/6 on 20 yds. 45/- per 100 yds p. & p. 3/6
CAR RADIO AERIALS 6/9. Whip antennae 50" long, collapsing to 11". One-hole fixing. Post 1/3
HEADPHONE 1/9. Single earphone and band. C-LR. Ideal for crystal sets and radio extensions, etc. P.p. 1/3
O.P. TRANSFORMERS 1/3. Salvage guaranteed. Std. size, 2-5 ohms. P. & P. 1/- 20 or £1, p. & p. 5/6

POPULAR RADIO OR R/GRAM CHASSIS ... 39/9
3 w/and and gram. s/het 5-valve international octal. Ideal table gram, but still giving high quality output. 4 knob control. 8" p.m. speaker 7/9 with order. Set of knobs 2/-. Chassis, 12" x 6" x 9". Less valves. Ins., carr. 5/6

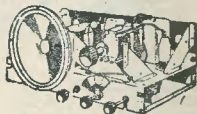Open SATURDAY all day Telephone 1LF 6001-3
DUKE & CO. (Dept. 1) 621/3 ROMFORD ROAD LONDON E12
FREE catalogue. Liverpool Street to Manor Park Station—10 mins.



LOUDSPEAKER EXTENSIONS 29/9

Fitted with 8" p.m. speaker. W.B. or Goodman's. Highest quality. Standard matching to any receiver (2-5 ohms). Switch and lead incl. Unrepeatable at this price. Money back guaranteed if not completely satisfied. Ins., carr. 3/6
8" Speakers, p.m., 8/9. At this price you can have one in every room. Let the lady of the house listen to that radio or TV program ... P. and p. 1/9




TV CHASSIS BARGAIN ... £19.19.6

Latest improved circuits. Higher e.h.t. (brilliant picture). Improved sensitivity (for greater range). Chassis easily adapted to any cabinet. As supplied to many well-known rental and hire companies. 17" Rectangular tube on adapted chassis. All channels. Valve line-up (5 valves): 6SN7, 6V6, EY51, two 6D2. Others 6L18, EL38, seven 6F1. TURRET TUNER 50/- extra. 12 months guarantee on tube, 3 months on chassis and valves. Complete and working on any channel 1-5. Less valves. With 5 valves £21.19.6. With all valves £25.19.6. Ins., carr. 25/- (incl. tube). State B.B.C. channel (and I.T.A. channel if TURRET TUNER required.)

14" TV CHASSIS, TUBE AND SPEAKER ... £13.19.6
As above with 14" round tube. Less valves. Guaranteed 3 months. With 5 valves £15.19.6. With all valves £19.19.6. TURRET TUNER 50/- extra. Ins. carr. 25/- (incl. tube).

RADIOSETTE & NURSERYETTE


(Featured in June Issue)

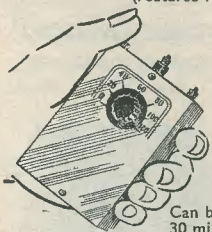

The ideal low cost transistor pocket radio for the beginner. The circuit utilises the new R.C.S. VARILoop-STICK transistor coil. A specially designed miniature .0004 tuning condenser permits the set to be in a case which fits the palm of your hand.

Can be built in 30 minutes

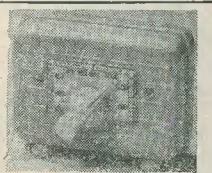All components are sold separately, full construction data including plan of parts, 2/-



The Nurseryette has been specially produced for those who require an attractive but inexpensive receiver for the children. It is safe to handle and will give months of service from the small battery included. The design includes the

R.C.S. VARILoop-STICK transistor coil and a miniature .0004 tuning condenser.

All components are sold separately, full construction data including plan of parts, 2/-
Postage: Under 10/-, 9d. Under 40/-, 1/6. Over 40/-, post free

30/-

R.C.S. PRODUCTS (RADIO) LTD.

11 Oliver Road London E17 Mail Order only

TRANSISTORWISE

RECO ONE TRANSISTOR SET

A low cost beginner's radio. Kit includes high gain ferrite core tunable inductance, super sensitive bellphone for excellent tone quality, variable capacitor for broadcast band tuning, transistor, diode, etc. Months of dependable operation from 1.5 volt cell. Complete with pocket plastic case and wiring diagram. All parts supplied separately.

PRICE 27/6 post and packing 2/6

RECO THREE TRANSISTOR KIT

Receives home and foreign stations, has high gain ferrite rod aerial, superior quality step-down transformer, sensitive balanced armature output, variable capacitor for tuning, sensitivity control, Yaxley switch, 3 transistors, diode, etc. Complete with plastic case. Uses 3 volt battery.

PRICE 49/6 post and packing 2/6

All parts sold separately
Parts list, wiring diagram for both above sets, 9d.

The RADIO EXCHANGE CO

(Dept. RC)

NEWPORT PLACE LEICESTER SQUARE
LONDON WC2 GER 2613

CLOSED ALL DAY SATURDAY

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/- per word. Trade advertisements will be accepted at 9d. per word, minimum charge 6/- per word. If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 8th of the month for insertion in the following month's issue.

PRIVATE

LINE O.P.T., 8kV, Frame O.P.T., scanning coils, focus unit, circuit. New, unused, 45/- Sound/vision chassis £3. 15 Portway, Frome, Som.

RI155. Overhauled. Built-in speaker, S. meter, RF, IF, AF gain controls. Separate power pack in matching case £8. Fradgley, West Hill House, Allerton Hill, Leeds 7. (Telephone 684720)

TAPE RECORDER. Aspden deck 721 and Hatfield amplifier in two cases £15. Box No. E142.

100 MAGAZINES. Radio Constructor, Practical Wireless, RSGB Bulletin, plus Newnes' Short Wave Manual £4 o.n.o. Morris, 88 Prescott Street, Birmingham 18.

WANTED Creed or McElroy Morse Code perforated tape sending unit. A.C. or D.C. motor, 230V or 110V. "East Keal," Romany Road, Oulton Broad, Suffolk.

NEW SWITCHED-TUNED FM Unit with A.F.C. Gold Hammer front panel engraved Home, Light, Third. Instant selection by three position switch £10.10.0. Jason FM unit with Jason dial £8.10.0. Write for details. Box No. E137.

COLLARÓ Mk. III Tape deck with Sonomag Pre-amplifier brand new. Owner going in for complete portable outfit. Cost 35 gns., accept 30 gns. Croxson, 37 Canterbury Avenue, Ilford. Telephone Val 3535.

WAVEMETER W1191 £4. Converted RA10DA £4 plus carriage. Details other surplus items. S.A.E. please, 43 Jermyn Road, Kings Lynn.

FOR SALE BC348, internal power pack, excellent condition, RF24 unit £11. Buyer collects. Circuit available. Heath, 47 Tulsmere Road, London, S.E.27.

SALE OR EXCHANGE. S2OR receiver £12. TUSB, V.F.O. £2. Meters, valves. 41 Clifford Avenue, Beeston, Notts.

BARGAINS. Constructor disposing of gear, S.A.E. for list. Jones, 63 Barcroft Street, Cleethorpes, Lincs.

6in CONSOLE Cabinet 30/-, enlarger 10/-, VCR517 10/-, 6 Kenton Gardens, Kenton, Middlesex. Telephone Wor 4846.

FOR SALE Hambander Communications Receiver. 1st class condition. One owner. 1.7 to 31 megacycles. Offers. Austin, 135 Shaftesbury Avenue, Kenton, Harrow, Middx. Telephone Wordsworth 9211.

ENTHUSIAST selling up has for disposal: unused 12,000ft reels Emitape in sealed boxes 26/-, New and guaranteed valves 6AM6, 6AL5, 6C4 4/-, 12AT7, 12AU7 5/-, PCF80, ECC80, PCC84, UCF80, ECF80 7/6. Many other items. Receivers, meters, speakers, transformers, etc., Send stamp for big list. O'Brien, 18 St. Helen's Road, Dorchester, Dorset.

NEW SURPLUS...

1A3	2/6	6L6M	11/6	803	20/-	EL41	10/-
1A5	5/6	6L7M	7/6	805	30/-	EL84	10/-
1LN5	4/6	6Q7GT	9/6	808	25/-	EM80	10/-
2A3	8/6	6SA7M	7/6	830B	15/-	EY51	11/6
2X2	3/6	6SG7M	7/6	866A	12/6	EZ40	8/-
3A4	7/6	6S17M	7/6	811	45/-	EZ80	8/-
3A5	9/6	6SK7M	6/6	1616	7/6	GZ32	10/6
3B7	6/6	6SL7GT	7/6	1629	4/6	HK24G	25/-
3D6	5/6	6SN7GT	6/6	DAF96	9/6	EY86	12/6
3O5GT	9/6	6SQ7M	7/6	DF96	9/6	KT330	9/6
3O4	8/6	6V6GT	8/6	DK96	9/6	PCC84	10/6
5B/25AM	6/6	6U4GT	12/6	DL96	9/6	PCF80	12/6
	21/-	6X4	6/6	DL33	9/6	PCF82	11/-
5R4GY	10/6	6X5GT	7/6	EA50	1/6	PL82	9/6
5U4G	8/6	7B7	9/-	EABC8010	-	PL83	10/6
5Y4G	6/6	7C5	9/-	EAF42	10/6	PCL83	12/6
6AC7M	5/6	7C6	9/-	EB34	2/6	PY80	9/6
6AG5	3/6	7S7	10/-	EB91	7/-	PY81	9/6
6AG7M	10/-	7Y4	8/6	EBC33	7/6	PY82	9/6
6AK5	5/6	12A6M	7/6	EB41	10/6	R19	12/6
6AL5	7/6	12AT6	8/6	EBF80	10/-	SP61	3/6
6AM6	7/6	12AU6	9/6	EBF89	10/-	TT11	4/-
6AQ5	8/6	12AU7	8/6	ECC82	9/6	U25	12/6
6AT6	8/6	12AH8	12/6	ECC83	9/6	UAF42	10/6
6AU6	8/6	12BE6	8/6	ECC84	11/-	UBC41	10/6
6B8G	4/6	12CBM	7/6	ECC85	10/6	UBF89	10/6
6BA6	8/6	12D7GT	9/6	ECF80	13/6	UCC85	10/6
6BE6	7/6	12Q7GT	9/6	ECF82	11/6	UCH42	10/6
6BR7	11/6	12K7GT	9/6	ECH42	10/6	UF41	10/6
6C4	5/6	12SC7M	2/6	ECH81	10/6	UF89	10/6
6C5M	5/6	12SK7M	7/6	ECL80	10/6	UL41	10/6
6FM6	6/6	12SQ7M	8/6	EF36	4/6	UY41	8/-
6F8G	4/6	12SR7M	7/6	EF37A	8/6	UY85	10/6
6F13	12/6	35L6GT	9/6	EF39	5/6	UABC80	10/6
6G6G	4/6	35Z4GT	8/6	EF41	10/6	VU39	9/6
6J5GT	5/6	35Z5GT	8/6	EF50(S)	5/6	VR105/308/6	
6J5M	6/6	42	7/6	EF55	7/6	VR150/307/6	
6J6	4/6	50L6GT	9/6	EF80	9/-	VR116	4/-
6K7G	5/6	80	8/6	EF85	10/6	Y570	3/-
6K8G	9/6	80	8/6	EF91	7/6	XP1.5	3/-
6K8M	10/6	446A	12/6	EL32	4/-	Z77	7/6
6H6M	3/6	801A	10/6				

SPECIAL OFFER

Transmitter/Receivers Army Type 17 Mk. 2. 44-61 Mc/s, complete with pair of h.r. phones, hand mike and valves. In as new condition, 45/- each or two for 79/6. Carriage paid England, Wales and Scotland only.

Special Valve Offer. 616, 6AG5, EL32, TT11, EF39, 6G6G, 6B8C, EF50, 37/6 doz. 12SC7M, 21/- doz.

Command Receivers BC454B. 3-6 Mc/s. Brand new in maker's cartons with 6 valves, 45/- each. Few only used, good condition, 1.5-3 Mc/s, 55/- each.

RF24 Units, 20-30 Mc/s. New with 3 SP61, 12/6 each, post paid.

Resistance Unit Type 231 with 12 heavy duty (10" long) 80 ohm carbon non-inductive resistors. Just right for the antenna match. 32/6 each, carr. paid.

M.C. Meters. 3 1/2" rd. fl. mtd. (2 1/2" dial), 0-1mA, 26/-; ditto but with very lightly damped movement and scaled 0-10, 18/6 each; 0-30mA, 0-250mA, 0-500mA, 0-2A, 13/6 each; 0-150V a.c. (1mA Basic with Rect.), 28/6; 2 1/2" rd. fl. (2" dial), 0-500µA, 17/6 each. All post paid.

Midget Mains Transformers (same size as std. spkr. o/p). Input 230/250V, o/p 220V 20mA, 6.3V 0.6A. Ditto but 175V 25mA, both types 11/9 each, post paid.

Whip Aerials, 4 section screw-in, 12' 6" long (part of BC610 whip), 15/6 each.
"PANL" Crackle Paint, 3/6 tin, post paid.

Jason FM Feeder Unit Kits (Local). All components, chassis, dial, instruction book, etc. £5.5.0, or with 4 valves, £6.12.6. Fringe version, £6, or with 5 valves, £7.15.0

Post 6d.

Free over £1 except where stated

JOHN ANGLIN

385 CLEETHORPE ROAD GRIMSBY Lincs
Telephone 56315

continued on page 143

SMALL ADVERTISEMENTS

continued from page 141

PRIVATE—continued

PROJECTION T.V. Mullard Optical Unit, complete with tube, scan and focus coils, all components for 25kV E.H.T. including E.H.T. can, and all parts peculiar to projection T.V. £7.10.0 o.n.o. A. Lane, 152 Marsh Lane, Stanmore, Middx. Telephone GRI 684 after 7 p.m., Lan 3762 Ext. 2, 9 a.m. to 5.30 p.m.

TRADE

FOR EARLY DISPOSAL Six brand new B.T.H. 12-in speakers, frequency response 30–12,000 c/s; 10 watts rating; flux 134,000 lines, 15 ohm speaker coil. Nett weight 14lb. Treated for tropical use, £5.7.6 each including U.K. post and packing. Also one sound tape recorder, Collaro deck, long-play tape, microphone and extension leads. Cost £58 new in May 1957. Best offer around £45 secures. Carriage paid U.K. Box. No. E144.

BEGINNER'S MORSE RECORDS (L.P. 33 $\frac{1}{2}$). Complete course with booklet designed to pass G.P.O. test at 12 w.p.m. easily. Only 45/- Send P.O. now, course by return. 45 Green Lane, Purley, Surrey. Telephone UPL 2896.

TRANSISTOR P.P. Amplifier, 4 transistors, complete kit 75/-. Transistor 18 Superhet Portable, latest, circuit, etc., 1/6. Lists. Osmbet Ltd., 14 Hillside Road, Tottenham, London, N.15.

DO YOU EVER REPAIR RADIOS AND T.V.s Then you require a service sheet. We have 1,000's and 1,000's of the actual ones used by the trade in stock for sale or hire. S.A.E. with enquiry. You also require our new, larger catalogue packed with exact replacement and servicing components. Price 1/-. M. Foy, 6 Wykebeck Gardens, Leeds 9.

PANL, recognised for many years as the unique one-coat black crackle finish. Brush applied, no baking. Available by post in $\frac{1}{8}$ th pint cans at 3/6 from G. A. Miller, 255 Nether Street, London, N.3.

ILLUSTRATED CATALOGUE No. 13 containing over 450 items of Government Surplus and Model Radio Control Equipment, 2/2. Refunded on purchase of goods, —2/6 overseas seamount—Arthur Sallis Radio Control Ltd., Department R.C. 93 North Road, Brighton. Telephone 25806.

LEARN as you do it—we provide practical equipment combined with instructions in Radio, Television, Electricity, Mechanics, Chemistry, Photography, etc. Write for full details to E.M.I. Institutes, Dept. RC47, London, W.4.

INCORPORATED Practical Radio Engineers' home study courses of radio and t.v. engineering are recognised by the trade as outstanding and authoritative. Moderate fee to a limited number of students only. Syllabus of Instructional Text is free. *The Practical Radio Engineer* journal, sample copy 2/-. 6,000 Alignment Peaks for Superhets, 5/-. Membership and Entry Conditions booklet, 1/-. all post free from the Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

continued on page 144

CABINETS & HI-FI EQUIPMENT

We can supply any Cabinet to your own specification


Veneered with finest selected walnut, beautifully polished to a medium shade; this attractive cabinet has generous storage space, with motor board sliding out smoothly on metal rollers. We can also supply and fit this or any cabinet with the latest Hi-Fi amplifiers, tuners, transcription units, record changers, speakers, etc.

Send for comprehensive illustrated catalogue of cabinets, auto-changers, speakers, etc., all available on easy H.P. terms.

LEWIS RADIO COMPANY

120 (RC10) Green Lanes · Palmers Green · London N13

Telephone BOWes Park 1155/6

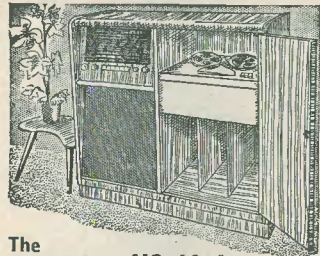

The 'Serenade' £12.19.6

SEND **Now** FOR YOUR COPY OF

ELECTRONICS

MADE EASY

For those engaged in radio or electronics 192 pages. 500 photographs and drawings

POST 6/6 PAID

POPULAR MECHANICS

109 JERMYN STREET LONDON SW1

QUALITY COMPONENTS

in stock for the

MULLARD 3 VALVE AMPLIFIER

and

510 AMPLIFIERS, FM TUNER circuits 3/6
912 AMPLIFIER, FM TUNER " 4/-
RADIO CONSTRUCTOR FM " 2/-
DENCO FM TUNER " 1/6
G.E.C. "FM PLUS" TUNER " 2/6

Price Lists available on request

J. T. FILMER

82 DARTFORD ROAD DARTFORD KENT

Telephone Dartford 4057

★ VALVES NEW TESTED AND GUARANTEED

1R5	8/6	6Q7GT	9/6	DK91	8/6	EF92	4/9
1S5	7/6	6SA7	8/-	DK92	9/-	EK32	8/6
1T4	7/6	6SL7GT	8/-	DK96	9/-	EL32	7/6
354	7/6	6SN7GT	8/6	DL92	7/6	EL41	10/-
3V4	8/6	6SS7	6/6	DL94	8/6	EL84	10/6
5U4G	8/6	6V6G	7/6	DL96	9/-	EL91	7/6
5Y4G	7/-	6V6GT	7/6	EA50	1/6	EY51	11/6
5Z4G	9/6	6X4	7/6	EB91	6/6	EZ35	8/-
6AG5	6/6	6X5GT	7/6	EBC41	9/6	EZ40	8/-
6AM6	6/6	12AT7	9/-	EBC33	8/6	KT33C	7/6
6AL5	8/6	12AU7	9/-	EBF80	10/-	KT66	11/6
6AT6	8/-	12AX7	9/-	ECC80	10/6	PCF82	11/-
6B8	7/6	12K8GT	10/6	ECC84	11/6	PL81	10/6
6B8G	7/6	12K7GT	8/6	ECC82	11/-	PL82	10/6
6BA6	8/6	12Q7GT	8/6	ECH81	10/6	PY81	10/6
6BE6	7/6	35Z4GT	8/6	ECH42	10/-	PCC84	11/6
6BR7	10/6	35L6GT	9/6	ECL80	10/6	U76	8/6
6BW6	8/6	807	6/9	EF36	7/6	UBC41	10/-
6G6G	4/9	5763	10/6	EF37A	14/6	UCH42	10/-
6J5G	5/6	DAF91	7/6	EF39	5/6	UF41	10/-
6J5GT	6/6	DAF96	9/-	EF41	10/-	UL41	10/-
6K7G	5/6	DF91	7/6	EF80	9/6	UY41	8/-
6K8G	9/6	DF96	9/-	EF85	10/6	W76	8/6
6L6G	9/6	DH76	8/6	EF91	8/6	X65	10/6

Matched Pairs. EL84, 23/-; 6V6G & GT, 17/-; 6BW6, 18/-; KT33C, 19/6; KT66, 27/6; 807, 14/6 per pair
P.P. Op. Transformers. Mr 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6
Volume Controls. All values, long spindle. L/S 3/-, SP 4/-, DP 4/9, ext. spkr. control, 3/-
W.W. Pots. Pre-set 3/-; 3W long spindle 5/6, SP 6/6
P.M. Speakers. 3 ohm. 5" 16/6, 6 $\frac{1}{2}$ " 17/6, 8" 21/-, 10" 25/-, 12" 30/-

Band III Converter Kits for all I.T.A. Transmitters. Complete kit of parts, including ready-wound coils, two EF80 valves, drilled chassis and wiring diagram. For a.c. mains 200-250V. £3 10s. 0d., p. and p. 1/6
As above less power pack components. Power required, 200V 20mA, 6.3V 0.6A. £2 5s. 0d., p. and p. 1/-
Teletron Band III Coil Set. Mk I 15/-; Mk II 17/6; Osmor Coil Set 17/6
Aerials. Band I from 13/6; Band II 17/7; Band III 16/6


Spare parts for Philips Radio and TV Receivers and most other makes supplied

P. and P. 6d. Over £1 post paid except where stated

R. COOPER G8BX

32 SOUTH END CROYDON SURREY CROYDON 186

THE TELETRON 'COMPANION'

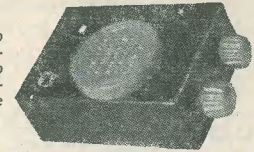

Our close proximity to main Teletron Distributors enables us to offer unrivalled service for all these items.

Case with chassis (drilled and punched) ...	8/6
Ferrite inductor FX25 (L.1) ...	15/-
Coil type 24 (L.2)* ...	3/6
R.F. Transistor (yellow/red) ...	21/-
Audio Transistor (yellow/green) each ...	10/-
Set of Resistors ...	1/7
Volume control with switch ...	7/-
Capacitor set ...	4/10
Ardente transformers D240 & D239, each ...	10/-
Wavechange switch ...	1/3
Balanced armature earpiece ...	5/3
Set of three batteries ...	1/1
Tag strip, wire, nuts, bolts ...	1/3
Transistor holders, each ...	1/-

*Not needed with above Transistors
Instruction leaflet including tuning scale 6d.
(included with FX25)

TRANSISTORS

Red Spot (equiv. OC71) 10/-, R.F. Blue Spot (1.6 Mc/s) 15/-, Superior type (packeted with data) limited stocks:— Audio 11/- each, R.F. (2.8 Mc/s) 21/- each

SUB-MINIATURE CAPACITORS BY T.C.C.

32 μ F 1 $\frac{1}{2}$ V, 6 μ F 3V, 10 μ F 3V, 4 μ F 6V, 8 μ F 6V, 2 μ F 12V, 4 μ F 12V, all at 4/9 each. Also 100 μ F 6V at 2/9, each. 8 μ F 15V (limited supplies), 2/9

TRANSISTOR HOLDERS. Enable transistors to be plugged in and out like valves, without danger from heat of soldering iron. For any type of transistor. Recommended by R.C. (June). 1/- each, 6 for 5/6, 12 for 10/9

SUB-MINIATURE V/controls with switch, 5k Ω semi-log as used in "Minimax" 9/6 each

NEON INDICATORS

Complete with built-in resistor and 9" leads. Single hole fixing—depth behind panel only 1". Very smart appearance, chrome bezel and $\frac{1}{8}$ " dome. Red, amber or opal, 3/10 each. Green 4/7 each

TYGAN—the non-creasing, fadeless, washable speaker fabric in 6 distinctive patterns. Approx. 3/9 square foot. Send 1/- for samples and quotation for size you require (credited on return). See page 840 of July issue.

LITESOLD SOLDERING IRON. The smallest made, 6" long, weighs $\frac{1}{2}$ oz. With $\frac{1}{8}$ " permanent non-wearing bit. Ideal for transistor assemblies, 21/6 (state voltage). Available for mains or 6 volt.

MULTICORE SOLDER, 4d. per yard (50/50). * 20ft reels (60/40 high tin), 2/6

*This is the new "SAVBIT" solder, which prolongs the life of the bit up to ten times. Also available in 1lb reels at 14/9.

PRECISION RESISTORS $\frac{1}{2}$ watt 1% high stability, 2/10 each

ALWAYS IN STOCK

All parts for "Minimax" and "Eavesdropper," Jason Tuners, Mullard Amplifiers, etc.

Send for our Catalogue price 5d.

Please add postage to all prices shown above

R. FAGELSTON (MAIL ORDER)

46 Hardwicke Road London N13

NEW EDITION

"Basic Mathematics for Radio and Electronics"

by F. M. Colebrook, B.Sc., D.I.C., A.C.G.I., revised and enlarged by J. W. Head, M.A. (Cantab), 18/4 by post—available from MODERN BOOK CO., 19 Praed Street, London, W.2. Immediate delivery.

GUARANTEED VALVES — Over 3,000 in Stock

EF92, EAC91, 6J6 6C4 4/6; 6K7, EC91, 5/6; 6AL5, 6SK7, R10, 3A4, 807, 6/-; 6AM6, EL91, 6X4, 6/6; 6BE6, 6CH6, 6F17, 6F33, 7/6; 12AT7, 12AX7, 12AU7, 6BA6, 6BW6, 8/-; 6BR7, 12E1, 85A2, 2D21, 10/-; EF86, 6L6M, 5B/225M, 5B/251M, 11/6

A. A. W. SKILLMAN
79A FRANCHISE STREET WEYMOUTH

BRASS, COPPER, DURAL ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE
3,000 STANDARD STOCK SIZES

No Quantity too Small List on application

H. ROLLET & CO. LTD

6 Chesham Place SW1 Telephone SLOane 3463

Also at Liverpool Birmingham Manchester Leeds

H.A.C. THE ORIGINAL SUPPLIERS OF SHORT-WAVE KITS

One-valve Kit, price 25/-. Two-valve Kit, price 50/-. Improved designs with Denco coils. All kits complete with all components, accessories and full instructions. Before ordering, call and inspect a demonstration receiver, or send stamped envelope for catalogue.

H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)
11 OLD BOND STREET LONDON W1

SMALL ADVERTISEMENTS

continued from page 143

TRADE—continued

JOIN THE INTERNATIONAL S.W. LEAGUE
Free Services to members including Q.S.L. Bureau Translation, Technical and Identification Depts.—both Broadcast and Fixed Stations, DX Certificates contests and activities for the SWL and Transmitting members. Monthly magazine, "MONITOR," containing articles of general interest to Broadcast and Amateur SWL's. Transmitter page and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership, including monthly magazine, etc., 15/- per annum.—Secretary, ISWL, 86 Barrenger Road, London, N.10.

COILS, COILS, COILS. We can supply coils for all frequencies, r.f. chokes, etc. Send s.a.c. for circuits and data.—The Teletron Co., 266 Nightingale Road, London, N.9.

MORSE CODE TRAINING. Special course for Beginners. Full details from (Dept. RC), Candler System Company, 52, Abingdon Road, London, W.8.

FREE. Brochure giving details in Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds, R.T.E.B., with other Professional examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to E.M.I. Institutes, Dept. RC28, London, W.4.



Radio Control Mechanisms

by

RAYMOND F. STOCK

A new publication—and the first devoted entirely to the subject of radio control linkage mechanisms. Complementary to *Radio Control for Model Ships, Boats and Aircraft* and to other books on radio control.

64 PAGES ART BOARD COVER
70 ILLUSTRATIONS

First Edition .. 4/6 plus 4d. postage

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

SCOTTISH INSURANCE CORPORATION LTD



62-63 Cheapside London EC2

TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing. A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) and (ii) costs only 2/6 a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's Office at the above address, a proposal will be submitted for completion.

NAME (Block Letters).....
If Lady, state Mrs. or Miss
ADDRESS (Block Letters).....

/JB

YOU CAN RELY ON US

We specialise ONLY in radio and electronic components, a comprehensive stock of which are held by us, to supply Government, educational and commercial laboratories. Can we be of some help to you, the experimenter and constructor? ?

QUALITY AMPLIFIER KITS

IN STOCK

ALL SPECIFIED PARTS FOR

MULLARD 3 WATT QUALITY AMPLIFIER
INCLUDING WYNALL TRANSFORMERS
MULLARD 510, F.M. UNIT, PRE-AMP
20 WATT AMPLIFIER

OSRAM 912, PASSIVE UNIT, PRE-AMP, F.M. UNIT

TRANSFORMERS FROM STOCK—

WYNALL, PARTRIDGE, GILSON, W.B., ELLISON

Detailed Price List Available on Request New Catalogue No. 14 on Request

Next to South Ealing Tube Station 65 Bus

82 SOUTH EALING ROAD
LONDON W5 Telephone EAL 5737

RADIO SERVICING CO