

PUBLISHED IN CONJUNCTION WITH

THE

RADIO CONSTRUCTOR

★ *Radio Reprint Series* ★

		Price	Postage
RR3	The "Argonaut" AM/FM—MW/VHF Tuner Receiver—A Jason design	2/-	4d.
RR4	The "Eavesdropper." 3-Transistor local station pocket receiver	1/6	2d.
RR5	The "Mercury" Switched-Tuned FM Tuner—A Jason design	2/-	2d.
RR6	The Cooper-Smith B.P.I. High Fidelity 10-12 watt Amplifier and Control Unit	2/6	4d.
RR7	A Versatile 2-Valve Audio Pre-Amplifier—A Mullard design	1/-	2d.
RR8	High-Gain Band-3 Pre-Amplifier	1/-	2d.
RR9	The "Jupiter" Stereophonic Amplifier and Pre-Amplifier	2/6	4d.
RR10	The Cooper-Smith "Prodigy" 6-watt High Fidelity Amplifier	2/6	4d.

Send stamped addressed envelope for

BROCHURE

giving details of ALL PUBLICATIONS

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141/2

Published in Great Britain by the Proprietors and Publishers

Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd 125 High Holborn London WC1 England also at Clacton-on-Sea

Obtainable abroad through the following Collets Subscription Service Continental Publishers & Distributors Ltd William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency Holland "Radio Electronica"

Registered for transmission by Magazine Post to Canada (including Newfoundland)

TRANSISTORISED LIGHT-OPERATED SWITCH

VOLUME 12
NUMBER 8
MARCH
1959

The RADIO Constructor



RADIO · TELEVISION · AUDIO · ELECTRONICS

The **MAYKIT**
TRANSISTORISED CAR RADIO



Described by
Richard Myers

Included in this issue
CORE-TUNED TRANSPORTABLE
THE AMPLIFONE
COMPREHENSIVE MIXER-FADER
BATTERY POWER UNIT
"JINGLEBELLS"—AMATEUR RADIO TELETYPE, Pt. 2
CRYSTAL STABILISATION FOR MODEL CONTROL

DATA
Publications 1/9

THE MODERN BOOK CO

Television Engineers' Pocket Book.
By J. P. Hawker. 12s. 6d. Postage 8d.

TV Fault Finding. A Data Publication.
5s. Postage 5d.

**How to Get the Best Out of Your
Tape Recorder.** By P. J. Guy
8s. 6d. Postage 6d.

A Beginner's Guide to Radio. By
F. J. Camm. 7s. 6d. Postage 8d.

Audio Design Handbook. By H. A.
Hartley. 23s. Postage 1s.

A Beginner's Guide to Television.
By F. J. Camm. 7s. 6d. Postage 8d.

Radio Valve Data. Compiled by
"W.W." 6th Ed. 5s. Postage 9d.

**Radio Control for Model Ships,
Boats and Aircraft.** By F. C. Judd.
Data Publication. 8s. 6d. Postage 7d.

Foundations of Wireless. By M. G.
Scroggie. 15s. Postage 1s. 3d.

**Solution of Problems in Telecom-
munications.** By C. S. Henson.
25s. Postage 1s.

Television Servicing Handbook. By
G. J. King. 30s. Postage 1s. 6d.

Oscilloscope Techniques. By A. Hass.
23s. Postage 1s.

**An Electronic Organ for the Home
Constructor.** By A. Douglas. 15s.
Postage 1s.

Radio Engineer's Pocket Book. By
F. J. Camm. 6s. Postage 6d.

We have the Finest Selection of British and American Radio Books in the Country
Complete catalogue 6d.

19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADDington 4185

**INTEREST
is at 4%
per annum**

(There is no deduction for
income tax, as this is paid by
the Society)



ESTABLISHED 1865

Savings in this old estab-
lished Building Society
combine sound invest-
ment with an attractive
return

The Duchess of Kent Permanent Building Society

Shares are in units of £25 each (maximum investment £5,000) . . . BUT, for the smaller saver, Subscription Share accounts may be opened with any sum from 1/- upwards. Interest payable half-yearly on Fully Paid Shares—credited annually on Subscription Shares.

Write for free brochure and further details or complete the coupon, and send to:—

The Secretary Mr. A. Neville Gillman, F.C.A.

Duchess of Kent Permanent Building Society 103 Cannon Street London EC4


Name.....
(If Lady, please state Mrs. or Miss)

Address.....R.C.
(Please use Block Capitals for both name and address)

FERGUSON choose the

Model **8** AvoMETER

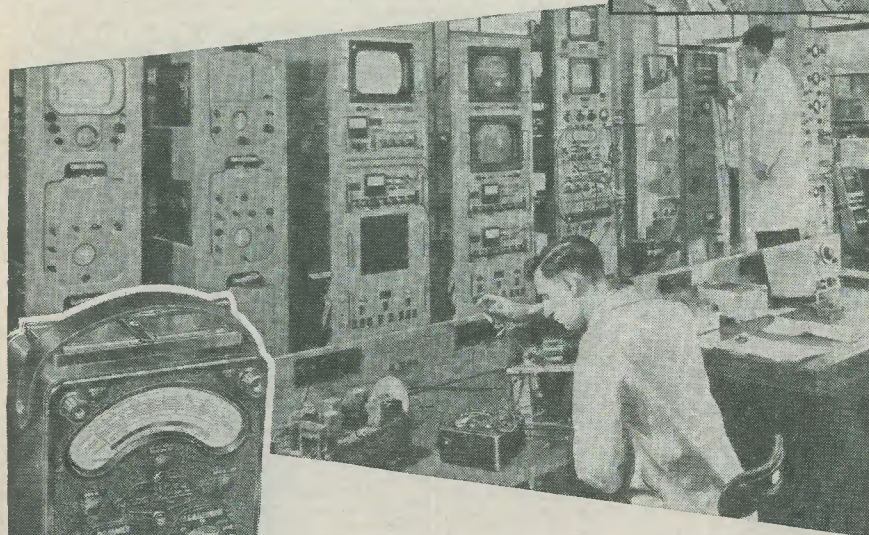for their Television & Electronic Laboratory



Photograph by courtesy of
Thorn Electrical Industries Ltd.

VOLTAGE AC/DC: 25mV to 2,500 volts.
CURRENT AC/DC: 0.5µA to 10 amps.

SENSITIVITY:
20,000 ohms per volt on all D.C. ranges.
1,000 ohms per volt on A.C. ranges
from 100 volts upwards.

RESISTANCE:
0 to 20 megohms (using internal batteries).
0 to 200 megohms (using external D.C. supply).
DECIBELS: —15dB to +15dB.

Various accessories are available
for extending the above ranges.


Write for fully descriptive Brochure

AVO LTD

AVOCET HOUSE • 92-96 VAUXHALL BRIDGE ROAD • LONDON • S.W.1 • Telephone: VICTORIA 3404 (12 lines)

FERGUSON are typical of the many leading manufacturers of electronic, radio and television equipment who rely on AVO instruments. The Model 8 AvoMeter shown in use is a 30-range self-contained AC/DC moving coil instrument, produced primarily for the electronic, radio and television engineer. The upper photograph shows a mounted pivot under examination. This is only one of many operations carried out in a special air-conditioned dust-free zone in the AVO factory to ensure the highest possible standards of accuracy and reliability.

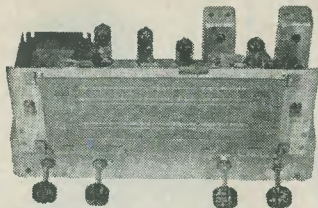Size: 8½ × 7¼ × 4½ inches.
Weight: 6½ lbs. (approx.) including leads.
List Price: £23 : 10s.



1959 RADIOGRAM CHASSIS

THREE WAVEBANDS S.W. 16 m.-50 m. M.W. 200 m.-550 m. L.W. 800 m.-2,000 m.
FIVE VALVES LATEST MULLARD ECH42, EF41, EBC41, EL41, EZ40
12-month Guarantee. A.C. 200/250V, 4-way switch. Short-Medium-Long-Gram. A.V.C. and negative feedback. 4.2 watts. Chassis 13 1/2" x 5 1/2" x 2 1/4". Glass dial 12 1/2" x 5 1/2" horizontal or vertical 10" x 4 1/2". 2 pilot lamps. Four knobs, walnut or ivory, aligned and calibrated. Chassis isolated from mains. Immediate delivery.

BRAND NEW £9.10.0 Carr. 4/6

TERMS: Deposit £5.5.0 and 5 monthly payments of £1 MATCHED SPEAKERS: 8" 17/6. 10" 25/-. 12" 30/-

★ GARRARD 4-SPEED SINGLE RECORD PLAYER 4SP ★
£8 AUDIO PERFECTION POST FREE

De Luxe Cabinet with amplifier and 6 1/2" speaker £6.15.0 or complete kit £14.10.0

BUILD THIS REPRODUCER BARGAIN SPECIAL SINGLE PLAYER KIT

COLLARO 4-speed Gram-Pick-up Unit Handsome portable case 17 1/2" x 13 1/2" x 7" with room to play 12" records £2. 5.0
Ready built 3 watt amplifier with two valves and 7" elip. speaker, printed circuit £3.12.6
or £9.15.0 complete kit post free

I.F. TRANSFORMERS 7/6 pair

465 kc/s slug tuning miniature can 2 1/2" x 1" x 1". High Q and good band width. By Pye Radio. Data sheet supplied.
Wearite M800 Midget I.F.S. 465 kc/s 12/6 pair
Wearite 550 Standard I.F.S. 465 kc/s 12/6 pair

New boxed VALVES 90-day Guarantee

1R5	8/6	6K8G	8/6	EASO	1/6	EZ80	9/6
1S5	8/6	6L6G	10/6	EABC8010	6/6	E1148	1/6
1T4	8/6	6N7M	7/6	EB91	6/6	HABC80	12/6
2X2	2/6	6Q7G	10/6	EBC33	8/6	HVR2A	7/6
354	8/6	6SA7	10/6	EBC41	10/6	MU14	10/6
3V4	8/6	6S17M	10/6	EBF80	10/6	P61	6/6
5U4	8/6	6SN7	8/6	ECC84	12/6	PCC84	12/6
5Y3	8/6	6V6G	7/6	ECH80	11/6	PCF80	11/6
5Z4	10/6	6X4	7/6	ECH42	10/6	PCF82	11/6
6AM6	8/6	6X5	7/6	ECL80	14/-	PLB2	11/6
6B8	5/6	7S7	10/6	ECL82	12/6	PEN25	6/6
6BE6	7/6	12A7	10/6	EF39	7/9	PL82	10/6
6BH6	10/6	12AU7	9/6	EF41	10/6	PY80	10/6
6BW6	10/6	12AX7	9/6	EF50	5/6	PY81	10/6
6D6	7/6	12BE6	9/6	EF50	8/6	PY82	10/6
6F6	7/6	12K7	8/6	Sylv.		SP61	5/6
6H6	3/6	12Q7	8/6	EF80	10/6	UBC41	10/6
6I5	6/6	35L6	9/6	EF92	5/6	UCH42	10/6
6I6	7/6	35Z4	9/6	EL32	5/6	UF41	10/6
617G	8/6	80	10/6	EL84	10/6	UL41	10/6
6K6GT	6/6	807	6/6	EY51	12/6	UY41	10/6
6K7G	5/6	954	1/6	EZ40	10/6	U22	10/6

C.R.T. ISOLATION TRANSFORMERS

For Cathode Ray Tubes having heater cathode short circuit and for C.R. Tubes with falling emission. Type A. Low leakage windings. Optional 25% and 50% boost on secondary: 2V, or 4V, or 6.3V, or 10.3V, or 13.3V, with mains primaries, 12/6
Our Latest Superior Product. Type A2. High quality low capacity 10-15pF. Optional boost 25%, 50%, 75%, 16/6 each
Type B. Mains input. Low capacity. Multi output 2, 4, 6.3, 7.3, 10 and 13V. Boost 25% and 50%. This transformer is suitable for all TV tubes. 21/- each.

RESISTORS. Preferred values. 20% 10 ohms to 10 meg, 1/4W 4d., 1/2W 4d., 1W 6d., 1 1/2W 8d.

HIGH STABILITY. 1/2W 1%, 2/- All preferred values 100Ω-10MΩ. Ditto 5% 100Ω-5MΩ 9d. each

WIRE-WOUND RESISTORS } 1/3
5 watt } 1/6
10 watt } 2/-
15 watt }

15,000 ohms-50,000 ohms, 5W, 1/9; 10W, 2/3.

WIRE-WOUND POTS 3W Lab. Colvern, etc. Pre-set min. TV type. Standard size Pots, 2 1/2" Knurled slotted knob. Spindle, high grade. All values 25 ohms to 25k, 3/- each. 30k, 50k, 4/- 6/6; 100k, 7/6
Ditto Carbon Track 30k W/W EXT. SPEAKER CONTROL 10Ω, 3/-

MAINS TRANSFORMERS

STANDARD. 250-0-250, 80mA, 6.3V tapped 4V 4A. Rectifier 6.3V 1A tapped 5V 2A and 4V 2A 22/6
Ditto 350-0-350 22/6
MINIATURE. 200V 20mA, 6.3V 1A 10/6
MIDGET. 22V 45mA, 6.3V 2A 15/6
SMALL. 220-0-220, 50mA, 6.3V 3A 17/6
STANDARD. 250-0-250, 65mA, 6.3V 3.5A 17/6
HEATER TRANS. 6.3V 1 1/2A 7/6
Ditto, tapped sec. 2, 4, 6.3V 1 1/2A 8/6
Ditto, sec. 6.3V 3A 10/6
Mullard "510" 300-0-300, 120mA, 6.3V 4A c.t., 6.3V 2A tapped 5V 38/6

O/P TRANSFORMERS. Heavy duty 50mA, 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Small pentode, 4/6. Hygrade push-pull 7 watts, 15/6. Heavy duty 10/20W 6k or 8k ct., 30/-

L.F. CHOKES 15/10H 60/65mA, 5/-; 10H, 85mA, 10/6; 10H 150mA, 12/6; 5H, 250mA, 16/6.

CRYSTAL MIKE INSERT by Acos 6/6

Precision engineered. Size only 3/8" x 1/8" ACOS 33-2 CRYSTAL DESK MIKE, 35/-

ALADDIN FORMERS and cores. 1/2" 8d., 3/8" 10d. 0.3" FORMERS 5937/8 and cans TV1/2. 3/8" sq. x 2 3/8" and 3/8" sq. x 1 1/8", 2/- complete with cores.

SLOW MOTION DRIVES. Epicyclic ratio 6-1, 2/3. TYANA. Midget Soldering Iron. 40W, 16/9.

FAMOUS REMPOY INSTRUMENT IRON, 25W, 17/6.

MAINS DROPPERS. 3" x 1 1/2". Three adj. sliders, 0.3A, 750 ohms, 4/3; 0.2A 1,000 ohms, 4/3

LINE ORD. 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 6d. per foot; 3-way, 7d. per foot

MIKE TRANSF. 50-1, 3/9; 100-1, topped, 10/6.

LOUDSPEAKERS. P.M. 3 ohm. 2 1/2" and 5", 17/6; 6" x 4" Rola, 18/-; 4" Hi-Fi Tweeter, 25/-; 8" Plessey, 19/6; 6 1/2" Goodmans, 18/6; 10" R.A., 30/-; 12" Plessey, 30/-; 10" x 6" R.A., 27/6; 12" Baker 15W 3 ohm or 15 ohm models, 105/-; Stentorian HF1012 10" 99/6.

CRYSTAL DIODES. G.E.C., 2/-; GEX34, 4/-.

40 CIRCUITS FOR GERMANIUM DIODES, 3/-

TUNING AND REACTION CONDENSERS 100pF, 300pF, 500pF, 3/6 each, solid dielectric.

H.R. HEADPHONES 4,000 ohms, brand new, 16/6 pr.

SWITCH CLEANER FLUID, squirt spout, 4/3 tin.

TWIN GANG CONDENSERS. 365pF, miniature. 1 1/2" x 1 1/2", 10/-; 0.0005 standard with trimmers, 9/-; less trimmers, 8/-; Midget 7/6; 50pF single, 2/6.

Aluminium Chassis. 18 s.w.g. Plain, undrilled, with 4 sides, riveted corners and lattice fixing holes, with 2 1/2" sides. 7" x 4", 4/6; 9" x 7", 5/9; 11" x 7" 6/9; 13" x 9", 8/6; 14" x 11", 10/6; 15" x 14", 12/6; 18" x 16" x 3", 16/6.

Volume Controls

Midget size. Long spindles. Guaranteed 1 year. All values 5,000 ohms to 2 Meg. No Switch D.P. Switch 3/- 4/9
Linear or Log Tracks

80Ω Coaxial Cable

Semi-air spaced Polythene insulated 1/2" dia. stranded core. Ideal Band III 9d. yd. Losses cut 50%
FRINGE QUALITY Air-spaced Coaxial 1/6 yd

Coaxial Plugs 1/- Double Socket 1/3
Sockets 1/- Outlet Boxes 4/6
Balanced Twin Feeder, per yd 6d., 80Ω or 300Ω
Twin Screened Balanced Feeder, 1/6 yd, 80 ohms
Trimmers. Ceramic 30, 50, 70pF, 9d.; 100pF, 150pF, 1/3; 250pF, 1/6; 600pF 750pF, 1/9. Phillips, 1/- each
BLACK CRACKLE PAINT. Air drying, 3/- tin
P.V.C. CONN. WIRE, 8 colours, single or stranded, 2d. yd. Sleeving 1, 2mm, 2d., 2, 3mm, 3d., 6mm, 5d. yd
NEON MAINS TESTER SCREWDRIVERS, 5/3
SOLDER RADIOGRADE, 3 yds 9d., 1/6 2/6

THE HIGH GAIN BAND III ITV PRE-AMP Tunable Channels 8 to 13. Gain 17dB, Cascade Circuit. Complete kit with ECC84 valve, plans and instructions, 29/6 less power, or 49/6 with power pack. Plans only, 6d. Band I B.B.C. version available for channels 1 to 5, same prices.

Miniature Contact Cooled Rectifiers. 250V 50mA, 7/6; 250V 85mA, 9/6. Selenium Rect. 300V 85mA, 7/6. Coils. Wearite "P" type, 3/- each. Osamor Midget "Q" type, adj. dust core, from 4/- each. All ranges. Teltron A.H.F. L & Med. T.R.F. with reaction, 3/6. Ferrite Rod Aerials. M.W., 8/9; M. & L., 12/6. T.R.F. Coils A/H.F., 7/- pair, H.F. Chokes, 2/6. Speaker Fret. Gold cloth, 17" x 25", 5/-; 25" x 35", 10/-; Expanded metal, silver, 15 1/2" x 9 1/2", 2/- each; Tygan. 4' 6" wide, 10/- ft; 2' 3" wide, 5/- ft. Samples

SUPERHET COIL PACK 27/6

Miniature size high Q coils. Short, Med., Long, Gram. switching, with connection diagram. 465 kc/s i.f.

Condensers. New stock, 0.001μF 7kV T.C.C., 5/6; ditto 20kV, 9/6; 100pF to 500pF Micas, 6d.; Tubular 500V 0.001 to 0.001μF, 9d.; 0.05, 0.1, 1/-; 0.25, 1/6; 0.1/350V, 9d.; 0.5, 1/9; 0.01/2,000V, 1/9; 0.1/2,000V, 3/6. Ceramic Condensers. 500V 0.3pF to 0.01μF, 9d. Silver Mica. 10% 5pF to 500pF, 1/-; 600pF to 3,000pF, 1/3; close tolerance (plus or minus 1pF), 1.5pF to 47pF, 1/6; ditto 1% 50pF to 815pF, 1/9; 1,000pF to 5,000pF, 2/-

NEW ELECTROLYTICS FAMOUS MAKES

TUBULAR	TUBULAR	CAN TYPES	
1/350V	2/-	64/350V 5/6	8/500V 3/-
2/450V	2/3	100/25V 2/-	16/500V 4/-
4/450V	2/3	250/25V 2/6	32/350V 4/-
8/450V	2/3	500/12V 3/-	100/270V 5/6
8/500V	2/9	8+8/450V 4/6	2,500/3V 4/-
16/450V	3/6	8+8/500V 5/6	6,000/6V 5/-
16/500V	4/-	8+16/450V 5/-	32+32/350V 4/6
32/450V	5/6	8+16/500V 5/6	50+50/350V 7/-
25/25V	1/9	16+16/450V 5/6	64+120/275V 7/6
50/25V	2/-	32+32/350V 4/6	64+120/350V 11/6
50/50V	2/-	32+32/500V 7/6	100+300/350V 12/6

Full Wave Bridge Selenium Rectifiers. 2, 6 or 12V 1/4A, 8/9; 2A, 11/3; 4A, 17/6 Free charger circuit
Charger Transformers. Tapped input 200/250V for charging at 2, 6 or 12V 1 1/2A, 15/6; 2A, 17/6; 4A, 22/6.
LONG PLAY "GEVAERT GEASONOR" 50% extra at standard prices. 1,700ft 7" reel, 35/-; 850ft 5" reel, 21/-.
SUPERIOR 1,200ft plastic tape, 21/-, 7" plastic reel.
EMITAPE 7" Long Play 1,800ft, 45/-.
INSTANT bulk tape eraser, 200/250V a.c., 27/6.



BRAND NEW AND BOXED Model UA8
OUR PRICE £6.19.6
STEREO MODEL UA12 £11.17.6

★ COLLARO ★ HIGH-FIDELITY AUTOCHANGER Latest Model Studio "O" pick-up 4 SPEEDS—10 RECORDS
BRAND NEW IN MAKER'S BOXES
OUR PRICE £7.19.6 post free

GARRARD 4-SPEED RECORD CHANGERS RC121/D MK II MODELS ★ With Plug-in Normal Head
AUDIO PERFECTION WIRED FOR STEREO
OUR PRICE £10.15.0 each Post Free
Plug in STEREO HEAD £2 extra

AUTOCHANGER ACCESSORIES
Suitable player cabinets (uncut boards) 49/6
Amplifier player cabinets with cut boards 63/-
2 valve amplifier and 6 1/2" speaker for above 72/6
3 valve amplifier and 6 1/2" speaker for above 95/-
Wired and tested ready for use

Wavechange Switches. 2 p 2-way, 3 p 2-way, short spindle, 2/6; 5 p 4-way 2 wafer, long spindle, 6/6; 2 p 6-way, 4 p 2-way, 4 p 3-way, long spindle, 3/6; 3 p 4-way, 1 p 12-way, long spindle, 3/6; wave change "MAKITS," 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer, 16/-; 4 wafer, 19/6; 5 wafer, 23/-; 6 wafer, 26/6
Toggle Switches, s.p. 2/-; d.p., 3/6, d.p.d.t., 4/-

JASON FM TUNER COIL SET, 26/-, H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/-.
Complete Jason FM Kit, with valves and Jason superior calibrated dial, £6.15.0, post free.
Mullard 3-3. Quality amplifier ready built, with power socket for tuner, £7.17.6.

Valveholders. Pax. int. oct., 4d. EF50, EA50, 6d. B12A, CRT 1/3. Eng. and Amer. 4, 5, 6 and 7 pin, 1/-
MOULDED Mazda and int. oct., 6d., B7G, B8A, B8G, B9A, 9d. B7G with can, 1/6. B9A with can, 2/6. Ceramic, EF50, B7G, B9A int. oct., 1/-; B7G with can, 1/9; B9A with can, 2/9.
TV Fault Finding, 5/- Quality Amplifiers, 4/6
Radio Valve Guide. Books 1, 2 or 3 5/- each
TRANSISTORS. Pye Goltop Audio V10/15A, 10/-; R.F. 3 Mc/s, V6/R2, 18/-; Sub-miniature Electrolytics 5μF 12V, 8μF 6V, 16μF 12V, 25μF 6V, 3/- each

Teltron Transistor Pocket Radios Designers Specified Kits
COMPANION PRINTED CIRCUIT THREE
Local station receiver kit, 4 1/2" x 3" x 1 1/2", £4.19.6
3 genuine Pye or Mullard transistors; plans 6d.

Transidyne Superhet Six 6" x 4" x 1 1/2" T.C.C. Printed Circuit, internal Ferrite aerial, Rola loudspeaker, push-pull output. All parts, cabinet 6 genuine Pye Goltop or Mullard transistors.
£11.19.6 Plans etc., 9d.
No surplus reject transistors supplied

48-HOUR POSTAL SERVICE

Our written guarantee with every purchase

RADIO COMPONENT SPECIALISTS

Buses 133 or 68 pass door. S.R. Stn. Selhurst

337 WHITEHORSE ROAD WEST CROYDON


Catalogue 6d.

Telephone THO 1665

P. & P. 1/-, over £2 post free. C.O.D. 1/6 (Export welcome. Send remittance and extra postage)

EXPRESS DESPATCH SERVICE

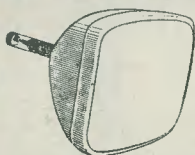Please phone to confirm Tube in stock. Send Telegraph Money Order. Tube despatched passenger train same day. This service only available with remittance by a Telegraph Money Order.



REGETTERED IMPROVED VACUUM TV TUBES


12 months guarantee

17" RECT. £7.10.0

14" RECT. £5.10.0

Our 12 months guarantee (six months full replacement, six months progressive) illustrates our whole-hearted confidence in the Tubes we offer. We sell many hundreds a week throughout the country and have done so for the past seven years. Many of them go to the Trade, i.e. to Insurance Companies, Renters and Retailers, who are thoroughly satisfied with our supplies. Remember, they also hold a 10 days money back guarantee. 9", 10", 14", 15" and 16" Round Tubes. Our special offer of these sizes £5. 12" TV Tubes £6. Three months guarantee on round tubes. Ins. carr. 15/6.

★ 17" TV CHASSIS, TUBE & SPEAKER

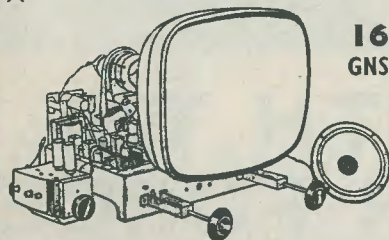

16 GNS.


17" Rectangular Tube on modified chassis. Supplied as single channel chassis covering B.B.C. channels 1-5, or, incorporating Turret Tuner, which can be added as an extra, at our special price to chassis purchasers of 50/-, giving choice of any 2 channels (B.B.C. and I.T.A.). Extra channels can be supplied at 7/6 each. Chassis size 12" x 14 1/2" x 11" less valves. Similar chassis are used by well-known companies because of their stability and reliability. With tube and speaker less valves, 16 guineas. Complete and working with valves and Turret Tuner, 24 guineas. 12 months guarantee on the tubes. 3 months guarantee on the valves and chassis. Ins. carr. (incl. tube) 25/-.

MIDGET RADIO 5 VALVE SUPERHET 49/6

5-valve superhet. Can be used on 110-250V mains. A.C. or A.C./D.C. Compact little set using 12K8, 12K7, 12Q7, 35L6 and 35Z4 GT valves. 5" speaker. Cabinet size 17" x 8" x 6". Carr. and ins. 3/6.

SUPER CHASSIS 99/6

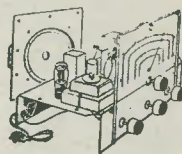5-valve superhet chassis including 8" p.m. speaker and valves. Four control knobs (tone, volume, tuning w/change switch). Four w/bands with position from gram p.u. and extension speaker. A.C. Ins. carr. 5/6.




Popular PLESSEY 12" TV CHASSIS 3/6

This is a real bargain for anyone wanting to make up their own TV at a very low cost. I.F.s 10.5-11.4 Mc/s. Simply adapted for a 12-channel Turret Tuner and can be modified to take a larger tube. AA chassis in one unit. Untested. Less valves, tube, speaker and scanning coils. (All can be supplied as extras.) Circuit diagram available at 3/6 or FREE with order. Carr. and ins. 10/6.

RECORD PLAYER CABINET 79/6

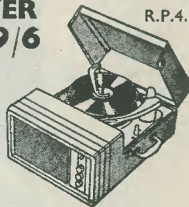Stylish cabinet by famous manufacturer. Cloth covered in contrasting colours (red and grey). Grilled front control panel. Size 15" x 19 1/2" x 8 1/2" deep. Beautifully made—a cabinet of which you can be really proud. Takes 4-speed B.B.C. Autochanger. 6" round or elliptical speaker. Room for any amplifier of your own choice. Carr. and ins. 4/6.



R.P.4.

Many other types of beautifully designed cabinets in stock from 49/6.

B.S.R. Monarch 4-Speed Autochanger £6.19.6

Incorporating auto and manual control complete with turnover crystal p.u. and sapphire stylus. P. P. and ins. 5/6.


COLLARO 4-SPEED AUTOCHANGER £7.19.6

12 Months Guarantee

AMPLIFIERS ★

PORTABLE AMPLIFIER Mk. D.4 6/6

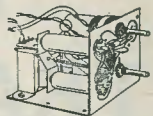Brand new. By famous manufacturer. Especially built for portable record players. Dimensions 4 1/2" x 3 1/2" x 4". A.C. only. 2 valves: EL84 as high gain output valve, EZ80 as rectifier. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.



PORTABLE AMPLIFIER Mk. D.1 59/6

Brand new. Latest design with printed circuit. Dimensions 7" x 2 1/2" x 4". A.C. only. Mains isolated. 2-3 watts output. Incorporating EL84 as high gain output valve. Volume and tone controls. Knobs 2/6 extra. P. & P. 33/6.

★ **STEREOPHONIC SOUND** ★

EXTENSION SPEAKERS 19/9

Polished oak cabinet of attractive appearance. Fitted with 8" p.m. speaker, W.B. or Goodmans, of the highest quality. Standard mounting to any receiver (2-5 ohm). Switch and flex included. Ins. carr. 3/6.



8" P.M. SPEAKERS 8/9

W/B o/p trans. fitted 10/- 6 1/2" p.m. speakers 12/6. 4" x 7" elliptical speakers 19/6. Post 2/9.

DUKE & CO.

(Dept. K3) 6221 ROMFORD ROAD MANOR PARK E12

TERMS AVAILABLE

Send for REE Catalogue

Open all day Sat. Closed Thurs. 1 p.m.

Telephone ILF 6001/3

◆ ◆ ◆ ◆ **REPANCO** ◆ ◆ ◆ ◆

HIGH GAIN COILS and QUALITY COMPONENTS for the constructor

TRANSISTOR COMPONENTS

- FERRITE SLAB AERIAL TYPE FS2. A new super-sensitive aerial, Long and Medium Wave, specially designed for transistor portable receivers. Complete with fixing brackets. Length 5 1/2" 13/6
- COMBINED OSCILLATOR AND 1st I.F. TRANSFORMER TYPE OT1 (315 kc/s), fully screened, 1 1/2" x 1 1/2" x 1 1/2" ... 11/6
- 2nd I.F. TRANSFORMER TYPE TT2 (315 kc/s), 1" x 3/8" dia. ... 5/-
- 3rd I.F. TRANSFORMER TYPE TT3 (315 kc/s), 1" x 3/8" dia. ... 5/-
- PUSH-PULL INTER-STAGE TRANSFORMER TYPE TT4. Ratio 1:1 ct. Stack 1 3/8" x 1 1/4" x 1 1/4" 8/6
- PUSH-PULL OUTPUT TRANSFORMER TYPE TT5. Ratio 15:1 ct. Stack 1 3/8" x 1 1/4" x 1 1/4" 8/-

MINIATURE RANGE—For pocket receivers

- FERRITE SLAB AERIAL TYPE FS3. Medium Wave only. With fixing grommets. Size 3" x 3/8" x 3/8" 7/6
- OSCILLATOR COIL TYPE XO8. Medium Wave only. Overall size 1/2" dia. x 1". Enclosed in Ferrite pots ... 5/-
- I.F. TRANSFORMER TYPE XT6. Suitable for 1st and 2nd I.F. 455 kc/s. Size 1/2" sq. x 1 1/4" ... 10/-
- I.F. TRANSFORMER TYPE XT7. Designed for 3rd I.F.T. or detector I.F.T. 455 kc/s. Size as XT6 ... 10/-
- PUSH-PULL INTERSTAGE TRANSFORMER TYPE TT9. Ratio 1:1 ct. Radiometal Core. Size 3/8" x 3/8" x 1 1/2" ... 12/6
- PUSH-PULL OUTPUT TRANSFORMER TYPE TT10. Ratio 8:1 ct. Matched to 3 ohm speaker. Size as TT9 ... 12/6

Practical and Theoretical circuits enclosed with each Repanco Transistor Component

COILS AND TRANSFORMERS FOR ALL-TRANSISTOR CAR RADIO

- Medium Wave Aerial Coil Type XMA16 ... 10/-
- Medium Wave H.F. Coil Type XMF17 ... 10/-
- Long Wave Aerial Coil Type XLA18 ... 6/9
- Long Wave H.F. Coil Type XLF19 ... 6/9
- Oscillator Coil Type XO15 ... 5/-
- Interstage Transformer Type TT1 ... 10/-
- Output Transformer (12 volt Radio) Type TT12 ... 12/6
- Output Transformer (6 volt Radio) Type TT13 ... 12/6

All this range boxed with circuit and practical diagram of all-Transistor Car Radio

REPANCO EASY-TO-BUILD RECEIVERS

- Constructors' Envelopes of easy wiring plans, instructions and detailed price lists of components
- THE HIWAYMAN ... Envelope 1/6 (post 3d.)
 - REPANCO ONE-VALVE ... Envelope 9d. (post 3d.)
 - REPANCO FM TUNER UNIT ... Envelope 1/6 (post 3d.)
 - REPANCO "THREE DEE" ... Envelope 9d. (post 3d.)
 - REPANCO "MAJOR-7" ... Envelope 1/6 (post 3d.)
 - REPANCO "MINI-7" ... Envelope 1/6 (post 3d.)


JUST RELEASED! A new comprehensive component catalogue for the radio enthusiast. With 56 pages and over 200 illustrations this offer should not be missed. Send 2/- postal order now. (Post free.)

RADIO EXPERIMENTAL PRODUCTS LIMITED

33 MUCH PARK STREET COVENTRY Telephone 62572

JSA.2 STEREOPHONIC AMPLIFIER

by G. G. Blundell

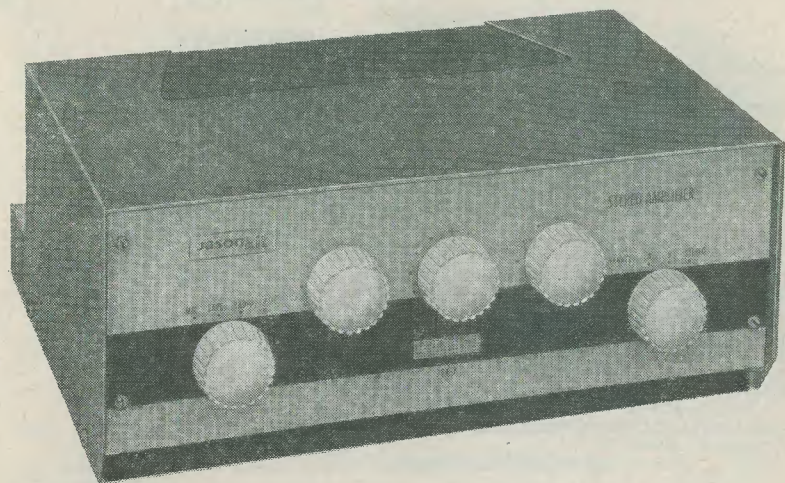

build it with an
authentic

Jason *kit*

This is one of a series of Jason amplifier and tuner designs offered in kit form. Cases and front panels are uniformly styled for shelf mounting. In the JSA.2 each section will deliver 3 watts between 70 and 10,000 c/s at a distortion rate of less than 1%. 18 dB of feedback is applied in each half, and the stereo balance operates on both channels giving a total difference each way of 5 dB. Building with a Jasonkit ensures your amplifier being exact to the designer's tested and proven specification.

THE JASON MOTOR & ELECTRONIC CO.,

AMPLIFIER

The Jasonkit for the JSA.2 is complete down to the last detail, including 5 valves. You save considerably by buying the kit complete as listed

	£ s. d.		£ s. d.
Chassis, base, cover, scale, screen plate	1 17 0	Nuts, screws, grommets, solder tags, spacers, p.v.c. wire, mains lead, etc.	6 6
1 mains transformer—MT248	2 2 0	CONDENSERS	
2 output transformers—OT3	1 4 0	1 32+32µF 350Vw with fixing clamp	7 6
1 mains selector plug and socket	3 0	1 50+50µF 275Vw with fixing plate	6 0
1 5-pin socket for spare power	6	2 25µF 25V working	4 0
1 2-pin socket for mains outlet	6	3 100µF 6V working	7 6
2 4-way audio input sockets with plugs and insulation plate	5 0	1 5µF 50V working	2 0
1 bulbholder	8	4 0.05µF 450V working	4 0
6 knobs	5 0	4 1,000pF 10%	2 8
1 set of tag strips	2 6	2 300pF 10%	1 4
2 B9 plugs	2 8	4 200pF	2 8
1 2-pole 4-way switch	4 0	RESISTORS	
1 2-pole 3-way switch	3 9	31 high stability 5% at 7½d. ea.	19 4½
1 2-pole 2-way switch	3 9	18 carbon ½W 20% at 4d. ea.	6 0
1 250Ω + 250Ω plus switch	16 0	4 carbon 1W 10% at 9d. ea.	3 0
2 1MΩ + 1MΩ potentiometer	1 8 0	VALVES	
1 300Ω preset potentiometer	2 0	2 EL84	1 12 0
2 low-loss B9 holders with can	2 0	2 ECF80	2 6 0
5 B9 holders	5 0	1 EZ81	1 1 0

TOTAL INCLUSIVE PRICE OF ALL PARTS BOUGHT TOGETHER **£13.19.0**

JASONKITS FOR TEST EQUIPMENT

Full details of the following Jasonkits gladly sent on request:

VALVE VOLTMETER EM.10—4½" scale, valves and case	£18.10.0
CRYSTAL CALIBRATOR CC.10 £14.10.0 Ready built	£18.19.0
OSCILLOSCOPE OG.10 with valves and tube	£22.10.0
AUDIO GENERATOR AG.10 10 c/s to 100 kc/s	£11.10.0
Ready built	£15.10.0
FM WOBBULATOR W.10	£9.0.0
STABILISED POWER PACK PP.10 with meter	£21.10.0
Less meter	£15.0.0


Further items for release shortly

3-4(E) GT. CHAPEL STREET OXFORD STREET LONDON W1

Between Tottenham Court & Oxford Circus Underground Stations

Telephone GERrard 0273/4

YOU DON'T MISS A SOUND

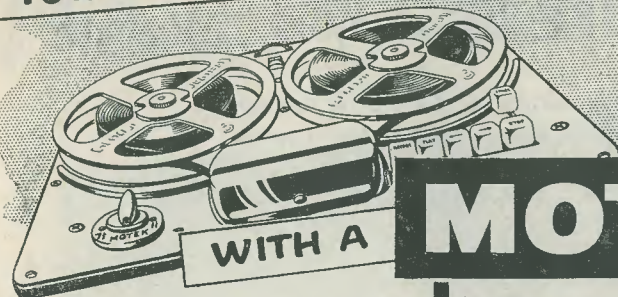

WITH A

MOTEK

GIVES THE MOST FOR LESS

No doubt about it, the Motek Tape Deck does its job more than perfectly. No wonder it's built into the finest recording machines.

Manufacturers and happy users alike feel confident with Motek — the confidence fine electrical engineering can give. Not just that but Motek is decked with five shining star features which find many followers:

Push Button Operation, Counter, Safety Erase Button, Pause Control, Three Speeds

Patents Pending. Details on request **LIST 21 GNS.**

MODERN TECHNIQUES

DHB/6362

Wedmore Street London N19

Telephone ARCHway 3114

Get these FREE CIRCUITS & WIRING DIAGRAMS

T.R.F. Circuits Mains Circuits Send
 Battery Circuits Filter Circuits 1/-
 Portable Circuits TV Converter Circuits (stamps)
 Sheet Circuits etc. etc.

OSMOR COILS are regularly used and recommended by designers writing in "Practical Wireless," "Wireless World" and "Radio Constructor." Why not follow the experts?


"Q COILS" • POTTED COILS • F.M. COILS
 All ranges

SPEAKER CROSS-OVER COILS
 TAPE COILS • ROD AERIALS
 SUB-MINIATURE COILS

COILS and I.F.s for Transistor Circuits • MIDGET I.F. TRANS. With ferrite cores

OSMOR 418 Brighton Road South Croydon Telephone CRO 5148/9

Fully Guaranteed Components

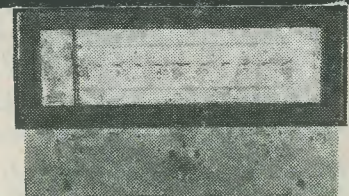

S. L. 16 DRIVE

A general purpose slide rule drive for FM/VHF units, short-wave converters, etc. Printed in two colours on aluminium, with a 0-100 scale, and provision is made for individual calibrations. Complete with bronze escutcheon and glass. **PRICE 13/9**

It's reliable if it's made by Jacksons

JACKSON BROS (LONDON) LTD.
 Kingsway • Waddon • Surrey
 Telephone CROydon 2754/5

'STEP-BY-STEP'.....

Heathkit

The exceptionally comprehensive, copiously illustrated Instruction Manual in each kit makes the successful building of every model certain, easy and fascinating. Pictorially and in simple language the Manual guides you "STEP-BY-STEP." It tells you exactly where every part goes and just how and when it should be fixed. It also explains the operation and servicing to suit the layman.

Even if you are an absolute beginner you, too, can confidently assemble any of these exceptional value-for-money Heathkit models.

You'll be delighted with the professional appearance and performance of the finished instrument and proud of the results of your work.

Millions of Heathkit instruments built as above are in regular use all over the world.

REMEMBER—BY BUILDING YOUR OWN HEATHKIT MODEL YOURSELF YOU SAVE AT LEAST HALF ITS COST!



EASY TERMS AVAILABLE

ARE YOU ON OUR MAILING LIST ?


Please send without obligation full details of the above Heathkits as ticked below. (Please write in block capitals)

Name		Address		
Model	Price Delivered			v here
DX-40U	£ s. d. 29.10.0	Covers all "Ham" bands, 80-10m. 75 watts CW., 60w. Pk. Controlled Carrier Phone, 40W to Aerial. The outstanding buy in its power class		
O-12U	34.15.0	5" Flat-face. General Purpose Oscilloscope. 3 c/s to 5 Mc/s. Rise Time 0.08µ secs. or less. Printed-circuit boards and cable harness make assembly easy		
V-7A	15.14.0	The radio serviceman's best friend and a must for the experimenter. Now at a price to suit the pocket. Measures AC/DC volts, ohms and dB.		
UXR-1	17.17.0 (incl. P.T.)	In the top flight of portables. It has a handsome real leather case and with a few hours easy assembly you have a set in the 30-guinea class		
S-88	25.5.6	Absolutely the latest in design. This model is a handsome 2-tone grey complete unit with elegant golden surround and relief. A real winner!		
SSU-1	10.9.0 (incl. P.T.)	This twin-speaker system is designed to meet the critical needs of the stereo enthusiast. Left in white wood for you to finish to own requirements		
UJR-1	2.19.6 (incl. P.T.)	Youngsters are not excluded from our kit programme. This special single transistor set is an excellent introduction to radio and an instructive present		

COMING SOON

S-33	Price to be advised	STEREO-MONAUURAL AMPLIFIER. Specially designed to meet the immense demand for a good, low-cost Stereo Amplifier Unit in kit-form	
VF-1U	Price to be advised	VFO Kit covering all Amateur Bands from 160 to 10 metres. Ideal for the Heathkit DX-40U and similar "Ham" Transmitters. In grey metal case	

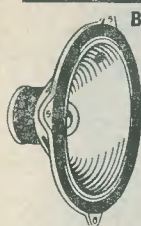DAYSTROM LTD • DEPT. RC3 • GLOUCESTER • ENGLAND
 A member of the Daystrom Group, manufacturers of
THE LARGEST-SELLING ELECTRONIC KITS IN THE WORLD



BAKERS (Selhurst) LOUDSPEAKERS

"The choice of the Connoisseur"
Rigid die-cast chassis and massive high flux magnets. First and foremost in the field of high quality moving coil loudspeakers. Damp-proof, dustproof and fully tropicalised. Full data and specification sent on receipt of 6d. stamp, or better still, call for demonstration.
12" Stalwart with foam suspension £6.15.0 plus 3/6 carr.
12" De Luxe with foam suspension £9.15.0 plus 3/6 carr.

HOME CONSTRUCTOR KITS IN STOCK

	Data	Kit
Mini-7 transistor pocket portable	1/9	£9.19.6
Transidyne transistor pocket portable	1/-	£12.19.6
Band III Pre-amplifier	1/3	£2.14.0
One-Valve Radio for beginner	1/-	£1.13.6
Mercury switched FM Tuner	2/4	£10. 0.0
Jason FM Tuner	2/4	£7. 7.6
Argonaut AM/FM Tuner	2/4	£14.10.0
Two-Valve Audio Pre-amplifier	1/3	£6. 0.0

We also stock all parts for Mullard '3-3,' Mullard 510, Mullard Tape Amplifiers Type A and C, Jason Jupiter Stereo Pre-amp and Amplifier, and the Jason JSA-2. Price lists on receipt of s.a.e.

TRANSISTORS

We are now able to offer BRAND NEW 1st GRADE PYE "GOLTOP" Transistors at really competitive prices. These are not rejects or seconds but the genuine 100% article. RF/OSC. Type V6/R4, price 21/-; I.F. amplifier Type V6/R2, price 15/9; Audio amplifier Type V10/50B, price 18/9. These will really make that pocket set go.

TAYLORMETER MODEL 127A

20,000 ohms per volt
20 Megohms. 20 Ranges

Large easy-to-read scale and robust construction make this the ideal Multimeter for all radio and television use. Compact and high-sensitivity combined. Full specification sent on receipt of s.a.e. **PRICE £10.**

Terms: Deposit £2.10.0 and six monthly payments of £1.7.6.



HIWAYMAN 4 VALVE ALL-DRY PORTABLE

A well-tried battery portable using latest high-efficiency ferrite rod aerial in superhet circuit. Medium and long waves. Can be built in four easy stages. Start now, ready for the holidays. Full constructional data and price list 1/9, post paid. Complete kit

of parts incl. cabinet £7.10.0 plus 2/6 post.

LOUDSPEAKER COMBINATION. Four acoustically matched Hi-Fi speakers complete with cross-over networks. Response 40 to 17,000 c/s. Power handling 12 watts. Full details of cabinet dimensions included. Available in 7.5 ohms and 15 ohms. **PRICE £10.5.4**, plus 3/6 carr. Send s.a.e. for full specification and details.

HOME RADIO (MITCHAM) LTD

Dept. C 187 London Road, Mitcham, Surrey
Shop hours 9-6.30, Weds. 1 p.m. MIT 3282



HERE AT LAST

NOW YOU CAN BUY
REAL MINIATURE COMPONENTS FOR MAKING UP
MINIATURE TRANSISTOR SETS

Send for price list of our comprehensive range

SPECIAL THIS MONTH

MINIATURE LOUDSPEAKERS—only 1 gn. including 7/8 P.T.
MINIATURE I.F. COILS (465-470) only 6/6
TRANSISTORS—Audio and R.F., specially packed from 7/6
MINIATURE RESISTORS—nearly every value in stock, 20%, 10% and 5%. Prices 4d.-8d., e.g. 10% 5d. Quantities of 24 upwards 3d. each

SPECIALISED ELECTRONIC COMPONENTS LTD

8 ECCLESTON SQUARE LONDON SW1

MAIL ORDERS ONLY

The

Radio Constructor

incorporating THE RADIO AMATEUR



Vol. 12 No. 8

MARCH 1959

ANNUAL SUBSCRIPTION 25/- (including postage)

CONTENTS

- 574 Suggested Circuits: A Transistorised Light-operated Switch, by G. A. French
- 578 In Your Workshop
- 583 Understanding Television, Part 15 by W. G. Morley
- 590 Crystal Stabilisation for Model Control by F. G. Rayer
- 592 Can Anyone Help?
- 593 A Core-Tuned Transportable, by A. S. Carpenter
- 598 The "Maykit" Transistorised Car Radio, Part 1 by Richard Myers
- 605 Book Reviews
- 606 Radio Miscellany, by Centre Tap
- 608 "Jinglebells"—Amateur Radio Teletype, Part 2 by Jim Hepburn, VE7KX
- 611 The Amplifone, by I. F. Gregory
- 615 Making a Glass Station Dial, by B. B. Rafter
- 617 A Battery Power Unit, by J. Hillman
- 621 A Comprehensive Mixer-Fader, by J. G. Ransome
- 623 An Explanation of Low Power Ultrasonics by R. Webb, M.I.P.R.E.

Editor

C. W. C. OVERLAND, G2ATV

Associate Editor

A. C. GEE, G2UK

Business Manager

J. H. BURROWS, A C A

Advertising Manager

F. A. BALDWIN, A M I P R E

Offices

57 MAIDA VALE LONDON W9

Telephone

CUNNINGHAM 6141
(2 lines)

Telegrams

DATABUX, LONDON

NOTICES

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

ARTICLES appearing in this magazine which describe kits are inserted only on condition that such kits, or special components thereof, are freely available at a trade discount to all retail advertisers.

OPINIONS expressed by contributors are not necessarily those of the Editor or proprietors.

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

ALL MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

TECHNICAL QUERIES should be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 Maida Vale London W9 REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."

Suggested Circuits

The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data

No. 100 A Transistorised Light-operated switch

IN THE NOVEMBER AND DECEMBER, 1956, issues of *The Radio Constructor*, the writer described switching devices capable of being operated by the incidence or interruption of light waves.¹ The light-sensitive element in these circuits was the phototransistor type OCP71, this having at that time just been introduced to the British market.

In these early devices the phototransistor operated a relay directly, and the circuits suffered from the disadvantage that this relay had to be a sensitive component capable of energising at currents of several milliamps only.

Some time after the articles had appeared the writer decided that whilst the circuits they described were practicable enough it would be desirable, when time and opportunity presented themselves, to design a circuit which obviated the necessity for the sensitive relay. This month's contribution in which a much more robust relay is employed, is the result of this decision.

The Circuit

The circuit of the new light-operated

¹ Suggested Circuits No. 72, "A Phototransistor Light-Operated Switching Circuit," and Suggested Circuits No. 73, "Phototransistor Control of Heavy Currents."

switching device appears in Fig. 1, and it will be seen that it is extremely simple and employs the minimum of components. Basic operation is very straightforward: current variations in the OCP71 phototransistor are amplified by the OC72, whose collector current then operates the relay. The device is powered by a 12-volt d.c. source.


Dealing with the circuit operation in greater detail, it will be helpful to commence with the phototransistor. When the OCP71 is connected up in the manner shown, its effective emitter-collector resistance varies according to the amount of light which falls upon it. It is quite permissible to leave the base of the phototransistor disconnected in a circuit of this nature; such a method of operation being, indeed, specified by the manufacturers when constant illumination is used. With an open-circuit base, phototransistor dissipation should be kept to a conservative level, and this point is carefully observed in the circuit of Fig. 1. The value chosen for resistor R_1 ensures that collector current cannot exceed 1mA (assuming the limiting case of zero volts drop in the OCP71) when resistor value and supply voltage are at their nominal figures. The maximum recommended value for OCP71 collector current is the markedly higher figure of 10mA.

The collector of the OCP71 connects

directly to the base of the OC72 amplifier transistor, with the result that the following process takes place. When the OCP71 is illuminated it draws current through R_1 , thereby keeping the flow of current in the base-emitter circuit of the OC72 to a low value. As a result the OC72 passes little collector current. When the OCP71 is not illuminated it draws a very small current through R_1 (if completely dark this current should be less than some $400\mu\text{A}$), whereupon an increased current flows through the OC72 base-emitter circuit. In consequence, the collector circuit of the OC72 now rises. Employing the circuit values shown in Fig. 1 the difference in OC72 collector currents between the illuminated and non-illuminated condition was found, in the prototype, to be very marked. With the OCP71 in the illuminated condition OC72 collector current was less than $200\mu\text{A}$. When the OCP71 was in the

An examination of energising currents and voltages for Post Office type 3,000 relays with two sets of change-over contacts showed that a coil resistance of 500Ω then fitted most comfortably into circuit requirements. A 500Ω relay of this type can energise reliably at a current of 20mA. Such a current would cause a drop of 10 volts in the relay coil, with the consequence that the remaining 2 volts would appear between collector and emitter of the OC72. This figure, 2 volts, together with the 20mA current flow, corresponds approximately to a collector dissipation in the OC72 of 40mW. At 30°C (86°F) the maximum allowable collector dissipation of an OC72 without a cooling fin is 112mW, and at 40°C (104°F) it is 87mW. When coupled to a heat sink the corresponding dissipation figures are 105mW and 117mW respectively. Thus, the working figure of 40mW offers a reasonable safety factor, although it would be

Fig. 1. The circuit of the light-operated switch

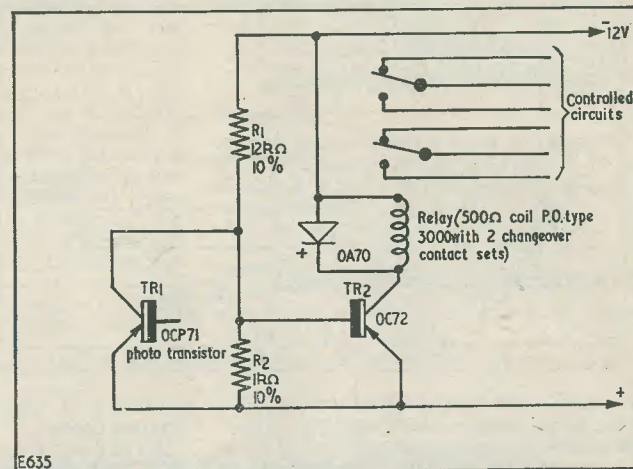

dark condition, OC72 collector current rose to 20.5mA. This very large change in OC72 collector current is, of course, more than adequate for reliable relay operation.

A coil resistance of 500Ω was chosen for the relay employed in the switching device because, from the point of view of economical construction and efficiency, it was desirable to select as low a resistance here as was commensurate with safe running of the OC72. The first limiting factor dictated by the OC72 was that, when this is connected as a grounded emitter amplifier having $1k\Omega$ resistance between base and emitter, the recommended maximum collector voltage is 16 volts. In consequence it was decided that a supply voltage of 12 (conveniently available from an accumulator or a simple mains unit) would represent a good choice for powering the unit.

desirable to couple the transistor to a heat sink in order to prevent excessive self-generated rise in temperature.

It will be noted that an OA70 crystal diode is connected across the relay coil. The purpose of this diode is to prevent the formation of a high reverse voltage in the relay coil if its energising current suddenly reduced in value, as might occur with sudden illumination of the OCP71. Such a reverse voltage would, of course, be the result of the consequently collapsing magnetic field in the coil. The crystal diode is so connected that it is not conductive when the lower end of the relay coil is positive. In the event of a sudden cessation of energising current, the lower end of the coil tends to swing negative with respect to the upper end, whereupon the diode conducts and prevents the reverse

voltage from reading too high a value. Without the diode the reverse voltage across the relay coil could reach a value which, added to the h.t. voltage, might cause the recommended maximum collector voltage for the OC72 to be exceeded.

Practical Points

A switching device of the nature we are considering here will find a number of applications, one of the most obvious being the operation of subsidiary circuits by the incidence or interruption of a light beam. In applications of this nature it will frequently be necessary for the OCP1 to be continually illuminated by a source of light. In such instances, a considerable economy in energising light power may be achieved by mounting the phototransistor in a tube fitted at one end with a convex lens, as is illustrated in Fig. 2.

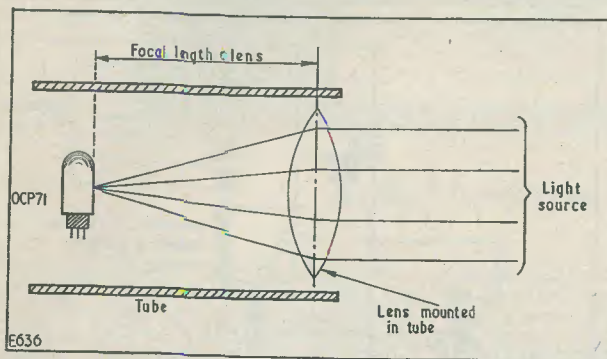


Fig. 2. When the OCP71 is illuminated by a single light source, considerable economy in energising light power may be achieved with the aid of a simple convex lens.

The convex lens does not need to be a costly item, as an inexpensive "magnifying glass" costing one or two shillings only should prove to be more than adequate. The focal length of such a lens may readily be found by using it to throw an image of the sun or of an electric light bulb on to a piece of paper. When the image is correctly focused, the focal length will then be the distance between that image and the lens. In the writer's prototype it was found possible with the aid of a cheap lens having a diameter of 1½ in to obtain reliable operation from a 12 watt bulb, without reflector, mounted some 6ft away. An advantage of the tube and lens arrangement of Fig. 2 is that extraneous light does not reach the phototransistor and cause unwanted actuation of the relay. Indeed, the circuit should function quite satisfactorily under normal conditions of ambient illumination. It must be mentioned before concluding on this particular subject, that there is no point in employing excessive light energy to illuminate the OCP71. Sufficient light energy

to reduce OC72 collector current to its minimum value is all that is needed. As an aid to constructors, Fig. 3 illustrates the sensitive area of the OCP71.

It was mentioned above that it would be preferable to couple the OC72 to a heat sink in order to prevent excessive self-generated temperature rise. Such a coupling may be achieved by lightly clamping the OC72 to a heat sink having the minimum dimensions of 1½-in square. A very adequate sink could be provided in practice by clamping the OC72 to a small metal chassis which also held the relay and, say, one or two tag-strips for lead-out connections and the like. This chassis should be kept cool and should not have any heat-dissipating components mounted on it. The clamp securing the OC72 to the chassis should be of metal and should encircle the metal case of the transistor over a large pro-

polarity, as incorrect connection may cause the OC72 to pass excessive collector current. Crystal diodes from "surplus," or otherwise dubious, sources should not be used in this circuit.

Finally, it must be pointed out that the circuit specifies a 500 ohm Post Office relay type 3,000, and that the reader is strongly advised to use a relay of this type for his own unit. A P.O. 3,000 relay with one or two sets of contacts will function satisfactorily, but energising current requirements may be excessive for reliable operation if more than two sets of contacts are fitted.³ The writer has not checked circuit operation with any other type of relay.

Setting Up

Due to the fact that the OC72 runs at a fairly high dissipation level it would be advisable, after construction, to check the unit for correct wiring, etc., at a reduced h.t. voltage before bringing it into full operation. For this check a milliammeter should be connected in series with the relay coil and the h.t. negative line, and an h.t. potential around 6 volts applied. With the OCP71 in the unilluminated condition a milliammeter reading of approximately 6mA should be given at this voltage, and should drop to a negligibly low value when the OCP71 is illuminated. Provided the preliminary test is satisfactory the full h.t. voltage may be applied, whereupon it should be found that the relay coil current lies

³ A suitable relay, fitted with two sets of change-over contacts, is available from H. L. Smith & Co. Ltd., 287 Edgware Road, London, W.2.

between 17 and 22mA with the OCP71 non-illuminated. If the current reading obtained for the dark condition falls slightly outside these figures it may be decreased by a small

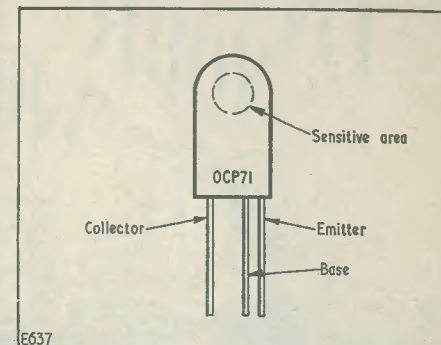


Fig. 3. This diagram shows the light-sensitive area of the OCP71. The type number should be on the same side of the phototransistor as is the light source.

increase in the value of R_1 , or increased by a small decrease in value of this resistor. In the absence of a milliammeter capable of reading currents of the order of 20mA, a high resistance voltmeter may be connected across the relay coil, and the readings provided by this instrument converted to current figures. Thus, to take an example, a voltage reading of 10 volts across the 500Ω relay coil would indicate a current flow of 20mA.

Mullard announce

A NEW SERIES OF EDUCATIONAL FILMSTRIPS

A new series of filmstrips dealing with the history and basic principles of important scientific developments has been announced by the Mullard Educational Service.

These filmstrips are aimed primarily at Secondary Modern pupils, but will also be useful for grounding Grammar School arts pupils in some science subjects.

The first strip, entitled "The History of Radio," is available now, and brief details are given below. The next, on "The History of Television," will be released shortly.

The introduction of the Secondary Modern series brings the number of filmstrips available from the Mullard Educational Service to over 30. These include a series covering the general principles of electronics at Grammar School level, and a series for technical college students taking the Ordinary National Certificate in electrical engineering.

"The History of Radio" (35 frames, colour)

"The History of Radio" reviews the progress made in telecommunications from the days of the first primitive telegraph and telephone systems. It outlines the discovery of electro-magnetic waves, illustrates Marconi's experimental work, including the historic transatlantic wireless transmission, and ends by describing modern radio communication techniques and showing examples of present-day broadcasting equipment. Wherever it is necessary to the development of the story, fundamental principles of electricity and magnetism are simply and concisely explained.

A comprehensive set of teaching notes is supplied with the strip, which is available from the distributors: Unicorn Head Visual Aids Ltd., 42 Westminster Palace Gardens, London, S.W.1, price 20s. a copy.

portion of its area in order to ensure good thermal contact.²

Some care needs to be taken to ensure that the 12-volt supply is sufficiently well-regulated to prevent the h.t. potential approaching the recommended maximum collector voltage for the OC72 (with 1kΩ base-emitter resistance) of 16 volts. Thus, it would be unwise to power the circuit with a 12 volt accumulator which was on continual charge, as the accumulators terminal voltage could rise dangerously close to the maximum figure or even exceed it. The requirements for voltage regulation apply similarly to mains power units.

Attention must also be paid to ensuring that the crystal diode connected across the relay coil is in good condition before it is soldered in position. A quick check for low forward resistance and high back resistance may easily be carried out with the aid of an ohmmeter. It is important to connect the diode across the relay coil with correct

² A suitable clamp is described in the manufacturer's literature.

IN YOUR WORKSHOP



In this month's episode, Smithy the Serviceman passes on to his assistant, Dick, some useful advice on video detectors and printed circuits

"F," SAID DICK, LEANING CONFIDENTIALLY over Smithy's shoulder, "you stuff a turkey with sage and onions, what do you stuff a parrot with?"

Recognising the signs, Smithy heaved an almost silent sigh. He allowed his attention to be detracted from his work.

"I wouldn't know," he remarked with resignation. "What do you stuff a parrot with?"

"You stuff it with Polyfilla," replied Dick.

After which, he retired to his bench laughing loudly. Despite himself, Smithy the Serviceman grinned; and he decided to accept the fact that Dick was in one of his joke-telling moods and that he would just have to be given his head until he had run out of gags. Dick's jokes sessions occurred every two months or so, and Smithy had discovered, after careful questioning, that his assistant picked up all his new stories from that uncle of his who happened also to be the steward of Smithy's club. The main thing that annoyed Smithy was that he himself never heard any of Dick's jokes at his club yet, whenever he tried to repeat them, everybody else at the club had heard them.

Crystal Diodes

On this particular morning, however, Dick's output of jokes was somewhat short-lived. Almost immediately after he had left

Smithy's side he ran into trouble and had to call upon the Serviceman for assistance.

The first of Dick's troubles became evident as he was looking thoughtfully at a rather venerable television chassis on the bench before him.

"Smithy," he called out after some moments, "what do you do with a television set whose video detector keeps breaking down?"

"It all depends upon the circumstances," replied the Serviceman briefly.

Leaving his own work he walked over to inspect the chassis on Dick's bench.

"Look," said Dick, "I had this chassis in a few months ago suffering from a lack of vision whereupon, after a little hunting around, I discovered that the video detector had shuffled off its mortal coil. The video detector employed in this receiver is a straightforward crystal diode, and, after removing its screening can so that I could fit a new unit, I got the chassis working O.K. The set has now come back to me again with exactly the same fault and I find that the video detector has once more gone kaput. I just don't get it."

"Not to worry," Smithy remarked. "This sort of thing is quite liable to happen every now and again with older sets of this type. Did you fit exactly the same type of crystal during your previous repair?"

"Not exactly," admitted Dick. "The original diode was an OA60, and I replaced it with the somewhat more up-to-date OA70."

"That shouldn't make any difference in this application," remarked Smithy. "Both types are intended as video detectors. Now let's take a closer look."

Smithy examined the faulty diode.

"Well," he remarked slowly. "I can see no evidence of your having over-cooked the crystal when you soldered it in. To begin with, you've left a good half-inch of wire between the body of the diode and its solder joints, and this is an excellent thing to do. I usually assume that a quarter of an inch is the absolute minimum safe distance between the body of a crystal diode and its solder joint, and your half-inch exceeds this comfortably. In addition, I see that you've taken good care not to bend the lead-out wires too close to the glass, where they could cause weakening of the structure."

"As a matter of fact," put in Dick a little proudly, "I remember that I even used a heat shunt during soldering."

"Very good," approved Smithy. "There are many people who would laugh their heads off at the very idea of using a heat shunt when soldering in crystal diodes, but I can't say that I agree with their point of view. I must concede, though, that one often-advocated method of applying a heat shunt by using a pair of taper-nosed pliers (Fig. 1 (a)), can only be seriously recommended to three-handed service engineers! However, there's no need to do that sort of thing if you're sensible. As you know, we use crocodile clip heat shunts (Fig. 1 (b)) in the Workshop and the time and inconvenience incurred by their use is negligible."

"You have to admit, Smithy," said Dick, a little plaintively, "that there are very many people who solder crystal diodes into circuit without heat shunts at all, and that they seem to get away with it. Do you think, perhaps, that we're being just a little too fussy?"

"Not at all," replied Smithy. "I would say with some confidence that those people who don't use heat shunts will find that a small percentage of the diodes they connect up refuse to work properly, have shifted characteristics, or fail at an early date. Mark you, this percentage may be quite low, but I still think it's good practice to obviate it altogether. Another point is that the heat shunt habit is a very useful acquisition when you start tackling transistors, as these are definitely susceptible to overheating."

"Anyway, we're getting off the beam. What started our present discussion was this chassis which causes video detectors to become faulty at regular intervals. I'm quite

happy that your previous replacement diode was O.K., and so we must look elsewhere. I presume that no h.t. was getting on to the diode?"

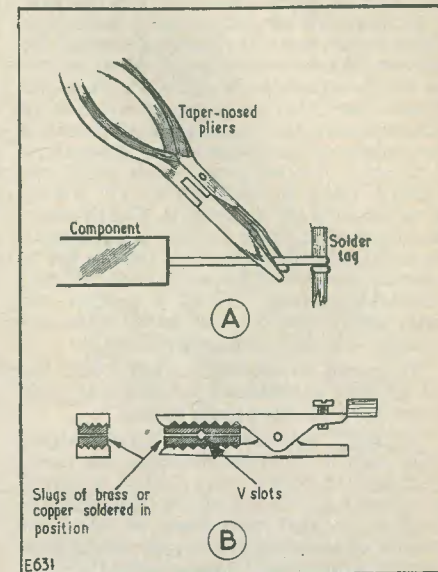


Fig. 1 (a) An often recommended method of applying a heat shunt. The taper-nosed pliers, applied to the component lead-out wire as shown, prevent the transference of excessive heat from the tag to the component body during soldering. (b) A much more convenient method of applying a heat shunt consists of clipping a crocodile clip, modified as shown here, to the lead-out wire. The slugs of brass or copper should have approximately the volume indicated by the diagram. The small V cuts ensure a positive location with the lead-out wire, together with somewhat greater thermal contact area

"Not a scrap," replied Dick. "The detector circuit is extremely simple: it consists of the secondary of the last i.f. coil, the crystal, and the load resistor in series. It would be extremely difficult for any h.t. to find its way across the diode."

"Fair enough," remarked Smithy. "All I can then diagnose is that the crystal is burning out because of the application of too high an i.f. voltage."

"Hey?"

"I'm quite serious," continued Smithy. "In some of these early sets, many of which

had either a very rudimentary a.g.c. system, or none at all, it is easily possible for the customer to accidentally turn up his contrast or sensitivity control too high and cause a fantastically high video i.f. voltage to be passed on to the video detector. This assumes, of course, that the set is being used in a strong signal area. If maladjustment of the contrast or sensitivity control occurs before the set is switched on, then the customer doesn't see the resultant over-contrast picture until e.h.t. appears—by which time the damage will have been done. I can think of all sorts of other eventualities which can similarly result in too high an i.f. voltage being passed to the video diode. For instance, the customer may have a wonky connection to his aerial, whereupon he finds that he has to screw up the gain of his set in order to get a reasonable picture. All of a sudden, the aerial connection becomes good again and—bingo!—bang goes another diode!

"It sounds to me," remarked Dick, "as though this business of overloaded video diodes is by no means new to you."

"It isn't," said Smithy. "That's why I made such a confident diagnosis just now. If the set had been a more modern job with, say, mean a.g.c. coming off the sync separator grid,¹ I wouldn't have been so confident because conditions of overload would then have been much less liable to occur."

"That's fair enough, I suppose," said Dick, dubiously, "but where do I go from here? If I put another crystal into this set how long will it be before *that* goes?"

"You do have something of a problem there," admitted Smithy. "When I bumped into this trouble in the old days, I used to warn the customer against over-running his set, and this warning usually resulted in fairly reasonable protection for the diode. Nowadays, however, I use a completely different idea, this consisting of replacing the diode with a type which has a higher turnover voltage. In your case I would recommend that instead of fitting another OA70 you fit an OA79. The maximum inverse voltage of an OA79 is twice that of an OA70 and it is intended for use in fairly low impedance circuits, such as f.m. ratio detectors and the like. You should find that it gives just as good a picture. I know that I've never had one go faulty since I started using them in receivers suffering from this sort of trouble."

"That's fine," said Dick enthusiastically, "I'll pop an OA79 in straight away. Incidentally, Smithy, why are video detector circuits nearly always screened?"

¹ In many receivers the grid of the sync separator goes negative with respect to chassis by a voltage proportional to the mean picture level. This voltage may be employed for a.g.c. purposes.

"For the same reason," said Smithy, "as are many other receiver detector circuits which rectify signals at high level. The process of detection causes the rectified half-cycles to resemble square waves, and these are liable to be very rich in harmonics of the detected frequency. Unless you apply a reasonable amount of screening to the detector circuit these harmonics may find their way back to the front end of the set. O.K.?"

"Sure," said Dick. "By the way, have you heard about the last word in automation?"

Smithy raised his eyes to the ceiling in mock despair.

"Go on," he intoned dolefully.

"Well," said Dick, "it consists of a black box with a switch on the front."

"Yes?"

"To set it in motion you push down the switch. Whereupon there is an immediate and furious whirring inside the box, the lid opens, and an arm comes out and turns the switch off."

Dick stopped and looked expectantly at Smithy, whose expression remained unaltered.

"That's it," finished Dick lamely.

"Oh," said Smithy.

With no further remark he returned to his bench where, unseen by his assistant, he allowed his face to relax into a wide grin.

Printed Circuits

Crushed, Dick returned to the receiver in front of him. He soldered in a new crystal of the type advised by Smithy, found that he obtained a satisfactory picture, and fitted the chassis back into its cabinet. A final check of the boxed set showed that all was well, whereupon Dick stowed it away on the "repaired" rack.

The next set Dick took to his bench was of a much more modern type. Dick quickly checked the performance of the receiver and removed its cabinet. After a while he gave a sharp exclamation of surprise.

"What's up?" said Smithy, turning round. "Would you credit it?" asked Dick, "but I'm blown if I haven't got another video detector up the wall!"

"That's very nice for you," commented Smithy. "The same fault twice running should give your diagnostic powers a pleasant rest."

"Do you think that this one went faulty due to too much signal level also?" asked Dick.

"It's doubtful, if it's a recent receiver," replied Smithy, "although I should check the a.g.c. line for shorts to chassis just in case."

He noticed that Dick's expression was becoming more and more disgruntled as he examined the chassis he had selected.

"What's the matter?" queried the Serviceman.

"I'm going to have a deuce of a job replacing *this* diode," said Dick lugubriously. "The manufacturers have parked it inside the same can as the coil it's connected to, and the coil is soldered to a printed circuit board by at least half a dozen tags."

The Serviceman walked over to look at the chassis.

"All I can say," he remarked eventually, "is that if you intend unsoldering the coil from the board, you must positively like unnecessary hard work. As you can see, the coils in this receiver are just the same as the coils in most other printed circuit television sets, insofar that the cans are held by spring clips and can be pulled off quite easily. Why don't you simply remove the coil can, nip out the faulty diode, and solder a new one in its place whilst the coil assembly is *in situ* on the board?"

"I must be getting a little dim in my old age, because that thought never even occurred to me," commented Dick. "Now that you mention it, your idea seems to be the obvious thing to do."

"Most definitely it is," replied Smithy. "Nevertheless, you'd be surprised at the number of people who go to all the trouble of unsoldering a coil from a printed board when all that's wrong with it is something which can be just as easily fixed by merely taking the can off. Even if the winding itself has gone faulty you can still quite often effect a repair after merely removing the can. Quite a few of the more modern television i.f. coils are wound with T.N.A. wire, so you don't have to bother about stripping it—you merely apply solder and a hot iron."

"It sounds to me," remarked Dick, "that you have decided to evolve your own techniques for printed circuits. What about components, other than i.f. coils, which are soldered to the board by a relatively large number of tags?"

"Well, you have to regulate your repair system according to the circumstances of each particular case," conceded Smithy, a little guardedly, "but there are quite a few components as well as i.f. coils which can be repaired whilst in position on the board. For instance, I've had one or two cases of supposedly open-circuit audio output transformers wherein the primary wire was taken from the winding to two tags on its periphery. All that was wrong with these transformers was that the primary wires had broken away at one or other of the tags. It was quicker to repair these wires than it was to unhitch the whole tranny from the board."

"Ah, yes," persisted Dick, "but the occasion must arise at some time when you

have to unsolder multi-tag components from a board. What then?"

"There are one or two bright ideas to fall back on then," replied Smithy. "If you possess a solder gun, one of these consists of making up a circular bit which is some $\frac{5}{8}$ to $\frac{7}{8}$ in in diameter (Fig. 2). You can then apply this bit to the board if you want to remove, say, a valveholder; whereupon it melts all the solder joints at once. Such a bit will usually tackle all the joints on i.f. coils and things like that as well, should this be necessary."

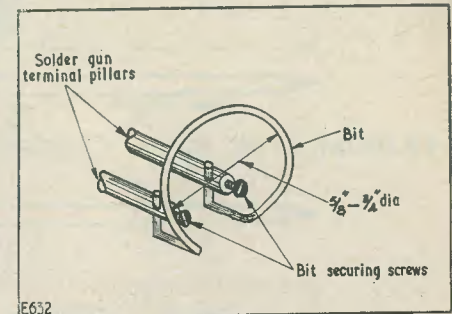


Fig. 2. A solder gun bit, shaped as shown here, can prove useful in removing valveholders and similar components from printed circuit boards

"An alternative idea consists of tackling one by one the joints which secure multi-tag components to the board. What you do in this case is to apply a wiped iron to each joint so that it automatically removes most of the solder. Whilst the joint is still hot you then brush it quickly with a toothbrush, thereby dispersing the remainder of the solder. When you've done this to all the joints holding the component, it is usually possible to lift it out quite easily. This process sounds a little long-winded, I must admit, but after you've done it a few times you soon get the knack of it."

"There is one method, however, that you should never use. You should never try to remove a multi-tag component by unsweating one tag at a time and simultaneously trying to rock the component. That's one of the surest methods of lifting the copper at the other tags that I know about."

"O.K.," said Dick. "I'll bear those points in mind. This printed circuit business certainly seems to have resulted in service engineers dreaming up new dodges."


"Service engineers," said Smithy, a little pompously, "have been dreaming up new dodges ever since radio started. It's part of the trade. As you go around you'll probably hear a few service engineers beefing about

printed circuits and pining for the old days when everything was conventionally wired. But I don't lay much store by such complaints. Service engineers are rather like farmers, they just love to grumble!"

Test Prods

"Talking about grumbles," remarked Dick, "you've just reminded me about a

you are doubtless interested in their construction, I'll tell you how they're made. The metal part of each prod is a 5in length of $\frac{1}{8}$ in brass rod having a $\frac{1}{2}$ in flat filed at one end and a point at the other (Fig. 3 (a)). After filing the flat and the point, the former is tinned and the whole rod cleaned, if necessary, with emery cloth. The next job consists of soldering the lead to the flat

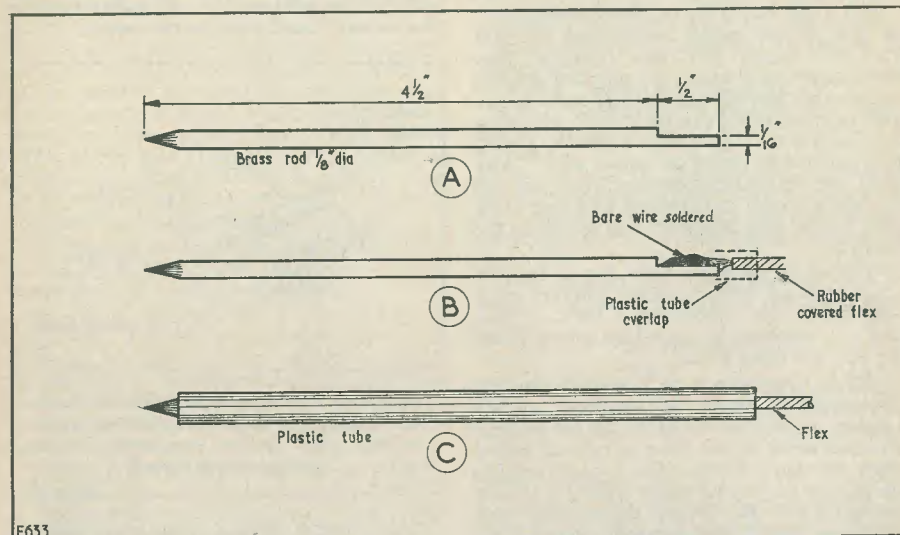

E633

Fig. 3. Successive steps in the construction of the test prods described by Dick

recent complaint of yours concerning the serviceability and upkeep of the test prods in this Workshop."

"I seem to remember saying something of that order," said Smithy, cautiously.

"I have an idea," continued Dick, "that your complaint occurred when you were checking the mains voltage a week or two ago. You may recall that the rubber insulation at the top of one of the prods you used had slipped away from the metal underneath." Dick paused for a moment, as though savouring a pleasurable memory. "You jumped around a little," he added.

"Merely an expression of *joie de vivre*."

"Quite so," said Dick. "At any event the occasion has resulted in my producing a pair of super-duper test prods which are not only strong but have really *tough* insulation.² As

(Fig. 3 (b)). A little p.v.c. tape over the joint provides extra strength here. The final process consists of covering the rod and the joint with 6in of 3mm plastic tube of the type used for the fuel lines of model aircraft, the requisite type being that which is knurled longitudinally on the outside. The plastic tube is a very tight fit on the rod, but if it is held in hot water for a few minutes it can be forced on. The tube should be passed over the rod until it is some $\frac{1}{8}$ in past the solder joint. The final job consists of trimming the tube at the pointed end of the rod to leave, say, $\frac{1}{4}$ in of brass showing (Fig. 3 (c)). The result of all this is a really tough and reliable test prod."

"It certainly seems to be good and strong," remarked Smithy, examining the prods which Dick showed him. "I think you'd better knock up a few more."

"O.K.," said Dick. "Incidentally, talking about hot water reminds me of a joke I want to tell you concerning a commercial traveller who ran out of petrol . . ."

² The design of these prods is due to reader D. R. Lett of Liverpool, who has had a pair in use for two years without failure.

UNDERSTANDING TELEVISION

PART 15

By W. G. MORLEY

The fifteenth in a series of articles which, starting from first principles, describes the basic theory and practice of television

LAST MONTH WE CONSIDERED, IN RATHER general terms, the overall requirements of the i.f. amplifier in a modern television receiver. We shall now carry on to a more detailed consideration of this part of the receiver.

The Vision I.F. Amplifier

The function of the vision i.f. amplifier is to amplify the vision i.f. signal passed to it by the tuner unit at the front end of the set. In consequence, the vision i.f. amplifier must have a frequency response which enables all video frequency sidebands to be amplified at correct level. A complicating factor is that the transmitted signal has one of its sidebands only *partially* suppressed. Fig. 81 illustrates the ideal British transmitter characteristic.¹ As may be seen, the sidebands resulting from the lower modulating frequencies appear on either side of the carrier.

Fig. 82 shows the response curve of an i.f. amplifier which would be capable of amplifying the video i.f. signal satisfactorily. It will be seen that the response is flat between approximately 35.9 and 37.65 Mc/s, after which it falls rapidly to a very low level at

the sound carrier frequency of 38.15 Mc/s. Below 35.9 Mc/s the response falls more gradually, it crossing the 34.65 Mc/s line (the intermediate frequency which corresponds

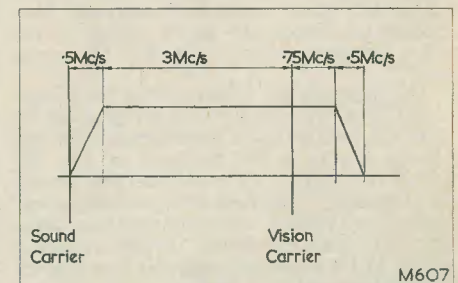


Fig. 81. The ideal British transmitter characteristic

to vision carrier) at a level which is approximately 50% of the total amplitude of the response. The response reaches a low level at 33.6 Mc/s approximately, this low level being maintained at the adjacent channel frequency of 33.15 Mc/s.²

¹ This characteristic is based on the information given in Fig. 20 and Table II of Understanding Television, part 4, published in the April 1958 issue.

² See last month's article.

The reason for the gradual drop in the response of Fig. 82 below 35.9 Mc/s is that this helps to counteract the effect of the partially-suppressed sideband on the vision carrier. If the i.f. response of the receiver were flat from 37.65 to 34.65 Mc/s, the lower modulating frequencies, which appear

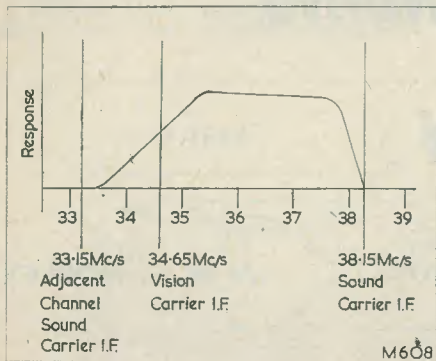


Fig. 82. A vision i.f. response capable of handling the transmitter characteristic of Fig. 81. (It will be remembered that, after conversion, the vision carrier i.f. falls below the sound carrier i.f.)

in both sidebands, would be passed to the video detector at a higher amplitude than the high frequencies which appear in one sideband only, and a distorted picture would result. The fall-off in response in Fig. 82 below 35.9 Mc/s causes both high and low modulating frequencies to be passed to the video detector at approximately the same level.

The necessity for ensuring that the sound signal does not reach the video detector at sufficient level to cause interference with the picture results in the response of Fig. 82 falling rapidly to a very low level just before 38.15 Mc/s. The desirability of ensuring protection against interference from the adjacent channel sound carrier similarly results in the response being at a low level at 33.15 Mc/s.

In practice it is difficult to obtain a vision i.f. response curve equivalent to that shown in Fig. 82 whilst employing the small number of valves and tuned circuits dictated by commercial manufacturing requirements. As a consequence, the vision i.f. response in practical receivers may be degraded by small amounts. These should not, however, cause any very noticeable degradation of the reproduced picture.

The response of Fig. 82 is flat between 37.65 and 35.9 Mc/s. In practice it is per-

missible for a deviation in response amplitude of 2dB to occur before any visible effect becomes obviously noticeable in the reproduced picture. (Some authorities give a figure of 3dB in response amplitude as the maximum obviously-noticeable variation.)³ Thus, the flat-topped response of Fig. 82 may change in amplitude level by 2dB and still be considered "flat."

Another manner in which the response curve of Fig. 82 may be modified in commercial receivers is concerned with the overall frequency range covered. Ideally, the response should be "flat" up to 37.65 Mc/s so that the highest modulating frequency of

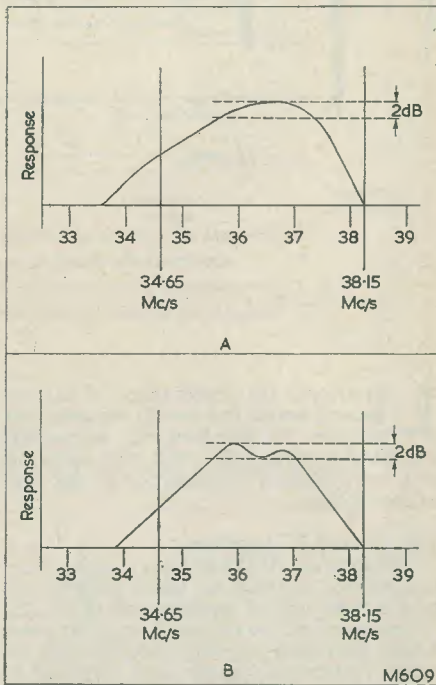


Fig. 83 (a) and (b) Typical examples of how the response of Fig. 82 may be degraded without excessive loss of picture quality. In both cases the sidebands of modulating frequencies above 2.5 Mc/s suffer attenuation

3 Mc/s may be amplified at correct level. In many practical televisions the vision i.f. response commences to drop at a frequency markedly below 37.65 Mc/s, with the result that modulating frequencies approaching 3

³ 2dB and 3dB are equivalent to voltage ratios of 1:1.26 and 1:1.41 respectively. The expression "dB" is an abbreviation for "decibel."

Mc/s are not amplified at full strength. Usually, such fall-off commences around 37.15 Mc/s, so that full amplification is provided for modulating frequencies up to 2.5 Mc/s only. A fall-off in response at a frequency lower than 37.15 Mc/s may be encountered in some receivers, but this is not a very desirable state of affairs.

An i.f. response curve typical of those liable to be found in commercial receivers is given in Fig. 83 (a). In this diagram we see a response which is "flat" within 2dB between, approximately, 35.9 and 37.15 Mc/s, which is consequently capable of handling the sidebands of video modulating frequencies up to 2.5 Mc/s without any obviously noticeable difference of level in the reproduced picture. The response curve of Fig. 83 (b) may occasionally be encountered; and this can similarly handle the sidebands of modulating frequencies up to 2.5 Mc/s. It will be noted that the response of Fig. 83 (a) is, in reality, a broad single-peak response, whilst that of Fig. 83 (b) has the double-humped shape normally associated with bandpass circuits.

Individual Tuned Circuits

The process of designing a vision i.f. amplifier capable of providing even the slightly degraded curves of Figs. 83 (a) or (b) is not by any means a simple process, and considerable care has to be taken to ensure that a number of conflicting requirements are satisfactorily met.

Whilst it may, at first sight, appear that a satisfactory response may be obtained by the use of a number of tuned circuits which are damped (by, say, connecting resistors across them) so that they individually give a broad response, such a technique has to be used with caution. This is due to the fact that the gain provided by an amplifier whose tuned circuits are excessively damped tends to be low. Despite this, damped tuned circuits are frequently encountered in vision i.f. amplifiers, a compromise being struck between gain and frequency response. Conflicting with the gain requirement is the point that, if a tuned circuit in a video i.f. amplifier functions very efficiently, giving thereby a sharp response, such a tuned circuit is liable to ring if shock-excited by an intermediate frequency equal to that to which it is tuned. The process of ringing may perhaps be a little better understood with the aid of Fig. 84 (a). In this diagram the tuned circuit oscillates in sympathy with the intermediate frequency during the time that it exists (points A to B in Fig. 84 (a)) but, when the intermediate frequency disappears, the tuned circuit continues to oscillate at the frequency to which it is tuned, causing a "damped train" of oscillations (i.e. a series of oscillations

continually decreasing in amplitude) to be passed on to the video detector. Such a damped train will appear on the picture. A tuned circuit having a sharp response curve may also be shock-excited into ringing when there is a sudden and large change in amplitude in the signal (say, from black to white or vice versa) whereupon, once more, a damped train of oscillations is passed to the video detector. (See Fig. 84 (b).)

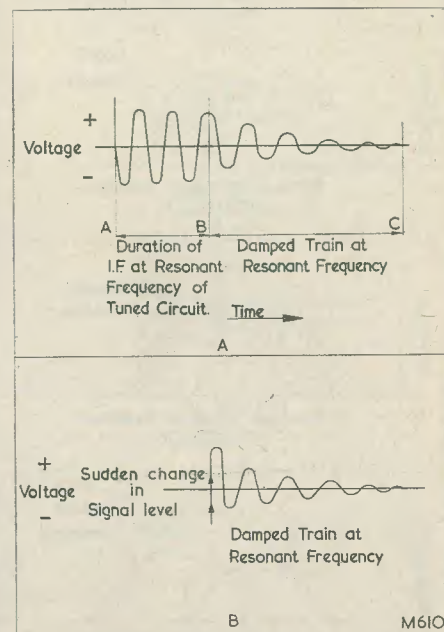


Fig. 84. A tuned circuit having a sharp response curve is liable to ring if excited by (a) several cycles of i.f. at its resonant frequency, or (b) a sharp change in signal amplitude

Another conflicting factor affecting the design of a vision i.f. amplifier is that this must be capable of offering a good transient response. Sudden changes in amplitude of the i.f. signal must be handled without the introduction of excessive distortion and must be passed to the video detector without appreciable delay or overshoot.⁴ As a rule of thumb it is normal to assume that if any tuned circuit in a vision i.f. amplifier has an excessively sharp response, the transient response may become degraded.

With the points just mentioned in mind, we may now consider the various manners in which the individual responses of a number

⁴ Transient response was dealt with in Understanding Television, part 2, February 1958 issue.

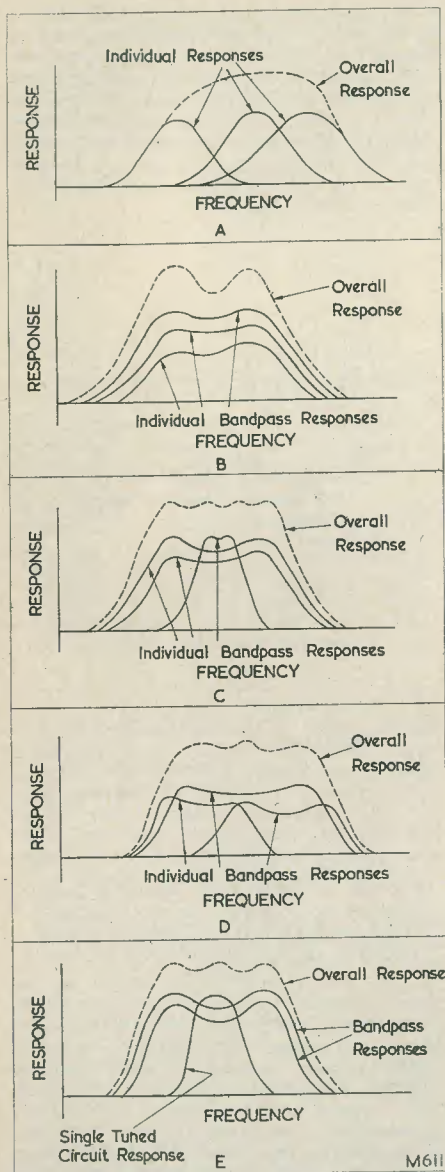


Fig. 85 (a) A relatively flat-topped composite response may be achieved by the combination of the responses of single tuned circuits resonating at different frequencies. (b) Here, a number of bandpass responses provide the composite response. (c) and (d) The tendency of response (b) to have an excessively deep trough may be alleviated by varying the

of tuned circuits may be combined so that a satisfactory overall response is obtained.

There are three basic methods of doing this. The first consists of employing a number of single tuned circuits, each adjusted to resonate at a different point within the band of frequencies it is intended to handle. This technique is described as "stagger tuning." A second system consists of employing bandpass coil pairs throughout the i.f. amplifier. The third method uses a combination of bandpass and single-tuned circuits.

Fig. 85 (a) shows how the individual responses of a number of stagger-tuned circuits may be combined together to provide a composite flat-topped response covering the desired band of frequencies. Fig. 85 (b) illustrates how bandpass coils may similarly be employed. Fig. 85 (b) also shows the fact that, if care is not taken, the individual double humped curves may result in a composite response which is, itself, excessively double humped. Such a tendency may be overcome, whilst still retaining bandpass circuits throughout, by such devices as are shown in Figs. 85 (c) and (d), wherein varying bandwidths and centre frequencies in the individual bandpass tuned circuits assist in raising the central trough of the composite curve.

Fig. 85 (e) illustrates a combination of bandpass and single-tuned circuits. This method of obtaining a composite curve is that which is most usually encountered in modern receivers.

It will be noted that all the composite response curves of Fig. 85 have "skirts" which fall slowly to zero level. Whilst the shape of either skirt in each response is acceptable for the lower frequency end of the i.f. response curve (see Fig. 82), it does not satisfy the requirement for a rapidly falling skirt at the high frequency end. In practice, the rapidly falling skirt is achieved by the addition of the sound rejector circuits.

Sound Rejector Circuits

We have already seen that it is necessary to employ special rejector circuits in the vision i.f. amplifier in order to ensure that the sound signal does not reach the video detector at sufficient strength to cause interference with the picture. We shall now examine the various types of rejector circuit which are employed in practical i.f. amplifiers.

One of the simplest types of sound rejector is that illustrated in Fig. 86 (a). The rejector

bandwidths and/or centre frequencies of some of the bandpass responses. (e) A composite response may be obtained by the combination of bandpass and single tuned circuit responses

tuned circuit in this diagram is adjusted to 38.15 Mc/s, whereupon it absorbs energy at that frequency from the i.f. coil to which it is coupled. There is no direct connection between the i.f. coil and the rejector coil, as the coupling is purely inductive. It is possible, by varying the spacing between the two coils, to make the circuit of Fig. 86 (a) provide varying degrees of rejection.

Another simple rejector circuit is illustrated in Fig. 86 (b). In this case the rejector

circuit is inserted in the coupling connection between a pair of bandpass tuned circuits. Yet another simple rejector circuit is illustrated in Fig. 86 (c). In this instance, a series tuned circuit connects directly across one of the i.f. coils, and it absorbs energy at the frequency to which it is tuned. A further method of employing a single tuned circuit for rejector purposes is shown in Fig. 86 (d). Here, a parallel tuned circuit resonating at the rejection frequency is connected in series

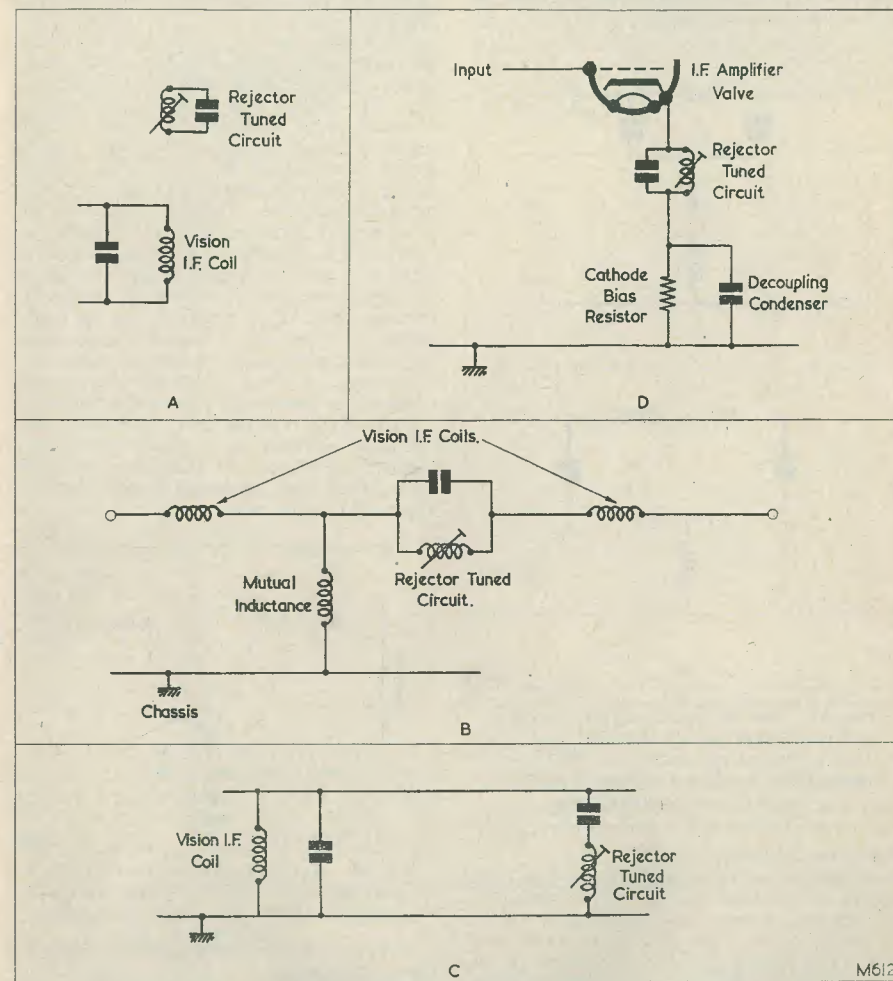


Fig. 86 (a) A simple absorption rejector circuit. The rejector coil is coupled inductively to the i.f. coil. (b) A bandpass network having a rejector tuned circuit inserted in the common connection between the two tuned coils. (c) Another absorption rejector circuit. (d) Attenuation at a fixed frequency may be obtained by inserting a parallel-tuned circuit in series with the cathode of an i.f. amplifier valve.

with the cathode of one of the i.f. amplifier valves. At frequencies removed from the rejection frequency this tuned circuit possesses a low impedance and has little effect on the functioning of the i.f. amplifier. At the rejection frequency the tuned circuit offers a high impedance, with the result that the valve functions in rather the same manner as it would if it had a high cathode bias. In consequence, it offers less amplification.

The circuits of Fig. 86 can all offer varying degrees of rejection according to the efficiency of the tuned circuits employed.

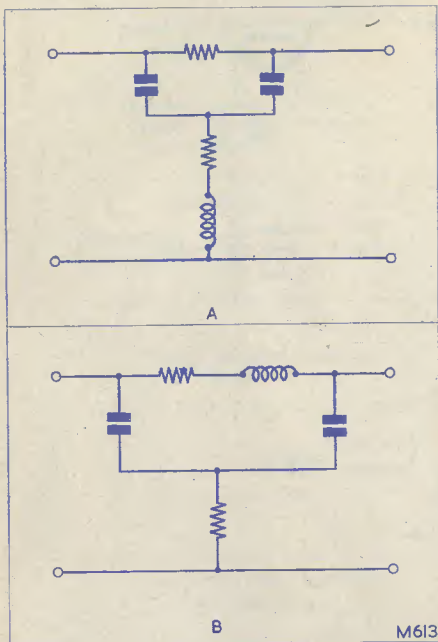


Fig. 87. Two bridged-T retractor circuits. The resistances shown in series with the coils represent the losses in these components and would not appear as physical items in practical networks

Adequate Rejection

In order to obtain complete freedom from sound interference on the picture presented by the cathode ray tube it is necessary for the sound i.f. to be some 40dB or more in level below the picture signal level.⁵ None of the circuits of Fig. 86 are capable of providing this degree of rejection on their own, although sufficient rejection would be feasible if two or more were employed in successive stages. As a result, more complicated and more efficient retractor networks are employed in

⁵ 40dB corresponds to a voltage ratio of 1:100.

commercially manufactured receivers. The most popular of these is the *bridged-T circuit*. Figs. 87 (a) and (b) illustrate two popular bridged-T networks. When the correct values of resistance, capacity and inductance are employed in either of the circuits a considerable amount of rejection is obtained, and it is possible for one circuit of this type to provide all the rejection needed in a vision i.f. strip. Usually, however, a bridged-T network is employed in combination with one of the more simple types of circuit shown in Fig. 86.

The sound rejection in a number of modern televisions is so sharp that the effect on the overall response is similar to that shown in Fig. 88. When this type of response is obtained it is desirable to adjust the fine tuner of the associated receiver such that the sound intermediate frequency falls into the centre of the rejection trough, or "dip," and not to either side. Failure to do this may cause sound interference on the picture.

When adjacent channel retractor circuits are fitted to a receiver these usually take up one of the simple forms illustrated in Fig. 86, because there is no necessity for as high a degree of rejection at this frequency as is required in the sound retractor circuits.

Finally, a minor point of terminology needs to be mentioned. In British literature, circuits of the type we have just discussed are normally referred to as sound or adjacent channel rejectors. In American literature such circuits are frequently called sound, or adjacent channel traps.

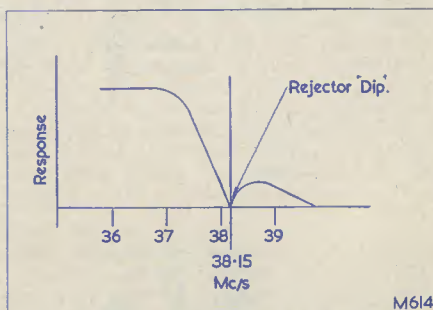


Fig. 88. If a network provides very sharp rejection, the overall i.f. response curve around 38.15 Mc/s may take up the shape shown here

Cross-Modulation

When two separate frequencies are handled by a single amplifier which introduces amplitude distortion,⁶ each of the frequencies is liable to modulate the other. This process is described as *cross-modulation*.

⁶ Amplitude, or non-linear, distortion occurs if different signal amplitudes are amplified unequally.

Cross-modulation can be very troublesome in vision i.f. amplifiers because its existence may allow the vision intermediate frequency to be modulated by the sound intermediate frequency, with the result that there is sound interference on the picture. Cross-modulation is liable to be particularly troublesome in the early stages of a vision i.f. amplifier because the sound i.f. may not be fully rejected at such stages. At the same time later stages, which handle larger signals, are more prone, in themselves, to amplitude distortion and hence cross-modulation. However, the risk of cross-modulation is less severe in later stages because adequate sound rejection in the early stages will, in normal designs, have been provided.

that, if the input signal is applied to a straight, or "linear" portion of the $I_a V_g$ curve, the anode signal will be similar in form to the input signal. If the signal is applied to a curved section of the $I_a V_g$ curve, the anode signal will be a distorted version of the input signal.

In order to obviate cross-modulation, the valves of a visual i.f. amplifier are normally biased so that the input signal is applied to a reasonably linear portion of their $I_a V_g$ curves. If the vision i.f. amplifier employs a.g.c., care is taken to ensure that at least the early valves of the amplifier do not receive bias voltages which would cause the input signal to be applied to badly curved sections of their $I_a V_g$ curves.

Fig. 89. The anode current-grid voltage curve of a typical i.f. amplifier valve. If the valve is biased at point A the input signal is applied to a relatively straight part of the curve, and the output waveform closely resembles the input. When the valve is biased at point B the input signal is applied to a noticeably non-linear part of the curve, with the result that the output waveform is a distorted copy of the input

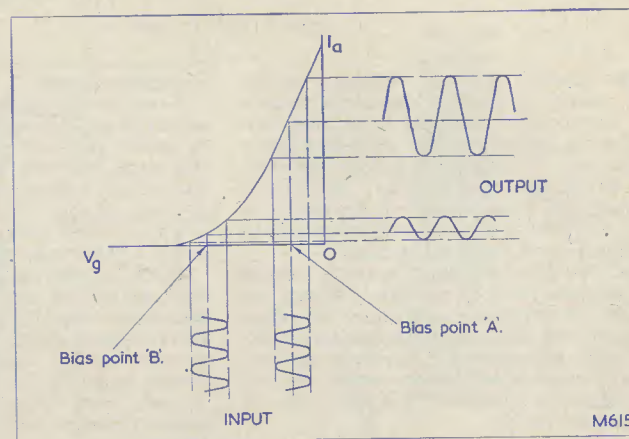


Fig. 89 illustrates the $I_a V_g$ curve of a typical i.f. amplifier valve. An input signal applied to the grid of the valve is reproduced by the anode in the form shown. The diagram should help to illustrate the fact

Next Month

In next month's article we shall continue to discuss the i.f. section of the television receiver.

Next Month . . .

Diomatic Frequency Controlled Switched FM Tuner

by P. C. MICHAEL

"Transistogram"—A Transistorised Portable Record Player

CRYSTAL STABILISATION for MODEL CONTROL

by F. G. RAYER

THE SIMPLE TYPE OF TUNABLE MODEL control transmitter can easily operate outside the permitted band, and harmonics can cause television interference over a wide area. Though such transmitters have the advantage of simplicity, economical running, and small size, there are occasions when a crystal controlled transmitter can be employed instead with advantage.

Such equipment cannot operate outside the permitted band, as wrong adjustment will prevent the transmitter operating. For short range, enough output can readily be achieved. The signal may also be used for the accurate calibration of a wavemeter, which in turn will allow a tunable transmitter to be adjusted correctly.

Surplus crystals are easily obtainable, and a frequency which falls within the permitted band, when multiplied by 2, 3 or 4, should be chosen. For example, a 9 Mc/s crystal, with a multiplier stage, will provide 27 Mc/s. Crystals requiring very much multiplication are best avoided.

The crystal forms the resonant part of the grid circuit, as in Fig. 1, and the valve commences to oscillate when L_1 is tuned to the same frequency. A simple capacity coupled stage provides multiplication. For a 9 Mc/s crystal, L_1 can thus tune to 9 Mc/s, and L_2 to 27 Mc/s.

With an active crystal, or fairly large h.t. voltage, direct multiplication may be achieved by tuning L_1 to a multiple of the crystal frequency. However, with some crystals oscillation will only arise when L_1 is tuned to the crystal frequency, especially in view of the fairly small h.t. voltage which may be convenient. For this reason, it is as well to limit multiplication to the following stage.


Resonance Check

A meter should be included in the h.t. supply to L_1 , or in series with the h.t. battery. A sudden drop in anode current, on tuning this stage, will then show that the valve has commenced to oscillate. A small power valve is most suitable. "All-dry" output tetrodes are satisfactory, and screen grid and anode may be wired together for triode operation.

The h.f. choke can often be omitted, but it increases output, and helps to assure oscillation with a small h.t. battery. Wiring should be reasonably short and direct. L_1 may be fixed, or can be wound upon a plug-in coil former, as in Fig. 4. For 9 Mc/s, 12 turns of 20 s.w.g. wire, occupying 1½ in on a 1½ in or similar diameter ribbed former, will be satisfactory.

L_2 will radiate sufficient r.f. to light a low-consumption bulb soldered to a 1-turn coil. After tuning L_1 for minimum h.t. current, it is thus only necessary to tune L_2 for maximum brightness of the bulb. An output on 27 Mc/s will then be obtained, provided L_2 and its associated condenser are so chosen that wrong multiples of the crystal frequency cannot be reached. Stray wiring, and the type of valve employed, exerts a fairly large influence on this stage, but 7 turns of 20 s.w.g. wire occupying 1 in winding space on a 1 in diameter ribbed former, as in Fig. 4, will usually be satisfactory.

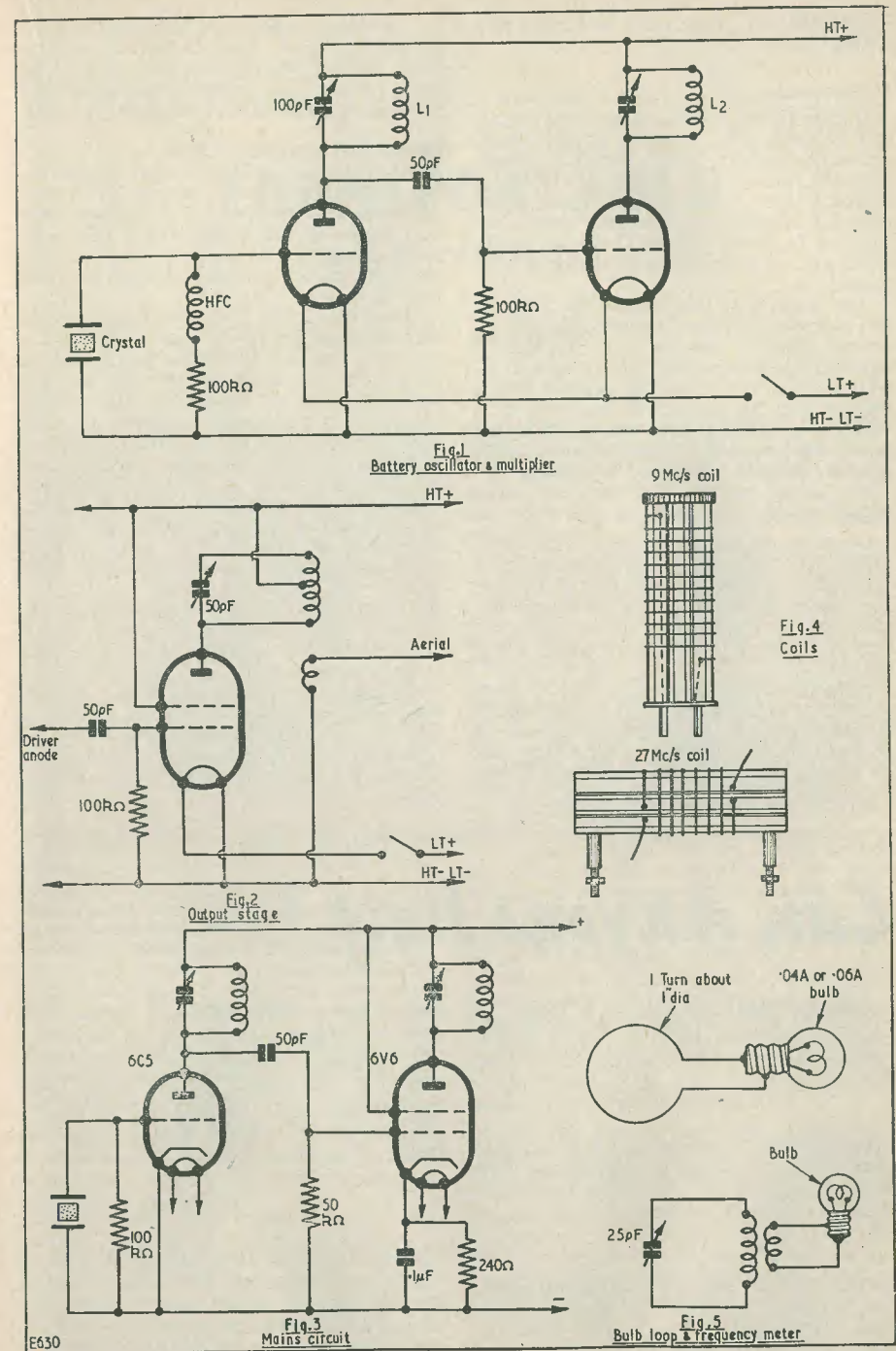If L_2 is not tuned correctly to 27 Mc/s, output drops, or ceases. With a 9 Mc/s crystal, no output would be obtained unless L_2 were tuned to 18 Mc/s or 36 Mc/s, instead of 27 Mc/s, and such a large error is extremely unlikely. This is quite unlike the results obtained with a self-energised tunable transmitter, which will radiate upon any frequency to which it is adjusted, so that operation just



outside the 27 Mc/s band is likely, with wrong tuning.

Output Stage

If more power is required, a power tetrode can be used. Fig. 2 shows a very simple circuit of this kind. With a large h.t. voltage, neutralisation may be required to prevent self-oscillation in this stage. This can be achieved by adding an extremely small fixed capacity from the grid to tank coil, in the usual way. A neutralising condenser is most suitable.

The aerial may be coupled by a 2-turn winding situated near the tank coil, or overwound upon it near the h.t. tapping. If required, efficiency can be increased by adding an h.f. choke in series with the 100kΩ resistor, and this can also be done in Fig. 1. When two anode circuits are tuned to the same frequency, a careful layout is necessary, to avoid stray coupling and oscillation.

Mains Circuits

Good results can be obtained with mains valves, and a mains operated transmitter is convenient for testing model control receivers and equipment at home. Such a transmitter may also be run from a 6V accumulator, with h.t. derived from a small rotary transformer.

A 2-valve circuit is shown in Fig. 3, which operates as already described, but with much increased power. Although bias would be obtained by grid rectification, cathode bias is provided for the 6V6, to avoid heavy currents when adjusting the tuning.

Coils have already been described, and are shown in Fig. 4. Smooth formers can be used, but will usually require a turn or so less. For the 27 Mc/s coil, a self-supporting winding, of 16 s.w.g. wire, is easily arranged.

Output and Frequency Check

Fig. 5 shows a bulb loop, used to tune the transmitter for maximum output. With low-power battery equipment, the loop has to be near the anode coil, in line with it. But with mains equipment, or higher power, the loop must not be too near the coil, or the bulb may blow.

When the crystal controlled transmitter is correctly tuned, it can be used to calibrate a frequency meter. The coil for this should have turns cemented in position, so that calibration is not lost, and the tuning condenser is fitted with a pointer or dial. Two turns of thin insulated wire, overwound upon the tuned winding, and also cemented in place, are taken to the bulb. Soldered connections are preferable to a bulb holder, as changing the bulb can slightly upset exact calibration. A 6V 0.3A bulb can be used for mains equipment, but a low consumption bulb is better for battery equipment.

The frequency meter is approached to the 27 Mc/s anode coil, and the meter tuning knob rotated for maximum glow. The exact resonant point is more accurately seen if the meter is kept at a sufficient distance, so that the bulb only just lights when tuning is correct. This calibration point may be used to adjust a tunable transmitter, in this case transmitter tuning being set for maximum glow.

Can Anyone Help?

Requests for information are inserted in this section free of charge, subject to space being available

Hallicrafter S38C Receiver.—P. J. Darke, of 5 Whalley Lane, Uplyme, Lyme Regis, Dorset, requires servicing data—all expenses paid.

* * *

"Hambander" Receiver.—J. Hibbard, of "Rose Cottage," Cat and Fiddle Lane, West Hallam, Nr. Derby, requires the circuit diagram or service sheet.

* * *

R1392 (95/155 Mc/s ex-Service Receiver).—P. Wright, of 111 Yew Tree Road, Birchencliffe, Huddersfield, W. Yorks, wishes to obtain the service manual.

Trans/Receiver RT34/APS-13.—J. Baldwin, of "The Dingle," Habberley Road, Bewdley, Worcestershire, asks for information in particular for details of the 7-pin plug connections. Any circuits lent will be returned and any expenses defrayed. Alternatively willing to purchase.

* * *

"Jason" Variable Tuned FM/VHF Tuner.—R. G. Hassler, of 30 Acheson Road, Birmingham 28, would be glad of any information that would enable him to fit a "Magic Eye" tuning indicator.

A Core-Tuned

TRANSPORTABLE

by A. S. CARPENTER

An unusual receiver, small in size and semi-portable

IT IS NOT USUAL, IN RECEIVERS COVERING the normal broadcast bands, to tune by means of a variable inductance tuner, but with the introduction of the Teletron FX25, self-tuned, dual-wave inductor (which made its debut in a transistorised circuit) such a method becomes possible. Experiments reveal that the unit can give an excellent performance when associated with valves, and the practical arrangement described here results in an efficient little receiver which is not expensive to construct.

Whilst aerial/earth sockets are provided it should not be thought that they are essential; in a great many locations the receiver will function admirably without either, as the inductor has been carefully positioned in order to obtain maximum self-pickup.

Care has been taken, too, to eliminate any possibility of the chassis becoming "live," and a negative bus-bar, to which the chassis is connected via a high voltage capacitor, makes it possible to ground the chassis in the usual way. No on/off switch is fitted to the prototype, in order to ensure that at all times when not in use the receiver is disconnected from the mains supply. In many cases this precaution might be considered unnecessary and a switch may be included, either in the flex input leads or incorporated in the regeneration/gain control. A switch of the double-pole variety must be used, however, whichever method is adopted.

As a slim construction was desired, the prototype chassis was made to order: bending one's own is not always a practical proposition when a perfectly symmetrical end-product is required!

The Circuit is shown in Fig. 1, where it can be seen that only two valves are employed, the first being used as a leaky-grid demodulator plus low frequency amplifier. Controlled regeneration assists the tuned circuit and greatly improves sensitivity, the particular mode of control being extremely docile in

operation. Feedback is obtained from the screen of V₁ and not from the anode.

Switching of the tuned circuit is ridiculously simple, the long-wave winding merely being shorted when medium-wave transmissions are required.


When the inductor is purchased a capacitor of 500pF will be found connected from tag 4 to tag 6, its purpose being to roughly tune both bands. In some cases it may be left *in situ* and will occupy the position C₄ occupies in the circuit diagram, so that the C₃ shown will not be required. The slight modification shown was made in order to obtain optimum results at the high frequency end of the medium-wave band as it was discovered that by cunning variations in the values of C₃, C₄, the output could be made to discriminate in favour of a particular section of either band.

The output stage and the power supply arrangements are conventional, the field winding of an energised type speaker being used as a smoothing choke. A permanent-magnet type may be used instead if desired, but a choke will then be needed.

Construction is not difficult, but to assist beginners both chassis drilling and point-to-point wiring diagrams are given (see Figs. 2, 3, 4, 7, 8). A simple L-shaped bracket needs to be made to hold the inductor and this is illustrated in Fig. 5—16 s.w.g. aluminium will be found suitable.

Once the chassis has been drilled the various components can be mounted, and to secure the speaker, a sheet of metal or plywood 6in square is recommended, the speaker being bolted to it after first cutting an aperture. The assembly may be bolted to the front flange of the chassis and held off by ½in spacers to avoid having to make a cut-out in the chassis itself.

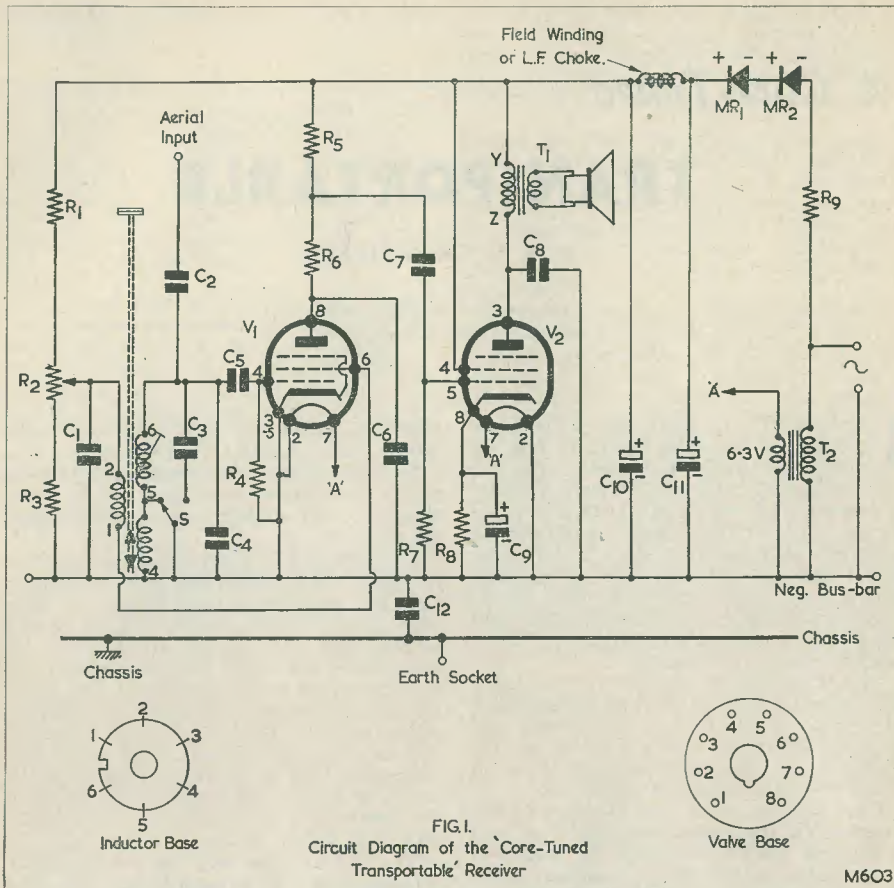All controls are placed at the side, and provided a cabinet not less than 9½in wide



M603

Capacitors

- C₁, C₇ 0.01μF
- C₂ 75pF
- C₃ 500pF (fitted to FX25—see text)
- C₄, C₅, C₆ 150pF
- C₈ 2,000pF
- C₉, C₁₀, C₁₁ 12+12+12μF electrolytic 350V

Resistors

- R₁, R₆ 47kΩ, 1-watt
- R₂ 10kΩ wirewound potentiometer (see text)
- R₃ 15kΩ, 1-watt
- R₄ 3.3MΩ
- R₅, R₇ 470kΩ
- R₈ 470Ω, 1-watt
- R₉ 100Ω, 1/4-watt

Valves

- V₁ 6SH7
- V₂ 6V6GT

Rectifiers MR₁₋₂

RM2 (2) or DRM2B (1) Brimar

Output Transformer

8,500Ω-3Ω

Inductor

Teletron, FX25

Speaker

5in energised (or see text)

Heater Transformer

230V input, 6.3V output at 1.5 amps.

Switch

Single pole, two-way

Chassis

8 1/4 in x 4 1/4 in x 1 1/2 in—Oliver & Randall Ltd., 53 Perry Hill, S.E.6

Miscellaneous

Aerial/earth socket, wire, solder tags, tagstrip—(6+1 earth), 3 control knobs, nuts, bolts, mains lead and 3-pin plug, bracket (see text), etc.

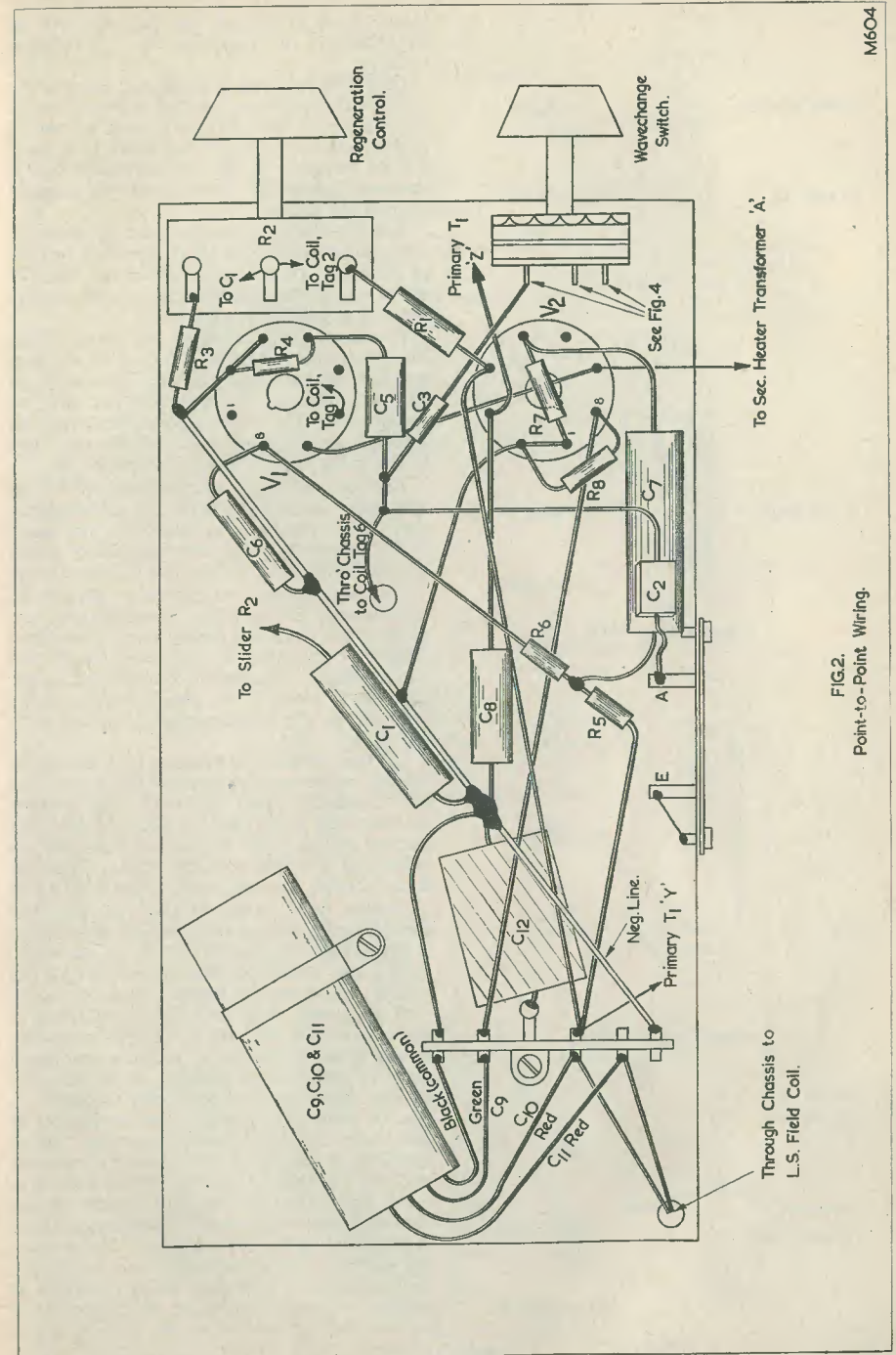


FIG. 2.
Point-to-Point Wiring.

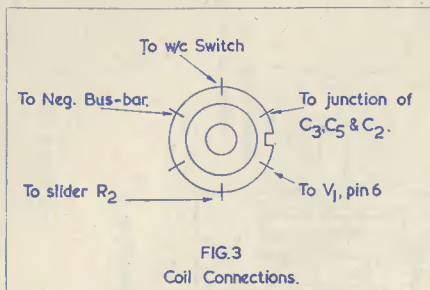


FIG. 3
Coil Connections.

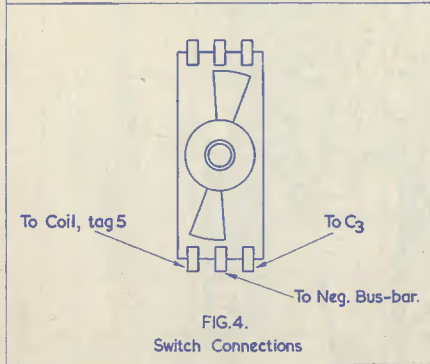


FIG. 4.
Switch Connections

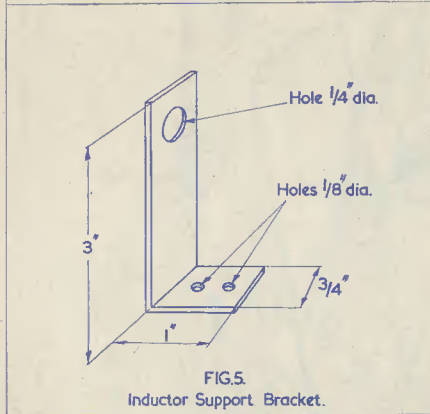


FIG. 5.
Inductor Support Bracket.

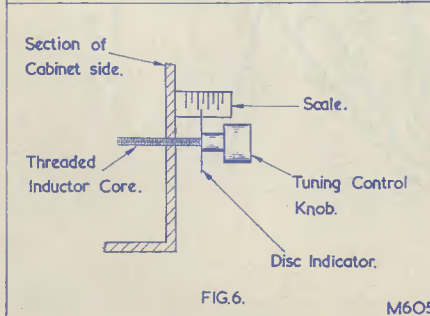


FIG. 6.
M605

internally is employed, no difficulty will be experienced in inserting the completed chassis.

Only one tag strip is used, and from a tag on this the negative bus-bar is run clear of the chassis in bare 22 s.w.g. wire across to pins 2 and 3, V_1 (pin 1 on this valve must not be included in the connection as this is the metallising pin). To this wire all negative returns are taken.

The electrolytic capacitors are all included in a single cardboard tube type but in case of difficulty, or for convenience, C_9 may be made a separate component, ample chassis mounting space being available.

Particular care should be taken when mounting the aerial/earth socket to see that no short-circuit exists between the aerial pin and the chassis. It is important, too, to ensure that C_2 is included, otherwise an external aerial plugged in will become live to the mains when the set is switched on.

Detailed wiring instructions are not necessary as the diagrams are self-explanatory: it is, however, advisable to use leads with differently coloured insulation when wiring the inductor to facilitate final checking.

On completion, no difficulty should be experienced in locating transmissions on either band when the tuning knob is manipulated. By adjusting R_2 , optimum results will be obtained. Reception should be crisp, clear and "beefy." R_2 should not be of the type where the spindle makes contact with the slider.

All that remains to be done is to house the chassis in the most attractive cabinet that one can construct, and as only the speaker occupies the front panel, a sheet of gold fret backed by plywood may cover this area, so achieving a contemporary style. Approximate internal dimensions are: 9 3/4 in x 5 in x 6 in.

Tuning scale. Due to the fact that the tuning knob spindle (with which is supplied a brass bush to enable fitting to be made with a 1/4 in knob aperture) screws in and out of the inductor, the normal type of tuning dial is useless. The total length of travel is approximately 1 in, and a suitable indicating device is shown in Fig. 6, where a graduated strip of celluloid or perspex is let into the cabinet side close to the control knob. A disc of white card glued to the inside edge of the knob acts as a rotating pointer. Alternatively, a length of 3/8 in diameter, wooden rod can be fixed to the end of the iron dust core and extended the full width of the cabinet so that it projects 1 1/4 in through a hole drilled for it in the opposite side. The projecting end may be painted white and graduated, the principle of operation being the same as before, viz, that its marked position relative to the cabinet indicates the desired transmission.

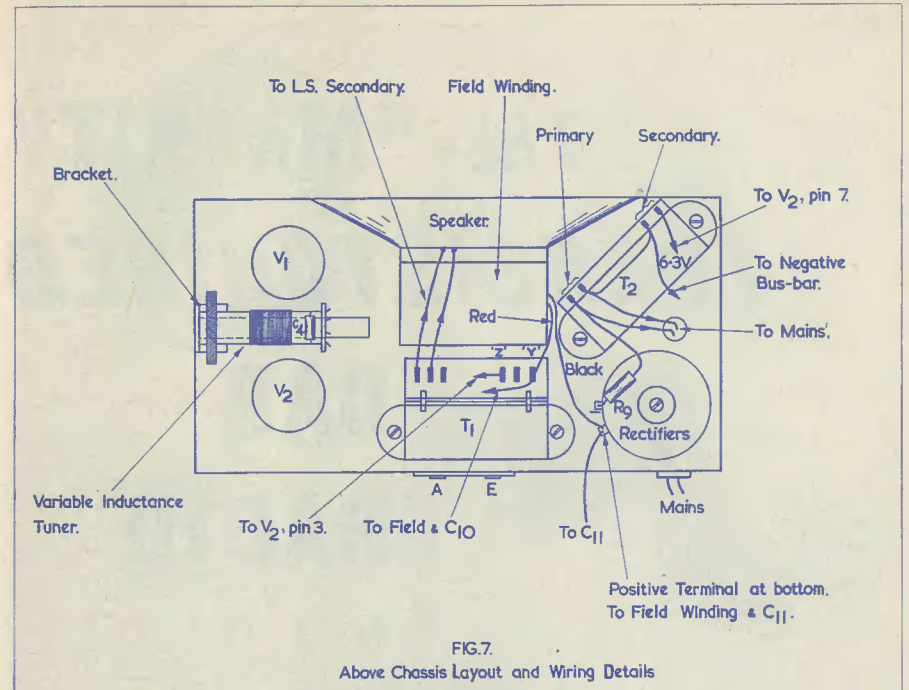


FIG. 7.
Above Chassis Layout and Wiring Details


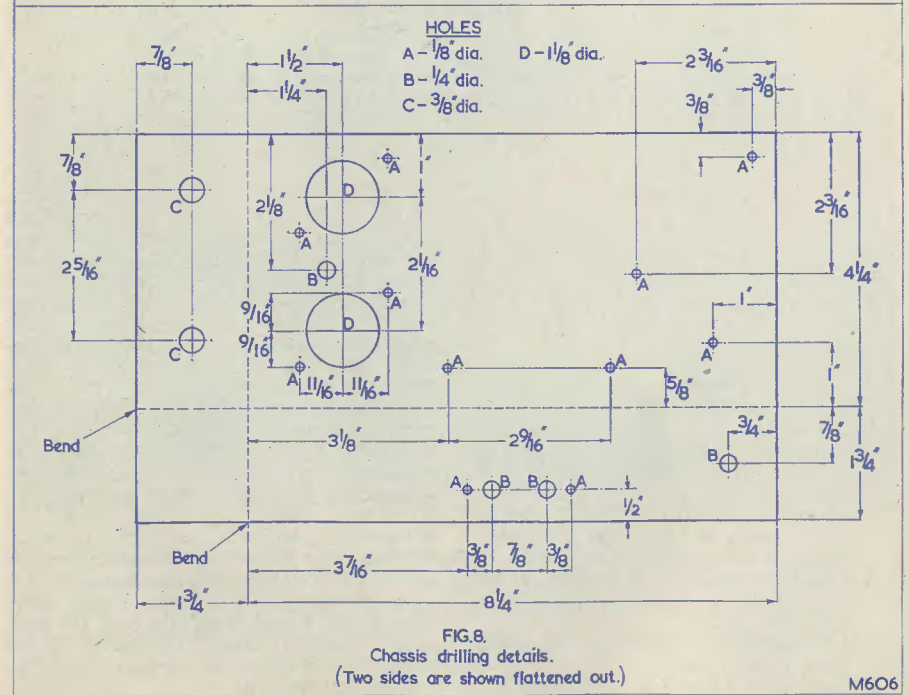


FIG. 8.
Chassis drilling details.
(Two sides are shown flattened out.)

M606

The "MAYKIT" TRANSISTORISED CAR RADIO

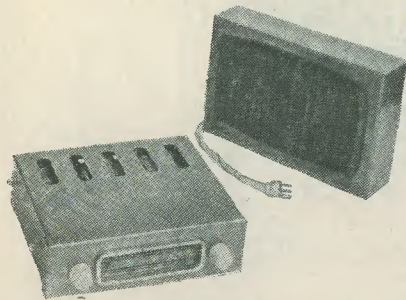

Part 1

by Richard Myers

This series describes fully a modern car radio design which may be built by any motorist—with or without experience of radio work—from the receipt of the components to the testing of the unit. Suggestions for car installation are included. The printed circuit and condensers are by T.C.C.

Test Report

Power supply voltage 14.4V d.c., gain control set to give an output of between 1 and 2 watts under strong signal conditions.

1. A.G.C. delay corresponds to 300mW.
2. With a.g.c. operative, a change of 40dB at the input gives a change of 3dB at the output.
3. Sensitivity figures at 640 kc/s, 2.5 microvolts for 100mW. At 1.43 Mc/s, 2.2 microvolts, 100mW.
4. *Signal-to-noise:* With a sensitivity of 2.7 microvolts at 640 kc/s, signal-to-noise is 20dB. At 1.43 Mc/s, sensitivity is 0.7 microvolts, signal-to-noise 20dB.
5. *Rejection:* At 640 kc/s, image rejection at 1.6 Mc/s is 60dB. At 1.43 Mc/s, image rejection at 2.4 Mc/s, 51dB.
6. *I.F. Rejection:* 200 kc/s is 39dB; at 640 kc/s, 10dB; at 1 Mc/s 38dB; and at 1.43 Mc/s 51dB.
7. *I.F. Sensitivity:* Input of 120 microvolts, 100mW out.
8. *Bandwidth:* 8.6 kc/s at 3dB points.

MANY PRESENT-DAY CAR OWNERS, whether brand new cars or not so new, aspire to the ownership of one of those "extras" so glibly advertised by the second-hand car marts! The "extra" referred to here is probably, after a heater-demister installation, the most important of the additional features among the whole bewildering host of extras currently being offered to the motorist.

The advantages of a car radio to the regular, or even the week-end motorist, are many—the most important being, apart from pride of ownership, the ability at will to keep in touch with events while on the road. Newscasts, sports events and results are among those which come readily to mind. Additionally, of course, the entertainment value—particularly to the passengers on that long journey—often appears to cut many miles off the route! Jocularly, even the most rabid "back-seat driver" is silenced by the lilting melodies often to be heard from the Continental stations!



Illustration showing Car Radio components as received. Top, left to right, speaker and output stage chassis with main chassis; power filter chassis, and front panel with outer receiver casing. Tuner unit, transformers and wires. Pre-packaged components for the various stages of assembly, etc. Valves, dial and printed circuit panel

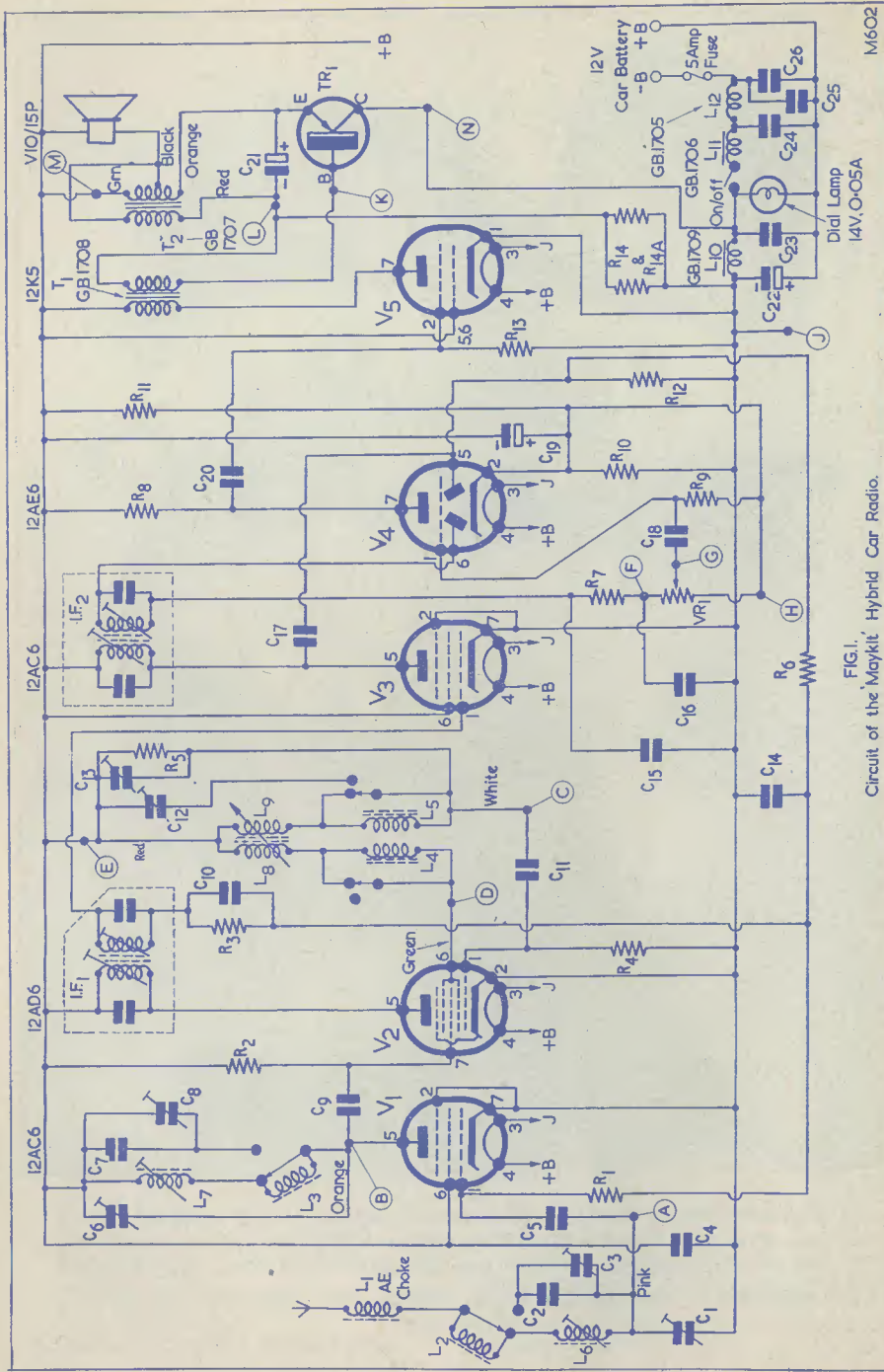


FIG. 1.
Circuit of the Maykit Hybrid Car Radio.

M602

COMPONENT LIST

Set out for easy reference to Fig. 1

Resistors

R1	2.2M Ω
R2	2.2M Ω
R3	2.2M Ω
R4	33k Ω
*R5	4.7k Ω (see text)
R6	3.3M Ω
R7	56k Ω
R8	330k Ω
R9	2.2M Ω
R10	10k Ω
R11	100k Ω
R12	2.2M Ω
R13	2.2M Ω
R14	470 Ω
R14a	470 Ω

Condensers

*C1	80pF trimmer
*C2	400pF
*C3	140pF trimmer
C4	0.05 μ F
C5	27pF
*C6	80pF trimmer
*C7	500pF
*C8	140pF trimmer
C9	220pF
C10	0.01 μ F
C11	27pF
*C12	140pF trimmer
*C13	80pF trimmer
C14	0.01 μ F
C15	100pF
C16	100pF
C17	30pF
C18	1,000pF

C19	25 μ F electrolytic
C20	10,000pF
C21	250 μ F electrolytic
C22	250 μ F electrolytic
C23	0.5 μ F
C24	0.5 μ F
C25	0.5 μ F
C26	3,300pF

Valves

V1	12AC6 Brimar
V2	12AD6 Brimar
V3	12AC6 Brimar
V4	12AE6 Brimar
V5	12K5 Brimar

Transistor

TR1 Newmarket V10/15P

Transformers and Chokes

T1	Driver trans: 80/30 Ω type GB1708
T2	Output trans: 30/30 Ω type GB1707
L10	L.F. choke, type GB1709
L11	R.F. choke, type GB1706
L12	R.F. choke, type GB1705 (Mayra Electronics Ltd.)

I.F. Transformers

Weyrad, type P40/1 (480 kc/s)
NOTE: Components marked * are part of the tuner unit.

Tuning Unit

MW/LW Car Radio (Mayra Electronics Ltd.)

Metalwork

Outer case, receiver chassis, filter box chassis, output stage chassis, front panel, chromium bezel, dial and drive assembly, etc. (Mayra Electronics Ltd.)

To construct the car radio about to be described, no special skill or equipment is required other than a small electric soldering iron, a medium and a small-sized screwdriver, a pair of cutters and pliers and a razor blade. The inclusion of a printed circuit ensures that assembly is kept at a minimum, and wiring errors hardly likely which, consequently, enables the results obtained to be very largely standardised from one receiver to another. The tuner unit is complete and pre-aligned, as are the i.f. transformers.

The new hybrid design uses five Brimar valves with transistor output, and the inclusion of an r.f. stage—no often found in car radios—ensures adequate volume level under all conditions. The receiver is for use with a 12 volt battery, with a consumption of only 1.5A. It is regretted that no 6 volt models are available. Two-knob control is a feature of the receiver, that shown on the left-hand side being on/off and volume, that on the right being both the wavechange and the manual tuning control. The wavechange (Long and Medium Wave), is effected by a pull-out mechanism. The radio outer metal case is of grey hammered steel, fully louvred for ventilation purposes, this having a standard size of 8in x 7in x 2½in to fit all modern cars.

The case itself contains the printed circuit and associated components, valves, tuner unit, and power supply filter box. The speaker and the transistor output stage are contained on a separate chassis, this stage being cable-connected to the receiver. Thus, the speaker unit is capable of being mounted, assembled as shown, at any suitable position at the front of the car according to the make and type or to the individual preference of the owner. Alternatively, of course, the actual output transistor, chassis, and associated components could be mounted in the front, i.e. under or behind the dashboard, and the speaker only, with a suitable metal grille or mesh, fitted at the rear of the car behind the back seat and under the rear window. In this latter instance, only the two speaker wires would have to be connected from the output transformer to the speaker—thus avoiding an unduly long inter-unit connecting cable.

As received, the components, any of which may be purchased separately, are as shown in the illustrations *except for the speaker cabinet*. In many types of cars this will not be required, it being shown here as an example for those who do require such a cabinet. The car radio supplier will, however, supply a very similar cabinet as an extra. A

adopt the method of assembly and construction described here, otherwise difficulty may be encountered at a later stage. The order and method has been carefully planned by the designers to ensure that no mistakes are made, no omissions possible, and no trouble experienced with the assembly and wiring. In addition to the foregoing, it is advisable for the constructor to open only those packets as stated in the order described. The remainder should be left sealed until they are required. In this manner, the motorist with no previous experience of radio will not tend to become confused with the various components required for each stage. Do not throw away the polythene packets, as some will be required later.

Step No. 1

Locate the printed circuit panel. Open packet No. 1 and identify the following components: R₁, R₂, R₃, R₉, R₁₂, R₁₃. All these have a value of 2.2MΩ (red, red, green). R₄—33kΩ (orange, orange, orange). R₆—3.3MΩ (orange, orange, green). R₇—56kΩ (green, blue, orange). R₈—330kΩ (orange, orange, yellow). R₁₀—10kΩ (brown, black, orange). R₁₁—100kΩ (brown, black, yellow). R₁₄ and R_{14a}—470Ω (yellow, violet, brown). Each individual resistor is marked with its appropriate circuit designation, i.e. R₁, R₂, etc. Two i.f. transformers (small metal cans marked "reg'd Design No. 884154"). One length of solder. Place these components on one side, open packet No. 2, and identify the following components: C₄, marked TCC 0.05μF type 346; C₅ and C₁₁, small white bodies marked 27±20%; C₉, small brown body marked 220; C₁₀, marked TCC 0.01μF type T383; C₁₄, marked TCC 0.01μF type T383; C₁₅, C₁₆, small white bodies marked 100±20%; C₁₇, small flat type marked 101 SMP 30pF ±20%; C₁₈, small white body marked 1000; C₂₀, lozenge shaped and marked TCC 10000pF CC1545. Five valveholders, four self-tapping screws and one transformer T₁ marked GB 1708.

Step No. 2

With the two packets now opened and the components identified, we now proceed to solder in position the components on the printed circuit panel, the copper connections of which are pre-fluxed.

Mount the valveholders into position first, and do this by pushing them firmly into position so that the tags are protruding through on the side with the shiny copper markings. Note here that any valveholder will fit into any of the five positions; it does not matter which one is fitted into any particular position.

Solder each valveholder into position on the circuit board in the order 1 to 5 and do

not forget to solder the central metal spigot. *The soldering should be done with a hot iron which must not be held on the printed circuit any longer than is necessary to make a good joint.*

Step No. 3

With each valveholder now fitted, proceed to solder into position each individual resistor. The positions for these are plainly marked on the circuit panel (see illustration). The best method of mounting the resistors, in order that no mistakes are made, is to first deal with R₁, R₂, R₃, R₉, R₁₂ and R₁₃, these all being 2.2 MΩ. The wires should be straightened, and then bent at right-angles to the resistor body, the wires then being inserted through the panel and soldered by the holes. With this completed, the surplus wire should then be removed with a pair of cutters. When soldering R₈ into position, note that the end wires, in this single instance, will have to be bent at right-angles at a greater distance from the component owing to the greater length of wire required to fit the resistor to the panel.

Again, when dealing with the remaining resistors, commence soldering the individual resistors in numerical order, i.e. from R₄ to R_{14a}. The missing resistor R₅ in the above sequence is to be found in packet No. 3, and will be dealt with at a later stage. Having dealt with the resistors, we now proceed to deal with the contents of packet No. 2, setting aside for the moment the i.f. transformers.

Step No. 4

Proceed to solder into position, in numerical order, the condensers contained in packet No. 2, commencing with C₄, which should be so positioned that the end marked with a black line is nearest to R₁. C₅, C₉, and C₁₁ may be mounted either way round. C₁₀ and C₁₄ should both be so positioned that the black mark is nearest to the space allocated to the first i.f. transformer (IFT₁ of Fig. 1). C₁₅ and C₁₆ may be mounted either way round, but note that C₁₅ does not make contact with the valveholder in any way. *Do NOT mount C₁₇ at this stage* but proceed to C₁₈, any way round, and C₂₀—but particularly note that the latter component must be mounted vertically.

Step No. 5

Having mounted all the condensers, except for C₁₇, proceed next to correctly position the i.f. transformers on the printed circuit panel. Note that either transformer will fit into the positions shown—it is not important which one is fitted to either position. Mount them so that the leads protrude through to the copper-plated side

of the printed panel, ensuring that the green spot on the base of the can is in the same corner as "G" shown on the panel. Bend over the two metal tags of the outer can and solder the i.f. leads into position, finally cutting off the surplus wire. With this completed, we can now solder into position the condenser C₁₇, this being so positioned that it is mounted vertically and *NOT* touching the metal casing of the i.f. transformer.

Step No. 6

The last component to mount on the panel is the transformer T₁ (marked GB 1708), from packet No. 2. It is only possible to

position this component the correct way round, there being three tags on one side and only two on the other, each corresponding to similar cut-outs on the printed panel. This transformer should be mounted on the same side of the panel as the other components.

Step No. 7

Bare both ends of three lengths of black p.v.c. wire, each about 1½ in long (it is only necessary to bare about ¼ in at each end), and solder one wire end to point K on the printed panel; the second wire end to point L and the third end to point M. The three free ends will be dealt with at a later stage.

(To be continued)

Book Reviews

RADIO TUBE VADE-MECUM (14th Edition). By P. H. Brans. 464 pages. Published by P. H. Brans Ltd., Antwerp. Distributed in England by Bailey Bros. & Swinfen Ltd., Hyde House, West Central Street, London, W.C.1. Price 32s.

There are hundreds of receiving and transmitting valves listed in the pages of this comprehensive data book. Valves made by most of the manufacturers in the world are to be found in the listings.

The various types are shown with those prefixed by figures first, in numerical order. Then follow types prefixed by letters, in alphabetical order. The data is presented over two pages at a time so that all details can be seen at a single opening of the book. The type number is followed by the name of the maker, the classification, then characteristics. A column then follows in which is given in abbreviated form the applications to which the valve can be put, together with some dynamic characteristics for those particular functions. The last column in the data gives a reference number for base details, which are separately tabulated at the end of the book.

A preface has been translated into eight languages. In this the use of the book is explained. Much of the information presented in the body of the data sheets is in abbreviated form. A very useful and convenient means of interpreting these conventions into understandable language is the book mark, which has printed on both sides all the abbreviations and their meanings. It is therefore possible to place this list at any opening of the book being studied, where it can be consulted immediately and without the inconvenience of having continually to turn to another page to interpret symbols.

Wherever possible direct equivalents for certain valve types are indicated in the tables. These identities refer to the similarities of electrical characteristics and operational data; where certain differences exist, these are indicated in the Addenda column. Large figures or letters on the page margins assist considerably in locating a particular valve quickly. In some instances this reference shows the first and last type listed on the page, and it is thought that this system could be used throughout the book to some advantage.

A GUIDE TO AMATEUR RADIO (7th Edition). Edited by Pat Hawker, G3VA. 72 pages, about 100 diagrams, tables and illustrations. Published by The Radio Society of Great Britain, New Ruskin House, 28/30 Little Russell Street, London, W.C.2. Price 3s. 6d., postage 6d.

This handbook should find considerable appeal among those seeking to learn the basic principles of amateur radio equipment, its operation and use, and the procedure adopted by amateur operators. Even while the writer had the review copy in his hands for scrutiny, a younger relative purloined it and is now in hot pursuit of the necessary qualifications to acquire a transmitting licence!

The Introduction sets out pretty nearly all the questions posed by those who ask what all this amateur radio business is concerned with, and gives lucid and informative answers. The chapter in Getting Started gives simple yet concise information on basic circuits for apparatus, characteristics of the amateur frequency bands, and station layout. A third chapter deals with the principles, design and operation of communications receivers, while the fourth chapter discusses the various parts of amateur transmitting equipment in some detail. Both these chapters have several sections dealing with particular aspects of the equipments being considered.

In the fifth chapter there is useful information concerning the Amateur (Sound) Licence, the conditions with which an applicant has to comply in order to obtain one, and suggestions on how he can study for the Radio Amateurs' Examination. The Syllabus for this examination is given, together with a typical examination paper set by the City and Guilds of London Institute.

The sixth chapter contains information useful to amateurs in operating their stations, such as the Q code, abbreviations commonly used in Morse code communications, country prefixes, and some hints and tips on DX operating. Finally, the seventh chapter tells of facilities and advantages in membership of the R.S.G.B. This handbook has been compiled by experienced amateurs and forms an excellent primer for the newcomer, who is sure to find in it much to interest him and whet his appetite for more knowledge and experience.

R.S.G.B. AMATEUR RADIO CALL BOOK (1959 Edition). Edited by John Clarricoats, O.B.E., G6CL. 72 pages. Published by The Radio Society of Great Britain, New Ruskin House, 28/30 Little Russell Street, London, W.C.2. Price 3s. 6d., postage 6d.

About 4,000 call-signs, names and addresses of amateur transmitting station operators in the British Isles are listed in the 57 pages forming the directory. The information contained therein is up-to-date at the time of going to press, and the publishers are provided with details of the Call Sign Records maintained by the G.P.O. to enable them to compile the published calls.

The book lists some 700 new call signs issued since the previous edition in 1957, in addition to which some 400 re-issued call signs have been included. Nearly 900 changes of address have been recorded and some 350 call signs cancelled. The /M (i.e. Sound (Mobile) licences) are no longer shown separately owing to the ever-increasing number of licensees availing themselves of this facility. The book also contains information concerning the aims and objects of the R.S.G.B., and full details of the QSL Bureau facilities available to members free of charge. An amateur transmitting station is hardly complete without a copy of this book on the operating desk, and one imagines that many short-wave listener stations would be similarly undressed in the absence of a copy.

W. E. THOMPSON

radio

miscellany

IT HAS COME AS QUITE A SURPRISE TO ME IN recent weeks to learn just how many of our fellow-hobbyists are garden-shedders. Well, at least they have the advantage of being able to work undisturbed and to be able to return next evening and find things just as they left them, even if there are difficulties about a garden shed which have to be ironed out. Previously, I have always thought that the styling of our particular dens as "shacks" was due to our self-effacing modesty, but that obviously wrong idea has now been somewhat revised. It is indeed often a pukka shack tucked away in an odd corner of the garden not wanted for anything else. Hence letters have continued to come in arising out of our earlier discussion on the subject of condensation. A reader has been good enough to send along a few tips on rust prevention and removal, gleaned from a recent article in the *Model Engineer*. The easiest way, apparently, to remove patches of rust from components and tools is to use one part of phosphoric acid to three parts of water. Application is best made by brushing, but care must be exercised not to get it on one's clothing. On the fingers no burns will result if they are rinsed in water soon after contact. The phosphoric acid, of a specific gravity 1.75, costs about two shillings a pint.

Incidentally, phosphoric acid is generally used industrially for de-rusting before painting, usually with a wetting agent. This treatment is widely adopted for the very excellent reason that there is little likelihood of rust re-forming on the metal underneath. Nor are the residues corrosive. For the protection of surfaces of tools, metal parts, etc., after cleaning, a solution of lanoline 30% to 70% by weight to white spirits is recommended. An adequate quantity for most purposes can be made up with 6 oz. anhydrous lanoline (costing about 1s. 3d.) added to one pint of turps substitute (white spirit). Dip the metal to be protected for about half a minute and allow to drain. The excess solvent will evaporate in a couple of hours leaving behind a protective film of lanoline.

Economy Corner

On the same subject, J.S. (Sidcup) says that his bedroom became so overcrowded with gear and tools he had to do something about an outside workshop as he had no further space to expand. So he sent for details to a firm who extensively advertise portable buildings. In due course he received a magnificent coloured catalogue and a book on greenhouse methods which he didn't want. The price list was on a little slip of paper in the bottom of the envelope—the whole lot costing 8d. postage. He says the catalogue was printed on super art paper and must have cost several shillings to print. When he studied the slip of paper containing the prices he nearly passed out, and decided it would be just about as cheap to move to a bigger house where he could have an indoor shack.

To cut a long story short, he eventually decided to build his own shed, although he had no previous experience of that sort of thing. He bought the timber and roofing felt from a big firm who delivered it to his doorstep, at a cost barely one-quarter of its prefabricated equivalent.

"And," he adds, "I have the door and windows just where I want them; not where somebody else decides to put them." He finishes up with a tip to others who might follow his example. "I made only one mistake which I might well mention for the benefit of others. Don't putty the glass in until you have finished painting the frames. I did, and all the putty fell off. It just doesn't cling to bare wood. It was a good job I used a few tacks, otherwise the glazing bill might have been doubled."

Another Tip

A further nice letter from our old friend L.H.B. (Abingdon, Berks) who, you will remember, has a daughter with ideas on escape routes for t.v. interference. By the way, many thanks, O.M., for Harwell House Magazine copies, safely received. He writes: "It is not generally realised by constructors

that a metal woodworkers' vice is often much more useful for radio work than the more usual engineers' vice. A 6-in carpenters' vice costs only 22s. 6d., and easily opens up to 5in, but one of the engineers' pattern with a comparable jaw capacity is a much more expensive item." He is right, too, although I cannot recall anybody drawing attention to it before. Worth bearing in mind by those newly starting off, or re-designing their workshops.

Incidentally, I recently added to my range of workshop "furniture." Treated myself to a ball-based vice which tilts to any angle up to 30 degrees in any direction. Can't say I have found any special use for it yet, but it's a nice sort of thing to have. Impresses visitors, too. Everybody who has come so far has played with it and adjusted it to all sorts of improbable angles. Then they ask the price and say "H'm." Next time I do the rounds I must see how many have bought one like it.

Hard Lines

In writing about the possible uses to which the vacant t.v. channels might be put, I

should be kept going for ten years. By that time our present sets will be so outdated that even the most parsimonious will have no cause for complaint.

Better Late than Never

Some years ago I wrote at length on what I thought to be a strange omission in all the American technical books I checked on—the absence of any mention of Oliver Heaviside. Within the Empire we perpetuate his memory by naming one of the ionized layers above the earth's atmosphere after him, in the same way we speak of the lower layer by calling it after Sir Edward Appleton. In the United States it is spoken of simply as an upper ionized layer and no credit is given to Heaviside.

Oliver Heaviside died at the age of 75 some 34 years ago, embittered and practically penniless, much of his work unpublished—and unpublicised. Recently, as the result of a close examination of many of his scribbled papers and formulae found long after his death, he has been proved to be an even greater original scientific thinker than previously believed. Perhaps with the full unravelling of his scientific notes he will

Centre Tap talks about items of general interest

mentioned a number of alternatives. One was to start 625-line transmissions to ease an export problem and at the same time enable an inexpensive (for viewers) gradual change-over as existing receivers become obsolete. J. A. C. (Gilda Crescent, Polegate) takes me to task over this, but I rather imagine his real idea is to provoke discussion. He says he recalls many technical writers advocating sticking to our 405 line system so convincingly that he has been won over to their way of thinking. He is satisfied, too, that B.B.C. transmission quality is good enough even for exhibition photographers, and hints that those who complain ought to look to their receivers!

I am afraid it is a bit too late to start an argument now, J.A.C. Since receiving your letter it seems that the Television Advisory Committee (set up to advise the Government on such points) suggest that we change over from our "old-fashioned" 405-line system to the international 625-line. They recommend that transmissions at the present standards

receive greater recognition here, and, at least, acknowledgment abroad.

How often in the history of scientific discovery have men with ideas a generation before their time been snubbed by their more orthodox contemporaries! Maybe today our attitude isn't always much more enlightened towards modern Heavisides.

I recall that when I wrote of the failure of American technicians to connect him in any way with the layer we name after him in the rest of the English-speaking world, I asked if any reader had found mention of the Heaviside Layer as such in an American work. No replies were received.

A good publicity agent seems to be a greater asset than a brilliant brain.

Unkind

Quote, from an amateur film critic: "Third rate? I'll say it was. Not even good enough for television."

Anyway, viewers, you will have to wait at least another twenty years before you see it.

JINGLEBELLS

AMATEUR RADIOTELETYPE

Part 2

By JIM HEPBURN, VE7KX

TO RECEIVE AN F.S.K. RADIOTELETYPE signal the receiver's beat frequency oscillator is turned on, the same as for C.W., and the receiver tuning adjusted to produce two audio tones from the RTTY signal representing the "space" and "mark" signals being transmitted alternately from the sending station. This has converted the F.S.K. signal to A.F.S.K., and in order to be compatible with audio frequencies adopted for amateur A.F.S.K. signals the receiver should be adjusted to give an audio signal of 2,975 c/s for the "space" frequency and 2,125 c/s for the "mark" frequency.

This two-toned audio signal must now be converted into d.c. pulses to operate the selector magnet in the teletype printer, and this is accomplished by the "converter" unit shown on the accompanying diagram, Fig. 2. In this converter the two audio signals are separated by tuned filters and rectified so that the 2,975 c/s signal applies a negative voltage and the 2,125 c/s audio a positive voltage to the grid of a d.c. amplifier stage, V_2 , which in turn drives the keyer stage V_3 . The input transformer T_1 is a midget 500 ohms line-to-voice coil transformer; this can be eliminated if it is desired to run the converter directly from the receiver speaker voice coil circuit, but as it will be necessary to make use of test equipment, audio oscillators and bandpass filters, etc., it is desirable to keep all station audio lines at 500 ohms impedance.

The transformers T_2 and T_3 are made up from high "Q" 88 millihenry toroids. These toroids are known locally (in Canada) as "load pot toroids" and are employed in vast quantities for telephone cable loading or "Pupin Coils." They are also available on the surplus market as the C-114 line loading coil having been used for army (U.S.) field telephone lines. These latter are encased in a small cast metal case and need to be depotted for this application. These coils have two windings which are connected in series to give

the 88 mH inductance. On each toroid a small link winding of six or four turns of small hook-up wire is added and these links are connected in series across the secondary winding of the input transformer T_1 . Link coupling is used in preference to capacity coupling to avoid stray capacities and possible resonances which might affect the tuning of these extremely high "Q" toroids. If these toroids are not available, small audio chokes of fractional henry inductance or the 500 ohms winding of midget speaker transformers may be substituted. However, these are very low "Q" inductances and it will be necessary to use several tuned stages in cascade, with probably additional amplification to achieve the selectivity of this simple toroid circuit.

The rectifier stage V_1 consists of a 12AU7 with the grid and anode of each section connected together to form diodes. A double diode such as the 6AL5 could also be used, but the 12AU7 was chosen to keep valve types to a minimum. The d.c. amplifier stage V_2 is one section of a 12AU7 and its anode supply is stabilised by an 8 μ F 150V condenser and two small neon bulbs in series. Condenser coupling is employed between the amplifier and keyer stages; this 0.5 μ F condenser should be of good quality and low leakage. The 6V6GT keyer stage V_3 has its screen voltage regulated at 60 volts by the 47k Ω screen resistor and another small neon bulb. The printer selector magnet is connected in series with the keyer tube anode and this coil is shunted with a 10k Ω 1-watt resistor to absorb transient surges created in the printer magnet coil. The keyer valve is normally conducting and the current through the printer magnet coil is adjusted to the required value (usually 30mA) by the adjustable 10k Ω 10-watt resistor. Should the printer be one that requires a 60mA coil current it will be necessary to add a second keyer valve in parallel and adjust resistor values and power supply requirements

accordingly. The cathode of the keyer valve is connected through the teletype machine keyboard contacts to ground. These contacts are normally closed and remain so during reception. The keyer valve is conducting during no-signal and space signal conditions; the positive mark pulse from the filter-rectifier stage is inverted by the d.c. amplifier and applied as a negative pulse to the grid of the keyer valve, cutting off the keyer valve and releasing the printer selector magnet.

Operation of the keyboard opens the cathode of the keyer valve, thus operating the printer for "local copy" from the keyboard.

valve and is subjected to full power supply voltage to ground. Should there be any doubt as to the insulation of the magnet windings, the magnet coil can be connected between the cathode and the keyboard contacts. However, this causes degenerative feedback into the grid of the keyer valve and pulse-shape distortion. If this circuit connection is used, the spare section of V_2 should be connected as a clamper diode between grid and ground of the keyer valve.

The only critical adjustment required to get this converter into operation is the tuning of the toroid filters. This requires a calibrated

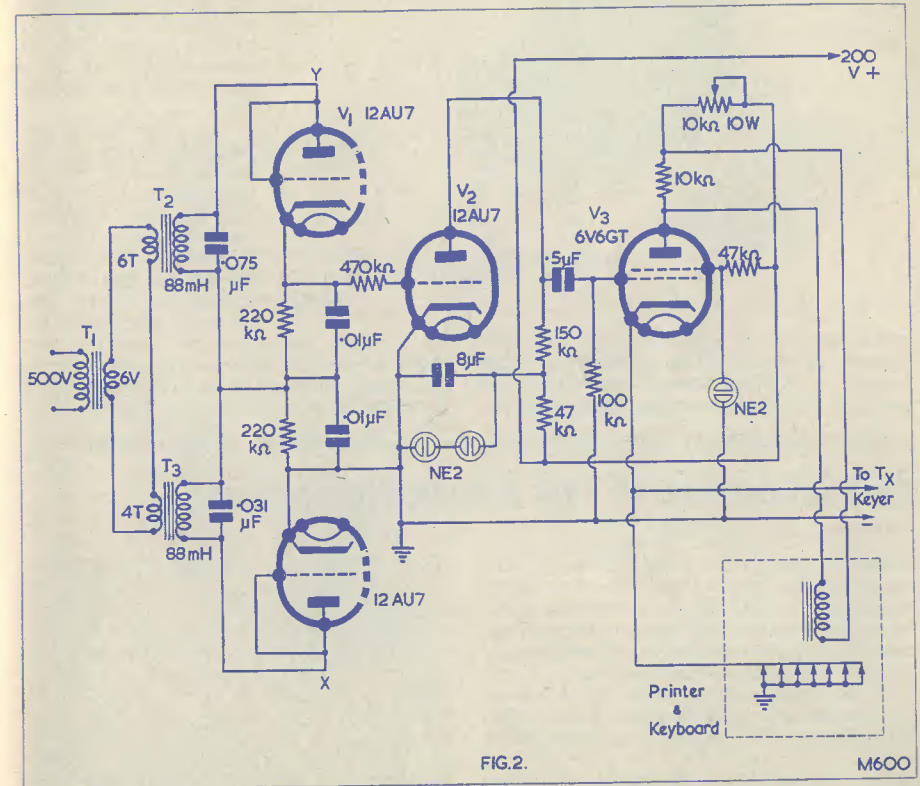


FIG. 2.

M600

The 60 volts regulated screen voltage appears across the keyboard contacts during this operation and a lead is brought out from the keyer valve cathode so that this keyed voltage can be used to control an RTTY radio transmitter. The receiver must be shut off or disconnected from the converter during transmission so that key clicks and noise will not feed through the converter and cause garbling.

In this circuit the printer magnet coil is connected in the anode circuit of the keyer

audio signal generator and either an oscilloscope or a valve voltmeter. Feeding the audio signal into the converter input and reading the d.c. voltage generated at the grid of V_2 , different values of condensers are connected across the tuned circuit until the frequency-voltage curve resembles that shown in Fig. 3. The ideal condition is when the positive and negative curves are the same height and cover equal areas, when random noise signals are balanced out and do not affect the keying. It may be necessary to adjust the number of link

turns and/or add shunt resistors to the tuned circuits to achieve a perfect balance. This detail is only required for weak signal work. On strong signals a five to one unbalance will still print perfect copy. An oscilloscope

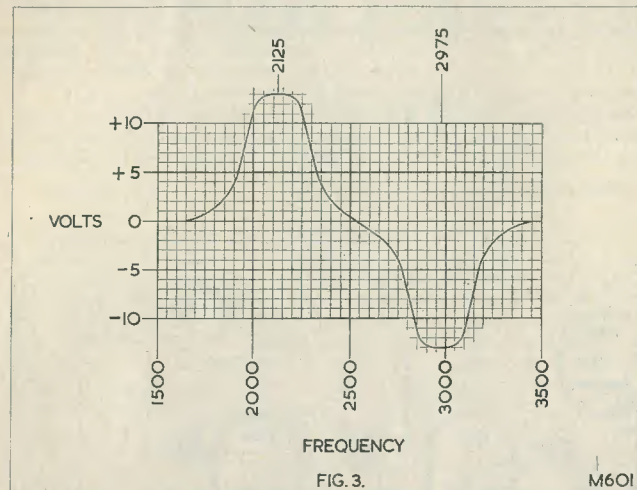


FIG. 3.

M6OI

makes an ideal indicator for tuning RTTY signals. Connect the horizontal input to the "space" or bottom anode of V_1 and the vertical input of the scope to the other anode

c/s. These dial divisions can be read to a tenth of a division, thus any audio frequency can be set up to an accuracy within three cycles.

An Explanation of Low Power Ultrasonics

—continued from page 626

tioned, and that is the successful use of ultrasonic soldering. Being able to solder aluminium in this way is extremely useful when it comes to repairing castings, and the aluminium speech coil wires of loudspeakers are also soldered by ultrasonics.

Before concluding, it might be as well to classify the generators available today. This is usually done by means of a small classified table.

As far as "Do-it-yourself" or home construction goes, it is inadvisable to think of building one's own equipment. A considerable amount of research has gone into achieving the present high standard of commercial equipment, and there is every indication that the prospects of being successful with a home-built equipment are remote. In the first place, a rather ambitious generator is necessary, giving 50-60 watts output as the minimum requirement. It is true that some public address amplifiers provide such an output quite easily and could be adapted to amplify the waves generated

from an oscillatory circuit. Provision can be made fairly easily for the polarising voltage for the transducer, but the story does not end there because one would have to consider the provision of the transducer for drilling which must be mounted on a suitable stand, or alternatively, a cleaning bath. It would be an interesting proposition which would open up a number of possibilities for the man with engineering and electrical instincts, and perhaps the day will come when some enterprising manufacturer will turn his thoughts to designing something in the nature of a kit partly assembled which will enable the average handyman to obtain the benefits of ultrasonic cleaning and drilling for jobs about the home or for his hobby.

In the meantime, there are efficient commercial equipments available to industry which are proving their worth every day in tackling problems which before use was made of ultrasonic waves were difficult, laborious, costly or even impossible.

of V_1 . A properly tuned space signal will show as a clean horizontal line and a mark signal as a clean vertical line, and a properly transmitted and tuned RTTY signal as a perfect right-angled cross. Any distortion, improper shift or incorrect tuning can be read off the scope pattern.

Power supply requirements for this converter are 50mA at 200 volts. Filtering and regulation are not critical; but this power supply should not be used for any other equipment, as the sharp massive pulses of the keyer output will affect any other gear drastically.


Very accurate audio frequencies can be obtained from a BC-221 frequency meter by beating its low frequency band against a 125 kc/s oscillator. On this band the BC-221 has a band-spread of forty dial divisions per thousand

MISCELLANEOUS

The AMPLIFONE

by

I. F. Gregory

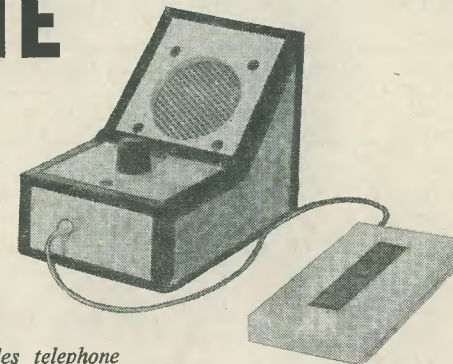

A neat and functional device which enables telephone conversations to be amplified and reproduced over a loudspeaker

IT IS A FUNDAMENTAL AXIOM OF MODERN living that, whilst the telephone has introduced many advantages and has resulted in considerable savings in time and energy, it has also been guilty of causing probably more general frustration and inconvenience than has any other electrical or electronic instrument. When it occurs, frustration is almost always due more to the human element than to the mechanics of the telephone itself, and it is probably at its worst when the telephone is employed for purposes of trade. A subscriber rings up a particular person at his place of business, only to be told by an impersonal operator that he must hang on until the required person has been found. After this initial contact, the process of hanging on may last for a few seconds only or it may extend to as long as ten minutes, during which time the caller is tied to his own telephone and is unable to take the receiver away from his ear in case he misses the person called up. Under these conditions it is impossible to concentrate fully on any other work. In addition, the vexations of hanging on frequently make themselves evident outside the realms of business, as many subscribers who have attempted to reach particular departments in large stores or other organisations will bear out. A typical instance occurs when the enquiry offices of some of the London railway stations are rung up, the state of affairs here having been sufficiently bad in the past to

cause letters of complaint to appear in such newspapers as *The Sunday Times*.

The inconvenience given by the telephone becomes very apparent when long conversations take place. The necessity of keeping the receiver held to one's ear means that a single hand only is free for purposes of making any notes that may be required.

The "Amplifone" overcomes these disadvantages at one step, this being due to the fact that it enables telephone conversations to be reproduced at loudspeaker level. In consequence, any subscriber who is told to hang on has merely to switch on his "Amplifone," whereupon he can place his receiver down on the table and concentrate on any other jobs he wishes to handle. As soon as the required person is found, the caller will be advised over the "Amplifone" loudspeaker. Similarly, when long conversations take place, it is necessary merely to turn on the "Amplifone" whereupon all information may be heard at comfortable level, both of the subscriber's hands being free for any action that may be desired. With the aid of the "Amplifone" it is in many cases possible to hold two-way conversations without the necessity of handling the handset at all. The telephone microphone is sensitive enough to pick up speech when it is quite some way away from the speaker's mouth and it may be kept in this position for, at least, local calls.

The "Amplifone" Circuit

An amplifying device of the type we are concerned with here has, apart from such obvious features as those of providing adequate volume and acceptable fidelity, to meet two special requirements. The first of these is that it must be capable of being brought into use at a moment's notice. This point makes it undesirable to employ an amplifier having mains valves because of the necessity of waiting for these to warm up after the amplifier has been switched on. A possible solution, that of keeping the mains

valve heaters supplied all the time and switching on h.t. only when the amplifier is required, is rather clumsy and wasteful of power. A battery-powered amplifier provides a much more attractive possibility; and battery costs can be kept to a very low level by the use of transistors. The "Amplifone" employs four readily obtainable transistors, these being powered by a 6-volt battery.

The second requirement of a telephone amplifying device is that no connections must be made directly to G.P.O. lines. This point is met in the "Amplifone" by the aid of a

special pick-up coil which is held close to the base of the telephone instrument, an inductive coupling being obtained with the transformer which is fitted therein.

The circuit of the "Amplifone" amplifier appears in Fig. 1. As may be seen, this consists of a conventional four-transistor amplifier whose input terminals are fed by the pick-up coil, and whose output connects to a 3 ohm loudspeaker. The first two transistors, TR₁ and TR₂, operate in earthed

that, once the volume control has been set to the level required by the user, it does not need to be adjusted further. Whether or not the volume control is combined with the on-off switch is left to the choice of the individual constructor.

Transistor TR₂ drives the two output transistors in a normal push-pull stage, adequate volume being provided for normal purposes. The two transformers T₁ and T₂ are miniature components and they are specified in the

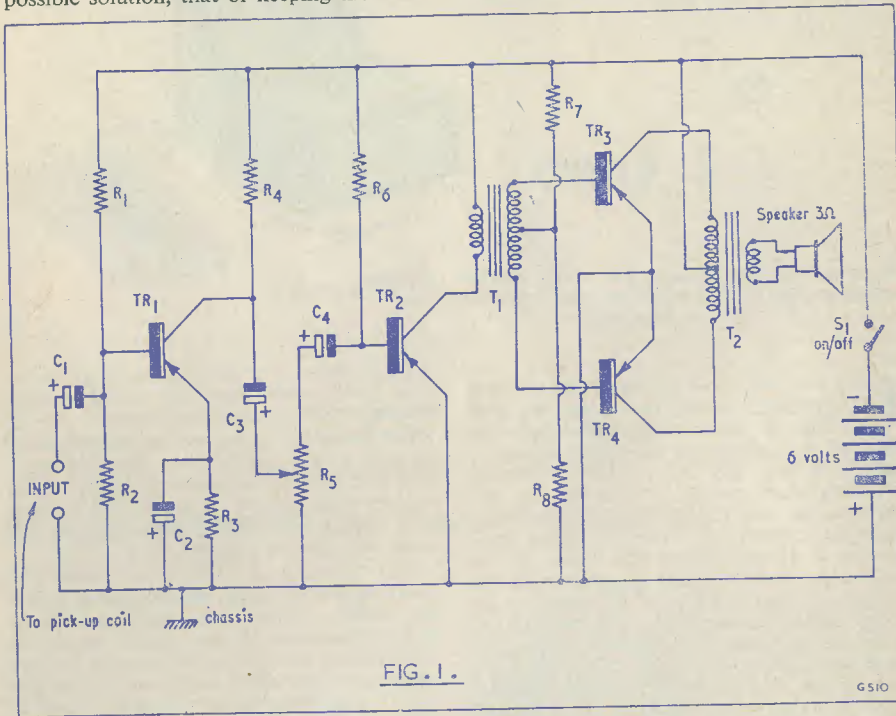


Fig. 1. The circuit of the "Amplifone" amplifier

Components List

Resistors

R ₁	47kΩ
R ₂	10kΩ
R ₃	470Ω
R ₄	2.7kΩ
R ₅	5 or 10kΩ potentiometer
R ₆	22kΩ
R ₇	4.5kΩ
R ₈	180Ω

Condensers

C₁, 2, 3, 4, 5 8μF 6 v.v. electrolytic

Transistors

TR₁, 2, 3, 4 "Red Spot," p-n-p, junction transistors

Transformers

T₁ Ardente, type T131
T₂ Ardente, type T132

Switches

S₁ On-Off, s.p.s.t. (May be combined with R₅, if desired.)

Speaker

Impedance - 3Ω

Battery

6V Type to suit individual amplifier cabinet layout.

Pick-Up Coil

As described in the text

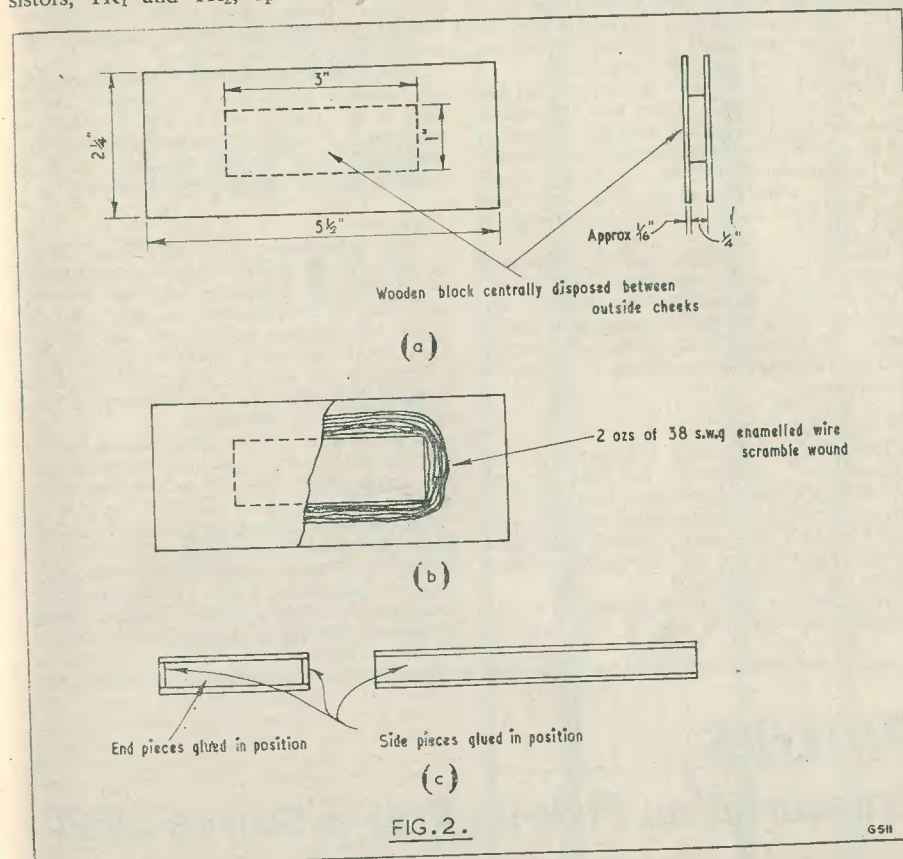


Fig. 2. The assembly of the pick-up coil. This consists basically of a 3 x 1 x 1/4 in wooden block to which are fixed two rectangular cheeks (a) The coil is then wound on the central wooden block (b) after which two end pieces and two side pieces are glued into position (c)

emitter stages, a volume control, R₅, being inserted between them. According to individual choice, R₅ may be combined with the on-off switch S₁, or it may be separate. The first alternative is worth consideration insofar that it allows a single panel control to be fitted; whilst the second gives the advantage

parts list by manufacturer and type number. The remaining part of the amplifier circuit proper consists of the speaker and battery. The pick-up coil does not form part of the amplifier unit, it being connected externally via a length of flexible two-way cable.

Due to the few components required in the

amplifier section, together with their small size, it is possible to make this part of the "Amplifone" very neat and compact. A photograph of the housing employed by the designer accompanies this article and gives an idea of the dimensions required. It should be pointed out that the amplifier fitted in this particular housing was laid out very comfortably with no emphasis on saving space, and that a significantly smaller cabinet could be used, should this be desired. The speaker employed in the designer's prototype is a 2½ in unit, and the power is provided by four U.16 "pen-type" cells connected in series-parallel to give a potential of 6 volts.

From the point of view of construction and layout, the amplifier offers few difficulties. The first transistor stage should, preferably, be mounted at the opposite end of the chassis (or component board) to the output stage. If the two transformers are fitted very close together they should be at right-angles to each other.

The pick-up coil can, most conveniently, be connected to the amplifier via a socket fitted to one of the walls of the cabinet. The designer used a miniature hearing-aid socket here. The length of lead between the pick-up coil and the amplifier may be left to individual preference.

The Pick-Up Coil

Due to the low input impedance of the "Amplifone" amplifier, the pick-up coil differs somewhat from the type of coil encountered with tape recorders and the like. The coil may be made at home with little trouble as there are no very critical points which have to be satisfied.

The pick-up coil is constructed in the manner illustrated in Fig. 2. As will be

noted, it consists basically of a wooden block to which are fitted two side cheeks. The latter should have a thickness of approximately ¼ in and may consist of wood or any suitable insulating material such as Perspex or Paxolin. The coil is wound on the central wooden block, after which side and end pieces are glued into position as shown in the diagram, giving a final "solid" effect. A hole may be made at one end of the assembly to take the lead-out cable, connections to the coil ends being made inside. The outer surface of the assembled coil unit may then be cleaned up as required.

The coil itself is simple to wind, it consisting of 2 ounces of 38 s.w.g. enamelled copper wire fitted as illustrated in Fig. 2. There is no need to count the number of turns provided that the correct weight of wire is employed. The coil is scramble-wound.

Operation

After completion, the "Amplifone" needs to be fitted up to the telephone instrument with which it is to be used. All that is necessary here is to switch on the amplifier and apply the pick-up coil to the base of the instrument, leaving it finally at the position which provides greatest pick-up of telephone speech. Coil positioning is liable to vary for different types of telephone.


It is possible in some cases that, at the full volume setting, feedback may occur between the loudspeaker and the telephone microphone. This will most probably occur if the "Amplifone" loudspeaker is directed towards the telephone microphone. The solution consists of orientating the loudspeaker. The final volume setting for the "Amplifone" amplifier is that which gives adequate output at normal telephone speech levels.

MAKING A GLASS STATION DIAL

by B. B. Rafter

MOST READERS WILL BE FAMILIAR WITH the Panel-Signs sets of transfers issued by the publishers of this magazine and designed to give a professional finish to the visible parts of home-constructed equipment. Many may not yet have realised the value of the fairly recent additions to Sets 3 and 4, the lists of names of the main Long, Medium and Short Wave stations to be found on the average dial plate. Indeed, the writer himself had not seen their possibilities until a friendly hint from the Editor in response to a desperate appeal got him out of a very awkward situation indeed.

It was the usual story; not leaving well alone. Some very extensive repairs had been carried out to modernise an "old-timer" for an elderly lady who couldn't bear to part with what had been her wedding present, an H.M.V. Model 486. As the rehabilitated warts poured over the bench, it seemed a good time to remove some of the dust and stains of the years from the glass station-dial, which had never been touched since the day it was fitted. Out it came, and into a bowl of tepid suds, just to ease the pain. Time for a few adjustments to the set, then out of the suds with the dial, a quick rub with a clean cloth and . . . large swathes of the pre-Copenhagen

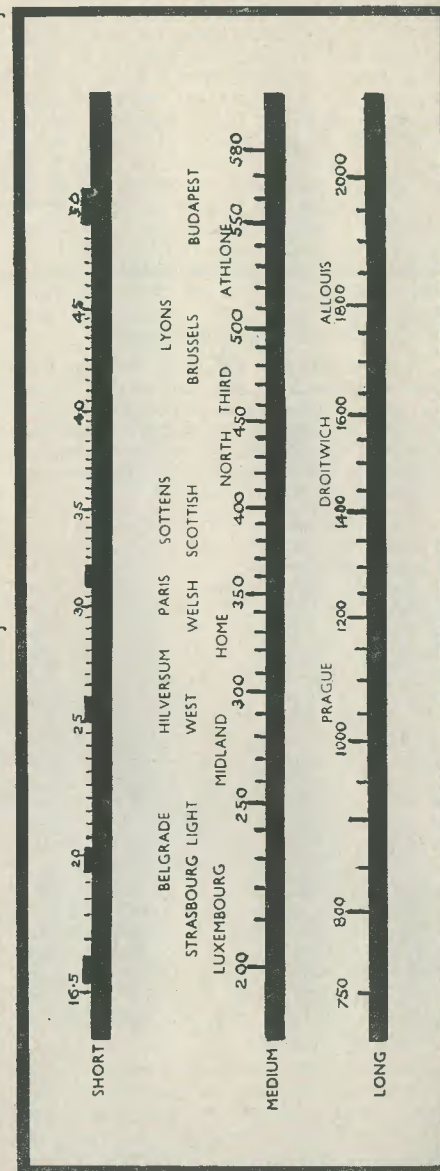

names and wavelengths came away on the cloth! Disaster!!

There was no returning the set to the owner with its dial in that condition. The makers, when approached, had, of course, run out

PHILIPS Transcription Pick-up Arm & Stereo Head

Philips Electrical Ltd. have introduced a Transcription Pick-up Arm (Type NG5400/S) fitted with a pick-up head (Type AG3060) which is designed for reproduction of stereophonic as well as monaural long-playing records. Arm and head complete sell at 15½ gns. (List £11 15s. plus P.T. £4 10s. 6d.).

The precision-engineered arm, well known for its association with the Philips magnetodynamic pick-up head, is professional in appearance, with a durable satin chrome finish. It is equipped with a micrometer

playing weight adjustment, and the arm pedestal and rest are adjustable in height so that the pick-up can be used with any separate turntable.

Close attention has been paid to the matter of minimising resonance and friction.

The crystal pick-up head has a diamond stylus and a frequency response of 30–12,000 c.p.s. The recommended load resistance for each channel is 500kΩ, and the output is approximately 0.5 volt for each channel. Suggested playing weight is 4–6 grams.

of spares before Hitler ran into Austria, where the original plates were made, being a sort of transfer on glass, station names in black on a white frosted background, with slots at the appropriate places for viewing the pointer. Restoration of the original in anything like its previous form seemed impossible, as did various other solutions that sprang to mind for either finding a three-wavelength glass dial of the same size (12½ in x 3½ in) with a pointer travel of exactly 8½ in, which nobody seemed to stock; or for changing the pointer travel to fit a substitute of reduced dimensions. The latter would have got us inextricably trapped in the higher maths, since the early H.M.V. lines used a sturdy gearbox on their reduction drives and it was not a question of just changing one drive drum for another.

Near-despair was finally relieved by the above-mentioned friendly hint by the Editor, who once, it seems, hand-painted his way out of a jam like this by the use of a technique known to the limners of mediaeval manuscripts! But that was before the days of Panel-Signs!!

A few experiments with some of the titles from Set No. 4 showed that admirable prints of bold black lettering about ⅜ in high could be made on glass, to show up extremely well against a background of white paper lit from behind. The following method was then adopted to produce a substitute for the wrecked scale. A piece of picture glass was cut to the same size as the original, together with a piece of good quality, translucent writing paper, same dimensions. In this paper were then cut, with a razor blade, three slots ½ in wide by 8½ in long, one above the other, spaced as in the original, to provide the wavelength scale behind which the pointer would be seen to travel along. Fortunately there was enough detail left along the original slots to enable it to be used as a template, so the paper mask was laid over it, slots coinciding, and the wavelength scale was marked in indian ink along the edge of each slot, Short Wave at the top, Medium below and Long at the bottom. The more neatly this was done, of course, the better the final job would look.

The next stage was to fix the paper wave scale behind the glass. A first attempt was made to do this merely by sticking it at the ends with Sellotape. Pasting or glueing to the glass was not possible, since the scale was to be lit from the back and perfect translucency would be spoiled. Owing, however, to varying conditions of humidity, it was found that the Sellotape was not sufficient to maintain a tension which would keep the paper scale flat against the glass at all times,

so another identical sheet of picture glass was cut and the paper scale fixed dead flat by sandwiching between the two glass plates bound together by Sellotape.

It remained to start printing the station names in neat groupings on the top of the glass above the appropriate wave scales. There were no Short Wave stations named on the original, thank the powers, so there remained the Long, which it was decided to cut down to three (Prague, Droitwich, Allouis) and the Medium band. Here, as no attempt was to be made to cut tiny slots under each name, as in the original, the names had to be placed with their centres corresponding approximately to the reading in metres on the scale below. A list was made of all the principal British Medium Wave stations, with wavelengths from Third (463) to Light (247) and a choice of the four best for this area (Third, North, Home, Midland) was made, these names to be placed lowest, that is just above the wave scale, for ease of reference.

The actual process of printing these transfers was incredibly simple, with results the writer would never have believed possible. The backing paper was removed from the complete sheet and each name cut out from the transparency as required, trailed across the surface of a saucer of clean water with a pair of stamp tweezers and placed in position on the glass above the proper section of the wave scale. Linearity was checked with a ruler after positioning, the tissue gently padded with a piece of blotting paper and left to dry. After this other names were added at each end of the bottom line (Athlone, at the right, Luxembourg at the left, then another line was begun, above the first and slightly staggered to the right (Brussels, Welsh, West, Light) and finally, above these a row of foreigners (Lyons, Sottens, Paris, Hilversum, Belgrade). This set of fifteen names very conveniently filled the space available and gave a useful choice and neat display, completed by the words Short, Medium and Long at the left-hand end of the wave-scale slots.

When all the transfers were dry, the tissue was slightly dampened with a cloth and peeled off with tweezers, to reveal a most satisfactory print. A little cleaning away of surplus gum and, when all was bone dry, a coat of transfer fixing varnish over the names completed the job, which, when fitted into the set, gave a smart, clean dial, perfectly adequate for all normal domestic requirements.

This method of making a station dial could be adapted to almost any home-constructed set, with most pleasing results.

A Battery Power Unit

by J. HILLMAN

THIS UNIT WILL SUPPLY BOTH L.T. AND H.T. for most battery sets, and provides a convenient source of supply for servicing these sets. It consists of two units, the main unit having the controls on it, and a plug-in unit with a flexible lead having various sockets on it to suit the different types of battery plugs. The off-load voltages are: L.T., variable from 0 to 7.5V.; H.T.₁, variable from 0V to 250V; H.T.₂, variable from 110V to 250V. With controls at maximum, on-load voltages are L.T. 3V at 1 amp; 7V at 100mA; H.T.₁ and H.T.₂ 250V at 80mA. The H.T.₂ variable control is rated at 3 watts and up to 15mA can be safely taken through it, whilst the H.T.₁ variable control is rated at 1 watt and up to 5mA can pass through it. For test purposes these figures can be exceeded, but not if the unit is to be kept on for very long.

Construction

First mark out the chassis in aluminium as Fig. 1 and bend the ½ in edges up at right-angles to form a shallow box. Drill ⅜ in holes at corners and secure with 6BA nuts and screws. Next cut out the panel as in Fig. 2 and bend up the ½ in edges at right-angles, then drill holes as marked out in Fig. 4. Now fix the panel to the chassis as in Fig. 5 and assemble components as in Figs. 7 and 8. Next fit components to switch block as in Fig. 10. For the wander plug sockets use plain sockets and drill ⅜ in holes; for the OBA terminals drill ⅜ in holes, and for the flexible lead drill a ⅜ in hole.

Wiring

Wire up as in Fig. 9, using stranded wire to cut down voltage drop in leads. For the flexible lead use 4ft lengths of 23/36 single rubber flex; five lengths are required, and

after connecting them to the various sockets on the switch block twist them together one by one to get a smooth cable, and finish off with a turn of insulating tape, finally soldering them to the valve plug as in Fig. 10.

Meter

The meter used had an F.S.D. of 500µA, with a resistance of 500 ohms; and the values of series resistors are as shown in Fig. 9. A 1mA meter may be used, but in that case the series resistors will be different and for a 100 ohm resistance meter the values will be: 3V range, 2,900 ohms; 15V range, 14,900 ohms (a 15kΩ will do); 150V range, 150kΩ; 300V range, 300kΩ. Meters having a greater full-scale deflection than 1mA may be used but will increase the consumption of the unit and will therefore lower the voltages which the unit will supply. The meter should be checked against a standard one if possible, as its accuracy is important to ensure that the sets are not over-run, especially on the l.t. ranges. If no meter is available to check against, then the meter can be checked against a freshly charged accumulator which has been allowed to stand off charge for several hours and which should read 2.2V.

The meter resistors are made up from standard 10% tolerance ones; the 5.17kΩ being made up of 4.7kΩ and 470Ω in series; the 278.2kΩ one is made up of 270kΩ and 8.2kΩ in series; whilst the 526kΩ one is made up of 470kΩ and 56kΩ in series.

The flexible lead plug is made from an old 5-pin valve. Wrap a cloth around the valve and break it with a hammer, remove all the broken glass and scrape out the old cement with a knife, and then apply a hot soldering iron to the tip of one pin and pull out the old wire from inside with a pair of pliers. The new lead can be threaded down inside

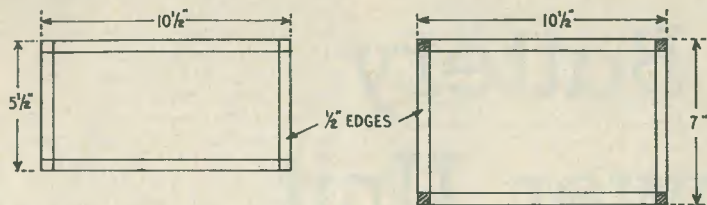


FIG. 1

FIG. 2

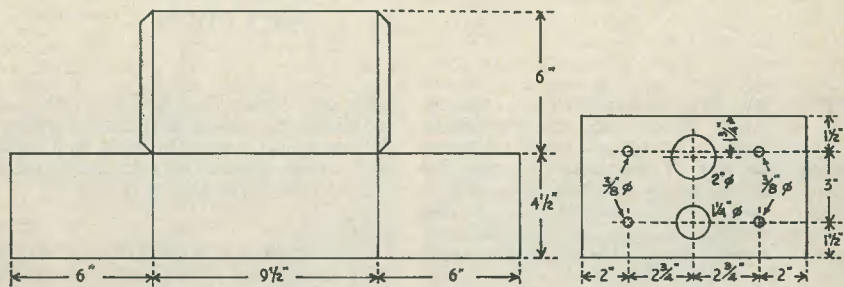


FIG. 3

FIG. 4

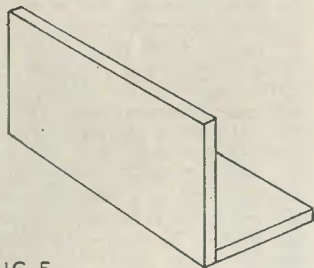


FIG. 5

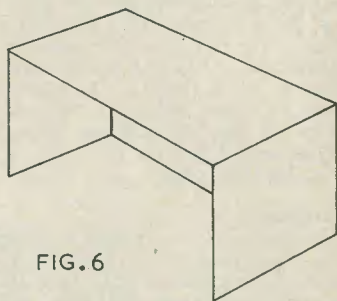


FIG. 6

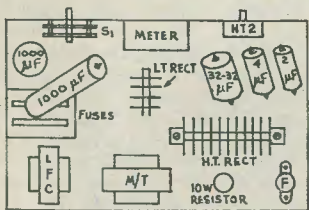


FIG. 7

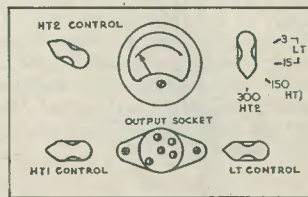


FIG. 8

G624

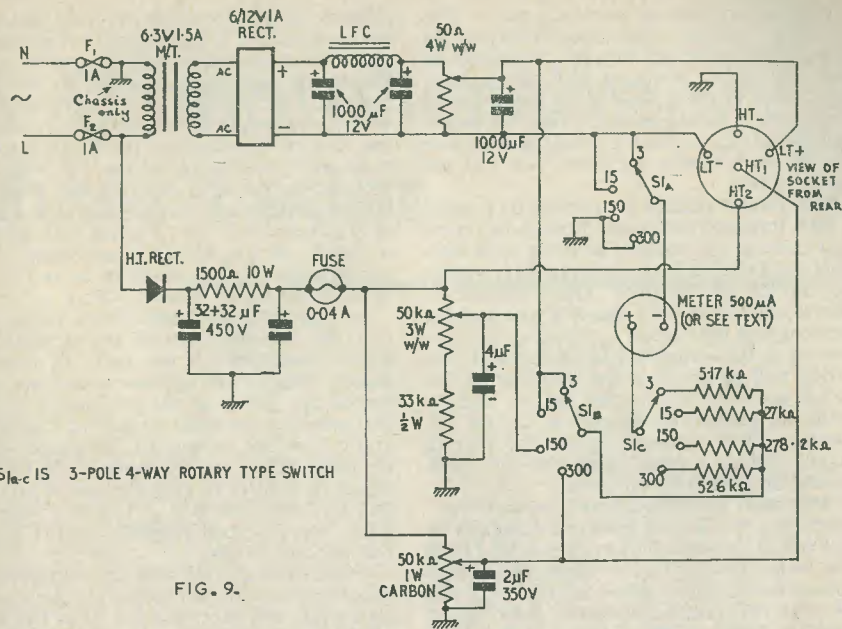


FIG. 9.

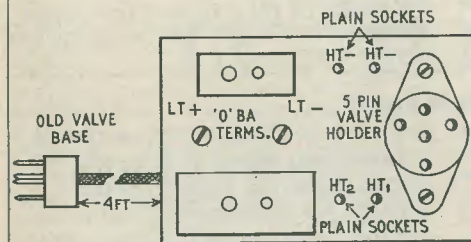


FIG. 10

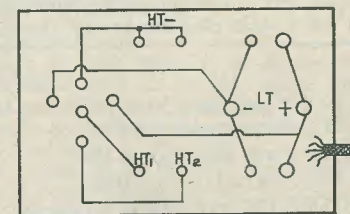


FIG. 11

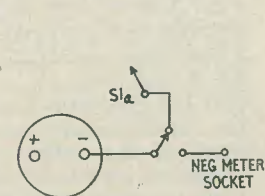


FIG. 12

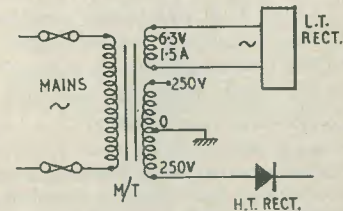


FIG. 13

G 523

A Comprehensive Mixer-Fader

by J. G. RANSOME

the pin and resoldered at the tip again. The l.f. choke was one that came from an old battery converter, but any l.f. choke will do provided that it is wound with heavy gauge wire, 16 or 18 s.w.g., so that the voltage drop across the winding is negligible. Failing a suitable l.f. choke, then a heater transformer can be used; ignore the mains side and use the l.t. side.

The 10-watt resistor is mounted by passing a 4BA threaded rod down through its centre and through the chassis, securing with 4BA nuts and bolts, and using a large plain washer on top of the resistor. There should, of course, be no contact between the resistor element and the fittings or chassis. The h.t. fuse is a 0.04-amp M.E.S. bulb, and this rating will ensure that the majority of the valves are protected in case the h.t. and l.t. leads are plugged in wrongly at the set. If, however, it is intended to use the unit to supply 80mA current, then the fuse bulb should be altered to 0.1 amp.

The meter can be used as a separate voltmeter but in this case it will be necessary to fit a S.P.D.T. switch in the negative lead from the meter to S_{1c} and a separate negative socket on the front panel as Fig. 12. The 3V and 15V positive socket is then the l.t. positive socket of the output and the 150V socket is the H.T.₁, whilst the 300V socket is H.T.₂.

When first connecting up the power supply lead use a 3-pin plug top so that the correct

polarity is observed, the live lead going to the lead marked L and the neutral lead going to the lead marked N. These markings are usually on the plug top when its cover is removed, but if there are no markings then with the large pin uppermost and looking at the back of the plug top, the L pin is to the right and the N pin to the left. If it is required to keep the unit isolated from the mains, then a mains transformer giving 250V at 80mA and 6.3V at 1.5 amps may be used in place of the heater transformer. The connections are then modified as in Fig. 13. (This is the better method.—Ed.)

In operating the unit always make sure that the variable controls are at minimum before switching on the unit, so that no excess voltages are applied to any set connected up. Bring up the l.t. control, having first switched the meter to the "l.t." position, and adjust the voltage to its correct value on load. Then switch meter to H.T.₁ and adjust its control to give the correct voltage, and similarly with H.T.₂. Use H.T.₁ for the lower voltages, including 90V, and H.T.₂ for the highest voltages.

When using the unit with sets incorporating automatic bias, do not plug in an earth to the set as this will short out the bias; this does not apply if an isolating mains transformer is used in the unit.

To finish off the unit, mark out a panel of aluminium as in Fig. 3, then cut out and bend to form a cover as Fig. 6.

List of Parts Required

- | | |
|---|---|
| 1 6.3V 1.5 amp, or 250-0-250V 80mA and 6.3V 1.5 amp mains transformer | 1 4.7k Ω $\frac{1}{2}$ -watt resistor 10%, see text |
| 1 6/12V 1-amp full-wave rectifier | 1 470 Ω $\frac{1}{2}$ -watt resistor 10%, see text |
| 1 L.F. choke or l.t. transformer | 1 27k Ω $\frac{1}{2}$ -watt resistor 10%, see text |
| 3 1,000 μ F 12V wkg tubular condensers | 1 270k Ω $\frac{1}{2}$ -watt resistor 10%, see text |
| 1 250V 80mA half-wave rectifier | 1 8.2k Ω $\frac{1}{2}$ -watt resistor 10%, see text |
| 2 1 $\frac{1}{2}$ in 1-amp fuses | 1 470k Ω $\frac{1}{2}$ -watt resistor 10%, see text |
| 1 twin fuseholder, baseboard mounting | 1 56k Ω $\frac{1}{2}$ -watt resistor 10%, see text |
| 1 32+32 μ F 450V wkg tubular condenser | 1 4 μ F 350V or 500V wkg tubular condenser |
| 1 1,500 Ω 10-watt wire-wound resistor | 1 2 μ F 350V or 500V wkg tubular condenser |
| 1 M.E.S. 0.04-amp bulb, any voltage | 2 British 5-pin valveholders |
| 1 M.E.S. holder, baseboard mounting | 4 plain metal wander plug sockets |
| 1 3-pole 4-way rotary switch | 2 0-BA terminals |
| 1 meter, 0.5mA or 1 mA | 1 M.2 all-dry battery socket |
| 1 50 Ω 4-watt wire-wound potentiometer | 1 S.2 all-dry battery socket |
| 1 50k Ω 3-watt wire-wound potentiometer | 20ft 23/36 single rubber flex |
| 1 50k Ω 1-watt carbon potentiometer | 1 6in x 3in x 1in wood switch block |
| 1 33k Ω $\frac{1}{2}$ -watt resistor 10% | 1 sheet aluminium 10 $\frac{1}{2}$ in x 12 $\frac{1}{2}$ in |
| | 1 sheet aluminium 10 $\frac{1}{2}$ in x 21 $\frac{1}{2}$ in |
| | Panel signs transfers, Set No. 4 |

LONDON AUDIO DEMONSTRATION

Heathkits (Daystrom Ltd.) have made arrangements to display and demonstrate their audio and other equipment at the Royal Hotel, Russell Square, W.C.1, from 2nd to 5th April, inclusive. The model S-88 Hi-Fi stereo amplifier and the SS-1 Hi-Fi speaker will be particularly featured.

THIS UNIT WAS ORIGINALLY DESIGNED FOR a friend who was suffering from "the tape bug." His requirements were for a two-channel high-gain mixer for two microphone inputs, the output of which could be mixed with the output from a gramophone. The actual circuit designed was for an amplifier-mixer for four channels, two high gain and two low gain, each channel of which could be mixed with any other or use made of all channels at once. The prototype has been in use for some time now and is giving quite pleasing results.

In order to keep the cost within reasonable limits, the circuitry has been devised for equipment which, to a certain degree, might be found in the "spares box" (modern euphemism). The high-gain channels are designed around the EF37A, but there is no reason for not employing valves of the EF40 type or EF86 variety; no circuit changes will be required. The EF37A is used in conventional circuitry and really needs no comment save for the fact that the decoupling provided by R_3 - C_2 , R_5 - C_4 is essential, to prevent cross-talk on the channels. The wiring to V_1 and V_2 must be as short as possible to avoid hum pick-up; mixing four sets of hum in a circuit like this is rather aimless! R_9 controls channel 1 gain, whilst R_{10} controls the gain of channel 2. The two load resistors marked R_L are to suit the impedance of the microphone being used; the original circuit used, rather wastefully, two 5 Meg Ω potentiometers here, and these were adjusted for best quality. The outputs from the two amplifiers are taken through R_{11} and R_{12} and thence via C_{14} to the channels 1 and 2 master control R_{25} , which controls the mixed level output from the microphone pre-amplifiers and passes it on to the master mixer.


The Low Gain Mixer

This mixer is, in effect, a triode version of the pentode high gain section. The signals are fed into the grids of the twin triode by way of R_{13} and R_{14} , which provide individual channel gain controls. The amplified signals are passed in the anode circuit via R_{19} and R_{20} through the coupling condenser C_{12} to the channels 3 and 4 master control and to the other side of the master mixer. The decoupling afforded by R_{15} - C_{11} will be found to be indispensable.

The Master Mixer

This is the unit where all of the incoming signals have a final mixing before being passed on to the main amplifier. The mixed signals from the high gain channels are put on to grid 1 (a) of the twin triode and the mixed signals from the low gain amplifier mixer are put on to grid 1 (b). The resultant signals are mixed in the anode circuits of this valve and passed via C_{13} and R_{27} , which latter acts as the master gain control, to the final amplifier.

The overall gain of the system is 16 x 150 or 2,400 for the microphone channels, and about 16 x 16 or 256 for the low level amplifier. The output for the system may be too high for the amplifier to be used, and if this is so, some simple attenuation circuits will have to be evolved. A cathode follower was used for feeding the output from the mixer into the tape recorder amplifier and this method of coupling was found to be excellent. For a simple fading system, for the lazy, the bias resistor R_{28} is switched; this by virtue of the discharge of the bypass condenser C_{15} which is very large and consequently discharges slowly, produces a slow fade—this being very useful for the busy chap who has probably his hands full with the recorder.

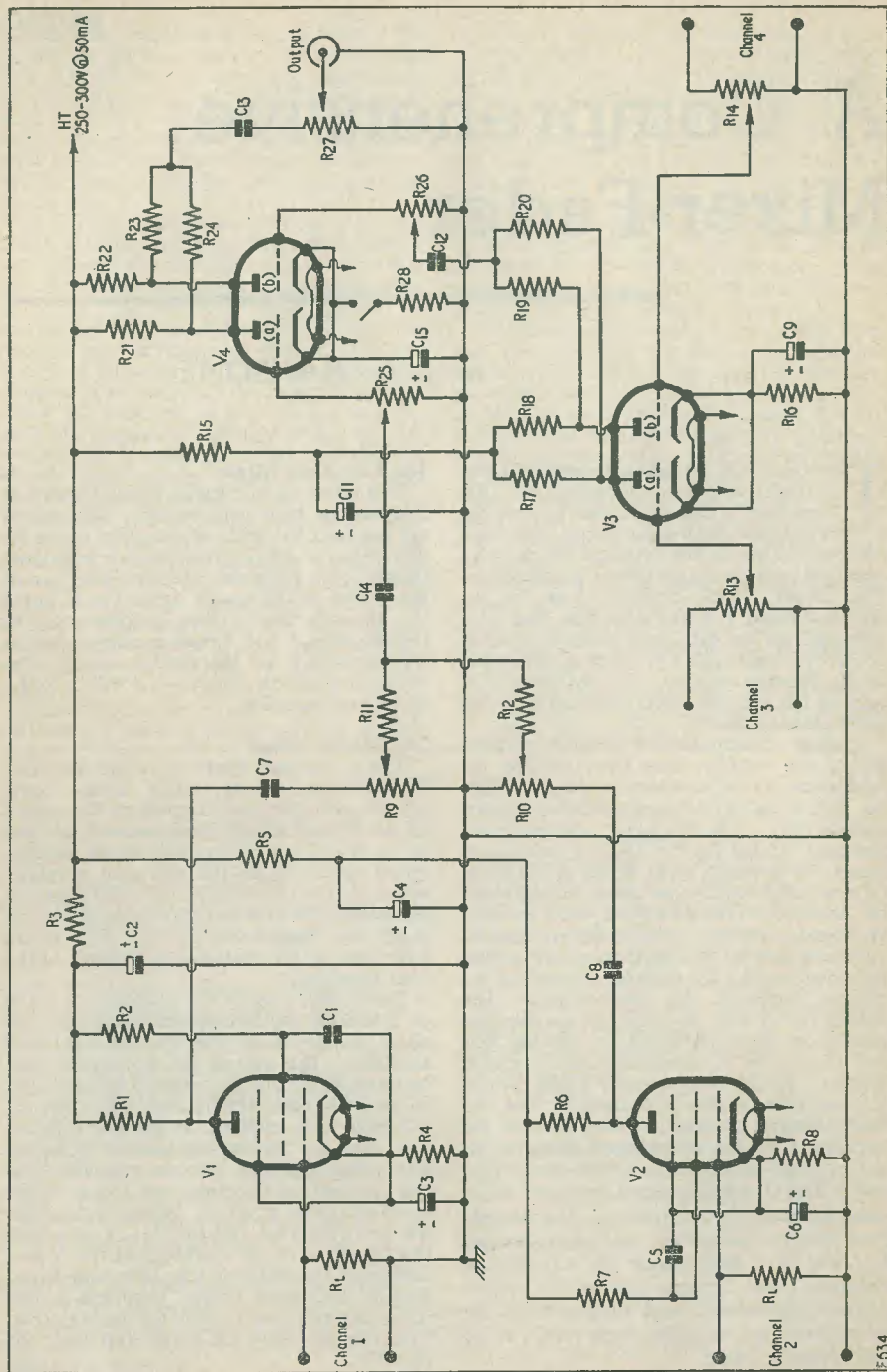

It may be inferred from the circuit diagram that the unit is riddled with lurking potentiometers, and in order to clear up any difficulty the use of each will now be given:

R₉ channel 1 gain control, R₁₀ channel 2 gain, R₁₃ channel 3 gain control, R₁₄ channel

4 gain, R₂₅ channels 1 and 2 master control, R₂₆ channels 3 and 4 master control, R₂₇ overall master control.

Each potentiometer may be labelled as to its function for easy reference.

Main Components List

Resistors

R₁, 6, 11, 12, 17, 18, 19, 20, 21, 22, 23, 24
220kΩ

R₉, 10, 13, 14, 25, 26, 27 500kΩ pot.

R₃, 5, 16, 28 3.3 kΩ

R₂, 7 1mΩ

R₄, 8 2.2kΩ

R₁₅ 47kΩ 1W

Condensers

C₇, 8, 12, 13, 14 0.05μF 350V

C₂, 4, 11 8μF, 350V electrolytic

C₃, 6, 9 25μF 25V electrolytic

C₁, 5 0.25μF 350V

C₁₅ 1,000μF 6V

Valves

V₁ 6SN7

V₂ 6SN7

V₃ 6SN7

V₄ 6SN7

MISCELLANEOUS

An Explanation of

LOW POWER ULTRASONICS

By R. WEBB, M.I.P.R.E.

IF THE BIBLE IS TO BE BELIEVED (AND FAR BE IT FROM ME TO DISCREDIT IT), the principle of ultrasonics was used by the attacking hosts who, by raising a great sound, caused the premature collapse of the walls of Jericho. Seriously, though, it was towards the end of the 19th century that it was first shown that fine particles could be agglomerated at the nodal or "no-movement" point of a sound-wave, and thus in a sense rendered visible. It had been realised for some time that vibratory waves did not cease at the upper limit of hearing, but continued to be propagated at much higher frequencies, and whistles and tuning forks capable of producing high frequency sound-waves had been constructed. The sound energy produced by these means was of extremely small magnitude, but interest in the subject increased with the discovery of piezo-electricity, for it was soon seen that a crystal element was capable of providing large power outputs when driven by a suitable alternating supply source of energy. The application of magneto-strictive materials for

the same purpose soon followed, and present-day research has been almost entirely built up around these sources of ultrasonic energy.

Wartime requirements—that is the 1914-18 war—showed a useful application of ultrasonics, in that under-water detection was developed when it became necessary to find out the whereabouts of enemy submarines and mines. The period 1919-1939 showed the first real effort being made to investigate the physical effects of high intensity sound, until today there is quite an army of interested research engineers progressing the subject, and it is the intention of this article to cover some of the various applications, together with certain basic methods of generation.

In the first place, let us be quite clear what the term ultrasonics means. The term is used to describe a vibratory wave of a frequency above that of the upper frequency limit of the human ear. Therefore, we are thinking of all frequencies above 16 kc/s. For a time the word "supersonic" was wrongly applied, and this term has now rightly taken its place as meaning "above the speed of sound."

As far as we are concerned, the frequency is only limited for our requirements by the type of transducer employed. The thing that decides the type of transducer is very largely the medium into which the waves are to be propagated, and the various frequencies conveniently allocate themselves to various applications. At the lower end of the ultrasonic band we find a suitable frequency for a transducer which can undertake drilling and soldering, this being of the order of 20 kc/s. For submarine detection, 30 kc/s transducers are suitable, whilst for flaw detection in metals and glass—for example—we move up to a maximum of 10–12 megacycles. A certain amount of heat is generated in the materials into which the waves pass. Making use of this property it is possible to scramble an egg without removing the shell, and plastics may be welded by this means. Again, an ice cube subjected to ultrasonic waves for a short time will break into small fragments when squeezed in just the same way as the sun will melt it—in other words, liquefaction has occurred. Similarly, if a block of wax is placed in the path of the wave it will melt in a pattern that shows the conical focusing of the beam inside the block.

Measurement of these ultrasonic frequencies is made by absorption type wavemeter for over 100 kc/s and by direct-reading frequency meter of the counting or integrating type for the range below 100 kc/s.

Generation

As far as the means by which the required ultrasonic wave is produced, we can break these up into four various types or methods, viz:

- Piezo-electric
- Magneto-strictive
- Jet and
- Electromagnetic.

I will describe each briefly.

The first one—piezo-electric or crystals—will be familiar to us; the main point in using this method is to remember that the crystal will present a mainly resistive load to its power supply equivalent to anything between 10 and 250 thousand ohms shunted by a capacitance of up to 100 pico-Farads. As mechanical energy generated by the crystal is primarily a function of voltage, it must be borne in mind that very close impedance matching to the supply will be necessary to develop a high voltage across the crystal. This impedance refers, of course, to quartz crystals; but as a matter of fact the most usually used material is a ceramic, barium titanate, which looks at something like 15 ohms plus 18,000pF but, of course, it is dependent on size, loading and frequency. Quartz is usually used for the higher ultrasonic frequencies (in the 5–10 Mc/s range)

whilst barium titanate is used for normal industrial frequencies up to 1 megacycle. The quartz does present some insulating difficulties for high power work.

Magnetostriction occurs when ferro-magnetic materials are subjected to a magnetic field, and a change in physical dimensions takes place. This physical change brings about a change in the magnetic properties of the material and is called magneto-striction. Nickel is such a material, and is used as a transducer for low and high power application such as drilling, cleaning, processing, etc. Ferroxcube is another material which is electrically suitable, but mechanically weak for our purpose, though it can be used in special circumstances. If a nickel rod is brought into a magnetic field, it is shortened. It will be seen that if the rod is not previously magnetised, it will vibrate with double the frequency of the alternating field, whereas if suitably pre-magnetised, the mechanical change in length will be in step with the applied alternating frequency. If there is resonance between the natural elastic period of the rod and the frequency of the alternating current, the amplitude of the oscillation will then be at its maximum, and sound waves of the same frequency will be sent out from the end of the rod.

With various materials the frequency varies with the length, e.g. a rod of nickel 12.5 cm long vibrates at a natural frequency of 20.4 kc/s, whilst the highest frequency obtainable is of the order of 60 kc/s for a piece about 4 cms long. In such a rod or tube, set in longitudinal oscillation by magnetostriction, we find sound waves are only emitted from the ends of the rod. This would be useless for such things as submarine work, and so a means of radiating in all directions in one plane must be found. The answer lies in using a circular ring set by magnetostriction into elastic oscillation in such a way that the ring forms a circle with a periodically changing radius, the sections of the ring only moving radially. Waves are then radiated from the outer edge in a radial direction. A ring of this sort may be excited by a toroidal winding through which an alternating current is sent.

Under the heading of jet can be grouped sonic and ultrasonic generators employing high velocity liquid or gas streams, such as resonant cavity whistles, pulsed liquid jets and gas and liquid operated sirens. One main advantage of jet generators is the simplicity of the power source, this being either a compressor pump or a high speed rotary movement. An example of this type of generator that comes to mind is the Galton dog whistle—a whistle which we cannot hear but to which dogs respond from quite astonishing distances.

The electromagnetic method of converting electrical energy to acoustic energy by the movement of a coil carrying a varying voltage in a magnetic field of constant intensity is well known; a loudspeaker or earphone is, of course, an everyday example. With slight modification to the moving coil system, it is possible to use it for ultrasonic frequency generation. In such a device the efficiency falls off considerably as the frequency increases and the system is rarely used, so that the application is really restricted to fatigue and vibration study at l.f.

Now, whilst all these various methods and applications are all very interesting, they cover a very wide field. It seems advisable, therefore, to concentrate on a particularly useful section of ultrasonics, viz. drilling, cleaning and cutting by low power generation (approx. 50 watts). Let us take drilling first. The chief advantage of ultrasonics for drilling is that materials which are too brittle to drill by ordinary means can be handled satisfactorily. It is, in fact, the only practical method of producing shaped holes in brittle material, and for round holes under $\frac{1}{2}$ in it is claimed to be the best method. The same small portable equipment can be used for cleaning and cutting, and has a number of biological applications which will be described later. Coming back to drilling, there is a saying which can be loosely applied to this effect: "If you can shatter it, you can drill it," thus indicating the suitability of the ultrasonic drill for materials such as ceramics, glass, tungsten carbide, germanium, synthetic gems, and similar materials which have previously presented difficulty when drilling has to be performed. An ultrasonic drill is used for drilling diamond dies for tungsten wire drawing where the wire has to be drawn down to something like 10–12 microns thickness. For this purpose, an ordinary sewing needle may be used, and how it is possible to use this needle for this process will become apparent when the principle of the drill is explained.

Explanation of Ultrasonic Drill Principles

In the drill-head, there is a laminated nickel stack, the clamp being secured at the nodal, or "no-movement" point. By setting up an alternating field round a nickel element the nickel tends to contract at approximately a frequency of 20 kc/s, this being the natural or resonant frequency of this transducer. (The frequency range of the generator is 16–25 kc/s.) Nickel is ideal for this particular purpose as it has a very high fatigue strength. The stack, or transducer, movement up and down is $\frac{3}{10}$ thou. at 20,000 c/s. Now $\frac{3}{10}$ will be insufficient movement for our purpose, so the problem arises as to how to increase this movement from $\frac{3}{10}$ thou.

to something of the order of 2 to 3 thou. The answer is to fit what is called a stub, or velocity transformer made of aly. bronze. The stack is drilled and tapped and this stub is screwed in tightly. Now if you visualise something the shape of a Rawlplug tool, you can realise the shape of one of the original types of these stubs. There is a mathematical law which the design of the stub follows which is rather outside the scope of this article. The material decides the length of the stub, and if you wish to have a size reducing to $\frac{1}{2}$ in we start off with the part of the stub which screws into the stack at $\frac{3}{4}$ in diameter, thereby giving a step up of amplitude of physical movement. This increase in amplitude is determined by the ratio of the square of the end diameters. There is a limit to this step up in amplitude and materials generally will not tolerate without fatigue or crack-up more than a 9:1 increase. To keep within this limit on this low power equipment the size of the working tip diameter cannot go below $\frac{1}{4}$ in, this giving a 9:1 increase of amplitude, that is from $\frac{3}{10}$ thou. to 2.7 thou. The working end of the stub is drilled and tapped to take any tool shape required. The user of the drill makes his own tools to screw into the stub, as they are quite simple to make and need only be of some tough material which is abrasive-proof. There is a law here that the diameter of the tool must never exceed the diameter of the working tip, in this case $\frac{1}{4}$ in, by more than 1/10 in, but they can be less than the diameter of this working tip. It is interesting to note whilst on this subject that a 6 thou. hole in soda glass has been achieved.

Materials

Pure nickel and various nickel alloys give good results, e.g.:

- (1) An alloy of 36% nickel–64% iron called "invar."
- (2) 68% nickel and 28% copper with small amounts of iron silicon, manganese and carbon called "monel."

The natural frequency of a nickel tube can be changed by filling with, say, lead. A proprietary brand of this is known as "Permaloy."

A word about the tools. As already stated, these can be of some tough material, such as tool or silver steel, and it is important to remember that it is not the tool which does the cutting. This is done by an abrasive carborundum powder suspended in water, known in the trade as slurry. The principle to remember is that the tool guides the slurry only. A further point is that it is usual to trepan the holes. This, in itself, is useful because if, for example, one is drilling glass, the piece removed may be required as a lens. As the user makes his own tools, he can lay

on a quantity of one particular shape if he has a large scale production job to do, although the wear on the tools depends entirely, of course, on the material one is drilling or cutting.

It is possible to obtain a depth of cut up to $\frac{1}{2}$ in in difficult materials at low powers only. If one attempts to drill any deeper, there arises a difficulty in feeding the slurry into the hole and, at the same time, cleaning out the chips of material which have been removed. You can, of course, drill from both sides at once. If you look into the tool kit of anyone habitually using one of these drills, you will find that an essential part of their equipment is a stick of plasticine. This is used on occasion to form a little cup round the drilling operation if the job has to be carried out horizontally, for example, drilling in a cornice.

How long does it take to drill a hole by this means? Examples of time required are as follows:

- a hole in glass $\frac{1}{8}$ in x $\frac{1}{8}$ in x 2mm. deep—20 seconds.
- a hole in silica $\frac{1}{4}$ in x 1 $\frac{1}{2}$ mm. deep—12 seconds
- a hole in tungsten carbide $\frac{1}{8}$ in dia. x $\frac{3}{8}$ in deep—38 minutes.

One should note here in this connection that the coarser the abrasive or slurry the quicker the result. A finer slurry will be slower, but will give a better finish: as an example, a slurry mixture of what is called 800 mech can achieve an accuracy of 2/10 thou, provided the mechanical design of transducer and stand is adequate for these accuracies.

It was mentioned that a 50 watt generator equipment can be used for cleaning. A point here is that the stub provided for this purpose is undrilled and untapped. Briefly, when the energy in an ultrasonic wave is sufficient to set up peak alternating pressures in the liquid greater than 1 atmosphere, a phenomenon known as cavitation takes place. During negative pressure cycles we expand the microscopic bubbles present in all liquids and during the positive pressure cycle we collapse this bubble and the high local pressures set up at the point of collapse, which speeds up our cleaning action. Fairly obviously, certain materials require certain cleaning agents and as an example a diamond ring would require hot caustic soda, whilst for quartz crystal cleaning distilled water is used. Incidentally, the cavitation zone has an area similar to the diameter of the probe used.

As regards biological applications, a rat's liver in water put through an emulsifying process becomes just like a table jelly. Apart from emulsifying things like that, there are a number of instances where ultrasonics is

materially helping research. For instance, disruption of bacterias, i.e. examination of cholera and whooping cough bacteria where the final break-up of the bacteria is achieved by subjecting them to ultrasonic waves. In the case of smallpox and chickenpox, after the virus has been successfully cultured or propagated from an infection in the blood stream the anti-gens are isolated so that a pure vaccine can be obtained and used for curative purposes.

We can classify dentistry under medical applications. You have, no doubt, heard of the ultrasonic dental drill which permits painless dentistry in respect of drilling teeth. Apart from being painless, there is another advantage in that the drill automatically ceases to drill when it has penetrated the hard outer shell of the tooth and does not plough into the soft centre which, with ordinary drilling, the dentist goes to no little trouble and uses his skill to preserve. As far as can be ascertained, it can be said that it is known that the dental drill cuts satisfactorily. It is as quick as existing dental engines, although they are now drilling mechanically at 150,000 revs per minute, a ball-race having been developed which appears to cope satisfactorily with this extraordinary speed. There does exist, of course, a very great danger in that control of such a mechanical drill can only be entrusted to a dentist well qualified to use it; one slip, of course, causing great damage in the mouth.

It is proved that the ultrasonic method is definitely painless, the frequency, as with hearing, being above the threshold; in this case, the pain threshold.

Slurry is a problem, the lower jaw being easier as one is drilling downwards and it is not difficult to accumulate and maintain the slurry in this position. At the moment, drilling upwards is not possible on account of this difficulty in accommodating the slurry, but experiments are going on to find a method of suspending the slurry medium for upper jaw drilling, although some humorist will no doubt immediately suggest that the patient stand on his head to overcome the difficulty! All this can be performed with a 50 watt generator with a water-cooled transducer. An interesting use of the dentist drill is that it can be used for engraving—for fine freehand work.

A further use of the ultrasonic drill is that it can be used for diesinking. As an example, if the rear of a sheet of glass is embossed by drilling half way through and then the back silvered, the effect when viewed from the front is quite pleasing.

There is another use of these low power generators which must, of course, be mentioned.

continued on page 610

G2AK FOR QUALITY AND SERVICE

HEADPHONES. H.R. type, 4,000 ohms, very sensitive. Only 12/6 pair. P. & P. 1/6 C.L.R. (low res.) 8/6, P. & P. 1/6

RECORD CHANGERS. Latest B.S.R. Monarch UA8 with manual and auto control, latest Ful-Fi Cartridge. List £9.15.0. OUR PRICE £7.15.0, carr. paid

MULTI-WAY CABLE. $\frac{3}{8}$ " diam. 7 colour coded wires. Ideal for mobile or inter-chassis connection. Any lengths cut, 1/3 per yard. P. & P. 1/6 min.

10-WAY CABLE (5 pairs). Screened and plastic covered. Any length cut, 2/- per yard P. & P. 1/6 min.

7-way (unscreened) 1/3 yard.
DUAL RANGE VOLTMETERS. Dual range 0-5v. and 0-100 M.C. 1,000 Ω /V. Ranges easily extended. With test prods and leads. Complete in solid leather carrying case $6\frac{1}{2}$ " x 5" x 2". A GIFT at 25/-. Post free.

ABSORPTION WAVEMETERS. 3.00 to 35.00 Mc/s in 3 switched bands, marked on scale. Complete with indicator bulb. A MUST for any ham shack. Only 17/6, post free.

Send for our new 56-page illustrated catalogue. P.O. or stamps, 1/6.

SPECIAL OFFER!

R.F. UNITS

Type	
24	switched { 16/6 each 11/6 each
25	
26 tunable	19/6 each
	P. & P. 3/6 each

100 KC/S CRYSTALS. American 3 pin based crystals. New condition. Worth £3.10.0. Only 25/-, post free.

R.F. CHOKES. 2.5mH, 120mA. Pie wound, 2/- each. Three or more post free

NATIONAL TYPE R-300 μ . Type R-300 μ pillar mounting choke, 1mH, 300mA, 3/- each or 6 for 15/-

SHADED POLE MOTORS. For tape decks or gram. units. 3-hole fixing, twin coil, closed field type, 200/240V, 50 c/s. 15/- each or 27/6 for 2. P. & P. 2/-

RACK MOUNTING PANELS. 9" x 5 $\frac{1}{2}$ " 7", 8 $\frac{1}{2}$ " or 10 $\frac{1}{2}$ " black crackle finish, 5/9, 6/6, 7/6 respectively, postage and packing 2/-

CHAS. H. YOUNG LTD (Dept. R)

110 DALE END BIRMINGHAM 4 (Tel. all departments) CEN 1635

AERIAL EQUIPMENT

COPPER WIRE. 14g. h.d.: 140' 17/-; 70' 8/6; 7/25 stranded; 140' 10/-; 70' 5/- plus 2/- P & P.

RIBBED GLASS INSULATORS. 3" 1/6 each or 6 for 7/6. P. & P. 1/6

TWIN FEEDER. 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K358 Telcon (round) 1/6 per yard. Post on above feeder and cable, 1/6 any length

SUPER AERIAL CABLE 1/6 a yard. P. & P. 1/6

CERAMIC FEEDER SPREADERS. Type F.S. 6" 9d. each or 8/- doz. P. & P. 2/-

CERAMIC "T" PIECES. Type AT for centre of dipoles 1/5 each or 3 for 4/- P. & P. 1/6

MOSLEY TRI-BAND BEAMS Orders for these will be handled in strict rotation.

T33 JR. 3 EL ... £25
TA32 JR. 2 EL ... £18
V3 JR. Vertical 3 Band ... £18

PLACE YOUR ORDER EARLY

Electronic E.M.A. Contractors

ALL ORDERS SATISFACTION OR MONEY REFUNDED

CONDENSERS, OIL FILLED, PAPER (PYRANOL). 15 μ F 600V wkg. ($4\frac{1}{2}$ " x $1\frac{1}{2}$ " x $3\frac{1}{2}$ " TH $1\frac{1}{2}$ "), 7/6; 10 μ F 600V wkg. ($4\frac{1}{2}$ " x $1\frac{1}{2}$ " x $3\frac{1}{2}$ " TH $1\frac{1}{2}$ "), 7/6; 4 μ F 1,000V wkg. ($4\frac{1}{2}$ " x $1\frac{1}{2}$ " x $3\frac{1}{2}$ " TH $1\frac{1}{2}$ "), 6/-; 1 μ F 600V wkg. ($1\frac{1}{2}$ " x $\frac{7}{8}$ " x $1\frac{1}{2}$ " TH $1\frac{1}{2}$ "), 2/-; 0.25 μ F 3,000V wkg. ($3\frac{1}{2}$ " x $1\frac{1}{2}$ " x $2\frac{1}{2}$ " TH $1\frac{1}{2}$ "), 5/-; 0.1 μ F 6,000V wkg. ($3\frac{1}{2}$ " x $1\frac{1}{2}$ " x $2\frac{1}{2}$ " TH $1\frac{1}{2}$ "), 6/-; 0.1 μ F 2,000V wkg. ($2\frac{1}{2}$ " x $1\frac{1}{2}$ " x $1\frac{1}{2}$ " TH $1\frac{1}{2}$ "), 3/6; 0.01 μ F 6,000V wkg. ($2\frac{1}{2}$ " x $1\frac{1}{2}$ " x $2\frac{1}{2}$ " TH $1\frac{1}{2}$ "), 4/- TH—Terminal height. Post and packing free.

WIREWOUND POTENTIOMETERS. 1,000 ohms x 1,000 ohms 4W $\frac{3}{8}$ " spindle, 4/6; 5,000 ohms 25W $1\frac{1}{2}$ " spindle, 4/6; 5,000 ohms 4W $\frac{3}{8}$ " spindle, 3/6; 5,000 ohms 2W $1\frac{1}{2}$ " spindle, 3/6; 10,000 ohms 4W $\frac{3}{8}$ " spindle, 3/6; 10,000 ohms 1W $1\frac{1}{2}$ " spindle, 2/6; 50,000 ohms 4W $1\frac{1}{2}$ " or $\frac{3}{8}$ " spindle, 3/6. Post and packing free.

DOUBLE CARBON POTENTIOMETERS (STEREO POTS). 500,000 x 500,000 ohms $\frac{3}{8}$ " spindle, 3/6; 100,000 x 100,000 ohms, $3\frac{1}{2}$ " spindle, 3/9; 200,000 x 200,000 ohms $\frac{3}{8}$ " spindle, 3/6. Post paid.

SLIDER RESISTORS, IDEAL FOR BATTERY CHARGERS, ETC. 3 ohms 10A 12" resistor, 9/-; 1.2 ohms 15A 7" resistor, 9/-; 11 ohms 4.5A 5" resistor, 8/6. Post and packing paid.

50 c/s A.C. RELAYS. 6V single break contact, small construction, 4/-; 115V single make, heavy contact, 4/6. New and boxed. Post and packing free.

DIODES. 1N21 microwave crystal diode; rectifiers up to 2,500 Mc/s, each individually packed in metal capsule, 3/- each, post paid. WX2S diodes, 1/- each, post paid.

VALVEHOLDERS. 829 or 832 porcelain, 2/- each. International octal amphenol 5/- doz.; nylon loaded bakelite 7/- doz. B9A and B7G 9/- doz. Post paid.

VALVES. 6V6GT, 6/6; 6AG7, 7/6; 6AC7, 6/6; 5U4G, 7/-; 25L6GT, 5/-; 6SL7GT, 7/6; 6SN7GT, 6/-; 6SJ7, 7/-; 6H6, 2/6; OD3 (VR150), 5/-; 72R (3B2), 7/-; 829 (3E29), 5/1/-; 446B, 14/6; 464A, 14/6; 3FP7 CRT Tube, 12/6. Post paid. All new and boxed.

METERS. 0-1mA d.c. meter, 2 $\frac{1}{2}$ " round flush fixing, by General Electric Co. New, boxed, 15/-; 0-150V a.c. meter, 2 $\frac{1}{2}$ " round flush fixing, 8/5V a.c. basic movement. By General Electric Co. New, boxed, 12/6; 0-25V d.c. 2" round, 8/6; 0-15A 2" round, 8/-; 0-20A 2" round, 7/6; 0-40A, 2" round, 7/-; 0-300mA thermo-couple 2" round, 3/9. All prices include post and packing paid.

BLOWER MOTORS with fan assembly, 115V a.c.-d.c. motor. Brand new units complete with dropper to run from 230-250V a.c. mains. 16/6 post paid.

MINE OR METAL DETECTORS No. 3 Mark II. Complete with two search coils, haversack, working instructions and operation chart. In strong wooden transit cases. All tested before despatch. 95/- plus 15/- carriage.

HALF-SECOND SWITCHING CLOCKWORK MOVEMENTS. These beautiful clock movements are brand new. Each in sound proof box. Ideal for photographic timer, flashing lights, time standard, etc. 10/6 post paid.

PANEL LIGHTS. Bakelite construction, red or green glasses. Single-hole fixing, screw-in lamp-holder, type 5C. 9d. each or 7/6 per doz, post paid.

41 COWBRIDGE HERTFORD Telephone Hertford 3316


HOME RADIO OF MITCHAM



MICROPHONES
Brand NEW boxed ACOS 33-2 crystal microphones for hand or desk use. Complete with switch and lead. High quality and omni-directional. Ideal for tape recorders, amplifiers, transmitters, public address, etc. Usual price 55/-. Our **SPECIAL PRICE** 35/-, plus 9d. post.

A NEW STENTORIAN TWEETER

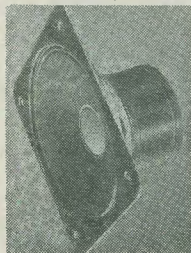Bring your radio or gramophone to LIFE with a tweeter. Hear all those top frequencies that you are missing. High sensitivity 9,000 gauss magnet, special cone and lightweight coil. Frequency response 3,000 to 17,000 c/s. Impedance 5 ohms or 15 ohms. MODEL T.359 **PRICE** 35/-, plus 1/- post. CX3000 cross-over network for above **PRICE** 30/-, plus 9d. post.



We carry the full range of "EDDYSTONE" short wave components and communications receivers. Send 6d. stamp for Eddystone component list. **SPECIAL OFFER TO CLEAR**
Woden heavy duty smoothing chokes. 10 Henry 300mA, 100 ohms open type chokes. Ideal for amplifiers, transmitters, etc. **PRICE** 5/-, plus 3/6 packing and post.

Dept. C 187 London Road, Mitcham, Surrey
Shop hours 9-6.30 p.m. Weds. 1 p.m. MIT 3282

Smith's
of
EDGWARE ROAD

DIRECT FROM MAKER TO USER!

HI-FI ENTHUSIASTS ALL OVER THE WORLD ARE BUILDING COOPER-SMITH AMPLIFIERS AND GETTING BETTER REPRODUCTION AT LOWER COST.

WHY NOT YOU?

The "Prodigy" High Fidelity 6-watt combined Control Unit and Amplifier
Complete Kit £13.7.6

The B.P.I. 10-watt High Fidelity Amplifier with separate Control Unit

Control Unit Kit £8. 3.0 complete
Main Amplifier Kit £12.12.0 complete

Booklets containing full constructional details and price list of components of either of the above, 2/8 post free, or supplied free with each kit.

These amplifiers can also be supplied laboratory built and tested. Call for demonstration.

287/289 EDGWARE ROAD LONDON W2
Telephone PAD 5891/7595

QUICK EFFICIENT UP-TO-DATE COMPONENT SERVICE!

Pocket Valve Radio

Anyone can build this beautiful precision Pocket Radio.

No knowledge whatever needed, our simple, pictorial plans take you step by step! You can't go wrong. Remarkably sensitive—covers all medium waves incl. Luxembourg, Home, Light. Size only 2" x 3" x 5 1/2".


Not a toy! but a real valve radio! Uses self-contained battery and is a really personal-phone, pocket radio with detachable rod aerial. Ideal for bedroom, garden, etc. We can supply all the parts necessary, for the **Special Price of 37/6** (plus 2/6 post, etc.). Personal-phone 4/6. Batteries extra—obtainable anywhere. **BUILD YOURS NOW!** (All parts sold separately.) Priced parts list, etc., 1/9. Big demand certain—send today! C.O.D. 2/- extra.

Can be Built for
37/6



Can be Built for

47/6

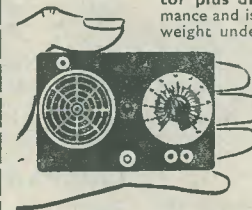

TWO TRANSISTOR POCKET SET

Build the "Sky Pixie" Vest-pocket two-transistor plus diode radio which gives a superb performance and is highly sensitive. Size only 4 1/2" x 3 1/4" x 3/8" weight under 7oz!—yet it is a three-stage receiver covering all medium waves, working entirely off a tiny "pen-light" battery. Every part tested before despatch! **Special step-by-step plans for absolute beginners. Total building cost including case, transistors, etc.—everything down to the last nut and bolt—ONLY 47/6 with plans.** Postage, etc., 2/- C.O.D. 2/- extra. (Parts sold separately. Priced parts list and plans 1/6.) **RUSH YOUR ORDER TODAY!**

PRINTED CIRCUIT POCKET SET

Build this 3-transistor pocket radio... Printed Circuit Version! The "Companion" is comparable in sensitivity to a three-valve battery set; it is exceptionally small in size (4 1/2" x 3" x 1 1/2") and is a self-contained pocket radio that does not need aerial or earth. It has built-in speaker and covers medium and long waves. This unique little set can be built for **only 97/6, everything included!** (plus post and packing 2/6). All parts sold separately. Price list, etc., 6d.

"MONEY REFUNDED IF PARTS RETURNED INTACT WITHIN SEVEN DAYS"

CONCORD ELECTRONICS (DEPT. RCS)

69 PRESTON STREET
BRIGHTON 1

For a really professional finish use . . .

PANEL-SIGNS TRANSFERS

Set No. 1: Receivers and Amplifiers

Five sheets 8 1/2" x 5 1/2" containing one large scale, twelve control panels and white wording. 3s. 6d. postage 2d.

Set No. 2: Test Equipment

Five sheets 8 1/2" x 5 1/2" containing two medium scales, twelve control panels and white wording. 3s. 6d. postage 2d.

Set No. 4: Wording

As set No. 3, but in black. 3s. 6d. postage 2d.


Published by

DATA PUBLICATIONS LTD

57 MAIDA VALE · LONDON W9

Telephone CUNningham 6141 (2 lines)


Telegrams Databux London

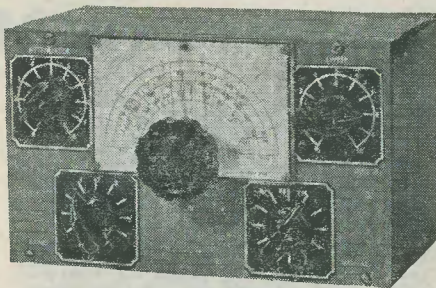

Set No. 3: Wording

Wording for Receivers, Amplifiers, Transmitters, Test Equipment and other Radio Apparatus, and Station Names. Five sheets, over 750 words and symbols. White. 3s. 6d. postage 2d.

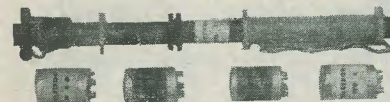Panel-Signs Transfers Fixing Varnish 1s. per bottle postage 6d.



TELETRON MINIATURE TRANSISTOR 42/-

Superhet coil kit (as illustrated) 470 kc/s I.F. Transformers and Oscillator coil in screening cans 3/8" x 1/2" dia. Dual wave Ferrite rod aerial 5 1/2" x 1/8" dia. Designed for the TRANSIDYNE miniature superhet receiver. Price 9d.

Descriptive folder with circuit and assembly instruction

TELETRON TYPE FX.25 15/- each

Self-tuned, dual wave Ferrite rod aerial.



TRANSISTOR I.F. TRANSFORMERS

High Q "potted" construction with Ferrite screw cores. Mounted in screening cans 1" x 3/8" dia., 6/6 each. Oscillator coil, 6/6. Transistor type Ferrite rod aerial for MW band, 10/- Selective crystal diode coil type HAX, 3/- each.

Type HAX.L (for LW band), 3/6. Dual wave TRF coils, type A/HF, matched pair, 7/-, with adjustable iron dust cores.

FERRITE ROD AERIALS Wound on high permeability Ferroxcube rod. Medium wave, FRM 4" x 5/16", 8/9. Dual wave FRD, 8" x 5/16", 12/9.



Send 5d. in stamps for complete data and circuits. All types available from advertisers in this Magazine and local component stockists

THE TELETRON COMPANY LIMITED
112b Station Road · Chingford · London E4 Telephone SIL 0836

SMITH'S OF EDGWARE ROAD

ELECTRONIC COMPONENTS
DISTRIBUTORS FOR OVER 25 YEARS

Four-sided Blank Chassis

Made in our own works from commercial quality half-hard aluminium of 16 s.w.g. thickness, these chassis will carry components of considerable weight and normally require no corner strengthening.

We are now able to supply same day any size of chassis in 1/8" steps up to 17". Depths 1/4", 3/8", 1", 1 1/4", 1 1/2", 2", 2 1/4", 2 1/2", 2 3/4", 3", at the following rates:

48 sq. in.* 4/-	176 sq. in. 8/-	304 sq. in. 12/-
80 sq. in. 5/-	208 sq. in. 9/-	336 sq. in. 13/-
112 sq. in. 6/-	240 sq. in. 10/-	368 sq. in. 14/-
144 sq. in. 7/-	272 sq. in. 11/-	and pro rata

Post 1/3 Post 1/6 Post 1/9

(*Length plus twice depth x width plus twice depth)

Stock Sizes

6" x 4" x 2" 5/-, 7" x 5" x 2" 5/6, 10" x 4" x 2 1/2" 6/9,
9" x 7" x 2" 7/-, 12" x 4" x 2 1/2" 7/3, 10" x 8" x 2 1/2" 8/6,
12" x 5" x 3" 8/6, 12" x 7" x 2 1/2" 8/9, 13" x 8" x 2 1/2" 9/9,
14" x 7" x 3" 10/6, 14" x 10" x 2 1/2" 11/6, 15" x 10" x 2 1/2" 11/9,
17" x 10" x 3" 14/-

1/2" flanges on two sides (inside or outside) 1/6 extra
Soldered corners (new process) 2/- extra
Panels any size up to 3ft at 4/6 sq. ft (sq. in x 3/d.)
Bases to fit: price as panels plus 1/6. For larger sizes and "specials" send for quotation, giving full particulars of your requirements. Trade and quantity discounts.

287/289 EDGWARE ROAD LONDON W2
Telephone PAD 5891/7595

Ask "ARTHURS" First

NOTE NEW ADDRESS AT
125 Tottenham Court Road
London WCI
Close to Warren Street Station

You will have the same service and obtain all your requirements in Radio Components, Electrical Goods, Accessories and Television as previously.

Test Instruments in stock include Avo, Advance, Cossor and Taylor. List on request

VALVE MANUALS AVAILABLE
Mullard 10/6 Brimar No. 7 6/-
Osrant Part 1, 2nd Edition 7/6
Post and packing 9d. each extra

Arthurs first

Est. 1919

Proprietors ARTHUR GRAY LTD
Gray House
125 Tottenham Court Road
London WCI
Telephone EUSton 5802/3/4

TV TUBE TROUBLE?

DON'T HAVE IT REPLACED HAVE IT REBUILT!

For a fraction of the cost of a new tube your old Cathode Ray Tube can be rebuilt completely to manufacturer's specification and returned to you in 72 hours.

Guaranteed for 7 months FROM THE INVOICE DATE

We can also supply 12", 14", 17" and 21" rebuilt tubes from stock, fitted with completely new Gun Units. For full details and price lists (Trade Terms available) contact:

VIDIO REPLACEMENT CO

Hales Street
Deptford High Street
London S.E.8
Telephone TID 4506



Transistor Supplies

Red Spots, 7/-; White Spots, 10/-; Yellow/Green, 7/3; Yellow/Red, 15/-; OC70, 21/-; OC71, 24/-; OC72, 30/-; OC45, 35/-; OC44, 40/-; Ediswan XA102, 40/-; XA104 (6 Mc/s), 18/-; XA103 (4 Mc/s), 15/-; XB105 (2 Mc/s), 12/6; XB104 (audio), 10/-; Electrolytics, sub-min., 2, 5, 8, 25, 50µF (15V), 3/-; Sub-min. transformers, Ardenite, D239; D240, 8/6; T1079, 12/-; D131, D132, 12/9; D167, 12/-; Mullard circuit trans., 13/6.

★

If you are disappointed with transistor circuits

TRY MORCO REFLEX

Send 8d. stamps now for our notes

★

We also supply all parts—

REPANCO MINI-7	£11.2.6
TELETRON COMPANION	£5.11.6
TRANSIDYNE	£12.6.6


TERMS—Cash with Order. Post extra; excess refunded.

MORCO EXPERIMENTAL SUPPLIES


8 & 10 GRANVILLE STREET SHEFFIELD 2
Telephone 27461

BAND III CONVERTER

Suitable Wales, London, Midlands, North Scotland, etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 27/6, plus 2/6 post and insurance. Data free with parts or available separately, 1/6. Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.



CHARGING SWITCHBOARD

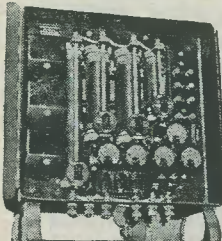

Offered at about one-twentieth of original cost. This is an ex-Government switchboard. It contains three reverse current relays, one voltmeter, one main ammeter, two secondary ammeters and three variable resistors for controlling circuits. These are original cases. Price £2.15.0, carr. 10/-, 1,260 watt model available, price £3.15.0.

BREAK-UP BARGAIN


The unit 3515 less valves and i.f. strip. This contains components valued at least £10 as follows:

- 20 Paper tubular condensers up to 1 µF
- 60 Carbon resistors, many high stability
- 40 Silver mica condensers
- 30 R.F. chokes
- 13 Octal valveholders
- 1 Yaxley switch
- 1 A.F. choke
- 2 Miniature variable condensers
- 1 Transformer
- 2 Mainsbridge condensers
- 1 Useful chassis size 18" x 11 1/2" x 7 1/2" with outer case

Plus hundreds of miscellaneous items, nuts, bolts, washers, tag strips, i.f. sockets, etc. All for 6/6, plus 5/- carriage up to 250 miles.

MEDRESCO HEARING AID

As supplied by National Health, completely overhauled and in good working order with six months guarantee. Only £3.15.0 post and ins. Complete with earphone and new ear plug but not batteries. These can be supplied as an extra for 5/- per set. Ardenite model as new—higher gain—and self-contained batteries, £7.10.0, or 10/- deposit and 16 fortnightly payments of 10/-.




If ordering by post, address to the Company nearest to you

Electronics (Eastbourne) Ltd. 66 Grove Road Eastbourne Sussex Telephone Eastbourne 6565 Half-day Wednesday	Electronics (Ruislip) Ltd. 42/46 Windmill Hill Ruislip Middlesex Telephone RUISlip 5780 Half-day Wednesday	Electronics (Croydon) Ltd. 266 London Road Croydon Telephone CROYdon 6558 Half-day Wednesday	Electronics (Finsbury Park) Ltd. 29 Stroud Green Road Finsbury Park N4 Telephone ARCHway 1049 Half-day Thursday
--	--	--	---

PULLIN SERIES 100 TEST SET

Undoubtedly a most useful instrument by a firm long famous for fine instruments. Entirely re-designed, it has a square movement with diacon plastic cover; this makes for a brighter, more readable scale, extra scale length and wider angle of vision. With the test set is included a pair of combined test prods and crocodile clips also a stand for inclining the meter at the best reading position. Ranges: a.c. volts: 0-10, 0-25, 0-100, 0-250, 0-500, 0-1,000; ditto d.c. A.C. current: 0-100mA; d.c. current: 0-2.5, 0-10, 0-100, 0-500 mA. Resistance: 0-1M and ins., or £1 deposit and 24 fortnightly payments of 10/-. **FREE GIFT**—All purchasers this month will receive a Series 100 range extender scale and data, which adds capacity 0-0.1µF in two ranges, inductance, e.h.t., and many others.

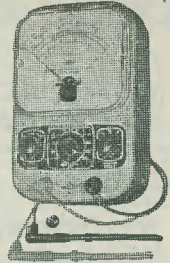

TUBE TESTER AND RE-ACTIVATOR

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but will also re-activate them. Supplied complete with full instructions. Price £3, plus 2/6 post and ins.

YAXLEY SWITCHES

4-pole, 2-way	1/6
12-pole, 2-way	1/6
6-pole, 3-way	2/-
3-pole, 3-way	1/6
9-pole, 3-way	2/-
2-pole, 4-way	2/-
4-pole, 4-way	2/9
4-pole, 5-way	2/6
2-pole, 5-way	2/6
1-pole, 12-way	2/6
2-pole, 12-way	4/6
6-position shorting switch	2/-

CATHODE RAY BARGAIN

VCR517C 6 1/2" (medium persistence) plug-in replacement for VCR97, offered at the bargain price of 8/6 each, plus 3/6 carriage.

MORGANITE POTENTIOMETERS

Single and 2-gang types available, standard size with good length spindle, all new and boxed. Single types 1/- each. Values available: 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 1MΩ, 2MΩ. Gang type, 3/- each. Values available: 5kΩ+5kΩ, 100kΩ+100kΩ, 500kΩ+500kΩ, 2MΩ+2MΩ.




TV MASKS

Latest type grey crystallate

14" 10/- 17" 12/-
Plus 1/- post

A.C./D.C. MULTIMETER KIT

Ranges: d.c. volts 0-5, 0-50, 0-100, 0-500, 0-1,000; a.c. volts: 0-5, 0-50, 0-100, 0-500, d.c. milliamps 0-5, 0-100, 0-500, ohms 0-50,000 with internal batteries. 0-500,000 with external batteries. Measures a.c./d.c. volts, d.c. current and ohms. All the essential parts including metal case, 2" moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions. Price 19/6 plus 2/6 p. & ins.



CLYNE RADIO LTD.



All "R.E.P." & "T.S.I." Components Available
Enquiries welcomed

ALL POST ORDERS AND CORRESPONDENCE TO
162 HOLLOWAY ROAD . LONDON N7
NOR 6295/6/7

18 TOTTENHAM COURT RD. LONDON W1
MUS 5929/0095
Callers welcome at both branches

A SUPERB NEW TRANSISTOR PRINTED CIRCUIT POCKET PORTABLE (BY PERDIO)



An attractive receiver employing 6 selected transistors and covering Medium and Long wavebands. Housed in smart blue, pink or cream plastic case, size 5 3/4" x 3 1/4" x 1 1/2", with tilt table stand and control knobs. All necessary components for construction of this beautiful receiver are available at a special inclusive price of £9.19.6 plus 2/6 P. & P., including comprehensive, easy-to-follow instructions (available separately price 2/6 post free).

Equipment to build yourself

• ALL PARTS AVAILABLE SEPARATELY •


WE ARE THE EXPERTS IN THIS FIELD AND CARRY THE MOST COMPREHENSIVE STOCKS IN THE COUNTRY

Send stamp for list!

CONSTRUCTOR'S BARGAINS!

E.M.I. 2 1/2" TWEETER with plastic cone. Brand new. 21/- plus 1/- P. & P.
10" RECOND. GOOD QUALITY LOUD-SPEAKER. Complete with o/p trans. As good as new. 17/6 plus 1/6 P. & P.
12" BAKERS SELHURST LOUDSPEAKERS. 15 ohms, 15 watt, 30-14,000 cps. Brand new. £4.10.0 plus 3/6 P. & P.
12" RICHARD ALLAN P.M. LOUDSPEAKER. 3 ohm speech coil. Brand new. Only 32/6 plus 2/6 P. & P.
10" LOUDSPEAKER. Ex-equip. as new. Less transformer. 3 ohm speech coil. 15/- plus 1/6 P. & P.
H.G.P. 59 CRYSTAL INSERT. Complete with l.p. and std. Sapphire Styli. Brand new. 18/- plus 9d. P. & P. Suitable for B.S.R. Monarch, etc.
CRYSTAL MIC. INSERTS. Ex-equip. but perfect. 4/6 each. Plus 9d. P. & P.
WIRING WIRE. 5 coils, 10 yards each, in different colours contained in cellophane bag. 5/- bag plus 9d. postage.
HEADSET SPECIAL. Excellent quality super lightweight low impedance magnetic headphones complete with button microphone attached and plastic ear moulds. By world-famous manufacturer. Absolutely brand new. 45/- pair. Plus 1/6 P. & P.

RADIOSETTE

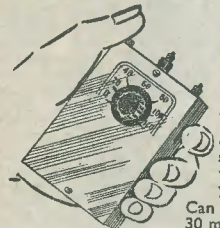


The ideal low cost transistor pocket radio for the beginner. The circuit utilises the new R.C.S. VARILoop-STICK transistor coil. A specially designed miniature .0004 tuning condenser permits the set to be in a case which fits the palm of your hand.

Can be built in 30 minutes **30/-**

All components are sold separately, full construction data including plan of parts, 2/-

ALL-WAVE RADIO **35/-**

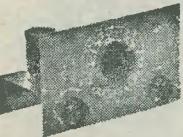Ideal for the beginner or for those requiring a simple stand-by receiver



This 1 valve S.W. receiver can be built for 35/- from our list of components, which can be purchased separately. It includes valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list.

Postage: Under 10/-, 9d. Under 40/-, 1/6
Over 40/-, post free

R.C.S. PRODUCTS (RADIO) LTD

11 Oliver Road London E17 Mail Order only

The Teletron TRANSIDYNE

Portable 6-Transistor Superhet Receiver with printed circuit

Circuit diagram with instructions available from most advertisers in this magazine, 1/- post free

SAM MOZER LTD

288 Hedge Lane London N13

Telephone PALmers Green 1748

Sole Distributors to the Trade



Radio Component Specialists since 1946. Staffed by Engineers and Radio Amateur Constructors who enthusiastically try to give you a square deal and

FULL VALUE FOR MONEY— Try Us!
SPEEDY MAIL ORDER SERVICE

BAND III TV CONVERTER

180 Mc/s-205 Mc/s
Suitable London, Birmingham, Northern, Scottish, Welsh and I.O.W. ITA transmissions.
Mk. 2 Model. Latest cascade circuit using ECC84 and EF80 valves giving improved sensitivity (12 dB) over standard circuits, built-in power supply a.c. 200-250V Dimensions only 6 1/2" x 3" x 3". Simple and easy to fit—only external plug-in connections. Wired aligned and tested ready for use. State channel required. Guaranteed. Bargain offer—good results or full refund. **ONLY £3.19.6** Carr. and pkg. 2/6
Band I/Band III changeover switch and B.B.C. aerial socket can now be fitted and wired to the above converter for 8/- extra.

CONDENSERS. Mica or s. mica. All pref. values. 2pF to 680pF, 6d. each. Ceramic types, 2.2pF to 5,000pF, 9d. each. Tubulars, 450V, Hunts and T.C.C. 0.001, 0.005, 0.01 and 0.1, 350V, 9d.; 0.02, 0.05, 0.1, 500V Hunts, T.C.C., 1/-; 0.25 Hunts, 1/6; 0.5 Hunts, 1/9; 0.001 6kV T.C.C., 5/6; 0.001 20kV T.C.C., 9/6, etc.
RESISTORS. Pref. values 10 ohms 10 megohms, 20% tol., 1/6, 3d.; 1/2W, 5d.; 1W, 6d.; 2W, 9d.; 10% h-stab., 1/4W, 5d.; 1/2W, 7d.; 5% tol., 1/4W, 9d.; 1% h-stab., 1/4W, 1/6
PRE-SET W/W POTS. TV knurled slotted knob type. 25ohms to 30,000 ohms, 3/-; 50,000 ohms, 4/-; 50,000 ohms to 2 Megohms (carbon), 3/-

VOLUME CONTROLS

Log. or lin. ratios, 10,000 ohms-2 Megohms. Long spindles. 1 year guarantee. Midget Ediswan type, 1 1/4" dia. No sw. 3/-, d.p. sw. 4/9

S.T.C. RECTIFIERS. E.H.T. types, K3/25 2kV, 5/-; K3/40 3.2kV, 6/9; K3/45 3.6kV, 7/3; K3/50 4kV, 7/9; K3/100 8kV, 13/6, etc. Mains types: RM1 125V 60mA, 4/9; RM2 125V 100mA, 5/6; RM3 125V 120mA, 7/6; RM4 250V 250mA, 16/-; RM4B type 250V 275mA, 17/6, etc.
LOUDSPEAKERS. P.M. 3 ohm, 2 1/2" Plessey, 17/6; 3 1/2" Goodmans, 18/6; 5" R. & A., 17/6; 6" Celest., 18/6; 7" x 4" Goodmans, 18/6; 8" Rola, 20/-; 10" R. & A., 25/-, etc.
SPEAKER FRET. Expanded bronze anodised metal: 8" x 8", 2/3; 12" x 8", 3/-; 12" x 12", 4/6; 12" x 16", 6/-; 24" x 12", 9/-, etc. TYGAN FRET (Murphy pattern): 12" x 12", 2/-; 12" x 18", 3/-; 12" x 24", 4/-, etc.

ANOTHER T.R.S. RECORD PLAYER WINNER

- LATEST 4-SPEED BSR Player unit (Model TU9) and "Ful-Fi" pick-up, £4.12.6, carriage 3/6
- 2-VALVE AMPLIFIER wired complete with speaker, etc., on mounting board, £3.5.0, carr. 2/6
- CONTEMPORARY STYLED LIGHT-WEIGHT CASE in maroon and grey, size 14 1/2" x 11 1/2" x 6", £1.7.6, carriage 2/6

SPECIAL OFFER
ALL 3 UNITS ONLY £9, Carriage 4/6

We can only show a small selection from our vast stocks in this advert. Write now for full Bargain Lists, 3d.



RADIO COMPONENT SPECIALISTS

70 Brigstock Road Thornton Heath Surrey Telephone THO 2188
Terms: C.W.O. or C.O.D. Post and packing up to 1/2 7d., 1lb 1/1, 3lb 1/6, 5lb 2/-, 10lb 2/9

RECORD PLAYER BARGAINS

New Reduced Prices
SINGLE PLAYERS. 4-speed BSR (TU9), 92/6; 4-speed COLLARO JUNIOR, £4.10.0; 4-speed GARRARD (4S.P.), £7.15.0, carr. and ins. 3/6
AUTOCHANGERS. 4-speed BSR (UA8), £6.19.6; 4-speed COLLARO, £7.19.6; 4-speed GARRARD (RC121/4D/MkII): plug-in head, stereo adapted, 10 gns., carr. and ins. 4/6. All above units are latest 4-speed models, fitted lightweight crystal pick-up and twin sapphire styli. Complete and ready to use.

FINEST SELECTION AVAILABLE ALL BRAND NEW AND GUARANTEED 80 OHM COAX CABLE

NOW ONLY 8d. YARD!
Highest Quality Cable, low-loss Polythene Aeraxial, semi-air spaced, feeder losses cut 50%. Standard 1/4" dia. Stranded core. Famous make.
20 yds 12/6, carr. 1/6 40 yds 20/-, carr. 2/-
Coax Plugs 1/-, Coax Sockets 1/-, Couplers 1/3, Outlet Boxes 4/6, B1-B3 Xover Unit 7/6

C.R.T. HEATER-ISOLATION TRANS.

New improved types—mains prim. 200/250V tapped. All isolation transformers now supplied with alternative no boost, plus 25%, and plus 50% boost taps at no extra cost, all in one transformer. 2V 2A type, 12/6; 6.3V 0.6A type, 12/6; 10.5V 0.3A type, 12/6; 13V 0.3A type, 12/6. P. and p. 1/6. Other voltages in course of production. Small size and tag terminated for easy fitting. P. and p. 1/6

EMITAPE RECORDING TAPE


ALL NEW AND BOXED
Type 88 (Stand.) Type 99 (Long Play)
3" ... 175ft ... 7/- 250ft ... 9/-
5" ... 600ft ... 19/- 850ft ... 24/-
5 1/2" ... 850ft ... 24/6 1,200ft ... 31/6
7" ... 1,200ft ... 30/- 1,800ft ... 45/-
Spare Reels (unboxed). 7" metal 1/6, 7" plastic (EMI) 3/6
RE-GUNNED TV TUBES—GENUINE OFFER
New heater, cathode and gun assembly can now be fitted to your old tube, re-evacuated and reconditioned virtually as new. Fully guaranteed to highest standards —as used by our own Service Department. 12" £8; 14" £8.10.0; 17" £10. We regret only Mullard and Mazda tubes at present. Delivery approximately 7 days. Carriage and insurance 12/6

MIDGET TRANSISTOR TYPE ELECTROLYTICS. T.C.C. 2µF, 4µF, 8µF, 6V, 3/6; 6µF, 10µF, 16µF, 3V, 3/6; 32µF, 15V, 3/6, etc.

VALVES—NEW BOXED—ALL GUARANTEED
1R5, 1T4, 7/6; 1S5, 1S4, 7/6; 3S4, 3V4, 8/-; 5Z4, 9/6; 6AT6, 8/6; 6K7, 6/6; 6K8, 8/6; 6Q7, 8/6; 6SN7, 8/6; 6V6, 7/6; 6X4, 7/6; 6X5, 7/6; 7C5, 9/-; 7Y4, 8/6; DAF96, 9/-; DF96, 9/-; DK96, 9/-; DL96, 9/-; 35L6, 10/6; EABC80, 9/6; EB91, 6/6; EBC41, 10/6; EBC33, 8/6; ECC84, 12/6; ECH42, 10/6; ECH81, 10/6; ECL80, 12/6; EF41, 10/6; EF80, 10/6; EF86, 14/6; EF91, 8/6; EY51, 12/6; EZ40, 8/6; EZ80, 8/6; MU14, 9/6; PCC84, 10/6; PCF80, 10/6; PCF82, 10/6; PCL83, 12/6; PL81, 14/6; PL82, 10/6; PL83, 11/6; PY80, 9/6; PY81, 9/6; PY82, 8/6; U25, 15/6; UY41, 8/6

SPECIAL—1R5, 1T4, 1S5, 1S4 or 3S4 or 3V4 per set 27/6
Hours 9 a.m.—6 p.m., 1 p.m. Wed.

Compare this! "5-VALVE PORTABLE RADIO"

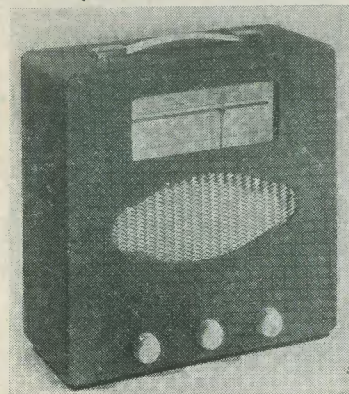

AC/DC portable radio—a well-known manufacturer's product, fully guaranteed and tested.

ONLY £7.12.6 pos 5/-

Portable polished wood cabinet ... 27/6 extra
Super rexine portable cabinet ... 37/6 extra

(As illustrated)

A REAL BARGAIN!

CRYSTAL MIC. INSERTS

3/4" square ... 3/6 1 1/2" round (Acos) ... 7/6
1/2" round (Acos) ... 5/- 2" round (Acos) ... 12/6
Suitable moulded plastic hand mic. case, only 2/6 P.P. 9d.

NEW BARGAIN CORNER

Perdio style Cabinet size 5 1/2" x 3 1/2" x 1 1/4" with fully screened 208+176pF ganged condenser, 3 ohm 2 1/2" speaker to fit; single ended 20:1 output transformer; 5-transistor printed circuit and complete circuit diagram.

ALL FOR ONLY 55/- P.P. 2/6

Ideal BASIS for a 5-transistor radio

AC/DC 200/250V PORTABLE-GRAM AMPLIFIER

Completely assembled on baffle board size 12 1/2" x 4 1/2" depth 3". Containing two Mullard valves type UL84 and UY85. Elac 7" x 4" elliptical speaker, volume control, tone control. Nothing else to buy, just plug in to mains and connect your pick-up to amplifier.

Absolute bargain 67/6 Carr. 2/6

373 MINIATURE I.F. STRIPS 9.72 MC/S



12/6 (less valves) 37/6 (with valves)
Postage and packing 2/6 (either type)

The ideal f.m. conversion unit as described in P.W., April/May 1957. Complete with 6 valves, three EF91s, two EF92s and one EB91. I.F.T.s, etc., in absolutely new condition. With circuit and conversion data.

426 CONTROL UNIT

Includes 4 EF50; 2 SP61, EB34; multibank switches; pots; transformer, etc. ONLY 30/- P.P. 5/-

All items supplied special inclusive price of

£9.19.6

P.P. 2/6

All components sold separately

Send for lists




SEND 3d. STAMP FOR NEW TRANSISTOR COMPONENTS LIST; QUARTZ CRYSTAL LIST; VALVE LIST; TRANSISTOR RECEIVER CIRCUITS, ETC.

HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

Opposite Edgware Road Tube Station

(DEPT. RCM)

Telephone PADdington 1008/9

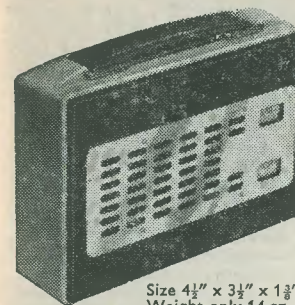

Size 4 1/2" x 3 1/2" x 1 1/8"
Weight only 14 oz.

Special Offer! POCKET TRANSISTOR RADIO

- ★ 6-transistor Superhet
- ★ Medium and long wavebands
- ★ Push-pull output
- ★ Built-in ferrite aerial
- ★ Attractive moulded cabinet with gold trimmings
- ★ Printed circuit
- ★ Fully guaranteed

The product of a well-known British manufacturer: a receiver of the latest design using Mullard and Ediswan transistors.

List price 17 gns. OFFERED AT ONLY £10.10.0 incl. batteries P.P. 2/6
NOT A DO-IT-YOURSELF—BUT A FULLY WORKING POCKET RADIO

This Portable 8-Transistor Superhet is tunable for both Medium and Long Waves and is comparable in performance to any equivalent commercial Transistor Set.

- ★ 8 EDISWAN Transistors
- ★ 250 Milliwatts output push-pull
- ★ All components identified
- ★ Medium and Long waves
- ★ Internal ferrite rod aerial
- ★ 7" x 4" elliptical speaker
- ★ Drilled chassis 8 1/2" x 2 1/2"
- ★ Point-to-point wiring and practical layout
- ★ Economical. Powered by 7 1/2V battery
- ★ Highly sensitive
- ★ Attractive lightweight contemporary case.

COMBINED PORTABLE/CAR RADIO

Two sets for the price of one

We can supply all these items including cabinet for £11.10.0, P.P. 2/6. All parts sold separately. Circuit diagrams and shopping list free.

Car Radio Conversion Components, 8/- extra
A.V.C., 4/3 extra. 325mW version, 40/- extra

NEW! Special 2 watt Power Stage usable with Any Battery Portable having an output Transformer

Size 9"x7"x3 1/2" Weight 4 lb

NEW! SOLAR-THREE

- ★ No BATTERIES!
- ★ No running costs! Uses light cells
- ★ Three transistors
- ★ Built-in Ferrite aerial
- ★ No aerial or earth

Send for free components list

A pocket transistor receiver working from daylight!

LATEST TRANSISTORS JUNCTION TYPE P.N.P.

EDISWAN XA104 6 Mc/s osc./mixer, r.f. amplifier 18/-
EDISWAN XA103 4 Mc/s i.f. and r.f. amplifier ... 15/-
EDISWAN XB104 1 Mc/s audio output and driver 10/-
(A pair in push-pull will give up to 250mW audio output)
Continental OC44 12 Mc/s osc./mixer, r.f. amp. ... 30/-
Continental OC45 6 Mc/s i.f. and r.f. amp. ... 25/-
Continental OC72 325mW in push-pull ... 20/-
Red Spot 800 kc/s audio amplifier ... 7/6
White Spot 2 to 5 Mc/s r.f. and i.f. amp. ... 12/6
Green/Yellow 600 kc/s audio amplifier ... 7/6
Red/Yellow 1.5 to 8 Mc/s r.f. and i.f. amp. ... 15/-

NEWMARKET POWER TRANSISTORS IN STOCK
Large range of sub-miniature transistor components in stock.
Send for new free list


HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

At junction of Edgware Road and Harrow Road

(DEPT. RCM)

Telephone PADdington 1008/9

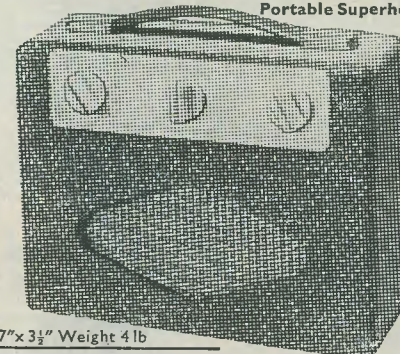
"THE TRANSISTOR-8" Push-Pull Portable Superhet



MAJOR-2

(Two-transistor pocket receiver)

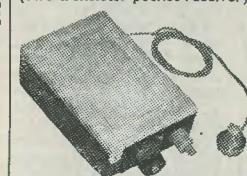
- ★ 4-stage reflex circuit
- ★ Variable tuning over medium waves
- ★ Highly sensitive
- ★ No aerial or earth
- ★ Economical
- ★ Drilled and mounted chassis
- ★ Size 4 1/2" x 3" x 1 1/4"
- ★ Internal ferrite aerial
- ★ Weight less than 4 oz
- ★ Complete layout diagram



All items can be supplied, including EDISWAN transistors, battery, case and personal phone, etc., for 72/6, post free. All components sold separately. Circuit and shopping list FREE. Call and Hear Demonstration Model.

MINOR-1

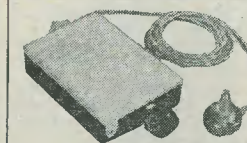- ★ Variable tuning on medium waves
- ★ 3-stage reflex circuit
- ★ Highly sensitive
- ★ Internal ferrite aerial
- ★ Drilled chassis
- ★ Long-life battery
- ★ Complete constructional details
- ★ Size 3" x 2" x 3/4"



Total cost, including transistor, personal miniature phone, case, battery and complete circuit and layout diagrams, 52/6 post free. All components sold separately. Circuit and shopping list FREE.

The TRANSIDYNE RECEIVER

(Page 119 Sept. '58)
Complete Kit £11.19.6
or less transistors £8.15.6
FREE—Special printed circuit
solder with each kit
Only genuine Teletron parts
Full details and price list 1/- post
free

Heavy duty 500pF differential condensers 3/-. Small solid dielectric variables, 0.0001µF 3/-; 0.0003µF 3/9; 0.0005µF 4/-. Resistors from 3d. each. Asstd. carbon (many 5%) 25 for 3/11, 50 for 7/6. Hi-Stabs 10% ½ watt 6d.; 10% 1 watt 9d.; 1% ½ watt 2/-. Many odd values available at lower prices. Send requirements for quotation. Ajax Crystal Set complete, 14/6; L.W. 15/-; Case and chassis 5/9. Teletron HAX coil 3/-. REP Dual Wave Xtal Coil 2/6. Headphones, lightweight, 14/- and 16/-; Nuts, bolts, washers, tags. Well assorted: 25 1/-; 72 2/9. 144 5/-. Miniature Neons 1/10.

TRANSMITTING KEYS

Heavy duty with 27 ins twin rubber cable, fitted robust jack plug. Ideal also for Morse practice. The plug alone is worth the price!
Limited number at 1/6 each

Sensitive Transistor Receiver

NEW LOW PRICE
(Page 298 Nov. '58)
All parts now available for this excellent receiver.
Complete Kit (less spkr.) £4-18-9
or less speaker and transistors £3.10.0
(S.A.E. for price list)
7" x 4" Speakers 22/6
(Others available)

TRANSISTOR ITEMS. Electrolytics 8µF 6V, 16µF 12.5V, 32µF 3V, 5µF 12.5V, 5µF 40V, 2.5µF 40V, 1.6µF 6V, 25µF 6V. All 3/- each; 100µF 6V 3/-; Paper 0.01, 0.001, 0.002, 0.005µF, all 8d. each. Transistor Holders 1/- each, 6 for 5/9, 11/- doz. Ardente T.1065 transformers (page 911—July), 12/-. Subminiature Speakers 1½" round, 27/-; 2" x 3" elliptical, 33/-. Sub-miniature Output Transformers, single-ended or p/p, 12/6. Volume Controls, button type (totally enclosed), 47k and 1MΩ, 2/6; preset skeleton type 5k, 2/6; spindle type, ½M, 1M, 2M, 4/3 (page 705—'R.C.' May). Ardente Deaf Aid Earpieces E.R.100, with cord and plug. Limited number at 13/9. Ardente Catalogue 6d. Transistors: Yellow/Red 15/-; White Spot 14/-; Yellow/Green 7/6; Red Spot 7/6

Multicore Solder 4d. yd, 19 ft reel 2/6, 1lb reel 14/9. Fine gauge for printed circuits, 40 ft reel 2/6. Switches, s/p from 2/3, d/p from 3/6. Ferrite Rods 8" x ½" diam., 2/-. Mains neon indicators with built-in resistor. Domed top, chrome bezel, 1" long ½" diam. Opal, red, amber, 3/10; green 4/7

We recommend the 'LITESOLD' soldering iron for all work and especially printed circuits. Mains or battery. 21/6 complete (state mains voltage)

CONNECTING WIRE p.v.c. 50ft coil, 5 colours, 1/9. Sleeving, 15 ft, asstd. colours and thicknesses, 8d. Tinned Copper Wire 24 s.w.g., 15ft 8d. Combined pack (3 above items) 2/9

NEW EDISWAN TRANSISTORS

Now in stock
XA104 R.F. (4 Mc/s) 18/-
XA103 I.F. (2 Mc/s) 15/-
XB104 A.F. 10/-

Also a full range of
PYE 'GOLTOP' r.f., a.f. and power transistors.
Enquiries welcomed

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-. Trade advertisements will be accepted at 9d. per word, minimum charge 6/-. If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

PRIVATE

FOR SALE. New ex-Government multi-range test-meter, normally 35s. each, £15 for crate of 22, carriage 35s. Box No. E.197.

FOR SALE. Expensive Decca trolley gram cabinet, walnut, £4, with autochanger £8. Photo available. Ferranti 18 gns. a.c. transportable radio, half price. Classical L.P. records, mint 21s. each. S.A.E.—9 Brenda Crescent, Thornton, Liverpool 23.

FOR SALE. Aspiden tape deck, 7in reel of tape, amplifier, speaker and microphone, £12, o.n.o. 9in TV, not repairable but good tube and 15 valves, 10s.—Ring BOW 9846 after 6 p.m.

FOR SALE. Handbooks 19 Set Mk. 2. Circuit, R.C. values. Full details. P. & P. 6s. H. Lewis, 16 Belle View, Belgrave Road, Birmingham, 12.

FOR SALE. Transistorised 3-channel radio control receiver, prototype described in August 1958 *Radio Constructor*, complete with 5 transistors, £5. Canadian Marconi crystal calibrator, generating 1 Mc/s, 100 kc/s and 10 kc/s markers, £2 10s. Od. 160/80/40 metres phone or c.w. transmitter/receiver, for portable or field use, a.c. mains or 12V battery, fully self-contained, £12.—Pearson, 37 Vale Road, Bushey, Herts.

FOR SALE. *Wireless World* 1954, 1956 and 1958, 1s. each plus postage.—Hawkins, 86 Alphington Road, Exeter.

SONOMAG adaptatape tape recorder (Mark IV Collar deck), new, unused, in maker's carton, £37 o.n.o.—222 Carshalton Road, Sutton, Surrey.

MURPHY V150 12in working tube U/S £4. White-Ibbotson wall projector, 4ft x 3ft picture, 12-channel tuner, complete working, requires attention, circuit supplied but no cabinet, £10. Pre-amplifiers, new, with EF54 valve made by Cossor 7s. 6d., postage 2s. 6d. New 4ft fluorescent batten fitting, 27s. 6d., carriage 3s. 6d.—381 Staines Road, Hounslow, Middlesex.

AMATEUR DISPOSING surplus stock, large quantity valves, etc. Send s.a.c. for list.—66 St. Anthony's Drive, Chelmsford, Essex.

FOR SALE. Glass dials, assorted, L.M. and L.M.S., M.S. 3s. each.—Gilpin, 119 Wulfric Road, Sheffield 2, Yorks.

WHAT OFFERS? "Mini-7," long and medium waves, carrying case, hearing aid phone.—Box No. E.198.

WANTED. 3H tapped choke, Bulglin LF43 or Varley DB18.—McLeod, "Rosdene," Forres, Morayshire, Scotland.

WANTED. Philco BP413 receiver.—Prouse, 5 Tresluggan Road, Plymouth.

FOR SALE. Portable top band Tx/Rx. Tx: EF40, EL91, EL41 mod., with carbon mic., EL41 co/pa. Rx: EF91, EF92, EL91, TRF. In black crackle cabinet 12in high, 8in wide, 7in back to front. Chrome handle on top. Rotary converter power supply, 12V input. With key, phones, 2 xtals, and whip antenna. Smart little unit, £12.—Box No. E.199.

NEW SURPLUS... BY RETURN

1A3	2/-	6Q7G	7/6	803	20/-	EY51	12/6
1L4	5/-	6Q7GT	9/6	830B	15/-	EY86	12/6
1R5	7/6	6SA7M	7/6	866A	15/-	EZ40	8/-
1S5	7/-	6SG7M	7/6	959	5/-	EZ80	8/-
1T4	6/-	6SH7M	5/-	1616	5/-	EZ81	8/-
2A3	8/6	6SJ7M	7/6	1629	4/-	GT1C	8/6
2X2	3/6	6SK7M	6/6	5763	10/6	GK32	12/6
3A4	4/6	6SL7GT	7/6	EA50	1/6	HZ24G	25/-
3Q4	7/6	6SN7GT	5/6	EABC8010/-		KT33C	9/6
3S4	8/6	6SO7M	7/6	EAC91	4/6	PCC84	10/6
5R4GY	12/6	6V6G	7/6	EAF42	9/-	PCF80	12/6
5Y3G	8/6	6V6GT	8/6	EB34	2/-	PCF82	10/-
5Y4G	6/6	6X4	6/-	EB91	4/6	PCL82	12/6
6AC7M	5/-	6X5GT	6/6	EBE33	7/6	PL81	14/6
6AG5	3/6	7B7	8/-	EBE41	8/6	PL82	9/6
6AK5	5/-	7C5	8/-	EBF80	9/-	PL83	10/6
6AL5	4/6	7C6	8/-	EBF89	9/6	PY80	8/-
6AM6	5/-	7S7	9/6	ECC82	8/6	PY81	8/6
6AQ5	8/6	7Y4	8/-	ECC83	9/-	PY82	9/6
6AT6	7/6	12A6M	6/6	ECC84	10/6	PY83	8/6
6AU6	7/6	12A7	8/-	ECC85	9/-	R19	12/6
6B8G	3/6	12A7	8/6	ECC86	12/6	TT11	4/-
6BA6	8/6	12AU7	8/6	ECC87	11/6	UAF42	9/-
6BE6	7/6	12AX7	9/-	ECC88	9/-	UAC41	9/6
6BH6	7/6	12AU6	9/-	ECC89	10/6	UBF89	9/6
6BJ6	7/6	12BE6	8/6	ECC90	12/6	UC85	9/6
6BR7	11/6	12C8M	7/6	ECC91	12/6	UCH42	9/6
6BW6	9/-	12K7G	6/6	EF36	4/-	UCH81	9/6
6C4	4/6	12Q7GT	6/6	EF39	5/-	UF41	9/6
6C5M	5/6	12SC7M	2/6	EF41	9/6	UF89	9/6
6F6M	5/6	12S7M	5/-	EF50	2/6	UL41	9/6
6J5GT	5/-	12SK7M	5/-	EF50(S)	4/-	UY41	8/6
6J5M	6/-	12SQ7M	8/6	EF80	7/6	UY85	8/6
6J6	4/-	35L6GT	9/6	EF85	8/6	UABC80	
6J7G	7/6	35Z5GT	8/6	EF86	14/-		10/6
6K7G	3/6	35Z4GT	6/6	EF89	9/6	VU39	9/6
6K8G	6/6	42	7/6	EF91	5/-	VR150/30	
6K8M	10/6	50L6GT	9/6	EL32	4/-		7/6
6H6M	3/6	80	8/6	EL41	9/6	VS70	3/-
6L6G	8/-	446A	10/6	EL84	9/-	XP1.5	3/-
6L6M	10/6	801A	7/6	EM80	9/6	Z77	5/-

M.C. Meters. 2½" rd. fl. (2" dial), 0-1mA, 21/-; Ditto but scaled 0-50V, 16/6. 0-500µA, 17/6. 2½" rd. plug in electrostatic 0-1-500V, 16/6. 2" sq. fl. 0-300V, 50-0-50A, 11/6. 0-50mA, 9/6.

R107 Front End for r.f. mix, osc. 3 bands 1.2-18 Mc/s (465 kc/s i.f.) with half-moon calibrated dial and slow motion drive. 40/-, carr. paid less valves.

Acos Stick Mikes, MIC39-1. List price £5.5.0. Few only new boxed less stand, 55/-; MIC33-1 (list 50/-), our price 32/6.

Transistors. Audio, yellow/green, 6/6; OC70, 12/6; OC71, 15/-; yellow/red r.f. to 8 Mc/s, 13/6.

Midget Mains Trans. (same size as std. o/p trans.) Input 230/250V, o/p 220V 20mA, 0.6A. Ditto but 175V 25mA. Both types 11/9 each, post paid.

Few only Trans./Rec. 17 Mk. 2. New 45/-, used 29/6; and Performance Meters NEW, 32/6 or 22/6 less valves. Both carr. paid. See previous ads.

SPECIAL OFFER OF VALVES IN £1 PARCELS

(plus 2/6 p/p per parcel irrespective of total value of order)

1A3, EA50, 12SC7M, 16 for £1
2X2, 6AG5, 6B8G, 6H6M, EB34, EF50, 1626, 12J5GT, 6K7G, EL32, TT11, 12 for £1
6AC7, 6C4, 6J6, 1616, 1629, EF50(S), EAC91, 12SJ7, 12SK7, 8 for £1
3A4, 801A, 1625, 5 for £1
6SN7, 6K8G, 12A6, 12K7GT, 12Q7GT, 35Z4GT, 3Q4, 5Y4G, 6BH6, 4 for £1

Fully shrouded Chokes 10H 100mA, 15/-.

Post 5d. to £1, 1/6 to £2 S.A.E. enquiries

JOHN ANGLIN

385 CLEETHORPE ROAD GRIMSBY Lincs
Telephone 56315

QUOTATIONS gladly given (S.A.E. please)
R. FAGELSTON (MAIL ORDER) Please add Postage to above prices
46 HARDWICKE ROAD · LONDON N13

★ VALVES NEW TESTED AND GUARANTEED ★

1R5	7/6	6X4	7/6	DK91	7/6	EF92	5/6
1S5	7/6	6X5G	6/-	DK92	9/-	EL41	10/-
1T4	6/-	12AH8	9/6	DK96	9/-	EL84	9/-
3S4	7/6	12A7	7/6	DL92	7/6	EL91	7/6
3V4	8/-	12AU7	7/6	DL94	8/-	EY51	10/6
5U4G	6/-	12AX7	9/-	DL96	9/-	EZ35	8/-
5Z4G	9/-	12K8GT13/6	8/6	EB91	5/6	EZ40	8/-
6AM6	6/9	12K7GT	8/6	EBC41	8/-	EZ80	8/-
6AL5	5/6	12Q7GT	7/-	EBF80	9/6	EZ81	8/6
6AT6	7/6	25A6G	10/6	ECC81	7/6	KT33C	9/6
6BA6	8/6	25L6GT	7/6	ECC82	7/6	PCF82	11/-
6BE6	7/6	35Z4GT	8/6	ECC83	7/6	PL82	10/6
6BR7	10/6	35L6GT	9/6	ECC84	8/6	PY81	8/-
6BW6	8/6	53KU	11/6	ECC85	11/-	PCC84	9/-
6J5G	5/6	807	6/9	ECH81	10/6	PCF80	9/6
6J7GT	8/6	5763	10/6	ECH42	10/-	U76	8/6
6K7G	2/6	DAF91	7/6	ECL80	12/6	UBC41	10/-
6K8G	7/6	DAF96	9/-	EF36	7/6	UCH42	9/-
6Q7GT	8/6	DF91	7/6	EF39	5/6	UF41	10/-
6SL7GT	8/-	DG96	9/-	EF41	9/-	UL41	9/6
6SN7GT	8/6	DH76	8/6	EF80	8/-	UY41	8/-
6V6G	7/6	DH77	7/6	EF91	6/9	W76	8/6

Matched Pairs. EL84, 23/-; 6V6G, 17/-; 6BW6, 18/-; KT33C, 19/6; KT66, 27/6; 807 14/6 pair

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any four, 27/6 per set
P.P. Op. Transformers. MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6
Volume Controls. All values, long spindle. L/S 3/-, s.p. 4/-, d.p. 4/9, ext. spkr. control 3/-
W.W. Pots. Pre-set 3/-; 3W long spindle 5/6, s.p. 6/6
P.M. Speakers. 3 ohm. 5" 16/6, 6½" 17/6, 8" 21/-, 10" 25/-, 12" 30/-, Bakers 12" 15 ohm 15W, 90/-
Coaxial Cable. 75 ohm ¼" stranded, 8d. yd; semi-air spaced, 9d. yd; screen cable single and twin, 9d. yd
Coaxial Plugs 1/- each; Sockets 1/- each
P. and P 9d. to £1; 1/6 to £2; over £2 post free. C.O.D. 2/6

R. COOPER G8BX 32 SOUTH END CROYDON Surrey CROYDON 9186

C.R.T. Isolation Transformers with nil, 25% and 50% boost, low capacity a.c. mains 200/250V for 2V 4V. 6.3V and 13V tubes. All 10/6 each

Valveholders. 4, 5, 7 pin English and U.S.A. B7G, B9A, 1.0 Mc. B8G, 9d. each; B7G, B9A with screening can, 1/6; B12A, 1/3 Aladdin formers ½" with core, 8d. each

Scotch Boy Recording Tape, 1,200ft reels, 27/- Jack Plugs, miniature standard, 3/-; Sockets 3/- 2-Gang Condensers, 0.0005 small size, 7/6

I.F. Transformers, 465 kc/s, small size, 7/6 pair
Capacitors, small mica, 5% 1pF to 100pF, 8d.; 120pF to 1,000pF, 9d.; 1,000V wkg. .01, .0015, .0025, .004, .005, 1/- each

Crystal Diodes, G.E.C., 1/6 each
Headphones, lightweight, 4,000 ohm, 16/6 pair
Ceramic Capacitors, close tol. 500V for V.H.F., 9d.
Paper Capacitors, tubular, .01, 1,000V, 1/-; 0.1 to 0.5 500V, 10d.

Paper Blocks, 4µF, 1,000 wkg., 3/6
Rectifiers, contact cooled, 250V 50mA, 7/6; 85mA, 9/6
Reaction Condensers, .0001, .0003, .0005, 4/6 each
Heater Trans. 200/240V, 6.3V, 1.5A, 7/6

Resistors, ½ and ¼W, insulated, 4d. and 6d.; 1W, 8d. 6W W.W., 1/-; 10W, 2/-

Electrolytics. Wire ends. 25/25V, 1/6; 50/50V, 2/-; 12/50V, 9d.; 8/450V, 2/-; 16/450V, 2/9; 16/500V, 3/6; 32/450V, 4/-; 8+8/450V, 4/6; 8+16/450V, 4/6; can types: 16/450V, 3/6; 16+16/500V, 6/-; 32/500V, 6/6; 32/450V, 6/6; 20+20/450V, 4/6; 6+14+120/275V, 7/6

Wavechange Switches, midget: 1p 12V, 2p 6W, 3p 4W, 4p 3W, 4p 2W, long spindles, 4/6

Toggle Switches. QMB, s.p.s.t., 2/-; s.p.d.c., 3/3; d.p.s.t., 3/6; d.p.d.c., 4/-

Chokes, 80mA, 15H, 8/6; 100mA 10H, 10/6; 150mA 10H, 14/6

Solder, Multicore, 4d. yd; Sleeving 2mm, 3d. yd

EDDY'S (NOTTM) LTD

Dept, RC 172 ALFRETON ROAD NOTTINGHAM

GUITAR PICK-UP "THE PLECTRO." Super hi-fi non-acoustical universal fitting, 3" x 1 1/2" x 1 1/4". High output. Complete with lead and plug. Full and easy instructions. 39/11 each, post, etc., 1/-.

MIDGET BATTERY ELIMINATORS. To convert most types battery portables to mains operation, 57/6. Size 3 1/2" x 2 1/2" x 1 1/2". Post 2/6. (Please state make and model number.)

MORSE TAPPERS. Plated contacts, adjustable gaps. Heavy duty, good quality, 3/6 each, post 9d.

GERMANIUM DIODES. 1/- each, 10/- doz. Post 4d.

ALL ABOVE ARE NEW AND GUARANTEED

NEON MAINSTESTER/SCREWDRIVERS, 4/6 each, post 6d.

JACK PLUGS. Standard type 1/11, post 4d.

TRANSISTORS. Yellow/green spot 6/11; R.F. yellow/red spot 13/11. Post 4d.

ACOS MIKE INSERTS 4/11 each. High quality. Can be used for tape recorders, baby alarms, musical instruments, etc. Post 9d.

THROAT MIKES 1/- each, 11/- doz. Post 6d. Can be used for electrifying musical instruments.

RECORDING TAPE. 1,200 ft plastic reels 7". 10/11, post 1/-.

TUBULAR WIRE END CONDENSERS (not ex-Govt.). 8µF 450V 1/9; 8 x 8µF 450V 2/9; 16µF 450V 2/9; 16 x 16µF 450V 3/9; 16 x 8µF 450V 3/11; 32µF 450V 3/9; 32-32µF 450V 4/- . Post 9d.

ALL ABOVE ARE NEW AND GUARANTEED

NEW AND SURPLUS GUARANTEED VALVES. ALL TESTED BEFORE DESPATCH

AZ1	12/6	ECC81	6/-	EF50	3/-	MU14	9/-	UF41	8/6	6C4	4/9	6SA7M	7/6	12AT6	10/6
AZ31	10/-	ECC82	8/-	EF50(R)	4/11	P61	2/11	1C5GT	12/6	6CH6	12/6	6SG7M	7/6	25L6GT	9/11
B36	15/6	ECC83	8/11	EF80	7/11	PCL83	13/6	1D5	10/-	6F1	9/-	6SH7M	7/6	25Z4G	9/11
CY31	12/11	ECC84	8/11	EF85	7/-	PL81	15/-	1H5GT	12/6	6F6M	7/6	6SL7GT	6/11	35L6GT	9/11
DAF96	8/6	ECC85	8/11	EF86	14/-	PL82	8/11	1R5	7/6	6F13	9/-	6SJ7M	7/6	35Z3	13/11
DF96	8/6	ECC80	12/6	EF91	6/9	PL83	10/6	1S5	7/6	6F15	11/-	6SK7GT	5/6	807(B)	3/9
DL96	8/6	ECC42	10/6	EF92	5/6	PY80	8/6	1T4	5/6	6H6M	3/6	6SN7GT	5/9	807(USA)	3/9
DK96	8/6	ECL80	12/6	EL41	9/6	PY81	8/6	3Q5GT	9/6	6J5GT	3/11	6V6G	5/11		5/6
EB34	1/11	EF36	4/6	EY86	12/6	PY82	9/6	5U4G	6/6	6J3M	3/11	6V6GT	6/6	954	1/6
EB91	5/11	EF37	5/-	EZ80	8/6	TD4	12/6	5Z4G	10/-	6K7G	2/11	6X5GT	6/6	955	3/11
EBC33	7/6	EF40	14/-	EZ81	8/6	U25	15/6	6A7	12/6	6K8G	7/6	10F1	9/6	956	2/11
EBC41	9/6	EF41	9/-	GTIC	15/6	UBC41	9/6	6B8G	2/11	6L6G	6/11	12AH7	7/6		
EBF90	9/6	EF42	11/-	L63	4/6	UCH42	9/9	6B16	7/6	6Q7G	8/6	12AH8	10/6		

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk

C.O.D. or C.W.O. only. S.A.E. with all enquiries. Postage and packing 6d. per valve extra. Over £3 FREE

Send 1/- for 56-page Illustrated Catalogue.

Trade enquiries invited

PP COMPONENTS LTD.

★ FOCUS MAGNETS AND T.V. SPARES

9/9. Brand new, 38 mm. Incorporating picture shift controls. P. & P. 1/3
5/9. Elac 35-38 mm. Permanent magnet. Salvage. P. & P. 1/9
12/9. Elac. Brand new. 35-38 mm. P. & P. 1/9
3/9. Plessey, 35 mm. Permanent magnet type. Salvage. P. & P. 1/9

★ FRAME OUTPUT TRANSFORMERS, 3/9.

To match low impedance coils. P. & P. 1/3

★ SCANNING COILS, 10/6. Low impedance.

38 mm. Brand new. P. & P. 1/3

SPECIAL OFFER

★ T.V. SLIDER CONTROLS, 5/- . 5 on a panel, 1kΩ, 5kΩ, 10kΩ and 2 at 50kΩ. Complete with knobs. P. & P. 1/-

★ 17" T.V. MASKS, 9/9. Brand new. Good quality. Grey or white plastic. P. & P. 2/3.

★ 12" T.V. MASKS, 1/9. Slightly soiled. Easily cleaned. Rubber. P. & P. 2/3

★ I.F. STRIPS—POWER PACKS

Sound & Vision Strip 5/9. S/het. Takes 6 EF91, 1 6D2, 1 6F14. Valves extra. Not tested. Free drawing. Post 2/6

Sound & Vision Strip Plessey 25/6. S/het. Takes 6 6F1, 2 6D2 valves (extra). Tested. Free drawing. P. 2/6

Power Pack & Amplifier 19/6. Output stage PEN45. Smoothed h.c. 325V 250mA. O.p. trans., choke, etc.; 4V 5A, 4V 5A centre tapped. Less valves. Not tested. Carr. 5/6

Power Pack & Amplifier 19/6

Power Pack & Amplifier 19/6

Power Pack & Amplifier 19/6

Power Pack & Amplifier 19/6

Power Pack & Amplifier 19/6

Timebase 4/9. Including scanning coil, focus unit, line trans., etc., less valves. Bargain. P. & P. 3/6

Co-ax. Cable 6d. yd. Good quality. Cut to any length. Post on 20 yds 1/6. 45/- per 100 yds. P. & P. 3/6

TRANSFORMERS

Mains Power Trans. 12/9. 350-0-350V 250mA, 4V 5A, 6.3V 5A, 4V 5A centre tapped. Drop through type. Post 3/9

Mains Power Trans. 12/9. 350-0-350V 250mA, 22V 3A, 6.3V 5A, 6.3V 4A, 4V centre tapped. Post 3/9

Mains Trans. 5/9. 280-0-280V 80mA, 6V-4V heaters. 200-250 prim. Post 2/3

Mains Trans. 3/9. 350-0-350V 80mA, 12V-4V heaters. 200-250V prim. Post 2/3

O.P. Trans. 1/3. Salvage, guaranteed. Standard size. 2-5 ohms. Post 1/- . 20 for £1, carr. 5/6

SPEAKERS 8" P.M. 5/9

Limited quantity of these modern type speakers. All tested and "money back guarantee." They have a slight cone fault that is repaired. Not affecting the quality. Post on 1, 2/6; 2, 3/6

SPEAKERS 8" P.M. 8/9

Ideal for extension in kitchen or bedroom. With o.p. transformer, 10/- . P. & P. 2/9

EXTENSION SPEAKER 19/9. Complete in attractive cabinet, with switch and lead. Ideal present. P. & P. 3/6

Car Aerials 6/9. Plated, whip antenna; 50" long, collapses to 11", 1-hole fixing. Post 1/-

Visconal Condensers 5/9. 0.1µF at 7kV working and 0.001µF at 12.5kV working. Post 1/-

P.P. COMPONENTS LTD

(Dept. C3) 219 ILFORD LANE ILFORD ESSEX
Stamp for FREE catalogue, Regret U.K. only
ILford 0295



SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/- . Trade advertisements will be accepted at 9d. per word, minimum charge 6/- . If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

continued from page 637

PRIVATE—continued

WANTED. Bug key. State price.—P. R. Cavanagh, 136 Duchess Road, Sheffield 2, Yorks.

SALE. Labgear Txing Coils, DSL/14; DSL/21, at 7s. 6d. each. Microphones, hand, No. 7 and No. 4A at 7s. 6d. each. Charging meter 30-0-30 amp., 5s. Eddy-stone Tx variable condenser, Type 831, 28-28pF. at 15s. Maxi-Q coils, chassis mtg., Range 1, white and yellow, at 2s. 6d. Morse keys on metal base, 3 1/2 in x 6 in. Neat job, 7s. 6d. G.E.C. xtal, 100 kc/s, 30s. Headset adaptors, high to low, at 5s. Pair R.F. meters, 0-3 amp. 2in sq., 10s. R.F. meter, 0-0.5 amp. 2in sq., at 5s. Ammeter d.c. 0-0.5 amp. 2in sq., at 10s. Volt meter, 2in sq., 0-20 at 5s. Battery testing volt meter, 12V/120V, 5s. Speaker in varnished wood cabinet, 12 x 12 x 6 in, 15s. Rotary converter, 12V in; 285V, 60 mA out, 10s. Rotary converter, 12V in; 480V, 40mA out, 10s. Transformers, inter-stage audio, 10s. Postage and packing extra on all items.—East Keal, Romany Road, Oulton Broad, Lowestoft, Suffolk.

AUTOMATIC MORSE CODE SENDER for sale. Suitable for C.W. call sign sending, etc. Hand tape perforator and reel paper tape. 230V, a.c., variable speed, £5.—Box E.196.

TRADE

100 TELEVISION SERVICE SHEETS, covering 330 models, 18s. 6d., details free. All types service sheets, sale/hire.—Hamilton Radio, BCM/DATA4, London, W.C.1.

ALMOST ANY COMPONENT, valve, tube, etc., available cheap from dismantled sets (Radio and Television) 1938-1958. Thousands of transformers, coils, etc., 9-10in tubes, 30s. EF80, EF91, EB91, 3s. 6d. each.—St. John's Radio, 156 St. John's Hill, S.W.11. BATtersea 9838.

MORSE CODE TRAINING. Special course for Beginners. Full details from (Dept. R.C.), Candler System Company, 52 Abingdon Road, London, W.8.

PANL, recognised for many years as the unique one-coat black crackle finish. Brush applied, no baking. Available by post in 1/4 pint cans at 3s. 9d. from G. A. Miller, 255 Nether Street, London, N.3.

THE INTERNATIONAL HAM HOP CLUB is a non-profit-making organisation open to RADIO AMATEURS and SHORT WAVE LISTENERS. OBJECT: To improve international relationships through an organised system of hospitality. MEMBERS offer overnight hospitality to visiting members, entrance fee 2s. 6d. ASSOCIATE MEMBERS invite radio amateurs to visit their stations. S.A.E. for FREE Associate membership. FAMILY EXCHANGE holidays arranged, also FRIENDSHIP LINKS between radio clubs. H.H.C.'s official journal, *Ham Hop News*, 5s. per annum. Hon. Gen. Secretary: G. A. Partridge, G3CED, 17 Ethel Road, Broadstairs, Kent.

continued on page 640

REVACUUMED TV TUBES

All Guaranteed 6 months, carr. and ins. 12/6
9-10", 3/16, CRM91, MW22/7-14, etc., £2.10.0. 12", CRM 121A-B, MW31/7-14-17-18, etc., £4.10.0. 14", 141K, MW36/24, CRM141/2, etc., £4.10.0. 15-16", 6901A, CRM153, etc., £5. 17", MW43/64, C17BM, CRM171, etc., £4.15.0

TRANSISTORS. Red Spot, 7/-; White Spot, 12/6

GUARANTEED VALVES—24-HOUR SERVICE															
6AM6	5/-	20P1	13/6	EF89	9/6	PY31	10/-	6BA6	6/6	B36	11/-	EF91	5/-	PY80	8/-
6BE6	6/6	EAF42	9/-	EL33	11/-	PY81	8/6	6C4	4/6	EB41	7/6	EL41	9/6	PY82	8/9
6C9	9/6	EB91	4/6	EL42	9/6	PY83	8/6	6D2	5/6	EBC33	7/-	EL84	9/6	PZ30	12/-
6F1	9/6	EBC41	9/-	EY51	11/-	SP61	3/-	6F12	6/6	EC91	4/6	EY86	15/-	U22	7/6
6F13	9/6	ECC81	7/6	EZ40	8/-	U24	12/6	6F14	11/-	ECC82	6/6	EZ41	10/-	U31	8/-
6F15	11/-	ECC83	8/6	EZ80	7/6	U801	16/-	6J6	4/6	ECC84	9/9	GZ32	10/-	UBA42	9/-
6L1	11/-	ECC85	9/-	KT33C	9/6	UBA41	9/-	6L18	9/6	ECH42	9/3	KT36	11/-	UBC41	8/6
6L19	9/6	ECL80	11/-	KT61	9/6	UCH42	9/6	6LD20	9/6	EF36	4/-	P61	2/6	UF42	9/-
6P28	11/-	EF39	5/-	PCC84	9/6	UF41	9/-	6X4	6/-	EF41	9/6	PCF80	9/6	UL41	8/6
10F1	9/6	EF42	12/-	GZ32	10/-	UL44	9/6	10P13	11/-	EF50(A)	3/6	PL38	13/-	UL46	9/6
10P14	12/-	EF50(B)	4/9	PL81	14/6	UUB	12/6	20D1	9/6	EF80	6/-	PL82	9/-	UY41	8/-
20F2	9/6	EF85	7/-	PL83	11/-	Z66	15/-								

For all details send 6d. for 12-PAGE LIST OF 800 SNIPS
Post 1/3 in £1. Min. 9d. No C.O.D.
10,000 SNIPS FOR CALLERS

TECHNICAL TRADING CO
350/352 FRATTON ROAD PORTSMOUTH

RADIO AMATEURS . . .

get your Licence in
Half The Usual Time!

You must be a good Morse operator! A "slap-dash" 12 w.p.m. neither satisfies the authorities, yourself, nor your operator friends. Morse operating is an exacting art unless your training is made simple and is based on sound fundamentals. For this reason, the Candler System was invented to take the "grind" out of Code tuition, turning a tricky subject into a pleasurable pursuit.

★ Send 3d. stamp for the "Book of Facts"

CANDLER SYSTEM CO
(Dept. 55 RC) 52b Abingdon Rd London W8
Candler System Company Denver Colorado U.S.A.

HIGH FIDELITY

Quality components of all types always in stock for the
MULLARD 2-VALVE PRE-AMPLIFIER
MULLARD 3-VALVE 3-WATT AMPLIFIER
MULLARD TAPE PRE-AMPLIFIER TYPE C
Circuits free on request

510 AMPLIFIER FM TUNER	circuits 3/6
912 PLUS AMPLIFIER	" 4/-
JUPITER STEREO UNIT	" 2/6
RADIO CONSTRUCTOR FM	" 2/-
MERCURY SWITCHED FM	" 2/-
DENCO FM TUNER	" 1/6

Price list available on request
J. T. FILMER 82 DARTFORD ROAD DARTFORD KENT
Telephone Dartford 4057

Forrest

Transistor Transformers
for Quality Equipment

H. W. FORREST (TRANSFORMERS) LTD.
349 Haslucks Green Road Shirley Solihull
Warwickshire Telephone SHirley 2483

**BRASS, COPPER, DURAL,
ALUMINIUM, BRONZE**

ROD BAR SHEET TUBE STRIP WIRE
3,000 STANDARD STOCK SIZES

No quantity too small List on application

H. ROLLET & CO LTD

6 Chesham Place SW1 SLOane 3463
Also at Liverpool Birmingham
Manchester Leeds

Perforators, Reperforators, Teleprinters, Spare Parts,
Terminals and V.F. Telegraph multi-channel units:
Testing Equipment: Telephone Carriers and Re-
peaters: Signalling Rectifiers 26B, 43A, RA87, etc.,
Relays, Transformers, Filters: Repeating and Retarda-
tion Coils: Racks, Relay Bases. British, American and
German Equipment.

BATEY & CO. Gaiety Works Akeman Street
Tring Herts Tel TRING 2183

BUILD YOUR OWN TAPE RECORDER

Two-speed, twin track tape deck, kit of parts £8.5.0
Amplifier kit £7.15.0 less valves. Cabinet and speaker
£3.19.0. Send for full details of these excellent kits.

Also available made up

WISEMAN'S

21A ANCASTER ROAD BECKENHAM KENT

H.A.C. THE ORIGINAL SUPPLIERS OF SHORT-WAVE KITS

One valve Super Sensitive All-dry Short-wave Receiver
Model "K." Complete kit including valve and chassis.
77/- (Other S.W. kits from 25/-) Before ordering
call and inspect a demonstration receiver, or send
stamped envelope for full specification, catalogue and
order form.

H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)
11 OLD BOND STREET LONDON W1

CARRIAGE PAID BARGAINS

Aerial D/F Loop Unit (matched cores) recent model
(new), 10/-; Heavy duty R.F. Dummy Loads in screened
box (new), 20/-; 500pF 3-gang condenser, 1155 type
(new), 7/6; T3180 Transmitter (new), 12/6; 6 volt high
speed sealed Relay (ex-equipment), 4/-.

J. AYRES

151 BRIGHTON ROAD SURBITON SURREY

Res/Cap Bridge

FOR

35/- ONLY

P. & P. 2/-

For checking all types of resistors and condensers

BUILT IN 1 HOUR! DIRECT READING!!

READY CALIBRATED !!!

Stamp for details of this and other instruments

RADIO MAIL Dept CG Raleigh Mews
Raleigh Street Nottingham

SMALL ADVERTISEMENTS

continued from page 639

TRADE—continued

INCORPORATED Practical Radio Engineers home
study courses of radio and TV engineering are
recognised by the trade as outstanding and authorita-
tive. Moderate fees to a limited number of students
only. Syllabus of Instructional Text is free. *The
Practical Radio Engineer*, journal, sample copy 2s.
6,000 Alignment Peaks for Superhets, 5s. 9d.
Membership and Entry Conditions booklet, 1s., all
post free from the Secretary, I.P.R.E., 20 Fairfield
Road, London, N.8.

JOIN THE INTERNATIONAL S.W. LEAGUE.
Free Services to members including Q.S.L. Bureau,
Amateur and Broadcast, Translation, Technical and
Identification Dept.—both Broadcast and Fixed
Stations, DX Certificates, contests and activities for
the SWL and transmitting members. Monthly
magazine, "MONITOR" containing articles of
general interest to Broadcast and Amateur SWLs,
Transmitter Section and League affairs, etc. League
supplies such as badges, headed notepaper and
envelopes, QSL cards, etc., are available at reason-
able cost. Send for League particulars. Membership,
including monthly magazine, etc., 21s. per annum.
—Secretary, ISWL, 86 Barrenger Road, London,
N.10.

SITUATIONS VACANT

AIR MINISTRY require **EXAMINERS** (unestablished)
for Aeronautical Inspection Service, Radio Division
at R.A.F. Units at Carlisle, Sealand, Henlow
(Bedfordshire) and in Gloucester and Wiltshire area.
Opportunities will arise for serving a tour of duty
overseas.

Also vacancies for **TECHNICAL GRADE III**
(Radio) unestablished, at Signals Command, R.A.F.
Medmenham, Bucks, for assistance in installation,
design and technical investigation of R.A.F. Radio/
Radar communication and approach aids.

Quals. C. & G. Inter. Group certificate in tele-
communications engineering or O.N.C. electrical or
equivalent theoretical knowledge, with experience in
industry or Services. Commencing salary age 28
and over £705 p.a. on Scale £625-£820 (men).
Prospects of promotion and establishment. Age up
to 55 years. Application to Air Ministry, C.E.4h,
Cornwall House, Stamford Street, London, S.E.1,
or any Ministry of Labour and National Service
office, quoting Borough 110/120.

A **VACANCY** has occurred in high-class City radio
specialists for salesman about 20. Knowledgeable
amateur considered, no previous sales experience
needed, but must be keen and of good appearance.
Apply giving brief personal details to City Sale &
Exchange Ltd., 93 Fleet Street, E.C.4.

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted
at 3d. per word, including address, minimum
charge 2/- Trade advertisements will be
accepted at 9d. per word, minimum charge 6/-.
If a Box Number is required, an additional
charge of 2/- will be made. Terms: Cash with
order. All copy must be in hand by the 12th
of the month for insertion in the following
month's issue. The Publishers cannot be held
liable in any way for printing errors or
omissions, nor can they accept responsibility
for the bona fides of advertisers.



SCOTTISH INSURANCE CORPORATION LIMITED

TELEVISION SETS RECEIVERS, TRANSMITTERS and other electronic equipment

Television Sets, Receivers and Short Wave Transmitters are
expensive to acquire and you no doubt highly prize your instal-
lation. Apart from the value of your Set, you might be held
responsible should injury be caused by a fault in the Set, or
injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and
Short Wave Transmitters, provides the following cover:

- (a) Loss or damage to installation (including in the case of
Television Sets the Cathode Ray Tube) by Fire, Explosion,
Lightning, Theft or Accidental External Means at any
private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or
damage to their property arising out of the breakage
or collapse of the Aerial Fittings or Mast, or through
any defect in the Set. Indemnity of £10,000 any one
incident.
- (ii) Damage to your property or that of your landlord
arising out of the breakage or collapse of the Aerial
Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less,
and for Sets valued at more than £50 the cost is in proportion.
Cover (b) and (ii) costs only 2/6 a year if taken with Cover (a),
or 5/- if taken alone.

Why not **BE PRUDENT AND INSURE** your installation
—it is well worth while **AT THE VERY LOW COST
INVOLVED**. If you will complete and return this form to
the Corporation's Office at the address below, a proposal will
be submitted for completion.

NAME (Block Letters).....

(IF LADY, STATE MRS. OR MISS)

ADDRESS (Block Letters).....

/JB

62-63 Cheapside London EC2