

THE SELRAY BOOK CO

BOOKS FOR THE CONSTRUCTOR

Basic Electricity. 5 parts, 12s. 6d. per part. Postage 6d. 55s. per set. Post free.

Basic Electronics. 6 parts, 12s. 6d. per part. Postage 6d. 66s. per set. Post free.

Completely revolutionary in their methods of training with startling success. Send for detailed prospectus.

Realistic High Fidelity. Hartley. 5s. Postage 6d.

High Fidelity Stereo Gramophone. For the Home Constructor. Easterling. 5s. Postage 6d.

Transistor Circuits No. 2. Sinclair. 2s. 6d. Postage 4d.

High Fidelity Tape Recorder. For the Home Constructor. Sinclair. 2s. 6d. Postage 4d.

High Fidelity Loudspeaker Enclosed. Babani. 5s. Postage 6d.

Transistor Superhet Receivers. Sinclair. 7s. 6d. Postage 6d.

Boys' Book of Crystal Sets and Simple Circuits. 2s. 6d. Postage 4d.

Practical Transistor Receivers. Sinclair. 5s. Postage 6d.

Transistor Circuits Manual. Gregory. 2s. 6d. Postage 4d.

Beginners' Guide to Radio. Camm. 7s. 6d. Postage 6d.

Servicing Transistor Receivers. Pettit. 6s. Postage 6d.

SEND STAMP FOR LISTS (150 Titles)

When ordering kindly add postage up to a total of 1s. only

Dpt. RC • 60 HAYES HILL • HAYES • BROMLEY • KENT • Telephone HURstway 1818

SCOTTISH INSURANCE CORPORATION LTD



62-63 Cheapside
London EC2

TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) and (ii) costs only 2/6 a year if taken with Cover (a) or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's Office at the above address, a proposal will be submitted for completion.

NAME (Block Letters).....
If Lady, state Mrs. or Miss
ADDRESS (Block Letters).....

J/B

Published in Great Britain by the Proprietors and Publishers

Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd 125 High Holborn London WC1 England also at Clacton-on-Sea Obtainable abroad through the following Collects Subscription Service Continental Publishers & Distributors Ltd William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency Holland "Radio Electronica"

Registered for transmission by Magazine Post to Canada (including Newfoundland)

COOPER-SMITH "BANTAM" 3-4 WATT AMPLIFIER, PART I


VOLUME 14
NUMBER 2
SEPTEMBER
1960

The RADIO Constructor



RADIO · TELEVISION · AUDIO · ELECTRONICS

A HETERODYNE FREQUENCY METER

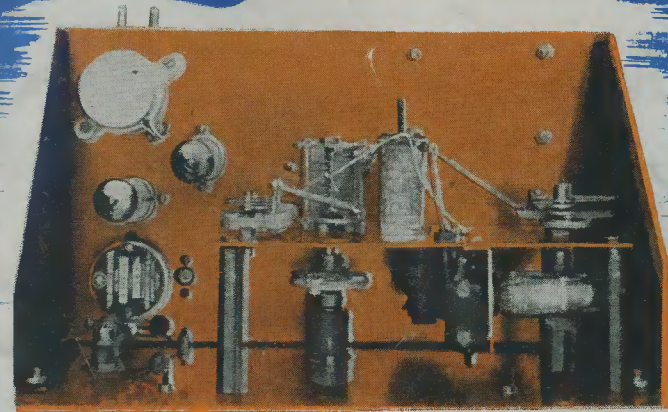

by D. Nobel, G3MAW
and D. M. Pratt, G3KEP

Contents include
SINGLE TRANSISTOR PHASE-SHIFT OSCILLATOR
BEGINNERS' SHORT WAVE RECEIVER
THE PHONE-GUARD
SIMPLE REFLEX SUPERHET
HIGH GAIN VHF AERIAL

DATA Publications 1/9

THE MODERN BOOK CO

Fundamentals of Semi-Conductors.
By M. G. Scroggie. 23s. Postage 1s.

Transistors Projects. 23s. Postage 1s.

Model Answers to C & G Exams.
Telecommunication Principles A and B. 7s. 6d. each. Postage 6d.

Marine Radio for Pleasure Craft.
By H. McKay. 23s. Postage 1s.

How To Use Meters. By J. F. Rider.
20s. Postage 10d.

Fun With Short Waves. By G. Davey.
11s. 6d. Postage 1s.

Valve and Teletube Manual. By
Brimar. No. 8. 6s. Postage 9d.

We have the Finest Selection of British and American Radio Books in the Country
Complete catalogue 1/-

19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADDington 4185

Practical Wireless Service Manual.
By F. J. Camm. 21s. Postage 1s.

Short Wave Receivers For The Beginner. A Data Publication. 6s.
Postage 6d.

Elements of Radio. By Marcus &
Marcus. 40s. Postage 1s. 6d.

Instructions To Radio Constructors.
By R. H. Warring. 12s. 6d. Postage 1s.

The Radio Amateur's Handbook.
By A.R.R.L. 1960 Ed. 32s. 6d.
Postage 2s.

Radio Valve Data 6th Ed. Compiled
by "W.W." 5s. Postage 9d.

A Beginner's Guide To Television.
By F. J. Camm. 7s. 6d. Postage 6d.

THE RADIO CONSTRUCTOR

BOUND VOLUMES

Attractively bound in blue cloth, with gold-blocked spine

Vol. 12, August 58 to July 59 £1.5.0. postage 1/9

Vol. 13, August 59 to July 60 £1.5.0. postage 1/9
(ready early October)

Where all issues of a volume
are returned for exchange 12s. 6d. postage 1/9

"Easibinders" for temporary
or permanent binding 12s. 6d. postage 9d.

Please note:—Indexes are available for Volume 13, August '59 to July '60 inc., price 6d. postage 2d. A limited number of indexes are also available for volumes 4, 6, 8, 11, and 12, at the same price.

DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9

more


for less... with the

MULTIMINOR

Use PRODCLIPS (Pat. No. 748811)
with the Multiminor

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be!

15/- per pair

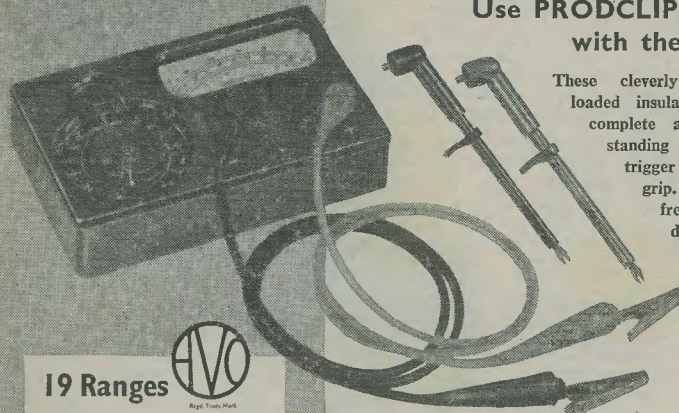

19 Ranges



D.C. Voltage	A.C. Voltage	D.C. Current
0—100mV	0—10V	0—100μA
0—2.5V	0—25V	0—1mA
0—10V	0—100V	0—10mA
0—25V	0—250V	0—100mA
0—100V	0—1000V	0—1A
0—250V		
0—1000V		
Resistance		
0—20,000Ω		
0—2MΩ		

List price £9. 10s.
complete with Test Leads
and Crocodile Clips
Leather case if required 39/-
Size 5 3/8" x 3 3/8" x 1 3/8"
Weight 1 lb. approx.

AVO LTD

MULTIMINOR

FITS THE POCKET



FILLS THE BILL

Write now for illustrated literature to:
AVOCET HOUSE • 92-96 VAUXHALL BRIDGE ROAD
LONDON • SW1


VICToria 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES
MM.12

The World-famous **Heathkit** range of equipment

For the Discerning who require the Best Performance at Minimum Price

HI-FI FM TUNER

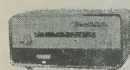

This model is available as two units which, for your convenience, are sold separately. They comprise a Tuner Unit, Model FMT-4U (£3.2.0 including Purchase Tax) with I.F. output of 10.7 mc/s and an Amplifier Unit complete with attractively styled cabinet, power supply and valves. Model FMA-4U (£10.10.6) making a total cost for the equipment of £13.12.6.

AMATEUR TRANSMITTER Model DX-100U




This is the most popular Amateur transmitter in the world and requires no introduction to "Hams" the world over. Covers all bands from 160-10 metres. Self-contained, including power supply, Modulator and V.F.O. £78.10.0

THE "CHEPSTOW".

This cabinet has specially been developed for those who require to house their equipment in as small a floor area as possible. Overall dimensions are 35" x 18" x 33" high.

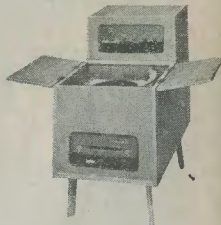It will accommodate Record Player, FM Tuner, Stereo Amplifier and where a Stereo Control Unit is used, one or more power amplifiers as well. An upper deck is available for the self-powered stereo amplifiers to ensure maximum heat dissipation. Left in the white, veneered for finishing to personal taste. £10.10.0



TRANSCRIPTION RECORD PLAYER


TRANSCRIPTION RECORD PLAYER, Model RP-1U. This new RP594 Collaro Transcription Unit has a Ronette Stereo Pick-up, giving excellent results on stereo or mono (33, 45, or 78 r.p.m.) discs. Complete with furniture-grade wooden plinth. £12.10.0



The "GLOUCESTER". It will house Tape Deck and/or Record Player—as well as FM Tuner and Stereo Amplifier, and storage space is provided for records, tapes and power amplifiers. Furthermore to meet the needs of those with whom room-space is an overriding consideration, provision is made in the cabinet ends for matched Hi-Fi Stereo Speaker Systems.

Mk. 1. Tape Deck or Record Player. £15.18.6

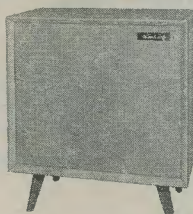
Mk. 2. Tape Deck and Record Player. £17.8.6



THE "GLOUCESTER"


THE "COTSWOLD". This is an acoustically designed enclosure 26" x 23" x 15 1/2" housing a 12" bass speaker with 2" speech coil, elliptical middle speaker together with a pressure unit to cover the full frequency range of 32-20,000 c/s. capable of doing justice to the finest programme source, its polar distribution makes it ideal for really Hi-Fi Stereo. Delivered complete with speakers, cross-over unit, level control, Tygan grille cloth, etc. All parts pre-cut and drilled for ease of assembly and left "in the white" for finish to personal taste. £19.18.6

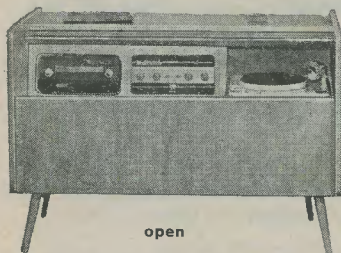BUY YOUR HI-FI EQUIPMENT ALL TOGETHER AS ONE OF OUR "PACKAGED DEALS" AND SAVE YOURSELF MORE MONEY!



open

THE "GLOUCESTER"

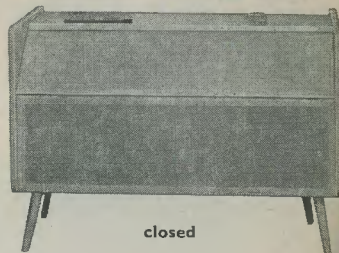

closed


DAYSTROM LTD DEPT. RC9 GLOUCESTER ENGLAND

Easily-built Equipment



of excellent quality

at much lower cost

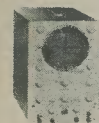

O-12U



DC-1U



S-33



DX-40U



AG-9U



UJR-1



MA-12

5" OSCILLOSCOPE: O-12U. "Y" sensitivity 10mV/cm., 3 c/s to over 5 Mc/s. Rise time, 0.08 µsecs. or less. Sweep, 10 c/s to 500 kc/s. Electronically stabilised. £34.15.0

2 1/2" PORTABLE SERVICE OSCILLOSCOPE: OS-1. Ideal instrument for service and portable use. Size 5" x 8" x 14". Wt. 10 1/2 lb. £18.19.6

DECADE CAPACITANCE BOX: DC-1U. Provides capacity values from 100 mmf to 0.11 mfd. in 100 mmf. steps. Ideal for experimental, development and design work. £5.18.6

VALVE VOLTMETER: V-7A. The World's largest-selling VVM. Measures Volts to 1,500 (DC & RMS) and 4,000 pk. to pk.; Resistance 0.1Ω to 1,000MΩ D.C. Sensitivity: 7,333,333 ohms per volt. £13.0.0

HI-FI STEREO 6 WATT AMPLIFIER: S-33. Low-priced but high quality; less than 0.3% distn at 2 1/2 watts per channel. £11.8.0

HI-FI STEREO 16 WATT AMPLIFIER: S-88. Superb reproduction for the man who wants the best in Hi-Fi. Only 0.1% distortion at 6 W/chnl. Many special features. £25.5.6

"HAM" TRANSMITTER: DX-40U. 75 W. CW; 60 W. pk. c/s phone; 40 W. into Aerial. £29.10.0

HI-FI SPEAKER SYSTEM: SSU 1. Ideal twin speaker/ducted-reflex cabinet for stereo/mono. in average room (left "in the white"). Legs £1.7.0 extra. £10.5.6

AUDIO GENERATOR: AG-9U. 10 volts, 10 c/s to 100 kc/s pure sine-wave. Switch-selected frequencies attenuation. £19.3.0

JUNIOR PERSONAL TRANSISTOR RADIO: UJR-1. Youngsters are not excluded from our kit programme. This special single transistor set is an excellent introduction to radio and an instructive present. £2.16.6

TRANSISTOR PORTABLE RADIO: UXR-1. In elegant solid hide case, with golden relief. Six transistors, dual-wave, fine reproduction, very easy to build. £14.18.6

SINGLE CHANNEL 12 WATT HI-FI AMPLIFIER: MA-12. Ideal for stereo conversions, etc. Generous auxiliary power provided. £9.19.6

COLLARO "STUDIO" TAPE DECK. This extremely attractive and compact 3-speed monaural tape deck features digital counter, pause control and piano-key switches. £17.10.0

(Following models not illustrated)

CAPACITANCE/RESISTANCE BRIDGE: C-3U. Measures capacity, 10pF to 1,000µF. Resistance 100Ω to 5MΩ; Pwr. Factor. £7.19.6

VARIABLE FREQUENCY OSCILLATOR: VF-1U. 10V output; covers 10 to 160 metres. £10.12.0

AUDIO WATTMETER: AW-1U. Up to 25 W. continuous, 50 W. intermittent. £13.18.6

AUDIO VALVE-MILLIVOLTMETER: AV-3U. 1mV to 300V A.C. 10 c/s to 400 kc/s. £13.18.6

ELECTRONIC SWITCH: S-3U. This extremely useful device extends your single-beam "scope" for double-beam uses. £9.18.6

DIRECT READING CAPACITANCE METER: CM-1U. Full-scale ranges of 0-100 mmf., 1,000 mmf., 0.01 mfd. and 0.1 mfd. £14.10.0

Money Saving "Packaged Deals" of Complete Stereo Equipment from £42.10.0


All prices include free delivery in U.K. Deferred terms available on orders above £10




OS-1




V-7A

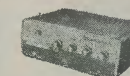

S-88

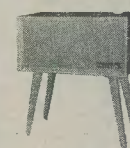

SSU-1

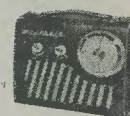

UXR-1



"STUDIO"

★ SEND THIS COUPON NOW FOR FURTHER INFORMATION

Without obligation please send me (Tick here)

BRITISH HEATHKIT CATALOGUE

FULL DETAILS OF MODEL(S)

(Please write in BLOCK CAPITALS)

NAME

ADDRESS

DAYSTROM LTD DEPT. RC9 GLOUCESTER · ENGLAND

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS


JASON LEADERSHIP IS MAINTAINED

The first successful FM Tuner in kit form was produced by Jason. The first range of matching hi-fi units, the first switched FM Tuner, the first switched FMT/TV Sound Tuner—all Jason. With Jason, progressive outlook combines with the best possible techniques to produce equipment ranking amongst the world's finest.

Good equipment PLUS

- **STYLING**
The keynote of all Jason audio equipment design is quiet "liveable-with" elegance that is not quickly out-dated.
- **WIDE CHOICE OF MODELS**
Amplifiers and tuners available cover practically all hi-fi listening requirements. Two amplifier and ten tuner designs to choose from.
- **HIGH PERFORMANCE STANDARDS**
Research, experiment and constant tests on production models ensure the very finest standards of reproduction with easy building for kit constructors and the easiest possible control arrangements throughout.
- **GOOD LITERATURE**
Copious and interesting literature is provided with all models. Circuit diagrams, vital technical information—all are well presented in a most readable manner.
- **DEMONSTRATIONS**
Available at all times in our London showrooms (up to 7.30 p.m. Thursdays for late shoppers) or at your local Jason stockist.

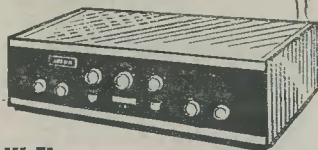N.B. When you buy Jason, you buy built-in reliability backed by one of the foremost names in British high-fidelity and supported by a well organised service department.



Jason

A COMPLETE PROGRAMME IN HI-FI

★ TUNER KITS (Valves extra except where stated)

FMT/1—The original Jason tuner	£5.19.0
FMT/2—As above, in shelf mounting case	£8.15.0
FMT/3—Variable FM with AGC control (in case)	£9.19.0
JTV/2K—Self-powered switched FM/TV sound	£14.19.0
Mercury II—Switched FM/TV Sound chassis	£10.14.0
Everest 7—Transistor Portable	£15.18.9
Everest 6—Transistor Portable	£13.19.9

★ MATCHING SELF-POWERED UNITS

J.2-10 Mk. III—Stereo/Mono Amplifier	39 gns.
J.10 Mk. III—Mono Amplifier	£24. 0.0
FMT/4—1961 variable FM Tuner (fringe)	£22.15.8
JTV/2—Switched FM/TV Sound Tuner	£25. 7.3

★ TEST EQUIPMENT KITS

Details on request

AUDIO & TEST EQUIPMENT IN KIT FORM AND READY BUILT

★ VALVES NEW TESTED AND GUARANTEED

1R5 6/6	6X4 7/6	DK92 7/6	EL84 10/6
1S5 6/6	6X5GT 6/6	DK96 8/-	EL91 7/6
1T4 4/6	12AH8 10/6	DL92 6/9	EY51 9/6
354 6/9	12AT7 7/6	DL94 7/6	EZ40 6/6
3V4 7/6	12AU7 7/6	DL96 8/-	EZ80 6/6
5U4G 6/-	12AX7 9/-	EB91 4/6	EZ81 7/-
5Y3GT 7/6	12BH7 10/6	EBC41 9/6	PL81 13/6
5Z4G 9/-	12K7GT 8/6	EBF80 10/6	PL82 10/6
6AK6 6/6	12K8GT 13/6	ECC81 7/6	PY81 8/-
6AL5 4/6	12Q7GT 6/6	ECC82 7/6	PY82 7/-
6AM6 4/6	25A6G 10/6	ECC83 7/6	PCC84 9/6
6AT6 7/6	25L6GT 9/-	ECC84 9/-	PCF80 9/-
6BA6 8/6	35Z4GT 8/6	ECC82 11/-	PCF82 11/-
6BE6 7/6	35L6GT 9/6	ECH81 10/6	PCL82 7/6
6BR7 10/6	5763 10/6	ECH42 8/6	R19 12/6
6BW6 8/6	DAF91 6/6	ECL80 9/6	U76 8/6
6J7GT 8/6	DAF96 8/-	EF41 8/6	UBC41 10/-
6K7G 7/6	DF91 4/6	EF80 8/-	UCH42 10/6
6Q7G 7/6	DF96 8/6	EF86 9/6	UF41 10/-
6SL7GT 8/-	DH76 8/6	EF91 4/6	UL41 8/-
6SN7GT 8/6	DH77 7/6	EF92 5/6	UY41 8/-
6V6G 7/6	DK91 6/6	EL41 9/-	W76 8/6

Matched Pairs. EL84, 23/-; EL85, 25/-; 6V6G, 17/-; 6BW6, 18/-; KT33C, 19/6; 807 14/6 pair.

SETS OF VALVES

DK96, DF96, DAF96, DL96, "REGENT"	29/6 per set
DK91, DF91, DAF91, DL92, or DL94	21/- per set
1R5, 1T4, 1S5, 354, or 3V4	21/- per set
6K8, 6K7, 6Q7, 6V6, 5Z4, "G" Types	27/6 per set
12K8, 12K7, 12Q7, 35L6, 35Z4, GT Types	35/- per set
ECH42, EF41, EBC41, EL41, EZ40	37/6 per set
UCH42, UF41, UBC41, UL41, UY41	35/- per set

P.P. Op. Transformers. MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6

P. & P. 6d., over £1 post paid. C.O.D. 2/6

R. COOPER G8BX 32 SOUTH END CROYDON SURREY CROYDON 9186

★ Volume Controls. All valves, long spindle. L/S 2/9, s.p. 3/9, d.p. 4/3; ext. spkr. control 3/-
P.M. Speakers. 3 ohms 5" 16/6, 6 1/2" 17/6, 8" 21/-, 10" 25/-; 12" 30/-; Bakers 12" 15 ohm 15WV, 90/-
Coaxial Plugs 1/- each; Sockets 1/- each.

C.R.T. Isolation Transformers with nil. 25% and 50% boost, low capacity a.c. mains 200/250V for 2V 4V, 6.3V and 13V tubes. All 10/6 each. P. & P. 1/6

Valveholders. 4, 5, 7 pin English and U.S.A. B7G, 59A, 10, M0, B8G, 9d. each; B7G, B9A with screening can, 1/6; B12A, 1/3; Aladdin formers 1/2" with core, 8d. each.

Jack Plugs. Miniature standard 3/-; Sockets 3/-

Capacitors. Small mica, 5% 1pF to 100pF, 8d.; 120pF to 1,000pF, 9d.; 1,000V wkg. .01, .0015, .0025, .004, .005; F, 1/- each

Crystal Diodes. G.E.C., 1/6 each

Ceramic Capacitors. Close tol. 500V for V.H.F., 9d.

Paper Tubular. .001-1 500V, 9d.; .25. 1/-; .5. 1/6; .01 1,000V, 1/-

Paper Blocks. 4uF, 1,000 wkg., 3/6; 4uF 250V, 2/6

Rectifiers. Contact cooled, 250V 50mA, 7/6; 85mA, 9/6

Reaction Condensers. .0001, .0003, .0005uF, 4/6 each

Heater Trans. 200/240V, 6.3V, 1.5A, 7/6, 3A 10/6

Resistors. 1/4 and 1/2W, insulated, 4d. and 6d.; 1W, 8d.; 6W W.W., 1/-; 10W, 2/-

Electrolytics. Wire ends. 25/25V, 1/6; 50/50V, 2/-; 12/50V, 9d.; 8/450V, 2/-; 16/450V, 2/9; 16/500V, 3/6;

32/450V, 4/-; 8+8/450V, 4/6; 8+16/450V, 4/6; can types: 16/450V, 3/6; 16+16/500V, 6/-; 32/500V, 6/6;

32/450V, 6/6; 20+20/450V, 4/6; 64+120/275V, 7/6

Wavechange Switches. Midget: 1p 12V, 2p 6W, 3p 4W, 4p 3W, 4p 2W, long spindles, 4/6


Toggle Switches. QMB, s.p.s.t., 2/-; s.p.d.t., 3/3; d.p.s.t., 3/6; d.p.d.t., 4/-; rotary s.p., 3/-

Chokes. 65mA 10H, 5/6; 80mA 15H, 8/6; 100mA 10H, 10/6; 150mA 10H 14/6

Chokes. 65mA 10H, 5/6; 80mA 15H, 8/6; 100mA 10H, 10/6; 150mA 10H 14/6

RCS "REGENT" 4-Valve Portable Superhet

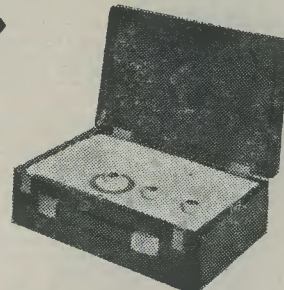Plans 9d. or details S.A.E. (as featured in June issue)



★ Economy "96" Range Valves

★ Medium and Long Waves

★ 6" High Flux Speaker

★ T.C.C. Printed Circuit and Condensers

★ Osborn Ferrite Aerial and Coils

★ Attache Case Cabinet 12" x 8" x 4" Rexine-covered

★ Ready-made Mains Unit available. Price 39/6

★ All components identified and of finest quality

Special Reduced Price (for limited period) if all components are purchased at one time.

£6.6.0

Carriage 4/-

Batteries extra 10/- set

CHAMPION VHF (FM) TUNER 88 to 96 Mc/s. In Factory Built. Ready for use. Features: This is a self-powered 200/250V a.c. VHF (FM) adaptor with 5 Mullard valves and superhet tuning heart. Operating data and a screened lead for connection to pick-up sockets of


any radio, radiogram or amplifier. Brand new. In maker's box. 12 months guarantee. List price 16 gns.

Our price £9 10. carr. 4/6

Maroon and cream cabinet 6" x 12" x 6" 20/- extra. Details S.A.E.

RADIO COMPONENT SPECIALISTS

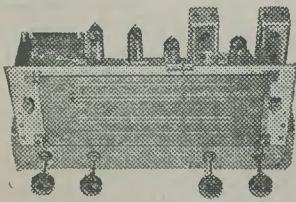337 WHITEHORSE ROAD WEST CROYDON Telephone THO 1665



1960 RADIOGRAM CHASSIS

THREE WAVEBANDS S.W. 16 m.-550 m. M.W. 200 m.-2,000 m. L.W. 800 m.-2,000 m. FIVE VALVES LATEST MULLARD ECH81, EF89, EBC81, EL84, EZ80 12 month Guarantee. A.C. 200/250V, 4-way switch, Short-Medium-Long-Gram. A.V.C. and negative feedback. 4.2 watts. Chassis 13 1/2" x 5 1/2" x 2 1/2". Glass dial, horizontal or vertical, size 10" x 4 1/2". 2 pilot lamps. Four knobs, walnut or ivory, aligned and calibrated. Chassis isolated from mains. Leaflet S.A.E.

BRAND NEW £9.10.0 Carr. 4/6

TERMS: Deposit £5.5.0 and 5 monthly payments of £1 MATCHED SPEAKERS: 8" 17/6. 10" 25/-. 12" 30/-.

LATEST "E.M.I." 4 SPEED SINGLE RECORD PLAYER

Acos 73 Hi-Fi Pick-up for LP, 78 and Stereo 7", 10" and 12" records. Silent motor heavy turntable, auto stop. Special offer £6.19.6 post free.

BUILD THIS REPRODUCER BARGAIN SPECIAL SINGLE PLAYER KIT

COLLARO 4-speed Gram-Pick-up Unit Handsome portable case 17 1/2" x 13 1/2" x 7" with room to play 12" records £3.15.0 Ready built 3-watt amplifier with two valves and 7" elip. speaker, printed circuit £2.50.0 or £9.9.0 complete kit post free

I.F. TRANSFORMERS 7/6 pair

465 kc/s slug tuning miniature can 2 1/2" x 1" x 1". High Q and good band width. By Pye Radio. Data sheet supplied. Wearite M800 Midget 465 kc/s 1 1/2" x 3/4" sq. 12/6 pair Weyrad Standard Size 465 kc/s 3 1/2" x 1 1/2" sq. 12/6 pair

New boxed VALVES 90-day Guarantee

1R5	7/6	6K8G	7/6	EA50	1/6	EZ80	7/6
1S5	7/6	6L6G	10/6	EABC80	8/6	E1148	1/6
1T4	6/-	6N7M	6/6	EB91	6/-	HABC80	12/6
2X2	3/6	6Q7G	8/6	EBC33	8/6	HVR2A	6/6
3S4	7/6	6SA7	6/-	EBC41	8/6	MU14	9/-
3V4	7/6	6S17M	6/6	EBF80	10/-	P61	3/6
5U4	7/6	6SN7	6/6	ECC84	9/6	PCC84	9/6
5Y3	7/6	6V6G	6/6	ECC80	9/6	PCF80	9/6
5Z4	9/6	6X4	7/6	ECH42	10/6	PCL82	11/6
6AM6	5/-	6X5	6/6	ECL80	10/6	PEN25	6/6
6B8	5/-	12A6	7/6	ECL82	10/6	PL81	12/6
6BE6	7/6	12AT7	8/-	EF39	5/6	PL82	10/6
6BH6	9/6	12AU7	8/-	EF41	9/6	PY80	7/6
6BW6	9/6	12AX7	8/-	EF50	5/6	PY81	7/6
6D6	6/-	12BE6	8/6	EF80	8/-	PY82	7/6
6F6	7/6	12K7	6/6	EF86	12/6	SP61	3/6
6H6	3/6	12Q7	6/6	EF92	5/6	UBC41	9/6
6J5	5/6	35L6	9/6	EL32	5/6	UCH42	9/6
6J6	5/6	35Z4	7/6	EL41	9/6	UF41	9/6
6J7G	6/6	80	9/6	EL84	8/6	UL41	9/6
6K6GT	6/6	807	5/6	EY51	9/6	UY41	8/-
6KT5	5/-	954	1/6	EZ40	7/6	U22	8/-

DK96, DF96, DAF96, DL96, 8/6 each or 30/- set

B.B.C. Pocket Transistor, M.W. and L.W. Radio Kit 32/6. Phones 7/6 or deaf aid earpiece 15/-.

Our written guarantee with every purchase

C.R.T. ISOLATION TRANSFORMERS

For Cathode Ray Tubes having heater cathode short circuit and for C.R. Tubes with falling emission, full instructions supplied. Type A. Low leakage windings. Optional 25% and 50% boost on secondary; 2V, or 4V, or 6.3V, or 10.3V, or 13.3V, with mains primaries, 12/6. Our Latest Superior Product. Mains Input Type A2. High quality low capacity 10-15pF. Optional boost 25% 50% 75% 16/6 each. Type B. Mains input. Low capacity. Multi output 2, 4, 6.3, 10 and 13V. Boost 25% and 50%. This transformer is suitable for all TV tubes. 21/- each.

RESISTORS. Preferred values. 20% 10 ohms to 10 meg, 1/4W 4d., 1/2W 4d., 1W 6d., 1 1/2W 8d., 2W 1/-.

HIGH STABILITY. 1/2W 1%, 2/-.

WIRE-WOUND RESISTORS. 25 ohms-10,000 ohms. 5 watt } 1/3 10 watt } 1/6 15 watt } 2/-

WIRE-WOUND POTS. Pre-set min. TV type. Knurled slotted knob. All values 25 ohms to 25k, 3/- each, 30k, 50k, 4/-.

MAINS TRANSFORMERS-200/250 AC STANDARD 250-0-250, 80mA, 6.3V tapped 4V 4A, Rectifier 6.3V 1A, tapped 5V 2A and 4V 2A 22/6

MINIATURE. 200V 20mA, 6.3V 1A 10/6

MIDGET. 220V 45mA, 6.3V 2A 15/6

SMALL. 220-0-220V 50mA, 6.3V 2A 17/6

STANDARD. 250-0-250 65mA, 6.3V 3.5A 17/6

HEATER TRANS. 6.3V 1 1/2A 7/6. Ditto, sec. 6.3V 3A 10/6. Ditto, tapped sec. 2, 4, 6.3V 1 1/2A, 8/6.

Mullard "510" Osram "912" 300-0-300, 120mA, 6.3V 4A c.t., 6.3V 2A tapped 5V 38/6

General Purpose Low Voltage. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V at 2A 22/6

O/P TRANSFORMERS. Heavy duty 50mA, 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Small pentode, 4/6. Hygrade push-pull 7 watts, 15/6. Goodmans heavy duty 10/20V 6k or 8k c.t., 30/-.

L.F. CHOKES 15/10H 60/65mA, 5/-; 10H, 85mA, 10/6; 10H 150mA, 14/-.

CRYSTAL MIKE INSERT by Acos 6/6 Precision engineered. Size only 1/2" x 3/8" ACOS CRYSTAL HAND or DESK MIKE, 27/6

ALADDIN FORMERS and cores. 1/4" 8d., 3/8" 10d. 0.3" FORMERS 5937 or 8 and cans TV1 or 2, 3/4" sq. x 2 1/2" or 3/4" sq. x 1 1/2", 2/- with cores.

SLOW MOTION DRIVES. Epicyclic range 6-1, 2/3. REMPLOY INSTRUMENT IRON, 230V 25W, 17/6.

MAINS DROPPERS. 3" x 1 1/2". With adj. sliders, 0.3A, 1,000 ohms, 4/3; 0.2A, 1,000 ohms, 4/3.

LINE ORD. 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 6d. per foot; 3-way, 7d. per foot.

MIKE TRANS. 50:1, 3/9; 100:1, potted, 10/6.

LOUDSPEAKERS. P.M. 3 ohm. 5" Rola, 17/6; 6" x 4" Rola, 18/-; 4" Hi-Fi Tweeter, 25/-; 8" Plessey, 19/6; 6 1/2" Goodmans, 18/6; 10" R.A., 30/-; 12" Plessey, 30/-; 10" x 6" R.A., 27/6; 12" Baker 15W 3 ohm or 15 ohm models, 90/-; Stentorian HF1012 10", 95/-.

CRYSTAL DIODES. G.E.C., 2/-; GEX34, 4/-.

40 CIRCUITS FOR GERMANIUM DIODES, 3/-.

H.R. HEADPHONES 4,000 ohms, brand new, 15/-.

SWITCH CLEANER FLUID, squirt sprout, 4/3 tin. TWIN GANG CONDENSERS. 365pF, miniature, 1 1/2" x 1 1/2" x 1 1/2", 10/-; 0.0005 standard with trimmers, 9/-; slim trimmers, 8/-; midget, 7/6; 50pF single, 2/6.

SHORT WAVE SINGLE 75pF, 100pF, 160pF, 7/- each. TUNING AND REACTION CONDENSERS. 100pF, 300pF, 500pF, 3/6 each, solid dielectric. RADIO & TV SERVICE SHEETS 2/6 plus S.A.E.

HIGH GAIN TV PRE-AMPLIFIERS BAND I B.B.C.

Tuneable channels 1 to 5. Gain 18dB. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PCC84 valves if preferred).

BAND III I.T.A.—Same prices Tuneable channels 8 to 13. Gain 17dB. ECC84 valve

Volume Controls Midget size. Long spindles. Guaranteed 1 year. All values 5,000 ohms to 2 Meg. No Switch D.P. Switch 3/- 4/6 Linear or Log Tracks

80Ω Coaxial Cable Post 1d. per yard extra Semi-air spaced Polythene Ideal Band III 6d. yd. Losses cut 50% FRINGE QUALITY 1/- yd. Air spaced Coaxial

Coaxial Plugs 1/- Panel Sockets 1/- Balanced Twin Feeder, per yd. 6d., 80Ω or 300Ω. Twin Screened Balanced Feeder, 1/6 yd, 80 ohms. Trimmers. Ceramic 30, 50, 70pF, 9d., 100pF, 150pF, 1/3; 250pF, 1/6; 600pF, 750pF, 1/9; Philips, 1/- each.

BLACK CRACKLE PAINT. Air drying, 3/- tin. P.V.C. CONN. WIRE, 8 colours, single of stranded, 2d. yd. Sleeving 1, 2mm, 2d.; 4mm, 3d.; 6mm, 5d. yd.

NEON MAINS TESTER SCREWDRIVERS, 5/- SOLDER RADIOGRADE, 4d. yd, 1/2 lb 2/6.

Aluminium Chassis. 18 s.w.g. Plain, undrilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2" sides. 7" x 4", 4/6; 9" x 7", 5/9; 11" x 7", 6/9; 13" x 9", 8/6; 14" x 11", 10/6; 15" x 14", 12/6; 18" x 16" x 3", 16/6.

Miniature Contact Cooled Rectifiers. 250V 50mA, 7/6; 250V 85mA, 9/6. Selenium Rect. 300V 85mA, 7/6.

Coils. Wearite "P" type, 3/- each. Osrom Midget "Q" type, adj. dust core, from 4/- each. All ranges.

Teletron D.W.R. L. & Med. T.R.F. with reaction, 3/6. Ferrite Rod Aerials. M.W., 8/9; M. & L., 12/6.

Ferrite Rods 8" x 3/8", 2/6. T.R.F. Coils A/HF, 7/- pair. H.F. Chokes, 2/6.

Speaker Fret. Gold cloth, 17" x 25", 5/-; 25" x 35", 10/-; Tygan, 4" 6" wide, 10/-; 2" 3" wide, 5/- ft. Samples, S.A.E.

Condensers. 0.001μF 7kV T.C.C., 5/6; ditto 20kV, 9/6; 0.1μF 7kV, 9/6; 100pF to 500pF Micas, 6d.; Tubular 500V 0.001 to 0.05, 9d.; 0.1, 1/-; 0.25, 1/6; 0.1/350V, 9d.; 0.5/250V, 1/9; 0.01/2,000V, 1/9; 0.1/2,000V, 3/6.

Ceramic Condensers. 500V 0.3pF to 0.01μF, 9d. Silver Mica. 10% spec to 500pF, 1/-; 600pF to 3,000pF, 1/3; close tolerance (plus or minus 1pF), 1.5pF to 47pF, 1/6; ditto 1% 50pF to 815pF, 1/9; 1,000pF to 5,000pF, 2/-.

NEW ELECTROLYTICS FAMOUS MAKES TUBULAR CAN TYPES

1/350V 2/- 50/350V 5/6 8/600V 9/-

2/350V 2/3 100/25V 3/- 32/350V 4/-

4/450V 2/3 250/25V 3/- 100/270V 5/6

8/450V 2/3 500/12V 3/- 2,500/3V 4/-

8/500V 2/9 8+8/450V 3/6 5,000/6V 5/-

16/450V 3/- 8+8/500V 5/- 32+32/350V 5/-

16/500V 4/- 8+16/450V 3/9 32+32/450V 6/-

32/450V 1/9 8+16/500V 5/6 32+32+32/350V 7/-

25/25V 3/9 16+16/450V 4/3 50+50/350V 7/-

50/25V 2/- 16+16/500V 6/- 64+120/350V 11/6

50/50V 2/- 32+32/350V 4/6 100+200/25V 12/6

Full Wave Bridge Selenium Rectifiers. 2, 6 or 12V 1 1/2A, 8/9; 2A, 11/3; 4A, 17/6. Free charger circuit.

Charger Transformers. Tapped input 200/250V for charging at 2, 6 or 12V 1 1/2A, 15/6; 2A, 17/6; 4A, 22/6.

P.V.C. PLASTIC RECORDING TAPE Long Play 7" reel, 1,700ft 32/6 Standard Play—5 1/2" reel, 1,200ft 22/6 7" reel, 1,200ft 21/- 5" reel, 850ft 19/6 5 1/2" reel, 850ft 17/6 3" reel, 225ft 7/6 5" reel, 600ft 15/- Spare Plastic Reels all sizes 3/-. Metal Reels 7" only 2/-.

"Instant" Bulk Tape Eraser and Head Defluxer, 200/250V A.C., 27/6. Leaflet, S.A.E.



BRAND NEW AND BOXED Model UA8 OUR PRICE £6.15.0

STEREO MODELS UA8 £7.19.6 UA14 £10.10.0

★ COLLARO ★ HI-FI AUTOCHANGER £7.19.6

4 SPEEDS—10 RECORDS or with Cabinet, Amplifier and Speaker

OUR PRICE £11.19.6 Carr. 5/6

★ GARRARD 4-SPEED RECORD CHANGERS MODEL 210 ★

With Plug-in Head for Monaural Stereo Heads £2 extra £10.10.0

AUTOCHANGER ACCESSORIES Suitable player cabinets (uncut boards) 49/6

Amplifier player cabinets with cut boards 63/-

2-valve amplifier and 6 1/2" speaker for above 79/6

3-valve amplifier and 6 1/2" speaker for above 95/-

Wired and tested ready for use

★ GARRARD 4-SPEED SINGLE RECORD PLAYER TA MK. II ★

£8.8.0 AUDIO PERFECTION Stereo wired

with plug-in GC8 Normal Heads Stereo Heads £2 extra MODEL 4 HF £18

Wavechange Switches. 2 p. 2-way, 3 p. 2-way, short spindle, 2/6; 5 p. 4-way 2 auto, long spindle, 6/6; 2 p. 6-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6; 3 p. 4-way, 1 p. 2-way, long spindle, 3/6; wavechange "MAKITS", 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer, 16/-; 4 wafer, 19/6; 5 wafer, 23/-; 6 wafer, 26/6.

Toggle Switches, s.p., 2/-; d.p., 3/6; d.p.d.t., 4/-.

JASON FM TUNER COIL SET, 29/-.

H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer and heater choke.

Circuit and component book using four 6AM6, 2/6. Complete Jason FMT.1 Kit, and Jason chassis with calibrated dial, 5 gns. 4 valves 20/-.

Valveholders. Pax. int. oct., 4d. EA50, EF50, 6d. B12A, CRT, 1/3. Eng. and Amer. 4, 5, 6 and 7 pin, 1/-.

MOULDED Mazda and int. oct., 6d., B7G, B8A, B8G, B9A, 9d. B7G with can, 1/6. B9A with can, 1/9.

Ceramic, EF50, B7G, B9A, int. oct., 1/-.

B7G, B9A cans, 1/- each. Valve and TV Tube equivalents, 9/6.

CAN FAULT FINDING, 5/-.

Quality Amplifiers, 4/6. Radio Valve Guide, Books 1, 2 or 3, 5/- each.

TRANSISTORS. Ediswan Audio XB112, 10/-.

R.F. 2 Mc/s XA103, 15/-; R.F. 4 Mc/s XA104, 18/-.

Red Spot 5/-; White Spot 7/6. Sub-miniature Electrolytics (15V) 1μF, 2μF, 4μF, 5μF, 8μF, 25μF, 50μF, 100μF, 3/-.

TELETRON POCKET RADIO KIT Transidyne Superhet Six 3" x 4" x 1 1/2" T.C.C. Printed Circuit, internal Ferrite aerial, Rola loudspeaker push-pull output. All parts, cabinet, 6 Ediswan transistors, GEX34 diode, £9.9.0 Details 9d.

RADIO COMPONENT SPECIALISTS

Buses 133 or 68 pass door. S.R. Stn. Selhurst.

THE RADIO CONSTRUCTOR

337 WHITEHORSE ROAD WEST CROYDEN

Telephone THO 1665

Post and packing charge 1/-, over £2 post free. C.O.D. 1/6 (Export welcome. Send remittance and extra postage)

SEPTEMBER 1960

FREE THIS BOOK WILL INTEREST YOU!

LEARNING the PRACTICAL WAY

RADIOSTRUCTOR
EQUIPMENT-COURSES

A NEW-PRACTICAL WAY of UNDERSTANDING

RADIO · TELEVISION · ELECTRONICS

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test Instruments; Photo-electrics; Nucleonics, etc.

FOR... Your Career... Your Own Business... An Absorbing Hobby...

Radiostructor—an organisation specialising in electronic training systems—offers a new self-instructional method using specially designed equipment on a “do-it-yourself” basis. You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact, you really have fun whilst learning! Fill in the coupon below, for full particulars—

RADIOSTRUCTOR
LEADS THE WORLD
IN ELECTRONICS TRAINING

POST NOW

To RADIOSTRUCTOR (Dept. G.31)
READING, BERKS.

Please send brochure, without obligation, to:

* NAME

* ADDRESS 9/60

* BLOCK CAPS PLEASE
(We do not employ representatives)

CHASSIS CHASSIS CHASSIS CHASSIS CHASSIS

A ★ COMPLETE ★ SERVICE

Stock sizes in 18 g. Aluminium 2" deep. All corners wrapped and rivetted-lattice fixing holes.

6" x 4" x 2"	4/3	10" x 7" x 2"	7/-	12" x 8" x 2"	8/-
8" x 6" x 2"	5/9	12" x 6" x 2"	7/6	14" x 10" x 2"	11/6

As above but in tin plate 6" x 4" x 2" 3/6 8" x 6" x 2" 4/6

Ready Drilled Chassis for Simple Reflex Superhet, as described on page 129, 9/6

SPECIAL CHASSIS - ANY SHAPE - 1/2 d sq. inch of blank plus 6d per bend - corner wrapping included

All the above post free or plus 2/- C.O.D.

PUNCHING and DRILLING TO YOUR REQUIREMENTS

P.J. PRODUCTS . 34 HIGH STREET . ERITH . KENT
S.A.E. for full details
TRADE ENQUIRIES WELCOMED

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee
“NO PASS—NO FEE”

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of “ENGINEERING OPPORTUNITIES” today—FREE.

BRITISH INSTITUTE OF ENGINEERING
TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/23), 29 Wright's Lane, London, W.8

WHICH IS YOUR
PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME
LETTERS AFTER
YOUR NAME!

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.E.
A.M.I.M.I.
I.I.O.B.
A.F.R.Ab.S.
B.Sc.
A.M.Brit.I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL
EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING
TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.
SCHOOL OF
ELECTRONICS

POST COUPON NOW!

Please send me your FREE 156-page “ENGINEERING OPPORTUNITIES” (Write if you prefer not to cut page)

NAME

ADDRESS

SUBJECT OR EXAM THAT INTERESTS ME

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD


A REVOLUTIONARY NEW BRITISH INVENTION!

- ★ Uses standard tapes
- ★ Plays at 7½" per. sec. or 3 other speeds
- ★ Records direct from radio or microphone

Ready to record. Complete with 600ft. of twin-track tape.

11 Gns.

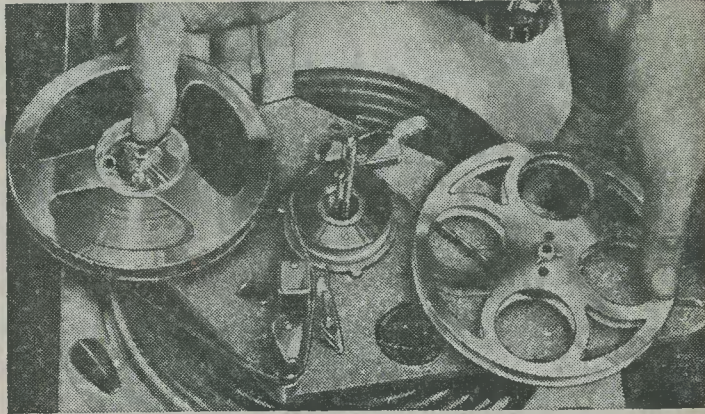Special moving-coil microphone extra.
EASY TERMS



Instantly turns any gramophone into a first-class Tape-Recorder and back into a record-player in a moment!

Gramdeck is completely new... a revolutionary and ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! Slip the Gramdeck on to your turntable and you have the finest tape-recorder you've ever heard! Lift it off... your gramophone is ready to play records again. There are no motors or valves to go wrong—and you get reproduction that has to be heard to be believed.

"Ingenious—simple... why on earth did no one think of it before!"—THE TAPE RECORDER.

"A British challenge to Continental tape recorder firms"—DAILY EXPRESS.

"Quality of reproduction excellent... real hi-fi results... potential is tremendous... both designer and manufacturer should be congratulated."—BRITISH RADIO & TV RETAILERS' REVIEW.

"Better than many so-called hi-fi recorders... robust... carefully designed... excellent value."—AMATEUR CINE WORLD.

Free!



Everyone is praising the Gramdeck. "The quality is at least equal to that obtained from a good microgroove disc," says a leading professional journal.

WORKS FROM ANY RECORD PLAYER OR RADIOGRAM

Gramdeck records and reproduces with a wonderful depth and breadth of tone. Because it uses equipment that is already in your gramophone it only costs a fraction of the high-quality tape-recorder you would normally require. Full details, specifications, photographs, easy terms, etc., are given in the Gramdeck Book. Send for your FREE copy today.

MADE BY THE FIRM THAT MAKES MICROWAVE WAVE-GUIDES FOR VISCOUNTS AND BRITANNIAS

FREE BOOK—POST NOW!

Please send me the Gramdeck Book—FREE and without obligation.
(Write if you prefer not to cut coupon.)

NAME.....

ADDRESS.....

GRAMDECK (Dept. RC/811)
29 Wright's Lane Kensington London W8

Gramdeck
GRAMOPHONE TAPE RECORDER

GRAMDECK TURNS A TURNTABLE INTO A TAPE-RECORDER

The decision is yours. To be a success in your chosen career; to qualify for the highest paid job... to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

TECHNICAL

TRAINING

in radio

television

and

electronics

engineering

with


Choose the RIGHT course,
RADIO AND TELEVISION
ENGINEERING . INDUSTRIAL
TELEVISION . RADIO AND TV
SERVICING . RADIO SERVICE
AND SALES . ELECTRONICS .
VHF/FM ENGINEERING .
COMPUTERS AND PROGRAMMING

ICS provides thorough coaching for professional examinations: A.M.B.R.I.T., City and Guilds Telecommunications, C. & G. Radio and TV Servicing, C. & G. Radio Amateurs.

LEARN AS YOU BUILD

Practical Radio Course

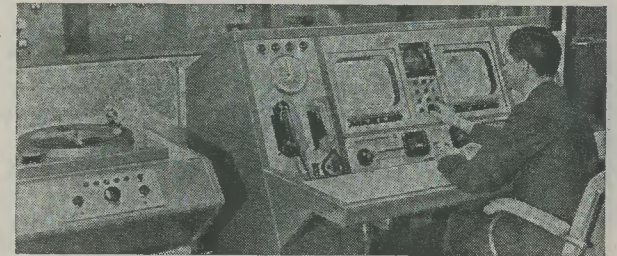Gain a sound up-to-professional-standards knowledge of Radio and Television as you build your own 4 valve T.R.F. and 5 valve superhet radio receivers, signal generator and high-quality multimeter. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill... ICS Practical Radio courses open a new world to the keen radio amateur.



THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER.

Post this coupon today: In return you will receive the FREE 60-page ICS Prospectus listing technical examinations and their appropriate ICS courses PLUS details of over 150 specialised subjects.

Other ICS courses include:

MECHANICAL, MOTOR, FIRE, CHEMICAL, ELECTRICAL AND CIVIL ENGINEERING, ETC. SELLING AND MANAGEMENT, ARCHITECTURE, WOODWORKING, FARMING, GARDENING, ART, PHOTOGRAPHY.

Please state subject on coupon



INTERNATIONAL CORRESPONDENCE SCHOOL

(Dept. 248) Intertext House Parkgate Road London SW11

NAME.....

ADDRESS.....

OCCUPATION..... AGE.....

SUBJECT..... 9,60

HOME RADIO OF MITCHAM


Shop Hours: 9-6.30 (Weds. 1 p.m.)

Telephone MIT 3282

Dept. AC
187 LONDON ROAD
MITCHAM, SURREY

"GLOBE-KING" SHORT WAVE RECEIVERS

MODEL 100/A

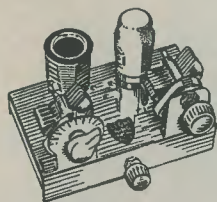


Designed especially for the newcomer to short wave radio, the GLOBE-KING kits enjoy world-wide popularity and give real long distance reception at minimum cost. The 100/A is a scientifically designed instrument which will give guaranteed results and no disappointments. High efficiency, low noise circuit with selected high grade components. Built up to a standard, not down to a price. Do not confuse with other cheap "ex-Govt" bargain offers. Leaflet on request. **KIT OF PARTS FOR SET INCLUDING 3 MATCHED COILS £3.19.6 post 1/-.** (Or ready built and tested, £4.9.6, post 1/-)

MODEL 200/A


Two-valve battery set in smart metal cabinet with loudspeaker. Matched coils covering 10 to 180 metres and high grade 55 to 1 reduction bandspread tuner. Jack socket for headphones. Leaflet on request. Available as kit of parts or ready built and tested.

MODEL 300/A

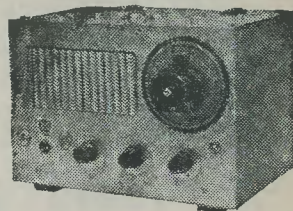Similar to the 200/A above but for A.C. mains operation 200/250V. Has panel indicator light and more power output. Available as a complete kit of parts or ready built and tested. Leaflet on request.



"THE CENTURION"

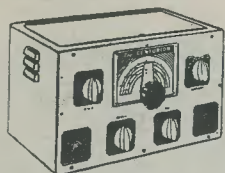


Short wave and medium wave battery receiver. Can be constructed as a one-valver and then the additional audio and r.f. stages can be added later as desired. All parts are standard and sold separately. Ready punched chassis and cabinet. Full constructional details of this set and many others in "Short Wave Receivers for the Beginner". Price 6/-, post 6d.

SHORT WAVE RADIO

Explore every corner of the world on short waves from your own fireside. Now is the time to start this absorbing and fascinating hobby. News from America, music from Brazil, sport from South Africa, and amateur radio stations in every part of the globe. Learn the Morse code and listen in to shipping, etc. You will be the envy of your friends and never have a dull moment this coming winter.

EDDYSTONE RECEIVERS

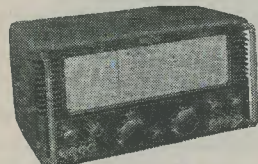


We carry the full range of the famous EDDYSTONE short wave components, and most receivers are also immediate or early delivery. Send 6d. stamp for the EDDYSTONE illustrated leaflets. Special priority for overseas orders and shipping arranged to any part of the world. We also stock and demonstrate the KW ELECTRONICS transmitters, etc.

HEADPHONES



For best results a pair of good earphones is essential. Lightweight 4,000 ohms headphone for all short wave sets, crystal sets, etc. New and boxed, 15/- Brown's popular type "F", 37/6. Ericsons, as recommended by Eddy-stone, £2.15.0. Please add 1/- post and packing to all orders.

SHORT WAVE TUNING CONDENSERS

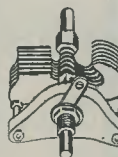

WAVEMASTER high grade condensers with brass vanes, air spacing and ceramic insulation. Single hole mounting and spindle at rear for easy ganging. 15pF 4/3, 25pF 4/6, 40pF 4/9, 50pF 5/-, 60pF 5/3, 75pF 5/6, 100pF 5/9, 160pF 6/-, 200pF 7/9, 250pF 9/3. Add 9d. post to order.

SHORT WAVE AERIALS

Metrolite 7/22 copper wire with clear plastic coating to prevent corrosion. 25ft 2/6, 50ft 4/6, 75ft 6/-, 100ft 7/6. 14 s.w.g. hard-drawn copper wire, enamelled, 5d. yard. Aerialite model 81 short wave dipole with balanced download, 35/- Egg insulators 5d. each. Pyrex short wave insulators, 2/9 each. Please add 1/- post and packing.

The Radio Constructor

Incorporating THE RADIO AMATEUR



SEPTEMBER 1960

Vol. 14, No. 2

Published Monthly

Annual Subscription 25/-
(including postage)

Editorial and
Advertising Offices

57 MAIDA VALE LONDON W9

Telephone
CUNningham 6141
(2 lines)

Telegrams
Databux, London

- 94 Suggested Circuits No. 118: A Single Transistor Phase-Shift Oscillator, by G. A. French
- 97 In Your Workshop
- 103 Can Anyone Help?
- 104 Understanding Television, Part 32, by W. G. Morley
- 113 Beginners' Short Wave Receiver (Building the "Globe King" 100/A Receiver), by James S. Kent
- 120 A Heterodyne Frequency Meter, by D. Noble, G3MAW, and D. M. Pratt, G3KEP
- 122 The Phone-Guard, by R. M. Summers
- 129 A Simple Reflex Superhet, by A. A. Baines
- 136 The Cooper-Smith "Bantam" 3-4 Watt Amplifier, Part 1, described by W. Holmes
- 139 Radio Topics, by "Recorder"
- 142 RTTY—In Theory and Practice, Part 5, by J. B. Tuke, G3BST
- 147 A High Gain VHF Aerial—The Quad Plus, by A. S. Carpenter
- 149 Trade Review—The Heathkit Balun Coil Set

© Data Publications Ltd, 1960

CONTENTS may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgment of source is given.

CONTRIBUTIONS on constructional matters are invited, especially when they describe the construction of particular items of equipment. Articles should be written on one side of the sheet only and should preferably be typewritten, diagrams being on separate sheets. Whether hand-written or typewritten, lines should be double spaced. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included. Photographs should be clear and sharp. Details of topical ideas and techniques are also welcomed and, if the contributor so wishes, will be re-written by our staff into article form. All contributions must be accompanied by a stamped addressed envelope for reply or return, and should bear the sender's name and address. Payment is made for all material published.

OPINIONS expressed by contributors are not necessarily those of the Editor or the proprietors.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

TECHNICAL QUERIES must be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

CORRESPONDENCE should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers, as appropriate.

REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."

suggested circuits

No 118. A Single Transistor Phase-Shift Oscillator

The Circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential data

AN A.F. OSCILLATOR IS ALWAYS A USEFUL item of equipment to have available, whether it be employed for experimental or service work or, even, for such commonplace applications as Morse practice and the like. It is extremely desirable that such an oscillator should be capable of providing a high level output into circuits of varying impedance, that its waveform should be good, and that it should be self-contained and portable.

The oscillator which forms the subject of this month's article meets all these requirements, and it has the further advantage of being relatively inexpensive. It employs a single transistor in a phase-shift circuit and the output waveform shows little distortion. It offers a high level output and is capable of feeding into a very wide range of impedances. Indeed, it may be coupled directly to a loudspeaker, whereupon it gives an audible tone at reasonably comfortable level. This fact alone makes the oscillator capable of a.f. signal tracing back from the loudspeaker, apart from any of the many other uses to which it may be applied. If the oscillator is coupled to headphones, the volume available is in excess of comfortable level.

Considering the simplicity of the circuit, frequency stability is quite reasonable, a shift in frequency of less than 5% from its nominal 1,000 c/s occurring when the impedance of the circuit to which the output terminals are connected changes from 1M Ω

to 100 Ω . If desired, this stability may be markedly improved by making slight changes to the circuit. The transistor employed is stabilised against thermal runaway. Finally, the circuit can be made into a small, compact and completely self-contained unit, power being obtained from a 9 volt battery with a current drain of slightly less than 5mA.

The Circuit

As may be seen from the accompanying circuit, a fairly conventional phase-shift oscillator arrangement is employed. The collector of the transistor, an OC72, couples into the phase-shift network C₄, C₁, C₂, C₃ and their associated resistors, these feeding back into the transistor base. Thus, the requirements of a phase-shift oscillator are set up. The values in the phase-shift network are experimentally determined to provide oscillation at a nominal frequency of 1,000 c/s. The output of the oscillator is taken directly from the collector of the transistor via the 0.01 μ F condenser C₆.

The resistors R₄, R₅ and R₇ provide a stabilising circuit. The electrolytic condenser C₅ bypasses the emitter resistor R₇. The resistor R₄ brings the transistor to its correct operating point, and its value is discussed later.

Design Features


Several features of the design require to be discussed at this stage.

The fact that the output connection is taken direct from the collector of the OC72 results in the small sacrifice of frequency stability referred to above. Considerably higher frequency stability would be provided by making R₆ a potential divider and tapping the output connection into a point approximately one-tenth down from the h.t. negative rail. This method of connection would, however, cause a heavy loss in output voltage, and it was felt that the advantage of the high level output which is given by coupling direct to the collector more than outweighs the small loss in frequency stability sustained thereby. Constructors who desire a high level of stability at a lower output level can, of course, modify the output coupling in the manner just described.

An improvement in long-term frequency stability may be achieved by connecting an electrolytic condenser of some 25 μ F or so

h.t. voltage of 9, and it was considered that these figures justified the inclusion of stabilising components.

It will be noted that all resistors are given a tolerance of 20% and that no tolerance is quoted for condensers, (whereupon it may be assumed that the latter will have the commercial tolerance, for paper condensers, of 20 or 25%, according to make and value). It is possible, in consequence, that some oscillators constructed to the circuit may run at frequencies removed from the nominal 1,000 c/s. When this occurs the frequency may be brought back to 1,000 c/s by the simple procedure of adjusting the value of one of the resistors in the phase-shift network; and the writer considered that such a process was much preferable to that of commencing with close tolerance resistors and condensers which would be both expensive and difficult to obtain.

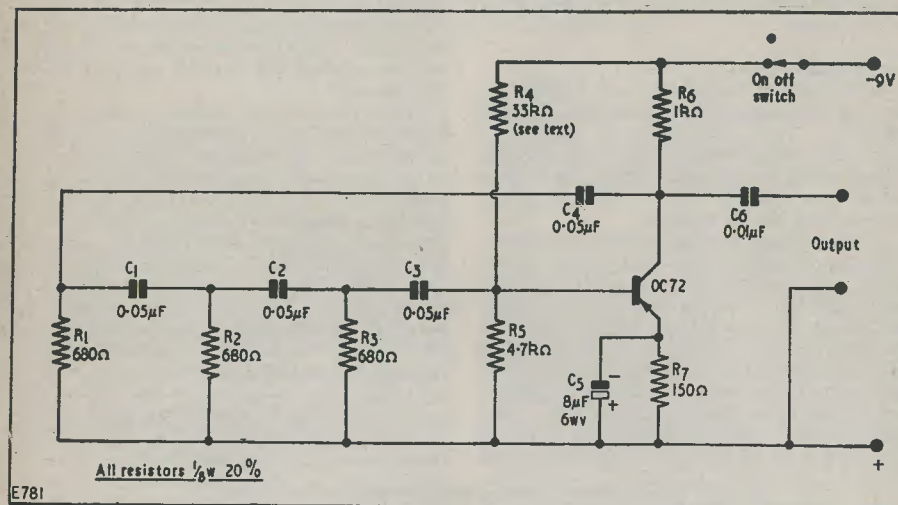

across the h.t. positive and negative rails. This condenser will then prevent shifts in frequency caused by increasing internal resistance in the 9 volt supply battery as it ages. As the result of checks carried out on the prototype the writer felt, however, that such alterations in frequency were not of a sufficiently high order to warrant the cost of the additional component. Nevertheless, the individual constructor who desires a high level of frequency stability may, here again, carry out the simple modification required. The writer found that there was no noticeable change in output frequency for varying supply voltage.

In the circuit the OC72 passes a collector current of slightly under 5mA at an applied

Setting Up the Oscillator

When the oscillator has been wired up it is necessary to ensure that R₄ has a value which causes optimum output to be given.

R₄ brings the transistor on to its most efficient operating point. Its value is not very critical, but it may vary for different transistors and for variations in value (within the tolerance stated) of components immediately connected to the transistor. It was found, with the prototype, that oscillation occurred reliably when R₄ lay between the limits 20k Ω and 45k Ω , optimum results being given at 33k Ω .

To find the best value of R₄ in a particular oscillator, this resistor should be temporarily replaced by a 50k Ω potentiometer in series

with a 15k Ω limiting resistor. The potentiometer should be initially set such that it inserts all its resistance into circuit. The output of the oscillator is next connected to an a.f. amplifier or to high resistance (2,000 Ω) headphones and a 9 volt supply applied. The temporary 50k Ω potentiometer is then adjusted slowly. As the resistance inserted by the potentiometer decreases, oscillation should commence and pass through a fairly flat peak in amplitude. The value of the potentiometer and 15k Ω resistor in series should be measured for the peak setting; and the two replaced by a single fixed resistor of the same value plus or minus some 5k Ω .

After R₄ has been set up all that remains is to adjust the frequency of the oscillator, should this be removed from 1,000 c/s. It should be possible to adjust the frequency by varying the value of one of the phase-shift resistors only, say R₁. Increasing its value will lower the frequency of oscillation, and reducing its value will increase the frequency of oscillation.

Performance Tests

Several performance tests were carried out on the prototype, and these are detailed below.

It was mentioned above that current consumption is slightly less than 5mA for a supply potential of 9 volts. The prototype drew 4.5mA at this voltage.

A further test was concerned with supply potential and the speed with which oscillations commenced when the supply voltage was applied. The recommended supply voltage is 9, and it was found that the oscillator gave a reliably high output when this was reduced to 7 volts. Below 7 volts oscillation amplitude noticeably dropped, and oscillations ceased at 5 volts. The recommended supply voltage may therefore be stated to lie between 7 volts minimum and

9 volts maximum.¹ It was found that, for all supply voltages between 7 and 9, oscillation commenced instantly on application of the supply voltage. (This test was not carried out for supply voltages below 7.) If it were decided to key the oscillator, the key could, therefore, be inserted in either supply lead.

Tests were also carried out on the oscillator whilst its output terminals were connected to the input terminals of an a.f. amplifier. The input resistance of the amplifier was 1M Ω . Fixed resistances were then connected across the output terminals of the oscillator. For fixed resistors down to 15k Ω there was negligible change in output voltage or frequency. As would be expected, below 15k Ω output voltage commenced to drop as the value of the parallel resistor decreased in value, the reduction being particularly evident for resistors below 1k Ω . Nevertheless, the circuit did not cease to oscillate even when a parallel resistor having a value as low as 100 Ω was connected across the output terminals. Slight changes in output frequency became evident for parallel resistors below 2k Ω or so.

When the oscillator output terminals were connected to a 3 Ω loudspeaker via a 50:1 transformer, the resulting tone was audible at a reasonably comfortable level. It is probable that a more careful choice of loudspeaker transformer ratio would have resulted in a louder tone from the speaker, but the writer did not proceed further with this particular test. Finally, a pair of low resistance (30 Ω) headphones were connected across the output terminals. In this case the tone was reproduced at a volume which was in excess of comfortable level.

¹ The supply potential should not exceed 9 volts, as this figure approaches the maximum limiting collector voltage specified by Mullard for the external base resistance used in this particular circuit.

COURSES OF INSTRUCTION. East London R.S.G.B Group

The following classes, organised by the East London R.S.G.B. Group, in conjunction with the Essex County Council, are available for all those interested in amateur radio.

1. Radio Amateurs Examination Course

Wednesday 7.15 to 9.15 p.m. Eight month course for those intending to take the examination.

2. Morse and Codes of Practice

Monday 7.30 to 9.30 p.m. Six month course for those who wish to learn Morse up to G.P.O. requirements for an amateur licence. Arrangements have been made with the G.P.O. for those who, in the opinion of the masters, have reached the required speed, to be tested at the College in the evening by a representative of the Post Office.

The venue for the above classes is: The Ilford Literary Institute, High School for Girls, Cranbrook Road, Ilford, Essex (adjacent to Gants Hill Station on the Central London Tube, and buses pass the door).


The fees for those living in the Essex County Council area are: 30s. for the R.A.E. Course; 20s. for Morse and Codes of Practice; 35s. for both Courses. Students from other parts of London will be admitted as out-County students provided the local authority is notified.

Enrolment nights: 5th to 8th September, 1960, 7 to 8.30 p.m.

Classes commence the week beginning 19th September, 1960.

These classes have been conducted for the past 12 years and 218 students have passed the R.A.E. examination. Those interested should, in the first instance, write to: Mr. C. H. L. Edwards, A.M.I.E.E., A.M.BRIT.I.R.E., 28 Morgan Crescent, Theydon Bois, Epping, Essex. For the reservation of a place, a stamped addressed envelope should be enclosed for reply.

In your Workshop

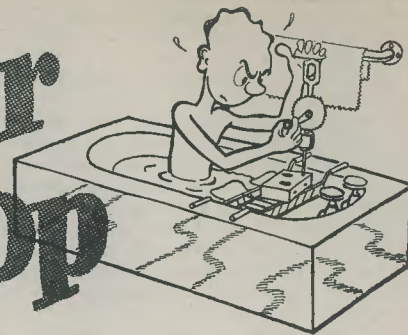

This month Smithy the Serviceman attempts, completely unsuccessfully, to retire to the seaside and Get Away From It All.

"A H," murmured Smithy blissfully to himself, as he basked in the late August sunshine, "this is the life!"

He smiled benignly at a puppy which had wandered up and was sniffing at his thinning hair. The puppy settled down alongside and quietly wagged his tail, evidently approving of Smithy's fragrance. Smithy turned over and sleepily reflected. "How pleasant it is to get away from work for a fortnight and forget altogether about condensers, resistors and intermittent faults!"

Raising himself on one arm he regarded his torso. The first fiery redness had now cleared almost completely, and his skin was taking on a very satisfactory light brown tan. The Serviceman then looked around and, spotting a little man close by with paper white skin, experienced a warm sensation of superiority. It was the first Saturday of his holiday—taken late this year because of pressure of servicing work—and he still had another week in which to deepen the shade of his tan. He wondered vaguely how his assistant Dick, left behind in the Workshop to carry on by himself, was progressing; then dismissed the thought from his mind.

Smithy next glanced at the laughing crowd swimming and splashing in the sun flecked sea. Ah well, he thought, I'll pop in for a swim myself shortly! And he congratulated himself once more on his complete freedom from all the cares and annoyances that radio and t.v. servicing brings in its train.

In the meantime the puppy had come to the conclusion that treasure of immense value lay hidden several feet below the surface of

the sand and was carrying out vigorous excavation work, holding up operations every now and again to insert a briskly enquiring explorative nose. Smithy watched and dozed.

It Could Only Happen To Smithy

The Serviceman was suddenly awakened from his daydreams by the barking of the puppy. Smithy felt too lazy to do more than look around him horizontally, and he saw a pair of red and yellow plimsolls, surmounted by mauve cavalry twill trousers approach him. The dog was evidently on very friendly terms with the person to whom these colourful accoutrements belonged, and he rushed excitedly towards him, eager to demonstrate the extent and capacity of the hole he had been digging. The mauve legs came closer and closer; and there was something about them which caused an abrupt unease in Smithy's mind. Unbelievably, he looked up. At the same time, the person, unbelievably, looked down.

"Oh, no!" they exclaimed in chorus.

There was a deathly hush.

"Dash it all," remarked Smithy aggrievedly.

"I purposely didn't even tell you where I was going for my holiday!"

"I know you didn't," said Dick, equally aggrievedly. "I'm on a coach trip with my girl friend for the day, and we just happened to pick this place."

A further moment passed as they adjusted themselves to the situation.

"Well, I suppose it can't be helped," said Smithy, eventually.

"I suppose not."

"I didn't know you had a dog."

"It's not mine, it's hers," replied Dick. "She's gone shopping for half-an-hour."

"On her own?"

"Of course. Only mugs go shopping with women."

With which sage observation Dick dropped the junior kitbag strung over his shoulder on to the sand, and squatted down beside Smithy. They remained moodily quiet, and watched the puppy as he chose a new stretch of sand in which to prospect. Smithy moved a little to one side to avoid the avalanche of sand which suddenly emanated from between the puppy's hind legs. Somehow, the sea seemed far away.

Dick was the first to break the silence.

e.h.t. regulation. As the brightness of the picture increased so also did the e.h.t. current, with the result that, due to poor regulation, e.h.t. voltage dropped."

Despite himself, Smithy could not help but relapse into his Workshop manner.

"And why does lowered e.h.t. voltage increase picture size?"

"Because", said Dick promptly, "it means that the electrons pass through the deflection field more slowly, and suffer more deflection thereby."

"Fair enough," approved Smithy.

"I found the fault very quickly in this case," said Dick, "because, as soon as I touched the outside graphite coating of the tube, I got a real dickens of a belt!"

Smithy chuckled.

well, in such circumstances, be dangerous."

"That's just about the size of things," agreed Dick. "This set had phosphor-bronze leaf springs which were supposed to contact the outside graphite. However, I had to take the tube out, bend the springs up, and pop it back again before I could get reliable contact. After that, everything went fine."

"Your adventure," said Smithy, "highlights a silly little snag which often occurs with t.v. sets. You may sometimes find, for instance, that the earthing springs are so positioned on the chassis that they only just manage to touch the edge of the outside graphite coating of the tube. If you get a tube whose outside coating has been skimmed a little you find your earthing contacts pressing against glass only! It's a thing to watch out for. Some manufacturers have a much better earthing idea, this consisting of what looks like spring curtain rod stretched out over the bulb of the tube. (Fig. 1 (b).) There's little risk of losing contact with this scheme. Even here, though, it is occasionally possible that with 21 inch tubes, which have a proportionately small area of outside graphite coating, there is a slight risk of the spring being accidentally shifted off the graphite."

No Vision

This seemed to exhaust the present subject, and Dick and Smithy fell silent once more. The sound of the bathers in the water reached Smithy's ears again, and he shifted uncomfortably.

"The next set I had a go at", Dick offered, "had what I thought at first to be a really queer sort of fault. It was an oldish model with a separate Band III converter, and it gave perfect sound with not a trace of vision whatsoever. I checked all the bottles and the voltages in the vision amplifier and i.f. strip, but everything seemed perfect. And yet there wasn't a trace of picture on the tube at all."

Smithy brought his thoughts back to the conversation.

"Did the set have vision a.g.c.?"

"If it had, it was a pretty elementary sort of a.g.c. There was a front panel contrast control, and a gain pot at the back; the latter giving a very fierce control."

"Your fault was the vision detector broken down," said Smithy laconically.

Dick looked disappointed.

"You've spoilt my story now," he complained. "I was just about to tell you how I located it. How do you know it was the vision detector?"

"I was making a slightly inspired guess," confessed Smithy, "based on my own experience. These earlier t.v.'s were usually designed to work on one channel only, whereupon there wasn't much point in

fitting comprehensive a.g.c. circuits. All you had to do was to set up the pre-set gain control at the back to give you acceptable contrast with the front panel control at the middle of its range. At that setting held good because there was only one station to receive anyway! These sets also tended to employ rather earlyish germanium diode vision detectors, such diodes having low turnover voltage figures. When receivers of this type are used in areas of high signal strength, excessively high settings of the gain control can cause the video signal passed to the detector to exceed turnover voltage; whereupon the latter goes pop!"

"That's what must have happened in this case," said Dick, "because the diode had completely broken down. Incidentally, if the video diode in this particular set was liable to break down fairly readily, I can't understand why the manufacturers went to so much

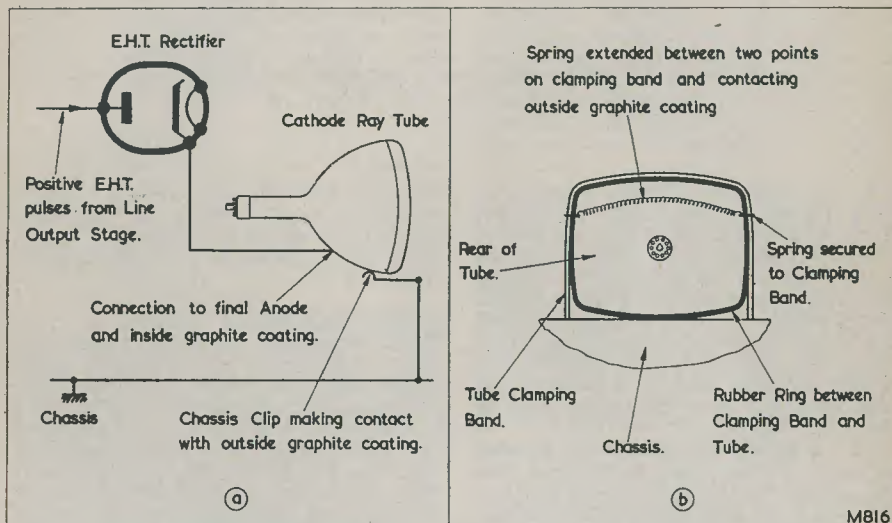


Fig. 1 (a) If the chassis clip connecting to the outside graphite coating of the cathode ray tube fails to make contact, the e.h.t. rectifier circuit loses its reservoir capacity and e.h.t. regulation suffers

Fig. 1 (b) A very reliable method of earthing the outside graphite coating. This diagram, giving a rear view of the tube fitted in a chassis, illustrates how a spring is extended across its bulb, thereby contacting the outside graphite at a large number of points

"Things are going pretty well in the Workshop," he remarked brightly.

"Oh yes," said Smithy non-committally.

"I cleared up that set I had in just before you started your holiday. You know, the one with the blooming picture!"

"By 'blooming'," said Smithy, collecting his thoughts, "I suppose you mean that the picture expanded in size as it got brighter."

"That's right," confirmed Dick. "I surmised that this was a classic symptom of poor

"There's no need to say any more," he laughed. "The only thing that can have happened was that the chassis contact to the outside graphite had gone open (Fig. 1 (a)) and so the e.h.t. rectifier had practically no reservoir capacity to work into. Also, the outside graphite, being unearthed, would soon pick up a charge which would be quite big enough to let you know all about it if you happened to touch it. Indeed, the shock, or the involuntary action following it, could

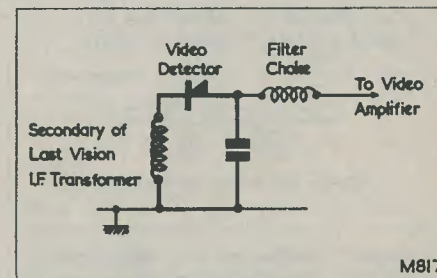


Fig. 2. Signals at the video detector are rectified at relatively low impedance. In consequence, radiation at i.f. harmonics can occur if the components and wiring immediately associated with the detector (shown here in heavy line) are not screened

trouble to hide it away. I had to take the vision detector coil assembly right out of the chassis before I could get at the diode!"

"The detector and its immediate circuit has to be well screened," explained Smithy. "That's why it was inside the coil can in your set. You'll usually find that the sound detector is similarly well screened. Both these detectors handle fairly high signal voltages at low impedance, with the result that you get almost a square wave in the circuit immediately around them. (Fig. 2.) Such a square wave is going to be rich in harmonics of the i.f., and these harmonics are liable to be radiated and picked up by earlier stages in the receiver if you don't screen the detector."

"What trouble would that cause?"

"If", replied Smithy, "an i.f. harmonic was close to, or fell inside, a channel you were receiving, you would get patterning on the

screen or whistles on sound. This effect could be especially noticeable if you happened to use an indoor aerial very close to the receiver, because such an aerial would be

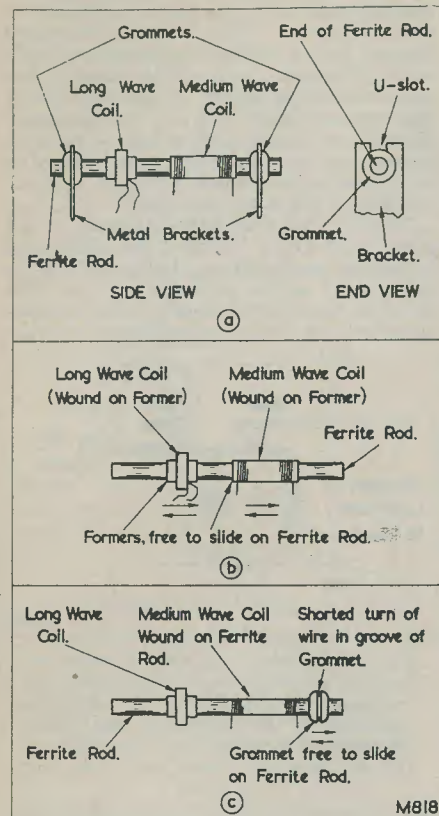


Fig. 3 (a) Typical ferrite rod aerial mounting brackets. When the brackets are made of metal the ferrite rod is held in U-slots in order that it may not be completely encircled by the metal

(b) When the Medium and Long wave coils are wound on formers, their inductance may be varied by sliding them along the ferrite rod

(c) Sometimes the Medium wave coil is fixed to the rod (or is wound directly on to it) whereupon adjustment of its inductance may be achieved by sliding an adjacent shortened turn along the rod

particularly liable to pick up any harmonics 'sprayed out' from the detector stages."

"So you wouldn't advise anyone having, say, one of those indoor V-aerials to place it on top of the cabinet?"

"I wouldn't advise them *not* to do so," replied Smithy, "but I would also say that, if putting the aerial on top of the cabinet caused patterning on picture or heterodynes on sound, they would be very sensible if they moved it some five to ten feet away."

Ferrite Rod Aerial

"My next job", commenced Dick (whilst Smithy groaned inwardly), "was concerned with a little transistor portable. I couldn't cure this one so I'm leaving it for you when you come back."

Smithy groaned again, audibly this time.

"Tell me the worst."

"The set wasn't working when it came in," replied Dick, "and on looking inside I found that the moulding which held the ferrite rod aerial in the middle had broken away. The ferrite rod had, in consequence, been clanging around inside the cabinet, and two of its connections had broken off. I re-made these connections and tied the rod back to what was left of the moulding, but I found that the set gave a very weak performance indeed. I tried the trimmers, but I couldn't get a maximum signal strength setting on either of the trimmers which tuned the ferrite rod aerial, so I presumed that the coils on this aerial had been damaged also. I thought it would be a nice job for you to start work with after your holiday!" concluded Dick brightly.

Smithy sighed.

"What did you tie the rod to the moulding with?" he asked, resignedly.

"Wire, of course."

"Bare wire?"

"Bare tinned copper. 22 s.w.g."

"And did you twist the ends together?"

"Not only did I twist them", said Dick proudly, "but I soldered over the twisted bits as well, for maximum security."

"You muggins!" exploded the Serviceman wrathfully. "Don't you realise that you have put the father and mother of all shorted turns right slap-bang in the middle of that poor little ferrite rod!"

Dick looked perplexed.

"Apart from the fact", continued Smithy censoriously, "that you should never have tied up a thing as brittle as a ferrite rod with wire anyway, your attempts at repair have not only caused it to lose most of its sensitivity, but have also caused the inductance of its coils to be thrown completely haywire. If you look at the mountings used for ferrite rods in commercial receivers you will have seen that, when these are made of metal, the ferrite rod goes into a U-slot. (Fig. 3 (a).) The U-slot doesn't allow the metal to completely encircle the rod and form a shorted turn and so you get no loss of efficiency."

Smithy stopped. The puppy had altered his digging position, and a shower of sand was suddenly projected against the Serviceman's face.

"Mind you," continued Smithy, his speech punctuated by expectorations of sand. "Shorted turns are sometimes added purposely to ferrite rods. In most cases you . . . Can't you control that sand-happy monster of yours?"

"Elvis," called out Dick in a commendably level tone.

The puppy obligingly stopped and directed an enquiring glance at Smithy's assistant.

"Find another hole!"

The puppy walked over, licked Dick's hand and flopped down on the sand beside him.

"Elvis?" queried Smithy. "That's a funny name for a dog, isn't it?"

"My girl friend chose it," replied Dick dispassionately. "It's her dog," he added, emphasising his lack of responsibility in the matter.

"Of course," said Smithy. "Where was I?"

"You said that shorted turns are sometimes added purposely to ferrite rod aerials."

"Oh yes, so I did! Now, in most cases you vary the inductance of a coil on a ferrite rod aerial by sliding it along the rod. (Fig. 3 (b).) The closer the coil goes to the centre of the rod, the greater its inductance. You treat this adjustment as a 'padding' operation during alignment. Sometimes, the medium wave coil is fixed to the rod, or may even be wound directly on it, whereupon adjustment of Medium wave inductance may be carried out by sliding along a shorted turn near the end of the rod at the Medium wave end. (Fig. 3 (c).) The shorted turn consists of a circle of wire fitted in the groove of a grommet and, since it is very close to the end of the rod, it does not, apparently, cause any loss of sensitivity."

Smithy stretched himself luxuriously.

"There won't", he said, smugly, "be any need for me to repair that set when I get back from my holiday! I would suggest that, first thing on Monday, you take off the wire fastening the ferrite rod, and tie the rod to the moulding, instead, with a strong twine such as dial cord. Slap some dope on the twine afterwards, and it'll be as firm as anyone could want. Also, the set will then work properly again, with the ferrite rod trimmers giving maximum sensitivity within their range."

"Fair enough," said Dick, equably. "That's one little job I'll save you from, anyway."

Picture Distortion

Smithy raised a suspicious eyebrow.

"I have no doubt", he said drily, "there are quite a few more."

"Bound to be," replied Dick cheerfully. "There's only me in the Workshop where previously there were two of us."

"I suppose that's a reasonable way of looking at things," conceded Smithy. He reflected that it would soon be time for him to have his swim. "How long did you say your girl friend would be away shopping?" he added pointedly.

"Half-an-hour," said Dick artlessly. "Now the next set that gave me trouble was a new 110 degree t.v. with a shocking trap."

"With a *what*?"

"Shocking trap. It was the worst case of trapezium distortion I've ever seen. The right hand side of the picture was only half the height of the left hand side."

"Ah," said Smithy, dismissing all thoughts of swimming from his mind, "now, if it had been very slight picture shape distortion I'd have suggested that you tried moving the pincushion correction magnets around to see if you could clear it. But the very severe case you mention is beyond the range of adjustment of such magnets. I presume that the trapezium wasn't the result of activities on your part?"

"Of course not." Dick was suitably shocked.

"Fair enough, then," said Smithy. "It's almost certain that we'll need a new deflector yoke for that receiver. When you get back, whip the existing one off and have a quick look round for an obvious fault in the frame windings and in the connections to them. The frame windings can be easily identified because they will almost certainly be wound on to the ring of ferrite material. Look for a really *obvious* snag, such as a wire broken away from its tag or a short circuit. If you can find such a snag, all well and good. If not, order up a new yoke straightaway, as the repair of the existing one will be beyond our capabilities."

"O.K., Smithy," said Dick absent-mindedly. His voice betrayed the fact that his thoughts were elsewhere.

"What's up?" enquired Smithy.

"I'm just thinking about what you said concerning pincushion correction magnets. Are they fitted to all 110 degree deflector yokes?"

"So far as I know, yes," replied Smithy, "but they aren't always capable of being adjusted. In some instances they're fixed by the manufacturer to the polythene moulding which houses the line coils, and shouldn't really be touched by the likes of us. Usually, though, they're stuck on the ends of small brass brackets (Fig. 4), whereupon you bend the brackets around until you get the correction you want."

"Well, now," said Dick thoughtfully.

"That explains another snag I was putting on one side for you!"

"Go ahead."

"This other set also suffered from picture shape distortion, but it was infinitely less severe than the trap case I've just mentioned. In fact most viewers would probably not have noticed it. I rather tended to put the set on one side as having a fault which lay more in your country than in mine, but I did notice that there was a bracket on either side of the yoke assembly, and that one held a magnet and the other didn't."

"There is little doubt that one of the magnets had fallen out of its holder," said Smithy. "That one's an oldie!"

"What I'll have to do then," replied Dick,

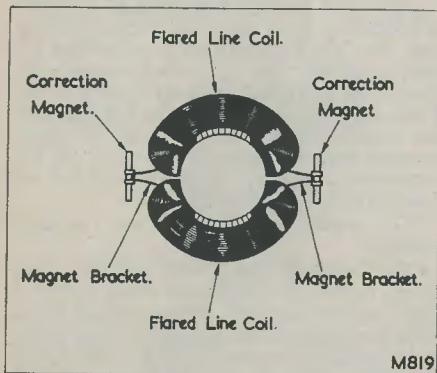


Fig. 4. On many 110° deflection yokes, picture shape correcting magnets are fitted to brackets positioned at the points where the line coils meet. The brackets are made of thin brass and are capable of being bent to any desired shape, thereby allowing the position of the magnets to be readily adjusted. The magnets themselves are in the form of small rods having diameters and lengths of the order of $\frac{1}{8}$ and 1 inch respectively

"is to find the old magnet and stick it back into the clamp again. After which the slight picture shape distortion should clear. Or, at least, it should clear after I've waggled the bracket round a bit."

"That would seem to be the drill," said Smithy, just a little acrimoniously. "If you're lucky you'll probably find the missing magnet lying around in the chassis, bridging h.t. positive down to chassis or something like that. It's own magnetism will, actually, make it liable to stick to ferrous metals such as transformer cores or the chassis. On the other hand, it could have slipped through the bottom of the cabinet, in which case it may well be lost." (Dick's face fell.) "However,"

continued Smithy, "we have a small graveyard of 110 degree yokes in the Workshop. You should be able to sort out a defunct one that looks the same as the one in your set and pinch a magnet off that." (Dick's expression brightened again.) "Don't forget that the magnet has got to go back right way round."

"Which way round will that be?"

"The one that clears the distortion," said the Serviceman shortly.

Printed Circuit Fault

Discussion of deflector yokes was now obviously at an end, and even the rhinoceros-hided Dick realised that there was a reluctance on Smithy's part to talk about technicalities. Dick mustered all his tact in an attempt to change the conversation.

"You're peeling an awful lot, aren't you?"

"Nothing of the sort," replied Smithy indignantly. "I'm acquiring a deep healthy tan."

"Your knees don't look very brown," commented Dick, examining the Serviceman critically.

"If", said Smithy heatedly, "you're going to look at me as though I were a specimen in a glass case I would prefer that we spent the few remaining minutes of our conversation discussing radio."

"Okeydoke," said Dick serenely. After all, he'd done his best. "Now I had a real stinker of a fault on a printed circuit receiver only a day or two ago; and so . . ."

"And so", interrupted Smithy, "you left it for me."

"Why, yes I did, actually," confessed Dick. "It was a little four valve battery portable and it came in suffering from weak reception. Armed with my trusty signal genny I soon discovered that one of the i.f. slugs wasn't tuning and so I whipped off the transformer can."

"The condenser across the tuned winding which didn't tune was a silver-mica which had gone open-circuit?"

Dick looked startled.

"How on earth did you know that?"

Smithy could not help but laugh at his assistant's surprised expression.

"It's the first thing I'd have looked for," he chuckled. "Carry on."

"Well, I popped in another condenser", resumed Dick, "and replaced the transformer can. I switched on and found that, whereas all the valves had lit up O.K. previously, only two of them lit up now! I checked the remaining two on the valve tester and they were perfect, yet when I replaced them in their sockets on the printed circuit board they still refused to light up."

Smithy grinned surreptitiously.

"I'm pretty certain what had happened,"

he said, "but I'm always interested in the processes of your mind. What did you do next?"

"Well, I checked for filament voltage on the pins of the two valveholders and there just wasn't any. And then I had a bright idea. I traced out the copper pattern on the board itself. Do you know, Smithy, there was no circuit on that board whatsoever which would supply i.t. negative to those two valves!"

Smithy raised a politely incredulous eyebrow.

"Honestly, Smithy," continued Dick, "there was just a little island of copper going to those two valveholder pins, and to a few odd condensers and resistors, but it didn't couple to the i.t. negative supply in any way whatsoever."

"Was one of your i.f. can mounting lugs soldered over to your 'island of copper'?"

Dick paused.

"Why, yes, I believe it was."

Smithy watched Dick's expressive face as it registered first puzzlement, then sudden understanding, and finally self-velexation.

The puppy suddenly gave a loud bark of recognition and rushed off across the sand.

"Don't you worry about that set," said Dick hastily, rising confusedly to his feet. "I'll clear it up when I get back! My girl friend's coming and I'll have to be on my way."

"Without even telling me how you're going to clear the fault?"

"O.K. Smithy," laughed Dick, getting ready to leave. "You win! When I put the i.f. can back I only soldered one of its two mounting plugs, because I thought that this would be good enough for testing purposes. I've just realised that the i.t. negative connec-

tion to the two valves which didn't light up was made via the can itself. If I'd soldered both lugs to the copper pattern on the board, everything would have been O.K."

Peace At Last

With which sentence, and with a final "Cheerio" over his shoulder, Dick rushed off to meet his companion. Smithy watched them as they walked away together across the sand. He realised that it might, perhaps, have been more sociable of Dick had he introduced his friend to Smithy, but previous meetings of this sort had tended to be catastrophically unsuccessful due to confusion in Smithy's mind over the names of Dick's current and previous flames.

Smithy brushed away the remaining sand from his hair and lay back happily. Thoughts of servicing and the Workshop faded gradually away. Peace at last!

"Excuse me."

Smithy opened one eye and saw that the little man with the paper white skin was sitting beside him.

"Yes?"

"I couldn't help hear you talking," said the little man, "about radio and television just now, and I was rather interested."

"Oh, yes," said Smithy non-committally.

"Are you in the trade?"

"Dear me, no," replied the little man. "I'm a greengrocer."

"Perhaps you're an amateur then?"

"Gracious me, no," said the little man. "I don't know the first thing about radio. What has happened is that I've got a little portable on the beach with me and I can't get a sound out of it at all. I've just brought it over and I wondered if you could have a look . . ."

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

H.M.V. Radiogram Model 580.—A. G. Stuart, 43 Castle Street, Aberdeen, wishes to obtain the circuit or service manual.

* * *

Tx Type 82 (40R/81).—T. Hannen, Sarden Cottage, Great Maytham, Rolvenden, Kent, would like to obtain a circuit diagram of this equipment. Also required is information regarding the h.t. voltage to supply and tapping points for operation of in-pulses.

* * *

Model 8 "True-View" Portable TV A33.—P. L. Grieveon, 46 Clarence Crescent, Sidcup, Kent, believes this receiver was a "direct-to-customer" supply by Jack Buchanan Enterprises. The service sheet or manual for this t.v. receiver is urgently required and any information on this early receiver would be greatly appreciated.

Transistorised Converter.—J. B. Wheatcroft, "Clevedon", 4 Littlemoor, Newbold, Chesterfield, would like to receive a circuit for a transistorised converter which would convert a low d.c. voltage (4-12V) to 270V d.c. for charging an electrolytic condenser which operates an electronic flash.

German Army Transmitter/Receiver Type 15WSEB.—J. R. Hardcastle, Rington Grange, East Keswick, Nr. Leeds, requires the circuit and information on this equipment. Particularly required is information re input socket connections and voltages. Also required are details for converting the RF26 unit for use on the 10, 15 and 20 metre amateur bands.

Indicator Units Conversion Data.—W. O'Brien, 33 Horace Road, Barton, Torquay, requires conversion data for indicator units to oscilloscopes suitable for radio and t.v.

UNDERSTANDING TELEVISION

PART 32

By W. G. MORLEY

The thirty-second in a series of articles which, starting from first principles, describes the basic theory and practice of television

IN LAST MONTH'S CONTRIBUTION TO THIS series we introduced the subject of the sync separator. We saw how the synchronising signals are clipped from the transmitted waveform and, also, how differentiated sync pulses were passed to the line sawtooth generator in order that the latter may remain in synchronism during the frame sync pulses. We shall now carry on to synchronising the frame sawtooth generator; and this will necessitate further reference to the synchronising waveform of the 405 line system which was published in last month's issue. (See Fig. 13, page 26.—ED.)

Integration

In order that the frame sawtooth generator may be kept in synchronism, it is necessary that it should receive synchronising information from the transmitted waveform. As was shown in Fig. 13, which illustrated the synchronising waveform for the 405 line system, eight broad frame synchronising pulses are transmitted at the end of each frame. In the manner in which they are transmitted such pulses cannot be applied directly to the frame sawtooth generator. In consequence synchronising information has to be obtained by some form of processing. We shall now examine how such processing may be carried out.

Fig. 193 (a) illustrates an *integrating circuit*. This consists of a series resistor followed by a condenser. In Fig. 193 (b) we apply a series of positive-going line sync pulses to the integrating circuit, the integrated signal at the output terminals being shown

below the pulses which are applied to the input.

At point "A" of Fig. 193 (b) we have the leading edge of the first positive-going pulse. Immediately after point "A" the condenser commences to charge to the new potential applied to the input terminals, its rate of charge being slow because of the series resistor. In consequence, there is a gradual rise in potential across the condenser. At point "B" the positive-going pulse ceases, whereupon the condenser commences to discharge, again slowly. At point "C" we have the leading edge of the next sync pulse and, at point "D", the end of that pulse. The voltage across the condenser commences, once more, to rise slowly at point "C", and to fall, slowly, at point "D". The process is repeated for each successive pulse applied to the input terminals.

In Fig. 193 (c) we apply both line and frame synchronising pulses to the integrating circuit. The input pulses shown are those given by clipping the even frame waveform of Fig. 13, and both line and frame pulses are positive-going. Up to point "P" in the diagram the output of the integrating circuit is similar to that shown in Fig. 193 (b), wherein line sync pulses only were integrated. Point "P" marks the leading edge of the first broad frame pulse and, once again, it defines the point where the condenser in the integrating circuit commences to charge. However, in this instance the length, in time, of the applied pulse is considerably longer than that of the previous line sync pulses, with the result that the condenser is able to

charge to a much higher potential than it did during the length of a line pulse. At point "Q" the first frame pulse comes to an end, and the condenser commences to discharge slowly. Very shortly afterwards, at point "R", we have the leading edge of the next frame pulse, and the condenser ceases to

potential across the condenser falls during the next few pulses to the average potential it held before point "P".

It will at once be seen that, due to the integrating circuit, the frame synchronising pulses have been made to produce a single jagged pulse having an amplitude consider-

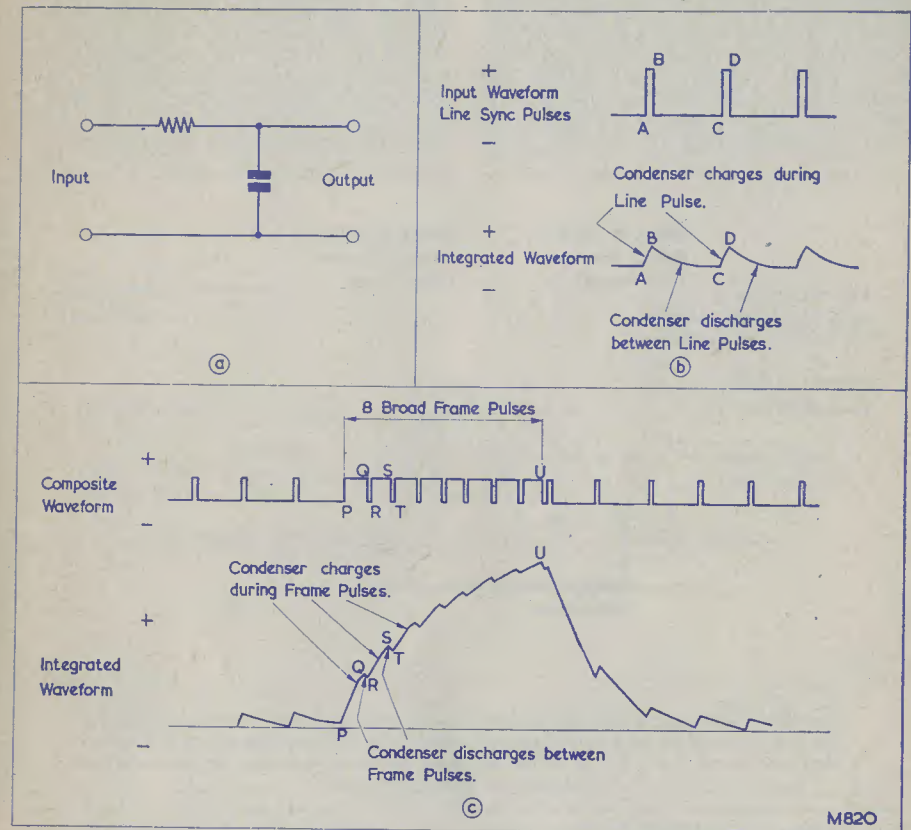


Fig. 193 (a) An integrating circuit

(b) The waveform appearing at the output terminals of the integrating circuit when line sync pulses are applied to its input

(c) If the composite synchronising waveform for the 405 line system (even frames) is applied to the integrating circuit, the broad frame pulses cause a single large integrated pulse to appear at its output

discharge and commences to charge once more. At points "S" and "T", the process is repeated, the condenser discharging over a relatively short time and charging over a relatively long time. The process continues until, at point "U", the trailing edge of the last frame pulse appears. After point "U" normal line sync pulses reappear, and the

ably greater than that of the integrated line sync pulses. The single integrated frame pulse does not have the sharp leading edge we have, up to now, associated with synchronising pulses, but it is still, nevertheless, quite suitable for application to a frame sawtooth generator for the purpose of initiating its flyback period.

Integrating Even and Odd Frames in the 405 Line System

An examination of Fig. 13 shows that the frame synchronising pulses for even and odd frames have the same number and shape. At the same time, the line sync pulses immediately preceding the frame pulses differ in timing for even and odd frames. On even frames the leading edge of the last line sync pulse is spaced by a period equal to one line away from the leading edge of the first broad frame pulse; whilst, on odd frames, the leading edge of the last line sync pulse is spaced by a period equal to half a line only from the leading edge of the first frame

potential starting point than does that for even frames. This higher potential is retained throughout the leading edge of the integrated pulse, and the result is shown in the diagram. If the integrated waveforms of Fig. 194 were applied directly to the frame sawtooth generator initiation of frame flyback would occur at a single potential, such as that at line "XY". It will be seen that the two waveforms of Fig. 194 do not cut the line "XY" at the same instant in time (relative to the leading edge of the first frame sync pulse). In consequence, direct application of the integrated pulses to the frame sawtooth generator must always result in a

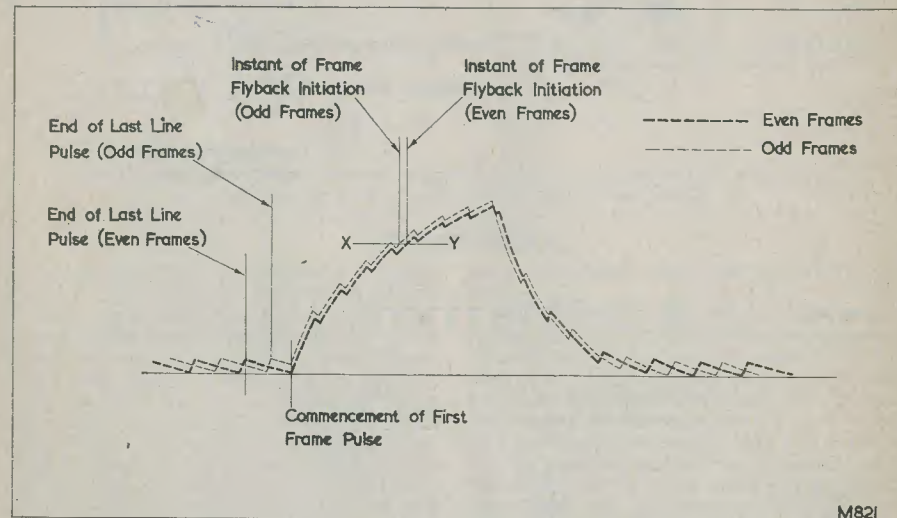


Fig. 194. Since, in the 405 line system, the last line sync pulse is spaced away from the first frame pulse by a period equal to a line of a half-line (according to whether the frame be even or odd) the integrated frame pulses do not have the same starting potential on alternate frames

pulse. This dissimilarity causes slight differences between the integrated frame pulses for even and odd frames.

Fig. 194 illustrates the integrated frame pulses given by even frames and odd frames superimposed upon each other. The waveform for even frames is shown in dashed line and that for odd frames in dotted line. The dashed line waveform is similar to that of Fig. 193 (c).

At the point when the leading edge of the first frame pulse appears it will be seen that the condenser in the integrating circuit has a higher charge for odd frames than it has for even frames, this being due to the fact that it has had less time to discharge since the last line pulse. Thus, the integrated frame pulse for odd frames commences at a higher

potential starting point than does that for even frames. This higher potential is retained throughout the leading edge of the first frame sync pulse) between frame flyback initiation on even frames and frame flyback initiation on odd frames.

The dissimilarity in time between the two integrated frame pulses, although small, is capable of seriously upsetting the goodness of the interlace given in the reproduced picture. Perfect interlace occurs when the lines of one frame lie exactly centrally between the lines of the other frame. The dissimilarity in time, evident in Fig. 194, would cause the lines in the frame following the integrated odd frame pulse to take up a position lower than the exactly central condition, because the frame flyback period immediately preceding them was initiated at

a relatively earlier time. In practical instances it is possible for the interlace under these conditions to be so poor that visible "pairing" takes place.¹ Examination of Fig. 194 will show that the dissimilarity in time between the odd and even integrated pulses varies for different heights of the line "XY". This effect was sometimes taken advantage of in early 405 line receivers wherein integrated frame pulses were applied directly to the frame sawtooth generator; setting-up instructions for such sets stating that the frame hold control should be adjusted to a position which gave best interlace. (Adjusting the frame hold control over the range in which frame synchronisation

employed, in one form or another, in all modern receivers. They are normally given such names as "pulse shaper", "interlace filter", and so on.

A typical and frequently employed circuit technique is illustrated in Fig. 195. In this diagram the presence of R_1 causes integrated pulses to appear across C_1 , these being applied, via a diode, to condenser C_2 in parallel with resistor R_2 . The time constant of C_2 and R_2 is normally considerably longer than that of the integrating circuit given by R_1 and C_1 . Also, C_2 normally has a larger value than C_1 . The sync pulses applied to R_1 and C_1 are negative-going (as would occur at the anode of a sync clipper following a

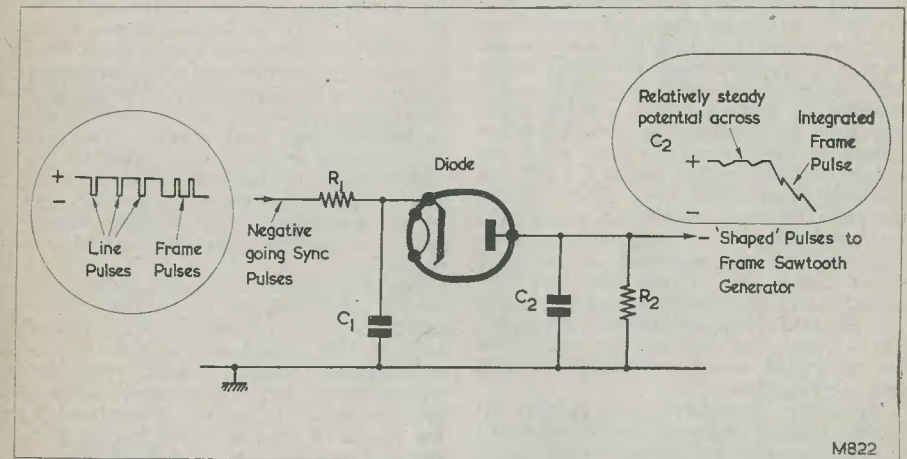


Fig. 195. A circuit which reduces the dissimilarity in time (relative to the leading edge of the first frame pulse) between alternate integrated frame pulses in the 405 line system

occurs has the effect of varying the height of line "XY" in Fig. 194. This is because it varies the negative voltage on the appropriate grid of the frame sawtooth generator at the moment when the integrated sync pulse is applied to it.)

Improving Interlace with the 405 Line System

A number of different circuit devices have been developed to overcome the dissimilarity in time between the integrated frame pulses for even and odd frames which occurs with the 405 line system. Such devices are

¹ "Pairing" is a loose term which usually describes the condition where interlace is sufficiently poor for adjacent pairs of lines in alternate frames to merge together, producing a picture having, apparently, only half the lines offered by the system. Sometimes, the term is used to describe obviously poor interlace without actual merging of adjacent lines.

cathode-modulated cathode ray tube). The small negative-going integrated line sync pulses between frame sync pulses cause C_2 to charge, via the diode, to a potential which is very nearly equal to their peak value. In consequence, the diode only conducts during integrated line sync pulse peaks, and the potential across C_2 is relatively steady. On the arrival of the frame sync pulses, an integrated pulse much larger than the line sync pulses appears across C_1 . The diode conducts during the leading edge of this large integrated pulse, causing C_2 to charge to a much higher potential than it held during the line sync pulses. The leading edge of an integrated pulse appears, therefore, across the plates of C_2 also. On the cessation of frame sync pulses both C_1 and C_2 discharge. Because of the longer time constant in C_2

and R_2 , C_2 discharges more slowly than C_1 and, for a period, the diode is non-conductive. When the potential across C_2 falls to the peak value of the integrated line sync pulses the diode conducts on their peaks, and the circuit reverts to the condition it held before the arrival of the frame sync pulses.

If the foregoing is considered a little more fully, it may be noted that between frame sync pulses—where the diode is non-conductive almost all of the time—the integrating circuit is formed by R_1 and C_1 . On the arrival of the frame sync pulses the diode becomes conductive, with the result that the integrating circuit is provided by R_1 and by C_1 in parallel with C_2 .

The integrated frame pulse across C_2 will, due to the additional capacity brought into circuit by the diode, have a lower amplitude and a less steep front than that which would be given by C_1 on its own. Provided that the pulse across C_2 is large enough to synchronise the frame sawtooth generator, this represents no disadvantage. The important feature of the circuit is that, since the integrated frame pulses across C_2 for odd and even frames both have almost exactly the same starting potential (i.e. a potential very nearly equal to the peak potential of the integrated line sync pulses held, as a relatively steady charge, in C_2) then both will have almost exactly the same shape and amplitude. The dissimilarity in time between the pulses shown in Fig. 194 does not then occur, and the controlled sawtooth generator should give good interlace.

A further, secondary, point is that the trailing edge of the pulse appearing across C_2 is the same for both odd and even frames because it is formed entirely by the discharge of C_2 into R_2 , the diode at this time being non-conductive. As a result, it may be stated that the circuit of Fig. 195 provides integrated frame pulses on odd and even frames whose leading and trailing edges are very nearly identical.

Most conventional frame "pulse shaping" circuits following integrating circuits in practical receivers employ the basic principle illustrated in Fig. 195, integrated frame pulses for odd and even frames being allowed to commence at very nearly the same starting potential. Indeed, many practical arrangements are almost identical to the simple circuit of Fig. 195, the main difference being that, since the integrating circuit is normally connected to the sync clipper anode, R_2 is returned to a fixed positive potential instead of to chassis. Alternatively, a large value d.c. blocking condenser may be inserted between the integrating circuit and the diode to enable R_2 to be returned to chassis.² Also, in practical circuits, it is usual to replace the

thermionic diode of Fig. 195 by a germanium diode or a Westector.³

Differentiating the Frame Sync Pulses in the 405 Line System

An alternative solution to the interlace difficulties associated with the 405 line system is given by obviating the integration process altogether. The frame synchronising information is, instead, extracted from the composite waveform by differentiation.

Fig. 196 (a) illustrates a synchronising waveform, applicable to an even frame in the 405 line system and having negative-going pulses, applied to a differentiating circuit. The latter has a longer time constant than would occur in a differentiating circuit intended to pass spike shaped pulses to the line sawtooth generator. Before point "A" in Fig. 196 (a) the leading edge of each successive line sync pulse causes the potential on the output terminals of the differentiating circuit to go rapidly negative. The condenser then discharges slightly until the trailing edge of the line sync pulse appears, whereupon the potential on the output terminals goes rapidly positive. Between line sync pulses, the condenser discharges slowly, causing the output potential to go slightly negative before the leading edge of the next line sync pulse.

The first broad frame sync pulse arrives at "A", whereupon the output of the differentiating circuit goes rapidly negative, to point "B", in the same manner as did it with the leading edges of the line sync pulses. The condenser then commences to discharge until point "C" is reached. Since, however, the length of time occupied by the broad frame sync pulse is much greater than that occupied by a line sync pulse, the condenser discharges by a larger amount between points "B" and "C" than it did during the line sync pulses. At point "C", therefore, the output potential of the differentiating circuit is more positive than it is at the end of a line sync pulse. Immediately after point "C" the first broad frame pulse ceases, and its trailing edge causes the output potential to go rapidly positive, reaching point "D". After point "D" subsequent broad frame pulses cause the output potential to go more and more positive, as shown in the diagram.

It will be seen that point "D" in Fig. 196 (a) is significantly more positive than any previous point in the waveform, and it is possible to synchronise a frame sawtooth generator with the section of "CD" which

² In the latter case the junction of the large value condenser and the diode would be held at a fixed average potential by a potentiometer between chassis and the h.t. positive rail.

³ "Westector" is a brand name applied to small metal-oxide rectifiers manufactured by Westinghouse Brake and Signal Co. Ltd.

lies between lines "WX" and "YZ". In practical arrangements it is desirable to clip the remainder of the differentiated waveform so that no point of it is more positive than point "D". The frame sawtooth generator can then have its flyback initiated only by the upper section of the sharp pulse-face "CD".

the trailing edge of the pulse. The output potential now goes rapidly positive, causing the sharp pulse-face "RS" to appear at the output of the differentiating circuit. A frame sawtooth generator capable, as in Fig. 196 (a), of being synchronised by potentials between lines "WX" and "YZ" would then have its flyback initiated by the sharp pulse-

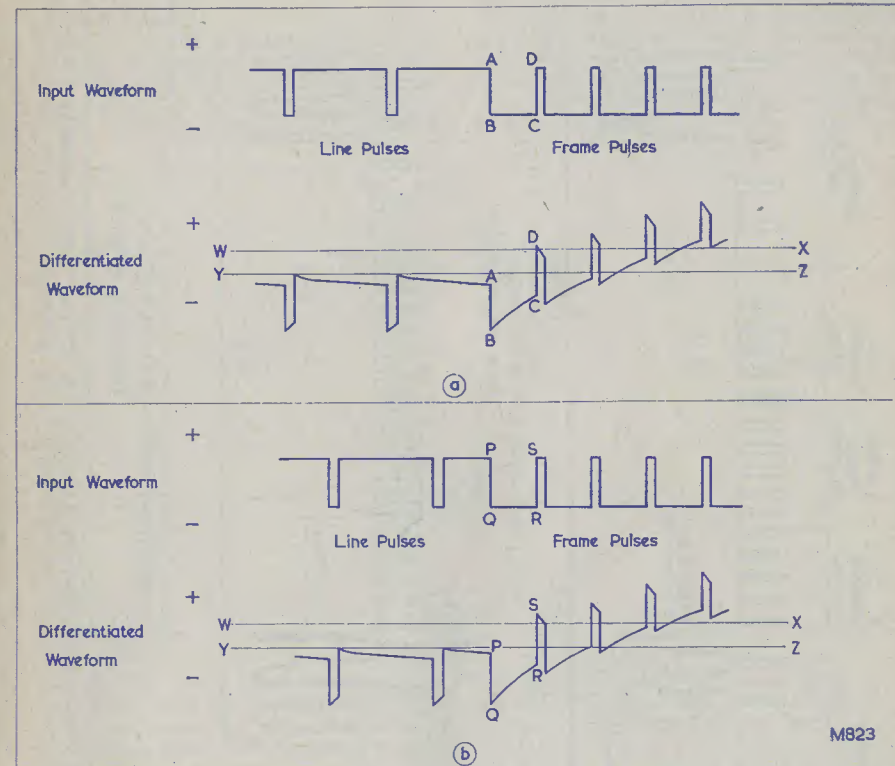


Fig. 196 (a) Obtaining a frame sync pulse in the 405 line system by differentiation. In this diagram the even frame waveform is differentiated

(b) Differentiating the old frame waveform

Fig. 196 (b) illustrates the results given by differentiating the composite waveform for odd frames. In this diagram the first broad frame pulse appears at point "P". Since the last line pulse is spaced away from point "P" by a half-line period only, the condenser in the differentiating circuit discharges less than it did before point "A" of Fig. 196 (a). In consequence, point "P" is slightly more positive than point "A". The leading edge of the first frame pulse causes the output potential to go rapidly negative, to point "Q", this being followed, at point "R", by

face "RS". Since the starting point of the first differentiated frame pulse, at "P", is slightly higher than point "A" in Fig. 196 (a), all subsequent parts of the differentiated waveform will also be slightly higher. Thus, the upper line "WX" cuts pulse-face "RS" at a relatively lower level than it cuts pulse-face "CD". This is of no importance, the entire point of the circuit being that between the limits "WX" and "YZ" frame synchronisation on both odd and even frames occurs at the same point relative to the leading edge of the first frame pulse, with the

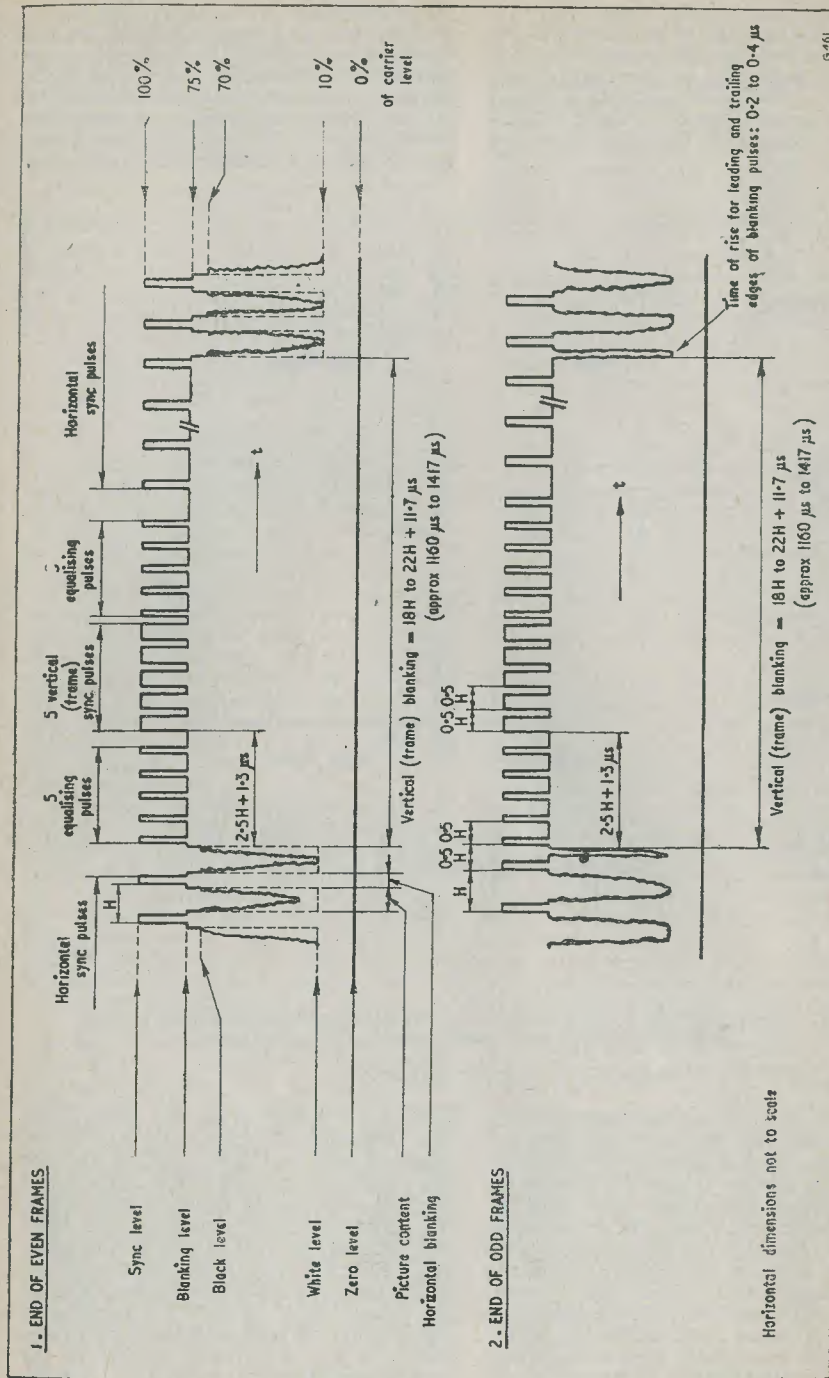


Fig. 18. (a) Synchronising waveform of the "C.C.I.R. 625 line" system. (Actually "625 line system for 7 Mc/s channel width.") The dimension H refers to the duration of 1 line

result that good interlace is possible. (In practice, the top sections of both "CD" and "RS" would, in any case, probably be clipped to the same level in the subsequent circuit which clipped the remainder of the differentiated frame pulse waveform.) It should be noted that both pulse-faces "CD" and "RS" correspond to the trailing edge of the first broad frame pulse.

Equalising Pulses

There is no necessity to employ circuit techniques of the type we have just considered ("pulse shaping" circuits or differentiating circuits followed by clippers) in receivers working on the C.C.I.R. 625 line

Fig. 18 (a)⁵ shows the sync pulse waveforms given at the end of even frames and at the end of odd frames. Commencing with the waveform for the end of even frames it will be seen that we have several positive-going line sync pulses⁶ before we reach the end of picture information. Immediately after the last line of picture information we have five equalising pulses. These pulses are half as wide as the line sync pulses and they are spaced out so that their leading edges are at half line intervals. After the last equalising pulse we have the first of five broad frame pulses, these being followed by a further five equalising pulses. After the last equalising pulse normal line sync pulses, spaced at

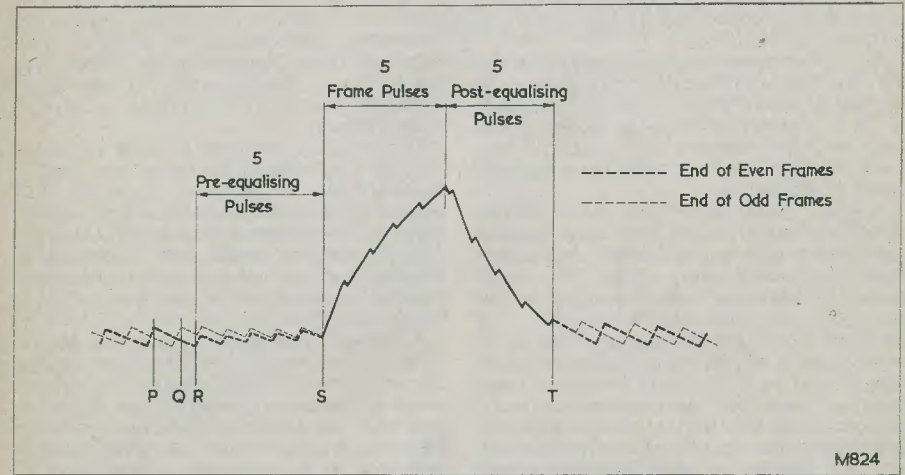


Fig. 197. With the American 525 and C.C.I.R. 625 line systems, the pre-equalising pulses cause the starting potentials for alternate integrated frame pulses to be very nearly equal. Also, the post-equalising pulses cause the formation of similar trailing edges. In consequence, alternate integrated frame pulses are nearly identical

or American 525 line systems. This is because, in these systems, equalising pulses are inserted into the signal to make the integrated frame pulses closely identical. Equalising pulses appear between the last line carrying picture information and the first broad frame pulse, and immediately after the last broad frame pulse.⁴ To understand the function of these pulses it will be sufficient to consider the C.C.I.R. 625 line synchronising waveform, this being very similar to the American 525 line synchronising waveform.

intervals of one line, reappear on the waveform.

In the waveform for the end of odd frames the picture information ends with a half line. We then have the first of five equalising pulses, to be followed by the five broad frame pulses. These are followed by a further five equalising pulses, after which normal line sync pulses appear once more. The leading edge of the first line sync pulse is spaced away from that of the last equalising pulse by a half line period.

In order to distinguish between the two sets of equalising pulses, those which appear

⁴ Complete information on the synchronising waveforms for the C.C.I.R. 625 line and American 525 line systems was given in "Understanding Television" Part 4, April 1958 issue.

⁵ Reproduced from the April 1958 issue.

⁶ Designated "horizontal sync pulses" in Fig. 18 (a).

before the frame pulses are called the *pre-equalising pulses* and those which appear after the frame pulses the *post-equalising pulses*.

Fig. 197 illustrates the result of integrating the two waveforms of Fig. 18 (a). The integrated waveform for the end of even frames is illustrated in dashed line, and that for the end of odd frames in dotted line.

Commencing with the end of even frames, and following the dashed line, we have, at "P", the commencement of the last line of picture information. This last line ends at "R", whereupon we have the first equalising pulse. Since the duration of this pulse is only half that of a normal line sync pulse, it causes the integrating condenser to charge to a lower value. Successive equalising pulses then produce the dashed waveform between "R" and "S".

At "Q" we have the commencement of the last half line of picture information given at the end of odd frames. This half line ends at "R". Following, now, the dotted waveform we have, between "R" and "S", the waveform given by integrating the equalising pulses which follow.

At "S" both waveforms have almost exactly the same potential. This is because identical waveforms—both consisting of five equalising pulses and having the same average voltage—have been applied to the integrating circuit between "R" and "S", and the condenser in the integrating circuit tends to take up a charge equal to the average voltage. After "S" the first broad frame pulse commences and is integrated in normal fashion. Since the starting potentials for the integrated pulses are almost exactly the same for both waveforms, both integrated pulses have almost identical leading edges. The integrated frame pulses continue to remain near identical during the post-equalising pulse period. When, at "T", the post-equalising pulses cease, the two waveforms become separate again, settling down after a few further lines to integrated line pulses of equal amplitude.

Since the integrated pulses in Fig. 197 are the same, or very nearly the same, for both the end of even and the end of odd frames, it follows that a frame sawtooth generator may be directly synchronised by them, and that good interlace will result.

The equalising pulses added to the composite waveform do not prevent the line sawtooth generator from remaining synchronised during the frame blanking period. We saw in Fig. 1917 that, in the 405 line

system, the line sawtooth generator has its flyback initiated by alternate differentiated pulses spaced at half line intervals during the frame synchronising period. Differentiating the C.C.I.R. 625 line system waveform causes pulses to appear at half line intervals not only during the frame pulse period, but also during the pre-equalising and post-equalising periods. As in the 405 line instance the line sawtooth generator has its flyback initiated by alternate half line pulses until the first normal line sync pulse appears once more, these half line pulses now appearing in the equalising periods as well as in the frame pulse period.

Frame Sync Pulse Amplitude

After the frame sync pulse has been separated from the transmitted signal and, if necessary, processed by any of the methods discussed above ("pulse shaping" circuits and the like) it is finally applied to the frame sawtooth generator, whereupon it initiates frame flyback.

It is a fairly common practice to ensure that the amplitude of the frame sync pulse is relatively low at the point at which it is applied to the sawtooth generator, and it may even be attenuated after processing to achieve this low amplitude.⁸ The result is that frame synchronisation in many receivers tends to occur over only a small range of the frame hold control.

The reason for employing a low amplitude synchronising pulse is that such a pulse corresponds to a similarly low degree of coupling between the input to the sync separator and the sync application point of the frame sawtooth generator. The sawtooth generator is, in consequence, less liable to have its flyback initiated by random bursts of impulsive interference.

Next Month

In next month's contribution we shall carry on to flywheel sync circuits.

Reference

The information given in Fig. 18 (a) is taken from Report No. 83, Television systems; Extract from the documents of the C.C.I.R. VIIIth Plenary Assembly, Warsaw, 1956. The term "field", where it appears in extracts from the report, has been changed to "frame".

⁷ Published in last month's issue.

⁸ Such attenuation may be provided by inserting a fixed resistor in series with the point of application to the sawtooth generator.

BOUND VOLUMES—"The Radio Constructor"

Bound volumes of the magazine (Vol. 13, August 1959 to July 1960 inclusive) will be available early in October. See advertisement inside front cover of this issue.

Beginners' Short Wave Receiver

Building the "GLOBE-KING" 100A RECEIVER

by JAMES S. KENT

In which our contributor describes, step-by-step, the construction of a simple receiver for Short wave operation. Presented specifically for the beginner, this article should be of great assistance to those about to embark on that never-to-be-forgotten venture—constructing the very first receiver

THE ABOVE HEADING HAS CAUGHT YOUR eye! You are a beginner who has acquired an interest in radio and you have ventured into this vast and strange new world for the first time. Having purchased this magazine, possibly for the first time, the designs, circuits and terms puzzle you immensely. You would like to build a simple radio set that would really work. There is no one to help or give you advice and you live, possibly, far from a radio shopping centre. All very bewildering and difficult, isn't it?

Nevertheless, the above heading has caught your eye! In time, and with the help of other articles and books, you will learn about the circuits and terms but here, and now, is something you can really "get your teeth" into and get down to as a practical start.

Firstly the tools required. All that you need for building a simple receiver, such as the one described here, are the following: pencil-bit type electric soldering iron, small pair of sidecutting pliers, a small screwdriver and penknife. The soldering iron, although possibly a little on the expensive side initially for the younger beginner, will prove to be cheap over the long period of its life.

Soldering

Before commencing operations it must be pointed out that good soldered joints should be made throughout the construction of the receiver—the additional resistance introduced by even one single poorly soldered connection will easily ruin the performance of an otherwise perfect set. Using a non-corrosive

solder and flux, "Multicore" radio/t.v. quality three-cored solder is recommended, carefully prepare each joint just prior to the actual soldering by cleaning the component wire ends and tags, etc. Using the blade tip of an ordinary pocket-knife, scrape clean and brighten all such wire ends, tags, etc. Having done this, apply to the joint, at the same time, both the solder and the iron—having first, of course, allowed the iron to reach its working temperature. Never carry the solder on the iron to the joint or "dwell" on the latter too long with the hot iron—both cause the solder to lose its tin content. Soldering is an acquired knack and one where practice makes perfect. For more information on this subject, together with an excellent introduction to the short waves, the beginner is recommended to purchase a copy of *Short Wave Receivers for the Beginner* (Data Publications Ltd.).

Preliminaries

Five easy-to-follow diagrams, together with illustrations of the completed receiver and the circuit diagram, are presented here in order to make the construction of this receiver as easy as possible. This is a practical article and those wishing to obtain knowledge of radio theory and circuit applications should obtain reasonably inexpensive books dealing with such subjects.¹

¹ Recommended books for the beginner, inexpensive, lucidly and clearly written, are: *Foundations of Wireless, 7th Edition*, by M. G. Scroggie, B.Sc., M.I.E.E., at 15s. net; *A Beginner's Guide to Radio*, by F. J. Camm, at 7s. 6d. net—both available from the Modern Book Co., 19 Praed Street, London, W.2.

Assembly and Wiring

Having obtained all the components, place a newspaper on the table or bench—this will avoid scratching the transfer already affixed to the front of the receiver. Using the nuts, screws and washers provided, mount into position both the valve and coil holders, as shown in Fig. 1, noting that the flanges of these are positioned under the chassis. Also note that three chassis solder tags must be mounted into position exactly as shown, one of these being a double tag. Fit these tags between the washers and the nuts. The nuts should be tightened down really firm, any tendency to movement will result in an intermittent fault later.

Stage 1

Following the large numerals in Fig. 1, commence wiring using plain tinned copper wire. Cut three lengths approximately $1\frac{1}{2}$ in each and use as follows:

- (1) Solder chassis tag to valveholder tag 1.
- (2) Solder chassis tag to valveholder tag 5.
- (3) Solder chassis tag to coilholder tag 2.
- (4) Solder chassis tag to black lead (thread this lead through grommet and prepare for soldering by cutting back approximately $\frac{1}{4}$ in of rubber insulation, then insert the wire end into the tag hole and solder at this point).

Stage 2

(5) Thread the red lead (see Fig. 2) through the rubber grommet and solder one end of the filament resistor R_3 , suitably shortened, to this lead after the latter has been bared. Next, solder the free end, suitably shortened, of R_3 , together with one wire end, suitably shortened, of the grid resistor R_1 to tag 3 of the valveholder.

(6) Solder the remaining end of R_1 and one end of C_5 , again having suitably shortened the wire ends, to tag 4 of the valveholder.

(7) Thread the free end of the yellow lead through the rubber grommet (one end of the aerial condenser C_1 is already connected to this as supplied). Take the wire ends, suitably shortened, of both the grid and the aerial condenser (C_5 and C_1 respectively) to tag 1 of the coilholder, and leave unsoldered for the present, two further connections being made later to this point. (See Stage 3, step 9.)

Stage 3

(8) Obtain a length of insulated sleeving, about $1\frac{3}{4}$ in in length, threading this over a length of plain tinned copper wire so that each end of the wire protrudes about $\frac{1}{4}$ in at each end of the sleeving. Solder this from tag 2 of the valveholder to tag 4 of the coilholder (see Fig. 3).

Obtain the bandspread variable condenser C_3 and secure to the front of the chassis in the aperture provided. Note that the fixed vanes (stator) shaft tip is the soldering point—as shown in Fig. 3. The two condenser mounting brackets can now be mounted (see Fig. 4), using nuts, screws and washers. Fit to these brackets the two remaining variable condensers—these are identical components and each can be fitted in either position. Secure into position the dial scale with the bandset condenser C_2 . (See Fig. 4.) Note that only the first nut is removed from these two condensers when mounting into position on the brackets. Under no circumstances should be second nut be removed or even unscrewed.

(9) (See Fig. 3). Cut two lengths of sleeving, one $1\frac{1}{4}$ in in length and the other $\frac{1}{2}$ in in length, and two wire lengths about $\frac{1}{2}$ in longer. Thread these wires through the sleeving so that approximately $\frac{1}{4}$ in protrudes at each end. Solder two ends to tag 1 of the coilholder together with the ends of the aerial and grid condenser wires previously left unsoldered. (Stage 2, step 7.) The best method of connecting the four wire ends is to first take a single wire and thread this through the tag hole, wedging the three remaining wires under this to secure them all into position, soldering only when this has been done. Solder the free end of the short wires to the bandspread condenser C_3 . The remaining sleeved wire should now be fed through the hole in the chassis (12), whereupon its other end is connected to the bandset condenser C_2 , soldering to the fixed vanes tag.

(10) Obtain the green lead and solder it to one end of the suitably shortened wire of the anode resistor R_2 . Thread the free end of this lead through the rubber grommet. (See Fig. 3.) Shorten the other wire end of R_2 and place through the coilholder tag 3 but do not solder as yet. Obtain a length of sleeving, some $2\frac{3}{4}$ in in length and a wire about $3\frac{1}{4}$ in long. Thread the wire through the sleeving and solder one end, together with the wire end of R_2 , to tag 3 of the coilholder. Feed the sleeved wire through the chassis at point (11), connecting its other end to the fixed vanes tag of the reaction condenser (C_4).

Stage 4

(11) Fit the control knobs to the various spindles, the smallest being fitted to the spindle of the bandspread control and the pointer knob to the bandset spindle. Fit the latter knob in such a manner that the pointer indicates zero when the condenser moving vanes (rotor) are completely out of mesh. At the other end of the scale, if this knob is correctly fitted, the indicator should be at

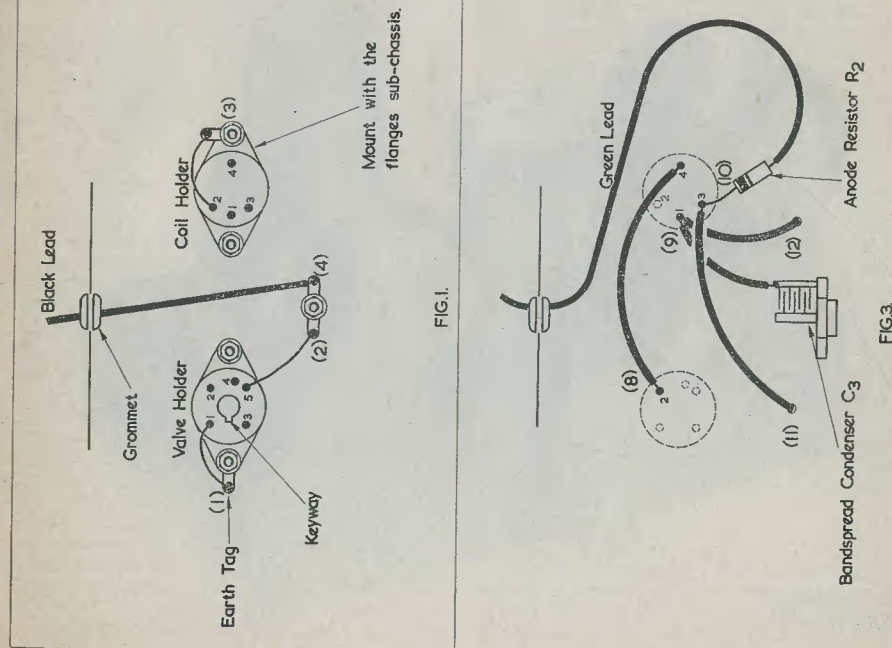


FIG. 1

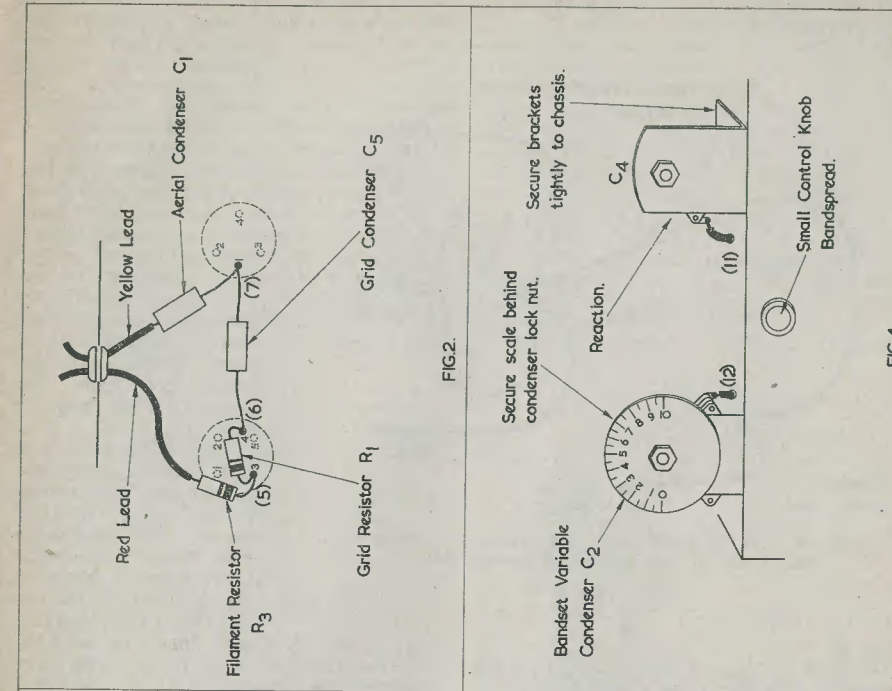


FIG. 2

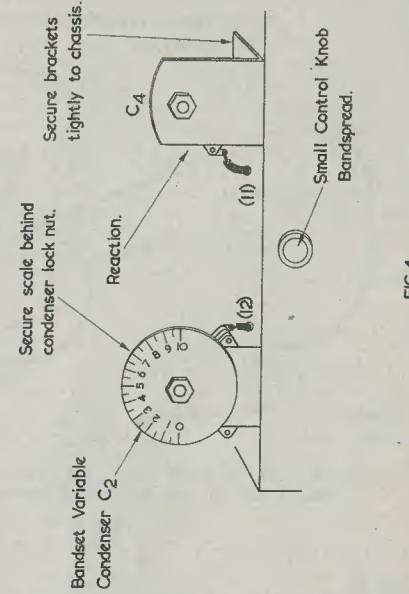


FIG. 4

point 10 with the moving vanes in full mesh—or maximum capacity.

A lead (13) should be cut to a suitable length and have both ends bared, whereupon one end is soldered to the positive (+) pin of the h.t. battery plug. The other end of this lead should be connected to the junction terminal block as shown. The negative lead (14) from the battery plug, similarly cut and bared, should next be soldered to the appropriate pin of the plug, the other end being soldered to the 3-volt battery positive (+) clip together with the black lead from the receiver. (See Stage 1, step 4.)

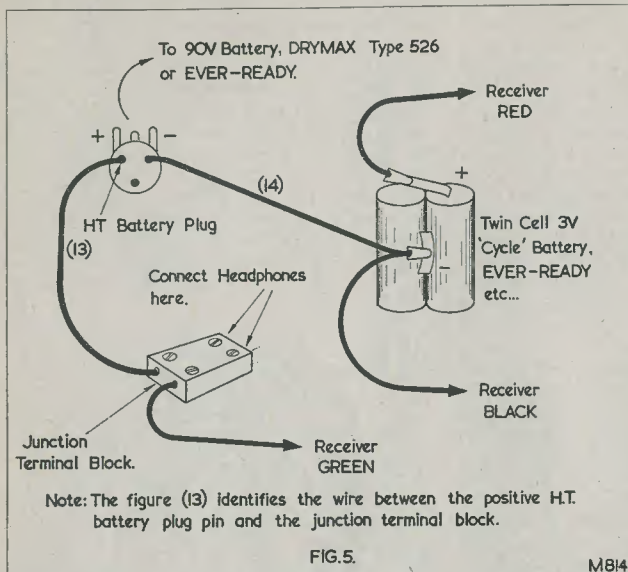



FIG. 5.

M814

Stage 5

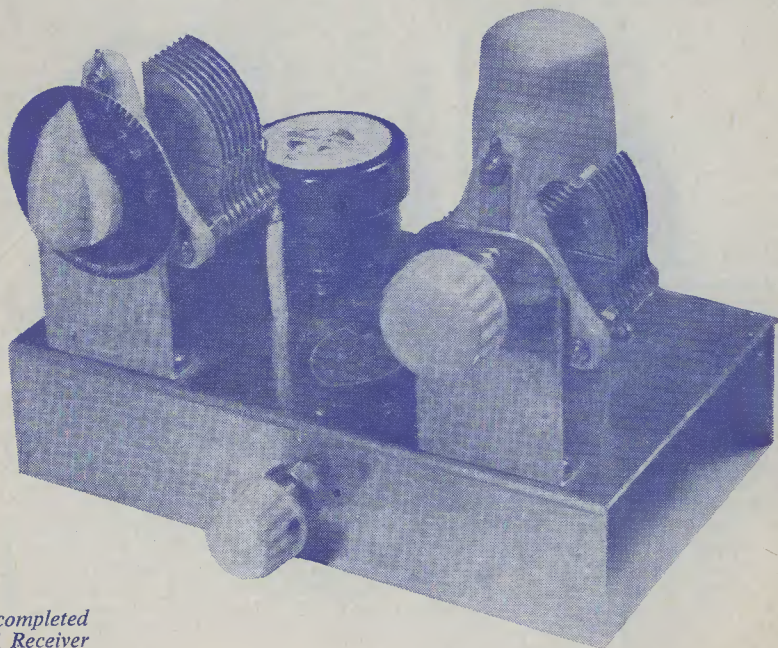(12) The h.t. battery plug should now be connected into circuit as shown in Fig. 5.

Stage 2, step 5), should finally be soldered to the 3-volt battery positive (+) clip. This completes the construction of the receiver.



The completed 100/A Receiver

Testing and Operating the Receiver

Connect the aerial and earth to the receiver, the former being connected to the receiver yellow lead. The aerial required with this receiver is not critical, and any length from 100 feet down to a few feet strung around the room will suffice. A short outdoor vertical aerial, some six to ten feet in length, would be ideal for testing purposes. The earth connection should preferably be made to a copper rod buried in moist earth and kept in a damp condition. An alternative earth connection may be provided by connection to a lead cold water pipe carrying the main water supply. Make the earth connection, at the receiver end, to any part of the metal chassis or the l.t. negative (-)

direction until it is just slightly inside the "click" position. (In this latter position the receiver is, in fact, oscillating.) Next, slowly rotate the bandset control throughout points 3 to 6, whereupon signals—either speech, music or morse—should be heard. To adjust for maximum gain on the signal required rotate the bandspread control slowly until the peak signal position is attained. This can now be further boosted by carefully adjusting the reaction control just off the point of oscillation. A little practice here will soon make the beginner conversant with the technique of Short wave tuning. To receive morse signals, the receiver should be slightly advanced into oscillation.

The various coils should now be inserted

Table I

Frequency Mc/s	Bandset	Band	Metres
Coil No. 1			
30-28	0 to 0.5	Amateur	10
25.5-26	2	Broadcast	11
21.75	5.5	Broadcast	13
21.5	6	Amateur	15
17.5	10	Broadcast	16
Coil No. 2			
15	0 to 1	Broadcast	19
14	1 to 1.5	Amateur	20
12	3	Broadcast	25
9.5	5.5	Broadcast	31
7.5	10	Broadcast	40
Coil No. 3			
7.3-7	0 to 1	Broadcast/Amateur	40
6.2-5.95	2	Broadcast	49
5.05-4.75	4	Broadcast	60
4-3.5	8	Amateur	80
3	10	Broadcast/Commercial	100

connection of the 3-volt battery with the aid of a crocodile clip.

Fit the negative (-) battery clip to the 3-volt battery. Do not fit the positive (+) battery clip yet. Insert the h.t. battery plug into the 90-volt h.t. battery. Insert the valve into the valveholder and coil No. 2 into the coilholder for the initial test.

Rotate the reaction control so that all the rotor vanes are out of mesh and set the bandset dial to read between 4 and 5 degrees. Next, connect the positive (+) clip to the 3-volt battery—the receiver is now switched on. (NOTE: The positive clip must be removed when the receiver is not in use—otherwise the batteries will very soon require renewing!)


Rotate the reaction control clockwise until a "click" is heard in the headphones. Now, bring this control back in an anti-clockwise

into the coilholder and the various bands explored. Generally speaking, it will be found that daylight periods are the best times for operating over the higher frequencies whilst darkness favours the lower frequencies. Morse signals can be tuned to the desired pitch for maximum readability by setting the reaction condenser in the oscillating position and then rotating the bandspread condenser until the required pitch is obtained.

This little receiver will be found ideal for those who aspire to the ownership of their very own first Short wave set—built entirely by their own hands.

Circuit

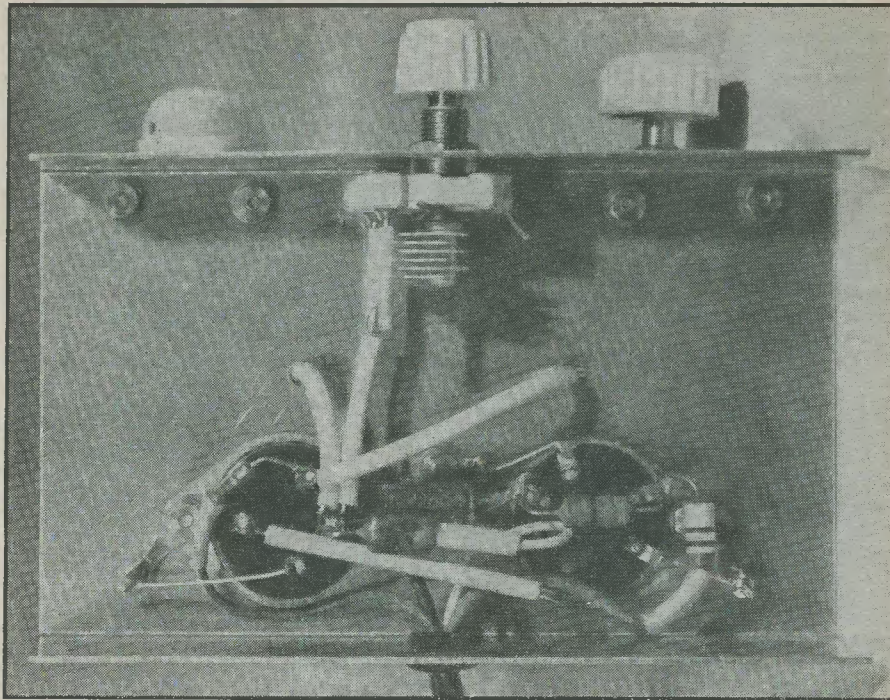This is shown in Fig. 6 and it will be seen that it represents an extremely simple design ideally suited to the beginner. The minimum components are used consistent with a



Under chassis view of the 100/A Receiver clearly showing the component layout

satisfactory performance over the Short wave ranges covered by the three coils, a further advantage being, of course, that the receiver is comparatively inexpensive.

The coil and valveholder tags are numbered, these being referred to in the text. It is unusual to present a circuit diagram at the end of a technical article and it has been done, in this instance, so that beginners can—with the aid of the preceding practical diagrams—construct the receiver without worrying about the theoretical circuit.

For those who care to do so, the theoretical symbols and wiring may be “filled in” as the wiring and soldering operations, in conformity with the textual instructions, proceed—using a ball-point pen for the purpose. In this manner, the beginner will learn the relationship between circuit representation and actual practical construction.

The circuit is designed around the Mazda HL23 valve used as a high gain detector. This valve has a 2 volt filament and offers many advantages in such a circuit. With a low filament drain, some 50mA (milliamps), it allows the choice of either 3-volt dry


battery or 2-volt accumulator operation. The 3-volt dry battery is both cheap and easily obtainable, giving a considerable length of service without the need to replace.

It should be noted that the 20Ω filament resistor R₃ should always be in circuit when operating the receiver from a 3-volt dry battery. If operation from a 2-volt accumulator is temporarily required, R₃ should be short-circuited, i.e. the resistor should be “bridged” or bypassed with a short length of p.v.c. covered wire. Where, of course, permanent operation from a 2-volt accumulator is envisaged, R₃ should be omitted from the circuit.

As was mentioned above, the receiver is switched off by removing the positive battery clip. When this clip is removed, the filament of the valve does not emit electrons and there is no current drain from the h.t. battery. The latter may, therefore, remain permanently connected.

The circuit is that of a simple leaky grid detector incorporating three plug-in type coils. The aerial is fed to the grid winding of whichever coil happens to be plugged into

circuit via the condenser C₁, the variable condensers C₂ and C₃ being the bandset and bandspread tuning controls respectively. The grid condenser C₅ and the grid resistor R₁ have values chosen to provide a time constant which will, together with the other circuit values, produce reaction which is free from backlash. This is of great importance if maximum sensitivity is to be obtained from the receiver. Reaction is obtained by positive feedback, energy being fed back, via the anode winding, to the grid winding of the coil. The amount of feedback is controlled by the reaction condenser C₄. R₂ prevents the radio frequencies at the anode from reaching the headphones.

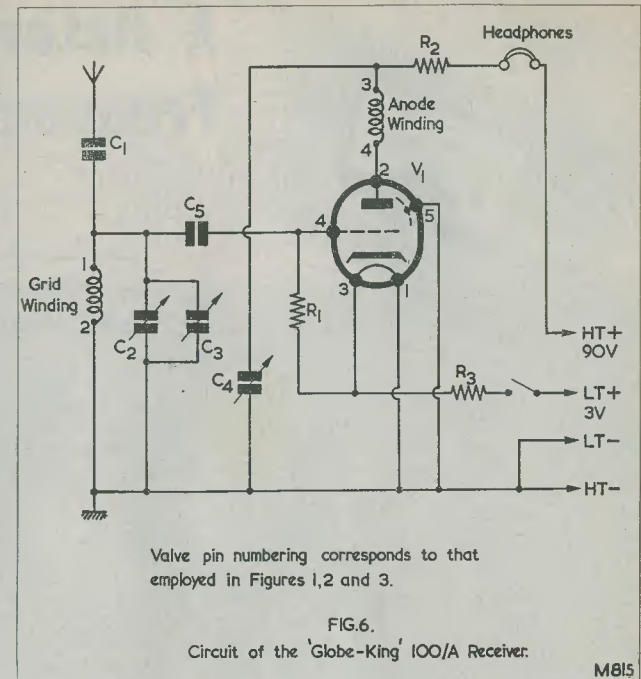

Components List

Resistors

- R₁ 3.3MΩ ¼ watt
- R₂ 1kΩ ¼ watt
- R₃ 20Ω ¼ watt

Valve

- V₁ Mazda HL23

Coils

- Set of 3 (Johnsons Radio) 10–100 metres.
- Additional coil 80–180 metres also available.

Condensers


- C₁ 5pF silver mica
- C₂ 140pF variable (Johnsons Radio)
- C₃ 10pF variable (Johnsons Radio)
- C₄ 140pF variable (Johnsons Radio)
- C₅ 0.0002μF mica

Miscellaneous

- Panel, chassis, mounting brackets, knobs, etc. (Johnsons Radio)

RADIO AMATEURS EXAMINATION AND MORSE CLASSES

Grafton Radio Society announce that they have again made arrangements with Holloway L.C.C. Evening Institutes for official courses in the Radio Amateurs Examination and Morse (both for beginners) to be held this winter at the Montem School, Hornsey Road, Holloway, London, N 7. The classes will meet on Mondays, with repeat lectures on Tuesdays and Wednesdays, commencing Monday, 26th September, for the R.A.E. course at 7.0–9.0 p.m. (Instructors: S. H. Iles (G3BWQ) and P. F. Bernal (G3KQZ), followed by the Morse at 9.0–10.0 p.m. Instructors: L. Barber and A. Ralph). The fee for either course is 20s., or 22s. 6d. for the two. Enrolment will be at the school any evening (7.30–9.0 p.m.) Monday to Friday during the week 19th–23rd September, but application in the first instance should be made to the Hon. Secretary of the Grafton Radio Society: A. W. H. Wennell (G2CJN), 145 Uxendon Hill, Wembley Park, Middlesex, so that a place may be assured.

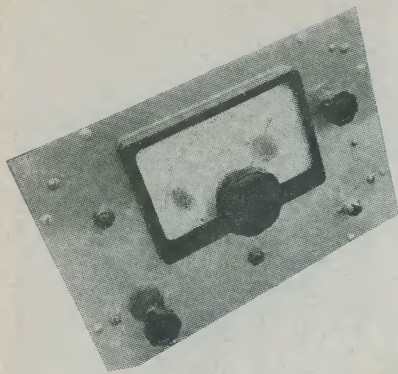

A Heterodyne Frequency Meter

By DAVID NOBLE, G3MAW
and DAVID M. PRATT, G3KEP

IT IS OFTEN DESIRABLE TO BE ABLE TO measure the frequency of a receiver accurately, and radio amateurs are required, by the terms of their licence, to be able to measure the frequency upon which they are operating. For accurate measurement of frequency, a simple interpolation frequency meter will give results to a very close tolerance provided that the crystal used in the unit is of sufficient accuracy. This type of frequency meter is used in conjunction with a receiver, and if it is required to measure the frequency of a transmitter, then the transmission is monitored on the receiver, and the receiver frequency measured.


A 100 kc/s crystal will produce harmonics every 100 kc/s, and these can be used to measure frequencies up to and over 30 Mc/s. However, this will not give intermediate

frequency range, and by the expense of a little more with respect to valves—two pentodes instead of a twin-triode—a continuous coverage interpolation type of frequency meter can be provided.

Circuit

The first valve (V_1) operates as a Pierce crystal oscillator. The condenser C_1 (40pF) is used to adjust the crystal to exactly 100 kc/s. This may be checked by listening to the Light Programme on 200 kc/s, and tuning the condenser for exactly zero beat. An "S-meter" or "magic eye" are useful if the receiver is so fitted, a beat period of several seconds can then be observed.

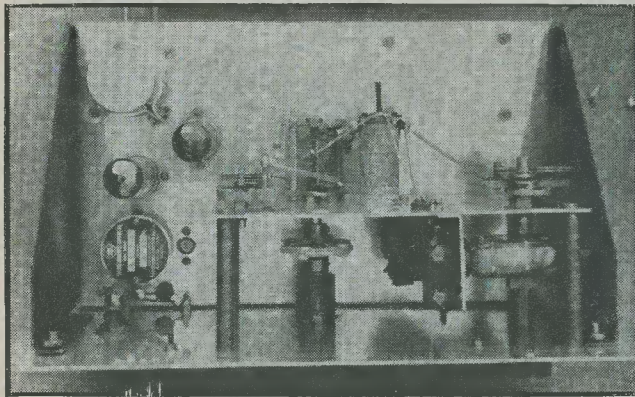V_3 is the variable interpolation oscillator. The main tuning condenser is C_{15} which is arranged to tune over a range of 100 kc/s.



Plan view of the frequency meter showing the constructional method adopted with the variable oscillator section. Note the vertical panel mounted to the front panel by means of the four brass pillars. The crystal oscillator section is shown to the left of the vertical sub-chassis

frequencies, nor, for amateur purposes, an accurate measurement of the band edges of the 40, 20 and 15 metre bands (7.15, 14.35, 21.45 Mc/s). While all the band edges could be provided by a following multivibrator on 10 kc/s, this does not give a continuous

The actual frequency of operation of the oscillator is not critical. In the prototype, with the coil data given, the oscillator operated from 3.9 to 4 Mc/s. C_{13} is a fine trimmer for initially setting up the oscillator, and C_{14} is a variable condenser of very low


capacity. This condenser has its spindle protruding through the front panel, its purpose being to set up the oscillator before use.

The two outputs from the oscillators are fed through 20pF condensers to the grid of V_2 . The valve operates as a mixer, and r.f. output is fed to the coaxial socket via an isolating condenser, C_8 . This provides an output of high harmonic content, and is coupled to the receiver with which the frequency meter is to be operated.*

Setting Up

A headphone jack is provided for setting up the equipment. As the dial is calibrated 0 to 100 kc/s, it will be necessary to ensure

* It should be noted that, at frequencies above 4 Mc/s, advancing the interpolating oscillator tuning condenser causes both a rising frequency and following frequency to appear within the 100 kc/s range under consideration. This should cause little difficulty in practice since it is almost invariably possible to use common sense and knowledge of tuning condenser direction against capacity to differentiate between the two signals.—EDITOR.

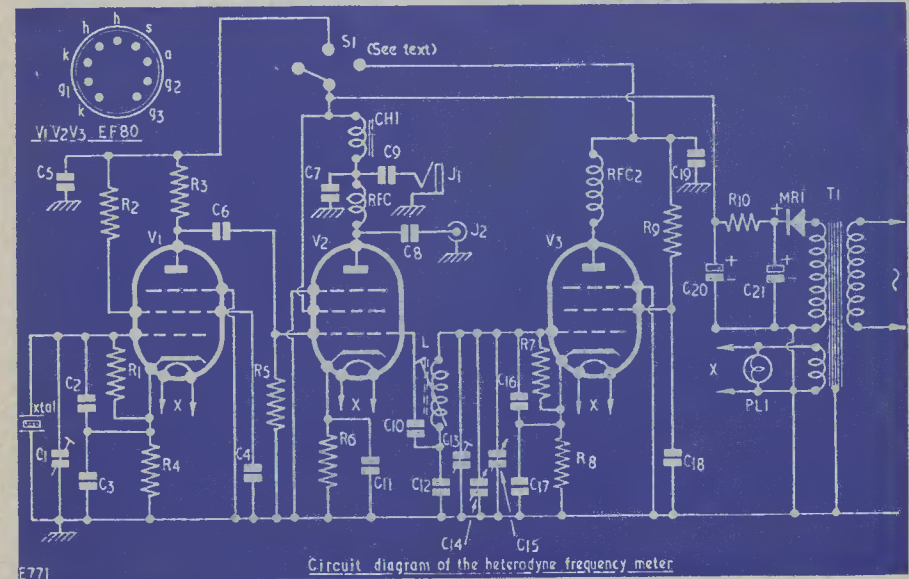

Circuit diagram of the heterodyne frequency meter

Components List

Resistors

- R_1 470k Ω $\frac{1}{2}$ W
- R_2 100k Ω $\frac{1}{2}$ W
- R_3 22k Ω $\frac{1}{2}$ W
- R_4 10k Ω $\frac{1}{2}$ W
- R_5, R_7 68k Ω $\frac{1}{2}$ W
- R_6 220 Ω $\frac{1}{2}$ W
- R_8 8.2k Ω $\frac{1}{2}$ W
- R_9 33k Ω $\frac{1}{2}$ W
- R_{10} 1k Ω 10W wire-wound

Condensers

- C_1 40pF air-spaced preset trimmer
- C_2 100pF silvered mica
- C_3, C_{12} 1,000pF silvered mica
- C_4, C_5, C_{19} 0.01 μ F 400V paper
- C_6, C_{10} 20pF silvered mica
- C_7, C_{11}, C_{18} 0.002 μ F 350V paper
- C_8 470pF silvered mica
- C_9 0.1 μ F 400V paper
- C_{13} 20pF preset trimmer
- C_{14} 8pF variable


- C_{15} 25pF variable
- C_{16}, C_{17} 390pF silvered mica
- C_{20} 32 μ F 350V electrolytic
- C_{21} 16 μ F 500V electrolytic

Miscellaneous

- RFC $_1, RFC_2$ 2.5mH r.f. choke
- Ch $_1$ L.F. choke
- L 25 turns, 24 s.w.g. enamelled copper wire, close spaced on $\frac{3}{4}$ in former with dust iron core
- V_1, V_2, V_3 EF80
- MR $_1$ 250V, 40mA metal rectifier
- S $_1$ 3 position progressively shorting wafer switch
- T $_1$ 250V, 40mA and 6.3V, 1A mains transformer
- PL $_1$ 6.5V, 60mA pilot bulb
- J $_1$ Headphone jack
- J $_2$ Coaxial output socket
- Xtal 100 kc/s quartz crystal

that the position of the condenser C_{15} , when its pointer is at 0 and 100 kc/s, produces a zero beat. This requirement is necessitated, of course, so that the variable oscillator will

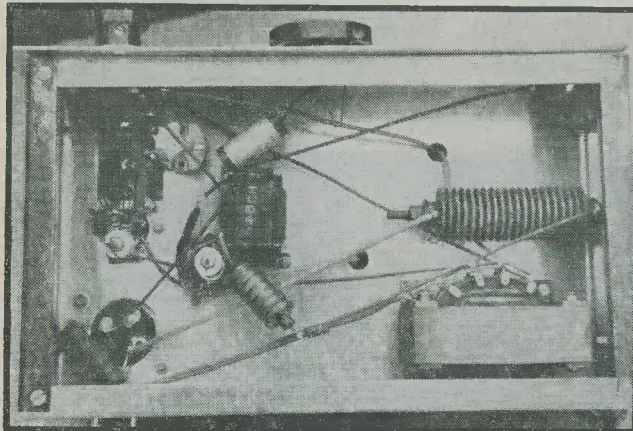approximately 200 volts, and l.t. of 6.3 volts a.c. The h.t. switch is of the progressively shorting type. Thus, in the first position neither of the oscillators are operat-



Under-chassis view of the frequency meter showing the position of the power supply and other components

be at zero beat with the harmonics from the crystal oscillator at these two positions. C_{14} is provided, therefore, to compensate for any drift in the instrument after it has been on for a considerable period.

Power Supply and Switching

An integral power supply employing a simple half-wave metal rectifier circuit is used. This provides an h.t. voltage of

ing; in the second position, only the crystal oscillator is working, and therefore the 100 kc/s harmonics will be detected; lastly in the third position, both oscillators are operating.

The unit was built on a chassis 10 x 6 x 2in, and fitted into a metal cabinet of proportionate dimensions. Screening is desirable with this unit in order to prevent any unwanted radiation and for that reason it is recommended that it be built into a metal case.

THE PHONE-GUARD by R. M. SUMMERS

The Phone-Guard is a device which gives visual warning of the ringing of a telephone bell. Its sensitive circuit is capable of responding also to any other sound of reasonable intensity

A DEVICE WHICH GIVES VISUAL INDICATION when a bell is rung can be extremely useful in a household wherein any member happens to be hard of hearing or where it is occasionally necessary to occupy a room in which the bell cannot normally be heard. The Phone-Guard has been developed to meet this situation, and it employs an inexpensive amplifier and relay energising circuit which causes the actuation of the relay contacts whenever the associated microphone picks up the sound of the bell. With the application described in this article the relay causes a lamp, or lamps, to be illuminated. The relay contacts can, of course,

cause any other electrical operation to take place, should this be desired, on the ringing of the bell. The device is sensitive; and it may be employed to give visual warning of the presence of sounds other than that given by a bell. It would, for instance, be perfectly suitable for use as a baby alarm, the crying of the baby causing the warning lamps to light. Other applications may readily suggest themselves to the reader.

The component values employed in the relay energising circuit of the Phone-Guard have been chosen to give optimum performance with G.P.O. bells. They will also prove adequate if the unit is employed to

detect alternative sounds, although small improvements in performance may result if time constants are adjusted slightly. This point is discussed in the article.

The Phone-Guard Circuit

The circuit of the Phone-Guard appears in Fig. 1. As may be seen few components are required. The two double triodes used are readily available, as are, also, the microphone transformer and relay. The only remaining components are seven fixed resistors, one potentiometer and four condensers, none of which need be a close tolerance type.

Examining the circuit in more detail it will be seen that the microphone couples to the grid of $V_{1(a)}$ via the step-up microphone transformer. This transformer has a ratio of 100:1 and R_1 , connected across its secondary, causes a reflected impedance of 3.3Ω to appear across the primary terminals. This input impedance is an adequate match for the loudspeaker which is employed as a microphone. The amplified signal on the anode of $V_{1(a)}$ is fed, via C_2 , to the sensitivity control R_5 . C_2 and R_5 form a simple high-pass filter, and help to make the circuit more responsive to transients than to sounds in the lower frequency range. This filter also

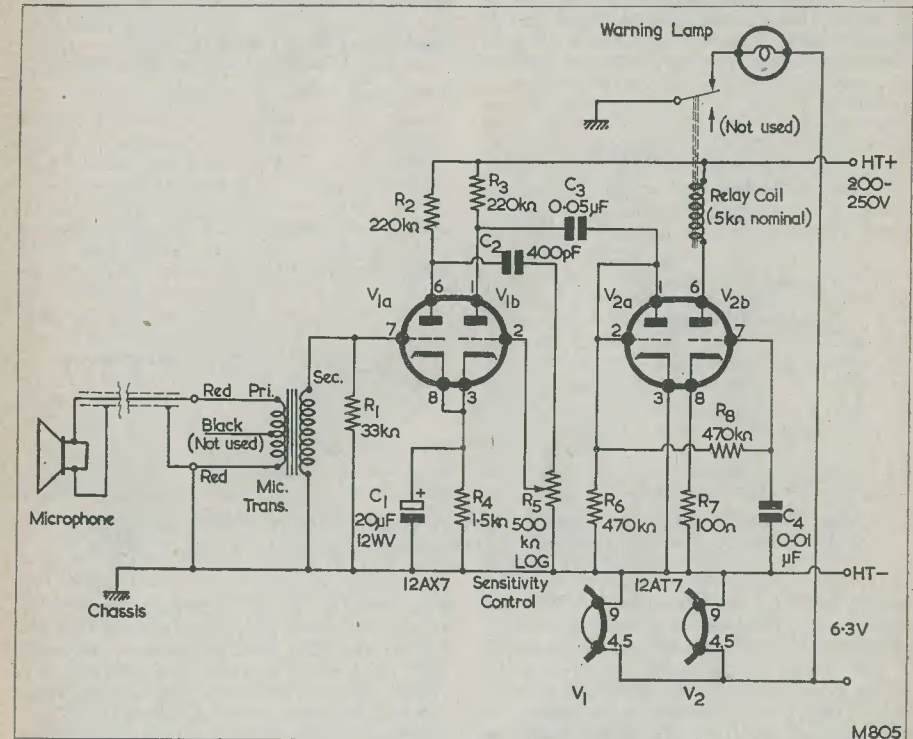


Fig. 1. The circuit of the Phone-Guard

The circuit functions by reason of the fact that sound picked up by a microphone (actually, a small loudspeaker) is amplified by $V_{1(a)}$, detected by $V_{2(a)}$ and fed, as a negative d.c. voltage, to the grid of $V_{2(b)}$. The relay is connected in the anode circuit of $V_{2(b)}$ and it de-energises when the negative voltage is applied to $V_{2(b)}$ grid, thereby causing the warning lamps, or whatever other external circuit is employed, to be switched on.

helps to reduce undesirable effects which may be caused by hum pick-up in the grid circuit of $V_{1(a)}$. R_5 , the sensitivity control, is connected in the grid circuit of $V_{1(b)}$ rather than in that of $V_{1(a)}$ as this position reduces the risk of random hum pick-up in the chassis wiring and, therefore, eases component layout requirements. $V_{1(b)}$ amplifies the signal passed to its grid, the amplified signal appearing across R_3 . Due, partly, to the presence of the high-pass filter C_2 and R_5 , it

is possible to dispense with separate cathode decoupling components for $V_{1(a)}$ and $V_{1(b)}$. Both cathodes are decoupled by the single bypass condenser C_1 , and their bias voltages are developed across the common bias resistor R_4 .

The circuit around V_1 provides an a.f. amplifier offering the very high overall gain of approximately 3,000 times, or 70dB. This high degree of gain offers a significant contribution to the sensitivity of the Phone-Guard.

The amplified signal on the anode of $V_{1(b)}$ is next fed, via condenser C_3 , to $V_{2(a)}$. $V_{2(a)}$ has its anode and grid strapped and functions as a shunt detector diode, the detected voltage appearing across R_6 . In the absence of signal, the voltage on the upper end of R_6 is slightly negative to chassis (due to contact potential in $V_{2(a)}$). When a signal is

The choice of valve employed in the V_2 position adds to the sensitivity of the device, in so far that the type specified has a short grid base. $V_{2(b)}$ will cut off completely for negative grid potentials around five to six volts.

The total h.t. current consumed by the Phone-Guard is of the order of 10mA only, this dropping to 1 to 2mA in the presence of a high-amplitude signal. Heater consumption is 6.3 volts at 0.6 amps (or 12.6 volts at 0.3 amps if the heaters are connected for 12.6 volt operation). These power requirements are low, and enable the Phone-Guard to be continually switched on with negligible consumption from the mains supply.

Operation with a Telephone Bell

As was mentioned earlier, the component

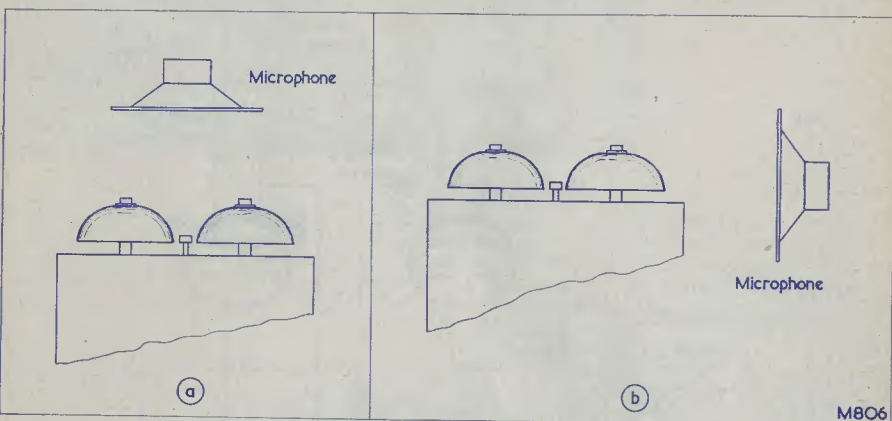


Fig. 2. The intensity of continued ringing from a telephone bell after the striker has come to rest is less if the microphone is mounted above the gongs, as in (a), than if it is mounted at their side, as in (b)

passed to $V_{2(a)}$ the upper end of R_6 goes negative to chassis by a potential which is proportional to the amplitude of the signal.

The voltage on the upper end of R_6 is fed to the grid of $V_{2(b)}$ by the low-pass filter R_8 , C_4 . These two components integrate the negative voltage from R_6 (which varies at the frequency of the amplified signal) and apply a relatively steady voltage to $V_{2(b)}$ grid. The cathode of $V_{2(b)}$ is biased by R_7 , with the result that, in the absence of a signal from V_1 , $V_{2(b)}$ draws (for an h.t. voltage of 225) approximately 7mA anode current. In the presence of a signal having the requisite amplitude, $V_{2(b)}$ anode current is reduced to a low value or becomes cut off altogether. In consequence of this wide variation in current, reliable and positive de-energising of the relay takes place when the actuating sound is picked up by the Phone-Guard microphone.

values around V_2 are especially intended for operation with a telephone bell. In order to see why they were chosen it is necessary first to quickly examine the methods employed by the G.P.O. for transmitting ringing currents to subscribers' telephones.

Ringing currents fed along subscribers' lines may come from manual exchanges or from automatic exchanges. So far as manual exchanges are concerned there are several methods of obtaining the ringing current. It may, for instance, be generated by a cranked ringing generator, whereupon the frequency of the ringing current and the length of time this current is applied to the lines are variable. Alternatively, the ringing current may be generated in the exchange at a nominal frequency of 16.66 c/s, this current being switched by a key. Here it is only the length of time the bell rings which is variable. A third alternative is where ringing is con-

trolled by an automatic exchange elsewhere, through which an incoming call has been routed—the incoming ringing current being “passed on”, as it were, by the manual switchboard operator. In this case, the ringing current and ringing periods will be the same as are given by automatic exchanges.

The larger, and some small, automatic exchanges provide interruption periods which result in the familiar “burr-burr . . . burr-burr” ringing cycle. The ringing current frequency here is again a nominal 16.66 c/s and the current is interrupted as follows: 0.4 sec. on, 0.2 sec. off, 0.4 sec. on and 2 sec. off. Small automatic exchanges may have ringing current generators which provide approximately 16 c/s, and in which the ringing current is interrupted at nominal periods of 0.75 sec. on and 0.75 sec. off.

It was decided, after reviewing these various ringing currents and ringing periods, that it would be advisable to design the warning device such that it was capable of operating with a sound consisting of approximately 32 transient pulses per second. (A 16 c/s ringing current causes the bell armature to strike its associated gongs 32 times per second.) Ideally, the circuit should be sufficiently quick-acting to enable the visual warning lamp to “follow” the ringing cycle given by the larger automatic exchanges. The device should certainly be sufficiently quick-acting to be able to “follow” the 0.75 sec. on, 0.75 sec. off, ringing cycle offered by the smaller automatic exchanges.

The time constant offered by C_3 , R_6 in the detector circuit of the Phone-Guard is approximately 0.025 sec. and it was felt that this would enable a high detected potential to be obtained for an input signal of 32 transient pulses per second without excessive discharge time when the ringing ceased. The time constant of R_8 and C_4 , at 0.05 sec. approximately, is shorter than that of C_3 and R_6 . It was found, in practice, that a short time constant here speeded relay operation significantly, but that care had to be taken to prevent it being so short as to allow relay chatter to occur. The values specified in Fig. 1 for R_6 and C_4 enable quick relay action to be realised without the risk of chatter.

On checking the unit in practice a difficulty arose which had not been foreseen. This was due to the fact that the telephone bell gongs continued to emit a relatively high amplitude ringing sound after movement of the striking armature had ceased. Because of this the negative voltage on the grid of $V_{2(b)}$ did not immediately drop to chassis potential at the end of a ringing period, but tended to decay at a rate proportional to the decay in actual sound.

As would be expected, the ringing of a bell gong after being struck is at its greatest strength along its sides, and is at its weakest at its top. In consequence, it was found that continued ringing of the bells after striking caused least trouble when the Phone-Guard microphone was positioned above them, as in Fig. 2 (a), than when it was positioned at their side, as in Fig. 2 (b). Unfortunately, many telephone installations have completely enclosed bells, and it is difficult to find a position for the microphone which causes minimum ringing pick-up.

Practical results achieved with various telephone installations were extremely good. When the microphone could be mounted as shown in Fig. 2 (a) it was found possible to have the relay operate in sympathy with the ringing period given by larger automatic exchanges without too critical an adjustment in the sensitivity control, R_5 . If sensitivity were advanced beyond the condition where the warning lamp “followed” the ringing cycle, it remained illuminated during the 0.2 sec. period, but extinguished during the 2 sec. period. The sensitivity setting required for this mode of operation was markedly broad and non-critical.

In cases where the bell was completely enclosed it was found possible to make the relay follow the ringing period, but the requisite setting of R_5 was critical. However, no difficulty was experienced in obtaining a reliable warning lamp cycle in which it remained illuminated during the 0.2 sec. period and became extinguished during the 2 sec. period.

In view of these findings it is felt that the setting of the sensitivity control (and hence, the mode of operation) would best be left to the choice of the person using the device. It should be remembered that it is possible to advance sensitivity such that, even with microphone positioning such as that of Fig. 2 (a), automatic exchange ringing causes the warning lamp to be continually illuminated. The reason for the continual illumination is that the amplified signal voltages applied to V_2 during the ringing period became so high at this sensitivity setting that the associated condensers cannot discharge during the 2 sec. “off” period. This method of operation has the advantage that the Phone-Guard is operating with considerable sensitivity “in hand” and the disadvantage that there is no continual switching on and off of the lamp to attract attention.

All the above tests were carried out on telephones connected to a large automatic exchange. There is little doubt, with small automatic exchanges offering the 0.75 sec. on and 0.75 sec. off ringing periods, that the setting of the sensitivity control which causes the relay to “follow” the ringing period

should be much less critical, as the "off" period is not as short as 0.2 secs. Here again, of course, the sensitivity control can be advanced such that the lamp is illuminated continually. With manual exchanges, where the length of the ringing period is variable, the sensitivity control merely needs to be set to a position which causes the relay to operate reliably when the bell rings.

Fitting the Microphone

As has already been mentioned, the microphone employed with the Phone-Guard consists of a loudspeaker. A small unit, 4in or less, should be used here. The speaker should have a voice coil impedance of 3Ω.

The speaker, functioning as a microphone,

for the screened cable would be provided by television coaxial cable. In some instances, however, it might be considered cheaper or more convenient to make the microphone connection via unscreened twin cable. This type of cable can be used provided that hum pick-up is not excessive; it should, for this reason, be kept well away from unscreened mains wiring. When unscreened twin cable is employed the input connection to the Phone-Guard amplifier should be balanced about chassis in the manner illustrated in Fig. 3. It may also be necessary to connect the amplifier chassis to earth. (An earth connection is not needed when the screened cable is employed.) Checks for hum pick-up level with unscreened microphone wiring may

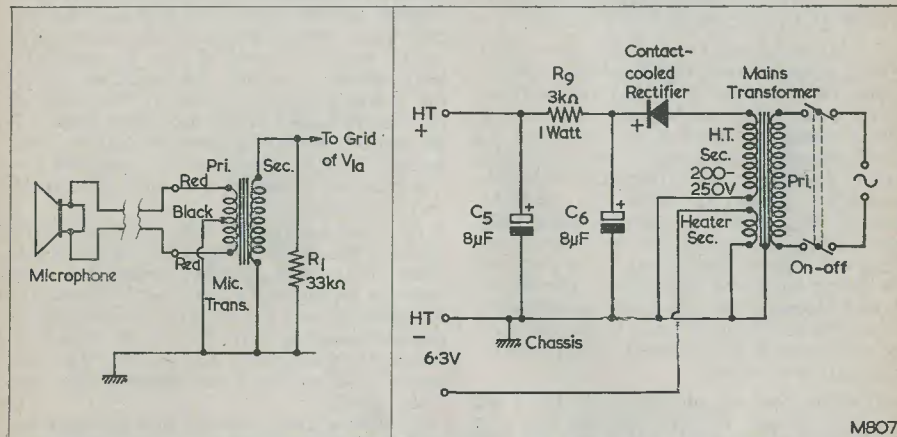


Fig. 3 (left). An alternative input circuit which may be used when the microphone is coupled to the amplifier via unscreened twin cable. With this method of connection it may be necessary to earth the chassis in order to reduce hum pick-up
Fig. 4 (right). A suitable power unit for the Phone-Guard. H.T. and heater current consumption are discussed in the text

should be mounted fairly close to the telephone bell. This ensures the existence of a high ratio between the sound level of the bell and the sound level of other noises in the household, and thereby guards against accidental operation of the relay for noises other than that from the bell. It is desirable to provide the speaker with a simple resilient mounting with the aid of polyurethane foam or any similar material, in order to prevent the direct transmission to it of sounds such as the slamming of doors, etc. Polyurethane foam may also be fitted behind the speaker in order to prevent sound pick-up on the back of the cone.

The circuit of Fig. 1 shows the microphone connected to the Phone-Guard amplifier via screened cable, such cable being employed to obviate hum pick-up. An excellent choice

be made by temporarily connecting a pair of high impedance phones across R_6 and listening to the amplified signal from V_1 .

Power Supplies

The power requirements of the Phone-Guard are low, and they may be adequately met with a power unit circuit of the type shown in Fig. 4. A contact cooled h.t. rectifier is illustrated in the diagram, but a valve or metal rectifier may be readily employed in its place, should this be desired. There is no necessity to regulate the h.t. output of the power unit. It should be remembered that the heater winding has to provide current for the warning lamp, or lamps, as well as for the heaters of the two double triodes.

It will be noted that the mains transformer

has a separate single-wave h.t. winding. A transformer of this type provides complete isolation from the mains, and its cost is only slightly higher than that of a conventional heater transformer. Isolation from the mains is essential in a device of this type, since it connects into wiring which is routed around the house.

If a power unit having the circuit of Fig. 4 is fitted on a separate chassis to that on which the amplifier and relay energising circuit are mounted, the interconnecting

The Relay

The relay specified for the Phone-Guard is a lightweight type having a quick action. The current drawn through its coil by $V_2(b)$ in the absence of signal is comfortably in excess of the minimum required for dependable energising and so its operation becomes extremely reliable. The relay should be set up such that, when energised, a gap of some 0.02 to 0.03in remains between the underside of the armature and the top of the core. This setting is not at all critical and its main

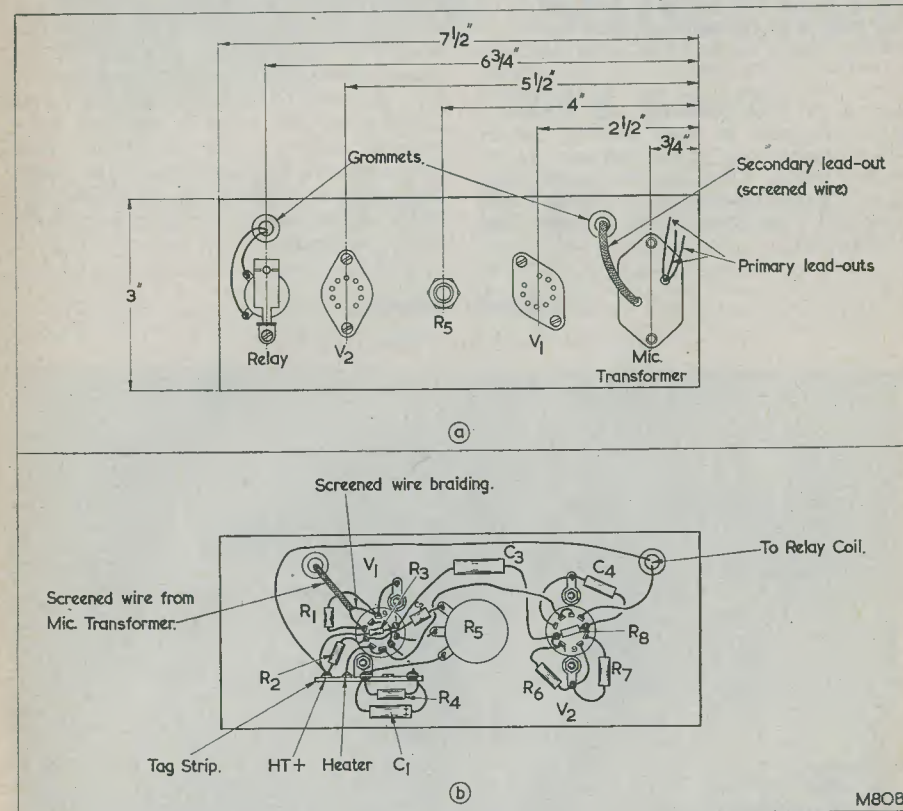


Fig. 5 (a) (above). Top view of chassis, showing suggested layout of components.
(b) (below). Below-chassis view of components and wiring. The warning lamp wiring and microphone input connections are completed above chassis and are not shown here

leads should not be longer than 2 ft. If longer interconnecting leads are employed the smoothing condenser, C_5 , should be fitted to the amplifier and relay energising circuit chassis, instead of on the power unit chassis. C_5 decouples the anode circuits of V_1 and V_2 as well as smoothing the rectified h.t., and long leads to this condenser may result in instability.

purpose is to help in providing quick de-energising when $V_2(b)$ anode current drops.

The moving contact of the relay is common to its armature and to its mounting bolt. If the relay switching circuit is wired up as shown in Fig. 1, securing the relay to the chassis automatically completes the circuit to the moving contact.

Other Applications

It is possible that the Phone-Guard may be employed for applications other than for visual indication of the ringing of a telephone bell. Where a sound other than from a bell actuates the device it may be found desirable to alter the values of C_3 and C_4 .

As they stand, C_3 and C_4 are quite satisfactory if it is intended to operate the device by speech. If the sound which operates the device is of a high pitched nature it should be possible to reduce the value of C_3 without losing sensitivity. Increasing the value of C_3 will increase the time taken for the relay to energise after the sound has ceased, and such a feature may be desirable in some applications. The value of C_4 may be reduced, if desired, to speed operation, but too low a value will result in relay chatter. Chatter will normally occur at the frequency of the applied sound. Large increases in the value of C_4 are not recommended, as these would merely slow up de-energising and energising of the relay.

Construction

Due to the small number of components involved, construction of the Phone-Guard is simple and quick.

The prototype was built on a chassis measuring 3in by 7½in by 1in deep and employed the component layout illustrated in Figs. 5 (a) and (b). Fig. 5 (b) also illustrates the wiring of the under-chassis components. This diagram does not include the power unit. In the writer's case the power unit happened to be mounted on a separate small chassis, and the reader may follow this practice if he so desires. Alternatively the chassis shown in Fig. 5 may be extended at the relay end to accommodate the mains transformers and other power unit components. Such a layout will provide more than adequate spacing between the mains transformer and the microphone transformer, and eradicate the risk of induced hum in the latter component.

List of Major Components

Amplifier and Relay Chassis (Fig. 1)

Resistors

(All fixed resistors 20% ¼W)

- R₁ 33kΩ
- R₂ 220kΩ
- R₃ 220kΩ
- R₄ 1.5kΩ
- R₅ 500kΩ potentiometer, log track
- R₆ 470kΩ
- R₇ 100Ω
- R₈ 470kΩ

Condensers

- C₁ 20μF, 12 w.v., electrolytic
- C₂ 400pF, 250 w.v., silver-mica
- C₃ 0.05μF, 250 w.v., paper
- C₄ 0.01μF, 250 w.v., paper

Valves

- V₁ 12AX7 (or ECC83)
- V₂ 12AT7 (or ECC81)

Microphone Transformer

Ratio 100:1, shielded, Cat. No. M22, Home Radio (Mitcham) Ltd.

Microphone

3Ω speaker, 4in or less

Relay

Lightweight, heavy-duty, Cat. No. Z70, Home Radio (Mitcham) Ltd.

Warning Lamps

6.3 volts. Quantity and type to suit individual requirements

Power Unit Chassis (Fig. 4)

Resistors

- R₉ 3kΩ 20% 1W

Mains Transformer

As specified in Fig. 4 and text

Switch

- 1 on-off switch

Condensers

- C₅, C₆ 8+8μF 250 w.v., electrolytic


Rectifier

Contact cooled (or equivalent metal or valve component)

BRADFORD TECHNICAL COLLEGE, Central Hall, Bradford 5 (Department of Engineering). A course of lectures in preparation for the City and Guilds of London Institute's Radio Amateurs Examination will be held during the forthcoming session on Wednesday evenings from 7 to 9 p.m. Lecturer: D. M. Pratt, G3KEP. Further information and details of registration, etc., may be obtained from the General Office, Telephone: 25763.

OPENSHAW TECHNICAL COLLEGE (Radio Club), Whitworth Street, Openshaw, Manchester 11. Classes for the R.A.E. examinations, written and Morse, will continue to be held during the 1960/61 evening session.

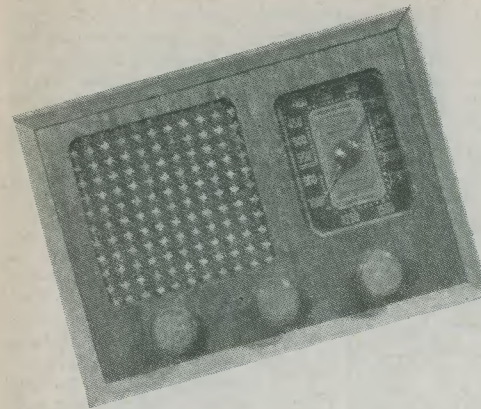The classes are arranged for first year candidates, and also a second year class is available for those who have passed part or all of the R.A.E. requirements, during which constructional work may be carried out, and the equipment tested, checked and calibrated under the college call sign G3NLT.



A Simple


Reflex Superhet

By A. A. Baines

THIS RECEIVER WAS BUILT TO FULFIL A requirement for a "second" mains radio that was capable of being easily transported from room to room and was to be of a small size in order to facilitate its use. Medium and Long wavebands were thought to be desirable and a good acceptable level of performance was essential, but an equally

exceeded expectations.

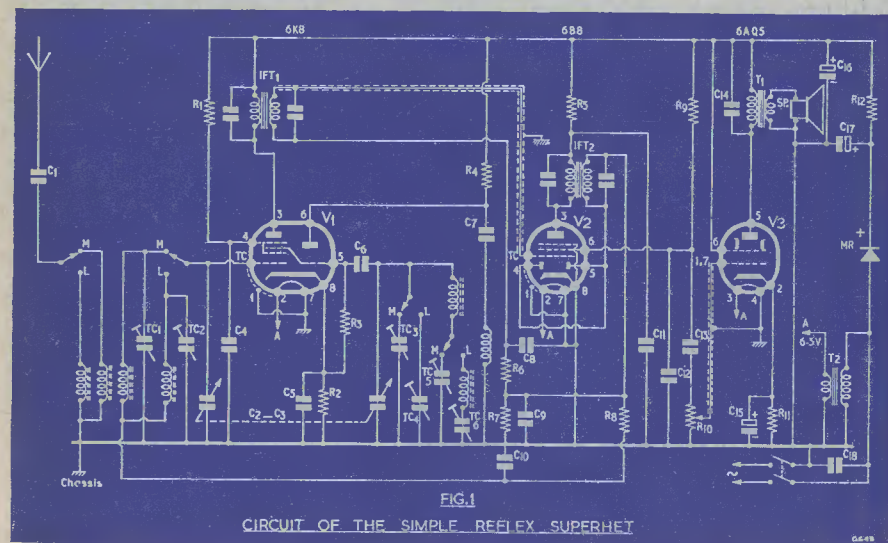Economy has resulted in a receiver using dual range coils, three valves in a reflex circuit, heater transformer, metal rectifier and resistance smoothing. Good surplus components were used where possible and although many components were already available, it is thought that with selective




important requirement was that the receiver had to be inexpensive to build. These requirements naturally mean that some compromises had to be made and quite a good deal of thinking, and searching through the spares box, was undertaken before the final design was completed. The finished article has, however, achieved the above aims quite successfully and its performance has

exceeded expectations. purchasing from advertisers in this magazine the total price of building this receiver, excluding cabinet, should not exceed £5 approximately.

The chassis size is 7¾ x 5in and by specifying metal or GT valves for V₁ and V₂, small i.f. transformers and a 3½in speaker, the internal cabinet size is no more than 7¾ x 5½ x 5¾in. Transportability is further faci-

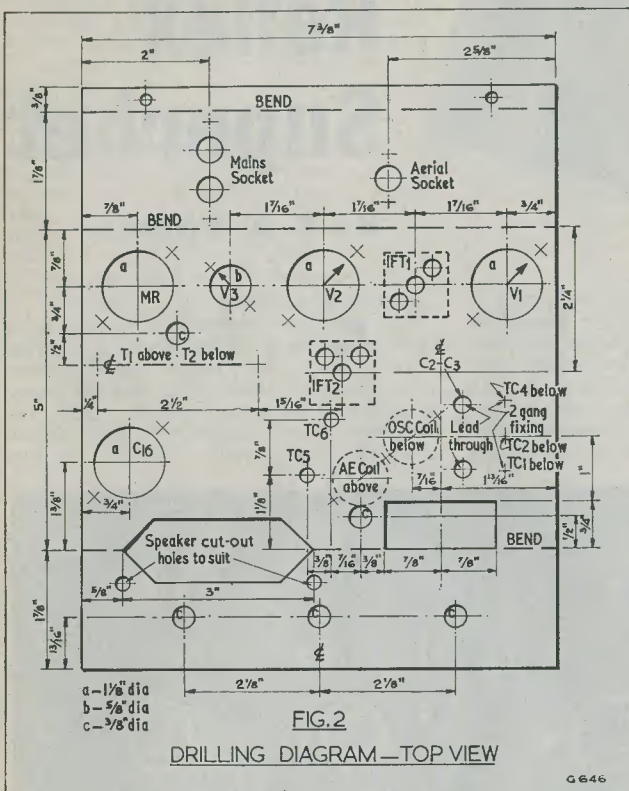tated by the need for a small aerial for all normal purposes; the aerials tried so far ranging from a 5in electrician's screwdriver inserted in the aerial socket to 8 feet of wire wound around the inside of the back of the cabinet. Consideration was given at one



time to the incorporation of a ferrite rod aerial but the idea was rejected solely on economic grounds. The above length of wire around the back of the cabinet has been quite suitable but a ferrite rod aerial and matching oscillator coils could easily be substituted if so desired.

Sensitivity and selectivity are excellent for such a radio; stations being received all around the dial from the Third on 464 metres to the Third on 194 metres, and the West Home Service on 206 metres and Luxembourg, 208 metres, are clearly separated without cross interference, this being no mean feat in the writer's district. Volume is more than ample for all normal purposes.

Circuit

Fig. 1 shows the circuit diagram from which it is seen the selected waveband of the

aerial windings of a dual wave coil is fed to V_1 , a 6K8 frequency changer in a conventional circuit. V_1 is coupled into the i.f. stage through a high "Q" i.f. dust cored transformer, IFT₁. This, and IFT₂, is of a miniature type measuring 2 x 1 x 1in. If the

transformers specified are used, IFT₁ must be removed from its screening can after straightening the lugs at the bottom and a length of p.v.c. flexible connecting wire soldered to the grid terminal of its secondary winding. The flexible wire is then threaded through the hole existing in the top of the can before replacing the transformer windings. This lead is the flying lead to the top cap of V_2 and it was not found to be necessary for it to be screened. Screening of this lead may, however, be desirable with other models built to the present design. The i.f. signals from the frequency changer are fed to a 6B8 double diode pentode valve operating in one instance as a normal pentode i.f. amplifier; in addition, the signals are demodulated by the strapped diodes. The audio voltages are now returned to the grid and amplified, the a.f. output being taken from the screen grid. Further to this, as the 6B8 has semi-variable μ characteristics, a measure of a.g.c. is fed back, both to this valve and to V_1 . A reflex circuit, such as the one described, has a tendency to accentuate any instability that might be present but in practice instability with this stage has never been experienced. A fairly comprehensive r.f. filter and decoupling network was built into the receiver initially to nullify any instability that might arise as a result of a rather cramped layout; but it is suggested that the circuit could be built without the decoupling resistor and condenser, R_5 and C_{11} , at first, incorporating these later only if they appear to be necessary when testing the receiver.

The output of V_2 is passed via C_{13} and R_{10} , through a screened lead to V_3 , C_{13} being as close as possible to R_{10} to minimise any possibilities of hum pick-up; no other

screening was found to be necessary on the original receiver. V_3 is a 6AQ5 and was chosen for its small size, although any similar valve, such as a 6BW6, could be utilised in this position after due regard to the appropriate value of the cathode resistor and valve holder. It should be noted, however, that if an octal based output valve is used, some alterations to the chassis layout may be desirable, the height of the cabinet consequently would have to be increased.

often vary in size from the specified parts. This action, of course, being mainly dictated by financial considerations! Although no miniaturised components, and only easily obtained standard items of small dimensions were utilised, it may be as well to obtain the major and larger parts before drilling and bending the chassis in order to ensure that these can be installed without difficulty.

A little forethought in the construction will be amply repaid and it is recommended

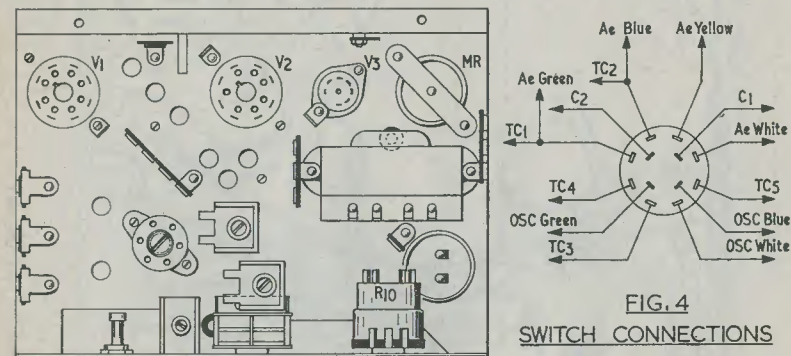


FIG. 3
UNDER-CHASSIS MAIN COMPONENT LAYOUT


G647

Resistance smoothing, together with a metal rectifier and a heater transformer, were used in the interests of economy and size, as already stated, and therefore heed must be taken of the warning that the chassis is "live". For this reason it is recommended that a double pole switch, incorporated with R_{10} , be used and that no direct connection to earth be made. Possibly because of the fairly high values of smoothing and reservoir condensers, the hum level of this receiver is not obtrusive. A surplus 80mA metal rectifier was obtained and mounted vertically on a strip of metal supported across an octal sized hole cut in the chassis; this hole greatly assisting in the maintaining of a cool temperature. A contact cooled rectifier of similar specification could, however, be substituted and a suitable position for mounting this would be on the rear wall of the chassis.

Construction

Details of the chassis dimensions are given in Fig. 2, but it will be noted that only the major dimensions are quoted—constructors generally using existing components which

that, where possible, the construction of the receiver is made as a series of sub-assemblies instead of the more usual sequence of heater wiring, grid, anode, feeds, etc. This recommendation is due to past experience with small receivers and it eliminates some of the difficulties associated with a hot soldering iron in a confined space full of wires, condensers and other small components! A typical sub-assembly would be the wave-change switch which should be wired up as in Fig. 4, preferably with different coloured p.v.c. wires; the connections to the coils, trimmers, etc., being made after installing the switch on the chassis. The switch actually used was a 4 pole 3 way rotary type with the third position rendered inoperative by bending up the appropriate stop tag on the front plate. A general view of the underneath layout of the chassis is given in Fig. 3 and a further diagram, Fig. 5, indicates the component layout. This diagram, together with the accompanying photographs should minimise any difficulties which may arise with the construction of the set. For clarification, some licence has been taken with the layout in Fig. 5 and, in practice, all signal

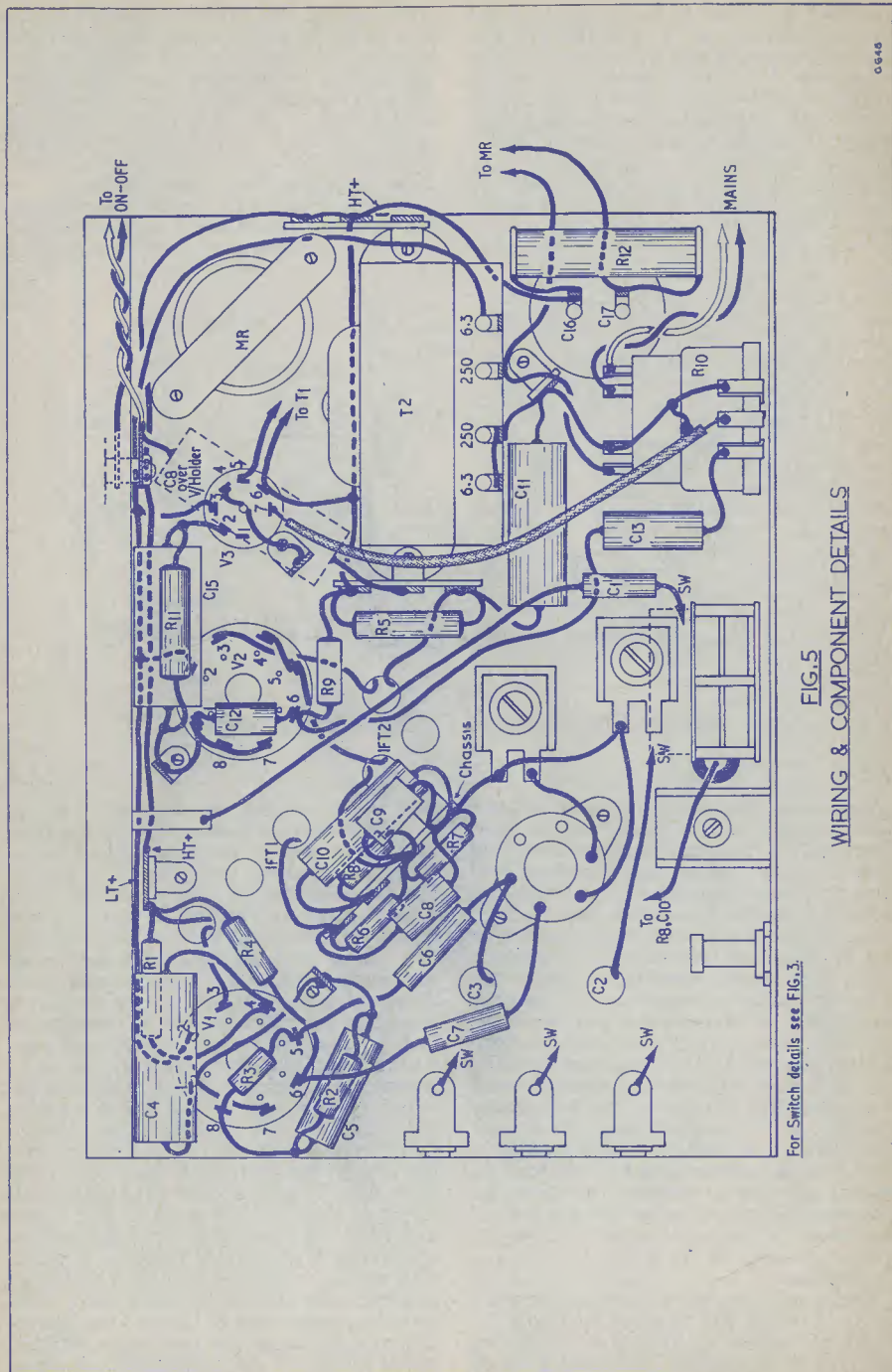

0646

FIG. 5
WIRING & COMPONENT DETAILS

For Switch details see FIG. 3.

leads should take the shortest and most direct route, provided that grid and anode leads do not run together. Signal leads should also be separated from h.t. or heater wiring, which can take a longer path. The heater wiring, in particular, should be tucked away in the fold of the chassis wherever possible. C₁₄, which is for tone control purposes, was mounted across the primary tags of the output transformer T₁ and the value of this condenser can be modified to suit personal requirements.

Alignment

Lining up the receiver without a signal generator should present no great problem.

lower wavelength is then found and trimmer TC₄ is adjusted for correct dial tuning and trimmer TC₂ varied to give maximum volume. A return is made to the Light Programme and, after tuning in this station, any shift in the dial position of the pointer is rectified by carefully altering TC₆. Likewise, any shift of the dial position of the lower wavelength station after this adjustment is corrected by means of TC₄. The Light Programme is checked again and any deviation of position can be corrected as before. This completes the alignment of the Long waves.

Switching to the Medium waves, the pointer is set to 464 metres and the padder


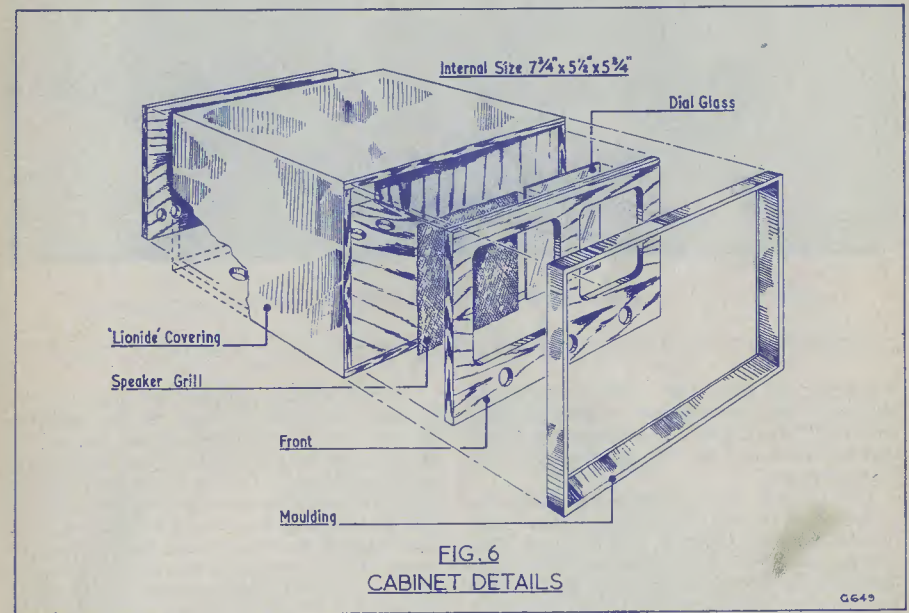


FIG. 6
CABINET DETAILS

If the padders and trimmers are set to approximately their mid-position, and the volume control set to maximum, it should be possible to tune in the local station. When this is received, ignoring the dial reading, the cores of the i.f. transformers are carefully adjusted to give maximum volume, i.f.t.₂ being adjusted first and followed by i.f.t.₁. As the transformers are aligned and the volume increases, signal input can be reduced to suit by shortening the effective length of the aerial. When no further improvement can be obtained, the Long waves are selected and the dial pointer set to read 1,500 metres. Padder TC₆ is then adjusted until the Light Programme is brought to the correct position on the dial as indicated by the pointer. A station of

TC₅ is adjusted to bring the Third Programme to the dial setting. Trimmer TC₁ can then be varied to give maximum volume. The West Region is then tuned in and TC₃ is adjusted to bring this station into line with 206 metres on the dial. Reverting back to the Third Programme, any shift of this station arising from the previous adjustment is corrected by small adjustments to TC₅ and similarly, TC₃ is altered to counteract any change from the dial position of the West Region. TC₁ should be finally adjusted for maximum volume at 206 metres. This completes the alignment of the Medium waves.¹

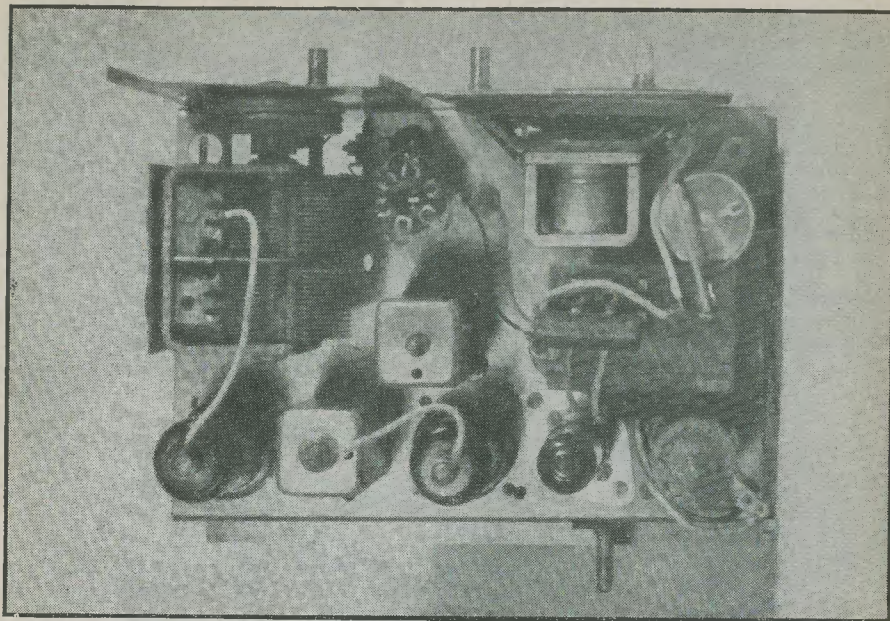The adjustments to be made are only of a small nature and a little care is required with the final touches. Sealing of the padders and



Above chassis view of the Reflex Superhet

trimmers is advisable when satisfactory alignment has been achieved to prevent them vibrating "off-station". The writer has found that his wife's nail varnish makes an excellent fixing solution!


The cabinet was constructed from $\frac{1}{4}$ in plywood with half-lap joints glued and pinned, finally covering with a decorative rexine. A row of ventilation holes was drilled in the bottom of the cabinet to which four small rubber feet were fixed. The back was made of thin plywood, this also having ventilation holes drilled together with clearance holes cut for the mains socket and aerial plug. Four short dowels approximately $\frac{1}{2}$ in long were fixed to the back, one in each corner, and around these were wound a length of thin covered wire acting as the aerial. The front face of the cabinet is of thin polished plywood with suitable apertures cut for the dial, speaker and spindles, and with a cloth grille and Perspex dial covering stapled to it. The front is supported by strips of decorative moulding these being glued around the edges and which also serve to cover the unsightly plywood face edges of the cabinet. If desirable, a fold-flat attache case handle could be added to the top of the cabinet. Fig. 6 gives a general view of the cabinet.

The completed receiver has been in continuous daily use for over a year and has proved to be reliable and satisfactory in every way; its performance has been particularly praised². The small cabinet size has proved useful in transporting the receiver and for tucking it away in confined spaces, for instance, on a book-case shelf. The only point to bear in mind with respect to similar locations is that a little space must be maintained at the back of the set to ensure a free flow of air.

Any qualms the writer had about using a reflex circuit have been dispelled and in future, when faced with the construction of a conventional superhet, he will seriously consider replacing the usual 6K7 and 6Q7, or their miniature equivalents, with a 6B8, particularly in view of the fact that the latter can be obtained for about 4s. on the surplus market!

¹Transmitters other than the two quoted here may, of course, be used for Medium wave alignment provided that their wavelengths are known and are close to those of the two signals specified.

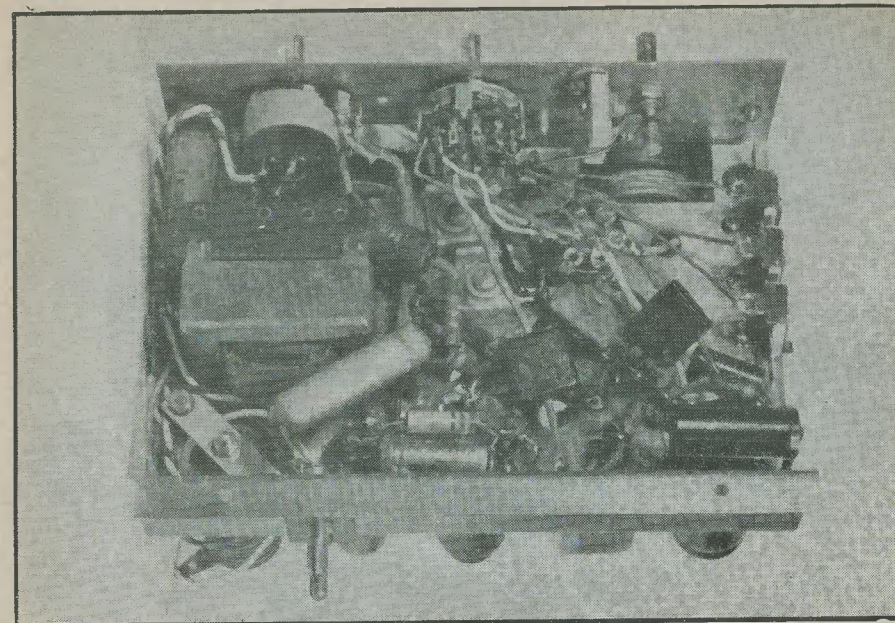²One difficulty initially encountered was acoustic feedback to the tuning condenser but this was completely eliminated by the use of rubber grommets in the holes through which the speaker bolts pass.



Showing component layout and wiring of the receiver constructed by the author

Components List

Resistors

R ₁	27kΩ 1W
R ₂	270Ω
R ₃	47kΩ
R ₄	47kΩ
R ₅	27kΩ
R ₆	100kΩ
R ₇	470kΩ
R ₈	2MΩ
R ₉	100kΩ
R ₁₀	500kΩ Pot. Log.
R ₁₁	220Ω 1W
R ₁₂	1kΩ 5W

All resistors $\frac{1}{2}$ W except where otherwise stated

Condensers

C ₁	0.02μF 750V
C ₂₋₃	500pF variable 2-gang
C ₄	0.1μF 350V
C ₅	0.1μF 150V
C ₆	100pF
C ₇	100pF
C ₈	470pF
C ₉	470pF
C ₁₀	0.05μF 150V


C ₁₁	0.1μF 350V
C ₁₂	300pF
C ₁₃	0.01μF 350V
C ₁₄	0.02μF 350V
C ₁₅	25μF 25V electrolytic
C ₁₆₋₁₇	24+24μF 350V electrolytic
C ₁₈	0.005μF 750V
TC ₁₋₄	70pF trimmers
TC ₅	550pF padder, variable
TC ₆	250pF padder, variable

Valves

V ₁	6K8
V ₂	6B8
V ₃	6AQ5

Miscellaneous

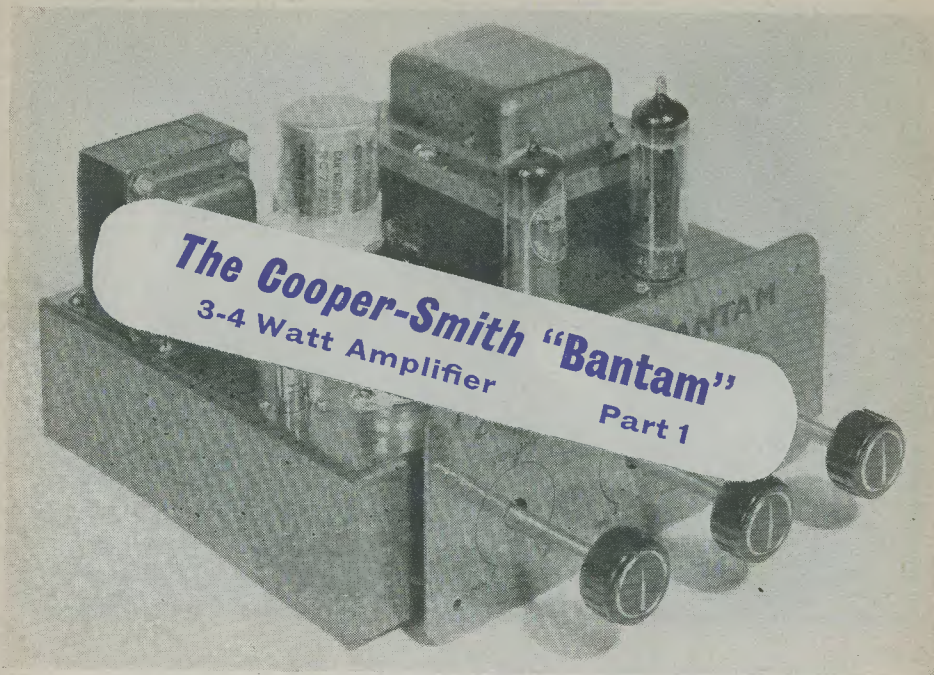Coils—Repanco SH4 dual range
 I.F.T. 1-2—Radio Component Specialists
 Speaker— $3\frac{1}{2}$ in 3Ω
 Metal rectifier 250V 60-80mA
 T₁ 40:1 output transformer
 T₂ 6.3V filament transformer
 4-pole 2-way wavechange switch
 I.O. valveholders—2 off
 B7G valveholder—1 off
 Dial, reduction drive



Described by W. Holmes

This article gives full constructional details of an inexpensive amplifier which is capable of a very high performance level

DESPITE THE FACT THAT PRESENT-DAY audio amplifying and reproducing equipment tends to be centred on complex and relatively costly amplifiers there is a very considerable demand amongst constructors for amplifiers which, whilst being capable of offering a high performance level, are smaller and less expensive. The Cooper-Smith "Bantam" falls into this category, and it has been designed to give a quality of reproduction which is considerably in advance of that provided by standard radios and radiograms. The "Bantam" possesses all the features normally found in much more complex equipment: it has continuously variable bass and treble controls, it contains its own mains power unit, it can provide heater and h.t. power for ancillary equipment such as f.m. tuner units and the like, and it is capable of driving speakers at either 15Ω or 3.75Ω impedance. The output stage is single-ended, the output valve specified being rated at a high power figure. This valve works into an output transformer having a generously heavy core,

negative feedback from its secondary being applied to the stage preceding the output valve.

As may be seen from the photograph at the head of this article, the completed amplifier presents a very neat and professional appearance. A separate escutcheon, also shown in the photograph, enables the amplifier to be mounted in a cabinet, if desired, the control spindles protruding through the escutcheon.

Technical features for the "Bantam" are as follows:

- Power Output: 3-4 watts.
- Frequency Response: 40-25,000 c/s ± 1 dB at 1 watt (tone controls flat).
- Tone Controls: Bass and treble cut and boost, continuously variable.
- Output Impedances: 3.75Ω and 15Ω.
- Input Sensitivity: 60mV for 3 watts output.
- Valves: ECF80, EL84 (or 6BQ5), EZ81.
- Spare Power: 250V at 45mA, 6.3V at 2A.
- Weight: 8½lb.
- Size: 8 x 6½ x 4½in.

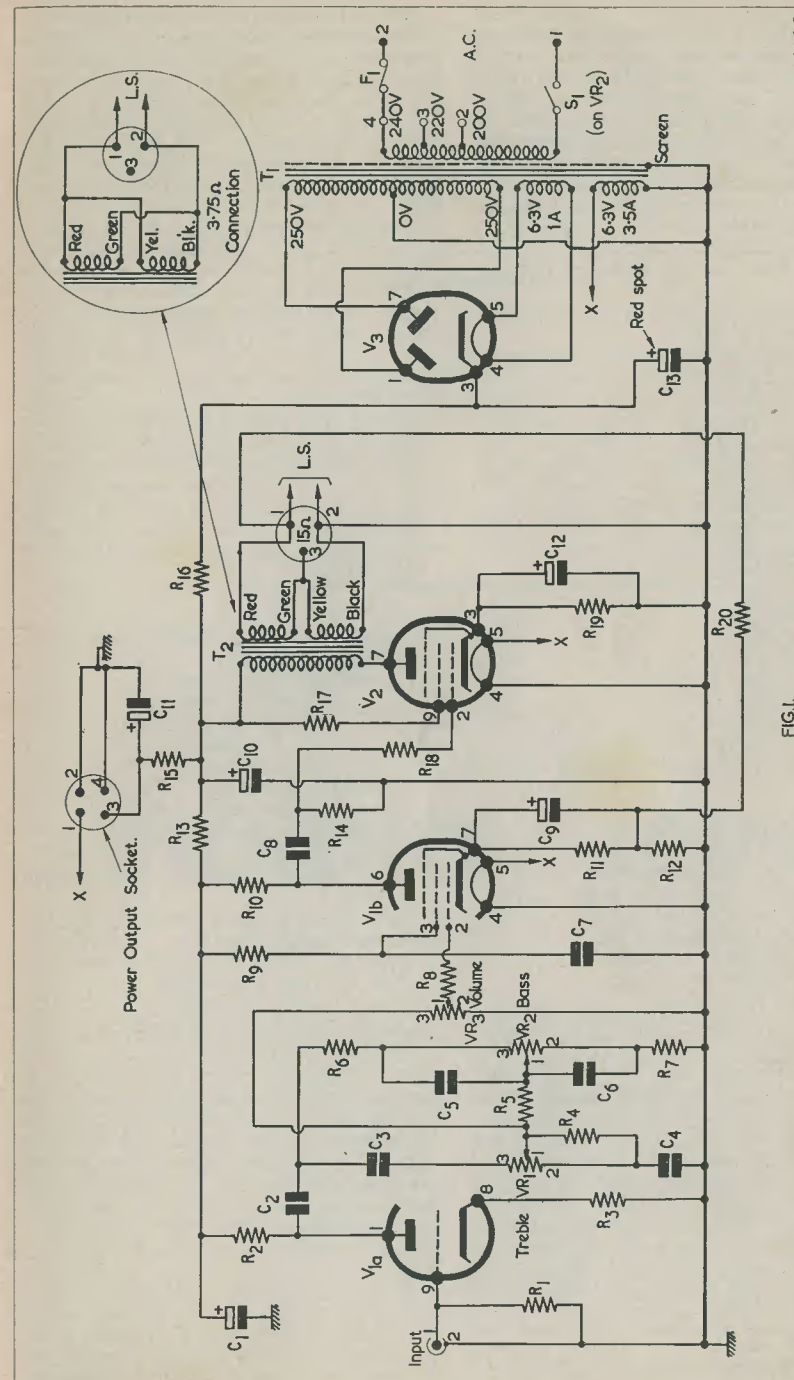


FIG. 1.

Fig. 1. The theoretical circuit of the Cooper-Smith "Bantam". The identification numbers on potentiometers and sockets apply to the similarly numbered tags in Fig. 2

The Circuit

The circuit of the Bantam appears in Fig. 1. The input signal is applied to the grid of $V_{1(a)}$, this being the triode section of an ECF80. $V_{1(a)}$ functions as a triode voltage amplifier and compensates for the loss of signal voltage occurring in the subsequent tone control circuit. A small degree of current negative feedback is applied to the input stage by means of the un-bypassed cathode resistor R_3 .

to the pentode section, $V_{1(b)}$ of the ECF80.

The pentode also functions as a voltage amplifier, the amplified signal appearing across its anode load, R_{10} . Due to the choice of valve and operating conditions, $V_{1(b)}$ anode has a relatively low impedance to chassis. The anode of $V_{1(b)}$, working at this relatively low impedance, then drives the grid of the output valve, V_2 , via the grid stopper, R_{18} .

The output valve functions in conventional

Components List

Resistors

R_1	1M Ω $\frac{1}{8}$ W 20%
R_2	100k Ω $\frac{1}{2}$ W 20%
R_3	1.2k Ω $\frac{1}{4}$ W 20%
R_4	47k Ω $\frac{1}{4}$ W 20%
R_5	39k Ω $\frac{1}{4}$ W 20%
R_6	68k Ω $\frac{1}{4}$ W 20%
R_7	6.8k Ω $\frac{1}{4}$ W 20%
R_8	1k Ω $\frac{1}{8}$ W 20%
R_9	470k Ω $\frac{1}{4}$ W 20%
R_{10}	100k Ω $\frac{1}{4}$ W 20%
R_{11}	1.8k Ω $\frac{1}{4}$ W 20%
R_{12}	100 Ω $\frac{1}{4}$ W 20%
R_{13}	22k Ω $\frac{1}{2}$ W 20%
R_{14}	1M Ω $\frac{1}{4}$ W 20%
R_{15}	See text
R_{16}	470 Ω 5W 20%
R_{17}	100 Ω $\frac{1}{4}$ W 20%
R_{18}	10k Ω $\frac{1}{8}$ W 20%
R_{19}	150 Ω $\frac{1}{2}$ W 20%
R_{20}	For 15 Ω output 22k Ω $\frac{1}{4}$ W 20% For 3.75 Ω output 10k Ω $\frac{1}{4}$ W 20%

Condensers

C_1	16 μ F 275 W.V. Daly
C_2	0.02 μ F 350 W.V. static
C_3	560pF silver mica, R.B.S.
C_4	8,000pF silver mica, R.B.S.
C_5	2,000pF silver mica, R.B.S.
C_6	0.02 μ F Moldseal
C_7	0.1 μ F 350 W.V. Static
C_8	0.05 μ F 350 W.V. Static
C_9	50 μ F 12 W.V. Daly
C_{10}, C_{13}	50+50 μ F, 350 W.V., with clip, Daly

C_{11}	8 μ F 350 W.V. Daly
C_{12}	50 μ F 25 W.V. Daly

Potentiometers

VR_1	250k Ω Log., A.B. Metal
VR_2	250k Ω Log with switch
VR_3	1M Ω Log., A.B. Metal

Valves

V_1	ECF80
V_2	6BQ5 or EL84
V_3	EZ81

Miscellaneous (all available from H. L. Smith & Co. Ltd.)

T_1	Mains Transformer, 250-0-250V 100mA, 6.3V 3.5A, 6.3V 1A
T_2	Output Transformer, Electro-Voice D91
	Valveholder B9A (2)
	Valveholder B9A with skirt (1)
	Mains plug and socket, Bulgin
	Speaker plug and socket (3-pin), Cinch
	Power output plug and socket (4-pin), Cinch
	Input plug and socket, coaxial
	Mains selector, fused 2A
	Tagstrips, 12-way (pair)
	Wire, sleeving, screws, nuts
	Chassis, punched, bronze
	Control panel, gold hammered
	Control knobs, gold insert (3)

The signal on the anode of $V_{1(a)}$ is fed to the tone control circuit around potentiometers VR_1 and VR_2 . This circuit¹ is one which has been well-proven in practice, and was successfully incorporated in the Cooper-Smith Mark II Control Unit.² The output from the tone control circuit is applied to the upper terminal of VR_3 , the volume control; the signal level tapped off by the slider of this control being fed, via the grid-stopper R_8 ,

manner, feeding into the speaker transformer T_2 , the secondary of which connects to the loudspeaker output socket. In the main circuit diagram the two secondary windings are connected in series, thereby offering an output impedance of 15 Ω . In the "inset", the secondary windings are connected in parallel, offering an output impedance of 3.75 Ω .

Negative feedback is obtained from the secondary of the speaker transformer via R_{20} . This resistor, with R_{12} , forms a fixed potentiometer which causes a proportion of the secondary output voltage to be injected

into the cathode of $V_{1(b)}$. For 15 Ω output operation R_{20} has a value of 22k Ω . For 3.75 Ω output operation (in which half the signal voltage given for 15 Ω operation is available across the secondary of T_2) R_{20} has a value of 10k Ω .

H.T. power in the "Bantam" is obtained by means of a mains transformer having a full wave h.t. secondary, rectification being provided by V_3 . V_3 cathode connects into the filter components C_{13} , R_{16} , and C_{10} , the output valve, V_3 , obtaining its h.t. supply from the smoothed voltage appearing across the latter condenser. Further smoothing is provided by R_{13} and C_1 , the voltage across C_1 being employed for $V_{1(a)}$ and $V_{1(b)}$.

The power supply has been designed to provide an h.t. output of 250 volts at a maximum current of 100mA. The amplifier current requirement is 55mA only, with the result that an h.t. voltage of 250, with a maximum current of 45mA, becomes available for ancillary equipment such as radio tuners, etc. Such equipment may obtain h.t. and heater power from the power output

socket shown in Fig. 1. Since individual requirements may vary, a value for the h.t. series resistor, R_{15} , has not been specified; this being chosen to suit the particular needs of the equipment envisaged. If, to take an example, the ancillary equipment were to require an h.t. supply of 200 volts at 40mA, then R_{15} would be required to drop 50 volts (from the 250 volts available in the amplifier)

at this current. From Ohms Law $R = \frac{E}{I}$ the required value for R_{15} under these circumstances would be $\frac{50}{0.04} = 1,250\Omega$. Should

the amplifier be purchased in kit form, either the value for R_{15} , or the voltage and current requirements of the associated equipment, should be specified.

A 6.3V heater supply is also available at the power output socket, this being obtained from the same heater winding of the mains transformer which feeds the heaters of $V_{1(a)}$, $V_{1(b)}$, and V_2 . The heater current available at the socket is 2A.



THE PILKINGTON COMMITTEE, DUE TO report in just under two years' time, has the unenviable task of sorting out what further alternative television programmes are to be transmitted in this country. My normal reaction to the setting up of a Governmental Committee is that this is an easy way to delay decisions. In this instance, however, I cannot help but feel that the situation is sufficiently complicated to fully merit the setting up of a committee in order that the very many views and opinions currently held may be examined and presented in digestible form. It is to be hoped that the requisite Governmental decisions resulting from the Committee's findings will be made within a reasonably short time of the latter being made known.

The Pilkington Committee was set up shortly after the publication of a report made by a previous body—the Television Advisory Committee.¹ The Television Advisory Committee has had a job to do which is at least as complicated as that now facing the Pilkington Committee. Amongst other things it had to recommend whether the existing 405 line standard was likely to remain adequate for all purposes for the next 25 years, to state whether there was any reason why the United Kingdom should not adopt a 625 line standard in Bands IV and V², and to see whether advantage could be

¹ Report of the Television Advisory Committee, 1960 H.M.S.O. Price 1s.

² Band IV is 470-582 Mc/s and Band V is 606-960 Mc/s.

gained from the use of higher standards (i.e. more lines) in Bands I and III. The Committee had, also, to investigate the possibilities of colour in Bands IV and V, recommend the best technical means of transmitting colour in these Bands, and to report on any proposals concerning colour made by the B.B.C. or I.T.A.

This was quite a sizable programme and the Advisory Committee has handled it very well indeed. It is a pity that the findings of the Committee have not been more accurately reported, particularly in the lay press. (Even in the august *Sunday Times* the television correspondent held forth learnedly about 405 lines *per inch*.)

Committee Findings

The findings of the Committee are, briefly, as follows. Firstly, the existing 405 line system will not be adequate for all purposes for the next 25 years. Secondly, assuming that television were to be confined to Bands I and III, a changeover to higher standards (more lines) would not be practicable on these Bands. Thirdly, Bands IV and V must be brought into use if it is intended to provide a 625 line system (even if no additional programme is intended) or to offer more than three programmes (whatever line standard is used). Fourthly, the use of Bands IV and V would offer the last chance to make a change in line standards, and, if such Bands and standards were used, a 625 line system with 8 Mc/s channel width should be employed. Fifthly, whatever colour system is used should be fully compatible; but that a decision concerning its introduction should only be made after a decision has been made on line standards. Sixthly, whatever decisions are made, the current 405 line services should be retained for many years so that existing receivers would not become prematurely obsolescent.

A factor touched on above is the reference to a 625 line standard with 8 Mc/s channel width. This is an extremely important point, because it qualifies almost all the argument at present being raised for and against an increase in the number of lines.

There are, at the time being, two 625 line standards currently operating in Europe. These standards are similar to each other in that both employ negative picture modulation (where increase in transmitter output causes decrease in picture brightness), frequency modulated sound, 50 frames per second and, of course, 625 lines per picture. They differ in channel width and vision bandwidth. One of these systems is that adopted by Western Europe. The Western Europe system has a channel bandwidth of 7 Mc/s and the vision signal occupies 5 Mc/s on one side of the carrier and 0.75 Mc/s (the vestigial sideband)

on the other side of the carrier. Thus, the maximum video signal the system can carry is 5 Mc/s. The Eastern Europe system (the O.I.R.T. system) is that employed by Russia and the satellite countries. It has 8 Mc/s channel width, and the vision signal occupies 6 Mc/s on one side of the carrier and 0.75 Mc/s (the vestigial sideband) on the other side of the carrier. The highest video signal that can be handled is, therefore, 6 Mc/s. The 625 line system with 8 Mc/s channel width proposed by the Advisory Committee is different again, because it is recommended that the vision signal in this system should occupy 5.5 Mc/s on one side of the carrier and 1.25 Mc/s (the vestigial sideband) on the other. This is the same as the Eastern Europe system, with the exception that the vision sideband loses 0.5 Mc/s which is gained by the vestigial sideband. Maximum video frequency is 5.5 Mc/s.

Picture Quality Improvement

What improvement in picture quality would we gain from the proposed 625 line system with 8 Mc/s channel width, as compared with our present 405 line system, which has a channel width of 5 Mc/s? It is quite easy to work this out mathematically. The 405 line system has 377 active lines (approximately 28 being lost in the frame blanking periods) and the 625 line system has approximately 585 active lines. Thus, the latter would give us a picture having 585 visible lines as against 377 in the 405 line system; that is, an improvement of 1.55:1 or 55%. The length of a line (less sync pulse) in the 405 line system is approximately 80.7 μ s, and the maximum video frequency is 3 Mc/s, of which each cycle takes up, obviously, $\frac{1}{3}$ μ s of time. Thus, we can fit 242 cycles of picture information, or 484 picture elements, into each line of the 405 line system.³ If the proposed 625 line system with 8 Mc/s channel width has the same line sync pulse as the Western Europe system, the active length of a line (less sync pulse) will be approximately 52.2 μ s. The maximum video frequency will be 5.5 Mc/s, with the result

that each cycle will occupy $\frac{1}{5.5}$ μ s; and the

maximum amount of cycles in an active line becomes 287. Which is equal to 574 picture elements. Thus the improvement in horizontal resolution over the 405 line system is 574:484, or 1.2:1. It follows that the improvements in picture quality given by the proposed 625 line system will, therefore, be an improvement in vertical resolution of 55% and an improvement in horizontal

³ 80.7 μ s divided by $\frac{1}{3}$ μ s equals 242.1. One cycle of picture information contains two picture elements, one white and one black.

resolution of 20%.

These results tie up with subjective tests mentioned in the Advisory Committee report. Viewers were asked to assess preference between 405 and 625 line pictures (the latter, during the tests, having a 5 Mc/s bandwidth); and it is reported that the 625 line pictures were noticeably better than the 405 line pictures with reference to visibility of lines. But, so far as an overall assessment of quality between the two systems was concerned, there was only a slight preference for the 625 line picture, and then only in areas of high field strength. (The 5 Mc/s 625 line pictures used in the tests would be able to resolve only 10% more picture elements per line than the 405 line pictures.)

Is It Worth While?

Accepting the improvement in picture quality—20% better horizontal resolution and 55% better vertical resolution—is the change from 405 lines to the proposed 625 line system worth while? A number of arguments have been raised against such a change, these stating, in the main, that the improvement in picture quality is too small, and that the 8 Mc/s channel width allows the use of fewer channels than does the current 5 Mc/s channel width of the 405 line system. The second point is undeniably true. Exponents of the first argument claim that all the new system can do is to reduce “lininess” in the reproduced picture. I cannot help but feel, myself, that reduced “lininess”, and the consequent increase in vertical resolution given thereby, is something which should not be sneered at.

Speaking for myself, I am whole-heartedly in favour of a change to the proposed system. I feel, apart from the improvement given in picture quality (and I'm prepared to admit that this isn't all that *fantastically* great), that other important advantages will be brought into being in the new system. The new system will, for instance, provide negative picture modulation which means that, in simple receivers, interference pulses will show up on the screen as black instead of white, and that a.g.c. voltage can be taken from the tips of the sync pulses instead of from average picture level (thereby obviating the case where contrast increases when the overall brightness of the picture decreases). The proposed scheme will also provide f.m. sound with its attendant suppression of impulsive interference. Further, it will give us frame sync signals with equalising pulses, thereby eliminating the circuit skulduggery used in present 405 line receivers to obtain good interlace. Finally, and, in my opinion, most important of all, it will enable us to manufacture receivers for the home market which, with little modification, will be

capable of being exported to all countries employing not only 625 but also 525 line systems. Such countries include Australia (625 line) and, of course, North America (525 line).

This final advantage may require a little amplification. It is not generally realised that a very large difference exists between a 625 line receiver and a 405 line receiver. Not only is there the obvious difference between line time base circuits and components, but there is also the fact that the two systems call for entirely different circuitry between the tuner unit and the vision and sound detectors. A 405 line receiver has separate vision and sound i.f. strips. A 625 line receiver has a single strip between the tuner unit and the vision detector, intercarrier sound being taken off that detector and fed into a separate intercarrier amplifier before application to the sound discriminator. The very large difference in the i.f. sections renders the two types of set so dissimilar that they cannot economically employ the same chassis layout and can by no means share the same production line. There would, on the other hand, be proportionately very little difference between a receiver intended for the proposed 625 line system, and one intended for export to a 625 or 525 line country. Also, strong home sales would iron out the production and performance snags likely to crop up in the export versions. 525 line receivers employ much the same stage layout as 625 line receivers (intercarrier sound, etc.) and their time bases can be near-identical. This is because the line frequency of the 525 line system is 15,750 c/s (as opposed to the 15,625 c/s in the 625 line system) and frame frequency is 60 c/s (as opposed to 50 c/s in the 625 line system). There are differences in recommended intermediate frequency and in intercarrier frequency, but these are not so great as to prevent a common chassis layout being employed in production receivers.

I would suggest, therefore, that arguments against the introduction of a 625 line system in this country are vastly outweighed by the advantages which would accrue. These latter consist of a small but significant improvement in picture quality (especially in vertical resolution), an improvement in interference suppression on both picture and sound, an improvement in the a.g.c. characteristic of cheaper receivers together with the easing of interlace problems, and the introduction of a domestic receiver export potential where production difficulties can be almost entirely overcome by large scale home market experience.

Getting the Record Straight

I am indebted to two readers who have

very kindly given me chapter and verse for the "sug and plocket" limerick I reconstituted from memory in the July issue. I am informed that the limerick originally appeared in the May 1954 issue of *Wireless World*, and its author was "M.F.R.". My correspondents⁴ give me the correct version, which is as follows:

An "n-pole free (male moulding) socket"
Means hard work for storemen who stock it;
Why not use the word "sug"
For a "fixed (female) plug",
And call a free socket a "plocket"?

Many thanks for helping me out.
My comments on the use of "oscilloscope" and "oscillograph" has prompted a letter from another reader.⁵ He states:
"In stating that 'oscillograph' is considered

to be more correct than 'oscilloscope', you appear to have transposed the two words. In its early days the c.r.o. was always referred to as an oscillograph, but it is now the established practice to reserve the term 'oscillograph' for instruments having facilities for photographing or otherwise recording the trace, instruments without these facilities being distinguished by the term 'oscilloscope'. The photographic or other record obtained from an oscillograph is termed an oscillogram, apparently by analogy with the words 'telegraph' and telegram."

I must confess that this is a view I hadn't thought of up to now. And my thanks for the information.

⁴ Mr. H. Bradbury, Hyde, Chester, and Mr. C. Pierrepont, New Malden.

⁵ Mr. R. R. Hamilton, Ashtead.

RTTY In Theory and Practice

by J. B. Tuke, G3BST

PART 5

WE NOW COME FINALLY TO THE CHOICE of a receiver system, the object of which being to convert the signals received from a distant r.t.t.y. station into d.c. reversals suitable for application to the teleprinter magnet. The equipment to be considered in this article will be that suitable for the reception of f.s.k. signals, since it has already been shown that, on the h.f. bands at any rate, this is the only practical system.

Let us first consider the task which the receiving terminal (and this expression includes the actual radio receiver, teleprinter circuit and any auxiliary equipment) must achieve. The signal, as picked up by the aerial, will consist of a wave having frequency shift keying for its modulation—one of the frequencies corresponding to Mark, and the other to Space, and these two radio frequencies have to be converted into d.c. voltages having opposite polarity. The receiving terminal must also be able to select the required signal from spurious signals—i.e. it must possess selectivity. It must only respond to frequency modulation as opposed to amplitude modulation. The signals finally delivered to the teleprinter must have

the correct voltage amplitude, and be independent of any changes in received signal amplitude. Telegraph distortion, if introduced at all, must be kept to a low figure. We will now consider these various requirements in greater detail under separate headings.

Selectivity

There are two main ways of dealing with this problem, (a) the use of a highly selective receiver, having a "square-topped" band-pass one kilocycle wide. This bandpass will accept an f.s.k. signal having an 800 c/s shift, together with sufficient sidebands to ensure low distortion. If we are sure the receiver can do this job to perfection then the signal from the receiver, at its intermediate frequency or second intermediate frequency, if it is a double superhet (which is normal for this type of work) is passed on to a frequency modulator detector which, in itself, does not contribute in any way to the selectivity but simply produces an output voltage, the direction of which is dependent upon the frequency being received.

(b) The alternative method is to have

most of the selectivity in the frequency modulation detector itself, or its close circuitry. In this case, the receiver converts the incoming f.s.k. signal into two very much lower frequencies (normally audio tones) the detector producing d.c. outputs from these two tones only, having sufficient inherent selectivity to ignore other nearby tones produced by interfering signals.

The choice before the amateur of one of the above systems is dictated largely by the capabilities of the receiver. System (a) can only be used if the receiver really does have the required selectivity characteristic. This is unlikely to be attained unless a multiple crystal filter is fitted or very low frequency triple conversion adopted. Adaptor units which accept a normal 465 kc/s i.f. can be made to convert this frequency to a lower one having the required filter at this point, but they are of necessity, very involved. It is of little use having a response which is "6dB down at 1 kc"—the 1 kc bandpass must have an almost vertical skirt. Without additional conversion, the average receiver in use at an amateur station is simply not suitable for this type of work, and unless suitable test gear is available experiments along this line are likely to lead to disappointment from the selectivity angle. If, however, a suitable receiver is available, then it is only a matter of picking up the final i.f. and passing it to an f.m. detector.

While the (a) system is not normally suitable for amateur use the alternative method is quite attractive. In this, the majority of the selectivity is in the detector. The f.s.k. signal is taken from the receiver at the normal a.f. output point in the form of two audio tones. These tones (one for Mark, the other for Space) together with any interference that may be present are applied to highly selective tuned a.f. circuits which may, or may not, be part of the detector circuit itself. These circuits, having regard to the low frequencies involved, have sufficient selectivity to have little or no response to any other frequencies apart from those chosen to represent Mark and Space. This set-up, which may be termed "receiver plus r.t.t.y. adaptor" is, in the usual case, more suitable for amateur application since it enables the normal station receiver to be used for r.t.t.y. and also permits quite phenomenal selectivity to be achieved with simple circuitry.

Whichever system is used, it cannot be too strongly emphasised that *selectivity is essential* for successful r.t.t.y. working. If there should be any response to signals more than 200 c/s away from the required signal then, under amateur conditions certainly, consistent reception cannot be expected.

Response to FM Signals Only

In some ways this could also be considered under the heading of selectivity since it concerns the rejection of unwanted signals but, as the mode of rejection is completely different, it will be considered separately. The rejection of amplitude modulated signals, or signals having any amplitude change, is necessary on two counts. Firstly, within reasonable limits, the voltage applied to the printer coils must not vary if the received signal is subject to fading. This point, however, can be dealt with quite well after the detector stage. In the second case, amplitude modulated interference such as phone or c.w. is obviously to be expected in association with the required signal, therefore if the detector is made insensitive to this type of signal then interference will not result.

The removal of amplitude modulation is achieved in the normal manner—that is by means of a limiter. This may be an r.f. limiter somewhere in the i.f. chain, or if the "r.t.t.y. adaptor" technique is employed, it may be an a.f. limiter between the receiver output and the adaptor input (although it may, of course, be part of the adaptor itself as far as construction goes). Whichever method is used it must work properly for, along with selectivity, satisfactory limiting is another "must" for r.t.t.y. working—its omission resulting in a.m. signals producing output, which is plainly a hopeless situation.

The Detector


Here again we can consider the two systems, previously described, separately. In the purely r.f. system, where a special receiver is used, the detector will act as the third unit in the chain, if we consider the first as a superhet receiver, and the second as a limiter. Having got rid of all interfering signals outside the passband in the receiver, and of all amplitude variations in the limiter, we now have to change the f.m. signals into d.c. reversals. Two circuits are common—the Foster-Seeley type, and the twin-tuned type—basic circuitry being shown in Fig. 1. A slight difference exists in the alignment, however. The twin-tuned circuit may be deliberately undercoupled so that the response curve relating d.c. output to r.f. input is non-linear, compared to the normal f.m. arrangement. This is to reduce the response to frequencies falling in between the Mark and Space values. It is not possible with single tuned circuits to produce this effect to any marked extent, but the curve to be achieved is that shown in Fig. 2 (b), Fig. 2 (a) showing the normal f.m. discriminator curve.

The output from either type of discriminator will consist of small reversal voltages varying in sympathy with the incoming f.s.k.,

and these voltages will eventually, after amplification, be applied to the printer.


Returning now to the audio frequency system, the detector requirements are rather different. Here we have two audio tones,

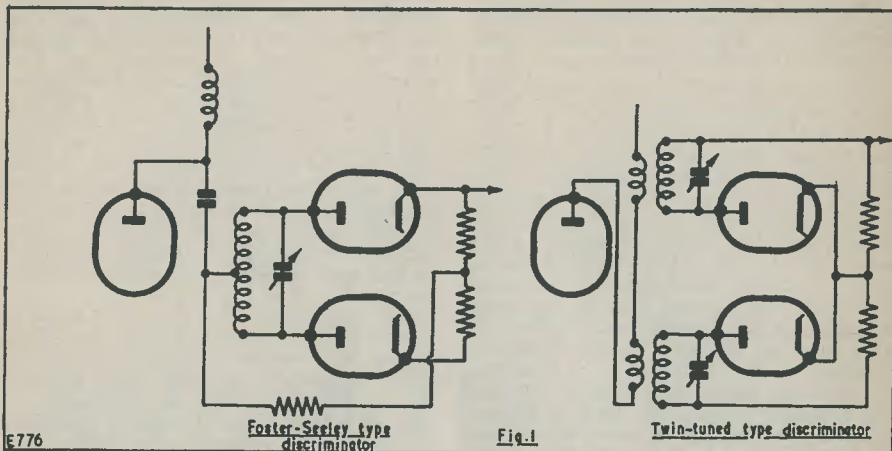combined in anti-phase, so that the direction of the current depends upon the incoming audio frequency. The detailed circuitry may be varied. For example, let us imagine that the two tones chosen to represent Mark and



one which has to be converted to d.c. in one direction, the other to d.c. in the reverse direction. We have also admitted that interference will be present and the detector must therefore not respond to any tones other than those of Mark and Space.

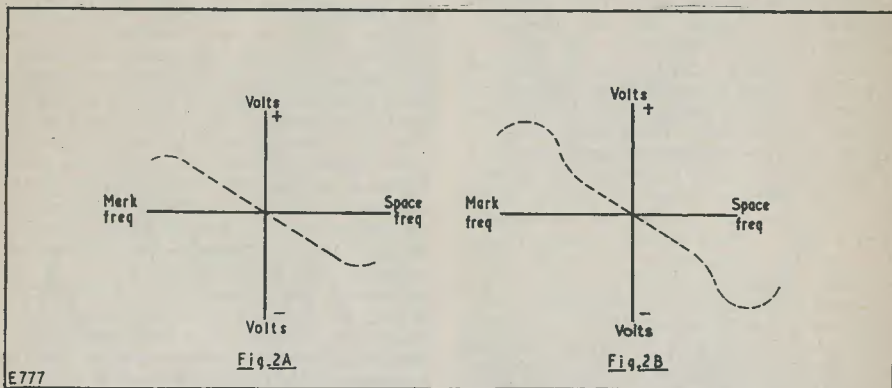Space are 1,000 and 1,800 cycles respectively. We may start off with a pair of tuned amplifiers, one on each frequency, connected side by side to a common input. After this selective filtering, the signals may then be amplified to the required degree and passed



A true discriminator on the Foster-Seeley lines at audio frequencies would be difficult to construct, and would also have little selectivity, so we must turn to other types of circuit.


The usual method is to arrange for two separate a.f. tuned circuits (one tuned to the Mark frequency, the other to the Space)

to the diodes. Alternatively, the signal from the receiver may be amplified "as it stands" to the required level, and then fed to a pair of diodes via two highly selective audio coupling devices—see Fig. 3. The choice of circuit is left to the individual, either method producing good results.

Whichever comes first, the tuning or the amplification, it is important to design the tuning circuits for high selectivity. This is not easy at audio frequencies and, although


conventional parallel inductance and capacity circuits are often used, trouble will almost certainly be experienced in getting a reasonable "Q". The highest quality inductances will be required—these will almost certainly have to be toroids. It may be necessary to use a number of these circuits in cascade to achieve the required result. An alternative method is to use RC bridge circuits and filters in place of the usual LC circuits.¹ The RC circuit is more convenient at audio

the appropriate voltage across the diode load, other frequencies produce little or nothing. This applies not only to frequencies either side of the Mark and Space frequencies, but to those in between as well. A correctly adjusted detector will print merrily away in the face of the most atrocious interference, while a poorly adjusted one will "garble" even with the slightest interference, it is therefore worthwhile going to some trouble obtaining the correct response.

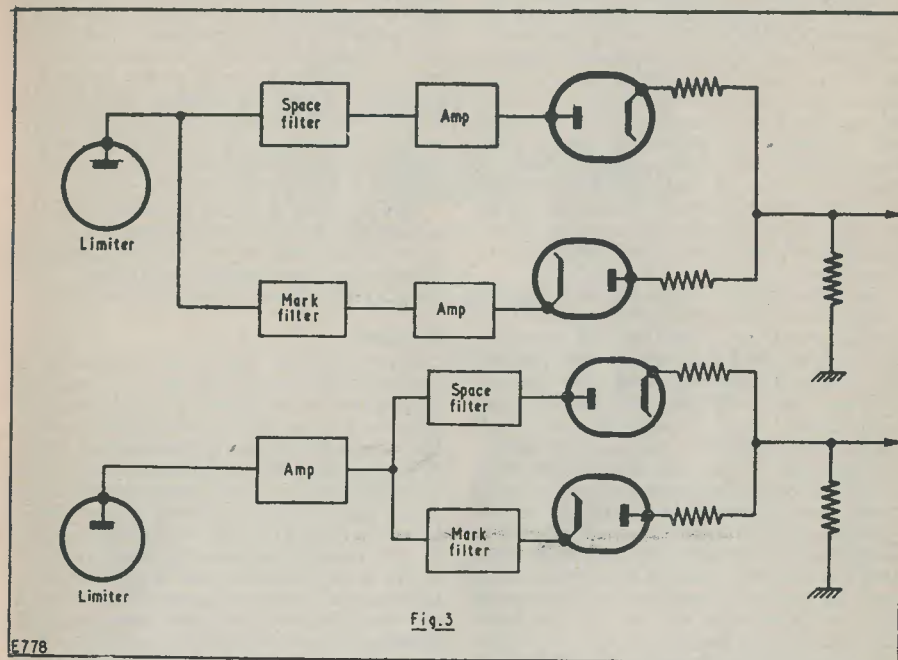

frequencies and also easier to adjust to a particular frequency since R can always be made variable, whereas L and C cannot, except in steps. It is permissible to use a certain amount of regeneration in order to improve selectivity—but it must not be carried to excess. Regeneration introduces "ringing"—the prolongation of the original signal beyond its original length, and this is, of course, telegraph distortion. Carefully controlled regeneration will, however, improve the selectivity very considerably long before distortion becomes noticeable. The response curve to be aimed for is shown in Fig. 4. This indicates that while the frequencies chosen for Mark and Space will produce

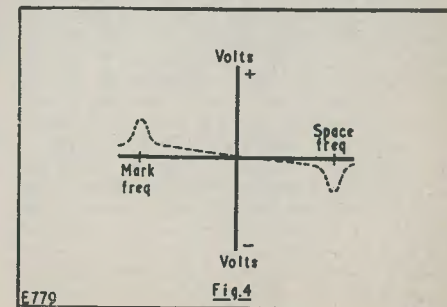Before leaving this type of circuit, we may consider for a moment what are the best a.f. tones to use for Mark and Space, since any two can be used providing they differ by the chosen value of shift—normally 800 c/s. Selectivity will be easier to achieve if low



¹ A more extended explanation of this method appeared in the March and April 1960 issues of the *Short Wave Magazine*, together with a circuit and constructional details of a terminal unit making use of these principles.—EDITOR.

frequencies are used—since the percentage shift is greater. But we have to remember that the minimum 20ms “burst” of signal is going to be turned into d.c. by the diode, and that if this consists of too few cycles some difficulty will be experienced in separating the a.c. and d.c. components. For example, a 20ms signal at 1,000 c/s will consist of 20 cycles. Assuming perfect separation of a.c. and d.c., the rise-time of the d.c. will be one-quarter of a cycle—i.e. a quarter of a millisecond. If we now consider the same 20ms signal, with a frequency of 100 c/s, the entire signal will only consist of 2 cycles, and the rise time will be 2.5ms. Since it is unlikely that perfect separation of a.c. and d.c. will be obtained, the rise-time (and consequently the fall-time) will probably be somewhat longer than shown here—and this is again a form of distortion. For this reason this example shows that the frequencies chosen cannot be too low; therefore it is inadvisable to choose figures much below 400 c/s if difficulty is to be avoided.

Two frequencies which are harmonically related must also be avoided—since if we chose, say 800 and 1,600 c/s, any harmonic distortion of the 800 c/s signal would appear as a 1,600 c/s signal and upset operation.

If too high a frequency is chosen, then harmonics of lower, interfering signals will produce response from the detector circuit. For example, if, say, the Space tone were 3,000 c/s, then an interfering signal on 1,500 cycles, being distorted in the limiter, would produce output. This effect must be present whatever frequencies are chosen but, if lower ones are used, the effect is not so noticeable since the overall a.f. response of the receiver may be deliberately reduced on the lower frequencies quite easily.

As can be seen, there are a number of conflicting requirements—but good results may be expected if the lower of the two frequencies is of the order of 400 to 500 c/s, with a shift of 800 c/s.

Final Stage

In this stage, the d.c. reversals appearing across the detector load are amplified and limited before being passed on to the printer itself. This may be accomplished by purely electronic, or by electro-mechanical means, or a combination of both. In the purely electronic method, the d.c. from the detector is used (after amplification) to trigger a bi-stable multivibrator. A pair of valves are set up in a bridge circuit, the teleprinter magnet coil being the cross arm of the bridge. If alternate valves conduct, current through the coils is reversed in sympathy. Clearly the current through the valves is independent of the trigger voltage so that

d.c. limiting is applied automatically. This arrangement is a good one, the follow-on action of the circuit being so rapid that no appreciable distortion is introduced. Its main drawback is complication and rather large power consumption.

The alternative method is to use the d.c. from the detector (again after amplification) operating a centrally polarised relay. The relay makes one contact, or the other, according to the d.c. polarity, switching the teleprinter coils to an external d.c. supply first in one direction and then in the other. The advantage of this method is its simplicity but, of course, some distortion must be introduced since the relay cannot operate in zero time. Providing a correct type of relay is used, this distortion is not serious. Again, current flowing in the printer coils is unaffected by the current from the detector so that d.c. limiting is automatic.

Having covered all the essential points in a receiving terminal, we will now look at one or two additional items which are frequently found in commercial equipments, and consider them from an amateur viewpoint.

Repeaters

We have seen that from one cause or another, the signal fed to the receiving teleprinter must suffer some distortion. Circuits do exist which take the output from the terminal unit, using it to trigger multivibrators operating in pulses of 20ms. The triggering time may be a short sample of the entire signal length, so that a completely “new” signal is produced by the repeater circuit, thereby removing all the distortion. Unfortunately, circuitry of this type is very complicated, it being questionable whether it is worth the trouble and expense involved. However, there is scope for experiment along these lines.

Diversity Reception

Commercial r.t.t.y. links use both frequency and space diversity. With the frequency diversity method, the signal is transmitted on two separate frequencies, received on two receivers, and then gated to reject the poorer of the two before being fed to a single printer. It is doubtful if any amateur would want to use this system on account of the extreme complications, quite apart from the fact that, in this country, simultaneous transmission on two frequencies is not allowed. In any event, the harmonic relationship of the amateur bands would not make this an attractive system since, for long distance working, it is unlikely that two bands would be “in” at the same time.

Space diversity simply means having two aerial systems separated by a short distance,

each being connected to a receiver, tuned to the same frequency. The outputs are again gated to reject the poorer signal, and being fed to a single printer. This could be used by amateurs, but it seems unlikely that it would prove popular to any great extent. Few of us have enough room for one aerial let alone for space diversity arrays.

It is hoped that these articles have unravelled some of the mysteries surrounding r.t.t.y. As with most radio systems, simple equipment will work adequately, but more consistent results can be achieved with

sophisticated equipment, a parallel being that a 10 watt transmitter, together with an 0V1 receiver, will work anywhere in the world on c.w.—yet most amateurs use far more complicated equipment. It is much the same with r.t.t.y.—better equipment will produce good results more regularly. The aims of r.t.t.y. users should be the emission of a stable signal with the EXACT value of frequency shift and, on the receive side, the maximum possible selectivity. If this is achieved, r.t.t.y. will print successfully under conditions which make c.w. difficult, and telephony downright impossible.

A High-Gain V.H.F. Aerial

The Quad Plus

By A. S. Carpenter

In which the author describes an experimental aerial array incorporating both quad and dipole elements

CONSIDERABLE INTEREST HAS BEEN AROUSED recently regarding the use of the Quad aerial for v.h.f. purposes since its gain is comparable, and can sometimes exceed, that of an 8-element Yagi. Furthermore, the Quad has a wider acceptance angle and a broader bandwidth than a Yagi, which is another point in its favour. As it is physically more compact than a Yagi it is well suited to loft or other indoor installation.

Readers unfamiliar with the Quad aerial should study Fig. 1 in which the essentials are shown. It has sides each effectively $\frac{1}{2}\lambda$ long and responds to horizontally polarised signals when the feed point opening is made as shown at (a) and to vertically polarised signals when the opening is made as shown at (b). The two loops, conveniently made into squares constitute, in effect, four half wave elements.*

The aerial, with a parasitic reflector spaced at 0.2λ (see Fig. 1 (a) or (b)), can be made to have a gain of some 8-10db over a dipole, hence its popularity for t.v. and v.h.f. use. Gain can be further increased by adding another loop in front to operate as a director. The loops should be broadside on to the transmitter.

An Improved Aerial

The writer has found that the unique combination of dipoles and Quads depicted in Fig. 2 gives still higher gain, probably

*In some instances the Quad assembly may be tuned by inserting a stub with a movable shorting bar into the reflector at a point corresponding to the outlet of the Quad.—Editor.

because it combines three vertical half wave elements (shown 1, 2, 3 in the diagram) and two quarter wave squares, all broadside to the transmitter.

Cable connections are made to the central point of the aerial and to facilitate accurate matching a $\frac{1}{4}\lambda$ stub is employed. The actual method of connecting coaxial cable is shown in Fig. 3. The point of connection will vary from aerial to aerial but should be approx. 3in from (b). Sliding clips are suggested, as at point (a) the impedance will be high whereas at point (b), there will be zero impedance due to the stub shorting bar (c). Somewhere, therefore from (a) to (b) the correct point can be found to suit the cable.

In areas of low signal strength it is essential to get as much resonant metal “skywards” as possible, especially at Band III frequencies, and a glance at Fig. 2 will reveal that there is as much metal involved here as in a 5-element Yagi. But, perhaps what is more important, is the fact that the “frontage” offered is much greater than that of the Yagi. The importance of supplying “frontage” is borne out by the numbers of twin Yagis (broadside/endfire arrays) erected in deep fringe locations.

To improve the broadside assembly illustrated in Fig. 2 all that becomes necessary is to add parasitic elements at front and back to make it a combination broadside/endfire assembly. The parasitic assembly may be made identical with the active one if desired, though the central vertical element will need neither stub nor opening, remaining as a

continuous length of rod. Perhaps the most effective and simplest method is to use a sheet reflector one wavelength square; although normal Yagi type parasitic elements may be used as reflectors and directors if preferred, these being 5% longer and shorter respectively than the dimension obtained from the formula mentioned later for (a) and (b).

Feed Point Impedance


The aerial, even when parasitic elements

Dimensions

The usual formula for finding the length of a half wave dipole in feet is $\frac{468}{f}$ or

alternatively $\frac{5,616}{f}$ if the length in inches is required. However, experiments would suggest that a better formula for the higher frequencies with an aerial of this kind is
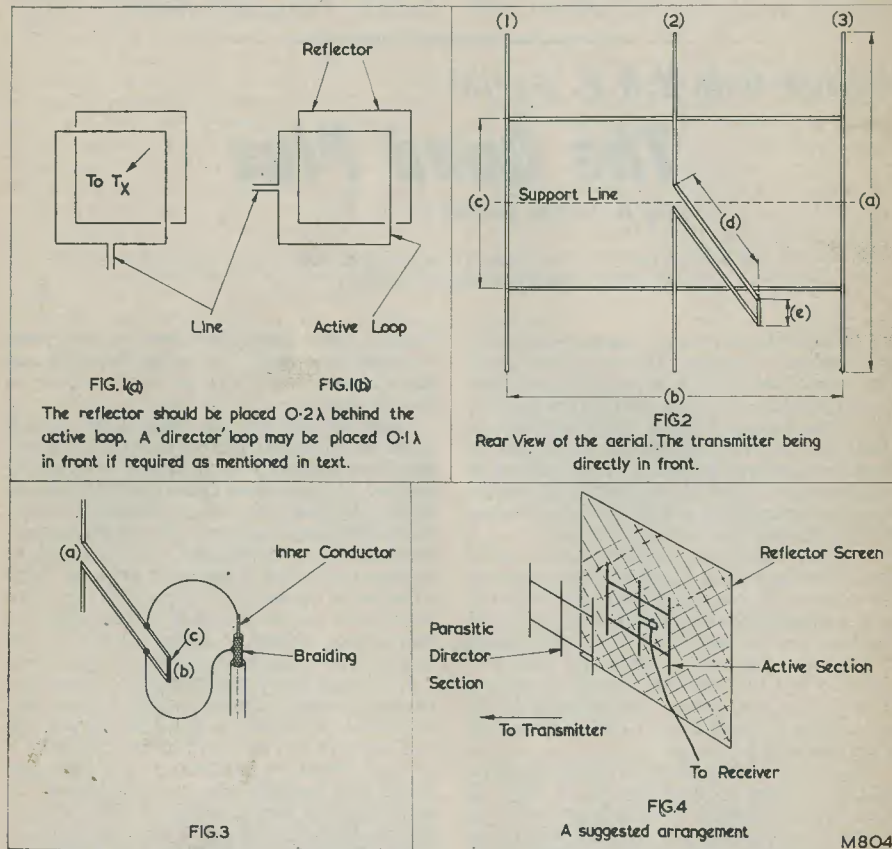
$$\frac{5,256}{f} \text{ ins per half wave.}$$



are added and spaced 0.2λ in front and back, is still of fairly high impedance. Despite this, 300-ohm balanced twin cable can be directly connected without serious mismatch. The matching section proves very useful however when 75-ohm cable is preferred, a good match resulting from connections made at approximately 2-3in from the shorted end as previously mentioned. Both types of cable have been used with the aerial during initial experiments.

To determine the various dimensions in inches, therefore, only two simple calculations need to be made and, referring to Fig. 2,

$$(a) \text{ and } (b) = \frac{5,256}{f} = (\frac{1}{2}\lambda \text{ dimensions})$$

$$(c) \text{ and } (d) = \frac{2,628}{f} = (\frac{1}{4}\lambda \text{ dimensions})$$

$$(e) = 1\frac{1}{2} \text{ in}$$

For f , insert the frequency of the desired transmission, i.e. if Channel 11 ITV is required insert 204.

Conclusion

Mechanical details are not given as interested readers will not be short of ideas. Alloy tubing not less than $\frac{3}{8}$ in diameter should be used and can be bent where necessary by heating slightly. The vertical elements may be of larger diameter than the horizontals if desired, or *vice versa* (although


this might modify the feed point impedance slightly), holes being drilled to permit the smaller ones to slide through the larger and bolts being finally passed through both to secure firmly. Points of low impedance (shown by the broken lines in the diagram) should be used for mounting purposes.

The aerial described is an efficient one and although the writer realises that further improvements are possible (and some keen enthusiasts will already have noted how) he prefers to leave it until actual tests have been made and such improvements confirmed.

TRADE REVIEW . . . Heathkit Balun Coil Set

One of the latest kits in the Heathkit range is of particular interest to the amateur transmitting enthusiast. The Balun Coil Unit fills a need which has long been felt by the amateur radio transmitter in this country, the home construction of this type of aerial tuning equipment presenting great difficulties that are not easy to overcome by those with the usual somewhat limited workshop facilities. The almost universal use of coaxial output facilities on present day amateur transmitters—and the equally common use of balanced fed aerial systems—makes the availability of such a unit even more desirable.

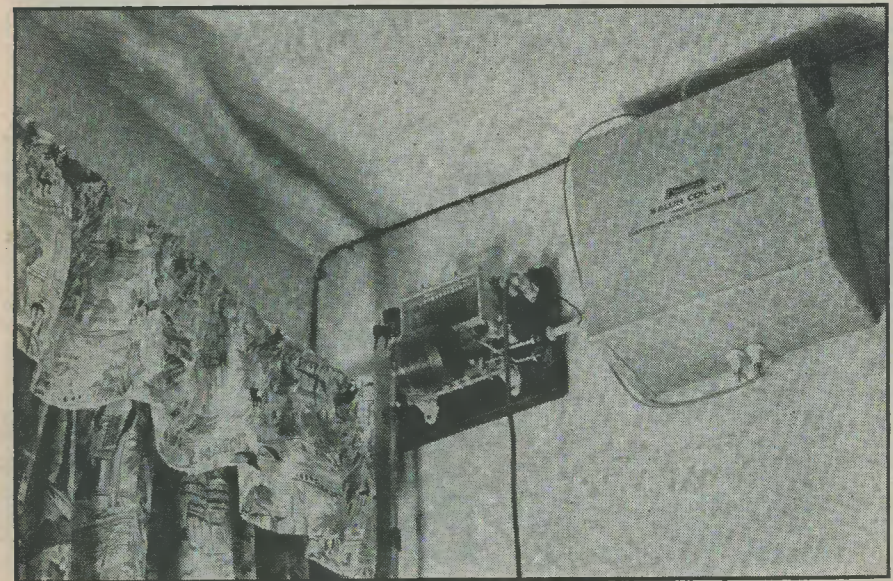The Heathkit Balun Coil Set, Model B-1U, will match unbalanced coaxial lines into balanced feeders of either 70Ω or 300Ω impedance. It can be used without any adjustment over a frequency range of 10 to 80 metres and will handle outputs of up to 250 watts.



The kit supplied complies with the usual Heathkit high standard and can be assembled in a very short time.

As will be seen from the accompanying illustration, it is contained, once constructed, within a small convenient sized case which may be fixed to the shack wall near the aerial system feeders.

Having thoroughly tested one of these units over the last few months, we can thoroughly recommend their use. It is an accessory which will further assist in enabling a quick change from band to band being made with the greatest convenience, disposing as it does, with the tuning of an aerial tuning unit of the more conventional type.

Smith's
of
EDGWARE ROAD

**COMPONENT
PRICE LIST**

Buy direct from the
Designers to ensure
100% results
Guaranteed for 3 years

All enquiries promptly
dealt with

Carriage free in U.K.

H. L. SMITH & CO. LTD

287/9 EDGWARE ROAD
LONDON W2

Telephone
Paddington 5891 & 7595

**THE COOPER-SMITH
"BANTAM" 3 WATT AMPLIFIER
WITH INTEGRATED CONTROL UNIT**

Complete resistor kit	7/9
Complete capacitor kit	23/11
Potentiometers	11/6
ECF80 (inc. P.T.)	16/2
6BQ5... .. (inc. P.T.)	12/4
EZ81 (inc. P.T.)	9/1
Mains Transformer	27/6
Output Transformer	18/9
Valve Holders, B9A (2)	1/6
Valve Holders, with skirt (1)	1/3
Mains plug & socket, Bulgin	3/9
Speaker plug & socket, (3-pin) Cinch	7½d.
Power output plug & socket (4-pin) Cinch	9d.
Input plug & socket coaxial	1/-
Mains selector, fused 2A	1/6
Tag strips, 12-way (pair)	1/6
Wire, sleeving, screws, nuts	1/6
Chassis, punched, bronze	10/-
Control panel, gold hammered	10/-
Control knobs, gold insert (3)	3/9
Instructions	1/6
Total	£8. 5. 7.


Inclusive price for complete kit **£7. 10. 0.**
Laboratory built and tested **£8. 5. 0.**

CLYNE RADIO LTD.



**Specialists in Equipment for
Home Construction** (Send stamp for
complete list)

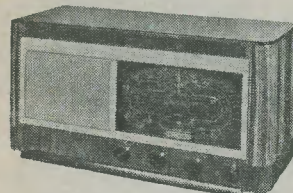FRUSTRATED EXPORT—Not Repeatable!
LONG, MEDIUM AND SHORT WAVES
SUPERHET RECEIVER



Manufactured by McCarthy for export. At present for operation on 6 volts, but conversion details supplied free. Valve line-up: 6K8G, 6K7G, 6Q7G, 6F6G, 6X5G and 6 volt 4-pin non-synchronous vibrator. 8" P.M. speaker, 4 watts output, p.u. socket, ext. i.s. socket, etc. Tone control. Fitted in polished wood cabinet, size 21½" x 10½" x 10½". These cabinets are slightly soiled owing to storage, but each is guaranteed unused, in serviceable condition, tested prior to despatch. Price £5.19.6 only plus P. & P. 7/6, plus 27/6 for A.C. Mains Conversion Components if required. **OUTSTANDING BUY!**



ALL POST ORDERS AND CORRESPONDENCE TO
162 HOLLOWAY ROAD · LONDON N7
NOR 6295/6/7

18 TOTTENHAM COURT RD. LONDON W1
MUS 5929/0095
99 CHEAPSIDE · LONDON EC2
MON 6860

NEW! NEW!
The "Wavemaster"


**7-Transistor 400 mW
Luxury Portable output**

To build yourself! Medium and Long Waves Push-Pull Superhet A.V.C. Perfect Car Radio reception. Size 10" x 6½" x 4½" at base tapering to 4" at top. Very attractive two-tone Vynide covered cabinet with cream and gold printed escutcheon plate, cream and gold knobs, handle and cabinet fittings. Weight complete with long-life 7½ volt battery—4½ lb. Mazda high-grade transistors throughout, high-flux 7" x 4" elliptical speaker, slow motion tuning, co-axial socket at rear for direct connection to car radio aerial. Improved reception by use of seven-section plated telescopic aerial disappearing into cabinet when closed, 34" above cabinet when fully extended. Construction simplified by bakelite chassis board with the following components already mounted: i.f. transformers (3), oscillator coil, trimmer bank, output transformer, interstage transformer, aerial brackets and earth bar. **SPECIAL INCLUSIVE PRICE** for all required components, full assembly instructions—nothing more to buy—is £10.19.6 plus 3/6 P. & P. Alignment service available. Full assembly instructions and individually priced parts list, all of which are available separately 2/6 post free.

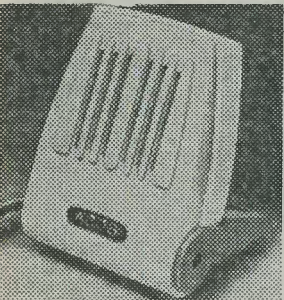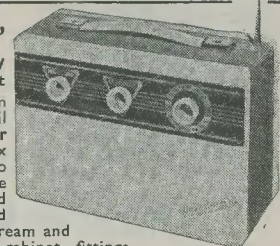


MICROPHONES. Acos Mic. 35 crystal (illustrated) 35/-, 1/3 p. & p. Acos Mic. 25-1 crystal, 25/-, 1/3 p. & p. Carbon hand mic. with switch, 7/6, 1/3 p. & p.

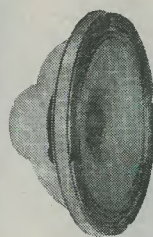**SOLO INSTRUMENT
SOLDERING IRON.** 220/240V., 25W., 3/16" bit, 24/-, plus 8d. p. & p.



LOUDSPEAKERS

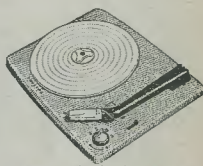Goodman's Axiom 110; (illustrated) 10"; 15Ω; 12,000 gauss; 10W; 40-15,000 c/s; £5.0.0.; 2/- p. & p. Axiom 112; as above, but 16,000 gauss; 12W; £8.10.0. Elac 9" x 5" High Fidelity; 3Ω; 40/3, 1/3 p. & p. 7" x 4" elliptical; 21/6, 1/3 p. & p. Polished walnut baffle 10" x 7½" for 7" x 4" L.S.; 18/6, 1/3 p. & p. T.S.L. Lorenz 4" x 1½" x 1" (the smallest yet); 3Ω; 1W; 120-14,000 c/s; 24/-, 1/3 p. & p.



PHILIPS high fidelity gram unit; 4 speed with pick-up lowering device, £10.10.0. 2/6 p. & p. Stereo head 30/- extra



TRANSISTORS

(6d p. & p.) Yellow/green spot, audio, 6/-, Yellow/red spot, R.F., 12/6. Ediswan XB104, audio, 10/-, Ediswan XA103, I.F., 15/-, Ediswan XA-104, R.F. & osc., 18/-, Mullard OC71, audio, 14/-, Mullard OC45, I.F., 23/-, Mullard OC44, R.F. & osc. 26/-.

TWEETERS

Goodman's Trebax 5k/20XL, 15Ω; 20W; 2,500-20,000 c/s; built-in crossover network and matched attenuator: £7.0.0. 2/6 p. & p. T.S.L. Lorenz LPH65; 2,000-17,000 c/s; 37/8, 1/3 p. & p. Crossover condenser 5/-extra.

KIRKMAN

(Dept. RC) 40 The Broadway
CRAWLEY
SUSSEX

**GET YOUR
AERIALS RIGHT
BEFORE WINTER**

HEADPHONES. H.R. type, 4,000 ohms, very sensitive. Only 12/6 pair. P. & P. 1/6. C.L.R. (low res.) 8/6. P. & P. 1/6.

NATIONAL H.R.O. CRYSTAL FILTER UNITS. 455 kc/s with crystal. Sel. and phasing controls. New boxed. ONLY 19/6. P. & P. 1/6.

MULTI-WAY CABLE. 3/8" diam. 7 colour coded wires. Ideal for mobile or inter-chassis connection. Any lengths cut, 1/3 per yard. P. & P. 1/6 min.

10-WAY CABLE (5 pairs). Screened and plastic covered. Any length cut, 2/- per yard. P. & P. 1/6 min. 7-way (unscreened), 1/3 yard.

ABSORPTION WAVEMETERS. 3.00 to 35.00 Mc/s in 3 switched bands, marked on scale. Complete with indicator bulb. A MUST for any ham shack. ONLY 19/6. Post free.

AERIAL EQUIPMENT

**SPECIAL OFFER
ROTARY CONVERTERS**

6V input, 250mA output. Only 5½" x 3" x 3". 17/6 each. P. & P. 3/-.

12V MINIATURE ROTARIES

Only 4½" x 2½" overall. Output 360V, 30mA or 310V, 70mA. NEW LOW PRICE 12/6 each or 22/6 for 2. P. & P. 1/6.

AR88 POWER TRANSFORMERS

Genuine R.C.A., few only. £2 each, carr. paid.

RELAYS (SEALED) 12 VOLT 1½" x 1" x 2" d.p.s.t. contacts. Beautiful job. ONLY 5/- each. P. & P. 9d.

AMERICAN "SIGNAL" MORSE KEYS Type M 100 with switch. This excellent, lightweight, fast key is currently priced at \$6.85 in U.S.A. and is offered at only 12/6 plus 1/6 P. & P.

RACK MOUNTING PANELS. 9" x 5½", 7", 8½" or 10½" black crackle finish, 5/9, 6/6, 7/6 and 9/- respectively, postage and packing 2/-.

COPPER WIRE. 14g. h.d.: 140' 17/-; 70' 8/6; 7/25 stranded: 140' 10/-; 70' 5/- plus 2/- P. & P.
RIBBED GLASS INSULATORS. 3" 1/6 each or 6 for 7/6. P. & P. 1/6.

TWIN FEED. 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K358 Telcon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.

SUPER AERIAL CABLE 1/8 per yard. P. & P. 1/6.

CERAMIC FEEDER SPREADERS. Type F.S. 6" 9d. each or 8/- doz. P. & P. 2/-.

CERAMIC "T" PIECES. Type AT for centre of dipoles, 1/5 each or 3 for 4/- P. & P. 1/6.

MOSLEY TRI-BAND BEAMS T33, JR, 3 EL £24.15.0
TA32 JR, 2 EL £17.10.0
V3 JR, Vertical 3 Band £7.10.0

PLACE YOUR ORDER EARLY
NEW MOSLEY POWER BEAMS. Write for details. 300 watt, 50 ohm COAX, 1½" dia., very low loss, 1/6 yard or 20 yards 27/6. P. & P. 1/9.

GHAS H. YOUNG LTD (Dept. R)
110 DALE END BIRMINGHAM 4 (Tel. all departments) CEN 1635



BRITISH-MADE DYNAMIC AND RIBBON MICROPHONES

*a model for every
requirement*

For whatever purpose a microphone is required—for studio recording, for P.A. indoors or out, for broadcasting, for tele-communications, there's a LUSTRAPHONE MICROPHONE designed specially for the job. With a range of dynamic and ribbon types (including models for stereo) starting in price from 67/6 for the world-famous "Lustrette" to twin ribbon stereo models for highest professional use, you are certain to find just the type of instrument you want.

LUSTRAPHONE MICROPHONES are completely British and have behind them the advantages of very many years of continuous experience in microphone design and development. You will see them again and again in TV and theatrical use and often you will find the recording that sounds better, the transmission that is clearer owes its quality to LUSTRAPHONE. These microphones are finely designed in appearance too, combining modern line with elegance that will not quickly outdate.

LUSTRAPHONE MICROPHONES are sold by leading stockists everywhere. Full descriptive literature on request.

LUSTRAPHONE LTD
ST. GEORGE'S WORKS REGENT PARK RD
LONDON NW1
Telephone PRImrose 8844

SMITH'S of Edgware Road

1910 GOLDEN JUBILEE YEAR 1960

BLANK CHASSIS

Precision made in our own works from commercial quality half-hard aluminium of 16 s.w.g. (1/16") thickness, these chassis go all over the world (and off it—in rockets!). Same day service for ANY SIZE, to nearest 1/16" and up to 17" of straightforward two, three or four-sided chassis. Orders for specials dealt with promptly if sent with clear instructions.

SOLDERED CORNERS. While these chassis, owing to their thickness, hardness and efficient folding, will carry components of considerable weight and normally require no corner strengthening, we can do this, if required, by a special soldering technique at 6d. extra for each corner.

FLANGES. 1/4", 3/8" or 1/2" flanges (inside or outside) 6d. extra for each bend.

PRICE GUIDE (normal chassis only)

Work out total area of material required, including waste, and refer to table below:

48 sq. in.	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata	
	Post 1/3		Post 1/6		Post 1/9

Discount for quantities. Trade enquiries invited. Spray finish arranged for quantities of 25 or over.

PANELS. The same material can be supplied for panels, screens, etc. Any size up to 3 ft. at 4/6 sq. ft. (sq. in. x 3/4). Post, up to 72 sq. in. 9d., 108 sq. in. 1/3, 144 sq. in. 1/6, 432 sq. in. 1/9, 576 sq. in. 2/-.

287/289 EDGWARE ROAD LONDON W2
Telephone PAD 5891/7595

HI-FI NEWS

The Magazine for ...

... The Sound Enthusiast

● HI-FI NEWS carries regular Constructors' features, reviews of all high fidelity and good quality audio equipment, and articles for both beginners and experienced readers. It is well produced and illustrated. We think you will like it—but sample it at our expense. Send 6d. for a specimen copy. Annual subscriptions are 27/6, or 30/- with annual index.

Price 2/- Monthly

HI-FI NEWS

99 MORTIMER ST LONDON W1

PORTABLE TRANSISTOR RECORD PLAYER


—BARGAIN OFFER ★ 6V operation (2 E/R Type 800 Batts. 1/4 each.)



- ★ 1 watt Push-Pull Output.
- ★ 4 Latest G.E.C. Transistors.
- ★ Garrard Fidelity Gram. Unit.

Size 11" x 8 3/4" x 5".

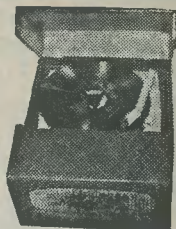COLOUR: 2 Tone Red/White with Polka Dot relief. Alternative Blue/Fawn with Polka Dot relief.



CABINET incl. Motor Board and 7" x 4" Speaker £1.19.6. Carr. 2/6.

COMPLETE RECORD PLAYER KIT
Bargain Price £7.19.6 Carr. 4/6.

GARRARD BA1 Gram Unit. £2.19.6. Carr. 2/6

SEND FOR FULL DETAILS NOW
LIMITED BARGAIN OFFER

RECORD PLAYER BARGAINS

All brand new latest 4-speed Models—fully guar.
Single Players—B.S.R. (TU9) with "FUL-FI" P.U. 90/- Garrard 4 S.P. with GC8 Crystall £6.17.6. Garrard TA Mk. 2 with Plug-in GC8 Head £7.19.6. Garrard 4HF Transcription Unit £18. Carr. 3/6.
Auto Changers—B.S.R. (UAB) £6.19.6. UAB Stereo £7.19.6. UA14 £7.19.6. Collaro Conquest £7.19.6. Garrard RC121/4D Mk. 2 2 9/8 gns. Carr. 4/6.

SPECIAL—NEW RELEASE

Garrard RC210, New 4-speed Autochanger Model with all the latest features and GC8 Plug-in Head, wired for Stereo. Bargain 10 gns. Carr. 4/6.
EMI 4-speed Single Player with Auto Stop/Start Dual Turnover Cartridge for Stereo and Monoaural L.P. and 78—Bargain Buy at £6.19.6. Carr. 3/6.

THE TOURIST PORTABLE

4 valve. Med. & L.W., lightweight battery Radio. Size only 8" x 5 1/2" x 4". Weight 3 1/2 lb with battery B114. Complete receiver component kit ... 57/6 P. & P. 1/6 Set 4 miniature valves (96 series) ... 35/- P. & P. 9d. 5" Speaker and O/put Trans. ... 21/- P. & P. 1/6 Cabinet, Dial and Knobs, etc. ... 22/6 P. & P. 2/- Latest superhet circuitry, dual ferrite aerial, delayed AVC and A.F. Neg. feedback. A remarkable little receiver with lots of punch and quality results.

Complete Kit—BARGAIN £6.10.0 post free

MAINS UNIT. Size as B114 Battery. Complete Kit 45/- P. & P. 1/6 Send for booklet now, 1/6 post free

RECORD PLAYER CABINETS

Contemporary styled, rexine covered cabinet in two-tone wine and cream, or mottled red with white polka dot. Size 18 1/2" x 13 1/2" x ht. 8 1/2", fitted with all accessories, including baffle board and anodised metal fret. Space available for all modern amplifiers and autochangers, as above, etc. Uncut record player mounting board 14" x 13" supplied.
Cabinet Price £3.3.0. Carr. and ins. 3/6.

2-VALVE 2-WATT AMPLIFIER with vol. and tone controls. Neg. feedback. A.C. 200/250V. Complete, ready wired to fit above cabinet. £2.17.6. P. & P. 1/-

6" Speaker and matching trans. 22/- P. & P. 1/6

VALVES—New Reduced Prices—All Guaranteed

1T4	6/-	DK96	9/-	ECL82	10/6	EZ80/81	7/6
1R5, 1S5	7/6	DL96	9/-	EF80	8/-	MU14	9/-
3S4, 3V4	7/6	EABC80	8/6	EF86	12/6	PCC84	9/6
5Z4	9/-	EF89	9/-	EF91	5/-	PCF80	9/6
DAF96	9/-	ECC85	11/6	EL84	8/6	PCL83	12/6
DF96	9/-	ECL80	10/6	EY51	9/6	PL81	12/6
				EY86	10/-	U25	12/6

TRANSISTORS—BVA 1st Grade—ex Mfrs. Mazda XA102, 16/6; XA101, 14/6; XC101, 10/6; OC70, 9/6; XB102, 10/-; XA103, 15/-; XA104, 18/-; OA70, 2/9. Hours 9 a.m.—6 p.m., 1 p.m. Wed.

RADIO COMPONENT SPECIALISTS

70 Brigstock Road Thornton Heath Surrey Telephone THO 2188
Est. 1946 Terms C.W.O. or C.O.D. Post and packing up to 1/6, 7d., 1lb. 1/1, 3lb. 1/6, 5lb. 2/-, 10lb. 2/9.

CRT HTR. ISOLATION TRANSFORMERS

New improved types, low capacity, small size and tag terminated, a.c. 200/250V. Secondaries nil, +25%, +50% BOOST for 2V, 4V, 6.3V, 10.5V, 12V or 13V tubes. Each type 12/6 each. P. & P. 1/6.

JASON FM TUNER UNIT KITS (87-105 Mc/s)

Tuner Coil Set, IFs and Ratio Detector, etc., 26/- Standard Model (FMT1)—as previously extensively advertised. Complete Kit—5 gns. Post free. Set of 3 spec. valves now only 20/-.

Model FMT2—attractively presented shelf mounting unit in enclosed metal cabinet with built-in power supply. Complete Kit £7. P. & P. 3/6. Set of 5 spec. valves, 37/6.

Latest Model—JTV2—Switched Band 1—2—3 AM/FM Unit with AFC. Kit £12.19.6. P. & P. 2/6.

New Jason Comprehensive FM Handbook 2/6, post free. 48-hr. Alignment Service, 7/6. P. & P. 2/6.

CONDENSERS—Silver Mica. All pref. values, 2pF to 1,000pF, 6d. each. Ditto ceramics, 9d. each. Tubulars 450V T.C.C., etc., 0.001—0.01µF and 0.1/350V, 9d. each. 0.02—1/500V, 1/- each. 0.25 Hunts 1/6, 0.5 T.C.C., 1/9, 0.001 6kV, 5/6, 0.001kV, 9/6.

RESISTORS—Full range 10 ohms—10 megohms 20p, 1/4W and 1/2W 3d., 1/2W 5d. (Midjet type modern rating), 1W 6d., 2W 9d. 10% Hi-Stub. 1/2W 5d., 1/4W 7d., 5% 1/2W 9d. 1% HI-STAB, 1/2W 1/6 (10—100 ohms 2/-).

LOUDSPEAKERS—P.M. 3 ohm, 2 1/2" Plessey 17/6, 3 1/2" Goodmans 18/6, 5" R. & A. 17/6, 6" Celes. 18/6, 7" x 4" Goodmans 18/6, 8" Rola 20/-, 10" R. & A. 25/-, 12" Plessey 30/-, etc.

SPEAKER FRET—Expanded bronze anodised metal 8" x 8" 2/3, 12" x 8" 3/-, 12" x 12" 4/6, 12" x 15" 6/-, 24" x 12" 9/-, etc.

TYGAN FRET (contemporary pattern)—12" x 12" 2/-, 12" x 18" 3/-, 12" x 24" 4/-, etc.


COAX 80-OHM CABLE. Now only 6d. per yd. High grade low loss. Aeraxial air-spaced Polythene Coax—famous manufacturer—standard 1/4" diameter Bargain prices. 20 yds. 9/-, P. & P. 1/6; 40 yds. 17/6, P. & P. 2/-; 60 yds. 25/-, P. & P. 3/-. Special lengths. Coax Plugs 1/-, Coax Sockets 1/-, Couplers 1/3. Cable end sockets 1/6. Outlet Box 4/6.

VOLUME CONTROLS—5k—2 Megohm. ALL LONG SPINDLES, MIDGET TYPE, 1 1/2" diam. Guar. 1 yr. LOG OR LIN. ratios less sw, 3/-, D.P. sw. 4/6. Twin gang stereo controls log. or linear less sw., 6/6. With d.p. sw. 8/-.

★★ NO EXTERNAL AERIAL OR EARTH—NO REACTION CONTROLS ★★
—EASY AS A B C TO BUILD AND A THRILL TO USE—

MAJOR-2 (Two-Transistor Pocket Radio)

IDEAL FOR BEGINNERS

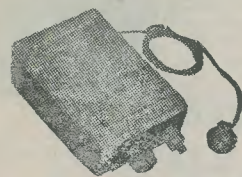


All components sold separately

- ★ 4-stage reflex
- ★ Medium wave; tunable
- ★ Very sensitive
- ★ No aerial or earth
- ★ Complete layout
- ★ Over 6 months on one battery
- ★ 4½ x 3 x 1½"
- ★ Weight only 4 oz.
- ★ Personal phone included.

TOTAL COST 69/6 P.P. 1/6 NEW BOOKLET FREE
RECEPTION GUARANTEED ANYWHERE!

MAJOR-3 (Three-Transistor Pocket Radio)

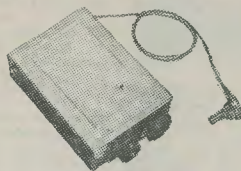

(As described in R.C., Sept. '59)

- ★ 5-stage Reflex Circuit
- ★ No Aerial or Earth
- ★ Miniature Volume Control
- ★ 3 Ediswan Transistors.
- ★ Medium Wave Tuning
- ★ Size 4½ x 3 x 1½"
- ★ Personal phone included.

TOTAL COST 87/6 P.P. 1/6 NEW BOOKLET FREE
FANTASTIC OUTPUT, TERRIFIC RECEPTION. GUARANTEED ANYWHERE

★★ NOT TOYS BUT REAL WORKING RADIOS! ★★

TRANSISTORS — NEW PRICES!

BRAND NEW AND GUARANTEED

XB102, 7/6; XA104, 15/-; XA103, 12/6; XC101 matched pairs, 25/- pr.; XA131, 35/-; OC44, 19/6; OC45, 18/6; OC71, 10/-; OC72 pairs, 30/- pr.; OC170, 35/-; V15/10P, 15/-; V15/20P, 25/-; XC141, 30/-; OC76, 15/-; SBO78, 7/6; SB305, 10/-; Red Spot, 3/6; White Spot, 5/-;
SEND FOR LIST OF 50 TYPES WITH DATA AND PRICES

"STEREO 3-D"

New high-gain circuit with full tone, balance and volume controls. Can be used with all types of records as well as stereo.

- ★ 2 WATTS PEAK PER CHANNEL. BUILT AND TESTED £5.7.6.
- ★ ECC83: 2-ECL82 VALVES.
- ★ MAINS 110/250V A.C. P.P. 2/-.

Complete with speaker sockets, calibrated dials, etc.

- ★ ★ Collaro 4-speed stereo auto-changer, ideal for use with above amplifier, £7.10.0. P.P. 3/6.
- ★ ★ 9" x 6" large magnet Elac speaker, for use with STEREO 3-D. 37/- pair. P.P. 1/6.

**ALL TRANSISTOR BABY ALARM
THE "BABY-SITTER"**



- ★ 100% Safe—Guaranteed
- ★ Fully Portable
- ★ No Mains—Battery Operated
- ★ Can be used over ANY Distance

USE IT AT HOME, TAKE IT ON HOLIDAY

Every Sound can be heard on large 5 inch Speaker

COMPLETELY ASSEMBLED WITH BATTERY £5.10.0 P.P. 2/6

— BE WITH YOUR CHILDREN ALL THE TIME —

(Illustrated leaflet free on request)

Our Specialities Transistors, Quartz Crystals
Valves, Miniature Components

Trade enquiries invited. Catalogues free. Compare our prices.

WE ARE ABLE TO SUPPLY MOST OF THE COMPONENTS USED ON CIRCUITS PUBLISHED IN THIS AND OTHER MAGAZINES AND BOOKLETS. WHERE THE EXACT ITEM IS NOT AVAILABLE WE CAN RECOMMEND A SUITABLE SUBSTITUTE WHERE POSSIBLE.

HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

Opposite Edgware Road Tube Station. PADddington 1008/9 OPEN MONDAY to SAT. 9-6, THURS. 1 o'clock

"CONTINENTAL-6" COMBINED PORTABLE/CAR RADIO

★★ EQUALLY SENSITIVE ON MEDIUM AND LONG WAVE BANDS ★★

SPECIFICATION

- 425mW Push-Pull Output
- 6 "Top-Grade" Ediswan Transistors
- New Type Printed Circuit with all Components Marked
- Full Medium and Long Wave Tuning
- High "Q" Internal Ferrite Aerial
- Car Radio Adaption Aid AVC
- Slow Motion Fingertip Tuning
- "Hi-Fi" Quality Speaker
- Size 9½" x 7½" x 3½". Weight 4½ lb.

ALL COMPONENTS AVAILABLE SEPARATELY
CALL FOR DEMONSTRATION

All the Continental and Local Stations at Your Fingertips

Wherever you are
"First Class in every way"



- ★ STEP BY STEP FULLY ILLUSTRATED INSTRUCTIONS
- ★ ALL COMPONENTS GUARANTEED

Total Cost of all Components
£11.10.0 P.P. 3/6
including Cabinet, Battery Transistors, Car Radio, AVC and all necessary items.

- ★ SIMPLE TO CONSTRUCT
- ★ NO TECHNICAL KNOWLEDGE REQUIRED
- ★ WORTH DOUBLE WHEN BUILT
- ★ EXCELLENT RESULTS ANYWHERE
- ★ DESCRIPTIVE LEAFLET FREE ON REQUEST

Continental Transistors

Direct Equivalent OC44 15/-
Direct Equivalent OC45 12/6
BRAND NEW GUARANTEED

Crystal Microphones

ACOS 39-1 Stick Microphone with screened cable and Stand (List 5 gns.). 39/6. P.P. 1/6.
ACOS 40 Desk Microphone with screened cable and built-in stand (List 50/-). 25/- P.P. 1/6.
ACOS 45 Hand Microphone with screened lead, very sensitive 39/6. P.P. 1/6.

**Special Offer of
MERCURY
BATTERIES**

1.3 volts, 500mA/H
Size ¾" diam. x ¾" length.
ONLY 1/3 ea. P.P. 3d. ea.
or 12/- dozen. P.P. 9d.
FOR ALL TRANSISTOR WORK

Telescopic Chrome Aerials

7-Sections, 3' 6" open; 6" closed. Ideal for Portable Receivers. Walkie-talkies, Radio Control, etc.

With Clips 12/6. P.P. 1/-
64" version with clips 17/6. P.P. 1/-.

Crystal Microphone Inserts

Latest ACOS 43-1, 2½" 12/6. P.P. 6d.
¾" square (ex-units) 3/6 ea. P.P. 6d.
ACOS 4½" 9/6. P.P. 6d.
Also ¾" by ½" 7/6. P.P. 6d.

**RED-SPOT
TRANSISTORS
3/6 each**

**WHITE-SPOT
5/- each**

NEW FREE LIST
ON REQUEST
Fully Guaranteed

POCKET MULTI-TESTERS

— BRAND NEW —

MODEL A-10 (500 Micro-amp. Movement). D.C. (2k per volt) 0/10/50/250/500/1,000 v. A.C. (2k per volt) 0/10/50/250/500/1,000 v. D.C. current 0/0.5/25/250 mA. Resistance: 0/10K/1 Meg. Size 5½" x 3½" x 1½". Weight 17 oz. Price £4.17.6. P.P. 1/6 inclusive of Test Prods, Instruction Book and Batteries.

MODEL B-20 (100 Micro-amp. Movement). D.C. 10,000 ohms per volt) 0/0.5/2.5 volts. D.C. (4,000 ohms per volt) 0/10/50/250/500/1,000 v. A.C. (4,000 ohms per volt) 0/10/50/250/1,000 v. D.C. Current, 0/0.1/2.5/25/250 mA. Size 5½" x 3½" x 2½". Weight 24 oz. Price £6.10.0. P.P. 1/6, inclusive of Test Prods, Instruction Book and Batteries. FULLY GUARANTEED

**"THE HOME
CONSTRUCTORS'
BEST FRIEND"**

EVERY DO-IT-YOURSELF ENTHUSIAST OR SERVICE ENGINEER CAN SAVE HOURS OF TIME USING ONE OF THESE METERS

EASY TO USE —
CHEAP AT THE PRICE

CRYSTAL CONTROLLED OSCILLATOR

3-12 Mc/s Spot Market Unit. Uses SB305 Transistor. Ideal for short wave calibrator, etc. All components (less crystal). 22/6. P.P. 1/-.

3-TRANSISTOR HEARING AID

High-gain circuit with built-in crystal microphone and battery. Includes miniature earphone. 3-Transformers. Size 3" x 2" x ¾". All components, 89/6. P.P. 1/-.

2 WATT OUTPUT TRANSISTOR AMPLIFIER

For connection to any battery portable to give up to 2W output. Works from 12V battery. Ideal for car radio use. Size 4½" x 3" x 2½", uses power transistor. All components (less speaker) 52/6. P.P. 2/-.
Ideal for use with Continental 6, etc.

TRANSISTOR TRANSMITTER

1.8 to Mc/s coverage. 3 transistors unit size 4½" x 3" x 1½". Range of 3-section rod aerial up to 300 yards. Includes built-in microphone, battery and 3-section rod aerial. All components, 57/6. P.P. 1/6.

SQUARE WAVE GENERATOR

2-Transistor. Chassis size 2" x 1½". 15V supply. All components, 20/- P.P. 1/-.

RF, IF AND AUDIO SIGNAL TRACER

Ideal signal peaker or quick fault-finder for receivers, amplifiers, etc. Size 4½" x 3" x 1½". All components, with 'phones, 37/6. P.P. 1/6. Less 'phones, 32/6. P.P. 1/6

250mW PUSH-PULL OUTPUT AMPLIFIER

For use with any 2, 3 or 4 transistor, earpiece or head-phone radio to give room-filling volume on 3" speaker. All components including 2 Ediswan transistors, speaker, battery, special input socket to take earpiece plug, cabinet, etc., 59/6. P.P. 1/6.
Ideal for use with Major-2 or Major-3.

RF AND IF SIGNAL TRACER

Ideal for tuning or fault finding on Medium and short wave receivers. All components 25/- P.P. 1/-.

Get these **FREE** CIRCUITS & WIRING DIAGRAMS

T.R.F. Circuits
Battery Circuits
Portable Circuits
S'het Circuits, etc.

Circuits are changed from time to time

Postage 1/- (Stamps)

OSMOR COILS are regularly used and recommended by designers writing in *Practical Wireless*, *Wireless World* and *The Radio Constructor*. Why not follow the experts?

"Q COILS" • POTTED COILS • FM COILS
All ranges

SPEAKER CROSS-OVER COILS

TAPE COILS • ROD AERIALS

SUB MINIATURE COILS

COILS and I.F.s for Transistor Circuits • MIDGET I.F. TRANS With ferrite cores

OSMOR


418 Brighton Road
South Croydon

Telephone CRO 5148/9

JACKSON

the big name in PRECISION components

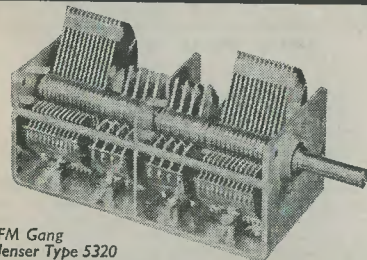Precision built radio components are an important contribution to the radio and communications industry. Be sure of the best and buy Jackson Precision Built Components



AM/FM Gang
Condenser Type 5320

JACKSON BROS. (LONDON) LTD
KINGSWAY, WADDON, SURREY

Telephone: Croydon 2754-5
Telegrams: Walfico, Souphone, London

12" Speaker and 5" Tweeter with coupling condenser by leading maker, 75/-. Less than half list price. Mains Transformers. Input 200/250V. Output tapped 3 to 30V 2A or 5, 11, 17V 5A. Each 24/6. F.W. Metal Rectifiers. 12/6 volt 1A, 7/6; 3A, 13/-; 4A, 17/6; 6A, 27/6; 24V 2A, 23/6. Mains Transformer and Rectifier, giving 12V 1A d.c. output, 19/6; 30V 2A, 33/6. Relays. We hold large stocks. Any contact combination and operating coil voltage supplied from 3/-. Special Offer. 12V relays with 2- or 4-make contacts, 6/-; 2 for 11/6; 3 for 16/6; 4 for 21/-.

Key Switches from 3/-. Toggle Switches d.p.d.t., 3/6. Micro Switches, M. & B., 5/6.

Nickel Nife Batteries. 1.2V 2.5A. Size 3" x 2 3/4" x 1". Practically everlasting, 6/-; or 3 for 16/-; 4, 21/-.

Army Morse Keys, 3/6, 6/- and 8/6. Lightweight Soldering Irons, 17/9.

H.S. Twist Drills. Set 7, 1/8", 1/4", 4/-; also Full Size in Plastic Wallet, 6/-. Set of 13, 9/6 and 17, 15/6, 1/8" to 3/8". Tubular Hacksaws (Eclipse Type), 11/9.

5 1/2" Side Cutters, 5/6. 5" Plated Round Nose Tapered Pliers, 5/-. Pocket Neon Testers with retractable Screwdriver, 5/6. 7" Flat Nosed Tapered Pliers, 8/6.

New 12" Speakers. 3 ohm, 32/6. Paxolin Panels, 12" x 6" x 1/8", 3/6.

Paxolin Tubing, 1 1/2" x 1/8" x 72", 17/6. Ideal for masts. Studio "O" Cartridges, 21/-.

American P.V.C. Tape. Finest Quality. 800ft reels, 19/-.

12V Miniature Relays. 1 1/2" x 1 1/2" x 1". Wgt. 1 1/2oz. S.P.C.O., 9/3. S.P.C.O. and 3m, 10/6.

All items post paid, new and guaranteed

LISTS SENT ON REQUEST

Post orders only to

THE RADIO & ELECTRICAL MART

c/o G.P.O. TUNBRIDGE WELLS KENT

REPANCO

Easy-to-build Receivers

	Envelopes
R.E.P. One Valve Radio	9d.
The Hiwayman. A 4 valve portable Radio	1/6
F.M. Tuner Unit. 5 valves plus tuning indicator	1/6
Twinette. A 2 transistor portable Radio ...	1/3
Three Dee. 3 transistor radio	9d.
Mini-7. 7 transistor pocket radio	1/6
Mini-3. 3 transistor pocket radio	1/3
Transeven. 7 transistor portable. (Preset stations)	1/6
Major-7. 7 transistor portable (Tunable) ...	1/6
Transistor Car Radio Receiver	2/-
Transistor Amplifier and Feeder Unit circuits	1/6

Please add towards postage

For details of our components send 6d. in stamps for 1960 catalogue

Radio Experimental Products Ltd

33 Much Park Street Coventry

Telephone 27114

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-. Trade advertisements will be accepted at 9d. per word, minimum charge 6/-. If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

PRIVATE

QUICK SALE. Experimenter's Outfit. M.C. Speakers; Meters, Weston & Ferranti, etc.; Power Transformers and chokes from 50s.; Avo Minor 20s.; Tatlock Mirror galvanometer; Cyldon Condensers; Valves pre-war, 10s. for 36. Write to: H.A.S., 43 Ferncroft Avenue, London, N.W.3.

FOR SALE. Newnes *Radio and Television Servicing*. Latest edition. Mint condition. Best offer secures. —47 Hotblack Road, Norwich, Norfolk.

FOR SALE. T.S.L. FM Tuner unit with cabinet and suitable aerial £10. Buyer collects. Recently aligned and tested. Perfect condition.—Box No. F112.

FOR SALE. Philips type 1800 projector unit with new c.r.t. and one spare. 50s. or multimeter.—Brassington, 64 Montague Tibbles, London, N.W.5.

FOR SALE. BC342 Communication receiver £10; Avo valve tester and manual £10; Long-medium coil pack 10s.; Acos Mic. 33-2 10s.—Bigwood, 39 Derwent Road, Whitton, Middx.

"FIVE BOB" SALE. R1355 working, RF25, tube unit with VCR97, radar units, valve parcels, etc. All 5s. each (plus carriage). Lists.—Box No. F114.

FOR SALE. Avo valve tester, 3 panels, manual adaptors £10; Collaro tape deck, new, £14; Avo multimeter £7 10s.; offer for Avo 7.—Mr. Piitts, 7 Chedworth House, Clapton, London, E.5.

TRADE

LEARN RADIO AND ELECTRONICS the NEW Practical way. Very latest system of experimenting with and building radio apparatus—"as you learn". FREE Brochure from: Dept. RC10 Radiostructor, 40 Russel Street, Reading, Berks.

FREE FROM THE I.P.R.E. Syllabus of famous radio and t.v. courses. Membership conditions booklet, 1s. Sample copy *The Practical Radio Engineer*, 2s. post free.—Secretary, 20 Fairfield Road, London, N.8.

MORSE CODE TRAINING. Special courses for Beginners. Full details from (Dept. R.C.) Candler System Company, 52 Abingdon Road, London, W.8.

PANL, recognised for many years as the unique one-coat black crackle finish. Brush applied, no baking. Available by post in eighth pint cans at 3s. 9d. from G. A. Miller, 255 Nether Street, London, N.3.

"WORLD RADIO HANDBOOK." Copies available, 1960 Edition, 16s. 6d., inc. post and packing from ISWL, 12 Gladwell Road, London, N.8.

1,000 INTERESTING ITEMS. List 3d.—Rogers, 31/33 Nelson Street, Southport, Lancs.

CATALOGUE No. 14. Government surplus and model radio control, over 500 illustrated items, 2s. (refunded on purchase), p.p. 6d.—Arthur Sallis Radio Control Ltd., 93 (E) North Road, Brighton.

WOULD YOU LIKE a free supply of Recording Tape every six months? If so, write to The High Fidelity Company, 18 Melville Road, Birmingham 16, for particulars.

continued on page 159

EDDY'S (NOTTM) LTD

172 Alfreton Road Nottingham Dept. RC

CAR RADIO KITS. 7 Transistor Long & Medium 2 watts output. R.F. stage and Auto Gain Control. (6 or 12 volts please state). Supplied with full instructions at 10 1/2 gns. Size 7 1/2" x 7 1/2" x 2 1/2". Speaker extra 17/11 if required. Post and Packing 5/-.

GERMANIUM DIODES 8d. each, 7/- doz. Post 6d.

THROAT MIKES 1/- . Post 6d. Could be used for electrifying musical instruments.

HEADPHONE CORDS. High Quality 6 ft. lengths 1/11 per pair. Post 6d.

TRANSISTORS Red Spot 3/9. White Spot 4/9. Post and Packing 6d.

DIMMER SWITCHES. Ideal for train speed regulators 1/11. Post 9d.

VIBRATORS 12 volt 4 pin, 4/11. Post 1/3.

NIFE ACCUMULATORS. Size 3" x 2 1/2" x 7/8" 7 amp hrs. 1.25 volts weight 13 ozs, 1/11 ea. Post and Packing 1/6 one only, add 9d. each cell.

VARIABLE CONDENSERS. .0005 small twin gang. Built in slowmotion drive 8/11. Post 1/6.

TUMBLER SWITCHES 250 volt 5 amp 1/- each. Post and Packing 6d.

GUITAR PICK-UPS. Super hi-fi non acoustical universal fitting. High Output. Complete with lead and plug. Full and easy instructions, 49/11. Post and Packing 2/6.

JACK PLUGS. Standard, 1/11. Post 9d.

HAND MIKES. Carbon, 3/11. Post 1/3.

SPEAKER GOLD GRILLE. 6 1/2" x 4", 1/- . Post 6d.

LUXEMBOURG EXPANDING AERIALS. Compact and easy to fit. No technical knowledge required. Greatly improves reception. 3/11. Post 9d.


ALL ABOVE ARE NEW AND GUARANTEED

NEW OR SURPLUS VALVES

Guaranteed and Tested by Return Post

1D5	7/6	6V6G	4/11	DK91	5/6	EL41	7/3
1L4	3/6	6V6GT	5/11	DK92	8/-	EL84	6/6
1R5	5/6	6V6M	8/6	DK96	6/11	EL85	10/6
1S5	4/9	12K7	5/3	DL96	6/11	EY51	7/11
1T4	3/11	12Q7	5/3	DM70	7/6	EY86	7/9
3Q4	7/-	25A6G	8/-	EB41	7/-	EZ40	6/3
3S4	5/11	25Z4G	7/3	EB91	3/9	EZ41	7/-
3V4	6/9	25L6GT	6/9	ECC81	5/3	EZ80	6/-
5Y3GT	5/9	35L6GT	9/-	ECC82	6/-	EZ81	6/9
6A7	10/-	35W4	6/9	ECC83	6/6	GT1C	6/11
6AG5	4/-	90AV	3/6	ECC84	8/3	P61	2/6
6B8G	2/11	95A	3/6	ECC85	8/-	PCC84	7/3
6BA6	5/11	95S	3/6	ECF80	9/-	PCF80	7/-
6B16	5/11	956	3/6	ECF82	9/-	PCL83	10/6
6C4	4/-	9001	3/11	ECL80	7/6	PCL82	7/6
6C6	4/9	9004	3/11	ECL82	10/-	PL36	10/9
6K7G	1/11	9006	3/11	EF36	3/-	PL81	8/9
6K8G	5/3	AZ31	8/9	EF37	7/6	PL82	7/-
6SN7GT	4/3	CL33	12/6	EF50	1/9	PL83	7/-
6SA7M	5/9	DAF91	4/9	EF80	5/6	PY31	8/3
6SG7M	4/9	DAF96	6/11	EF86	9/9	PY80	7/-
6SJ7M	5/11	DF91	3/11	EF89	7/-	PY81	5/9
6U4GT	10/6	DF96	6/11	EF91	3/6	PY82	6/3

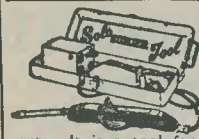Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk. Postage and Packing 6d. per valve extra. C.O.D. or C.W.O. only. C.O.D. charge 3/- extra. S.A.E. with enquiries.



SOLO SOLDERING TOOL only 12/6
110V, 6V or 12V (special adaptor for 200/250V, 10/- extra). Automatic solder feed including a 20ft reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and non-burn. In light metal case with full instructions for use. Post 3/6.

RECORD PLAYER CABINET R.P.2 59/6
Made by famous manufacturer. In polka dot cloth with clipped lid and carrying handle. 16" x 14 1/2" x 8 1/2" deep. Carr. & Ins. 4/6. Will take B.S.R. Monarch 4-speed Autochanger, £6.19.6; 7" x 4" Elliptical Speaker, 15/9; our Mk. D.1 Portable Amplifier, 59/6.

RECORD PLAYER CABINET R.P.9 19/6
Exceptional offer. A lightweight portable record player cabinet by famous manufacturer. 14 1/2" x 11 1/2" x 6". Colours: cream and rust. Complete with moulded deckboard of attractive design. Takes a B.S.R. TU9 single player; 2 control amplifier and a 5" round speaker. P. & P. 4/6.

SPEAKER SALE! All sizes and prices. Brand new 15/9. 8" x 3" Specially made for record and tape cabs. P. & P. 2/9.

15/9. 7" x 4" Ideal for Record Player Cabs. P. & P. 2/9
12/9. 5" P.M. round. 3 Ω speech coil. Flux density 8,500 gauss. P. & P. 2/3.

Contemporary Extension Speaker, 19/9. Ideal for extra stereophonic sound! Beautifully made, includes 8" speaker. P. & P. 3/9

DUKE & CO. (LONDON) LTD.
621/3 ROMFORD RD
MANOR PARK E12
Telephone ILFord 6001/3

REPANCO HIGH GAIN COILS

Dual Range Crystal Set Coil, Type DRX1 2/6
Dual Range Coil with Reaction, Type DRR2 4/-
Matched Pair Dual Range, T.R.F. Coils, Type DRM3 pair 8/-
Pair Dual Range Superhet Coils, Type SH4 pair 8/-
Miniature Iron Dust Cored Coils, Type "R" each 3/3

Range	Aerial	H.F.	Ocs.
800 2,000 m.	RA2	RHF1	RO1
190 550 m.	RA2	RHF2	RO2
70 230 m.	RA3	RHF3	RO3
15 50 m.	RA4	RHF4	RO4

Ferrite Rod Aerial, Dual Range Type FR1 12/6
Miniature I.F. Transformers, Type MSE (465 kc/s) pair 12/6
Standard I.F. Transformers, Type TCG (465 kc/s) pair 13/6
Send S.A.E. for latest Repanco Component Catalogue Telephone 62572

Radio Experimental Products Ltd

33 Much Park Street COVENTRY
Telephone 62572

TRADE (continued from page 157)

THE INTERNATIONAL HAM HOP CLUB is a non-profit making organisation open to RADIO AMATEURS and SHORT WAVE LISTENERS. OBJECT: To improve international relationships through an organised system of hospitality. MEMBERS offer over-night hospitality to visiting members, entrance fee 2s. 6d. ASSOCIATE MEMBERS invite radio amateurs to visit their stations. S.A.E. for FREE Associate membership. FAMILY EXCHANGE holidays arranged, also FRIENDSHIP LINKS between radio clubs. H.H.C.'s official journal, *Ham Hop News*, 5s. per annum. Hon. Gen. Secretary: G. A. Partridge, G3CED, 17 Ethel Road, Broadstairs, Kent.

FIND TV SET TROUBLES IN MINUTES from that great book *The Principles of TV Receiver Servicing*, 10s. 6d., all book houses and radio wholesalers. If not in stock, from Secretary I.P.R.E., 20 Fairfield Road, London, N.8.


SERVICE SHEETS, valves, components, books, transistor and short wave kits. Lists 3d.—Hamilton Radio (R), 237 Sedlescombe Road N., Hastings.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free Services to members including Q.S.L. Bureau. Amateur and Broadcast Translation. Technical and Identification Dept.—both Broadcast and Fixed Stations. DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, "MONITOR," containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 21s. per annum.—Secretary ISWL, 12 Gladwell Road, London, N.8.

AGENCIES OFFERED. Ability to do simple repairs on radios an advantage. Genuine offer for start of spare time business. Future prospects.—Reply Box No. F113.

"LITON" PHOTO-ELECTRIC PARKING LIGHT SWITCH

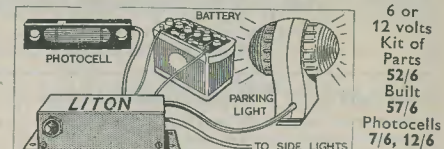will switch your lights on at dusk—off at dawn, automatically. Controlled by daylight. Transistorised.



BURGLAR ALARM—GARAGE DOOR OPENER—LIGHT SAVER, Kit, £4.12.6. Built £5.10.0. Send 6d. stamp for full details and circuit of each device.

"ST. JOHN'S RADIO" 156 St. John's Hill SW11

"GLOBE-KING"

Amateur Radio Kit, model 100/A

can be obtained from the following Stockists:

HOME RADIO (MITCHAM)
187 London Road Mitcham Surrey

SHORT-WAVE (HULL) RADIO
30-32 Prince's Avenue Hull

RADIO EXPERIMENTAL PRODUCTS
33 Much Park Street Coventry

Write for free copy catalogue (enclose stamp for postage) to:

JOHNSONS (Radio) St. Martins Gate Worcester

TRANSISTOR COMPONENTS

REPANCO... FS2 13/6; OT1 11/6; TT2 5/-; TT3 5/-; TT4 8/6; TT5 8/-; FS3 7/6; XL1 3/6; X08 5/-; XT6 10/-; XT7 10/-; also Cools... DRX1 2/6; DRR2 4/-; DRM3 8/-; SH4 8/-; MSE iF's 12/6 pr; "R" coils 3/3 each. FR1 aerial 12/6. Miniature resistors 10% 6d; Miniature condensers 1, 2, 5, 8, 25, 50, 100 mfd 3/-.
SELECTED Transistors... Red spots 5/-; White spot 6/-.
All Mullard and Ediswan Transistors in stock.
SELECTED Germanium diodes 1/6; GEX34 4/-; OA70, OA79 and OA81 4/- each.
Shopping List available for Mullards "Circuits for Audio Amplifiers."

L. F. HANNEY

77 Lower Bristol Rd. Bath S.A.E. for LIST please

NEW SURPLUS... BY RETURN

1L4	3/6	6K8G	5/6	12SC7M	2/6	ECC83	6/6
1R5	6/-	6K8M	9/-	12SJ7M	5/-	ECH42	10/6
1S5	6/-	6H6M	2/-	12SK7M	5/-	EF36	2/6
2A3	8/6	6L6G	7/-	12SQ7M	8/6	EF39	3/6
2X2	2/6	6L6M	9/-	35Z5GT	8/6	EF50	1/6
3A5	9/-	6Q7G	7/6	35Z4G	5/-	EF50(S)	2/6
3Q4	5/6	6Q7GT	9/-	42	7/6	EF86	11/6
5R4GY	9/6	6SA7M	6/-	50L6GT	9/6	EP91	3/-
6AC7M	4/-	6SJ7M	5/6	80	6/6	EL32	3/-
6AG5	3/6	6SL7GT	5/6	446A	10/6	EL41	9/6
6AK5	5/-	6SN7GT	4/-	830B	8/6	EM80	9/6
6AL5	3/-	6ST7M	5/-	959	5/-	GT1C	6/6
6AM6	3/-	6V6G	7/6	1629	4/-	GZ32	10/-
6AU6	6/-	6X4	5/6	5763	10/6	KT33C	6/6
6B8G	2/6	12A6M	5/-	AR8	3/-	PCC85	9/-
6BA6	6/-	12A7	7/-	DC70	4/-	PCF82	7/6
6BH6	5/6	12A6	7/6	DET24	10/-	PEN25	4/-
6B16	5/6	12A7	5/6	DF73	4/-	PY80	6/6
6F32	2/6	12AX7	6/6	DL70	4/-	PY83	7/6
6F6M	5/6	12BE6	7/6	EAS0	1/6	TT11	3/-
6J6	3/6	12CBM	7/6	EAC91	3/-	VLS631	10/-
6J7G	5/-	12K7G	5/-	EB91	3/-	VP23	3/-
6K7G	2/-	12K8M	10/-	EBC33	5/-	VR150/30	
		12Q7G	5/-	ECC82	5/6		7/6

Post and Packing 6d. per valve. Free over £2

TAPE DECKS—BSR Monarch. Brand new and boxed, only £9 each, plus 3/6 carr.

COLLARO JUNIOR. 4 speed single player with Acos HGP54 turnover crystal pick-up. Brand new boxed, only £3.10.0 each. plus 3/6 carr.

ELECTROSTATIC VOLTMETERS 2 1/2" RD, plug-in, 0-1500V., 16/6 each.

S.A.E. ENQUIRIES

JOHN ANGLIN

385 CLEETHORPE ROAD GRIMSBY Lincs.
Telephone 56315

Ask "ARTHURS" First

NOTE NEW ADDRESS AT
125 Tottenham Court Road
London WC1

Close to Warren Street Station

You will have the same service and obtain all your requirements in Radio Components, Electrical Goods, Accessories and Television as previously.

Test Instruments in stock include Avo, Advance, Cossor and Taylor. List on request

VALVE MANUALS AVAILABLE
Mullard 10/6 Brimar No. 8 6/-
Osram Part 1, 2nd Edition 7/6
Post and packing 9d. each extra

Arthurs first

Est. 1919

Proprietors ARTHUR GRAY LTD

Gray House
125 Tottenham Court Road
London WC1

Telephone EUSton 5802/3/4

TELEKIT SUPPLY

104 High St. Beckenham Kent
Phone: Beckenham 3720
30 Catford Hill London SE6
Phone: Forest Hill 9658
Early closing 1 p.m. Wednesday

STEREO 19 gns.

Complete & Working

Consisting: Collaro Auto Changer with "Acos 73" Cartridge, Quality Amplifier 2 x 2 watts, two Hi-Flux 8" Speakers.
We stock and advise on: Kits, Amplifiers, Transistors, TV Tubes, Valves, Tapes and Tape Decks and Record Players, etc.

ALL OUR GOODS ARE GUARANTEED

Premier RADIO

23 TOTTENHAM COURT ROAD LONDON W1 Telephone MUSEum 3451/2
and 309 EDGWARE ROAD LONDON W2 Telephone PADdington 6963

Dramatic Price Reductions

AVANTIC SPA11 10 watt (per channel) combined Stereophonic Amplifier and Pre-amplifier. Dimensions: 14½" x 8½" x 4". Original Price 28 gns. **OUR PRICE** 19 gns. P. & P. 7/6.

AVANTIC SP21 Stereophonic Pre-Amp, Control Unit designed for use with the DL7-35 Power Amplifier. Power requirements 6.3V at 1.3A A.C., 250V at 5mA D.C. Dimensions 14½" x 9" x 4". Original Price £28.10.0 **OUR PRICE** £16.19.6 P. & P. 5/-.

AVANTIC PL621 20 watt monaural Amplifier, frequency response 10 c/s-30 Kc/s 1dB. L.S. impedance, 4, 8, or 16 ohms, Dimensions 14" x 8½" x 7½". Original Price 29 gns. **OUR PRICE** 19 gns. P. & P. 7/6.


AVANTIC DL7-35 Power Amplifier, power output 54 watts peak, Valve line-up: GZ34, 2-EL34, ECC83, EF86. L.S. impedance 4, 8, or 16 ohms switch selected. Original Price 30 gns. **OUR PRICE** £16.19.6. P. & P. 7/6.

WHY NOT TAKE ADVANTAGE OF THIS WONDERFUL OFFER!

Two DL7-35 Power Amplifiers, SP21/2 Stereo Control Unit. **COMBINED PRICE** 47 Gns.

Full Descriptive Literature Available

THE EASY-SIX

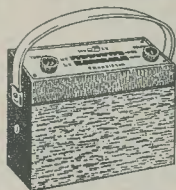

6-Transistor Battery Portable

May be built for **£9.15.0** plus 3/- p.p.

Ever-Ready PP7 Battery extra 3/3

STAR FEATURES: ★ six 1st grade Mullard Transistors, ★ internal Ferrite Rod Aerial, ★ provision for Car Radio Aerial, ★ 5" Loudspeaker ★ printed circuit, with component positions indicated, ★ pre-assembled Dial

Assembly, ★ 500 milliwatts output, ★ full medium and long waveband coverage, ★ attractive two-tone Blue/Cream Vynide covered Cabinet dimensions 8½" x 6½" x 3", ★ full point-to-point instructions supplied, ★ weight—3. lb. with Battery.


The "MID-FI" A NEW DESIGN 4½ WATT AMPLIFIER KIT

95/- plus 3/- P. & P.

Technical specifications: separate bass and treble controls. Valve line-up EF86, EL84, EZ80. Voltage adjustment for a.c. mains from 200/250 volts, 3 or 15 ohms impedance. Negative feedback. Size 7" x 5" x 2", overall height 5". Silver hammered finish chassis.

Powerful! Personal! Portable!

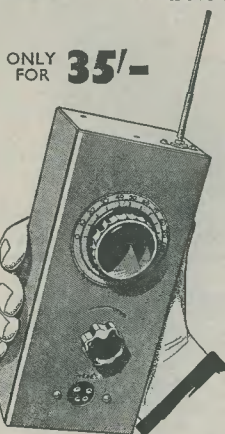- ★ Sturdy metal case
- ★ No holes to drill
- ★ Detachable rod aerial
- ★ All batteries self-contained
- ★ Can be built in 1 hour
- ★ Covers medium waves
- ★ Loud clear tone
- ★ Selective tuning
- ★ All parts are sold separately



ONLY FOR **35/-**

This delightful set is designed to give you a completely personal portable radio.

Bronze-finished case. Ideal for the beach, the bedroom, the office—in fact, anywhere.

Send 2/- for wiring diagram and component price list

R.C.S. PRODUCTS (RADIO) LTD
11 Oliver Road London E17 Mail Order Only

For Safety's Sake use AVO Prodclips



Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads. Post Free **15/-** per pair

AVO LTD AVOCET HOUSE
92-96 VAUXHALL BRIDGE RD., LONDON, SW1
VICtoria 3404 (12 lines)

A Member of the Metal Industries Group of Companies
2PC

TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

rewinds to all makes

H. W. FORREST (TRANSFORMERS) LTD.,
Shirley, Solihull, Warwickshire
Telephone SHIrley 2483

NYLON. P.T.F.E.

ROD BAR SHEET TUBE STRIP WIRE
No quantity too small List on application

BRASS COPPER BRONZE ALUMINIUM LIGHT ALLOYS
H. ROLLET & CO LTD

6 Chesham Place SW1 BELGravia 4300
Also at Liverpool Birmingham Manchester Leeds

Teletypewriters, Perforators, Reperforators

Tape Readers, Pen Recorders, Terminals and V.F. Telegraph multi-channel units, Test Frames and Testing Equipment. Telephone Carriers and Repeaters, Signalling Rectifiers and Relays, Transformers, Transmit and Receive Filters, Repeating and Retardation Coils, Uniselectors, Racks, Relay Bases, Remote Control Transmitters: British, American and German Equipment.

BATEY & CO., Gaiety Works, Akeman Street, Tring, Herts. Telephone Tring 2183 and 2310

SERVICE SHEETS. 14 Days Free Hire

Line Output Transformer Specialists. All Makes/Models from 65/- Volume Controls 3/- Switched 4/9. Resistors ½ watt, ½ watt 6d. each. Hystab 10% ½ watt 10d. Wirewound 10% 5 watt 1/3. 10 watt 1/6. Sub-Miniature Electrolytics 1µF, 2µF, 4µF, 5µF, 25µF, 50µF, 100µF, 15V. 3/- each. Coax.Cable 6d. per yd. Crystal Diodes 2/- GEX34 4/- Max. Coils 3/- each. R.E.P. DRR2 4/- All Repanco and Teltron components in stock. All transistors stocked.

Service sheet free hire on all orders over 25/- Deposit 5/- extra returnable. P. & P. 1/-, over £2 free. S.A.E. all enquiries.

WYNDSOR TELEVISION SERVICE
ST. ALBANS ROAD BARNET HERTS.
Telephone BAR 1769

QUALITY COMPONENTS FOR CONSTRUCTORS

capacitors, resistors, coils, valves, diodes, controls, chassis, transformers, speakers, pick-ups, cart-ridges, styli and all types of components in stock.

CONSTRUCTIONAL PUBLICATIONS

Mullard Circuits for Audio Amplifiers	... 8/6
Mullard Tape Pre-amp "C"	... 2/6
Quality Amplifiers, 7 designs	... 4/6
Jason F.M. Variable Tuners	... 2/6
Jason F.M. and T.V. Mercury 2	... 3/6
Jason F.M. and T.V. JTV2	... 3/6

Price lists available on request

J. T. FILMER 82 DARTFORD ROAD
DARTFORD KENT
Telephone Dartford 24057

H.A.C. THE ORIGINAL SUPPLIERS OF SHORT-WAVE KITS

One valve Super Sensitive All-dry Short-wave Receiver Model "K". Complete kit including valve and chassis 77/- (Other S.W. kits from 25/-) Before ordering call and inspect a demonstration receiver, or send stamped envelope for full specification, catalogue and order form.

H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)
11 OLD BOND STREET LONDON W1

SPECIAL AMATEUR LICENCE MORSE COURSE

COMPLETELY NEW METHOD takes all the drudgery out of learning Morse. Passes secured in all cases, even after previous failures.

By using specially prepared recordings (3 speed L.P. player required) students learn automatically and without effort, perfect Morse in half the time required by any other method. Please S.A.E. full details.

G3HSC 45 GREEN LANE PURLEY SURREY

"GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS

for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for postage. Kits from 79/6 obtainable at your dealers or direct from sole manufacturers.

JOHNSONS (Radio)
ST. MARTINS GATE — WORCESTER

RADIO AMATEURS...

get your Licence in

Half The Usual Time!

You must be a good Morse operator! A "slap-dash" 12 w.p.m. neither satisfies the authorities, yourself, nor your operator friends. Morse operating is an exacting art unless your training is made simple and is based on sound fundamentals. For this reason the Candler System was invented to take the "grind" out of Code tuition, turning a tricky subject into a pleasurable pursuit.

★ Send 3d. stamp for the "Book of Facts"

CANDLER SYSTEM CO
(Dept. 55 RC) 25b Abingdon Rd., London, W8
Candler System Company, Denver, Colorado, U.S.A.

3000 and 600 type relays brand new boxed and surplus, 4, 50, 100, 492, 500, 1000, 2000, 6500, Ohms, contacts etc. Resistors Capacitors, Valves, Meters, etc. SV-4X/450A eqvt £10 each. 832 £1 each, 807 7/6 each, CV36 (klystron). Large quantity of enamelled and silk-covered wire to be sold as a lot. Discount for quantity. Prompt reply to postal inquiries.

★ ★ ★

ABEL RADIO LTD

283 EDGWARE ROAD LONDON W2
Telephone AMB 8614