

# THE **Radio Constructor**


RADIO  
TELEVISION  
AUDIO  
ELECTRONICS

VOLUME 17 NUMBER 1  
A DATA PUBLICATION  
PRICE TWO SHILLINGS

August 1963

HIGH QUALITY

**Modulator  
Design**

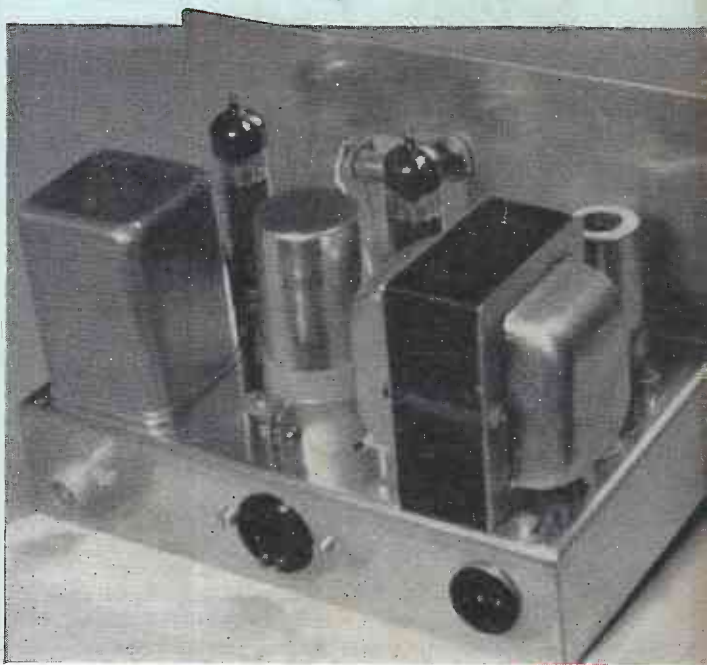

## THE MODERN BOOK CO

**Understanding Amateur Radio.** By A.R.R.L. **18s.** Postage 1s. 3d.

**The Radio Amateur's Handbook.** By A.R.R.L. 1963 ed. **36s.** Postage 2s. 6d.

**Electronic Organ Handbook.** By H. E. Anderson. **40s.** Postage 1s.

**TV Fault Finding** A Data Publication. **5s.** Postage 6d.

**Fun With Radio-controlled Models.** By E. L. Safford. **25s.** Postage 9d.

**Learn Electronics By Building.** Easy to build projects. By J. Schroeder. **27s.** Postage 1s.

**Maintenance Manual.** By Mullard. **16s.** Postage 1s.

**Radio Valve Data 7th ed.** Compiled by "WW". **6s.** Postage 10d.

**Semiconductor Circuit Design.** By R. V. Leedham. **7s. 6d.** Postage 6d.

**Basic TV Course.** By G. Kravitz. **30s.** Postage 1s.

**Elementary Telecommunications Examination Guide.** By W. T. Perkins. **17s. 6d.** Postage 9d.

**Manual of Sound Recording.** By J. Aldred. **75s.** Postage 1s.

**A Beginner's Guide to Radio.** By F. J. Camm. **7s. 6d.** Postage 6d.

**Cabinet Handbook.** By G. A. Briggs. **7s. 6d.** Postage 6d.

**Worked Radio Calculations.** By A. T. Witts. **15s.** Postage 6d.

**Hi Fi For Beginners.** By J. Borwick. **7s. 6d.** Postage 6d.

We have the Finest Selection of British and American Radio Books in the Country  
Complete Catalogue 1s.

**19-21 PRAED STREET (Dept RC) LONDON W2**

Telephone PADDington 4185

## THE DUCHESS OF KENT PERMANENT BUILDING SOCIETY

*Member of the Building Societies Association*



ESTABLISHED

1865

Savings in this old established Building Society combine sound investment with an attractive return  
Shares are in units of £25 each (maximum investment £5,000) . . . BUT, for the smaller saver, Subscription Share accounts may be opened with any sum from 1/- upwards. Interest is payable half-yearly on Fully Paid Shares—credited annually on Subscription Shares—all interest accrues monthly

WITHDRAWALS AT SHORT NOTICE

**INTEREST IS AT  $3\frac{3}{4}\%$  PER ANNUM**

(There is NO DEDUCTION FOR INCOME TAX, as this is paid by the Society)

FOR FURTHER INFORMATION APPLY TO

**DUCHESS OF KENT  
PERMANENT BUILDING SOCIETY**

**103 Cannon Street London EC4**

Telephone **MANsion House 8011**

Please send to me, without obligation, free brochure and a copy of the audited statement of accounts. (I understand that I shall not be troubled with circulars or calls by representatives)

Name .....


(If lady, please state Mrs. or Miss)

Address .....

.....R.C.

(Please use Block Capitals for both name and address)

# TRANSISTORISED COMMUNICATIONS RECEIVER

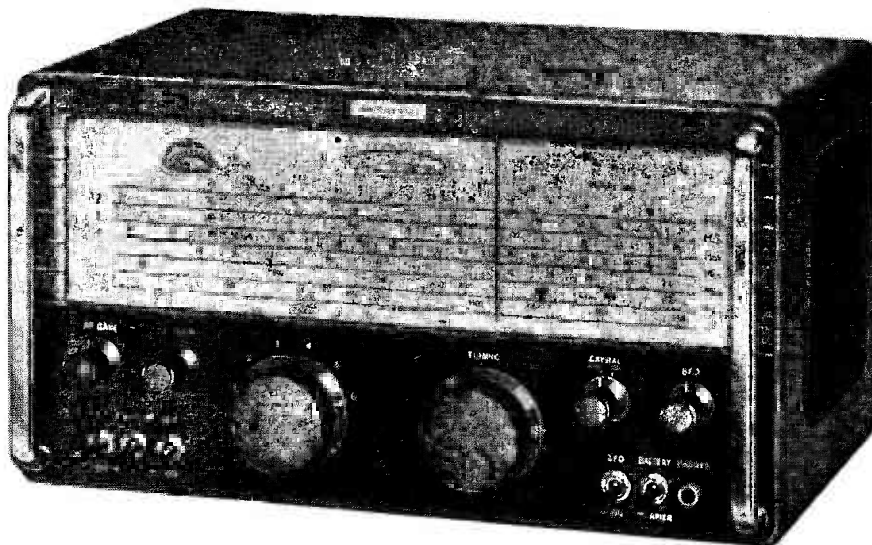

## —*the* **EDDYSTONE '960'**

500 kc/s-----to-----30 Mc/s

- Nineteen semi-conductor devices
- Six ranges cover 500 kc/s to 30 Mc/s
- Good frequency resolution
- High sensitivity
- Two selectivity positions—one with crystal filter
- Excellent frequency stability
- Audio output up to one watt
- Precision slow motion drive
- Internal heavy duty battery
- Provision for using external power supply
- Robust construction
- High reliability
- Modern styling and finish

*Illustrated brochure giving full specification and other information available on request from the manufacturers:*

**STRATTON & CO. LTD**

Telephone Priory 2231/4

**BIRMINGHAM 31**

Telex 33708

# Scottish Insurance Corporation Ltd

38 EASTCHEAP • LONDON • EC3



## TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) (i) and (ii) costs only 2/6 a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's Office at the above address, a proposal will be submitted for completion.

NAME (Block letters).....  
(If lady, state Mrs. or Miss)

ADDRESS (Block letters).....

/JB

# ANOTHER TAPE RECORDER BARGAIN

Mfrs.' end of production Surplus Offer



A 24 gns. Tape Recorder offered at the bargain price of only 15 gns. plus 10/- Carr. Supplied in 3 Units already wired and tested. A modern Circuit for quality recording from Mike, Gram or Radio, using latest B.S.R. Twin Track Monardeck Type TD2.

Valve line-up—EF86, ECL82, EM84, E2280 and Silicon Diode.

- 2 tone Cabinet and 8" x 5" Speaker. Size 14" x 10 1/2" x 7 1/2" **£3.10.0** + 5/- carr.
  - Wired Amplifier complete with 4 valves, Front Panel, Knobs **£5.12.6** + 3/6 carr.
  - B.S.R. Monardeck Type T.D.2 **£7. 7.0** + 4/6 carr.
  - Accessories—Mike, Tape, Screened Lead, Plugs, etc. **£1. 1.0** + 2/- carr.
  - COMPLETE KIT** comprising items above **15 gns.** + 10/- carr.
- Leaflet, Circuit and Instruction 2/- post free

New Boxed	VALVES	All Guaranteed	Electrolytics	All Types	New Stk. TUBULAR CAN TYPES		
1T4	6/-	ECC83 8/-	PCC84 9/6	25/25V	1/9	8+8/450V	4/6
1R5	7/6	ECL82 10/6	PCF80 9/6	50/12V	1/9	16+16/450V	5/6
1S5	7/6	ECL80 10/6	PCL83 12/6	50/50V	2/-	32+32/275V	4/6
354	7/6	EF80 8/-	PCL84 12/6	100/25V	2/-	50+50/350V	6/6
3V4	7/6	EF86 12/6	PL81 12/6	8/450V	2/3	60+250/	
DAF96	9/-	EL84 8/6	PL82 9/6	4/350V	2/3	275V	12/6
DF96	9/-	EY51 9/6	PL83 10/6	16+16/450V	5/6	100+300/	
DK96	9/-	EY86 10/6	PY32 12/6	32+32/450V	6/6	275V	12/6
DL96	9/-	EZ81 7/6	PY81 9/6	1000/25V	3/9	2000+4000/	
ECC81	8/-	GZ32 12/6	PY82 7/6			6V	3/6
ECC82	8/-	EM84 9/6	U25 12/6			Erskin Multicore Solder	60/40 3/6

per yard. 1/2 lb. 2/6, etc.

## NEW BRITISH RECORDING TAPE

Famous Mfr. Bulk Purchase—Genuine recommended Tape Bargain. Uncond. Guar. Fitted Leader & Stop Foils (except 3").

Standard (PVC base) Long Play (PVC base) D'ble Play (Mylar base)

3"	150ft. ...	3/9	225ft. ...	4/9	300ft. ...	6/6
5"	600ft. ...	11/6	900ft. ...	15/-	1,200ft. ...	25/-
5 1/2"	850ft. ...	14/6	1,200ft. ...	17/6	1,800ft. ...	32/6
7"	1,300ft. ...	17/6	1,800ft. ...	22/6	2,400ft. ...	42/3

Post and Packing—3" Reels 6d. Each additional Reel 3d. 4" to 7" Reels 1/- Each additional Reel 6d.

EMPTY TAPE REELS (Plastic): 3" 1/3; 5" 2/-; 5 1/2" 2/-; 7" 2/3.

PLASTIC REEL CONTAINERS (Cassettes): 5" 1/9, 5 1/2" 2/-, 7" 2/3

Jack Plugs. Standard 2 1/2" Igranic Type, 2/6. Screened Ditto, 3/3. Miniature 1 1/2", 2/3. Screened Ditto, 2/6.

Jack Sockets. Open Igranic Moulded Type, 3/3. Closed Ditto, 3/9. Miniature Closed Type, 1/9. Sub-min (deaf aid) ditto, 1/3.

Phono Plugs 1/-, Phono Sockets (open), 1/-, Ditto Closed, 1/6. Twin Phono Sockets (open), 1/6.

Soldering Irons. Mains 200/220V or 230/250V. Solon 25 watt Inst., 22/6. Spare Elements, 4/6. Bits, 1/- 6s watt, 27/6 etc.

Alumin. Chassis. 18g. Plain Undrilled, folded 4 sides, 2" deep. 6" x 4", 4/6, 8" x 6", 5/9, 10" x 7", 6/9, 12" x 6", 7/6, 12" x 8", 8/- etc.

Alumin. Sheet. 18g. 6" x 6", 1/-, 6" x 9", 1/6, 6" x 12", 2/-, 12" x 12", 4/6 etc.

## MULLARD "3-3" HI-FI AMPLIFIER

### 3 VALVES 3 WATT



3 ohm and 15 ohm Output  
A really first-class Amplifier giving Hi-Fi quality at a reasonable cost. Mullard's latest circuit. Valve line-up: EF86, EL84, EZ81. Extra H.T. and L.T. available for Tuner Unit addition. This is the ideal companion Amplifier for FM tuner units.

TECHNICAL SPECIFICATION—Freq. Response: ± 1dB, 10 kc/s. Max. Bass Boost 14dB at 80 c/s sensitivity: 100MV for 3W output. Output Power (at 400 c/s): 3W at 1% total harmonic distortion. Hum and Noise Level: At least 70dB below 3W.

COMPLETE KIT (incl. valves, all components, wiring diagram and special quality sectional Output Trans.) ONLY £6.19.6 carr. 4/6. Complete wired and tested, 8 gns. Wired power O/P socket and additional smoothing for Tuner Unit, 10/6 extra.

Bronze Escutcheon Panel, Printed Vol., Treble, Bass, On-Off, supplied with each Kit. Recommended Speakers—R. & A. 12" with tweeter 52/6, WBFH10-12 £4.7.6, Goodmans Axiette £55.0, Axium 10 £6.5.0. Carr. extra

Volume Controls—5K-2 Meg. ohms, 3" Spindles Morganite Midget Type. 1 1/2" diam. Guar. 1 year. LOG or LIN ratios less Sw. 3/-. D.P. Sw. 4/6. Twin Stereo less Sw. 6/6. D.P. Sw. 8/-.

### COAX 80 OHM CABLE

High grade low loss Cellular air spaced Polythene—1/2" diameter. Stranded cond. Famous mfrs. New only 6d. per yard. Bargain

Prices—Special lengths:  
20 yds. 9/-. P. & P. 1/6  
40 yds. 17/6. P. & P. 2/1-  
60 yds. 25/-. P. & P. 3/-  
Coax Plugs 1/-. Sockets 1/-  
Couplers 1/3. Outlet Boxes 4/6.

Close Tol. S/Micas—10% 5pF-500pF 8d. 600-5,000pF 1/-. 1% 2pF-100pF 9d. 100pF-500pF 11d. 575pF-5,000pF 1/6. Resistors—Full Range 10 ohms—10 megohms 20% 1 and 1/2W 3d., 3W 5d. (Midget type modern rating) 1W 6d., 2W 9d. Hi-Stab 5% ±1W 10 ohms 1 megohm 6d. Other values 9d. 1% ±W 1/6. W/W Resistors 25 ohms to 10K SW 1/3, 10W 1/6, 15W 2/-. Pre-set T/V Pots. W/W 25 ohms—50K 3/-. 50K-2 Meg. (Carbon) 3/-.

### JASON FM TUNER UNITS

Designer-approved kit of parts:  
FMT1, 5 gns. 4 valves, 20/-  
FMT2, £7. 5 valves, 37/6  
JTV MERCURY 10 gns.  
JTV £13.19.6. 4 valves, 32/6.

NEW JASON FM HANDBOOK, 2/6. 48 hr. Alignment Service 7/6. P. & P. 2/6.

Speakers P.M.—3 ohms 2 1/2" E.M.I. 17/6. Goodmans 3 1/2" 18/6, 5" Rola 17/6. 6" Eiac 18/6, 7" x 4" Goodmans 18/6, 8" Rola 20/-. 10" R. x A. 25/-. 9" x 6" Goodmans 25/- E.M.I. Tweeter 29/6.

Speaker Fret—Expanded gilt anodised metal 1/2" x 1/2" diamond mesh, 4/6 sq. ft., multiples of 6" cut. Max. width 4 ft. 4 ft. x 3 ft. 47/6. Carr. extra

TYGAN FRET (contemp. pat.) 12" x 12" 2/-. 12" x 18" 3/-. 12" x 24" 4/-. 18" x 18" 4/6.

BANDCAUST Speaker Cabinet Acoustic Wadding, 12" wide, any length cut 1-6 ft.

### BARGAINS 4-SPEED PLAYER UNITS

Single Players carr. 3/6  
Garrard-SRP10 £5.5.0  
B.S.R. Latest Model TU12 72/6  
E.M.I. Junior "985" 67/6

Auto-Changeers carr. 5/-  
Garrard AT6 Mono 9 gns.  
Garrard "Auto-Slim" £6.15.0  
Collaro C60 £6.19.6  
B.S.R. (UA14) £6.10.0

ENAMELLED COPPER WIRE—1/16 reels, 14g-20g, 2/6; 22g-28g, 3/-; 36g-38g, 4/3; 39g-40g, 4/6, etc.

PVC CONNECTING WIRE—10 colours (or chassis wiring, etc.)—Single or stranded conductor, per yd., 2d. Sleeving 2d. yd.

### TRANSISTOR COMPONENTS

Midget I.F.'s—465 kc/s 1/2" diam. 5/6  
Osc. Coil—1/2" diam. M/W. 3/3  
Osc. coil M. & L.W. 5/9  
Midget Driver Trans. 3.5:1 6/9  
Ditto O/Put Push-pull 3 ohms 6/9  
Elect. Condensers—Midget Type 15V 1mfd-50mfd, ea. 1/9. 100mfd. 2/-

Ferrite Aerial—M. & L. W. with car aerial coupling coil, 9/3.

Condensers—150V. wkg. .01 mfd. to .04 mfd., 9d. .05 mfd., .1 mfd., 1/- .25 mfd., 1/3. .5 mfd., 1/6, etc.

Tuning Condensers. J.B. "00" 208+176pF, 8/6. Ditto with trimmers, 9/6. 365pF single, 7/6. Sub-min. 2" DILEMIN 100pF, 300pF, 500pF, 7/-.

Midget Vol. Control with edge control knob, 5kΩ with switch, 4/9, ditto less switch, 3/9.

Speakers P.M.—2" Plessey 75 ohms, 15/6. 2 1/2" Continental 8 ohms, 13/6. 7" x 4" Plessey 35 ohm, 23/6.

Ear Plug Phones—Min. Continental type, 3ft. lead, jack plug and socket. High Imp. 6/-, Low Imp., 7/6.

### TRANSISTOR BARGAINS

Brand New—BVA 1st Grade

OC44	8/6	OC70	5/6
OC45	8/-	OC71	6/-
OC81	7/6	GEX34	2/9
2/OC81	15/6	OQ70	2/9
GET114	6/6	OAB1	2/9
OC72	7/6		

TRIMMERS, Ceramic (Compression Type)—30pF, 70pF, 9d.; 100pF, 150pF, 1/3; 250pF, 1/6; 600pF, 1/9.

PHILIPS, Bee Hive Type (conc. air spaced)—2-8pF, 1/-; 3-30pF, 1/-.

KNOS—Modern Continental types: 9d. or Ivory with Gold Ring, 1" dia., 9d. each; 1 1/2", 1/- each; Brown or Ivory with Gold Centre, 1" dia., 10d. each; 1 1/2", 13c. each. LARGE SELECTION AVAILABLE.

METAL RECTIFIERS—STC Types—RM1, 4/9; RM2, 5/6; RM3, 7/6; RM4, 16/-; RMS, 21/-; RM4B, 17/6.

### BARGAIN CORNER

Brand New. Mfrs. surplus 1st grade  
1 OC44 & 2 OC45, 15/6.  
1 OC181D & OC81, 13/6.  
All above and OAB1, 32/6 post free.  
1 Meg. VOL Controls D.P. Sw. 1/2" flattened spigule. Famous Mfrs. 4 for 10/- post free.

### RECORD PLAYER CABINETS

Contemporary style, rexine covered cabinet in mottled red and white polka dot. Size 18 1/2" x 13 1/2" x ht. 8 1/2", fitted with all accessories including baffle board and anodised metal fret. Space available for all modern amplifiers and auto-changeers, etc. Uncut record player mounting board 14" x 13" supplied.

Cabinet Price £3.3.0 Carr. and Ins. 5/-

### 2-VALVE 2 WATT AMPLIFIER

Twin stage ECL82 with vol. and neg. feedback tone control. A.C. 200/250V with knobs, etc., ready wired to fit above cabinet. £2.17.6. P. & P. 1/6. 6" Speaker and trans. 22/- P.P. 2/-

### COMPLETE R/PLAYER KIT. DITTO RECORD PLAYER KIT

As ill. inc. BSR UA14 Unit with BSR UA20 Unit. New Reduced Price £12.10.0 Carr. 7/6 Reduced Price £11.10.6 Carr. 7/6



Send for detailed bargain lists, 3d. stamp. We manufacture all types Radio Mains Transf. Chokes, Quality O/P Trans., etc. Enquiries invited for Specials, Pro-types for small production runs. Quotation by return.

### RADIO COMPONENT SPECIALISTS

70 Brigstocke Rd., Thornton Heath, Surrey  
Tel 2188 Hours: 9 a.m., —6 p.m., 1 p.m. Wed. Terms C.W.O. or C.O.D. Post and Packing up to 1/2 lb 9d., 1 lb., 1/3 3lb., 2/3 5 lb., 2/9 8 lb. 3/6.

**Heathkit**  
DAVETROM

# Enjoy Yourself and Save Money

**SINGLE SIDEBAND ADAPTOR. Model SB-10U.** May be used with most A.M. transmitters. Less than 3W R.F. input power required for 10W output. Operation on 80, 40, 20, 15 and 10m bands on U.S.B., L.S.B. or D.S.B. **£39.50**



SB-10U

**AMATEUR TRANSMITTER. Model DX-40U.** Covers all amateur bands from 80 to 10 metres; crystal controlled. Power input 75W C.W., 60W peak controlled carrier phone. Output 40W to aerial. Provision for V.F.O. Filters minimise TV interference. **£33.19.0**



DX-40U

**GRID-DIP METER. Model GD-1U.** Functions as oscillator or absorption wave meter. With plug-in coils for continuous frequency coverage from 1.8 Mc/s to 250 Mc/s. **£10.19.6**



GD-1U

**Q MULTIPLIER KIT. Model QPM-1.** May be used with receivers having 450-470 kc/s I.F.; provides either additional selectivity or signal rejection; self powered. **£7.12.6**

**2½" SERVICE 'SCOPE. Model OS-1.** Light, compact portable for service engineers. Dim. 5" x 8" x 14½" long. Wt. 10½lb. **£19.19.0**



S-33



COLLARO



UXR-2

**LATEST MODEL! "OXFORD" LUXURY TRANSISTOR PORTABLE Model UXR-2.** Specially designed for use as a domestic, car or personal portable receiver. Many features, including solid leather case. Send for full details! **£14.18.0**

**DE LUXE STEREO AMPLIFIER. Model S-33H.** De luxe version of the S-33 with two-tone grey perspex panel, and higher sensitivity necessary to accept the Decca Deram pick-up. **£15.17.6**

**HI-FI 6W STEREO AMPLIFIER. Model S-33.** 3 watts per channel 0.3% distortion at 2.5W/chnl., 20dB N.F.B. Inputs for Radio (or Tape) and Gram, Stereo or Monaural, ganged controls. Sensitivity 200mV. **£13.7.6**

**COLLARO "STUDIO" TAPE DECK.** The finest buy in its price range. Operating speeds: 1½, 3½ and 7½ p.s. Two tracks "wow" and "flutter" not greater than 0.15% at 7½ p.s. Long Term Speed stability better than 0.5%. **£17.10.0**

Prices include free delivery in U.K.

## ★ We guarantee that without previous experience

**5" OSCILLOSCOPE. Model O-12U.** Has wide-band amplifiers, essential for TV servicing, FM alignment, etc. Vertical frequency response 3 c/s to over 5 Mc/s, without extra switching T/B covers 10 c/s to 500 kc/s in 5 ranges. **£38.10.0**



O-12U

**ELECTRONIC SWITCH. Model S-3U (Oscilloscope Trace Doubler.)** Enables a single beam oscilloscope to give simultaneous traces of two separate and independent signals. Switching rates approx. 150, 500, 1,500, 5,000 and 15,000 c/s. Sig. freq. response 0-100 kc/s. ±1dB. Separate gain controls and sync. output. Sig. input range 0.1-1.8V r.m.s. **£11.15.6**



S-3U

**RESISTANCE CAPACITANCE BRIDGE. Model C-3U.** Measures capacity 10pF to 1,000µF, resistance 100Ω to 5MΩ and power factor. 5-450V test voltages. With safety switch. **£9.5.0**



C-3U

**AUDIO SIGNAL GENERATOR. Model AG-9U.** 10 c/s to 100 kc/s, switch selected. Distortion less than 0.1%, 10V sine wave output metered in volts and dB's. **£21.9.6**



AG-9U


**TRANSISTOR INTERCOM. Models XI-1U & XIR-1U.** The master unit uses a 4-transistor amplifier, constructed on a printed circuit board, and an internal 9V battery. Remote stations use a similar battery for call only. Up to five remote units can be ordered for each master. **£4.7.6**

XI-1U (master) **£10.19.6**

**SUGDEN MOTOR UNIT "CONNOISSEUR CRAFTSMAN".** Heavy duty motor operating at 33½ and 45 r.p.m. Very heavy 12" turntable. Virtually no rumble. **£16.6.6**



"GLOUCESTER"

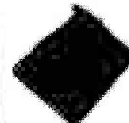

GL-58



AM/FM TUNER

**HI-FI AM/FM TUNER. Model AFM-1.** Available in two units which, for your convenience, are sold separately. Tuning heart (AFM-T1)—£4.13.6 incl. P.T. and I.F. amplifier (AFM-A1)—£20.13.0. Printed circuit board, 8 valves. Covers L.W., M.W., S.W., and F.M. Built-in power supply. Total **£25.6.6**

**HI-FI EQUIPMENT CABINETS.** Our four cabinets meet a wide variety of tastes and requirements: the "CHEPSTOW" designed for those who have little floor space, the contemporary "MALVERN" for the Tape and Gram. enthusiast, and the "GLOUCESTER" Mk. I and II for those with traditional tastes. Supplied "in the white". Prices from **£11.12.6** to **£18.10.0**

An additional range of assembled and finished cabinets is now available from us, details on request.

**GOLDRING LENCO TRANSCRIPTION RECORD PLAYER. Model GL-58** with G-60 pick-up arm and Ronette 105 cartridge. **£18.19.2**

**GARRARD AUTO/RECORD PLAYER. Model AT-6.** With Ronette 105 cartridge. **£13.12.1** With Decca Deram pick-up **£14.6.1**

**HI-FI MONO AMPLIFIER. Model MA-5.** A general purpose 5W Amplifier, with inputs for Gram., Radio. Presentation similar to S-33. **£10.19.6**

**4 W-B TRANSISTOR PORTABLE RECEIVER. Model RSW-1.** In a handsome leather case it has retractable whip aerial and socket for car radio use. Covers Med., Trawler and two S wave bands. **£19.17.6**

**HI-FI SINGLE CHANNEL AMPLIFIER. Model MA-12.** 12W output, wide freq. range, low distortion. **£11.9.6**

**POWER SUPPLY UNIT. Model MGP-1.** Input 100/120V, 200/250V. 40-60 c/s. Output 6.3V, 2.5A A.C. 200, 250, 270V, 120mA max. D.C. **£5.2.6**



MA-12



RSW-1

**250**

**AMERICAN HEATHKIT MODELS MANY PREVIOUSLY UNOBTAINABLE**


All for direct delivery from U.S. Plant to your U.K. address. Illustrated Catalogue and full details of Mail Order scheme can be obtained from us for the nominal charge of 1/- post paid.

SEND FOR FREE ILLUSTRATED BRITISH CATALOGUE TO

# Building Your Own Equipment



RA-1

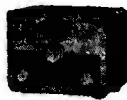

VF-1U



GC-1U

**NEW MODEL! AMATEUR BANDS RECEIVER. Model RA-1.** To cover all the Amateur Bands from 160-10 metres. Many special features, including: half-lattice crystal filter; 8 valves; signal strength "S" meter; tuned R.F. Amplifier Stage. Full specification sheet available on request. **£39.6.6**

**THE "MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U.** With 4 piezo-electric transmitters, variable tuned B.F.O. and Zener diode stabiliser, this is an excellent fully transistorised general purpose receiver for Amateur and Short wave listeners. Printed circuit boards, telescopic whip antenna, tuning meter and large slide-rule dial, 10 transistors. **£39.17.6**

**AMATEUR TRANSMITTER. Model DX-100U.** The world's most popular, compact and completely self-contained Amateur Transmitter. Covers all amateur bands: 160-10 m. 150W d.c. input. Careful design has achieved the stability and high performance for which the DX-100U is noted and no less than 35 disc ceramic capacitors reduce TVI to a minimum. **£74.19.0**

**VARIABLE FREQUENCY OSCILLATOR. Model VF-1U.** Calibrated. 160-10 m. Fundamentals on 160 and 40 m. Ideal for our DX-40U and similar transmitters. **£11.17.6**

*Deferred terms available over £10*



V-7A



MM-1U



RF-1U

**VALVE VOLTMETER. Model V-7A.** 7 voltage ranges d.c. volts to 1,500. A.C. to 1,500 r.m.s. and 4,000 peak to peak. Resistance 0.1Ω to 1,000MΩ with internal battery. D.C. input impedance 11MΩ. dB measurement, has centre-zero scale. Complete with test prods, lead and standardising battery. **£13.18.6**

**MULTIMETER. Model MM-1U.** Ranges 0-1.5V to 1,500V A.C. and D.C.; 150μA to 15A D.C.; 0.2Ω to 20MΩ. 4 1/2" 50μA meter. **£12.10.0**

**R.F. SIGNAL GENERATOR. Model RF-1U.** Up to 100 Mc/s fundamental and 200 Mc/s on harmonics and up to 100mV output on all bands. **£12.15.6**

**AUDIO WATTMETER. Model AW-1U.** Up to 25W continuous, 50W intermittent. **£15.15.0**

**AUDIO VALVE MILLIVOLTMETER. Model AV-3U.** 1mV-300V A.C. 10 c/s to 400 kc/s. **£14.17.6**

**AUDIO SINE-SQUARE WAVE GENERATOR. Model AO-1U.** Covers 20 c/s to 150 kc/s and square waves to 50 kc/s in four ranges. Maximum output 10V, distortion less than 1%. **£13.15.0**

## Anyone can build any of these Heathkit models



TA-1S



Truvox D83



FM TUNER



SSU-1

**TAPE RECORDING/PLAYBACK AMPLIFIER.** Thermometer type recording indicators, press-button speed compensation and input selection. Printed Circuit Board. Mono Model TA-1M **£19.2.6** Stereo Model TA-1S **£24.10.0**

**HI-FI FM TUNER. Model FM-4U.** Also available in two units. R.F. tuning unit (£2.15.0 incl. P.T.) with I.F. output of 10.7 Mc/s, and amplifier unit, with power supply and valves (£12.6.0). Total **£15.1.0**

**TRUVOX D83/2 & D83/4 TAPE DECKS.** High quality mono/stereo tape decks. D83/2, 2 track, **£31.10.0** D83/4, 4 track, **£29.8.0**

**STEREO CONTROL UNIT. Model USC-1.** Push-button selection, accurately matched ganged controls to ±1dB. Negative feedback, rumble and variable low-pass filters. Printed circuit boards. **£19.10.0**

**AVAILABLE SHORTLY! MONO CONTROL UNIT, Model UMC-1** Designed to work with the MA-12 or similar amplifier requiring 0.25V. or less for full output. 5 inputs. Baxandall type controls. **£8.12.6**

**TRANSISTOR PORTABLE. Model UXR-1.** Pre-aligned I.F. transformers, printed circuit. Covers L.W. and M.W. Has 7" x 4" loudspeaker. Real hide case. **£12.11.0**

**TELEPHONE AMPLIFIER. Model TTA-1.** Easy-to-assemble. Transistorised, enables hand-free conversation. Ivory toned cabinet. **£7.9.6**



UXR-1



TTA-1

Assembled models also available — prices on request.



UJR-1



S-99



THE "COTSWOLD"

**HI-FI SPEAKER SYSTEM. Model SSU-1.** Ducted-port bass reflex cabinet "in the white". Two speakers. Vertical or horizontal models with legs **£11.12.0** without legs **£10.17.6**

**CAPACITANCE METER. Model CM-1U.** Direct-reading 4 1/2" scale. Full-scale ranges 0-100μF, 0-1,000μF, 0-0.01μF and 0-0.1μF. **£15.15.0**

**HEATHKIT ELECTRONIC WORKSHOP. Model EW-1.** This educational kit will teach and amuse your children. It can make 21 exciting experiments including transistor radios, burglar alarm, radio or TV silencer, intercom, etc. **£7.13.6**

**JUNIOR TRANSISTOR RADIO. Model UJR-1.** Single transistor set. Excellent introduction to radio. An instructive present. **£2.7.6**

**HI-FI STEREO AMPLIFIER. Model S-99.** 18W output. Ganged controls. Stereo/mono gram., radio and tape recorder inputs. Push-button selection. Printed circuit construction. **£27.19.6**

**THE "COTSWOLD".** This is an acoustically designed enclosure 26" x 23" x 15 1/2" housing a 12" bass speaker with 2" speech coil, elliptical middle speaker together with a pressure unit to cover the full frequency range of 32-20,000 c/s. Capable of doing justice to the finest programme source, its polar distribution makes it ideal for really Hi-Fi Stereo.

**COTSWOLD "MFS" SYSTEM.** Specially developed to give best possible results in small rooms. This minimum floor space model is based on standard Cotswold. Size: 36" high x 16 1/2" wide x 14 1/2" deep. Either Model, **£23.4.0**

Without obligation please send me (Tick here)

**FREE BRITISH HEATHKIT CATALOGUE**

**FULL DETAILS OF MODEL(S)**

(Please write in BLOCK CAPITALS)

NAME

ADDRESS

**DAYSTROM LTD** DEPT. RC8 GLOUCESTER

DEPT. RC8

# SPECIAL OFFER!

## OBTAINABLE ONLY FROM RADIO & T.V. COMPONENTS LTD

### THE *Elegant Seven* COMBINED PORTABLE & CAR RADIO

The Radio with the "STAR" features

- ★ 7-transistor superhet. Output 350mW
- ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12¼" x 8¼" x 3¼"
- ★ Horizontal tuning scale, size 11½" x 2½", in silver with black lettering
- ★ All stations clearly marked
- ★ Ferrite-rod internal aerial
- ★ I.F. 470 kc/s
- ★ Operated from PP9 battery
- ★ Fully comprehensive instructions and point-to-point wiring diagram
- ★ Printed circuit board, back-printed with all component values
- ★ Fully tunable over medium and long waveband
- ★ Car-aerial socket
- ★ Full after-sale service

Parts list and circuit diagram 2/6. FREE with parts



**ONLY  
£5.9.6**

Plus 5/6 Postage and Packing


**RADIO & T.V. COMPONENTS (ACTON) LTD** 21D High St., Acton, London, W3  
Open 9 a.m.-6 p.m. including Sats. Early closing Wed.

equal to top studio  
quality . . .  
build it yourself or  
buy it complete

In kit form for assembly 20 gns  
Assembled and tested 25 gns



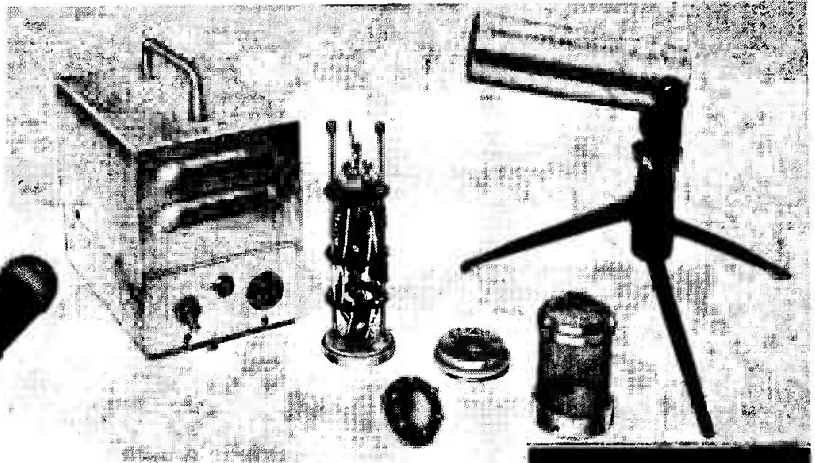Output impedance:  
600 ohms cathode follower



This is a microphone of outstanding performance with an unusually high output (150mV) which enables it to be fed into any amplifier or tape recorder. Available in kit form, with easy step-by-step manual or assembled, tested and ready for use. ONE YEAR FREE replacement/service guarantee with either version. Write, call or telephone for technical specification—and remember, delivery is from stock.



World distribution

**CHATEAU PRODUCTIONS LTD**

Distributors of Professional Electronic Recording Equipment

25 DENMARK STREET • LONDON • W1 Telephone: COV 3026



# FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

## Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

## We definitely Guarantee

### “NO PASS—NO FEE”

Whatever your age and experience you cannot afford to miss reading this famous book. If you are earning less than £25 a week send for your copy of “ENGINEERING OPPORTUNITIES” today—FREE.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Incorporating E.M.I. Institutes)  
(Dept. SE/23), 29 Wright's Lane, London, W.8

## WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building, Plastics,  
Draughtmanship,  
Television, etc.

## GET SOME LETTERS AFTER YOUR NAME!

A.M.I. Mech. E.  
A.M.I.C.E.  
A.M.I. Prod. E.  
A.M.I.M.I.  
I.I.O.B.  
A.F.R. Ae. S.  
B.Sc.  
A.M. Brit. I.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc., etc.

## PRACTICAL EQUIPMENT

Basic-Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

## INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

## B.I.E.T. SCHOOL OF ELECTRONICS

## POST COUPON NOW!

- Please send me your FREE 156-page “ENGINEERING OPPORTUNITIES” (Write if you prefer not to cut page)
- NAME.....
- ADDRESS.....
- SUBJECT OR EXAM THAT INTERESTS ME.....



THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD



POSTAL ENQUIRIES and MAIL ORDERS to Dept. R.C.,  
**STERN RADIO LTD**  
6-12 TUDOR PLACE  
TOTTENHAM COURT RD  
LONDON, W.1  
Telephone MUSeum 6128/9

DEMONSTRATIONS and SHOWROOMS at  
**STERN RADIO LTD**  
109 FLEET STREET  
LONDON, E.C.4  
Tel. FLEet Street 3812/3  
OPEN: 9 a.m. to 6 p.m.  
SAT. Close 1 p.m.

DEMONSTRATIONS and SHOWROOMS at  
**PREMIER RADIO**  
23 TOTTENHAM COURT RD  
LONDON, W.1  
Tel. MUSeum 3451/2  
OPEN: 9 a.m. to 6 p.m.  
THURS. Close 1 p.m.

We are pleased to announce that all Stern Products are now available from  
**CLYNE RADIO LTD., 12 Suffolk House, George Street, Croydon.** Telephone **MUN 3250**

## THE “TWIN THREE” STEREO AMPLIFIER

ASSEMBLED AND TESTED for £9.0.0 (Carr. & Ins. 5/- extra)

Based on a recent design by MULLARD LTD., is ideally suited for use in PORTABLE RECORD PLAYERS for which purpose we offer a specially designed case:  
It incorporates MULLARD ECL 86 Valves, separate BASS and TREBLE CONTROLS and produces up to 3 watts per channel. Frequency response 40 c/s to 30 Kc/s, size 11½ in. x 3 in. x 5 in.  
To construct a STEREO PORTABLE RECORD PLAYER we offer:-  
Assembled AMPLIFIER with two ROLA 8 in. x 5 in. LOUDSPEAKERS and PORTABLE CASE for £16.10.0 (Carr. and Ins. 10/- extra).



## THE MULLARD 33/RC

HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-WATT MULLARD “3-3” DESIGN. KIT OF PARTS ..... £8.8.0

ASSEMBLED AND TESTED ..... £11.10.0

Complete to the MULLARD specification including PARMEKO OUTPUT TRANSFORMER. Switched inputs for 78 and L.P. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available. (Carr. & Ins. 6/6)



## THE MONO-GRAM

A small Amplifier of genuine high quality performance. Incorporates new MULLARD ECL 86 Valve, separate BASS and TREBLE controls and produces up to 3 watts undistorted output.

KIT OF PARTS £4.10.0 ASSEMBLED and TESTED £6.0.0 (Carr. & Ins. 3/6)

Perfectly suited for Portable Installations for which purpose we offer... PORTABLE CASE £3.10.0, the AMPLIFIER (Kit) and 8 x 5 in. SPEAKER (£1). All for £9.0.0. Alternatively with ASSEMBLED AMPLIFIER £10.0.0. (Carr. & Ins. 5/-)

The case quoted above will accommodate some 4 speed Single Record Units. A larger model for auto-changer is available for extra 10/-. With this Equipment a COMPLETE PORTABLE RECORD PLAYER CAN be built for from £14.0.0.



## THE MULLARD 510/RC AMPLIFIER

The popular complete “5-10” incorporating Passive Control Unit, and providing up to 10 watt output with an input of 600mV. Specified components and new MULLARD VALVES. Includes PARMEKO MAINS TRANSFORMERS and choice of the latest PARMEKO or PARTRIDGE output Transformers. Surplus Power available for Tuner.

Price: COMPLETE KIT ..... £12.0.0

ASSEMBLED AND TESTED ..... £16.0.0

(Carr. & Ins. 7/6) with PARTRIDGE OUTPUT TRANSFORMER £1.6.0 extra.



## THE “TUDOR” STEREO AMPLIFIER

PRICE ONLY £15.0.0 (Carr. & Ins. 7/6)

A self-contained Shelf Mounting Amplifier designed to provide high quality stereophonic and monophonic reproduction. Each channel provides a rated output of 6 watts and for monophonic operation approx. 12 watts is produced. Separate BASS and TREBLE CONTROLS. Cabinet in Black Crackle. Size 14” x 6” x 4”.



# ACCLAIMED THE MOST AMAZING RECEIVER EVER


You've never seen or heard a transistor set design like this before. Small enough to conceal in one hand, the Sinclair "Slimline" gives choice of British and European programmes with staggeringly good quality from its own internal ferrite rod aerial. With its entirely new R.F. Reflex Circuit, superhet selectivity is achieved without any of the latter's problems of alignment. And it's so easy to build with its neat printed circuit board and well illustrated and presented instructions. Success is assured before you begin to build even if you are new to receiver construction.

Such dramatic new standards within even smaller dimensions are made possible through the wonderful new MAT Transistors in circuitry developed exclusively to exploit their amazing characteristics—yet it costs so little to build this minute receiver with its giant performance—so start yours NOW!

THE PERFECT SET FOR YOUR HOLIDAY!


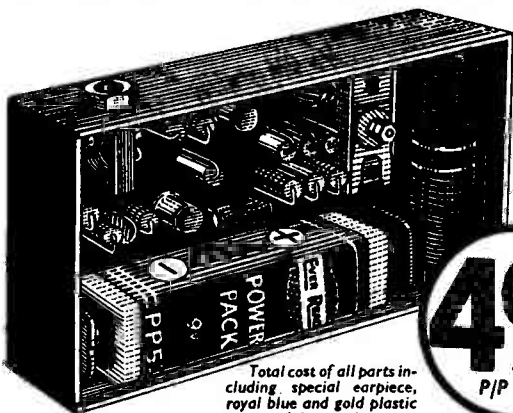
## THE SINCLAIR "SLIMLINE" MICRO-RADIO RECEIVER



Total cost of all parts including special earpiece, royal blue and gold plastic case and instructions.

**BUILT IN A COUPLE OF HOURS**

**2 3/4" x 1 5/8" x 5/8" COMPLETELY SELF-CONTAINED**

Approx.

**49% P/P 1/6**

**RECEIVES HOME, LIGHT, THIRD AND COUNTLESS EUROPEAN STATIONS WITH FANTASTIC EASE AND QUALITY**

### M.A.T. TRANSISTORS MAKE THIS WONDERFUL PERFORMANCE POSSIBLE.

These amazing new Micro Alloy Transistors take transistor performance into entirely new fields by their coverage of A.F., I.F., R.F., and V.H.F. frequency bands, they provide far greater gain for less power consumption so that two MAT Transistors can do the work of three ordinary types with considerable saving in space, components and cost. Each one is carefully tested before leaving the factory. For full description, send for our book "22 TESTED CIRCUITS USING MICRO-ALLOY TRANSISTORS", price 5/9, including postage.



Long gold-plated leads assure perfect contact.

MAT 100 7/9 MAT 101 8/6  
MAT 120 each MAT 121 each

Comprises brand new sub-miniature components, genuine MAT TRANSISTORS, elegantly designed plastic case and calibrated tuning control with high-quality featherweight earpiece; also thoughtfully presented step-by-step instructions.

AND STILL THEY COME IN! MORE CONSTRUCTORS WRITE . . . "Building was quite easy. I have used my 'Slimline' in cars and on trains and it has been remarkably efficient." C.V.L., Gillingham "The quality from the earpiece provided is excellent. Have brought in dozens of stations on this set . . . a most companionable little receiver."

T.L.B., London, N.8 "Quite fantastic. I would never have thought quality, selectivity and volume could be so good from so small a set. It looks smart, too." E.K.H., Basingstoke

To SINCLAIR RADIONICS LTD., 69 HISTON ROAD, CAMBRIDGE

Please send Parts for building Sinclair "Slimline" Micro-Radio Receiver . . . . .  
 "22 Tested Circuits Using Micro Alloy Transistors" . . . . .  
 . . . . .MAT 100 . . . . .MAT 120 . . . . .MAT 101 . . . . .MAT 121 Transistors  
 for which I enclose Cash/Cheque/Money Order for £ . . . . .  
 Mark off items required

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

BLOCK LETTERS PLEASE \_\_\_\_\_ RCB

**SINCLAIR radionics LTD**  
**69 HISTON ROAD, CAMBRIDGE**

# SCOTTISH INSURANCE CORPORATION, LTD

38 EASTCHEAP · LONDON · EC3

Established 1877

## THE SHEDDING OF A LOAD

An ACCIDENT can cause serious financial embarrassment. Could you meet your commitments on the National Insurance Benefit?

A "SCOTTISH" Policy will carry the load for you if you are disabled by ANY ACCIDENT and will pay compensation for as long as two years for any one accident.

For a BENEFIT of £10 PER WEEK the premium varies between £2 10s. 0d. and £4 10s. 0d. per annum according to occupation, and the premium can be paid half-yearly or quarterly if desired.

If you will complete and return this form to the Corporation's office at the above address, a quotation will be sent with a proposal for completion, or write for details quoting reference /JB.

NAME (Block Letters).....

OCCUPATION.....

ADDRESS (Block Letters).....

/JB

# EXCITING DESIGNS FOR TRANSISTOR ENTHUSIASTS




## SINCLAIR Micro-Amplifier

OUTPERFORMS TYPES  
20 TIMES LARGER

Smaller than a threepenny piece, this fantastic masterpiece of transistor circuitry has a power gain of 60dB (1,000,000 times) and a response within  $\pm 1$ dB from 30 to 50,000 c/s. Will drive any type of earpiece or even a loudspeaker, and is a valuable tool in the hands of the keen experimenter. Kit is complete with instructions and FREE Circuits and Data showing amplifier used with high and low imp. P.U.s, microphones, stereo headphones, radios, transmitters, etc.

28/6  
complete

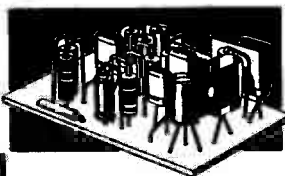

Sensitivity ... 0.5mV  
Power Gain ... 80dB  
(100 million times)  
50-20,000 c/s  $\pm 3$ dB  
Size: 2½" x 1½" x ¼"

59/6

## SINCLAIR TR.5 FIVE TRANSISTOR COMBINED PRE-AMP. AND HALF-WATT POWER AMPLIFIER

This radically new amplifier employs the latest circuitry techniques to produce a perfectly clean half-watt of audio power even from such low output sources as tape heads, modern pick-ups and microphones. Each amplifier is supplied ready built for immediate use and is unconditionally guaranteed for 12 months.

CIRCUIT—5 matched transistors and a temperature compensating diode in a transformer-less complementary-symmetry configuration.

POWER OUTPUT—500mW undistorted into a 15Ω loudspeaker.

POWER REQUIREMENTS—10mA quiescent and 150mA peak from 9V battery or power supply.

### READY BUILT AND TESTED

with each amplifier. Circuits and Data showing how to use the TR5 with low and high imp. P.U.s, tape heads microphones, in many different radio circuits, as a guitar amplifier, as hi-fi mono or stereo amp. with only tone controls added, as powerful intercom., etc.

# Sinclair Radionics Ltd

DEPT. RC85

69, HISTON ROAD, CAMBRIDGE

FREE

# HOME RADIO of MITCHAM

DEPT. RC, 187 London Road, Mitcham, Surrey. MIT 3282

Shop hours 9.0 a.m. to 6 p.m. (Wed. 1 p.m.)

## TRANSFILTERS

Transfilters are ceramic filters which take the place of tuned i.f. transformers in transistor superhets. As they operate at the first overtone of their fundamental frequency it is advisable to precede them with one conventional tuned circuit. Three types are available: TO-01 Resonant tuned, TO-02 Anti-resonant tuned, and TF-01 which is a two-connection type that replaces the emitter by-pass capacitor and gives increased selectivity. Further details are available in "Transistor Circuits for the Constructor" No. 4, price 3/6, postage 1/6.

The following transfilters are in stock:


TO-01 A	455KC	7/6
TO-01 B	465KC	7/6
TO-01 D	470KC	7/6
TO-02 A	455KC	7/6
TO-02 B	465KC	7/6
TO-02 D	470KC	7/6
TF-01 A	455KC	6/-
TF-01 B	465KC	6/-
TF-01 D	470KC	6/-

WE STOCK THE FULL RANGE OF THE NEW MULLARD POLYESTER CAPACITORS.

WE HAVE A COMPLETE RANGE OF ALL HEATHKIT MODELS IN STOCK



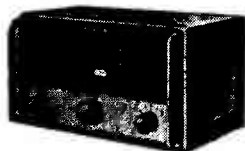We have a large selection of Communications Receivers, both new and second-hand, with a full range of new Eddystone Receivers including the model 960 which is completely transistorised



## CEIBALINE

A sound-absorbing material made by Kapok Ltd. This is the perfect material for lagging the inside surfaces of high fidelity loudspeaker enclosures to improve quality of sound reproduction. It is rot proof, fire resistant and will not support moths or other insects. It is easily cut to size with scissors and has a special self-adhesive backing for instant fixing. It is made only in a width of 2ft 9in and costs 2/6 per square foot. Set out below is a table of prices.

33" x 4" ...	2/6	33" x 40" ...	22/6
33" x 9" ...	5/-	33" x 45" ...	25/-
33" x 13" ...	7/6	33" x 49" ...	27/6
33" x 18" ...	10/-	33" x 53" ...	30/-
33" x 22" ...	12/6	33" x 57" ...	32/6
33" x 26" ...	15/-	33" x 62" ...	35/-
33" x 31" ...	17/6	33" x 66" ...	37/6
33" x 36" ...	20/-		



of this famous catalogue  
**NOW READY!**

- \* 200 PAGES plus a page of useful formulae
- \* Over 800 illustrations
- \* Over 5,000 components clearly listed and priced



This is the 4th Edition and 8th reprinting of our Catalogue. In addition to enlarging it we have re-arranged many sections for easier reference. Customers who purchased earlier editions will need no encouragement to obtain this one. To new customers we would point out that of 5,000 items listed all but 14 are actually in stock, and that this unique catalogue is backed by a Mail Order Service second to none!

Obtainable only from

**HOME RADIO OF MITCHAM**

ONLY  
**2'6**  
PLUS 1' POST AND PACKING

POST COUPON TODAY  
Write CATALOGUE on top left of envelope.  
Enclose P.O. 3/6

Name .....

Address .....

Home Radio Ltd. (RC), 187 London Road, Mitcham, Surrey

# THE Radio Constructor

Incorporating THE RADIO AMATEUR

Vol. 17, No. 1

Published Monthly

Annual Subscription 30/-  
(including postage)

*Editorial and  
Advertising Offices*  
57 MAIDA VALE LONDON W9

*Telephone*  
CUNningham 6141  
(2 lines)

*Telegrams*  
Databux, London

## AUGUST 1963

Superhet Transistor Radio Receiver, <i>by P. Green</i>	12
Suggested Circuits No. 153: Low-Cost Variable Voltage Power Unit <i>by G. A. French</i>	18
Low-Cost High Fidelity Amplifier, <i>by G. A. Stevens</i>	21
Can Anyone Help?	26
Inexpensive Medium and Short Wave Receiver, <i>by Ian Macdonald</i>	27
News and Comment	31
Understanding Radio, Part 24, <i>by W. G. Morley</i>	32
An Electric Thermometer, <i>by K. Berry</i>	36
Trade Review, Sound Effects Records	39
In Your Workshop	40
Book Review	45
High Quality Modulator Design, <i>by D. Noble, G3MAW and D. M. Pratt, G3KEP</i>	46
An Introduction to Colour Television, Part 3, <i>by J. R. Davies</i>	50
Kit Review, The "Hiker" 4-Transistor Portable Receiver	55
Single Transistor Loudspeaker Receiver, <i>by Sir Douglas Hall, K.C.M.G., B.A.(Oxon.)</i>	57
Two-Transistor Timer with Positive Feedback, <i>by M. D. Devenish</i>	59
Preparing Radio Panels, <i>by J. Anderson</i>	61
Identifying Surplus American Electronic Equipment, <i>by Ken Greenberg</i>	62
Radio Topics, <i>by Recorder</i>	64

© Data Publications Ltd, 1963

CONTENTS may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgment of source is given.


TECHNICAL QUERIES must be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

CONTRIBUTIONS on constructional matters are invited, especially when they describe the construction of particular items of equipment. Articles should be written on one side of the sheet only and should preferably be typewritten, diagrams being on separate sheets. Whether hand-written or typewritten, lines should be double spaced. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included. Photographs should be clear and accompanied by negatives. Details of topical ideas and techniques are also welcomed and, if the contributor so wishes, will be re-written by our staff into article form. All contributions must be accompanied by a stamped addressed envelope for reply or return, and should bear the sender's name and address. Payment is made for all material published.

OPINIONS expressed by contributors are not necessarily those of the Editor or the proprietors.

CORRESPONDENCE should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers, as appropriate.

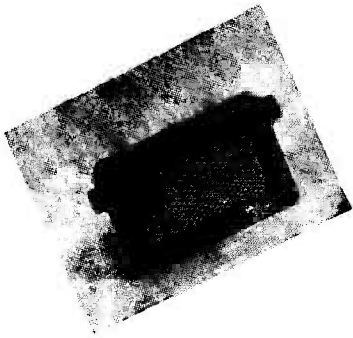REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."



# Superhet Transistor Radio Receiver

By P. GREEN

THE TRANSISTOR RADIO HAS BROUGHT BACK TO the constructor the old days of building his own receiver. Today, the constructor's objective is to build his own transistor set. Many circuits have been published, with articles describing their construction, but these are mostly miniature sets in which the sizes of the speaker and ferrite rod aerial are limited. There are, also, straight and reflex circuits, with which good results can be obtained from local stations.

This state of affairs does not satisfy many constructors, for whom the superhet is the only answer to their requirements. The assembly of a superhet transistor radio is well worth while, and very little

extra effort and expense is involved. Also, the constructor will be much happier with the results.

The design of the transistor superhet described here is a departure from miniature layouts, although the overall dimensions of the receiver (excluding knobs) are still only  $7\frac{1}{2} \times 4\frac{1}{2} \times 2\frac{1}{2}$  in. The cabinet is constructed from a polythene case which is available in various pleasing colours. A 6 x 4 in loudspeaker is employed, and the finer quality of sound available from this relatively large unit is something to be proud of.

## The Circuit

The circuit of the receiver appears in Fig. 1 and,


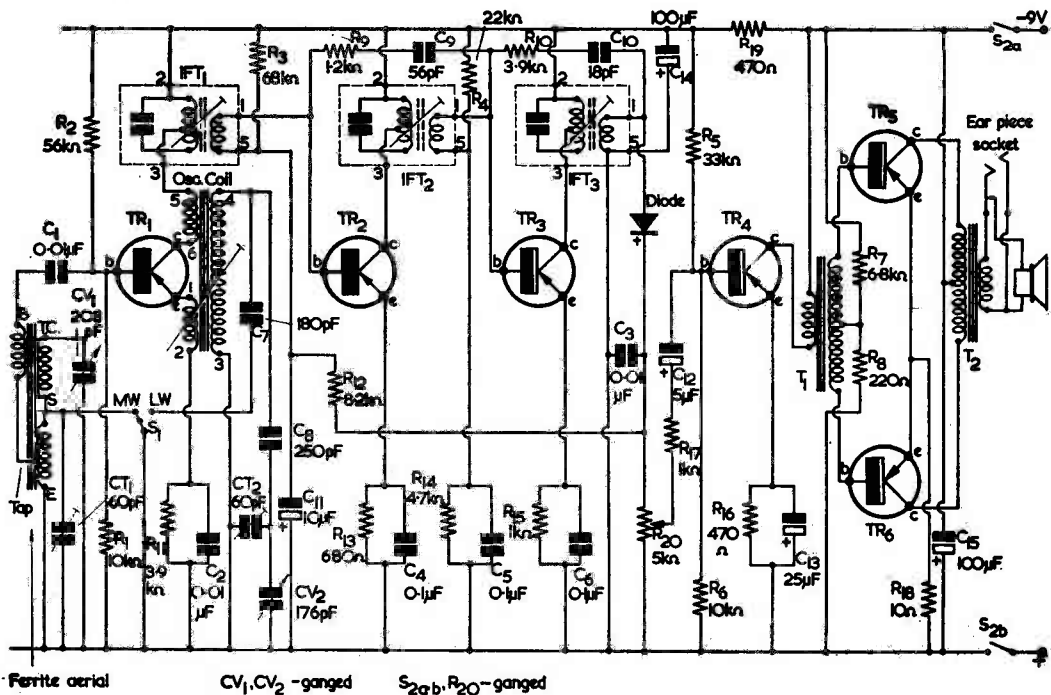


Fig. 1. The circuit of the receiver

as may be seen, it employs a standard superhet design. The ferrite rod aerial couples into the mixer/oscillator transistor TR<sub>1</sub>, in the collector circuit of which is connected the first i.f. transformer IFT<sub>1</sub>. The secondary of IFT<sub>1</sub> feeds transistor TR<sub>2</sub> which, in turn, drives TR<sub>3</sub> by way of IFT<sub>2</sub>. The secondary of IFT<sub>3</sub> couples into the detector circuit provided by diode D<sub>1</sub>, R<sub>20</sub> and C<sub>3</sub>, an a.g.c. voltage being fed back to the base of TR<sub>2</sub> by way of R<sub>12</sub>. The detected a.f. tapped off R<sub>20</sub> is fed, via R<sub>17</sub> and C<sub>12</sub>, to the driver transistor TR<sub>4</sub> which then couples, by way of transformer T<sub>1</sub>, to the output transistors TR<sub>5</sub> and TR<sub>6</sub>.

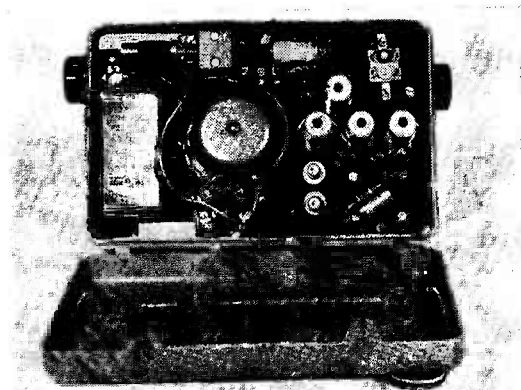It will be noted that the Components List specifies both Ediswan and Mullard transistors. Ediswan transistors were used in the prototype, but the Mullard alternatives may be employed equally well in receivers using the present circuit.



The components inside the case (in this illustration, the long wave ferrite frame coil is shown, incorrectly, with its tag ring on the inside)

### Components List

#### Resistors

(All fixed resistors  $\frac{1}{4}$  watt 10%)

R <sub>1</sub>	10k $\Omega$
R <sub>2</sub>	56k $\Omega$
R <sub>3</sub>	68k $\Omega$
R <sub>4</sub>	22k $\Omega$
R <sub>5</sub>	33k $\Omega$
R <sub>6</sub>	10k $\Omega$
R <sub>7</sub>	6.8k $\Omega$
R <sub>8</sub>	220 $\Omega$
R <sub>9</sub>	1.2k $\Omega$
R <sub>10</sub>	3.9k $\Omega$
R <sub>11</sub>	3.9k $\Omega$
R <sub>12</sub>	8.2k $\Omega$
R <sub>13</sub>	680 $\Omega$
R <sub>14</sub>	4.7k $\Omega$
R <sub>15</sub>	1k $\Omega$
R <sub>16</sub>	470 $\Omega$
R <sub>17</sub>	1k $\Omega$
R <sub>18</sub>	10 $\Omega$
R <sub>19</sub>	470 $\Omega$
R <sub>20</sub>	5k $\Omega$ miniature volume control (log track) with switch

#### Transistors

TR <sub>1</sub>	XA102 or OC44
TR <sub>2,3</sub>	XA101 or OC45
TR <sub>4</sub>	XB103 or OC71
TR <sub>5,6</sub>	XC101 or OC72 (Matched pair)

#### Diode

D <sub>1</sub>	OA81
----------------	------

#### Switches

S <sub>1</sub>	Wavechange s.p.s.t. (see text)
S <sub>2(a), (b)</sub>	On/off d.p.s.t. (Part of R <sub>20</sub> )

#### Speaker

6 x 4in, 3 $\Omega$  impedance (see text)

#### Capacitors

C <sub>1</sub>	0.01 $\mu$ F
C <sub>2</sub>	0.01 $\mu$ F
C <sub>3</sub>	0.01 $\mu$ F
C <sub>4</sub>	0.1 $\mu$ F
C <sub>5</sub>	0.1 $\mu$ F
C <sub>6</sub>	0.1 $\mu$ F
C <sub>7</sub>	180pF 10%
C <sub>8</sub>	250pF 10%
C <sub>9</sub>	56pF 2%
C <sub>10</sub>	18pF 2%
C <sub>11</sub>	10 $\mu$ F, electrolytic, 6V wkg.
C <sub>12</sub>	5 $\mu$ F, electrolytic, 6V wkg.
C <sub>13</sub>	25 $\mu$ F, electrolytic, 6V wkg.
C <sub>14</sub>	100 $\mu$ F, electrolytic, 12V wkg.
C <sub>15</sub>	100 $\mu$ F, electrolytic, 12V wkg.
CT <sub>1</sub>	60pF trimmer
CT <sub>2</sub>	60pF trimmer
CV <sub>1,2</sub>	176/208pF twin-gang (Jackson Bros type 00, without trimmers or slow motion drive)

#### Inductors

	Ferrite Rod Aerial, Osmor type PW/FR1
	Oscillator Coil (Red), Osmor type PW/01
	IFT <sub>1,2</sub> Osmor type PW/2 (White)
	IFT <sub>3</sub> Osmor type PW/3 (Blue)
T <sub>1</sub>	Driver transformer type LT44, (Clyne Radio Ltd)
T <sub>2</sub>	Output transformer type LT700, (Clyne Radio Ltd)

#### Miscellaneous

	Expanded metal speaker grille, 6 $\frac{1}{2}$ x 3 $\frac{1}{2}$ in
	Earpiece and earpiece socket
	External battery socket (optional)
	Battery type PP6, Paxolin panel
	2 Knobs, Polythene lunch box (Woolworths)
	7 $\frac{1}{2}$ x 4 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in, screws, nuts, rivets, etc.

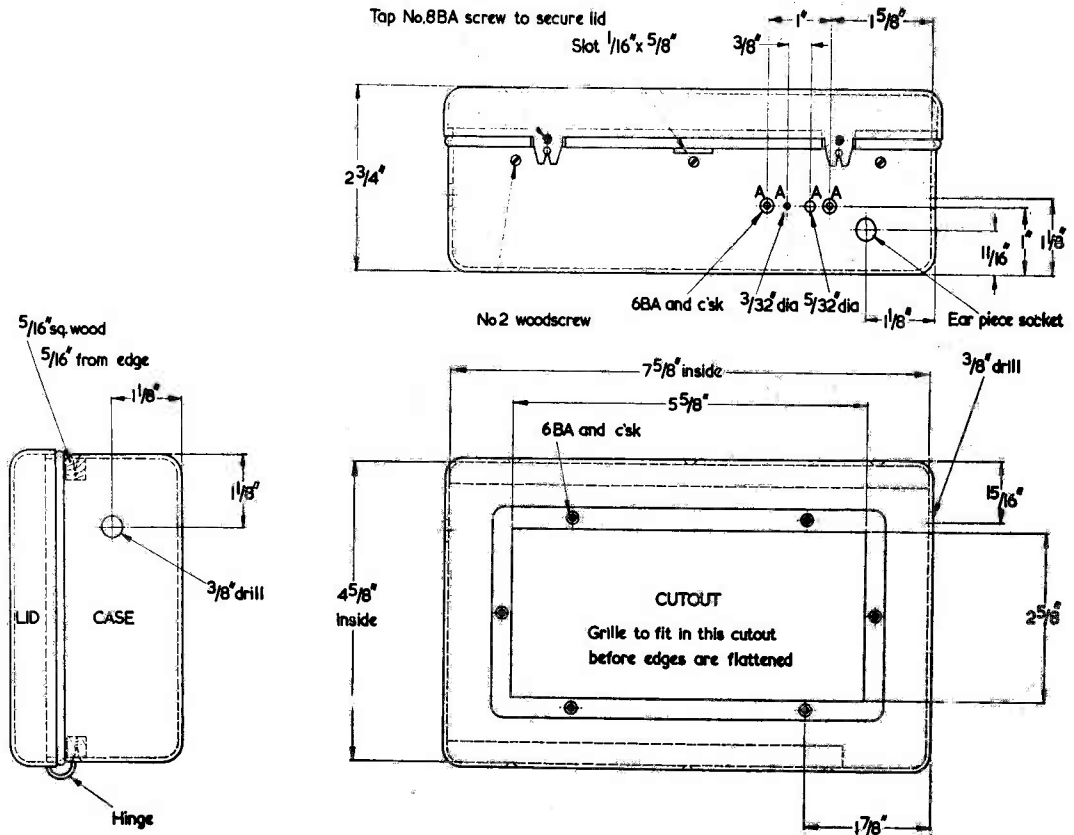


Fig. 2. Drilling and cutting the polythene case. The holes marked "A" should only be drilled if an external supply socket is to be fitted. This point is discussed in the text

**Construction**

Construction may commence with the cabinet. This consists of a converted polythene lunch box (available at Woolworth's stores) which is modified as shown in Fig. 2. The hole in the bottom for the grille can be cut out with a penknife, whilst the other holes must be carefully drilled. Countersinking should be carried out with the drill held in the hand. Note that two pieces of wood  $\frac{5}{16}$  in square are secured to the two long sides of the case. These will later hold the Paxolin panel on which the main components are mounted. The holes marked "A" in Fig. 2 are for an optional socket whose function is described at the end of this article. They should

not be drilled at this stage unless it has been decided to employ such a socket. See under "External Connections".

The baffle board (Fig. 3) and speaker grille may now be fitted behind the speaker cut-out. The edges of the grille are flattened so as to fit between the baffle board and the sides of the case, as shown in Fig. 4.

Fig. 5 illustrates the manner in which the speaker, baffle board and Paxolin panel are mounted inside the case. It is essential that the speaker employed has a round magnet having a diameter less than  $2\frac{1}{2}$  in. The speaker must be mounted such that it does not interfere with the semicircular cut-out in

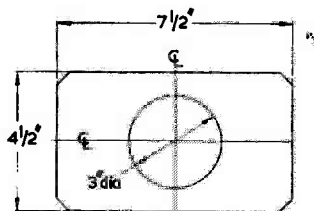


Fig. 3. The baffle board. This is made of  $\frac{1}{4}$  in hardboard

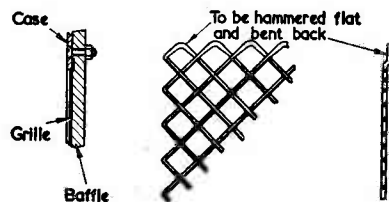


Fig. 4. How the grille is fitted



the Paxolin panel. As may be noted from Fig. 5, the speaker is not mounted centrally on the baffle board.

The Paxolin panel has next to be cut and drilled out, and the requisite dimensions are given in Fig. 6. It will be seen that no dimensions are given for the holes which take the two 60pF trimmers. The writer employed a double trimmer here, but single trimmers may be used instead, if desired.

Next to be made is the tuning capacitor support shown in Fig. 7. This has two 6BA nuts soldered to it in order to facilitate mounting, these corresponding with two holes on  $\frac{1}{2}$ in centres in the Paxolin panel.

The capacitor support is followed by the wave-change switch blade, which is cut out from  $\frac{1}{2}$ in brass. See Fig. 8, which also shows the switch assembly. The contacts shown in this diagram are taken from an old Yaxley switch wafer,  $\frac{1}{8}$ in roundhead copper rivets being employed to fasten these, and the blade, to the Paxolin panel. A washer should be placed on the end of the rivet near the panel before riveting.

The transistor lead-out wires may next be threaded with coloured sleeving for identification, employing

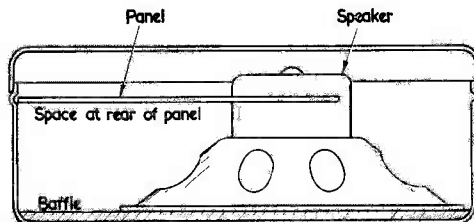


Fig. 5. Internal layout after assembly

red for emitter, green for base, and white for collector. This sleeving will assist in identifying the leads when wiring up.

### Assembly

The assembly of the major components to the Paxolin panel may now commence. Their positions are shown in Fig. 9. It will be seen from this diagram that two double tags are eyeleted to the panel to provide connections for the speaker, and that a further two tags are fitted for the negative and positive supply lines to the board. It is necessary

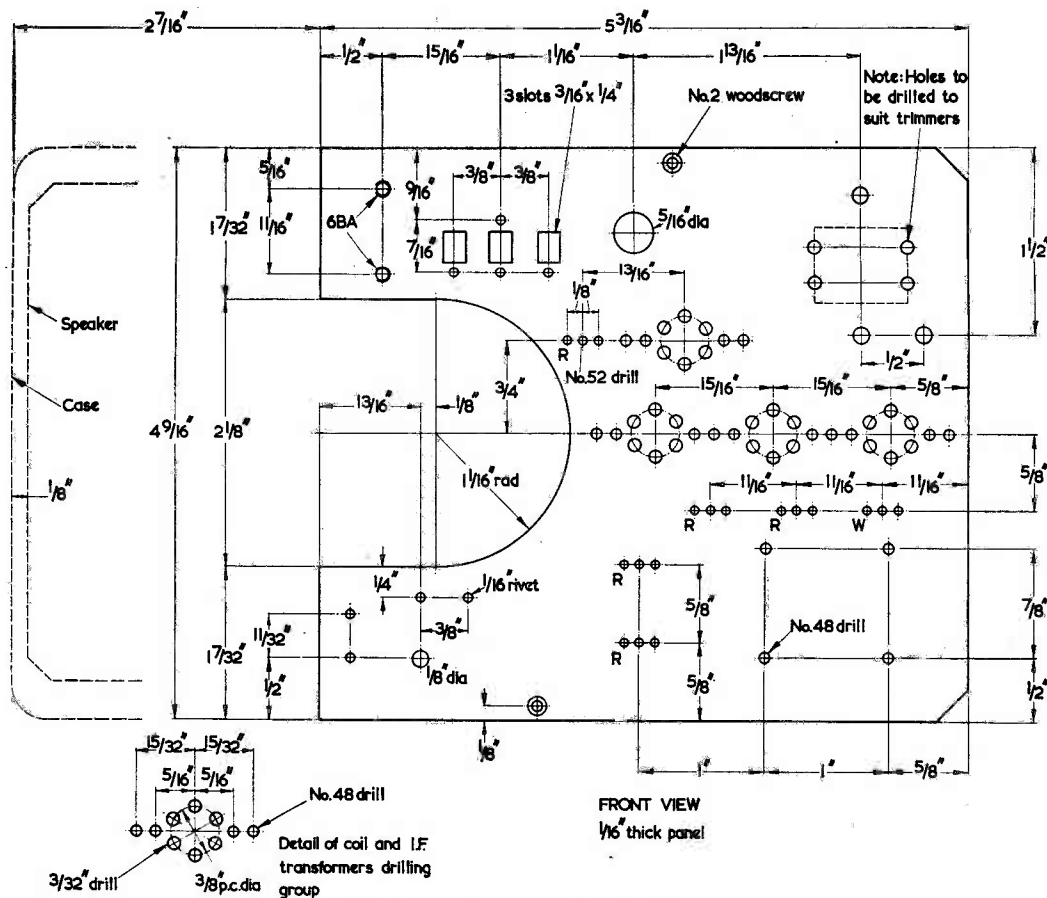


Fig. 6. The dimensions of the Paxolin panel

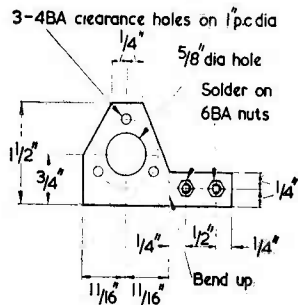


Fig. 7. The tuning capacitor support. The material is 0.032in mild steel

also to provide a mounting for the ferrite frame. As may be seen from Fig. 8 and the illustrations, this mounting was given in the prototype by a fibre clamp, secured by two 6BA screws. The ferrite frame aerial must, of course, clear the Paxolin panel and the wavechange switch contacts. The ferrite rod is not finally mounted at this stage.

The transistor lead-outs are next threaded through the holes provided for them. These holes are identified in Fig. 10 by the letters "W", "G" and "R", which indicate whether the associated sleeving should be white, green or red. The i.f. transformers and oscillator coil may next be fitted, this being done by passing the mounting lugs through the appropriate holes and then back through the adjacent holes as in Fig. 11. Fig. 11 illustrates also how the i.f. coil lugs may be soldered together. The orientation of the oscillator coil and i.f. transformers is shown in Fig. 10. T<sub>1</sub> and T<sub>2</sub> are fitted by passing their mounting lugs through the panel, fitting a washer on each and soldering over. Finally, mount the tuning capacitor to its bracket and bolt this to the panel.

### Wiring Up

A start can now be made in wiring up. Fig. 10 shows the wiring layout of the underside of the

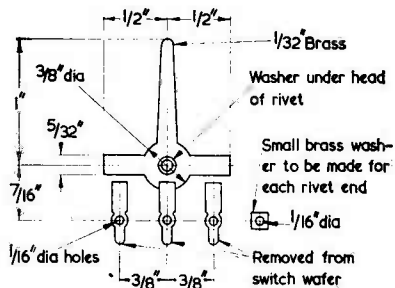


Fig. 8. Details of the wavechange switch

panel. The positive supply line may first be fitted, this connecting to all earthy points. (It may be necessary to temporarily remove the tuning capacitor bracket whilst connecting to the trimmers.) The negative line may next be soldered in, and this can stand off the panel by about 1/4in. Bare 22 s.w.g. tinned copper wire may be used here, and it will become self-supporting after it has been soldered to a few points. Thread on a short length of sleeving at the supply terminal tags, red for positive and black for negative; this will provide a good reminder to avoid mistakes. All the straight direct connections may next be made, employing thin p.v.c. covered wire. A number of capacitors, C<sub>2</sub>, C<sub>4</sub>, C<sub>5</sub> and C<sub>6</sub>, have resistors in parallel with them. These resistors may be primarily soldered across the capacitors and the resulting assembly then soldered into circuit on the panel.

The remaining capacitors, resistors and other components can now be fitted as shown in Figs. 9 and 10, a heat shunt being applied to all transistor leads during soldering. Note that the neutralising components, R<sub>9</sub>C<sub>9</sub>, R<sub>10</sub>C<sub>10</sub> are pre-assembled,

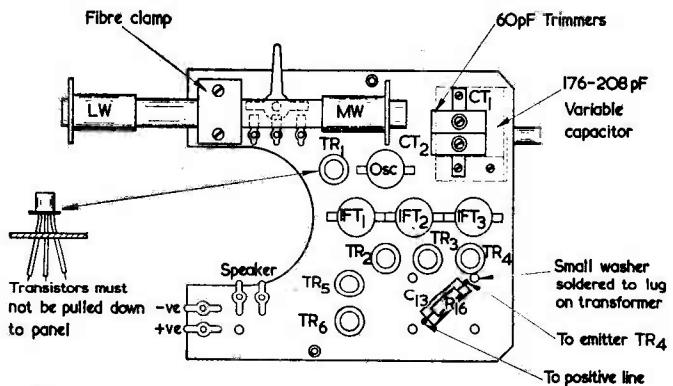


Fig. 9. The principal components above the chassis

and are mounted by connecting the assembly junctions to tag 1 of each i.f. transformer.

The ferrite rod aerial is next fitted to the panel and it is connected into circuit as shown in Fig. 12. Fig. 9 shows the positions taken up by the Medium and Long wave coils on the ferrite rod. The leads from the ferrite rod aerial to the panel components need to be flexible. These leads are approximately 6in long and they pass through the 1/8in hole under the Medium wave coil before passing on to the appropriate circuit points.

After carefully checking all wiring on the panel, this may be fitted into the case, and mounted in place on the wooden sections previously fitted. It should be noted that external connections have to be made to the speaker, the earpiece socket, the volume control and the on/off switch. The earpiece socket is fitted in the position indicated in Fig. 2, and this, with the speaker, is wired up as shown in the circuit diagram of Fig. 1. The connections to the volume control may be made

following Figs. 1 and 10. It should be remembered that the positive and negative supply lines from the panel are connected to the battery via the switch contacts on the volume control. The photograph illustrating the interior of the case shows the layout of the components here. The PP6 battery is fitted with its terminals away from the volume control, in order to prevent short circuits to the metal case or terminals of the latter.

### Testing

When the receiver has been completed it may be tested and aligned. Since the i.f. transformers and oscillator coil are supplied pre-aligned, little adjustment, if any, will be required with these components. I.F. alignment may be carried out with the aid of a modulated signal generator feeding an output at 470 kc/s to the "Tap" tag of the ferrite rod aerial. Signal generator output should be kept as low as possible to avoid a.g.c. voltages masking the effects of core adjustment.

R.F. alignment is carried out in the conventional manner and, as no standard tuning scale is fitted, there should be no necessity to adjust the core of the oscillator coil. The position of the Medium wave coil on the ferrite rod should be adjusted for optimum


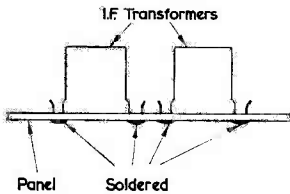
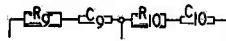


Fig. 11. The method of securing the i.f. transformers and oscillator coil

signal strength for a signal at the low frequency end of the Medium waveband, trimmer  $CT_2$  then being adjusted for optimum results at the high frequency end. This procedure may need to be repeated several times for best overall results. On the Long waveband, set the tuning capacitor to receive the Light Programme on 1,500 metres (200 kc/s) and adjust  $CT_1$  and the position of the Long wave coil on the ferrite rod for optimum results. If more accurate tracking is required, on this band, the position of the coil may be adjusted at the low frequency end of the band, and  $CT_1$  adjusted at the high frequency end.
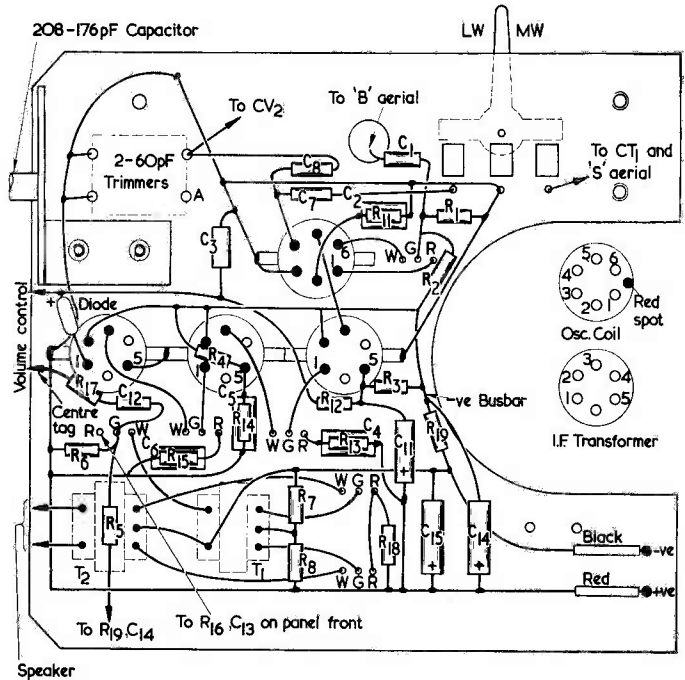
### External Connections

As has already been stated, a socket is available



This combination to be soldered in at tag no. 1 on each I.F. transformer

Fig. 10. The wiring on the underside of the panel


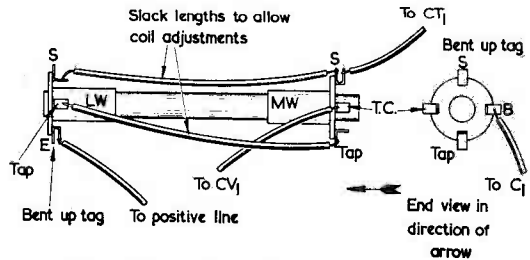



Fig. 12. Connections to the ferrite rod aerial

for an earpiece. Such a socket may also be employed for connection to an external loudspeaker.

It is also possible, with the prototype, to connect an external battery, should this be desired. A 2-way socket is fitted to the holes marked "A" in Fig. 2, whereupon the external battery may be plugged in at this point, as shown in the accompanying illustration. The use of a large external battery may prove economical, if the receiver is to be employed for long periods. The dimensions for the "A" holes given in Fig. 2 apply to the particular plug and socket employed by the writer, and may be modified for alternative plugs and sockets. It is important, however, to employ non-reversible types in order to ensure that the external battery is not applied with incorrect polarity.

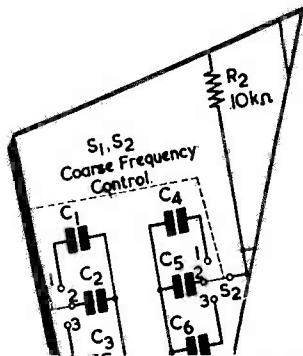

## suggested circuits

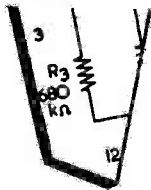

The circuits presented in this series have been designed by G. A. French, specially for the enthusiast who needs only the circuit and essential data

### No. 153 Low-Cost Variable Voltage Power Unit

**A**N H.T. POWER UNIT WHICH is capable of offering a wide range of readily adjustable voltage outputs is always a useful item of equipment in the experimenter's or service engineer's workshop. Usually, such devices tend to be based on stabilised power pack principles and are, in consequence, somewhat expensive. This month's Suggested Circuit is for a simple h.t. power unit which is capable of providing a range of output voltages from about 60 to 350 (according to load and the secondary voltage of the mains transformer employed) at currents up to 50mA or more. The unit requires few more components than are needed in a conventional half-wave rectifier circuit, and it may in consequence be built at little greater cost. No voltage stabilising techniques are employed and the regulation of the circuit is considerably poorer than would be given in a fully stabilised unit. In practice, the regulation is about twice as bad, at some output voltages, as that of a conventional half-wave power unit. It is felt that this is not, for many applications, a serious disadvantage, and that it is counter-balanced by the low cost of the unit and its simplicity.

#### The Circuit

The circuit of the power unit is shown in Fig. 1, and it will be

noted that it employs a mains transformer having a single wave h.t. secondary winding which offers a voltage between 200 and 250. This voltage is applied to the anode and screen-grid of a PL81, the cathode being connected to the reservoir capacitor  $C_1$ . The rectified voltage across  $C_1$  is smoothed by the choke (or smoothing resistor) and  $C_2$ , and is then applied via the current reading meter to the output terminals. A shunt voltmeter monitors the output voltage. The grid of the PL81 is connected to the slider of  $R_2$ , this latter component being the variable voltage control.

To explain the action of the circuit, it is helpful to commence with the half-cycle which causes the anode and screen-grid of the PL81 to go negative of chassis. Under this condition the control grid is also negative, and the valve passes no current.

On the following half-cycle the anode and screen-grid go positive. So also does the control grid, the positive voltage here varying according to the position of the slider of  $R_2$ . In consequence, cathode-follower action takes place, and the voltage on the cathode becomes dependent upon that on the control grid.

Since it only conducts during positive half-cycles, the PL81 functions also as a rectifier. In common with normal half-wave rectifiers

it then causes charging pulses to be fed to the reservoir capacitor during each positive half-cycle. It is whilst the reservoir charging currents flow that the grid potential takes control, and the setting of  $R_2$  then governs the actual voltage to which the reservoir capacitor charges. When the slider of  $R_2$  is at the bottom end of its track, the rectified voltage across  $C_1$  is at minimum. When the slider of  $R_2$  is at the top of its track, the voltage across  $C_1$  is maximum.

#### Choice of Valve

Although the circuit is extremely simple in basic principle, a number of difficulties arise with respect to the valve chosen.

The first requirement of the valve is that it should be capable of passing a high current; and the most suitable types generally available which meet this requirement are audio output valves or line output valves. At the same time the valve is subject to high peak inverse voltages. In general, line output valves are more capable of working with such voltages than are audio output valves and it is for this reason that a PL81 is suggested here.

For a 250 volt h.t. secondary the maximum possible p.i.v. on the anode and screen-grid of the valve (relative to cathode) is 700 volts. Maximum p.i.v. figures are not, of

course, available for the PL81, and it is possible that the valve is over-run in the present circuit. When the slider of  $R_2$  is at the top of its track, a p.i.v. of 700 volts on the control grid (relative to cathode) may also appear. The PL81 has a maximum negative grid voltage rating of 1kV, but this is under line output conditions in which the voltage has a maximum duration of 18 $\mu$ S only. In consequence, there may, again, be over-running of the valve.

In order to check these points, the author employed a PL81 in a prototype circuit with a transformer having a secondary voltage of 300. The PL81 performed quite satisfactorily, and there was no evidence of any trouble due to the high voltages applied to its electrodes. In consequence it would seem reasonably safe to employ a PL81 in similar circuits, particularly if the secondary voltage is not greater than 250; i.e. 50 volts less than that used by the author for checking the circuit. Due to the possibility of over-running the valve, however, the author cannot *guarantee* that other PL81's will behave in similar manner, and the circuit is experimental in this respect.

The PL81 is intended for series operation and has a heater voltage of 21.5 at a current of 300mA. This voltage is not available from standard transformers, and it may be necessary to add a suitable heater winding to an existing transformer, or to obtain the voltage by other means. There are a number of transformers available on the component and surplus markets which could be pressed into service (with, perhaps, series resistors) to provide a heater voltage for the PL81. An alternative idea would consist of employing an EL81 (with a heater voltage of 6.3 at 1.05A) instead of the PL81. However, the EL81 is not exactly equivalent to the PL81 although it is employed, generally, in similar line output circuits. The EL81 cannot, therefore, be *guaranteed* as being entirely reliable in the present circuit, and its use must be considered as being experimental also.

These factors may make some experimenters consider the inclusion of a fuse to protect the circuit in case of valve failure. Such a fuse could be inserted between the upper terminal of the mains transformer h.t. secondary and the anode and screen-grid of the valve. Since it will also be passing reservoir capacitor ripple current, the fuse will need a value somewhat higher than the smoothed current drawn

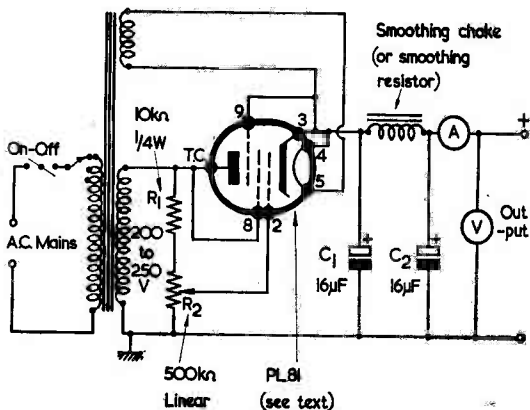


Fig. 1. The circuit of the variable voltage power unit

from the output terminals of the unit.

A resistor,  $R_1$ , is inserted between the upper end of  $R_2$  and the upper terminal of the secondary. The purpose of this resistor is to prevent the control grid from reaching the same potential as the anode and screen-grid when high output voltages are required. If the control grid were to have the same potential as the anode and screen-grid a relatively heavy positive grid current may flow and this would be an undesirable feature.

It is necessary to connect one side of the heater to the cathode of the valve to ensure that the maximum heater-cathode potential is not exceeded. With the PL81 this is 200 volts, whilst the corresponding figure for the EL81 is 100 volts. The transformer heater winding insulation must be capable of withstanding the rectified voltages which appear between the valve cathode and chassis.

The PL81 has a maximum cathode current of 180mA, but, due to the low regulation of the unit, it would be impracticable to draw a current as heavy as this from the present circuit. A maximum current around 50mA would seem to be a reasonable figure, and this can be provided by a number of inexpensive mains transformers with single wave h.t. secondaries. The range of output voltages available will then, of course, depend upon that given by the secondary.

#### Other Components

The remaining components in the circuit require little comment.

Either a smoothing choke or a smoothing resistor may be employed, according to the experimenter's wishes. A 1.2k $\Omega$  component rated

at 3 watts should be satisfactory for a smoothing resistor. The use of a resistor will, of course, degrade the regulation of the circuit but not, for most requirements, by an excessive amount.

A current reading meter in series with the positive output terminal is a desirable adjunct, and it is very helpful for determining circuit conditions in equipment fed by the unit. Such equipment could, for instance, be initially connected to the unit with  $R_2$  slider set to the bottom end of its track.  $R_2$  slider could then be slowly advanced, the current drawn by the equipment being monitored by the meter as the h.t. voltage increases. The current reading meter could have a full-scale deflection of 50 or 100mA.

A voltmeter across the output terminals is also shown, but many experimenters will probably dispense with this and rely upon a testmeter connected across the output terminals whenever the power unit is employed. If a voltmeter is fitted to the unit, it is assumed that it will have a sensitivity of around 1,000 $\Omega$  per volt, which is quite adequate for the present purpose. Such a voltmeter will then also function as a bleeder resistor, and will discharge  $C_1$  and  $C_2$  when the power unit is switched off or when  $R_2$  slider is changed to a lower setting. If the voltmeter is not incorporated it would be advisable to fit a bleeder resistor in its place. For the present application, a value around 220k $\Omega$  at 1W would be adequate. It should be mentioned that some form of bleed is essential as, otherwise, the output voltage may remain at a high figure even after  $R_2$  has been adjusted for a low output voltage

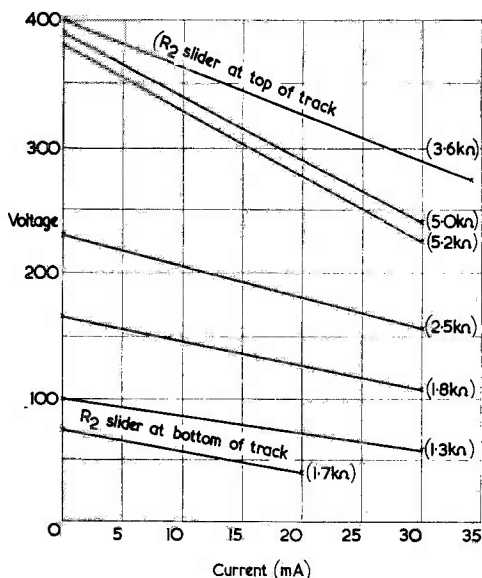


Fig. 2. Voltages obtained under no-load and loaded conditions with the prototype

A 220kΩ bleeder gives a time constant of about 8 seconds in conjunction with  $C_1$  and  $C_2$ , and this figure should be adequate with a simple circuit of the type under discussion.

No working voltage is specified for  $C_1$  and  $C_2$ , as these depend on the h.t. secondary voltage of the mains transformer employed. The working voltage should be 350 for secondary voltages between 210 and 250. For secondary voltages below 210 the working voltage may be 300.

The potentiometer,  $R_2$ , is a conventional carbon track component.

#### Results With The Prototype

As was mentioned above, the circuit was checked with a prototype, the secondary voltage of the transformer employed being 300. To provide severe operating conditions for the PL81,  $R_1$  was omitted, the upper end of  $R_2$  being connected directly to the upper terminal of the transformer secondary. The secondary resistance of the transformer employed was fairly high, at 450Ω, whilst the primary resistance was 100Ω. Voltages across  $C_1$  were measured for varying loads and for various settings of  $R_2$ .

The results are given in Fig. 2. It will be noted that, off load,

the voltages across  $C_1$  varied between 75 and 400 according to the setting of  $R_2$ . Also shown are the voltages resulting from various loads, the currents drawn being mostly at 30mA. Each straight line joins the voltages given under no-load and loaded conditions for a particular setting of  $R_2$  and its slope shows the regulation resistance under these conditions, this resistance being indicated at the right hand side. Thus, one line demonstrates that a voltage of 100 off load drops to 60 when a current of 30mA is drawn. Under these conditions, therefore, 30mA corresponds to a voltage drop of 40, and results in a regulation resistance of 1.3kΩ. The same effect would be given by a 1.3kΩ resistor in series with a 100 volt supply having perfect regulation. The resistance inserted by the transformer, say 600Ω, contributes to the regulation resistance, and this figure could be subtracted from the regulation resistances shown in Fig. 2, if a more accurate picture of circuit performance were required.

It will be seen that regulation resistance is fairly low for voltages below 240 or so, and that it then gets progressively higher as voltage increases. This corresponds, to some extent, to the performance given by a conventional half-wave rectifier circuit. The regulation resistance increases—but not to an unusable value—at the higher voltages, and it then reduces slightly when  $R_2$  slider is at the top end of its track. It is possible that this final improvement is the result of the onset of grid current (which is prevented, in Fig. 1, by the inclusion of  $R_1$ ).

Throughout the tests with the prototype, the PL81 functioned correctly and gave rise to no trouble.

## Building contract placed for new BBC and VHF sound relay station for Shetland

The B.B.C. announces that a contract has been placed with Messrs. Pearson & Tawse Ltd., of Angusfield, Aberdeen, for the construction of the buildings for the new Shetland television and v.h.f. sound relay station which is to be built at Ward of Bressay, some three miles south-east of Lerwick, and for its associated receiving station at Fitful Head. The Shetland station will receive its programme for re-transmission from the B.B.C.'s Orkney station. The Orkney transmission will be picked up at Fitful Head from where the television programmes will be fed by radio link and the three sound programmes by Post office line to the Shetland relay station.

The Shetland station is one of a number of additional stations which the B.B.C. is building to extend and improve the coverage of its television and v.h.f. sound services. The date for the start of the service is dependent upon the completion of the buildings, on which work has now started, but it is hoped to have the new station in operation within about twelve months.

By  
G. A. STEVENS

# Low-Cost High Fidelity Amplifier

*The difficulties involved in constructing a high fidelity amplifier at low cost are well known to audio enthusiasts. This article describes an ingenious approach to the problem and its author offers some thought-provoking views on the subject of the output transformer.*

RECENTLY, THE WRITER HAD TO DESIGN A SERIES of 10 watt amplifiers to professional standards and driven at the normal level for such equipment, i.e. OdBm (or 1mW across a 600 $\Omega$  resistor). This is, in terms of voltage, 775mV. It was important to make each amplifier as cheaply as possible whilst still retaining the highest standards of performance, and considerable care was devoted to designing a circuit with these ends in view. The final design was capable of being built for £6 to £7 only.

The most expensive items in any normal power amplifier are the inductors; these comprising the mains and output transformers and the smoothing choke. Since no compromise could be made in the choice of mains transformer, all economies had to be carried out on the smoothing choke and output transformer. Now, whilst in normal domestic audio amplifiers R-C smoothing has virtually ousted the use of chokes, this is not considered adequate in professional equipment in view of the stringent signal/noise ratio required. However, after several trials it was found that by double-decoupling the supply to the output stage, professional requirements could be met without the use of a choke, the only additional cost being that incurred by using a triple instead of a double capacitor. Since the triple capacitor was available at low cost, there was a considerable saving in cost and space.

## The Output Transformer

The output transformer presented a more difficult problem. A transformer designed to sell cheaply means that the manufacturer has had to make economies, particularly in the amount of iron used for the core. This in turn limits the power output, especially at low frequencies, due to magnetic saturation of the core material. However, if a given transformer can deliver 10 watts at 1 kc/s it will be satisfactory if, at the lower frequency limit (about 30 c/s), it can deliver not less than 25% of its rated output, which in this case is 2.5

watts. If the sounds that make up normal speech or music are analysed into their respective frequencies, it can be shown that, for a 10 watt composite signal, the low frequency components form usually less than 1 watt. Obviously the ratio varies with different types of programme material but even an organ, say, gives very little output at low frequencies where core saturation is liable to become evident. Also, since the full 10 watts of the amplifier would not normally be used except to handle transients, which by their nature contain little low frequency components, an additional amount of power becomes available.

Another difficulty arises due to the presence of negative feedback, which includes the transformer. Due to too low a primary inductance at low frequencies, and to too high a leakage inductance and capacitance at high frequencies, a cheap transformer gives rise to phase shifts in an amplifier which can cause peaks in the response, and eventually, if too much feedback is applied, oscillation or squegging. However, by designing an amplifier so that its phase shifts compensate for those in the transformer, and by deliberately controlling the frequency response, quite large amounts of feedback can be applied. In the present design, 19dB of feedback is applied over the main loop and, although the output transformer cost less than a £1, no core saturation took place from 30 c/s upwards for powers of 5 watts or less, giving thereby a very adequate power response at low frequencies. At high frequencies the loop gain of the amplifier is reduced by  $C_3$  to avoid instability. Also, a transformer was chosen with an untapped secondary giving a 15 $\Omega$  output only (since most high grade speakers are of this impedance) and the simplification of the secondary winding reduces the leakage inductance.

An important consideration in keeping the cost down was in the choice of valves. Whilst double valves (viz. ECL82, ECL86) would initially be cheaper, when one section aged or developed a fault the whole unit would have to be replaced.

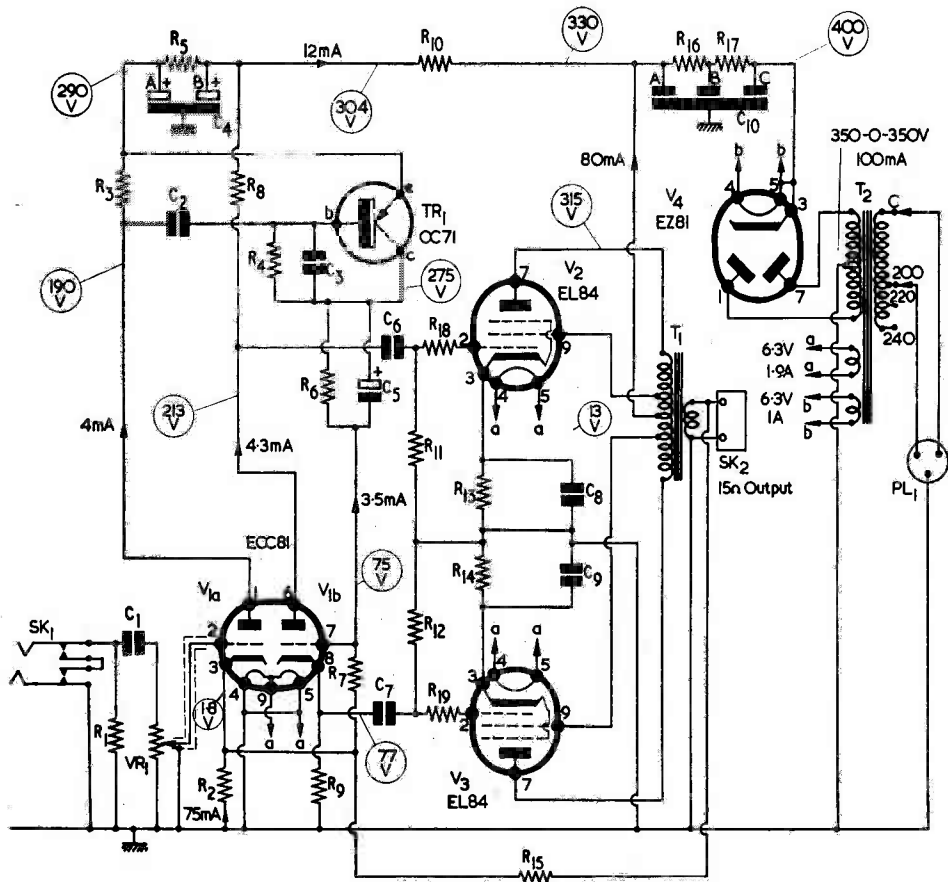


Fig. 1. The circuit of the amplifier, showing voltages and currents at various points. Voltage readings were taken with a Model 8 Avometer (20,000Ω per volt) but, since most points in the circuit are at low impedance, a less sensitive meter could be used

### Components List

#### Resistors

R <sub>1</sub>	600Ω	½ watt	10% carbon
R <sub>2</sub>	270Ω	½ watt	5% carbon
R <sub>3</sub>	22kΩ	½ watt	10% carbon
R <sub>4</sub>	470kΩ	½ watt	10% carbon
R <sub>5</sub>	1.8kΩ	½ watt	10% carbon
R <sub>6</sub>	56kΩ	1 watt	10% Carbon
R <sub>7</sub>	22kΩ	½ watt	10% carbon
R <sub>8</sub>	18kΩ	½ watt	1% H.S.
R <sub>9</sub>	18kΩ	½ watt	1% H.S.
R <sub>10</sub>	2.2kΩ	½ watt	10% carbon
R <sub>11</sub>	330kΩ	½ watt	10% carbon
R <sub>12</sub>	330kΩ	½ watt	10% carbon
R <sub>13</sub>	330Ω	½ watt	5% carbon
R <sub>14</sub>	330Ω	½ watt	5% carbon
R <sub>15</sub>	3.9kΩ	½ watt	5% carbon
R <sub>16</sub>	330Ω	5 watts	10% wirewound
R <sub>17</sub>	470Ω	5 watts	10% wirewound
R <sub>18</sub>	1kΩ	½ watt	10% carbon
R <sub>19</sub>	1kΩ	½ watt	10% carbon
VR <sub>1</sub>	1MΩ		pot. log track

#### Capacitors

C <sub>1</sub>	0.5μF, 150V wkg. paper
C <sub>2</sub>	1μF, 150V wkg. paper
C <sub>3</sub>	2,000pF, 5% silver mica
C <sub>4(a),(b)</sub>	16+24μF, 350V wkg. electrolytic
C <sub>5</sub>	1μF, 250V wkg. electrolytic
C <sub>6</sub>	1μF, 250V wkg. paper
C <sub>7</sub>	1μF, 250V wkg. paper
C <sub>8</sub>	250μF, 25V wkg. electrolytic
C <sub>9</sub>	250μF, 25V wkg. electrolytic
*C <sub>10(a)</sub>	80μF, 450V wkg. electrolytic
C <sub>10(b)</sub>	40μF, 450V wkg. electrolytic
C <sub>10(c)</sub>	20μF, 450V wkg. electrolytic

#### Transformers

T <sub>1</sub> *	Output transformer 7000Ω anode-to-anode. Taps at 20%
T <sub>2</sub>	Mains transformer. Secondaries: 350-0-350V at 100mA, 6.3V at 1.9A, 6.3V at 1A. (Ellison type MT127 would be suitable)



**Valves**  
 V<sub>1</sub> ECC81  
 V<sub>2</sub> EL84  
 V<sub>3</sub> EL84  
 V<sub>4</sub> EZ81

**Transistor**  
 TR<sub>1</sub> OC71

**Sockets**  
 SK<sub>1</sub> Jack socket  
 SK<sub>2</sub> Small speaker output socket

**Tagboards**

2 off, vertical mounting, each with two rows of 16 tags

Since the output valves have to be replaced more frequently due to their high dissipation, the final choice consisted of a pair of EL84's. Here again, separate cathode bias resistors were used so that the cathode currents are automatically balanced without having to choose matched valves, this also avoiding the need to change both valves should one fail.

**The Circuit**

As may be seen from Fig. 1, a transistor is employed in the early stages of the amplifier. By using a transistor, a stage gain in excess of 500 may be obtained without trouble with induced hum from the heaters. Due to its low input impedance the transistor has to be driven by one half of an ECC81 (V<sub>1(a)</sub>). V<sub>1(a)</sub> offers nothing towards the amplification of the circuit. Indeed there is a reduction in the a.f. voltage from the grid to the anode but this is unimportant since the function of this stage is purely to provide a current

drive to the transistor. The voltage attenuation serves to reduce the overall noise and hum caused by V<sub>1</sub>, as well as microphony.<sup>1</sup> The output impedance of V<sub>1(a)</sub>, together with its linearity, is improved by leaving the cathode bias resistor R<sub>2</sub> unbypassed, this also providing a convenient point for the application of the main feedback loop. The signal is then fed via C<sub>2</sub> into the base of the transistor TR<sub>1</sub>. Since TR<sub>1</sub>, in order to be able to drive the phase splitter fully, has to have 15 volts between emitter and collector, it is advisable to use only first grade transistors here, and not any of the surplus variety which have very large characteristic spreads and may easily break down. The bias for the transistor is provided by R<sub>4</sub> which compensates for the normal spread of characteristics, and which provides negative feedback. The signal is now d.c. coupled to the grid of V<sub>1(b)</sub>. The

<sup>1</sup> The overall gain from the grid of V<sub>1(a)</sub> to the grid of V<sub>1(b)</sub> is about X100-200 (including an approximate loss of X3 in V<sub>1(a)</sub> due to the function of this valve as a current generator).—EDITOR.

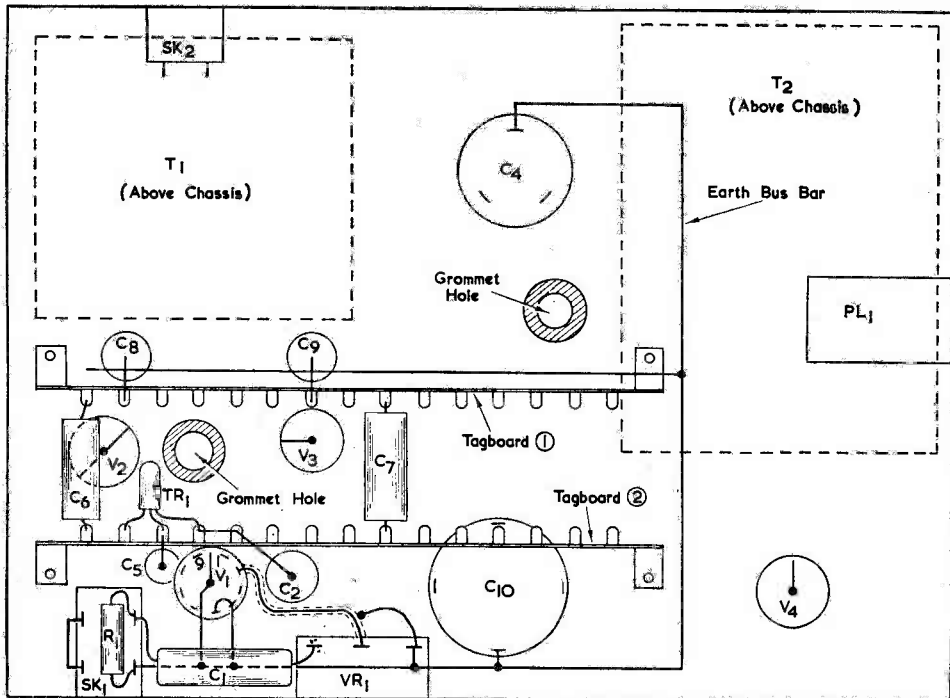


Fig. 2. The layout of the main components below the chassis

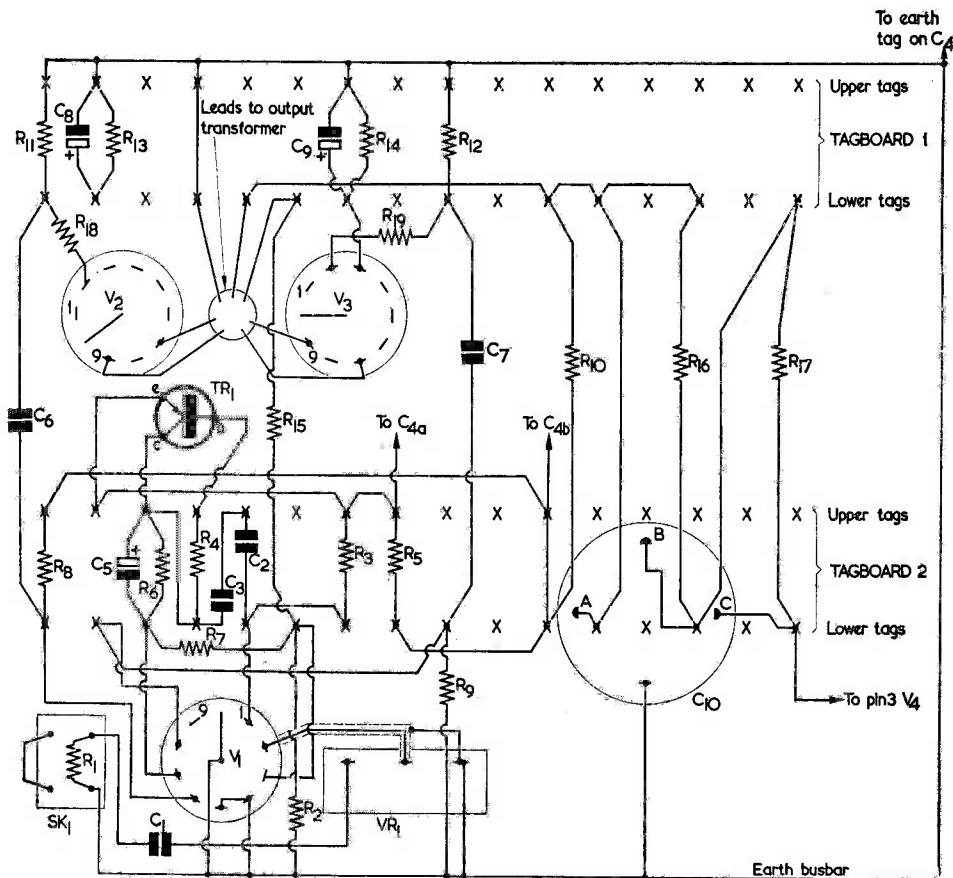


Fig. 3. The wiring and components around  $V_1$ ,  $V_2$  and  $V_3$ . In this diagram the tagboards are shown opened out flat, individual tags being indicated by crosses

divider chain  $R_6R_7$  is coupled to the upper end of  $R_2$  in order to help provide correct bias for  $V_{1(a)}$  whilst keeping the value of  $R_2$  down in order that it shall not produce too much reduction of gain.

Although the original amplifier was designed to work from a 775mV signal across 600 $\Omega$ , the sensitivity may be improved by the substitution of an OC75 for the OC71 in the  $TR_1$  position.  $R_1$  can, also, under these circumstances, be completely removed since it only serves to match the low impedance output source from the pre-amplifier with which this unit was intended to be used.

$V_{1(b)}$  functions as a conventional split load phase-splitter. Its outputs, from anode and cathode, are fed to the control grids of the two output valves  $V_2$ ,  $V_3$ , via their respective coupling capacitors.

The output stage is of the distributed load type with the screen-grids tapped at 20% along the windings. The cathodes of the valves are each separately biased and decoupled to help balance the currents through the output transformer. The values of the decoupling capacitors  $C_8$  and  $C_9$  have been made large by usual standards, in order

to improve the phase response at low frequencies. Modern capacitors are now made as physically small as units having a tenth of the capacitance several years ago, and those specified do not take up excessive space. One side of the 15 $\Omega$  output to the speaker is earthed, the other being connected via  $R_{15}$  to the cathode of  $V_{1(a)}$  to provide the main feedback loop.

The power supply is conventional, using R-C smoothing throughout. As previously explained, the use of double decoupling ( $R_{16}R_{17}C_{10}$ ) ensures that hum level is reduced to a very low level, and it should be mentioned that, by employing a 350V transformer, the smoothing resistors can be made sufficiently large in value to allow for a 70V d.c. drop across them. Since the amplifier only consumes about 92mA there is sufficient reserve to feed about 5-10mA from  $C_{10(a)}$  to a pre-amplifier if needed.

#### Construction

The amplifier was built on an aluminium chassis measuring 7 x 10in, as shown in the layout diagram, Fig. 2. No trouble should be found in construction provided this layout is followed. Sufficient space

has been left around both transformers to allow for variations in their size without cramping any other component. Whilst it was not needed in the original, a base plate on the chassis might be useful if the amplifier is mounted above any other unit that may radiate hum into the wiring. So far as the reduction of hum is concerned, there are one or two important wiring points that should be adhered to. The first of these concerns the earthing in the amplifier. All earths are taken to a J-shaped busbar made of 16 s.w.g. tinned copper, one end of which connects to the earth tag on SK<sub>1</sub> (the input jack socket), the other end terminating at the earth tag of C<sub>4</sub> as illustrated in Fig. 2. Both C<sub>4</sub> and C<sub>10</sub> should be isolated from the chassis either by putting tape between their cans and their mounting clips or, as in the writer's amplifier, by the use of prong mounting capacitors mounted on insulated plates. The upper row of tags on tagboard 1 are also connected to the main busbar by another length of 16 s.w.g. wire, see Fig. 2. The chassis connection to the busbar is made via a tag placed under one of the fixing screws for V<sub>1</sub> valveholder.

The heaters of V<sub>1</sub>, V<sub>2</sub> and V<sub>3</sub> are connected by a tightly twisted pair of wires, and the only connection to chassis is at pins 4 and 5 of V<sub>1</sub> to the busbar. It was found that centre-tapping the heaters made no appreciable difference in the hum level compared with that given by the present method, and so this simpler scheme was adopted.

The only other point in the construction that is not immediately apparent from the layout diagrams is that one of the fixing holes for tagboard 1 is under the mains transformer, and so it should be countersunk and the tagstrip mounted before the transformer is fitted. The wiring layout for the main components on the tagstrips is given in Fig. 3.

### Performance

When the wiring is completed and checked, the amplifier may be turned on and the voltage checked against those marked in the circuit diagram. Small

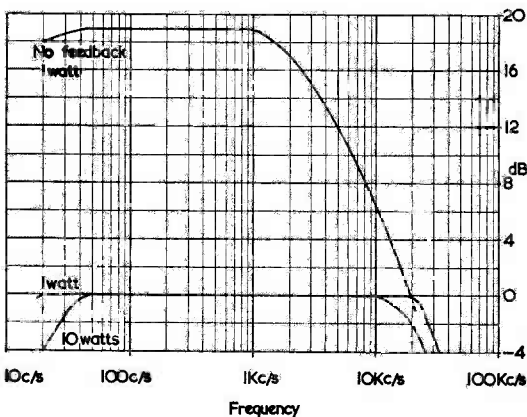


Fig. 4. The frequency response of the amplifier

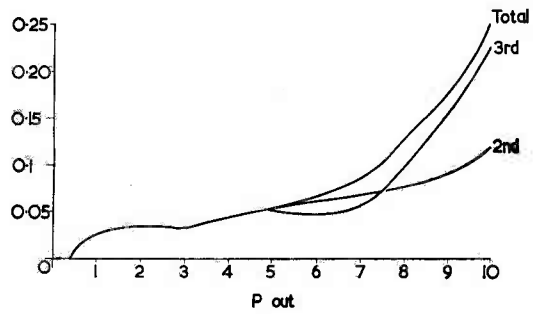


Fig. 5. Distortion at 1 kc/s

differences are to be expected but large variations should be investigated, as they indicate either faulty components or wiring errors. Particular care must be taken with the circuitry associated with the transistor. If, on switching on, the amplifier breaks into oscillation, it should be switched off at once, and the connections to the secondary of T<sub>1</sub> should be reversed.

TABLE  
Amplifier Performance

Power Rating*	10 watts
Frequency Response*	Below 10 c/s to 30 kc/s ±3dB
Distortion*	0.1% at 7.5 watts output
Input Level	0dBm (1mW across 600Ω) =775mW
Signal/Noise Ratio	-90dB (0dB=10 watts)
Feedback (in main loop)	19dB

\* Measured with continuous sine wave drive. With normal speech or music the maximum output, and output level for a given distortion, will be increased by a factor of 10 to 20%.

The distortion and frequency response figures of the original amplifier are shown in Figs. 4 and 5.



The power response was taken at 10 watts, but although the feedback maintained the output voltage down to 25 c/s, core saturation caused distortion of the wave shape and so, as previously stated, the power level should be restricted to about 4 to 5 watts at these frequencies.

Even with the ear placed close to the speaker enclosure the hum and noise level was completely inaudible. Since the earlier versions of the ECC81/12AT7 used to be rather prone to microphony, the amplifier was checked for this by tapping the valve gently, whereupon the microphonic noise was almost inaudible. In normal use no microphony

was apparent at all.

All the relevant performance figures are set out in the Table. Unfortunately, due to lack of a suitable generator, it was not possible to plot the response below 20 c/s, but at this figure the phase and amplitude response was so good that the response must extend down to a much lower frequency before falling off. Since the application of a continuous sine wave shifts the d.c. working points of the valves, the power ratings given in the power output and distortion figures will be improved by a considerable factor with normal speech and music.

## CAN ANYONE HELP?

*Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.*

**Bosch Car Radio.**—P. A. Booker, 6 The Ridings, Hare Hill, Addlestone, Surrey, would like the circuit and data of this 12V American model X636-12. Valve line-up 77, 77, 78, 75, 42, 84.

\* \* \*

**Indicator Unit Type 97.**—P. N. Roberts, 31 George Frederick Road, Sutton Coldfield, Warks, requires the circuit or manual.

\* \* \*

**Raymond TV Model F11B.**—H. Wildash, 4 Bibury Avenue, Woodhouse Park, Wythenshawe, Manchester, 22, wishes to acquire the service sheet or manual, also the present address of the manufacturer.

\* \* \*

**Minivox C Tape Recorder.**—R. Hutchinson, 102 Durley Avenue, Pinner, Middx, requires the circuit diagram. Also would like to receive information on the construction of a mains unit to eliminate the batteries.

\* \* \*

**R.G.D. Mk.103 Tape Recorder.**—R. J. Ridge, 13 Sycamore Drive, Finchfield, Wolverhampton, Staffs, would like to borrow or purchase the operating instructions and/or circuit diagram for this recorder.

\* \* \*

**Philips Radiogram BX600A.**—A. Jaques, 185 Bisham Road, Blackpool, Lancs., requires the service sheet for this Dutch built chassis.

\* \* \*

**Indexes.**—R. K. Lloyd, Box 1164, Lusaka, North Rhodesia, Central Africa, would like to obtain indexes for *The Radio Constructor* 1961 and 1962; *Practical Wireless* from 1950 onwards and *Wireless World* 1950 to 1955 inclusive.

**TR5043 Unit.**—C. Hall, St. Peter's College, Saltley, Birmingham, 8, would like to buy or borrow the circuit diagram and any other information in respect of this unit which comprises the BC625A transmitter and the BC624A receiver.

\* \* \*

**BC348.**—E. A. Bilton, 26 Beulah Hill, London. S.E.19, requires the circuit or manual, borrow or purchase.

\* \* \*

**Receiver type R100-URR.**—M. P. Donaghy, P.O. Box 790, Salisbury, Southern Rhodesia, urgently requires the circuit or manual, together with any modification details.

\* \* \*

**Twin Tube Unit 110QB/13.**—A. G. Gaunt, 6 The Bungalows, Leeming Bar, Northallerton, Yorks., is in need of any information with respect to this unit—especially interested in conversion of this, or an old B.B.C. only TV receiver, to an oscilloscope—*all letters answered.*

\* \* \*

**R1224A Receiver.**—F. Bending, "Seychelles", 108 St. Katherines Road, Exeter, Devon, would like to purchase the service manual of this battery operated receiver.

\* \* \*

**Band I (40 Mc/s).**—J. Newgas, Madison Lodge, Compton Avenue, London, N.6. Will any reader who has developed any circuits for a cheap transistor receiver or a crystal radiation detector please contact the above reader.

# Inexpensive Medium and Short Wave Receiver

by Ian Macdonald

Our contributor describes a three valve receiver covering the Medium and Short wavebands which will be of particular interest to the experimenter. A special feature of the receiver is a novel reaction circuit which allows very simple coils to be employed

**T**HIS RECEIVER IS INTENDED BOTH FOR BEGINNERS and for experimenters. Although the design employs only one tuned circuit, it performs well on both the bands covered. In the prototype, coils for the Medium and Short waveband are used, but it is possible to wind coils to cover other ranges as well, should this be desired.

## The Circuit

The circuit appears in Fig. 1. In this diagram,  $V_1$  functions as a leaky-grid detector, the associated grid capacitor and grid leak being  $C_3$  and  $R_3$ . The cathode of  $V_1$  taps, via  $S_2$ , into either  $L_1$  or  $L_2$ , whereupon the circuit takes up the form of an electron-coupled oscillator. This configuration allows the provision of reaction whilst employing coils which consist of a tapped tuned winding only. Reaction control is effected by potentiometer  $R_1$ , which varies the voltage on the screen grid

The aerial connection is made at the cathode. It will be noted that, as with reaction windings, no aerial coupling windings are needed at all.

Capacitors  $C_5$  and  $C_6$  bypass r.f. voltages appearing at the anode of  $V_1$ .<sup>1</sup> This anode is coupled, via screened cable, to  $C_7$  and, thence, to the grid of  $V_2$ . The anode and screen grid of  $V_2$  are strapped together, with the result that this valve functions as a triode a.f. amplifier, the signal on its anode being passed, by way of  $C_{10}$ , to the volume control  $R_8$ . A further r.f. bypass component is provided by  $C_9$ . The slider of  $R_8$  connects to the grid of output valve  $V_3$ , which feeds the speaker in conventional manner.

The receiver circuit does not include a power

<sup>1</sup> It is possible that a single 200pF capacitor, connected at the anode in the  $C_5$  position, would function as well as the two 100pF components shown.—EDITOR

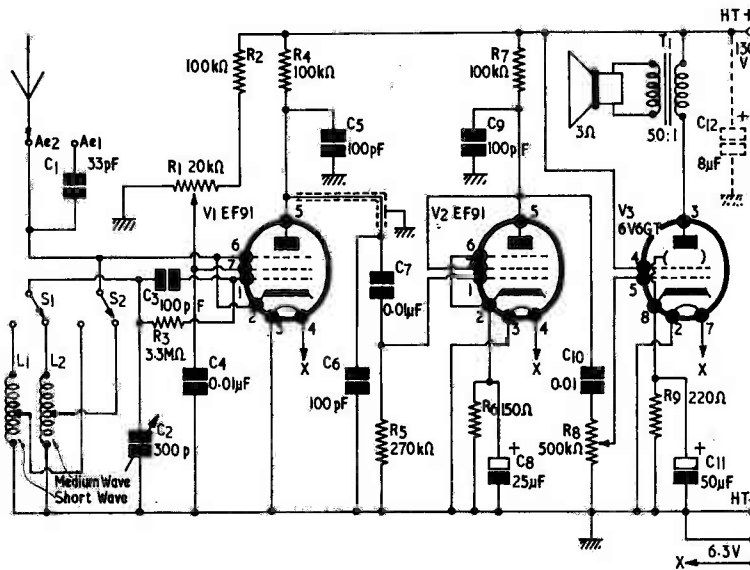


Fig. 1. The circuit of the receiver. In the practical layout, resistor  $R_4$  connects to the anode of  $V_1$  at the remote end on the screened cable

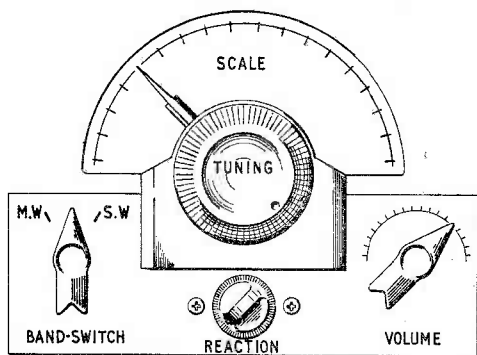


Fig. 2. The layout of the controls



Above-chassis view of the receiver

supply, as it is felt that many constructors will either have a suitable supply already available, or have access to a receiver or similar item of equipment which can provide the voltages needed.

The power requirements of the receiver are 6.3V at 1.05A for the heaters, and approximately 130V h.t. at 35mA. The h.t. supply should have a smoothing capacitor connected across its output terminals. If such a capacitor is not fitted, an additional  $8\mu\text{F}$  capacitor should be connected between the h.t. positive line and chassis in the receiver itself, as shown, in dotted line, by  $C_{12}$  in Fig. 1. Such a capacitor may be desirable, in any case, if the leads to the power supply are long.

### Construction

The large components are mounted as shown in Figs. 3 and 4. Some of the resistors and capacitors are mounted on a 12-way tagboard positioned on the underside of the chassis, whilst the remainder are mounted between the valves and the coils.

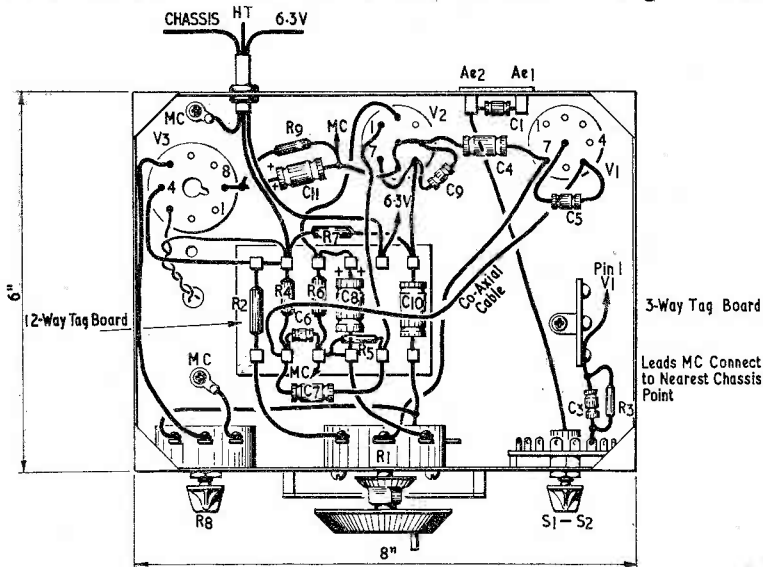


Fig. 3. The principal components below the chassis

The layout shown in Fig. 3 should be followed as closely as possible, and wiring should be kept short. Coaxial cable is used between the anode of  $V_1$  and  $C_7$  to prevent undesirable feedback. A slow-motion drive for  $C_2$  is necessary as tuning is sharp. Any drive may be utilised, and that employed in the prototype was removed from an R1132A receiver, obtainable on the surplus market. This gives a ratio of 36:1 and has proved very successful. The loudspeaker is not shown as it is mounted externally. A cabinet may, of course, be built to house both the receiver and speaker if desired.


### Coil Design

Coil design is of a very simple nature, since each coil consists of one winding only, with a tap for the cathode connection.

Regardless of the frequency coverage, all coils employed with this circuit should have the tap approximately one quarter of the total number of turns from the earthy end of the winding.

The Short wave coil is wound with 20 s.w.g. enamelled copper wire, and consists of 15 turns. The first 8 turns are wound on the former, and the next 7 turns are interwound with these. The tap then appears on the 12th turn. The finish of the winding is the earthy end of the coil. The former is of  $\frac{3}{4}$ in diameter, the winding being spaced over a length of  $\frac{3}{4}$ in on the former. (See Fig. 5 (a)).

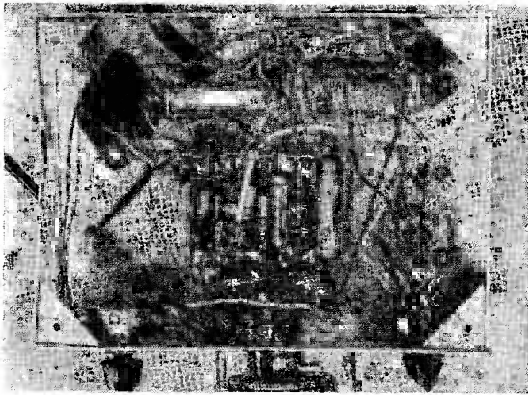The coil for Medium waves employs 32 s.w.g. d.c.c. copper or litz wire. It consists of 100 turns, wound in 10 layers of 10 turns each. The complete coil



Showing layout of components below the chassis

covers a length of lin on a lin diameter Paxolin former. The coil was impregnated in wax after completion, as shown in Fig. 5 (b).

Aerial coupling windings were tried but found unnecessary. The set performs satisfactorily with coils of the type just described up to 35 Mc/s. On frequencies higher than 35 Mc/s the receiver becomes unstable and difficult to tune properly. It will, however, operate very well on low frequencies down to about 500 kc/s.

#### Aerials

Two socket positions are provided. Ae1 is the Short wave aerial connection and Ae2 is the Medium wave aerial connection. However, the Ae2 socket may be used for all bands if prevailing reception conditions are good.

A long wire of about 40 feet using single 5 amp mains flex will work satisfactorily on Medium waves, and on Short waves up to 10 Mc/s. For higher frequencies the aerial should be shorter for best results.

#### Operation

The loudspeaker is connected directly to the output transformer by means of a twisted flex. If phones are preferred, a socket to suit a normal jack plug can be fitted on the rear panel of the chassis behind V<sub>3</sub>.

The tuning scale employed in the prototype is marked in degrees (i.e. 0 to 180) and a calibration chart can be made by logging the stronger stations and noting their frequencies. Alternatively, the dial can be calibrated directly.

The Medium wave coil described is tunable from 200 to 400 metres, due partly to the low capacitance in C<sub>2</sub>. If it is required to tune over the whole of the Medium waveband it would be preferable to make S<sub>1</sub> and S<sub>2</sub> a 3-way switch and fit an extra Medium wave coil.

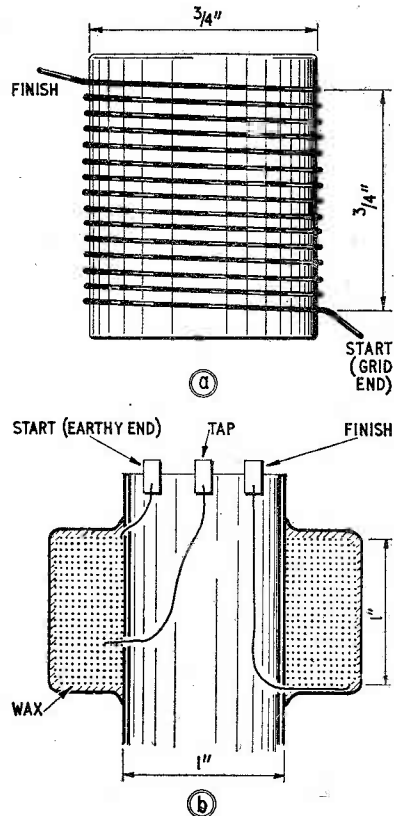


Fig. 5 (a). The short wave coil, L<sub>1</sub>, for 18 to 35 metres. This comprises 15 turns of 20 s.w.g. enamelled copper wire, the last 7 turns being interwound between the first 8 turns. The cathode tap (not shown here) appears at the 12th turn from the start

(b). The medium wave coil, L<sub>2</sub>, which covers 200 to 400 metres. It consists of 100 turns of 32 s.w.g. d.c.c., or litz, wire wound in ten layers of 10 turns each. The tap is made 25 turns from the start

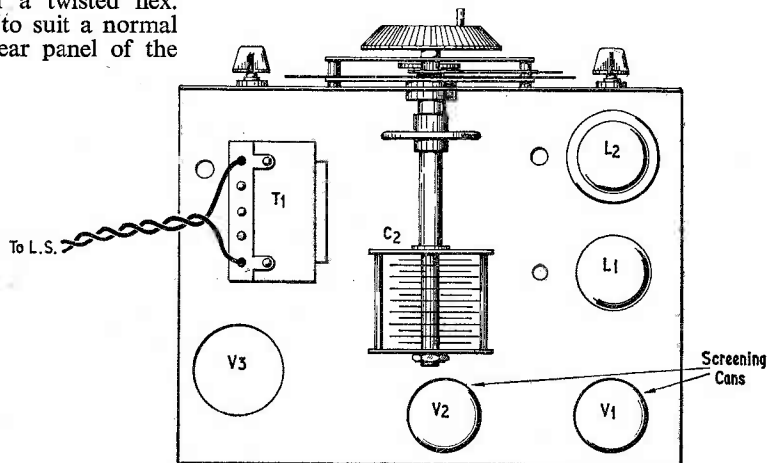


Fig. 4. The above-chassis layout

One coil could then tune from 200 to 400 and the other from 350 to 700 metres.<sup>2</sup>

Many constructors may wish to dispense with the Medium wave coil and fit an extra Short wave coil instead. The coil described here tunes from 18 to 35 metres approximately. Experimenting with different coils for the Short waves can be very interesting. So long as the comments concerning coil winding given here are borne in mind,

no difficulties should be experienced.

The wavechange switch can have as many ways (up to 6-way) as required, this enabling different coils to be switched in.

<sup>2</sup> The relatively low coverage on Medium waves may be partly due to a high self-capacitance in the coil, and this could be reduced by dispensing with the wax impregnation. Increased coverage would be given, also, by employing a larger capacitor in the C<sub>2</sub> position.—  
EDITOR.

### Components List

#### Resistors

(All fixed resistors  $\frac{1}{2}$  watt unless otherwise stated)

- R<sub>1</sub> 20k $\Omega$  wirewound pot
- R<sub>2</sub> 100k $\Omega$
- R<sub>3</sub> 3.3M $\Omega$
- R<sub>4</sub> 100k $\Omega$
- R<sub>5</sub> 270k $\Omega$
- R<sub>6</sub> 150 $\Omega$
- R<sub>7</sub> 100k $\Omega$
- R<sub>8</sub> 500k $\Omega$  pot, log track
- R<sub>9</sub> 220 $\Omega$ ,  $\frac{1}{2}$  watt

#### Capacitors

- C<sub>1</sub> 33pF, silver mica
- C<sub>2</sub> 300pF variable
- C<sub>3</sub> 100pF, silver mica
- C<sub>4</sub> 0.01 $\mu$ F, paper
- C<sub>5</sub> 100pF, silver mica
- C<sub>6</sub> 100pF, silver mica
- C<sub>7</sub> 0.01 $\mu$ F, paper
- C<sub>8</sub> 25 $\mu$ F, 12 V wkg., electrolytic
- C<sub>9</sub> 100pF, silver mica
- C<sub>10</sub> 0.01 $\mu$ F, paper
- C<sub>11</sub> 50 $\mu$ F, 12V wkg., electrolytic
- C<sub>12</sub> 8 $\mu$ F, 250V wkg., electrolytic (if required—see text)

#### Inductors

- L<sub>1</sub> Short wave coil—see text
- L<sub>2</sub> Medium wave coil—see text
- T<sub>1</sub> Speaker transformer, ratio 50:1

#### Valves

- V<sub>1</sub> EF91
- V<sub>2</sub> EF91
- V<sub>3</sub> 6V6GT

#### Switches

- S<sub>1</sub>, S<sub>2</sub> 2-pole 2-way single wafer wavechange switch

#### Miscellaneous

- 2 B7G valveholders with skirts and screening cans
- 1 International octal valveholder
- 1 Slow motion gear, dial and knob, with spindle coupling
- 3 Pointer knobs (2 only if R<sub>1</sub> is type shown in illustration)
- 1 Aerial socket panel
- 1 12-way tagboard (See Fig. 3)
- 1 3-way tagstrip (See Fig. 3)
- 1 Chassis 8 x 6in, aluminium

## EMI TV CAMERAS PROVIDE SHOW PREVIEW

Visitors to the British Industries Fair in Zurich will be able to see a preview of some of the principal exhibits before they enter the exhibition.

Nine EMI closed-circuit television cameras, positioned at suitable points in the three main exhibition halls, will transmit pictures of the various stands and displays to receivers erected in the main entrance hall of the Hallenstadion.

The latest EMI Type 8 all-transistor cameras will be used. These cameras are completely self-contained and will be linked directly by co-axial cable to a bank of nine standard domestic TV receivers in the entrance hall.

In general the cameras will show panoramic views of the exhibition but some will be fitted with special lenses which will allow close-up shots of display details.

Among the special events which will be televised on closed-circuit by the cameras will be the official opening ceremony on 2nd September.

## BRADFORD TECHNICAL COLLEGE

### Department of Engineering

Courses will be held for City and Guilds Radio Amateurs' Examination (Lecturer: D. M. Pratt, G3KEP) and G.P.O. Amateur Radio Morse Test (Instructor: A. W. Walmsley, G3ADQ) during the 1963-64 session on Wednesday evenings from 7 to 9 p.m.

The Morse class may only be attended if a pass has been obtained in the Radio Amateurs' Examination.

The fee for each course is £1 10s. (over 18). There is no fee for students under the age of 18.

Registration takes place from 6.30-8.30 p.m. on Monday and Tuesday, 9th and 10th September, at Bradford Technical College, Great Horton Road, Bradford 7.

Further details of the courses may be obtained from G3KEP.



# News and Comment

## I.A.R.U.

Some 80 delegates, representing 18 European countries, attended the recent International Amateur Radio Union Region 1 conference in Malmo, Sweden. These conferences are held every third year in a different country and at them matters affecting amateur radio are discussed and recommendations made to the respective national societies.

Such topics as the relationship between amateur bands and the new Geneva Radio Regulations; the European Band Plan with special reference to top band; rules for Dx and v.h.f. contests; co-operation of amateur scientific observers with professional workers during the International Quiet Sun Year; Radio Amateur Emergency Networks (a paper on this subject was given by our Managing Editor, Dr. Arthur C. Gee, G2UK); Amateur Radio News Bulletins, etc.

At the opening session, one of the subjects which aroused particular interest was the "intruder watch" operated on behalf of the Radio Society of Great Britain by Major Haylock, G3ADZ. Major Haylock and a group of short wave listeners monitor the amateur bands and check on all unauthorised radio transmissions which appear in them. The frequencies of these are measured and they are identified if possible, details being sent via the R.S.G.B. to the G.P.O., who endeavour to check such illegal activity if they possibly can do so. It was hoped by delegates at the conference that somewhat similar schemes could be brought into action by other national amateur radio societies.

The "intruder watch" is another of those R.S.G.B. services which rarely attracts the attention of the average radio amateur enthusiast, but which has in its quiet way done much to remove jammer and offending commercial stations, broadcast station harmonics, etc. from the amateur bands.

## Electronic Ear

Two Californian brothers—a neuro-surgeon and the head of an electronics firm—have devised an electronic ear that has given hearing to a woman born completely deaf. John and James Doyle now hope

to perfect techniques which will give hearing to many more people who cannot be helped by standard hearing aids.

In a series of experiments, Dr. John Doyle, of the University of Southern California School of Medicine in Los Angeles, implanted his brother's electronic device in the skull of nine patients, all of whom were able to discern sounds afterwards. The artificial ear weighs only two ounces and causes no discomfort when recessed into the skull.

An outside microphone picks up sounds, and the device stimulates an auditory nerve deep within the cochlea, an internal passage of the human ear. This in turn, transmits the sound to the brain.

James Doyle says his device works with totally deaf persons whose auditory nerves were thought to be completely inactive. He is now working on a thinner version of the artificial ear, which it should be possible to implant under the skin without recessing it into the skull.

## Road Safety Record

From an idea by F. C. Judd, A.Inst.E., a popular contributor to this magazine and author of our recently published *Radio Control for Models*, the first gramophone record on road safety has been created. The stars of the record are Jack Warner, known to 15,000,000 viewers as P.C. Dixon of Dock Green, and Coco the Clown, O.B.E., otherwise Nicholai Poliakov, circus idol of children everywhere.

*The two stars have given their services free and donate the entire royalties of the record sales to charities.*

The script for Jack Warner's recording was written by F. C. Judd, who also produced the master sound tracks, complete with authentic effects.

Few people know that Jack Warner is an experienced racing driver and knows only too well the hazards that face everyone who takes a vehicle on the roads of Great Britain today. He began his working life as a motor mechanic and after studying motor engineering,

became a car testing driver in France, which accounts for his familiarity with the French language.

Coco, O.B.E., of Bertram Mills Circus, International clown and author is known to millions of children everywhere. Of equal merit is his work for Road Safety, which began as the result of a serious accident to a child. It is this story that Coco tells on the record; "The Story of Charlie" which carries a vital message to all children. The recording was made by F. C. Judd when Coco told the story to some 300 young children at a school in South London. This is a story that must be told to every child and only the soft appealing voice of Coco can impart the vital message it contains.

Coco has won many awards for his road safety campaign. He is a star driver and a Knight of the Road, but his most coveted is the Order of the British Empire bestowed upon him recently for one of the most outstanding efforts on the part of one man to keep death off the roads.

Further information may be obtained from: F. C. Judd, 174 Maybank Road, South Woodford, London, E.18. Telephone: BUCK-hurst 9315.

## Simultaneous Translating System

The Westminster Theatre, London, will, it is believed, be the first theatre in the United Kingdom to install a simultaneous live translating system which will enable parties of 25 or more foreign visitors to follow the action of the play in their own language.

Some months ago, when a party of German visitors visited the theatre to see "Through the Garden Wall", the management hired the translating equipment as an experiment. Each visitor was given a small transistorised receiving set, equipped with earphones, and a German translation of the play was relayed from the projection room. The experiment was so successful that the management decided to install the equipment permanently. The plan is to engage one actor and actress for each of the translations. With the present receivers it will be possible to have four translations of the performance being given at one time. The receivers have a numbered dial and foreign visitors will be informed which number to turn to receive the translation in their own language.

The equipment which has been installed by Phillips is the same in principle as that which is used by the United Nations.

The twenty-fourth in a series of articles which, starting from first principles, describes the basic theory and practice of radio

part 24

# understanding radio

By W. G. MORLEY

**I**N LAST MONTH'S CONTRIBUTION TO THIS SERIES we continued our discussion on iron-cored transformers by examining leakage inductance, transformer efficiency and impedance matching. We shall now carry on to several practical applications of iron-cored transformers.

## Some Practical Applications

Iron-cored transformers are very frequently employed in radio work, and a common application is given in the power supply circuits for valve radio receivers. Valve radio receivers require two sources of supply, one being at a low voltage for the valve heaters and the other being at a high voltage for the high tension circuits. We shall examine heater and high tension circuits in detail when we come to discuss the valve, but it is sufficient for the present purpose to recognise the fact that such supplies are required.

A typical transformer suitable for meeting heater and high tension requirements is shown in Fig. 144 (a). The transformer primary connects to the mains supply via the receiver on-off switch, and the two secondaries feed the heater and h.t. circuits respectively. The heater secondary, or "heater winding", would offer, typically, 6.3 volts at some 0.5 to 1.5 amps; whilst the high tension secondary would normally offer some 200 to 300 volts at currents ranging from 30 to 75mA.

A receiver is normally built on a metal chassis and it is convenient to use the large area of metal this provides as a common point for the various circuits in the receiver. The transformer of Fig. 144 (a) could then be wired up in the manner shown in Fig. 144 (b), wherein one end of each of the secondary windings is connected to the receiver

chassis.<sup>1</sup> This is a practice which will be found in a number of receivers.

A very important feature of the circuit of Fig. 144 (b) is that, whilst the transformer provides the heater and high tension voltages required by the receiver, there is no direct connection between the chassis and the a.c. mains supply. The chassis is completely isolated from the mains supply and there is no risk of shock if it is touched. In consequence, all the metal appendages which are fitted to the chassis, such as knob spindles, chassis mounting bolts, etc., are similarly isolated from the mains supply.

An alternative type of receiver power transformer is illustrated in Fig. 144 (c). In this case, the transformer has a heater secondary only, and the receiver obtains its high tension supply direct from the a.c. mains. Since the mains supply now replaces the high tension secondary, one side of the mains input is connected to the receiver chassis. When compared with Fig. 144 (b) the circuit of Fig. 144 (c) has the advantage of employing a cheaper transformer, and of thereby saving cost. On the other hand, it has the disadvantage that the chassis is now connected to the mains supply and that there is a very real danger of serious shock if the chassis, or any of its metal appendages, is accidentally touched. In consequence, the chassis of a receiver having a power supply circuit such as that of Fig. 144 (c) has to be completely enclosed in an insulating cabinet, and all external metalwork must be isolated from the chassis or suitably covered by insulating materials. In the case of knob spindles, such insulation would be provided

<sup>1</sup> It will be noted that Fig. 144 (b) introduces a new circuit symbol, this representing the receiver chassis.

by the knobs themselves.

The type of transformer employed in the circuit of Fig. 144 (c) is frequently described as a *heater transformer*, since its function is to provide a voltage for the valve heaters only. In general, all transformers which offer power for radio receivers are described loosely as "mains transformers", in order to differentiate them from any other transformers which may be employed in the receiver. When a receiver chassis is connected to one side of the mains supply, as in Fig. 144 (c), the receiver is described as having a "live" chassis.

There is another form of "live" chassis power supply which may be briefly mentioned here. In this, the high tension supply is obtained direct from the mains, as in Fig. 144 (c). The valve heaters are not, however, fed from a heater transformer. They are, instead, wired up in series and connected across the mains supply via a resistor of suitable value. This type of power supply does not employ a transformer and it is often described as a *transformerless power supply* in consequence. As with the circuit of Fig. 144 (c), the chassis is connected to one side of the mains supply and the same precautions against shock have to be observed.

A somewhat dramatic example of what may be achieved with the aid of transformers is offered by the familiar National Grid network which carries electrical power across the country. The potential of the supply appearing across conductors in the National Grid is very high, and a figure of 132,000 volts is quite representative. The Supergrid operates at 275,000 volts, whilst equivalent systems in Sweden and Russia operate at about 400,000 volts. The function of the Grid system is to ensure that power generated at one end of a Grid "transmission line" may be absorbed at the other end with as little loss as possible in the line itself. Such loss will be given by the power dissipated, as heat, in the inevitable resistance in the line by reason of the current which flows through it. It is also desirable, on economic grounds, to employ as thin a conductor for the line as is reasonably practicable. The solution to these two requirements consists of employing a transformer to step up the voltage at the generator end of the line to a very high figure, and of using a second transformer at the receiving end to step the voltage down again, as shown, in simplified form, in Fig. 145. At the generating and receiving ends, there is a low voltage at a high current but, over the line itself, there is a high voltage at low current. In consequence, losses due to the resistance of the line are kept at a low level, and it becomes possible to effectively transmit very large powers by way of conductors which are, themselves, capable of carrying relatively small currents only.

Although this method of operation lies outside the field of radio, the principle involved is of importance. When, in radio work, power has to be transmitted over a cable or a line, it is quite often desirable to keep losses due to the resistance of the cable at a low level by employing a transformer at one or both ends. The cable is then caused to

carry a low current at a relatively high voltage.

### Magnetic Shielding

Because of their leakage inductances, all iron-cored transformers cause a magnetic field to appear about them. In some cases this field may result in an undesired coupling with another iron-cored transformer or inductor, whereupon it becomes necessary to reduce this coupling to an acceptable minimum.

The simplest and most obvious method of reducing the effect of the unwanted coupling is to position the two iron-cored components at a distance from each other. Further alleviation may be obtained by orienting them in relation to each other, and it is usually found that a low coupling is provided when the core axes are at right angles to each other, as in Fig. 146. Another technique consists of winding the transformer which radiates the field in

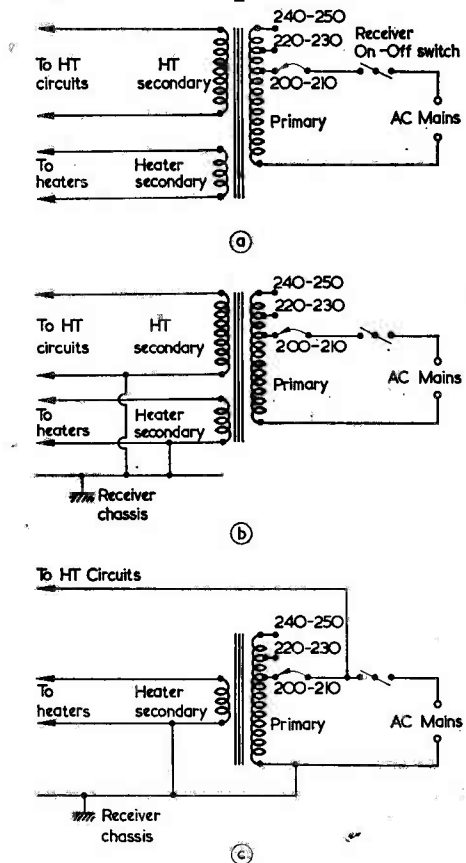


Fig. 144 (a). A typical mains transformer, as employed in a valve radio receiver. The taps in the primary allow for different mains supply voltages  
 (b). In a practical receiver, one side of the h.t. secondary and one side of the heater secondary may be connected to chassis  
 (c). An alternative arrangement consists of dispensing with the h.t. secondary of the transformer and of applying the mains input direct to the h.t. circuits

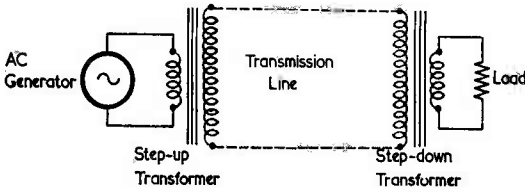


Fig. 145. Illustrating, in simplified form, the operating principle employed for transmitting electrical power over long distances

such a manner that its external field is low, and this may be achieved with a construction of the type illustrated in Fig. 147. Equal sections of the primary and secondary appear in both windings, with the result that each produces an equivalent and opposing field. The two fields tend to cancel each other out, particularly in the plane which passes between the windings at right angles to the laminations. However, transformers of this type are considerably more expensive to manufacture than conventional components and are not generally encountered in normal radio work.

The coupling between two iron-cored components may be reduced by introducing *magnetic shielding* between the two. In Fig. 148 (a) we see that the field from the iron-cored transformer on the left is capable of causing an unwanted coupling with a second iron-cored component on the right. In Fig. 148 (b) a shield made of high permeability material is interposed between the two components. The lines of force which reach the shield now flow through it instead of through the air, which has much lower permeability, and they do not extend beyond the shield. In consequence, the effect of the unwanted coupling is reduced.

In practice, the process of interposing a magnetic shield between two components, as in Fig. 148 (b), does not completely remove the coupling, because the field appears over a much wider area than can be occupied by a flat shield. For greater effectiveness it is desirable to have one of the components completely enclosed inside the shield, as in Fig. 148 (c).

It is more usual to shield the iron-cored component which is affected by the field than the component which generates it. The field about the affected component is bound to be weaker than that around the component which generates it, with the result that a given thickness of shield material has a

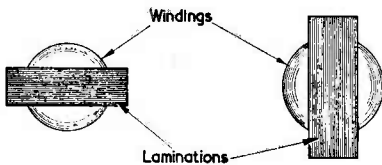


Fig. 146. The magnetic coupling between two iron-cored components may be reduced by mounting them with their axes at right angles, as shown here

greater shielding effect. In addition, it frequently happens that the affected component is smaller than the component which generates the field, a factor which makes it economically preferable to shield the former.

Fairly adequate magnetic shielding may be provided by mild steel sheet, and it is a common practice to house iron-cored components which may be affected by external fields in mild steel containers. Much more effective shielding is provided by the high permeability materials such as Mumetal. Mumetal is very frequently used when highly efficient magnetic shielding is required.

### The Choke

When, before we came to the subject of transformers, we dealt with inductance, we omitted any reference to the *choke*. This omission was intentional, and was due to the fact that chokes cannot be discussed in full without an understanding of iron cores.

A choke is, quite simply, an inductor, and its

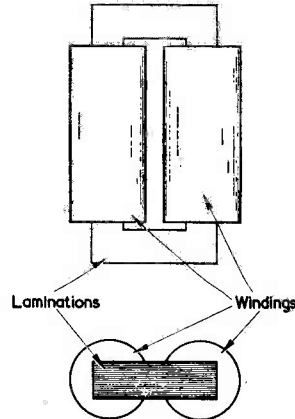


Fig. 147. A method of transformer construction which results in reduced external magnetic field. Equal sections of the primary and secondary appear in both windings

function is to offer an inductive reactance in any circuit in which it is fitted. Normally, a choke allows the passage of direct current, but it offers a relatively high impedance to radio frequencies or to audio frequencies. In some instances a choke is employed to offer a high impedance to radio frequencies and a low impedance to audio frequencies.

In the same manner as transformers, chokes may be either air-cored or iron-cored. Chokes intended for operation at radio frequencies are almost invariably air-cored, and components of this nature are, indeed, normally referred to as *radio frequency chokes*. They are presented on a circuit diagram by the standard symbol for inductance, and are usually identified by the letters "R.F.C." alongside, as in Fig. 149 (a).

Practical radio frequency chokes take up a number of forms, according to their inductance and function, and several typical examples are illustrated in Fig. 150. In Fig. 150 (a) the choke consists of several wave-wound pies connected in series to offer a low self-capacitance. This point is of some importance in radio frequency choke design because a high self-capacitance may offer a low capacitive reactance and thereby partly nullify the effect of the choke's high inductive reactance. The choke of Fig. 150 (b) employs a single wave-wound pie, whilst that of Fig. 150 (c) consists of a single layer of winding wire only. It is fairly usual to wind r.f. chokes on plastic formers in which the lead-out wires are imbedded. Quite frequently, single-pie or single-layer chokes are wound on

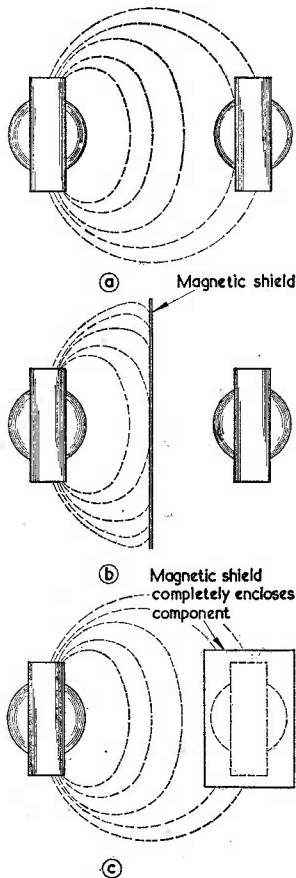


Fig. 148 (a). In this diagram the stray field from the iron-cored component on the left couples with that on the right  
 (b). If a magnetic shield is interposed between the two components, the stray field which approaches the shield flows through it instead of through the lower permeability air  
 (c). For efficient shielding, one of the components has to be completely enclosed by the shield. Small holes are provided in the shield to allow lead-out wires to pass through

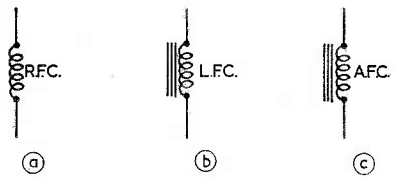


Fig. 149. Circuit symbols for (a) an air-cored r.f. choke, (b) an iron-cored low frequency choke and (c) an iron-cored audio frequency choke

conventional ceramic-coated composition rod resistors. In some cases, these resistors are intended to modify the functioning of the choke by offering resistance in parallel with it but the resistors are more frequently employed merely as convenient and inexpensive formers with lead-out wires. In the latter instance, the resistance value would be of the order of  $1M\Omega$  or more, in order to avoid applying too low a resistance across the inductive reactance of the choke.<sup>2</sup> An alternative technique, with single-layer chokes, consists of employing a rod of iron dust material as the former, the lead-out wires being imbedded directly into the ends of the rod. The iron dust material offers a high resistance between the lead-out wires, and it also enables the required choke inductance to be achieved with fewer turns.

Iron-cored chokes are almost invariably employed at frequencies lower than the radio frequencies, and are frequently referred to as *low frequency chokes* in consequence. They are represented by the standard symbol for iron-cored inductors with,

<sup>2</sup> When resistors are used as formers for r.f. chokes, it is very desirable that low tolerance types (i.e.  $\pm 20\%$ ) be employed. Closer tolerance resistors may have been subjected during manufacture to a "copper spray", which operates as a short-circuited turn inductively coupled to the choke. See "Understanding Radio", Part 4 November 1961 issue.

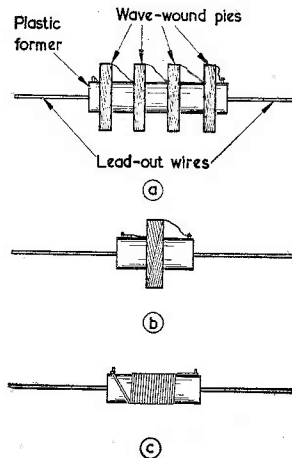


Fig. 150. Representative examples of r.f. chokes. A choke with four wave-wound pies is shown in (a), a single-pie choke in (b) and a single-layer choke in (c).

sometimes, the letters "L.F.C." alongside, as in Fig. 149 (b). Chokes intended to offer a reactance at audio frequencies are normally iron-cored also, although air-cored chokes for this function may quite often be encountered. Such chokes are usually described as *audio frequency chokes*, and the letters "A.F.C." are sometimes printed alongside their circuit symbols. See Fig. 149 (c).

Low frequency chokes, and iron-cored audio frequency chokes, are fitted with laminations in the same manner as an iron-cored transformer, and they have the same general construction. Iron-cored chokes are usually called upon to pass a direct current whilst offering a relatively high inductive reactance to a low frequency alternating current. The presence of the direct current has a considerable effect on the performance of the choke, because it applies a constant magnetising force to the core. If this magnetising force is too great the core may become saturated, and the choke will offer a low inductance. Because of this effect, the laminations in a low frequency choke intended to pass a direct current are always butt-jointed to reduce the flux

density in the core. Despite this precaution, the inductance of a choke may still vary according to the direct current which flows through its winding, and it is usual to specify a low frequency choke in terms of its inductance for a particular direct current.

An interesting variation on low frequency choke design is offered by the *swinging choke*. Some power supply circuits require a choke which needs to have a high minimum inductance for low direct currents and a low minimum inductance for high direct currents. Instead of employing a choke which provides a high inductance at all levels of current, it then becomes more economic to use a swinging choke, which offers the high inductance at the low currents only. The core of the swinging choke tends towards saturation as the direct current which flows through it increases, and the inductance it offers falls in consequence, as is permissible in the application.

#### Next Month

In next month's issue we shall carry on to the subject of air-cored transformers.

AN

# Electric

By K. Barry

# THERMOMETER

**T**HE OBJECT OF THIS DESIGN WAS TO PRODUCE A simple circuit which could be used to measure the cylinder head temperature of an automobile engine. The temperature sensitive element chosen to operate this device was a disc type thermistor specially mounted for surface measurement. This is used in conjunction with a moving coil meter and results in a thermometer with a useful range of 30°-100° C. (86°-212° F.).

#### Circuit Details

The circuit is shown in Fig. 1. A 12 volt supply is used, and this is dropped by  $R_1$  to about 5.7 volts across  $Z_1$ , a zener diode. The diode ensures that a substantially constant voltage is fed to the meter circuit, thus making the meter reading independent of the battery voltage (over the range 10-20 volts). The potential across  $Z_1$  is reduced by means of the potentiometer,  $R_2$ ,  $R_3$ , and the voltage developed across  $R_3$  is applied to the meter via the thermistor.

The resistance of the thermistor falls as its temperature rises, thus allowing a larger current to flow. Whilst the type of thermistor employed may be new to many constructors, they will probably be familiar with the thermistor used for limiting heater current surges in equipments using tubes with series connected heaters.

The meter recommended is a 500 $\mu$ A instrument, but a 0-1mA meter would probably do just as well.

#### Construction and Calibration

In the prototype unit, all the components other than the thermistor were mounted on a piece of synthetic resin bonded paper (commonly known as "Paxolin") and this was secured to the rear of the meter by means of its terminals. The thermistor was bolted to a piece of one sixteenth of an inch thick brass of size 2 $\frac{1}{4}$  x 1 in, and with a three-eighths of an inch diameter hole at one end. This was clamped to the cylinder head by one of the head retaining nuts. (See illustration.) The thermistor unit should be mounted as far away from the fan as possible to prevent its being cooled by the fan blast,

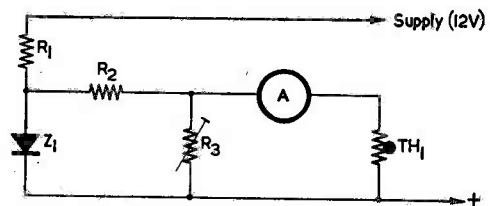


Fig. 1. The basic circuit of the thermometer

and it should be "lagged" (or thermally insulated) by winding several layers of paper around the unit and securing this in position with adhesive tape.

When the components have been wired, it is necessary to calibrate the device. A suitable method of doing this is to fill an aluminium pan with water, then stick the thermistor to the outside of the pan with adhesive tape.

The water should be brought to the boil and allowed to simmer gently for ten minutes. The thermistor should be connected to the rest of the circuit and the supply connected, whereupon it should be possible, by adjusting  $R_3$ , to obtain a full scale reading on the meter. When this has been carried out, a conventional mercury thermometer should be inserted into the water and the pan removed from the heating source. The meter reading should now be noted for given readings of the thermometer as the water slowly cools. The water should be stirred whilst the water is cooling, as water is a poor conductor of heat and considerable variations in temperature in different parts of the pan will otherwise occur.

When taking these readings it will probably be found easier to take measurements at about every  $10^\circ\text{C}$ . (or  $18^\circ\text{F}$ .) and plot a graph from which the precise meter indication for any temperature can be obtained. Having obtained these results the meter may be used as it stands, with a conversion table or curve to enable the exact temperature to be determined. Alternatively, the original calibrations may be removed and a fresh "temperature scale" inscribed in their place.

### Results

The results obtained by the author are given below. A convenient way to use the meter without resorting to re-calibration is to mark a small "band" on the meter scale covering the normal operating temperature of the engine plus or minus  $5^\circ\text{C}$ . (or  $9^\circ\text{F}$ .). This band will show where the pointer should normally lie, and any abnormal tendency may readily be detected.

#### Typical Results


Temperature ( $^\circ\text{C}$ .)	30	40	50	60	70	80	90	100
Meter Reading	21	29	39	51	63	77	89	100*

For the purpose for which this unit was designed, a high degree of accuracy is not really necessary, and examination of these results suggests another simple method of use without resorting to re-calibration of the meter. If  $R_3$  is adjusted so as to increase the meter readings by five, then the following results should be obtained:

Temperature $^\circ\text{C}$	30	40	50	60	70	80	90	100
Meter Reading	26	35	44	56	68	83	94	105
Error $^\circ\text{C}$	-4	-5	-6	-4	-2	+3	+4	+5

The worst error, it will be seen, is  $6^\circ$  at  $50^\circ\text{C}$ ., whilst at  $70^\circ\text{C}$ ., which is a typical cylinder head

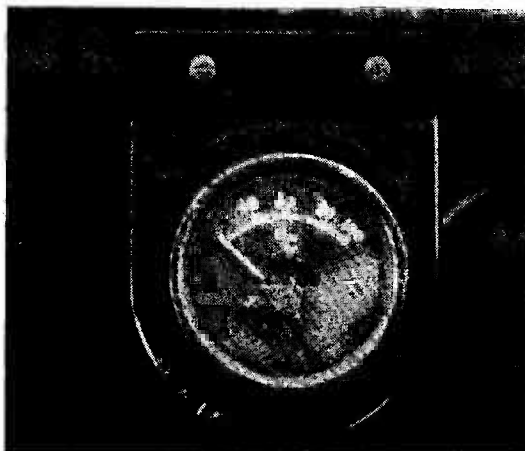\* These figures assume, of course, that a meter reading of 100 corresponds to full scale deflection.—EDITOR.



The meter fitted in a car

temperature, the error is only  $2^\circ\text{C}$ .

The author chose, however, to re-calibrate the meter he used. This was done in the following manner.

Having first obtained a calibration curve, the meter case was removed, and the meter scale painted all over with matt black cellulose. When this was dry, the meter was connected in series with another  $500\mu\text{A}$  meter, a variable resistor, and a dry battery. The current through the meter was adjusted by means of the rheostat, and was set so that the second  $500\mu\text{A}$  meter gave a reading corresponding to that obtained on the original meter during temperature calibration at  $40^\circ\text{C}$ . A small dot was then marked with a soft pencil on the scale of the meter being calibrated. This process was repeated at currents corresponding to 60, 80 and  $100^\circ\text{C}$ . The scale of the meter was then released from the movement, and an arc linking the four pencil dots was drawn in white drawing ink. Short vertical lines were then marked over the pencil dots and the temperature readings marked. (A drawing of the scale is shown in Fig. 2.) When the ink was dry, the scale was replaced and the meter reassembled.

### Installation and Use

The meter may either be mounted on the dash—


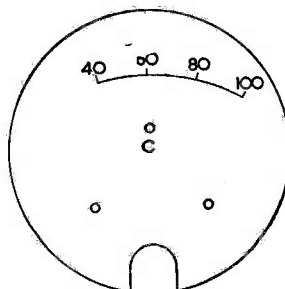


Fig. 2. The appearance of the re-calibrated meter scale

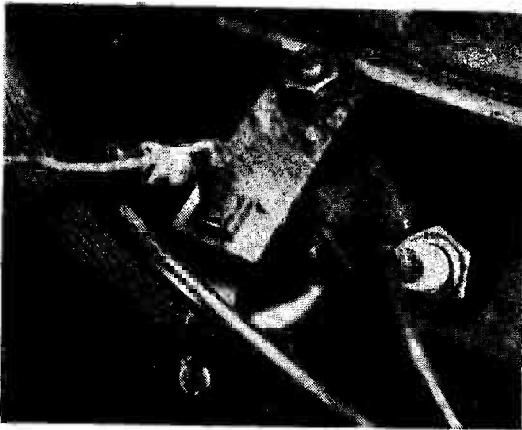

The thermistor mounting bracket secured to the cylinder head

if space permits—or on a small sub-panel which is then itself screwed to the dash (see Fig. 3 and illustration). The latter method is the easier and has the advantage of easy removal if it is desired to transfer the instrument to another vehicle.

When the meter and the thermistor unit have been installed, it only remains to connect them up. If the components other than the thermistor are mounted on the rear of the meter then all that is required is a lead to the “live” side of the battery, and one to a good chassis earth. A third lead to the thermistor unit is required. No earth or return lead from the thermistor is necessary, since one side of the thermistor is electrically connected to the metal mounting plate and the return circuit will be made via the engine.

A further use for this device is that of measuring the temperature of a hot water storage tank and giving a remote indication at some convenient point (e.g. with the meter mounted near the boiler).

#### Battery Polarity

The circuit given in Fig. 1 is only suitable for vehicles in which the positive pole of the battery is connected to chassis. For vehicles in which the

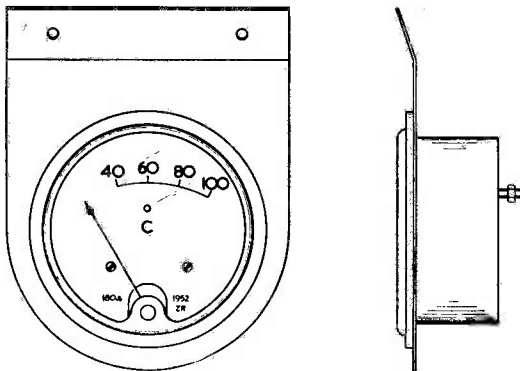


Fig. 3. The meter mounting bracket

negative pole of the battery is earthed  $Z_1$  must be reversed. Also, the lead marked SUPPLY ( $-12V$ ) becomes ( $+12V$ ), whilst the earth line marked + becomes  $-$ . No damage will result through a brief accidental reversal of the supply, though a prolonged reversed connection may damage the zener diode through excessive heating.

#### Adding a Fourth Resistor

Since making the original prototype, the author has constructed a second thermometer. In this case, an attempt was made to obtain a linear scale, since this would make it unnecessary to remove the original meter scale markings. The attempt was partially successful, and results in a linear scale from 40 to 100° C. The meter readings against temperature are given below.

Temperature (° C.)	30	40	60	80	100
Meter Reading	32	39	60.5	81	100
					(=full scale)

For this second thermometer, all that was done was to remove the original numbering (0–500) from the meter scale and insert the numbers 40, 60, 80, and 100 at the points corresponding to 200, 300, 400, and 500 respectively on the old scale. The scale up to the 40° C. mark was left un-numbered. The modification to the circuit necessary to obtain a linear scale simply consists of the addition of a 1.6k $\Omega$  resistor ( $R_4$ ) connected in parallel with the thermistor. Since this value is not available in 10% resistors it may be necessary to use a series or parallel combination, say 1,500 + 100 or 820 + 820. It is possible that the exact value of shunting resistor required will depend on the particular thermistor used, whereupon the use of a 2.5k $\Omega$  rheostat as the shunting resistor may be more convenient. When the correct value for this rheostat and  $R_3$  have been found, there is no reason why they should not be replaced by suitable fixed resistors. (As a matter of interest, in both thermometers made by the author  $R_3$  was finally formed by a 33 $\Omega$  resistor shunted by a 500 $\Omega$  resistor.)

With regard to calibration, when the “linearising” resistor ( $R_4$ ) is connected and set to 1.6k $\Omega$  approximately, a similar procedure to that outlined earlier is used.  $R_3$  is adjusted for full scale at 100° C., whilst the “linearising” resistor,  $R_4$ , is adjusted at 40° C. for a correct meter reading.  $R_3$  should then be re-set if necessary at 100° C. and a further check made at 40° C. to ensure the final correct setting for  $R_4$ .

#### Components List

$R_1$	330 $\Omega$ 10% 1 watt
$R_2$	1.2k $\Omega$ 10% ¼ watt
$R_3$	50 $\Omega$ wirewound potentiometer
$Z_1$	OAZ201 (Mullard)
$TH_1$	KB23 (Standard Telephones and Cables Ltd.)
$M_1$	0–500 $\mu$ A moving coil meter



EDITOR'S NOTES.—We are informed by Standard Telephones and Cables Limited that the KB23 thermistor may be obtained direct from their distributors at the retail price of 34s. 6d. each, inclusive of postage and packing. Distributors suggested are Messrs. Townsend-Coates Limited, 167 London Road, Leicester.

The data on the KB23 quotes a maximum operating temperature of 80° C. Standard Telephones and Cables Limited tell us that the protective resin around the block, which was the reason for this restriction, has now been modified, and that it is possible to use the KB23 thermistor at temperatures up to 120° C.

## trade review . . .

# Sound Effects RECORDS

We have received samples of the new Sound Effects records MFX-1 and MFX-2, these being the first and second respectively in a series of six such recordings to be issued to the general public.

Our well-known contributor F. C. Judd, A.Inst.E., Technical Editor of *Amateur Tape Recording* magazine, is the originator of all the master recordings for the series. We recently met Mr. Judd—quite by accident—at Liverpool Street Station, where he was busily engaged in obtaining a recording of a diesel locomotive commencing a long haul!

We found that the realism obtained on quite an ordinary record player was very impressive and undoubtedly these records will find a ready sale among those requiring to reproduce such effects.

MFX-1 contains 14 effects—Police Car, Police Launch, Lion Roar, Aircraft Landing, Building Falling, Road Drills, Ships Siren, Storm at Sea, Railway Trains (3, various), Car Door and Starter, Central Line Tube Train, and Cell Door.

MFX-2 features the following 12 effects—American Police Car Sirens (5, various), Applause, Car Crash, Glass Breaking, Footsteps (6, various), City-Waterloo Tube Train, Workmen hammering, and Orchestra Tuning-up.

All the sounds contained in these recordings are authentic although, in some instances, the mixing of several sounds has been carried out in order to create a "portrait in sound" such as the car crash on side 1 of MFX-2.

Lifelike reproductions of these effects can be achieved by using high fidelity reproducing equipment, particularly



if the sounds are to be copied on to magnetic recordings or used for stage drama, or cine film sound-tracks, etc.

These two records are on sale through regular dealers at 7s. 6d. each, and the great advantage to amateur recordists, cine film enthusiasts and amateur dramatic societies, etc., is that they may be used, for amateur purposes only, free of copyright. Our illustration above shows part of the record (45 r.p.m.) and the two-colour glossy sleeve.

For readers who are interested, an advertisement for these recordings appears elsewhere in this issue.

## *Improved Silicon Rectifier Ratings*

Westinghouse Brake and Signal Co. Limited have recently increased the current ratings of two high power silicon diodes types SxAN125 and SxBN200.

The SxAN125 range is now rated at 150 amperes in single-phase half-wave circuits, 300 amperes in single-phase bridge circuits and 420 amperes in three-phase circuits, at junction temperatures of 170°C.

Voltage ratings from 100 to 1,200 volts p.i.v. are readily available.

The rating of the SxBN200 range has been increased to 200 amperes in single-phase circuits and will provide 400 amperes and 575 amperes in single-phase bridge and three-phase circuits respectively. The diodes will operate at a continuous junction temperature of 170°C which, coupled with high thermal conductivity between junction and base, permits the use of small heat sinks.

# IN YOUR WORKSHOP



This month, Smithy the Serviceman, accompanied as always by his able assistant Dick, leaves the Workshop to sample the delights of the English countryside in August. However, this does not prevent him from continuing the discussion on intermittent faults which he started last month

**T**HERE'S NOTHING," SHOUTED Smithy above the din of the traffic, "like going out into the country to get some fresh air!"

Dick jumped hastily into the ditch as a ten-ton lorry thundered past. Black diesel exhaust fumes shrouded the pair, rendering speech impossible for several moments. Dick eventually drew in breath to reply, but his words were lost in the sudden roar of a sports car, closely followed by a team of motor-cyclists with both throttles and silencers wide open. There was a short respite, to be violently shattered, as a motor-coach in full song rushed by. Someone in the coach threw an empty ice-cream tub at the Serviceman.

But Smithy was not to be defeated, and he walked defiantly on, followed by an increasingly reluctant Dick. The vehicles continued their plunging journey past the two. Three-wheelers, cars, lorries, articulated vehicles, buses, vans, coaches, motor-cycles, trailers and caravans, they all swept by, leaving Dick and Smithy tramping their solitary way along the isolated and perilous grass verge.

Suddenly, Dick ran along in front of Smithy, narrowly avoiding death in the process as a vast pantechicon swayed crazily by at forty miles an hour. Dick disappeared. The perspiring Serviceman followed quickly, to find that his assistant had discovered a lane leading off the main road, and was already sitting on top of

a gate some distance along it. Smithy followed, and the roar of the headlong traffic eased down to a distant hum.

## Ever-Open Door

"Blimey," said Dick, as Smithy approached him. "I'm glad I've got away from *that* clatter!"

Smithy nodded and leaned against the gate.

"If I'd known," continued Dick bitterly, "that this is what happens when you suggest a quiet summer afternoon walk in the countryside, I'm jolly certain I would never have joined you."

"Nonsense," retorted Smithy. "The trouble with you is that you expect to have it easy all the time."

"There's another thing, too," continued Dick. "I don't like going for a walk with someone who is as exhibitionist as you are!"

"As *what*?"

"As exhibitionist," repeated Dick surveying the deeply affronted Serviceman with a cold and critical eye. "*Everybody* was looking at those awful old khaki shorts of yours!"

"I've never heard such rubbish in all my life," exploded Smithy. "Shorts are the obvious thing to wear when you go for a walk in the country. What is more, my shorts are perfectly respectable."

"I'll say they are," replied Dick. "Seeing that the bottoms are half way between your knees and your ankles."

"I see no reason," said Smithy, with dignity, "why I should discuss

with you what I wear. Anyway, let's wander along this lane a bit."

"O.K." said Dick, "at least there's nobody down here to see us!"

Smithy snorted and purposefully started to walk down the lane. There were trees on either side and, as the pair advanced, they found that these were getting thicker and thicker. Eventually, they were walking through a veritable avenue of trees, the branches of which met over their heads and allowed a more gentle version of the August sunlight to diffuse through. The racket of the main road was now lost and forgotten, and the silence was disturbed only by the rustle of the leaves and the murmur of midges. It was very peaceful.

"We never," remarked Dick suddenly, "finished that discussion."

"I beg your pardon," said Smithy, jerked out of his reverie. "What discussion?"

"The one on intermittent faults, of course," replied Dick. "Don't you remember? We'd just got on to intermittent soldered connections on video chokes, after which you said we'd have a further natter the next time we had a few moments spare."

"Dash it all," grumbled Smithy. "Don't you ever close the hangar down? I've been looking forward to getting out of the Workshop for ages, and what happens? You start talking about work!"

"Well," persisted Dick, "we *do*

have a few moments spare now, don't we?"

"I suppose so," said Smithy resignedly. "And I suppose I won't get any peace until I give you the gen you want. How far had we got to, anyway?"

"We were talking about intermittent connections with wound components," replied Dick. "And you told me to particularly suspect soldered joints where the coil wire insulation is of the solder-through variety. You said that these joints were liable to give rise to intermittents because the wire insulation wasn't always satisfactorily dealt with at the factory."

"Oh yes," said Smithy "I recall it now. I should have added that there's another type of intermittent solder joint you get with wound components also. This is given by the connections you have with coils that are wound in sticks."

"In sticks?"

"That's right. In order to save production time, multi-layer coils, such as are used on l.f. chokes and iron-cored transformers, are normally wound in batches. You start off by putting, on the winding machine mandrel, a single long former which usually consists of specially treated paper material. (Fig. 1 (a)). You then start to wind the coils, of which there may be some four to sixteen or more side by side, according to the type of coil and the winding machine. (Fig. 1 (b)). As soon as one layer of wire has been wound on, the machine automatically inserts a sheet of interleaving paper, this being as wide as the former. When you've finished you have a complete set of coils—which you call a stick of coils—wound on the common former. The next thing to do is to cut these into separate coils; and you do this on the machine, with the aid of pre-positioned knives. (Fig. 1 (c)). The final result is that you have a quantity of identical coils, after a total winding time which is only slightly more than that for one coil only."

Dick frowned.

"Well, that's certainly a money-saving idea," he said. "I'm a bit puzzled, though, as to how you make connections to the start and finish of each winding."

"That," pronounced Smithy, "is what I'm leading up to. One technique consists of simply hooking out the start and end turn of each winding after it has been removed from the winding machine mandrel. A turn or so of the actual winding wire is pulled out, and it provides

its own lead-out wire. The alternative method is to apply a narrow strip of copper foil across the whole stick whilst it's on the winding machine mandrel, and of soldering the coil wire to this. (Fig. 1 (d)) When the stick is wound, the knives cut the strips off flush with the edges of the individual windings, and the lead-out wires are then soldered to the ends of the strips."

"But that means," protested Dick, "that you've got to force your soldering iron bit into the winding itself."

"That's right," agreed Smithy cheerfully. "Still, there's only inter-

leaving paper at the winding edges and it's quite easy to make a quick joint without seriously charring the paper."

"I don't quite get the gist of all this," said Dick. "If you've got an intermittent joint at the point where the lead-out wire is connected to the strip, it should be perfectly easy to detect this *and* to repair it."

"True enough," replied Smithy. "Although you must remember that, by the time the winding reaches the service engineer, it will have been wax or varnish impregnated. And so a new solder joint will not be as easy as all that

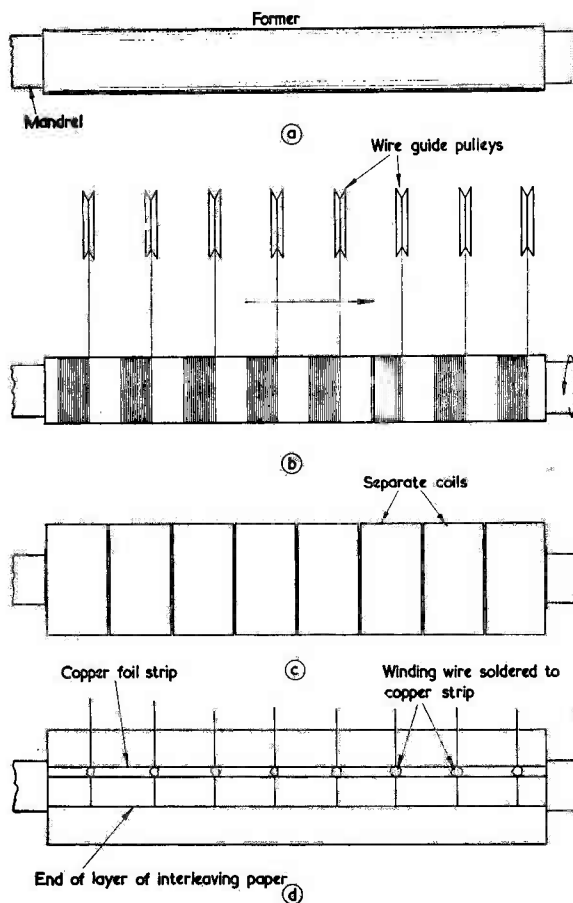


Fig. 1. Showing, in simplified form, how a stick of multi-layer coils is wound. In (a), the former is fitted to the winding machine mandrel. The coil is partly wound in (b), in which diagram the mandrel rotates on its axis whilst the wire guide pulleys move laterally so as to lay the wire evenly. In (c), the completed stick is parted, after being covered with an insulating paper tape, into its separate coils. The process of making connections with copper foil strip is shown in (d). The unwanted projecting wires from the joints are cut away after soldering. In a practical winding procedure, the former, interleaving paper and copper strip would be wider than is required for the coils themselves, the waste material at the ends being cut off after the stick is completed

to carry out. But you've missed my point. I'm not concerned with the joint between the lead-out wire and the copper strip. Instead, I'm concerned with the joint between the copper strip and the *winding wire*. If *this* goes intermittent you've had it. The joint between the winding wire and the strip is internal, and it can only be reached by stripping down the coil. Also, it's a fairly good candidate for the intermittent stakes, because it's one of the few joints which can't be subsequently inspected at the factory."

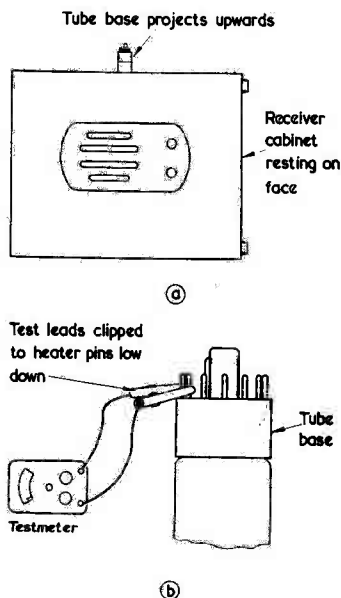


Fig. 2 (a). To make good an intermittent c.r.t. heater pin connection, the receiver is first placed on its face so that the tube base projects upwards (b). Two ohmmeter leads are then clipped to the heater pins low down. A soldering iron, together with a little solder and flux, is then applied to one of the pins, whereupon the ohmmeter will indicate whether the joint has been made good again

"Well, I'm blown," said Dick. "I hadn't quite looked at it in that light. What sort of coils are manufactured with this copper strip idea?"

"As I said just now," remarked Smithy, "copper strip connections are common with I.F. chokes and iron-cored transformers. In the latter category you'll find such things as small mains transformers, speaker transformers and vertical output transformers. The technique is

even employed for line output transformers, but you will very rarely find it giving you intermittents with those components."

"Why's that?"

"Because line output transformers handle high voltages. You may remember I referred to wetting voltages the last time we discussed this subject. If you have a poor connection inside a line output transformer you've got a really jumbo-sized wetting voltage to bridge the gap. When there's an actual break, this voltage will cause a spark to appear which will soon burn the conductors away. In other words, it is very rarely that line output transformers go intermittent due to poor connections. If a poor connection appears, the voltages in the transformer are such that it burns out completely, and you've got a component which is permanently u/s."

#### Other Intermittent Connections

"That's true enough," remarked Dick thoughtfully. "I don't think I can even recall an intermittent which has been caused by a line output transformer. Are there any other intermittents which may be given by poor solder connections?"

"Quite a few," replied Smithy. "One you bump into occasionally occurs at the bases of cathode ray tubes. If the tube has a Bakelite duodecal base you occasionally find that one of the heater lead-out wires from the glass has an intermittent solder connection inside its pin. There is, in fact, rather an interesting point here. From my own experience, I've found that this particular snag seems to occur far more frequently with receivers in which the c.r.t. heater is run from a mains transformer than in receivers where it is connected in a series heater string. I would guess that this phenomenon is due, once more, to wetting voltages."

"You don't," objected Dick, "have television sets with mains transformers these days."

"Yes you do," contradicted Smithy. "Although I will admit that they're very few and far between. Nevertheless, I can think of one recent model, at least, which employs such a transformer. And this brings me to a second interesting point. Which is that, when the c.r.t. screen goes blank because of the open circuit tube heater connection, there is a tendency to look inside the cabinet, see all the valves glowing away merrily, and assume that the tube heater is glowing as well. As, of course, it would be in a normal series-string

set. You will even get a correct voltage reading across the heater tags on the tube base socket, but you can waste a lot of time looking for snags elsewhere if you don't also check visually that the heater is actually operating."

"That's something to remember," commented Dick. "How do you clear the snag?"

"It's usually simple enough," replied Smithy. "The first thing to do is to ensure that the Bakelite base is well and truly secured to the glass of the tube. These bases frequently work loose, and it's probably their subsequent movement relative to the glass which causes the trouble in the first place. If the base isn't secure, you should stick it down firmly with a good adhesive. When this has set, you then attempt to repair the open-circuit joint from outside. There's no need to remove the tube from the set to do this; all you have to do is put the cabinet on its face so that the tube base sticks upwards. (Fig. 2 (a)). The tube socket has to be removed from the base for the repair operation. You first of all fit two ohmmeter clips to the pins (Fig. 2 (b)) and then apply a little paste flux of the type which is suitable for electrical joints, such as Fluxite, to the end of one pin. You next apply the iron and a little solder to the tip of the pin. The solder and flux will run down the inside of the pin and, if you're lucky, the ohmmeter will indicate low resistance if they cause the previously bad joint to become good. At which point you remove the soldering iron, and all is well. If you're unlucky, the ohmmeter will still indicate an open-circuit, and this means that you've started operations on the wrong pin. So you repeat the process with the other pin."

"That's quite a business," said Dick, impressed. "Does it always work?"

"It has done with me," replied Smithy, "but I certainly wouldn't guarantee it as being 100% predictable. It's one of those jobs which should only be tackled by those who feel confident of doing it properly. The important thing to remember is that you only need a little additional solder, and that the iron should only be applied for a short time. It doesn't matter if you apply excess flux because, if this is of a reliable quality, it will remain inert after the job is completed. You must realise that the joint you've re-made will still be in the dicey category and that you want to avoid any possible

mechanical movement or shock to the base or pin afterwards. You don't, for instance, want to leave a blob of solder at the tip of the pin after you remove the iron, because this will have to be cleaned off before you can get the tube socket back on again. A process which may well cause your repaired joint inside the pin to go open-circuit again."

"It doesn't sound a very reliable repair," commented Dick.

"It isn't," agreed Smithy, "but it's better than ditching the tube for an o/c heater!"

"Do you get any intermittent connections to the other pins?"

"Not so often," commented Smithy. "The heater pin connections seem to be the favourite. The current passed by the connections in the other pins is, of course, very small, and you could have quite a high resistance before you get into trouble."

#### Ceramic Capacitors

By now, the pair had left the tree-lined section of the lane, and were walking between low hedge-rows. Idly, Dick pulled a stick from one of the hedges and slashed at the grass bank with it.

Rounding a corner, they were suddenly confronted by a cow.

"Now this is a bit of the countryside," said Dick enthusiastically. "It must be about ten years since I last saw a cow as close as this."

"I don't know about that," said Smithy, watching the animal somewhat fearfully. "Cows are meant to be in fields, you know, not walking about in the middle of lanes without proper supervision."

The cow lumbered up and examined Smithy with great interest. Her soft brown eyes gradually lowered until they came to rest on his shorts, whereupon her gaze became transfixed. With an air of complete fascination, she pushed her head forward and sniffed noisily. Smithy jumped back.

"Dash it all," he said nervously. "That brute's positively dangerous."

"It's those shorts of yours," replied Dick cheerfully. "She's never seen anything like them before!"

"Well, let's get on past her," said Smithy testily. "I came out for a walk, not to be messed about by hulking great animals like this."

They walked past the cow, Smithy taking great care to ensure that Dick was interposed between the beast and himself. As they wandered on, the cow turned her head round and gazed with utter absorption at Smithy's rear.

"Do you know," remarked Dick, "you've absolutely made that cow's day for her! She'll really have something to tell the other cows now when she gets back to them."

"Don't be silly," replied Smithy, his confidence returning as they moved further away. "Anyway, let's get back to those intermittent faults we've been talking about."

"Righty-ho," said Dick, equably. "Are there any other soldered connections inside components which may cause trouble?"

"I think I've covered most of the more usual ones," said Smithy. "Apart, that is, from disc ceramic capacitors. Although, to be truthful, the occasional troubles you get with these components has more to do with the silvering on the ceramic than with the actual soldering itself."

"Fair enough," said Dick. "Fire away!"

"As you know," said Smithy, "a disc ceramic capacitor consists basically of a round slab of ceramic with silvering on either side. The lead-out wires are then soldered to that silvering. (Fig. 3 (a)). The bond between the silvering and the ceramic is usually quite strong, and should be capable of withstanding a reasonable amount of pulling on the lead-out wires. Also, the capacitor is given an outside coat of hard insulating material which helps to increase its strength so far as tension on the wires is concerned."

"I'm with you," remarked Dick, "all the way."

"Right," said Smithy. "Now, these capacitors will normally give you excellent service, but you may occasionally find one which has been badly manhandled either in the receiver factory or during subsequent servicing. What happens then is that the silvering about the solder joint gets very slightly pulled away from the ceramic. (Fig. 3 (b)). Usually, the result is an obviously faulty capacitor but, if the silvering stays very close to the ceramic, you may still get sufficient capacitance for some circuit functions. Such as, for instance, decoupling applications where the circuit does not really require by any means as much capacitance as the capacitor normally offers. In these cases, the slightest mechanical shock can cause the capacitor to change from a good to a no-good condition, or vice versa."

"Wouldn't the fault be obvious?" queried Dick. "I mean, wouldn't you see an obvious break in the outside insulated covering?"

"Not always," said Smithy. "There might be just a faint crack around

the area where the silvering has pulled away. Also, this could be covered by dirt and grime, or the capacitor could be tucked away in a corner where it's difficult to see. At all events, faulty ceramic capacitors of this nature can sometimes give you the dickens of a lot of trouble. The only good thing about them is that the fault normally becomes permanent if you bend the capacitor about a bit, or if you tap it."

"Are there any other snags with disc ceramics?"

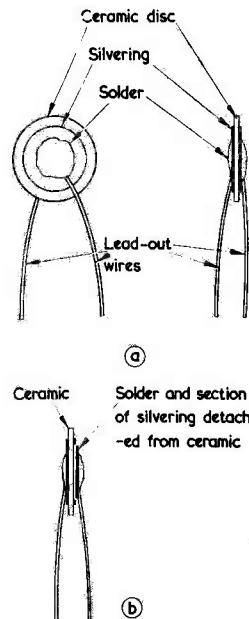


Fig. 3 (a). A typical disc ceramic capacitor without its final insulated covering  
(b). Due to excessive tension on the lead-out wires, the solder joint and part of the silvering may become detached from one surface of the ceramic. Again, the final insulated covering is not shown

"There's an occasional one," said Smithy, "which you might encounter if you're unlucky enough. If the silvering process isn't carried out properly at the capacitor factory you may get "islands" of silvering on one or other of the ceramic surfaces. (Fig. 4 (a)). Such islands may be joined to the main body by a very narrow band of silvering (Fig. 4 (b)) and, if this connection becomes unreliable, you have a case of varying capacitance. This is a rare fault, admittedly, but it's one of the things that can happen." "How do you locate it?"

"If," replied Smithy, "the nature of your intermittent fault is such that you suspect varying capacitance in the ceramic you would, in the normal course of events, swap it anyway. The fact that the intermittent clears with the new component then confirms that the previous one was faulty. Alternatively, you might be able to bring the faulty condition on by tapping the capacitor, or by warming it up slightly by holding a miniature soldering iron near it."

"That's not very conclusive, is it?" commented Dick.

"It isn't," agreed Smithy. "But then, the nature of intermittent faults is such that their repair is hardly every conclusive."

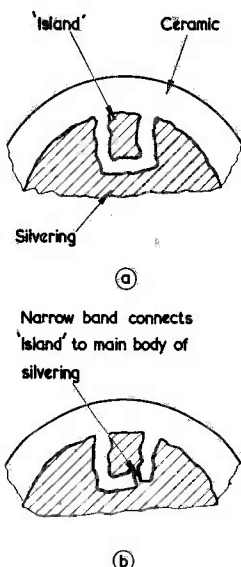


Fig. 4 (a). Detail showing how "islands" of silvering may appear on the surface of a ceramic capacitor

(b). A possible source of intermittent variations in capacitance is given when an "island" is connected to the main body of silvering by a very narrow band, as shown here

#### Intermittent Oscillator

There was silence for a moment, as they traversed another corner.

"Blast," said Smithy, "more cows!"

They were confronted, this time, by a veritable army of cows. Dick noticed a closed gate alongside them.

"I suggest we sit on this until they go by," he suggested hastily. "We'll never get through that lot."

Gratefully, Smithy clambered on the gate and the pair perched in silence, watching the cows as they ambled along in slow procession. There was, once again, evidence of a speculative interest in Smithy.

"Why do they keep looking at me like that?" said Smithy, irritably. "I find it quite unnerving!"

"If," chuckled Dick, "you were an old cow lying about in a field all day, you'd look around at anything new, if only to break the monotony!"

The cows continued on their course. There appeared to be an inexhaustible supply of them.

"What I can't understand," complained Smithy, "is how so many animals can be let loose like this. Surely, someone must have the responsibility for them. They must, after all, represent a fantastically high capital expenditure."

At long last, the end of the bovine cavalcade came into view. As the lost animal passed him Smithy was amazed to see that they were under the control of a diminutive youth about twelve years old.

"Hey, sonny-boy," called out Smithy, assuming the sugary accents of a fond uncle, "are you really looking after all those cows on your own?"

The boy, obviously annoyed at Smithy's patronising tones, looked at him in disgust. His eyes noticeably widened as he took in the full details of the Serviceman's nether attire.

"Cor," he remarked derisively, "if it ain't old Knickerbocker Glory his-self!"

Stung to the quick, Smithy lapsed into red-faced silence, a condition which he maintained for the next few minutes whilst the gate shook wildly to the suppressed chuckles of his assistant. The boy walked out of sight.

"You asked for that one," laughed Dick. "I've been telling you about them all day long, but you wouldn't listen to me. Fancy going out in a pair of gash old surplus shorts like that!"

"Gash old surplus?" said Smithy, outraged. "Let me tell you that I was issued with these!"

"Issued with them?" gasped Dick. "When?"

"During the war, of course," snapped Smithy. "Don't forget that, during the years when you were throwing your rattle out of your pram, I was defending my country!"

"Come off it, Smithy," said Dick scornfully. "Don't tell me that the Pioneer Corps were ever issued with khaki drill!"

"I am not going to discuss the matter further," said Smithy with dignity. "So far as I'm concerned, shorts for walking are *de rigueur*."

"So far as those shorts are concerned," commented Dick, "I'd say they were *de rigueur mortis*."

Smithy refused to answer, and he eased himself gently off the gate. He resumed his progress along the lane, with Dick walking by his side. Dick decided to return to the previous topic.

"I've got an intermittent fault on the bench right now," he remarked chattily. "I was going to ask you about it when we start work again."

"What are the symptoms?" asked Smithy, manifestly relieved at the change of conversation.

"Well," said Dick, "so far as I can see, there's something queer with the tuning capacitor. It's a Medium and Long wave valve set, and sometimes it works like a bomb and sometimes it's as dead as a doornail. It all seems to depend upon where the tuning capacitor is set."

"Tell me more."

"If," said Dick, "I switch it on and try and tune in a station at the low frequency end of the Medium wave band, there's not a sausage. If I then tune up to the high frequency end its works O.K. The funny thing is that, after I've tuned in a station at the high frequency end, it's all right at the low frequency end as well!"

"Is it the same on long waves?"

"I don't know," confessed Dick. "I've only had time to try it out on Medium waves up to now."

"It sounds to me like a worn-out oscillator valve," remarked Smithy. "If the oscillator valve is on the verge of packing in, it may still summon up enough strength to commence oscillating when you're at the high frequency end of the band, because this corresponds to a high L C ratio in the oscillator tuned circuit. Once the valve has started to oscillate it will continue to do so, even if you return to the more inefficient tuned circuit conditions at the low frequency end of the band. It's operating in the same way as a reaction circuit with bad backlash. Once you go into oscillation with such a circuit you have to reduce feedback quite a lot before you can come out of oscillation again."

"So the cure," remarked Dick, "is to fit a new oscillator valve?"

"That's right," said Smithy. "If that doesn't work the oracle, check

the grid capacitor and the anode feedback capacitor if there is one. These may have gone low in value and caused a reduction in feedback. There are other obvious faults which could cause the trouble, too, such as shorted turns in the feedback winding, a high value anode resistor, and so on. But the valve itself is by far the most likely customer." "I'll try that," said Dick, "as soon as we start work again."

#### Break For Tea

"Hallo," said Smithy, "it looks

as though we're approaching a village."

A cluster of cottages came into sight, to be succeeded by a typical village street. An occasional lorry or car passed by but there was, otherwise, an air of complete serenity.

"There's a sign down there," remarked Dick, "which says 'Farmhouse Teas'."

"So there is," agreed Smithy. "Let's investigate."

And this they did. If we were to return to Dick and the amply

attired Smithy some twenty minutes later, we would find them sitting out in a rose-bedecked garden whilst a middle-aged and motherly countrywoman set out in front of them two heaped plates of ham and eggs, to be attacked by the pair with much gusto and great helpings of H.P. Sauce. Which only goes to show that it is still possible to stumble on parts of rural England by the simple process of walking down a country lane.

Provided, of course, you choose the right lane.

---

## book review . . .

**TRANSISTOR TELEVISION RECEIVERS: A Survey of World Circuitry, British, American, German, Russian, Japanese.** By T. D. Towers, M.B.E., M.A., B.Sc., A.M.I.E.E., Grad. Brit. I.R.E. Published 11th July, 1963, by Iliffe Books Ltd. 194 pages including 188 diagrams. Size 10in by 7½in. Price 55s. net (by post 56s. 6d.).

The change from valve to transistor television receivers has been slower than that in other electronic devices, but in many countries, such as America, Japan, Switzerland and France, it is rapidly gaining momentum and Great Britain is bound to follow the lead. The slow development was due to the high cost of transistors, now falling rapidly in price, and to the difficulty in transistorising certain sections of the circuitry now overcome with the development of more effective transistors, though extreme difficulty is still being experienced in obtaining enough power to drive the larger television tubes. The tendency has therefore been to concentrate on small and medium sized sets. Japan has specialised in the development of very small sets (5-6in screens) using microminiaturisation techniques, and now produces these on a commercial scale for domestic, industrial and executive use.

The author has combed the world to obtain circuits from every country working on transistor receivers, and so has at his fingertips a unique store of information. In this book he has taken from the various countries the designs of each section of the receiver and has critically compared and contrasted them. A most valuable feature of his survey is the fact that all the circuits have been redrawn in a similar style, making for ease of comparison. In all there are nearly 190 circuit diagrams, for which the present large format has been chosen to show them to the best advantage.

T. D. Towers, the Chief Applications Engineer of Newmarket Transistors Ltd., first gives the reader a clear perspective of the subject. He then devotes a chapter to each of the following, tuners; vision i.f. amplifiers; video; amplifiers; audio i.f. amplifiers; synchronising circuits; field deflection circuits; line deflection circuits; picture tubes and associated circuits; power supplies. A further chapter discusses the transistor as an electronic device, how it operates and how it should be handled and tested. Finally, there is a useful chapter on the servicing of transistor television receivers.

This book—the first in its field, with its survey of designs from the United Kingdom, U.S.A., France, Germany, Russia and Japan—will be invaluable to all designers who wish to keep abreast of current developments and be prepared for the future.

**CONTENTS:** Preface—Acknowledgements—The Transistor in the Television Receiver—Transistor Tuners—Transistor Vision I.F. Amplifier—Video Amplifier—Sound Sections of Transistor Television Receivers—Sync Separator Circuits—Field Time Base Circuits—Line Time Bases—The Picture Tube and Associated Circuits—Power Supplies in Transistor Television Receivers—Transistors for Television Receivers—Servicing Transistor Television Receivers—Index.

---

## Catalogue Received . . .

Home Radio Ltd., 187 London Road, Mitcham, Surrey.

We have just received our copy of the latest catalogue (4th Edition, June 1963) and this 194-page publication, 7½ x 9½in, is available direct from them at 2s. 6d. per copy.

This lavishly illustrated component catalogue is, without a doubt, one of the finest radio retail shopping guides available in this country. The Index is comprehensive and any required item, no matter how small, is quickly traced—the type number, manufacturer and price all being listed.

The present edition has not only been enlarged but has also been subjected to some rearrangement, this achieving a better layout and an attractive presentation of the many hundreds of items listed and illustrated.

This latest catalogue should find a place on every constructor's bookshelf where it will serve both as an easy shopping guide and as a veritable mine of component information.

**Cover Feature**



# High Quality Modulator Design

By D. NOBLE - G3MAW  
and D. M. PRATT - G3KEP

HAVING COMPLETED THE EXPERIMENTAL TRANSMITTER for the 4 metre band described in the June 1963 issue<sup>1</sup>, a suitable modulator was required in order to operate on telephony. It was decided that, as far as possible, the finished appearance of the modulator should match that of the transmitter. In order to achieve this, the modulator is built into a cabinet of similar dimensions to those of the transmitter, and both cabinets are similarly painted.

With a good crystal microphone the quality produced is of a high standard, comparing favourably with other amateur signals.

The output stage is capable of providing sufficient output to fully modulate any transmitter running up to 20 watts input.

The unit has a built-in power supply providing 250 volts at 60mA for h.t. and the usual 6.3 volts for the heaters. However, it may be desired to use the unit while operating portable or mobile and, for this reason, provision is made for feeding in external h.t. and l.t. supplies.

## Circuit

The first stage is an EF86 operating in a high gain amplifier circuit. This valve is a low noise pentode particularly suitable for the early stages of high gain audio equipment. It is designed to have extremely low hum and microphony characteristics.

Between the input socket and the valve an RC network is provided. This behaves as an r.f. filter, thus avoiding feedback caused by r.f. pick-up on the microphone cable being detected by the valve.

The output of V<sub>1</sub> is fed via the gain control to the

<sup>1</sup> David Noble and David Pratt, "Transmitter Design for 4 Metres", *The Radio Constructor*, June 1963.

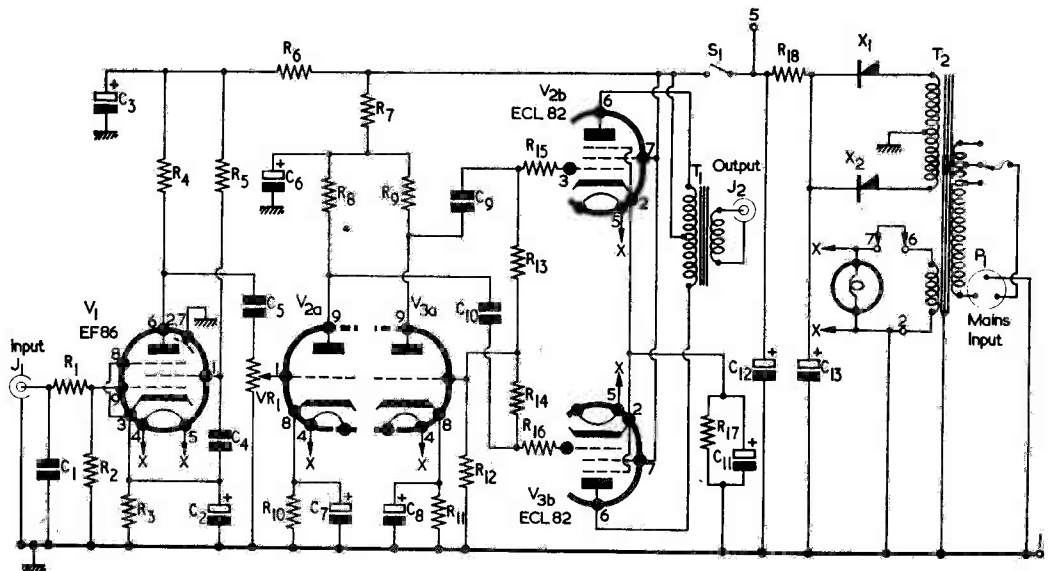


Fig. 1. The circuit of the modulator. The circuit points designated 1, 2, 5, 6 and 7 correspond to the appropriate pins of the octal valveholder mounted at the rear of the chassis. It will be noted that there is no switch in the mains input circuit




paraphase phase-splitter utilising the triode sections of two ECL82 valves. In order to obtain a balanced output from this stage it is important that several of the components be accurately matched. These are the two anode load resistors  $R_8, R_9$ ; the two coupling capacitors  $C_9, C_{10}$ ; and the two grid resistors  $R_{13}, R_{14}$ . Although the actual values themselves are not very critical, the pairs of components should be matched to within 2%. Of the matched pair  $R_{13}$  and  $R_{14}$  should, preferably, have the higher value.
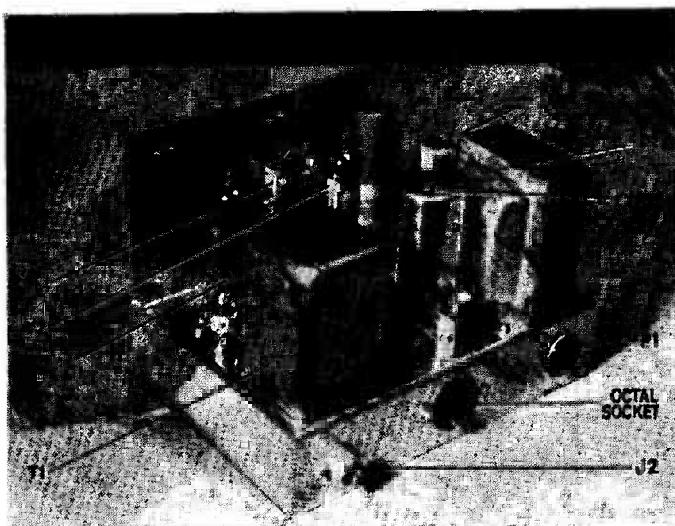
### Output Stage

The output stage consists of the pentode sections of the ECL82 valves operating in Class  $AB_1$ . Common cathode bias components ( $C_{11}, R_{17}$ ) are used for the two valves. The resistor should be of the wirewound type rated to dissipate 2 watts. The screen grids of the valves are connected directly to the h.t. line.

The anode-to-anode load impedance of the output valves employed in this modulator is  $10k\Omega$ . The modulation transformer used is taken from the SCR522 transmitter, and this is obtainable from time to time on the surplus market. The SCR522



Three-quarter rear view of the modulator

transformer has a turns ratio of 2:1, and it conveniently matches the anodes of the ECL82 pentodes to  $2.5k\Omega$  load such as that presented by an r.f. power amplifier stage operating at 250 volts and 100mA. The SCR522 modulation transformer satisfactorily matches the modulator to the 4 metre

### Components List

Resistors (All fixed resistors  $\frac{1}{2}W$  10% unless otherwise stated)

$R_1$	100k $\Omega$
$R_2$	2.2M $\Omega$
$R_3$	2.2k $\Omega$
$R_4$	220k $\Omega$ , high stability
$R_5$	1M $\Omega$ , high stability
$R_6$	33k $\Omega$
$R_7$	22k $\Omega$
$R_{8, 9}$	100k $\Omega$ , matched (see text)
$R_{10, 11}$	1.2k $\Omega$
$R_{12}$	1M $\Omega$
$R_{13, 14}$	1M $\Omega$ , matched (see text)
$R_{15, 16}$	10k $\Omega$
$R_{17, 18}$	390 $\Omega$ , 2W, wirewound
$VR_1$	500k $\Omega$ pot, log track

#### Capacitors

$C_1$	39pF, tubular ceramic
$C_2$	50 $\mu$ F, 12V wkg., electrolytic
$C_3$	16 $\mu$ F, 350V wkg., electrolytic
$C_4$	0.47 $\mu$ F, 400V wkg., polyester
$C_5$	0.1 $\mu$ F, 350V wkg., polystyrene
$C_6$	8 $\mu$ F, 350V wkg., electrolytic
$C_{7, 8}$	50 $\mu$ F, 12V wkg., electrolytic
$C_{9, 10}$	0.1 $\mu$ F, 350V wkg., polystyrene, matched (see text)
$C_{11}$	50 $\mu$ F, 50V wkg., electrolytic
$C_{12, 13}$	50 + 50 $\mu$ F, 350V wkg., electrolytic

#### Valves

$V_1$	EF86
$V_{2, 3}$	ECL82

#### Rectifiers

$X_{1, 2}$	BY100
------------	-------

#### Transformers

$T_1$	SCR522 Modulation Transformer (see text)
$T_2$	Mains transformer. Secondaries: 250-0-250V 60mA, 6.3V 2A, R.S.C. (M/C) Ltd., 5 County Arcade, Leeds 1. (see text)

#### Switch

$S_1$	s.p.s.t. toggle switch. Bulgin type S600/PD
-------	---

#### Plugs and Sockets

$J_1$	Coaxial socket. Belling-Lee type L604/S
$J_2$	Insulated coaxial socket. Belling-Lee type L603/B
$P_1$	Mains input plug. Bulgin type P429. (Matching socket is Bulgin type P430)

3	B9A valveholders
1	Octal valveholder
1	Pilot lamp fitting. Bulgin type D180

#### Miscellaneous

1	Pilot lamp, m.e.s. 6.3V 0.15A
1	Knob
1	5-way tagboard (i.e. 5 tag pairs). Bulgin type C120
2	15-way tagstrips
1	Chassis (as Figs. 2 and 3). This fits into Cabinet type W, available from H. L. Smith & Co.

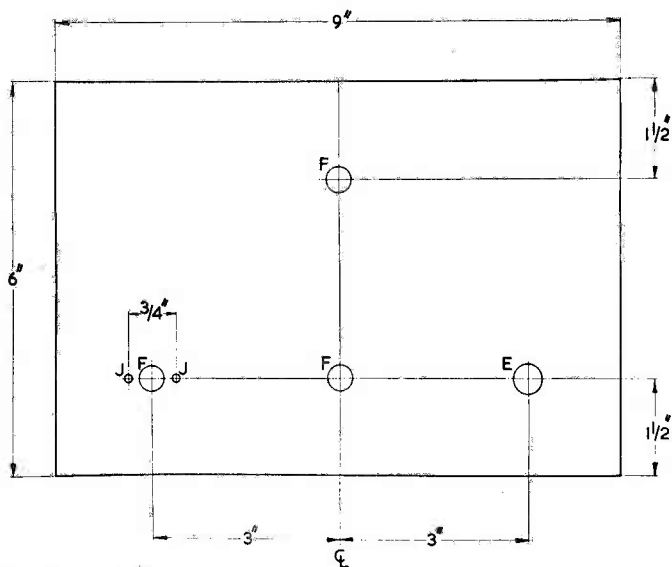


**TABLE**  
**Holes on Chassis and Panel Drawings**

Hole	Dimension
A	1 1/2" dia.
B	1 1/4" dia.
C	1 1/8" dia.
D	3/4" dia.
E	1 5/8" dia.
F	3/8" dia.
G	5/16" dia.
H	3/32" dia.
J	1/8" dia.

listed in the Table. A Bulgin 5-way tagboard type C120 is used for the components associated with V<sub>1</sub>, while for V<sub>2</sub> and V<sub>3</sub> two 15-way tagstrips are used.


An octal socket is provided at the rear of the chassis to enable the h.t. and l.t. voltages to be measured. It is recommended that the pin connections indicated on the circuit diagram be used. If desired, the socket is suitable for feeding ancillary equipment, e.g. an audio oscillator. An external power supply may also be fed into this socket while working portable or mobile. So that this can be achieved, it is necessary to disconnect the heater winding of the internal mains transformer, and this



Material: 16 swg Aluminium

Fig. 3. The front panel

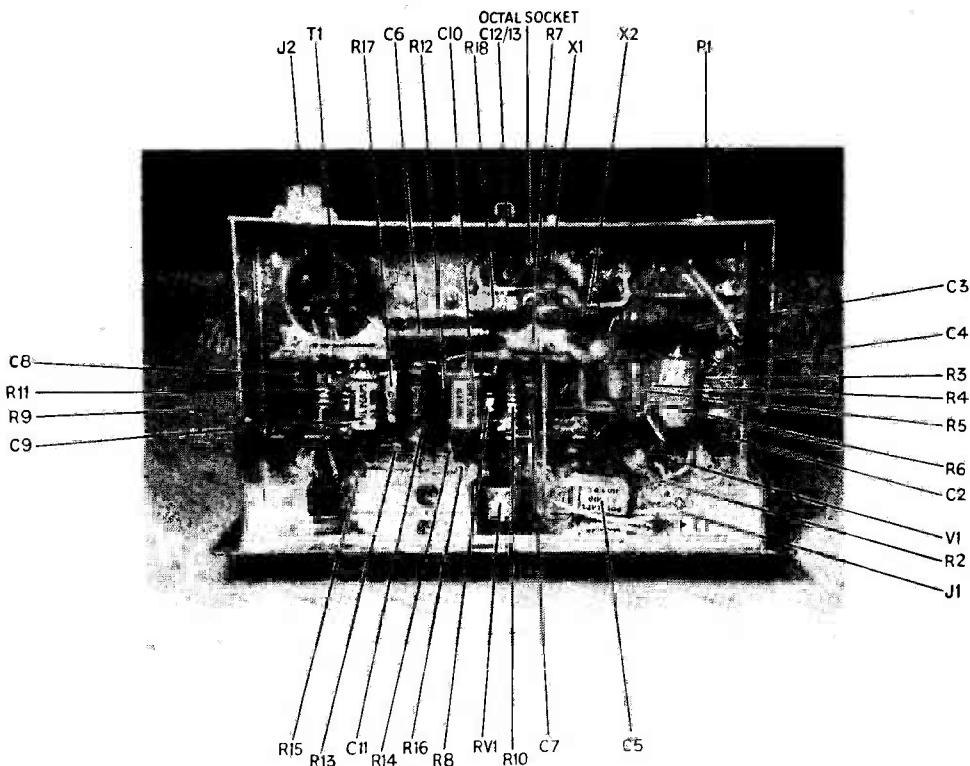is done by using a jumper lead between pins 6 and 7 of the octal socket. On removal of this jumper the heater winding is disconnected. Thus, except while



Underside view of the modulator showing the positions of the various components

using the modulator from an external supply, pins 6 and 7 of the socket should be connected together. The rear of the chassis also carries the Bulgin three-pin mains connector, and a Belling-Lee insulated coaxial socket for the audio output.

No difficulty should be experienced in assembling the unit, particularly if the recommended components are used. The photographs show the positions of the major components.

#### Testing

After completing the modulator, a 2.5kΩ load should be connected across the secondary of the modulation transformer. This may consist of a

2.4kΩ and a 100Ω wirewound resistor connected in series. If an oscilloscope is available this may be connected across the 100Ω resistor, and the distortion of the amplifier measured with a sinusoidal input.

If no test gear is available, a pair of high impedance headphones may be used as a load, but care must be exercised in advancing the gain control in order not to damage the phones or eardrums!

#### Conclusion

This little modulator should provide a reliable audio source for any low power transmitter. It will be of particular interest to the newcomer to Amateur Radio who is contemplating building equipment to form the basis of his station.

## An introduction to . . .

# COLOUR TELEVISION

By J. R. DAVIES

PART 3

**I**N THE SECOND ARTICLE IN THIS SERIES WE SAW how, in the transmitted colour television signal, the chrominance subcarrier and its sidebands can be interleaved between the sidebands of the luminance signal, thereby enabling the chrominance information to be transmitted within the same bandwidth as is occupied by the luminance signal. We learned also that, when the transmitting camera scans a white scene,

$$Y = 0.59G + 0.30R + 0.11B$$

where Y represents the voltage amplitude of the luminance signal, G the voltage amplitude of the "green" tube signal, R the voltage amplitude of the "red" tube signal, and B the voltage amplitude of the "blue" tube signal. It is possible to transmit chrominance information by means of the R-Y and B-Y colour difference signals, the R, B and G signals being reclaimed at the receiver by combining these with the Y luminance signal. It was further noted that, when the transmitting camera scans a monochrome scene (i.e. black, greys and white) the colour difference signals drop to zero.

#### The N.T.S.C. Primary Colours

Fig. 6 shows the C.I.E. Chromaticity Diagram, this being marked up with the three primary colours employed in the N.T.S.C. colour system. It will be noted that these primary colours do not correspond *exactly* with the spectrum colours which appear on the outside curved line of the Diagram. For instance, the N.T.S.C. primary green does not correspond to

the fully saturated spectrum green, although it is very close to this colour. The N.T.S.C. primary blue is similarly desaturated, and it is slightly removed in hue from the spectrum blue also. There is, again, a slight difference in hue between the N.T.S.C. primary red and the spectrum red, although it can be seen that the N.T.S.C. primary red is a fully saturated colour. These small discrepancies do not detract from the performance of the colour system to any very great extent, and the primary colours chosen for the N.T.S.C. system are such that they may be readily reproduced by practical cathode ray tube phosphors.

The colours given by additive mixing of the N.T.S.C. primary blue and the N.T.S.C. primary green lie along a straight line drawn, on the Diagram, between these two points. The same applies to the colours which may be produced by additive mixing of the N.T.S.C. primary green and the N.T.S.C. primary red, and by additive mixing of the N.T.S.C. primary red and the N.T.S.C. primary blue. The three lines joining the N.T.S.C. primary colours form a triangle, as illustrated in Fig. 6. If the *three* N.T.S.C. primary colours are mixed additively, it then becomes possible to reproduce any of the colours which are contained within this triangle.

Whilst the N.T.S.C. primary colours can provide reproduction of any of the colours inside the triangle of Fig. 6, they are incapable of reproducing colours which fall outside. They can allow the *hue* of colours outside the triangle to be reproduced,

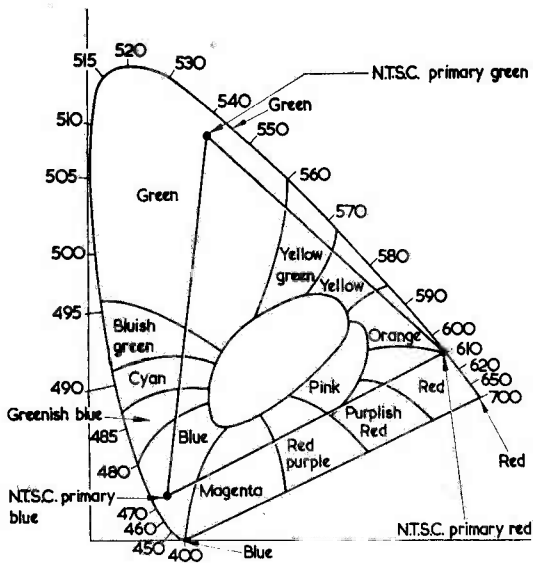


Fig. 6. The positions which the N.T.S.C. primary colours take up on the C.I.E. Chromaticity Diagram. By means of additive mixing, it is possible to reproduce any of the colours which lie within the triangle

but at reduced saturation only. This state of affairs is not as serious a disadvantage as it may at first sight appear, because the deeply saturated colours around the edge of the Chromaticity Diagram are, in any case, seldom encountered in natural life. In practice, the range of colours enclosed by the triangle joining the N.T.S.C. primary colours is significantly greater than that which can be given by colour reproductions employing established printing techniques. The latter are, as we know, quite capable of offering adequate reproductions.

### The I and Q Signals

We have seen that it is possible to transmit colour information in the N.T.S.C. system by way of the Y, the R-Y, and the B-Y signals. At the same time, we have noted that colour information is carried by the chrominance subcarrier, this being amplitude modulated in quadrature (i.e. at 90° phase difference) by the I signal and the Q signal. We shall now examine the form which the I and Q signals take up in relation to the R-Y and the B-Y signals, dealing also with the modulation of the chrominance subcarrier.

It is most convenient to start with the R-Y and B-Y signals, introducing the I and Q signals later. It is helpful, further, to make the temporary assumption that it is the R-Y and B-Y signals which modulate the chrominance subcarrier in quadrature, and not the I and Q signals.

The statement concerning quadrature modulation may be more clearly understood if we say that we have two chrominance subcarriers which have the same frequency, but which differ in phase by 90°. One of these subcarriers is then modulated by the R-Y signal and the other by the B-Y signal. We may represent the phase relationship between the

two subcarriers by means of a vector diagram, as in Fig. 7 (a), this clearly demonstrating the 90° phase difference. The length of each vector then corresponds to the amplitude of the modulating signal.

As in any similar vector diagram, we may obtain a single vector which indicates the resultant phase and amplitude given by the combination of two out-of-phase quantities. Thus, if the transmitter camera were to scan a colour which caused the R-Y signal to be equal to the B-Y signal, we would obtain a resultant vector lying midway between them, as in Fig. 7 (b).

Let us next examine what resultant vector we obtain when the transmitter camera scans a fully saturated colour, such as red.<sup>1</sup> A fully saturated

<sup>1</sup> It is assumed here that there is negligible difference between a fully saturated colour and the corresponding N.T.S.C. primary colour.

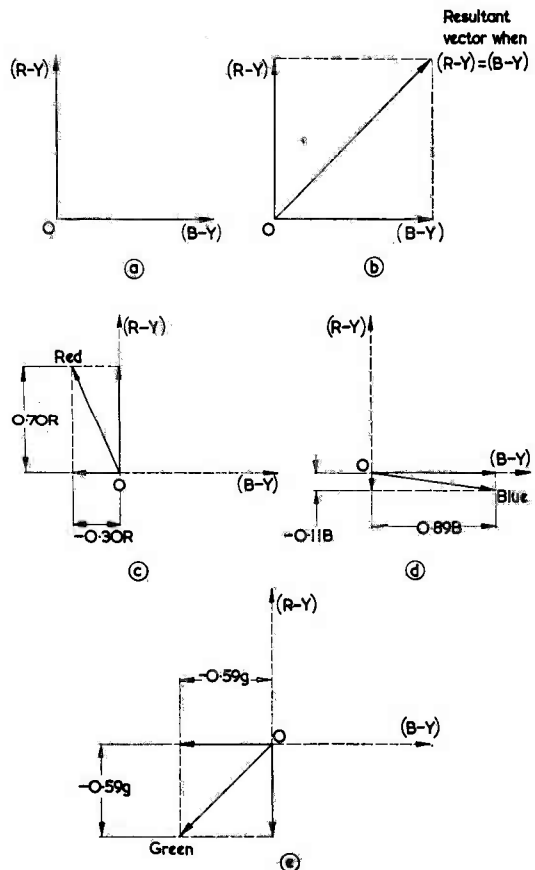


Fig. 7 (a). If the chrominance subcarrier were modulated by the R-Y and B-Y signals, the phase relationship and modulating amplitude could be represented by a vector diagram, as shown here (b). The resultant vector given when the amplitudes of the R-Y and B-Y signals are equal (c). The resultant vector for fully saturated red (d). The resultant vector for fully saturated blue (e). The resultant vector for fully saturated green

red contains no green or blue information, with the result that, in the equation

$$Y = 0.59G + 0.30R + 0.11B,$$

both G and B are equal to zero.

We then have

$$\begin{aligned} Y &= 0.30R, \\ R - Y &= R - 0.30R \\ &= 0.70R. \end{aligned}$$

so that

$$\begin{aligned} \text{At the same time, since B is equal to zero,} \\ B - Y &= 0 - 0.30R \\ &= -0.30R. \end{aligned}$$

The resultant corresponding to fully saturated red then appears in the position shown in Fig. 7 (c),

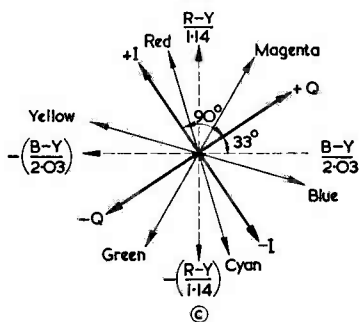
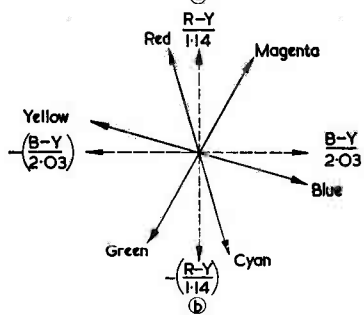
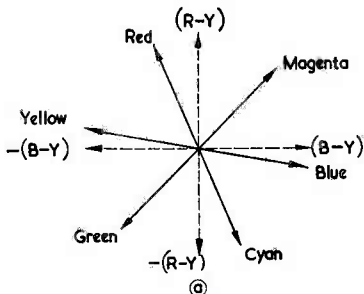


Fig. 8 (a). Since other colours may be formed by combinations of the primaries, it becomes possible to show these as vectors on the R-Y and B-Y axes. Each colour then corresponds, in hue, to the angular position of its vector and, in saturation, to the length of its vector

(b). Before transmission, the R-Y and B-Y signals have to be weighted by dividing them by 1.14 and 2.03 respectively

(c). Adding the I and Q signals to the R-Y and B-Y axes. It is the I and Q signals which actually modulate the chrominance subcarrier

and it corresponds to 0.70R on the R-Y axis and -0.30R on the B-Y axis.

It is worthwhile repeating this exercise with another colour, such as fully saturated blue. A fully saturated blue contains no red or green information, so that, in the formula

$$Y = 0.59G + 0.30R + 0.11B,$$

both G and R are equal to zero.

As a result,

$$\begin{aligned} Y &= 0.11B, \\ B - Y &= B - 0.11B \\ &= 0.89B. \end{aligned}$$

and

$$\begin{aligned} \text{Also, since R is equal to zero, we have} \\ R - Y &= 0 - 0.11B \\ &= -0.11B. \end{aligned}$$

The resultant which corresponds to fully saturated blue may then be drawn as shown in Fig. 7 (d).

If we carry on to a fully saturated green, we have the case where both R and B are equal to zero, whereupon

$$\begin{aligned} Y &= 0.59G, \\ R - Y &= 0 - 0.59G \\ &= -0.59G, \\ \text{and} \\ B - Y &= 0 - 0.59G \\ &= -0.59G. \end{aligned}$$

The resultant for fully saturated green then appears midway between the negative sections of the R-Y and B-Y axes, as illustrated in Fig. 7 (e).

Since all other colours are the result of combinations of two or three of the primary colours, it is possible to similarly plot these about the R-Y and B-Y axes, giving us a diagram such as that shown in Fig. 8 (a). It is interesting to note that these colours appear around the R-Y and B-Y axes in the same order as they appear around the centre of the C.I.E. Chromaticity Diagram.

Fig. 8 (a) illustrates the fact that any colour may be represented as a single resultant vector indicating the phase of a single chrominance subcarrier. The length of the resultant vector then corresponds to the modulation amplitude and, in consequence, to the saturation of the colour. Since the colours appearing around the intersection of the R-Y and B-Y axes correspond to the colours which appear around the centre of the C.I.E. Chromaticity Diagram, it follows that any colour in that Diagram (within the triangle joining the N.T.S.C. primary colours) may be represented by the phase and length of a resultant vector.

If the R-Y and B-Y signals are handled by the colour television system at their correct amplitude (relative to the luminance signal) the combined signal amplitude given when saturated colours are transmitted becomes excessive and cannot be handled without distortion and possible transmitter overload. In consequence, the R-Y and B-Y signals have to be reduced in amplitude, relative to the luminance signal, at the transmitter. In practice, the R-Y signal is divided by 1.14 and the B-Y signal by 2.03. The necessary correction for this reduction is then made at the receiver. The R-Y and B-Y signals are described, after reduction, as being *weighted*.

Because of the weighting factors introduced at the transmitter, our diagram of Fig. 8 (a) must now become altered to that of Fig. 8 (b), wherein the R-Y

axis changes to  $\frac{R-Y}{1.14}$  and the B-Y axis changes to

$\frac{B-Y}{2.03}$ . In all other respects, however, Fig. 8 (b)

offers the same information as Fig. 8 (a). Since the B-Y axis is divided, in length, by a larger number than the R-Y axis, all that has happened is that the diagram of Fig. 8 (b) has been compressed horizontally. The result is a shifting of the angular positions of the vectors which represent the various colours.

We may now introduce the I and Q signals.

It is always desirable to keep the information in the chrominance subcarrier as small as possible. At the same time, we know that the eye is capable of defining some colours in fine detail considerably more readily than it can define other colours. The I and Q signal technique takes advantage of this characteristic of the eye, and allows a high level of useful chrominance information to be transmitted with maximum economy of bandwidth.

The I and Q signal vectors appear on the R-Y and B-Y axes in the manner shown in Fig. 8 (c). These signals may be obtained, at the transmitter, by suitable manipulation of the colour signals from the camera.<sup>2</sup> It is the I and Q signals which actually modulate the chrominance subcarriers, and not the R-Y and B-Y signals, as we have assumed up to now. It will be seen that the I and Q vectors are displaced from each other by 90°, in just the same manner as are the R-Y and B-Y axes. They may, in consequence, similarly modulate two subcarriers having a phase difference of 90°, and enable single resultant vectors (corresponding to the amplitude and phase of a single subcarrier) to be obtained.

The positive I vector has a direction lying between red and yellow, and it corresponds, in fact, to a reddish-orange. If this particular colour, in its fully saturated state, were presented to the transmitter camera, only the I subcarrier would be transmitted, as there is no colour information for the Q signal. The negative I vector has a direction corresponding to a colour in the greenish-blue range. If this colour, in its fully saturated state, were presented to the transmitter camera, the I subcarrier would, again, be the only one transmitted. However, since the negative I vector is in the opposite direction to the positive I vector, the chrominance subcarrier will have suffered a phase reversal of 180°.

The same points apply to the Q signal. The positive Q signal vector corresponds to colours in the magenta range, and the negative Q signal vector corresponds to colours in the yellow-green range.

The colours which the eye can detect most readily in fine detail are the reddish-oranges and the greenish-blues. The magentas and the yellow-greens can, on the other hand, only be distinguished in coloured areas which are much larger. Because of

this, we have the case where the I signal corresponds to colours for which the eye has maximum discrimination, whilst the Q signal corresponds to colours for which the eye has minimum discrimination. It is for this reason that the I and Q signals are employed, and the angular position of their vectors has been purposely chosen to take full advantage of these characteristics of the human eye. The I and Q signals are given bandwidths which ensure that the optimum amount of useful colour information is transmitted without any wasteful expenditure in bandwidth. This requirement is achieved by giving the I signal a bandwidth of 1.5 Mc/s and the Q signal a bandwidth of 0.5 Mc/s.<sup>3</sup>

<sup>3</sup> These figures apply to the American 525 line system. Other systems, with different video bandwidths, may employ different I and Q bandwidths also.

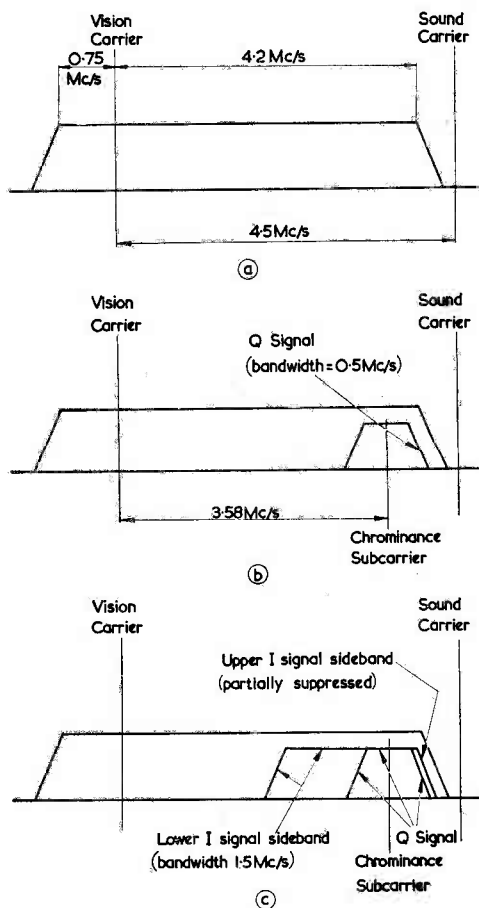


Fig. 9 (a). The ideal transmitter characteristic for monochrome transmission in the American 525 line system. (A nominal video bandwidth of 4.2 Mc/s is assumed.)

(b). Adding the Q signal. There is room inside the video passband for both sidebands of the Q signal. (c). The lower sideband of the I signal may also be transmitted in full, but the upper sideband has to be partially suppressed.

<sup>2</sup> Such manipulation can, indeed, be given by combining the colour signals in simple matrices employing resistive networks.

We may now consider what occurs when a scene is scanned by the colour television camera. All colour information in the scene which gives chrominance signals having frequencies lower than 0.5 Mc/s are handled by both the I and Q signals, thereby allowing full colour reproduction to be achieved at the receiver. Where there is fine colour detail which results in a chrominance signal having a frequency in excess of 0.5 Mc/s the Q signal disappears, because it corresponds to a range of colours over which the eye is least sensitive. Chrominance signals between 0.5 and 1.5 Mc/s are then handled by the I signal on its own, this providing the reddish-oranges and greenish-blues to which the eye is most sensitive.

### The Transmitted Signal

The ideal transmitter characteristic for a monochrome American 525 line signal has the appearance shown in Fig. 9 (a). (A nominal video bandwidth of 4.2 Mc/s is assumed). Let us now add the chrominance subcarrier signals, employing the bandwidths and frequencies pertaining to the American N.T.S.C. system,

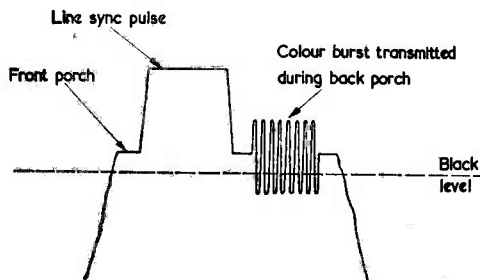


Fig. 10. The colour burst, which is superimposed on the back porch of the line sync signal

In Fig. 9 (b) we introduce the Q signal with its bandwidth of 0.5 Mc/s. The suppressed chrominance subcarrier appears at 3.58 Mc/s (corrected to 3 significant figures), and it is possible for both sidebands of the Q signal to be transmitted whilst still remaining within the confines of the overall 4.2 Mc/s video bandwidth.

The I signal has a bandwidth of 1.5 Mc/s. Its upper sideband would extend to 5.08 Mc/s if it were transmitted in full, and would appear outside the overall video bandwidth. In consequence, part of the upper sideband of the I signal has to be suppressed, whereupon it takes up the appearance

shown in Fig. 9 (c). The lower sideband of the I signal is transmitted in full.

In Figs. 9 (b) and (c) we see that, if the chrominance subcarrier were not suppressed, it would be capable of beating with both the vision carrier and the sound carrier, causing interference to appear in monochrome or colour receivers in the form of patterning. The use of a suppressed subcarrier reduces the interference by a considerable amount. The energy in the chrominance subcarrier sidebands may still cause interference beat signals, however, these increasing in intensity as the saturation of the colours presented to the transmitter camera increases. It is possible to reduce the visible effect of such beat signals by a suitable choice of chrominance subcarrier frequency. In the American N.T.S.C. system, the chrominance subcarrier frequency is 3.579,545 Mc/s.

### The Colour Burst

Because the chrominance signal is transmitted on a suppressed subcarrier, it is necessary for the subcarrier to be reinserted at the receiver before detection can take place. The subcarrier frequency at the receiver is obtained from a local oscillator, and it is essential that this be synchronised with the transmitter subcarrier not only in frequency but also in *phase*. The importance of obtaining correct phase relationship is immediately evident from an examination of the vector diagrams of Fig. 8. If the reinserted subcarrier were not synchronised in phase with the transmitter subcarrier, the transmitted colours would not be accurately reproduced by the receiver.

The local oscillator in the receiver is synchronised by means of a transmitted *colour burst*; this consisting of approximately 9 cycles at subcarrier frequency which are superimposed on the back porch of the line sync pulse, as shown in Fig. 10. These bursts may then be employed for synchronising the local oscillator, using principles which are similar to those encountered in line flywheel sync circuits. The colour burst is not transmitted during vertical sync pulses.

Part of the colour burst cycles appear above black level. It is possible, as a result, for these to become visible on the receiver cathode ray tube screen if there is inadequate blanking during the line retrace period. The visible effect under these conditions is at a minimum when the phase of the colour burst frequency corresponds to that of the negative B-Y vector of Fig. 8. In consequence, the phasing of the colour burst is made equivalent to  $-(B-Y)$ .

(To be continued)

## INDEX VOLUME 16

The index for Volume 16 (August 1962–July 1963) of *The Radio Constructor* is now available. Direct Subscribers will receive a copy of the index with this issue of the magazine.

Copies of the index are available direct from us, 6d each plus 3d postage, etc.



# Kit Review

# The Hiker

## 4-Transistor Portable Receiver


**T**HE "HIKER" 4-TRANSISTOR RECEIVER HAS BEEN designed to cover both the Medium and Long waves and also to be contained within any case or cabinet of the user's choice. A small front panel is fitted to the printed circuit board, on which the majority of the main components are fitted—see illustration.

The construction process is easily carried out and takes only a couple of hours or so to complete, the printed circuit considerably assisting in this respect.

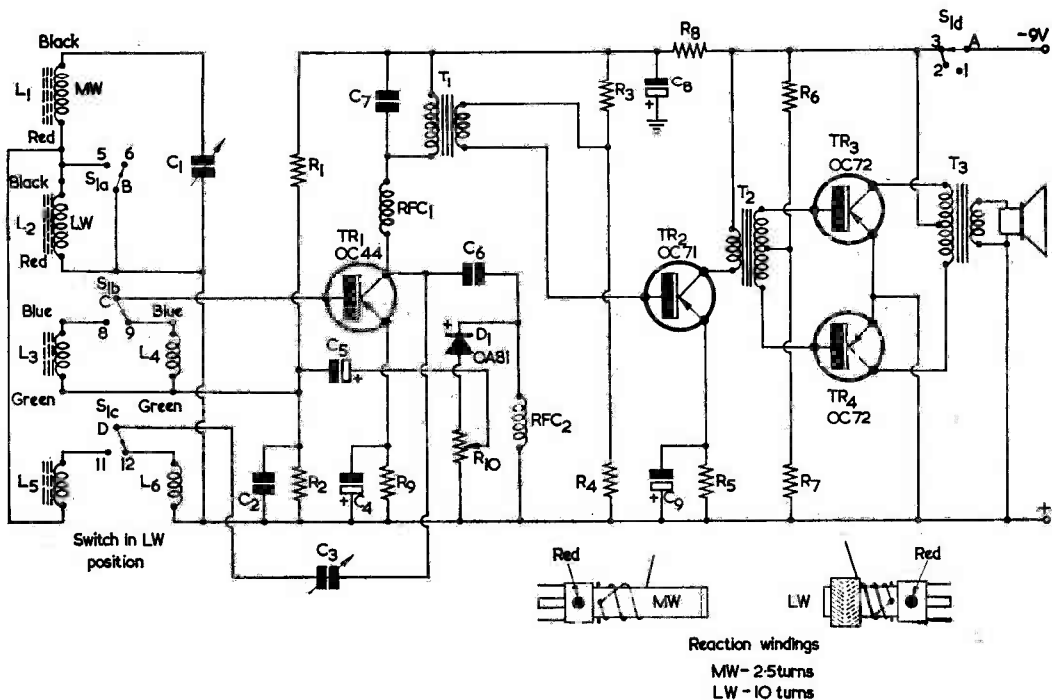
### Circuit

This is shown in the accompanying diagram, from which it will be seen that TR<sub>1</sub> operates as a reflex amplifier with reaction. The coils shown are mounted on a ferrite rod and the 4-pole 3-way switch is illustrated in the Long wave position.

S<sub>1</sub>(a), (b), (c) of the switch operates as the wavechange control, whilst the remaining part of the switch (S<sub>1</sub>(d)) is utilised as the on/off control. In the Long wave position, both L<sub>1</sub> and L<sub>2</sub> are tuned by the variable capacitor C<sub>1</sub> (300pF); the reflex winding (L<sub>4</sub>) and the reaction winding (L<sub>6</sub>) both being brought into circuit. On Medium waves, L<sub>1</sub> is tuned by C<sub>1</sub>, L<sub>2</sub> (Long wave winding) being short-circuited by S<sub>1</sub>(a). The switches S<sub>1</sub>(b) and S<sub>1</sub>(c) respectively bring into circuit the windings L<sub>3</sub> (reflex) and L<sub>5</sub> (reaction). The amount of positive feedback (reaction) applied to L<sub>1</sub>, L<sub>2</sub> from the collector of TR<sub>1</sub> (OC44) is controlled by C<sub>3</sub>. The potentiometer R<sub>10</sub>, connected between diode D<sub>1</sub> (OA81) and chassis, acts as the volume control by varying the rectified signal voltage applied (via L<sub>3</sub> or L<sub>4</sub>) to the base of TR<sub>1</sub>. The inclusion of RFC<sub>1</sub> and RFC<sub>2</sub> ensures that the required r.f.



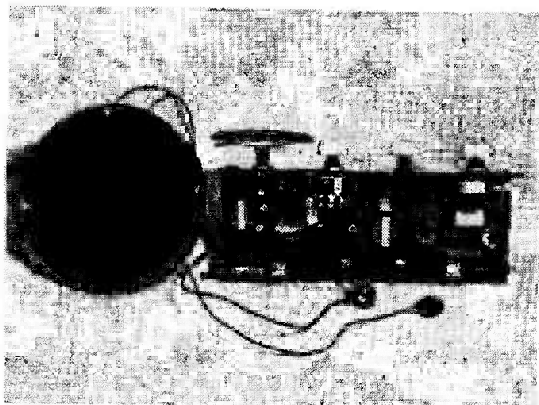Reaction windings  
MW - 2.5 turns  
LW - 10 turns  
Wound in the opposite direction to the aerial coil with cotton covered enamel copper wire, approx. 30swg.



General view of the "HIKER" transistor receiver

voltage is applied to  $C_3$  and diode  $D_1$ . The resultant rectified and amplified audio signal is next fed, via the transformer  $T_1$ , to the base of the following transistor  $TR_2$  (OC71). Operating in the earthed emitter mode,  $TR_2$  acts as the driver stage, its output signal being applied to both  $TR_3$  and  $TR_4$  (OC72) via the driver transformer  $T_2$ .  $T_2$  provides

the correct impedance match into the push-pull output pair of transistors. The output from  $TR_3$  and  $TR_4$  is finally fed to the primary of  $T_3$  (output transformer) and thence to the speaker.

The coils are shown as an inset in the diagram, the illustration clearly showing the correct method of assembly with respect to these components.

#### Operating Hints

Once completed, the receiver should be operated as follows. Fully open the reaction capacitor ( $C_3$ ) and turn the switch  $S_1$  to the centre position (Medium wave). Tune in the desired station by rotating the variable capacitor  $C_1$  and increase gain by closing  $C_3$  until the receiver is just below the point of oscillation. Adjust the volume control  $R_8$  for the required amount of audio output. It will be found that the receiver has good selectivity characteristics for a single tuned circuit design, this being due to the high Q of the  $FR_2$  ferrite aerial and the use of reaction. The aerial assembly can be utilised to improve selectivity by altering the orientation of the receiver.

The "Hiker" receiver is available direct from Repanco Ltd, O'Brien's Buildings, 203-269 Foleshill Road, Coventry, complete constructional details being provided with each kit of parts.

### Components List

#### Resistors

$R_1$	68k $\Omega$
$R_2$	10k $\Omega$
$R_3$	47k $\Omega$
$R_4$	10k $\Omega$
$R_5$	680 $\Omega$
$R_6$	6.8k $\Omega$
$R_7$	150 $\Omega$
$R_8$	470 $\Omega$
$R_9$	680 $\Omega$
$R_{10}$	10k potentiometer

#### Switch

$S_1$ (a), (b), (c), (d) 4-pole, 3-way

#### Speaker

3 $\Omega$  5in round

#### Ferrite Aerial

$FR_2$  (Repanco Ltd).

#### R.F. Chokes

$RFC_1$ , Type  $RF_1$  (Repanco Ltd)  
 $RFC_2$ , Type  $RF_2$  (Repanco Ltd)

#### Transformers

$T_1$  Type TT49 (Repanco Ltd)  
 $T_2$  Type TT45 (Repanco Ltd)  
 $T_3$  Type TT46 (Repanco Ltd)

#### Capacitors

$C_1$	300pF variable
$C_2$	0.02 $\mu$ F
$C_3$	100pF variable
$C_4$	100 $\mu$ F electrolytic 6V wkg.
$C_5$	8 $\mu$ F electrolytic 6V wkg.
$C_6$	100pF s. mica or ceramic
$C_7$	0.01 $\mu$ F
$C_8$	100 $\mu$ F electrolytic 9V wkg.
$C_9$	100 $\mu$ F electrolytic 6V wkg.

#### Semi-Conductors

$TR_1$	OC44 Mullard
$TR_2$	OC71 Mullard
$TR_3, TR_4$	OC72 Mullard (matched pair)
$D_1$	OA81 Mullard

#### Printed Circuit Board

Complete with front panel and brackets (Repanco Ltd)

#### Battery

9V Vidormax type VT9

#### Miscellaneous

Battery studs, screws, wire, etc.

# Single Transistor Loudspeaker Receiver

By Sir Douglas Hall, K.C.M.G., B.A. (Oxon)

An ingenious single transistor circuit which offers a loudspeaker output when a strong local signal is available

**W**HETHER IT IS BEER OR DECIBELS, there is a fascination in getting a quart out of a pint pot. In the 1920s, when valves cost a lot and lit up the room with their heavy current consumption, the single valve reflex was to be seen in many homes which were close to a transmitter. Reflex circuits have come back into vogue with the advent of the transistor, but appear nearly always in the earlier stages of the circuit only. There are difficulties in designing a single transistor reflex circuit capable of giving reasonable results on a loudspeaker, as high frequency transistors can only handle a few milliwatts of power, and most low frequency transistors are useless at frequencies round about 1 Mc/s.

This is a description of a circuit which will give about 20 milliwatts of power output from a local station transmitting in the Medium wave-band. Provided a sensitive loudspeaker is used, not smaller than 7 x 4in, or 6½in round, this is

sufficient volume for quiet programme value in quite a large room. It is more than enough for bedside listening. As a test whether the local station is local enough, it can be said that the circuit will be satisfactory if even weak headphone signals can be received on a simple crystal set without undue interference from another station. But it is strictly a local station receiver with the tuning pre-set to one frequency.

## The Transistor Employed

The transistor used is a GET114 or GET103. There is nothing to choose between these, but one or the other should be used. The advantage of these transistors is that, although they are designed for low frequency use, their  $\alpha$  cut-off frequency is about 1 Mc/s for an average specimen. Also, they will oscillate at rather higher frequencies than this, provided, of course, they

are used as common base amplifiers.

A common base amplifier gives less gain than a common emitter amplifier, but if high frequency amplification is obtained through reaction there is no difference, as the same maximum reaction amplification is obtained on the threshold of oscillation in each case. If Fig. 1 is studied, it will be seen that  $L_1$  and the section of  $L_2$  between points 3 and 4 provide the necessary coupling, and that the reaction control  $R_1$  will produce oscillation as its slider moves near to  $C_3$  (provided that the capacitance of  $C_3$ , in parallel with  $C_4$ , is of a suitable value for the particular transistor in use). A total of about 1,000pF will probably be found to be right, but there is sufficient variation in the capacitance of  $C_3$  to compensate for the differences in characteristics of different transistors. This, of course, assumes that a first-grade transistor will be used, of one or other of the two types recommended.

The very considerably amplified signal appearing in the tuned circuit  $L_1 C_1$  is applied to the diode  $D_1$  by way of the whole of the secondary coil,  $L_2$ . There is sufficient self-capacitance in the windings of  $T_1$  for rectification to take place, and no external capacitor should be added. The low frequency signal, amplified by  $T_1$ , is applied to the base of the transistor which, at low frequencies, will be seen to operate as a common emitter amplifier.

## The Aerial

The aerial is connected, through  $C_6$ , to the base of  $TR_1$ . An alter-

## Components List

### Capacitors

- $C_1$  250pF Trimmer (see text)
- $C_2$  500pF
- $C_3$  750pF Trimmer
- $C_4$  500pF (see text)
- $C_5$  100 $\mu$ F, 12 v.v., Electrolytic
- $C_6$  0.01 $\mu$ F
- $C_7$  0.01 $\mu$ F

### Resistors

- $R_1$  250 $\Omega$ , wirewound pot
- $R_2$  47k $\Omega$

### Transformers

- $T_1$  Output transformer type MRT/2, Elstone
- $T_2$  Output transformer type TT5, Repanco

### Coil

- $L_1, L_2$  See text and Fig. 2

### Semi-conductors

- $TR_1$  GET114 or GET103
- $D_1$  OA81, Mullard

### Switch

- $S_1$  s.p.s.t. on/off switch

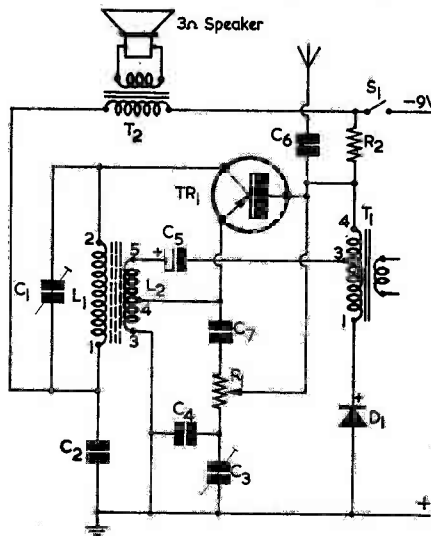


Fig. 1. The circuit of the single transistor receiver

native arrangement would be to use  $L_2$  as an aerial coupling coil, but the connection shown in Fig. 1 works better, particularly with a high capacitance aerial. There is probably very little real (as against regenerative) high frequency amplification, but there is the advantage that the aerial causes very little damping of the tuned circuit and can therefore be tightly coupled—as is required in a simple local station receiver where selectivity is not a problem. The impedance between aerial and earth is low, but so is the internal impedance of the transistor between base and emitter. Indeed, what would normally be a very inefficient aerial can give excellent results, and it will probably be found that a connection to a cold water tap does very well, notwithstanding its own contact with earth. Also, a separate earth should be used and, because of the possibility that both aerial and earth may be at the same direct current potential,  $C_6$  is included to prevent the base of  $TR_1$  finding itself without negative bias on its emitter.

In the case of the prototype, results on a fairly good outside aerial and a very good outside earth are inferior to those obtained using a cold water pipe as aerial and the earth socket of a power plug as earth! One of the reasons for the circuit's predilection for high capacitance aerials is that capacitance between base and earth (and hence between aerial and earth) is necessary for reaction. Within reason, the more capacitance that can be introduced by a signal-producing device the less has to be added externally, and the aerial input impedance of the circuit is consequently not reduced so drastically. For the same reason, the circuit is very demanding in its need for a good earth connection, and functions badly without one.

It will be seen that there is no stabilising resistor in the emitter circuit, but this is not required (and, indeed, cannot be efficiently introduced) because of the effect of the rectifier,  $D_1$ . It will be found that, with  $R_1$  at its minimum position, some 8 to 12mA will flow through  $TR_1$  (depending on the exact characteristics of  $TR_1$  and  $D_1$ ). As the local station is brought up by reaction the current will drop until, near the point of oscillation and assuming a strong signal, it may be as little as 2 to 3mA. This drop in current is due to the positive potential applied to the base of  $TR_1$  by  $D_1$ , in opposition to the standing negative bias provided by the potentiometer formed by  $R_2$ ,  $T_1$  and  $D_1$ . If  $TR_1$  heats

up and tends to take more current, increased reaction takes place owing to the increased efficiency of  $TR_1$ . A larger positive potential is produced by  $D_1$ , and the current drops. The circuit has pre-set tuning, so there will always be a signal for  $D_1$  to rectify. It is presumed that the listener will not leave the receiver switched on when the transmitter is not operating. However, even if he did go to sleep before the programme finished, it is doubtful whether  $TR_1$  would suffer!

### Specified Components

This is a circuit which requires certain specified components and may not work with substitutes. The author has tried several different transistors, and the only one which worked anything like as well as the GET114 and the GET103 was, curiously enough, a very cheap Red Spot surplus type without any branding.  $D_1$  should be a first grade OA81 and not a surplus type. It is important that its resistance should not vary beyond the normal limits of an OA81.

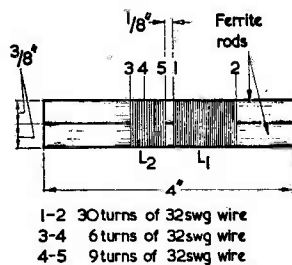


Fig. 2. Winding details for  $L_1$  and  $L_2$

$T_1$  plays a very important part. It should be an Elstone valve type output transformer No. MRT/2, and is connected to give a step-up ratio of 3:1. A transistor transformer does not work as well in this position. Although other valve output transformers might be satisfactory, the circuit has been designed round the MRT/2, which costs no more than some transistor transformers. It is, of course, rather larger, though still small for its type. The numbers shown in Fig. 1 will be found stamped on the transformer. Its secondary is left disconnected.

$T_2$  is a Repanco TT5, and if a different transformer is used it should have similar characteristics. The whole of the primary winding is used. The coil  $L_1$   $L_2$  is non-standard and must be made. As it is essential for it to have a high  $Q$  in order to encourage  $TR_1$  to

oscillate in the Medium waveband, the coil is wound on ferrite rod, but there is no intention that the circuit should be used without an external aerial and earth. Two 4in lengths of  $\frac{1}{8}$ in rod are required, and can be made by snapping a standard 8in rod in two. The two rods are bound together with Sellotape, as shown in Fig. 2.  $L_2$  is wound on first, consisting of 15 turns of wire, close wound, with a tapping at the end of the sixth turn.  $L_1$  follows in the same direction after a gap of  $\frac{1}{2}$ in, and consists of 30 turns, close wound. 32 s.w.g. wire is used for both windings, which should be roughly at the mid-point of the rods. The windings are covered with Sellotape.

$C_1$  is specified as a 250pF trimmer, and this value is suitable for most local stations likely to be used. But 100pF would be more suitable for stations below about 260 metres, and 500pF for the North Home Service on 434 metres.

It has been emphasised that this circuit is only suitable for local station reception in fairly good reception areas. More distant stations can be received, weakly, but cannot be brought up satisfactorily in strength as there will be instability and backlash in the reaction circuit on weak carrier waves. With a strong signal the reverse bias produced by  $D_1$  results in a smooth build up.

### Setting Up

In order to set the receiver up for the local station,  $R_1$  should be adjusted to its maximum position (i.e. with its slider at the end connected to  $C_3$ ) and  $C_3$  opened right up.  $C_1$  should be adjusted until signals are heard and then  $C_3$  tightened gradually,  $C_1$  being simultaneously slackened off a little to keep the signal in tune, since there is interaction between the two trimmers. This process should be continued until the signal is at its loudest without oscillation. If there should be oscillation on the local station with  $C_3$  wide open,  $C_4$  should be removed from the circuit.

It is up to the constructor to decide whether he wishes to arrange things so that  $R_1$  can just be taken to its maximum position without oscillation, or whether he prefers oscillation to set in near the maximum setting. The second alternative allows for a fall in voltage of the battery as it ages.

For good results there should be a drop of at least 4mA in the current taken by  $TR_1$  as  $R_1$  is advanced from its minimum position to a position just short of oscillation,

and this will be achieved unless the local station is too far away or the aerial or earth not up to requirements. With a strong signal from the local station the current may drop to as little as 2mA, which is too low to provide reasonable output; and in these circumstances listening should

be done at a setting of  $R_1$  rather below the maximum possible. About 5 to 6mA provides an output of 20 milliwatts and is easy on the battery. Because of the a.g.c. action produced by  $D_1$ , there is little increase in amplification if reaction is increased to a point

where the current drops below 5mA. It is, no doubt, obvious that a milliammeter with a maximum reading of about 15mA is very useful in setting up this receiver, as the a.g.c. effect makes audible effects a little difficult to judge. But a meter is by no means essential.

# Two-Transistor Timer with Positive Feedback

By M. D. DEVENISH

*An Ingenious timing circuit which offers consistent timing periods with very quick relay operation*


**A** RECENT ARTICLE IN THE "SUGGESTED CIRCUIT" series\* describes a two-transistor timer which offers quick de-energising of the relay at the end of the timing period. This is achieved by connecting a battery in series with the capacitor in the time constant circuit, this battery maintaining the first transistor in a cut-off condition until the period is nearly complete.

The timer circuit described in the present article employs a somewhat similar basic principle. However, a positive feedback circuit has been incorporated which makes relay operation very much quicker than in the earlier design. Also, the circuit may be operated from a single 9 volt battery, instead of the two batteries previously required.
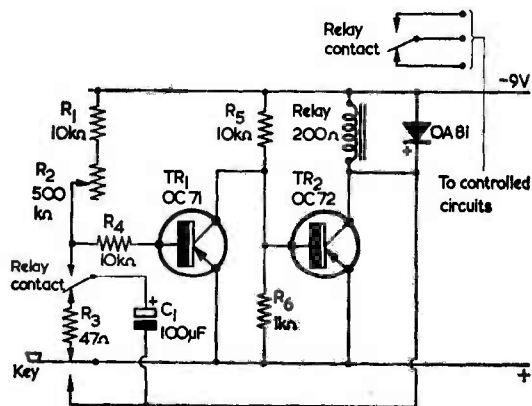
### The Circuit

The writer's circuit appears in Fig. 1. The relay employed has two sets of contacts (shown "detached" from the coil and in the de-energised condition), one of these appearing in the base circuit of  $TR_1$  whilst the other controls the external circuit. The operation of the timer may be described in the following manner.


Initially,  $TR_1$  is conducting and  $TR_2$  non-conducting, the base current of  $TR_1$  through  $R_1$ ,  $R_2$  and  $R_4$  being such that the collector current passing through  $R_5$  produces a large enough voltage drop across this resistor to cut off  $TR_2$ . The relay is thus de-energised. Also, the upper plate of  $C_1$  is returned, via the relay contact,  $R_3$  and the operating key, to the positive battery potential. The lower plate of  $C_1$  is at the collector potential of  $TR_2$ . As  $TR_2$  is non-conducting, this plate will be nearly at the negative battery potential. Upon depression of the key to initiate



the timing cycle, the upper plate of  $C_1$  is first isolated from the positive battery terminal by the key contact. The positive potential is then applied both to the lower plate of  $C_1$  and to the lower end of the relay coil. This causes a change of potential of nearly 9 volts on  $C_1$ , driving the upper plate nearly 9 volts positive relative to the positive battery potential, and it also energises the relay. When the relay makes its contacts, the upper plate of  $C_1$  is connected to the base of  $TR_1$ , thus cutting off the collector current of this transistor, and allowing  $TR_2$  to draw base current through  $R_5$ . Thus the feed to the relay is maintained via  $TR_2$ . When the key is released the voltage on the lower plate of  $C_1$  is maintained by the direct connection from the collector of  $TR_2$ , which is now nearly at the battery positive potential.

The capacitor  $C_1$  next proceeds to discharge through  $R_1$  and  $R_2$  via the relay contact. The timing period is determined by the time constant of this circuit, and may be altered by varying  $R_2$ .

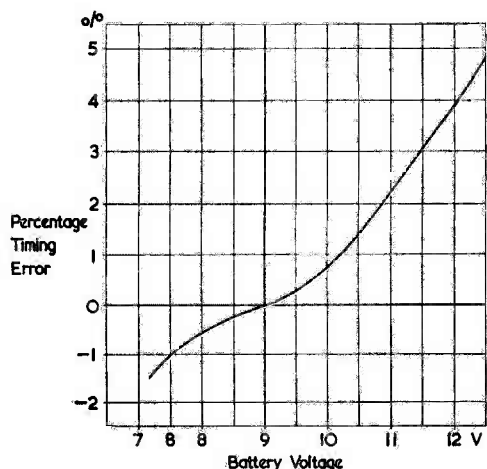\*"Suggested Circuit" No. 143, "Electronic Timer with Fast Relay Operation", *The Radio Constructor*, October 1962.



As soon as the potential on the upper plate of  $C_1$ , and therefore the base of  $TR_1$ , rises above the positive battery potential,  $TR_1$  starts to conduct. This, in turn, reduces the base current of  $TR_2$ , which starts to cut off. As it does so, its collector begins to go negative. This negative voltage is fed back via  $C_1$  to the base of  $TR_1$ , causing a very rapid build-up of current in  $TR_1$ , and, consequently, a very rapid cut-off in  $TR_2$ . This action results in extremely fast relay operation. As soon as the relay de-energises, the upper plate of  $C_1$  is returned to positive battery potential via  $R_3$ , and the unit is automatically reset for subsequent use.

In view of the extremely fast relay operation, it is essential that a diode be connected across the relay coil to prevent high voltages being induced at the collector of  $TR_2$ . Also, with the large amount of positive feedback, a limiter resistor,  $R_4$ , is essential in series with the base of  $TR_1$ .

It is impracticable to draw a graph of relay current versus time, as was given for the previous design, because the change in current is too rapid for any meter to follow. To verify this point, the writer increased the value of  $C_1$  to  $5,000\mu\text{F}$  and connected a meter across  $TR_2$ . The timer ran for 39 minutes and then the relay contacts snapped open, apparently absolutely simultaneously with the first hint of movement of the meter needle.

#### Tests

A series of tests were carried out for a fixed setting of  $R_2$ . The timings were found to be consistent to within  $\pm 0.75\%$ .


Tests were also conducted on the effect of varying battery voltage, and the results are shown graphically in Fig. 2, in the form of percentage timing variations from the time obtained with a 9 volt

supply. It will be noted that this error is within  $\pm 1\%$  from 7.5 to 10 volts. It should therefore be reasonable, assuming the battery to be within 0.5 volt of its nominal value, to claim an overall accuracy of  $\pm 1\%$ .

Fig. 3 is provided to give an idea of what maximum timings may be expected from various values of  $C_1$ . The precise timings obtained will of course depend upon the leakage resistance of the capacitor actually used for  $C_1$ .
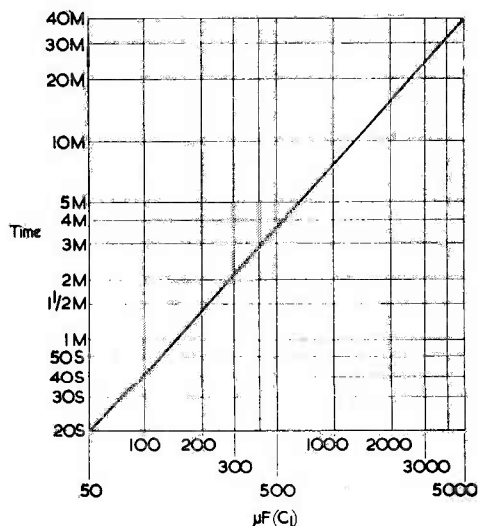
#### Points of Design

A 9 volt supply was employed for the timer because of the wide variety of batteries of this voltage available. It was also felt that a mains version might be constructed, using one of the advertised 9 volt battery eliminator packs.



A  $200\Omega$  P.O. type 3000 relay was chosen, it being fitted with two change-over contacts. This relay was found to operate at 7.2 volts, and it gives very reliable operation on the 9 volt supply. It is well within the handling capabilities of the OC72 transistor. The values of the bias resistors were decided on the basis of a current gain of 50 per transistor.

In the author's finalised design it is proposed to use a capacitor of approximately  $200\mu\text{F}$ , to give about 1.5 minutes time. It is also felt that a logarithmic potentiometer in the  $R_2$  position would be an asset, as the non-linear scale resulting would provide for greater accuracy in setting the shorter timings.

Next Month . . .

3-TRANSISTOR RECEIVER

ELECTRICAL SPEEDOMETER

# Preparing Radio Panels

By J. Anderson

**P**REPARING RADIO PANELS MAY, AT first sight, seem rather a strange subject for an article, and the reader may feel that such a topic barely merits writing about. However, the average constructor takes pride not only in the performance but in the appearance of his equipment, and it is worth spending a little more than the usual time on preparing a panel which is not only clearly labelled and well laid out, but which is also pleasing to the eye.

## Panel Material

The first concern, of course, is the material of which the panel is to be made. Assuming access to a suitable drill, there is no material to equal hard steel, especially if the panel is to play a part in supporting the internal chassis and controls. If, on the other hand, the controls are to be mounted on a frame, with only the spindles projecting through the panel, then dural or aluminium is better, as it will save a surprising amount of weight.

The layout of the controls must be planned before the panel is prepared. In many cases, and particularly in high-frequency equipment, layout will be in part dictated by the internal screening and the necessary shortness of all leads. If complete flexibility is available, it is usually better to have sockets at the foot or at one end of the panel to keep trailing leads out of the way, and controls which require delicate adjustment at the top for the same reason. "Logical progression" of controls is also sensible, as is given by placing the controls in rough order of their position in the circuit, starting at one end. It is worthwhile noting here that the more delicate controls, such as tuning, are often placed at the right-hand end, as most people are right-handed.

When the control layout has been planned, the panel should be well sandpapered down, back and front, and then washed with spirit or petrol to ensure a grease free surface for

painting. Drilling, of course, will be carried out at this stage. If the reader wishes to smarten-up an item of ex-Government equipment, then the sanding down stage will be an ideal starting place.

## Painting

Paint is best applied in two coats to allow for greater permanency, and a hard lacquer is best. Plastic enamels, whilst cheap and smart, wear and scratch quickly.

The colour of the panel will, of course, be dictated by the taste of the individual although, in general, light grey or black are good choices from the point of view of cleanliness and clarity. If the case around the unit is separate, then the panel can be the same colour or a few shades darker.

When the second coat of paint has hardened the control wording should be applied. "Panel Sign" transfers are ideal for this, being very easily applied. A small pair of tweezers may be a useful aid here. For knobs which operate "click switches" with several positions, it is wise to fit the control temporarily in place with its knob, this ensuring absolute accuracy in positioning the markings.

After the transfers have had a period of drying out, a coat of clear varnish makes an ideal finish, either over the transfers alone, or over the entire panel as an additional protection. If the panel has been finished in matt paint (which is very liable to collect dust) then matt varnish can be obtained to cover the transfers, but this should be applied thinly. Convention dictates that the transfers be above the controls, but if the apparatus is to be placed permanently on a shelf above the work bench, or at the top of a rack, it should be obvious as to where the transfers are best sited.

## Knobs and Sockets

"Handles", or knob-protectors, at each end of the panel (or one

horizontal in the middle for a small panel) are an excellent idea, and look attractive if finished several shades lighter than the panel itself. A final touch is provided by a set of matching knobs, skirted knobs being best for keeping dust out of the hole behind them, and for keeping fingers off the paint. High-voltage switches and plugs are often painted red for safety reasons, but this is of doubtful value and usually succeeds in giving a rather garish overall effect.

Many items of ex-Government equipment have small test panels on them, these carrying a row of studs or sockets. The test panel on the R107 is an example in point, and is one which is probably quite well known. This sort of dust collector can be replaced with a small panel carrying only two meter sockets and a Yaxley switch to select the metering point, giving thereby a much more "hand-built" appearance to the entire set. The balancing of large panel components should be borne in mind. A large mains plug should obviously be at the opposite end of the panel from a large vernier tuning dial, and if the unit carries two meters they are best placed one on each side of the mid-line rather than one above the other. Large labels and a multiplicity of red lights are to be avoided, and so are over-large ventilating apertures because of the effects of hand capacitance. If a loudspeaker is to be fitted directly to the front panel, the latter must be very securely fixed to prevent rattling. It should also be attached at several points to the chassis or frame to "kill" the metallic sound which usually results from using the panel as a baffle.

In conclusion, when finishing off your next construction job think of the effect the remark, "I made it myself" will have on a non-technical person—and aim for that professional finish.



# Identifying Surplus American Electronic Equipment

By Ken Greenberg

**A**ERICAN MILITARY ELECTRONIC EQUIPMENT IS designated by a series of letters and numbers which often can tell you much about its original use and purpose. Presently available surplus radio equipment is designed according to one of three systems.

## Signal Corps System

This is the oldest equipment coding system and has been discontinued because there was no way of knowing from the designations which individual equipments belonged to a complete system. Here are some of the most common prefix letters used and their meanings:

SCR	Set Complete Radio
AN	Antenna
BC	Basic Component
DM	Dynamotor
VT	Vacuum Tube
PL	Plug
FT	Mount, Rack or Adapter
RA	Rectifier Power Supply
TS	Test Set

Under this designation system an overall equipment was SCR, followed by an arbitrary number and suffix letter which represented the model or modification. However, using this system there was no way to determine, for example, whether the BC-453A is the receiver or the BC547A the transmitter in the SCR-274N. Also, you could not tell from the designation that the SCR-274N was used in aircraft for two-way radio communications. As you can see, this system does not have much identification value.

## Navy Model Letter System

Although no longer used to any extent, there is still much naval equipment in use identified by this system. The assignment of letters depends on the primary function of the equipment. The first letter indicates the basic purpose of the equipment, except where the word "MARK" is used to indicate Bureau of Ordnance equipment.

These first letters are explained in Table I.

The second letter indicates the order the designation was assigned, except for the letter X which is used to indicate experimental equipment. The letters TA, for example, would indicate the first transmitting equipment assigned, TB the next and so on. Triple letters like TAA, TBA, etc., are used when the alphabet is exhausted.

## "AN" System

All American military services are now using the Joint Nomenclature System ("AN" System) to identify electronic equipment, including independent units that are not parts of specific equipment. Complete systems are designated by three equipment indicator letters that follow AN/, and signify kind of installation, type of equipment and its purpose. These indicator letters are explained in Table II.

Using the letters in Table II, the AN/ARC-3 is, for example, identified as follows. The A means it is installed in an aircraft, the R means it is radio equipment and the C means it is used for transmitting and receiving communications. The number 3 indicates this was the third equipment designated with the letters ARC. System indicator letters "AN" do *not* mean that the Army, Navy and Air Force all use the same equipment, but simply that the type number was assigned in the "AN" system.

Independent units not part of, or used with, specific sets have a type number consisting of a component indicator letter, a number, the slant (/), and whatever equipment indicator letters (from Table II) apply. Using the R44/ARR-5 as an example, R44 is the independent component designation of an Airborne Radio Receiver (No. 5 in the ARR series). The "AN" system component indicator letters are listed in Table III.

From the preceding information, you should be able to identify much of the American surplus equipment you come in contact with personally, or see advertised in publications. Knowing the original installation, use and purpose may very well prevent you from acquiring a worthless piece of equipment.

TABLE I

### Navy Model Letter System

A	Airborne installations
B	IFF
CX	Commercial experimental
D	Radio direction finding
E	Emergency power
FS	Frequency shift keying
G	Aircraft transmitting (superseded by "A")
J	Sonar listening (receiving)



- K Sonar transmitting
- L Precision calibrating
- M Combined radio transmitting and receiving
- MARK Fire control radar
- N Sonar navigational aids (echo sounding)
- O Operator training and measuring
- P Automatic transmitting and receiving
- Q Sonar ranging
- R Radio receiving
- S Search radar
- T Radio transmitting (includes combination transmitting and receiving)
- U Remote control (automatic keyers)
- V Radar repeaters

- W Combined sonar ranging and sounding
- X Experimental
- Y Navigational and landing aids
- Z Navigational and landing aids (superseded by "Y")

In sonar equipment, the first letter indicates the general use of the equipment. The second designates the type of projector used as follows:

- QA Quartz steel
- QB Rochelle salt
- QC Magnetostriction
- QD Depth determining
- QG Magnetostriction (split-lobe)

**TABLE II**

**"AN" System Equipment Indicator Letters**

<i>Installation</i>	<i>Type of Equipment</i>
A Airborne (installed and operated in aircraft)	A Invisible light, heat radiation
B Underwater mobile (submarine)	B Pigeon
C Air transportable (obsolete)	C Carrier (wire)
D Pilotless carrier	F Photographic
F Ground fixed	G Telegraph or teletype (wire)
G Ground, general ground use	I Interphone and public address
K Amphibious	K Telemetering
M Ground mobile	M Meteorological
P Ground, pack or portable	N Sound in air
S Water surface craft	Q Radar
T Ground, transportable	P Underwater sound
V Ground, vehicular (in vehicles not primarily designed for carrying electronic equipment)	R Radio
U General utility (two or more general installation classes. Airborne, shipboard and ground)	S Special types (magnetic, etc.)
W Underwater, fixed	T Telephone
	V Visual and visible light
	X Facsimile or television

*Purpose*

- A Auxiliary assemblies (not complete operating sets)
- B Bombing
- C Communications (receiving & transmitting)
- D Direction finder
- G Gun directing
- H Recording (sound, photographic & meteorological)
- J Countermeasures (receiving & transmitting)
- L Searchlight control
- M Maintenance & test assemblies
- N Navigational aids (altimeters, beacon compasses, depth sounding, instrument landing)
- P Reproducing (photo and sound)
- Q Special (or combination of types)
- R Receiving or listening
- S Detecting and/or range and bearing
- T Transmitting
- W Remote control
- X Identification and recognition

**TABLE III**

**"AN" System Component Indicator Letters**

AB Supports, antenna	CK Crystal kits
AM Amplifiers	CM Comparators
AS Antenna assemblies	CN Compensators
AT Antenna	CP Computers
BA Battery, primary type	CR Crystals
BB Battery, secondary	CU Coupling devices
BZ Signal devices, audible	CV Converters (electronic)
C Control articles	CW Covers
CA Commutator assemblies, Sonar	CX Cords
CB Capacitor bank	CY Cases
CG Cables & transmission line (R.F.)	DA Antenna, dummy

DT	Detecting heads	RD	Recorders and reproducers
DY	Dynamotors	RE	Relay assemblies
E	Hoist assembly	RF	Radio frequency components
F	Filters	RG	Cables and transmission line, bulk R.F.
FN	Furniture	RL	Reel assemblies
FR	Frequency measuring device	RP	Rope and twine
G	Generator	RR	Reflectors
GO	Goniometers	RT	Receiver and transmitter
GP	Ground rods	S	Shelters
H	Head, hand and chest sets	SA	Switching devices
HC	Crystal holder	SB	Switchboards
HD	Air conditioning equipment	SG	Generators, signal
ID	Indicating devices	SM	Simulators
IL	Insulators	SN	Synchronisers
IM	Intensity measuring device	ST	Straps
IP	Indicators, cathode-ray tube	T	Radio and radar transmitters
J	Junction devices	TA	Telephone apparatus
KY	Keying devices	TD	Timing devices
LC	Tools, line construction	TF	Transformers
LS	Loudspeakers	TG	Positioning devices
M	Microphones	TH	Telegraph apparatus
MD	Modulators	TK	Tool kits or equipments
ME	Meters, portable	TL	Tools
MK	Maintenance kits or equipments	TN	Tuning unit
ML	Meteorological devices	TS	Test equipment
MT	Mountings	TT	Teletypewriter and facsimile apparatus
MX	Miscellaneous	TV	Tester, tube
O	Oscillators	U	Connectors, audio and power
OA	Operating assemblies	UC	Connectors, R.F.
OS	Oscilloscope, test	V	Vehicles
PD	Prime drivers	VS	Signalling equipment, visual
PF	Fittings, pole	WD	Cables, two conductor
PG	Pigeon articles	WF	Cables, two conductor
PH	Photographic articles	WM	Cables, multiple connector
PP	Power supplies	WS	Cables, single conductor
PT	Plotting equipments	WT	Cables, three conductor
PU	Power equipments	ZM	Impedance measuring device
R	Radio and radar receivers		

# Radio Topics . . .

By RECORDER

## MORALITY.

This is a word which, until recently, many of us have rarely considered or even thought about. At the time of writing these notes—and due to events outside this column's range—the subject of morality (not entirely unalloyed by cant) has been continually and insistently hammered home to every one of us in every newspaper we pick up. We have suddenly realised that morality is important.

My own thoughts on morality have run largely on the subject of petty theft, and follow my reading about a series of shop-lifting cases reported in a local newspaper. After consideration I have found, somewhat

to my surprise, that peccadilloes of this type are judged, so far as generally accepted ethics are concerned, not by their nature at all but by their *degree*. That this state of affairs is true can, I feel, be borne out very well by taking examples from the field of manufacture, wherein small and relatively inexpensive parts are handled in large numbers at a high rate of consumption. I don't think that modern mass-production methods have resulted in the unanticipated appearance of a self-regulating level which divides acceptable behaviour from the non-acceptable, because a self-regulating level of this type has been in existence for many years. Few

people raised an eyebrow if, a hundred years or so ago, the butler retired to bed slightly squiffy on his master's port. Nevertheless, I do feel that modern mass-production methods have spread the opinion that "perks are legitimate" over a far wider range than has ever existed before.

## "It Won't Be Missed"

Should you ever call on a large factory which produces radio or television receivers, you may find it instructive to keep an eye on the pavement over the last fifty yards or so before you arrive at the gate. If you look hard enough, it is very probable that you will see at least

several small resistors and capacitors lying around on the ground. These will have reached the street because, during working hours, they fell into the trouser turn-ups of men employees—or were caught in the skirts or dresses of female employees—and then became subsequently dislodged as the employees walked home after the end of work. The important point is that nobody at the factory will have missed these odd few components at all. This is because, when high quantity mass-production schedules are in operation, small resistors and capacitors are, quite simply, not counted!

Let us assume that one of the production lines in the factory is turning out a sub-assembly which requires, amongst other things, one 27kΩ 10% ½ watt resistor. Production is aimed at 2,000 per day, and those responsible for keeping the line provisioned have to ensure that the operator who fits the resistors always has a good supply of them available. The resistors will be kept in a small bin, or container, in front of the operator, and we could say that a line-feeder (i.e. a person whose job it is to keep all bins on the line replenished) drops 200 resistors into this bin ten times a day. Now, these 27kΩ resistors will be received in quantities of, say, 1,000 from the resistor manufacturer. The boxes in which the resistors arrive will each be marked as containing 1,000, and nobody would doubt this marking. To make up 200 resistors for the line-feeder, the storeman then takes advantage of a 99-to-1 scale. Two resistors from the box are placed in the "1" pan of the scale, and the box is then emptied into the "99" pan until the scale balances. There should then be 99 times as many resistors in the "99" pan as there are in the "1" pan, with the result that the two pans now provide 198 plus 2 resistors for the line-feeder. Since the resistors are selected by weight, it is quite possible that the line-feeder may take with him several resistors too many or several resistors too few.

The resistors are dropped into the operator's bin from time to time as production proceeds, and no sleep is lost if one or two drop on to the floor or get lost in any other way. So long as the number of resistors entering the factory corresponds *approximately* to the number of sub-assemblies leaving it, everyone is happy. The system is perfectly economic since it is cheaper to lose a few resistors than it is to employ someone to count them individually.

Let us next assume that one of the men working at the factory has a faulty television receiver at home in

which a 27kΩ 10% ½ watt resistor has gone open-circuit. He can, of course, buy a replacement resistor at a radio shop for some 3d. to 6d. Alternatively, he can pick one out of the operator's bin and take it home for nothing. He could, even, pick the resistor up off the factory floor, whereupon he would have obtained a component which might otherwise have been swept up and thrown away. The man is, let's face it, *stealing* that resistor from the factory, but generally accepted morality would not be censorious of his action. Generally accepted morality would, instead, take the view that the factory "won't miss it"; an opinion which is, as we have just seen, perfectly true. The resistor *won't* be missed.

So we now have the case where generally accepted morality will not raise a complaint if one resistor is taken home from a factory. Let's raise the ante: our employee takes home two resistors. Is this acceptable behaviour? By taking home two resistors our employee has now entered the domain of the shop-lifter. The retail value of two resistors is approximately the same as that for a small tin of baked beans. If you are caught pinching a tin of baked beans from a Supermarket you may quite possibly find yourself charged, later to appear in court. However, we are still in the range where *misdeemeanour* is heavily qualified by degree. Generally accepted morality would not object very strongly about the two resistors. They still "wouldn't be missed." At the same time, it is fairly easy to explain away the odd tin of baked beans; and a Supermarket manager might think twice before making a court case out of a small theft of this nature. So let us raise our sights again. Our factory employee now walks out with two dozen resistors and a couple of electrolytics. Similarly, the shop-lifter tries to make off with a chicken. Ah, says generally accepted morality, wagging a finger, now that *is* naughty. Someone who tries to take as much as all that *deserves* to be caught!

Logically, there is no sense in this at all. A theft is a theft whether it be of one resistor or five thousand resistors. But generally accepted morality does not take this view, and the single-resistor man remains uncondemned.

I cannot help but feel that this outlook is almost entirely due to the present-day availability of large quantities of relatively inexpensive, mass-produced and *unaccounted* items. These items are stored, issued and used on a quantity tolerance basis,

and as long as the amount finally emerging agrees, within the tolerance, with the amount which *should* emerge, nobody complains. If a small quantity of the items disappears whilst they are being handled, the output will still be within tolerance and so, says generally accepted morality, no harm is done. This comfortable state of affairs is severely disrupted, however, when the 5,000-resistor man appears on the scene. In this instance we have a quantity discrepancy which is well outside the tolerance. It can be readily spotted, and the result is that we have a criminal.

#### Generally Accepted Morality

I have been very careful to use the phrase "generally accepted morality" up to now because I feel that the lack of condemnation of the single-resistor man—or of the single-nut and bolt man, or of the single-ball-point pen man—is a phenomenon which anyone with a pair of ears can confirm for himself by listening to normal conversation. I appreciate also that some readers will have standards which are higher than those which are generally accepted. Nevertheless, it should not be forgotten how very easy it is to become a single-resistor man. I should imagine that many of the most saintly of us have been guilty of at least one act of the "it won't be missed" variety, even if it only consists of something as innocuous as taking home a few inches of insulating tape.

It is impossible to get away from the fact that, so far as theft is concerned, what is generally accepted as crime is, in practice, a crime only because of its degree. In modern times we are surrounded by inexpensive mass-produced items which are never counted, and these appear not only in the factory (which I have referred to here only because it offers the most striking illustration) but in almost every other place of work. This environment surrounds far more of us than occurred some fifty years or so ago, whereupon far more of us are subject to the blandishment of "it won't be missed."

Whether this fact has resulted in a shift in our national attitude towards theft is something I would not like to comment on.

#### Television Society Trophy

Turning to quite a different matter, I have pleasure in including, this month, an illustration of an individual and handsome trophy which will be playing a large part in the future affairs of the Television Society. This trophy will be held

each year by the recipient of the Geoffrey Parr International Television Engineering Award. Commencing next year, the International Television Engineering Award will be presented either to an individual or to a team in recognition of an outstanding contribution to television engineering or an associated science.

As some readers will already know, Geoffrey Parr evinced a deep interest in the Television Society over many years. He joined as a Fellow in 1934 and became Hon. Lecture Secretary in 1936 and, later, Editor of the Journal of the Television Society. In 1946 he was elected Hon. Secretary, which position he retained until his retirement on 9th May, 1961. Mr. Parr died soon after this, and the Council of the Society felt that they wished to perpetuate his name by creating the Award.

The Society commissioned John McCarthy, A.R.C.A., to design the trophy. It is executed in stainless steel and depicts two sine waves at right angles to each other. It is based, therefore, on a fundamental aspect of television transmission.

#### Belling-Lee U.H.F. Field Trials

To hand are the results of the first preliminary series of tests on the new

u.h.f. television transmissions which have been carried out by Belling and Lee, Ltd. These tests covered London and the Home Counties, and it is



The Geoffrey Parr Award trophy, to be presented each year by the Television Society. Executed in stainless steel, it depicts two sine waves at right-angles to each other

pointed out that the results obtained are given by "spot tests" only. Reception conditions in some places may vary, even from house to house.

Space does not allow the many findings in the Belling-Lee report to be printed here, but I shall quote a few of the results for the North London districts to give an idea of what may be expected when full transmissions commence. Measurements were obtained using an aerial of 6dB gain 36ft above ground level,\* and decibel figures are at the receiver aerial terminals, with 0dB=1μV.

In the North London area, signal strength was 78 to 79dB and quality very good at Highgate Hill and Barnet, dropping to signal strengths between 66 and 77dB, with quality good, at Hoddesdon (High Street), Enfield, Bounds Green and Broxbourne. At Welwyn Garden City (53dB) and Mill Hill (57dB) quality was fair, and at Hertford (36dB) and Finchley (N. Circular Road) (40dB) it was very poor.

\* In some instances, 3 and 9dB aerials were tested, the measurements being rationalised to a 6dB aerial to allow comparisons to be made. Results are for Channel 34, which gave better results than Channel 44.

**FREE** THIS BOOK WILL INTEREST YOU!

LEARNING the PRACTICAL WAY

**FOR** ... Your Career  
... Your Own Business  
... An Absorbing Hobby

**RADIOSTRUCTOR** EQUIPMENT COURSES

## A NEW-PRACTICAL WAY of UNDERSTANDING

### RADIO · TELEVISION · ELECTRONICS

Including: Transistors; VHF/FM; Hi-Fi Equipment; Computers; Servo-Mechs. Test Instruments; Photo-electrics; Nucleonics; etc.

Radiostructor—an organisation specialising in electronic training systems—offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis. You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact, you really have fun whilst learning!

# RADIOSTRUCTOR

LEADS THE WORLD  
IN ELECTRONICS TRAINING

## POST NOW

To RADIOSTRUCTOR (Dept. G149), READING, BERKS.  
Please send brochure, without obligation, to:

\*Name

\*Address

(We do not employ representatives)

\*Block Caps Pressed




----- Our Latest Publication

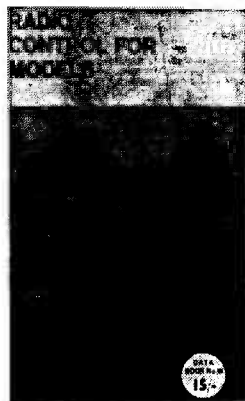
# RADIO CONTROL FOR MODELS

SHIPS, BOATS AND AIRCRAFT

BY F. C. JUDD With sections on servo-mechanisms by **RAYMOND F. STOCK**



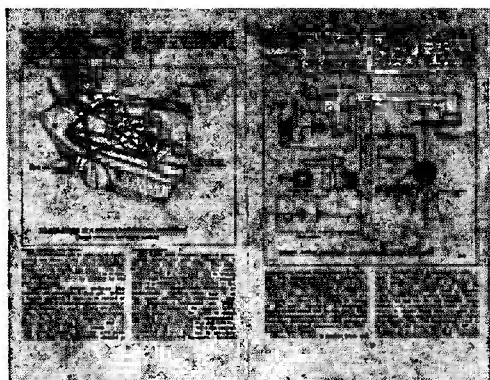*More than 200 illustrations — circuits, working diagrams, photographs & tables. Each page is packed with information*



## 192 Pages

## 15s.

This book is basically an amalgamation of "Radio Control for Model Ships, Boats and Aircraft" and "Radio Control Mechanisms". Additional material has been added on Multi-Channel Operation; Transistorised Radio Control Receivers—Simple and Three-Channel; A Compact Efficiency Aerial; Deac Battery Information; Licence Conditions, etc.



To Data Publications Ltd., 57 Maida Vale, London, W.9

Please supply.....copy (ies) of your latest publication "RADIO CONTROL FOR MODELS" DATA BOOK No. 16 at 15s. each, postage 9d.

NAME .....

ADDRESS.....

.....  
**BLOCK LETTERS PLEASE**

## SMALL ADVERTISEMENTS

*continued from page 67*

and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 21s. per annum.—Secretary, ISWL, 12 Gladwell Road, London, N.8.

**THE INTERNATIONAL HAM HOP CLUB** is a non-profit-making organisation open to RADIO AMATEURS AND SHORT WAVE LISTENERS. OBJECT: To improve international relationships through an organised system of hospitality. MEMBERS offer overnight hospitality to visiting members, subscription 10s. per annum. ASSOCIATE MEMBERS invite radio amateurs to visit their stations. Associate membership 5s. per annum. FAMILY EXCHANGE holidays arranged, also FRIENDSHIP LINKS between radio clubs. The Club's official journal is free to both Full and Associate Members.—Hon. Gen. Secretary: G. A. Partridge, G3CED, 17 Ethel Road, Broadstairs, Kent.

**CASES, CHASSIS, PANELS, CABINETS,** Tubular Frames, etc. Quotations by return. Unpainted or stove enamelled, any finish. "One off" with pleasure. Engraved Trafalite labels. Quality assured.—Moss Watson, 40 Mount Pleasant Street, Oldham, Lancs.

**FOR SALE.** Mullard Transistors, brand new. OC71, OC72, OC44, OC45, OC170, 4s. each. OC42 transistors 2s. 6d. each. Post paid.—J. Robinson, Radio & TV, 4 Highcliffe Road, Blackley, Manchester 9.

**REPANCO.** Coils, Chokes, Transformers and Ferrite Aerials for the Home Constructor. Send 3d. stamp for latest catalogue.—Radio Experimental Products Ltd., 33 Much Park Street, Coventry, Wars.

### PRIVATE

**FOR SALE.** Erskin 13A d/beam c.r.o. with r.f. probe and spare c.r.t. Perfect working order, £20. Also Taylor 67A sig. gen. 100 kc/s to 240 Mc/s. As new, £14.—"Rose Cottage", Seine Lane, Enderby, Leicester. Telephone: Narborough 2337.

**FOR SALE.** Linear L45 5 watt quality amplifier, for use with record player or microphone. Small size, 6 x 5 x 6in. 200-250V a.c. mains power supply, £5.—Box No. F175.

**WANTED.** 1 150mA square flush meter.—G3PTD, 185 Bispham Road, Blackpool.

**FOR SALE.** Nombrex transistorised signal generator 220 kc/s to 220 Mc/s, £5. Mains signal generator 100 kc/s to 200 Mc/s, £4. Assembled Heathkits: Resistance/capacitance bridge C-3U (slightly modified), £6. Sine/square wave generator AO-1U, £9. "Wavemaster 7-transistor portable M. & L. wave, 10 x 7 x 5in, £5. Philishave, 2 heads, 110 and 240 volts, with case, 90s. All in good working order and condition. Further details available. Offers considered.—Box No. F179.

*Continued on page 71*

### SPEAKERS BY GOODMAN'S, ELAC, PLESSEY, etc.

4" square 12/-	P & P 1/6
5" round 12/-	1/6
7" x 4" elliptical 13/6	1/6
8" x 5" elliptical 16/6	2/-
10" x 6" elliptical 23/6	2/-

### VISCONOL CONDENSERS T.C.C.

at half list price!

	Each
0.001 mfd 6kV CP56 QO ...	3/-
0.001 mfd 10kV CP56 VO ...	4/-
0.0025 mfd 2.5kV CP55 HO ...	3/-
0.0025 mfd 5kV CP56 QO ...	3/-
0.005 mfd 3kV CP56 HO ...	3/-
0.005 mfd 5kV CP56 QO ...	5/-
0.025 mfd 2.5kV CP56 HO ...	5/-
0.05 mfd. 5kV CP57 QO ...	9/-
0.05 mfd 10kV CP59 TO ...	10/-
0.1 mfd 5kV CP58 QO ...	10/-
0.25 mfd 2.5kV CP57 HO ...	9/-
0.5 mfd 25kV CP57 X ...	20/-

P & P 1/- each

### OUR FAMOUS READIPACKS!

No. 1 100 resistors 1/4w. to 5w. 10 ohm to 50 meg.
No. 2 25 condensers 1pF to 1,000pF 5% to 20%
No. 3 20 condensers 1,000pF to 0.01 mfd
No. 4 12 condensers 0.01 mfd. to 0.1 mfd
No. 5 25 Hi-Stub resistors 1, 2 & 5% 10Ω-25 meg.
No. 6 10 w/w Resistors 6 ohm-82 Kohm
No. 7 4 Carbon controls volume, tone, etc.

All at 8/6 each POST FREE!

### SWITCHES for MULLARD circuits to specification and "Mullard approved".


TR2 2V Pre-Amp ...	12/9
TR3 3V Pre-Amp ...	12/9
TR4 3V Pre-Amp Lo/Pass Fitr ...	10/9
TR5 3V Pre-Amp Hi-Pass Fitr ...	8/4
TR6 3V Tape Amp Rec/Play ...	16/6
TR7 3V Tape Amp Eqz ...	7/4
TR8 Tape Pre-Amp Rec/Play ...	16/6
TR9 Tape Pre-Amp Eqz ...	7/4
TR10 Stereo Pre-Amp Selector ...	18/6
TR11 Stereo Pre-Amp Ch/E ...	9/6
TR12 Stereo Pre-Amp Stereo-Mono ...	9/6

P & P 1/- per switch

## TELE-RADIO (1943) LTD

189 EDGWARE ROAD, LONDON, W2  
PADdington 4455

BEST HOLIDAY SET

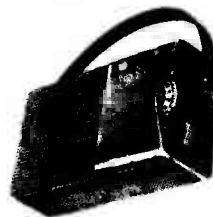

5½ x 3½ x 2

After Sales Fault-finding  
GUARANTEE

Coloured illustration

COMPONENT LISTS ON REQUEST

CONSTRUCTIONAL BOOKLETS 2/6

Trade and Retail

**OSMOR** 418 BRIGHTON ROAD  
S. CROYDON CRO 5148

**The Directors and Staff of**  
**Data Publications Ltd.**  
**and "The Radio Constructor"**  
**offer their heartiest congratulations and**  
**good wishes to the Radio Society of Great Britain**  
**on the completion of**  
**"Fifty years' service to Amateur Radio"**

### AUTHENTIC SOUND EFFECTS CONTRAST 45 r.p.m. RECORDS

*(approved by leading record reviewers and record magazines)*

- MFX-1** 14 EFFECTS—Police Car—Police Launch—Lion Roar—Aircraft Landing—Building Falling—Road Drills—Ships Siren—Storm at Sea—Railway Trains (3 various)—Car Door and Starter—Central Line Tube Train Cell Door, etc.
- MFX-2** 12 EFFECTS—American Police Car Sirens (5 various)—Applause—Car Crash—Glass Breaking—Footsteps (6 various)—City-Waterloo Tube Train—Workmen hammering—Orchestra Tuning-up.
- AFX-1** 15 WILD ANIMAL SOUNDS and jungle background—Lions, Tigers, Elephants, Puma, Rattlesnake, Alligator, Sealions, Eagles, Viper, Chimpanzees, Gibbons, Bell Bird, etc., etc.
- TFX-1** 11 BRITISH RAILWAY TRAINS—Arrival Main Line—Departure Main Line—and Express Steam and Diesel (with whistles)—Goods Trains—Train over points and Crossings—Central Line Tube Train arrive and depart, etc., etc.

**AVAILABLE SHORTLY:** Electronic sounds and music—Sounds of London and further selections of mixed sound effects.

**TWO COLOUR GLOSSY SLEEVE** gives full details of each separately tracked effect and timing.

Price 8s. including tax, postage and special packing (each record) (retail price 7s. 6d. inc. tax).

Direct mailing from

**F. C. JUDD (Sound Recording)**

174 Maybank Road, South Woodford, London, E.18

### CAR RADIO AERIALS



Special offer of British made aeriels. All heavily chromium plated. Supplied with approx. 4ft screened lead and car radio plug with fitting instructions.

- |               |   |             |
|---------------|---|-------------|
| <b>Type 1</b> | Window clip-on. Suitable for transistor radios. Closed 13", extended 33" each   | <b>17/6</b> |
| <b>Type 2</b> | As Type 1 but for mounting on car gutter. each  | <b>17/6</b> |
| <b>Type 3</b> | Single hole fixing for wing mounting. Closed 22½", extended 44" each  | <b>15/6</b> |
| <b>Type 4</b> | As Type 3 but 3-section. Closed 18", extended 47" each  | <b>21/9</b> |
| <b>Type 5</b> | Universal for mounting on roof, side, rear, top of wing. Spring loaded joint enables aeriels to be inclined at any angle. Closed 20", extended 37" each | <b>25/9</b> |

Post and Packing 1/6 per aerial (No C.O.D.)

### ELECTRIC MOTORS AT A FRACTION OF ORIGINAL COST

Made for use with cine projectors, but ideal for small models, fans, small lathes, display set-ups, rewinding, etc. Very robust, heavy duty construction. 1/40th h.p. 200/240V a.c. Capacitor start, for clockwise and anti-clockwise rotation. Approx. dimensions: dia. 3½", width over body 3", spindle length 1½" (protrudes ¾" at back of motor), spindle dia. ¼", 1,450 r.p.m., weight 3½lb. Complete with capacitor.

Plus 3/- post and packing each **31/6**

## BERWICK ELECTRONICS LTD

**70 BERWICK STREET** (Off Oxford Street)  
**LONDON W1** GERRARD 8152  
**and at 100 TIB STREET MANCHESTER**



## SMALL ADVERTISEMENTS

*continued from page 69*

**TWO-METRE** enthusiasts attention! QQVO3-20A valves at £1 each, plus postage.—Box No. F178.

**FOR SALE**, Televet. Little used. Half initial price.—Jones, Tudno View, Benllech, Anglesey.

**AMATEUR GIVING UP** hobby has following items for sale. Avo valve tester, £6 15s. Multi-range test meter scaled ohms, volts and milliamps, 17s. 6d. Cossor 339 oscilloscope, £9 15s. Two new 12in hi-fi speakers, each fitted with electrostatic tweeter, 50s. each. Reflectograph model 500 professional tape recorder, £50. All items carriage free. Insurance if required, 10s. extra. C.O.D. 2s. 6d. extra.—Box No. F180.

**FOR SALE**. AR88 540 kc/s to 32 Mc/s, phones and speaker, far above average, £35. Heathkit QU12 c.r.o. sig. gen. and other bench test equipment. 8 vols. *Radio and TV Servicing*. Up to 62 components, TV tubes, 3 years copies *Practical Wireless*, *Practical Television*, *Wireless World*, *The Radio Constructor*. A complete workshop for £50.—2 Whitmore Street, Palfrey, Walsall, Staffs.

**WANTED**. Will purchase knobs and dials for Halli-crafter SX28A also knobs and front panel and case for BC348. Or would swap Hallicrafter S20R.—Bilton, 26 Beulah Hill, London, S.E.19.

**FOR SALE**. R1155L new valves, £6. Good condition. Also power pack, £3.—W. Iley, Riverside Cottage, Bolingey, Perranporth.

**WANTED**. Wearite or similar tape head defluxer.—Collins, 18 St. John's Church Road, Folkestone, Kent.

### SITUATION VACANT

**PUBLIC SCHOOL MAN** under 25 required as trainee for electronic and/or mechanical engineering design and development work on machines to make fibreglass products. Starting salary £936. Write, giving details of experience, education and interests to Fibrelite Industries, Trafford Hall, Chester.

## PANL BLACK CRACKLE PAINT

Give your metalwork a really professional finish.  
Easily applied by brush. Air drying.

Available by post from

**THE BRUCE MILLER CO. LTD**  
249 COASTAL CHAMBERS  
BUCKINGHAM PALACE ROAD SW1

4/- per  $\frac{1}{2}$  pint can which includes application instructions, postage and packing

## SITUATION VACANT

### LABORATORY ASSISTANTS

preferably with academic qualifications equivalent to O.N.C. (Elec.Eng.) are invited to apply to—

### International Aeradio Limited

Good promotion prospects.  
Superannuation.  
Cheap holiday air travel.  
Holiday arrangements respected.

Write to:

**The Personnel Officer,**  
**International Aeradio Limited,**  
**Hayes Road, SOUTHALL,**  
**Middlesex.**

## REPANCO COMPONENTS FOR THE HIKER

(as featured in this issue)

	s.	d.
Aerial Type FR2	12	6
Chokes Type RF1 and RF2	6	0
Interstage Transformer Type TT49	5	0
Driver Transformer Type TT45	5	0
Output Transformer Type TT46	5	0
Printed Circuit, Panel and Brackets	12	6

Send 3d. stamp for latest Repanco Component Cat. and Hiker Parts list.

**RADIO EXPERIMENTAL PRODUCTS LTD.**  
33 Much Park St.  
Coventry

## E. R. NICHOLLS 46 LOWFIELD ROAD SHAW HEATH STOCKPORT BUMPER PARCEL

100 Assorted Resistors	1 Small Chassis containing
50 Assorted Condensers	60 components
1 5in 3 ohm Elac Speaker	2 Westectors
1 Isolating Transformer	2 Thermistors
4 Terminal Blocks.	100 Cartridge Fuses
2 Rotary Toggle Switches	

ALL FOR 20/-, Post free in U.K.

20ft Steel Telescopic Mast, 50/- High Stab Resistors 6d. ea.  
List now ready for Paper Block Condensers, Valves, Oscillators, Test Sets. S.A.E. please.

Mail Order to  
33/35 CARRINGTON FIELD STREET STOCKPORT CHESHIRE

# CHASSIS and CASES by



287/9 Edgware Road  
London W2  
TELEPHONE  
PADDINGTON 5891/7595

**BLANK CHASSIS—Same Day Service**  
Of over 20 different forms made up to YOUR SIZE.  
Order EXACT SIZE you require to nearest 1/16th.  
(Maximum length 35", depth 4".)  
Specials dealt with promptly.

**SEND FOR ILLUSTRATED LEAFLETS**

or order straight away, working out total area of material required and referring to table below which is for four-sided chassis in 18 s.w.g. (for 16 s.w.g. add 1/6th).  
48 sq. in. 4/- 176 sq. in. 8/- 304 sq. in. 12/-  
80 sq. in. 5/- 208 sq. in. 9/- 336 sq. in. 13/-  
112 sq. in. 6/- 240 sq. in. 10/- 368 sq. in. 14/-  
144 sq. in. 7/- 272 sq. in. 11/- and pro rata  
P. & P. 2/6 P. & P. 2/9 P. & P. 3/-


Discounts for quantities. Finishes arranged for quantities of 25 or over.

**FLANGES** (1/2" or 3/4", 6d. per bend.  
**STRENGTHENED CORNERS**, 1/- each corner.  
**PANELS**

Any size up to 3ft at 4/6 sq. ft. 18 s.w.g. (16 s.w.g. 5/3).  
Plus postage and packing.

**CASES**

ALUMINIUM, SILVER HAMMERED FINISH		Type W	
Type	Size	Type	Size
U	4 x 4 x 4"	Y	8 x 6 x 6"
U	5 1/2 x 4 1/2 x 4 1/2"	Y	12 x 7 x 7"
U	8 x 6 x 6"	Y	13 x 7 x 9"
U	15 x 9 x 9"	Y	15 x 9 x 9"
W	8 x 6 x 6"	Z	17 x 10 x 9"
W	12 x 7 x 7"	Z	19 x 10 x 8 1/2"
W	15 x 9 x 8"		* Height

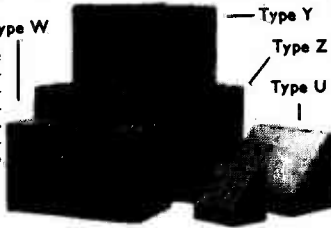

Type Z has removable back and front panels.  
Type U all-screwed construction.

The thrills of VHF Amateur Radio can now be yours for as low as 39/6!—complete kit (by post 2/6 extra)—tuneable range, 70–150 Mc/s. Write today for interesting literature, s.a.e. please. If a newcomer to Short-Wave radio, ask for a free copy of world-famous "Globe-King" S.W. kits and other receivers, etc.—stamp for post please, not s.a.e.

**Johnsons (Radio) St. Martin's Gate Worcester**

**BRASS · COPPER · DURAL · ALUMINIUM · BRONZE  
STAINLESS STEEL**

ROD, BAR, SHEET, TUBE, STRIP, WIRE. 3,000 STANDARD STOCK SIZES.  
No Quantity too small List on application

**H. ROLLET & CO LTD**  
6 CHESHAM PLACE SW1 BELGRAVIA 4300  
Also at Liverpool, Birmingham, Manchester, Leeds, Glasgow

**SUMMER BARGAINS**

50% to 75% price reductions on standard catalogue lines. Unrepeatable. Send for details stating if you have our illustrated catalogue No. 12.

**Southern Radio and Electrical Supplies**  
SORAD WORKS REDLYNCH SALISBURY WILTS  
Telephone Downton 207

**Quality Components FOR CONSTRUCTORS**

capacitors, resistors, coils, valves, transistors, controls, chassis, transformers, speakers, pick-ups, cartridges, stylus, and all types of components in stock.

CATALOGUE AVAILABLE ON REQUEST  
**J. T. FILMER** 82 DARTFORD ROAD  
DARTFORD KENT  
Telephone Dartford 24057



**LISTEN TO THE WORLD on TELSTAR**  
our 1-VALVE SHORT WAVE RADIO  
Receives speech and music from all over the world. Price includes valve and one coil covering 40–100 metres. Can be extended to cover 10–100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. Total Building Costs 35/-, P. & P. 2/- Send 2/- for wiring diagram and parts list.

R.C.S. PRODUCTS (Radio) Ltd., 11 Oliver Road, London, E.17

**140FT. AERIAL INSTALLATION**

First Government release of these brand new Marconi Coil Aerial tuning systems, enabling operators to work their receivers or transmitters to their best efficiency. Containing a drum of 140ft copper aerial wire with insulators, etc., feeding into the matching unit, size 13" x 8 1/2" x 9 1/2", with slow motion tuning using Nos. 0–999. Originally intended for the 52 TX-RX, a must for any poor reception areas and serious operators. 300 only. 35/-, post 5/-; two post paid.

Dept. Q J.T. SUPPLY 150 Meadow Lane Leeds 11

**THE RADIO CONSTRUCTOR — BOUND VOLUMES AVAILABLE**

Volume 13, August 1959 to July 1960 £1.5.0 postage 2/3

Volume 14, August 1960 to July 1961 £1.5.0 postage 2/3

WE REGRET VOLUME 15 IS NOW SOLD OUT

**DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9**


# German radio exhibition 1963 Berlin

from August 30 to September 8  
in the Funkturm exhibition halls



Information from: German Tourist Information Bureau, 61, Conduit Street, London W1

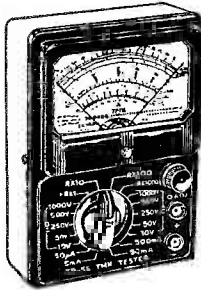★ TRANSISTORS ★ ZENERS ★ VALVES ★ QUARTZ CRYSTALS ★ THESE ARE OUR ★  
DIODES RECTIFIERS TUBES COMPONENTS SPECIALITIES  
EQUIPMENT, COMPONENTS AND INFORMATION IN OUR LATEST 68-page CATALOGUE. 2/- Post Free




**MODEL TP55**  
A.C./D.C. voltage up to 1,000 in 5 ranges.  
D.C. current 4 ranges up to 500mA. 4 range resistance to 10 meg. Capacity dB scales, etc.

20,000 ohms/volt  
Fully Guaranteed  
**£5.19.6**

With Test Leads, Battery and Instruction. Size 5½" x 3½" x 1½"

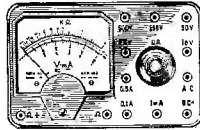**DETAILS ON REQUEST**

- ★ **MODEL EP50K** 50,000 ohms per volt £9.19.6
- ★ **MODEL EP30K** 30,000 ohms per volt £6.19.6
- ★ **MODEL ITI-2** 20,000 ohms per volt. 5 gns.
- ★ **EPI0K** 10,000 ohms per volt. 65/-
- ★ **CABY MI** 2,000 ohms per volt. 54/-



**45/-** 1,000 ohms per volt  
**Model PT34**


0/10/50/250/500/1,000 volts A.C./D.C. 0/1/100/500 mA D.C. Resistance 0/100kΩ.

Ideal pocket size multimeter for all radio and domestic work.

Size 3½" x 2½" x 1½" with battery, leads and instructions.

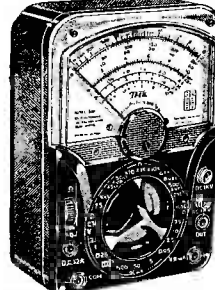**4-WAVEBAND COMMUNICATIONS RECEIVER**

550 kc/s to 30 Mc/s—BFO Noise Lim.—A.V.C.—"S" Meter—Bandspread, etc. £25. P.P. 7/6. Brand New. Fully Guaranteed.



**30,000 ohms per volt. Model 500 £8.19.6**

8 Ranges D.C. volts to 1kV. 7 Ranges A.C. volts to 1kV. 5 Ranges D.C. current to 12 amps.

3 Range resistance to 60 meg. Short circuit buzz test. Output meter dB, etc., etc. Size 6½" x 4½" x 2½". With Leads, Batteries and Instructions.



**75/-**

**2,000 ohms per volt Model THL33**

0/10/50/250/500/1,000 volts D.C.

0/10/50/250/500/1,000 volts A.C.

0/500μA/10/250mA D.C. Resistance 0/10k/100k/1 Meg Capacity and dB ranges, etc. Size 5½" x 4½" x 1½" with Batteries, Test Leads and Instructions.

**A SELECTION FROM OUR STOCKS**

Full Details in our Latest Illustrated Catalogue, 2/- Post Free

1. 2,000 ohm Headphones ... 12/6
- 4,000 ohm Headphones ... 14/-
- Stereo Phones 2 x 8 ohm ... 27/6
2. Make your own printed circuits. Full details with 3 boards 6" x 3", etc. 19/6
3. Crystal Microphones (P.P. 1/6 any type)
- Acos 39-1 Stick Microphone ... 32/6
- Acos 40 Desk Microphone ... 15/-
- Acos 45 Hand Microphone ... 25/-
- Lapel/Hand Microphone ... 12/6
- MC24 Stick Microphone ... 25/-
- 100C Stick with Stand ... 39/6
- BM3 Stick with Stand ... 52/6
- Lapel/Hand Magnetic ... 12/6
4. Transistor Megaphone £12.10.0.
5. 250mW 4-Transistor Amplifier, built ready to use ... 37/6 P.P. 1/6
6. Complete Test Lead Kits ... 8/6
7. Miniature Vernier Dial 8:1, reduction marked 0/100 for ½" spindles, 1½" diam., 12/6; 2" diam., 14/-; 3" diam., 16/-.
8. 931A Photomultiplier. Brand new with base ... 60/-

**DEAC RECHARGEABLE BATTERIES**

- (a) 18 volt 100mA/H 4" x 1" diameter. Brand new, sleeved, 30/-.
  - (b) As above but 150mA/H, 35/-.
- Both types easily split into any multiple of 1.2 volt. Brand new.

9. CV2886 (M2H) Liquid Sampling Geiger Tube, 370 volts, 22/6. P.P. 1/-.
10. Antex Miniature Mains Soldering Iron, ⅜" bit, 29/6, P.P. 1/-.
- Pocket Iron with Pouch, 30 watt, 220/250 volt, 18/6.
- Solon 15 watt, ⅜" bit, 22/6, P.P. 1/-.
11. Pocket Radio Booster Unit, for any radio. Improves output and quality. Size 9½" x 3½" diam., 27/6, P.P. 1/-.
- Size 8" x 2½" diam., 25/-, P.P. 1/-.
- Ideal for using pocket radios in car.
12. 125mW 9 volt Sub-min. 3-Transistor Amplifier, 2" x 1" x 1", 29/6.
13. Telephone Coil for any amplifier or Recorder, 12/6, or fitted Miniature Jack Plug, 14/-.
14. Crystal Contact Microphone for guitars, etc., 12/6.

15. Personal Earphones: 600 ohm, 10/6; 1,000 ohm, 12/6. Crystal, 8/6; 8/10 ohm, 9/6. Fitted leads, jack plugs and sockets.
16. Battery Record Players. Single speed 45 r.p.m. 6-7½ volt player, 49/6. Two Speed, 33 and 45 r.p.m. 9 volt player, 92/6. Four-speed 9 volt player, 5 gns.
17. Transistor Baby Alarm, as previously advertised. £5.10.0, P.P. 2/-.
- Also Telephone Amplifier, £5.10.0, P.P. 2/-.
18. 4-Transistor 2-way Intercom, £7.10.0. 2-Transistor 2-way Intercom, 89/6.
19. SRP10 Mains 4-speed Garrard single player, £5.7.6.
20. Miniature 3-Press Button Switches, 6-pole, 2-way and on/off, 5/-, P.P. 9d.
21. Transistor Signal Injector, 42/6. For circuit testing and checking.
22. 8" 15 ohm double cone Hi-Fi Speaker, 79/6. Complete range of Hi-Fi speakers stocked. Leaflets on request.
23. 12-way Selector Tube, GS12C (CV 1740), 25/- each.
24. Quartz Fibre Pocket Dosimeters 0/150R and 0/500R, 12/6 each.
25. 6-Transistor speaker superhet Pocket Radio ready to use. Complete with leather case, phone, etc., 79/6, P.P. 2/-.
- Fully guaranteed. De Luxe version, 94/6, P.P. 2/-.
26. 8 watt de luxe Stereo Amplifier. Mono/stereo inputs full controls. Gold hammer finish, £9.10.0, P.P. 3/6. Leaflet on request. Also 15 watt and 30 watt.
27. Sub-miniature Jack Plug and Socket, 2/6. Sub-miniature Screened Plug, 2/-.
28. Standard Jack Plug, 2/6. Standard Screened Jack Plug, 3/6.
29. 12" 15 ohm Hi-flux Quality Speakers, only 35/-, P.P. 2/-.
30. Tuning Indicator and Battery Level Meter. Miniature Meter (400μA) for Recorders, Transmitters, etc., 24/6.
31. Crystal Microphone Inserts: 2", 10/6; 1½", 7/6; ¾", 3/6; Acos 39-1, 15/-.
32. Stereo Amplifier, 2 watts each channel. Brand new, 79/6, P.P. 2/-.
33. Transistor All Wave Signal Generator. 165 kc/s to 350 Mc/s in 7 Bands. Variable output. CW, RF, mod RF, £7.18.6, P.P. 2/6, with battery, test prod, etc. Leaflet on request. New improved model.
34. Type 38 Transmitter/Receiver. 5-valve, 7.4-9 Mc/s, 22/6, P.P. 2/6 (sold without guarantee).
35. Valve Voltmeter, AC/DC/Resistance, etc., £9.19.6, P.P. 5/-.
36. STC F15 Thermistors, 6/-; R53, 15/-.
37. ORP12 L DR Cell, 12/6; ORP60 Cell, 9/6; OCP71 Photo trans., 27/6.
38. Half Track Record/Playback Tape Heads. 2kΩ impedance, 15/-.
39. NEW TRANSISTORISED CAPACITANCE/RESISTANCE BRIDGE. 6 ranges. 1 ohm to 100 Meg. 1pF to 100 mfd., £7.2.3, P.P. 2/6. Leaflet on request.
40. 6" x 7" Printed Circuit Panels for etching, 4/- post free.
41. Recording Tape: 5" 600ft, 12/6; 5" 900ft, 15/-; 7" 1,200ft, 18/6; 7" 1,800ft, 25/-.
- Excellent quality.
42. DC to AC Converter. Converts 12 volts DC, i.e. car battery, to 230 volts AC up to 15 watts. Ideal for using electric razor, etc., in a car. All-Transistor complete kit, 57/6, P.P. 1/6.
43. Collaro Mains Twin Track Tape Decks. Brand new, 10 gns, P.P. 3/6.
44. Garrard Autoslim 4-speed auto-changers. Plug-in head type complete with head, £7.10.0. P.P. 3/6.

**SUBSTITUTION BOXES**

- ★ Capacitor Box. Provides 9 standard values from 0.001μF to 0.22μF at 600 volt working, 29/6.
- ★ Resistor Box. Provides 24 standard values at 1 watt. 15 ohms to 10 meg., 37/6.

Each box fully calibrated with insulated leads. Invaluable for service and design.

**FIELD STRENGTH METER**

Measures transmitter carrier waves from 1 Mc/s to 200 Mc/s in 5 switched fully adjustable ranges. Contains 200μA meter for carrier level and earphone for modulation. Requires no connection to transmitter. Self-contained, ready for use, 69/6, post free.

**HENRY'S RADIO LTD**

PADddington 1008/9

303 EDGWARE RD., LONDON W2

Open Monday to Sat. 9-6, Thurs. 1 o'clock

**PLEASE TURN TO BACK PAGE**


Published in Great Britain by the Proprietors and Publishers Data Publications Ltd. 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd. Oxford Road Clacton-on-Sea England

Obtainable abroad through the following Collects Subscription Service Continental Publishers & Distributors Ltd. William Dawson & Sons Ltd. Australia and New Zealand Gordon & Gotch Ltd. Electronics Publications (Australia) South Africa Central News Agency Holland "Radio electronica"

**SPECIAL REDUCTION  
NEW LOW TOTAL PRICE**

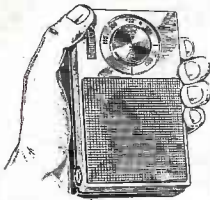**"CAPRI" POCKET-6  
6-TRANSISTOR SUPERHET**



Size only  
4 1/2" x 2 3/4" x 1 1/4"

**REALLY  
POCKET  
SIZE!**

The most compact 6-transistor and diode radio with speaker available to the home constructor. Features the latest in miniature components and circuitry. Supplied with Mullard transistors and two-tone moulded cabinets in red/white or blue/white with gold fittings. All components are supplied in packets and clearly identified. A printed circuit is used with fully illustrated building instructions. Push-pull output coupled with a sensitive and selective circuit make the "CAPRI" hard to beat. Fitted Earphone/Record Socket. Full tuning on medium waves with long wave Light. Illustrated leaflet on request.

TOTAL COST **79/6** P.P. 2/-  
(Battery 2/6)  
★ Slip it into your Pocket ★

**HENRY'S RADIO LTD**

303 EDGWARE ROAD LONDON W2  
PADdington 1008/9

Open Monday to Sat. 9-6. Thurs. 1 o'clock

**LATEST SUMMER CATALOGUE  
NOW 68 PAGES 10" x 7 1/2"**  
Fully detailed and illustrated 2/- post free  
**THIRD EDITION IN 9 MONTHS**

**THE "CONTESSA"**

★ **COMBINED PORTABLE AND CAR RADIO** ★

AMAZING SENSITIVITY AND SELECTIVITY ON MEDIUM AND LONG WAVEBANDS


★ The easiest Superhet Radio to build on the market. Features clearly marked printed circuit and packaged components with full illustrated building instructions. Full tuning of medium and long wave bands with unbeatable sensitivity and selectivity. Excellent tone and volume with over 600mV push-pull output.

★ Clearly marked horizontal station dial with slow motion tuning. Two-colour blue or beige cabinets with gold handles, grilles and fittings. Size 10 1/2" x 7 1/2" x 3 1/2". Include car aerial socket, recording sockets.

★ 6 Mullard Transistors and 2 Diodes.  
**Guaranteed the Best Obtainable**


★ **Attractive Appearance—Reliable Design—Quality Performance** ★  
**UNBEATABLE FOR QUALITY AND VALUE**

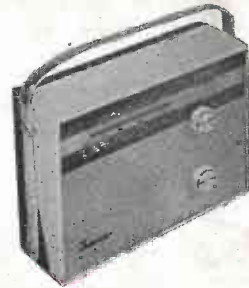Fully Detailed and Illustrated Leaflet on request



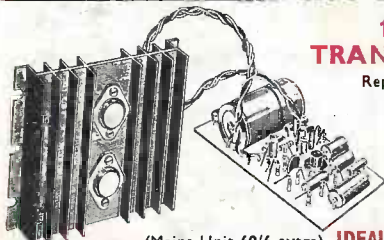**TOTAL COST**

**£9.19.6** P.P. 3/6  
**NO EXTRAS TO BUY**



**10 WATT HI-FI  
TRANSISTOR AMPLIFIER**

Replace that Valve Amplifier with this High Fidelity Amplifier

- 40 C/S TO 20 KC/S ±1dB
- LESS THAN 0.3% DISTORTION
- 100mV INPUT FOR 10 WATTS OUTPUT
- MAINS OR BATTERY ANY VOLTAGE 4 1/2 to 24

(Mains Unit 69/6 extra) **IDEAL FOR ALL MONO AND STEREO**


Supplied complete with booklet showing HI-FI EQUIPMENT including preamplifiers, mixers, stereo, public address, etc. Can be used with any commercially available valve or transistor preamps, tuners, etc.

Booklet available separately 1/6 post free

PERFORMANCE EQUIVALENT TO VALVE AMPLIFIERS OF FOUR TIMES THE PRICE AND MANY TIMES THE SIZE

Built ready to use  
**£5.19.6**  
P.P. 2/-

Call for demonstration—any time.

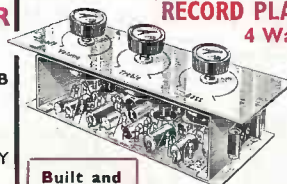

**7-TRANSISTOR  
RECORD PLAYER/RADIOGRAM  
4 Watt (Peak) Amplifier**

- Full Treble and Bass boost and cut
- 40 c/s to 20 kc/s ±3dB
- Inputs for Pick-ups, Radio Tuners, Microphones, mixers, etc.

- 15 ohm Speaker (8" x 5" 22/6 extra)
- 12 to 18 volts mains or battery
- Size only 6" x 2 1/2" x 2"

Ideal for mains or battery, portable or domestic record players, grams, etc.

Ideal for car use.  
Mains Unit 80/- extra Call for demonstration  
● **BOOKLET FREE ON REQUEST** ●

Built and Ready to Use  
**£5.19.6**

P.P. 2/-  
(Complete with full descriptive Booklet)

**HI-FI TRANSISTOR PRE-AMP.**

★ Full Function Preamplifier for 9 to 40 volts operation. Designed for above but suitable for any amplifier. 5 controls. Printed circuit 9" x 2 1/2".

Built 99/6, P.P. 2/-.

**BATTERY ELIMINATORS AND CHARGERS**


Run your radio or amplifier from mains

1. For PP3 or equivalent 9 volt Pocket Radio Battery 18/6. P.P. 1/-
2. For PP4, PP7, PP9, PP10, 9 volt Portable Radio and Equipment Supplies up to 300mA 49/6, P.P. 2/-
3. De Luxe version of No. 1, also charges PP3 type batteries. 24/6, P.P. 1/-
4. Rechargeable PP3 battery. Runs as long as 100 batteries. Completed with charger unit 25/-, P.P. 1/-

**HI-FI EQUIPMENT**

New range of modern mono and stereo hi-fi amplifiers with pre-amps in stock. Also speakers, record decks, etc. 8 watt, 15 watt, 30 watt tuners, etc., etc. Leaflets on request. See new catalogue.

**3 1/4 Watt 4 Transistor  
Amplifier**

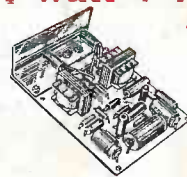

- Improved Version
- 1 1/2 watt peak output.
- ±3dB 70 c/s to 12 kc/s.
- Output to 3 ohm speaker
- 9 volt operated

Built and Tested **59/6 OR 52/6**  
P.P. 1/6 Kit of Parts P.P. 1/6

**"MINIRANGER"**

3-Transistor plus 2 Diodes. Smallest radio to build yourself. Printed circuit, full tuning. **ONLY 3" x 2" x 3/4"**. Over 20 stations.

TOTAL COST **49/6** P.P. 1/6


**METER BARGAINS**

- 50 Microamp 2" square MC ... 36/-
- 1mA 2" square MC ... 25/-
- 1mA 2 1/2" Flush round ... 30/-
- 2 1/2" Moving Coil double range Voltmeter centre zero. 30-0-30 and 3-0-3 volts. Ideal for transistor tester or voltage measurements, 12/6, post free.
- 0/500 microamp, 2 1/2" flush mounting DC ... 20/-
- 0/500µA 2" FR ... 15/-
- 2 1/2-0-2 1/2mA, 2 1/2" flush DC ... 12/6
- 0/15 volt M.1. 2 1/2" FR ... 8/6

**Miniature Panel Meters**  
\*0/50µA (DC) 39/6 \*0/5mA (DC) 27/6  
\*0/500µA (DC) 32/6 \*0/300V (DC) 27/6  
\*0/1mA (DC) 27/6 Vu Meter 42/6  
\*S\* Meter 35/- All Brand New Boxed.  
\*Available Clear Plastic Front or Black Moulded. State which.

**"QUINTET"  
POCKET  
RADIO**

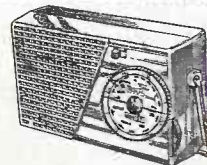Size 5 1/2" x 3" x 1 1/2"  
5-Transistor, plus Diode MW/LW to build.



**79/6** P.P. 2/-

**BOTH MODELS AS PREVIOUSLY ADVERTISED**  
★ ALL PARTS SOLD SEPARATELY. BOOKLETS FREE ON REQUEST ★