


RADIO CONSTRUCTOR

& ELECTRONICS

Vol. 26 No. 2

SEPTEMBER 1972

20p

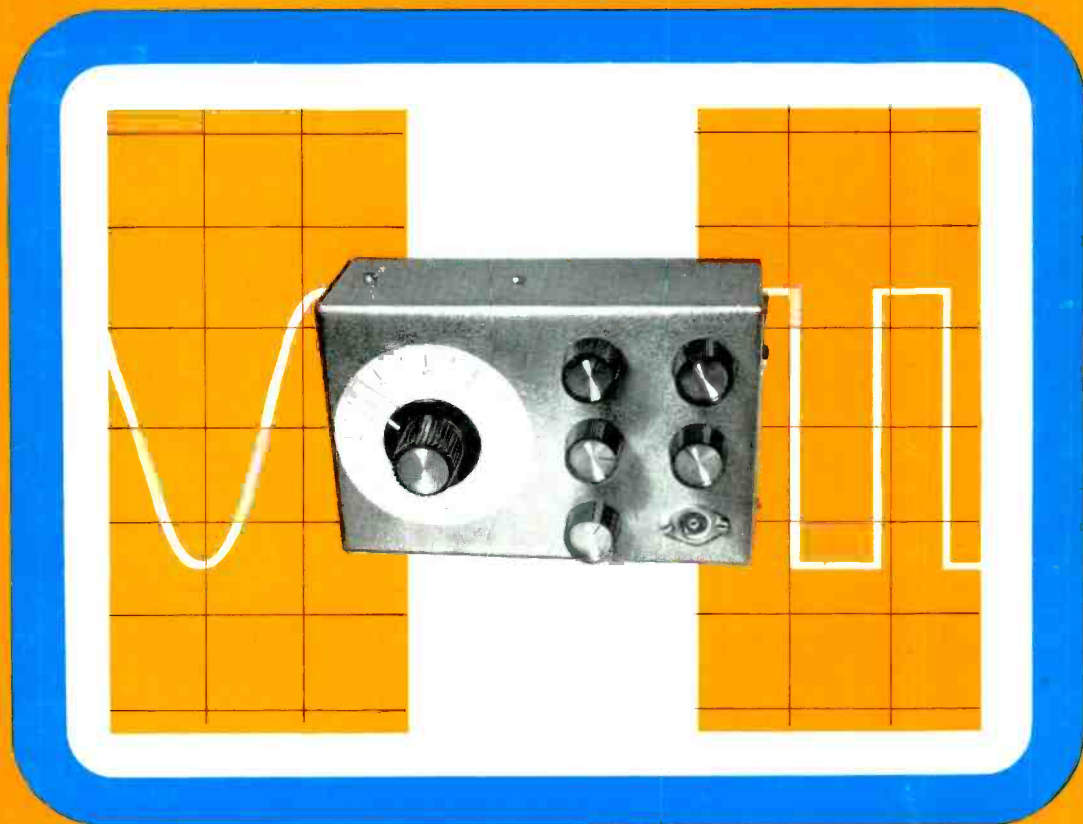


A.F. SIGNAL GENERATOR

This generator offers both sine and square wave outputs and it covers 15Hz to 150kHz in four ranges

Special
IN THIS ISSUE

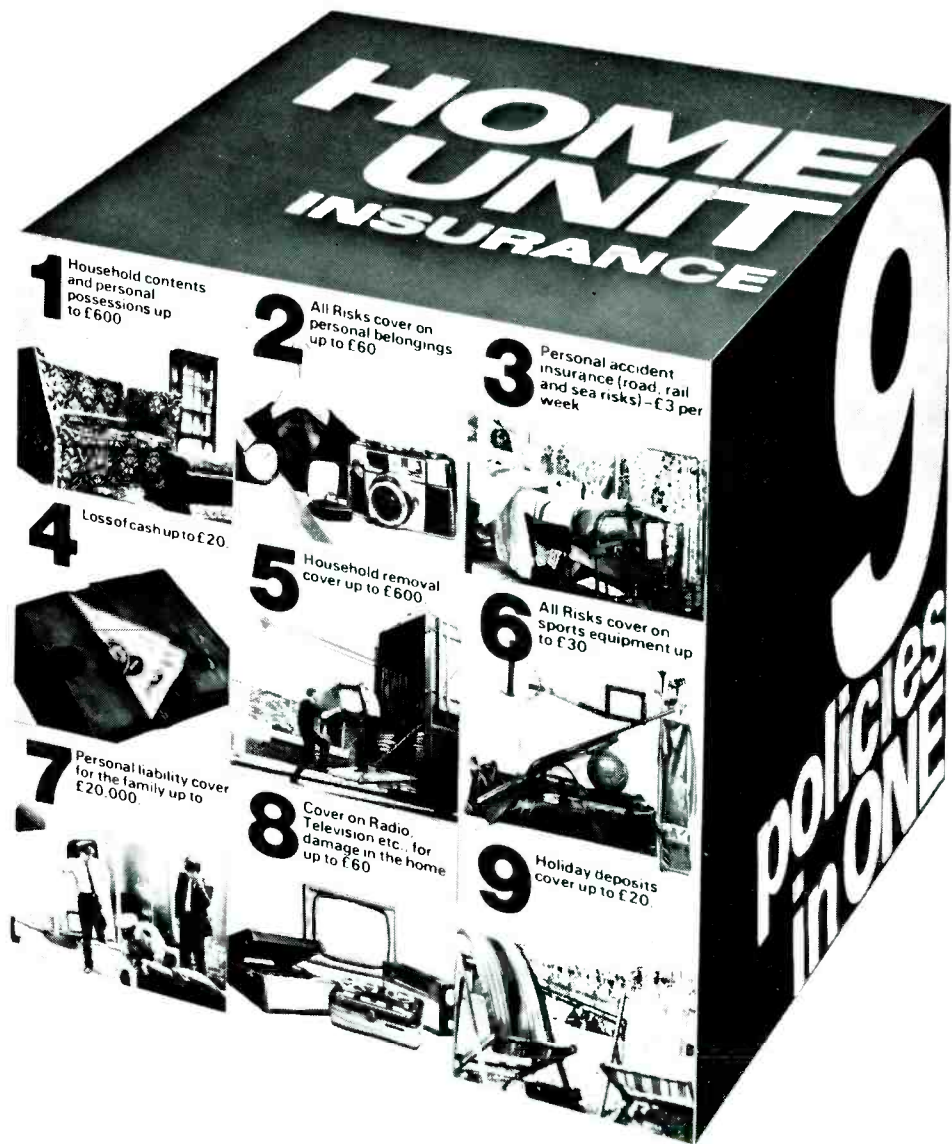
ELECTRONIC METRONOME
SHORT WAVE CRYSTAL SETS



1 Household contents and personal possessions up to £600



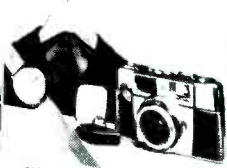
2 All Risks cover on personal belongings up to £60



3 Personal accident insurance (road, rail and sea risks) - £3 per week



4 Loss of cash up to £20

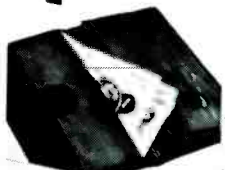

5 Household removal cover up to £600




6 All Risks cover on sports equipment up to £30



7 Personal liability cover for the family up to £20,000



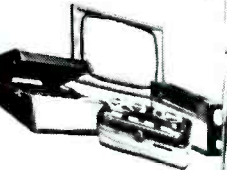8 Cover on Radio, Television etc., for damage in the home up to £60



9 Holiday deposits cover up to £20



Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units (or 1/3 units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances And remember - as you buy more possessions just add more Home Units at any time.

THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue,
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

.....

.....

COMPONENTS

HOBBYIST - AMATEUR - DOMESTIC SURPLUS
INDUSTRIAL - BULK OFFERS

JUST A FEW OF OUR BARGAINS ARE LISTED BELOW - PAY US A VISIT
OR SEND STAMPED ADDRESSED ENVELOPE FOR A QUOTE ON YOUR REQUIREMENTS

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AF116	15p	2N3055	45p	T.O.3 Mica washers	2p
AC188	25p	2N2401	15p	UNMARKED TESTED	
AD161	30p	Centercel Diodes	5p		
AD162	30p	6-110 volt, 0.6 amp. nominal bridge rect.	BY127	8p	
Matched pair	50p	encapsulated with built in Heat Sink	BC107-8-9	5p	
BFY52	16p		2N2926	5p	
ORP12	43p				

1 1/2 glass fuses— 250 m/a or 3 amp (box of 12)	6p
3" tape spools	4p
FX2236 FerroX Cubes	5p
PVC or metal clip on M.E.S. bulb holder	3p
All metal equipment Phono plug	2p
Bulgin, 5mm Jack plug and switched socket (pair)	20p
12 volt solenoid and plunger	25p
250 RPM 50 c/s locked frequency miniature mains motor	50p
200 OHM coil, 1 1/4" long, hollow centre	10p
Relay, P.O. 3000 type, 1,000 OHM coil, 4 pole c/o	60p

SWITCHES

Pole	Way	Type	
4	2	Sub. Min. Slide	10p
6	4	} Wafer Rotary	12p each
1	11		
4	3		
3	7		
2	5		
1	3		
1	3	+ off Sub. min. edge	10p
1	3	13 amp small rotary	12p
2	2	Locking with 2 to 3 keys	£1.50

RESISTORS

1/8 - 1/2 watt	1p
1 watt	1 1/2p
Up to 10 watt wire	8p
15 watt wire wound	10p

SKELETON PRESETS

5K or 500K	3p
------------	----

SAFETY PINS

Standard size, 10 for 4p

VALVES - NEW AND BOXED

DY86	44p	EM87	90p	PL84	46p
EB91	26p	EL84	36p	PY81	40p
ECC82	36p	EY86	46p	PY82	42p
ECC83	36p	EZ80	30p	PY88	52p
ECH81	44p	PCC84	50p	UABC80	58p
EABC80	46p	PCC89	62p	UCL82	50p
EBF89	44p	PCF80	38p	UL84	50p
ECL82	44p	PCF82	50p	UY85	42p
ECL86	56p	PCL82	38p	UM84	32p
EF80	36p	PCL84	50p	UCH81	44p
EF85	44p	PCL85	64p	6BA6	26p
EF86	44p	PCL86	56p		
EF91	52p	PL36	78p	MANY OTHERS	
EF183	40p	PL81	72p		
EF184	44p	PL83	56p		

RESETTABLE COUNTER

6-14 volt, 6 digit, illuminated, fully enclosed. £2.50

DIE CAST ALLY BOX

4 5/8 x 3 5/8 x 2 1/8 with lid 50p

5K switched volume control	15p
5K Log Pot	10p
1meg Tandem Pot	15p

BSR TD2 TAPE TRANSPORTER

With 4 track heads £2.50

STEEL BOX WITH LID

10 x 5 1/2 x 3" grey hammer finish £1

RELAY

6 volt, 2 pole c/o heavy duty contacts 50p

ELECTROLYTICS

Mullard C426, TCC, CRL, CCL, HUNTS, STC SUB MINIATURE, ETC.

MFD	Volt	MFD	Volt	
16	50	20	12	} 4p each
260	12	100	6	
50	50	100	25	
100	18	100	6	} 2p each
125	10	6	3	
8	50	8	6	} 3p each
12	20	25	6.4	
10	20	250	18	} 7p each
8.2	20	500	6	
50	25	400	16	} 6p each
2.5	64	8	500	
25	25	100	200	10p

CONDENSERS

MFD	Volt	
0.005	500	} 2p each
0.001	1,250	
3.3PF	500	
500 PF	500	} 2p each
2,200PF	500	
3,300PF	500	} 3p each
0.1	350	
0.1	500	} 5% each
0.25	150	
0.056		} 350V
0.061		
0.066		} 4p each
0.069		
0.075		} 5p each
0.08		
0.1	1,500	} 4p each
0.25	350	
0.5	350	} 5p each
0.22	250	
Mullard Polyester		

TUNING GANG

100PF, 50PF, 33PF 20p each

TRIMMERS

30 PF Beehive }
12PF P.T.F.E. } 10p each
2,500PF 750V }

WIREWOUND SLIDER

150 OHM, 250 OHM 5K 4p each

INDICATORS

12 volt red or mains neon amber, push fit round, chrome bezel 15p each

Rotor with neon indicator, as used in Seafarer, Pacific, Fairway depth finders 20p each

WIREWOUND POTS

250, 350 OHM, 1K, 4 watt, 10K, 20K, 50K, all at 10p each

RECORD PLAYER CARTRIDGE

ER.5XME Mono, with turn over stylus, single hole fixing 35p

GREEN INDICATOR

Takes M.E.S bulb 10p

CONNECTOR STRIP

Belling Lee L1469, 12 way polythene. 5p each

CAN CLIPS

1" or 1 1/8" 2p

T.O.5 HEATSINKS

Style 154 high conductivity 5p

PAXOLINE

2 3/8 x 4 3/4 x 1/8" or 3 x 2 1/2 x 1/8" 2p

4 5/8 x 1/2 x 1/8" 2 for 1p

220K 3 watt resistors 2p

VALVE RETAINER CLIP, adjustable 2p

OUTPUT TRANSFORMERS

Sub-miniature 20p

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11

Open 10 a.m. till 8 p.m. Monday to Saturday

Phone 01-223 5016

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE

LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.

-the lowest prices!

74 Series T.T.L. I.C.'S DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any I.C.'s. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed

BI-PAK Order No.	Price and qty. prices			BI-PAK Order No.	Price and qty. prices		
	1-24	25-99	100 up		1-24	25-99	100 up
BP00-BN7400	0.15	0.14	0.12	BP86-BN7486	0.82	0.80	0.82
BP01-BN7401	0.15	0.14	0.12	BP90-BN7490	0.67	0.64	0.58
BP02-BN7402	0.15	0.14	0.12	BP91-BN7491AN	0.87	0.84	0.78
BP05-BN7403	0.15	0.14	0.12	BP92-BN7492	0.87	0.84	0.88
BP04-BN7404	0.15	0.14	0.12	BP93-BN7493	0.87	0.84	0.88
BP05-BN7405	0.15	0.14	0.12	BP94-BN7494	0.77	0.74	0.68
BP07-BN7407	0.18	0.17	0.16	BP95-BN7495	0.77	0.74	0.68
BP08-BN7408	0.18	0.17	0.16	BP96-BN7496	0.77	0.74	0.68
BP09-BN7409	0.18	0.17	0.16	BP100-BN74100	1.78	1.65	1.58
BP10-BN7410	0.18	0.17	0.16	BP104-BN74104	0.97	0.84	0.88
BP13-BN7413	0.20	0.20	0.24	BP105-BN74105	0.97	0.84	0.88
BP16-BN7416	0.43	0.40	0.38	HP107-BN74107	0.40	0.38	0.38
BP17-BN7417	0.43	0.40	0.38	BP110-BN74110	0.55	0.53	0.50
BP20-BN7420	0.15	0.14	0.12	BP111-BN74111	1.25	1.15	1.00
BP30-BN7430	0.15	0.14	0.12	BP115-BN74115	1.00	0.95	0.90
BP40-BN7440	0.15	0.14	0.12	BP119-BN74119	1.25	1.25	1.10
BP43-BN7441	0.67	0.64	0.58	BP121-BN74121	0.67	0.64	0.58
BP42-BN7442	0.67	0.64	0.58	BP141-BN74141	0.87	0.84	0.88
BP45-BN7443	0.67	0.64	0.58	BP164-BN74164	1.40	1.40	1.30
BP44-BN7444	1.95	1.85	1.75	BP150-BN74150	1.00	1.70	1.90
BP45-BN7445	1.95	1.85	1.75	BP151-BN74151	1.00	0.95	0.90
BP46-BN7446	0.97	0.94	0.88	BP153-BN74153	1.20	1.10	0.85
BP47-BN7447	0.97	0.94	0.88	BP154-BN74154	1.40	1.70	1.90
BP48-BN7448	0.97	0.94	0.88	BP155-BN74155	1.40	1.30	1.20
BP50-BN7450	0.15	0.14	0.12	BP156-BN74156	1.40	1.30	1.20
BP51-BN7451	0.15	0.14	0.12	BP160-BN74160	1.80	1.70	1.90
BP52-BN7452	0.15	0.14	0.12	BP161-BN74161	1.80	1.70	1.90
BP54-BN7454	0.15	0.14	0.12	BP164-BN74164	2.00	1.90	1.80
				BP165-BN74165	2.00	1.90	1.80
				BP181-BN74181	3.75	3.50	3.40
				BP182-BN74182	0.97	0.94	0.88
				BP190-BN74190	3.50	3.25	3.00
				BP191-BN74191	3.50	3.25	3.00
				BP192-BN74192	2.10	1.95	1.75
				BP193-BN74193	2.10	1.95	1.75
				BP195-BN74195	1.10	1.05	0.95
				BP196-BN74196	1.30	1.20	1.00
				BP197-BN74197	1.80	1.70	1.60
				BP198-BN74198	5.50	5.00	4.00
				BP199-BN74199	5.50	5.00	4.00

PRICE-MIX. Devices may be mixed to qualify for quantity prices.
PRICES for quantities in excess of 500 pieces mixed, on application.
Owing to the ever increasing range of TTL 74 Series, please check with us for supplies of any devices not listed above, as it is probably now in stock. WARE 3442.

BI-PAK DO IT AGAIN!

50Wpk 25w (RMS)

0.1% DISTORTION HI-FI AUDIO AMPLIFIER THE AL50



- ★ Frequency response 15Hz to 100,000 - 1dB. **ONLY £3.25p each**
- ★ Load - 3, 4, 8 or 16 ohms.
- ★ Distortion - better than 1% at 1KHz.
- ★ Signal to noise ratio 80dB.
- ★ Supply voltage 10 - 35 Volts.
- ★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and ALSO was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT - TESTED - GUARANTEED.

STABILISED POWER MODULE

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (rms) per channel, simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications, including:- Disc Systems, Public Address, Intercom Units, etc, Handbook available 10p.

STABILISED POWER MODULE SPM80 £2.95

TRANSFORMER BMT80 £1.95 p & p 25p.

SPECIAL COMPLETE KIT COMPRISING 2T, AL50's, 1, SPM80 & 1, BMT80 ONLY £11, FREE p & p

LOGIC DTL 930 SERIES I.C.'s

ROCK BOTTOM PRICES

Type No.	1-24	25-99	100 up
BP930	1.2p	1.1p	1.0p
BP932	1.2p	1.1p	1.1p
BP933	1.2p	1.1p	1.1p
BP935	1.2p	1.1p	1.1p
BP936	1.2p	1.1p	1.1p
BP944	1.2p	1.1p	1.1p
BP945	2.5p	2.4p	2.2p
BP946	1.2p	1.1p	1.0p
BP948	2.5p	2.4p	2.2p
BP951	8.5p	8.0p	8.5p
BP962	1.2p	1.1p	1.0p
BP963	4.0p	3.5p	3.5p
BP964	4.0p	3.5p	3.5p
BP967	4.0p	3.5p	3.5p
BP969	4.0p	3.5p	3.5p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

LINEAR I.C.'s— FULL SPEC.

Type No.	1-24	25-99	100 up
BP 201C-BL201C	63p	59p	49p
BP 701C-BL701C	63p	59p	49p
BP 702C-BL702C	63p	59p	49p
BP 702-72702	63p	59p	49p
BP 709-72709	63p	59p	49p
BP 709F-72709C	63p	59p	49p
BP 719-72710	63p	59p	49p
BP 711-72711	63p	59p	49p
BP 741-72741	75p	69p	57p
7A 702C-7A702C	43p	35p	27p
TAA 263-	70p	60p	55p
TAA 292-	90p	75p	70p
TAA 550	170p	158p	150p

NUMERICAL INDICATOR TUBES

MODEL	CD66	GR 116	3015F
Anode voltage (Vdc)	170 min	175 min	5
Cathode cur'nt(mA)	2.3	14	14
Numeral h'ght (mm)	16	13	9
Tube height (mm)	47	32	22
Tube diameter (mm)	19	13	12
I.C. driver rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All indicators 0.9 + Decimal point: All side viewing: Full data for all types available on request.

STOP PRESS! NOW OPEN

BI-PAKS NEW COMPONENT SHOP

A wide range of all types of electronic components and equipment available at competitive prices.

18, BALDOCK ST. (A10), WARE, HERTS. Tel.: 61593
OPEN 9.15-6 TUES. to SATS. FRIDAYS UNTIL 8 p.m.

BI-PAK

P.O. BOX 6, WARE - HERTS

Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	..	18p
DTB4 Transistor & Valve circuitry for D.P. Coils	..	18p
DTB9 Valve Type Coil Pack Application circuitry	..	18p
MD.1 Decoder Circuitry for Stereo Reception	..	21p

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers

FREE

in the
October issue

Practical AERIAL DATA Wall Chart

Remember the quality of your reception is governed by the efficiency of your aerial! Whether for DX'ing, FM radio or television, this highly detailed chart illustrates all the types of aerial and explains how to choose and construct the ideal one for each purpose.

and these special features:

The pre-tuned Car/Portable Radio

Full building instructions using just 6 cheap transistors to provide 4 pre-tuned switch channels—3 medium, 1 long wave.

Audio Reference Source

This project describes a unit that's a fraction of the cost of an a.f. signal source but 95% as useful.

The 'Logiprobe'

Easy to build, gives you a visual indication of the logic level in TTL systems.

Plus many more
constructional features in —
October issue on sale September 1

20p

PRACTICAL WIRELESS

BI-PRE-PAK



COMPLETE TELEPHONES

Normal household type as supplied to the Post Office, ex. G.P.O. Only **95p** each. p. & p. 35p each.



TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

ONLY 50p

p. & p. 15p.

TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V. 0.5 to 2mA.	50p
B79	4	1N4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B89	200	Mixed Capacitors. Approx. quantity, counted by weight.	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H28	20	OC200/1/2/3 PNP Silicon uncoated TO-5 can	50p
H30	20	1-Watt Zener Diodes. Mixed Voltages 6.8 - 43V.	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short Lead Transistors. NPN Silicon Planar types	50p

UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes. Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types PNP, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706, B395A, etc.	50p
B1	50	Germanium Transistors PNP, AF & RF	50p
H4	40	250mW Zener Diodes DO-7 Min. Glass Type	50p
H14	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p
H17	20	3 amp Silicon Stud rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers. 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied.	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy. TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.


FULLY TESTED AND MARKED SEMICONDUCTORS

6p		6p	
AC107	0-15	OC170	0-23
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-15	OC201	0-25
AC176	0-20	2G301	0-13
ACY17	0-20	2G303	0-13
AF239	0-30	2N711	0-50
AF186	0-20	2N1302-3	0-15
AF139	0-30	2N1304-5	0-17
BC154	0-20	2N1306-7	0-20
BC107	0-10	2N1306-9	0-22
BC108	0-10	2N3819FET	0-40
BF194	0-15	2N4416FET	0.35
BC109	0-10	2N4416FET	0.35
BF274	0-20	OC20	0-50
BFY50	0-15	OC33	0-30
BSY25	0-13	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-25
BSY29	0-10	OC36	0-37
BSY95A	0-10	AD149	0-30
OC43	0-15	AU149	1-25
OC44	0-13	AU170	0-25
OC45	0-10	25034	0-50
OC71	0-10	2N3055	0-50
OC72	0-10	Diodes	0-10
OC81	0-13	AA742	0-07
OC81D	0-13	OA95	0-07
OC83	0-18	OA79	0-07
OC139	0-13	OA81	0-07
OC140	0-15	IN914	0.06

F.E.T. PRICE

BREAKTHROUGH!!

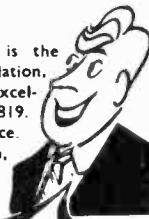This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+ 20p each.



A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs **£3.50**, post paid.

A MUST for Colour T.V. Alignment.

Our famous P1 Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P1, only 50p 10p P & P on this Pak.

FREE CATALOGUE

FOR TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS.



8 RELAYS FOR £1

VARIOUS TYPES P. & P. 25p.

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL50S and PY500 valves. As removed from colour receivers at the factory.

NOW ONLY 50p each post and packing 23p.

Quantity	1-10	10-50	50-
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's. Per Set	25p	20p	15p
OA47 Gold-Bonded Diodes. Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7.5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5.1, 8.2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

SL403D Audio Amp. 3-Watts 1.50 1.32
709C Linear Opp. Amp. 25p 20p 15p
Gates, Factory Marked and Tested by A.E.I. 25p 22p 10p

J. K. Flip-Flop Factory. Marked and Tested by A.E.I.

SN7490 Decade Counter	40p	35p	30p
UL914 Dual 2 I/P Gate	60p	60p	55p
	40p	35p	30p

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines: **B.P.I. Transistor Equivalents and Substitutes;** 40p

This includes many thousands of British U.S.A., European and C.V. equivalents. **The Hi-Fi Radio Valve & Transistor Data Book 9th Edition; P. & P. 21p** 75p

Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME:

ADDRESS:

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX, SS0 9DF
TELEPHONE: SOUTHEND (0702) 46344

IN THIS CATALOGUE




10p
post paid
in U.K.

- 96 Pages
- Transistors, with technical specs.
- I.Cs with working diagrams
- Resistors, capacitors, components
- Diagrams, tables, information
- GENUINE DISCOUNTS

ELECTROVALUE LTD. Dept. RC.4
28 St. Judes Rd., Englefield Green, Egham, TW20 0HB
9-6 daily: 1.0 p.m. Sat. Telephone Egham 3603

REVERBERATION UNIT KIT Mk III

6 transistor reverberation chamber to which microphones, instruments, etc., may be connected for added dimensional effect. The output is suitable for most amplifiers and the unit is especially suitable for use with electronic organs. A ready-built spring and transducer assembly is used.
Complete easy-to-build kit, with constructional notes and circuits £7.50. Pre-drilled and printed case £2.00 extra. All parts available separately.

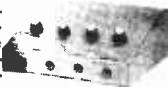


WAH-WAH PEDAL KIT Mk III

The Wilsic Wah-Wah pedal comprises a SELECTIVE AMPLIFIER MODULE KIT, containing all the components to build a two transistor circuit module, which may be used by the constructor for his own design or fitted to the FOOT VOLUME CONTROL PEDAL (as photo) converting it to Wah-Wah operation. This pedal is in strong fawn plastic and fitted with output lead and screened plug. Selective amplifier module kit £1.75. Foot Volume control pedal £5.13. COMPLETE KIT £6.50. Add 38p for assembly of module.



WILSIC VIBRATO UNIT

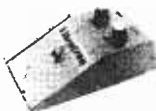A new kit to build a self-contained vibrato foot switch unit. 4-silicon transistor circuit in tough grey hammered finish metal cabinet. Variable speed and depth controls and on-off foot switch. Ideal for guitars but unsuitable for high level inputs.
COMPLETE KIT £5.25, all parts available separately.



THE WILSIC BOOK OF CIRCUITS contains the full instructions for the Reverb unit, Wah-Wah pedal and our Vibrato unit.
PRICE ONLY 15p

SEND 5p in stamps for latest catalogue (Spring 1972) of Hi-Fi components, guitars, etc., etc. Friendly, high-speed service.




WILSIC ELECTRONICS LTD.
6 COPLEY ROAD, DONCASTER, YORKS

Latest Bound Volume No. 24

of

"The Radio Constructor" FOR YOUR LIBRARY

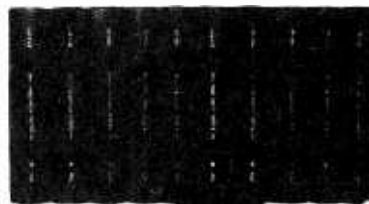

Comprising
772 pages
plus index

AUGUST 1970
to JULY 1971

PRICE £2.00 Postage 29p

BOUND VOLUME NO. 23

OF

"THE RADIO CONSTRUCTOR"
AUGUST 1969 to JULY 1970

Limited number of this volume still available

PRICE £1.88 Postage 29p

We regret all earlier volumes are now
completely sold out.

Available only from
DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN

**PRECISION
POLYCARBONATE CAPACITORS**

Fresh Stock - Fully Tested and Guaranteed

Close tolerance professional capacitors by well-known manufacturer. Excellent stability and extremely low leakage. All 63V D.C.
 0.47µF: ±5% 30p; ±2% 40p; ±1% 50p; Size 1/4" x 1/4" x 1/8"
 1.0 µF: ±5% 40p; ±2% 50p; ±1% 60p; Size 1" x 1/2" x 1/8"
 2.2 µF: ±5% 50p; ±2% 60p; ±1% 75p; Size 1" x 3/4" x 1/8"
 4.7 µF: ±5% 70p; ±2% 90p; ±1% 115p; Size 1 1/2" x 3/4" x 1/8"
 10.0 µF: ±5% 110p; ±2% 140p; ±1% 180p; Size 1 3/4" x 3/4" x 1/8"
 15.0 µF: ±5% 160p; ±2% 210p; ±1% 270p; Size 1 3/4" x 1" x 1/8"

NEW! - TANTALUM BEAD CAPACITORS

Values available .22, .47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V. All at 9p each; 6 for 50p; 14 for £1.00. Special pack, 6 of each value (72 capacitors) for £5.00.

TRANSISTORS: BC107; BC108; BC109 (please state which), all at 9p each. 6 for 50p; 14 for £1.00; May be mixed to qualify for lower price. All brand new to full manufacturer's specification.

POPULAR DIODES: IN914 - 7p each; 8 for 50p; 18 for £1.00
 IN816 - 9p each; 6 for 50p; 14 for £1.00. IS44 - 5p each; 11 for 50p; 24 for £1.00. All brand new and marked.

400mW ZENER DIODES: Values available 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15 volts. All new and marked. All at 12p each; 5 for 50p; 12 for £1.00.

RESISTORS: Carbon film 1/2 watt 5%. Range 2.2Ω-2.2MΩ E12. Series i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades. All at 1p each. 8p for 10 of any one value; 70p for 100 of any one value. Special development pack 10 off each value 2.2Ω to 2.2MΩ (730 resistors) for £5.00.

440V A.C. CAPACITORS: 0.1µF: Size 1 1/4" x 1/2", 25p each
 0.25µF: Size 1 3/8" x 3/8", 30p each 0.5µF: Size 1 1/2" x 3/4", 35p each
 1.0 µF: Size 2" x 3/4", 45p each 2.0µF: Size 2" x 1", 75p each
 Suitable for use on C.D. ignition, 250V A.C. motors, etc.

5p post and packing on all orders below £5

V.ATTWOOD, Dept C.3., P.O. Box 8, Alresford, Hants.

RADIO AMATEURS

**The Radio Society of Great Britain
is YOUR national society**

**YOU NEED THE RSGB!
THE RSGB MUST HAVE
YOUR SUPPORT!**

Membership benefits include:

- Representation at MPT and IARU
- Monthly journal, *Radio Communication*
- Technical publications
- QSL Bureau
- Contests, HF and VHF
- Operating awards

Write for full particulars of membership to:

**The General Manager, RSGB (RC),
35 Doughty Street, London WC1N 2AE**

Now! **A FAST EASY
WAY TO LEARN BASIC
RADIO & ELECTRONICS**



Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home - the fast, modern way. Give yourself essential technical 'know-how' - like reading circuits, assembling standard components, experimenting, building - quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The TECHNATRON Outfit contains everything you need, from tools to transistors - even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN - but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build - and it's a good one - is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course - but it teaches the real thing. The easy to understand, practical projects - from a burglar-alarm to a sophisticated Radio set - help you master basic Radio and Electronics - even if you are a 'non-technical' type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of 'OPPORTUNITIES IN TELECOMMUNICATIONS/TV AND RADIO'. This brand new booklet - just out - tells you all about TECHNATRON and B.I.E.T.'s full range of courses.



FREE

**BRITISH INSTITUTE
OF ENGINEERING
TECHNOLOGY**

Dept. B9, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

Please send book and full information - free and without obligation.

NAME..... AGE.....
(BLOCK CAPITALS PLEASE)

ADDRESS.....



OCCUPATION.....

To B.I.E.T. Dept. B9, Aldermaston Court, Reading RG7 4PF

That's Summer that was!!



Summer was so late arriving this year that it nearly slipped by without our noticing it! Already we are tucking the lawn mower in for its winter hibernation, and once again "the nights are drawing in." HOORAY! - that means we can really get cracking on those electronic projects that have been buzzing around at the back of our minds.

The first step is to get the *components* lined up. And the best way to do that? Simple - get a copy of the Home Radio Components Catalogue. Then we can quickly and clearly see what we need and how much it costs. We'll know too that either by sending an order or by calling in at the Mitcham shop, we can get just what we want "off the shelf". The catalogue costs 70p, including post and packing, or 50p over the counter. Every copy contains 10 vouchers, totalling a value of 50p when used as instructed - so you can soon get back the cost of the catalogue. Over 8,000 items are listed, over 1,500 of them illustrated, and free supplements are supplied regularly to keep you up-to-date.

Post the coupon today, or call at our shop S.A.P. - we're open 9 to 5.30 Monday to Saturday, except Wednesday, 9 to 1.

Our CREDIT ACCOUNT SERVICE makes it so simple to purchase

Our customers find this service a very simple and convenient way of purchasing all their radio and electronic components. We supply pre-paid envelopes and order forms, and no matter how many orders you send us you make only one payment per month. There are

several other advantages too - full details and entry forms are included in our catalogue.



**24 hr. Phone Service
Ring 01-648 8422**

It would help us considerably if we knew whether this was your first Home Radio Components Catalogue. If it is please place a tick in the box.

The price of 70p applies only to catalogues purchased by customers in the UK and to BFPO addresses.

POST THIS COUPON with your cheque or postal order for 70p

This is my first H.R. Components Catalogue

Name _____

Address _____

**HOME RADIO (COMPONENTS) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD.**

RADIO & ELECTRONICS CONSTRUCTOR

RADIO CONSTRUCTOR

& ELECTRONICS



Incorporating
THE RADIO AMATEUR

SEPTEMBER 1972

Vol. 26 No. 2

CONTENTS

Published Monthly (1st of Month)
First Published 1947

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141
Telegrams Databux, London

© Data Publications Ltd., 1972. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £2.70 (U.S.A. and Canada \$7.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.


Production.—Web Offset.

ELECTRONIC METRONOME by M. G. Argent	74
AUTOMATIC BATTERY MONITOR (Suggested Circuit 262) by G. A. French	77
NOTES ON SEMICONDUCTORS (Further Notes – 10. Vive La Difference) by Peter Williams	79
NEWS AND COMMENT	80
SHORT WAVE CRYSTAL SETS by J. Braunbeck	82
THE 'JUBILEE' 8-WATT AMPLIFIER – Part 2 by J. R. Davies	84
RADIO AMATEUR EXAMINATION COURSES	90
MEASURING SMALL CAPACITORS by R. E. Stewart	92
TRADE NEWS	94
QSX by Frank A. Baldwin	95
A.F. SIGNAL GENERATOR by R. A. Penfold	96
IMPROVED DIGITAL DISPLAY by D. A. Nicole, G8CYJ	104
SHORT WAVE NEWS by Frank A. Baldwin	106
CYCLOPS (Electronic Robot) – Part 3 by L. C. Galitz	108
IN YOUR WORKSHOP	114
RADIO TOPICS by Recorder	120
RADIO CONSTRUCTOR'S DATA SHEET No. 66 (Meter Shunts I)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

The Radio Constructor is printed by Carlisle Web Offset.

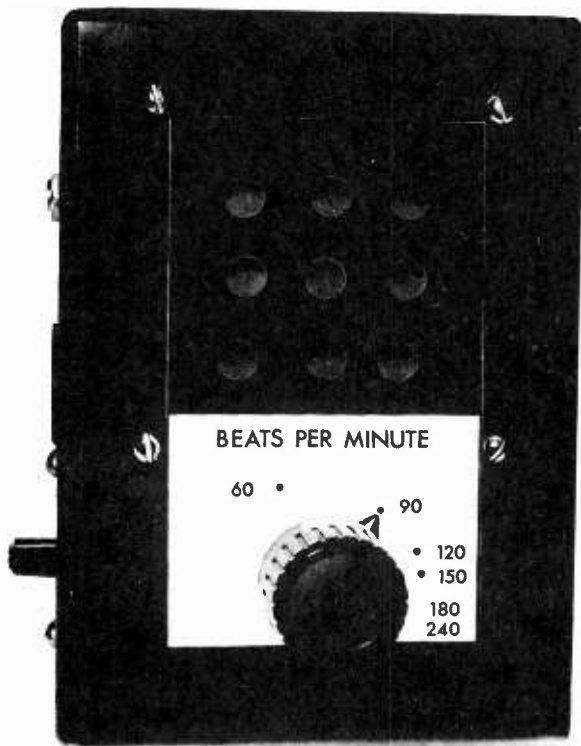OCTOBER ISSUE WILL BE
PUBLISHED ON OCTOBER 2nd



ELECTRONIC METRONOME

by
M. G. Argent


The unijunction relaxation oscillator and amplifier unit described here can be used as a metronome either on its own or coupled to a more powerful amplifier.

THIS IS AN EASY TO BUILD UNIT INCORPORATING inexpensive components, and it offers advantages over a conventional metronome which costs much more.

THE CIRCUIT

The circuit, shown in Fig. 1, consists basically of a unijunction transistor, TR1, which functions as a relaxation oscillator driving a current amplifying stage, TR2 and a loudspeaker.

The principle, briefly, of the unijunction transistor can be explained in the following manner. An equivalent circuit for the unijunction transistor is shown in Fig. 2. If a positive voltage rising in amplitude with respect to base 1 is applied to the emitter, a time will come when the emitter-base diode, shown as D1, becomes forward biased, whereupon current will flow via D1 and rB1. Referring back to Fig. 1, the rising voltage appears across C1 due to the fact that, as soon as the unit is switched on, C1 charges up via RV1 and R1. The speed at which C1 charges is determined by the values of C1, RV1 and R1. In this case RV1 is the frequency control of the unit.

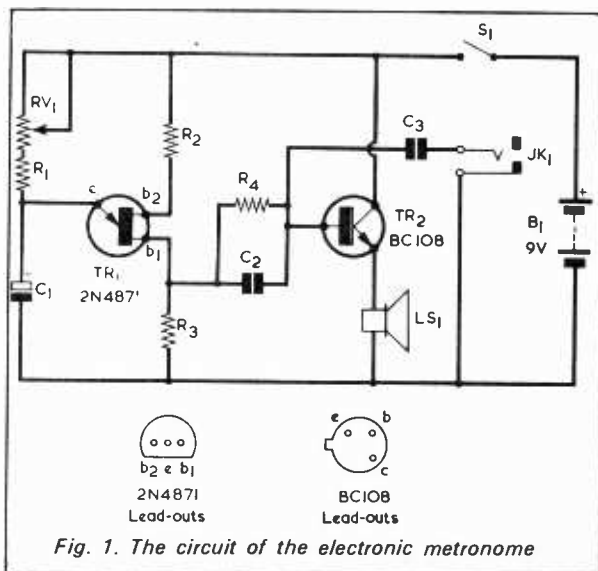

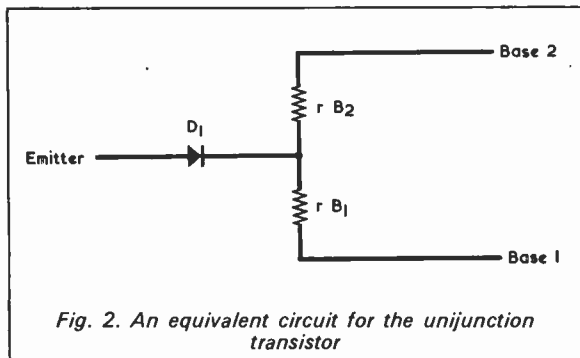


Fig. 2. An equivalent circuit for the unijunction transistor

When the voltage across C1 reaches the point where D1 becomes forward biased, C1 is rapidly discharged through the emitter, base 1 and R3. Because of this current through R3 a voltage appears across it. Capacitor C1 then commences to charge again and the process is repeated when the voltage across it is sufficiently high to forward bias diode D1 once more.

The resultant waveform across R3 is a series of voltage spikes or pulses. These are fed via R4 and C2 to

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 10%)

R1	10k Ω
R2	100 Ω
R3	1k Ω
R4	56k Ω
RV1	100k Ω potentiometer, log

Capacitors

C1	10 μ F electrolytic, 10V. Wkg.
C2	0.01 μ F, Mullard miniature foil.
C3	2,200pF, paper or plastic foil.

Transistors

TR1	2N4871
TR2	BC108

Loudspeaker

LS1	35 Ω loudspeaker, 2 $\frac{1}{2}$ in. (see text)
-----	---------------------------------------------------------

Switch

S1	Miniature slide switch.
----	-------------------------

Socket

JK1	2.5 or 3.5mm. jack socket
-----	---------------------------

Battery

B1	9 volt battery, type PP4 (Ever Ready)
----	---------------------------------------

Miscellaneous


Battery connectors
Veroboard, 0.15in. matrix, 7 strips by 16 holes
Knob
Plastic case (see text)

the base of TR2, which drives the loudspeaker. The purpose of R4 and C2 is to reduce the lower frequency response of the circuit so as to give more of a click in the loudspeaker than a thud.

There is a facility also to connect the unit to an external amplifier, for use with groups where the unit alone would not be loud enough. This output is taken via C3 to jack socket JK1. C3 has a low value which further reduces the lower frequency response since, otherwise, damage may result to the speaker or speakers of the external amplifier. This facility is a great advantage over the conventional metronome.

CONSTRUCTION

The circuitry is assembled on a piece of 0.15in. matrix Veroboard measuring approximately 2 $\frac{1}{2}$ in. by 1 $\frac{1}{2}$ in., with the strips running lengthwise. There are 7 strips, each with 16 holes. The component and copper sides of the board are shown in Fig. 3. Only two 'cut-aways' are required, and these may be made with a small drill or spot face cutter. RV1 is connected such that the resistance it inserts into circuit decreases as it is rotated clockwise. The layout is by no means critical, and the unit could be built into an existing amplifier. The author used a small black plastic case with lid measuring 3 $\frac{1}{2}$ by 4 $\frac{1}{2}$ by 1 $\frac{1}{2}$ in. and this enabled the circuit to be made up as a neat self-contained unit. If a plastic case of this size cannot be obtained, a small plywood housing of around the same dimensions could be constructed instead. The board and battery were held in position with the aid of a polystyrene ceiling tile cut to size.

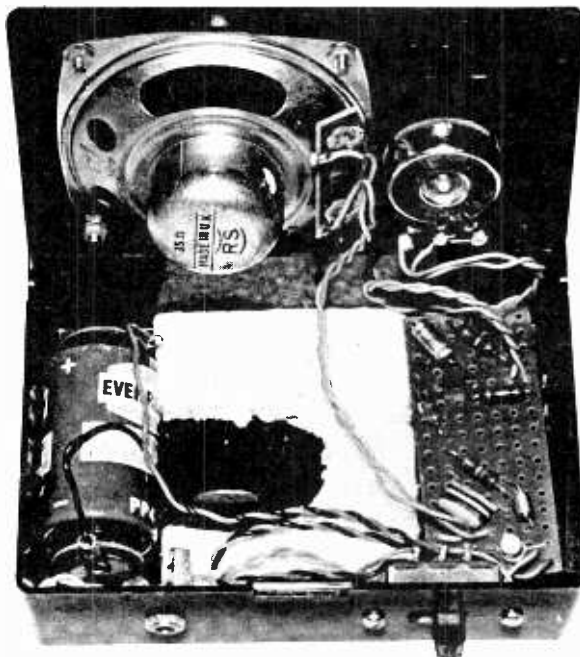

A view inside the metronome case. The on-off switch and jack socket are mounted on the side remote from the case hinge

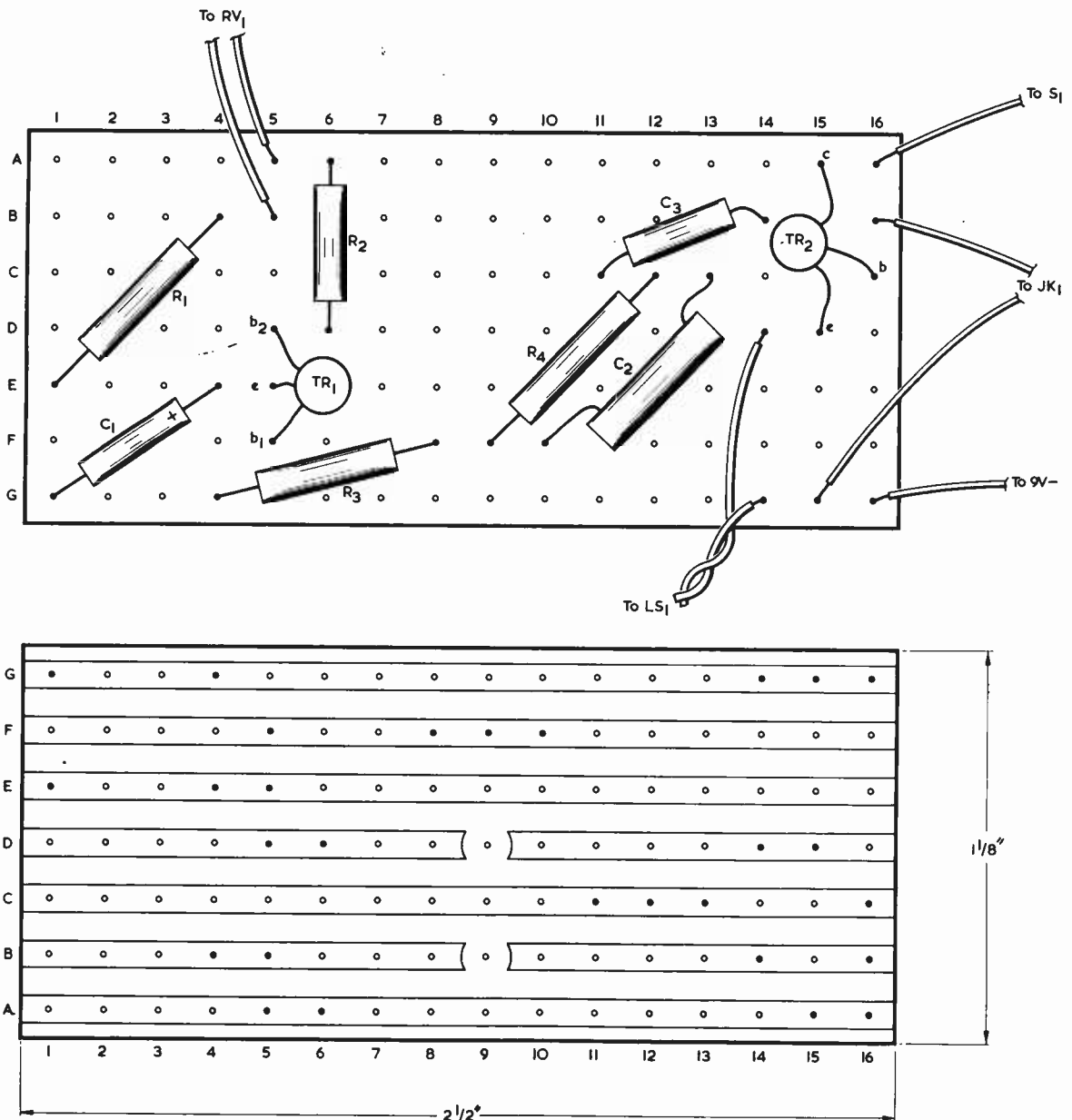



Fig. 3. The component and copper sides of the Veroboard

The 2N4871 unijunction transistor is available from LST Electronic Components Ltd., 7 Coptfold Road, Brentwood, Essex. The 35Ω speaker employed by the author is an R.S. Components type, obtainable from retailers of R.S. Components parts, including Celectron-E, P.O. Box No. 1, Llantwit Major, Glamorgan, CF6 9YN.

The easiest way of calibrating the unit is to check it against a stop-watch, but if the constructor has an oscilloscope with a calibrated slow timebase this would be more accurate. Once calibrated, the unit will be found extremely stable. Current consumption from the 9 volt battery is of the order of 2 to 4mA, rising to the higher value as frequency is increased. ■

AUTOMATIC BATTERY MONITOR

by G. A. FRENCH

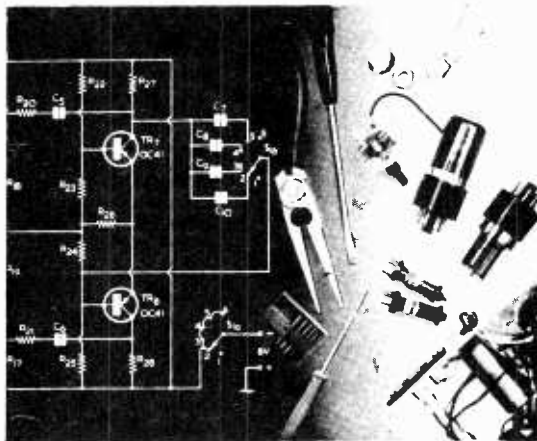

SOME ITEMS OF BATTERY-OPERATED electronic equipment incorporating semiconductors, including in particular test gear, are intended to be used only when the battery voltage is above a certain specified level. If the battery voltage falls below the prescribed level the equipment may still function, but its performance becomes erratic or gives rise to incorrect measurements.

The user of such equipment may not, however, be aware that its battery voltage has fallen below the critical level. The only way in which the satisfactory operation of the equipment can be assured is to measure the voltage of its battery from time to time or, for complete certainty, on each occasion that the equipment is used. A requirement of this nature tends to be irritating and time-consuming. A possible answer consists of providing the equipment with a built-in voltmeter which continually indicates battery voltage, but this can be a relatively expensive solution.

The voltage monitoring device to be described in this month's contribution to the 'Suggested Circuit' series offers an alternative approach. Inserted in series with one of the equipment battery leads are components which cause the supply to be applied only when the battery voltage is above a predetermined level. When the battery voltage falls below this level the equipment simply does not switch on. Thus, non-functioning of the equipment automatically indicates that a new battery is required; with the results that the equipment cannot be operated at a battery voltage that is too low, and that no voltage measurements are needed.

Before proceeding further it must be emphasised that the circuit to be discussed is in the experimental category and that it is primarily

intended to function with equipment which draws, by way of resistive circuits, a current of the order of 10mA or more from the supply. In practice, successful operation with equipment which draws a lower current is perfectly feasible, but this point may only be determined by actual experiment with the equipment concerned. A further factor is that the monitoring circuit causes some 0.65 volt of battery voltage to be lost, and that it requires setting up to the operating voltage by an empirical approach which involves the insertion of silicon diodes. On the credit side are the facts that the circuit functions completely automatically and draws no extra current from the battery.

The monitoring circuit components will not be overloaded in terms of voltage and current if the equipment with which they are used is designed to operate from a dry battery whose voltage does not exceed 18 volts.

CIRCUIT OPERATION

The circuit of the automatic battery monitor appears in Fig. 1. Here, thyristor TH1 is inserted in series with the negative supply to the equipment in which the monitor is fitted. Connected across it are zener diode ZD1, limiter resistor R1, and as many forward biased silicon diodes as are required to provide the desired operating potential for the device.

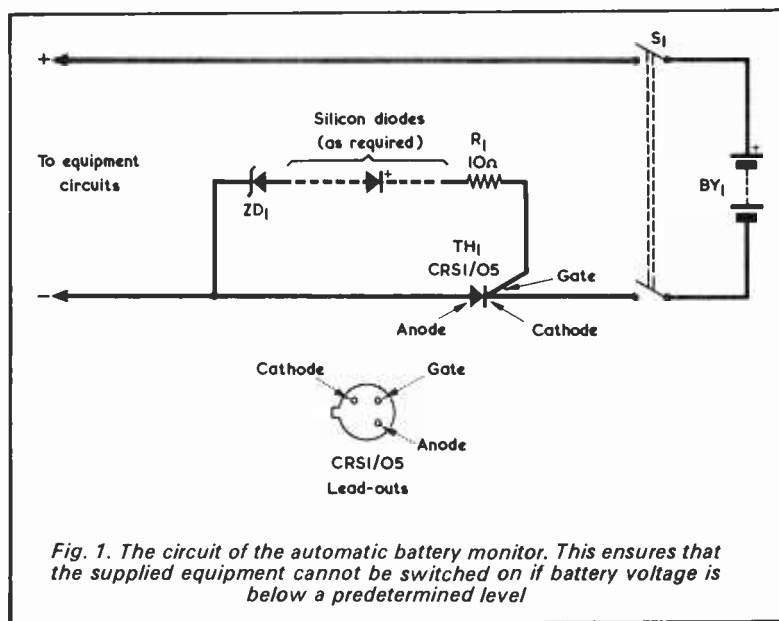


Fig. 1. The circuit of the automatic battery monitor. This ensures that the supplied equipment cannot be switched on if battery voltage is below a predetermined level

When switch S1 is closed the thyristor and the associated components are coupled to the battery via the supplied equipment. Assuming a resistive path between the equipment supply lines, a positive voltage is applied to the anode of the thyristor and to zener diode ZD1. If this voltage is sufficiently high, ZD1 (together with whatever silicon diodes are in series with it) allows sufficient gate current to flow in the thyristor to turn it on. The thyristor in its conductive state then allows the full battery current to flow to the equipment, offering in the process a voltage drop of about 0.65 volt between its anode and cathode. There is, now, no triggering current to the gate but this fact is unimportant since, once it has fired, the thyristor remains in the conductive state. It can only be returned to its non-conductive state by turning off S1.

If when S1 is closed the battery voltage is too low, either too small a triggering current or none at all is passed to the gate of the thyristor and it does not fire. In consequence, the supplied equipment cannot operate.

PRACTICAL TESTS

The writer checked out the circuit in practice, using a fixed resistor to represent the circuits of the supplied equipment. BY1 was replaced by a power supply having a variable voltage output. See Fig. 2(a). ZD1 was a 6.2 volt 5% 250mW zener diode and, initially, no silicon diodes were in circuit whereupon ZD1 connected directly to R1. It was found that the circuit operated reliably when the fixed resistor representing the equipment circuits had a value of about 1.3k Ω or less. With a 1k Ω resistor the thyristor became conductive when S1 was closed for all voltages from the power supply in excess of 7.6 volts. Below this voltage the thyristor did not fire.

Some equipment will have a large

value electrolytic capacitor across its supply lines and so the experiment was repeated with a 1,000 μ F capacitor added, as in Fig. 2(b). This time the thyristor fired for all voltages from the power supply in excess of 6.5 volts, and did not become conductive at lower voltages. It is patent that, at the instant of closing S1, the capacitor was nearly equivalent to a short-circuit, and this explains why it caused the voltage at which triggering occurred to be lower. As before, the circuit did not operate when the resistor had a value in excess of about 1.3k Ω .

Both with and without the capacitor, the dividing line between voltages which fired the thyristor and those which did not was well-defined and sharp. If the battery voltage was very slightly lower than that needed to fire the thyristor, a small gate current flowed through the resistor representing the supplied equipment. Such a current would be insufficient to cause operation of any equipment connected in place of the resistor.

Next, a silicon diode was inserted between the zener diode and the 10 Ω limiting resistor, being connected with the polarity shown in Fig. 1. This caused the voltage at which the thyristor fired to be raised by approximately 0.6 volt. Adding more silicon diodes in series increased the voltage by a further 0.6 volt per diode.

Summing up the results of the experiment it can be stated that the circuit worked reliably when the resistor representing the equipment circuits had a value which caused some 6mA or more to flow after the thyristor fired. Taking into account spread in thyristor characteristics, it would seem safe to say that the circuit should function correctly if the resistive paths in the supplied equipment circuits caused 10mA or more to flow after the thyristor fires, and that reliable operation is quite possible at lower currents but has to be proven by experiment. The resistive paths will

normally be given by such things as base bias potentiometers and the like. There is, however, another factor which needs to be taken into account, since it has to be remembered that the transistors in the supplied equipment circuits will themselves tend to draw current at quite a low voltage and that this current will add to that flowing through the resistive paths. Thus, it is possible for the monitoring circuit to function even when the current through the resistive paths of the equipment is, on its own, insufficient. But this point can, again, only be determined by practical experiment.

A second finding is that the voltage at which the thyristor fires is, for a given zener diode and quantity of silicon diodes, reduced when a large value electrolytic capacitor happens to be connected across the equipment supply lines.

SETTING-UP

The setting-up of the monitoring circuit is considerably eased if a variable voltage power supply is to hand, since it is then merely necessary to increase the output voltage of the supply to the level where the thyristor fires. If such a power supply is not available it is necessary to use a battery having single cells from which tapings in 1.5 volt steps can be obtained.

First, select a 200 to 400mW zener diode whose nominal voltage is about 1 volt below that at which the circuit is desired to operate, and connect it directly between the anode of the thyristor and the 10 Ω resistor. No silicon diodes are fitted at this stage. Connect the monitoring circuit to the equipment with which it is to be used and then switch S1 on and off, increasing the supply voltage between each closure of the switch. If the circuit is capable of operating with the particular equipment employed, the thyristor should fire at some voltage which is higher than the zener diode voltage. If this voltage is greater than the desired one, replace the zener diode with one having a lower voltage rating and repeat the process. Should the firing voltage be equal to that desired, then the monitoring circuit is finally set up and ready for use. If the firing voltage is lower than the desired one, insert one or more silicon diodes between the zener diode and the 10 Ω resistor as required, or fit a higher voltage zener diode and start again. The silicon diodes, incidentally, can be of any type. Miniature silicon rectifiers such as the IN4001 represent a good choice, particularly as they take up very little space.

In the diagrams it is assumed that the on-off switch is a double-pole type. Circuit operation remains unaltered if a single-pole on-off switch is used instead, and this may be inserted in either the positive or the negative line from the battery. ■

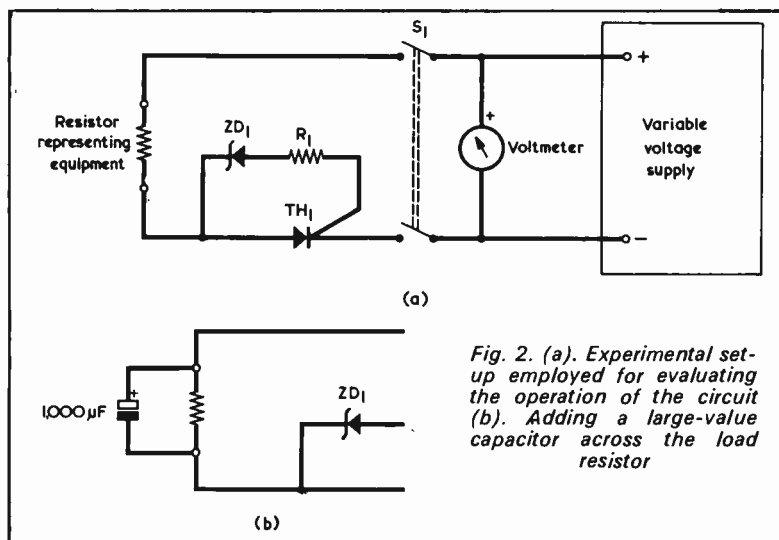


Fig. 2. (a). Experimental set-up employed for evaluating the operation of the circuit (b). Adding a large-value capacitor across the load resistor

Further Notes—10 VIVE LA DIFFERENCE

by


Peter Williams

Our contributor develops the electronic thermometer theme introduced last month, and describes a differential thermometer having higher sensitivity together with greater freedom from inaccuracies due to changes in supply voltage.

TO CARRY THE BRIDGE IDEA EMPLOYED IN LAST month's topic a stage further, consider the properties of the circuit shown in the diagram. If the transistors in this diagram are held at the same temperature then the bridge may be readily balanced by fine adjustment of R1. Then each transistor is almost equally affected by supply voltage changes and the zero drift is very small.

TEMPERATURE DIFFERENCE

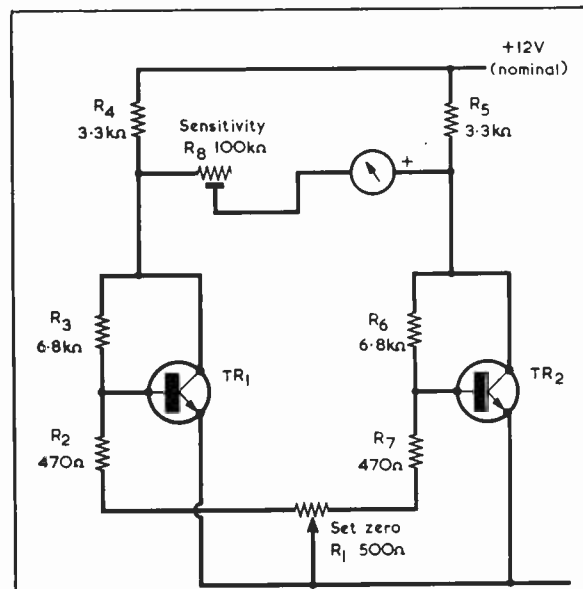However any difference in temperature between the transistors produces a proportional unbalance again of



An electronic differential thermometer which is capable of a high degree of sensitivity. All fixed resistors are $\frac{1}{2}$ watt 5%. The two thermistors are high-gain silicon and should be of the same type with similar characteristics. In use, TR1 is held at the higher temperature

order 20mV/K (that is 20mV/°C by the old convention since the unit of temperature is now called the Kelvin) With a sensitive meter it is quite possible to distinguish an unbalance of this order and temperature differences of a few degrees can be measured with some accuracy provided that adequate calibration can be carried out first. This can be done by immersing the transistors in water at different temperatures determined by conventional thermometers (though care must be taken that the transistors are not immersed for too long). Distilled water is preferable since its low conductivity ensures that if the leads are immersed there is minimum disturbance to the circuit bias levels.


The procedure with the circuit in use is then to adjust the zero control (R1) with the transistors at the same temperature, and the sensitivity control (R8) to give a reading appropriate to the desired full-scale value when the transistors are at a known difference in temperature.

If desired, different values of R8 can be switched in to provide different temperature differential ranges. The zero setting will not remain perfect when the transistors are kept at an equal but much higher temperature than the original calibration point, but the error is small for well-matched transistors – they should be selected if possible for equal Vbe values at equal collector currents and temperature.

The higher sensitivity available with this form of circuit is allied to a further advantage when the thermal properties of power transistors are to be investigated. If one transistor is at ambient temperature, and the other in contact with the power transistor then the temperature rise due to internal heating is directly measurable. The effects of various heat-sinks can thus be readily investigated. It is useful to add a spot of silicone grease to the contact area to aid thermal contact, and care should be taken to minimize curvature of the surfaces in contact. Inevitably some error is introduced if the test procedure (immersion in water) is different from the experimental procedure (surface contact). However the simplicity of the circuit together with its tolerance of supply variation makes it well worth experimenting with. As before the meter sensitivity is not too critical but should be as high as possible with 0–50 μ A the ideal. By increasing the current levels throughout, other meters can be catered for.

This for the time being concludes the look at d.c. applications of the transistor, and next time we shall look at a circuit that has some claims to being the world's simplest amplifier.

HUNDRED YEARS OF TIMEKEEPING TECHNOLOGY

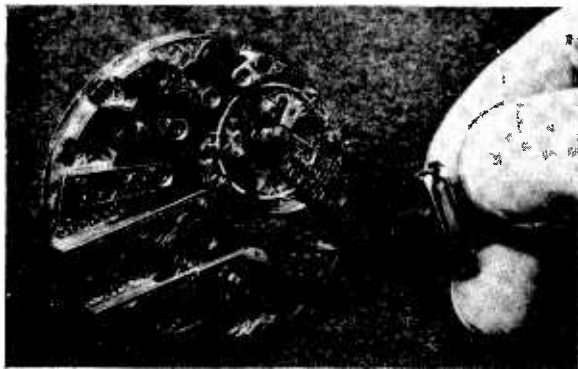

A Geneva lever watch movement contrasted with the smallest 32 kHz quartz watch crystal yet developed.

The Geneva lever movement, from the Science Museum, South Kensington, is approximately one hundred years old. Featuring a club-toothed escape wheel operating at 15,000 beats per hour, it represents the most accurate form of lever escapement, capable of keeping time to within 5 or 10 seconds a day.

The quartz crystal, mounted longitudinally in a cold-welded case measuring 15 x 5 mm, 3 mm high, and developed by ITT Components Group Europe, operates at 32,768 cycles per second. Largely unaffected by temperature changes at normal ambient levels, and resistant to repeated 100 g shocks that would undoubtedly destroy the older mechanism, it is capable of maintaining accuracy to within one minute a year.

NEXT MONTH'S VERY SPECIAL ISSUE.

Our next issue will be the most important one that we have published.

There will be included FREE in each copy a sample Veroboard of 0.15 in matrix having 7 strips by 16 holes. This Veroboard will be suitable for the construction of any of three very attractive projects, all especially designed by our Technical Editor - J. R. Davies.

The projects are - an I.C. AMPLIFIER, a SIGNAL INJECTOR and a RADIO 2 TUNER.

These projects form part of the "exciting plans for the future" mentioned in our July issue. We have not only added "Electronics" to our title, to bring it into line with our contents, but also extra pages - altogether a bumper issue.

There will obviously be a great demand for the SPECIAL OCTOBER issue, to be on sale 2nd October, and supplies will be limited. To make sure of a copy readers are advised to place an order with their news-agent NOW.

BRITISH ASSOCIATION OF RADIO CONTROL SOARERS

The object of the Association is to band together all those with radio control soaring as their prime hobby interest, to co-ordinate the activities of R/C Soarers for their mutual benefit, and to further and protect the interests of the R/C flier.

The Association hope to form a number of Project Groups for work and research on different aspects of the hobby.

Readers interested in Radio Control Flying should write to the Hon. Secretary, B.A.R.C.S., 64 Wellington Road, Hampton Hill, Middlesex, for further details.

LOW COST RADAR BEACON FOR MARINE NAVIGATIONAL BUOYS

Positive identification of marine buoys and markers on a ship's radar screen is made possible with a new pulse-coded radar beacon, or Racon, introduced by EMI. Fitted to a navigational buoy, this solid-state transponder transmits a coded signal which results in an enhanced echo on a ship's radar.

The coded transmission is triggered off by the scanning signals of a ship's radar - these signals being picked up in the Racon by an RF receiver via a slotted wave-guide aerial. Transmitted every 40 seconds, the RF output of the transponder is slowly swept over the marine frequency band with a fast amplitude-modulated waveform superimposed on it to broaden effectively the bandwidth of the ship's radar.

On the ship's PPI display, the beacon's signal pinpoints the position of the navigational marker by appearing as a line of 'dashes' commencing from the buoy's position. This line of radar echoes measures about 3,000 yards long on the PPI range scale and can be identified by the Racon's pre-set code.

Cylindrical in appearance, it weighs about 20 lb. and is 9" high and has a diameter of 8".



RADIO & ELECTRONICS CONSTRUCTOR

COMMENT

SOME SEPTEMBER EVENTS

The Star Short Wave Club of Leeds is again holding a grand junk sale, on behalf of the Radio Amateur Invalid Bedfast Club.

The sale is being held in two parts on 6th September and 27th September at New Inn Hotel, Bramley Town Street, Leeds 13, commencing at 7.30 pm.

Donations of equipment from readers interested in helping this good cause would be gratefully received.

Details from T. Leeman, 115 Asket Drive, Seacroft, Leeds, LS14 1HX.

A scene at a recent sale is shown in the accompanying photograph.

● An International Broadcasting Convention is to be held at Grosvenor House, London, from 4th to 8th September.


● The British Amateur Television Club will hold its 1972 Amateur Television Convention on Saturday 16th September, commencing at 10.30 am and closing at 6.30 pm.

Once again, by kind permission of the I.B.A., the convention will be held at their headquarters - 70 Brompton Road, Knightsbridge, London.

IN BRIEF

● An associate company of L.S.T. Components Ltd., called Arrow Electronics Ltd., has recently been formed to provide a source of guaranteed "mail order" components for the electronics enthusiast. A catalogue with special order forms and pre-addressed envelopes, combined with an easy to use catalogue coding facilitate a rapid component supply service.

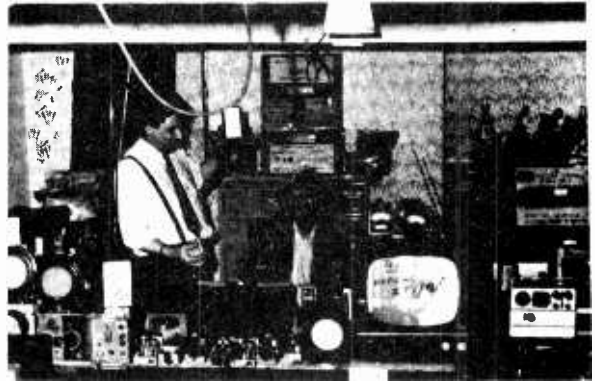The address of the new company is Arrow Electronics Ltd., 7 Coptfold Road, Brentwood, Essex.



● A new side window photomultiplier tube for use in spectrometer applications where wide spectral coverage is necessary, has been introduced by the Electron Tube Division of EMI Electronics Ltd., at Hayes, Middlesex.

● Just published by Jermyn Distribution of Vestry Estate, Sevenoaks, Kent, is a 16 x 24 in. wall chart listing the full range of Raytheon's Linear Integrated Circuits that are available ex-stock.

● SDS Components Ltd., Gunstone Road, Hilsea Trading Estate, Portsmouth, Hants. now despatch all parcels via Securicor to provide a 48-hour delivery service to customers in England, Scotland and Wales.

● Following full stability tests, the Post Office has accepted the Ferranti microwave telecommunications equipment linking the Isles of Scilly with the mainland.

● The 1972/73 edition of its stock catalogue has been published by ITT Electronic Services. Copies may be obtained from them at Edinburgh Way, Harlow, Essex.

GIANT RADIO EAR TO PROBE DEEP SPACE

The present generation of mankind may be able to tune in on intelligent civilisations used in radio-astronomy beyond Earth, if Congress appropriates the money to start building the VLA, America's proposed super-powerful radio observatory. The National Science Foundation, under whose aegis the radiotelescope would be designed and constructed, said that an array of antennas resembling the giant "dishes" used to track spacecraft, would be set up in geometric patterns to pick up and focus signals emanating from the edge of the universe, 13,000 to 16,000 million light years away. The pattern would be an extension of the interferometer technique (placing antennas in a pattern some 24 miles long at least part time, in "passive listening" for radio signals in a high-altitude site in the south-western part of the United States. well away from earth-generated background noise. It is likely that any new very large antenna would be used.

The National Science Foundation, under whose aegis the radiotelescope would be designed and constructed, said that an array of antennas resembling the giant "dishes" used to track spacecraft, would be set up in geometric patterns to pick up and focus signals emanating from the edge of the universe, 13,000 to 16,000 million light years away. The pattern would be an extension of the interferometer technique (placing antennas



He likes to think of all those T.V. Sets flickering out "Normal Service will be resumed as soon as possible."

SHORT WAVE CRYSTAL SETS

by
J. Braunbeck

Our contributor describes a fascinating method of reception which borrows from the early days of radio to open up an entirely new field for the experimenter

BY TRADITION, THE CRYSTAL SET IS A RECEIVER FOR medium and long waves. But there is no technical reason for this limitation and it can only be explained historically.

The long range propagation of short waves had not been discovered until valve receivers were well established, so nobody cared about crystal sets when listening commenced on the short wave bands. The crystal set was considered to be dead, a thing of the past and suitable for the Kensington Science Museum only.

Nevertheless, the crystal set can still have its fascinating side for any amateur constructor who wants to achieve results by investing in a minimum number of components. And what can be more suitable for experiments than a crystal set which lets you listen to stations thousands of miles away? A type of crystal set, it may be added, which was never built in its appropriate period of history.

SHORT WAVE PROPAGATION

Short waves are known to bridge large distances with only moderate transmitter power, and a considerable part of amateur radio activity is based on this fact. But low power amateur transmitters are not the only short wave stations in operation. There also exist quite a number of high powered short wave broadcast stations, whose output may be compared with that of medium wave transmitters. These high power short wave transmitters sometimes produced high field strengths in faraway places. Such field strengths are comparable with those of a local medium or long wave transmitter and are therefore suitable for reception by a crystal set.

CONVENTIONAL CIRCUIT

A crystal set for short waves does not necessarily have to be very different from one intended for medium wave reception. Of course, the tuning coil has to have fewer turns and, in order to obtain optimum results, the aerial has to be matched as accurately as possible to the tuning circuit.

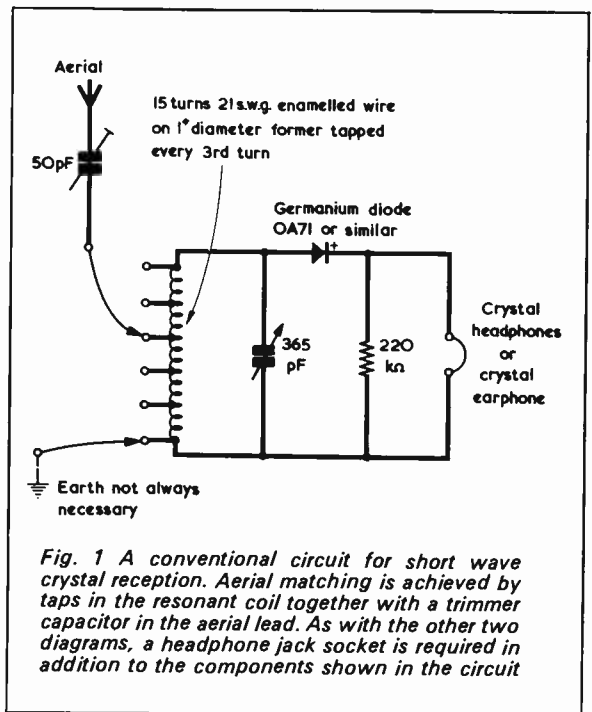


Fig. 1 A conventional circuit for short wave crystal reception. Aerial matching is achieved by taps in the resonant coil together with a trimmer capacitor in the aerial lead. As with the other two diagrams, a headphone jack socket is required in addition to the components shown in the circuit

Fig. 1 shows a working circuit and, here, there are a number of taps on the tuning coil together with a variable capacitor in series with the aerial. The optimum tap for the aerial connection has to be found by trial and error, as also does the best setting of the series aerial capacitor. Both the aerial matching adjustments and the tuning are interdependent since one affects the other, with the result that operating the set tends to become somewhat like a game of skill. One should not, however, complain too much about this. Our fathers or grandfathers had much more trouble in simply looking for a suitable spot on the crystal for the cat's whisker, whereas all we

RADIO & ELECTRONICS CONSTRUCTOR

have to do is to merely solder into circuit a germanium diode. The germanium diode should, incidentally, be a high quality component. It is a good idea to try a few specimens in the circuit, after completion, to find which one gives best results.

The receiver uses either crystal headphones or a crystal earphone. As a crystal phone has almost infinite d.c. resistance, the 220kΩ resistor is included to complete the diode circuit. If this resistor is omitted, strong signals might build up an electric charge across the crystal phone and thereby block the germanium diode.

The aerial should not be too long. About 20 to 30ft. of aerial length will give best results. Though an outdoor aerial is almost always superior in performance, an indoor wire will frequently cope quite well. It is probable that only inhabitants of concrete and steel framed buildings, in which indoor radio reception is generally poor, will be compelled to resort to an outdoor aerial. An earth connection is not always necessary, as the capacitance to earth of the set and the operator may often be sufficient.

AVOIDING AERIAL TROUBLE

Obviously, the main problem in building a short wave crystal set consists of finding the best way of getting the short wave signal out of the aerial and into the tuning circuit. Though this problem can be solved by employing a matching circuit like that shown in Fig. 1, there is an even simpler solution. One gets all the energy from the aerial into the tuning circuit if the aerial is itself made part of the tuning circuit.

This can be done quite easily by making the resonant coil large enough to act as an aerial loop. For the short wave range a single loop of about 2 or 3ft. diameter will have the required inductance. Though it is advantageous to construct a suitable wood or cardboard framework to support the loop, it may also be simply 'laid out' in a makeshift manner. In neither case does it seem to be absolutely necessary for the loop to be circular, and it can even be given a square or rectangular shape.


A means should, however, be provided for rotating the loop, preferably around a vertical axis. If this is done it will be found that the crystal set receives different stations with different loop positions. In order to avoid mechanical construction problems it could be helpful to tape the loop to the surface of a wooden door. Opening and closing the door then effectively rotates the loop.

Fig. 2 shows a short wave set employing a loop and having no aerial matching problems. If the constructor is content to employ the loop laid out in a loose manner the actual set may be made quite small. This version could be particularly suitable for excursions and vacations. Usually, the loop will be indoors, and it should work well in nearly all buildings with the exception of those which are concrete and steel framed. In this latter case it is advisable to place the loop as near as possible to a window or balcony.

An earth connection will not be necessary. On the other hand, it may prove helpful if hand-capacitance effects to the set or to the loop prove troublesome.

RESONANT LINE CIRCUIT

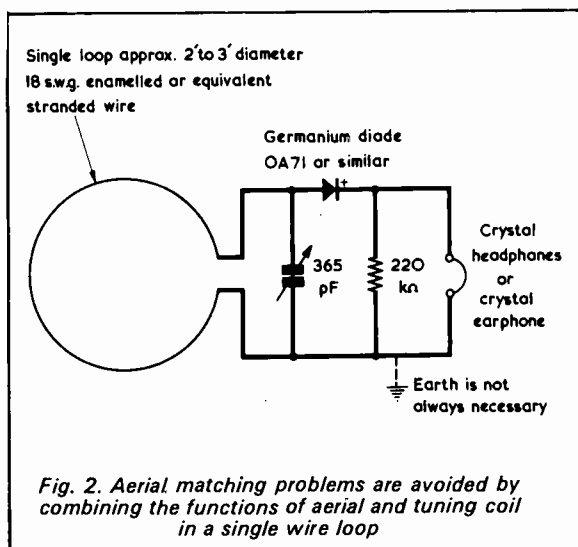There is yet another way to tune the crystal set and provide an aerial for it. Take two parallel wires and short-circuit one end. Across the other end will appear an r.f. voltage if the wires are subjected to an electro-





magnetic wave whose wavelength is four times their length. A quarter wavelength parallel wire system of this nature behaves like a resonant circuit, and is quite often employed as one in ultra high frequency circuits.

Used in the short wave range a parallel wire system is not quite so convenient as it is with higher frequencies, but it can still be made up. The system can be tuned by varying its length mechanically, but a simpler method consists of connecting a variable capacitor across the open end. The circuit shown in Fig. 3 makes use of the latter approach.

The parallel wires can consist of 300Ω flat twin feeder (available from Home Radio under Cat. No. AF5). Though there should not be too many bends in the feeder it does not need to be completely straight. It can, for instance, be fixed on a wall around a few corners. For initial experiments the feeder may be laid out flat on the floor.

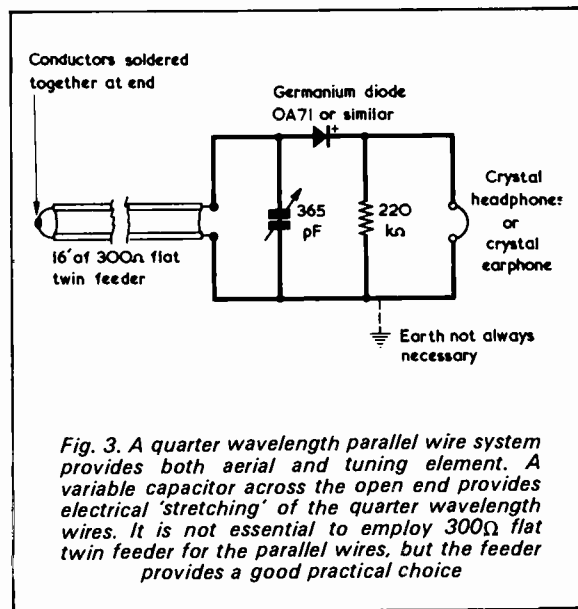The prototype built by the author uses a feeder 16ft. long, which corresponds to a little less than 5 metres.



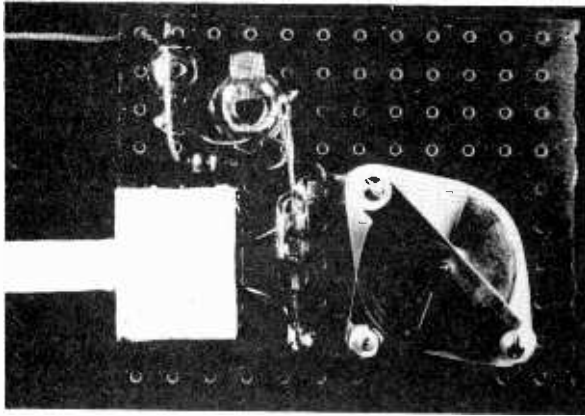

This experimental short wave crystal set is provided with terminals which may be connected to a quarter wavelength wire pair. Though wiring is not critical, all high frequency connections should be as short as possible

Thus, the set is provided with a quarter wavelength parallel wire system for the 20 metre band. However, the variable capacitor electrically 'stretches' the parallel wires, so that wavelengths up to the 31 metre band can be received. Like the other circuits, this set does not need an earth connection, though in some situations such a connection may give an improvement in performance.

The accompanying photograph shows a receiver employing the twin feeder. This couples into the perforated board at the lower left hand side, connecting to a 2-way terminal block and thence to the tuning capacitor. (The exposure, which was made sufficiently long to bring out the darker aspects of the subject, results in both the feeder and terminal block being reproduced as fully white.)

RESULTS TO BE EXPECTED

The propagation of short waves is subject to a number of variable influences and one cannot, therefore, predict what station will produce a fieldstrength suitable for crystal sets at any given place or time. On the other hand there are many short wave stations all over the world, which makes it fairly probable that some stations should be heard at any time. The user of a crystal set is, of course, completely powerless to prevent fading. In spite of these limitations it is still fascinating to listen to voices and music from a few thousands of miles away without any amplifier or energy source.

There are no noticeable differences in sensitivity between the three circuits described here. At the author's home in Vienna, Austria, the 31 metre band transmission from the European Service of the B.B.C. comes in loud and clear nearly every evening. Among other stations received more or less regularly are Tirana (Albania), Ankara (Turkey), Tangier (Morocco), Moscow and Paris. ■

The 8-Watt

Part 2

IN LAST MONTH'S ISSUE WE EXAMINED THE CIRCUIT OF this 8 watt amplifier, then discussed the components. We finished by assembling the chassis and mounting the major parts on it. We now proceed to the wiring.

WIRING-UP

To ease working, the wiring-up steps are numbered. This not only ensures that all connections are made correctly, but it also enables the wiring to be stopped at any time and resumed later. It is merely necessary to complete the step in process, make a note of its number, then start again later at the next step. To ensure that a component lead-out or wire is not connected to a tag that has already been soldered, soldering should only be carried out when expressly stated. This means that, where more than one wire connects to a tag, all the wires are so connected before they are soldered to that tag.

It will have been noticed in last month's issue that the tags of the four 5-way tagstrips are numbered from 1 to 20. This numbering is repeated in the diagrams given this month. A further point is that the four non-earthly tags in each of the Lektrokit 5-way tagstrips have two connection holes, one 'upper' (i.e. further away from the chassis) and one 'lower'. This fact simplifies wiring since it ensures that an excessive number of wires need not be connected at a single tag hole. In the instructions which follow, reference is made to the upper and lower connection holes of these tags. It is assumed in the diagrams that the lower connection hole is on the same side of the tagstrip as the mounting lug and that the upper connection hole is on the opposite side. See the inset in Fig. 7. In practice the upper and lower connection holes are both on the same side of the strip.


Wiring should be carried out with the aid of a small well-tinned electric soldering iron, using radio-type resin-cored solder such as Multicore 'Ersin' or 'Savbit'. On no account should a paste or liquid flux be used.

A few of the component lead-outs require to have sleeving passed over them since they run close to other wires and tags. The instructions state where sleeving is necessary. There should be no need to sleeve the remaining component lead-outs if these are spaced out adequately. All resistor and capacitor lead-outs should be kept reasonably short, cutting off the excess wire as necessary.

'JUBILEE'

Amplifier

by J. R. Davies

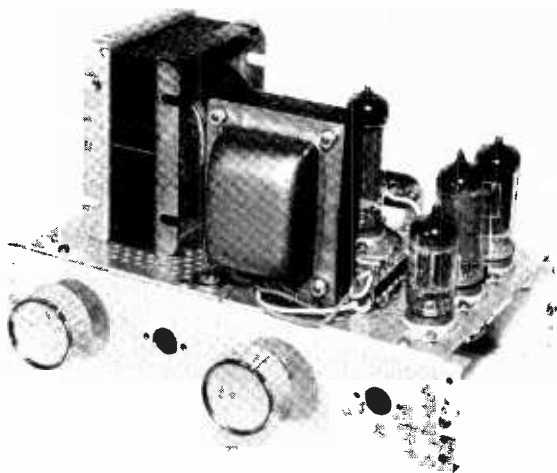

In this concluding article, full details of wiring-up are given, together with test voltages and final constructional information

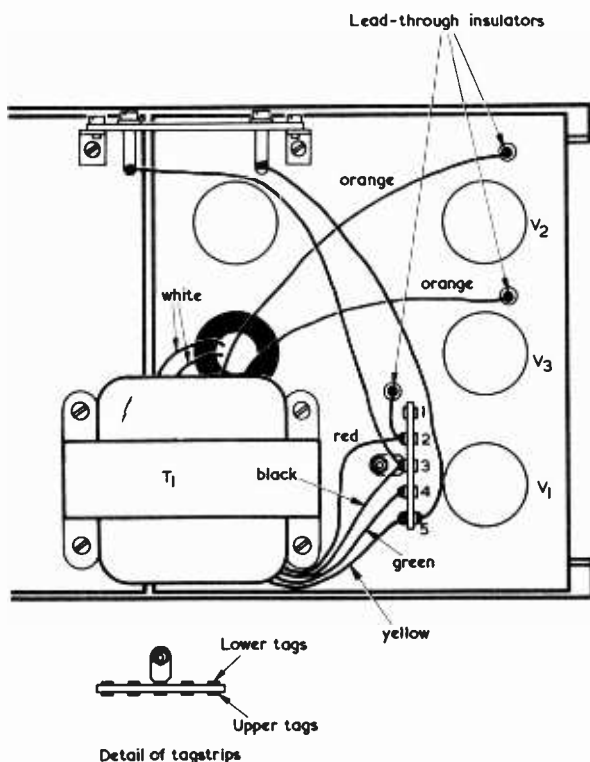


Fig. 7. The output transformer connections above the chassis

OUTPUT TRANSFORMER

We commence at the output transformer.

1. Refer to Fig. 7, which shows output transformer wiring above the chassis. Shortening as necessary, connect the yellow transformer lead to tag 5 (lower) and solder. Similarly shortening, connect the green lead to tag 4 (lower) and solder. Similarly shortening, connect the black lead to tag 3. Similarly shortening, connect the red lead to tag 2 (lower). Connect a wire between tag 2 (lower) and the adjacent lead-through insulator. Solder at the insulator and at tag 2 (lower).

2. Connect a wire between tag 3 and the left-hand tag (left-hand as shown in Fig. 7) of the 2-way terminal strip. Solder at that tag and at tag 3. Connect and solder a wire to the right-hand tag of the 2-way terminal strip. Connect and solder its other end to tag 2 (upper) if a 15Ω output is required, to tag 4 (upper) if an 8Ω output is required, or to tag 5 (upper) if a 2.5Ω output is required. (The 2.5Ω output is satisfactory for a 3Ω speaker). Fig. 7 shows this wire connected to tag 5 (upper).

3. Without shortening, connect the two orange leads to the two remaining lead-through insulators, as illustrated in Fig. 7. Solder at the insulators temporarily only. These two wires may need to be transposed later if it is found that the negative feedback circuit has incorrect phase.

4. The primary of T1 is wound, in practice, in two sections, each with a white lead which connects to h.t. positive. Pass the two white leads from T1 through the ½ in. grommet.

MAINS TRANSFORMER

5. Fig. 6 was published last month to illustrate the correct method of mounting the mains transformer T2. This diagram also gave wiring details and we now return to it. Connect the 'SC' (short for 'screen') tag

25 JUBILEE AMPLIFIER

of T2 to the adjacent chassis solder tag. Solder at the chassis tag. Connect a wire from the 'O' h.t. winding tag between the two '250' tags to the 'SC' tag. Solder at the 'O' h.t. winding tag.

6. Locate the 'O' and '6.3' heater winding tags at the bottom left of the transformer (bottom left as shown in Fig. 6). Connect R17 (220Ω) between the 'O' heater winding tag and the 'SC' tag. Connect R18 (220Ω) between the '6.3' tag and the 'SC' tag. Solder all the connections at the 'SC' tag.

7. The wires next to be added are all routed along the rear of the mains transformer and pass through the 3/4 in. grommet to the chassis underside. Their route is visible in the photograph showing the upper view of the chassis. The wires should be laid along the chassis surface as neatly as possible and they will later be secured in position by a clip. Refer next to Figs. 6 and 8.

Connect a wire 2 ft. long to the 'O' heater winding tag at the transformer bottom left. Solder at the 'O' tag. Connect a second wire 2 ft. long to the adjacent '6.3' heater winding tag. Solder at the '6.3' tag. Run the two wires along the rear of the mains transformer and through the 3/4 in. grommet. On the underside of the chassis the two wires are twisted together, (they need not be twisted above the chassis) and, following the route shown in Fig. 8, pass to V2 valveholder.

Shortening as necessary, connect one wire (it does not matter which) to pin 4 of V2 and the other to pin 5 of V2. Connect two further wires to pins 4 and 5 of V2, and solder at pins 4 and 5.

8. Twist together the two wires from pins 4 and 5 of V2 and, shortening as necessary, connect one of these (it does not matter which) to pin 4 of V3 and the other to pin 5 of V3. Connect two further wires to pins 4 and 5 of V3, and solder at pins 4 and 5.

9. Twist together the two wires from pins 4 and 5 of V3 and, shortening as necessary, connect and solder one of these (it does not matter which) to pin 9 of V1. Shortening as necessary connect the other wire to pin 4 of V1. Join together pins 4 and 5 of V1 with a short length of bare wire. Solder at pins 4 and 5. This now completes the heater wiring for V1, V2 and V3.

10. Returning to Fig. 6, connect and solder two 18 in. lengths of wire to the two '250' h.t. winding tags of the mains transformer. Pass these round the rear of the transformer and through the 3/4 in. grommet. Turn the chassis over and, shortening as necessary, connect and solder one wire (it does not matter which) to pin 1 of V4, and connect and solder the other wire to pin 7 of V4.

11. Turning again to Fig. 6, locate the 'O' and '6.3' heater winding tags at the top right of the mains transformer. Connect and solder two 18 in. wires to these two tags. Pass these wires round the rear of the transformer and through the 3/4 in. grommet. Again turn the chassis over and, shortening as necessary, connect and solder one wire (it does not matter which) to pin 5 of V4. Connect the other wire to pin 4 of V4. Join together pins 3 and 4 of V4 with a short length of bare wire. Connect a wire between pin 3 of V4 and tag 10 (lower). Solder at pins 3 and 4 of V4 and at tag 10 (lower).

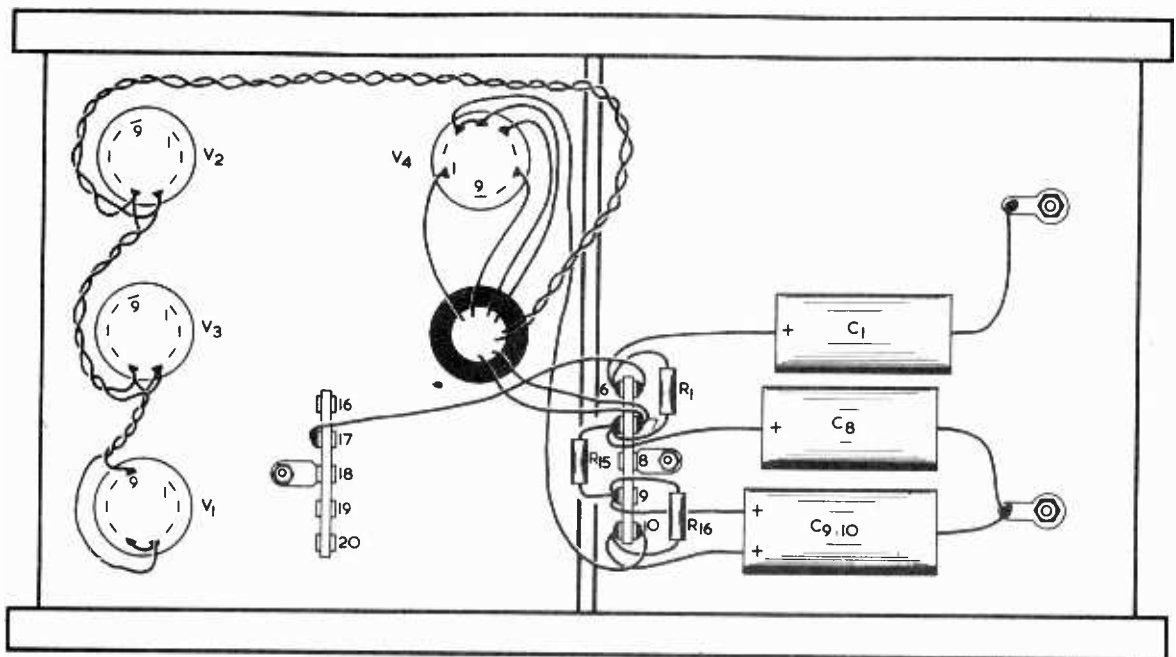


Fig. 8. Heater and power supply wiring

POWER SUPPLY COMPONENTS

12. The connections to T2 secondary are now completed and we proceed next with fitting the power supply components. These are also shown in Fig. 8. Take up the dual electrolytic capacitor C9, C10 (32+32 μ F) and examine its positive lead-outs. If one of these is coded red connect this lead-out to tag 10 (upper) and connect the other positive lead-out to tag 9 (upper). If no colour coding is provided on the capacitor either of the positive lead-outs may connect to tag 10 with the other lead-out connecting to tag 9. Connect R16 (470 Ω 5 watts) between tag 10 (upper) and tag 9 (upper). Solder at tag 10 (upper). Connect the negative lead-out of C9, C10 to the adjacent chassis tag.

13. Shortening as necessary, connect and solder the two white leads from output transformer T1 to tag 7 (lower). (These wires were passed through the $\frac{1}{4}$ in. grommet in Step 4.)

14. Connect the positive lead-out of C8 (50 μ F) to tag 7 (upper). Connect the negative lead-out of C8 to the adjacent chassis tag, as shown in Fig. 8. Solder at the chassis tag. Connect R15 (270 Ω 2 watts) between tag 9 (upper) and tag 7 (upper). Solder at tag 9 (upper).

15. Connect together tag 6 (lower) and tag 17 (lower). Solder at tag 6 (lower). Connect R1 (27k Ω 5%) between tag 7 (upper) and tag 6 (upper). Connect the positive lead-out of C1 (50 μ F) to tag 6 (upper) and its negative lead-out to the adjacent chassis tag, as illustrated in Fig. 8. Solder at tag 6 (upper) and the chassis tag.

SIGNAL WIRING

16. The wiring in Fig. 8 is now complete and we proceed next to the signal wiring shown in Fig. 9. Connect pin 9 of V2 to pin 3 of V2. Connect pin 9

Lead-through insulators


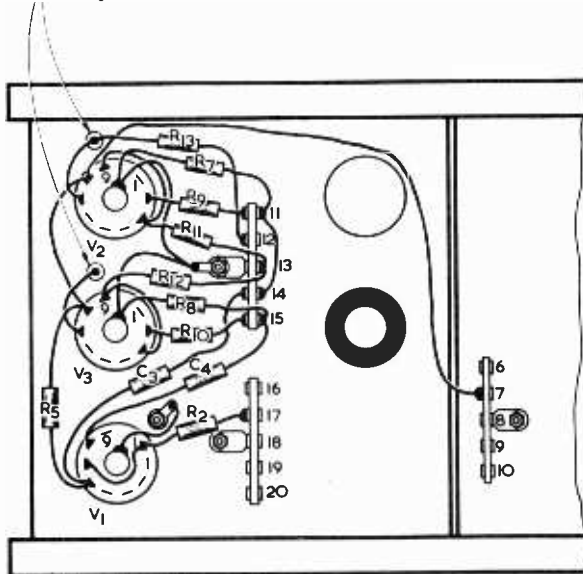


Fig. 9. Initial steps in the signal wiring

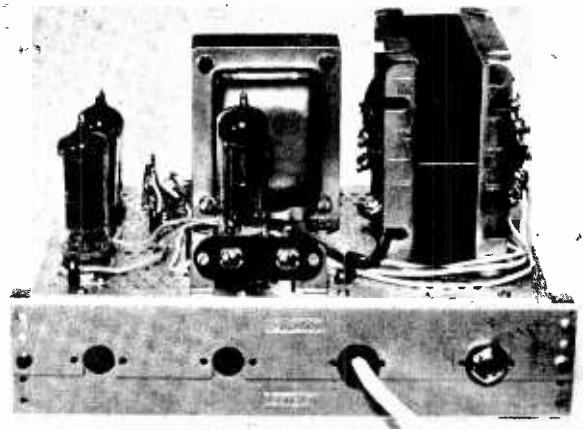

A view of the rear of the amplifier. The speaker terminal strip is in the centre with the rectifier immediately behind

of V3 to pin 3 of V3, soldering at pin 3 of V3. Connect the chassis tag alongside tag 13 to the centre spigot of V2. Connect this same chassis tag to the centre spigot of V3. Solder at the chassis tag. (Some B9A valveholders have a tag between pins 1 and 9 which is integral with the centre spigot and which can take the centre spigot connections. With other B9A valveholders it is necessary to connect directly to the spigot itself.) All the wires fitted in this step should be pressed against the chassis underside so as to leave room for the components which follow.

17. With the wire following the route shown in Fig. 9, connect tag 7 (upper) to pin 8 of V2. Solder at tag 7 (upper). Connect pin 8 of V2 to pin 8 of V3. Solder at pin 8 of V2. Fitting sleeving over its lead-outs connect R5 (27k Ω 2%) between pin 8 of V3 and pin 6 of V1. Solder at pin 8 of V3.

18. Connect pin 7 of V3 to the adjacent lead-through insulator. Solder at pin 7 of V3. Connect pin 7 of V2 to the adjacent lead-through insulator. Solder at pin 7 of V2. Fitting sleeving over the lead-out which connects to tag 12, connect R13 (47k Ω) between the lead-through insulator last dealt with and tag 12 (lower). Solder at the lead-through insulator and at tag 12 (lower).

19. Fitting sleeving over the lead-out which connects to pin 6, connect C3 (0.022 μ F) between pin 6 of V1 and tag 14 (lower). Solder at pin 6 of V1 and tag 14 (lower). Connect R10 (4.7k Ω) between pin 2 of V3 and tag 15 (lower). Solder at pin 2 of V3 and tag 15 (lower).

20. Connect C4 (0.022 μ F) between pin 8 of V1 and tag 15 (upper). Connect R8 (470k Ω) between the centre spigot of V3 and tag 15 (upper). Solder at the centre spigot and at tag 15 (upper). Connect R12 (270 Ω 1 watt) between pin 9 of V3 and tag 13.

21. Connect R9 (4.7k Ω) between pin 2 of V2 and tag 11 (lower). Solder at pin 2 of V2 and tag 11 (lower). Connect R7 (470k Ω) between the centre spigot of V2 and tag 11 (upper). Solder at the centre spigot of V2. Connect tag 11 (upper) to tag 14 (upper). Solder at tag 11 (upper) and tag 14 (upper). Connect R11 (270 Ω 1 watt) between pin 3 of V2 and tag 13. Solder at pin 3 of V2.

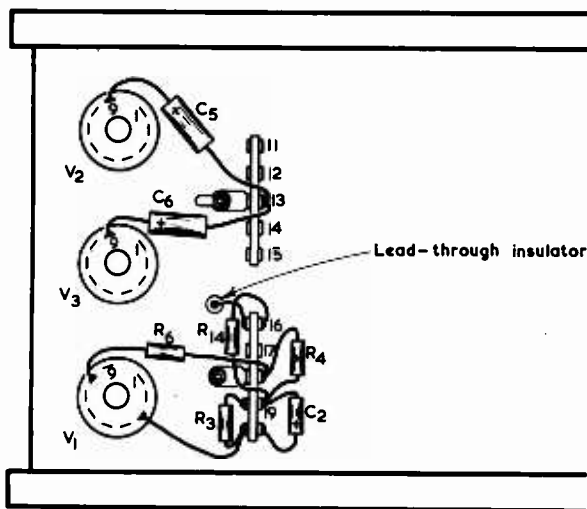


Fig. 10. The components which are fitted prior to the installation of VR2/S1

22. Connect the chassis tag adjacent to V1 to V1 centre spigot. Solder at the chassis tag. Connect pin 1 of V1 to pin 7 of V1. Solder at pin 7 of V1. Connect R2 (100k Ω) between pin 1 of V1 and tag 17 (lower). Solder at pin 1 of V1 and tag 17 (lower).

23. We next turn to Fig. 10. Connect the positive lead-out of C5 (80 μ F) to pin 9 of V2 and the negative lead-out of C5 to tag 13. Solder at pin 9 of V2. Connect the positive lead-out of C6 (80 μ F) to pin 9 of V3 and the negative lead-out of C6 to tag 13. Solder at pin 9 of V3 and at tag 13. Connect the lead-through insulator adjacent to tag 16 to tag 16 (lower). Solder at the insulator and at tag 16 (lower).

24. Connect pin 3 of V1 to tag 20 (lower). Solder at pin 3 of V1. Connect R3 (2.2k Ω) between tag 19 (lower) and tag 20 (lower). Solder at tag 19 (lower)

and at tag 20 (lower). Connect R6 (27k Ω 2%) between pin 8 of V1 and tag 18. Solder at pin 8 of V1. Connect R4 (100 Ω) between tag 18 and tag 19 (upper). Solder at tag 18.

25. Connect R14 (750 Ω) between tag 16 (upper) and tag 19 (upper). Solder at tag 16 (upper). Connect the positive lead-out of C2 (25 μ F) to tag 20 (upper) and the negative lead-out of C2 to tag 19 (upper). Solder at tag 20 (upper). VR2/S1 is fitted in the next Step (see Fig. 11), and C2 should be so positioned that it will not foul this component.


TONE CONTROL CIRCUIT

26. The spindle of VR2/S1 is cut to the desired length and this control is fitted to the front chassis rail assembly at the second hole from the V1 end, as illustrated in Fig. 11. It should be orientated such that its right-hand potentiometer tag (right-hand as shown in Fig. 11) is furthest away from the chassis underside. If it has a locating lug this will need to be bent away or cut off.

27. Connect the lead-through insulator between V2 and V3 to the left-hand tag of VR2, running the wire under the tagstrip with tags 11 to 15, as shown in Fig. 11. Solder at the insulator and at the left-hand tag of VR2. Connect C7 (0.01 μ F) between tag 19 (upper) and the centre tag of VR2. Solder at tag 19 (upper) and the centre tag of VR2. Connect tag 12 (upper) to the right-hand tag of VR2. Solder at tag 12 (upper) and the right-hand tag of VR2.

28. Fit the $\frac{1}{4}$ in. grommet to the rear chassis rail assembly at the third hole from the V2 end. Pass the 3-core mains lead through this and strip off its outer covering. Connect and solder the earth lead (green and yellow) to tag 8 (upper). Connect and solder the live lead (brown) to one of the tags of switch S1. Pass the neutral lead (blue) through the $\frac{1}{4}$ in. grommet and connect it to the 'O' primary tag of mains transformer T2. Fit a plastic clip (Lektrokit Part No. LK2831) over the mains lead and clamp this to the chassis with a 6BA nut and bolt at any convenient

Fig. 11. Adding VR2/S1 and the mains input lead

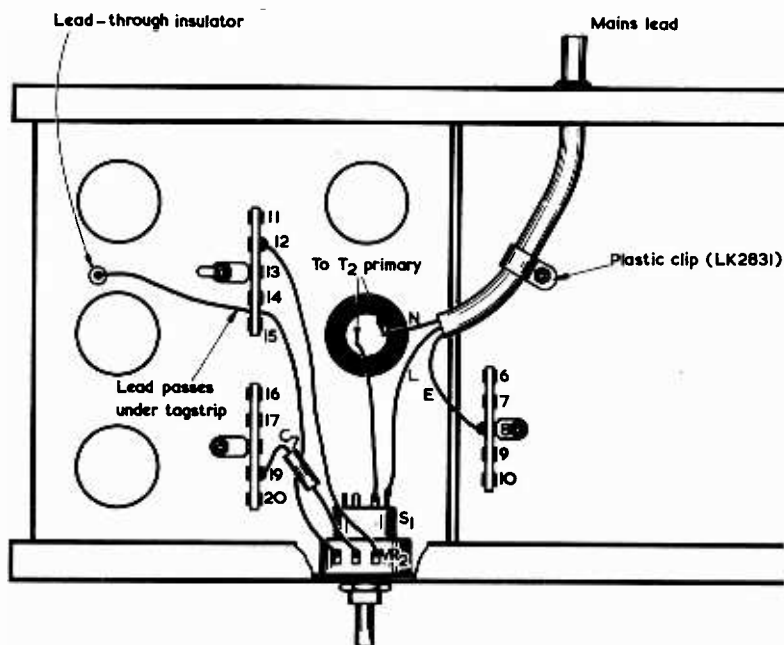

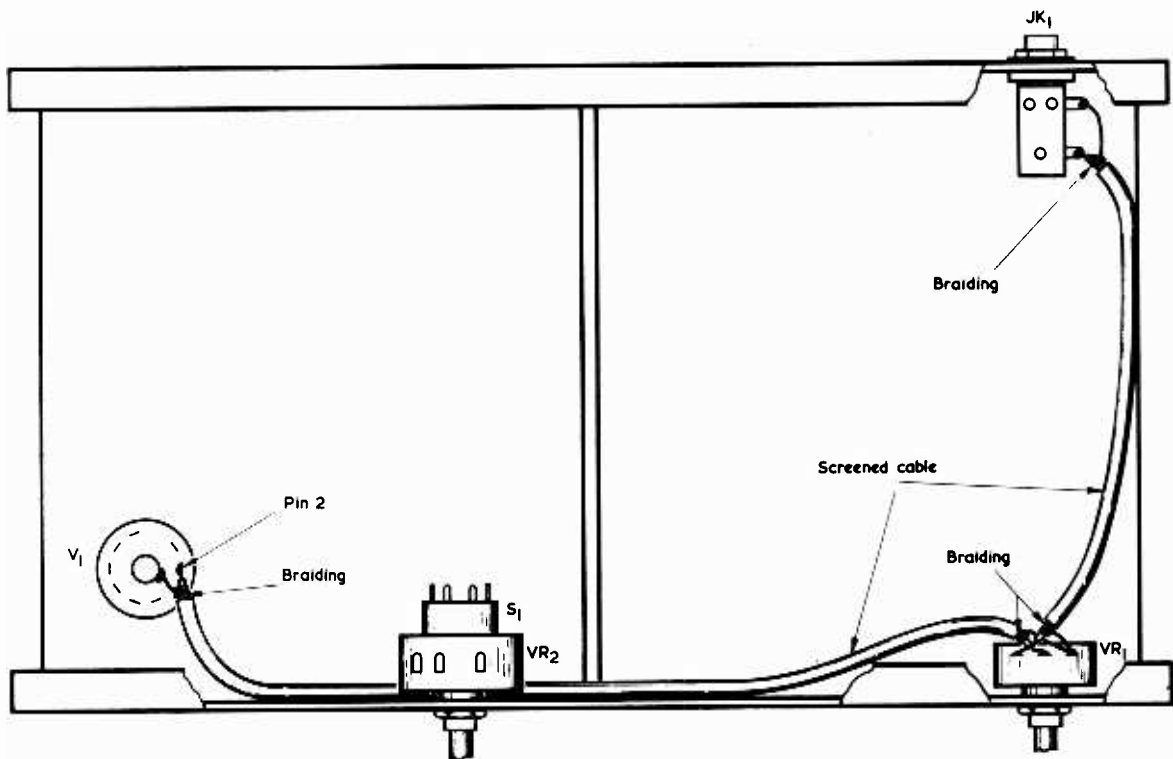


Fig. 12. The final wiring steps involve the fitting of VR1 and the input jack

point near the $\frac{1}{4}$ in. grommet. Solder at the 'O' tag.

29. The positions of the tags on S1 may vary with different makes or models of switch. With the aid of a continuity tester (such as a test-meter switched to an ohms range or a battery and bulb in series) locate the switch tag which corresponds to that to which the live mains lead has just been connected. Connect this tag to either the '200', '230' or '250' primary tag of mains transformer T2, according to the local mains voltage. (For 240 volt mains connect to the '250' tag). Solder at the tag of S2 and the primary tag of T2. Fit a 3-way mains plug at the free end of the mains lead, making certain that the live lead (brown) connects to the live pin, the neutral lead (blue) connects to the neutral pin, and the earth lead (green and yellow) connects to the earth pin.

VOLUME CONTROL CIRCUIT

30. The next components to be fitted are volume control VR1 on the front chassis rail assembly and input jack JK1 on the rear chassis rail assembly. See Fig. 12. The spindle of VR1 should be cut to the desired length before it is mounted, and its tags project away from the chassis underside. Both components are mounted at the chassis rail assembly holes furthest from the V1 end of the chassis. Should it happen that the locating lug of VR1 coincides with the adjacent 6BA clear hole in the chassis rail assembly this factor may be taken advantage of when mounting this component. If not, the locating lug must be bent away or cut off. As was mentioned last month, should JK1

be the jack socket specified a $\frac{3}{8}$ in. washer needs to be fitted under its securing nut to enable it to be properly mounted in the Lektrokit chassis rail hole.

31. Take up the screened cable and strip one end. Connect the braiding to the centre spigot of V1 and the inner conductor to pin 2 of V1. Solder at the centre spigot and at pin 2 of V1. (Soldering at the centre spigot also completes the connection from the adjacent solder tag which was made in Step 22).

32. Pass the screened lead along the chassis under VR2/S1 and, shortening as necessary, connect its inner conductor to the centre tag of VR1 and its braiding to the right-hand tag (right-hand as shown in Fig. 12) of VR1. Solder at the centre tag of VR1. Strip one end of the remaining screened cable and connect its inner conductor to the left-hand tag of VR1 and its braiding to the right-hand tag of VR1. If the potentiometer employed has a metal back which is not, by reason of its construction, common with its mounting bush (and thence with chassis) connect the metal back of VR1 to its right-hand tag. Solder at the left and right-hand tags of VR1 and, where applicable, at its metal back.

33. Run the screened cable just fitted along the chassis underside to input jack JK1. Shortening as necessary, connect its braiding to the tag of JK1 which is nearer the rear chassis rail assembly and connect its inner conductor to the remaining tag of JK1. Solder at both tags of JK1.

34. Fit knobs to VR1 and VR2/S1. Insert a 12AU7 into V1 valveholder, a 6BW6 into V2 valveholder, a 6BW6 into V3 valveholder and an EZ81 into V4

valveholder. Fit a Lektrokit plastic clip (Part No. LK2831) above the chassis over the leads from the $\frac{3}{4}$ in. grommet to T2 primary and secondary tags so that these are kept tidy. The position of the clip may be judged from the photograph showing the top of the chassis. If the 2-way terminal strip has been fitted correctly and its tags soldered neatly, the latter should not interfere with V4. Should this occur, however, the appropriate tag should be bent out of the way.

NEGATIVE FEEDBACK

35. The amplifier is now complete, with the exception of the checking of the negative feedback phasing. Visually examine the wiring that has been carried out and ensure that there is no risk of short-circuits due to stray pieces of wire or 'blobs' of solder. If an ohmmeter is available check for short-circuits between the h.t. positive line (at tag 7) and chassis. The ohmmeter needle will give an initial kick as its test prods are applied due to charging current in the h.t. electrolytic capacitors. Because of these capacitors the ohmmeter will probably give a lower resistance reading when applied with one polarity, than it does when applied with the opposite polarity.

36. Connect a loudspeaker to the amplifier at the terminal strip at the rear and, with VR2/S1 switched off, plug the supply lead into the mains. Switch on and listen carefully. If, after the valves warm up, the amplifier goes into oscillation, switch off *immediately*. The oscillation indicates that the feedback is positive instead of negative, whereupon the orange leads from transformer T1 to the lead-through insulators which were connected in Step 3 have to be changed over. Should these leads have to be changed over, do so with temporary connections and check again. When all is well, the orange leads may be shortened as necessary and soldered permanently to the lead-through insulators. The 'Jubilee' audio amplifier is now complete and ready for use.

FINAL DETAILS

A few final points need to be mentioned before concluding this article.

It will be found that, immediately after switching on the amplifier, a slight hum is audible from the speaker. This reduces to a negligible level when the valves warm up and the negative feedback loop becomes operative. This is the hum which was referred to in last month's issue.

The accompanying Table shows voltages obtained with the prototype, as measured with a 20,000 ohm per volt meter. These readings should be looked upon as offering a guide only. Tolerances in components and valve characteristics, together with other factors, cause the figures in the Table to be approximate only, and small discrepancies encountered in individual amplifiers do not necessarily imply a fault condition.

TABLE
Voltage Readings

All voltages are with respect to chassis

Circuit Location	Chassis Point	Voltage
Cathode V4	Tag 10	270V
Junction R16, R15	Tag 9	230V
Screen-grids V2, V3	Tag 7	210V
Anode V1 (b)	Pin 6, V1	137V
Cathode V1 (b)	Pin 8, V1	73V
Anode V1 (a)	Pin 1, V1	70V
Cathodes V2, V3	Pin 3, V2, V3	11V

No particular precautions need to be observed when employing the amplifier. If housed in a cabinet, holes in the bottom and the back of the latter should be provided for ventilation purposes. The amplifier should not be operated without a loudspeaker connected to it.

(Concluded)

RADIO AMATEUR EXAMINATION COURSES

A course to prepare students for the R.A.E. in May/June 1973 will again be held at the Gosforth Evening Institute, Gosforth Secondary School, Regent Avenue, Gosforth, Northumberland, commencing in September 1972.

Designed specifically for the R.A.E.s, the course is also ideal for anyone wanting to get an insight to radio theory having just taken up radio or electronics generally as a hobby or professionally.

Held on a Tuesday/Wednesday of each week from 7 pm to 9 pm, candidates may sit the R.A.E. at the school.

Enquiries to D. R. Loveday, G3FPE, 5 Carlton Road, Benton, Newcastle-upon-Tyne.

Theory classes for the Radio Amateurs' Examination will be held in the 1972/3 session at Beckenham and Penge Adult Education Centre, 28 Beckenham Road, Beckenham, Kent, commencing Tuesday 19th September at 7.00 pm.

Application for enrolment may be made by post to the Area Office, 244 Croydon Road, Beckenham, Kent, BR3 4DA from 29/8/72.

The lecturer is R. E. Piper, G3MEH.

It is anticipated that an R.A.E. course will be held again at the Birkenhead Technical College, Borough Road, Birkenhead. Classes will be held on Thursday evenings, the lecturer being L. Roberts G3 EGX.

Enquiries to A. Seed G3FOO, 31 Withert Avenue, Bebington, Wirral, Cheshire.

A Radio Amateurs' Examination Course is to be held at the Glasgow College of Nautical Studies, 21 Thistle Street, Glasgow C.5.

The Course will meet at the College on Tuesdays and Thursdays from 7 pm to 9.30 pm commencing Tuesday 12th September 1972. Enrolment will take place at the College at 7 pm on the opening evening, and the fee for the course is £3.00 payable on enrolment. Students under the age of 18 on 1st August, 1972, will not be required to pay a fee.

The Syllabus of the course embraces theory, licence conditions and morse instruction. No prior knowledge is assumed or required.

RADIO & ELECTRONICS CONSTRUCTOR

FREE VEROBOARD IN NEXT MONTHS ISSUE



**LOOK
FOR
THIS
COVER**

**ON SALE
2ND OCTOBER
PRICE 20p**

Copies may also be obtained direct from the Publishers, 26p. including postage. Published by Data Publications Ltd., 57 Maida Vale, London W.9.

**MANY OTHER
ARTICLES –
EXTRA PAGES**

<p>PROJECT 1 SIGNAL INJECTOR</p>	<p>Very suitable for beginners – consists of a wide-band signal injector which is capable of injecting an amplitude modulated signal into any medium and long wave receiver having a ferrite rod aerial – a useful and inexpensive item of test equipment.</p>
<p>PROJECT 2 RADIO 2 TUNER</p>	<p>A fairly complex assembly making full use of the connection points on the Veroboard. A pre-tuned Radio 2 Tuner incorporating two transistors. Current consumption from the 9 volt battery is of the order of 2mA only.</p>
<p>PROJECT 3 INTEGRATED CIRCUIT AMPLIFIER</p>	<p>Designed around the readily available R.C.A. CA3020 i.c., this a.f. amplifier offers a high level of performance and relatively few components are needed – output in excess of 300mW, input impedance 50kΩ.</p>

Make very certain of your copy **ORDER NOW!**

MEASURING SMALL CAPACITORS

by
R. E. Stewart

Ambiguities and errors in the measurement of low-value capacitors can be eradicated by the use of the 'screened' lead technique.

THE MEASUREMENT OF LOW VALUE CAPACITORS, BELOW some 20pF or so, can raise quite a few practical problems. This is because there are stray capacitances between the individual sections of the capacitor and earth and between its two lead-outs. In a small ceramic capacitor having lead-outs spaced by about 8mm., as in Fig. 1, the stray capacitance between the two leads may well be of the order of 0.5pF or more.

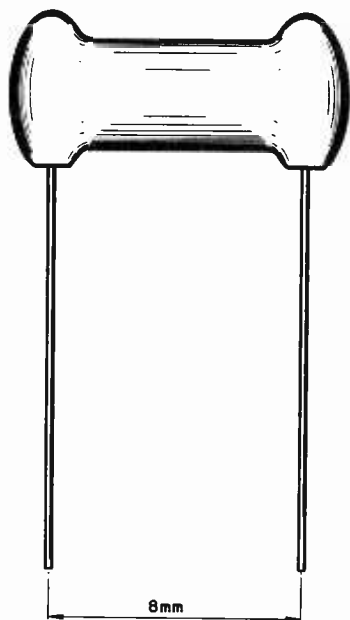


Fig. 1. A typical low value ceramic capacitor with side lead-outs

'SCREENED' LEADS

Difficulties due to stray capacitances are overcome in industry by measuring the capacitance of low value capacitors with the leads 'screened'.

An illustration of the technique is given in Fig. 2, in which a capacitor under test is inserted into a contact jig. Note that each capacitor lead passes down a metal channel and that a springy leaf contact bears against it. The jig is constructed such that the spacing between the entry points for the capacitor leads is equal to the lead-out spacing.


The jig is employed in the following manner. First of all the capacitance between the two sections of the jig is measured without a capacitor inserted. The capacitor to be measured is next inserted and the new capacitance measured. The *difference* between the two readings is then calculated and this is stated to be the value of the capacitor. Thus, if the capacitance in the jig before the capacitor is inserted is 3.6pF, and this increases to 7.4pF when the capacitor is inserted, the value of the capacitor is 7.4 minus 3.6pF, or 3.8pF.

This approach is employed at capacitor factories and it will be noted that it measures the capacitance within the body of the capacitor only. Whatever additional capacitance is added by the lead-outs and by stray capacitances to earth cannot then affect the capacitance figure given, and the method enables the capacitor manufacturer to produce low value capacitors without subsequent arguments with his customers about their values. If the manufacturer's customers choose to change the capacitance by connecting his wares into circuit with long leads positioned close together, or by mounting the capacitor bodies close to a metal chassis, he can hardly then be blamed for an apparent shift in value.

The technique shown in Fig. 2 is often referred to as capacitor measurement with the lead-outs 'screened'. The term is understandable since the jig screens the lead-outs from each other and also from earth.

RADIO & ELECTRONICS CONSTRUCTOR

Fig. 2. An example of a capacitance measuring contact jig. Part of the right hand contact assembly is shown cut away to illustrate the construction

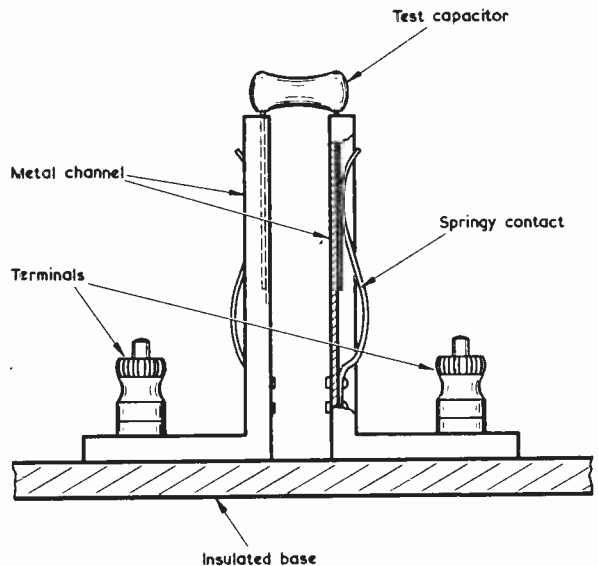

It is easy to make up a single 'screened' lead contact jig which will give results that are quite adequate for the amateur workshop or small laboratory, and a suitable method of construction is shown in Fig. 3(a). The jig consists of two hollow metal cylinders some

hand. The capacitor leads are simply inserted down the central holes in the cylinders as in Fig. 3(b) whereupon, if the leads are sufficiently clean, adequate contact is given to the two cylinders to enable a capacitance measurement to be obtained.

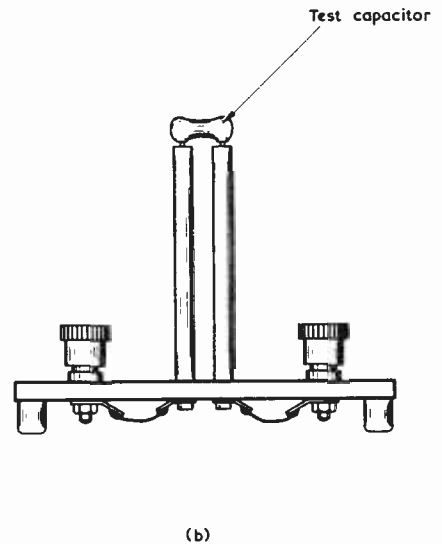
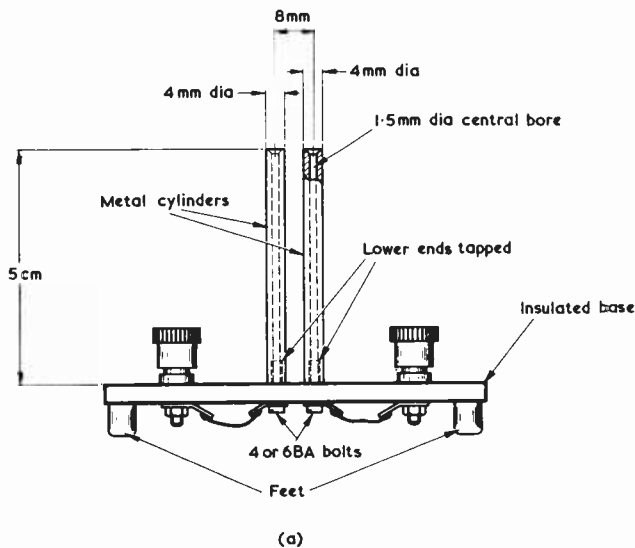


Fig. 3(a). A simple capacitance measurement jig with tentative dimensions


(b) The measurement jig in use. The value of the capacitor is the capacitance of the jig with the capacitor inserted minus the self-capacitance of the jig on its own

5cm. long mounted vertically on a small base made of insulating material such as Paxolin or Perspex. The cylinders are tapped centrally at their base and are secured with 6BA or 4BA screws, as convenient. Two leads soldered to tags mounted under the screw heads connect the cylinders to two large terminals for ease of connection to the capacitance meter. The dimensions given in Fig. 3(a) are tentative only and may be varied slightly to suit whatever material happens to be on

SEPT

The two cylinders can consist of brass turned on a lathe. However, it is more than probable that a well-stocked junk-box will yield a source of metal tubing, or similar, which can be pressed into service without the necessity of extensive metal-work. The metal of which the cylinders are made is unimportant provided that it has a surface which does not tarnish or oxidise readily, since it would then offer poor contact to the capacitor leads.

'METHOKLONE' S A NEW SOLVENT FROM ICI

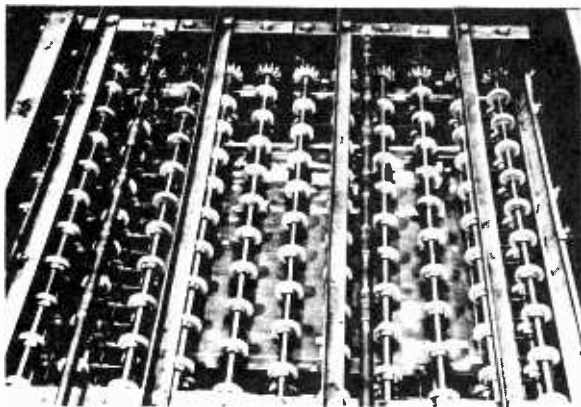

ICI Mond Division is marketing a new solvent - 'Methoklone' S - a specially formulated product designed for many cleaning applications, particularly in the manufacture of printed circuit boards, where there is need for a powerful solvent to remove resists. The use of photo-sensitive resists, especially the newer, dry film resists, demands a solvent capable of removing the polymerised product and 'Methoklone' S is ideal for this purpose.

The new solvent has a low boiling point, is non-flammable and has high solvent power.

'Methoklone' S will also remove decorative metal after etching; protective lacquer from electric motors and electric components; printing ink from printing machinery components; pitches and waxes from semi-conductors etc. For further information write to: Imperial Chemical Industries Ltd., Thames House North, Millbank, SW1.

AUSTEN SOLDERMASTER MK V

Charles Austen Pumps Limited who introduced their Soldermaster desoldering tool for removing faulty multi pin components from boards and for salvaging reusable components from faulty assemblies at a time when multi pin components were first being introduced in electronic circuits, have developed a new unit, the Soldermaster Mk. V; this meets the requirements of Companies who favour the use of temperature controlled irons for use on the latest type of microminiature multi pin components and boards.

A Weller 100 watt temperature controlled iron has been adapted for use with the new unit. It is fitted with a solder catch pot and an interchangeable hollow bit through which the operator may apply a vacuum. An Austen Capex Mk. II diaphragm pump driven by a shaded pole motor provides the vacuum source, it is mounted on a bakelite base fitted with a carrying handle and an iron rest. The noise level of the pump has been reduced to a minimum by fitting a polypropylene expansion chamber. The pump is


protected from resin fumes by a cleanable microfilter.

Six bits are supplied with the standard unit, the bit holder being designed to facilitate quick interchange. The Weller temperature controlled iron, while safeguarding components and boards by preventing excessive bit temperature rise, reduces bit erosion and gives much faster temperature recovery when used continually for desoldering.

The bit sizes range from 0.078" to 0.125" outside diameter and are suitable for component pins of 0.020" to 0.063" diameter. A moulding which holds the complete range of bits is incorporated in the instrument.


The Soldermaster Mk. V is a compact unit weighing only 6½ lbs. and measuring 7½" x 6" x 6" high.

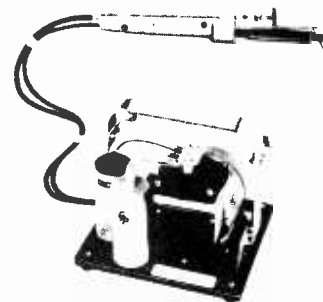Full details are available from Charles Austen Pumps Ltd., 100 Royston Road, Byfleet, Surrey.



VERO ELECTRONICS INTRODUCE VEROBXES

Vero Electronics announce the introduction of a new range of extruded aluminium enclosures to be sold under the name of Veroboxes (R). These consist of a range of eight different stock sizes of extruded boxes. The boxes are made up of combinations of two types of extrusion 50 mm wide which slot together. The precision joints tighten under stress and are rigidly secured when the cover plate screws are fitted. Finned sides act as an effective heat radiating surface. Two .15 mm slots are provided on the inside face of each extrusion to accommodate either printed circuit cards or metal deck plates. They are supplied in kit form for ease of storage and despatch. Details from: Vero Electronics Ltd., Industrial Estate, Chandlers Ford, Hampshire. SO5 3ZR.

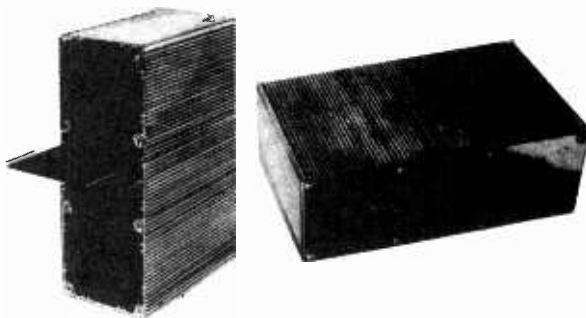

RADIO & ELECTRONICS CONSTRUCTOR



Q S X

by

Frank A. Baldwin

(All Times GMT)

In the opening paragraphs of this feature in the July issue, the subject of unidentified stations was briefly discussed and in particular, two such stations were mentioned, these being Kuwait on **4968** and Tananarive on **4985**. Neither of these however were positive identifications, it merely being suggested that the times quoted, the languages used and the programme contents, could possibly fit Kuwait and Tananarive. Since then other observations have been made by various operators with the results recounted below.

Dealing with the frequency, transmissions in Arabic were heard both by the writer and two other operators during early May but later in the same month, just 1kHz away – on **4967** – a transmission in Portuguese turned out to be CR6RE Radio Clube de Malange, Angola. Three enthusiasts, operating independently, logged the Angolan, in one case part of the station identification being heard.

What are we to make of all this? The ability of the operators is undoubted, their reputes beyond question, all being seasoned SWL's of long standing. The answer is probably that they were all correct and that Kuwait did in fact briefly return to an old channel for some unknown (to the writer) purpose. The Arabic language is not used by Angolan stations but is one that is instantly recognisable by two of the operators who identified the language as such – each having lived in the Arabic world for a period of time. The Portuguese language is also easily recognisable to broadcast band enthusiasts of long-standing, undoubtedly therefore CR6RE was heard. Times and conditions could also however play a part in all this, as seasoned SWL's are well aware. It is quite possible to hear one station without any trace of the other.

What of the second channel, that of **4985**? Well, a similar situation exists. Since the tentative suggestion

that Tananarive was the station heard, and that the unknown language used was Malgache following the news in French, other operators have identified the Portuguese language – this suggesting that the transmitter could be CR6RB Radio Ecclesia, Angola. Perhaps again all are right, varying conditions allowing each station to be heard at slightly differing times on separate days.

If you, the reader, care to join in the fun, keep an open mind and ear and tune to **4968** from around 1930 to 2130, remembering to vary to **4967** from time to time. Also tune to **4985** from around 1930 through to 2200, braving the late-summer static and the commercial QRM at the same time!

● UNUSUAL LOGGING

Turning to another matter, reader H. Green of Brixham, Devon, tells me that he has regularly logged VNG on **12000** at good signal strengths every morning over the past two years from 0600 to 0800, the station expressing appreciation of his reports and tape recordings, replying with a QSL card. Some interference is experienced to the signals of VNG from a USSR station at 0625. But HG does not end there, he goes on to inform me that the **7500** VNG signals are also regularly noted in the mornings but that the signals are very much weaker than those of **12000**. Even this however is not the end of H. Green and his sterling efforts. His definition of a 'realistic' unusual logging is VNG on **4500** from between 1900 and 2000, frequently in company with a transmission emanating from China. Additionally, he has also noted Sydney Airport Tower giving forecasts on weather and visibility for various Australian airfields on **10010**. Considering HG 'uses' an ancient valve type receiver" which originally cost 50p, but which has since been 'put right', it says a lot for his ability as an operator. Let us hear from you again HG.

The only unusual logging we can offer this time is the reception of Phnom-Penh, Kmere Republic, at 0250 on a measured **4908**. Unusual in the fact that (a) signals were like those of a local station (SINPO 44444) and (b) we were awake! The programme consisted of the usual chants, local music and the clashing of gongs, drum beats and tinkling bells.

● LATIN AMERICA

A couple of early morning sessions

on the 60m band produced the usual Venezuelans and a few others but nothing spectacular – we must have chosen the wrong mornings! In any event, general observations point to the fact that the LA's have not been coming through so well this year coupled with the fact that the noise level has been higher than ever. However, we did log the following –

- 4760 0310** YVPP Radio Frontera, San Antonio, Venezuela, with the usual LA songs and music. Schedule 1000 to 0400, 2kW.
- 4830 0305** YVOA Radio Tachira, San Cristobal, announcements and identification in Spanish. Schedule 1000 to 0400, 1kW.
- 4860 0303** YVQE Radio Maracaibo, LA music and commercials. Schedule 0900 to 0400, 10kW.
- 4865 0259** PRC5 Radio Clube do Para, Belem, Brazil, LA music and closing at 0300. Schedule 0900 to 0300, 2kW.
- 4870 0257** YVKP Radio Tropical, Caracas, commercials in Spanish. Schedule 1000 to 0400, 5kW.
- 4900 0243** Radio Juventud, Barquisimeto, usual LA mx. Schedule 1000 to 0400, 10kW.
- 4940 0252** YVPA Radio Yaracay, San Felipe, LA mx and songs. Schedule 1000 to 0400, 10kW.
- 4945 0255** HJDH Radio Colosal, Neiva, Colombia, talk in Spanish. Schedule 24 hours, 2.5kW.
- 4960 0240** YVOA Radio Sucre, Cumana, LA music. Schedule 1000 to 0430 1kW.
- 4990 0237** Radio Barquisimeto, distinctive LA guitar music. Schedule 1000 to 0400, 15kW.
- 5030 0235** YVKM Radio Continente, Caracas, LA music. Schedule 0900 to 0400, 10kW.
- 5055 2310** ZYX24 Radio Cultural de Cuiaba, Brazil, announcements in Portuguese and LA music.
- 15115 0220** HCJB Quito, Ecuador, in English to USA and in parallel on **9605** and **11745**.

A. F. SIGNAL



Cover Feature


R. A.

THIS INSTRUMENT PROVIDES HIGH QUALITY SINE AND square waves from 15Hz to 150kHz over four switched ranges. These ranges are listed in the Table.

The instrument is completely self-contained, power being provided by an internal 9 volt battery. Current consumption from this battery is approximately 6mA for sine wave output, and 8mA for square wave output.

The maximum sine wave output is approximately 500 mV r.m.s., and the maximum square wave output is 5V peak-to-peak. The overall dimensions of the prototype are only 6 by 4 by 2½ in.

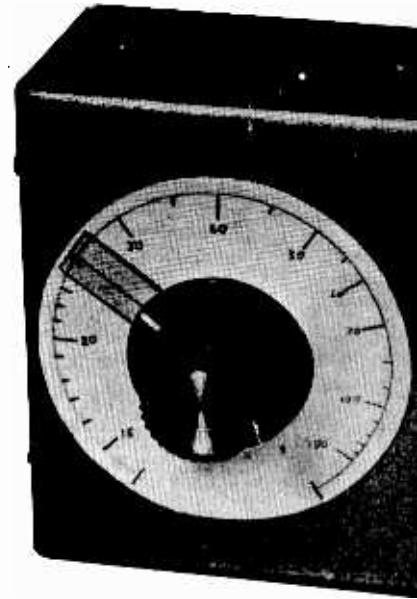The generator is suitable for making nearly all types of test on audio equipment, such as checking for distortion with the sine wave output, and for transient response with the square wave output. Five silicon transistors are used in the circuit, which has been kept as simple as possible.



THE WIEN BRIDGE NETWORK

Fig. 1 shows the theoretical circuit of a Wien Bridge network. This is a frequency selective network which gives a valley-type response curve. When R1 is equal to R4 and C1 is equal to C2, as is usually the case in practical versions of the bridge, the frequency of operation can be found from the equation

$$f_o = \frac{1}{2\pi R_1 C_1}$$

The circuit is really a phase shift network, having zero degrees phase shift at the frequency of operation.

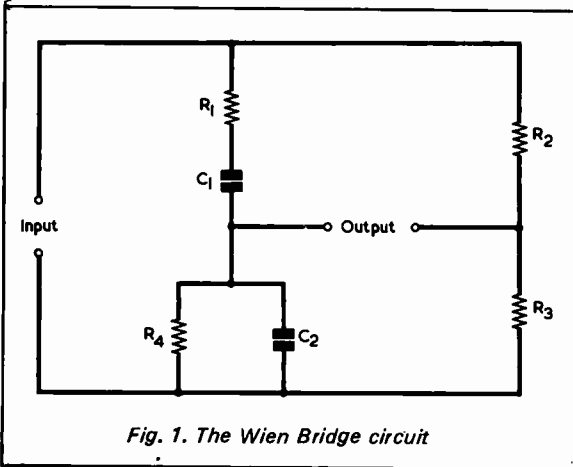


Fig. 1. The Wien Bridge circuit

Range (SI position)	TA
1	
2	
3	
4	

This generator offers both sine covers 15Hz to 15

GENERATOR



ifold



E

frequency coverage

Hz	- 150Hz
kHz	- 1.5kHz
5kHz	- 15kHz
50kHz	- 150kHz

and square wave outputs and it kHz in four ranges

Therefore, if we connect this network between the input and the output of an amplifier which has its input and output signals in phase, and providing the gain of the overall circuit is at least unity, it will oscillate at the operating frequency of the Wien Bridge network. The amplifier need have a gain of only 3 to compensate for losses in the Wien Bridge network, and thus give an overall gain of unity.

The output of the oscillator will not be the required sine wave unless the gain of the overall circuit is maintained at exactly unity. There is then only sufficient gain for the circuit to oscillate at the frequency of the response peak, and at no other, and thus an almost pure sine wave is produced.

The skeleton circuit of a simple Wien Bridge oscillator is shown in Fig. 2. As the input to the amplifier is at a relatively high impedance, resistors R2 and R3 of Fig. 1 are not required in the circuit. The network output is taken from across R4 and C2.

Since the amplifier needs a gain of only 3, a considerable amount of negative feedback can be used to give the circuit a wide bandwidth and low distortion. The feedback is given by taking the collector load of TR2 to the emitter circuit of TR1. Direct coupling is used in order to obtain the best possible frequency response. Feedback is also applied via the variable resistor, this being adjusted to give exactly unity gain.

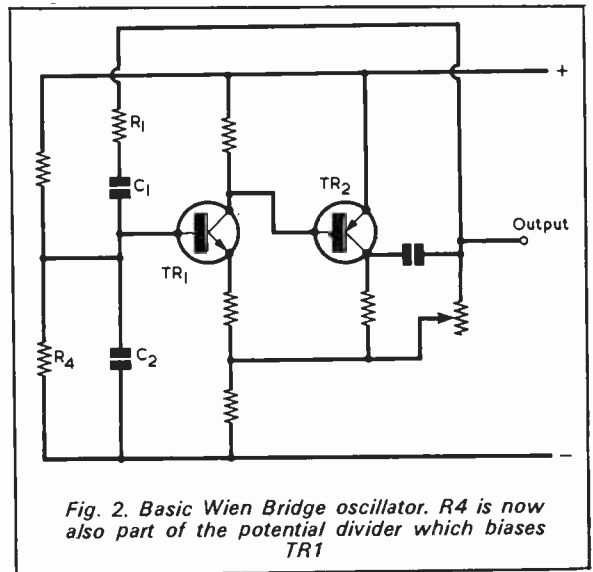


Fig. 2. Basic Wien Bridge oscillator. R4 is now also part of the potential divider which biases TR1

THE CIRCUIT

The circuit diagram of the complete signal generator is given in Fig. 3. Here, TR1, TR2 and TR3 form the Wien Bridge oscillator. This differs from the simplified version shown in Fig. 2 in three ways.

First, the two resistors of the Wien Bridge network have been replaced by a dual-gang variable resistor, VR1,2. This is capable of varying the operating frequency of the unit over the range selected. Second, the two capacitors in the network have been replaced by C1 to C8, any two of these being switched into circuit by the range switch, S1(a)(b). This gives the unit its four frequency ranges. Third, an emitter follower, TR3, has been added at the output of the circuit, to give a much lower output impedance. The variable resistor of Fig. 2 now appears as VR3 and couples to the emitter of TR3 and not, as occurred previously, to the collector of TR2.


The emitter load for TR3 is the potentiometer VR4. This control gives a linear variation, enabling the output to be varied from zero to maximum.

The output from the Wien Bridge oscillator is next taken, via S2(c) in position 2, to the simple step attenuator given by R9, R10 and R11, and thence, by way of S3, to the output socket. Alternatively the output may be taken, by S2(d) in position 3, to the squaring circuit given by TR4 and TR5. In the first of these two instances, the sine wave outputs selected by S3, with VR4 at maximum, are approximately 500mV, 50mV and 5mV r.m.s.

For optimum accuracy in terms of frequency C1 to C8 inclusive should be close tolerance components. Non-electrolytic capacitors to the values required are available in 1% tolerance from Home Radio under Cat. Nos. 2FG25 (1,000pF), 2FG29 (0.01μF), 2FG33 (0.1μF) and 2FG37 (1μF). The 1μF value is also available, in tolerances of 5%, 2% and 1%, from V. Attwood, P.O. Box 8, Alresford, Hants. Capacitors having wider tolerances may be used at the expense of accuracy of frequency.

SQUARE WAVE

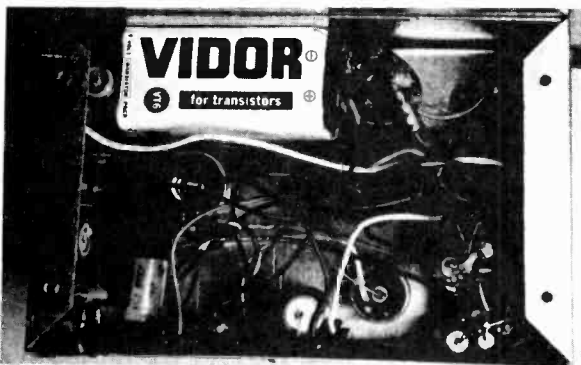There are two basic methods of obtaining a square wave from a sine wave. One method is to generate a sine wave having a very high voltage amplitude and to feed this into a clipping circuit. The other approach consists of applying the sine wave to a Schmitt trigger, and that is the method used here.



A view inside the case of the generator

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5%)

R1	3.3kΩ
R2	1kΩ
R3	680Ω
R4	4.7kΩ
R5	1.5kΩ
R6	150Ω
R7	5.6kΩ
R8	100Ω
R9	6.2kΩ
R10	620Ω
R11	68Ω
R12	8.2kΩ
R13	3.3kΩ
R14	18kΩ
R15	15kΩ
R16	1.2kΩ
R17	560Ω
VR1,2	10kΩ + 10kΩ dual gang potentiometer, linear.
VR3	25kΩ potentiometer, linear
VR4	1kΩ potentiometer, linear.
VR5	50kΩ preset potentiometer, skeleton

Capacitors

(C1-C8 close tolerance - see text)

C1	1μF
C2	0.1μF
C3	0.01μF
C4	1,000pF
C5	1μF
C6	0.1μF
C7	0.01μF
C8	1,000pF
C9	100μF electrolytic, 10 V. Wkg.
C10	400μF electrolytic, 10 V. Wkg.
C11	100μF electrolytic, 6.4 V. Wkg.
C12	25μF electrolytic, 10 V. Wkg.
C13	150pF disc ceramic
C14	100μF electrolytic, 10 V. Wkg.

Transistors

TR1	BC171
TR2	2N3702
TR3	BC113
TR4	2N2926 Yellow
TR5	2N2926 Yellow

Switches

S1	3-pole 4-way, miniature rotary (see text)
S2	4-pole 3-way, miniature rotary.
S3	4-pole 3-way, miniature rotary (see text)

Battery

B1	9-volt battery type PP6 (Ever Ready)
----	--------------------------------------

Miscellaneous

- 1 large knob
- 5 small knobs
- 1 coaxial socket
- Battery clips
- Paxolin for component boards
- Aluminium for case
- Nuts, bolts, etc.

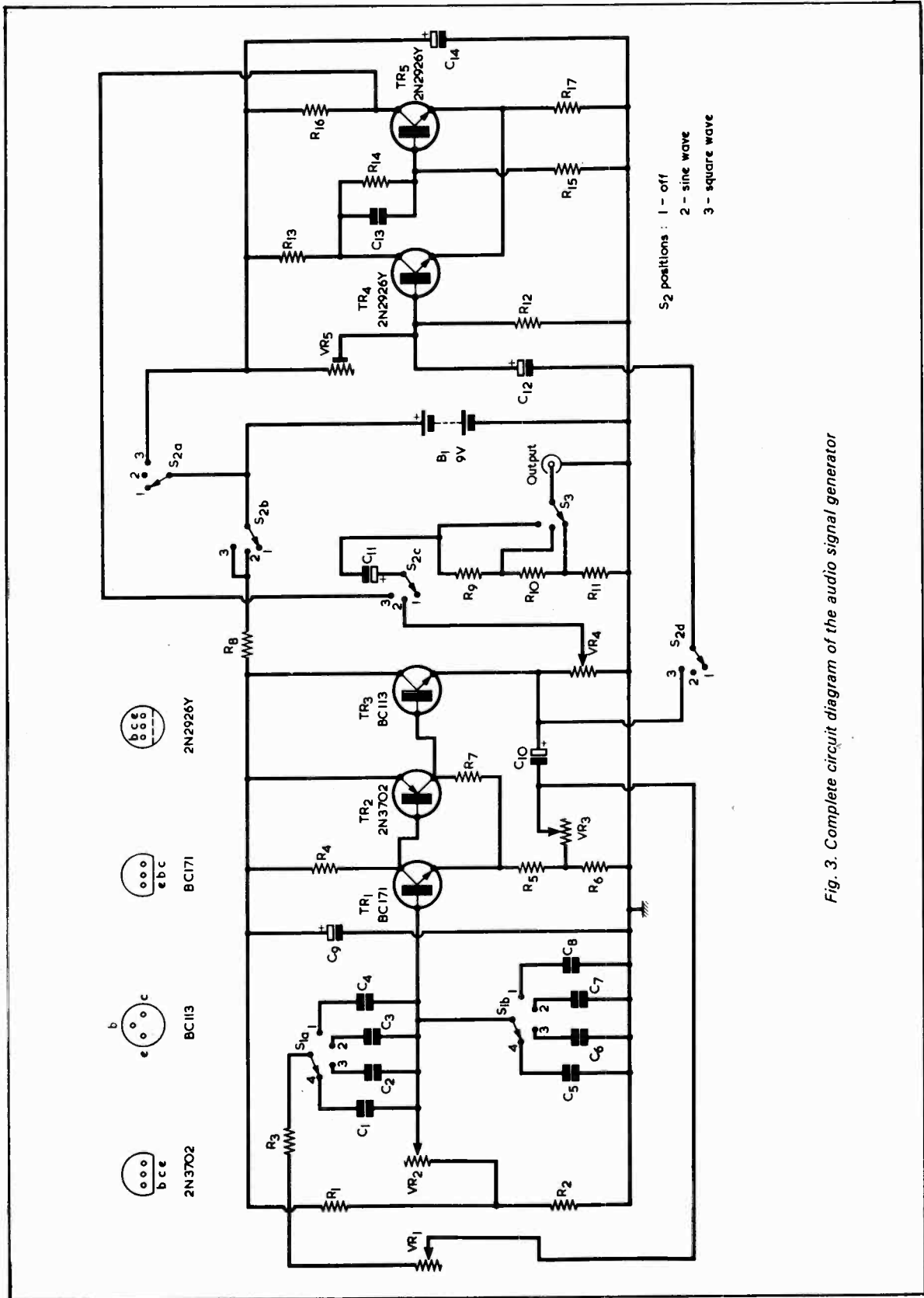


Fig. 3. Complete circuit diagram of the audio signal generator

TR4 and TR5 appear in the Schmitt trigger circuit. VR5 is adjusted such that TR4 is normally off and TR5 is normally on. When a negative-going half-cycle from the Wien Bridge oscillator is applied at the input, i.e. the base of TR4, there is no effect in the circuit since TR4 is already turned off. As soon as a positive-going half-cycle commences, however, TR4 begins to turn on and TR5 to turn off. A regenerative action then takes place, causing TR4 to turn hard on very quickly and TR5 to quickly turn off.


VR5 is adjusted to give a biasing current to TR4 which is just below the point at which, without an input, the regenerative action occurs. Thus, the positive-going half-cycle will have only just commenced when the circuit becomes triggered, causing the voltage at TR5 collector to suddenly swing much higher. TR5 collector will remain at this high level until the input voltage at TR4 base falls to nearly zero, whereupon the Schmitt trigger will return to its original condition and the voltage at TR5 collector will quickly return to its previous value.

An almost square wave is thus produced at TR5 collector. Capacitor C13 is included between TR4 and TR5 to improve the wave shape at high frequencies.

The output of the squaring circuit is taken from TR5 collector and is passed, when S2(c) is in position 3, to the attenuator given by R9, R10 and R11. There is no continuously variable output control for square waves, and S3 selects outputs of approximately 5V, 500mV and 50mV peak-to-peak.

THE CASE

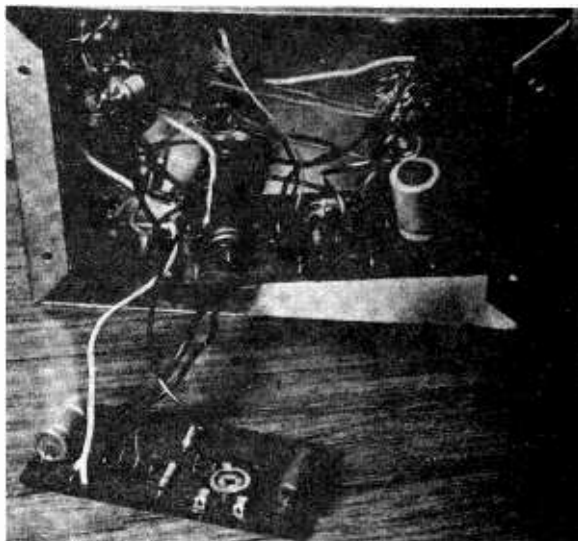The prototype signal generator is housed in a home-made aluminium case measuring 6 by 4 by 2in. This is constructed from 18 or 20 s.w.g. sheet aluminium and details are given in Fig. 4. Readers should not have



Here, the two component boards are removed from their positions to enable their assembly to be seen more clearly

difficulty in fitting the components in this housing but it must be stressed that they need to be small or miniature. Ensure that there will be room for the PP6 battery under VR1,2, and if necessary slightly reposition the hole for this component. The spacing between the mounting holes for S1 and S2 is only 1¼in., but this should just comfortably allow two miniature rotary switches to be mounted side by side. The single potentiometers, VR3 and VR4, should be small types with a body diameter of about ⅝in. or less. Capacitor C14 needs to be a reasonably small component also, as it will otherwise not be possible to fit the battery.

Once the aluminium sections illustrated in Fig. 4 have been cut out, all the holes shown in this diagram should be drilled before any bending is carried out. The way in which the parts of the case fit together can be ascertained from Fig. 4, since the two holes marked '1' fit together, as do the two holes marked '2', those marked '3', and so on. Note that, in the diagram, what will eventually be the rear ends of the two sides are shown towards the front panel. All the flanges are ½in. wide and the positions of flange holes can be adjusted from the one which is shown dimensioned in the diagram. Thus, hole '6' is ⅜in. from the side edge. Holes '5', '7' and '8' are similarly dimensioned. Holes '1' to '4' are 6BA clear and will take ¼in. 6BA bolts when the case is assembled. Holes '5' to '8' on the side flanges are for self-tapping screws, whilst holes '5' to '8' on the back are self-tapping screw clearance. The mounting holes for the controls are ⅜in. diameter.

The mounting holes for the two component boards can be marked out from the component boards themselves, using the latter, before the components are fitted, as templates. This process can be carried out after the case has been assembled. The four holes required are 6BA clearance and the mounting bolts are 1in. or more in length. The component boards are stood off from the case surface by insulated spacing washers, and their positions can be adjusted from Fig. 7 and the photographs.

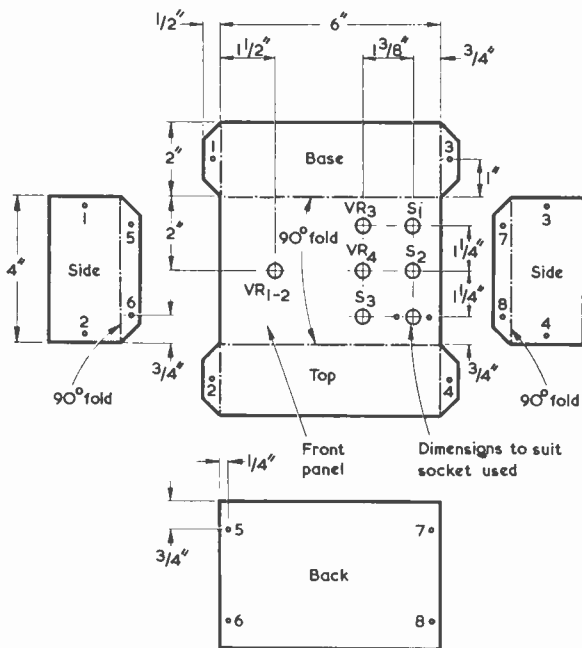


Fig. 4. Details of the aluminium case for the instrument

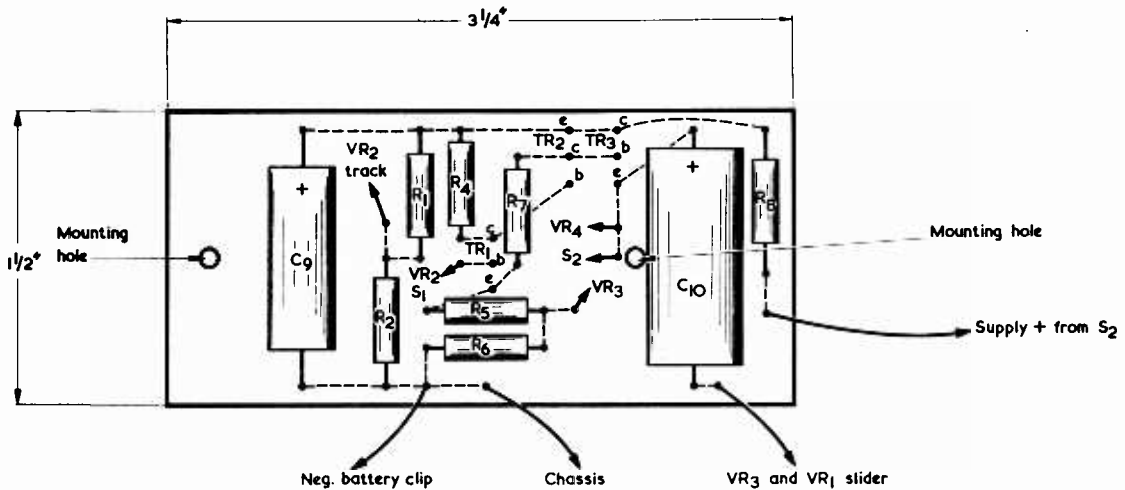


Fig. 5. The components and wiring on the Wien oscillator board

If the constructor does not wish to build his own case, there are several commercially produced aluminium cases of around the same dimensions and one of these could be employed instead.

When the case is completed, it may be left with a natural finish or it can be painted. (The painting will have to be carried out after the circuit boards have been cut out and drilled so as to enable their mounting holes to be made). The prototype was given a coat of hammer finish paint.

ELECTRICAL CONSTRUCTION

Most of the signal generator circuit is built up on two component boards, one for the Wien Bridge oscillator and the other for the Schmitt trigger. Details of the board on which the oscillator is assembled are given in Fig. 5, and details of the board for the Schmitt trigger in

Fig. 6. These diagrams are reproduced full size.

The method for producing the completed boards is to cut pieces of Paxolin to the required size and trace, and then drill the holes, at the places indicated in the diagrams. Component leads are next passed through the appropriate holes and bent over at right angles. The leads are then soldered together as indicated by the dotted lines in the diagram. Bare tinned copper wire of around 22 s.w.g. can be used to bridge any gaps if component leads are too short to reach the other leads to which they are to be connected. The lead connecting R8 to the collector of TR3 (see Fig. 5) must be covered with insulated sleeving where it crosses the lead to C10.

Mounting holes in the boards are drilled 6BA clear, and smaller holes are drilled for the component leads. To prevent the wiring on the underside of each board short-circuiting to the case, insulated spacing washers are placed over each securing bolt, appearing between the

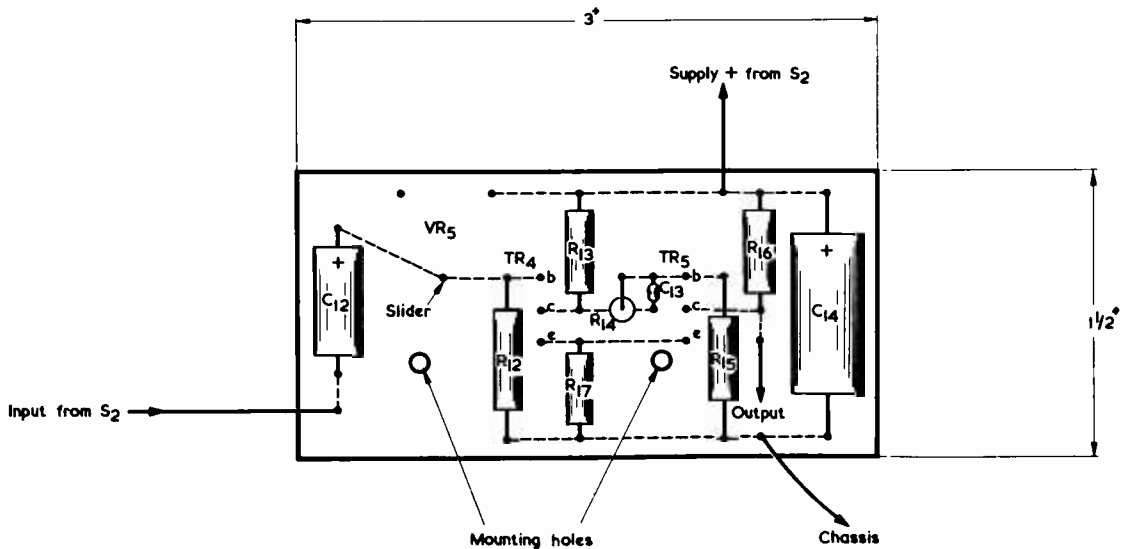


Fig. 6. The Schmitt trigger board. In company with Fig. 5 this is reproduced full size and may be traced

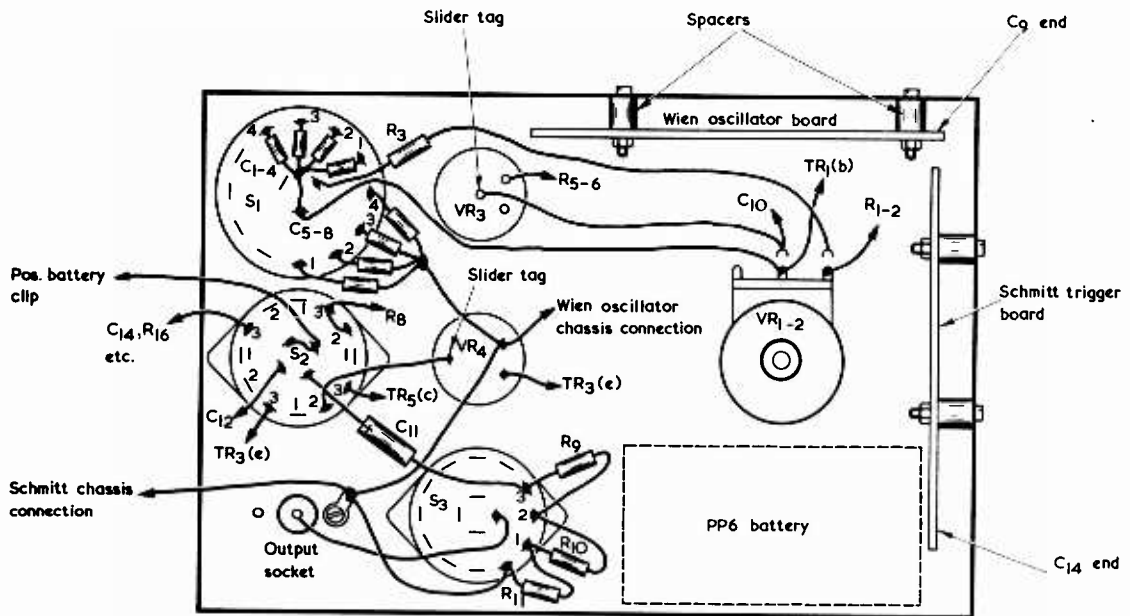


Fig. 7. The wiring inside the case. Note that one end of R11 is anchored to an unused switch tag

board and the case. These spacing washers are approximately $\frac{1}{4}$ to $\frac{3}{16}$ in. long and may be cut from a piece of narrow bore Paxolin tubing or, say, from the barrel of a discarded ball point pen.

A diagram illustrating the wiring to the controls is given in Fig. 7. The positions of the tags of S1, S2 and S3 are those encountered in the switches employed in the prototype any may vary for different switches. It is best to check the contacts which correspond to the switch arm tags with a continuity tester, and wire up accordingly. It will be noted that only two poles of S1 and one pole of S3 are used. Because of this, S1 could be 2-pole 4-way and S3 could be 1-pole 3-way, but it will probably be found easier to obtain the switches as

specified. The battery is mounted in the space under VR1,2. It fits in fairly tightly. If it is found to be a little loose, foam rubber can be packed in as required.

CALIBRATION

Calibrating the generator can be a bit of a problem, as an accurate signal generator and an oscilloscope are required for this, and anyone building the generator is unlikely to already possess such equipment. Those who own the required equipment, or can gain access to it, can calibrate the generator using the Lissajous figure method. It can also be calibrated against an audio frequency meter, should one be available.

Another rear view of the generator



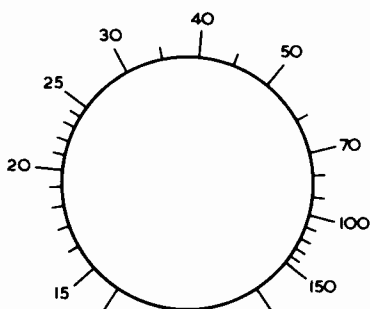


Fig. 8. A suitable scale (reproduced half-size) which may be used if no other means of calibration is available

For those who are unable to use either of these methods, the scale shown in Fig. 8 can be traced out and enlarged (it is reproduced half-size) and used on the instrument. Owing to variations between different potentiometers this scale will only give approximate indications of frequency, but it will nevertheless be helpful for virtually all of the applications in which the generator will be employed.

USING THE GENERATOR

The generator has six controls. The dual gang potentiometer, VR1,2, varies the frequency over the range selected by S1. S2 is the function switch and it causes the unit to be switched off on position 1, whilst positions 2 and 3 select sine and square wave outputs respectively.

VR4 provides a continuously variable control over the sine wave output. S3 is the 3-position attenuator switch, and it controls both sine and square wave outputs.

VR3 is the feedback control. When it is turned right back, so that it inserts minimum resistance into circuit, there should be no output from the unit. If the control is advanced, a point will be reached where the circuit begins to oscillate. For the highest quality sine wave output, VR3 should be advanced to a point where the oscillation is just sustained. For the square wave output VR3 should be advanced such that the circuit is oscillating strongly.

The preset potentiometer, VR5, is adjusted in the following manner. Connect a multimeter set to read 10 volts f.s.d. between TR5 collector and chassis. Turn VR5 fully clockwise, so that it inserts maximum resistance. Switch on the unit by setting S2 to position 3 and adjust VR3 so that the sine wave oscillator does not run. If VR5 is now adjusted for a much lower resistance the voltage read by the meter will, at some setting, suddenly swing to a much higher level, around 8 volts. The final setting required in VR5 is just before this point i.e. VR5 should insert the minimum possible resistance without the voltmeter reading rising to the higher level.

Simple Short-Wave Receivers

by F. A. Baldwin



★ FOUR DESIGNS –
1, 2 and 3 Valves

★ INTRODUCTION TO SHORT-WAVE LISTENING –
14 Comprehensive Sections

★ WORKSHOP PRACTICE

★ SOLDERING NOTES

★ RECEIVER AND BENCH
POWER SUPPLIES etc. etc.

FOR ONLY

140 PAGES **80p** Postage 6p

TO DATA PUBLICATIONS LTD
57 Maida Vale London W9 1SN

Please supply.....copy(ies) of 'Simple Short-Wave Receivers', Data Book No. 19

I enclose cheque/crossed postal order for.....

NAME.....

ADDRESS.....

.....

.....

.....

BLOCK LETTERS PLEASE

IMPROVED

DIGITAL

DISPLAY

by

D. A. Nicole, G8CYJ

Our contributor describes a digital display based on that which appeared in the January 1972 issue. The revised circuit saves four diodes for a single digit display and also enables a single set of gating diodes to be employed in a two-digit display.

THIS ARTICLE DESCRIBES TWO IMPROVEMENTS WHICH can be made to Suggested Circuit No. 254, 'Pilot Lamp Digital Display', published in *The Radio Constructor* for January, 1972.


HALF-WAVE OPERATION


Since there is at least one diode in series with each lamp, the rectifier bridge, D1 to D4, can be omitted and the switching circuit run direct from a.c., as in Fig. 1. This will be half-wave rectified by the diodes and will not interfere with circuit operation. The energy

content of the waveform, however, is now only half of its original value, and to compensate for this the transformer secondary voltage must be increased to

$$12.6 \times \sqrt{2} = 17.5V.$$

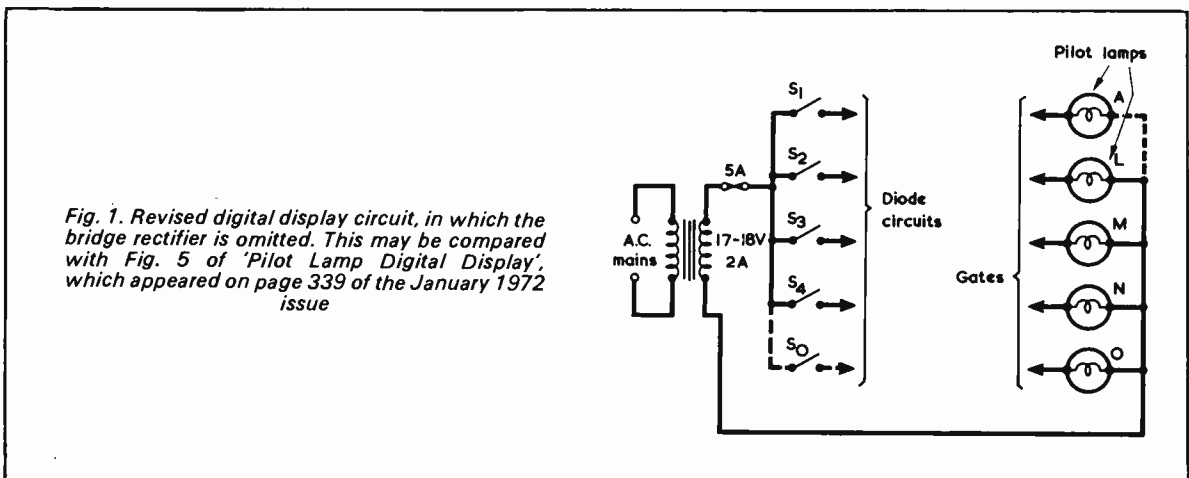A 17V or 18V transformer would work well in practice. As the revised circuit uses only the same power as before, the secondary current rating can be reduced in proportion to the increase in voltage. Thus a 2A secondary should be satisfactory. The diodes are also subjected to a slightly higher inverse voltage (25V), but this is well within their rating.



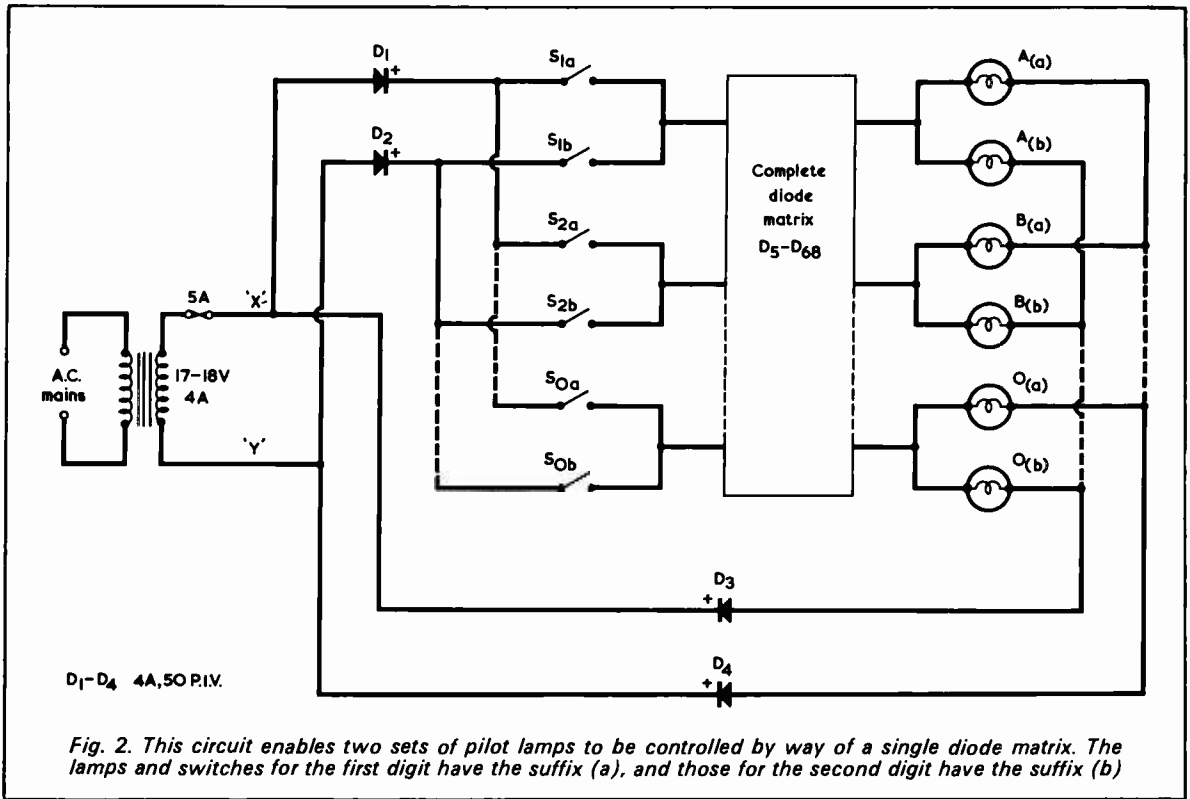

TWO-DIGIT DISPLAY

In the first paragraph of the preceding article it was suggested that the circuit could be duplicated to drive two sets of lamps. However, it would in principle be possible to use the one matrix of coding diodes to drive as many sets of lamps as are desired, this being done by rapidly switching the lamps and switches for each digit into the matrix in turn. With more than two sets this becomes very complicated, requiring transistor switches, but it can be achieved very easily for two digits. The output from a 17-18V 4A transformer is half-wave rectified to give two separate outputs, 180° out of phase. See Fig. 2. These outputs are fed individually to the switches, combined through the diode matrix, which is identical to that in the original circuit, and then the current is then routed through the correct set of bulbs.

A more detailed explanation can be given by stating initially that, when point 'X' in Fig. 2 is positive of point 'Y', conventional current flows through D1, through whichever of switches S1(a) to S0(a) is closed, through the diode matrix, which includes the ABC gate, GHI gate, etc., and then through the required

lamps of A(a) to O(a). The reverse biased diodes D2 and D3 prevent any current flowing through S1(b) to S0(b) or lamps A(b) to O(b). Conversely, when 'Y' is positive of 'X', current flows through the 'b' group of lamps and switches, the 'a' group being isolated by D1 and D4. Thus, the overall effect is of independent control of the two lamp sets by the switch banks.

EDITOR'S NOTE

Full-wave rectification of the a.c. supply was incorporated in the original circuit to reduce the effect of flicker, which is evident in some bulbs when run from a half-wave rectified supply. However, the half-wave flicker with the bulbs employed in the circuit is, in practice, negligibly low, whereupon the improvements described in this article are particularly valuable. The circuits in the original article take up too much space to merit reproduction so soon after the article appeared. If desired, the January 1972 issue may be obtained direct from the publishers at 20p plus 6p postage. ■

Digital Frequency Monitor

In Fig. 6 of this article on page 743 of the last July issue, Preset 2 was shown as passing to the main counter. It should, instead, have been labelled as passing to the input gate and divider.

SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

CLUB NEWS

We commence this month with news about various clubs which may interest some readers. There are many clubs, leagues or societies, which cater for the short wave listener interest, such organisations producing a news sheet or journal at regular intervals, usually monthly, and various other services together with a wealth of information necessary for the active pursuit of the hobby. The majority of these clubs are devoted to the interests of the broadcast bands enthusiast whilst a few also additionally provide for the amateur bands listener.

World Dx Club publishes a monthly bulletin 'Contact', this consisting of 24 duplicated quarto-sized pages plus the cover. This club covers both the broadcast and amateur interests, the annual subscription rate is £1.50 for U.K. and Eire residents. A sample copy of 'Contact' may be obtained for 10p from the Secretary, Clive Jenkins, 11 Wesley Grove, Portsmouth. PO3 5ER.

South African Dx Club is anxious to obtain new members and their bulletin 'Dx News' is often quoted in many Dx programmes around the world, the information contained therein being informative and authoritative. Further information with respect to sample copies and rates etc., may be obtained from Gerry Wood, P.O. Box 24, Plumstead, C.P., Republic of South Africa.

Union of Asian Dx-ers exists for those who are interested in Dx from the Asian point of view. Of interest to broadcast band listeners, the Union is headed by G. Victor Goonetillike who is probably the best known Dx'er in all Asia. For further details write to G. V. Goonetillike, Galle Walauwa, Piliyandala, Republic of Sri Lanka and enclose one International Reply Coupon.

British Association of Dx'ers, often quoted in these columns, is devoted entirely to broadcast band interests and issues its journal 'Bandspread' on a fortnightly basis by first class post. The latest edition to hand, Number 40, was of sixteen foolscap-sized sheets packed with information for the s.w.l. Additionally, extra publications dealing with specific aspects of Dx-ing are often included for no extra charge. Only up to date news items are published and members must be actively engaged in broadcast band Dx-ing and report on a regular basis. The charge for this first class service is £3.00 per annum for U.K. residents and the address is - BADX, 16 Ena Avenue, Neath, Glam.

Next month we shall include more information on other clubs providing services specifically for the short wave listener.

NOW HEAR THESE

This month we commence with an item of news from the South American continent.

● BRAZIL

Radio Nacional Brasilia, listed on **15445**, has been

logged on **15448** (19.42 metres) at 2327 with a commentary in English, station identification and a request for reports. Also heard at 2221 with an English programme on **15448** and at 2154 on **11720** (25.60m), and from 2143 to 2206 on **15448** with music, programme in English and a request for reports, all according to BADX. The listed power is 10kW.

● LEBANON

Radio Beirut has replaced the **15355** channel with that of **15170** (19.78m) for the English, Arabic and French services for Europe from 1830 to 2030.

● INDIA

AIR Delhi is now operating on a new frequency for the service in French to South East Asia, being logged on **11725** (25.59m) 100kW at 1115, this probably replacing the **21660** channel.

● ALGERIA

The service in French from Radio Algiers for the Middle East may be heard on **11835** (23.55m) and on **15420** (19.45m) from 2100 to 2300.

● SOUTH KOREA

VOFK Seoul has been logged on **15335** (19.56m) by BADX operators at 0630 with sign-off in French and then into English with a newscast. The listed power is 50kW.

● JORDAN

Radio Amman was recently logged with the service in English at 1705 when a newscast was radiated on **9560** (31.38m). The programme in English is broadcast from 1630 to 1730 on this channel and also on **7155** (41.92m) from 1100 to 1300.

● COSTA RICA

TIFC San Jose, 'Faro del Caribe' ('Lighthouse of the Caribbean') has been heard daily ending the English programme at 0430 on the regular **9645** (31.10m) channel (2kW). The parallel **6037** (49.69m) channel was almost inaudible.

● SOUTH AFRICA

Radio RSA has been logged by a BADX operator on **15160** (19.79m) at 1000 with the service in English to Australia, a new frequency on the recommendation of the operator concerned (Bob Padula - an Australian Dx'er) which shows just how useful a 'top flight' short wave listener like BP can be on occasions.

● BELGIUM

ORU Brussels has been heard at 0630 signing-on with the news in French on a new frequency of **15110** (19.85m).

● ARGENTINA

LRA32 Buenos Aires has been logged on the regular **9690** (30.96m) channel at 0507 with Paraguayan songs and Spanish announcements with station identification at 0512.

TIME-CHECK

The stations mentioned in NOW HEAR THESE are listed here on a time-check basis for the convenience of readers.

RADIO & ELECTRONICS CONSTRUCTOR

<i>GMT</i>	<i>Freq.</i>	<i>Stn.</i>	<i>Rcvd.</i>
0415	9645	TIFC San Jose	
0507	9690	LRA32 B. Aires	
0630	15110	ORU Brussels	
1000	15160	Johannesburg	
1100	7155	Amman	
1115	11725	Delhi	
1630	9560	Amman	
1830	15170	Beirut	
2100	11835	Algiers	
2100	15420	Algiers	
2221	15448	R. N. Brasilia	

CURRENT SCHEDULES

● INDIA

Transmissions in English to the U.K. and Western Europe from All India Radio are now radiated as follows - from 1800 to 1910 on **7215** (41.58m), **9525** (31.50m) and on **11620** (25.82m). From 1945 to 2045 on **7215**, **9525**, **9912** (30.27m) and on **11620**. From 2045 to 2230 on **7215**, **9525**, **9912** and on **11620**.

● HOLLAND

The current schedule of Radio Nederland, in English to Europe, is from 1400 to 1520 on **6020** (49.83m) and from 1830 to 1950 on **6020**, **6085** (49.30m) and on **21570** (13.91m) on weekdays. On Sundays, the 'Happy Station Sunday Programmes' are radiated from 0930 to 1050 on **6020**, **6410** (46.82m) and on **7275** (41.24m). From 1400 to 1520 on **6020**; from 1830 to 1950 on **6020**, **6085** and on **21570**. The address is - Radio Nederland, P.O. Box 222, Hilversum.

● GHANA

The external service from Accra, 'Voice of the Revolution', in English to Europe, is from 2045 to 2215 on **9545** (31.43m). To the U.S.A. from 2000 to 2100 on **9760** (30.74m) and on **11850** (25.32m).

● ISRAEL

The service in English from Jerusalem is now broadcast to Europe from 2035 to 2115 on **6170** (48.62m) and on **9625** (31.17m) and to Africa on **9009** (33.30m). (BADX).

● SOUTH KOREA

The English service schedule of VOFK Seoul is as follows - to North America from 0300 to 0330 on **15335** (19.56m); to South Asia and Australasia from 1200 to 1230 on **9640** (31.12m) and from 1400 to 1430 on **15335**; to Europe from 0630 to 0700 on **15335**. (BADX).

● CUBA

Radio Havana now has the English schedule as follows - to Northern Europe from 2010 to 2140 on **17815** (16.84m); to the U.S.A. from 2050 to 2150 on **15285** (19.63m), from 0100 to 0450 on **11930** (25.15m), from 0100 to 0600 on **11815** (25.39m), from 0330 to 0600 on **11760** (25.51m) and from 0630 to 0800 on **9525** (31.50m). (BADX).

SEPTEMBER 1972

● CHINA

Radio Peking currently broadcasts in English to Europe from 2030 to 2130 on **6610** (45.38m), **6825** (43.37m), **7590** (39.53m), **8490** (25.33m) and on **9030** (33.22m). From 2130 to 2230 on **6610**, **6825**, **7590**, **8490**, **9030** and on **11675** (25.70m).

AROUND THE DIAL

● BANGLADESH

Radio Bangladesh, still varying in frequency around **17930** (16.73m), was recently logged at 1235 with news and comment in English. It has also been heard on **9690** (30.96m) from 0230 to 0301 mixed with signals from the BBC to South Asia and in parallel, in the clear, on **15520** (19.33m) with the General Overseas Service of R. Bangladesh.

● HAITI

According to reports, 4VEJ Cap Haitien has raised power from the listed 2.5kW to 10kW on the usual **11835** (25.35m) channel and has an English programme from 2300 to 0200. (WDXC).

● IVORY COAST

Abidjan now radiates a service in English from 1820 to 1955 on the regular **11920** (25.17m) channel on weekdays, the power is 100kW.

● NORTH VIETNAM



Hanoi currently radiates the news in English at 1000 and at 1530 on **10040** (29.88m) and at 2000 on **15005** (19.99m).

S.W.L. PUBLICATION

There are many such publications, both commercial and private, dealing with broadcast band interests but one that may possibly interest readers of these columns is 'Latin American Commercials'. This 24-page booklet is available direct from Nils Ingelstrom, Vavstolsvagen 1, 161 48 Bromma, Sweden, for either nine IRC's or 70p U.K. currency. Written by two Swedish Dx'ers, it provides a comprehensive list of the commercials used by Latin American stations and also contains information on the music of this part of the world (LA mx), programme formats and speech habits. Both of the authors recently visited Latin America and are therefore recognised authorities on all aspects of LA Dx'ing.

MIDDLE EAST DX'ERS

Middle East Dx Club, 5 Cologne 91, Remscheid Str. 97, West Germany, will provide a diploma to any Dx'er who has heard at least ten Middle East broadcast stations (Afghanistan, Yemen, S. Yemen, Iraq, Israel, Jordan, Iran, Kuwait, Lebanon, Muscat and Oman, Qatar, Dubai, Saudi-Arabia, Syria, Turkey, Egypt and Cyprus), seven IRC's should be sent with supporting QSL cards. The cards will be returned with the diploma, the address for applicants is - Gerhard Schreier, Diploma Manager, 6902 Sandhausen, Albert Schweitzer Str., 2, West Germany.

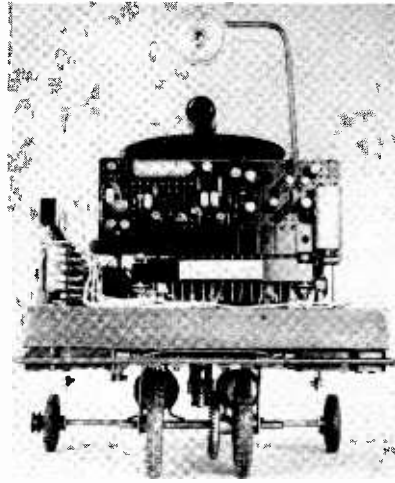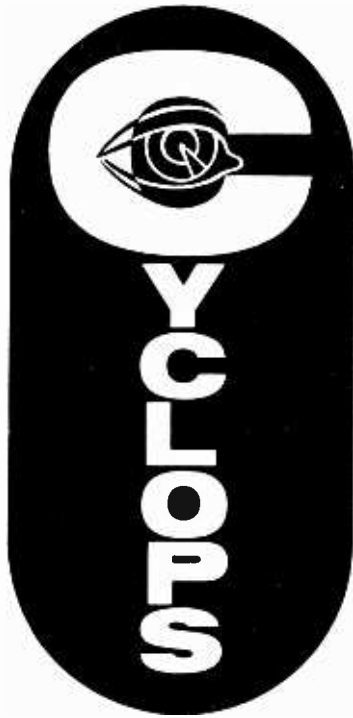

PART THREE

by
L. C. Galitz

This article is the third in a series dealing with robots and cybernetic devices, and it continues with the construction details of Cyclops. This month, a description of the basic reflex circuitry is given

IN THE FIRST ARTICLE IN THIS SERIES IT WAS STATED that Cyclops is positively tropic towards light of a moderate intensity, and negatively tropic towards light of a high intensity. He is also negatively tropic towards material objects, and the touch stimulus should override the effects that any particular light stimulus produce.

BASIC OPERATION

Reference to Fig. 13 will show how this is accomplished. The output from the photocell which forms Cyclops' eye is fed to a pre-amplifier, after which it passes to three Schmitt triggers. Following the Schmitt trigger with the highest threshold (i.e. lowest sensitivity) is an inverter, the output of which passes to one input of each of two two-input And-gates. The other input of each And-gate connects to one of the other Schmitt trigger outputs. The output of the upper And-gate in Fig. 13 operates a relay which inhibits the scan motor, and the output of the lower And-gate passes to another relay which inhibits both scan and drive. Under no-light conditions, therefore, there will be zero output from each of the three Schmitt triggers, and there will thus be a logic one from the inverter, resulting in each gate having a logic nought on one input, and a logic one on the other input.

Under these conditions, neither scan nor drive is inhibited, and Cyclops will explore the terrain randomly. If he then comes across a light some distance away, and if it is of sufficient brilliance to operate the Schmitt trigger with the lowest threshold, there will

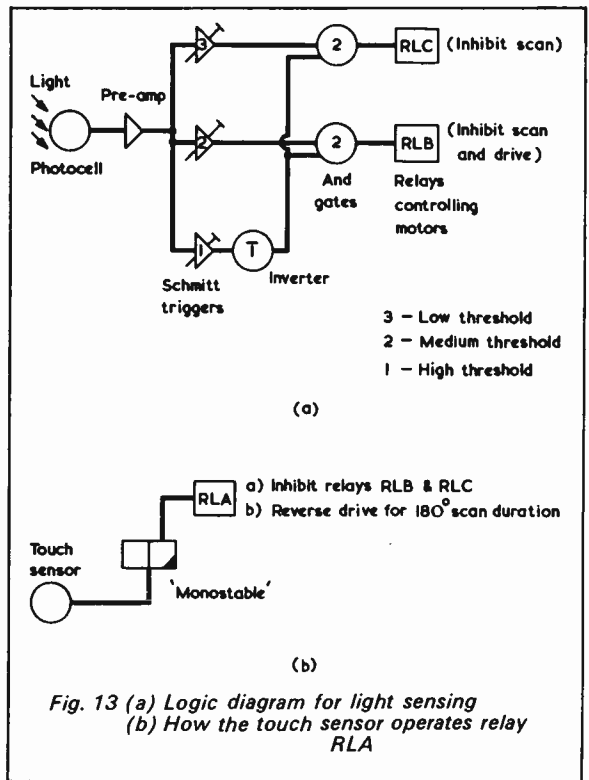


Fig. 13 (a) Logic diagram for light sensing
(b) How the touch sensor operates relay RLA

now be logic ones on both the inputs of the upper And-gate, this being the one whose output operates the relay which inhibits scan only. In consequence, Cyclops will stop exploration and commence homing into the light as detailed in the first article.

When he comes sufficiently close to the light source the medium threshold Schmitt trigger also fires, whereupon both And-gates have logic ones on each of their inputs. The lower And-gate operates the relay which inhibits drive as well as scan. Thus Cyclops will stop in front of the light to 'recharge his batteries'.

Should the light be so powerful as to 'dazzle' him, the high threshold Schmitt trigger will fire as well as the other two. However, the inverter inverts the output of the high level Schmitt trigger and thus, in this situation, the And-gates have logic ones on the inputs connected to the low and medium threshold Schmitt triggers, but logic noughts on the inputs connected to the inverter. Therefore the scan and drive inhibition is itself inhibited, causing Cyclops to ignore extremely bright lights.

The touch sensor consists of microswitches at the ends of each side of the chassis, making eight microswitches in all. Bars are fixed between the buttons of the two microswitches on each side of the chassis, so that when Cyclops bumps one of his sides on an object, either one or both microswitches operate. All the microswitches are wired in parallel and go to the input of the obstacle-avoiding circuitry which, on receiving an input, operates a relay via a monostable. This relay disconnects the coils of the other two relays, so that any inhibition of drive and/or scan is itself inhibited. The third relay also reverses the drive direction of the main drive motor, and therefore, on bumping into an obstacle, irrespective of whether Cyclops is scanning, homing into a light, or even recharging his batteries, he will reverse, execute a turn, and then move off in the direction opposite to the one in which he was moving when encountering the obstacle. The latter feature is accomplished by arranging the duration of the monostable to be equal to the time the scan motor takes to turn the main drive assembly through 180°.

THE CIRCUIT

It is necessary now to turn to the circuit diagram given in Fig. 14.

The 'monostable' operating the avoid mechanism consists of R1, C1, D1, TR1, relay coil RLA/4 and contact RLA1. When any of the touch sensor microswitches operates, R1 is connected to the negative rail via the microswitch contacts and the normally closed contacts RLA1. This connection causes C1 to charge up quickly and TR1 then operates the relay, being turned on by the voltage across C1. Contacts RLA1 open and C1 discharges through the base circuit of TR1, until TR1 eventually switches off and RLA/4 de-energises. By now, Cyclops will have managed to extricate himself from most objects, but in some tricky circumstances, e.g. the family cat, he may still be entangled. If a touch sensor closes once more he will move forward very briefly in the time it takes to charge C1 again. In some cases this will free him but otherwise he will go through the avoid cycle again until he does eventually free himself. This short jerk between cycles is due to contacts RLA1, and it often proves useful when negotiating difficult situations.


The photocell X1 and resistor R2 form a potential divider at the base of the pre-amplifier, TR2. This is in the common collector mode, offering high input impedance and high current gain. Wired in its emitter circuit are three preset potentiometers, the wipers of each passing to a Schmitt trigger. These potentiometers set the threshold values for the triggers. The first Schmitt trigger consists of TR3, TR4 and R4 to R8. Due to the fact that the inverted output of this trigger is required, the output is taken from the first collector rather than the second. The second Schmitt trigger consists of TR5, TR6 and R9 to R13, whilst the third Schmitt trigger consists of TR13, TR14 and R16 to R20. The outputs from these latter two Schmitt triggers are taken from the usual collectors, i.e. those of TR6 and TR13 respectively.

The two And-gates are formed by TR7, TR8, TR11, TR12, R14 and R15. These four transistors are n.p.n. types, and the gates operate by using the current sinking logic mode. In order for the output of each gate to be negative, i.e. at logic one, both transistors must be cut off, and as they are n.p.n. devices, both transistors require a negative bias on their bases for this to occur. In all other cases, the current through the emitter resistor is 'sunk' through either one or both transistors.

The output of each gate passes to a relay driver transistor working in the common collector mode, and there is the usual diode across the relay coil preventing transients from damaging the driving transistor.

The common coil connection of the relays is taken via a break contact, RLA2, of RLA/4; and thus, when the obstacle avoiding circuitry comes into action, both RLB/1 and RLC/1 cut out.

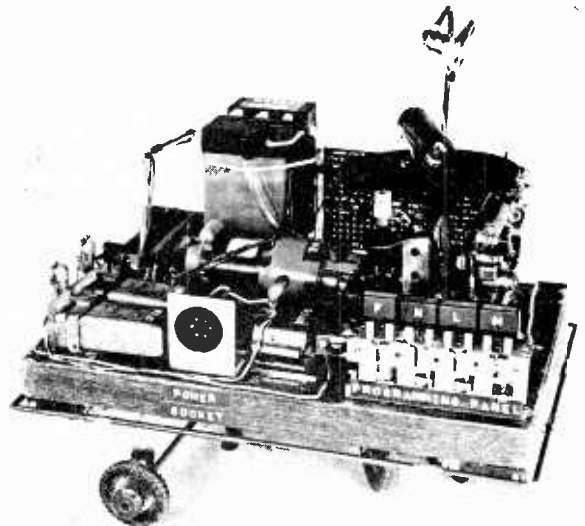The rather elaborate on/off switching is due to the fact that two on/off switches are used in the prototype. One switch, S1, switches on the basic reflex circuitry only, whilst the other, S2, switches on the learn circuits



Side view of Cyclops. The Veroboard assembly in front of the eye support unit, and the horizontal device (actually a dry reed switch) behind the accumulator, are added after the circuitry described in this and next month's issue has been completed

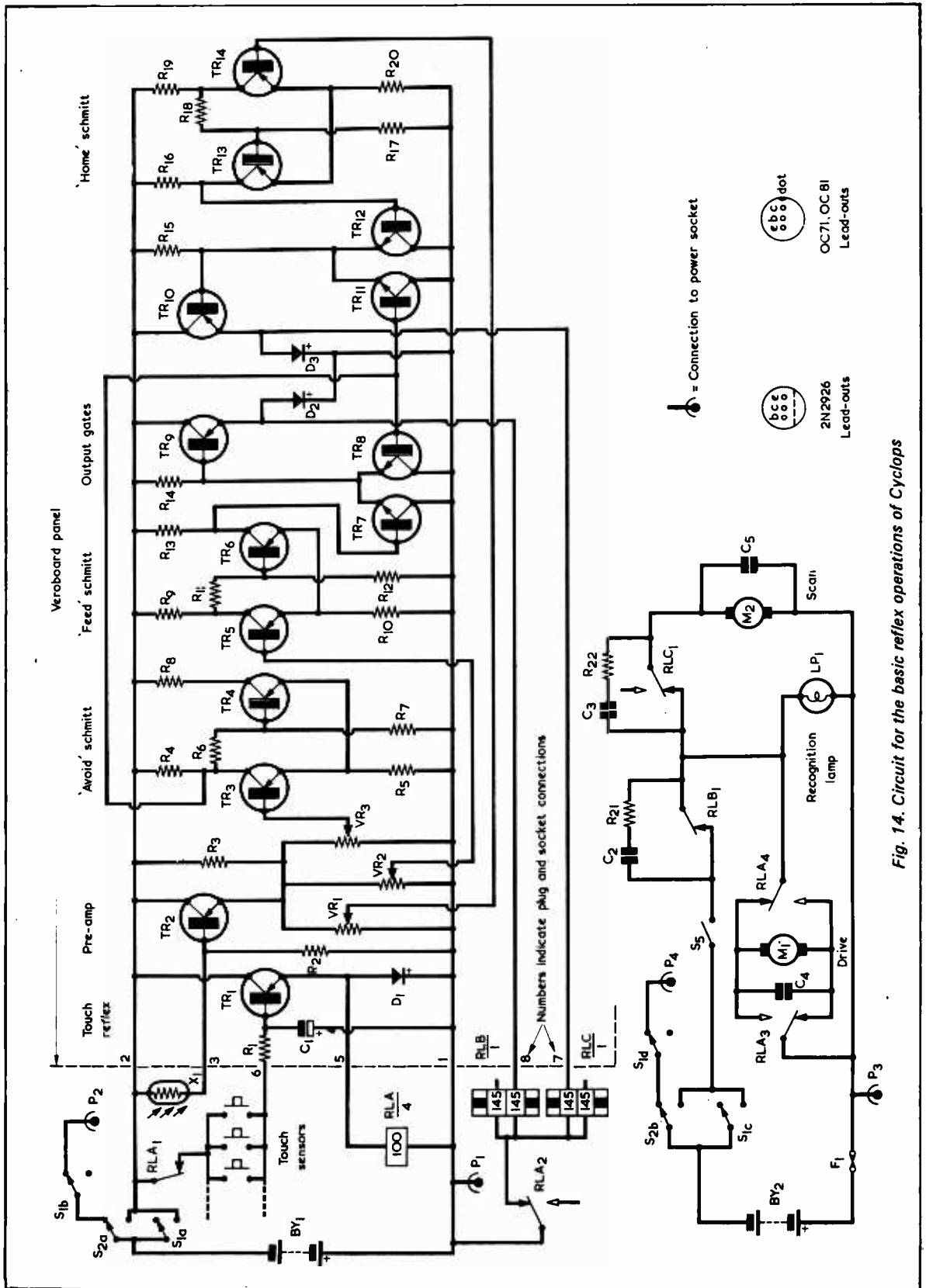


Fig. 14. Circuit for the basic reflex operations of Cyclops

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 10%)

R1	1k Ω
R2	47k Ω
R3	47k Ω
R4	4.7k Ω
R5	470 Ω
R6	22k Ω
R7	10k Ω
R8	4.7k Ω
R9	4.7k Ω
R10	470 Ω
R11	22k Ω
R12	10k Ω
R13	4.7k Ω
R14	1k Ω
R15	1k Ω
R16	4.7k Ω
R17	10k Ω
R18	22k Ω
R19	4.7k Ω
R20	470 Ω
R21	10 Ω
R22	10 Ω
VR1	10k Ω potentiometer, skeleton
VR2	10k Ω potentiometer, skeleton
VR3	10k Ω potentiometer, skeleton

Capacitors

C1	50 μ F electrolytic, 12 V.Wkg. (may require adjustment)
C2	0.1 μ F Mullard polyester, 125 V.Wkg.
C3	0.1 μ F Mullard polyester, 125 V.Wkg.
C4	0.1 μ F Mullard polyester, 125 V.Wkg.
C5	0.1 μ F Mullard polyester, 125 V.Wkg.

Semiconductors

TR1	Any p.n.p. transistor capable of driving relay, e.g. OC81
TR2-TR6	Any p.n.p. transistor, eg. OC71
TR7, TR8	2N2926
TR9, TR10	As TR1
TR11, TR12	2N2926
TR13, TR14	As TR2-TR6
D1-D3	Any silicon diode, e.g. OA200

Photocell

X1	ORP12
----	-------

Switches

(S1 to S4 are available from G. W. Smith & Co. (Radio) Ltd., 3 Lisle St., London, W.C.2. as a complete unit, described as a 'Standard 4-Button Press-Button Unit'. This offers more contacts than are required for the present

application. The 8 microswitches are also available from G. W. Smith & Co. (Radio) Ltd.)

S1	4-pole changeover
S2	3-pole changeover
S3	3-pole changeover
S4	Single-pole, push-to-make release-to-break
S5	s.p.s.t., slide switch
8-off	microswitches, Bonella single-pole-normally open

Relays

(All relays are available from G. W. Smith & Co. (Radio) Ltd.)

RLA	Post Office 3000 relay, 100 Ω coil, 3 break-before-make changeover contacts, 1 break contact
RLB, RLC	Sealed Siemens High Speed Relay, 145 Ω + 145 Ω coil, 1 changeover contact

Lamp

LP1	6.3V, 0.3A, m.e.s. lamp
-----	-------------------------

Connectors

Power Supply:	Bulgin P194 6-way plug and socket (Home Radio Cat. No. P194)
Veroboard:	R. S. Components 8-way edge connector (Home Radio Cat. No. BTS41)

Batteries

BY1	6V 225 mA/H Deac rechargeable battery (Ripmax Ltd.)
BY2	6V 2 A/H accumulator, e.g. Yuasa MBC1-6 6N2-2A (Motor-cycle dealers).

Miscellaneous

Verobard,	0.15 in. matrix, 3 $\frac{1}{2}$ in. \times 2 $\frac{1}{4}$ in., 14 strips \times 24 holes
1-off	Meccano perforated strip, part 2a
1-off	Meccano perforated strip, part 3
1-off	Meccano perforated strip, part 6a
1-off	Meccano coupling, part 63
2-way	connector block
Tank clip	(for securing BY1) (Ripmax Ltd.)
1-off	fuse and holder rated at 5A if accumulator not used
Insulating	washers
Perspex	brackets
Rods	
Torch	reflector
Photocell	tube

in addition. The contacts of S2 which control the learn circuits will be discussed in a later article. When both switches are in the off position, the battery terminals are connected to a power supply socket for recharging purposes. Because higher voltages are used for recharging than the batteries supply normally, it was felt that this safety measure which allows the charger to be connected to the batteries only when both

switches are off, was desirable. Naturally, if normal batteries are to be used, or if the learn circuitry is either to be omitted or switched on all the time, the switching can be made less complex.

There was also a need in the prototype for the electronics to be switched on without power being supplied to the motors, and S5 is used when Cyclops is to be run whilst 'paralysed'. This feature is useful in all

versions of the robot for such purposes as setting the various thresholds, and for testing the electronics; and therefore should be included.

The motor circuitry is quite straightforward. RLC1 cuts power to the scan motor, whilst RLB1 cuts power to the drive motor and to the recognition lamp. Contacts RLA3 and RLA4 reverse the direction in which the drive motor runs. Fuse F1 is included to protect BY2, whilst C2, C3, R21 and R22 and relay contact spark suppressors. C4 and C5 are included to limit interference from the motors.

COMPONENTS

All resistors and capacitors are standard components as specified in the accompanying Components List. The diodes are all silicon, and all the transistors apart from TR7, TR8, TR11 and TR12 are p.n.p. silicon or germanium. Transistors TR7, TR8, TR11 and TR12 are silicon planar n.p.n. devices, and due to the Veroboard configuration, should be the types having plastic enclosures with the wires in the e-c-b sequence. A suitable type is the 2N2926. X1 is an ORP12 light dependent resistor. The Veroboard connector block and the power supply socket are as specified in the Components List.

Relay RLA/4 is a G.P.O. 3000 type having a 100Ω coil and four sets of contacts. Three of these must be changeover and break before make, even though RLA2 is at the moment only used as a break contact. Later on, the make contact will be used as part of the learn circuits. The fourth contact need only be a break contact. Relays RLB/1 and RLC/1 are both identical, and are sealed Siemens high-speed relays having dual coils. These are chosen because, firstly, high speed action is required, especially for RLC/1, since if scanning cuts out too late, Cyclops will miss the light source. Secondly, dual coils were used because it is then much easier to isolate the basic reflex circuitry from the learn circuitry, which comes later. Switches S1 to S4 were, in the prototype, all in one bank. (S3 and S4 are used in the learn circuits). The bank consists of four push-button switches. The two centre ones are interdependent, i.e. if one is pushed the other releases; and the two outside ones are independent, being of the push-to-make push-to-break variety, one of which was modified to be push-to-make release-to-break. However, if it is so desired, the switches could all be independent of one another, and mounted on a control panel. S5 is a miniature slide switch. The recognition lamp LP1 is as specified in the Components List, and is mounted in a reflector taken from an old torch.

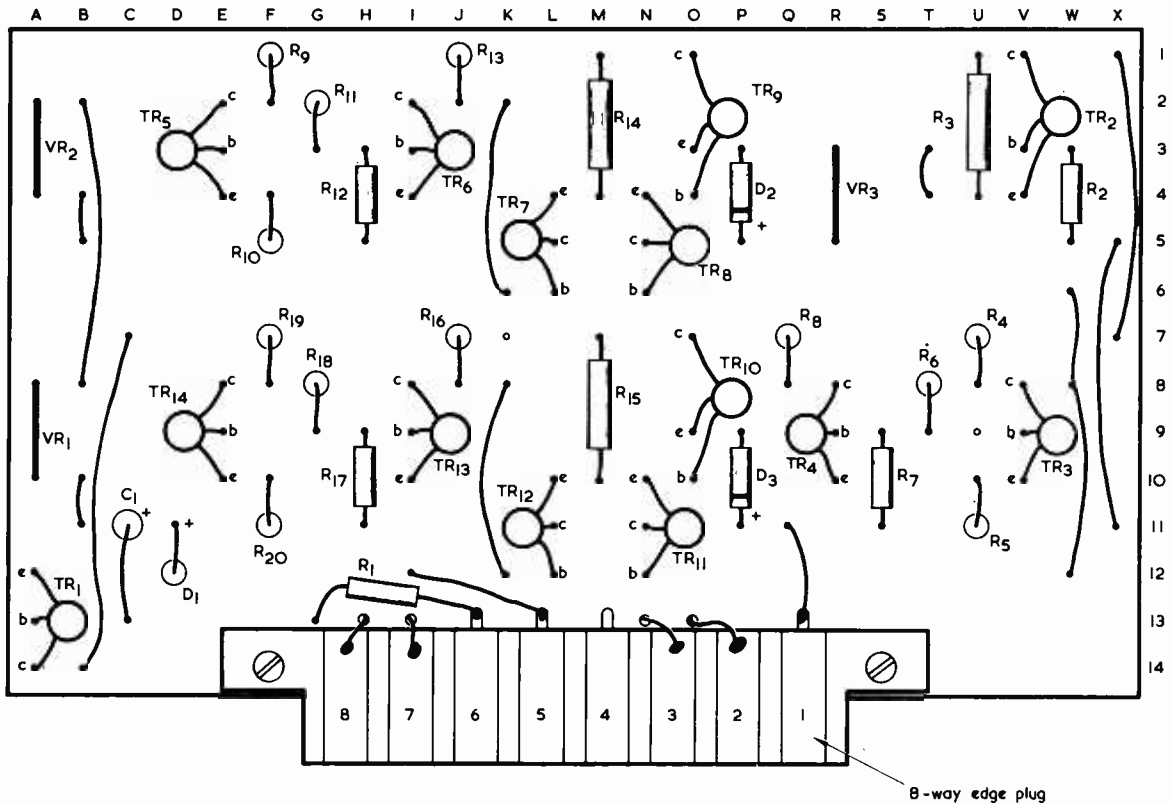


Fig. 15. The component side of the Veroboard which carries the basic reflex electronics

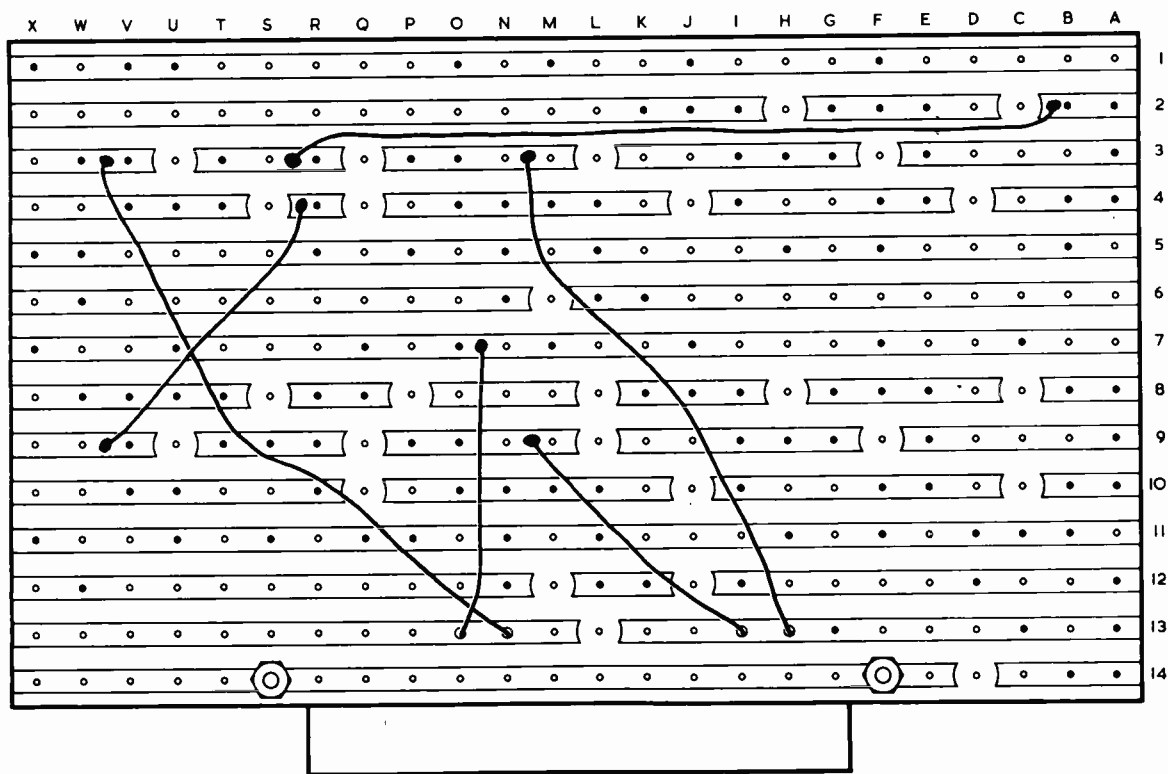


Fig. 16. The copper side of the Veroboard. Note that the links are soldered to the strips between holes and not at the holes themselves

Battery BY1 is a 6V 225mA/H Deac, whilst BY2 is a 6V 2A/H accumulator. On the other hand, if the expense of buying rechargeable power sources is not desired, BY1 could be a PPI, and BY2 could be an Ever Ready 'Lantern' battery type 996. However, both of these are too large to fit in the existing positions on the chassis, and the latter would have to be redesigned to take the batteries if this option was chosen. The fuse F1 is integral with the accumulator, but if batteries are chosen, it must be fitted separately.

VEROBOARD ASSEMBLY

The area of the circuit diagram to the right of the dotted line in Fig. 14 is built on a piece of 0.15 in. Veroboard having 14 strips with 24 holes. This fits into an R.S. Components 8-way edge connector, and a suitable plug for this is required. If necessary, this plug may be cut out, from a further piece of 0.15 in. Veroboard, to the shape shown in Fig. 15, which shows the component side of the board. The copper side is shown in Fig. 16.

If desired, constructors may wire up the board completely, following Figs. 15 and 16. Alternatively, they may prefer to wait until the main chassis wiring has been completed (to be described in Part 4) whereupon they can then proceed by mounting the components on the board in stages. In this case, the pre-amplifier should first be built, and then tested. Next, each of the Schmitt triggers should be built, and tested

by short-circuiting the top of the respective potentiometer to the negative rail and varying the position of the wiper whilst monitoring the output of the Schmitt trigger. The latter should, at a particular position of the wiper, suddenly jump from approximately 0.75 volt to about 5.5 volt. Finally, the And-gates and relay driver transistor stages should be built and tested. If construction and testing is carried out in this way, all the links and wires should be added *last*. The avoid circuitry (TR1, R1, C1 and D1) may be left till later.

Whatever method of Veroboard assembly is employed, it is first of all necessary to secure the 8-way edge plug to the panel at holes F14 and S14 by means of 6BA nuts and bolts. These two holes will require enlarging for this purpose. Then, the breaks in the Veroboard strips are made, as in Fig. 16, using a spot face cutter or a suitable drill. It should be noted that R1 connects to strip 13 at G13. The wires that pass through to the edge plug at holes H13, I13, N13 and O13 are insulated and do *not* make contact with the strip. The wires used must have insulation that does not melt readily when soldering at the plug tags. The polarities of the diodes and the transistor connections particularly those for TR7, TR8, TR11 and TR12 should be carefully checked.

A Components List accompanies this article, and it should be noted that some of the items listed are referred to in Part 4 of this series, which will be published next month.

(To be continued)

In your workshop



WITH A SIGH OF SATISFACTION, Smithy leaned over and turned off the master switch on his bench. This switch controlled all the mains sockets on the bench, including those for test equipment, receivers under repair and his soldering iron.

"Ah well," he grunted contentedly, "that's another day's work over."

He rose and stretched himself luxuriously, then proceeded to divest himself of his overall jacket. He next turned towards his assistant.

"Hallo," he remarked, "what's up with you?"

"With me?"

"Yes, with you," repeated Smithy. "Normally, when it's packing-up time for the day you're straining at the leash to get away. You look as though you're not even *contemplating* getting away tonight."

"To tell you the truth," replied Dick, "I'm thinking of pressing on with a little private job after hours. Can I stay on in the Workshop for a bit, Smithy? I'll lock up afterwards and let you have the keys tomorrow morning."

ZENER DIODES

"A private job, eh?" commented Smithy warily. "What sort of a private job?"

"Well," said Dick, "what's happened is that I've just bought by mail-order a Bumper Bargain Parcel of 200 unmarked and untested manufacturers' surplus zener diodes. What I now want to do is to get these sorted out into their different zener voltages, and I'd need some of the Workshop gear to do this."

A momentary gleam, quickly suppressed, appeared in Smithy's eyes.

This month Smithy the Serviceman, aided as always by his able assistant Dick, turns his thoughts to equipment suitable for analysing the performance of zener diodes. In the process, Dick is able to construct a simple but quite comprehensive zener diode tester which is capable of checking zener characteristics over a wide range of currents.

"That sounds interesting," he remarked with studied carelessness. "Let's have a look at those diodes."

Eagerly, Dick leaned over towards the rear of his bench, picked up a cardboard box and took off the lid. The box contained a large number of small metal-clad devices, these having varying outlines and colours.

"Humph," grunted Smithy. "you've certainly got a mixed bag there. So far as I can tell from a quick look they all seem to be in the 200 to 400mW range."

"They are," confirmed Dick. "That's what it said in the ad."

"How," asked Smithy, "had you intended checking them to find their zener voltages?"

"I hadn't," confessed Dick, "quite made up my mind as to how I was going to set about that. Have you any suggestions?"

"There are quite a few ways it can be done," said Smithy. "The most obvious approach consists, of course, of fixing up a power supply offering a direct voltage greater than the highest zener voltage to be expected, and of coupling this to each zener diode in turn via a resistor. You then connect a voltmeter across the zener diode whereupon, if the diode is connected right way round, the voltmeter will show its zener voltage at the particular current it happens to be passing." (Fig. 1.)

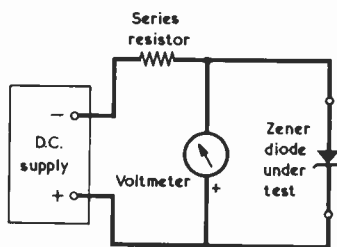


Fig. 1. The zener voltage of a zener diode can be determined with the aid of this circuit. The approach has the disadvantage that zener current varies according to the zener voltage

"That sounds a bit messy to me," objected Dick. "High voltage zener diodes will be passing smaller currents than low voltage ones."

"True enough," agreed Smithy. "The idea is reasonable enough but it doesn't give perfect results."

He paused, pursing his brow in thought.

"What would be much better," he remarked after a few moments, "would be to have a transistor acting as a constant current device in series between the power supply and the zener diode under test. The constant current transistor could be preset

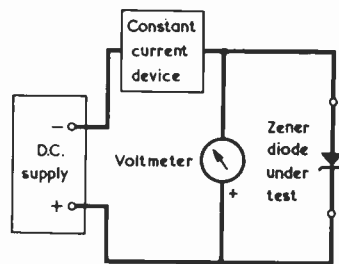


Fig. 2. An attractive alternative approach consists of replacing the series resistor with a transistor connected as a constant current device

to give any current figure you require with the result that, provided the available voltage is higher than any of the zener diode voltages, that constant current will flow through all diodes being checked, regardless of their zener voltages." (Fig. 2.)

"Blimey, Smithy," said Dick enthusiastically, "that sounds a smashing idea. Wouldn't the circuitry involved be rather complicated, though?"

"Not at all," replied Smithy. "You could assemble the whole thing in quite a short time. All the parts would fit on a small chassis with a front panel, and the latter would require holes for - let me see now - two toggle switches, a push-button, two pots, two test sockets or test terminals, and a meter. The latter, incidentally, would be a 0-100µA job."

"I've got an old chassis and panel from a home-made testmeter which I stripped down a month or so ago," said Dick keenly. "Its front panel has got quite a few holes in it for controls, and it's got a hole for a meter."

Excitedly, Dick bent down and rummaged amongst the large quantity of tattered cardboard boxes which always seemed to accumulate under his bench. He suddenly gave a cry of triumph and emerged carrying a small chassis and panel assembly, the panel already having the holes he had referred to. Proudly, he blew off the dust, then finally wiped his find clean with a rag.

"That," said Smithy, approvingly, "would seem to be just the job. Now, the next thing to do is to decide what is the range of zener diodes we intend to check. The zener diodes that are available these days cover a pretty fantastic range of voltages and powers. Some diodes, for instance, offer zener voltages of no less than 100 volts. However, in normal home-constructor applications we are much more liable to deal with the lower voltage and lower power types. I'd say that if we had a zener diode checker which coped with zener voltages up to some 25 volts, and which could provide controlled zener currents from 1mA to 100mA, then we would meet virtually all day-to-day requirements."

"Just a minute, though," he exclaimed as a thought suddenly struck him. "We don't have to use a mains transformer giving 30 volts. We could use one of those inexpensive battery charger transformers which offer 17 volts at 1 amp. These are quite cheap, and I'm pretty certain we've got one knocking around in the spares cupboard. All we then need do is to couple the 17 volt secondary to a voltage doubler rectifier and we'll get just the voltage we require."

As Smithy spoke, Dick was already walking towards the spares cupboard. He returned shortly, bearing a small mains transformer.

"Is this the sort of thing you mean?" he enquired. "This transformer's got a 17 volt secondary with taps at 7 and 11 volts."

"That's the type of transformer I mean," confirmed Smithy. "Its normal function is to charge accumulators by way of a rectifier, whereupon the 17 volt tap is employed for 12 volt batteries, the 11 volt tap for 6 volt batteries and the 5 volt tap for 2 volt batteries. Incidentally, you have to be a bit careful when buying charger transformers because the secondary voltages are sometimes quoted in terms of the batteries they are intended to charge. Thus, the 11 volt tap may be referred to as a '6 volt tap, and so on. What we require here is a charger transformer

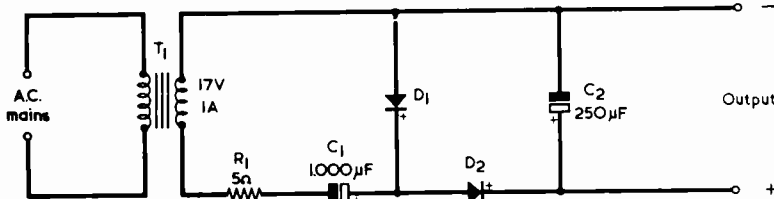


Fig. 3. The voltage doubler power supply circuit employed in Smithy's zener diode checker. A suitable transformer for T1 is Home Radio Cat. No. TC7

VOLTAGE DOUBLER

"Those figures seem to be more than sufficient to me," said Dick. "It sounds as though this zener diode tester will need a power supply offering rather more than 25 volts at up to 100mA."

"True enough," confirmed Smithy. "For reasons which I'll explain shortly, the maximum current required from the supply will be nearer 140mA than 100mA. Dash it, I've just thought of a snag here!"

"What's that?"

"We'll obviously need a mains power supply to provide these voltages and current figures, and this will require a mains transformer offering a secondary voltage of about 30 volts or so. The trouble is that low-cost transformers offering a voltage of this nature aren't all that readily available."

Smithy pondered for a few moments.

which offers an actual a.c. voltage of 17 volts on its secondary."

Smithy turned to his bench and quickly scribbled out a circuit on his note-pad. (Fig. 3.)

"There you are," he remarked, passing the pad over to Dick. "Here's the circuit for the power supply section of the zener diode checker."

Dick looked doubtfully at Smithy's diagram. The most casual of observers would have noted the distinct expression of incomprehension which appeared on his face.

"Okay?" queried Smithy.

"Not really," replied Dick. "To be perfectly frank, I'm not quite certain how this circuit works."

"Come on, now," said Smithy a little irritably. "It's nothing other than a straightforward voltage doubler rectifier circuit."

"To you it may be straightforward,"

Your Local Supplier

LONDON

Established 1910

H. L. SMITH & CO. LTD.

Comprehensive stocks of components by all leading makers

287-9 EDGWARE ROAD
LONDON W2 1BE

Tel: 01-723 5891

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP

Tel: 01-723 4185/2926

ST. HELEN'S RADIO

Hi-Fi Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS
LONDON, W.10

Tel: 01-969 3657

NEW
15 watt Hi-Fi
£3.75 plus 25p postage & packing
each
AMPLIFIERS

7 TRANSISTORS - GUARANTEED PRINTED CIRCUIT - TESTED DESIGN BUILT - INSTRUCTIONS

A great new 15 watt HiFi amplifier is now available at the low cost of £3.75. Just look at the specification—Power 15 Watts R.M.S., frequency response 15-19000 c/s. Signal to noise ratio better than 70 db. Harmonic distortion 0.1%. Input sensitivity 750 mv into 2k. These make the H. Electronics HiFi amplifier the best at its price—order now.

H-ELECTRONICS.
105, Grange Road, London, S.E.25

grinned Dick cheerfully. "But to me it's nothing short of unfathomable!"

"Oh, all right then," said Smyth resignedly. "It looks as though I'll have to tell you how it works before we can get any further. To start off with, consider first the mains half-cycles which cause the upper end of the 17 volt transformer secondary to go positive. D1 and C1 form a standard half-wave rectifier circuit and, on these half-cycles, D1 conducts and causes C1 to become charged up such that its right-hand plate is positive. If there is no load on the output of the supply, C1 charges up to the peak value of the alternating voltage on the mains transformer secondary. Are you happy with that bit?"

"Yep," replied Dick. "It's all quite clear up to now."

"Good," returned Smyth. "Now let's look next at the half-cycles which cause the lower end of the 17 volt secondary to go positive. D1 does not conduct on these half-cycles and plays no part in what goes on. But D2 does conduct. Relative to the upper negative rail, the voltage applied to D2 consists of the positive half-cycles at the lower end of the secondary plus the voltage

stored as a charge in C1. Again assuming no load, C2 then becomes charged up to twice the peak value of the alternating voltage on the secondary."

"Gosh, I see it all now," exclaimed Dick. "What happens when you connect a load?"

"The voltage across C2," replied Smyth. "drops to a value which is lower than twice the peak voltage according to the current drawn by the load. C1 charges up on the first lot of half-cycles and discharges into C2 on the second lot of half-cycles. Incidentally, I said just now that, without a load, C1 charges to peak value and C2 charges to twice peak value. If we use silicon rectifiers, which in practice we are going to do in our zener diode tester, a voltage of about 0.6 volt is dropped across each rectifier when it conducts. So, under no-load conditions the voltage across C1 will be peak voltage minus 0.6 volt and that across C2 will be twice peak voltage minus 1.2 volts."

"Fair enough," said Dick. "What's the purpose of R1?"

"That's merely a surge limiting resistor," explained Smyth. "It could, incidentally, be 4.7Ω if a 5Ω resistor

can't be obtained."

FULL TESTER CIRCUIT

"Well," said Dick, "that's got the power supply bit cleared up. What about the rest of the zener diode tester circuit?"

"I'll draw that up for you now," said Smyth.

For several minutes Smyth worked carefully at his note-pad. He then triumphantly placed his pen on the bench and showed the circuit he had drawn to Dick. (Fig. 4.)

"Here we are," he said proudly. "Now in the complete circuit for the tester we have the voltage doubler supply which we have just discussed. Its output voltage couples to the constant current circuit which incorporates the BD124, this being a silicon power transistor. The base of the BD124 is held firmly at about 1.8 volts positive of the negative supply rail, this being the forward voltage drop across the three silicon rectifiers D3, D4 and D5. R2 causes these rectifiers to pass a forward current of some 30 to 40 mA, which brings them well into

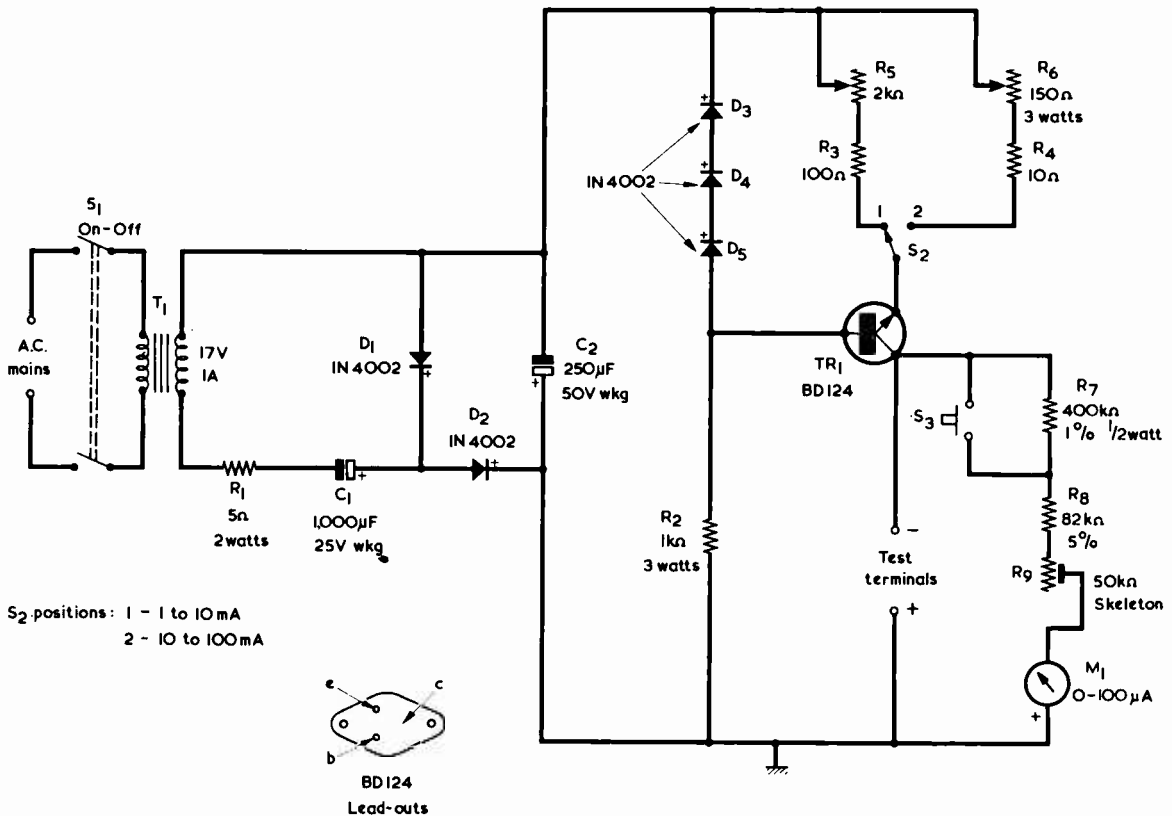


Fig. 4. Complete circuit of the zener diode checker. Full-scale deflection in the meter corresponds to 50 volts when S3 is open and to 10 volts when S3 is pressed. Unless otherwise specified, fixed resistors are ½ watt 10%. R5 may be a standard-size linear carbon track potentiometer, but a wire-wound component here would be preferable. The zener diode to be checked is connected to the test terminals

their conductive region."

"Isn't that rather a high current?"

"It's a little more than is required for the constant current application," agreed Smithy, "but I've chosen a fairly high current here because it will improve the regulation of the output voltage from the power supply when little or no current is drawn through the BD124."

"That constant current circuit," remarked Dick, "is a pretty familiar arrangement these days, isn't it?"

"Oh, definitely," stated Smithy. "It keeps popping up all over the place and it represents a particularly useful attribute of the transistor. The voltage between the emitter of the BD124 and the negative supply rail is about 1.2 volts, since approximately 0.6 volt is dropped across the base-emitter junction. If we insert variable resistance between the emitter and the negative rail we can vary the constant current which the transistor passes in its collector circuit. Should we set up the emitter resistance such that a constant current of 10mA is given in the collector circuit, that current will flow at all collector potentials from slightly positive of the base voltage to the full voltage on the positive supply rail."

"Is the current in the emitter circuit pretty well the same as that in the collector circuit?"

"Pretty near. Actually it's a little larger, since it's the collector current plus the base current. You'll notice that, in my circuit, you can switch in R5, which offers a current range of 1 to 10mA, or R6, which offers a current range of 10 to 100mA. R3 and R4 are current limiting resistors, and they ensure that you cannot accidentally set up the checker to too high a current."

"I see," said Dick. "Incidentally, why have you chosen a power transistor as the constant current device?"

"Because it may have to dissipate a fair amount of power. Let's assume that you get a voltage of around 32 volts from the power supply and that you short-circuit the test terminals when the emitter resistance is set up for a constant current of 100mA. Very nearly 3.2 watts will then be dissipated in the BD124. In practice it will have to be mounted on a heat sink. A flat metal plate about 2 inches square should be quite adequate."

Dick absorbed this information in silence then turned his attention to another part of the circuit.

"I suppose," he remarked, "that the 100 μ A meter is used as a voltmeter."

"That's right," confirmed Smithy. "Normally, it has a full-scale deflection corresponding to 50 volts, this changing to 10 volts when S3 is pressed. The idea is that you switch on the unit, whereupon the meter indicates the voltage between the collector of the BD124 and the positive line. You next set up the emitter resistance to the current value you require and connect the zener diode to be checked to the

test terminals. The meter reading then drops to the zener voltage of the diode. If this is lower than 10 volts you press the push-button to obtain a more precise reading. The reason for having a push-button rather than an ordinary switch is that there is then less risk of accidentally applying a high current to the meter when it's switched to read 10 volts."

"Why have you put a pre-set potentiometer in series with the meter?"

"Purely for convenience. The sensitivity of a voltmeter incorporating a 100 μ A meter is 10,000 Ω per volt. R7, at 400k Ω , drops 40 volts at full-scale deflection. At the same time, R8 and R9, together with the meter resistance, drop 10 volts at full-scale deflection. You could, if you liked, have a single close tolerance fixed resistor in place of R8 and R9, this having a value equal to 100k Ω minus the meter resistance. But it's easier to have an ordinary 5% resistor and a pre-set skeleton pot in series instead. All that you then have to do is to set up the pre-set pot with the aid of another voltmeter."

CONSTRUCTION

With an air of finality, Smithy rose and walked towards the hook on which his raincoat was hanging.

"Hey," said Dick, alarmed. "Where are you off to?"

"I'm going home," replied Smithy firmly. "You seem to forget that we packed in work about half an hour ago."

"Couldn't you hang on," asked Dick, "until I've actually made up this zener diode tester?"

"Dash it all," retorted Smithy. "I've already given you the circuit for it. How much longer do you want me to stay here?"

"Only for a little while," wheedled Dick. "I can get the tester made up in no time at all, and I'll just need your help for a few moments in getting it set up."

Smithy sighed.

"Oh, all right then," he said resignedly. "But you'll have to be quick about it. You should be able to find all the components you require in our spares cupboard or out on the benches."

Gleefully, Dick took up the circuit Smithy had drawn out and shot over to the spares cupboard. Consulting the diagram he started to take out the components that were required.

"Hallo," he remarked. "We don't seem to have any IN4002 rectifiers in stock."

"Not to worry," replied Smithy. "Any small silicon rectifier with a current rating of 1 amp and a peak inverse voltage rating of 100 volts or more will be more than adequate for D1 and D2. D3 to D5 can be any small

Your Local Supplier

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.

70-72 Holdenhurst Road
Bournemouth

Telephone 25232

SURREY

WITWORTH TRANSFORMERS TV Line out-put transformers

Manufacturers of the largest range in the country. All makes supplied.

Free catalogue.

Modern

BAIRD, BUSH, GEC, PHILIPS

Replacement types ex-stock.

For "By-return" service, contact London

01-948 3702

Tidman Mail Order Ltd., Dept. R.C.

236 Sandycombe Road,

Richmond, Surrey TW9 2EQ

Valves, Tubes, Condensers, Resistors,

Rectifiers and Frame out-put Transformers,

Mains Transformers also stocked.

Callers welcome.

SUSSEX

E. JEFFRIES

For your new television set
tape recorder, transistor radio
and hi-fi equipment

PHILIPS, ULTRA, INVICTA
DANSETTE, MASTERADIO, PERDIO,
MARCONI, PHILCO FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

ELECTRONIC COMPONENTS
RADIO & TELEVISION

For the convenience of Irish
enthusiasts we supply

The Radio Constructor

Data Books and

Panel-Signs Transfers

Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

AUDIO AMPLIFIERS



16 Transistor & Valve Designs for the Home Constructor

Amplifiers for Tuner Units, Record Players, Tape Recorders, Public Address, etc., etc.

Includes contributions by such well-known authors as

A. S. Carpenter, A. Kinloch, E. Govier, G. A. French, F. G. Rayer, P. F. Bretherick, K. Jones, D. Aldous, R. Murray-Shelley, C. Swires, G. A. Stevens and V. E. Holley

Edited by J. R. Davies

124 pages

PRICE 53p

Postage 6p

To: DATA PUBLICATIONS Ltd.,
57 Malda Vale London W9

Please supply copy(ies) of "Audio Amplifiers", Data Book No. 18. I enclose cheque/

crossed postal order for.....

Name.....

Address.....

.....

.....

.....

.....

.....

.....

.....

.....

silicon rectifiers. Incidentally, I should have told you that the two pots in the emitter circuit of the BD124 need to be fitted with pointer knobs, and they'll need scales behind them on the front panel. Temporary paper scales will do for the time being."

Very soon the Workshop was the scene of a great stir and flurry on the part of Dick as, labouring like a man possessed, he set to work with screwdriver, pliers and soldering iron. Fortunately, the chassis and panel assembly he had unearthed already offered quite a number of conveniently positioned holes and the amount of metalwork involved in fitting the zener diode tester components to it was very small. He made the heat sink for the BD124 from a small piece of tinplate. Rather than insulate the transistor from the heat sink he soldered the sink to several tags of a tagstrip so as to insulate it from chassis, and then bolted the transistor directly to it. Smithy nodded his approval at this approach.

After a surprisingly short time, Dick announced that the tester was complete. Smithy walked over to inspect Dick's handiwork and to check for wiring errors.

"Very good," he commented in a satisfied tone. "Despite the rush, you've made quite a nice job of it."

Dick beamed with pleasure.

"I tell you," he remarked proudly, "I may not be too hot on the theory of electronics, but when it comes to the practical side I'm a real gone kiddy, mate!"

"All right, all right," said Smithy, as he consulted his circuit diagram. "Now before we do anything else let's see what sort of voltage we've got available for testing purposes. First set up R9 so that it inserts maximum resistance. Then switch on and measure the voltage across the 1kΩ resistor, R2."

Dick adjusted R9 as Smithy had requested, then connected the zener diode tester to the mains and switched on. The needle of the 0 - 100µA meter on the front panel rose to indicate approximately 72µA.

"So far," he stated, "so good. There are no little puffs of smoke coming out of the works as yet!"

He switched his testmeter to a volts range and applied its test prods across the 1kΩ resistor.

"I'm getting a reading," he called out, "of 36 volts."

"Good," said Smithy, obviously pleased. "This means that, at low currents, this gubbins will be able to check zener voltages very nearly up to that value. Now the next job is to set up R9. Connect your testmeter between the positive supply rail and the junction of R7 and R8 then tell me what it says."

Dick reapplied the test prods and switched his testmeter to a lower voltage range. (Fig. 5.)

"The testmeter's reading about 6.4 volts."

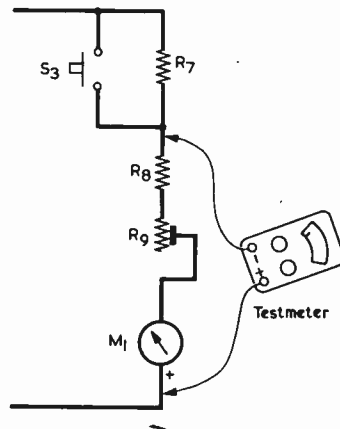


Fig. 5. Setting up R9. This component is adjusted for similar voltage indications in M1 and the testmeter

"Fair enough," commented Smithy. "The actual reading you'll get here depends of course, on the sensitivity of the testmeter. Now adjust R9 until both the testmeter and the 100µA meter give the same reading, with 100µA on the meter in the testmeter corresponding to 10 volts. Don't forget that one needle will rise as the other falls."

With an expression of heavy concentration, Dick carefully adjusted the pre-set potentiometer.

"Both meters are now giving the same reading," he said eventually.

"Good," said Smithy. "You can disconnect the testmeter. The next job is to calibrate R5 and R6. Start off by setting S2 to the '1 to 10mA' position and adjust R5 to give maximum resistance. Then connect your testmeter, switched to read current, across the test terminals. You'd better switch the testmeter to a high current range initially in case there's excessive current due to a fault condition."

As requested, Dick set R5 to insert maximum resistance, switched his testmeter to a high current range and connected it to the test terminals. (Fig. 6.) The testmeter needle was barely deflected. Dick successively selected lower current ranges until he finally obtained a useful reading.

"The testmeter," he remarked, "is indicating about 0.8mA."

"Excellent," said Smithy. "Check next that you can adjust R5 for a range of current readings from 1 to 10mA. There'll be a bit of potentiometer travel outside this range at both ends but that doesn't matter."

Dick quickly checked the current range offered by R5.

"It's just as you say, Smithy," he said. "R5 gives a range, over most of its track, from 1 to 10mA."

"Right," returned Smithy. "The next job is to calibrate R5 in terms of current. For the time being it will be

sufficient to mark on its scale just the 1, 2.5, 5, 7.5 and 10mA points. You can make a more comprehensive calibration later on when you've got a bit more time."

CHECKING PERFORMANCE

Dick took a pencil from his pocket and marked, on the temporary paper scale behind the pointer knob of R5, lines corresponding to readings of 1, 2.5, 5, 7.5 and 10mA in his testmeter.

"You now," said Smithy, "put S2 in position 2 and repeat the process with R6, only this time the range is from 10 to 100mA. Just in case there's anything wrong, start off with the testmeter switched to a high current range and with R6 at maximum resistance, then cautiously reduce the resistance given by R6."

Dick followed Smithy's advice and shortly announced that R6 was offering a satisfactory current range from 10 to 100mA. At Smithy's bidding he next calibrated the scale for R6 at the points corresponding to 10, 25, 50, 75 and 100mA.

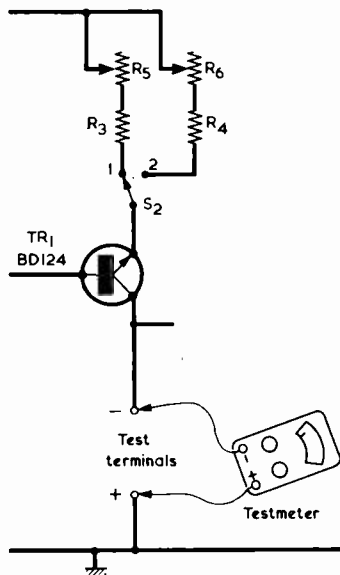


Fig. 6. Calibrating R5 and R6. This process is carried out with the testmeter switched to suitable current ranges

"That's very good," commended Smithy. "We should next check that we are getting a constant current from that BD124. Find a 2k Ω standard size pot and insert it in series with the meter."

Smithy's assistant once more visited the spares cupboard. He quickly returned with the potentiometer and connected it in series with his testmeter. (Fig. 7.)

"Set up R6 in the tester for a current of 15mA," Smithy continued, "then adjust the 2k Ω potentiometer. That

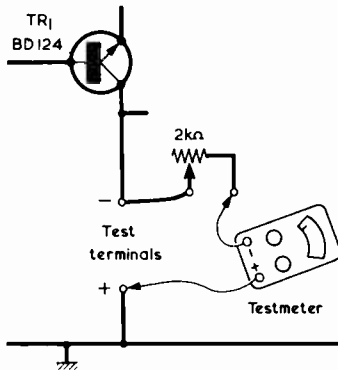


Fig. 7. Inserting a 2K Ω potentiometer in series with the testmeter provides a check on the efficiency of TR1 as a constant current device

15mA reading should remain virtually unaltered at all settings of the 2k Ω pot."

Looking closely at his testmeter, Dick turned the spindle of the 2k Ω potentiometer.

"This is quite fantastic," he remarked. "I can't see any movement in the meter needle at all, and it just stays fixed at 15mA. Well, we've certainly got a constant current here! Any other tests, Smithy?"

"Just a few voltage measurements, and then we've finished. Take your testmeter off the test terminals, switch it to read voltage and connect it across R2 again. Next, short circuit the test terminals, then tell me the voltages across R2 for currents of 25mA, 50mA and 100mA. You get those by adjusting R6, of course."

"No sooner said," grinned Dick, "than done! Hang on a jiffy while I reconnect the testmeter. Ah, here we are. Well now, at a current of 25mA, the voltage across R2 is 34 volts, at 50mA it's 32 volts, and at 100mA it's 28 volts."

"That's not bad at all," commented Smithy. "The zener testing voltage is restricted to a little less than 28 volts at 100mA and to a little less than 32 volts at 50mA. These voltages should accommodate pretty well all of the zener diodes we are likely to encounter in simple electronic work. Right now, we're all set to check out those zener diodes of yours. I think a current of 10mA will be adequate for the small diodes that you have here."

Smithy walked over and seated himself in front of the now completed diode tester. He set up R6 for 10mA, took a diode from Dick's box and connected it to the test terminals. The meter reading dropped to 24 on its scale.

"That," remarked Smithy, "is a 12 volt zener diode. Let's try another one."

NEW BOOKS

ABC'S OF
ELECTRONIC POWER
By Rufus P. Turner £1.50

THE MANUAL OF
CAR ELECTRONICS
By Rudolph F. Graf &
George J. Whalen £3.50

99 WAYS TO IMPROVE
YOUR HI-FI
By Len Buckwalter £1.50

PRACTICAL DESIGN
WITH TRANSISTORS
(Rev. Edition)
By M. Horowitz £2.40

The Mazda Book of PAL
RECEIVER SERVICING
By D. J. Seal £3.50
(Published: Foulsham Tech.)

INTRODUCTION TO
VIDEO RECORDING
By W. Oliver £1.50
(Published: Foulsham Tech.)

FOULSHAM-SAMS
TECHNICAL BOOKS
(W. FOULSHAM & CO. LTD.)
VEDVIL RD., SLOUGH, BUCKS, ENGLAND

The
RADIO CONSTRUCTOR

ANNUAL
SUBSCRIPTIONS
to this magazine
may be obtained
through your
newsagent
or direct from the
publishers
ONLY £2.70
per year, post free

Please send remittance with name
and address and commencing issue
required to:

DATA PUBLICATIONS LTD
57 Malda Vale London W9 1SN

He picked up another diode and coupled it to the tester. The meter needle fell to around 15. Smithy pressed S3, whereupon the needle rose to 76.

"And that," said Smithy, as he released S3 and then removed the diode, "is a 7.6 volt diode."

He picked up a third diode and connected it to the tester. The meter needle fell almost to zero. Smithy pressed S3 and the meter needle rose to indicate slightly more than half a volt.

"It looks," said Dick, who had been following Smithy's actions with avid attention, "as though you've got a faulty diode there. It must have a short-circuit in it or something."

"It's more probable," replied Smithy "that I've connected it to the tester wrong way round. Don't forget that a zener diode is just an ordinary silicon diode when the current flows through it in the forward direction."

Smithy changed over the diode connections whereupon the tester indicated that the device had a zener voltage of 8.3 volts. Smithy next swung R6 over the range of 10 to 25mA, demonstrating to Dick that the zener voltage increased only slightly at the higher currents.

FURTHER SUPPLY

"This is absolutely fascinating," said Dick. "All you've got to do is to simply connect the zener diode and the tester tells you its zener voltage with no further trouble."

"That's pretty well the substance of it," averred Smithy. "And you can, of course, adjust zener current to any value you like from 1 to 100mA and thereby find the zener characteristic as well. You mustn't, of course, pass more current through the zener diode than its wattage rating allows. The highest voltage appearing across the test terminals is always less than 36 volts, so there's no great shock risk if you should accidentally touch those terminals. If you're worried about shock you can, in any case, switch off the tester whilst you're connecting and disconnecting the zener diodes, switching it on for the reading only."

"I think it's a jolly good tester," said Dick, gazing at the instrument fondly. "Another thing is that it also lets you find the correct polarity for the diode. You could use it for checking the polarity of ordinary diodes too, and for finding out whether they're silicon or germanium."

"That's true enough," confirmed Smithy. "A silicon diode will give a forward voltage reading of about 0.6 volt whilst a germanium diode will give a reading of less than 0.25 volt. Now let's have a look in my bench drawer."

As Dick watched him curiously, Smithy walked over to his own bench, opened a drawer and produced a cardboard box which was an exact


duplicate of that on Dick's bench. The look of sudden suspicion on Dick's face rapidly changed to one of furious revelation when Smithy took off the lid of the box, to reveal contents that were precisely similar to those in Dick's box.

"By a strange quirk of circumstances," remarked Smithy casually, "it so happens that I, also, have purchased by mail-order a Bumper Bargain Parcel of 200 unmarked and untested zener diodes. I received mine last week but, I'm afraid, I've felt rather too lazy to actually make up a tester for sorting them out. However, seeing that we now have such a tester available I shall be delighted to take advantage of it when you have finished checking your own diodes."

"Why," spluttered Dick indignantly, "you crafty old twister! You've been pretending all along that you were giving up your spare time to help me out, when what you were actually doing was conning me into making up a tester for *your* components which *you* were too idle to build!"

"Another way of looking at the situation," said Smithy gently, "is that if I hadn't had a need for the tester myself I would not then have had the inducement to devote a considerable amount of my spare time in helping you build it."

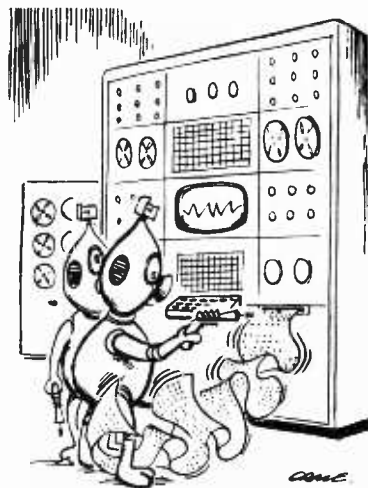And by the time his outraged assistant had mustered up a suitable reply to this argument Smithy had already returned his box of diodes to his bench drawer, picked up his raincoat and quitted the Workshop for the day. ■



"Resistance - is - useless - Take - me - to - your - programmer!"

Radio Topics

By Recorder

GLASS-CASED CARTRIDGE FUSES ARE familiar devices, but it is surprising how little many of us know about their modes of operation.

To start off with, quite a few people have the impression that a glass cartridge fuse blows at the current at which it is rated. If the fuse is of the type familiar in electronic equipment such is *not* the case. The rating of a fuse of this type is normally the maximum *carrying* current it can handle, and the fuse should be capable of passing this current without rupture for 1,000 hours. To find the blowing current you have, theoretically, to look it up in the fuse manufacturer's literature! This is, to say the least, a process which can hardly be described as being convenient. Fortunately, you can be pretty certain in practice that small glass cartridge fuses will blow at 2 to 3 times the current at which they are rated although, even then, they may not break the circuit instantaneously. At higher currents a much quicker blowing, and consequent breaking of the circuit, is given.

CHOOSING A FUSE

These particulars apply only to glass cartridge fuses of the type we use in electronic gear. Other types of fuse may be rated in different manner. For instance, the glass types with pointed brass end-caps that are encountered in car electrical systems are rated at their blowing current, and not at their maximum carrying current.


Another variant in the cartridge fuse field is the delayed action or anti-surge type, which is capable of withstanding a short surge without blow-

ing. Fuses of this nature are inserted in circuits where there is a relatively heavy switch-on surge, as occurs for instance between the rectifier and reservoir capacitor in a mains power supply. Bulgin 'Pak' fuses are typical examples of the anti-surge type and will normally resist currents of 75% above rating for 120 seconds, and currents of 100 to 175% above rating for 5 to 30 seconds. These fuses blow in less than 1 second at 200% above rating. Other types of anti-surge fuse are also available.

There are several recommended approaches towards selecting the fuse rating for a circuit. One school of thought counsels that a fuse should have a rating which causes it to blow at the 'danger current' in the circuit in which it is to be used, even if this 'danger current' is much higher than the normal standing current. 'Danger current' is the level at which the risk of expensive burn-out in one or other of the components is likely to become serious, and the fuse employed should then be rated at about a third of this current. In electronic work, unfortunately, it is usually difficult to define a 'danger current' because the term tends to be rather meaningless. When the current in an electronic circuit rises by even a small amount above its normal level then it is obvious that something is wrong and it would seem reasonable to expect that the fuse would give some level of protection. This is where an alternative approach towards fuse selection comes into play. This second school of thought recommends that a fuse in an electronic circuit should have a rating which is the next figure above the normal standing current the fuse will have to pass. Should there be surges in the circuit, an anti-surge type should be used.

This second method of choosing a fuse is the better, although most of us know from experience that a fuse rated just above standing current will tend to burn out, even under perfectly normal fault-free running conditions, more frequently than a fuse having a higher current rating again. However, it is impossible to lay down any hard and fast rule here. If fuse failure under fault-free conditions becomes a nuisance, just fit a fuse that is one step higher in current rating. Many service engineers will recall that set-manufacturers occasionally increase the recommended rating of fuses fitted to their products because of a high incidence of unexplained fuse failures in the field. Finding the best fuse rating for a circuit is just one of the many practical problems of electronic design.

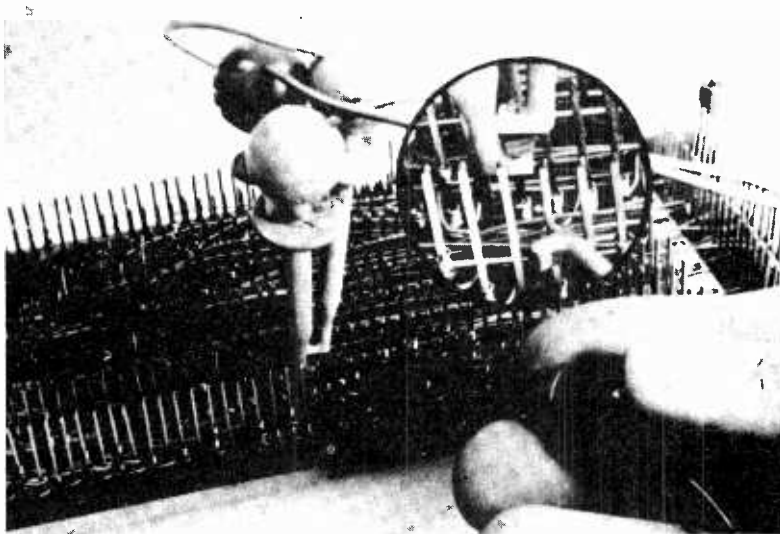Fuses are also, unhappily, not of much use in modern circuits employing silicon semiconductor devices. If an overload causes a silicon device to be taken beyond breakdown level, it will almost always break down before any fuse in series with it breaks the circuit.



A family of 'E-Z-Mini-Hooks' in action. These provide reliable temporary connections in crowded layouts

So, there we are. Fuses are very useful devices, but the selection of a suitable type can sometimes be tricky. And they may not give quite the circuit protection that we fondly imagine they do.

IMPOSSIBLE HOOKER

'Impossible hooker' is the term applied by its manufacturers to the 'E-Z-Mini-Hook', several of which can be seen in the accompanying photograph where they are making temporary connections in a crowded wire-wrap terminal layout. If you pronounce the 'Z' of 'E-Z' in the American manner, i.e. 'zee', the choice of letters becomes more obvious.

The 'E-Z-Mini-Hook' is 2½ in. long, and has a nylon body down the inside of which travels a gold plated beryllium copper conductor shaped at the end in the form of a hook. This hook emerges against internal spring pressure if the spherical top of the body is pressed, and it may then be passed over any wire or small tag. When the top of the body is released, the wire or tag is held firmly between the hook and the bottom surface of the nylon, thereby providing a reliable connection for testing or jumpering purposes. The connection from the hook is carried by a thin insulated lead which is taken out from the spherical top of the body.

There is a small hole at the bottom of the moulding into which the end of the hook retracts when it is not extended. This hole is large enough to allow small tag spills to pass through, thereby providing another means of temporary connection. In both methods of connection there is no risk of short-circuit to adjacent conductors. In the enlarged section of the photograph, two 'E-Z-Mini-Hooks' are connected to a tag which passes

through the hole in the moulding. The third is connected by means of the extended hook.

'E-Z-Mini-Hooks' are flash-tested up to 4kV, will operate on running test up to 2kV, and have a current capability of 1.5A. They are available singly or in a number of assemblies in which they are wired to other 'E-Z-Mini-Hooks' or to plugs and sockets of various types. Further details are available from the U.K. and Ireland distributor, British Central Electrical Co., Ltd., Briticent House, New Street, Ringwood, Hampshire.

RECTIFIER POLARITY

Finally, a little hint which can possibly save you quite a bit of grief.

When wiring up a mains power supply using unbranded silicon rectifiers, always fit the reservoir and smoothing capacitors last. And, before you do so, connect a testmeter switched to a volts range to the circuit points where the reservoir capacitor will connect, and then apply the mains input. This will confirm for certain whether or not the voltage which will be applied to the electrolytics is of correct polarity. The voltmeter will, of course, give a lower reading than will occur when the electrolytics are fitted later, but this doesn't matter. The whole function of the test is simply to confirm polarity.

The reason for the test is that one can never be entirely sure which lead-out of an unbranded rectifier is anode and which is cathode. Ohmmeter tests for rectifier polarity tend to be confusing and the most satisfactory method is to check the polarity when a rectifier is in its working circuit. Better to be safe, with a simple quick voltmeter test, than sorry, with a couple of broken-down electrolytics!

THE MODERN BOOK CO

BASIC TELEVISION

New Picture Book Manual in the Common Core Series

£3.50

Postage 20p

Practical Transistor Novelty Circuits
by H. Ness 40p *Postage 5p*

T.V. Technician's Bench Manual
by G. W. Wilding £2.50 *Postage 12p*

A Mullard Minibook Semiconductor Devices 38p *Postage 5p*

Tape Recorders
by H. W. Hellyer £2.25 *Postage 12p*

Making & Repairing Transistor Radios
by W. Oliver £1 *Postage 10p*

Servicing with the Oscilloscope
by Gordon J. King £1.80 *Postage 12p*

Servicing Transistor Radio Receivers
by F. R. Pettit 75p *Postage 7p*

The Mazda Book of Pal Receiver Servicing
by D. J. Seal £3.50 *Postage 15p*

Handbook of Transistor Equivalents and Substitutes
by B. B. Babani 40p *Postage 5p*

Beginner's Guide to Radio
by Gordon J. King £1 *Postage 10p*

Using an Oscilloscope
by D. W. Easterling 70p *Postage 7p*

Principles of Transistor Circuits
by S. W. Amos £1.50 *Postage 10p*

Radio Data Reference Book
by G. R. Jessop £1 *Postage 10p*

20 Solid State Projects for the Car and Garage
by R. M. Marston £1.20 *Postage 7p*

Transistor Circuits in Electronics
by Haykin £2.50 *Postage 12p*

Practical Wireless Service Manual
by Newnes £1.50 *Postage 10p*

T.V. Fault Finding 405/625 Lines
by J. R. Davies 50p *Postage 7p*

Radio Valve & Transistor Data
by A. M. Ball 75p *Postage 10p*

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the.....issue of THE RADIO CONSTRUCTOR

16 words at 4p
= 64p.

**ALL WORDING
IN
BLOCK LETTERS
PLEASE**

I enclose remittance of.....being payment at 4p a word. MINIMUM 60p.
Box Number, if required, 10p extra.

NAME.....
ADDRESS.....

Copy to be received four weeks prior to publication. Published on the 1st of every month.

SMALL ADVERTISEMENTS

Rate: 4p (9d) per word. Minimum charge 60p (12/-).
Box No. 10p (2/-) extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W9 1SN)

SERVICE SHEETS (1925-1972) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex. Telephone: Hastings 29066.

BUILD IT IN a DEWBOX robust quality plastic cabinet 2 in. x 2½ in. x any length. S.A.E. for details. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. Write now - right now.

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p. post free.

NEW CATALOGUE NO. 18, containing credit vouchers value 50p, now available. Manufacturers new and surplus electronic and mechanical components, price 23p post free. Arthur Sallis Radio Control Ltd., 28 Gardner Street, Brighton, Sussex.

FOR SALE: VHF KIT, 80 - 180 MHz. Receiver, tuner, converter. World wide sales. Incomparable. £4.00 or s.a.e. for literature. Johnsons (Radio C), Worcester WR1 2DT.

SHARPEN YOUR RESPONSES with Vernitron ceramic i.f. resonators. Set of four TF-04 442, 455kHz, with associated capacitors for bandwidth 2, 4, 5.7, 7.5, 10 or 12kHz (state which), £1.85, U.K. post 5p. Mail order only. AMATRONIX LTD., 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

MECCANO FOR "CYCLOPS" - Special Pack of all Meccano parts required - £2.98 including postage. Send off today to *The Meccano Spare Parts Specialists* and start building! "Everything Meccano" at M. W. MODELS, 165 Reading Road, Henley-on-Thames, Oxon. Telephone 3342.

A.T.U. KIT £4.50; assembled £5.50 (plus 30p P/P in both cases). Covers Short Wave Amateur & Broadcast bands, Marine bands, etc. Artificial earth/aerial bandswitch (complete aerial plus aerial peaking system for SOLID STATE sets) doubles as extremely efficient 'earthing' system for Communications Receivers and Transmitters £4.50 (plus 30p P/P). 3p stamp for full range of Partridge World Record Aerial, and aerial systems. BOX 6, Partridge Electronics Ltd., Broadstairs, Kent.

'SHORTWAVE VOICES OF THE WORLD', £1.55; an exceptional book. *World Radio TV Handbook*, £2.80. *How To Listen to the World*, £1.35. Under £2 postage 10p worldwide. I.R.C./3p for price list. (Mail only). David McGarva, Box 114B, Head Post Office, Edinburgh, EH1 1HP.

FOR SALE: V.H.F. Signal Generator, perfect order, £9 Buyer collects. Also quantity valves, mostly new. Badman, 34 South Street, Sheringham, Norfolk. Telephone: Sheringham 2502.

FOR SALE: Cossor transistorised portable LW, MW and VHF. Black leather. 6½ x 4 x 2 in. £3. Box No. G179.

(Continued on page 125)

BENTLEY ACOUSTIC CORPORATION LTD.

38 Chalcot Road, Chalk Farm
LONDON, N.W.1.
01-722-9090

The Old Police Station
Gloucester Road
LITTLEHAMPTON Sussex
PHONE 6743

Please forward all mail orders to Littlehampton

OA2 .30	12BE6 .30	EB34 .20	ELL80 .75	PL82 .28	UY41 .38
OB2 .30	12K5 .50	EB91 .10	EM80 .37	PL83 .30	UY85 .31
3UG4 .30	19AQ5 .24	EB041 .48	EM81 .37	PL84 .28	X41 .50
5V4G .33	20P4 .89	EB081 .29	EM83 .75	PL904 .60	AC165 .23
5Y3GT .25	30C15 .35	EBF80 .30	EM84 .31	PL908 .90	AD140 .36
5Z4G .33	30C17 .74	EBF83 .38	EM87 .34	PL909 .30	AD449 .50
630L2 .53	30C18 .58	EBF89 .26	EY51 .29	PL902 .75	AD161 .45
6A05 .21	30F35 .61	EC92 .34	EY81 .35	PY3372 .50	AD162 .45
6A76 .18	30FL1 .58	ECC311 .50	EY83 .54	PY81 .24	AF114 .25
6A08 .19	30FL2 .58	ECC81 .16	EY87/6 .27	PY82 .22	AF115 .15
6B16 .39	30FL4 .66	ECC82 .19	EY88 .40	PY83 .26	AF121 .30
6B46 .19	30L15 .55	ECC83 .21	EZ40 .40	PY88 .31	AF126 .18
6B66 .20	30L17 .65	ECC84 .28	EZ80 .19	PY900 .95	BC107 .13
6B16 .43	30P12 .69	ECC85 .32	EZ81 .20	PY900 .31	BC108 .13
6B16 .39	30P18 .58	ECC86 .38	EZ82 .22	PY901 .30	BC113 .20
6BR7 .79	30PL1 .57	ECC87 .27	HVR2 .53	QOQ03/	BC118 .23
6BW6 .72	30PL13 .75	ECF82 .25	KTW61 .63	10 1.20	BCZ11 .38
6BW7 .50	30PL14 .62	ECF86 .64	KTW62 .63	R19 .28	BF159 .25
6BZ6 .31	30PL15 .87	ECH42 .57	KTW63 .50	PY82 .22	BF163 .20
6C4 .28	35A3 .48	ECH81 .25	KT66 .80	U25 .62	BF180 .30
6CU5 .30	35L6GT .42	ECH83 .38	KT66 .44	U25 .63	BY100 .18
6F1 .59	35W4 .23	ECH84 .34	PC86 .44	U191 .56	BY126 .15
6F18 .45	32Z4 .24	ECL80 .28	PC97 .42	U251 .51	BY127 .18
6F23 .65	35Z5 .30	ECL81 .28	PC90 .29	U301 .40	OA81 .09
6F28 .60	50C5 .32	ECL83 .52	PCC84 .27	U801 .76	OA91 .09
6H6GT .15	50L6GT .45	ECL84 .54	PCC88 .39	UABC80	OA95 .09
6K7G .10	DAF91 .20	ECL86 .33	PC89 .42	UBC81 .30	OC23 .38
6K9G .16	DAF96 .33	ECL89 .42	PCF89 .46	UBC82 .38	OC24 .38
6L6GT .39	DF91 .14	EFA1 .58	PCF80 .26	UBF80 .28	OC25 .38
6Q7G .43	DF96 .34	EF80 .21	PCF82 .30	UBF89 .28	OC35 .32
6U4GT .60	DK91 .26	EF83 .54	PCF84 .40	UC92 .35	OC44 .30
6V6G .17	DK92 .35	EF84 .44	PCF86 .44	UC94 .33	OC45 .30
6X4 .20	DK96 .35	EF86 .27	PCF801 .28	UC95 .33	OC46 .15
7Y4 .60	DL92 .23	EF89 .23	PCF802 .37	UC98 .31	OC70 .13
9D7 .78	DL96 .35	EP91 .17	PCF806 .35	UC92 .35	OC71 .11
10F1 .75	DL96/2 .22	EP92 .25	PCF82 .29	UC91 .29	OC72 .20
10F18 .35	DY802 .29	EF183 .25	PCL83 .54	UC92 .30	OC74 .23
12A6 .63	EBOCC1.65	BF184 .27	PCL84 .32	UC93 .48	OC75 .11
12AC6 .40	E80F 1.20	BH90 .34	PCL805 .37	UF41 .50	OC78 .15
12AE6 .40	E80F 1.60	EJ24 .44	PCL86 .44	UC98 .29	OC79 .15
12AE6 .48	E180F .90	EL41 .53	PD500 1.44	UF85 .34	OC81 .11
12AE18 .23	EABC80	EL42 .53	PN45 .40	UF86 .63	OC81D .11
12AU6 .21		EL84 .21	PFL200 .50	UF89 .27	OC82 .11
12AV6 .28	EAF42 .48	EL73 .23	PL36 .44	UL41 .44	OC84 .20
12BA6 .60	EAF801.50	EL95 .32	PL81 .42	UL84 .28	OC84 .24

All goods are unused and boxed, and subject to the standard 90-day guarantee. Terms of business: Cash or cheque with order only. No C.O.D. orders accepted. Post/packing charge 3p per item subject to a minimum of 9p per order. Orders over £5 post free. All orders despatched same day by first class mail. Complete catalogue with conditions of sale 7p post paid. Any parcel insured against damage in transit for only 3p extra per order. Business hours 9 a.m.-5.30 p.m. Sats. 9 a.m.-1 p.m. Littlehampton closed Sats. No enquiries answered unless S.A.E. enclosed for reply.

TECHNICAL TRAINING in Radio, Television and Electronic Engineering

Let ICS train You for a well-paid post in this expanding field. ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma Courses in Radio, TV Engineering and Servicing, Colour TV Servicing, Electronics, Computers, etc. Expert coaching for:

- * C.G. TELECOMMUNICATION TECHNICIANS CERTS
- * RADIO AMATEURS EXAMINATION
- * GENERAL RADIOCOMMUNICATIONS CERTIFICATES
- * C.G. RADIO SERVICING THEORY

CONSTRUCTOR COURSES

Build your own transistor portable, signal generator, multi-test meter—all under expert guidance. POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

Member of the ABCC.

Accredited by the C.A.C.C.

Name _____ Age _____

BLOCK CAPITALS PLEASE

Address _____

INTERNATIONAL CORRESPONDENCE SCHOOLS

RA 33

INTERTEXT House,
Stewarts Road,
London SW8 4UJ

ICS
Gets you there.

RADIO OPERATORS

**DO
YOU
HAVE**

PMG I
PMG II
MPT
2 YEARS'
OPERATING
EXPERIENCE

?

POSSESSION OF ONE OF
THESE QUALIFIES YOU
FOR CONSIDERATION
FOR A RADIO OFFICER
POST WITH THE
COMPOSITE SIGNALS
ORGANISATION

On satisfactory completion of a 7 months specialist training course, successful applicants are paid on scale rising to £2365 pa; commencing salary according to age - 25 years and over £1664 pa. During training salary also by age, 25 and over £1238 pa with free accommodation.

The future holds good opportunities for established status, service overseas and promotion.

Training courses commence every January, April and September. Earliest possible application advised.

Applications only from British-born Male and Female UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered.

Full details from:


**Recruitment Officer,
Government Communications
Headquarters,
Room A/1105,
Oakley Priors Road,
CHELTENHAM,
Glos., GL52 5AJ.
Tel: Cheltenham 21491. Ext. 2270.**

NEW STYLE SELF-BINDER

for "The Radio Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

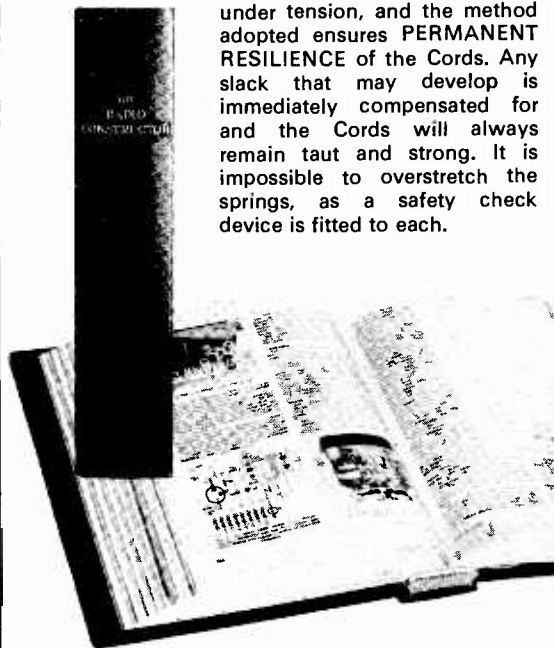

PRICE **75p** P. & P. 14p

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 123)

RADIO CONTROL FOR MODELS. We supply all components and materials necessary to construct a professional multi-channel control system. S.A.E. for leaflet. Mail order only. Aercon Developments, 85 Netherfield Road, Sandiacre. Nottingham.

FOR SALE: Turmix Swiss kitchen mixer, with liquidiser and 3 sets stirring attachments. 240V, 50Hz Full working order. £5. Box No. G182.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £2.00 per annum. (U.K. and British Commonwealth), overseas 6 Dollars or £2.50. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

FOR SALE: *Radio Constructor*, *Practical Wireless* & *Practical Television* magazines. Reasonable prices. Single issues. All enquiries answered. S.A.E. G. Charnley, 18 Nether Street, Finchley, London N12 7NL.

ARE YOU A MOTORING ENTHUSIAST? The Seventy Motor Club caters for all types of motor sport-racing, rallies, hill climbs, etc. Monthly Bulletin free to members. For full details write to: The General Secretary, Colin Peck, "Dancers' End", St. Winifred's Road, Biggin Hill, Kent.

FOR SALE: Tannoy p/a type weather-proofed microphone, £1. Marine freq. xtals, 2009, 2306, 2381kHz. ¼ in pin spacing. £1 each. Box No. G185.

TECHNICAL & INFORMATION SERVICES. For readers of *The Radio Constructor* with specific design and installation difficulties, in the fields of radio and television, novelty electronics, and related add-on R. and TV and tape equipment. For diagrams, circuits etc. available to readers own needs for specific projects. Problems dealt with. Enclose no money. Write to: 25 Poynter Road, Bush Hill Park, Enfield, Middlesex.

HOLIDAY ACCOMMODATION. Burwood Lodge Hotel, Dawlish Road, Teignmouth, South Devon. Especially suitable for parents with young children. Facing south, on the cliffs, direct access by private path to the sea. Mothers' kitchen, automatic washing machines, baby listening service. Licensed lounge. Ample free parking.

TRANSFORMERS REWOUND. Output or mains types. Specials made to order at reasonable prices. S.A.E. Enquiries. Ratcliffe, 18 Beech Avenue, Thongsbridge, Huddersfield, Yorks., HD7 2SX.

"MEDIUM WAVE NEWS" Monthly during Dx season - Details from: K. Brownless, 7 The Avenue, Clifton, York.

FOR SALE: Heathkit radio gear: Oscilloscope £37, Sine/square generator £22, Millivoltmeter £19, Valve-voltmeter £20, Wattmeter £25, Quad 22 and Armstrong 12-12 watt stereo amplifier £39. All in excellent condition. Box No. G190.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 1495.



MICROJET WELDER
A TINY FLAME BUT BIG RESULTS
PLANE TYPE
£11.50

A precision tool using a combination of butane and compressed oxygen. Two pencil lead thin flame sizes. Adjustable to 5,000°F. Cuts metals, welds, brazes and solders etc. gold and silver. Ideal for repair and construction work, model engineering, electricians, silversmiths, dental, modelling jewellery, computer servicing. Up to 40 min. operation on fuel supplied. Replacement set 2 Oxygen, 1 Butane cylinders, £1.50 inc. post. Our price £11.50 + 31p. & p. Send £11.81.



SUITS FOR ALL DOMESTIC APPLIANCES & POWER TOOLS INTRODUCTORY PRICE ONLY
£1.69

Store cable tidily. Heavy duty 3-core cable fitted unbreakable rubber standard 13 amp fused 3-pin plug & 3-pin socket. Saves trouble fitting yourself. For Domestic Appliances, Garden Power Tools, Hedge Trimmers, Mowers, etc. 30ft. app. cable & FREE storage reel £1.69 + 41p p. & p. Send £2.10. 15ft. app. £1.20 + 35p p. & p. 50ft. app. £2.20 + 41p p. & p. 75ft. app. £3. 50p p. & p. 100ft. app. £3.75 + 55p p. & p. 50 ft. app. 'Roverpoint' cable with winder reel, socket, plug, carry handle. £3.99 + 41p p. & p.



BINOCULAR MAGNIFIER
FOR PROFOUND CLOSE-UP WORK LEAVES DOWN HONORING PRICE

See close up work with less eye strain and fatigue. Lightweight adjustable headband. Powerful optically ground lenses from Continental glassworks. Can be worn over normal glasses. An essential aid in electronics, modelling, industry, Home and workshop, stamp collecting, jewellers, watch-making and any fine work. 2½x magnification. £5.25 + 35p p. & p. Send £5.60 3x model 50p extra. State model. TWIN-BEAM SPEC-LAMP - Worn just like a pair of spectacles. Two powerful spot lamps illuminate working area. Can be worn with Binocular Magnifier. Batt. operated. Only £1.90 + 10p p. & p. Send £2.



3 DISTRIBUTION PANEL

Safe and quick. FOUR 13 amp 3-pin shuttered Socket Outlets Red neon warning indicator operates when in use. Only £2.40 + 35p p. & p. Total £2.75. Also Da Luxe Model (illus.) PLUS On/off switch PLUS Magnetic Contact Braker - If you draw too much current it switches off automatically. PLUS 30ft. (9 metres) approx. lead, £6.75 + 40p p. & p. Total £7.15. Bonus offer: if required, set of four fused 13 amp plugs 50p extra. Post free if ordered with above.

National Giro Account No. 553-8254

JOHN DUDLEY & CO. LTD. (Dept. RC.2), 361 Cricklewood Lane, London, N.W.2. Tel.: 01-458 5917. Callers welcome. Easy parking.

FREE TO AMBITIOUS ENGINEERS

- THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

SEND FOR YOUR FREE COPY TO-DAY

NEW OPPORTUNITIES is a highly informative 76 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses administered by our Specialist Electronics Training Division - explains the benefits of our free Appointments and Advisory service and shows you how to qualify for five years promotion in one year.

PRACTICAL EQUIPMENT INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with all the practical equipment you need, plus Basic Practice and Theoretical Courses for beginners in Radio, TV, Electronics, etc.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
Dept. (B10), Aldermaston Court, Reading RG7 4PF

SEND OFF THIS COUPON TO-DAY!

Tick subjects that interest you:

AMSE (Elec) City & Guilds Certificate RTEB Certificate
Radio Amateurs' Exam DMG Certificate Colour TV
Electronic Engineering Computer Electronics Radio and TV
Servicing Practical Electronics Practical TV and Radio
Please send booklets & full information without cost or obligation.

NAME..... AGE.....
(BLOCK CAPITALS PLEASE)

ADDRESS

.....

.....

OCCUPATION.....

To: BIET Dept. B10, Aldermaston Court, Reading RG7 4PF
Accredited by the Council for the Accreditation of Correspondence Colleges

(Continued on page 127)

RADIO MODELLER



ELECTRONIC BOOKS

● MODEL RADIO CONTROL

Detailing both Theory and Practice, this book, by leading authority Paul Newell, will become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system.

134 pages. Price £2.25 U.K. Postage 13p

● SINGLET SET

The Singlet Transmitter, Superhet and Super-regen receivers, are now all three available in one book. Complete construction details with full size p.c. layout, components list etc. Ideal introduction to the hobby for the home constructor. 20 pages.

Price 30p. U.K. Postage 3p

● LOW COST PROPORTIONAL

Modellers who want to save money buy this volume when converting single channel equipment to simple proportional. They find a wealth of really up to date information in the clear descriptions, full size practical and working drawings, plus over a dozen circuit modules for pulse proportional units.

118 pages.

Price £1.05 U.K. Postage 11p



ON SALE NOW at all leading shops or direct from:-

RADIO MODELLER, BOOK SALES, 64 Wellington Road, Hampton Hill, Middx.

PLAIN-BACKED NEW STYLE SELF-BINDERS

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

for your other magazines
(max. format 7½" x 9½")



PRICE **70p** P. & P. 14p

Available only from:-

Data Publications Ltd. 57 Maida Vale London W9 1SN

COLOURS: MAROON OR GREEN
(If choice not stated, colour available will be sent)

SMALL ADVERTISEMENTS

(Continued from page 125)

WANTED URGENTLY for cash by dedicated fisherman, pair portable transistorised trans/receivers, self contained. Good condition. Box No. G191.

FOR SALE: *Radio Constructor* November 1949 to June 1970 complete. *Wireless World* November 1939 to December 1964. *Practical Wireless* 1949 to 1959. *Television* 1st issue April 1950 to 1963. Plus others. Lists. Priest, 21 Levens Grove, Blackpool, Lancs.

FOR SALE: Widescreen Cine Outfit. 9.5mm Prince cine camera fitted with Zenoscope Anamorphic lens, 9.5mm Specte projector with adaptor for Zenoscopic lens, widescreen 60 in. by 30 in., six 9.5mm cassettes for camera. £50. Box No. G192.

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p, five sheets for 10p, postage 3p. Data Publications Ltd., 57 Maida Vale, London W9 1SN.

WORLD DX CLUB covers all aspects of SWLing on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.38 a year. Enquiries to Secretary, WDXC, 11 Wesley Grove, Portsmouth, Hants., PO3 5ER.

URGENTLY REQUIRED: Pre-war Lissen A.C. Skyscraper receiver and Lissen Hi-Q components. Litherland, 11 Birch Grove, Chippenham, Wiltshire. Telephone: Chippenham 50707.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:- The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

"GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK". Contains circuits, data, illustrations and valuable information for British/USA receivers, trans/receivers. Includes modifications to sets and test equipment. Price £2.85, p.p. 15p. Wanted all types of communications receivers and test equipment. Top Prices paid. What have you? Gerald Myers (RC), 18 Shaftesbury Street, Leeds LS12 3BT.

THE BRITISH AMATEUR ELECTRONICS CLUB. A club for all who are interested in electronics as a hobby. Quarterly Newsletter sent free to members. Subscription 50p per year. Details from Hon. Secretary, J. G. Margetts, 17 St. Francis Close, Abergavenny, Mon.

ESSEX GARDENERS. Buy your bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

WINGS APPEAL SEPT. 11th-16th



SEPTEMBER 1972

To All Users of Industrial Electronics

Take advantage of our very competitive prices and high quality workmanship.

DESIGN AND CONSTRUCTION OF INDUSTRIAL ELECTRONICS EQUIPMENT. INDUCTION HEATING GENERATORS. METAL DETECTORS, POWER SUPPLIES, AUTOMATION AND CONTROL EQUIPMENT. HIGH QUALITY SHORT DELIVERY TIMES, TWO YEARS GUARANTEE

DESIGNS CONSTRUCTED TO CUSTOMERS OWN SPECIFICATIONS

WRITE FOR FULL DETAILS TO:

"E.B.E.H. A. KYPRIOTIS"

LABORATORIES OF INDUSTRIAL ELECTRONICS

OFFICE
ANDROMAHIS 50, KALLITHEA
ATHENS, GREECE

FACTORY
PAPAFLESSA 3, TSAKOS
AGHIA PARSKEVI
ATHENS, GREECE

YUKAN SO PROFESSIONAL THE
SELF-SPRAY YUKAN AEROSOL WAY -

Get these air drying **GREY HAMMER**
NOW! OR **BLACK WRINKLE**
(CRACKLE) finishes

Yukan Aerosol spraykit contains 453g. fine quality, durable easy instant spray. No stove baking required. Hammers available in grey and blue, 90p car. pd. Modern Eggshell Black Wrinkle (Crackle) producing a 3D textured finish, 90p car. pd., all at 85p per push-button self-spray can at our counter. Also durable, heat and water resistant Black Matt finish (350g. self-spray cans only) 75p car. pd.

SPECIAL OFFER: One can plus optional transferable strap-on trigger handle (value 25p) for 86p car. pd. Choice of 13 self-spray plain colours and primer (motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:
DEPT:RC/YUKAN, 307a EDOWARE ROAD, LONDON W2 1BN

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too. *Now British ever better*

Other Yukan Air Drying Aerosols, 453g. or 80p car. pd. include: Fine Chromate, Clear Lacquer, Maraline Grey, Blue.



SYNTHESISER MODULES

Voltage-controlled modules for synthesiser construction and other musical MIRACLES! Catalogue 15p. D.E.W. Ltd., 254 Ringwood Road; Ferndown, Dorset.

MORSE MADE EASY!!!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.) Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed. Beginner's Section only £3.30. Complete course £4.50 (Overseas £1 extra). Details only, 4p stamp. 01-680 2896

G3HSC/Box 38, 45 GREEN LANE, PURLEY, SURREY.

127

CHASSIS and CASES by



H. L. SMITH & CO. LTD.
287/9 Edgware Road
London W2 1BE
TEL: 01-723 5891

BLANK CHASSIS

FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6x4x2"	34p	17p	10x8x2 1/2"	64p	30p
7x4x1 1/2"	33p	16p	12x7x2 1/2"	66p	33p
7x5x2"	40p	19p	12x9x2 1/2"	76p	36p
8x4x2"	38p	19p	13x8x2 1/2"	76p	36p
8x5 1/2 x2"	44p	21p	14x7x3"	80p	36p
9x7x2"	50p	26p	14x10x2 1/2"	88p	47p
10x4x2 1/2"	50p	21p	15x10x2 1/2"	92p	50p
12x4x2 1/2"	55p	22p	17x10x3"	£1.10	55p
12x5x3"	66p	26p	Plus post and packing		

TO FIT OUR CASES

7x5 1/2 x1 1/2"	38p	21p	12x6 1/2 x2"	60p	33p
7x5x2"	43p	21p	14x8 1/2 x2"	74p	44p
11x6 1/2 x1 1/2"	48p	30p	15 1/2 x9 1/2 x2 1/2"	94p	52p
11x6 1/2 x2"	55p	30p	17 1/2 x9 1/2 x2 1/2"	£1.05	59p


Plus post & packing

PANELS: Any size up to 3ft. at 36p sq. ft. 16 s.w.g. (18 s.w.g. 32p). Plus postage and packing

CASES ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
N	8x6x2"	£1.00	W	12x7x7"	£2.50
N	6x6x3"	£1.05	W	15x9x8"	£3.15
N	4x4x2"	80p	Y	8x6x6"	£2.25
U	4x4x4"	95p	Y	12x7x7"	£2.80
U	5 1/2 x4 1/2 x4 1/2"	£1.15	Y	13x7x9"	£3.15
U	8x6x6"	£1.45	Y	15x9x7"	£3.35
U	9 1/2 x7 1/2 x3 1/2"	£1.55	Z	17x10x9"	£4.15
U	15x9x9"	£3.00	Z	19x10x8 1/2"	£4.35
W	8x6x6"	£1.90			*Height

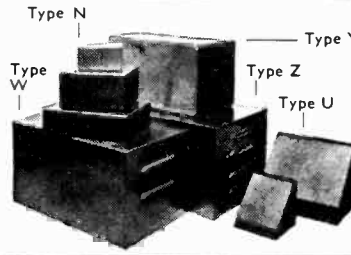Type N has removable bottom. Type U removable bottom or back, Type W removable front, Type Y all screwed construction. Type Z removable back and front. Plus p.&p.



B. H. COMPONENT FACTORS LTD. DEPT. RC P.O. BOX 18, LUTON, BEDS. LU1 1SU

BARGAIN PRICES MONEY BACK GUARANTEE

ELECTROLYTIC CAPACITOR BARGAIN PACKS		ELECTROLYTIC CAPACITORS		CERAMIC DISC.		TRANSISTORS		MULLARO POLYESTER		INTEGRATED CIRCUITS	
5 x 1mfd 25V	30p each!	0.64mfd 50V 21p	100mfd 25V 4p	1pF 500V 2p	2N705	10p	C280	250V	SN7400N	18p	
10 x 2mfd 10V	50p	1mfd 50V 21p	100mfd 50V 8p	5pF 750V 2p	2N708	13p	0.01, 0.015, 0.047, 3p.	SN7401N	18p		
5 x 2mfd 10V	50p	1mfd 25V 21p	200mfd 6V 4p	10pF 750V 2p	2N1303	17p	0.068, 0.1, 0.15, 4p.	SN7410N	18p		
4 x 8.4mfd 50V	50p	1mfd 50V 3p	250mfd 6V 4p	20pF 750V 2p	2N3866	80p	0.22, 5p, 0.68, 10p.	SN7430N	15p		
10 x 25mfd 50V	50p	2mfd 10V 21p	250mfd 10V 4p	25pF 750V 2p	2N3055	80p	1.5, 5, 20p.	SN7440N	25p		
4 x 50mfd 10V	50p	2mfd 15V 21p	250mfd 15V 8p	40pF 750V 3p	BC108	11p		SN7470N	30p		
1 x 100mfd 50V	50p	2.5mfd 50V 3p	250mfd 25V 8p	80pF 750V 2p	BC730	22p		SN7483N	£1.20		
		4mfd 10V 3p	400mfd 10V 5p	75pF 750V 2p	BFY51	20p		SN7493N	80p		
		6.4mfd 50V 3p	500mfd 10V 5p	100pF 750V 2p	BFY88	40p		UL914	30p		
		8mfd 25V 3p	500mfd 12V 8p	120pF 750V 2p	BFX87	28p					
		8mfd 40V 3p	500mfd 25V 10p	220pF 750V 2p	BSX21	18p					
		10mfd 6V 3p	640mfd 10V 8p	1000pF 50V 2 1/2p	BSX80	50p					
		10mfd 15V 3p	1000mfd 3V 8p	4700pF 30V 2p	CA07	28p					
		10mfd 25V 3p	1000mfd 6V 8p	0.01 uF 30V 2p	C426	27p					
		10mfd 50V 4p	1000mfd 12V 10p	0.022 uF 30V 2p	P346A	8p					
		18mfd 15V 3p	1000mfd 25V 18p	0.047 uF 30V 2p	VA05A	10p					
		16mfd 28V 3p	1000mfd 50V 35p	0.1 uF 25V 4p	OC38	40p					
		20mfd 25V 3p	2000mfd 12V 10p		OC38	43p					
		25mfd 25V 3p	2000mfd 25V 25p		OC71	12p					
		25mfd 40V 3p	2500mfd 12V 10p		OC75	18p					
		25mfd 50V 4p	2500mfd 25V 25p		OC83	18p					
		32mfd 50V 4p			Red Panel Neon	15p					
		40mfd 6V 3p			Int. Resistor	15p					
		50mfd 10V 3p									
		50mfd 50V 7p									
		64mfd 10V 4p									
		64mfd 15V 4p									
		64mfd 25V 4p									
		64mfd 40V 5p									
		100mfd 6V 3p									

TERMS: CASH WITH ORDER. POST AND PACKING FREE ON ORDERS ABOVE £5. FOR SMALLER ORDERS PLEASE ADD 10p. DISCOUNT: ABOVE £10-10%, £20-15%. WE HAVE MANY COMPONENTS NOT ADVERTISED. ENQUIRIES WELCOME. WITH S.A.E. PRICE LIST 5p. DATA SHEETS 5p. TRADE AND EXPORT ENQUIRIES WELCOME.

DATA BOOK SERIES

- DB5 TV FAULT FINDING**
124 pages. Price 50p, postage 6p.
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK**
80 pages. Price 45p, postage 6p.
- DB16 RADIO CONTROL FOR MODELS**
192 pages. Price 75p, postage 8p.
- DB17 UNDERSTANDING TELEVISION**
512 pages. Price £2.10, postage 25p.
- DB18 AUDIO AMPLIFIERS**
128 pages. Price 53p, postage 6p.
- DB19 SIMPLE SHORT WAVE RECEIVERS**
140 pages. Price 80p, postage 6p.

I enclose Postal Order/Cheque for in payment for
NAME
ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable from your local bookseller.

Data Publications Ltd., 57 Maidea Vale, London W9 1SN

Please mention THE RADIO CONSTRUCTOR when writing to advertisers

Meter Shunts I

The Table lists shunt values, to 3 significant figures, for meter resistances from 25Ω to 1,500Ω, with particular reference to meter resistances around 1,000Ω. Multiplying factors are in the series 3-10-30. Thus, the shunt required to cause a 1,000Ω 0-100μA meter to read 30mA f.s.d. is 3.34Ω.

Meter Resistance	X3	X10	X30	X100	X300	X1,000	X3,000
25Ω	12.5Ω	2.78Ω	0.862Ω	0.253Ω	0.0839Ω	0.0250Ω	0.00833Ω
50Ω	25Ω	5.55Ω	1.72Ω	0.505Ω	0.167Ω	0.0501Ω	0.0167Ω
75Ω	37.5Ω	8.33Ω	2.59Ω	0.758Ω	0.251Ω	0.0751Ω	0.0250Ω
100Ω	50Ω	11.1Ω	3.45Ω	1.01Ω	0.334Ω	0.100Ω	0.0333Ω
250Ω	125Ω	27.8Ω	8.62Ω	2.53Ω	0.839Ω	0.250Ω	0.0833Ω
500Ω	250Ω	55.5Ω	17.2Ω	5.05Ω	1.67Ω	0.501Ω	0.167Ω
750Ω	375Ω	83.3Ω	25.9Ω	7.58Ω	2.51Ω	0.751Ω	0.250Ω
800Ω	400Ω	88.9Ω	27.6Ω	8.08Ω	2.68Ω	0.801Ω	0.267Ω
850Ω	425Ω	94.4Ω	29.3Ω	8.59Ω	2.84Ω	0.851Ω	0.283Ω
900Ω	450Ω	100Ω	31.0Ω	9.09Ω	3.01Ω	0.901Ω	0.300Ω
950Ω	475Ω	106Ω	32.8Ω	9.60Ω	3.18Ω	0.951Ω	0.317Ω
1,000Ω	500Ω	111Ω	34.5Ω	10.1Ω	3.34Ω	1.00Ω	0.333Ω
1,100Ω	550Ω	122Ω	37.9Ω	11.1Ω	3.68Ω	1.10Ω	0.367Ω
1,200Ω	600Ω	133Ω	41.4Ω	12.1Ω	4.01Ω	1.20Ω	0.400Ω
1,250Ω	625Ω	139Ω	43.1Ω	12.6Ω	4.18Ω	1.25Ω	0.417Ω
1,300Ω	650Ω	144Ω	44.8Ω	13.1Ω	4.35Ω	1.30Ω	0.433Ω
1,400Ω	700Ω	156Ω	48.3Ω	14.1Ω	4.68Ω	1.40Ω	0.467Ω
1,500Ω	750Ω	167Ω	51.7Ω	15.2Ω	5.02Ω	1.50Ω	0.500Ω

U.K.'s LARGEST ELECTRONICS CENTRES! HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.




NOW OPEN!

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381/8382
354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736
309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963

303 BARGAIN STORE SPECIAL OFFERS 01-723 1008 All Mail to: 303, Edgware Rd., London, W.2.

ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.

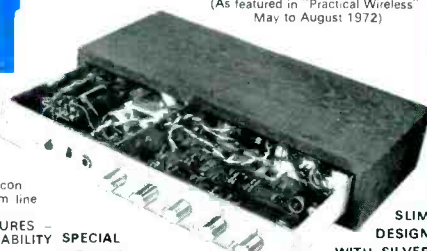BUILD THE TEXAN 20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER



(As featured in 'Practical Wireless' May to August 1972)

FREE TEAK CABINET with complete kits

FEATURES New slim design with 6 - IC's, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work
HIGH QUALITY AND STABILITY ARE PREDOMINATE FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION
FACILITIES On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Mag. P.U. Radio Tuner. Aux Can be altered for Mic. Tape. Tape head etc. (Parts list Ref. 20 on request)
(Parts list Ref. 20 on request).
Design approved kits only available from Henry's

SPECIAL KIT PRICE £28.50 P&P 45p

SLIM DESIGN WITH SILVER TRIM.
Overall chassis size 14 1/2" x 6" x 2" high

(Complete with FREE TEAK CABINET)

RECORD DECKS CHASSIS (Post 50p)

SP25/3	£10.75	HT70	£15.00
MP80	£10.40	MP610	£14.15
AP76	£18.95	GL72	£22.25
WITH PLINTH/COVER (Post 70p)			
MP60	£17.20	TD150AB	£41.45
HT70	£21.60	PL12AC	£35.25
HL(GL75)	£35.25	BD2	£32.25
MP610	£20.35		
CART PLINTH/COVER (Post 70p)			
(HL) AP76/G800/PC			£29.95
(HL) SP25-3/G800/PC			£18.95
HT70/G800/PC			£27.00
(HL) 2025TC/9TAHCD/PC			£13.50
MP60/SC5MD/PC			£17.25
(HL) GL75/G800E/PC			£44.15
(HL) GL72/G800/PC			£34.50

ULTRASONIC TRANSDUCERS

Operate at 40Kcs up to 100 Kcs. Ideal remote switching and signalling. Complete with data and circuits.
PRICE PER PAIR £5.90 Post 10p

LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet
TYPE 150 6 watt, 3, 8 or 15 ohms **£2.20**, Post 22p
TYPE 150TC Twin cone version **£2.75**, Post 22p
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. **£3.85**, Post 25p
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. **£1.70**, Post 28p



POLISHED CABINETS 150, 150TC, 450 **£4.60**, Post 30p.

TEST EQUIPMENT

SE250B	Pocket Pencil Signal Injector	£1.90
SE500	Pocket Pencil Signal Tracer	£1.50
TE15	Grid Dip Meter 440 KHz - 280 mHz	£13.45
500	30 K/Volt Multimeter	£9.25
	With leather case	£10.50
200H	20K/Volt Multimeter	£4.20
	With case	£4.85
AF105	50K/Volt Multimeter	£8.50
	With case	£9.50
U4341	AC/DC Multimeter with transistor tester	£10.50
	with steel case	£15.95
TE20D	RF Generator 120KHz - 500MHz, Carr 35p	£17.50
TE22D	Audio Generator 20Hz - 200KHz, Carr 35p	£17.50
T03	3" Scope 1 1/2Hz - 1 1/2MHz, Carr 50p	£39.00
GI-5	3" Pulse Scope 10Hz - 10MHz, Carr 50p	£39.00
TE65	Valve Voltmeter 28 ranges, Carr 40p	£17.50



TEXAS PUBLICATIONS

1-100 watt Amplifiers and Pre-Amplifier. Layouts and data **£1.25**
77 pages
700 page IC Data Book (No. 2) All T.T.L.I.C. **£6.00**
420 page Transistor Data (No. 3) **£6.00**
340 page Transistor Data (No. 4) **£6.00**
(Post etc. 20p each)

MARRIOTT TAPE HEADS 4 TRACK MONO or 2 TRACK STEREO

"17"	High Impedance	£2.00
"18"	Med Impedance	£2.00
"36"	Med-Low Imp.	£3.50
	Erase Heads for above	75p
"63"	2 track mono - Hi Imp.	£1.75
"43"	Erase Head for above	75p

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)
XN3, XN13, GN40-9 Side view with data **85p**
GNP-7, GNP-8 0-9 Side view with decimal points and data **95p**
3015F 7-segment £2 each, £7 per 4 with data.
12 and 24 hour clock circuits for above.
Ref. No. 31 15p.



NEW MW/LW TUNER TO BUILD ML-3

Uses Mullard Module. Slow motion tuning.
Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2".
TOTAL COST TO BUILD £4.85 Post 15p. All parts sold separately - Leaflet No. 6.

BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BAND-WIDTH, PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION, MONO AND STEREO.
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it - VHF FM gives the REAL sound. All parts sold separately - Free Leaflet No. 3 & 7.
TOTAL £6.97, p.p. 20p. Decoder Kit **£5.97**.
Tuning meter unit **£1.75**.
Mains unit (optional) Model PS900 **£2.47**, Post 20p.
Mains unit for Tuner and Decoder PS1200 **£2.62**, Post 20p.



"BANDSPREAD" PORTABLE TO BUILD




Printed circuit all-transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra sensitivity. Also slow-motion geared tuning. 600mW push pull output. Fibre glass-PVC covered cabinet. Car aerial socket. Attractive appearance and performance. **TOTAL COST TO BUILD £7.98** p.p. 32p (battery 22p).
All parts sold separately - Leaflet No. 2.

PA-DISCO-LIGHTING

UK's Largest Range - Write phone or call in. Details and demonstrations on request.
DJ30L 3 Channel sound to light unit 3Kw **£28.50**
DJ40L 3 Channel Mic (built in) to light 3 Kw **£37.50**
DJ70S 70 watt Disco amp/mixer **£49.75**
DISCOAMP 100 watt Disco amp/mixer **£67.50**
DJ105S 30 watt Disco amp/mixer **£31.00**
Anti-Feedback Quality Mic **£11.50**
SDL 12" 50 watt 8 ohm Full range Speaker **£12.95**
DECKS Use MP60 or SP25/3 see above. Matching cartridge SC5M **£2.62** Ref. No. 18.



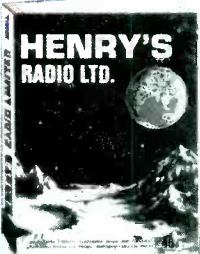FIBRE OPTICS LIGHTING EFFECTS PROJECTORS SPOTS DIMMERS MIXERS Everything for PA Disco - Lighting FREE Stock List. Ref. No. 18.



CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics - plus data, circuits and information

10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post Paid (40p FOR CALLERS)
PLUS! FIVE 10p VOUCHERS

Send to this address - Henry's Radio Ltd (Dept. RC), 3 Albemarle Way London, E.C.1. - for catalogue by post only. All other mail and callers to "303", see above.

SINCLAIR PROJECT 60 MODULES - SAVE POUNDS

Z30 **£3.57** 250 **£4.37**
STEREO **£6.97** PZ5 **£3.97**
PZ6 **£6.37** PZ8 **£4.77**
Transformer for PZ8 **£2.95**
Active Filter Unit **£4.45**
Stereo FM Tuner **£16.95**
IC12 **£1.80** Q16's **£15** pr
Post etc. 20p, per item



PACKAGE DEALS Post 25p
2 x Z30, Stereo 60, PZ5 **£15.95**
2 x Z30, Stereo 60, PZ6 **£18.00**
2 x Z50, Stereo 60, PZ8 **£20.25**
Transformer for PZ8 **£2.95**
PROJECT 605 KIT **£19.95**

MINIATURE AMPLIFIER

5 transistor, 300mW o/p. Fitted volume and sensitivity control 9 volt operated
£1.75 each P/P 15p

QUALITY SLIDER CONTROLS

60mm stroke sliders and ganged. Complete with knobs 5K, 10K, 25K, 100K, 500K, 1 meg, Log and Lin. 45p each, 10K, 25K, 50K, 100K, Log and Lin ganged, 75p each.

HI-FI & TAPE EQUIPMENT

Acknowledged as UK's largest stockists with lowest prices plus 12 months guarantee. Write or call for FREE 16 page lists (Ref 17)

TRANSISTORS - IC's - RECTIFIERS SCR's - TRIACS etc.

NEW FREE LISTS Ref. No. 36 on request

MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

All the parts you need plus Data and Circuits - Get a Catalogue - it's all in there!
Prices subject to change without notice. E.60 E.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday.

H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H