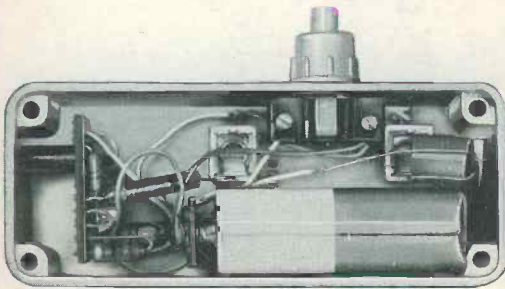


RADIO & ELECTRONICS CONSTRUCTOR

Vol. 26 No. 9


APRIL 1973

20p



CRYSTAL MICROPHONE PRE-AMPLIFIER

AUDIBLE CONTINUITY TESTER

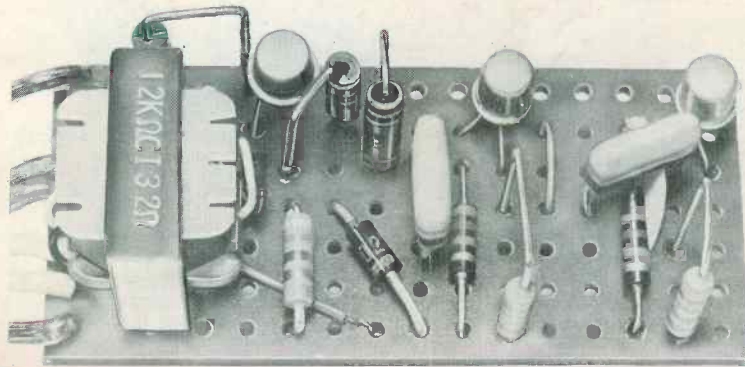

ALSO THE 'HYBRIDYNE' MEDIUM
FEATURED WAVE PORTABLE RECEIVER



Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine!
You can build up to the cover you need by additional units

(or ½ units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances And remember - as you buy more possessions just add more Home Units at any time.

THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue,
Southend-on-Sea, Essex, SS2 6BT

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

It pays to be protected by a **General Accident** company

20/9468

PRECISION

POLYCARBONATE CAPACITORS

Close tolerance professional capacitors by well-known manufacturer. Excellent stability and extremely low leakage. All 63V D.C.

0.47 μ F:	$\pm 5\%$ 30p;	$\pm 2\%$ 40p;	$\pm 1\%$ 50p
1.0 μ F:	$\pm 5\%$ 40p;	$\pm 2\%$ 50p;	$\pm 1\%$ 60p
2.2 μ F:	$\pm 5\%$ 50p;	$\pm 2\%$ 60p;	$\pm 1\%$ 75p
4.7 μ F:	$\pm 5\%$ 70p;	$\pm 2\%$ 90p;	$\pm 1\%$ 115p
6.8 μ F:	$\pm 5\%$ 95p;	$\pm 2\%$ 115p;	$\pm 1\%$ 150p
10.0 μ F:	$\pm 5\%$ 110p;	$\pm 2\%$ 140p;	$\pm 1\%$ 180p
15.0 μ F:	$\pm 5\%$ 160p;	$\pm 2\%$ 210p;	$\pm 1\%$ 270p

NEW! — TANTALUM BEAD CAPACITORS

Values available .1, .22, .47, 1.0, 2.2, 4.7, 6.8 μ F at 35V, 10 μ F 25V, 15 μ F 20V, 22 μ F 15V, 33 μ F 10V, 47 μ F 6V, 100 μ F 3V. All at 9p each; 6 for 50p; 14 for £1.00. Special pack, 6 off each value (78 capacitors) for £5.00.

TRANSISTORS: BC107; BC108; BC109 all at 9p each. 6 for 50p; 14 for £1.00; AF178 at 42p each or 3 for £1.00. All brand new and marked.

POPULAR DIODES: IN914 - 7p each; 8 for 50p; 18 for £1.00 IN916 - 9p each; 6 for 50p; 14 for £1.00. IS44 - 5p each; 11 for 50p; 24 for £1.00. All brand new and marked.

400mV ZENER DIODES: Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15 volts. All new and marked. All at 10p each; 6 for 50p; 14 for £1.00.

SILICON PLASTIC RECTIFIERS 1.5 amp wired-ended D027. 100 PIV at 8p each or 4 for 30p; 400 PIV at 9p each or 4 for 34p; 800 PIV at 14p each or 4 for 50p.

RESISTORS: Carbon film 5% $\frac{1}{2}$ w at 40°C, $\frac{1}{4}$ w at 70°C. Range 2.2 Ω -2.2M Ω . E12 series i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades. All at 1p each. 8p for 10; 70p for 100 of any one value. Special pack 10 off each value 2.2 Ω to 2.2M Ω (730 resistors) for £5.00.

440V A.C. CAPACITORS: 0.1 μ F: Size 1 $\frac{1}{8}$ " x $\frac{1}{2}$ ", 25p each
0.25 μ F: Size 1 $\frac{3}{8}$ " x $\frac{5}{8}$ ", 30p each
0.5 μ F: Size 1 $\frac{3}{8}$ " x $\frac{3}{4}$ ", 35p each
1.0 μ F: Size 2" x $\frac{3}{4}$ ", 45p each
2.0 μ F: Size 2" x 1", 75p each
Suitable for use on C.D. ignition, 250V A.C. motors, etc.

5p p. & p. on all orders below £5. Please add 10% V.A.T. after 1st April

MARCO TRADING (Formerly V. ATTWOOD)

Dept. E. 1, The Maltings, Station Road, Wem, Salop

RSGB BOOKS FOR YOU

A GUIDE TO AMATEUR RADIO by Pat Hawker, G3VA

Extensively revised, this new (15th) edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby.

96 pages

90p post paid.

AMATEUR RADIO TECHNIQUES

by Pat Hawker, G3VA Fourth edition
Aimed at extending the readers' awareness of new devices and techniques. Provides a source book for many useful circuits and aeriels. An *ideas* book rather than a constructional manual, but an *ideas* book that will prove its value time and time again.

256 pages

£1.80 post paid

RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. Complete coverage of the technical and constructional fields. A superb hard-bound volume.

£4.10 post paid.

These are three of a complete range of technical publications, log books and maps, all obtainable from:

RADIO SOCIETY OF GREAT BRITAIN
35 Doughty Street, London, WC1N 2AE

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home — the fast, modern way. Give yourself essential technical 'know-how' — like reading circuits, assembling standard components, experimenting, building — quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified study method and the remarkable **TECHNATRON Self-Build Outfit** take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors — even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, and you can use it again and again.

You **LEARN** — but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build — and it's a good one — is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course — but it teaches the real thing. The easy to understand, practical projects — from a burglar-alarm to a sophisticated Radio set — help you master basic Radio and Electronics — even if you are a 'non-technical' type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of "NEW OPPORTUNITIES". This brand new booklet — just out — tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BRE 04 ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

CL BRE 04

NAME..... AGE.....
(BLOCK CAPITALS)

ADDRESS.....

SUBJECT OF INTEREST.....

THE MODERN BOOK CO

WORLD RADIO AND TV HANDBOOK 1973

A Complete Directory of International Radio & Television £3.20

TRANSISTOR AUDIO & RADIO CIRCUITS
by Mullard £2.00

EASY WAY TO SERVICE RADIO RECEIVERS by Leo G. Sands £1.10

TRANSISTOR CIRCUIT GUIDEBOOK
by Byron Wels £1.30

110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR
by R. M. Marston £1.30

TEN-MINUTE TEST TECHNIQUES FOR ELECTRONICS SERVICING
by E. C. Carlson £1.10

COLOUR T.V. WITH PARTICULAR REFERENCE TO THE PAL SYSTEM
by G. N. Patchett £3.20

ADVANCED RADIO CONTROL
by E. L. Safford £1.10

SOLID-STATE PROJECTS FOR THE EXPERIMENTER by Wayne Green £1.30

MODEL RADIO-CONTROL
by Ed. L. Safford £1.40

MAKING AND REPAIRING TRANSISTOR RADIOS by W. Oliver £1.10

FOUNDATIONS OF WIRELESS & ELECTRONICS by M. G. Scroggie £2.00

USING ELECTRONIC TESTERS FOR CAR TUNE-UP by A. Wanninger £1.30

104 EASY TRANSISTOR PROJECTS YOU CAN BUILD by R. M. Brown £1.30

BEGINNER'S GUIDE TO TV REPAIR
by G. Zwick £1.10

HOW TO READ ELECTRONIC CIRCUIT DIAGRAMS by R. M. Brown £1.40

ELECTRONIC PUZZLES & GAMES
by M. Mandl £1.30

DIGITAL ELECTRONICS
by B. Ward £1.40

50 PHOTOELECTRIC CIRCUITS & SYSTEMS by P.S. Smith £1.40


ALL PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

NOW AVAILABLE . . .

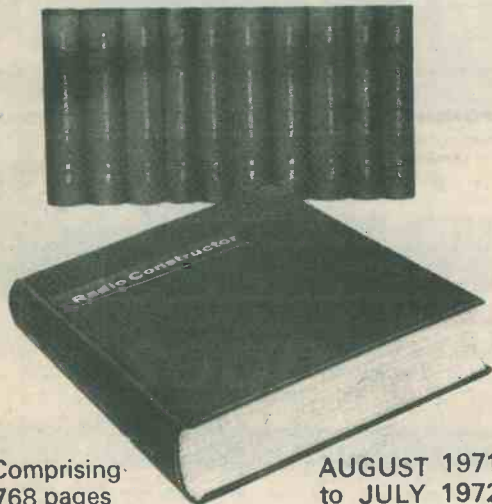

Comprising
768 pages
plus index

AUGUST 1971
to JULY 1972

LATEST

BOUND VOLUME

No. 25

of

**"The Radio Constructor"
FOR YOUR LIBRARY**

PRICE £2.00 P&P 29p

BOUND VOLUME NO. 23 (August 1969 to July 1970)
BOUND VOLUME NO. 24 (August 1970 to July 1971)

Limited number of these
volumes still available.

PRICES Volume 23 £1.88 Postage 29p Volume 24 £2.00 Postage 29p

We regret all earlier volumes are now completely sold out.
Available only from

DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON, W9 1SN

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC 107	22p	AD 149	55p	BC 143	33p	BD 131	55p	BF 179	33p	C 444	38p	2G 301	21p	2N 1611	22p	2N 2924(R)	11p	2N 3906	30p
AC 113	22p	AD 161	36p	BC 145	49p	BD 132	66p	BF 180	33p	C 450	24p	2G 302	21p	2N 1889	35p	2N 2924(B)	11p	2N 4058	13p
AC 115	25p	AD 162	36p	BC 147	11p	BD 133	71p	BF 181	33p	MAT 100	21p	2G 303	21p	2N 1890	35p	2N 3010	77p	2N 4059	11p
AC 117K	22p	AD 168	40p	BC 148	11p	BD 135	44p	BF 182	44p	MAT 101	22p	2G 304	21p	2N 1891	49p	2N 3011	15p	2N 4060	13p
AC 122	13p	AD 162(MP)	60p	BC 149	13p	BD 136	44p	BF 183	44p	MAT 120	21p	2G 306	44p	2N 1893	40p	2N 3053	50p	2N 4061	13p
AC 125	18p	ADT 140	55p	BC 150	22p	BD 137	49p	BF 184	27p	MAT 121	22p	2G 308	44p	2N 2147	77p	2N 3054	55p	2N 4062	13p
AC 126	18p	AF 114	26p	BC 151	20p	BD 138	55p	BF 185	33p	MPE 102	46p	2G 309	38p	2N 2148	64p	2N 3055	55p	2N 4284	18p
AC 127	18p	AF 115	26p	BC 152	18p	BD 139	60p	BF 188	44p	MPE 104	40p	2G 319	22p	2N 2160	66p	2N 3391	15p	2N 4285	18p
AC 128	18p	AF 117	26p	BC 154	33p	BD 140	66p	BF 194	33p	MPE 105	40p	2G 339A	22p	2N 2192	38p	2N 3391A	17p	2N 4286	18p
AC 132	18p	AF 118	26p	BC 153	31p	BD 145	88p	BF 195	13p	OC 19	40p	2G 339	22p	2N 2193	38p	2N 3392	15p	2N 4287	18p
AC 137	15p	AF 118	38p	BC 157	20p	BD 175	66p	BF 196	15p	OC 20	69p	2G 345	17p	2N 2217	24p	2N 3395	15p	2N 4288	18p
AC 137	15p	AF 124	33p	BC 158	13p	BD 176	66p	BF 197	15p	OC 22	42p	2G 371	17p	2N 2218	22p	2N 3395	18p	2N 4290	18p
AC 141	15p	AF 125	27p	BC 159	13p	BD 177	71p	BF 200	49p	OC 23	46p	2G 371B	13p	2N 2219	22p	2N 3402	23p	2N 4291	18p
AC 141K	18p	AF 126	31p	BC 160	49p	BD 178	71p	BF 202	41p	OC 24	61p	2G 373	18p	2N 2220	24p	2N 3403	23p	2N 4292	18p
AC 142	15p	AF 127	31p	BC 161	55p	BD 179	77p	BF 207	49p	OC 25	42p	2G 374	18p	2N 2221	22p	2N 3404	31p	2N 4293	18p
AC 142K	18p	AF 129	33p	BC 162	55p	BD 180	77p	BF 258	66p	OC 26	27p	2G 377	38p	2N 2222	22p	2N 3405	46p	2N 4294	18p
AC 151	16p	AF 178	55p	BC 168	13p	BD 185	71p	BF 259	93p	OC 28	55p	2G 378	17p	2N 2223	22p	2N 3406	16p	2N 4295	18p
AC 154	22p	AF 179	55p	BC 169	13p	BD 186	71p	BF 262	60p	OC 29	55p	2G 381	17p	2N 2224	24p	2N 3407	31p	2N 4296	18p
AC 155	22p	AF 180	55p	BC 170	13p	BD 187	77p	BF 263	60p	OC 35	46p	2G 382	17p	2N 2225	26p	2N 3408	26p	2N 4297	18p
AC 156	22p	AF 181	49p	BE 171	15p	BD 188	77p	BF 270	38p	OC 36	55p	2G 401	33p	2N 2226	26p	2N 3409	82p	2N 4298	18p
AC 157	26p	AF 186	49p	BE 172	15p	BD 189	82p	BF 271	33p	OC 41	22p	2G 414	27p	2N 2227	26p	2N 3410	10p	2N 4299	18p
AC 165	22p	AF 239	40p	BC 173	13p	BD 190	82p	BF 272	88p	OC 42	26p	2G 417	27p	2N 2228	26p	2N 3411	11p	2N 4300	18p
AC 166	22p	AL 102	71p	BC 174	15p	BD 195	93p	BF 273	38p	OC 44	16p	2N 388A	38p	2N 2229	23p	2N 3412	11p	2N 4301	18p
AC 167	22p	AL 103	71p	BC 175	24p	BD 196	93p	BF 274	38p	OC 45	14p	2N 388A	60p	2N 2230	23p	2N 3413	11p	2N 4302	18p
AC 168	26p	AS 2	27p	BC 177	21p	BD 197	99p	BF 275	38p	OC 46	11p	2N 404	22p	2N 2231	18p	2N 3414	11p	2N 4303	18p
AC 168	26p	AS 2	27p	BC 177	21p	BD 197	99p	BF 275	38p	OC 46	11p	2N 404	22p	2N 2232	18p	2N 3415	11p	2N 4304	18p
AC 176	22p	AS 27	33p	BC 178	21p	BD 198	99p	BF 279	30p	OC 71	11p	2N 404A	31p	2N 2233	18p	2N 3416	11p	2N 4305	18p
AC 177	26p	AS 29	27p	BC 180	21p	BD 199	99p	BF 281	24p	OC 72	15p	2N 524	46p	2N 2234	18p	2N 3417	11p	2N 4306	18p
AC 178	31p	AS 50	27p	BC 181	26p	BD 205	88p	BF 84	24p	OC 75	15p	2N 527	54p	2N 2235	18p	2N 3418	11p	2N 4307	18p
AC 179	31p	AS 51	27p	BC 182	11p	BD 206	88p	BF 87	26p	OC 76	16p	2N 599	49p	2N 2236	18p	2N 3419	11p	2N 4308	18p
AC 180	18p	AS 52	27p	BC 182L	11p	BD 207	88p	BF 88	24p	OC 77	16p	2N 696	14p	2N 2237	18p	2N 3420	11p	2N 4309	18p
AC 180K	22p	AS 54	27p	BC 183	11p	BD 208	88p	BF 89	24p	OC 78	16p	2N 697	14p	2N 2238	18p	2N 3421	11p	2N 4310	18p
AC 181	18p	AS 55	27p	BC 183L	11p	BD 209	88p	BF 91	22p	OC 81	16p	2N 698	14p	2N 2239	18p	2N 3422	11p	2N 4311	18p
AC 181K	22p	AS 56	27p	BC 184	11p	BD 210	88p	BF 92	22p	OC 82	16p	2N 699	14p	2N 2240	18p	2N 3423	11p	2N 4312	18p
AC 187	24p	AS 57	27p	BC 184L	11p	BF 117	49p	BF 53	22p	OC 83	16p	2N 706	9p	2N 2241	18p	2N 3424	11p	2N 4313	18p
AC 187K	22p	AS 58	27p	BC 186	13p	BF 118	49p	BF 53	22p	OC 83	16p	2N 706A	9p	2N 2242	18p	2N 3425	11p	2N 4314	18p
AC 188	24p	AS 21	44p	BC 187	31p	BF 119	49p	BF 54	22p	OC 84	16p	2N 708	13p	2N 2243	18p	2N 3426	11p	2N 4315	18p
AC 188K	22p	BC 167	10p	BC 207	12p	BF 121	49p	BF 55	22p	OC 85	16p	2N 711	13p	2N 2244	18p	2N 3427	11p	2N 4316	18p
AC 197	22p	BC 108	11p	BC 208	12p	BF 122	55p	BF 55	22p	OC 86	16p	2N 718	26p	2N 2245	18p	2N 3428	11p	2N 4317	18p
AC 198	22p	BC 109	11p	BC 209	12p	BF 123	55p	BF 56	22p	OC 87	16p	2N 718A	26p	2N 2246	18p	2N 3429	11p	2N 4318	18p
AC 199	22p	BC 113	11p	BC 212L	12p	BF 127	55p	BF 57	22p	OC 170	27p	2N 726	31p	2N 2247	18p	2N 3430	11p	2N 4319	18p
AC 200	22p	BC 114	16p	BC 213L	12p	BF 152	60p	BF 58	22p	OC 171	27p	2N 727	31p	2N 2248	18p	2N 3431	11p	2N 4320	18p
AC 201	22p	BC 115	16p	BC 214L	12p	BF 153	60p	BF 59	22p	OC 201	31p	2N 744	22p	2N 2249	18p	2N 3432	11p	2N 4321	18p
AC 21	17p	BC 116	16p	BC 225	27p	BF 154	49p	BF 60	22p	OC 202	31p	2N 914	15p	2N 2250	18p	2N 3433	11p	2N 4322	18p
AC 22	17p	BC 116	16p	BC 226	27p	BF 155	49p	BF 61	22p	OC 203	31p	2N 918	15p	2N 2251	18p	2N 3434	11p	2N 4323	18p
AC 27	19p	BC 117	16p	BC 226	27p	BF 156	53p	BF 62	22p	OC 204	31p	2N 918	15p	2N 2252	18p	2N 3435	11p	2N 4324	18p
AC 28	21p	BC 118	11p	BC 30	24p	BF 157	60p	BF 63	22p	OC 205	31p	2N 929	23p	2N 2253	18p	2N 3436	11p	2N 4325	18p
AC 29	38p	BC 119	33p	BC 31	28p	BF 157	60p	BF 64	22p	OC 206	31p	2N 930	23p	2N 2254	18p	2N 3437	11p	2N 4326	18p
AC 30	31p	BC 120	88p	BC 32	28p	BF 158	60p	BF 65	22p	OC 309	44p	2N 930	23p	2N 2255	18p	2N 3438	11p	2N 4327	18p
AC 31	31p	BC 122	13p	BC 33	24p	BF 159	66p	BF 66	22p	P 366A	47p	2N 1131	22p	2N 2256	18p	2N 3439	11p	2N 4328	18p
AC 34	23p	BC 126	20p	BC 34	24p	BF 160	44p	Bu 105	44p	C 11E	33p	2N 1132	24p	2N 2257	18p	2N 3440	11p	2N 4329	18p
AC 35	31p	BC 125	20p	BC 35	24p	BF 161	44p	C 400	33p	OC 71	47p	2N 1302	44p	2N 2258	18p	2N 3441	11p	2N 4330	18p
AC 36	31p	BC 134	20p	BC 71	20p	BF 163	44p	C 407	27p	ORP 12	44p	2N 1303	44p	2N 2259	18p	2N 3442	11p	2N 4331	18p
AC 40	18p	BC 135	13p	BC 72	15p	BF 164	44p	C 424	22p	ORP 61	46p	2N 1304	44p	2N 2260	18p	2N 3443	11p	2N 4332	18p
AC 41	19p	BC 136	16p	BC 73	15p	BF 165	44p	C 425	22p	ORP 61	46p	2N 1305	44p	2N 2261	18p	2N 3444	11p	2N 4333	18p
AC 44	40p	BC 137	16p	BC 74	15p	BF 167	24p	C 426	22p	ST 140	14p	2N 1306	44p	2N 2262	18p	2N 3445	11p	2N 4334	18p
AD 130	40p	BC 139	31p	BD 12	77p	BF 173	24p	C 428	22p	ST 141	14p	2N 1307	44p	2N 2263	18p	2N 3446	11p	2N 4335	18p
AD 140	53p	BC 140	31p	BD 121	71p	BF 174	24p	C 428	22p	TIS 43	33p	2N 1308	44p	2N 2264	18p	2N 3447	11p	2N 4336	18p
AD 142	53p	BC 141	33p	BD 123	71p	BF 177	38p	C 441	33p	UT 46	30p	2N 1309	44p	2N 2265	18p	2N 3448	11p	2N 4337	18p
AD 143	42p	BC 142	33p	BD 124	66p	BF 178	33p	C 442	33p	UT 46	30p	2N 1309	44p	2N 2266	18p	2N 3449	11p	2N 4338	18p

DIODES & RECTIFIERS

55p	AA 119	9p	BY 130	17p	OA 47	71p
55p	AA 120	9p	BY 131	23p	OA 70	71p
55p	AA 121	9p	BY 132	23p	OA 79	71p
55p	AA 122	10p	BY 133	46p	OA 81	71p
55p	AA 123	10p	BY 134	46p	OA 85	10p
55p	AA 124	10p	BY 135	46p	OA 90	61p
55p	AA 125	10p	BY 136	46p	OA 91	71p
55p	AA 126	10p	BY 137	46p	OA 95	61p
55p	AA 127	10p	BY 138	46p	OA 100	61p
55p	AA 128	10p	BY 139	46p</		

The largest selection

NEW LOW PRICE TESTED S.G.R.'S.

PIV	1A	3A	5A	5A	7A	10A	16A	30A
50	0.251	0.271	0.361	0.381	0.511	0.55	0.581	1.261
100	0.271	0.261	0.311	0.311	0.351	0.44	0.391	1.151
200	0.381	0.401	0.54	0.54	0.621	0.67	0.821	1.761
400	0.471	0.511	0.611	0.611	0.751	0.821	1.021	1.921
600	0.561	0.621	0.75	0.75	0.841	1.061	1.371	
800	0.651	0.77	0.88	0.88	0.99	1.12	1.53	4.10

SILICON RECTIFIERS—TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
	(D07)	(S016)	Plastic (S016)	(S016)	(S010)	(S010)	(S032A)
50	0.04	0.051	0.051	0.071	0.151	0.23	0.66
100	0.04	0.061	0.051	0.141	0.171	0.25	0.821
200	0.051	0.10	0.061	0.151	0.22	0.26	1.10
400	0.061	0.14	0.071	0.22	0.30	0.40	1.371
600	0.071	0.171	0.11	0.251	0.371	0.49	2.041
800	0.11	0.181	0.12	0.271	0.401	0.60	2.20
1000	0.12	0.271	0.151	0.33	0.501	0.69	2.75
1200	—	0.361	—	0.42	0.621	0.821	—

TRIACS

VBO	2A	6A	10A
	T05	T066	T048
	£p	£p	£p
100	0.33	0.55	0.77
200	0.55	0.66	0.821
400	0.821	0.99	1.21

DIACS
FOR USE WITH TRIACS
BR100 (D32) 40p each

FREE
One 50p Pak of your own choice free with orders valued £3 or over.

BRAND NEW TEXAS GERM. TRANSISTORS Coded and Guaranteed

Pak No.	QCT	QVT
T1	243713	0671
T2	211374	0675
T3	211216	0621D
T4	21381T	0681
T5	21392T	0682
T6	21344B	0644
T7	21345B	0646
T8	21397R	0678
T9	21399A	2N1302
T10	21417	AF117

All 50p each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. OUR price 27p each.

120VCB NIXIE DRIVER TRANSISTOR. Sim. BSX21 & C407, 2N1893 FULLY TESTED AND CODED ND 120, 1.26 18p each. TO E N.P.N. 25 up 16p each 100 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal to 18 Eqt. ZTX300 pb each. Any Qty.

POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP
Coded G100. BRAND NEW TO-3 CASE. P088. REPLACEMENTS—OC25—29—30—36—36. NKT 401—403—404—405—406—430—451—482—483. T13027—3028, 2N450A, 2N456A—457A—458A, 2N611 A & B. 2G220—222. ETC. VCB0 90V VCB0 50V IC 10A FT. 30 WATTS Hie 30-170.
PRICE: 1-24 52p each, 25-99 44p each, 100 up 41p each

SIL. G.P. DIODES £p
300mW 30 .0.55
40PTV(Min.) 100 .1.85
Sub-Min. 500 .5.50
Full Tested 1,000 .9.90
Ideal for Organ Builders.

AD161/AD162 NPN
M/P COMP GERM TRANS. OUR LOWEST PRICE OF 61p PER PAIR

AD161/AD162 NPN
M/P COMP GERM TRANS. OUR LOWEST PRICE OF 61p PER PAIR

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED In Every Pak. or money back.

Pak No.	Description	£p
U1	120 Glass Sub-Min. General Purpose Germanium Diodes	55p
U2	60 Mixed Germanium Transistors AF/RF	55p
U3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	55p
U4	40 Germanium Transistors like OC81, AC128	55p
U5	60 200mA Sub-Min. Silicon Diodes	55p
U6	30 Sil. Planar Trans. NPN like BSY95A, 2N706	55p
U7	16 Sil. Rectifiers Top-Hat 750mA Vltg. Range up to 1,000 V55p	
U8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	55p
U9	20 Mixed Voltages, 1 Watt Zener Diodes	55p
U10	20 BAY50 charge Storage Diodes DO-7 Glass	55p
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	55p
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	55p
U13	30 PNP-NPN Sil. Transistors OC200 and 2S 104	55p
U14	150 Mixed Silicon and Germanium Diodes	55p
U15	25 NPN Sil. Planar Trans. TO-5 like BFV51, 2N697	55p
U16	10 3Amp Silicon Rectifiers Stud Type up to 1,000 PIV	55p
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	55p
U18	8 6Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	55p
U19	25 Silicon NPN Transistors like BC108	55p
U20	12 1.5Amp Silicon Rectifiers Top-Hat up to 1,000 PIV	55p
U21	30 AF Germanium Alloy Transistors 2G300 Series & OC71	55p
U23	30 MADT's like MH: Series PNP Transistors	55p
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	55p
U25	25 300 MHz NPN Silicon Transistors 2N708, BSY27	55p
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	55p
U27	12 NPN Germanium AF Transistors TO-1 like AC127	55p
U29	10 1Amp SCR's TO-5 can, up to 600 PIV CRS1/25-60	£1.10
U30	15 Silicon Silicon Planar Trans. NPN 2N2926	55p
U31	20 Sil. Planar Plastic NPN Trans. Low Noise Amp 2N3707	55p
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	55p
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	55p
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	55p
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	55p
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	55p
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 2S322	55p
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	55p
U39	30 RF Germ. PNP Transistors 2N1303/5 TO-5	55p
U40	10 Dual Transistors 6lead TO-5 2N2060	55p
U41	25 RF Germanium Transistors TO-5 OC45, NKT72	55p
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	55p
U43	25 Sil. Trans. Plastic TO-18 AF RC1133/114	55p
U44	20 Sil. Trans. Plastic TO-5 BC115/116	55p
U45	7 3A SCR. T066 up to 600 PIV	£1.10

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR TO-18 Lens end NPN 8im. to BP 25 and P21. BRAND NEW, Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up 50p each 50p 44p 27p

F.E.T.'S

2N3819	31p
2N3820	55p
2N3821	38p
2N3823	35p
2N5458	49p
2N5459	69p
BW 10	69p
MPT105	401p

NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 99p each. Red cover edition.

2N3055
115 WATT SIL. POWER ECH 55p each

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK SEND FOR FREE LIST.

VCB0 100V VCB0 50V IC 10A. HFE type 100/10 3mHz. OUR PRICE PER PAIR: 1-24 25-99 100 prs. prs. prs. 60p 60p 55p

QUALITY TESTED SEMICONDUCTORS

Pack Description	Price £p
Q1 20 Red spot transistors PNP	55p
Q2 16 White spot R.F. transistors PNP	55p
Q3 4 OC 77 type transistors	55p
Q4 6 Matched transistors OC44/45/81/81D	55p
Q5 4 OC 75 transistors	55p
Q6 5 OC 72 transistors	55p
Q7 4 AC 128 transistors PNP high gain	55p
Q8 4 AC 126 transistors PNP	55p
Q9 7 OC 81 type transistors	55p
Q10 7 OC 71 type transistors	55p
Q11 2 AC 127/128 Comp. pairs PNP/NPN	55p
Q12 3 AF 116 type transistors	55p
Q13 3 AF 117 type transistors	55p
Q14 3 OC 171 H.F. type transistors	55p
Q15 7 2N2926 Sil. Epoxy trans. mid colour	55p
Q16 2 2N2980 low noise Germ. Trans.	55p
Q17 5 NPN 2 x ST.141 and 3 x ST. 140	55p
Q18 4 MADT's 2 x MAT 100 & 2 x MAT 120	55p
Q19 3 MADT's 2 x MAT 101 & 1 x MAT 121	55p
Q20 4 OC 44 Germanium transistors A.F.	55p
Q21 4 AC 127 NPN Germanium transistors	55p
Q22 20 NKT transistors A.F. R.F. coded	55p
Q23 10 OA 202 Silicon diodes sub-min	55p
Q24 8 OA 81 diodes	55p
Q25 15 IN914 Silicon diodes 75V 75mA	55p
Q26 8 OA95 Germanium diodes sub-min	55p
Q27 2 10A 600 PIV Sil. rectifiers IA245R	55p
Q28 2 Silicon power rectifiers BYZ 13	55p
Q29 4 Silicon trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	55p
Q30 7 Sil. switch transistors 2N706 NPN	55p
Q31 6 Sil. switch transistors 2N708 NPN	55p
Q32 3 PNP SIL trans. 2x2N1131, 1x2N1132	55p
Q33 3 Silicon PNP Transistors 2N1171	55p
Q34 7 NPN Sil. trans. 2N2969, 500MHz (code P97)	55p
Q35 3 Sil. PNP TO-5, 2x2N2930 & 1x2N2905	55p
Q36 7 2N3846 NPN Sil. trans. 300 MHz NPN	55p
Q37 3 2N3053 NPN Silicon transistors	55p
Q38 7 PNP trans. 4 x 2N3703, 3 x 2N3702, 55p	
Q39 7 NPN trans. 4 x 2N3707, 3 x 2N3705, 55p	
Q40 7 NPN trans. 4 x 2N3707, 3 x 2N3708, 55p	
Q41 3 Plastic NPN TO-18 2N3904	55p
Q42 6 NPN transistors 2N5172	55p
Q43 7 BC 107 NPN transistors	55p
Q44 7 NPN trans. 4 x BC 108, 3 x BC 109, 55p	
Q45 3 BC 113 NPN TO-18 transistors	55p
Q46 3 BC 116 NPN TO-5 transistors	55p
Q47 6 NPN high gain trans. 3 x BC167, 3 x BC168	55p
Q48 4 BCY 70 PNP transistors TO-18	55p
Q49 4 NPN trans. 2 x BFV51, 2 x BFV52	55p
Q50 7 BSY 28 NPN switch trans. TO-18	55p
Q51 7 BSY 36A NPN trans. 300MHz	55p
Q52 8 BY100 type silicon rectifiers	£1.10
Q53 25 Sil. & germ. trans. and all mxd new £1.65	

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Calculation of L, C and R of tuned circuits. Reactance and self inductance. Area of circles. Volume of cylinders. Resistance of conductors. Weight of conductors. Decibel calculations. Angle functions. Natural Logs. & "e" functions. Multiplication & division. Squaring, cubing and square roots. Conversion of W and H. A must for every electronic engineer and enthusiast. Size 23cm x 4 cm, complete with case and instructions. PRICE EACH: £3.68!

DTL & TTL INTEGRATED CIRCUITS INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and part Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	12 x 7400	55p	UIC46	5 x 7446	55p	UIC86	5 x 7486	55p
UIC01	12 x 7401	55p	UIC47	5 x 7447	55p	UIC87	5 x 7487	55p
UIC02	12 x 7402	55p	UIC48	5 x 7448	55p	UIC88	5 x 7488	55p
UIC03	12 x 7403	55p	UIC49	5 x 7449	55p	UIC89	5 x 7489	55p
UIC04	12 x 7404	55p	UIC50	12 x 7450	55p	UIC90	5 x 7490	55p
UIC05	12 x 7405	55p	UIC51	12 x 7451	55p	UIC91	5 x 7491	55p
UIC06	12 x 7406	55p	UIC52	12 x 7452	55p	UIC92	5 x 7492	55p
UIC07	8 x 7407	55p	UIC53	12 x 7453	55p	UIC93	5 x 7493	55p
UIC08	8 x 7408	55p	UIC54	12 x 7454	55p	UIC94	5 x 7494	55p
UIC09	12 x 7410	55p	UIC55	12 x 7455	55p	UIC95	5 x 7495	55p
UIC10	12 x 7410	55p	UIC56	12 x 7456	55p	UIC96	5 x 7496	55p
UIC11	8 x 7411	55p	UIC57	8 x 7470	55p	UIC100	5 x 74100	55p
UIC12	12 x 7420	55p	UIC72	8 x 7472	55p	UIC121	5 x 74121	55p
UIC13	8 x 7413	55p	UIC73	8 x 7473	55p	UIC141	5 x 74141	55p
UIC14	8 x 7414	55p	UIC74	8 x 7474	55p	UIC181	5 x 74181	55p
UIC15	12 x 7430	55p	UIC75	8 x 7475	55p	UIC184	5 x 74184	55p
UIC16	12 x 7440	55p	UIC76	8 x 7476	55p	UIC193	5 x 74193	55p
UIC17	5 x 7441	55p	UIC77	5 x 7477	55p	UIC199	5 x 74199	55p
UIC18	5 x 7442	55p	UIC78	5 x 7478	55p	UIC199	5 x 74199	55p
UIC19	5 x 7443	55p	UIC79	5 x 7479	55p	UIC 11	25 Asat.	£1.65
UIC20	5 x 7444	55p	UIC80	5 x 7480	55p			
UIC21	5 x 7445	55p	UIC81	5 x 7481	55p			
UIC22	5 x 7446	55p	UIC82	5 x 7482	55p			
UIC23	5 x 7447	55p	UIC83	5 x 7483	55p			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES 18, BALDOCK STREET (A10), WARE, HERTS. TEL: 61593. OPEN MON. - SAT. 9.15 a.m. to 6 p.m. FRIDAY UNTIL 8 p.m.

All Mail Orders please add 10p post and packing. Send all Orders to Bi-Pak P.O. Box 6, Ware, Herts.

-the lowest prices!

74 Series T.T.L. I.C.'s

Bi-Pak Still Lowest in Price.
Full Specification Guaranteed.
All Famous Manufacturers.



	1	25	100+		1	25	100+
SN7400	0.161	0.151	0.13	SN7490	0.731	0.701	0.64
SN7401	0.161	0.151	0.13	SN7491	£1.10	£1.04	0.99
SN7402	0.161	0.151	0.13	SN7492	0.731	0.701	0.64
SN7403	0.161	0.151	0.13	SN7493	0.731	0.701	0.64
SN7404	0.161	0.151	0.13	SN7494	0.84	0.81	0.75
SN7405	0.161	0.151	0.13	SN7495	0.94	0.91	0.85
SN7406	0.38	0.34	0.31	SN7496	0.94	0.91	0.85
SN7407	0.38	0.34	0.31	SN74100	£1.81	£1.78	£1.70
SN7408	0.30	0.28	0.26	SN74101	£1.061	£1.06	1.02
SN7409	0.30	0.28	0.26	SN74102	£1.061	£1.06	1.02
SN7410	0.161	0.151	0.13	SN74103	£1.061	£1.06	1.02
SN7411	0.271	0.261	0.251	SN74104	£1.061	£1.06	1.02
SN7412	0.28	0.24	0.21	SN74105	£1.061	£1.06	1.02
SN7413	0.32	0.291	0.261	SN74106	£1.061	£1.06	1.02
SN7414	0.471	0.44	0.42	SN74107	£1.061	£1.06	1.02
SN7415	0.471	0.44	0.42	SN74108	£1.061	£1.06	1.02
SN7416	0.161	0.151	0.13	SN74109	£1.061	£1.06	1.02
SN7417	0.55	0.53	0.491	SN74110	£1.061	£1.06	1.02
SN7418	0.55	0.53	0.491	SN74111	£1.371	£1.261	£1.21
SN7419	0.491	0.46	0.44	SN74112	£1.10	£1.091	0.99
SN7420	0.491	0.46	0.44	SN74113	£1.481	£1.37	£1.21
SN7421	0.491	0.46	0.44	SN74114	0.44	0.401	0.371
SN7422	0.55	0.53	0.491	SN74122	£1.54	£1.43	£1.21
SN7423	0.55	0.53	0.491	SN74123	£3.08	£2.97	£2.86
SN7424	0.55	0.53	0.491	SN74141	0.731	0.701	0.64
SN7425	0.491	0.46	0.44	SN74145	£1.86	£1.84	1.83
SN7426	0.491	0.46	0.44	SN74146	£1.86	£1.84	1.83
SN7427	0.491	0.46	0.44	SN74147	£1.86	£1.84	1.83
SN7428	0.77	0.71	0.66	SN74151	£1.10	£1.04	0.99
SN7429	0.151	0.151	0.13	SN74152	£1.98	£1.87	£1.76
SN7430	0.481	0.46	0.44	SN74153	£1.98	£1.87	£1.76
SN7431	0.88	0.82	0.77	SN74154	£1.54	£1.43	£1.32
SN7432	0.70	0.68	0.66	SN74155	£1.54	£1.43	£1.32
SN7433	0.70	0.68	0.66	SN74157	£2.09	£1.98	£1.87
SN7434	0.161	0.151	0.13	SN74160	£1.98	£1.87	£1.76
SN7435	0.161	0.151	0.13	SN74161	£1.98	£1.87	£1.76
SN7436	0.731	0.701	0.64	SN74162	£4.40	£4.12	£3.85
SN7437	£1.43	£1.27	£1.32	SN74163	£4.40	£4.12	£3.85
SN7438	£1.98	£1.94	£1.921	SN74164	£2.42	£2.36	£2.31
SN7439	£1.081	£1.03	0.97	SN74165	£2.471	£2.42	£2.361
SN7440	£1.10	£1.06	£1.041	SN74166	£3.85	£3.81	£3.70
SN7441	£1.10	£1.06	£1.041	SN74174	£2.53	£2.42	£2.31
SN7442	0.181	0.151	0.13	SN74175	£1.78	£1.68	£1.64
SN7443	0.161	0.151	0.13	SN74176	£2.75	£2.64	£2.53
SN7444	0.161	0.151	0.13	SN74177	£2.75	£2.64	£2.53
SN7445	0.161	0.151	0.13	SN74178	£2.75	£2.64	£2.53
SN7446	0.161	0.151	0.13	SN74179	£2.75	£2.64	£2.53
SN7447	0.161	0.151	0.13	SN74180	£2.20	£1.98	£1.921
SN7448	0.32	0.28	0.261	SN74181	£6.05	£5.60	£5.221
SN7449	0.32	0.28	0.261	SN74182	£2.20	£1.98	£1.921
SN7450	0.401	0.38	0.35	SN74184	£3.85	£3.81	£3.70
SN7451	0.401	0.38	0.35	SN74185	£2.11	£2.06	£2.031
SN7452	0.491	0.47	0.46	SN74189	£2.09	£2.03	£1.98
SN7453	0.44	0.43	0.42	SN74192	£2.14	£2.09	£2.031
SN7454	0.731	0.701	0.64	SN74193	£2.20	£1.98	£1.921
SN7455	£1.32	£1.261	£1.21	SN74194	£2.97	£2.86	£2.75
SN7456	0.94	0.91	0.851	SN74195	£2.20	£1.98	£1.921
SN7457	£1.21	£1.151	£1.091	SN74196	£1.98	£1.87	£1.76
SN7458	£1.10	£1.04	0.99	SN74197	£1.98	£1.87	£1.76
SN7459	£3.85	£3.85	£3.74	SN74198	£1.98	£1.87	£1.76
SN7460	0.35	0.34	0.31	SN74199	£3.05	£2.90	£2.85
SN7461	£6.05	£5.771	£5.50				

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0.1% DISTORTION
HI-FI AUDIO AMPLIFIER
THE AL50



- ★ Frequency response 15Hz to 100,000 - 1dB. **ONLY**
- ★ Load - 3, 4, 8 or 16 ohms. **£3.58 each**
- ★ Distortion - better than 0.1% at 1KHz. ★ Supply voltage 10 - 35 Volts.
- ★ Signal to noise ratio ★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and ALSO was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT - TESTED - GUARANTEED.

STABILISED POWER MODULE SPM80



AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (rms) per channel, simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer M780, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 62mm x 106mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disco Systems, Public Address, Intercom Units etc. Handbook available 10p. PRICE £2.95

TRANSFORMER BMT80 £2.15 p. & p. 25p. STEREO PRE-AMPLIFIER, TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this module made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATION
Frequency Response 20Hz - 20KHz ± 1dB
Harmonic Distortion better than 0.1%
Inputs: 1. Tape Head 1.25 mV into 50KΩ
2. Radio, Tuner 35 mV into 50KΩ
3. Magnetic P.U. 1.5 mV into 50KΩ
All input voltages are for an output of 260mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB, from 20Hz to 20KHz. 10p.
Base Control ± 15dB @ 20Hz Treble Control ± 15dB @ 20KHz
Filters: Rumble (High Pass) 100Hz
Scratch (Low Pass) 8KHz
Signal/Noise Ratio better than -66dB
Supply Input overload + 26dB + 35 volts @ 20mA
Dimensions 292mm x 82mm x 35mm Price £13.75

SPECIAL COMPLETE KIT COMPRISING
2 AL50's, 1 SPM80, 1 BMT80 and 1 PA100 **ONLY £23.23 FREE p & p.**

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS
Postage and packing: add 10p. Overseas add extra for airmail
Minimum order 50p. Cash with order please.
Guaranteed Satisfaction or Money Back

LINEAR I.C.'s— FULL SPEC.

LOGIC DTL 930 SERIES I.C.'s ROCK BOTTOM PRICES

Type No.	1-24	25-99	100 up
BP 201C - SL201C	69p	58p	49p
BP 701C - SL701C	69p	55p	49p
BP 702C - SL702C	58p	49p	44p
BP 700 - 72700	39p	37p	33p
BP 709P - 7A709C	39p	37p	33p
BP 710 - 72710	48p	46p	44p
BP 711 - 7A711	49p	47p	44p
BP 741 - 72741	35p	50p	46p
7A 703C - 7A703C	31p	28p	26p
TA A263	77p	66p	60p
TA A263	99p	82p	77p
TA A360	187p	174p	165p
EA1000	£2.89		

Type No.	1-24	25-99	100 up
BP930	13p	12p	11p
BP932	14p	13p	12p
BP933	14p	13p	12p
BP934	14p	13p	12p
BP936	14p	13p	12p
BP944	14p	13p	12p
BP945	27p	26p	24p
BP946	13p	12p	11p
BP948	27p	26p	24p
BP951	71p	66p	60p
BP952	13p	12p	11p
BP953	44p	42p	38p
BP954	44p	42p	38p
BP957	44p	42p	38p
BP959	44p	42p	38p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

NUMERICAL INDICATOR TUBES

MODEL	CD66	GR 116	3015F
Anode voltage (Vdc)	170	175	5
Cathode cur't (mA)	2.3	14	
Numeral h'ght (mm)	16	13	9
Tube height (mm)	47	32	22
Tube diameter (mm)	19	13	12
I.C. driver rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.87	£1.71	£2.09

All indicators 0.9 + Decimal point: All side viewing: Full data for all types available on request.

BTL MICROLOGIC CIRCUITS

	1-24	25-99	100 up
Epoxy TO-5 case	39p	36p	30p
uL900 Buffer			
uL914 Dual 2/p gate	39p	36p	30p
uL923 J-K flip-flop			
Date and Circ. Booklet for IC's			
Price 7p.			

DUAL IN LINE SOCKETS 14 & 16 Lead Sockets for use with DUAL IN-LINE I.C.'s. TWO RANGES PROFESSIONAL AND NEW LOW COST.

Prof. Type No.	1-24	25-99	100 up
TS014 pin type	33p	30p	27p
TS016 pin type	38p	35p	31p
Low Cost No.			
BPS 14	16p	14p	12p
BPS 16	17p	15p	13p

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AC127 .. 10p	AF239 .. 35p	BFX88 .. 20p
AC187/8 .. 14p	BC107/8/9 .. 7p	BSV64 .. 40p
AD149 .. 35p	BCY40 .. 25p	OC35 .. 28p
AD161 .. 27p	BCY70 .. 14p	2N706 .. 8p
AD162 .. 27p	BCY71 .. 18p	2N2219 .. 19p
Matched pair .. 50p	BD131 .. 40p	2N2401 .. 15p
AF116 .. 12p	BD132 .. 50p	2N2904 .. 17p
AF117 .. 12p	BD135 .. 35p	2N2905 .. 21p
AF139 .. 30p	BFY51 .. 10p	2N2907 .. 18p
AF178 .. 40p	BFY52 .. 12p	2N3055 .. 35p
AF180 .. 45p	BFX29 .. 25p	2N3053 .. 15p

BRIDGE RECTIFIERS

Amp	Volt		
1/2	1,600	BYX10	30p
1	140	OSH01-200	30p
1.4	42	BY164	35p

Plastic types

BRIDGE RECTIFIERS

Amp	Volt		
2	30	LT120	30p
0.6	6-110	EC433	

Encapsulated with built-in heat sink .. 15p

THYRISTORS

Amp	Volt		
1	400	CRS1/40	30p
1	240	BTX18-200	30p
1	240	BTX30-200	30p
5.6	700	BT106	85p
6.5	300	BT102-300R	42p
6.5	500	BT102-500R	60p
6.5	500	BT107	90p
6.5	500	BT108	90p
6.5	500	BT101-500R	68p
6.5	500	BT109-500R	90p
20	600	BTW92-600RM	£3.00
15	800	BTX95-800R Pulse Modulated	£12

1 AMP RECTIFIERS

IN4002	100 volt	4p
IN4003	200 volt	5p
IN4004	400 volt	7p
IN4005	600 volt	9p
IN4006	800 volt	10p
IN4007	1,000 volt	15p

HIGH POWER RECTIFIERS

	Amp	Volt	
BYX38-600	2.5	600	25p
BYX38-300	2.5	300	20p
BYX38-900	2.5	900	28p
BYX38-1200	2.5	1,200	30p
BYX49-600	2.5	600	25p
BYX48-300	6	300	27p
BYX48-900	6	900	40p
BYX48-1200	6	1,200	60p
BYX72-300R	10	300	35p
BYX72-500R	10	500	43p
BYX42-300	10	300	40p
BYX42-600	10	600	45p
BYX42-900	10	900	55p
BYX42-1200	10	1,200	75p
BYX46-300*	15	300	2.50
BYX46-400*	15	400	£2.90
BYX46-500*	15	500	£3.20
BYX20-200	25	200	35p
BYX52-300	40	300	£1.75
BYX52-1200	40	1,200	£2.25

*Avalanche type

N50 ohm free plug (UG21D/U)	50p
N50 ohm square socket (UG58A/U)	50p
1" Terryclips, black plastic coated, or chrome finish	4p
Cinch 10-way terminal block	15p
Pair of LA2407 Ferrox cores with adjuster	25p
Chrome Car Radio facia	15p
Rubber Car Radio gasket	10p
DLI Pal Delayline	£2.00
Relay socket	12p
Take miniature 2PCO relay	
B9A valve can	2p
0-30 in-5 segments, black pvc, 360° dial, silver digits, self adhesive, 4 1/4" dia.	15p

OPTO ELECTRONICS

ORP12	43p	BPX29 Photo transistor	80p
BPX40	25p		
BPX42	£1		
BPY10	75p		
BPY68	75p		
BPY69	£1		
BPY77	75p		

Diodes

BPX29 Photo transistor 80p

CQ11B Infra red transmitter £4

TRIACS

Amp	Volt		
6	400	BT110-400 Plastic	75p
25	900	BTX94-900	£6.50
25	1200	BTX94-1200	£9

DIAC BRI00 .. 30p

PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp .. £1

F.E.T.'s

BFW10	40p
BSV79	90p
BSV80	80p
N. Channel	
BSV81 M.O.S.T.	£1

PAPER BLOCK CONDENSER

0.25MFD	800 volt	30p
1MFD	400 volt	15p
2MFD	250 volt	20p
2MFD	1.5 kv	50p
15MFD	150 volt	25p

WIREWOUND SLIDER

150 Ohm, 250 Ohm 5K 4p each

INDICATORS

12 volt red or mains neon amber, push fit round, chrome bezel 15p each

Rotor with neon indicator, as used in Seafarer, Pacific, Fairway depth finders 20p each

100MFD 250/275V electrolytic can 20p

DEE PLUG

McMurdo DA15P 15 way chassis plug 20p

Fairway 18009 Coax. socket 5p

TIE CLIPS

Nylon self locking 3 1/2" 1p; 7" 2p

CINCH 150

12 way edge socket 10p

Phillips Iron Thermostat 15p
 Bulgin 2-pin flat plug and socket 10p
 McMurdo PP108 8 way edge plug 15p
 300 ohm moving coil insert 4103D 1 3/4" diameter. Make ideal mike or speaker for communication work 25p

TESTED UNMARKED OR MARKED AMPLE LEAD EX NEW EQUIPMENT

AC128	6p	OC44	6p
ACY17-20	8p	OC71	6p
BC179	10p	OC72	6p
BCY30-34	10p	OC200-5	6p
BY127	8p	2N2926	5p
BZY88 series	6p	Germanium diode	3p
OA5/7/10	10p	GET111	20p
OA47/81	4p	GET120	
OA200-5	6p	(AC128 In 1"sq. heat sink)	20p
OC23	20p		
OC29	25p		

8 way Cinch standard 0.15 pitch edge socket 20p

U.E.C.L. 10 way pin connector 2B6000 OA1P10 20p

U.E.C.L. 20 way pin connector 2A60000A1P20 30p

U.E.C.L. 10 way pin socket 2B606001R10 20p

U.E.C.L. 20 way pin socket 2B60800A1R20 30p

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE

LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11


Open 10 a.m. till 8 p.m. Monday to Saturday

Phone 01-223 5016

EXTRA! in **PRACTICAL WIRELESS**


**8-PAGE
SUPPLEMENT**
with 8 step-by-step
constructional
articles on these
simple projects!

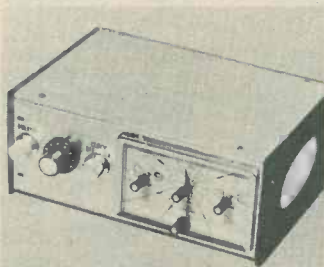Easy to follow instructions from the top designer of these items for the modern home makes each project simple and satisfying to construct. Take your pick. This fully illustrated supplement is printed on eye-catching green paper for easy identification.




RADIO ALARM CLOCK
Uses tape tuner with an amplifier.

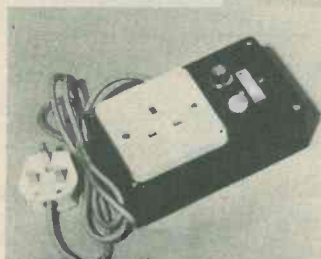And another reason for getting this rewarding and extra large issue is to find out about next month's competition with 4 special prizes of **digital multi-meters** each worth almost £50. **Show your metal and make some of these!**



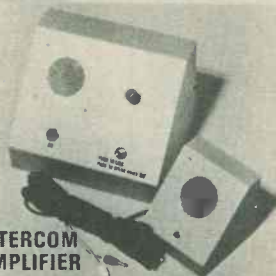LAMP DIMMER
Reduces the lighting level at the turn of a knob.




INTERCOM AMPLIFIER
2-way communication for kitchen, garage, workshop or sickroom.




LIGHT POWERED RADIO
Operated by daylight, or strong artificial light.



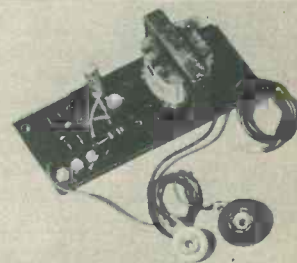
BABY ALARM
Transmits sound of baby crying or door or telephone bells.



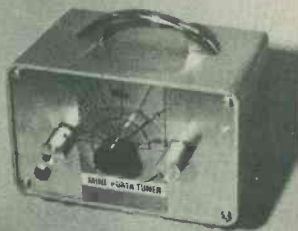TWO-TONE DOORBELL
Has pleasant-toned peal effect.



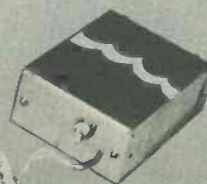TAPE TUNER
Portable medium wave tuner to feed a tape recorder or amplifier.



WATER LEVEL DETECTOR
Warns when water in bath or tank reaches a predetermined level.

Many more constructional articles plus our regular features all in the **May** issue on sale April 6.

price **20p**

BI-PRE-PAK



COMPLETE TELEPHONES

Normal household type as supplied to the Post Office, ex. G.P.O. Only **95p** each. p. & p. 35p each.



TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

ONLY 25p

p. & p. 15p.

TESTED AND GUARANTEED PAKS

M2	4	Photo Cells, Sun Batteries, 0.3 to 0.5V, 0.5 to 2mA.	50p
M79	4	1N4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
M81	10	Keed Switches, mixed types large and small	50p
M99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
M4	250	Mixed Resistors. Approx. quantity counted by weight	50p
M7	40	Wirewound Resistors. Mixed types and values.	50p
M9	2	OCF71 Light Sensitive Photo Transistor	50p
M20	20	OC2001/213 PNP Silicon uncodded TO-8 can	50p
M30	20	1 Watt Zener Diodes, Mixed Voltages 6.0 - 43V	50p
M35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
M30	30	Short lead Transistors, NPN Silicon Planar types.	50p
M39	10	Integrated Circuits: 6 Gates, 8MC 9624 Flip Flops, 8MC 945.	50p
M40	20	BFY502, 2N696, 2N1613, NPN Silicon uncodded TO-5	50p

UNMARKED UNTESTED PAKS

M66	150	Germanium Diodes Min. glass type	50p
M83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
M84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
M86	100	Sil. Diodes sub. min. 1N914 and 1N916 types	50p
M88	50	Sil. Trans. NPN, PNP equiv. to OC2001/2N706A, 85Y95A, etc.	50p
B1	50	Germanium Transistors PNP, A.F. & R.F.	50p
M6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
M24	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p
M17	20	1/2 amp. Silicon Stud rectifiers, mixed volts	50p
M15	30	Top Hat Silicon Rectifiers, 750mA, Mixed volts	50p
M16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
M20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OVER TRANSISTORS IN STOCK 1,000,000

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors.

Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality. Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc. Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9, etc. R.F. NPN and switching NPN Types also. Please state type of transistor required when ordering. ALL AT 500 for £3, 1,000 for £5, 10,000 for £40

OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR VARIOUS TYPES P & P 25p £1

VALUE ADDED TAX

On orders of £4 or over. See below:
We will give a discount to customers who send in an order for £4 or over. This discount will be equal to the V.A.T. rate current at this time. If your order does amount to £4 or over, all you need to send is the total cost of goods and postage as stated in this advertisement. No addition for V.A.T. is needed. V.A.T. for orders under £4.
If the total cost of goods plus postage and packing is less than £4, kindly add 10% (10p in the £) to your remittance. Incorrect amounts will delay your order.

Please read very carefully:



A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs £3.50, post paid.

A MUST for Colour T.V. Alignment.

Our famous P1 Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P1, only 50p 10p P & P on this Pak.

FREE CATALOGUE

FOR TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS.



100,000 Plastic Power Transistors

in stock, more on way

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min.	HFE Min.
40 watt	15	15
	1-12	13-25
40 watt	20p	18p
90 watt	24p	22p
Range 2	VCE Min.	HFE Min.
	1-12	13-25
40 watt	30p	28p
90 watt	35p	33p

Complementary pairs matched for gain at 3 amps. 10p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each
Now new low profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

- B.P. Transistor Equivalents and Substitutes. 40p
 - This includes many thousands of British U.S.A. European and C.V. equivalents. The Iliffe Radio Valve & Transistor Data Book 9th Edition P & P 21p
 - Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. 75p
- Send for lists of publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

MINIMUM ORDER 30p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX, SSO 9DF
TELEPHONE: SOUTHEND (0702) 46344

Ever had Component Problems?



1. Problems of choosing your components?
2. Problems of getting them quickly?
3. Problems of locating a supplier?

CHEER UP!



HOME RADIO (COMPONENTS) LTD have created a catalogue and an organisation that between them solve your problems simply & economically

PUT US TO THE TEST

FIRST YOU'LL NEED THE CATALOGUE. SEND COUPON with 75p CHEQUE or P.O. YOU'LL NEVER SPEND 15 BOB BETTER!



The Catalogue is crammed full with details of 6,785 items, of which about 1,750 are illustrated. It costs only 75 pence, including post and packing, and each copy contains 10 vouchers worth 5p each.

Of course, you can call at our shop (we're open 9 to 5.30 Monday to Saturday, except Wednesday 9 to 1) and get just what you want straight off the shelf. Incidentally, a catalogue bought this way will cost you only 55 pence. Whether you order by post or buy over the counter you should join our Credit Account Service. It's the simple and convenient way of buying all your radio and electronic components. We supply pre-paid envelopes and order forms, and no matter how many orders you send us you make only one payment per month. Full details and entry forms are in the catalogue.

Only 55p. plus 20p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 75p.

The price of 75p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

Name _____

Address _____

HOME RADIO (Components) LTD.
Dept. RC, 234-240 London Road, Mitcham CR4 3HD

RADIO & ELECTRONICS CONSTRUCTOR

RADIO & ELECTRONICS CONSTRUCTOR

APRIL 1973

CONTENTS

Vol. 26 No. 9

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 Telegrams
Databux, London

© Data Publications Ltd., 1972. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £2.70 (U.S.A. and Canada \$7.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

The Radio & Electronics Constructor is printed by Carlisle Web Offset.

MAY ISSUE WILL BE
PUBLISHED ON MAY 1st

AUDIBLE CONTINUITY TESTER by P. T. Jenkins	548
TWO COLOUR CATHODE RAY TUBES by J. B. Dance, M.Sc.	551
HIGH INPUT IMPEDANCE AMPLIFIER (Suggested Circuit 269) by G. A. French	552
NEWS AND COMMENT	554
POWER SUPPLY DESIGN by A. Foord	556
NEW PRODUCTS	563
HIGH RESISTANCE VOLTMETER by P. James	564
TIN IN THE ELECTRONICS INDUSTRY	566
CRYSTAL MICROPHONE PRE-AMPLIFIER by R. A. Penfold	568
RECENT PUBLICATIONS	571
THE 'HYBRIDYNE' MEDIUM WAVE PORTABLE RECEIVER by Sir Douglas Hall, K.C.M.G., M.A. (Oxon)	572
MODIFICATIONS TO CYCLOPS – Part 1 by L. C. Galitz	579
SHORT WAVE NEWS by Frank A. Baldwin	584
IN YOUR WORKSHOP – Tape Recording	586
CONSTRUCTOR'S DATA SHEET No. 73 (Resonant Frequencies – 1)	iii

AUDIBLE CONTINUITY

A simple item of test equipment which enables continuity checks to be carried out without the necessity of watching a meter.

THE CONTINUITY CHECKER DESCRIBED IN THIS ARTICLE was built up on a piece of Veroboard having a hole spacing of 0.15 in. The piece employed has 7 strips, each with 16 holes, and was, actually, the sample Veroboard which was given away free with the October 1972 issue of *Radio and Electronics Constructor*. A suitable piece can, of course, be cut from a standard Veroboard if the reader does not have the free sample on hand.

An audible continuity tester is an extremely helpful device for such requirements as the identification of tags in a complicated wavechange switch or the tracing out of wiring, since it enables the user to know when electrical continuity between two points is established without having to take his eyes from the connections.

CIRCUIT

The circuit of the continuity tester is given in Fig. 1, and it will be seen that this incorporates a multivibrator. The multivibrator is given in the circuitry immediately around TR1 and TR2 which are both transistors type BC107. The multivibrator runs at around 500Hz, with the collector of TR2 coupling to a 3Ω speaker via C3, R6 and transformer T1. It is necessary to include R6 as, otherwise, the inductance of the transformer primary adversely affects multivibrator operation. The audible level from the speaker is more than adequate for normal workshop use.

No supply is applied to the multivibrator when the two 'Test' terminals are open-circuit. Under these

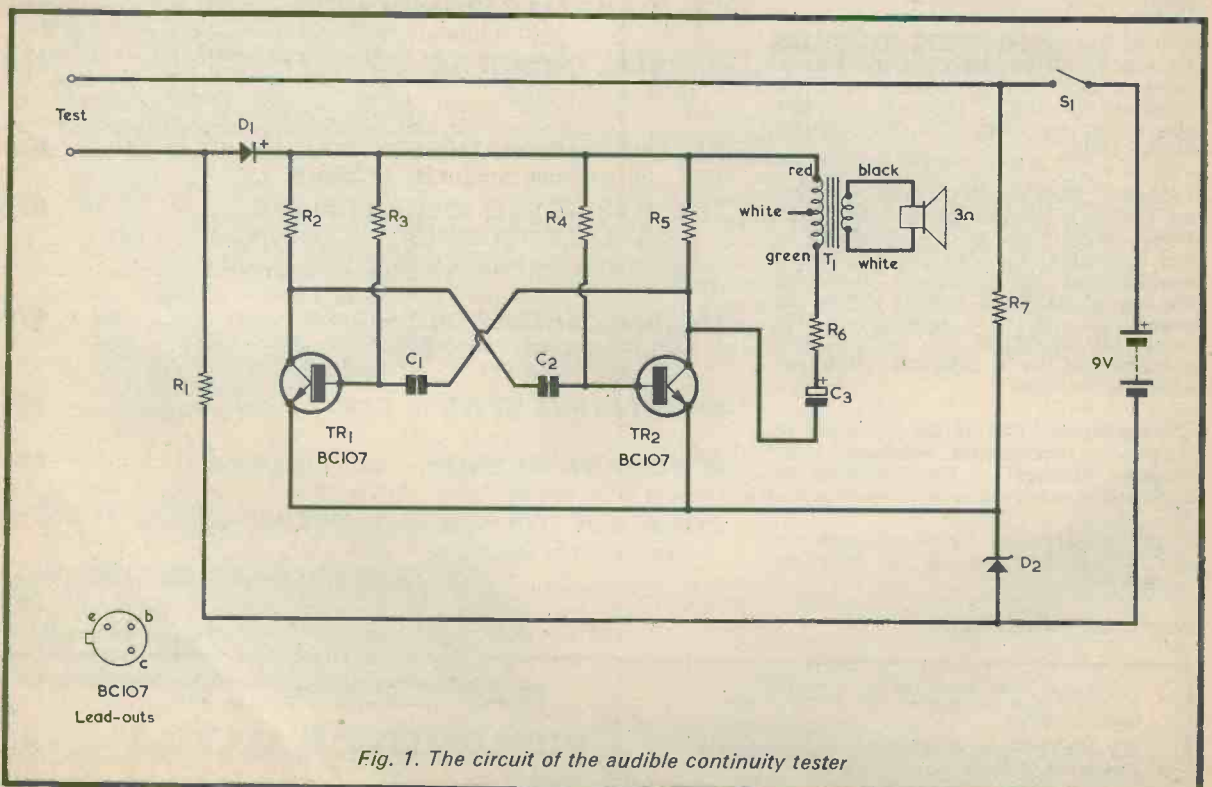



Fig. 1. The circuit of the audible continuity tester

TESTER



Cover Feature

- 1

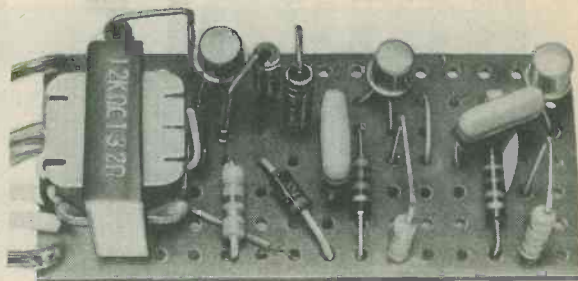

By P. T. Jenkins

conditions, the upper end of R1 is at the same potential as the negative line from the 9 volt battery and diode D1 is reverse-biased. At the same time, approximately the nominal zener voltage of 3.9 volts is caused to appear across D2 due to the presence of R7.

When the 'Test' terminals are short-circuited, the positive supply line is applied to the multivibrator via the diode D1 which is now conducting. Also, the voltage across the zener diode remains fixed at approximately 3.9 volts. Since approximately 0.6 volt is dropped across D1, a voltage of 4.5 volts becomes available to operate the multivibrator, which runs and causes the speaker to reproduce the 500Hz tone. Thus, the continuity tester produces an audible tone when the two 'Test' terminals are connected together.

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt miniature 10%)

R1	470 Ω
R2	2.7k Ω
R3	22k Ω
R4	22k Ω
R5	2.7k Ω
R6	470 Ω
R7	10k Ω

Capacitors

C1	0.047 μ F, Mullard Miniature Foil type C280
C2	0.047 μ F, Mullard Miniature Foil type C280
C3	4 μ F, 10V Wkg., Mullard miniature electrolytic

Transformer

T1	Output transformer type LT700 (Eagle)
----	---------------------------------------

Semiconductors

TR1	BC107
TR2	BC107
D1	1N4001
D2	3.9 volt zener diode, 200-250mW

Switch

S1	S.P.S.T. toggle
----	-----------------

Miscellaneous

Veroboard, 0.15in. matrix, 7 strips by 16 holes
3 Ω speaker
9 volt battery
2 test sockets and plugs
2 test leads with prods or clips

The reason for including D2 and R1 is to restrict the sensitivity of the continuity tester when the test leads are connected to a circuit possessing resistance. An operating voltage is only applied to the multivibrator when the resistance across the 'Test' terminals is low enough to produce, at the upper end of R1, a sufficiently high voltage for D1 to conduct. In practice, the multivibrator commences to run, producing a very weak tone, when the resistance between the 'Test' terminals is about 350 Ω . Lower values of test resistance produce increased volume of the reproduced tone, the latter being at its loudest when the 'Test' terminals are short-circuited.

The current drawn from the 9-volt battery is 0.5mA when the 'Test' terminals are open-circuit, and it rises to 22mA when they are short-circuited.

All the resistors used for making up the tester are $\frac{1}{4}$ watt miniature types. C1 and C2 are Mullard Miniature Foil type C280 (Home Radio Cat. No. 2EH47) and C3 is a Mullard Miniature electrolytic capacitor (Home Radio Cat. No. 2CH12). Diode D1 can be any silicon diode, and the 1N4001 specified fits comfortably onto the board. Diode D2 can be any 3.9 volt zener diode rated at 200 to 250mW.

CONSTRUCTION

The first procedure in construction consists of cutting the copper strips at the appropriate points. These are shown in Fig. 2, which illustrates the component and copper sides of the completed board. Cut the strips at holes A13, B4, B8, B11, C4, C10, C14, D9, E9 and G10.

Next, take up the output transformer, T1, and carefully file or snip its mounting lugs such that they are capable of being passed through holes G14 and B14. Do not, however, actually fit the transformer yet.

Consulting the upper diagram in Fig. 2, connect the two speaker leads to holes F16 and E16, and the two test leads to holes D16 and C16. Connect a link between holes C15 and A15. This link should consist of thin insulated wire. Shortening as necessary, and whilst the transformer is resting but not mounted on the board, connect the black and white secondary leads of T1 to holes F15 and E15. Then, whilst gently manoeuvring the secondary wires so that they do not become trapped under the transformer, pass the transformer lugs through holes G14 and B14 and solder the lugs at these holes. The transformer need not be pressed tight against the board; its mounting will be quite satis-

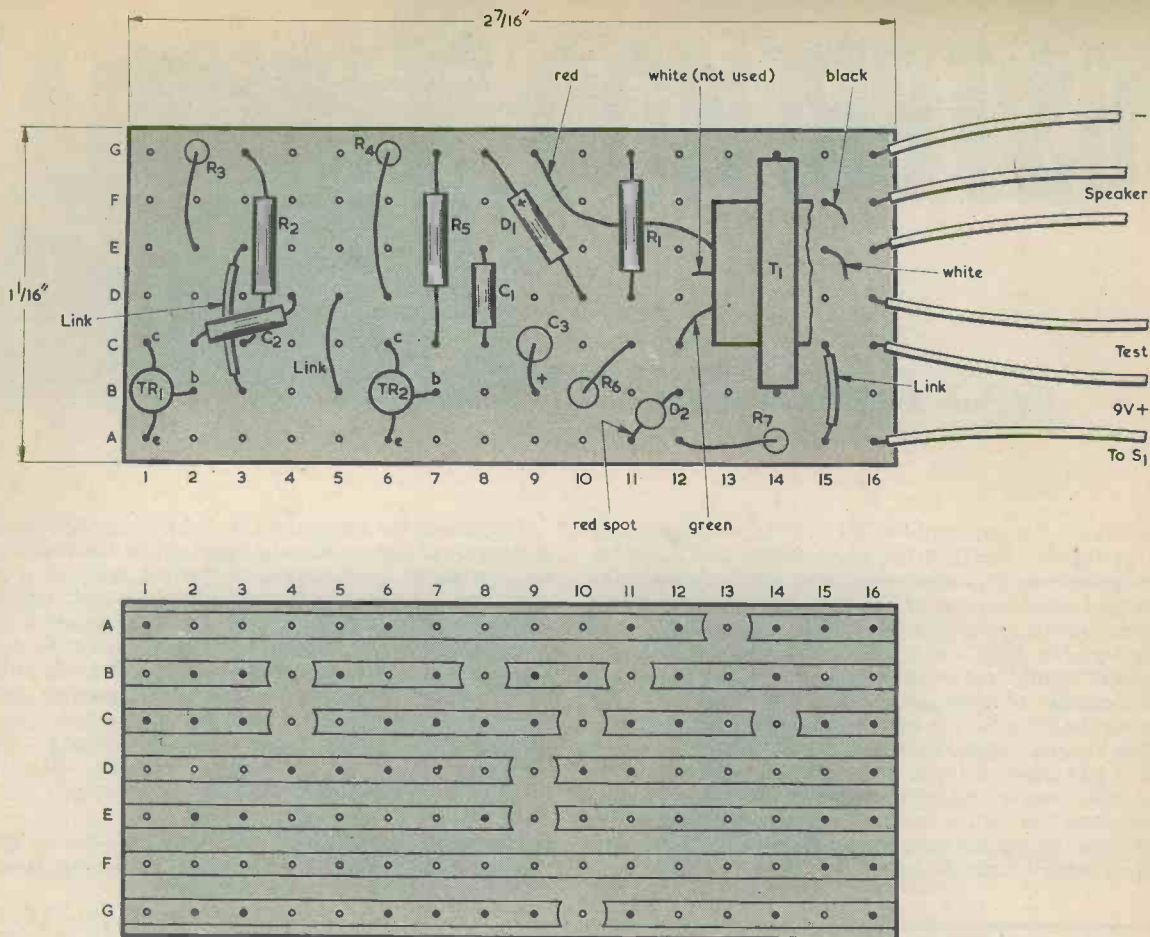


Fig. 2. How the continuity tester is assembled on the Veroboard

factory provided that sufficient of each lug passes through its hole to enable a satisfactory solder joint to be made. The reason for fitting the link and the other wires before mounting the transformer is that this component covers their connection points. The transformer is shown partially cut away in Fig. 2 to enable these connection points to be seen. Whilst dealing with the transformer, a further point is that its two lugs also provide a link via the transformer frame, between holes G14 and B14.

Connect the red primary lead of transformer T1 to hole G9, and the green primary lead to hole C12. The white primary lead is not used; any exposed end it may have should be cut off and the lead coiled up out of the way. It must not be allowed to short-circuit against the transformer frame or any other conductor. All of the transformer leads may, of course, be cut to a suitable length before they are connected into circuit.

Next fit an insulated wire link between holes E3 and B3, positioning this such that free access is available to hole C3. Fit a bare wire link between holes D5 and B5.

Following Fig. 2, fit the following components, which are all mounted horizontally: R2, R5, D1 and R1. The positive end of D1 connects to hole G8. Fit the zener diode, D2, to B12 and A11 with the lead-out which should connect to the positive side of the circuit in which it is used at hole A11. This lead-out is usually

identified by a red spot on the outside of the diode case. Next fit capacitors C1 and C2. C2 straddles R2 and the insulated link between holes E3 and B3. Fit C3 vertically, with its positive lead-out at hole B9. Follow this with the fitting of R3, R4, R6 and R7, all of which are mounted vertically.

Fit the two transistors, a negative battery lead to hole G16 and a positive battery lead to hole A16. This last lead connects to the battery via S1.

The continuity tester is now complete and ready for use. If a voltmeter is available, check that approximately the zener voltage appears across D2 when the two test leads are short-circuited. For this test, the voltmeter may, for convenience, be connected between the negative battery lead and strip A1 to A12. If the voltage across the diode is less than 1 volt it has been connected the wrong way round. A zener diode connected wrong way round will also cause the tester to give an output when the 'Test' terminals are connected to values of resistance much higher than 350Ω.

The completed Veroboard assembly, the speaker and the battery can be housed in any conveniently sized plastic or wooden case, this having switch S1 and two test sockets on its front panel. Two flexible test leads terminated in prods or clips are also required, and these are plugged into the test sockets.

Two Colour Cathode Ray Tubes

by J. B. Dance, M.Sc.

The presentation of colour pictures for radar displays incurs techniques that are quite different from those used for domestic colour television

THE AMOUNT OF INFORMATION WHICH MUST BE displayed on some types of cathode ray tube screens is now very great. One of the ways in which this increased amount of displayed information can be more quickly evaluated involves the use of cathode ray tubes which can display two or more colours.

PHOSPHOR LAYERS

One might expect such tubes to employ the same type of techniques as those employed in colour television tubes, such as the three gun shadow mask tube. Although these tubes can produce excellent television colour pictures, the resolution provided by the groups of three dots of different phosphors is inadequate for high resolution radar tubes. The latter may be required to have a spot diameter of about 0.3mm. diameter and be capable of displaying information at any or all of about a million points on the tube face.

A high resolution cathode ray tube with a two colour display can be made by employing a layer of one phosphor deposited on the inside of the glass face of the tube with a layer of another type of phosphor deposited on the first phosphor. A thin inert layer which will not emit light is used to separate the two phosphors.

When the accelerating voltage applied to the tube is relatively low, the electron beam is absorbed in the first phosphor it meets. If, however, the accelerating voltage is increased, the electrons will have enough energy to penetrate through the one phosphor and excite the phosphor nearest the glass envelope of the tube.

The use of an inert layer between the phosphors helps to provide greater colour purity by preventing premature excitation of the phosphor nearest the glass by

electrons of relatively low energy. The decay times of the two phosphors can be selected to suit the requirements of the particular application concerned.

MODES OF OPERATION

In one type of two colour tube a single electron gun is employed, the energy of the electron beam being changed by varying the potential applied to the final anode of the tube. The two colours are actually displayed sequentially, but if the tube voltage is switched very rapidly, they appear virtually simultaneously. In some tubes a post deflection acceleration electrode is used and it is then possible to prevent the change of accelerating voltage from affecting the deflection sensitivity and the focusing of the tube.

Another type of tube employs two electron guns. The anodes of such a tube are at the same potential, but one of the cathodes is at a much greater negative potential than the other cathode. Each electron gun then excites its own phosphor.


Two colour tubes being developed at present operate at typical accelerating voltages of 8kV and 13kV, but it is possible to generate some intermediate colours by the use of an intermediate accelerating voltage.

APPLICATIONS

It seems likely that two colour tubes will be used in oscilloscope displays, warning systems, computer displays, airline traffic schedule boards, seat reservation displays, etc. Developmental work has been carried out by The M-O Valve Company, London W6 7PE, and a range of tubes is now available.

HIGH INPUT IMPEDANCE AMPLIFIER

by G. A. FRENCH

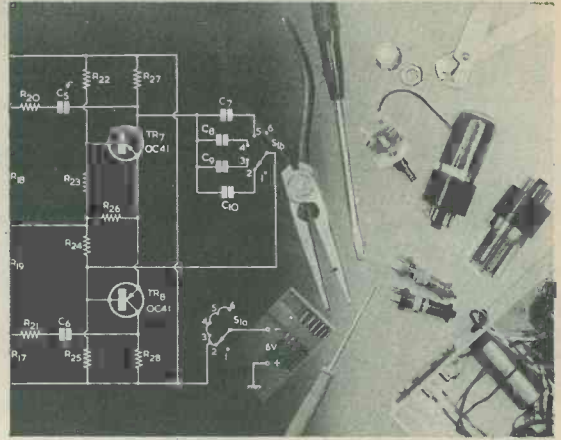


THIS MONTH'S ARTICLE IN THE 'Suggested Circuit' series is devoted to a simple a.f. amplifier which may be employed for general purpose work where a high input impedance is required. It is particularly useful for amplifying the output from a ceramic gramophone pick-up, and it can be similarly loaded by other

inputs having the same voltage amplitude. With a 25Ω speaker the output power available before the onset of clipping is of the order of 300mW, and the quality of reproduction is comparable with that given by the larger type of transistor battery portable radio. A somewhat unusual bias technique enables feedback to be applied overall

without additional components.

THE CIRCUIT

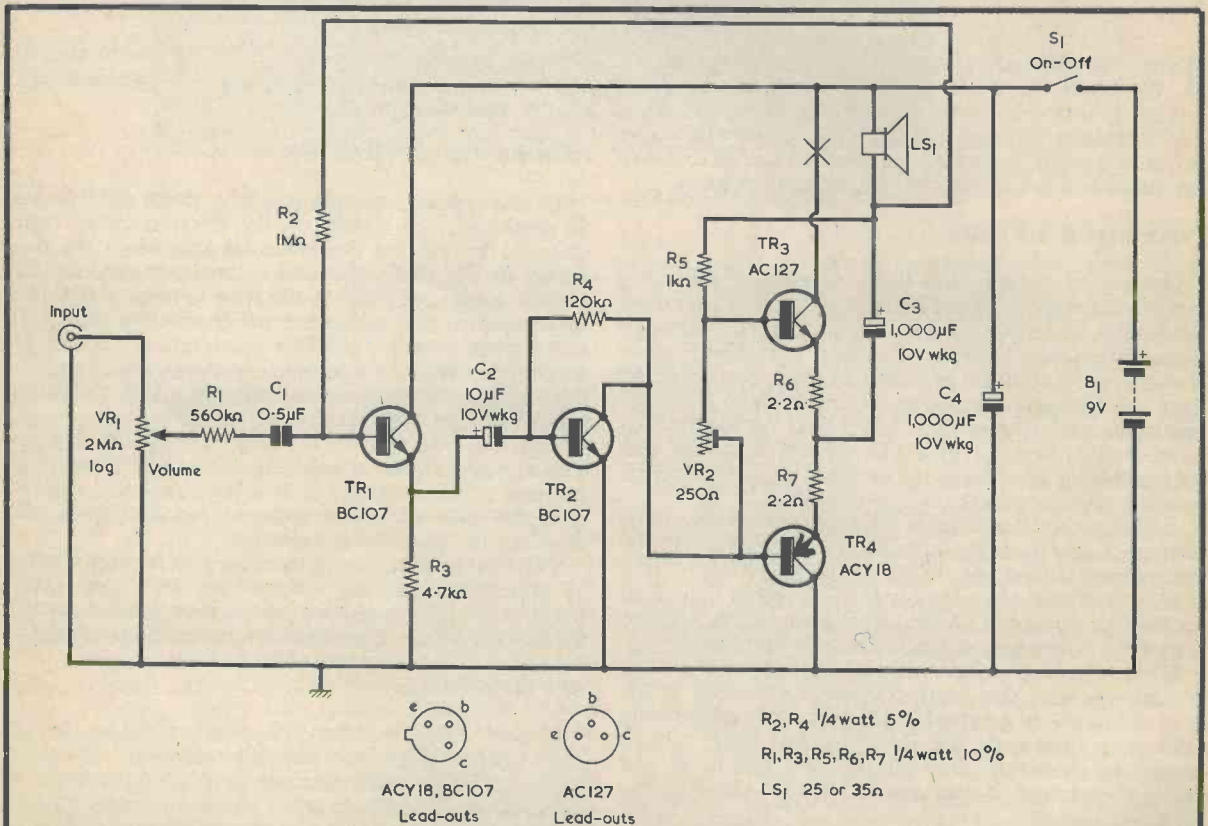The circuit of the amplifier appears in the accompanying diagram, and it will be noted that it employs two silicon transistors in the first stages, these being followed by two germanium transistors in a complementary emitter follower output stage.



The circuit of the amplifier. This can be coupled direct to a ceramic pick-up and it offers an output of 300mW when a 25Ω speaker is used.

The input signal is applied to volume control VR1, whose slider couples to the base of TR1 via R1 and C1. The impedance at TR1 base is such that the input impedance of the amplifier is approximately 700k Ω when VR1 slider is at the top end of its track. The input impedance increases gradually up to 2M Ω as VR1 slider moves down its track towards the minimum volume end. These impedance figures are sufficiently high to enable a ceramic pick-up to be connected directly to the amplifier input.

TR1 functions as an emitter follower and it offers no voltage amplification. Its emitter couples to the base of TR2, which is connected in the common emitter mode. TR2 provides both voltage and current amplification, the latter being sufficient to drive the two output transistors, TR3 and TR4. Apart from a small crossover range for small signal deviation, only TR3 is conductive for positive half-cycles at the collector of TR2 and only TR4 is conductive for negative half-cycles. When conductive, each output transistor operates as an emitter follower and the overall output stage is a conventional Class B complementary design. The collector current for TR2 is obtained via the speaker, R5 and VR2; and a.f. coupling to the speaker is achieved via C3. The two low-value resistors, R6 and R7, are included to prevent thermal runaway in the output transistors.

Finally, S1 is the on-off switch, whilst C4 is a high-value electrolytic capacitor which ensures that a low impedance is still present across the supply rails when the battery ages and its internal resistance increases.

All the transistors except TR2 act as emitter followers, whereupon they may be expected to contribute little distortion to the signal as it is amplified. TR2 is, however, called upon to provide a wide collector voltage swing whilst driving the output transistors, and it cannot do this without contributing a significant degree of distortion. A slight reduction in this distortion is given by returning the bias resistor, R4, to TR2 collector, thereby introducing a small level of negative feedback. But the distortion produced by TR2 is mainly reduced to an acceptable level by coupling TR1 bias resistor, R2, to the lower terminal of the loudspeaker. This overall feedback loop encompasses the whole amplifier including the speaker, and enables the quality of reproduction to be adequate for an inexpensive amplifier of this type.

The values of R2 and R4 are such as to cause the emitter of TR1 and the collector of TR2 to be reasonably close to half supply voltage level for virtually all transistors type BC107, regardless of spread in hFE.

In practice, the collector voltage of TR2 should have a value which causes the junction of R6 and R7 to lie at some 4 to 5 volts positive of the

negative supply rail. This means that a peak voltage of at least some 4 volts in either direction is available to drive the speaker before clipping takes place. A peak voltage of 4 corresponds to an r.m.s. voltage of 2.8 with the result that, from V^2/R , an output power of slightly more than 300mW is feasible with a 25 Ω speaker.

COMPONENTS AND CONSTRUCTION

All the components used in the amplifier are readily available. It is important that the transistors employed be those specified. The fixed resistors are as indicated in the diagram. VR1 is a standard panel-mounting potentiometer and it can be ganged with S1, if desired. VR2 may be a skeleton pre-set potentiometer. The electrolytic capacitors can have higher working voltages than those indicated, should components with such working voltages be easier to obtain. The quiescent current drawn by the amplifier is around 10mA, this rising to 50mA or so on volume peaks. A suitable 9 volt battery is the Ever Ready PP9.


Construction should raise no problems and virtually the only layout requirement is that the components in the input circuit, i.e. VR1, R1, C1 and R2, be kept away from those in the output circuit. The input circuit is also very slightly susceptible to hum, but there is no necessity to screen the components concerned if mains leads are not allowed to approach them closely. The complete amplifier can be enclosed in a metal case which is common with the negative supply rail, and this will ensure that all internal components are automatically screened. The coupling from a ceramic pick-up, or similar high impedance source of signal, to the amplifier input socket should be made via a screened lead.

The connection between the collector of TR3 and the positive supply rail should be omitted during initial wiring. The connection is indicated by a cross in the diagram. When the wiring, apart from this connection, has been completed and checked, a current reading meter is inserted between the collector of TR3 and the positive supply rail. VR2 is set so that it inserts minimum resistance into circuit, a 9 volt battery is connected and S1 is switched on. The resistance inserted by VR2 is then slowly increased until the meter indicates about 7mA. The amplifier is next switched off, the meter removed and the collector of TR3 connected permanently to the positive supply rail. It is important to ensure that VR2 is not accidentally set to insert too high a resistance, as the output transistors may then pass excessive current. The amplifier is now set up and complete, and it may be checked out with a ceramic pick-up or similar a.f. signal source.

BUY THIS BEST SELLER

T.V. FAULT FINDING

405/625 LINES

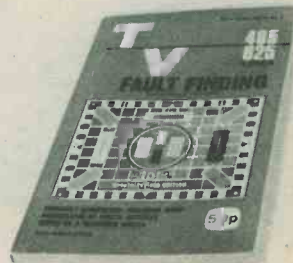

REVISED & ENLARGED

Edited by J. R. Davies

124 pages Only 50p

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

Price 50p from your Bookseller

or post this Coupon together with remittance for 56p (to include postage) to

DATA PUBLICATIONS LTD.
57 Malda Vale, London, W.9

Please send me the 4th revised edition of TV Fault Finding, Data Book No. 5

I enclose cheque/crossed postal order for.....

NAME


ADDRESS

.....

.....

R.C. Block Letters Please

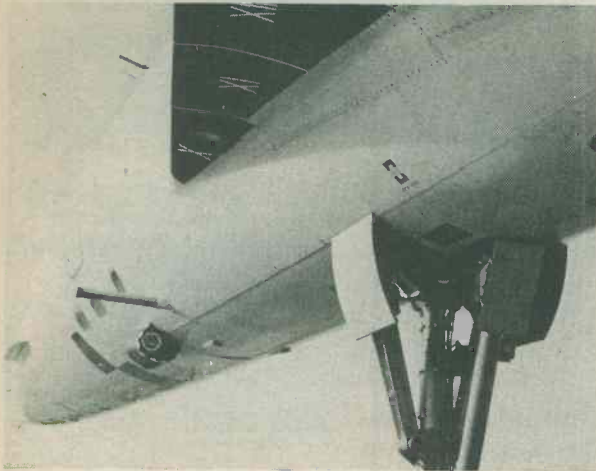COLD WORK FOR CONCORDE CLOSED-CIRCUIT TV CAMERA



Aimed rearwards under the fuselage and port wing of Concorde 002, an all-weather THV-1160 closed-circuit television camera from Bell & Howell provides key pictures of the aeroplane's latest flight-test programme for study by BAC engineers. The camera is visible (left) inside the bubble-type housing

Airborne in temperatures falling to -30°C , a closed-circuit television camera mounted on the outside of Concorde 002 is serving as a flying "eye" for engineers of the British Aircraft Corporation during the current flight-test programme. Giving a rearward view under the port wing, the camera feeds pictures of the complete aerofoil, including the engine intakes, to video recording equipment in the aircraft.

A THV-1160 from Bell & Howell, the camera is an all-weather type with a built-in heating system to combat the extreme cold of high altitudes. Low temperature operation is fundamental to the present tests, which are concerned with the formation and dispersal of ice.

This THV-1160 is a Bell & Howell modified version of a standard monochrome Vidicon camera made by Thomson-CSF Audiovisuel of France. It has been adapted to operate under external sync control and its housing has been pressurised, it is otherwise the normal 1160 camera.

A second closed-circuit camera, a THV-1100, has been installed inside Concorde 002. This supplies a digiclock input for superimposition on the video recordings. The signal is routed, through a Viscount keying system, to the video tape equipment, IVC type 821. Another 821 is on the ground for replaying the recordings.

The IVC 821 was chosen for use in Concorde mainly because it is a full-bandwidth VTR with read-after-write facility for the video track.

PEACE AT A PRICE

PEACE at a price – that's what is offered to parents and neighbours of teenagers who like to play, or learn to play the guitar. An idea which could revolutionize relations between the generations in some households, was described on BBC World Service's *New Ideas*.

The Guitar Set headphone allows the musician to practise on the electric guitar . . . in silence! The sound he produces is transmitted to the pair of headphones he wears which are plugged directly into the guitar itself.


There is no need to feed the sound through a special amplifier; the built-in twin miniaturised amplifiers are powered from a self-contained set of batteries, and you can, of course, control the volume of the headset.

It could prove a useful system for musicians and music schools. The system – the makers say – gives sound reproduction of excellent quality. The Guitar Set sells in Britain at just under £20 – not too bad a price to pay perhaps for peace and quiet?

EMI SUPPLIES NIGERIA WITH TV OUTSIDE BROADCAST VEHICLES

EMI has recently provided two monochrome television outside broadcast vehicles, worth over £155,000, to the Nigerian Broadcasting Corporation for its Channel Ten service based on Lagos. The 18 ft. long vans, complete with mobile power generators, were airfreighted to West Africa in time for the Second All African Games held in Lagos during January.

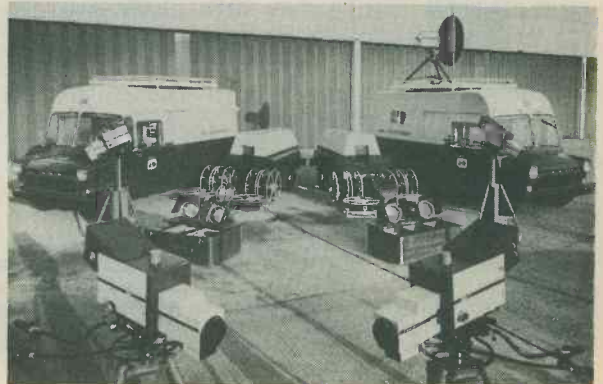The photograph below shows a line-up of the vans and their respective EMI '2004' monochrome cameras, cabling, lighting and generator, prior to departure from EMI Sound & Vision Equipment Ltd. at Hayes, Middlesex.



RADIO & ELECTRONICS CONSTRUCTOR

COMMENT

FARADAY LECTURE IN LONDON

The London delivery of "Navigation - land, sea, air and space", the 44th in the series of Faraday Lectures organised by the institution of Electrical Engineers, took place recently at Central Hall Westminster.

Man's navigational instinct is far inferior to that of many animals and he has therefore had, over the ages, first to develop the art and then to apply his scientific and technological skills to devising instruments that enable him to explore his own planet and the universe beyond.

Electrical engineers have played a major part in the development of navigational aids from the time of Michael Faraday in the early 19th century, with his experiments on electromagnetic induction, to the present day and the development of the directional gyroscope which is used by the Lunar Rover for navigating the moon's surface. With increasing numbers of people travelling greater distances on business and pleasure, with the growth of sailing and flying as hobby activities and with manned voyages into space, almost everyone relies to some extent on the electrical engineer who plays his part in designing navigational systems that not only extend the capability of man but also ensure his safety - at an acceptable cost.

"Navigation - land, sea, air and space" was the title of the Faraday Lecture delivered by Dr. Andrew Stratton, Director of the Defence Operational Analysis Establishment, and his Deputy Lecturer, Wing Commander (Retd) E. W. Anderson, Navigational Adviser of Smiths Industries Limited. They told the story of the development of navigation from the days when the stars were our only guide to the sophisticated instruments of today which have helped to make it possible for man to reach the moon.

PACKAGED POWER GOES TO MONTE CARLO RALLY



Driving a Sunbeam Stiletto in this year's Monte Carlo Rally, Andy Michailidis had a significant advantage over his competitors in the event of his car sustaining crash damage. Anywhere along the route between Glasgow and Monte Carlo, Andy was able to use mains-powered tools to effect emergency repairs.

This was made possible by a power unit manufactured by Jermyn Distribution, which provided a 250V, 50Hz, electrical power supply from car batteries. Supplying almost a third of a kilowatt, the unit was used to power an electric drill and a sheet metal cutting machine.

The Rally was Andy Michailidis' eighth international rally and his co-driver, Philip Bond, has driven in two similar events. Both drivers are convinced that the small amount of extra space taken by the Jermyn power supply and the extra weight were a small price to pay for the convenience of their own personal mains power supply.

Jermyn Distribution designed the power supply for domestic use during power cuts.

IN BRIEF

● Microwave 73, the first international conference and exhibition to be devoted to the microwave and allied industries, will be opened by HRH the Duke of Kent.

Microwave 73 will be held in Brighton from 19th to 21st June.

● LST Electronic Components Ltd., of Brentwood, Essex, expect a substantial expansion of their business following the sale of the company's equity to Crellon Holdings Ltd.

Prior to the sale of the equity LST was a privately-owned company founded by Mr. Peter Clarke, who remains Managing Director of LST and Arrow Electronics Ltd.

APRIL 1973

Mr. Clarke is a radio amateur with the call sign G3LST, hence the name of the company.

● The membership lists of The Radio Amateur Invald and Bedfast Club show that they had more than 160 licensed members, and more than 240 SWL members at the commencement of this year.

● With the growing importance of the UK offshore oil industry, with its specialised radio communication requirements creating a vast market in its own right, the Marconi International Marine Co. Ltd., a GEC-Marconi Electronics company, has formed an Oil Industry Division under the management of Mr. G. H. W. Johnson.



POWER SUPPLY DESIGN

by A. Foord

How to design stabilized power supplies with the aid of zener diodes, transistors and integrated circuits.

THE POWER SUPPLY IS AN ESSENTIAL PART OF EVERY electronic equipment. In its simplest form it may consist of nothing more than a transformer, rectifier and smoothing circuit, but frequently more elaborate arrangements are needed so that an overall system can meet the stringent performance we expect today. Integrated circuits, for example, may demand well defined power supply levels.

In research and development where time and staff are at a premium it is sometimes more economical to buy complete power supplies than to develop them 'in house', especially if a high performance is required. However in consumer and home constructor applications, where low cost is a prime requirement, power supplies must be designed and constructed to suit the application. An easy and flexible approach is to use readily available components to construct a basic unregulated supply, and then add a suitable voltage regulator to provide the stabilization.

In this article we will consider how modern regulated power supplies are designed using either discrete components or integrated circuit voltage regulators.

BASIC ZENER DIODE SHUNT REGULATOR

The simplest method of regulating the output voltage from a basic unregulated supply is by using a series dropping resistor and a shunt zener diode, as in Fig. 1. Here the series resistor R can be assumed to be the sum of the internal source resistance and an external resistor. If the input voltage rises then more current flows through the zener diode and a greater voltage drop is produced across R. The output voltage will

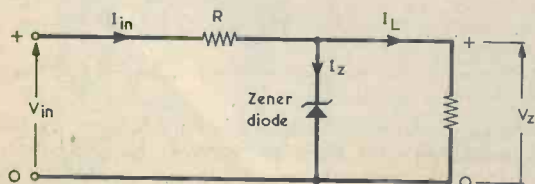


Fig. 1. The simple zener diode shunt regulator

always be equal to the zener diode voltage. The basic equation is:

$$I_{in} = I_z + I_L$$

The maximum power is dissipated in the zener diode when the load current is zero and the input voltage is at maximum. This is given by:

$$P_{max} = V_z \times I_z(max)$$

$$\text{where } I_z(max) = \frac{V_{in(max)} - V_z}{R}$$

This must not exceed the rated power capacity of the diode. When the value for R is determined, the limiting case where V_{in} is minimal and the load current is maximal must be used. R must be small enough to allow the minimum permissible zener diode current to flow, so that the diode slope resistance is low. (Normally, the minimum permissible zener diode current would be found from manufacturers' data, and it is recommended that diodes are not run below the current at which the nominal characteristics are quoted. If this is not known they should not, as a very rough guide, be run below one-tenth of their maximum permissible dissipation.) Simple equations using Ohm's Law will give the various parameters in the circuit for the maximum and minimum input voltage and load current conditions. Ripple is reduced by a factor which depends on the value of R and the effective impedance of the zener diode (which may be about 3Ω for a diode dissipating 2 watts). One circuit for a 27V supply is shown in Fig. 2.

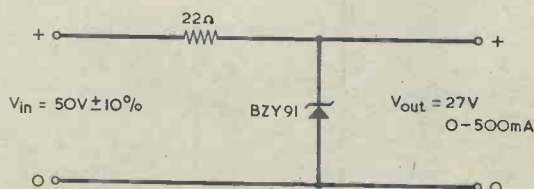


Fig. 2. A practical circuit for a 27 volt supply

RADIO & ELECTRONICS CONSTRUCTOR

The minimum zener diode current is about 100mA and the maximum diode power dissipated is about 34 watts. If the maximum ambient temperature were 65°C a heat sink with a thermal resistance of 1.0°C per watt would be safe. A Mullard type 50D extruded heat sink which was 10cm. long would be correct.

This circuit has the disadvantage that considerable power is dissipated in the zener diode under no-load conditions. Since both high power zener diodes and large heat sinks are difficult to obtain, particularly by home constructors, a zener diode circuit of this nature would only be used to supply small load currents. As small zener diode (400mW or 1.5W) are much more readily available the approaches shown later would be more applicable for the relatively large output current (500mA) illustrated here.

TWO STAGE ZENER DIODE SHUNT REGULATOR

When a particularly stable reference is required, for example in a digital voltmeter, a two stage regulator may be used, as in Fig. 3. This improves the stabilization against input voltage changes although the load and temperature stability is not improved very much. For best results temperature compensated zener diodes can be obtained which consist of a zener diode and a forward biased diode in series, so that the overall combination has a very low temperature coefficient.

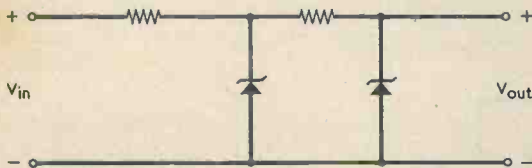


Fig. 3. The basic 2-stage zener diode regulator

SIMPLE SHUNT TRANSISTOR REGULATOR

A simple shunt transistor regulator can be constructed where a low power zener diode is used, see Fig. 4. The transistor can be regarded as an emitter follower and the output voltage will be the sum of the zener voltage and the base to emitter voltage (about 0.7V) of the transistor.

Although highly developed shunt regulators can be constructed, in general it is more efficient if the regulating element (usually a transistor) is in series with the supply.

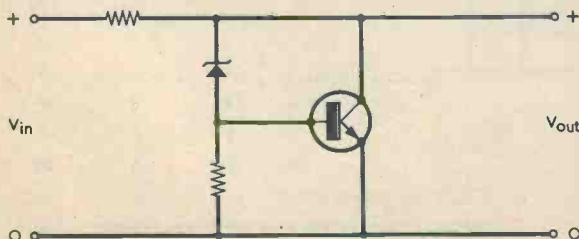


Fig. 4. A simple shunt transistor regulator

APRIL 1973

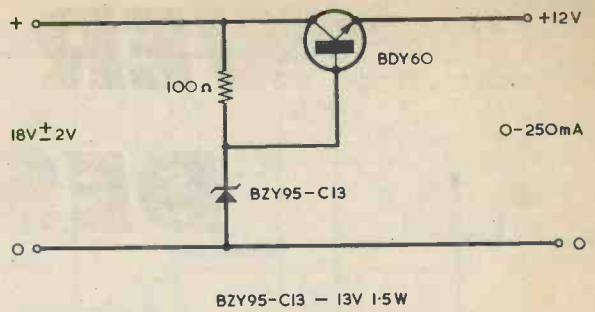


Fig. 5. A simple series regulator for a 12 volt supply

BASIC SERIES REGULATOR

The simplest form of series regulator is shown in Fig. 5. The transistor is used as an emitter follower where the base voltage is maintained constant. Design is straightforward in that the zener diode current must under all conditions be sufficient to maintain the diode at a low impedance. The unregulated supply must be chosen so that there is always a few volts across the transistor, even under maximum load conditions. However, using too high an unregulated supply increases the transistor dissipation without need.

FEEDBACK STABILIZED POWER SUPPLY

The previous regulator circuit can be considered as a device (the transistor) which compares a reference voltage with the output voltage (load current times load resistance) and brings them near to equality. In general terms a feedback stabilized supply will break down into the sections shown in Fig. 6. A reference

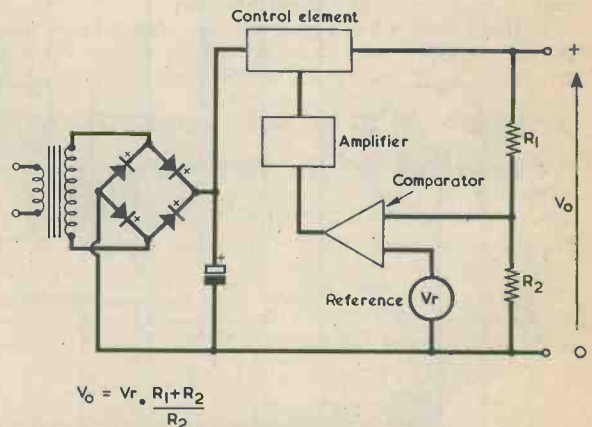


Fig. 6. The basic feedback regulated supply

voltage is compared with the output voltage, any error is amplified and used to control the output level. Depending on the gain round the loop such a circuit can give an excellent performance in terms of ripple and regulation if proper care is taken with the design.

557

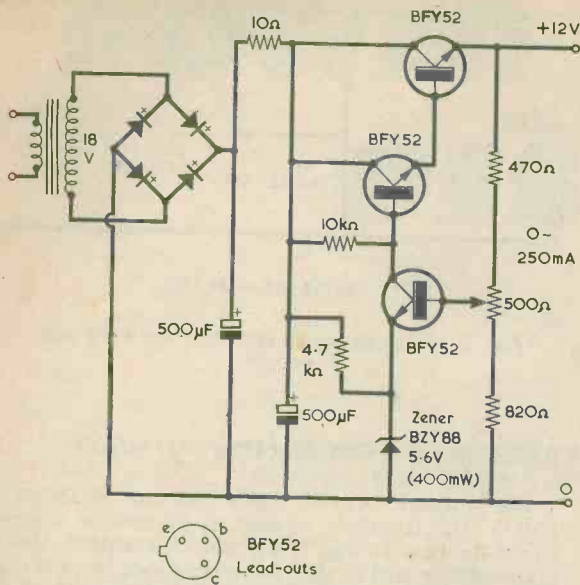


Fig. 7. A feedback regulated supply for 12 volts

A discrete component 12V supply is shown in Fig. 7. The series transistor dissipates up to 4 watts and should be mounted on a heat sink of thermal resistance 10°C per watt. The design is then suitable for ambient

temperatures up to 50°C. Output ripple is about 2mV peak to peak and the voltage regulation is 5%.


Although more elaborate circuits can be constructed using discrete components it is advantageous to use integrated circuits where an improved performance is required.

15 VOLT 100mA SUPPLY

The circuit for this supply is shown in Fig. 8. The $\mu A741$ is a general purpose operational amplifier and can be used in this type of circuit where a special purpose voltage regulator is not justified. The unregulated d.c. supply is applied through TR1 and the low value resistor R3 to the output. The output voltage is reduced by a potentiometer chain and compared with the reference. Any error is amplified by the $\mu A741$ and used to correct the base voltage of TR1. Protection against an excessive load current is provided by R3 and TR2. As the current through R3 increases, TR2 becomes turned on and reduces the base current available to TR1. The supply tends to become a constant current rather than a constant voltage one, and the current is limited to:


$$I_L(\max) = \frac{0.7}{R_3} \text{ amps.}$$

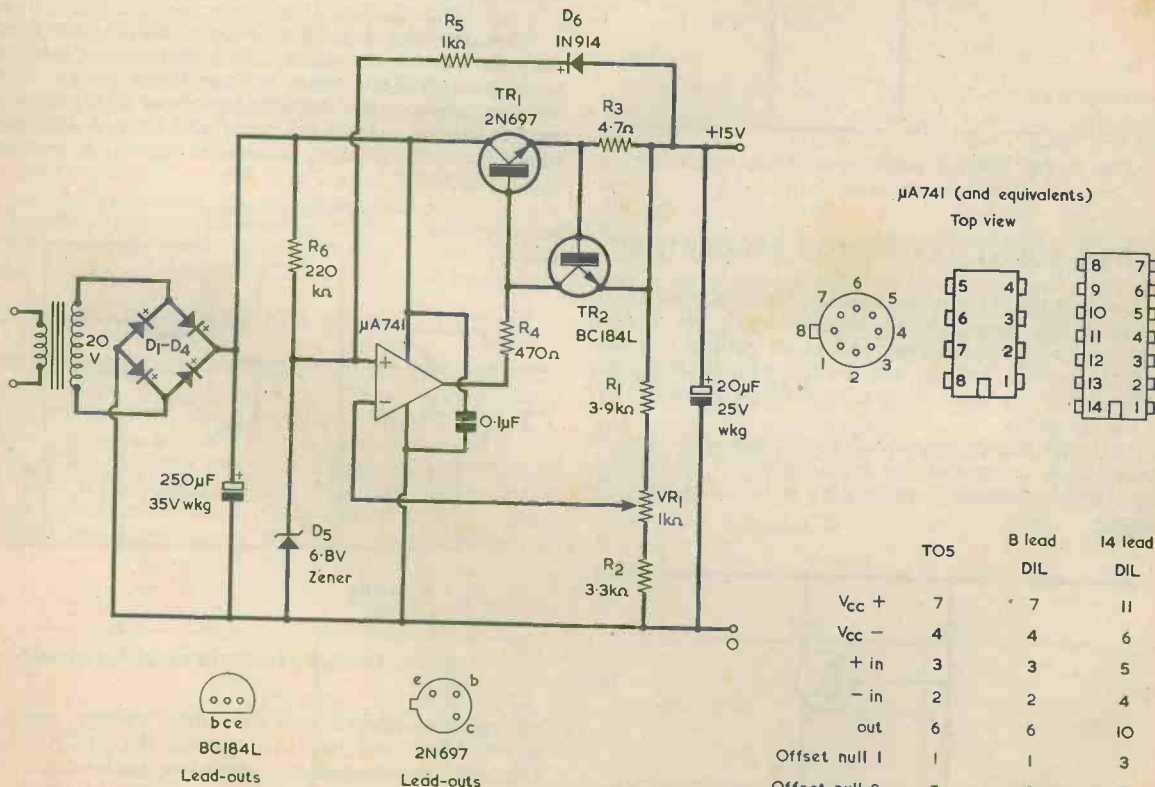The supply for the zener diode is taken from the output because this improves the performance. With this arrangement there may be a problem about starting



$\mu A741$ (and equivalents)

Top view

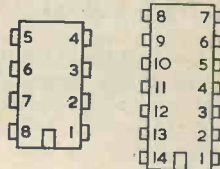

	TO5	8 lead DIL	14 lead DIL
V _{CC} +	7	7	11
V _{CC} -	4	4	6
+ in	3	3	5
- in	2	2	4
out	6	6	10
Offset null 1	1	1	3
Offset null 2	5	5	9

Fig. 8. A +15 volt supply using the $\mu A741$ integrated circuit

conditions when the supply is first switched on. The problem is overcome by R6 which supplies a small amount of current to the zener diode until the output is greater than 7 volts, when D6 conducts to provide the usual zener diode current.

The short-circuit current is limited to about 150mA. The hum and noise on the output is 2mV peak-to-peak at the full load current of 100mA. The power dissipated by the 2N697 will depend on the mean value of the unregulated supply under load, but would typically be 1 watt. This is within its rating if its case is kept below 100°C, so a heat sink must be used. Under short circuit conditions it may dissipate 3 watts or more, which is beyond its ratings on an infinite heat sink. The unit can be considered to be protected against a temporary short-circuit only, unless a slightly larger transistor is used.

To power operational amplifiers both positive and negative supplies are required. If identical regulator circuits are used then two separate transformer windings are needed, as in Fig. 9. If complementary regulators can be designed then a single (or centre-tapped) transformer winding can be used, as shown in Fig. 10.

A wide range of equivalents to the $\mu A741$ can be used in the circuits of Fig. 8 and Fig. 10. In the 8 lead T05 package, these include L141TI, MC1741CG, TBA221, LM741C, CA3056, SN72741L, $\mu A741C$ and LIC741C/5. In the 8 lead d.i.l. package, equivalents are 7410PA and SN72741P. Equivalents in the 14 lead d.i.l. package are L141BI, MC1741CP, LM741CN, SN72741N and LIC741C/14. A further equivalent, the 741C, is available from Henry's Radio both in T05 and d.i.l.; whilst the 7410PA is an R.S. Components product. No connections are made to the offset null terminals.

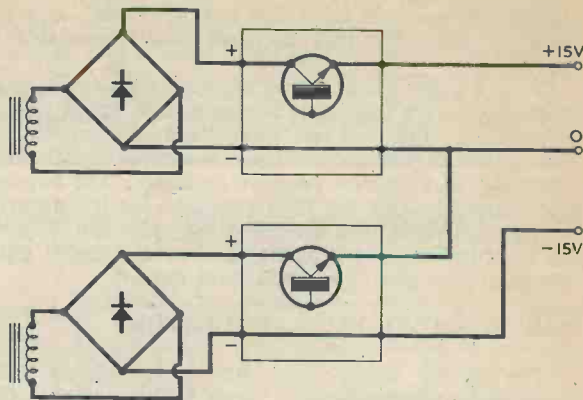


Fig. 9. If identical regulators are used then separate transformer windings are needed for dual supplies

VOLTAGE REGULATOR INTEGRATED CIRCUITS

Since the $\mu A741$ can work with a total supply rail of between about 6V and 30V, its use in the manner just described is suitable for power supplies from 6V to 24V or so. If several power supplies are required then it may be worthwhile using an integrated circuit specifically designed for power supply use. Most semiconductor manufacturers make suitable voltage regulators for positive, negative, or more recently, dual positive and negative outputs. The current available depends on the package; in general a current of up to

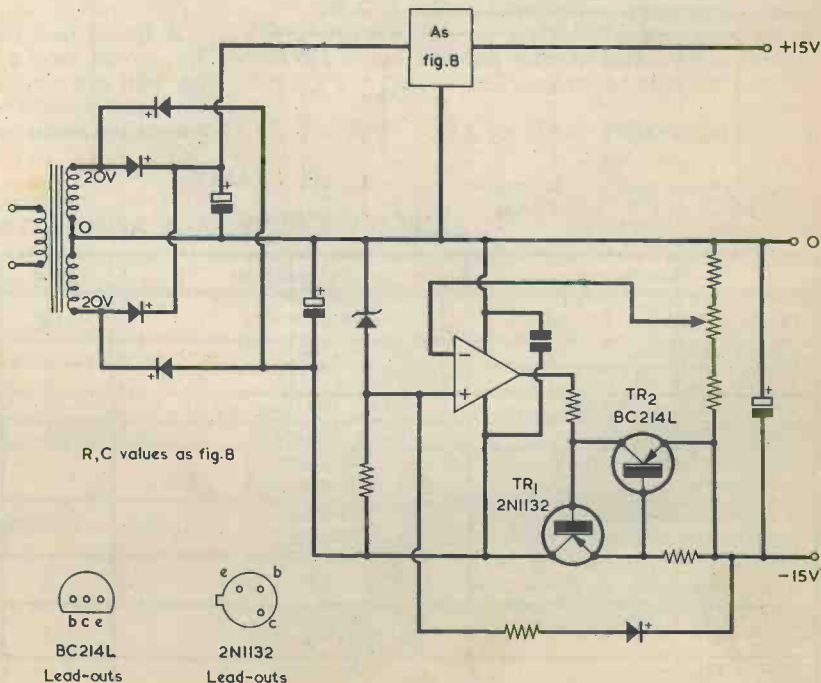


Fig. 10. Where complementary regulators are used two separate transformer windings are avoided

100mA is possible from the package itself, and an external transistor may be used to increase this if required.

Recent developments tend to require fewer external components for frequency compensation, short circuit protection, and voltage adjustment. It would be worthwhile comparing the many available types before deciding on a general purpose regulator. The circuits are designed along the lines indicated for the discrete component regulators and a few examples can be used to illustrate the types available. Manufacturers' data sheets always give full applications data.

THE SG309 VOLTAGE REGULATOR


The SG309 voltage regulator is completely self-contained and produces a 5 volt output suitable for driving logic integrated circuits. It is available in two packages, a T03 version which provides up to 1A and a T05 package which gives up to 200mA, depending on the power dissipated in the package. In large digital systems a 'rough' supply of 10V could be used with local regulation on each individual card. This reduces the problems of short switching spikes remaining on the power supply lines, which produce unpredictable results!

The parameters for the SG309 are shown in the Table, with a typical operating circuit in Fig. 11. It has built-in current limiting and thermal shut-down to protect it against excessive power dissipation, making it essentially destruction proof. The transformer and reservoir capacitor are chosen to keep the rough supply between 7V and 25V from no load to full load.

TYPICAL HEATSINK REQUIREMENTS

Suppose that the mean input voltage is 14V under the full load current, for the T03 version, of 1A. Voltage dropped across SG309 = 14 - 5 = 9V. Power dissipated in SG309 = 9 x 1 = 9 watts. Maximum permitted junction temperature = 125°C. Thermal resistance from junction to case = 3°C per watt.


∴ base temperature = 125 - 3 x 9 = 98°C.

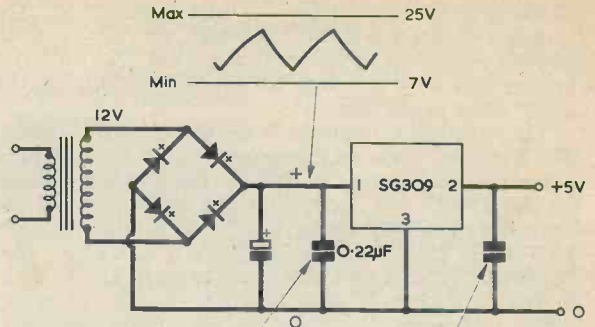

Place across regulator terminals if some distance from reservoir capacitor

Not essential, but may improve transient response

Connection diagrams

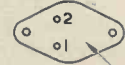

Case 3

Underside views

Fig. 11. A 5 volt supply using the SG309

Assuming an ambient temperature of 30°C, then the required heat sink thermal resistance is:

$$\text{Heat sink thermal resistance} = \frac{98 - 30}{9} = 7.6^\circ\text{C per watt}$$

A finned heat sink of dimensions 4in. by 1.5in. by 2in. would have a thermal resistance of about 3.5°C per watt and would provide a good safety margin. If a 9V transformer and suitable capacitor were used to reduce the mean voltage developed across the SG309

TABLE

SG309 5-VOLT VOLTAGE REGULATOR

Parameter	Conditions	Min.	Typ.	Max.	Units
Output Voltage		4.8	5.0	5.2	V
Line Regulation	Vin 7 - 25V		4	50	mV
Ripple Rejection	10Hz - 10kHz		75		dB
Output Noise Voltage	10Hz - 10kHz		40		µV r.m.s.
Output Impedance	10Hz - 10kHz		0.1		Ω
Thermal Resistance, junction to case	(a) T05 case (b) T03 case		15 3		°C/W °C/W
Thermal Resistance, junction to ambient	(a) T05 case (b) T03 case		150 35		°C/W °C/W
Maximum Junction Temperature				125	°C
Maximum Current	(a) T05 case (b) T03 case			0.2 1.0	A A
Power Dissipation (infinite heat sink)	(a) T05 case (b) T03 case			2 20	W W

then its power dissipation will be reduced. It is useful to note that the case is directly earthed so that in many applications the integrated circuit can be directly bolted to the chassis and a separate heat sink avoided.

The SG309 regulator may be obtained from Rastra Electronics Ltd., 275 King Street, Hammersmith, London, W6 9NF.

R.S. COMPONENTS REGULATORS

Regulators similar to the SG309 are also available in higher voltages. The R.S. Components type MVR series provide 5, 12 or 15V at 600, 500 and 450mA respectively. They are in T03 cans and, when used with the recommended R.S. Components transformers, the output ripple is typically 1mV.

The MVR 5V regulator should be employed with R.S. Components mains transformer type 633, the MVR 12V regulator with the transformer type 632 and the MVR 15V regulator with the transformer type 634. The circuit is the same as for the SG309, with the reservoir capacitor having a value of 10,000 μ F and the capacitor following the regulator a value of 10 μ F. The rectifier may be the R.S. Components silicon bridge type REC41A, which is rated at 1.8A with a p.i.v. of 100V.

These regulators, transformer and rectifier may be obtained from suppliers of R.S. Components products, including Chromasonic Electronics, 56 Fortis Green Road, London, N10 3HN or Celectron-E, P.O. Box No. 1, Llantwit Major, Glamorgan, CF6 9YN.

CA3055 VOLTAGE REGULATOR

This R.C.A. voltage regulator is designed to deliver up to 100mA over an adjustable output voltage range of 1.8 to 34 volts. A typical power supply circuit is shown in Fig. 12. Ripple might be less than 0.2mV at a


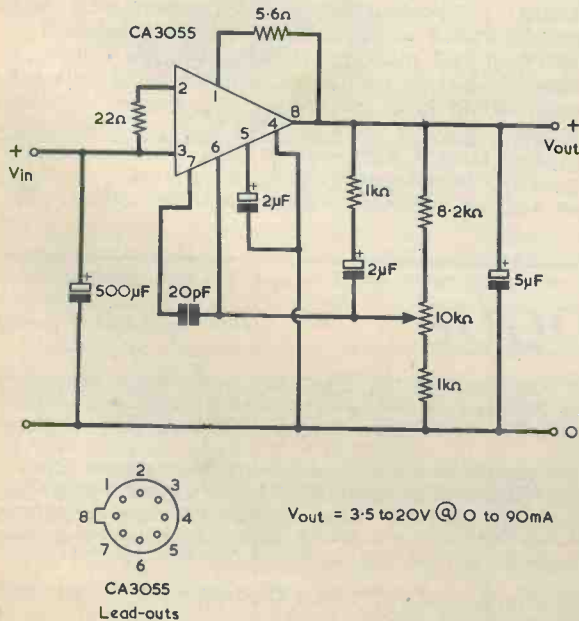


Fig. 12. A low current supply using the CA3055

APRIL 1973

90mA current load. The regulator has short-circuit protection, a temperature compensated reference voltage, and current limiting. The device can be used for high current regulation, switching regulation, shunt regulation, and positive or negative voltages. The CA3055 is available from A. Marshall and Son Ltd., 28 Cricklewood Broadway, London, NW2.

SG3501 DUAL VOLTAGE REGULATOR

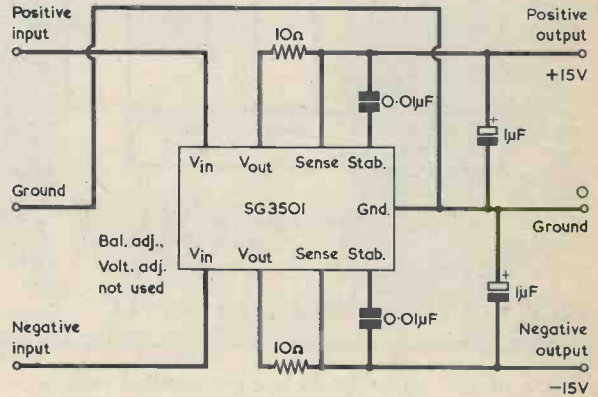

SG3501 Lead-outs

Top view

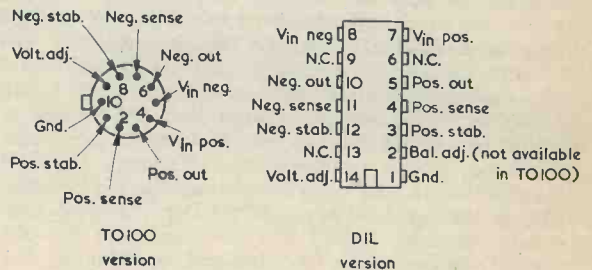


Fig. 13. A low current dual regulator using the SG3501

This is a dual polarity tracking regulator which provides balanced positive and negative output voltages at currents up to 100mA. It is internally set for ± 15 V but a single external adjustment allows both outputs to be varied simultaneously from 8 to 23 V. There is provision for adjustable current limiting and currents over 4 amps can be supplied if external power transistors are added. The minimum input to output differential is 2 volts. The maximum input voltage is 25 V. One circuit for a basic ± 15 V, 50mA regulator is shown in Fig. 13 with a high current (4 amps) version in Fig. 14. The two power transistors must be mounted on adequate heat sinks. The types employed may be selected on the basis of current and voltage capability, with low frequency devices preferred to minimise the risk of oscillation.

The SG3501 regulator can be obtained from Rastra Electronics Ltd. at the address given earlier.

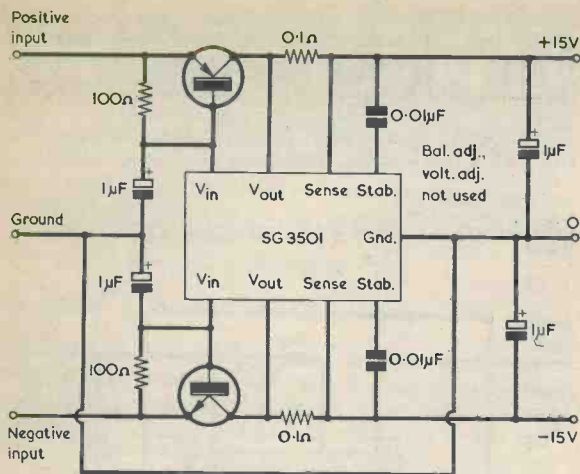


Fig. 14. A high current dual regulator using the SG3501

HIGH VOLTAGE REGULATED SUPPLY USING 741

One of the difficulties in using integrated circuits in high voltage regulated supplies is that the maximum device supply voltage is limited. This may be overcome by the outline arrangement shown in Fig. 15, designed around a $\mu A741$ (or one of its equivalents). Diodes D1, D2, D3 supply the amplifier with its correct operating voltages which are referenced to the output, so that output levels of 200V or more can be achieved. D1 maintains the amplifier positive supply terminal at 6V above the output voltage. D2 keeps the inverting input at 10V below the output voltage, and D3 maintains the required 30V across the amplifier supply terminals.

There is always more negative feedback through D2 (which has a low impedance) than there is positive feedback through the potential divider chain, so that the loop remains stable. The division ratio for the potential divider chain is obtained by making the chain's output 10V less than the regulator output voltage.

Short-circuit protection may be added as previously indicated although the series transistor dissipation

will be high under short-circuit conditions. In this application and in high current regulators where the series transistor dissipation is excessive under short circuit conditions it is possible to add fold-back current limiting. This reduces the current to a low value as the output voltage falls to zero, and hence avoids dissipation difficulties.

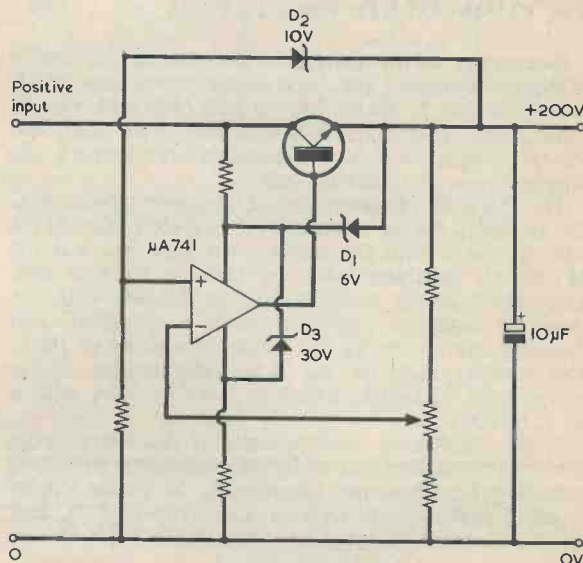


Fig. 15. A high voltage, low current supply using a $\mu A741$

CONCLUSION

We have seen how typical voltage regulator integrated circuits can be used on their own or with external components to provide a convenient and straightforward approach to power supply design. The high loop gain made possible by using an integrated circuit enables an overall performance to be achieved which would have meant the use of many discrete components a few years ago. We have not considered constant current regulators or high power switching regulators because such circuits have a rather limited use and are confined to specialised applications. ■

CATALOGUE

Currently available is the latest catalogue of Home Radio (Components) Ltd., 234-240 London Road, Mitcham, CR4 3HD. This is larger than previous Home Radio catalogues, its 250 pages, at $11\frac{1}{2}$ by $8\frac{1}{2}$ in., having a 25% greater area. It has a very attractive cover showing Dame Barbara Hepworth's famous sculpture 'Theme on Electronics', commissioned by Mullard Ltd., and reproduced by their kind permission.

The catalogue covers virtually every component likely to be required by the home-constructor and serious experimenter. No less than 6,785 components are listed, and there are 1,750 clear illustrations. The pages are attractively set up and easy to consult, and a browse through the catalogue can be both educational and productive of ideas for future projects. The components appear in general alphabetical order, but there is in any case a comprehensive index which enables any individual part to be located. An invaluable feature is the provision of Catalogue Numbers for the items, thereby eliminating ambiguities when ordering.

A noteworthy and up-to-date feature of the catalogue is the presentation of 'Theme On Electronics', by Barbara Hepworth, on its front cover.

Covering the gamut from aerial attenuators to zener diodes, this helpful catalogue is strongly recommended to anyone interested in the hobby of electronics. Details are given of methods of payment (including Credit Accounts) and of ordering. The catalogue costs 55p plus 20p post and packing, and includes ten free vouchers for 5p each.


New Products

COAXIAL RELAYS

After extensive life testing Hatfield Instruments announce a range of low-priced 2, 4, and 6-way single-pole relays to enable complex and remote switching functions to be realised in a compact and convenient form. Specification quotes a minimum life expectancy of 1,000,000 operations although prototypes have been tested to over 5,000,000 operations.

The relays have all internal contacts hard gold plated and are available for 12 or 24 volt use. For maximum isolation the unused ways are grounded though non-shorting and terminated types (50 OHM or 75 OHM) are also available. Further developments are in hand to extend the range up to a single-pole 12-way version.

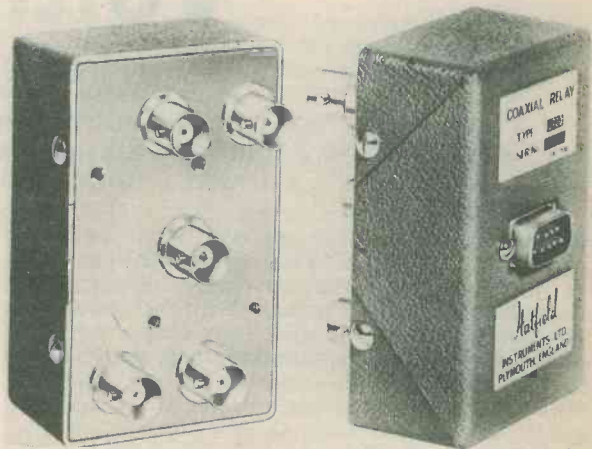Further details from: Hatfield Instruments Ltd., Burrington Way, Plymouth, Devon PL5 3LZ.



STEREO HEADPHONES FROM MARANTZ

Pyser Britex (Swift) Limited, the sole U.K. distributors for Marantz International audio equipment, have just introduced a new set of stereo headphones to complement the existing range of Marantz products now available in this country.

Designated Model S.D.I., the headphones, pictured here, are finished in 'Marantz Gold' spray with black leather ear cushions and headband. The yokes are fully adjustable and pivoted.

The new headphones, which are available from accredited Marantz stockists, come complete with a 10 ft. spiral lead and are expected to retail at £11.50. *Specification details* - Frequency Response: 20 .HZ-20 KHZ. Impedance: 8 OHM. Input: 1.0 watt per channel. Pyser Britex (Swift) Limited, 2nd Floor, Roussel House, North End Road, Wembley, Middlesex.

TV PORTABLE FROM ITT

A battery/mains portable television with a performance to match its good looks is ITT's first offering in 1973. It retails at £69.


The screen, housed in a pleasing matt black non-reflective surround, offers a bright, sharp picture using the latest 12" slim-line 110 degree tube.

The brushed aluminium fascia is fitted with sliding volume and brightness controls with calibrated scales and push-button Varicap selections of BBC1, BBC2 and ITV. There is also provision for fourth channel tuning. A separate on/off switch leaves all other controls unaltered in operation.

AFC, contrast and pre-set tuning controls are easily accessible at the back of the set, where the loop aerial connection and external aerial socket are also to be found. The long mains lead stores tidily away on moulded cleats.

The Featherlight Super 12 weighs just over 16 lbs and the special lead supplied allows the use of a 12v car battery or similar power source for location viewing. Use of the battery lead automatically disconnects the mains circuitry.

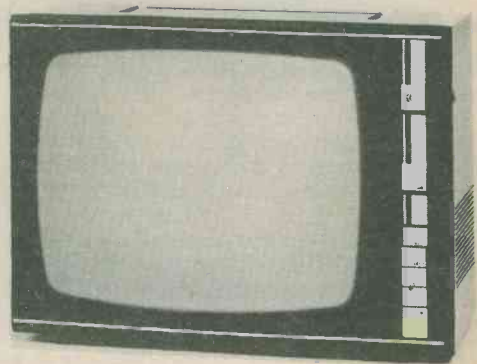ITT Consumer Products Ltd., Maidstone Road, Sidcup, Kent DA14 5HT.



High Resistance Voltmeter

by P. James

This easily constructed voltmeter offers three ranges up to 0-20V, and has the especially attractive feature of drawing a very small current from the circuit being checked.

DESPITE ITS SIMPLICITY, THE ELECTRONIC VOLTMETER described here offers a surprisingly good performance. Its main advantage is that its input resistance is exceptionally high. With the prototype it was found that there was little, if any, change in reading when a $10M\Omega$ resistor was inserted in series with one of the test leads.

The unit has three ranges, these being 0-5V, 0-10V and 0-20V.

THE CIRCUIT


The circuit of the voltmeter appears in the accompanying diagram, and it will be seen that it is powered by the two batteries B1 and B2. B1 offers 27 volts and consists in practice of three 9 volt batteries in series. All four batteries can be small types, such as the PP3 or PP4.

Two flexible leads terminated in test prods are connected to the test terminals. The voltage applied to the positive test terminal is coupled via R1 and D1 to the two transistors, TR1 and TR2. These are silicon n.p.n. transistors type BC107, and are connected together as a compound emitter follower offering a very

high level of current gain. The emitter of TR2 couples to meter M1 via whichever of the series resistors, R2 to R4 and VR1 to VR3, is selected by range switch S1. The variable resistors are adjusted such that the meter gives full-scale deflection when the emitter of TR2 is approximately 5 volts above the negative terminal of M1 on Range 1, approximately 10 volts on Range 2 and approximately 20 volts on Range 3. It is of advantage for the three sets of series resistance to be pre-set, as opposed to employing close tolerance components, since they may then be adjusted to take up varying performances in the transistors. The process of adjustment, which is described later, is very simple.

Because of the very high current gain offered by TR1 and TR2, the current drawn from the voltage source being checked is extremely low. Rectifier D1 is incorporated to ensure that high reverse base-emitter voltages cannot be applied to the transistors if the test prods should happen to be connected with incorrect polarity to a circuit being checked. A level of protection is also provided by R1 and C1. The base of TR1 is susceptible to a.c. and r.f. fields and, without R1 and C1 in circuit, there could be high meter readings if the positive test prod were touched by the finger. This effect

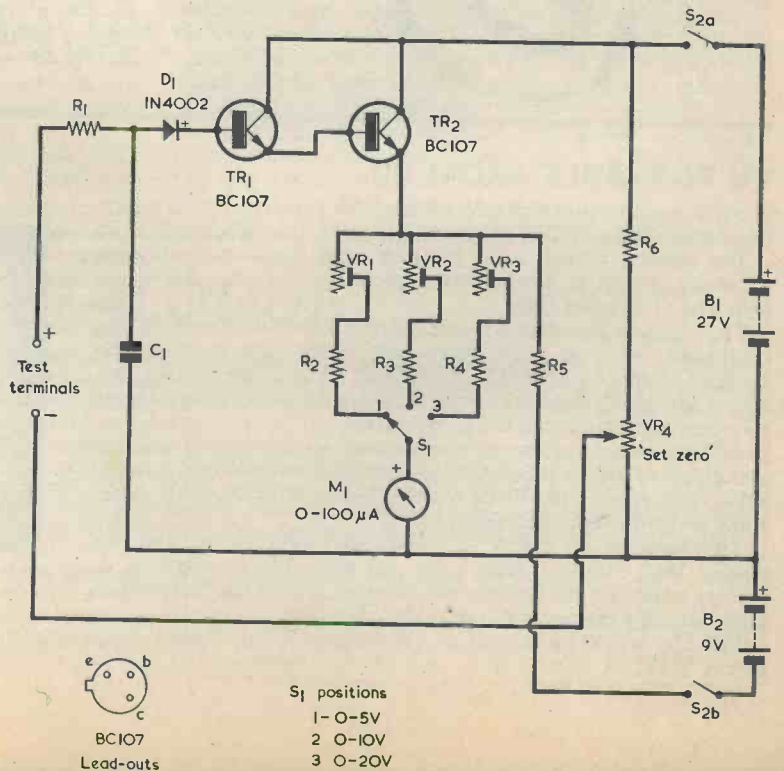The circuit of the high resistance voltmeter. This draws negligible current from the circuit whose voltage is being measured



clears when R1 and C1 are in circuit, although it may still be found that small random readings are given when the positive test prod is touched. These do not affect the accuracy of the instrument because the test prods should, of course, be held by their insulated sections when readings are being taken. R1 also provides current limiting.

When a reading is taken, the voltage at the junction of D1 and R1 is about 1.8 volts positive of that at the emitter of TR2. This is because there are three silicon junctions between these two points, each offering a drop of approximately 0.6 volts. It is necessary for the negative test terminal to be at the same potential as the positive terminal when there is zero voltage input, and this is achieved with the aid of VR4, which is set up for a zero reading in M1 with the two test prods short-circuited together. The setting of VR4 holds good for all three ranges, and the potentiometer only requires re-adjustment when battery voltage changes.

Resistor R5 and battery B2 ensure that TR1 and TR2 are still passing current when, with zero voltage input, the voltage at the emitter of TR2 is equal to that on the negative terminal of M1. There is a consequent improvement in linearity of readings at the lower voltages.

The current drawn from the 27 volt battery consists partly of that flowing through meter M1, which varies, according to the voltage being measured, from zero to 100µA, plus slightly more than 100µA passing through R6 and VR4. A current varying from about 40 to 140µA, according to the voltage being measured, is drawn from

both batteries via R5. These currents are so low that the working life of the batteries should not be much shorter than their shelf life.

CONSTRUCTION

The voltmeter should be assembled in a small insulated case. An insulated case is required because neither of the test terminals is connected directly to a low impedance part of the circuit and a metal case could cause complications so far as earthing is concerned. A case made of plywood would be quite adequate. S1, S2, VR4, the test terminals and the meter should be mounted on the front panel.

After the unit has been assembled the sliders of VR1, VR2 and VR3 should be set to the centres of their tracks and the voltmeter switched on by means of S2(a)(b). Next, the voltmeter is zeroed by connecting the two test prods together and adjusting VR4 for zero reading in M1.

The ranges can next be set up. This process is carried out with the aid of another voltmeter which is connected in parallel with the test terminals of the unit. If a source of continuously variable voltage is available, this may be adjusted to give an output of 5 volts, 10 volts and 20 volts respectively. VR1, VR2 and VR3 are then set up on Ranges 1, 2 and 3 for full-scale readings in M1. In the absence of a variable voltage supply, Range 1 may be set up by connecting both voltmeters to a 4.5 volt battery, Range 2 by connecting to a 9 volt battery and Range 3 by connecting to an 18 volt battery (two 9 volt batteries in series). In this case VR1, VR2 and VR3 are adjusted to give readings in M1 which correspond with those in the second voltmeter.

The results given by the circuit are due to the fact that the transistors specified have, in general, very low leakage currents. In practice, these are lower than the maximum leakage currents specified by the manufacturers and there is a slight risk that some BC107's may not give the same performance as in the author's instrument. The writer has, however, used a number of different BC107's in circuits of this nature and, in every case, these have exhibited the low leakage current exhibited here. Readers constructing the voltmeter must accept the slight possibility (outside the writer's experience) that some devices may exhibit a high leakage current, within specification, whereupon the input resistance of the voltmeter will not be as high as occurs with the prototype.

The input resistance may be checked by applying the voltmeter to a source of voltage on any range and noting the reading obtained. A 2MΩ resistor should then be inserted in series with the positive test lead and the voltmeter re-applied to the source of voltage. If there is no change, or negligible change, in voltage reading then the voltmeter can be assumed to have a satisfactorily high input resistance. With the author's model it was, as mentioned earlier, possible to insert a 10MΩ resistor with no significant change in reading. Naturally, it is necessary for C1 to have a high insulation resistance, and this capacitor should be a modern plastic foil component.

The voltmeter may give random readings when the test terminals are open-circuit. These are mainly due to the small amount of leakage current still existing in TR1, and they are not in evidence when the test prods are connected to the circuit whose voltage is to be measured.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

R1	220kΩ
R2	39kΩ
R3	75kΩ
R4	150kΩ
R5	220kΩ
R6	220kΩ
VR1	25kΩ pre-set potentiometer, skeleton
VR2	50kΩ pre-set potentiometer, skeleton
VR3	100kΩ pre-set potentiometer, skeleton
VR4	25kΩ potentiometer, linear

Capacitor

C1 0.02µF plastic foil

Semiconductors

TR1	BC107, Mullard
TR2	BC107, Mullard
D1	IN4002

Switches

S1	Single pole 3-way, rotary
S2(a)(b)	D.P.S.T., toggle

Batteries

B1	27 volt battery (three 9 volt in series)
B2	9 volt battery


Meter

M1 0-100µA meter

Miscellaneous


Test terminals	Battery connectors
Test leads and prods	2 pointer knobs
	Materials for case

TIN IN THE ELECTRONICS INDUSTRY

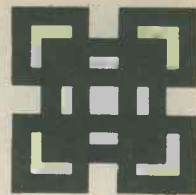


THE PRODUCTS OF THE ELECTRONICS INDUSTRY, BE they transistor radios, TV sets or communications apparatus or computers or a myriad other items of complex gadgetry, are now accepted as facts of modern living. The growth of the industry has been, and continues to be, phenomenal. Furthermore, with growth has come a spread in the range of products, which now embraces both low cost, mass-produced portable equipment and highly specialised and expensive communications and control systems.

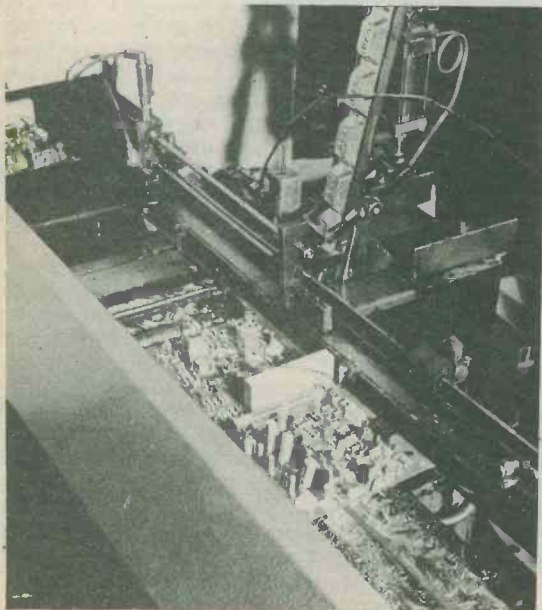One thing common to all types of apparatus is the use of tin or its alloys as an essential material of construction. The more important uses of tin in electronics are as solder alloys and for coatings. However, tin alloys or chemical compounds of tin contribute to many new and interesting devices.



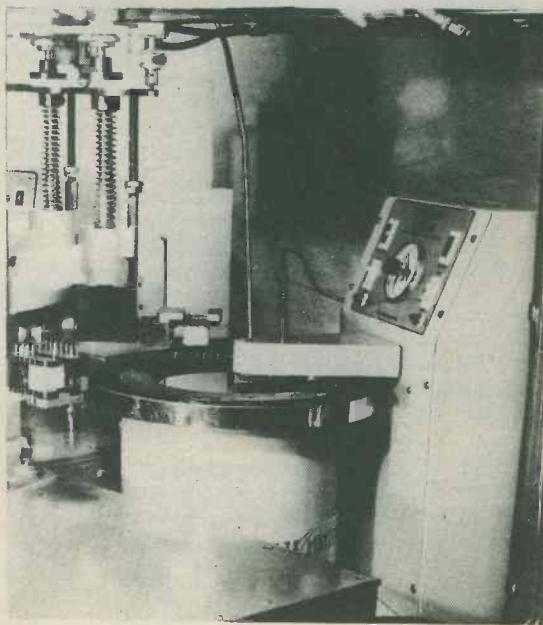Printed circuit assemblies being soldered on a wave soldering machine at a modern factory. Courtesy: British Radio Corporation, Enfield, Middlesex.



Part of the Soldip machine for mechanised soldering, showing the solder pot with movable arm for removing surface dross. Courtesy: Solbraze Ltd., Erith, Kent.

SOLDERING

Soldering with tin-rich, low-melting alloys provides the fastest and most reliable method of making electrical connections and the soldered joint is the essential basis of virtually every electronic circuit.

For specialised operations, a wide range of individual forms of solder alloys has become available within recent years. Pre-forms – small or miniature shapes made from solder and often with self-contained flux – can be produced to almost any specification and are particularly useful in certain applications, e.g. for soldering multi-layer printed circuit boards or for joining semiconductors.



Perfect solder joints in vertical wire terminations. Results such as this can be readily achieved with modern printed circuit mass soldering techniques. Courtesy: Tin Research Institute.

Solder alloys are also available in paste or cream form, which again usually incorporate a flux. These preparations find use in many mechanised soldering processes.

Automated production lines enable hundreds of electrical connections to be soldered within the space of a few seconds and the combination of printed circuit technology and mechanised soldering methods produces efficient and reliable results.

TIN AND ALLOY COATINGS

Reliability is further ensured by correct preparation of surfaces prior to soldering. Here again, coatings of tin or high-tin alloys are the best and most widely used means of retaining solderability in storage.

Modern developments in coating technology have led to a wide variety of coatings being available. Tin or tin-lead alloys may be electroplated as matte or as bright coatings and today the large-scale manufacturer may employ continuous plating production lines for the manufacture of printed circuits. For many applications hot dip or flow-melted coatings may be desirable. The low melting point and good alloying properties of tin and its alloys enable hot dip coatings to be readily applied to a variety of substrate metals.

LESSER-KNOWN USES OF TIN

Alloys of niobium and tin are in the class of materials known as superconductors, that is, at very low temperatures their electrical resistance falls to an infinitesimally small value. Such superconductors can be used to make high field magnets and a potentially important material of construction for high power electrical transmission cables. Experimental and prototype power systems are already in operation.

Tin-tellurium alloys have been developed for laser beam operated detectors for monitoring atmospheric pollution. In another sphere, tin oxide/glass combinations are widely used to make precision electrical resistors, whilst a small but interesting application for organotin compounds in electronics lies in the manufacture of liquid scintillators used as counting devices for radio isotope work. ■

The information in this article supplied by courtesy of the Tin Research Institute.

APRIL 1973

RADIO & ELECTRONICS CONSTRUCTOR

OUR NEXT ISSUE FEATURES

LOW-COST BURGLAR ALARM

Incorporating reliable techniques, this burglar alarm system offers a high level of protection to the flat dweller or householder.

THE 'HIFLEX' PERSONAL RECEIVER

Although this receiver employs only two transistors, reflex operation provides two stages of r.f. amplification before detection, together with a further two stages of a.f. amplification after detection.

MODIFICATIONS TO CYCLOPS

Part 2

ISOLATED TRIAC CONTROL CIRCUIT (Suggested Circuit 270)

The triac, sometimes referred to as a triode thyristor, is an interesting device which offers a number of useful applications. It has a trigger action and is capable of switching on an alternating current when a much smaller control current is fed to its gate. It can therefore be used in place of a relay, compared with which it has the advantages that switch-on and switch-off are virtually instantaneous and that there are no contacts or mechanical parts to wear out.

PLUS

MANY OTHER ARTICLES

PRICE 20p

ON SALE 1st MAY

ORDER YOUR COPY NOW

Copies may also be obtained direct from the Publishers, 26p. including postage. Published by Data Publications Ltd. 57 Maida Vale, London W9




CRYSTAL MICROPHONE

By R. A. F.

CRYSTAL MICROPHONES ARE VERY POPULAR AMONG amateur users, as they are generally inexpensive but nevertheless give a fairly high quality output. Unfortunately, they have the disadvantage that they are only really suitable for use with amplifiers which have a high input resistance if a wide frequency response is to be obtained.

HIGH IMPEDANCE

This high input resistance is required because of the series self-capacitance of the microphone, which may be of the order of 1,000 to 2,000pF. At a first approximation, a crystal microphone may be regarded as a voltage generator in series with this self-capacitance, as illustrated in Fig. 1. If the load resistor, which represents the input resistance of the amplifier to which the microphone connects, has a low value, then the reactance of the self-capacitance can become greater than this value at the lower audio frequencies. The result is that much of a low frequency voltage is developed across the series capacitance rather than across the load resistor, and low frequency voltages are not in consequence applied to the amplifier at their full amplitude. Thus, coupling a crystal microphone to an amplifier whose input resistance is too low results in a loss of bass response. Normally, a crystal microphone should couple to an input resistance of the order of $1M\Omega$ or more.

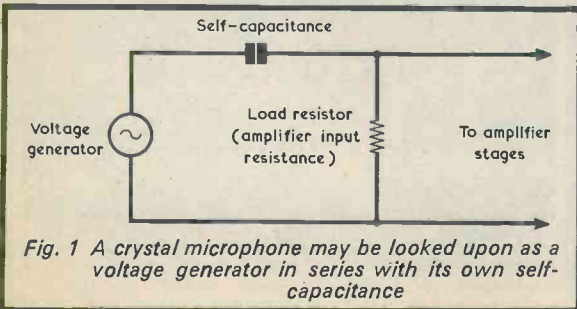

Cover Feature
-2

SELF-CONTAINED UNIT

The unit to be described here is completely self-contained and the parts are fitted in a case measuring only $3\frac{3}{8}$ by $1\frac{1}{2}$ by $1\frac{1}{2}$ in. It matches the high impedance of a crystal microphone into the low resistance input of a transistor power amplifier.

The complete circuit of the impedance matching pre-amplifier is given in Fig. 2. This uses a general purpose


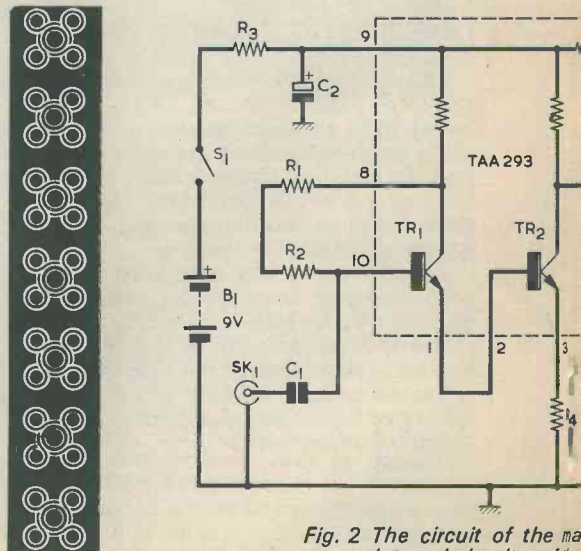


Fig. 2 The circuit of the impedance matching pre-amplifier and the internal circuitry of the transformer.


CRYSTAL PRE-AMPLIFIER

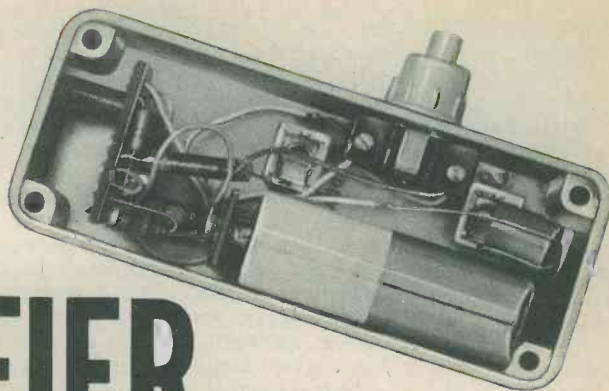

Penfold

Details of a simple integrated circuit pre-amplifier which enables the high impedance of a crystal microphone to be matched to the low input resistance of a transistor a.f. amplifier.

integrated circuit amplifier type TAA293 as a basic element, only a few external discrete components being required to complete the circuit. The i.c. type TAA293 is available from several suppliers, including G. W. Smith & Co. (Radio) Ltd., 11-12 Paddington Green, London, W.2. Since the output from a crystal microphone is relatively low, the pre-amplifier also provides a small amount of gain to boost the signal to a level high enough to drive most amplifiers.

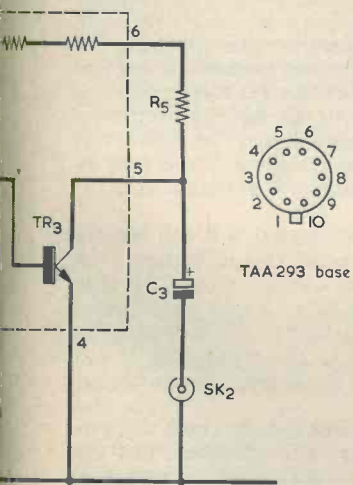

Matching pre-amplifier. The integrated circuit is inside broken line



COMPONENTS

Resistors

(All miniature $\frac{1}{4}$ or $\frac{1}{2}$ watt, 10%)

R1	8.2M Ω
R2	8.2M Ω
R3	3.3k Ω
R4	560 Ω
R5	3.3k Ω

Capacitors

(All miniature types)

C1	0.22 μ F.
C2	10 μ F electrolytic, 10 V.Wkg.
C3	10 μ F electrolytic, 10 V.Wkg.

Integrated Circuit

I.C. type TAA293

Switch

S1 s.p.s.t. switch (see text)

Battery

B1 9 volt battery type PP3 (Ever Ready)

Sockets

SK1	3.5mm. jack socket
SK2	3.5mm. jack socket

Miscellaneous

Verobard, 0.1in. matrix, 10 strips by 9 holes
Diecast box type 7969P (Eddystone)
Battery clips
Wire, etc.

The circuit of the unit is quite straightforward. The area inside the broken line in Fig. 2 represents the internal circuitry of the i.c., the discrete components being those outside this area. The input transistors (TR1 and TR2) are connected in a configuration similar to that of a Darlington pair, giving a very high current gain. The 560Ω resistor R4, in the emitter circuit of TR2, produces a large amount of voltage negative feedback which gives the circuit its very high input impedance. Resistors R1 and R2 bias the two input transistors. Due to their high values they have little shunting effect on the input impedance. Two resistors connected in series are used since a single resistor of sufficient resistance is not generally available.

TR3 is operated as a common emitter voltage amplifier, taking its bias current and input signal from the collector of TR2. The two internal resistors between terminals 6 and 9 together with the discrete 3.3kΩ resistor, R5, form the collector load for TR3. The output is taken from the collector of TR3 via C3. R3 reduces the 9 volt supply to a level of around 4 volts whilst C2 provides a bypass capacitance. C1 is the input coupling capacitor. The total current consumption is approximately 1.5mA only.

The maximum recommended supply voltage for the TAA293 in a circuit configuration such as that of Fig. 2 is 7 volts. As is explained later, the unit is initially checked with a 6 volt supply to ensure that wiring errors do not cause an excessive voltage to be applied. When this test is completed, the 9 volt supply is finally connected up.

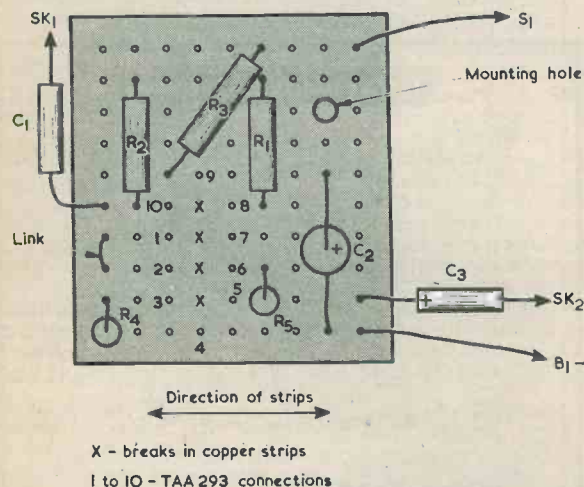


Fig. 3 Layout of parts on the Veroboard. This view is of the component side of the board, with the copper strips underneath

ASSEMBLY

Most of the components are mounted on a piece of 0.1in. matrix Veroboard having 10 copper strips by 9 holes. The layout of the board, as seen from the components side, is shown in Fig. 3. It is necessary to cut the board from a larger piece, and then cut the copper strips on the reverse side of the board as indicated. The board is then ready for the components to be mounted.

The link wire should be connected first as this is somewhat awkward to connect if left until the end, and is easily forgotten altogether.

To minimise the risk of damaging the i.c. due to

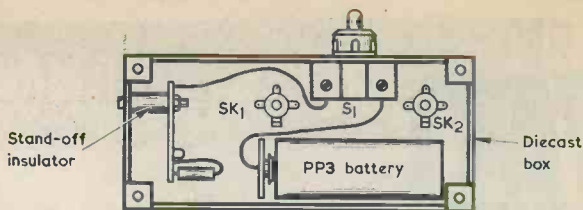


Fig. 4 The layout inside the diecast box

overheating, this should be the last component to be mounted. Great care must be taken when soldering it into circuit. Only one lead-out of capacitors C1 and C3 is connected to the board. The remaining lead-outs connect to the input and output jack sockets.

It is not necessary for the input and output wiring inside the metal case to be screened, as these are screened by the metal case. This arrangement has been found to be perfectly stable in practice. All external input and output connecting leads must of course be screened to prevent stray pick-up of mains hum, etc. The outer braiding of the external input and output screened leads connects to the metal case of the unit via the sleeves of the input and output jack plugs.

An Eddystone diecast box type 7969P is used to house the pre-amplifier. This box is available from Home Radio under Cat. No. E7969. The general layout inside the box is shown in Fig. 4. The on-off switch used with the prototype is a push-on type obtained from Woolworth's stores, but a miniature slide switch would be equally suitable although less easy to fit.

The component board is mounted by means of a 3/4in. 8BA bolt and nut. A stand-off insulator, cut from a piece of narrow-bore Paxolin tubing, or similar, is employed to space the copper strips on the underside of the board clear of the inside surface of the box. The earth connection to the diecast box is made at the tag of socket SK1 which couples to the jackplug sleeve. The dimensions of the box are such that the battery is held in place when the lid is screwed on.

CASE FINISH

The exterior finish of the case is rather rough and it will require cleaning. A Brillo pad is excellent for this purpose. The case may be painted, or it can be polished to give a very attractive finish, as was the prototype.

As a finishing touch, legends may be positioned alongside the input and output sockets. These may be obtained from Panel-Signs Set No. 3, available from the publishers of this journal.

When the unit has been completed, a 6 volt battery should be temporarily connected to the battery clips and the unit switched on. The voltage across C2 is then measured. If this is of the order of 2 to 3 volts then it may be assumed that the integrated circuit is drawing an adequate current through R3. The temporary 6 volt supply is then removed and the correct 9 volt battery connected up.

Finally, should there be instability when the pre-amplifier is connected to the main amplifier, this will probably be due to the wide bandwidth of the integrated circuit. The cure is to connect a low-value capacitor of 100 to 1,000pF between leads 3 and 5 of the integrated circuit. This capacitor must be a miniature type as there is very little space to accommodate it inside the case. ■

RECENT PUBLICATIONS



TRANSISTORIZED RADIO CONTROL FOR MODELS. By D. W. Aldridge.
164 pages, 5½ x 8½ in. Published by W. Foulsham & Co., Ltd. Price £2.50.

This book is intended for the constructor who prefers to assemble his own radio control equipment rather than purchase it ready made. As the author rightly points out, there is more pleasure to be obtained from operating home-built gear than in using commercially available 'black boxes'. The systems described in *Transistorized Radio Control for Models* are mainly intended for model boat control and, as such, do not have to be extremely small in size or light in weight. The basic principles are still, of course, capable of miniaturisation. The major types of model control up to, but not including, the more advanced levels of multi-proportional control are covered. The author considers that advanced multi-proportional control, with its attendant complicated test equipment, is best left to specialist manufacturers.

The book commences by giving a general explanation of radio control systems, then carries on to steering systems, receivers and transmitters. The construction of a wavemeter, transmitter and superhet receiver are next dealt with, after which steering systems employing mark-space control, simple proportional and progressive techniques are described. Included in the remainder of the book are chapters describing a four channel pulse system, the tuned reed system, tuned chokes and a proportional circuit which permits the use of tone controls for secondary channels and which was specially devised by the author.

The book is written in down-to-earth style by a model enthusiast for other enthusiasts, and offers sensible advice which can be followed by anyone who can wield a soldering iron and has sufficient knowledge of electricity and electronics to understand the principles involved in simple radio control systems.



TELEVISION INTERFERENCE MANUAL. By B. Priestley, G3JGO.

100 pages, 148 x 210mm. (5½ x 8¼ in.) with spiral binding. Published by Radio Society of Great Britain. Price 80p.

The amateur transmitting enthusiast who lives in a crowded urban area has many difficulties, not least of which is that of TV interference. Anyone who has had experience with transmitter operation can readily visualise the situation in which breakthrough occurs on a nearby receiver which has, to all intents and purposes, an otherwise impeccable performance. Apart from input overloading by the transmitted signal, any non-linear item including even a corroded solder joint in the receiver or its aerial system can result in cross-modulation and consequent breakthrough. Interference may also, of course, be caused by out-of-band spurious radiations from the transmitter.

The problems of the amateur are further increased by the social difficulties arising from TV interference. The owner of a £300 colour set is not likely to respond kindly to the suggestion that it may be his receiver which is at fault and not the transmitter. Even if the transmitter is blameless, a layman can hardly be expected to accept this fact if, so far as he can see, his set is obviously working correctly when the transmitter is off the air.

Television Interference Manual sets out to advise the amateur on ways of preventing TV interference, dealing with the subject both from the engineering and the social points of view. Much of the book is devoted to methods of producing a clean transmission and it is pointed out that this must be achieved before attempting to solve the problem at the receiver. Also included is a chapter on breakthrough in hi-fi systems, and one of the appendices gives details on Post Office interference investigation methods.

The author is a specialist in the field of TVI, and the book will be a valuable addition to the library of the amateur transmitter. It can, if desired, be obtained by mail order direct from RSGB Publications, 35 Doughty Street, London, WC1N 2AE, in which case the post paid price is 90p.



ABC'S OF INDUSTRIAL ELECTRONICS. By J. A. Wilson.

102 pages, 135 x 215mm. (5¼ x 8½ in.). Published by W. Foulsham & Co. Ltd. Price £1.50.

This work is in the Foulsham-Sams Technical Book series, and consists of an American text with an introductory chapter for English readers. It deals with the electronic systems which are encountered in industry and in manufacturing processes.

The first chapter of the book discusses the transducers used in industrial electronics systems, switching components and the types of amplifiers employed; and this is followed by two chapters devoted to power supplies and amplifier control systems. The fourth chapter gives an introduction to counting systems and logic circuits, this being succeeded by a chapter which discusses the logic circuits employed in industrial control. The final chapter deals with numerical control systems.

The book covers a very wide range, from fluidics to t.t.l. circuits, and probably because of this does not discuss any particular subject in great depth. It offers a useful introduction to the techniques used in industrial control systems and enables the basic principles of these techniques to be understood.



THE 'HYBRIDYNE' MEDIUM WAVE PORTABLE RECEIVER

by

Sir Douglas Hall, K.C.M.G., M.A. (Oxon)

Despite the fact that this medium wave portable employs a t.r.f. circuit it provides comprehensive automatic gain control. Incorporated in the receiver are three transistors and one DL96 valve.

SOME, IF ASKED TO NAME THREE circuit devices which they considered to be obsolescent, might mention the valve, the frame aerial, and the use of reaction. The author's comment would be that despite the obvious advantages of the transistor, the valve is still superior in some respects; that a frame aerial with, say 10 in. sides, though bulky, can be very much more sensitive than any normal ferrite rod; and that no-one seems to think that Q multiplication circuits are old-fashioned, though Q multiplication is only a modern name for reaction.

The useful combination of the very high thermal stability of the valve and the high mutual conductance of the transistor has been used to obtain amplified a.g.c. in three previous designs, these being two car radios and a mains transportable.* The present design makes use of the same basic principles in a battery operated design, but an important new feature is incorporated by means of which the a.g.c. loop now includes a reaction circuit. Previously, although reaction was used, this was unaffected by the a.g.c. circuit. The result with the new circuit is not only amplified a.g.c. but a circuit which changes an inherently unstable condition to sensitive stability

*Sir Douglas Hall, 'Design of Universal Car Radio', *The Radio Constructor*, April 1969; 'The "Droitwich" Car Radio', *The Radio Constructor*, November 1971; 'Hybrid Transportable Receiver', *The Radio Constructor*, November 1969.

as soon as a station of reasonable signal strength is tuned in. In other words, the receiver may be set to an oscillating condition and then any fairly powerful signals can be tuned in without touching the reaction control except, perhaps, between widely separated parts of the tuning scale. Weak stations can still be brought in by critical reaction adjustment in the usual way. It may be found that with a really powerful local station, oscillation can not be produced even with reaction set to maximum.

THE CIRCUIT

The circuit is shown in Fig. 1. L2 is a medium wave frame aerial with a 10 in. side, and the signal is applied from the tuned circuit given by L2 and VC3 to the base of TR1, a high amplification p.n.p. transistor connected as a common emitter amplifier. A suitable tapping is taken from L2 for the base of TR1, and in addition C2, which is bypassed by R1 for d.c., provides a further capacitive tap. It is permissible, though not really necessary to experiment with the value of C2. If it is too large there will be a lack of selectivity and 'rough' control of reaction. If too small there will be loss of sensitivity. L1, with VC1 and VC2 in parallel, offers a high impedance collector load for TR1 which will accordingly give large voltage amplification. VC2 and VC3 are the two sections of a 2-gang tuning capacitor. VC1 is a trimmer across the tuned circuit which has the lower stray capacitances. L1, it should be mentioned, is a Denco miniature

dual-purpose valve-usage aerial input coil. Only its tuned winding is in circuit and its coupling winding is ignored.

The amplified signal at the collector of TR1 is then applied to V1. Because of C5 and R4, and the small positive bias at the grid, V1 acts as a leaky-grid detector. The grid is about 1.5V positive of the negative rail because of the silicon diodes D2 and D3, and this bias is held constant notwithstanding the condition of the battery. Similarly, the screen-grid potential is held steady at about 6V positive because of the zener diode D1, in conjunction with D2 and D3. Anode voltage will fall with an ageing battery but a characteristic of the pentode valve is its high output impedance, as a consequence of which anode current remains steady despite falling anode potential. This is provided, of course, that signal grid potential and screen-grid potential remain constant.

The two diodes, D2 and D3, can be any silicon diodes or small silicon rectifiers, such as the 1N4002.

R6 acts as an r.f. load and allows reaction to be applied to the base of TR1 via C7 and VR2. Note that reaction is given over both stages. The phase at the anode of V1 is the same as that at the base of TR1, so no coupling coil is necessary and the base tap can be employed.

The reaction control VR2, has a log track and is connected so that reaction increases as it is turned anti-clockwise. This provides very smooth control.

L3 is the large winding of a microphone or crystal pickup transformer.

RADIO & ELECTRONICS CONSTRUCTOR

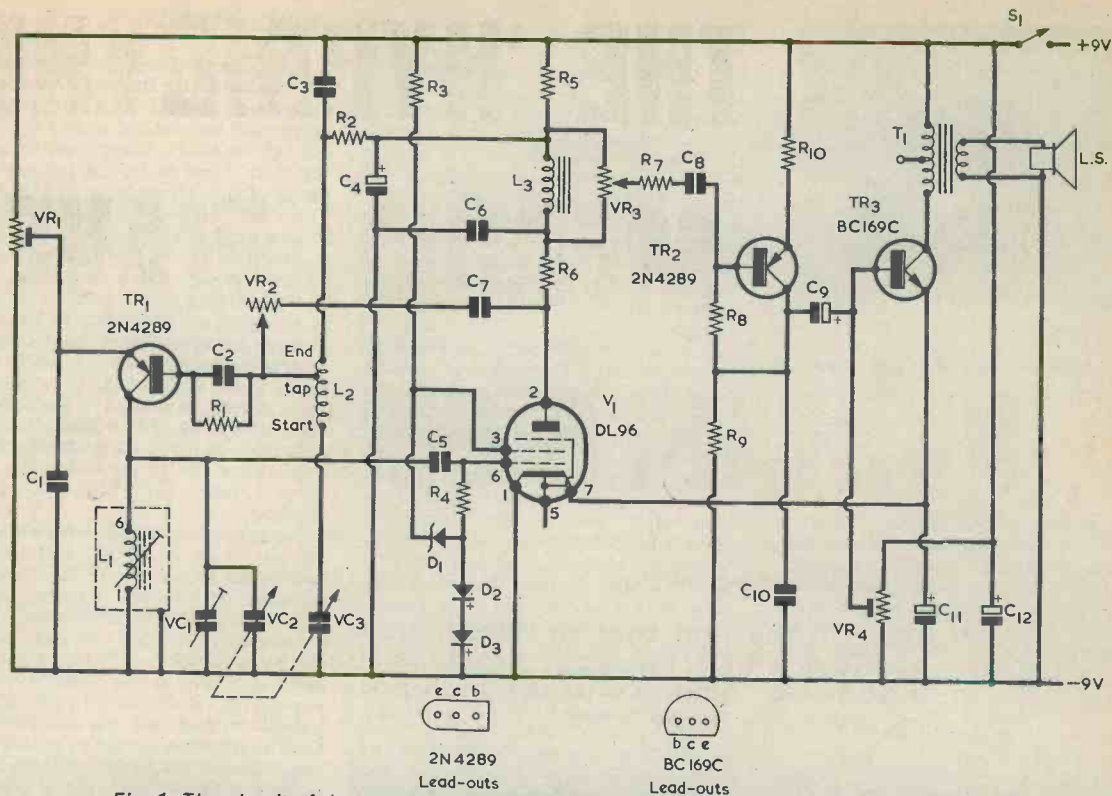


Fig. 1. The circuit of the medium wave portable receiver. The inductor L2 is a frame aerial

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R1	10k Ω
R2	10k Ω
R3	1.5k Ω
R4	3.9M Ω
R5	18k Ω
R6	3.3k Ω
R7	47k Ω
R8	2.2M Ω
R9	1k Ω
R10	1k Ω
VR1	25k Ω pre-set potentiometer, skeleton
VR2	500k Ω potentiometer, log track
VR3	1M Ω potentiometer, log track, with S1
VR4	25k Ω pre-set potentiometer, skeleton

Capacitors

C1	0.1 μ F paper or plastic foil
C2	100pF silvered mica or ceramic
C3	0.1 μ F paper or plastic foil
C4	1 μ F electrolytic, 10 V. Wkg.
C5	180pF silvered mica or ceramic
C6	1,000pF silvered mica or ceramic
C7	180pF silvered mica or ceramic
C8	0.1 μ F paper or plastic foil
C9	8 μ F electrolytic, 4 V. Wkg.
C10	0.22 μ F paper or plastic foil
C11	400 μ F electrolytic, 4 V. Wkg.
C12	1,000 μ F electrolytic, 10 V. Wkg.
VC1	40pF trimmer, mica
VC2-3	365 + 365pF 2-gang variable capacitor type 0 (Jackson Bros)

Inductors

L1	Denco Miniature Dual Purpose coil, valve usage, Blue, Range 2
L2	Frame aerial, see text

L3	Microphone transformer (only primary used) type TT53 (Repenco)
T1	Output transformer type T/T7 (R.S. Components)

Semiconductors

TR1	2N4289
TR2	2N4289
TR3	BC169C
D1	Zener diode, 4.7V 200-250mW
D2	Silicon diode
D3	Silicon diode

Valve

V1	DL96
----	------

Switch

S1	S.P.S.T. (part of VR3)
----	------------------------

Speaker


3 Ω speaker, 8 in. by 5 in.

Batteries

2-off 4.5 volt batteries type 126 (Ever Ready)

Miscellaneous

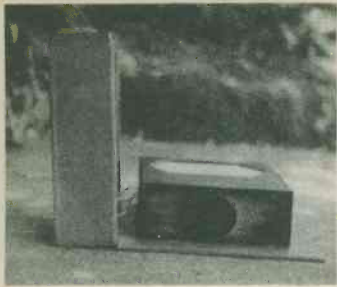18-way R.S. Components standard size groupboard (Home Radio Cat. No. BTS10)
 Epicyclic drive type 4511 (Jackson Bros)
 Clip for coil can
 32 s.w.g. enamelled wire
 B7G Valveholder
 Plywood
 Hardboard
 Fablon or Contact
 Speaker fabric
 Nuts, bolts, etc.



The receiver is operated with the case opened and the frame aerial vertical

(No connections are made to the other winding.) With the small current passing through L3 it offers an inductance of the order of 200H. This enables V1 to give good voltage amplification notwithstanding the very low direct voltages available for its screen-grid and anode. R5 is a decoupling resistor used in conjunction with C4. Because of V1's function as a leaky-grid detector, the current passed by the valve will drop with the receipt of a signal and, consequently, the voltage drop across R5 will fall. R5 is connected via decoupling components R2 and C3 back to the base of TR1 which thereby receives bias which varies according to the amplitude of the signal being received. The pre-set potentiometer VR1 is adjusted so that, with no signal being detected by V1, a collector current of 150 μ A passes through TR1. A potentiometer is used here rather than a simple series resistor in the emitter circuit since it helps to reduce variations in the emitter potential for changes in the base voltage. A series resistor would give d.c. negative feedback and would reduce the effect of the a.g.c. In practice, even a small signal detected by V1 will cause sufficient change in TR1 bias to result in a significant drop in collector current. A large signal will almost cut TR1 off. Not only does good a.g.c. result but the effect of the reaction is also automatically varied, and this helps additionally in keeping the signal strength steady.

An audio signal appears across L3. VR3 acts as a volume control, and the signal from its slider is fed through the stopper resistor R7 and the capacitor C8 to TR2. TR2 is a p.n.p. common emitter amplifier with 100% voltage feedback at the emitter, and it matches the high output impedance of V1 to the much lower input impedance of the output transistor TR3. This arrangement is used in preference to an emitter follower as the presence of a resistor in the collector lead enables a simple form of negative feedback of d.c. to be used in providing base bias through R8. Also, a p.n.p. device is

used rather than n.p.n. as the latter would mean that the surge through C9, on switching on, could cause a large current to flow momentarily through TR3. As will be explained later, it is this current which also flows through the filament of V1 which could consequently be damaged. In theory, TR2 can be dispensed with, the secondary of the microphone transformer being used to provide correct matching for TR3. But this involves a drop of 25 times in voltage gain which cannot conveniently be tolerated. TR2, though offering no voltage amplification in itself, yet prevents a fall of amplification by 25 times from taking place. To all intents and purposes the stage may therefore be credited with an effective gain in the present circuit of 25 times.

TR3 is straightforward common emitter output transistor with base bias set by VR4 so that it passes a current of 25mA. The filament of V1 is used as an emitter resistor for TR3 so that the normal drawback encountered with the use of a battery valve - the need for a separate filament battery - is avoided. The voltage across the filament can drop appreciably, with an ageing battery, without the anode current of V1 being affected.

The output transformer chosen gives exactly the right ratio for maximum undistorted output for the conditions prevailing, but the Repanco TT56 is a near-equivalent and could be used instead, if desired. The R.S. Components transformer specified may be obtained from Chromasonic Electronics, 56 Fortis Green Road, London, N10 3HN.

FRAME AERIAL

It is suggested that the frame aerial be made first. Its construction is illustrated in Fig. 2. Two pieces of hardboard are cut out as in Fig. 2 (a), a small hack-saw being used to make the slots. Next to be cut out are two pieces of $\frac{1}{4}$ in. plywood, as in Fig. 2 (b). These are screwed or pinned together to take up the form shown in Fig. 2 (c). A length of 32 s.w.g. enamelled wire is passed through the hole for the start of the winding and is held in position by wedging a match-stick in the hole. 21 turns are wound on, either clockwise or anti-clockwise, with 3 turns to each set of slots. The end of the winding is then passed through the appropriate hole, and is locked in position there. A tapping is made by soldering about 8 in. of fine flex to the end of the 18th turn, 3 turns from the end of the winding.

Next, two pieces of $\frac{1}{4}$ in plywood are cut out 11 in. by $3\frac{1}{2}$ in., and another two pieces 10 $\frac{1}{2}$ in. by $3\frac{1}{2}$ in. These are screwed or pinned together as in Fig. 3 (a) and a hardboard back measuring 11 in. by 11 in. pinned into place behind them. The frame aerial is fitted centrally in this assembly, as in Fig. 3 (a), and secured with screws passed through the hardboard back. Only two screws should be used at this stage in case the aerial winding needs to be modified. Next, cut a piece of hardboard to the dimensions shown in Fig. 3 (b) and fit two small hinges to it, as illustrated. Screw the hardboard frame to the front of the assembly of Fig. 3 (a), again using only two screws at this stage.


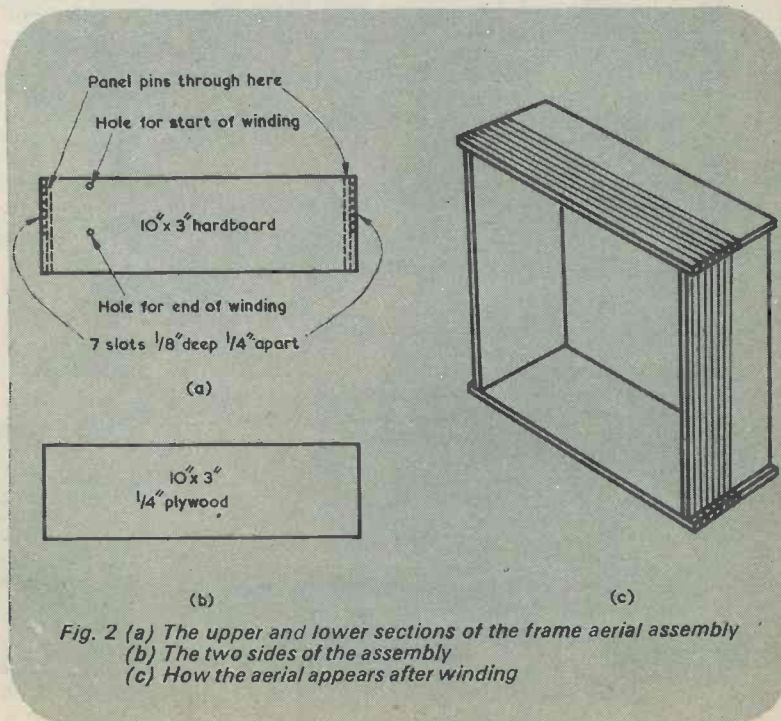


Fig. 2 (a) The upper and lower sections of the frame aerial assembly
(b) The two sides of the assembly
(c) How the aerial appears after winding

Fig. 3 (a) The aerial is fitted inside an 11 by 11 in. frame
 (b) Front cover for the assembly of (a)

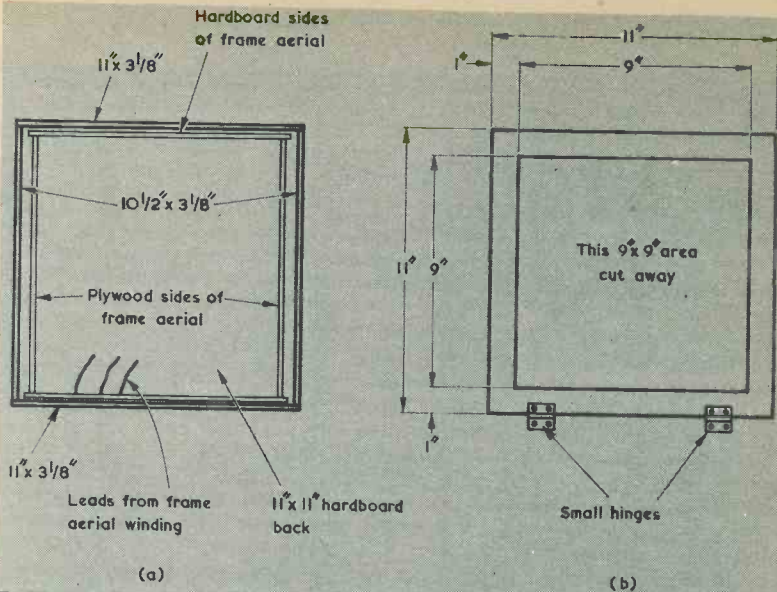

RECEIVER ASSEMBLY

Next turn to Fig. 4 (a). Cut two pieces of plywood and two pieces of hardboard as shown and screw or pin them together to make a 4-sided frame without top or bottom. The bottoms of the pieces are all at the same level so that, at the top, sides B and C project higher than sides A and D by $\frac{1}{8}$ in. The hardboard control panel shown in Fig. 4 (d) will later be positioned behind side A, and this side has a cut-out to allow access to the controls. The shape of the cut-out is evident from Fig. 4 (a) and the photograph showing the controls.

Cut a piece of plywood 11 in. by 11 in. Cover this with Fablon or Contact. Similarly cover the frame of Fig. 4 (a) with Fablon or Contact. Do not cover the frame aerial assembly at this stage. Temporarily attach the hinges, already screwed to the frame aerial assembly, to the 11 in. square plywood, as shown. It is now necessary to screw the frame of Fig. 4 (a) to the 11 in. square section, so as to take up the position shown in Fig. 4 (b). This must be done so that the 11 in. square section, acting as a lid, can be closed onto the frame aerial assembly, with the 4-sided frame of Fig. 4 (a) settling neatly inside with room available for knobs protruding slightly at side A. This means that the frame of Fig. 4 (a) must be fixed to the lid slightly off centre, as shown in Fig. 4 (b). Side D comes close up against the inside of the frame aerial assembly when the lid is closed. One way to achieve the correct position is to apply transparent plastic cement to the bottom edges of the Fig. 4 (a) assembly, and allow this to become tacky. Then the assembly can be held lightly, but free to be moved slightly as may prove necessary, until it is ascertained that the lid can be closed correctly. When the correct position has been found the cement

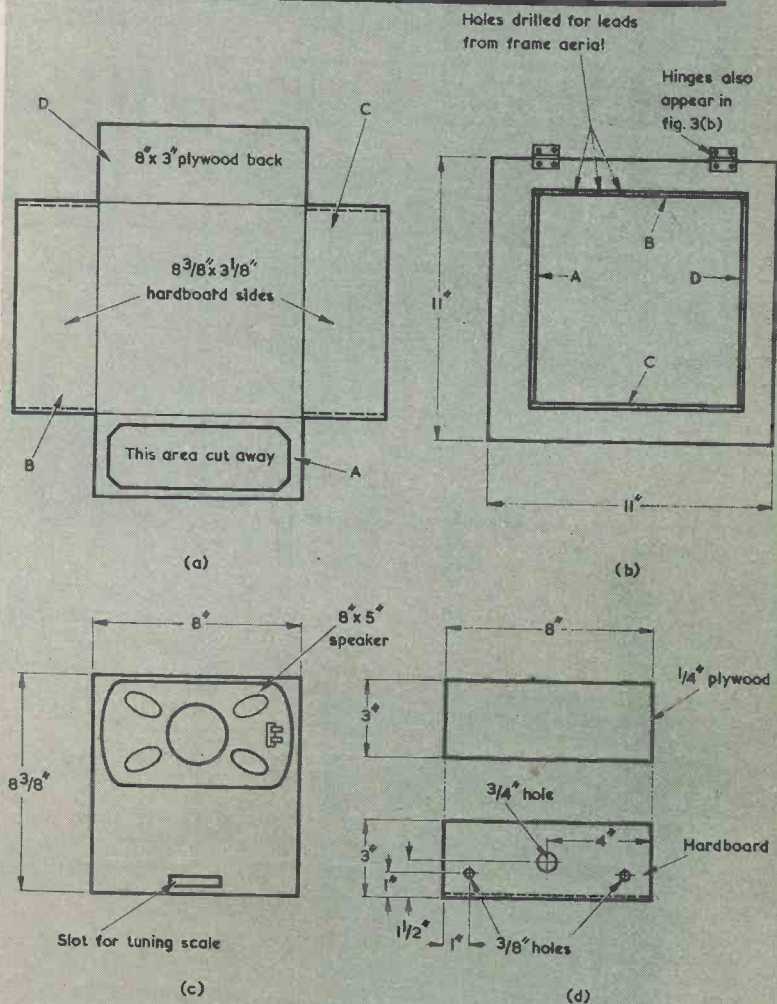


Fig. 4 (a) The four sides of the receiver chassis housing
 (b) Fitting the housing to the receiver lid
 (c) The top panel, on which the speaker is mounted
 (d) The receiver "chassis" comprises a plywood baseboard and a hardboard control panel

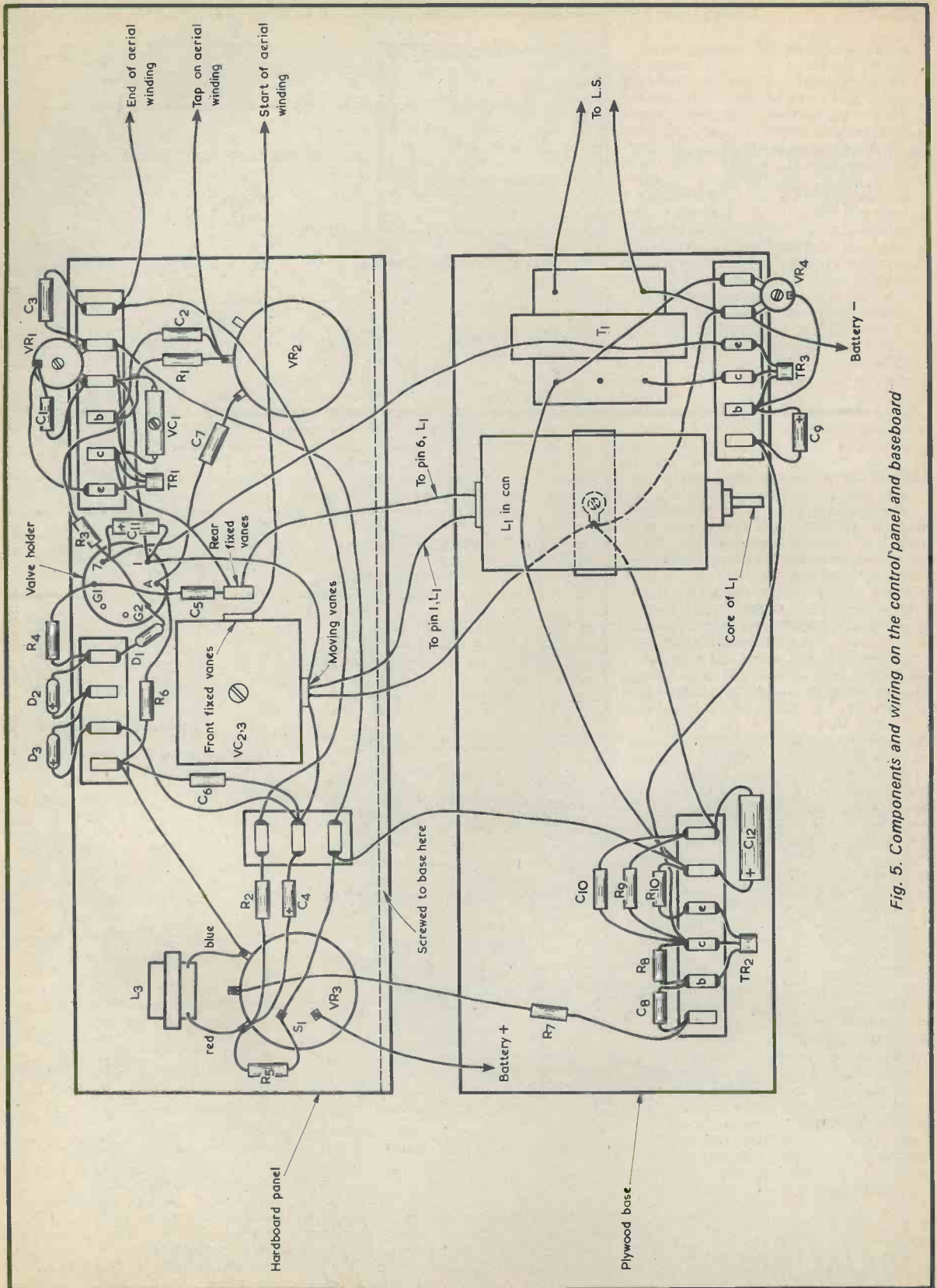


Fig. 5. Components and wiring on the control panel and baseboard

can be left to dry and then small screws can be passed through the lid into the Fig. 4 (a) assembly to give extra strength.

Next cut a piece of hardboard as in Fig. 4 (c). Cut out a suitable aperture for the 8 in. by 5in. speaker, which may be mounted over a piece of gauze. At this stage do not cut out the slot for the tuning scale and do not cover with Fablon or Contact.

Cut and drill a piece of hardboard as in Fig. 4 (d) and also cut a piece of plywood as shown. These will form the panel and baseboard respectively for the receiver 'chassis'.

Mount components as shown in Fig. 5. The tuning capacitor, VC2-3, is mounted on a small plywood sub-panel, as indicated in Fig. 6, this being held away from the main panel by two 1½ in. 4BA bolts fitted with 3 nuts each. The epicyclic ball drive is mounted on the inside of the main panel at its exact centre, where the ¾ in. hole has been cut out. The end of the tuning capacitor spindle is fitted inside the ball drive and the nuts on the 4BA bolts adjusted and tightened so that the whole assembly is held solid.

L1 is fixed by means of its plastic nut through a hole drilled in the centre of the can in which the coil is supplied. A second hole is drilled through the centre of the bottom of the can, and two different coloured leads, soldered to pins 1 and 6 respectively of the coil, pass through this hole. A rubber grommet should be fitted at the hole. The lid is then screwed onto the can and the whole is held in a clip which is screwed to the baseboard, with a solder tag acting as a washer for the screw. The two transformers, L3 and T1, may be cemented into position, or tin plate clamps may be made with feet and holes for screws. It will be seen that there are 5 sets of tagstrips, three of them 6-way, one 4-way and one 3-way. These are all cut from an R.S. Components standard size 18-way tag board. The tag strips on the panel are fixed with 8BA countersunk bolts and nuts. Countersunk wood screws are used to fix the tag strips to the plywood base.

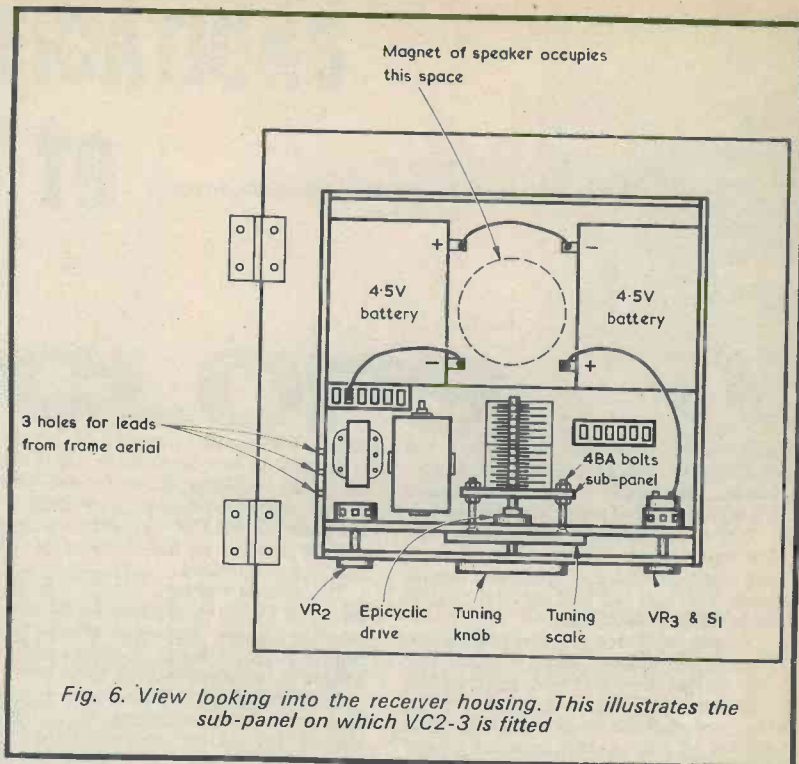


Fig. 6. View looking into the receiver housing. This illustrates the sub-panel on which VC2-3 is fitted

In Fig. 5 the valveholder is shown turned through 90° for clarity. In fact it is fitted with a bracket and held so that pins 1 and 7 are furthest from the panel, and the valve lies over the tag strip on which TR1 is mounted. The bracket should be high enough to allow good clearance for components mounted on this tag strip.

All wiring with the exception of the connections to the frame aerial and speaker and the wires between the panel and the baseboard of Fig. 5 should now be carried out. The panel may then be screwed to the baseboard and the connecting leads between them soldered in. These look long in Fig. 5 but are, in fact, quite short when the two parts have been secured together.


The lead from L1 to the frame of VC2-3 should be connected temporarily only at this stage, as the connection is opened later during the setting up operation.

Now, cover the front panel of the chassis with Fablon or Contact, then cut a plywood wheel, 2½ in. in diameter, and with a ½ in. hole at its centre. Fix with adhesive a ¼ in. wide strip of white cardboard round its periphery. This functions as a tuning scale. Push-fit this wheel over the slow-moving wider section of the ball drive, if necessary winding on a turn or two of Sellotape to make a tight fit. Place the complete chassis assembly in the box, as in Fig. 6, leaving just enough space between the front of the panel

The inside of the receiver housing with the speaker panel removed



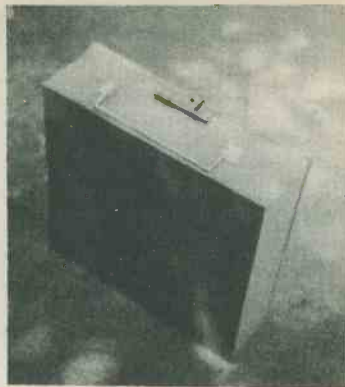When the case is closed the receiver can be easily carried around



and the inside of side A to allow the tuning scale wheel to turn freely. Secure the chassis to the 11 in. square lid with the aid of small wood screws.

Place the speaker panel over the box containing the chassis and mark the position of the slot for the tuning scale. Cut this out and cover the panel with Fablon or Contact.

Attach, anchoring in any convenient manner, lengths of about 8 in. of fine flex to the start and end leads of the frame aerial. Pass these, and the tap lead, through the three holes in the box shown in Fig. 6 and connect to the appropriate points on the chassis as indicated in Fig. 5. Connect up the two batteries as shown, and connect the speaker, using leads which are long enough to enable the speaker panel to be placed clear of the box when setting up and, later, when changing batteries.

Fit the knobs. These should be shallow types or they will foul the inside of the frame aerial assembly when the case is closed.

SETTING UP

Adjust VR1 fully clockwise with its slider up against the track end connected to C3, and VR4 with its slider up against the track end connected to battery negative. This is also fully clockwise as shown in Fig. 5. Set the core of L1 with about $\frac{1}{4}$ in. protruding and have VC1 at minimum capacitance. Turn VR2 and VR3 fully clockwise.

The receiver is at its best on the floor or ground. This brings out the bass nicely. So place it on the ground for setting up. Clip a voltmeter across pins 1 and 7 of the valveholder with negative at pin 1, switch on and

adjust VR4 until a reading of 3 volts is given *with new batteries in use*. Take care not to allow the slider of VR4 to pass too high a positive voltage to the base of TR3 or excessive voltage will be applied to the filament of V1 and it may burn out.

Disconnect the lead from L1 to the frame of VC2-3 and connect a current-reading meter between these two points. Adjust VR1 to give a reading of 150 μ A. Reconnect the lead to VC2-3.

Now find a station near 200 metres and peak it by adjusting VC1. VR2 should be turned anti-clockwise to increase sensitivity. Then find a station around 450 metres and peak it by adjusting to core of L1. Repeat this operation two or three times to find the best compromise settings. If the core of L1 is too far out, or VC1 is at too low a capacitance, there may be instability. There will be no uncontrollable instability when the circuits are correctly trimmed, but as trimming becomes more accurate it will be found necessary to turn VR2 further clockwise to prevent oscillation. If it appears that with the core of L1 fully into the coil the latter still does not have sufficient inductance for correct tracking, remove one turn from the start end of the frame aerial. If the core cannot be screwed far enough out, add one turn. Neither of these modifications are at all likely to prove necessary. When listening to a fading station reaction should be adjusted to the critical point during a trough in the signal. If it is so adjusted during a peak, there will be oscillation during troughs.

As soon as trimming has been satisfactorily carried out the frame aerial assembly can be properly

screwed together and covered with Fablon or Contact. The inside of this assembly should be lined with thin cardboard panels covered with Fablon or Contact. This material will also hold the leads from the aerial firmly to the inside of the frame.

The scale on the wheel can be calibrated and the case fitted with a handle together with a catch to keep the lid shut during transit. It is obvious that the receiver must be open in use and that the lid is then horizontal. In fact it then becomes a base, with the frame assembly standing up and being orientated according to the position of the station. The unencumbered frame aerial provides good pickup and a very clear, hiss-free signal. The total current consumption of the receiver is 27 to 28mA from the 9 volt battery.

A large number of stations on wavelengths between 190 and 600 metres will be received, at good quality and volume. This new circuit is very free from vices. The only characteristic of the receiver which could possibly be so defined is a tendency for hand-capacitance effects on weak stations around 200 metres. These effects can be reduced by using a large diameter knob for tuning, enabling right hand finger tip control to keep the hand away from 'live' components behind the left hand side of the receiver panel. The effects are also reduced by using the receiver on the floor or ground. In any case, the matter is of little importance as most signals worth listening to will operate the a.g.c. circuit whereupon any hand-capacitance effects disappear with the reduction in reaction amplification.

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is the cover price stated on the issue, plus 6p postage.


Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

We regret that we are unable to supply photo copies of articles where an issue is not available.

Libraries and members of local radio clubs can often be very helpful where an issue is not available for sale.

MODIFICATIONS TO

CYCLOPS

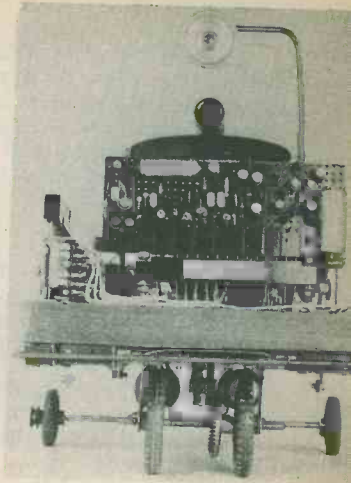

Part 1
by L. C. Galitz

Cyclops, or Cybernetically Controlled Light Oriented and Powered System, was featured in our issues for July to December 1972. The present 2-part series describes modifications which may be carried out to enable him to exhibit further reactions to his environment.

REGULAR READERS WILL HAVE FOLLOWED THE SERIES on Cyclops which appeared in the last July to December issues inclusive. (These back-issues may be obtained by post from Data Publications, Ltd. at 20p plus 6p post each, or at £1.20 plus 21p post for the set of six.)

When we left Cyclops he was free to roam about his environment without offering anything in return for this privilege. Details will now be given of how to make him work for his living and, also, to see what happens when we try to make him work too hard.

CONDITIONED REFLEX

With the conditioned reflex unit on Board 2, we can present to the two inputs and the two outputs any combination of meaningful senses and responses, and the board, as a central core, will be ready to build up a conditioned reflex.

As the cost of building several conditioned reflex units is prohibitive, the next best solution is to have switching on the inputs and outputs of the conditioned reflex unit, and thus enable Cyclops to demonstrate several different versions of conditioned response, using only one conditioned reflex unit.

The first response that can be added is to attempt to make Cyclops work for a living. In the preceding series we saw that the basis of training animals in a circus is to reward it with food upon performing a trick successfully, and this can be extended to Cyclops.

Suppose we put a weight on Cyclops' back. Being a rather lazy animal, we might expect him to go into a tantrum and shake it off. However, we wish to train Cyclops to carry the weight, and so we must give him some sort of reward, and a good reward would be food. With Cyclops light is food, because it is assumed that light, by way of solar cells, can be converted to electricity, which is Cyclops' staple diet.

APRIL 1973

Thus if, every time we place a weight on his back, we shine light in his eye it would not seem unreasonable if Cyclops decided that it would be a good idea to put up with the weight.

It should now become obvious that if we present the output of some load sensing mechanism to the Sn input, and the output from RLC to the Ss input, and then if we connect the En output to the obstacle avoiding mechanism, we have satisfied the conditions outlined above. On receipt of Sn, a load, the conditioned reflex unit will evoke En, (in other words, the obstacle avoiding mechanism) and Cyclops will try to shake the load off his back. However, if Sn is coupled with Ss (in other words, light) after a while, instead of Sn evoking En, it will evoke Es. However, nothing is connected to Es and thus, after conditioning, the placing of a load on Cyclops' back will have no effect at all, and he will carry the load.

ANXIETY NEUROSIS

Cyclops is, after all, only a bundle of electronics, and if we try and ask too much of him, and tease him, it would not be surprising to find him behaving neurotically. Suppose that every time he tried to move off someone applied a magnet such that he had to stop for a while. Then, as he moved off after a short pause of 'playing dead' suppose he once more received a magnetic stimulus such that again he had to stop. After a while, the very act of moving off would mean the application of a magnet, and so Cyclops would stop in anticipation of this. However, when he tried to move off once more the very act of starting would trigger the conditioned reflex again, and he would have to stop. Thus Cyclops would move around in short jerks – a sad state indeed – until the conditioned reflex unit forget the association between starting to move and magnets. Naturally, if the conditioned response were continually reinforced,

Cyclops would continue nervously twitching and never recover from his attack of neurotic depression.

The way this state of affairs may be simulated is by connecting to the Sn input some device which senses when Cyclops just starts moving, and by connecting the magnetic sensor to the Ss input. One could then connect RLB to Es output, and the conditions just outlined would then evoke a fit of neurotic depression.

THE CIRCUIT

Before considering the conditioned reflex input switching, there are a number of modifications to be carried out first which do not alter the mode of operation at present, but are essential for correct operation later on.

Previously, only RLB was connected to En output, and it was convenient to connect the En output gate to the Sn monostable to provide the delay required for RLB operation. Now, however, other circuits are connected to En output which do not need the delay. Thus, the En output must be converted such that there is no delay and a delay circuit incorporated at the relay itself, seeing that other circuits, whose outputs are non-delayed, are also required to operate RLB.

In order to detect when the motors start operating, the voltages on both of the coils of RLB are monitored. Rather than use RLC contacts which, being connected directly to the motors, are rather noisy, a similar circuit monitors the voltage on RLC coil. These two circuits, plus the RLB delay circuit, are all mounted on a third piece of Veroboard, and the circuit of this third board is given in Fig. 1.

Dealing with the RLB delay circuit first, when D12 receives a negative pulse (from TR31 in Fig. 27 - Part 5 of the previous series) C14 charges by way of R53, and the voltage across it rises almost instantaneously to the full pulse potential. The voltage across C14 is moni-

tored by TR34 whose output passes directly to a Schmitt trigger. If the voltage across C14 exceeds a certain amount the Schmitt trigger fires, and the voltage at TR36 collector rises to nearly the negative rail potential. This turns TR37 on, which operates RLB. As C14 discharges, eventually a point will be reached where the Schmitt trigger switches off, and RLB de-energises. There are, of course, simpler ways of arranging a delay circuit, but in order to simplify the circuit to be described in the next paragraph, the voltage across RLB coil must either be high or low, rather than a smoothly varying one as would be obtained if the Schmitt trigger were omitted. The delay circuit would still work, but the following circuit would not.

It would no doubt be simpler just to employ a relay across the drive motor to detect whether the motors were running, but a neater approach, which eliminates further moving parts, is to use solid-state electronics to detect whether RLB is energised or not.

To do this, R60 connects to one coil and R61 connects to the other of the coils of RLB. R62 causes a potential divider to be set up, and the junction of this potential divider is connected to the base of TR38, which is wired in the common emitter mode to give high voltage gain. TR39 inverts the output from TR38. When any of the coils are energised TR38 switches on, thus switching off TR39, whose collector consequently goes negative by virtue of the resistor going up to the negative rail in the input circuitry of the conditioned reflex unit (R37 in Fig. 27). When both of the coils are de-energised, and the motors start, the collector of TR39 goes positive, which is the effect desired, so that the monostable in the input circuitry of the conditioned reflex unit is triggered.

A similar circuit monitors the voltage on the basic reflex coil of RLC only, for reasons to be explained in a moment. This time, when the coil operates TR33 turns on causing the collector to go positive, which is the effect

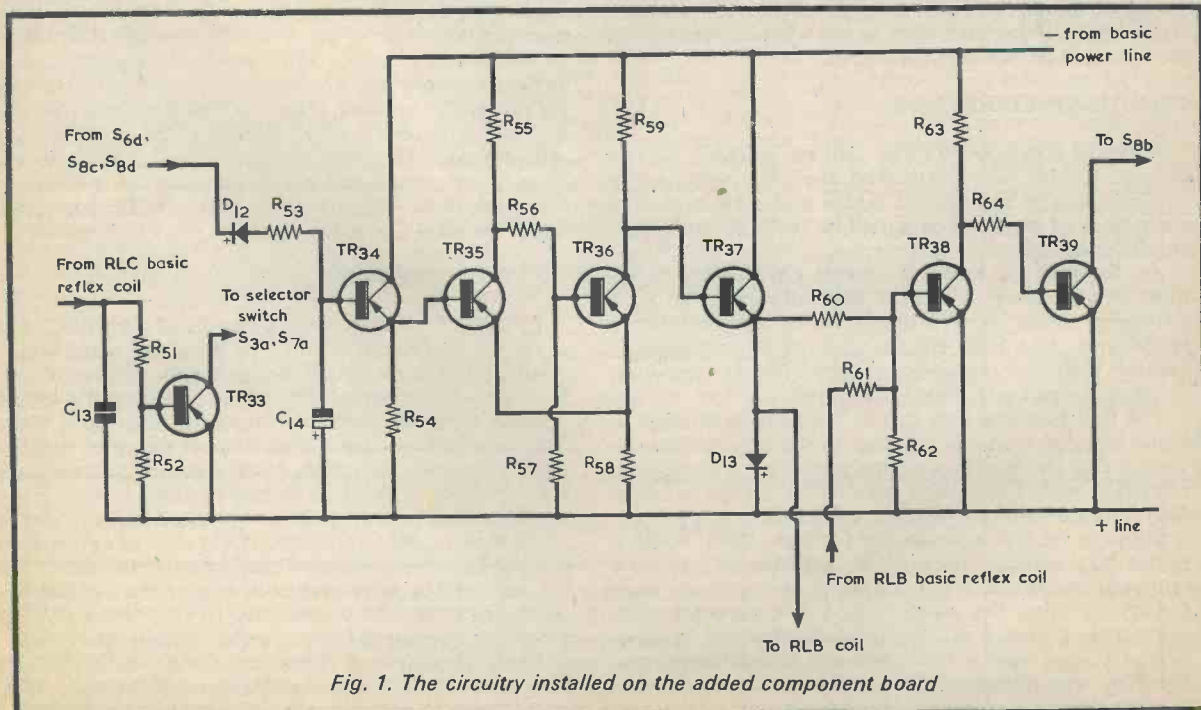


Fig. 1. The circuitry installed on the added component board

desired in this case. (TR33 couples via the switching circuits to pin 3 of Board 2.) C13 eliminates any noise on the input.

The inhibit Ss gate in the original design was included to prevent automatic reinforcement of conditioning when it was not required, because in certain cases, such as conditioning to light, the operation of Es automatically evoked Ss. The discerning reader will now notice that the circuit which detects the operation of RLC is connected to the coil operated by the basic reflex circuitry and, therefore, when the conditioned reflex circuitry operates RLC, no pulse is automatically fed back to Ss.

We similarly do not want automatic reinforcement of either of the two new conditioned reflexes, as neither are defensive, but seeing that there is nothing connected to Es in the weight training mode, and seeing that operation of RLB does not operate the reed switch in the anxiety neurosis mode, the inhibit Ss gate can now be totally dispensed with.

The Ss input circuitry is now changed to that shown in Fig. 2. Resistor R23 and capacitor C6 provide the circuitry required to trigger the monostable. The circuitry around TR15 and TR16 will be explained later.

Now that the delay for RLB has been dealt with by circuitry on the new board, the input of the En output gate that originally went to TR21 collector to provide the delay, now goes to Sn directly. However, in order for the gate to function correctly, the base of TR27 must be taken negative to cut TR27 off when Sn operates. When Sn operates it goes positive, and thus an inverter in the form of TR32, R49 and R50, is interposed between Sn input and the En output gate.

LOAD SENSING

There are several ways of arranging a mechanism such that, when a load is placed on Cyclops' back, the output goes positive. The easiest is to have a large hinged plate upon which loads can be carried, with the hinge operating a microswitch, and this is the method

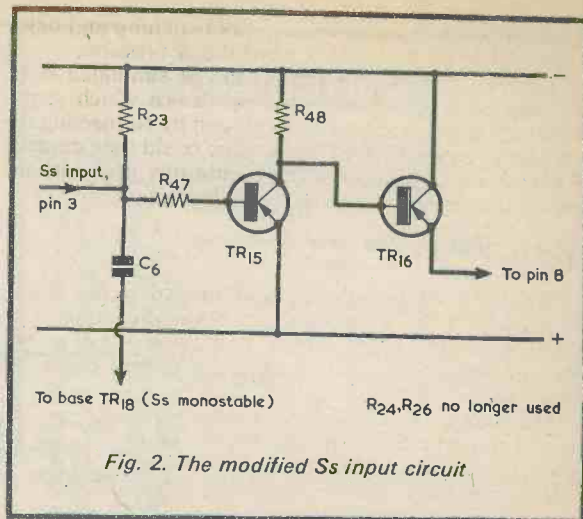


Fig. 2. The modified Ss input circuit

employed. One terminal of the microswitch is connected to the positive supply line, whilst the other terminal connects to the conditioned reflex input selector switch.

SELECTOR SWITCH

The conditioned reflex switching is carried out by an added 3-button interlocking push button unit, each switch having 4 changeover contacts. The inputs and outputs now provided are listed in Table I. The first button selects the old S3, so that the original two conditioned reflexes may be selected. The second button connects up the inputs and outputs in such a way that Cyclops is ready to learn how to carry loads. The third button connects the conditioned reflex unit so that Cyclops is susceptible to nervous breakdowns.

There are a number of extra components in the modifications whose functions have not yet been explained.

Table 1
Conditioned Reflex Connections

Reflex	Ss	Sn	Es	En
Touch	RLA2	Magnet Sensor, X2	RLA Delay Circuit. Pin 6, Board 1	RLB delay circuit. D12-Connection 1, Board 3
Light	RLC Sensor. TR33-Connection 5, Board 3	Magnet Sensor, X2	RLC Coil	RLB delay circuit. D12-Connection 1, Board 3
Weight	RLC Sensor. TR33-Connection 5, Board 3	Load Sensor, S9	—	RLA delay circuit. Pin 6, Board 1
Anxiety	Magnet Sensor, X2	RLB Sensor. TR39-Connection 7, Board 3	RLB delay circuit. D12-Connection 1, Board 3	—

Fig. 3. The new En output circuit

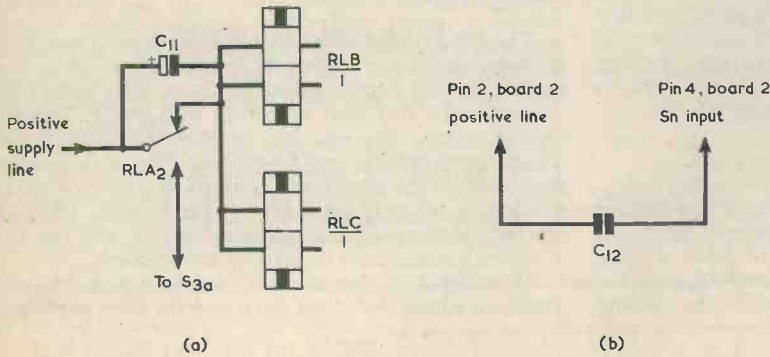
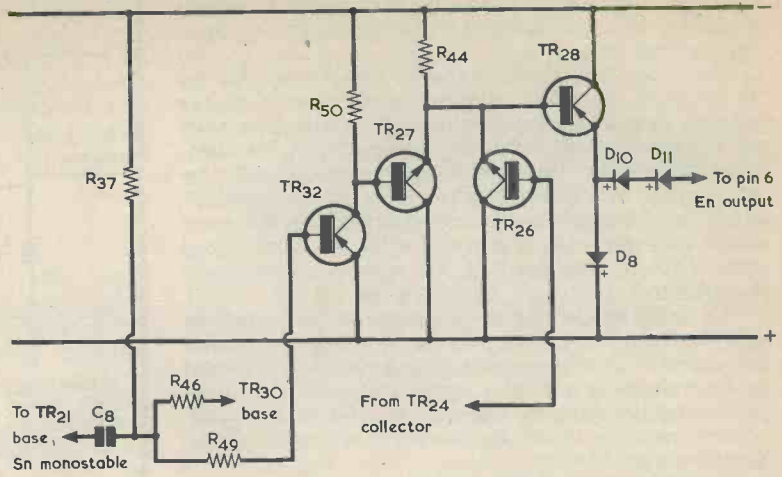


Fig. 4. (a). Suppression capacitor C11 is fitted as shown here
(b). Adding suppression capacitor C12

Two of these, C11 and C12, are shown in Fig. 4.

Even though the potential dividers eliminate spurious triggering of the monostables, pulses appear when RLA2 disconnects the common connection of all the coils from the positive line. The other ends of the coils tend to jump from 0.5 volt to 1.5 volt in nearly all cases. C11, connected across RLA2 contacts, eliminates the sharp pulse completely. C12 similarly reduces noise on the Sn input, being wired between pins 2 and 4 of the socket for Board 2.

When conditioning to touch or light is selected, the reed switch connects to Sn whilst D12 connects to En, so that detection of a magnetic field causes the robot to stop. However, when anxiety neurosis conditioning is selected, the reed switch is connected to Ss input and D12 is connected to Es. Unfortunately, no provision has been made to cause Es to be evoked by Ss and so, in this special case where existing circuitry does not do this, an extra circuit has to be brought in. Whenever Ss input goes positive, TR15 turns off allowing TR16

to switch on. When the selector switch is in the anxiety conditioning position, the emitter of TR16 connects to D12, and thus the reed switch which is connected to Ss input under these circumstances operates the RLB delay circuit.


There are two extra diodes, D10 and D11, connected in series with the En output. It was found that the voltage on the En output was too high when Cyclops was in the unconditioned state, preventing release of RLA when En reverted to the off state. Similarly, the voltage was high enough when Cyclops was in the conditioned state to cause RLB to operate when Sn was given, even though the voltage on the output rose to only 1.5V instead of the usual 5V. Rather than include extra components in the gate to keep the voltage down, two silicon diodes were used to drop the output by about 1.35V. This was found to be sufficient to prevent an output appearing when it was not supposed to, whilst not being too high to prevent the gate operating when it was meant to.

COMPONENTS

The additional parts required are listed in the accompanying Components List. Some of the components, including in particular those under 'Miscellaneous', will be referred to in detail when the constructional information is given in next month's issue. The Veroboard and Perspex parts should not be obtained until further comments in the next article have been read.

The selector switch, S6-S8, is a miniature 3-button type, each button controlling a 4-pole changeover switch, and is such that depression of one button releases another that is already depressed. It was obtained from G. W. Smith & Co. (Radio) Ltd., 3 Lisle Street, London, W.C.2.

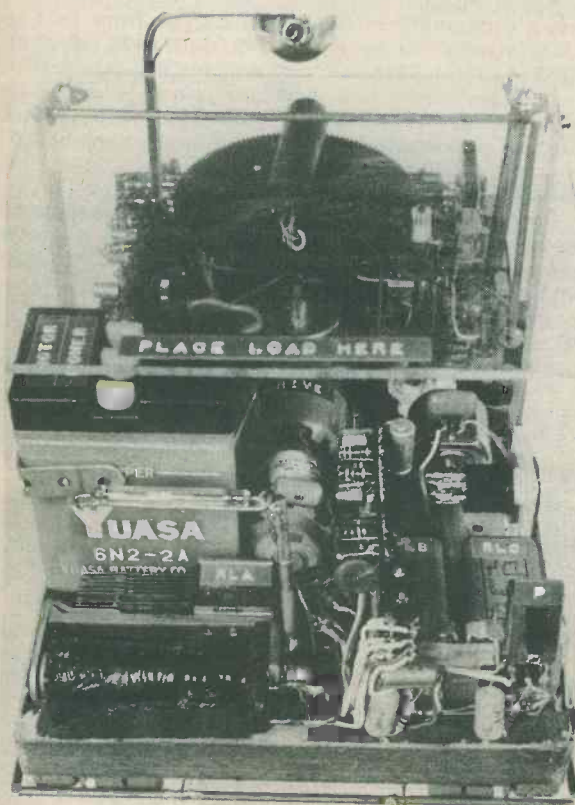S9 is the load microswitch and this has to be quite sensitive, so that the lightest of loads causes it to operate. The microswitch specified meets this requirement.



Cyclops, from behind, after the modifications. Board 3, with C11 below, is in the foreground with S5, in its new position, at the right. At the top is the Perspex load-carrying plate, with the Perspex brackets at left and right. The bracket on the right carries the microswitch, S9. The load-carrying plate tension spring is to the left of the microswitch actuating rod

COMPONENTS

Resistors

(All $\frac{1}{2}$ watt 10%)

R23	(new value) 2.2k Ω
R47	27k Ω
R48	5.6k Ω
R49	56k Ω
R50	2.2k Ω
R51	27k Ω
R52	2.2k Ω
R53	10k Ω (see text)
R54	12k Ω
R55	4.7k Ω
R56	22k Ω
R57	10k Ω
R58	470 Ω
R59	4.7k Ω
R60	22k Ω
R61	22k Ω
R62	2.2k Ω
R63	6.8k Ω
R64	15k Ω

Capacitors

C11	125 μ F electrolytic, 10 V. Wkg.
C12	0.1 μ F
C13	0.05 μ F
C14	100 μ F electrolytic, 6 V. Wkg.

Semiconductors

TR32-TR39	Any p.n.p. transistors of medium gain, i.e. greater than 60
D10-D13	Any silicon diodes

Switches

S6-S8	Three push-button unit, each section with 4-pole changeover contacts (see text)
S9	Sensitive microswitch, e.g. Bulgin S530 (Home Radio Cat. No. WS104)

Miscellaneous

- Veroboard, 0.15 in. matrix, 2 $\frac{3}{4}$ in. \times 1 in. (6 strips \times 18 holes - see text)
- 8-way plug and socket (optional - see text)
- 1-off piece $\frac{1}{2}$ in. Perspex, 6 $\frac{1}{2}$ in. \times 6 $\frac{1}{2}$ in.
- 2-off pieces $\frac{1}{2}$ in. Perspex, 6 $\frac{1}{2}$ in. \times $\frac{3}{4}$ in.
- 2-off Meccano angle brackets, part 12
- 1-off Meccano screwed rod, 2 in., part 81
- 1-off Meccano rod 8 in., part 13a
- 1-off Meccano rod 5 in., part 15
- 2-off Meccano rods 1 $\frac{1}{2}$ in., part 18a
- 1-off Meccano tension spring 2 in., part 43
- 3-off Meccano bolts
- 6-off Meccano nuts


In the prototype, Board 3 was mounted on a miniature 8-way plug, with a corresponding socket on the chassis. However, the board is quite small and connections could be soldered direct to it if preferred.

All the diodes are silicon, and the transistors are as specified in the Components List.

(To be continued)

SHORT WAVE NEWS

FOR DX LISTENERS

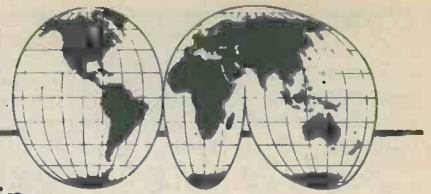

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

We commence this month with a report on the reception of signals from Radio Hanoi, North Vietnam, on a measured frequency of **4892** (61.32 metres) on several occasions around the 2230 mark, at which time announcements and identification in Vietnamese are made. This transmission is part of the service to South Vietnam and also the domestic programme.

The domestic/S. Vietnam programme is radiated at various time periods from 0920 through to 0530 on **3365** (89.15m), **4715** (63.62m), **6380** (47.02m), **7740** (38.75m), **10015** (29.95m) and on **10095** (29.71m).

The service for S. Vietnam only is as follows - **4892** (measured but listed **4895**) (61.32m) from 1557 to 1858 and from 2129 to 2400; **7105** (42.22m) from 0925 to 1858 and from 2129 to 0530 and on **10050** (29.85m) from 0925 to 1555 and from 0100 to 0530.

The External service (Main Network) radiates a thirty minute programme in English on **10040** (29.88m) and **15105** (19.86m) at 0100, 0200, 1000, 1300 and at 2230.

The Second Network, to Indochina, on **7080** (42.37m) and **7800** (38.46m) radiates a half-hour programme in English from 1000 and from 1300.

Note: all the channels listed above are subject to some 10kHz variation (i.e. plus or minus 5kHz).

CURRENT SCHEDULES

● EGYPT

The Arab Republic of Egypt broadcasts to the non-Arab world in various languages throughout the day, that for the English transmission to Europe is on **9805** (30.59m) from 2145 to 2300 with the newscast at 2200. A broadcast in English is made from 1315 to 1430 on **17920** (16.74m) directed to South and Southeast Asia. From 1730 to 1845 on **17655** (16.99m) to East, Central and South Africa and from 2030 to 2200 on **17725** (16.92m) to West Africa. A further programme in English is directed to North America from 0200 to 0330 on **9475** (31.66m).

Programmes for the Arab world are radiated from Cairo throughout most of the day, listen for instance from 1630 to 1635 on **15475** (19.38m) or **17745** (16.90m) for a news summary in Arabic in the "Voice of the Arabs" service, or from 2030 to 2045 on **7050** (42.55m) or on **9850** (30.45m).

The Palestine service can be heard when signing-on at 1400, in Arabic, on **15475** (19.38m), **17625** (17.02m) and on **17745** (16.90m).

The Arab Maghrib service is on the air from 2130 to 2135 on **7050** and on **9850**.

The "Sudan Corner" programme from sign-on at 1200 through to 1625 on **9475** (31.66m) and on **11915** (25.17m).

The "Voice of the Palestine Revolution" operates from 1730 to 1930 on **9755** (30.75m). Another interesting transmission on this latter channel is that of the "Holy Qur'an Station", consisting of readings from the

Holy Qur'an, from 0400 to 0900, 1200 to 1730 and from 1930 to 2100. (Qur'an, westernised incorrectly to Koran)

● ALBANIA

Radio Tirana broadcasts in English to Europe as follows - from 0630 to 0700 on **7065** (42.46m) and on **9500** (31.57m); from 1630 to 1700 on **7065** and on **9480** (31.64m); from 1830 to 1900 from 2030 to 2100 and from 2200 to 2230 on the two latter channels.

● GERMANY (EAST)

Radio Berlin International, "The Voice of the GDR", has a programme in English to Europe from 1815 to 1900 on **6080** (49.34m), **6115** (49.05m), **6125** (48.97m), **7185** (41.75m), **7215** (41.58m) and on **7300** (41.09m).

In English to the U.K. and Eire from 2130 to 2215 on all the above channels plus **9730** (30.83m) and from 2245 to 2330 on all the foregoing channels except **7215**.

● BULGARIA

Radio Sofia radiates programmes in English directed to the U.K. and Eire from 1930 to 2000 on **6070** (49.42m) and on **9700** (30.92m). Also from 2130 to 2200 on the same two channels.

● VATICAN CITY

Vatican Radio broadcasts in English to the U.K. and Eire from 1500 to 1515 on **9645** (31.10m), **11740** (25.55m) and on **15120** (19.84m); from 2045 to 2100 on **7250** (41.37m); **9645** and on **11740**.

● KOREA (NORTH)

Radio Pyongyang does not currently operate a service in English to Europe or the U.K. but does radiate in English to Africa, the Near and Middle East, from 1800 to 2000 on **3560** (84.26m) **6580** (45.59m) and on **9515** (31.52m).

● KOREA (SOUTH)

Seoul, the "Voice of Free Korea", directs a programme to Europe in English from 0630 to 0700 on **15335** (19.56m).

● ROUMANIA

Radio Bucharest has an English service to Europe from 1300 to 1330 on **11940** (25.12m), **15250** (19.67m) and on **17710** (16.93m). From 1930 to 2030 on **7195** (41.69m) and on **9570** (31.34m) and from 2100 to 2130 on **6150** (48.78m) and **7225** (41.52).

● POLAND

Radio Warsaw operates an English service to Europe as follows - from 0630 to 0700 on **7285** (41.18m), **9540** (31.44m) and on **9675** (31.00m); from 1200 to 1300 on **7285** and **9540**; from 1600 to 1630 on **6035** (49.71m), **7125** (42.10m), **7285** and **9540**; from 1830 to 1900 on **6035**, **7125**, **7285** and **9540**; from 2030 to 2100 on **6035** and **9540** and from 2230 to 2300 on **5995** (50.04m), **6135**, **7285** and on **9540**.

RADIO & ELECTRONICS CONSTRUCTOR

●KUWAIT

Radio Kuwait has a service in English for listeners in Europe, India, Pakistan and Sri Lanka from 0430 to 0700 on **15345** (19.55m) and from 1630 to 1900 on **15345** and on **9520** (31.51m).

●JORDAN

The Hashemite Kingdom of Jordan has a Foreign Language service from Amman, the English periods of which are - from 1100 to 1130 on **7155** (41.92m) and from 1630 to 1730 on **9560** (31.38m).

●AUSTRALIA

Radio Australia, Melbourne, operates a transmission directed to the U.K. and Europe in English from 0645 to 0745 on **11765** (25.49m) and from 0700 to 0745 on **9570** (31.34m).

●FINLAND

The FBC from Helsinki has an English schedule for Europe as follows - from 1400 to 1430 on **9550** (31.41m), **11755** (25.52m), **15185** (19.75m) and on **21605** (13.88m); from 1800 to 1830 on **9550**, **11755**, **15185** (not Tuesdays) and on **21605**; from 2030 to 2100 on **9550** and **11755**.

●SYRIA

Damascus has an English programme for Europe from 2030 to 2200 on **15165** (19.78m).

●IRAQ

Radio Baghdad has an English transmission directed to Europe from 1930 to 2020 on **9745** (30.78m).

The Home Service "Voice of the Masses" operates almost throughout the day and night, part of this schedule can be heard (in Arabic) from 1800 to 2305 on **7225** (41.52m) and from 1900 to 2305 on **3960** (75.75m).

The "Voice of Palestine, Voice of the Palestine Revolution", the programme of the Palestine Liberation Organisation, can be heard from 1630 to 1730 on **3960**.

AROUND THE DIAL

Radio Iran is currently using the additional channel of **15137** (19.81m) in parallel with the usual **15085** (19.88m) for the Domestic service from 0720 to 1430.

We have logged Radio Tehran on the unlisted channel of **9620** (31.18m) with the programme in English from 2000 to 2030, the frequency was not amongst those announced.

●AUSTRALIA

Radio Australia can often be logged during the afternoons, we heard them at 1620 on **7145** (41.98m) with identification in English and light music, also in parallel on **7235** (41.46m). This is part of the service to South and Southeast Asia which is as follows - from 1400 to 1500 on **9570** (31.34m) and on **11790** (25.44m); from 1430 to 1500 on **11765** (25.49m); from 1500 to 1730 on **5975** (50.20m), **6160** (48.70m), **7145**, **7235**, **9550** (31.41m), **11765** (25.49m), **11945** (25.11m) and from 1515 to 1730 on **9680** (30.99m).

●CUBA

Havana may be heard, with identification both in Arabic and French, at 1659 on **17735** (16.91m).

●PAKISTAN

Radio Pakistan has been entered into our log at 1330

on **21590** (13.89m) when we heard identification and a news comment in English.

Also heard on **9470** (31.67m) at 2023 with programme of local music and songs and on **7340** (40.87m) at 2030 with the news in English for the U.K.

Another channel on which Pakistan has been logged is that of **3940** (76.14m) at 1619 with a talk in English on Pakistan affairs. This is the Rawalpindi transmitter.

●CANADA

Radio Canada may be heard at 1900 on **11860** (25.29m) when a programme in English and Canadian news is radiated.

●ITALY

RAI Rome has an English programme, with the news at 1930, on **9710** (30.89m).

●BULGARIA

Radio Sofia can be heard on **9700** (30.92m) at 1930 with both the world and local news in English.

●SOUTH AFRICA

RSA has a newscast in English at 1900 on **15175** (19.76m). Johannesburg can also be heard with Interval signal and identification in English at 0757 on **21545** (13.92m).

●ECUADOR

HCJB Quito, may be logged at 1230 on **21460** (13.97m) at which time we heard the English programme preceded by identification, three short and one long 'pip' and time-check.

●MOZAMBIQUE

Radio Clube de Mozambique is listed on **4855** (61.79m). We logged them recently on a measured **4854.5** at 2000 when three chimes and station identification in Portuguese were heard. This is part of the Portuguese service, evening schedule of which is from 1530 to 2210.

R.C. Mozambique can also be heard on **4925** (60.91m) around 2000, we logged them at 2011 when a talk in Afrikaans was heard. This is the English/Afrikaans service, evening schedule from 1500 to 2200.

●ANGOLA

CR6RZ Emisor Official, Luanda, operates from 1700 to 2400 on **4820** (62.24m) we logged them at 2247 when a programme of Portuguese music and songs was being radiated.

CR6RG Radio Commercial de Angola, Sa da Bandeira, can often be heard around 2030 on **4795** (62.56m).


●SAO TOME

Radio Clube de Sao Tome operates on **4807** (62.40m) and can be heard around 1950 or so, usually with songs in Portuguese and local music. A mystery about this one is that it is apt to vanish from the scene for whole periods of time but the writer offers the tip - try on Friday evenings.

●CONGO

An interesting Dx station, recently logged for the first time, is that of a regional transmitter at Pointe Noire on a measured **4843** (61.94m) when a programme in French was heard. This transmitter relays Brazzaville from 0500 to 2000, we logged it at 1935.

In your workshop

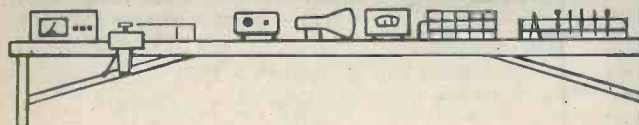

In this episode, Smithy the Serviceman concludes the discussion on tape recorders which he started last month, and devotes his time to enlightening Dick on the subject of the magnetic tape transfer characteristic. He also, incidentally, demonstrates some surprising vagaries in his approach to matters of dress.

"NOW, WHAT ON EARTH HAS happened to them?"

Smithy set down his tin mug of tea and glanced over at his assistant. Dick was searching diligently over the surface of his bench, which was in its usual cluttered condition.

"What have you lost?"

"Some crocodile clips," replied Dick. "I had four nice and shiny new crocodile clips on my bench yesterday which I was going to fit on some of my test gear leads when I had the time. But I can't find them anywhere now."

Smithy absorbed this information.

"Whilst," he commented, "I applaud your diligence in looking for those crocodile clips during lunch-break, I'd much prefer it if you'd sit down quietly instead. You're getting on my nerves. clattering things about on your bench all the time."

BIAS CURRENT

"As you like," replied Dick unexpectedly. "If I sit down will you do me a favour?"

"That depends."

"Will you," asked Dick, "continue the discussion we started during our last gen-session? If you remember, you promised to explain why an a.c. bias signal is applied to the record head of a tape recorder during recording."

"Did I?" queried Smithy absently. "Ah yes I remember, now that you mention it. Well, for the sake of peace and quiet, I'll give you the gen you want. So fill up my mug again, then come on over to my bench."

Eagerly, Dick rose and took Smithy's mug to the tea pot situated near the Workshop sink. He soon returned with the mug, its precious cargo steaming cheerfully.

"Before we get on to technical matters," said Smithy as he took the mug, "there's something I've been meaning to tell you all morning. And that is that I don't think those trousers of yours are at all the sort of thing to wear in a reputable establishment such as this."

Dick looked down at his widely flared nether garments.

"What's wrong with them?"

"Anybody who wears trousers like that," pronounced Smithy firmly, "should be scrubbing decks, not fixing radios and TV's."

But Dick was more interested in tape recording than in standards of dress.

"Let's get on," he said keenly, "with this a.c. bias thing."

"Oh, all right," said Smithy resignedly, as he pulled his note-pad towards him. "I must, however, warn you that the particular subject we're going to deal with is a wee bit sticky in places so I'll need your full attention."

He fell silent for a moment, as he collected his thoughts.

"Now, at our last gen-sesh," he resumed, "we considered the function of the erase oscillator in a tape recorder. This oscillator produces a sine wave, which has to be kept as pure as possible, at a frequency of 40kHz or more. The sine wave is fed to the erase head. The recording tape passes the erase head first and then carries on to the record head which, in the usual low-cost type of domestic tape recorder, operates as a playback head also when the recorder is switched over to that function."

"That's right," put in Dick. "When the recorder is switched to record, the erase head wipes the tape clean of any previous signal it might have had on it, whereupon it's all ready to have a

new signal applied to it at the record head." (Fig. 1).

"Correct," said Smithy. "Also, a small proportion of the erase alternating current is fed to the record head as bias."

"And that," chimed in Dick, "is where I got lost last time! I just don't get this business of an alternating bias current at all."

"Fair enough," commented Smithy.

"Well now, if you're going to find out why we need an a.c. bias current you have first got to understand what happens when the tape is magnetised by the signal which is being recorded. And before you can understand that, you've got to take in a bit of basic magnetic theory."

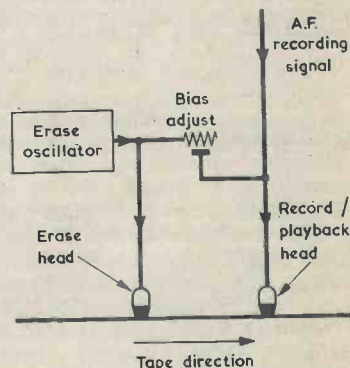


Fig. 1. When a tape recorder is switched to record, the full output of the erase oscillator is fed to the erase head and a small amount, as bias, to the record/playback head, the latter now functioning as a record head

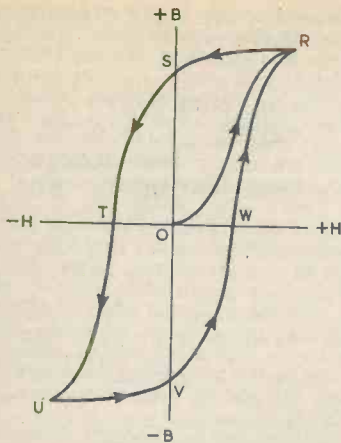


Fig. 2. The familiar BH hysteresis loop for successive cycles of magnetisation of a magnetic material. The dimensions and shape of the curve vary for different materials

Smithy pulled a ball-point pen from the cluster in his top pocket and proceeded to sketch out a diagram. (Fig. 2).

"What's that?" he asked.

"I suppose," said Dick thoughtfully, as he examined the diagram, "that it's a curve of some sort. It seems to have a familiar look about it."

"Can you remember it appearing in any basic iron-cored transformer theory you've encountered in the past?"

Dick looked more closely at the curve.

"Why, that's it!" he exclaimed suddenly. "It's an electromagnetic hysterical loop!"

Smithy turned a long-suffering glance towards the ceiling.

"If," he remarked in a hollow tone, "the future of our Electronic Age has to depend on the likes of you, Heaven rest the next few generations. It's not a 'hysterical' loop, you great big hairy steaming nit, it's a *hysteresis* loop. The word 'hysteresis' applies to any effect where, if you apply a force to a quantity, then reverse the force and bring it back to its starting point, the quantity does not revert to its old state. You have a hysteresis effect here, as I'll show you."

"What," interrupted Dick, "do the letters H and B stand for? You've shown the horizontal line as H and the vertical line as B."

"I have, indeed," agreed Smithy. "But before we get on to those letters I must next tell you that this loop shows what happens when a magnetic material undergoes a number of cycles of magnetising force. This state of affairs occurs in particular in an iron-cored transformer, where the magnetic material is the iron core of the trans-

former and the magnetising force is provided by passing on alternating electric current through the primary of that transformer; and that is why you encounter the curve when you're doing basic transformer theory. However, the loop applies also to any other instance where a magnetic material undergoes a changing magnetising force. And now for those two letters. The letter H stands for magnetising force and the letter B stands for the magnetic flux density which the magnetising force causes to appear in the magnetic material."

"Flux density," repeated Dick musingly, "Is that the same as magnetic field strength?"

"It is," confirmed Smithy. "But it's a little more correct, technically, to refer to it as 'flux density'. Let's start, now, by saying that our magnetic material is completely demagnetised and that we have zero magnetising force. This situation is represented at the point O, where the B and H axes intersect. We next begin to increase the magnetising force with a polarity which corresponds with its going to the right towards +H. This causes the flux density to increase also, and the latter rises from the zero point O towards the height corresponding to point R. We are approaching saturation in the piece of magnetic material at point R, and there is no real advantage to be gained in taking the magnetising force beyond this level."

"The flux density," commented Dick, "hasn't gone up in a very linear manner, has it?"

"It hasn't," agreed Smithy. "The rise in flux density from O to R is slow at first, then it speeds up to a maximum in the central part of the line. After that, it slows down again. The only nearly linear section of the OR line is the part in the middle. We shall now press on to the next operation, which consists of reducing magnetising force back to zero again. This does not, however, cause the flux density to reduce to zero also. Instead, the flux density merely goes down a little bit, falling only to point S on the B axis. This effect is the result of the residual magnetism which is left in the magnetic material, and the flux density of this residual magnetism is equal to the height of point S above point O. This height also represents the 'remanence value' of the magnetisation."

COERCIVITY

"How," asked Dick, "do you get the residual magnetism down to zero?"

"By increasing the magnetising force in the opposite direction. Which means, in our diagram, by taking the magnetising force from the zero point O to the left, towards the -H end of the H axis. If we do this we will eventually reach the point T, at which point flux density is again zero. But, as you can see, we've had to use quite a lot of magnetising force in the -H direction

to achieve this. For the record, the length of the line OT on the horizontal axis is a measure of the coercive force applied, or of the coercivity of the magnetic material."

"Okeydoke," said Dick brightly. "So far as I can see from the loop, if we continue to increase magnetising force in the -H direction by the same amount as we did in the +H direction, we will eventually arrive at point U, which is dead opposite the first peak at point R."

"That's right," stated Smithy. "Should we next start changing H in the right-hand direction so that it first decreases to zero and then increases on the +H side, we finally come back again to point R. In doing so, the loop passes through points V and W in turn, and the curve U, V, W, R has the same shape as the curve R, S, T, U."

"Well, all that seems reasonable enough," remarked Dick cheerfully. "When we start with a demagnetised piece of magnetic material and pass it through a number of cycles of magnetising force starting from zero, the graph for magnetising force and flux density initially traces out the line OR. After that, successive cycles of magnetisation take the relationship around the outside loop."

"You've got it," confirmed Smithy.

"Now, it so happens that for our present discussion, where we're talking about the magnetisation of moving tape, we're only interested in the part of the curve which goes from O to R and then drops down again to S."

Smithy tore the top sheet from his note-pad and, in so doing, glanced down at the side of his bench.

"Damn it, Dick," he expostulated, "those trousers of yours really *are* too bad. I honestly think I'll have to tell you not to wear them in here again."

"Don't say you're still on about them," protested Dick aggrievedly. "What you don't seem to know is that these trousers of mine have been greatly admired by my friends. I decided to start wearing them in here today to brighten the place up a bit."

"Do they," asked Smithy querulously, "have to be such a *bright* scarlet?"

"If," Dick stated loftily, "you followed fashion a bit more closely you'd know that these trousers represent the very latest in current trends."

"To my mind," retorted Smithy crossly, "they just look common."

Dick's face approached the colour of his trousers at this superlative epithet.

"At any event," he replied furiously, "I don't go around with half a dozen pens poking out of my breast pocket. Blimey, mate, the top front left of your jacket looks like the diapason pipes of the organ at Canterbury Cathedral."

"A man in my position," snorted Smithy, highly offended by this sudden attack, "*always* has a lot of pens in his

breast pocket. It's expected of him."

"Also," said Dick cuttingly, "I don't wear braces."

Smithy's jacket was already unbuttoned and, with a contemptuous flourish, Dick flicked it open to reveal the accessories in question.

"Well, really," spluttered the affronted Serviceman, "this is tantamount to bodily assault."

But Dick had spotted something at the end of one of the braces supports.

"Ye gods," he gasped. "What's this?"

"Get your hands off me," said Smithy hastily, as Dick peered more closely, "and don't go poking your nose into things that don't concern you."

"I thought," chuckled Dick, "that one of those braces buttons looked a little funny. It is, too. It isn't a button at all - it's an 0.1 μ F disc ceramic!"

"I'm having trouble with the dry cleaners," explained Smithy, patently embarrassed by Dick's discovery. "They've mislaid my other working suit and I had to dig out this old one. The trousers had a braces button missing and so I made do with that capacitor as an alternative."

He stopped for a moment, and his old authority gradually returned.

"It makes a jolly good button, too," he stated aggressively. "You just push the two lead-outs through the fabric at two points that are slightly spaced apart, then twist the wires together on the inside. The braces loop then goes over the body of the capacitor."

"Blow me," said Dick, continuing his examination of Smithy's garments, "there's something else here, too."

He turned one of Smithy's jacket flaps over.

"I must," he remarked unbelievably, "have seen everything now. One of your jacket buttons is held on with a bit of black enamelled wire twisted round a 2BA washer at the back of the material. Dash it all, Smithy, can't you sew a button on properly?"

Smithy pushed his assistant's hands away from him and rose in dignity.

"I am a service engineer," he stated pompously, "and not a seamstress; and I use the products appropriate to my calling. Now, if you've quite finished messing around with my clothing I'd be obliged if you'd go and get me another mug of tea."

As his grinning assistant walked over to the Workshop sink, the ruffled Smithy carefully preened himself and settled his clothes properly once more. Dick returned with the mug. This act of obedience to Smithy's command restored the Workshop to its proper condition, with Smithy in his rightful place as Service Manager, and Dick in the more lowly niche of Staff.

what it was we were talking about a few minutes ago. Ah yes, I remember now. I'd explained the BH hysteresis loop to you and I then said that, so far as magnetic tape is concerned, the only part of the loop we're interested in is the bit where the magnetising force goes up to maximum in one direction and then returns to zero again."

"Why is that?" asked Dick, as his mind once more concentrated on technical matters. "What about the remainder of the outside of the hysteresis loop?"

"We can forget about that," replied Smithy, "by making the assumption, which is certainly true for the lower audio recording frequencies, that the magnetisation of the tape only follows the first section of the loop. The subsequent parts of the loop are not applied to the tape because it has by then left the record head gap where the magnetising force appears. Let's see what happens to a particle in the magnetic coating of the tape at the moment of passing the record head gap. This particle is raised to a flux density which is proportional to the record current flowing in the record head winding, after which it leaves the head and is

subjected to no further magnetising force. The flux density in the tape then drops to the residual, or remanence, value."

"Oh, I see," said Dick quickly. "Each particle in the tape is taken up to a value on the OR line in the hysteresis loop, after which it drops to the corresponding remanence value."

"That's it," confirmed Smithy, picking up his pen and drawing some further sketches. "Let's next look at a few of the remanence values we're likely to get on the tape. I'll start off by drawing an initial curve in which the magnetising force takes the flux density as high along the OR curve as it did in the hysteresis loop diagram, then I'll add its drop to remanence level. Here you are."

Dick looked at Smithy's diagram. (Fig. 3(a)).

"Well, that," he remarked, "is perfectly clear. It's the same as we had in the overall hysteresis curve when we went from point O to point R and then back again to point S."

Smithy sketched out three further diagrams. (Figs. 3(b), (c) and (d)).

"And here," he remarked, "are three more examples. In the first of these the magnetising force takes the

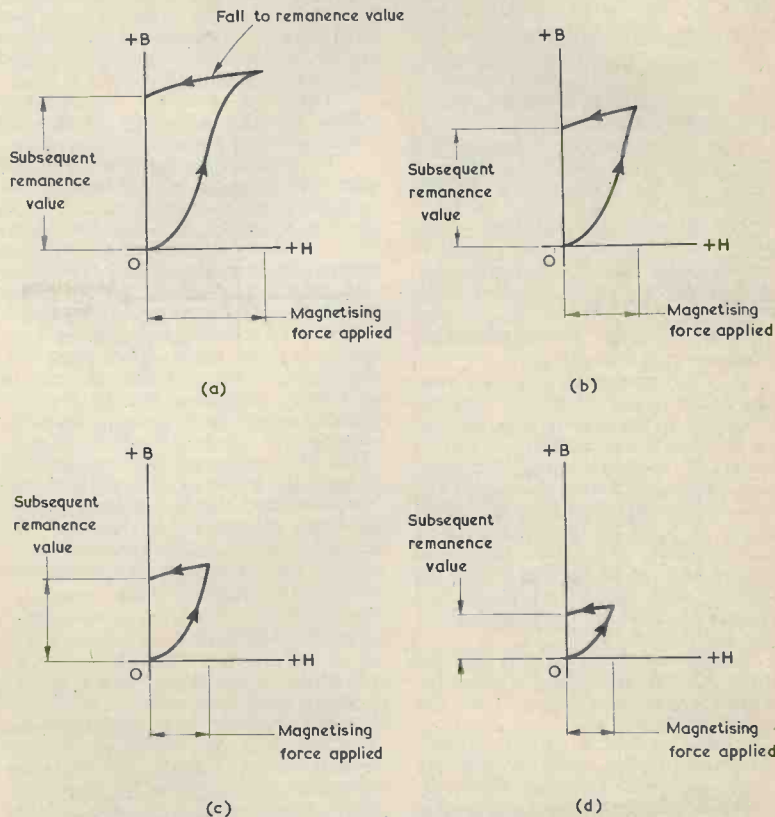


Fig. 3 (a) Subsequent remanence value in recording tape for the magnetising force shown
(b) (c) (d) The remanence values given by progressively reducing magnetising forces

TRANSFER CHARACTERISTIC

Smithy took a sip from the mug and marshalled his scattered wits.

"Let's see," he said, "if I can recall

flux density about three-quarters of the way up the original OR curve, the second takes it about half-way up and the third about a quarter of the way up. In each case there's a subsequent drop to remanence value. Do you notice anything about these drops to remanence value?"

Dick examined the diagrams critically.

"I can't see anything in particular," he remarked. "Apart from the pretty obvious fact that the amount of drop to remanence in each instance is approximately proportional to the height of the curve before the drop commences."

"That," said Smithy, pleased, "is just what I wanted you to say. Since the falls to remanence value are proportional to the peak flux density in each case it follows that, if we were to draw a curve showing final tape remanence value against magnetising force, this curve would have just about the same shape as did our original OR curve. If we used the same flux density units on the vertical axis as in the previous case, the only difference would be that the new curve would be smaller in height."

Smithy drew the curve in question. (Fig. 4(a)).

"There you are," he remarked.

"That's the curve showing tape remanence value against magnetising force. But this curve shows only half of the complete picture because, with an alternating signal current applied to the record head, there will be magnetisation with opposite polarity as well. This will produce remanence values of flux density in the bottom left-hand quadrant of our diagram in exactly the same way as in the top right-hand quadrant, and we obtain a bottom left-hand curve which is a mirror image of the top right-hand curve. I'll sketch it out now."

Smithy added the second part of the curve. (Fig. 4(d)).

"Phew," said Dick. "We seem to have covered a lot of ground just to arrive at this curve."


"There have been a few things to consider," conceded Smithy. "But it was necessary to start off with the original hysteresis loop, pick the initial magnetisation section out of this, then make the hop from the flux density produced by the magnetising force to the remanence value which is left when the magnetising force is removed. Now this final curve I've drawn is a very important one because it represents the transfer characteristic of the tape. It defines the flux density which is left on the tape, and which will later activate the playback head, for the varying magnetising forces which are produced by the record head as the tape passes it."

"I see," commented Dick. "I assume that the magnetising force applied to the tape is proportional to the recording signal amplitude at the record head."


"It's proportional," said Smithy, "to

the amplitude of the recording signal current flowing in the head winding. It's necessary here to think in terms of the signal current only in the head winding, and not in terms of the signal voltage across the winding or the power dissipated in it."

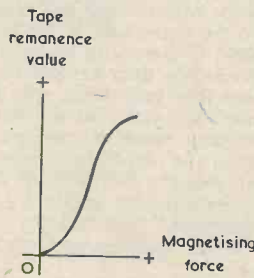"Thinking in terms of current only seems sensible enough to me," stated Dick, critically. "For instance, when we talk of the magnetising force given by, say, a solenoid coil we normally refer to this as so many amp-turns, the amp bit being the current in the coil and the turns bit being the number of turns the coil has."



(a)

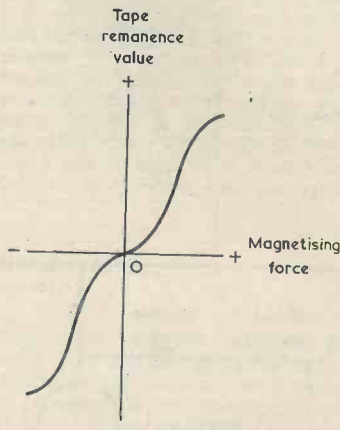

(b)

Fig. 4 (a) The curve showing tape remanence value against magnetising force is similar to the curve OR of Fig. 2

(b) To accommodate magnetising forces of both polarity, the curve of (a) is repeated in the opposite quadrant. The complete curve shown here is the transfer characteristic for the tape

Your Local Supplier

LONDON

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP
Tel: 01-723 4185/2926

ST. HELEN'S RADIO

HI-FI Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS
LONDON, W.10
Tel: 01-969 3657

Electrolytic Capacitors by Mullard, Plessey, Erie, etc.

UF/V
1250/25, 2000/35, 2200/25,
4700/16, 8000/30, 10,000/15,
10,000/25, 1000+1000/40, 16+
16/500. All 35p each, post free.
2000/50, 2500/50, 5000/50,
10,000/50, 12,500/50, all at 50p
each, post free.
16+16/350, 32+16/350, 32+
32/350, 40+40/250, 50+50/300,
80+80/450, 100+100/385, all
at 25p each, post free.

ELEKON ENTERPRISES

224a, St. Paul's Road, Highbury Corner,
London N.1

DEVON

Massive Clearance Bargains
Bargain Component Parcels contain Resistors, Capacitors, Switches, Knobs, IF's, Transistor Panels, etc., etc., 6 lb nett weight £1.00, p.p. 40p.

Computer Panels, Assorted Types, 4 lbs. nett weight £1.00, p.p. 30p.
Assorted Electrolytic Capacitors, 6 lbs. nett weight, £1.00, p.p. 40p.
Mullard Ferrite Magnets $\frac{1}{8}'' \times \frac{1}{8}'' \times \frac{1}{8}''$, 100 for £1.25, p.p. 16p.
Brand New Erie Electrolytic Capacitors, 250UF 25V $1\frac{1}{4}'' \times \frac{1}{2}''$ Wire-ended, 8p each, 100 for £6.50.

XEROZA RADIO

1 East Street, Bishops Tawton, Devon

Your Local Supplier

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.

70-72 Holdenhurst Road
Bournemouth
Telephone 25232

LEICESTERSHIRE

ENSIGN ELECTRONICS.

43" 8 Section Telescopic Aerials	35p
New Marked 2N3055 Transistors	35p
New Slide Switches. Special Offer 4 for	30p
Miniature Battery Level Meters. 0-600 Ma F.S.D.	50p
100 Mixed High Stability Resistors (New)	35p
New 12 Volt Plug in Relays. (11 Pin Base)	60p
Silicon Bridge Rectifiers. 50 volt 1 amp	30p
PLUGS STD Jack Plugs 12p, 3 pin Din Plugs	12p
10 1/2" Revox Tape Spools	40p
67 Foot Wire Aerials, Marked every foot	60p
Headphones with Boom Mic (used)	£1-45
Sets of Spare valves for 62 set (new)	£1-35
Geiger Counter - Contamination Meter No 1	
Separate Probe - Runs off 4 x HP7 Batteries	£4-25
Set of 6 U.S.A.F. maps - Large - All Different	60p
B7G Bases 7p B9A Bases 7p	
50 volt Disc Capacitors, 0.05 mjd, 0.02 mjd,	
0.002 mjd 12 for 15p 50 for 50p.	

Send to: Dept R.C., 30 High Street, Quorn,
Nr Loughborough, Leics.

SURREY

WITWORTH TRANSFORMERS

TV Line out-put transformers

Manufacturers of the largest range in the
country. All makes supplied.

Free catalogue.

Modern

BAIRD, BUSH, GEC, PHILIPS
Replacement types ex-stock.

For "By-return" service, contact London
01-948 3702

Tidman Mail Order Ltd., Dept. R.C.

236 Sandycombe Road,
Richmond, Surrey TW9 2EQ

Valves, Tubes, Condensers, Resistors,
Rectifiers and Frame out-put Transformers,
Mains Transformers also stocked.
Callers welcome.

SUSSEX

E. JEFFRIES

For your new television set
tape recorder, transistor radio
and hi-fi equipment

PHILIPS, ULTRA, INVICTA
DANSETTE, MASTERADIO, PERDIO,
MARCONI, PHILCO FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

D.C. BIAS

"That's the idea," affirmed Smithy. "Coming back to the tape recorder head, the recording signal is normally fed to this by what is called a 'constant current' circuit. A circuit of this nature is required because, since the record head is essentially an inductive component, it offers an impedance which increases with the recording signal frequency. With the earlier valve recorders it was a simple process to provide a 'constant current' arrangement, as all that had to be done was to supply the record head from a voltage amplifier anode by way of a fixed resistor whose value was much higher than the impedance of the head at the highest frequency to be recorded. The valve anode then worked into a load whose total impedance only altered by a small amount over the whole audio frequency range, whereupon the current in the record head winding was, near enough, proportional to voltage amplitude at the anode for all audio frequencies." (Fig. 5(a)).

"What about present-day transistor recorders?"

"Well," said Smithy. "You can't get as high a voltage swing at the collector of a transistor as you can at the anode of a valve because the supply voltage is much lower. The series resistor idea is still common in transistor recorders, nevertheless, but the lower voltage available means that the head impedance and resistor values are a lot smaller. A scheme you'll encounter in some transistor recorders employs a step-up transformer at the stage which feeds the record head. This steps up the audio voltage available, whereupon the fixed

series resistor arrangement becomes comparable with that in a valve recorder." (Fig. 5(b)).

Smithy took a further draught from his mug.

"However, we're digressing a bit here," he continued, "as our main interest at the moment is in the a.c. bias that's applied to the record head."

"That transfer characteristic you drew just now," said Dick, returning to Smithy's sketch, "doesn't look very linear to me."

"It's anything but," agreed Smithy, as he tore the next sheet from his pad and proceeded to draw a further diagram. "The worst bit is in the middle, on either side of the zero point. If we apply a sine wave current to the record head it will appear, as remanent magnetisation on the tape, in extremely distorted form."

Smithy completed the diagram, then showed it to Dick. (Fig. 6(a)).

"As you can see," he went on, "the non-linear part of the characteristic causes the centre of the sine wave on the tape to be all squashed up. If the sine wave has a large amplitude, its peaks also get compressed."

"The two central bits of the characteristic above and below the zero line look fairly linear," commented Dick. "Couldn't you apply the sine wave to one of them?"

"You could," said Smithy, busy again with his pen. "And a suitable way of doing this would be by feeding a direct current to the record head in addition to the audio current. This is known as d.c. bias, incidentally, and it shifts the sine wave over to one side." (Fig. 6(b)).

Dick looked with interest at the latest diagram Smithy had drawn out.

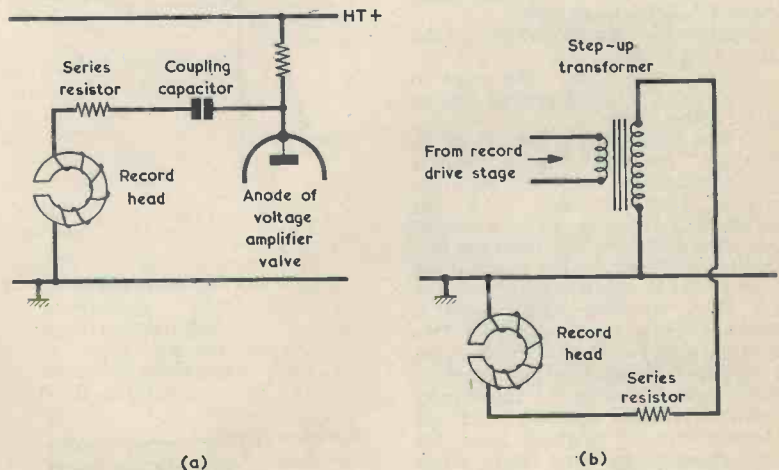


Fig. 5 (a) A 'constant current' record head drive circuit can be easily provided in a valve tape recorder

(b) Some transistor recorders have a step-up transformer to provide a high voltage swing for a 'constant current' circuit. The transformer, via suitable taps, may also drive the speaker when the recorder is switched to playback

Your Local Supplier

YORKSHIRE

**PASSINGHAM'S
ELECTRONICS**
for Government Surplus
Radio & T.V. Components
Electronic Components
also postal service
**PASSINGHAM'S
ELECTRONICS**
5 Dale Street
Bradford 1
Yorkshire

EIRE

PEATS for PARTS
ELECTRONIC COMPONENTS
RADIO & TELEVISION

*For the convenience of Irish
enthusiasts we supply*

The Radio Constructor
Data Books and
Panel-Signs Transfers

Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

**RADIO & ELECTRONICS
CONSTRUCTOR**

**ANNUAL
SUBSCRIPTIONS
to this magazine
may be obtained
through your
newsagent
or direct from the
publishers
ONLY £2.70
per year, post free**

*Please send remittance with name
and address and commencing issue
required to:*

DATA PUBLICATIONS LTD
57 Malda Vale London W9 1SN

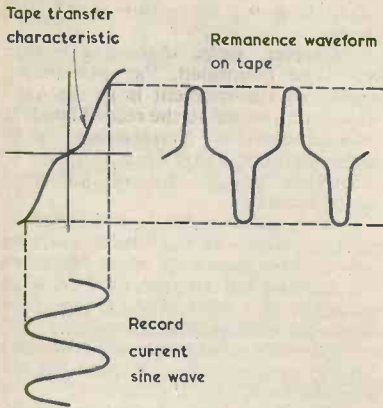


Fig. 6 (a) If a sine wave current is applied graphically to the tape transfer characteristic, the corresponding tape remanence waveform can be drawn on the right. In this instance the remanence waveform is heavily distorted

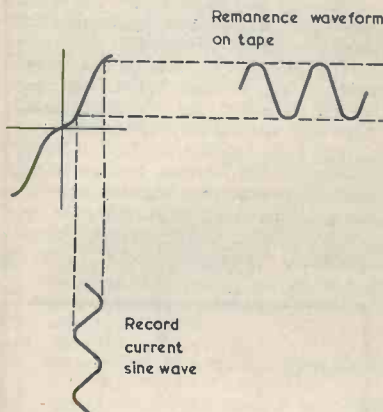


Fig. 6 (b) D.C. bias shifts the record current sine wave to a linear section of the transfer characteristic. Provided the record current amplitude is reasonably low the remanence waveform does not have excessive distortion

"That looks fairly practicable," he remarked. "Provided the sine wave amplitude isn't too large, the waveform on the tape should be reasonably free from distortion."

"True enough," said Smyth. "But in practice the d.c. bias approach doesn't work very well. The main difficulty is that the tape becomes continually magnetised and this results in noise. D.C. bias was used in early experimental recorders, but it was soon abandoned when the a.c. bias approach was discovered. The a.c. bias current, which as we have already mentioned is of the order of 40kHz or more, is given an amplitude which causes its peaks to be at the centres of the two linear sections of the transfer characteristic. Like this."

Smyth scribbled out a further sketch. (Fig. 7(a)).

"If now," he continued, "we add an audio sine wave current at the record head, the bias peaks are deflected to the left and right in our

diagram in sympathy with the sine wave. The resulting remanent magnetisation on the tape consists of a series of peaks which are produced by way of the two linear sections of the transfer characteristic. The average remanent value between these two sets of peaks then takes up a form which is a virtually distortion-free version of the recording sine wave current. Here's what happens."

Smyth quickly drew out yet a further diagram. (Fig. 7(b)).

"Blimey," remarked Dick, impressed. "The a.c. bias current certainly overcomes the non-linearity in the transfer characteristic of the tape. Why, even a tiny little signal amplitude will still be effectively applied to the linear sections of the characteristic."

"It will."

"Hang on a minute," said Dick. "You haven't drawn any bias cycles in the right-hand remanence waveform. What's happened to them?"

"They disappear after the tape leaves

Tape transfer characteristic

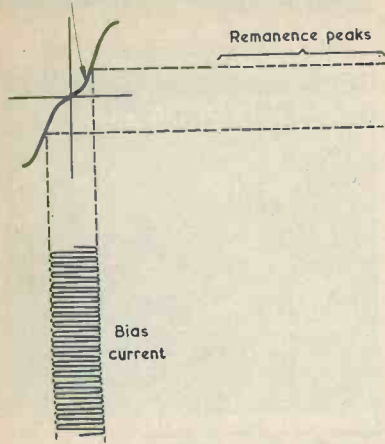


Fig. 7 (a) A high frequency current applied to the tape transfer characteristic

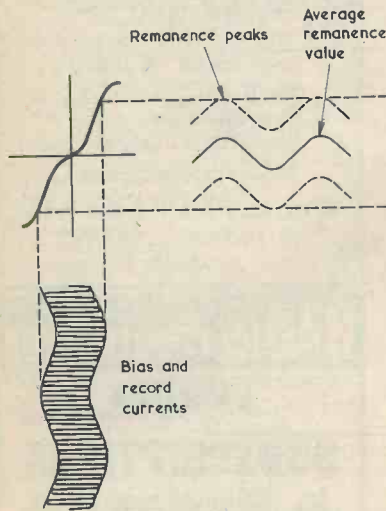


Fig. 7 (b) When an a.f. sine wave is added to the bias current the average remanence value on the tape is similarly a sine wave. In practice, the bias frequency will be higher than indicated here, and the peaks closer together

MYSTERY SOLVED

"What's wrong with that? Why buy shoe laces when there's a cheaper alternative available?"

"Do you know, Smithy," commented Dick, "you're just a walking electronic store-room. When you get undressed at night, you must need a box spanner and a soldering iron to get everything undone."

Smithy made no reply and glowered at his assistant.

"Oh, well," stated that worthy airily, "since we've finished talking about tape recorders, there seems to be nothing left for me to do but to resume my hunt for those four crocodile clips of mine."

"I'll return them to you," remarked Smithy unguardedly, "when I get my trousers back from the cleaners."

"You'll do what?" stuttered Dick. "Don't tell me that you're wearing crocodile clips as well."

An embarrassed expression crossed over Smithy's face.

"It so happened," he explained reluctantly, "that the zip fastener on my trousers broke yesterday afternoon just before I was leaving the Workshop. I've now got the two flaps joined together by those crocodile clips equi-spaced on the inside!"

And even Smithy, student of human character that he was, had to confess himself completely dumbfounded as his assistant broke into a full minute of uncontrollable and hysterical - sorry, hysterical - laughter.

the record head," explained Smithy. "Audio recording tape has a self-demagnetising effect at very high frequencies and so it cannot retain the bias cycles."

"Stap me," remarked Dick. "Why, this is really fascinating. What the a.c. bias does is to put the recording signal on to the linear sections of the transfer characteristic whilst the tape is actually passing the record head. After that, it quietly fades away from the scene."

"Precisely," concurred Smithy, pushing his note-pad away from him with a purposeful gesture. "And that finally explains why a.c. bias allows low-distortion recordings to be obtained on magnetic tape."

He rose and drained his mug, then glanced down irritably at his assistant.

"And I wish," he added severely, temporarily forgetting his own sartorial shortcomings "that those horrible pants of yours would quietly fade away from the scene as well. They're most unsuitable."

"At least," retorted Dick, irritated by Smithy's insistence on the unsatisfactory nature of his trousers, "they are proper clothes and not just bits and pieces held together with wire and components like you wear. Hello, I've just noticed something else."

Dick peered down at Smithy's smartly polished brown shoes.

"What have you seen now?" "It's those shoes of yours," breathed Dick incredulously. "They aren't tied up with laces at all. They're tied up with lengths of brown p.v.c. wire!"



Yell out to dad something's wrong with the TV and watch his face when he comes through the door!

WATFORD

ELECTRONICS

35 CARDIFF ROAD WATFORD HERTS

MAIL ORDER. POST & PACKING 10p ON ORDERS UNDER £2 CALLERS SATURDAYS ONLY 10.30 a.m.—5.30 p.m.

RESISTORS

High stability, low noise, carbon film resistors
Tubular Miniature High Power Resistors.

Power Watts	Tolerance	Range	Values Available	Price 1-99 100+
1/4	5%	2.2-2.2M	E12	1p 0.8p
1/2	5%	2.2-10M	E12	1p 0.8p
1	5%	2.2-10M	E12	2p 1.5p
4	10%	1-10 ohm	E12	6p

Quantity prices available for any selection.

Ignore fractions on total order.

CAPACITORS

ELECTROLYTICS, GENERAL PURPOSE, MINIATURE
AXIAL LEAD.

MULLARDS 015, 016, 017 SERIES.

1uf 63V 6p	10uf 63V 6p	150uf 25V 6p
1.5uf 63V 6p	15uf 63V 6p	220uf 25V 11p
2.2uf 63V 6p	22uf 63V 6p	470uf 25V 13p
3.3uf 63V 6p	47uf 63V 6p	680uf 25V 20p
4.7uf 63V 6p	100uf 40V 6p	1000uf 25V 25p
6.8uf 63V 6p		

POLYESTER FILM CAPACITORS.

MULLARDS C296 SERIES.

400V DC.

uf: 0-001, 0-0015, 0-0022, 0-0033, 0-0047, 0-0068, 0-01, 0-015, 0-022, PRICE EACH 2 1/2 p.

uf: 0-033, 0-047, 0-068, 0-1 PRICE EACH 4p.

uf: 0-15 price 6p, 0-22 price 7p, 0-33 price 10p

uf: 0-47 price 13p.

160V DC.

uf: 0-1, 0-15 price 4p, 0-22 price 5p, 0-33 price 6p, 0-47 price 7p

0-68 price 10p, 1-0 price 13p

MULLARDS C280 SERIES. P.C. MOUNTING.

400V DC

uf: 0-01, 0-015, 0-022 price 3p, 0-033, 0-047 price 4p.

250V DC

uf: 0-068, 0-1, 0-15 price 4p, 0-22, 0-33 price 5p,

uf: 0-47 price 7p, 0-68 price 10p, 1-0 price 11p.

CERAMIC CAPACITORS

WORKING VOLTAGE 50V DC, Plaquette body with 25mm leads.
Range: 22pf-10,000pf price each: 2p.

JACK PLUGS AND SOCKETS

Standard screened	12p	2.5 mm screened	8p
Stereo screened	30p	3.5 mm screened	10p
Standard socket	12p	2.5 mm sockets	7p
Stereo sockets	15p	3.5 mm sockets	7p

DIN PLUGS

2 pin, 3 pin, 5 pin
(180° or 240°) plugs
12p, sockets 8p.

SWITCHES

Toggle Single Pole Single Throw 15p
Toggle Double Pole Double Throw 18p
Slide Switch 10p

SEMICONDUCTORS.

TRANSISTORS:

AC 125	12p	BC 109	8p	OC 35	40p
AC 126	12p	BC 147	12p	OC 42	10p
AC 127	12p	BC 148	12p	OC 44	10p
AC 128	12p	BC 149	12p	OC 45	10p
AD 161	30p	BD 131	60p	OC 70	10p
AD 162	30p	BD 132	60p	OC 71	10p
AF 114	12p	BF 194	15p	OC 72	10p
AF 115	12p	BF 195	15p	2N2926R	9p
AF 116	12p	BFY50	22p	2N29260	9p
AF 117	12p	BFY51	22p	2N2926V	9p
BC 107	8p	OC 26	40p	2N2926G	10p
BC 108	8p	OC 28	40p	2N3055	55p

ZENER DIODES

BZY88 Series. Power Dissipation 400mW. 5% tolerance.
Range: 3.3V to 30V. Price 12p each.

LINEAR IC'S (DIL packaging).

709 30p DIL Sockets. 14 and 16 pin. Price 15p each.
741 32p 8 pin. Price 23p
723 80p

DIODES & RECTIFIERS.

OA 85 7p IN4148 6p
OA 90 5p BYZ10 6amp 800V 20p
OA 91 5p BYZ13 6amp 200V 16p
1N4001 6p.
1N4004 7p Bridge Rectifier
1N4007 8p W01 1A 100V price: 35p.

POTENTIOMETERS

Carbon Track 1K-2M, log or linear, Single Gang, price 12p.

5K-2M, log or linear, Dual gang, price 37p.

5K-2M, log or linear, Single gang with switch 24p.

Knobs for above: 8p each

High Quality Professional Knobs

Alluminium Small 10p Black (1") with chrome rim 15p

SLIDER POTENTIOMETERS

SINGLE 10K, 25K, 50K, 100K, log or linear price: 35p

DUAL GANG 10K+10K, etc above values, log or linear price 50p
KNOBS for above price 10p

PRESET POTENTIOMETERS SKELETON.

Horizontal or vertical mounting, 0-25W Miniature.

Price: 5p each.

VEROBOARD

	0-1	0-15
	MATRIX	MATRIX
2 1/2 x 3 1/2	22p	16p
2 1/2 x 5	24p	24p
3 1/2 x 3 1/2	24p	24p
3 1/2 x 5	27p	27p
17 x 2 1/2	75p	57 1/2 p
17 x 5 (plain)		82p
17 x 3 1/2 (plain)		60p
17 x 2 1/2 (plain)		42p
Pin insertion tool	52p	52p
Soft face cutter	42p	42p
Pkt of 50 pins	20p	20p

HEAD PHONES: Hosi-
den 'STEREO' DH-02V-
S 8ohm, individual volume
and tone control, Soft Ear
Padding, Light weight.
Price: £2.85 only, p & p
15p.

**COMPACT CASSET-
TES:** EMI make, excellent
sound reproduction, low
noise. C60 45p, C90 55p,
C120 75p

DC POWER SUPPLIES

Variable D.C. O/P:
3, 4.5, 6, 7.5, 9, 12v
Current 300—500 mA
Price: £3.50 only p & p 15p

POST THIS COUPON FOR
CATALOGUE

Please enclose 10p stamps for
catalogue which contains
details of items listed in this
advert, and more. (Catalogues
are free with order of £2 or
more.)

TO: WATFORD ELECTRONICS, 35 CARDIFF ROAD, WATFORD,
HERTS., ENGLAND.

NAME

ADDRESS

LOUDSPEAKER BARGAINS



Fane pop 100 watt 18" 8/15 ohm	£21.45
Fane pop 60 watt 15" 8/15 ohm	£12.26
Fane pop 50 watt 12" 8/15 ohm	£10.17
Fane pop 25/25 watt 8/15 ohm	£5.94
Fane pop 15 12" 15 watt 8/12 ohm	£4.40
Fane 122/10 a or 122/12	£9.90
Fane Crescendo 15" 8 or 15 ohm	£27.50
Fane Crescendo 12" 8 or 15 ohm	£24.20
Fane 8" d/cone 808T 8 or 15 ohm	£2.64
Fane 8" d/cone, roll surr. 807T, 8 or 15 ohm	£3.16
Baker Group 25 3, 8 or 15 ohm	£6.00
Baker Group 35 3, 8 or 15 ohm	£7.50
Baker De Luxe 12" d/cone	£9.62
Baker Major	£7.50
EMI 13 x 8, 3, 8 or 15 ohm	£2.25
EMI 13 x 8 type 150 d/cone 3, 8 or 15 ohm	£2.58
EMI 13 x 8 type 450 /tw 3, 8 or 15 ohm	£3.85
EMI 13 x 8 type 350 8 ohm	£3.25
EMI 63" 93850 4 or 8 ohm	£2.80
Elac 9 x 5 RM 109 15 ohm	£2.53
Elac 9 x 5 59 RM 114 8 ohm	£2.53
Elac 63" d/cone 6 RM 220 8 ohm	£2.59
Elac 4" d/cone roll surr. 6 RM 171 8 ohm	£3.22
Elac 4" tweeter TW4 8 or 15 ohm	£1.21
Celestion PS3 for Unilux	£2.16
Celestion MF 1000 25 watt horn 8 or 15 ohm	£10.45
Elac 5" 3 ohm	£1.75
Elac 7" x 4" 3 or 8 ohm	£1.52
Elac 8" x 5" 3, 8 or 15 ohm	£1.93
Wharfedale Bronze 8 RS/DD	£3.11
Wharfedale Super 8 RS/DD	£5.50
Wharfedale Super 10 RS/DD	£9.80
Goodmans 8P 8 or 15 ohm	£13.80
Goodmans 10P 8 or 15 ohm	£4.49
Goodmans 12P 8 or 15 ohm	£11.55
Goodmans 15P 8 or 15 ohm	£17.05
Goodmans 18P 8 or 15 ohm	£29.70
Goodmans Twinaxiom 8	£6.79
Goodmans Twinaxiom 10	£7.61
Goodmans Axent 100	£6.60
Eagle DT 33 dome tweeter 8 ohm	£4.95
Eagle HT 15 tweeter 8 ohm	£3.46
Eagle CT 5 tweeter 8 ohm	£1.21
Eagle MHT 10 tweeter	£3.30
Eagle CT 10 tweeter	£1.92
Eagle X overs CN 23, 28 216	£1.10
Kef T27	£4.67
Kef T15	£5.50
Kef B 110	£5.16
Kef B 200	£7.42
Kef B 139	£10.72
Kefkit 2	£24.75
Richard Allan 12" d/cone 3 or 15 ohm	£2.20
Richard Allan 8" 3, 8 or 15 ohm	£2.27
10" x 6" 3, 8 or 15 ohm	£1.92
8" x 5" 3 or 8 ohm	£1.38
7" x 4" 3 or 8 ohm	£1.38
3" 8 ohm or 80 ohm	£0.65
23" 64 ohm	£0.65
Speaker matching transformer 3/8/15 ohm	£1.10
Adastra Hiten 10" 10 watt 8 or 15 ohm	£2.80
Adastra Top 20 12" 25 watt 8 or 15 ohm	£6.32

STEPHEN SPEAKER KITS AND CABINETS

send for illustrated brochure and list of recommended speakers.

CAR STEREO SPEAKERS - ask for leaflet

PA/Disco amplifiers: (carr. and ins. (£1.00))	
Baker 100 watt	£46.00
Linear 30/40	£25.00
Linear 40/60	£30.00
Linear 80/100	£50.00

FREE with speaker orders over £7 "HiFi Loudspeaker Enclosures" book

All units guaranteed new and perfect.
Prompt despatch.
Carriage and insurance 25p per speaker.
(Tweeters and Crossovers 15p each).

WILMSLOW AUDIO

DEPT RC

SWAN WORKS, BANK SQUARE,
WILMSLOW, CHESHIRE. SK91HF



THE RADIO AMATEUR OPERATOR'S HANDBOOK

12TH EDITION - FULLY REVISED

MAKE SURE OF YOUR COPY NOW!



80 PAGES ONLY 45p

P. & P. 6p

- ★ AMATEUR PREFIXES
 - ★ AMATEUR CODES
 - ★ LOCAL TIME CONVERSIONS
 - ★ 8 MAPS
 - ★ FREQUENCY/WAVELENGTH CONVERSION TABLES
 - ★ POST OFFICE REGULATIONS
- MANY OTHER ESSENTIAL ITEMS**

Post this coupon, together with P.O. for 51p (to include postage) to DATA PUBLICATIONS, 57 MAIDA VALE, LONDON, W9 1SN

Please send me the New Edition of "THE RADIO AMATEUR OPERATOR'S HANDBOOK" DATA BOOK No. 6

I enclose cheque/crossed postal order for

NAME

ADDRESS

BLOCK LETTERS PLEASE

RADIO & ELECTRONICS CONSTRUCTOR

SMALL ADVERTISEMENTS

Rate: 4p (9d) per word. Minimum charge 60p (12/-).
Box No. 10p (2/-) extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W9 1SN

CATALOGUE NO. 18, containing credit vouchers value 50p, now available. Manufacturers new and surplus electronic and mechanical components, price 23p post free. Arthur Sallis Radio Control Ltd., 28 Gardner Street, Brighton, Sussex.

BUILD IT in a **DEWBOX** robust quality plastic cabinet 2 in. x 2½ in. x any length. S.A.E. for details. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. Write now - right now.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p. with free Fault Finding Guide. Catalogue 15p. Please send S.A.E. with all orders/enquiries. Hamilton Radio. 47 Bohemia Road, St. Leonards-on-Sea, Sussex. Telephone Hastings 29066.

WANTED: Early books on wireless, pre-1925. Details to Box No. G198.

DIRECT FROM MANUFACTURER - a comprehensive catalogue of UHF & VHF/FM aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.I.Y. enthusiast. Complete with useful installation hints. Send 3p stamp to: **CLAYDEW ENTERPRISES (RE)**, 261 Hardest Street, London S.E.24.

EXPERIMENTERS, MODEL MAKERS & CONSTRUCTORS. Hundreds of unusual items cheap. Catalogue 5p. Grimsby Electronics, 64 Tennyson Road, Cleethorpes, Lincs., DN35 7LF. (Mail order only).

CHROMASONIC ELECTRONICS. New list 10p. post free. Data Dept., 56 Fortis Green Road, London, N10 3HN.

VERNITRON CERAMIC RESONATORS for i.f. filtering. FM4, 10.7MHz (bandwidth 235kHz), matched pair £1.50. 455kHz types: TF-01A, 38p; TO-02A, 45p; TF-04 442, 40p; TFN-3A kit, £1.50; TFN-3ADX, £1.50; TF-2D5, 40p. Data supplied with orders. Mail order only. U.K. post 5p. **AMATRONIX LTD.**, 396 Selsdon Road, South Croydon, Surrey, CR2 0DE.

THE BRITISH AMATEUR ELECTRONICS CLUB. A club for all who are interested in electronics as a hobby. Quarterly Newsletter sent free to members. Subscription 50p per year. Details from Hon. Secretary, J. G. Margetts, 17 St. Francis Close, Abergavenny, Mon.

FOR SALE: VHF KIT, 80 - 180 MHz. Receiver, tuner, converter. World wide sales. Incomparable. £4.00 or s.a.e. for literature. Johnsons (Radio C), Worcester WR1 2DT.

5 N-CHANNEL FETS TYPE 3819E for £1.00. Full spec. devices complete with circuit details for building voltmeter, timer, ohmmeter, etc., or send 10p for full list of FETS and other top quality transistors available at bargain prices. Redhawk Sales Ltd., 45 Station Road, Gerrards Cross, Bucks. Mail order only.

(Continued on page 597)

APRIL 1973

BENTLEY ACOUSTIC CORPORATION LTD.

The Valve Specialists

The Old Police Station, Gloucester Road, LITTLEHAMPTON Sussex. PHONE 6743

OA2 .30	12K5 .50	EABC80	EL84 .21	PD500 1.44	UF89 .27
OB2 .30	12K7GT .34	EAF42 .48	EL85 .40	PEN45 .40	UL41 .54
5U4G .30	12QGT .34	EL91 .50	EL86 .38	PEN45DD	UL84 .28
5V4G .33	19A05 .24	EB34 .20	EL92 .23	PFL200.50	UY41 .38
5Y3GT .25	20P6 .89	EB91 .10	EL93 .25	PL36 .46	X41 .50
5Z4C .33	30A5 .64	EB91 .10	EL94 .25	PL81 .42	AC165 .25
6A0Q5 .21	30C15 .55	EB91 .10	EL95 .25	PL82 .28	AD140 .36
6AT6 .18	30C17 .74	EBF31 .30	EM80 .37	PL83 .30	AD149 .50
6AU6 .19	30C18 .58	EBF33 .30	EM84 .31	PL84 .28	AD161 .45
6AV6 .28	30F1 .57	EBF89 .26	EM87 .34	PL501 .60	AD162 .45
6BE6 .20	30FL1 .58	EC22 .34	EM88 .37	PL508 .90	AF114 .25
6BH6 .43	30FL2 .58	ECC35 .95	EM89 .26	PL509 .75	AF115 .15
6B6 .39	30FL4 .66	ECC81 .16	EM89 .26	PL509 .75	AF126 .18
6BR7 .79	30L15 .55	ECC82 .19	EM81 .37	PL5372 .50	AF127 .18
6BW6 .72	30L17 .65	ECC83 .21	EM83 .75	PL501 .60	AF128 .18
6BW7 .50	30P12 .69	ECC84 .28	EM84 .31	PL501 .60	AF128 .18
6BZ6 .31	30P19 .55	ECC85 .32	EM87 .34	PL501 .60	AF128 .18
6C4 .28	30PL1 .57	ECC88 .35	EM87 .34	PL501 .60	AF128 .18
6C4 .28	30PL13 .75	ECC88 .35	EM87 .34	PL501 .60	AF128 .18
6E5 .55	30PL14 .62	ECC82 .25	EM87 .34	PL501 .60	AF128 .18
6F1 .59	30PL15 .87	ECC85 .64	EM87 .34	PL501 .60	AF128 .18
6F18 .45	35A3 .48	ECC86 .50	EM87 .34	PL501 .60	AF128 .18
6F23 .65	35L6GT .42	ECC87 .50	EM87 .34	PL501 .60	AF128 .18
6F28 .60	35W4 .23	ECC88 .35	EM87 .34	PL501 .60	AF128 .18
6HG0T .15	35Z4 .24	ECC89 .32	EM87 .34	PL501 .60	AF128 .18
6K7 .10	35Z4 .24	ECC90 .27	EM87 .34	PL501 .60	AF128 .18
6K8G .16	50C5 .52	ECC91 .37	EM87 .34	PL501 .60	AF128 .18
6L6GT .39	50L6GT .45	ECC92 .28	EM87 .34	PL501 .60	AF128 .18
6Q7GT .43	90C1 .59	ECC93 .52	EM87 .34	PL501 .60	AF128 .18
6R7M .43	90C2 .70	ECC94 .54	EM87 .34	PL501 .60	AF128 .18
6V6GT .27	DAF91 .20	ECC95 .33	EM87 .34	PL501 .60	AF128 .18
6X4 .20	DAF96 .33	EF22 .63	EM87 .34	PL501 .60	AF128 .18
7Y4 .60	DP91 .14	EF41 .58	EM87 .34	PL501 .60	AF128 .18
9D7 .78	DF96 .34	EF80 .21	EM87 .34	PL501 .60	AF128 .18
10F1 .75	DK91 .26	EF83 .54	EM87 .34	PL501 .60	AF128 .18
10F18 .35	DK92 .35	EF85 .25	EM87 .34	PL501 .60	AF128 .18
12A6 .63	DK96 .35	EF86 .27	EM87 .34	PL501 .60	AF128 .18
12AC6 .40	DL92 .23	EF89 .23	EM87 .34	PL501 .60	AF128 .18
12AE6 .48	DL96 .35	EF91 .17	EM87 .34	PL501 .60	AF128 .18
12AT6 .23	DY87/6 .22	EF92 .28	EM87 .34	PL501 .60	AF128 .18
12AU5 .21	DY802 .29	EF183 .25	EM87 .34	PL501 .60	AF128 .18
12AV6 .28	E80CC1 .65	EF184 .27	EM87 .34	PL501 .60	AF128 .18
12BA6 .20	E809 .120	EF189 .34	EM87 .34	PL501 .60	AF128 .18
12BA6 .20	E88CC .60	EL34 .32	EM87 .34	PL501 .60	AF128 .18
12BE6 .30	E180F .90	EL41 .53	EM87 .34	PL501 .60	AF128 .18
12J7GT .33	EA50 .27		EM87 .34	PL501 .60	AF128 .18

All goods are unused and boxed, and subject to the standard 90-day guarantee. Terms of business: Cash or cheque with order only. No C.O.D. orders accepted. Despatch charge 9p per order up to three items, each additional item 3p extra. Orders over £5 despatched free. All orders despatched same day by first class mail. Complete catalogue with conditions of sale 7p post paid. Any parcel insured against damage in transit for only 3p extra per order. Business hours 9 a.m.-5.30 p.m., Mon.-Fri. Closed Sats. Please enclose S.A.E. with all enquiries.

Learn to understand electronics for your hobbies

1. Lerna-Kit course

Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered.

- (1) BUILD AN OSCILLOSCOPE.
- (2) READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS.
- (3) CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK.

2. Become a Radio-Amateur

Learn how to become a radio-amateur in contact with the wide world. We give skilled preparation for the G.P.O. licence.

FREE! Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY, CHANNEL ISLANDS.

NAME _____
ADDRESS _____

BLOCK CARS PLEASE

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	..	20p
DTB4 Transistor & Valve circuitry for D.P. Coils	..	20p
DTB9 Valve Type Coil Pack Application circuitry	..	20p
MD.1 Decoder Circuitry for Stereo Reception	..	21p

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers

NEW STYLE SELF-BINDER

for
"Radio & Electronics
Constructor"



The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached

to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

PRICE
75p
Plus 7p V.A.T.
P. & P. 14p

Available only from:—

Data Publications Ltd. 57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 595)

BUILD THE MULLARD C.C. TV CAMERA. Complete kits now available from Crofton Electronics. Send large s.a.e. for details to: 15-17 Cambridge Road, Kingston-Upon-Thames, Surrey. Reply by post. No callers please.

WANTED: Copy of the original RTTY Manual produced by the British Amateur Radio Teleprinter Group. Box No. G206.

"WORLD RADIO TV HANDBOOK" 1973, £2.90 "HOW TO LISTEN TO THE WORLD", £2.00. CONFIDENTIAL FREQUENCY LIST, stations' QSL policies, etc., £1.80. Callbooks: USA £3.95, rest of world £3.10, British Isles 70p. First class post included. David McGarva, Box 114 (REC), Edinburgh, EH1 1HP.

PRICE BREAKTHROUGH. Brand new transistors. Mullard OC42, OC76, OC77, all at 6p each. Mullard OC23, 23p. Unijunction UT46, 25p, equivalent to 2N2646, BEN300. Diode eqvts., 1N914, 2p, OA91, 3p. Guaranteed. Nek Electronics, 28 Carnegie Road, St. Albans, Herts.

"DIGITAL COMPUTER LOGIC & ELECTRONICS". Four volume self-instructional course. £2.95 including p. & p. Money back guarantee. Cambridge Learning (RC), 8a Rose Crescent, Cambridge.

FOR SALE: Foulsham-Sams & other Radio & T.V. books. as new. Half current price. Box No. G210.

COMPONENTS GALORE. Pack of 500 mixed components, manufacturers' surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., pots, coils, etc. Tremendous value. Send £1 plus 10p p. & p. Caledonian Components, Strathmore Road, Thornton, Fife.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:- The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £2.00 per annum. (U.K. and British Commonwealth), overseas 6 Dollars or £2.50. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.


TESTED SILICON NPN TRANSISTORS, like BC108. 4 for 12p, 10 for 25p. S.A.E. please. Box No. G211.

FOR SALE: Unmarked, untested diodes, BA144, OA91, BZY88, 100 for 50p. Silicon planar transistors, ZTX300, BC107/8/9 types, 50 for 50p. Reed switch inserts 5p, 10 for 40p. Selenium solar cells 10p. Marked tested components: IN4007 rectifiers 15p, 5 for 50p. BC108C 6p, 10 for 50p. Post 5p. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

SHEET METALWORK. 12/14/16/18/s.w.g. Alumin/M-steel. Quotations - sketch plus s.a.e. Assorted component parcels, £1.50 post paid, (£6 value), try one. M.R. guarantee. M.S.K. Electro, 7 Shap Drive, Warndon, Worcester.

(Continued on page 599)

APRIL 1973

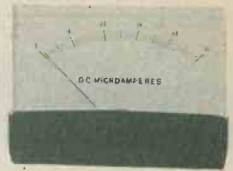

MULTIMETER Model 200H, 20,000 ohm/volt £4.80. 30µA, 50µA or 100µA METERS £2.50.

POTENTIOMETERS Lin or Log 12p; with DP Switch 24p; Dual Ganged 36p; Special offer 5K with DP switch 16p. JB3 Junction Box £1.20; JB 11 £1.95. 500µA TUNING METERS 50p. CARTRIDGES: Compatible ACOS GP91-3 90p; Stereo GP93-1 £1.15. CAPACITORS 100mF 25v 5p; 220mF 25v 5p; 400-200-50-16mF 300v 30p; 0.1 500v DC 300v AC 4p. MINIATURE INDICATOR LAMPS (5 colours) 11p; 6 or 12v Bulbs for above 4p. MAINS NEONS panel mounting (red, green, clear) 15p. HEADPHONES: High Impedance (2,000 ohm) 90p; STEREO 8 ohm £1.95; Stereo/Mono 8/16 ohm £2.10. RECORDING TAPE; 5" LP 900ft. 45p; 5 1/2" LP 1,200ft. 60p; 7" LP 1,800 ft. 81p.

Large S.A.E. for List No. 5. Special Prices for quantity quoted on request. Add 10p for P&P on orders under £5.

M. DZIUBAS

158 Bradshawgate, Bolton, BL2 1BA. Lancs.

FREE TO AMBITIOUS ENGINEERS

THE LATEST EDITION OF NEW OPPORTUNITIES

SEND FOR YOUR FREE COPY TO-DAY

NEW OPPORTUNITIES is a highly informative 76 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern home study courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics courses administered by our Specialist Electronics Training Division - explains the benefits of our free Appointments and Advisory service and shows you how to qualify for five years promotion in one year.

PRACTICAL EQUIPMENT INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with all the practical equipment you need, plus basic practice and theoretical Courses for beginners in Radio, TV, Electronics, etc.

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

AMSE (Elec) City & Guilds Certificate RTEB Certificate
Radio Amateurs' Exam DMG Certificate Colour TV
Electronic Engineering Computer Electronics Radio and TV
Servicing Practical Electronics Practical TV and Radio

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. (BRE 16), Aldermaston Court, Reading RG7 4PF
Accredited by the Council for the Accreditation
of Correspondence Colleges

QC BRE 16

NAME
(BLOCK CAPITALS PLEASE)

ADDRESS.....

OTHER SUBJECTS..... AGE.....

COMPUTER SURPLUS

Calvern Precision Pots. Full Range. Beckman 100k 2-gang gold-plated contacts. Metal Rects: LT, HT. Diodes, Relays.

1,000 B9A valves, special valves 12E1, 5R4GY. G400/1k. 5B/255M, QS150/45. QS10CQE, GS10CAF.

TRANSISTOR COMPONENTS

Voltmeters, oscilloscopes, power packs. 10 types mains trans.

RADIO AND TELEVISION COMPONENTS

100 boxed alloy chassis with components, size 9"x3"x3", 17"x8"x3", 17"x12"x7". Steel 16"x15"x1½". Side plates available. Chrome handles 3", 6", 12" 6, 10, 32 way plugs and skts., multi-coloured cable for above. Toggle switches, wafer switches, chrome panel lights, neon panel lamps, clear and coloured. 6.3v FIL. transformers. Special mains transform 250-0250, 430-390.0, 390-450. C350 M/A LT. 6.30, 6.3 1 amp, 180-180 100 M/A. 6.30, 6.3 4 amp, 2.5. 02.5 4 amp.

ALL PRICES ON APPLICATION

A. T. GREENER, 141 CROFTON LANE,
ORPINGTON, KENT.

Telephone Orpington 31138 9 a.m. to 10 p.m.

THE 'PLUS' CATALOGUE

+ Technical data + Countless bargains + Discounts



+
25p

REFUND VOUCHER

The Electrovalue Catalogue now costs 25p (post free, surface mail) and is well worth it for its technical information. But we include with it a 25p refund voucher for spending on orders for £5 or more. You will find this catalogue a great money saver in every way.


- 96 Pages. (4th printing)
- Transistors, with technical specs.
- I.Cs with working diagrams
- Resistors, capacitors, components
- Diagrams, tables, information
- GENUINE DISCOUNTS

ELECTROVALUE LTD. Dept.
28 St. Judes Rd., Englefield Green, Egham, TW20 0HB R.C.4
9-6 daily: 1.0 p.m. Sat. Telephone Egham 3603

PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines

(max. format 7½" x 9½")

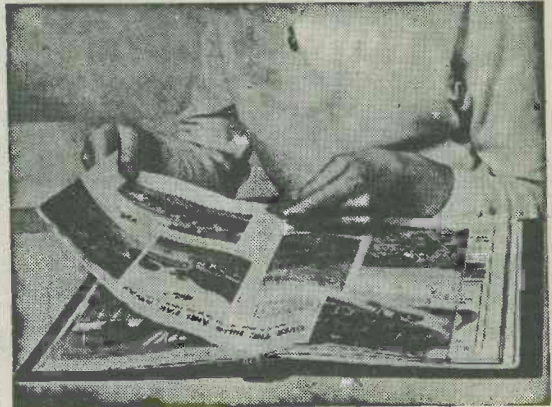

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE **70p** P. & P. 14p

Plus 7p V.A.T.

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 597)

SHORT WAVE MAGAZINE, now in its 36th year and published monthly, covers the whole field of Radio Amateur transmission and reception including regular news features (DX, VHF, Clubs and SWL) and the design, construction and operation of Amateur Radio equipment of every type. Cover price 25p at newsagents. Specimen copy 30p post free, first class. Annual subscription £3.00 (or £2.75 second class posting) year of 12 issues. Circulation Dept. (R), Short Wave Magazine Ltd., 55 Victoria Street, London, SW1H-0HF. Telephone: 01-222-5341/2.

WANTED: Radio & TV service manuals 1955 onward. Brotherton, 3 Forge End, Stapleford, Cambridge. Telephone: Shelford 3587.

IRISH READERS. Up to 20% off stereo amplifiers, tuners, decks, speakers, etc. Free catalogue from: **Beirne Bros.** (RC), 13 Auburn Terrace, Athlone, Co. Westmeath, Ireland.

"MEDIUM WAVE NEWS" Monthly during Dx season - Details from: **K. Brownless**, 7 The Avenue, Clifton, York.

Radio Constructor and *Practical Wireless*, 1969-1972. *Motor Sport*, 1961-1968. *Science Journal*, 1965-1967. Single issues for sale. Reasonable prices. All enquiries answered. **G. Charnley**, 18 Nether Street, Finchley, London N12 7NL.

FOR SALE: Heathkit I0-18U 5" laboratory oscilloscope, £29. IG-82U sine-square generator 20Hz-1MHz, £19. Both in mint condition, fully operational, complete with manuals. **McCullough**, 373 Old Holywood Road, Redburn, Holywood, Co. Down, N.Ireland.

FOR SALE: The Bandmaster, 20-80 Metres plus 194-580M. Plug-in Denco coils. As described in *The Radio Constructor*, August 1971. Working, requires alignment. £10 inc. Browns phones. S.A.E.: **Blackwood**, Oast Cottage, Kemsing, Sevenoaks, Kent.

ARE YOU 17 OR UNDER AND A DX-ER? If so, why not join the Youth DX-Club International. Full details from: **Bartletts**, Culmstock, Cullompton, Devon.

FOR SALE: New Emsac 2M converter, I.F. 28-30MHz. £16. **Oats**, 13 Bevan Rise, Trethomas, Mon.

WORLD DX CLUB covers all aspects of SWling on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.38 a year. Enquiries to Secretary, **WDXC**, 11 Wesley Grove, Portsmouth, Hants., PO3 5ER.

BURGESS K series double-break Microswitches, two circuit 25 amps up to 250 volts AC, 15 amps up to 460 volts AC, in boxes of ten, £2.50 post 15p. **STROBOSCOPE FORKS**, 125 cycles, £1.50 post paid. **FREQUENCY METERS**, 45/55 c.p.s., 230 volts AC, 6 inch diameter flush round, £10 each, post 70p. **MEGGERS**, 500 volts range, 0-1000 Meg ohms - infinity, metal case, in good working order, £15 each, post 70p. **BRIDGE MEGGERS**, series 1, 1,000 volts range 0-Meg ohms - infinity, complete with resistance box 0/9999 ohms in sealed case, £70 each, carriage £1. **POWER FACTOR AND WATTAGE UNITS** for model 7 Avometers, fitted PF sockets, £7.50 each, post 65p. **MINIATURE DIGITAL INDICATOR**, size of digits $\frac{1}{8}$ inch, illuminated by 28 volt lamps reading 0 through 9 with decimal points, £3 each, post paid, send for illustrated details. **L. Wilkinson (Croydon) Ltd.**, Longley House, Longley Road, Croydon, Surrey. Telephone: 01-684-0236.

APRIL 1973

SYNTHESISER MODULES

Voltage-controlled modules for synthesiser construction and other musical MIRACLES! Catalogue 15p. **D.E.W. Ltd.**, 264 Ringwood Road, Ferndown, Dorset.

MORSE MADE EASY!!!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.) Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. **18-W.P.M.** in 4 weeks guaranteed. **Beginner's Section only £3.30. Complete course £4.50 (Overseas £1 extra).** Details only, 4p stamp. **01-660 2896**

G3HSC/Box 38, 45 GREEN LANE, PURLEY, SURREY.

FREQUENCY LIST TRANSFERS

We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p, five sheets for 10p, postage 3p.

DATA PUBLICATIONS LTD.,
57 Maida Vale, London W9 1SN.

Get paid for your hobby!

Become an expert in Radio, Television and Electronic Engineering.

Take an ICS home study course, specially designed to help you gain the qualifications that will entitle you to higher pay and a more interesting career.

ICS individual tuition has a long-standing reputation for success in these important examinations: C & G Telecommunications Certs., Radio Amateurs Examination, General Radiocommunications Certs., C & G Radio Servicing Theory.

Alternatively, you can choose an ICS colour/mono T.V. servicing course or practical radio and electronics courses that provide essential practical experience *as you build*. Transistor portable receivers, signal generators, multi-test meters. And whatever you build is *yours to keep*. All components are supplied **PLUS** expert coaching in basic electronic theory and practice.

Post this coupon *today* for a **FREE** Course Guide and find out how to turn your hobby into money.

Please send me, without obligation, my **FREE BOOKLET** on Radio, Television and Electrical Engineering.

Name.....Age
(BLOCK CAPITALS)

Address

..... Occupation

ICS your key to the door
of opportunity

International Correspondence
Schools, Dept. 233H, Intertext
House, Stewarts Road, London
SW8 4UJ

ESSENTIAL BOOKS

HOW TO MAKE WALKIE-TALKIES FOR
LICENSED OPERATION

40p. Post & packing 10p.

The Government Surplus Wireless Equipment Handbook. Gives circuits, data, illustrations and valuable information for British/USA receivers, transmitters, trans./receivers. With modifications to sets and test equipment. Latest impression £3.25 including postage. Directory of Government Surplus Wireless Equipment Dealers. Gives full details of surplus wireless equipment stores and dealers including addresses, plus equipment and spares they have available. A valuable book. Only 35p plus 10p postage & package. (Allow 14 days for delivery.) A New Guide to Hi-Fi For Beginners. By J. R. Hey Tech.(CEI) MSERT. Before buying Hi-Fi equipment you must read this latest publication. It may save you pounds. An excellent guide to the purchase of ready made Hi-Fi equipment. Price only 40p. P. & P. 10p. Handbook of Transistor Equivalents and Substitutes. Includes many thousands of British, USA and Japanese Transistors. 78 pages. Only 40p P. & P. 5p. World's Short Wave, Medium & Long Wave Radio Stations & FM and TV Listing. 35p. P. & P. 5p. Cosmic Radio Waves. Start a new hobby - Radio Astronomy. This big book of 444 pages is an ideal handbook for the beginner and established enthusiast. Numerous photographs and illustrations. Published by Oxford University Press. Price £2.50. P. & P. 25p.

DEPT. RC. GERALD MYERS, Bookseller & Publisher.
18 SHAFESBURY STREET, LEEDS LS12 3BT

DX-TV

The 2nd edition of the illustrated booklet, "Long Distance Television" by Roger W. Bunney is now available, covering all aspects of the DX-TV hobby. Contents include: World-wide channel allocation charts, signal propagation, receiver requirements with basic modification details, aerials and preamplifiers, "off-screen" photography, station identification, test cards, etc.

The publication, costing 50p (including surface postage world-wide) is available from:

WESTON PUBLISHING
33 Cherville Street, Romsey, Hants SO5 8FB

MEN! £50p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

Pay prospects? £2,500 + p.a.

After training, our exclusive appointments bureau — one of the world's leaders of its kind — introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators Training Centre

P20, Oxford House, 9-15 Oxford Street W.1.

Telephone: 01-734-2874

127 The Piazza, Dept. P20, Piccadilly Plaza, Manchester 1

Telephone: 061-236 2935

AUTOMATIC EMERGENCY SUPPLY

250v 50Hz-150 watt Inverter. Full kit of parts excluding meter. Circuit as appeared in December P.W. Complete kit-£16.95+80p P. & P.

OTHER INVERTERS AVAILABLE IN KIT FORM

150 Watt - £13.50+60p P. & P. 75 Watt - £7.80+60p P. & P.
300 Watt - £17.90+85p P. & P. 40 Watt - £5.20+40p P. & P.
25 Watt - £2.60+20p P. & P.

All above operate from 12v. battery and give 250v-50Hz. Output. 24 volt types are also available, alternative outputs or taps can be supplied. Transformers and/or Transistors can be supplied separately.

SPECIAL OFFER

12v. Fluorescent lights, suitable for tents, caravans, houses or secondary lighting for factories, hotels, etc. 12 inch-8 watt-£3.40 post paid. 21 inch-13 watt-£4.20 post paid. Large discounts available for quantities.

TEXAN AMPLIFIER

Fibre glass P.C. board - £2.00+10p P. & P.

Transformer - £4.00+30p P. & P.

Other components including Teak Cabinet - £24.00+ Postage.

ASTRO ELECTRONICS

6, BARNES ROAD, CHESTERFIELD, DERBYSHIRE

DATA BOOK SERIES

- DB5 TV FAULT FINDING**
124 pages. Price 50p, postage 6p.
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK**
80 pages. Price 45p, postage 6p.
- DB16 RADIO CONTROL FOR MODELS**
192 pages. Price 75p, postage 8p.
- DB17 UNDERSTANDING TELEVISION**
512 pages. Price £2.10, postage 25p.
- DB18 AUDIO AMPLIFIERS**
128 pages. Price 53p, postage 6p.
- DB19 SIMPLE SHORT WAVE RECEIVERS**
140 pages. Price 80p, postage 6p.

I enclose Postal Order/Cheque for.....in payment for.....

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable from your local bookseller.

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

RESONANT FREQUENCIES I

The Table gives calculated resonant frequencies, in MHz, for tuned circuits having inductances from 0.1 to 20 μ H and capacitances of 5pF, 20pF, 80pF and 320pF. Thus, 10 μ H and 20pF are resonant at 11.2MHz.

Inductance (μ H)	5pF	20pF	80pF	320pF	Inductance (μ H)	5pF	20pF	80pF	320pF
0.1	225	112	56.2	28.1	6.0	29.1	14.5	7.27	3.64
0.2	159	79.5	39.7	19.9	7.0	26.9	13.4	6.72	3.36
0.4	112	56.2	28.1	14.0	8.0	25.2	12.6	6.30	3.15
0.7	85.1	42.5	21.3	10.6	9.0	23.7	11.9	5.93	2.97
1.0	71.2	35.6	17.8	8.90	10	22.5	11.2	5.62	2.81
1.3	62.5	31.2	15.6	7.81	11	21.5	10.7	5.37	2.69
1.7	54.6	27.3	13.6	6.82	12	20.5	10.3	5.01	2.56
2.0	50.4	25.2	12.6	6.30	13	19.7	9.85	4.92	2.46
2.5	45.0	22.5	11.2	5.62	14	19.0	9.52	4.76	2.38
3.0	41.1	20.5	10.3	5.14	15	18.4	9.20	4.60	2.30
3.5	38.1	19.0	9.52	4.76	16	17.8	8.90	4.45	2.22
4.0	35.6	17.8	8.90	4.45	17	17.3	8.65	4.32	2.16
4.5	33.6	16.8	8.40	4.20	18	16.8	8.40	4.20	2.10
5.0	31.8	15.9	7.95	3.97	19	16.3	8.15	4.07	2.04
5.5	30.4	15.2	7.60	3.80	20	15.9	7.95	3.97	1.99

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

BUILD THE TEXAN


FREE TEAK CABINET with complete kits
FEATURES New slim design with 6 - IC's, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners, Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.
HIGH QUALITY AND STABILITY ARE PREDOMINANT FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector, Mag. P.U., Radio Tuner, Aux. Can be altered for Mic. Tape, Tape head etc. (Parts list Ref. 20 on request.)
 Constructional details Ref. No. 21 30p
 Designed approved kits distributed by Henry's Radio Ltd.

SPECIAL KIT PRICE **£28.50**

Complete with FREE TEAK CABINET P & P 45p

20+20 WATT INTEGRATED I.C. STEREO AMPLIFIER

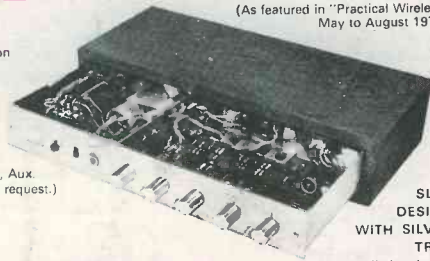(As featured in "Practical Wireless" May to August 1972)



SLIM DESIGN WITH SILVER TRIM
 Overall chassis size 14 1/2" x 6" x 2" high

ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. no 14 on request.

I.C. RECEIVER

ZN 414 Radio integrated circuit as featured in *Practical Wireless*, January 1973, *Practical Electronics*, February 1973. Price £1.20

BATTERY TAPE DECK

Garrard 9 volt Tape deck with heads, etc.. As previously advertised. Limited quantity. £9.50 post 30p.

LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish, Italian. £1.49 per course. £5.50 per set of four.

ULTRASONIC TRANSDUCERS
 Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and new I.C. circuits. PRICE PER PAIR £5.90. Post 10p.

MARRIOT TAPE HEADS 4 TRACK MONO or 2 TRACK STEREO

"17" High Impedance £2.00
 "18" Med Impedance £2.00
 "36" Med-Low Imp. £3.50
 Erase Heads for above 75p
 "63" 2 track mono - Hi Imp. £1.75
 "43" Erase Head for above 75p

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)
 XN3, XN13, GN4 0-9 Side view with data 85p
 GNP 7, GNP 8 0-9 Side view with decimal points and data 95p
 3015F 7-segment £2 each. £7 per 4 with data.
 12 and 24 hour clock circuits for above. Ref. No. 31 15p.

MINIATURE AMPLIFIER

5 transistor, 300mW o/p. Fitted volume and sensitivity control 9 volt operated. £1.75 each P/P 15p.

DISCO SPOTBANK

as illustrated on the front cover of *Practical Wireless*, April '73. £12.75 p. & p. 35p.

QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs 5K, 10K, 25K, 100K, 250K, 500K, 1 meg. Log, and Lin. 40p each. 10K, 25K, 50K, 100K, 250K. Log, and Lin. ganged. 60p each.

HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES.
 FREE 24 page detailed brochure (Ref. no. 17).
 You can see the savings!

LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
TYPE 150TC Twin cone version £2.75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.
POLISHED CABINETS 150, 150TC, 450 £4.60. Post 30p.
ASSEMBLED IN POLISHED CABINETS (50 ohms)
 Series 6 (Assembled 150TC) per pair £16.50 post 70p
 Series 8 (Assembled 450) per pair £18.95 post 70p



NEW MW/LW TUNER TO BUILD ML-3

Uses Mullard Module, Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". TOTAL COST TO BUILD £4.85. Post 15p. All parts sold separately - Leaflet No. 6.



"BANDSPREAD" PORTABLE TO BUILD

Printed circuit all-transistor design using Mullard RF/IF Module Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning. 600mW push-pull output. Fibre glass PVC covered cabinet. car aerial socket. Attractive appearance and performance. TOTAL COST TO BUILD £7.98 p.p. 32p. (Battery 22p.) All parts sold separately - Leaflet No. 2.



HENRY'S CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics - plus data, circuits and information.

10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post Paid

(40p FOR CALLERS)

PLUS FIVE 10p VOUCHERS

Send to this address - Henry's Radio Ltd. (Dept. RC), 3 Albemarle Way, London, E.C.1. for catalogue by post only. All other mail and callers to "303", see above.



HIGH QUALITY CASSETTES

The best UK low noise tapes but at a special price. "Living Sound" cassettes meet the highest international standard (IEC 94A). Full guarantee. Post paid. Made by EMI especially for Henry's

	3 for	6 for	10 for
C60	1.10	2.00	3.10
C90	1.47	2.85	4.65
C120	1.80	3.50	5.60

TEST EQUIPMENT


JUST A SELECTION

SE250B Pocket Pencil Signal Injector £1.90
 SE500 Pocket Pencil Signal Tracer £1.50
 THL33D Robust 2K/Volt. £4.55 With case £4.99
 TE15 Grid Dip Meter 440 KHz - 280 mHz £13.45
 500 30 K. Volt Multimeter £9.25. With leather case £10.50
 200H 20K/Volt Multimeter £4.20. With case £4.95
 AF105 50K/Volt Multimeter £8.50. With case £9.50
 U4341 AC/DC Multimeter with transistor tester with steel case £10.50
 TE20D RT Generator 120KHz 500MHz £15.95
 TE22D Audio Generator 20Hz 200KHz £17.50
 Carr 35p
 CI5 3" Pulse Scope 10Hz - 10mHz £39.00
 Carr 50p
 TE65 Valve Voltmeter 28 ranges Carr 40p £17.50
ALL NOMBREX MODELS IN STOCK



BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BAND-WIDTH, PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO.
 A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it - VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.
TOTAL £6.97, p.p. 20p. Decoder Kit £5.97.
 Tuning meter unit £1.75.
 Mains unit for Tuner and/or Decoder P56/12 £3.25. Post 20p.

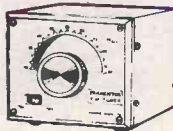

PA-DISCO-LIGHTING

UK's Largest Range - Write phone or call in. Details and demonstrations on request.

DJ30L 3 Channel sound to light unit 3Kw £29.50
 DJ40L 3 Channel Mic (built in) to light 3Kw £38.75
 DJ70S 70 watt Disco amp/mixer £49.75
 DISCOAMP 100 watt Disco amp/mixer £65.85
 DJ105S 30 watt Disco amp/mixer £32.25
 Anti-Feedback Quality Mic. £11.50
 DJ700 70 watt £52.75
 DJ500 50 watt P.A. Amp £43.95
 DJ300 150 watt rms Group Valve Amp £86.00
 ● Portable Discos - Details on request
 ● Credit terms for callers



SINCLAIR PROJECT 60 MODULES - SAVE POUNDS

Z30 £3.57 Z50 £4.37
 STEREO 60 £7.97 P25 £3.97
 P26 £6.37 P28 £4.77
 Transformer for P28 £2.95
 Active Filter Unit £4.45
 Stereo FM Tuner £16.95
 IC12 £1.80. O16's £15 p.p.
 Post etc. 20p per item.
PACKAGE DEALS Post 25p.
 2 x Z30, Stereo 60, P25 £15.95
 2 x Z30, Stereo 60, P26 £18.00
 2 x Z50, Stereo 60, P28 £20.25
 Transformer for P28 £2.95
 PROJECT 605 KIT £19.95



Huge range of transistors and semi-conductors in stock. Free brochure. Ref. 36 on request.

VAT

Prices DO NOT include Value Added Tax. From 1st April, 1973 10% must be added and shown separately to your total order (inclusive Post/packing). Help us to help you receive your order without delay.

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
 354-356 High Fidelity and Tape Equipment 01-402 5854/4736
 309 PA-Disco-Lighting High Power Sound 01-723 6963
 303 Special offers and bargains store
 All mail to 303 Edgware Road, London W2 1BW

Open: 9 am - 6 pm
 6 days a week
 (309 closed
 Thursday)
 All stores open
 all day Saturday