

RADIO & ELECTRONICS CONSTRUCTOR

JUNE 1979
Volume 32 No. 10

Published Monthly
(3rd of preceding Month)

First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone Telegrams
01-286 6141 Databux, London

© Data Publications Ltd., 1979. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £7.50, Overseas £8.50 (U.S.A. and Canada \$18.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production— Web Offset.

PP9 ELIMINATOR UNIT — A simple and inexpensive unit to fit into battery compartment of a transistor radio by M. V. Hastings	600
NEWS AND COMMENT	604
REMOTE CONTROL GARAGE LIGHT — Suggested Circuit by G. A. French	606
DESIGNING REFLEX CIRCUITS by Sir Douglas Hall, Bt., K.C.M.G.	608
TUNE-IN TO PROGRAMS Becoming Dszy by Ian Sinclair	610
IN NEXT MONTH'S ISSUE	613
SHORT WAVE NEWS — For DX Listeners by Frank A. Baldwin	614
BASIC SHORT WAVE RADIO—An uncomplicated t.r.f. design covering 1.2 to 24MHz by R. A. Penfold	616
WORKSHOP POWER SUPPLY (conclusion) by R. A. Penfold	622
NEW PRODUCT	626
DOUBLE DECCER SERIES — How to control a lamp, or a relay, by successive sound signals — by Ian Sinclair	627
THE SNIPER — (Conclusion) by E. A. Parr	629
THE "SLOW PICTURE" — The TV with a fault in time — In Your Workshop	632
RADIO TOPICS by Recorder	638
THE TRIAC — Electronics Data No. 46 For the Beginner	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

**THE JULY ISSUE
WILL BE PUBLISHED
ON 4th JUNE**

SEMICONDUCTORS

TRANSISTORS

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	£0.22	8C119	£0.25	BD183	£0.95	8PX25	£1.45	TIP418	£0.48	2N2712	£0.22
AC113	£0.20	8C120	£0.40	BD184	£1.10	8SX19	£0.18	TIP41C	£0.48	2N2714	£0.22
AC115	£0.20	8C125	£0.17	BD185	£0.88	8SX20	£0.18	TIP42A	£0.48	2N2905	£0.18
AC117	£0.30	8C126	£0.22	BD186	£0.88	8SY25	£0.16	TIP42B	£0.48	2N2904A	£0.21
AC117K	£0.34	8C132	£0.18*	BD187	£0.75	8SY26	£0.16	TIP42C	£0.48	2N2905	£0.18
AC121	£0.20	8C134	£0.18*	BD188	£0.75	8SV27	£0.16	TIP2955	£0.60	2N2905A	£0.18
AC122	£0.14	8C135	£0.15*	BD189	£0.78	8SV28	£0.16	TIP3055	£0.60	2N2908	£0.16
AC125	£0.18	8C136	£0.18*	BD190	£0.78	8SV29	£0.16	TIS43	£0.22	2N306A	£0.19
AC127	£0.18	8C139	£0.32	BD196	£0.90	8SV38	£0.19	TIS90	£0.18*	2N2970	£0.22
AC128	£0.18	8C140	£0.30	BD197	£0.95	8SV39	£0.19			2N2974	£0.22
AC128K	£0.26	8C141	£0.28	BD198	£0.95	8SV41	£0.29			2N2923	£0.15*
AC132	£0.20	8C142	£0.22	BD199	£0.99	8SV51	£0.25			2N2924	£0.15*
AC134	£0.20	8C143	£0.22	BD200	£0.99	8SV95	£0.13			2N2925	£0.15*
AC137	£0.20	8C145	£0.46	BD201	£0.80	8SV95A	£0.13	ZTK107	£0.10*	2N2926	£0.15*
AC141	£0.22	8C147	£0.07*	BD202	£0.80	8RV39	£0.45	ZTK108	£0.10*	2N2926B	£0.08*
AC141K	£0.30	8C148	£0.07*	BD201/202	£0.70	8U105	£1.45	ZTK109	£0.10*	2N2926B	£0.08*
AC142	£0.20	8C149	£0.07*	BD203	£0.80	8U105/02	£1.95	ZTK300	£0.12*	2N2926B	£0.08*
AC142K	£0.30	8C150	£0.20*	BD204	£0.80	8U204	£0.80	ZTK301	£0.12*	2N3010	£0.65
AC151	£0.20	8C151	£0.22*	BD203/204	£1.70	8U205	£1.40	ZTK302	£0.16*	2N3011	£0.16
AC153	£0.22	8C152	£0.20*	BD205	£0.80	8U208	£1.90	ZTK303	£0.16*	2N3053	£0.16
AC153K	£0.30	8C153	£0.25*	BD206	£0.80	8U208/02	£2.25	ZTK304	£0.20*	2N3054	£0.40
AC154	£0.20	8C154	£0.19*	BD207	£1.00			ZTK330	£0.15*	2N3055	£0.40
AC155	£0.20	8C157	£0.10*	BD208	£1.00			ZTK500	£0.13*	2N3391	£0.20*
AC156	£0.20	8C158	£0.10*	BD222	£0.47	E1222	£0.38	ZTK501	£0.12*	2N3391A	£0.20*
AC157	£0.25	8C159	£0.10*	BD225	£0.47			ZTK502	£0.16*	2N3392	£0.20*
AC165	£0.20	8C160	£0.26	BD232	£0.55	MAT100	£0.19	ZTK503	£0.12*	2N3393	£0.20*
AC166	£0.20	8C161	£0.22	BD233	£0.55	MAT101	£0.19	ZTK504	£0.25*	2N3394	£0.20*
AC167	£0.20	8C167	£0.12*	BD234	£0.55	MAT120	£0.19	ZTK505	£0.12*	2N3395	£0.20*
AC168	£0.25	8C168	£0.12*	BD235	£0.55	MAT121	£0.19	ZTK506	£0.12*	2N3402	£0.21*
AC169	£0.20	8C169	£0.09*	BD236	£0.55	MJ481	£0.95	ZTK507	£0.12*	2N3403	£0.21*
AC171	£0.25	8C169C	£0.10*	BD237	£0.55	MJ481	£0.95	ZTK508	£0.12*	2N3404	£0.29*
AC176	£0.18	8C170	£0.09	BD238	£0.60	MJ490	£0.95	ZTK509	£0.12*	2N3414	£0.18*
AC176K	£0.25	8C171	£0.09*	BD239	£0.60	MJ490	£0.95	ZTK510	£0.12*	2N3415	£0.18*
AC178	£0.25	8C172	£0.09*	BDY11	£1.30	MJ491	£1.15	ZTK511	£0.12*	2N3416	£0.18*
AC179	£0.25	8C173	£0.09	BDY17	£1.80	MJE340	£0.45	ZTK512	£0.12*	2N3417	£0.29*
AC180	£0.20	8C174	£0.15*	BDY20	£0.80	MJE370	£0.80	ZTK513	£0.12*	2N3614	£1.00
AC180K	£0.28	8C175	£0.35*	BDX77	£0.90	MJE377	£0.60	ZTK514	£0.12*	2N3615	£1.00
AC181	£0.20	8C177	£0.16	BF115	£0.22	MJE520	£0.45	ZTK515	£0.12*	2N3616	£1.00
AC181K	£0.28	8C178	£0.16	BF116	£0.22	MJE521	£0.65	ZTK516	£0.12*	2N3618	£1.05
AC187	£0.18	8C179	£0.16	BF118	£0.75	MJE295	£0.90	ZTK517	£0.12*	2N3646	£0.09*
AC187K	£0.28	8C180	£0.25	BF119	£0.75	MJE305	£0.80	ZTK518	£0.12*	2N3702	£0.08*
AC188	£0.28	8C181	£0.25*	BF121	£0.50*	MJE340	£0.52	ZTK519	£0.12*	2N3703	£0.08*
AC188K	£0.28	8C182	£0.09*	BF123	£0.80*	MPB113	£0.52	ZTK520	£0.12*	2N3704	£0.07*
ACV18	£0.35	8C182L	£0.09*	BF125	£0.80*	MPF102	£0.28	ZTK521	£0.12*	2N3705	£0.07*
ACV18K	£0.35	8C183	£0.09*	BF126	£0.50*	MPF104	£0.35	ZTK522	£0.12*	2N3706	£0.08*
ACV19	£0.35	8C183L	£0.09*	BF152	£0.25*	MPF105	£0.35	ZTK523	£0.12*	2N3707	£0.08*
ACV20	£0.35	8C184	£0.09	BF153	£0.25*	MPSA05	£0.20	ZTK524	£0.12*	2N3708	£0.07*
ACV21	£0.35	8C184L	£0.09*	BF154	£0.22*	MPSA06	£0.20*	ZTK525	£0.12*	2N3708A	£0.07*
ACV22	£0.35	8C186	£0.22	BF155	£0.35	MPSA65	£0.20*	ZTK526	£0.12*	2N3709	£0.07*
ACV27	£0.35	8C187	£0.22	BF156	£0.28	MPSA66	£0.20*	ZTK527	£0.12*	2N3710	£0.07*
ACV28	£0.35	8C188	£0.22	BF157	£0.28	ND120	£0.18	ZTK528	£0.12*	2N3711	£0.07*
ACV29	£0.50	8C208	£0.11*	BF158	£0.28			ZTK529	£0.12*	2N3772	£1.60
ACV30	£0.35	8C209	£0.12*	BF159	£0.28*			ZTK530	£0.12*	2N3773	£2.20
ACV31	£0.35	8C212	£0.09*	BF160	£0.30*			ZTK531	£0.12*	2N3819	£0.18
ACV34	£0.35	8C212L	£0.09*	BF162	£0.30*	DC19	£0.85	ZTK532	£0.12*	2N3820	£0.35
ACV35	£0.35	8C213	£0.09*	BF163	£0.30*	DC20	£1.85	ZTK533	£0.12*	2N3821	£0.60
ACV36	£0.35	8C213L	£0.09*	BF164	£0.30*	DC22	£1.50	ZTK534	£0.12*	2N3823	£0.60
ACV40	£0.35	8C214	£0.09*	BF165	£0.60*	DC23	£1.60	ZTK535	£0.12*	2N3903	£0.10*
ACV41	£0.35	8C214L	£0.09*	BF167	£0.24	DC24	£1.35	ZTK536	£0.12*	2N3904	£0.10*
ACV44	£0.35	8C225	£0.28*	BF173	£0.20	DC25	£1.00	ZTK537	£0.12*	2N3905	£0.10*
AD130	£0.70	8C226	£0.36*	BF176	£0.38*	DC26	£1.00	ZTK538	£0.12*	2N3906	£0.10*
AD140	£0.85	8C228	£0.18*	BF177	£0.26	DC28	£0.80	ZTK539	£0.12*	2N4007	£0.12*
AD143	£0.75	8C251	£0.18*	BF178	£0.26	DC29	£0.80	ZTK540	£0.12*	2N4008	£0.12*
AD149	£0.80	8C251A	£0.18*	BF179	£0.30	DC35	£0.90	ZTK541	£0.12*	2N4059	£0.14*
AD161	£0.35	8C301	£0.28	BF180	£0.30	DC36	£0.90	ZTK542	£0.12*	2N4060	£0.14*
AD162	£0.35	8C302	£0.29	BF181	£0.30	DC41	£0.20	ZTK543	£0.12*	2N4061	£0.12*
AD170	£0.70	8C303	£0.28	BF182	£0.30	DC42	£0.22	ZTK544	£0.12*	2N4062	£0.12*
AD180	£0.55	8C304	£0.38	BF183	£0.30	DC44	£0.24	ZTK545	£0.12*	2N4284	£0.18*
AF114	£0.25	8C327	£0.16*	BF185	£0.20	DC45	£0.20	ZTK546	£0.12*	2N4285	£0.18*
AF115	£0.25	8C328	£0.15*	BF186	£0.26*	DC70	£0.14	ZTK547	£0.12*	2N4286	£0.18*
AF116	£0.25	8C337	£0.15*	BF187	£0.26	DC71	£0.25	ZTK548	£0.12*	2N4287	£0.18*
AF117	£0.25	8C338	£0.15*	BF188	£0.40	DC72	£0.24	ZTK549	£0.12*	2N4288	£0.18*
AF118	£0.25	8C339	£0.15*	BF189	£0.40	DC74	£0.26	ZTK550	£0.12*	2N4289	£0.18*
AF124	£0.30	8C441	£0.30	BF194	£0.10*	DC75	£0.30	ZTK551	£0.12*	2N4290	£0.18*
AF125	£0.30	8C442	£0.30	BF195	£0.10*	DC76	£0.30	ZTK552	£0.12*	2N4291	£0.18*
AF126	£0.30	8C460	£0.38	BF196	£0.10*	DC77	£0.50	ZTK553	£0.12*	2N4292	£0.18*
AF127	£0.30	8C461	£0.38	BF197	£0.12*	DC78	£0.50	ZTK554	£0.12*	2N4293	£0.18*
AF139	£0.35	8C478	£0.20	BF199	£0.14*	DC81	£0.22	ZTK555	£0.12*	2N4294	£0.18*
AF174	£0.60	8C547	£0.10*	BF200	£0.30	DC82	£0.24	ZTK556	£0.12*	2N4295	£0.18*
AF179	£0.60	8C547	£0.10*	BF202	£0.30	DC83	£0.24	ZTK557	£0.12*	2N4296	£0.18*
AF180	£0.60	8C548	£0.10*	BF222	£0.90	DC84	£0.38	ZTK558	£0.12*	2N4297	£0.18*
AF181	£0.58	8C549	£0.10*	BF224	£0.17	DC89	£0.38	ZTK559	£0.12*	2N4298	£0.18*
AF186	£0.58	8C550	£0.14*	BF240	£0.17*	DC10	£0.80	ZTK560	£0.12*	2N4299	£0.18*
AF239	£0.38	8C556	£0.14*	BF241	£0.17*	DC169	£0.35	ZTK561	£0.12*	2N4254	£0.40
AL03	£1.18	8C557	£0.12*	BF244	£0.30*	DC170	£0.35	ZTK562	£0.12*	2N4255	£0.40
ASV26	£0.38	8C559	£0.14*	BF258	£0.25	DC171	£0.35	ZTK563	£0.12*	2N4256	£0.40
ASV27	£0.40	8C30	£0.55	BF259	£0.35*	DC200	£0.95	ZTK564	£0.12*	2N4257	£0.40
ASV28	£0.38	8C31	£0.55	BF262	£0.60*	DC201	£1.20	ZTK565	£0.12*	2N4258	£0.40
ASV29	£0.38	8C32	£0.60	BF263	£0.60*	DC202	£1.95	ZTK566	£0.12*	2N4259	£0.40
ASV30	£0.38	8C33	£0.55	BF267	£0.30*	DC203	£0.85	ZTK567	£0.12*	2N4260	£0.40
ASV51	£0.30	8C34	£0.60	BF270	£0.30*	DC204	£0.90	ZTK568	£0.12*	2N4261	£0.40
ASV52	£0.30	8C35	£0.60	BF271	£0.31	DC205	£1.15	ZTK569	£0.12*	2N4262	£0.40
ASV54	£0.30	8C36	£0.60	BF272	£0.80			ZTK570	£0.12*	2N4263	£0.40
ASV55	£0.30	8C37	£0.15	BF273	£0.36*			ZTK571	£0.12*	2N4264	£0.40
ASV56	£0.30	8C38	£0.14	BF274	£0.38*			ZTK572	£0.12*	2N4265	£0.40
ASV57	£0.30	8C39	£0.14	BF275	£0.38*			ZTK573	£0.12*	2N4266	£0.40
ASV58	£0.30	8C40	£0.14	BF276	£0.38*			ZTK574	£0.12*	2N4267	£0.40
ASV59	£0.30	8C41	£0.14	BF277	£0.38*			ZTK575	£0.12*	2N4268	£0.40
ASV60	£0.30	8C42	£0.14	BF278	£0.38*			ZTK576	£0.12*	2N4269	£0.40
ASV61	£0.30	8C43	£0.14	BF279	£0.38*			ZTK577	£0.12*	2N4270	£0.40
ASV62	£0.30	8C44	£0.14	BF280	£0.38*			ZTK578	£0.12*	2N4271	£0.40
ASV63	£0.30	8C45	£0.14	BF281	£0.38*	</					

OSTS

Since AMBIT introduced the "One Stop Technology Shop" to our service, we have been pleased to see just how many users of electronic components appreciate our guarantee to supply goods only from BS9000 approved sources. More than ever, professional and amateur electronics engineers cannot afford to waste time on anything less than perfect pedigree products.

SEE THE AMBIT AD TOO!

CD4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4527	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	18p	4067	40p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4016	52p	4075	20p	4541	141p
4017	80p	4076	90p	4543	174p
4018	80p	4077	20p	4549	399p
4019	50p	4078	20p	4553	440p
4020	93p	4081	20p	4554	153p
4021	82p	4082	20p	4556	77p
4022	90p	4085	82p	4557	386p
4023	17p	4086	82p	4558	117p
4024	76p	4089	150p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	190p	4561	65p
4027	85p	4096	105p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	680p
4030	58p	4099	122p	4569	303p
4031	250p	4160	90p	4572	25p
4032	100p	4161	90p	4580	600p
4033	145p	4162	90p	4581	319p
4034	200p	4163	90p	4582	164p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4134	95p	4585	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	83p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	58p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	150p	4511	148p		
4046	130p	4512	98p		
4047	99p	4513	206p		
4048	60p	4514	260p		
4049	55p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4821	236p		

Micromarket PRICES SLASHED

6800 series	8216	1.95	2114	£10
	8224	3.50	2708	£10.55
6800P	£6.50			
6820P	£6		Development	
6850P	£2.75		MEK6800	£220
6810P	£4		TK80	£306
6852	£3.65			
MEMORIES				
	2102	£1.70	AMI, Signetics,	
8080 series	2112	£3.40	Ti, Intersil,	
	8080	£6.30	Harris etc. OA	
	2513	£7.54		
	4027	£5.78		

TTL: Standard AND LP Schottky

	'N'	'LSN'		'N'	'LSN'		'N'	'LSN'		'N'	'LSN'		'N'	'LSN'		'N'	'LSN'
7400	13	20	7455	35	24	74126	57	44	74185	134		74377	124				
7401	13	20	7460	17		74128	74		74188	275		74378	93				
7402	14	20	7463			74132	73	78	74190	115	92	74379	130				
7403	14	20	7470	28		74133		29	74191			74386	37				
7404	14	24	7472	28		74136	90	40	74192	105	180	74390	140				
7405	18	26	7473	32		74138		60	74193	105	180	74395	139				
7406	38		7474	27	38	74139		60	74194	105	187	74396	133				
7407	38		7475	38	40	74141	56		74195	95	137	74398	180				
7408	17	24	7476	37		74142	265		74198	99	110	74399	150				
7409	17	24	7478			74143	312		74197	85	110	74445	92				
7410	15	24	7480	48		74144	312		74198	150		74447	90				
7411	20	24	7481	86		74145	65		74199	160		74490	140				
7412	17	24	7482	69		74147	175		74248		90	74668	110				
7413	30	52	7483A			74148	109		74249		93	74670	249				
7414	51	130	7484	97		74150	99		74251		90	MISCELLANY					
7415	20	24	7485	104	99	74151	64	84	74253		105	NE555	30p				
7416	30		7486		40	74153	64	54	74257		108	NE558	78p				
7417	30		7489	205		74154	96		74258		153	NE558	180p				
7420	16	24	7490	33	90	74155	54	110	74259		420	ICM7217	950p				
7421	29	24	7491	76	110	74156	80	110	74260		153	ICM7208	1495p				
7422	24	24	7492	38	78	74157	67	65	74261		60	ICL7106CP					
7423	27		7493	32	99	74158		60	74266		60	ICL7106P					
7425	27		7494	78		74159	210		74273		124	LCD DVM IC					
7426	36	27	7495A	65	99	74160	82	130	74275		312	LCD DVM KIT					
7427	27	29	7496	185	120	74161	92	78	74279		52	3 1/2 digit LCD					
7428	35	32	7497	185		74162	92	130	74283		120	display 1150p					
7430	17	24	74100	119		74163	92	78	74290		95	ICL7107 LED					
7432	25	24	74104	63		74164	104		74295		100	DVM kit 206p					
7433	40	32	74105	62		74165	105		74298		100	ICM7216 - 8 digit					
7437	40	24	74107	32	38	74166			74324		157	10MHz DFM/					
7438	33	24	74109	63	38	74167	20		74325		242	timer £19.82					
7440	17	24	74110	54		74168			74326		247	(for LED C.Cath)					
7441	74		74111	68		74169		200	74327		237	SCALAR ICs					
7442	70	99	74112	88		74170	230	200	74327		100	8629 150MHz					
7443	115		74113		38	74172	625		74352		715	divide by 100					
7444	112		74114		38	74173	170		74353		100	420p					
7445	94		74116	196		74174	87	120	74362		49	95H90DC 780p					
7446	94		74118	83		74175	87	110	74365		49	11C90DC 1400p					
7447	82		74119	119		74176	75		74366		49	8618 - new/divide					
7448	56	99	74120	115		74177	78		74367		43	by 100 or 10					
7449	99	99	74121	25		74180	85		74368		49	for 120/60MHz					
7450	17		74122	46		74181	165	350	74373		77	450p					
7451	17	24	74123	48		74182	160		74374		77						
7453	17		74124			74183			74375		60						
7454	17	24	74125	38	44	74184	135										

Voltage Regs

NEW LOW PRICES

7800 series UC TO220 package 1A all 95p
 7900 series UC TO220 package 1A all £1
 78MUC series TO220 package 1/2A all 90p
 78LCP series TO92 100mA all 35p

L200 up to 3A/adjustable V&A 195p

78MGT2C 1/2amp adjustable volts 175p
 79MGT2C 1/2amp adjustable volts 175p
 723C precision controller 65p

MAINS FILTERS FOR NOISE/RFI etc

1 amp in IEC connector £4.83
 5 amp in 'wire in' case £3.87
 NE550A 73p

LINEARS non-consumer

BIMOS

CA3130E	84p
CA3130T	90p
CA3140E	36p
CA3140T	72p
CA3160E	90p
CA3160T	99p

Op amps

LM301AH	67p
LM301AN	30p
LM308H	121p
LM308N	97p
LM318H	279p
LM318N	224p

OPTO 7 seg displays

0.43" High Efficiency HP:

5082-7650	red CA	
5082-7653	red CC	
5082-7660	yellow CA	233p
5082-7663	yellow CC	
5082-7670	green CA	
5082-7673	green CC	

0.3" Standard HP

5082-7730	red CA	
5082-7740	red CC	147p

0.5" Fairchild

FND500	red CC	150p
FND507	red CA	150p
NE531N	105p	

The ICL7216BPI is still the cheapest way to make a full 8 digit/ 10MHz frequency counter/timer, and with 10 external components + display - it is also one of the simplest. For £19.82, it takes a lot of beating. The mains filters have been extended now to include a gamp IEC version at £5.10, and with the amount of electronic noise on the average supply (next door's fridge, for instance) it is a really worthwhile addition to any sensitive equipment. LPSN TTL now includes many more of latest types, all - of course - are absolutely prime first quality types. And don't forget our range of OPTO displays includes Hewlett Package high efficiency 0.43" types in all colours - renowned as the finest quality in the market. For other types of component - discrete LEDs, radio and audio devices, tuner modules, kits etc., see our other advertisement for more details - or send for the AMBIT catalogue system. Part one (45p) includes details of our background 'standard' items, and the new part two includes all the latest introductions and developments, plus a rundown on OSTs.

2 Gresham Road, Brentwood, Essex.

Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.



Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure without obligation to:

British National Radio & Electronic School
 P.O. Box 156, Jersey, Channel Islands.

NAME _____
 ADDRESS _____

Block caps please

THIS is the Catalogue you need to solve your component buying problems!



- About 2,500 items clearly listed and indexed
- Profusely illustrated
- 128 A-4 size pages, bound in full-colour cover

- Bargain List of unrepeatable offers included free
- Catalogue contains details of simple Credit Scheme
- Price includes packing and postage

Send the coupon today with cheque or P.O. for £1.25

Please write your Name and Address in block capitals

NAME

ADDRESS



POST THIS COUPON
WITH CHEQUE OR P.O. FOR
£1.25

HOME RADIO (Components) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD
egd. No. 912966, London
R.

HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD. Phone: 01-648 8422

ambit international [®]

PARTS FOR CURRENT PW PROJECTS ... FROM AMBIT INTERNATIONAL
VHF FM monitor RX: A complete kit of parts for this project, which we firmly believe will be an established "standard" for years to come. The kit includes a 5 channel switched crystal oscillator added to the board end, using diode switching. Uses cheaper 3rd OT crystals, employing original oscillator as x3 stage. Price depends on filter selected (we have various types) and whether or not chip capacitors are required. More notes on the kit from our own lab. £25-£35 kit.
VMOS POWER TRANSISTORS FOR PW WINTON £9.95 pair * 2SK133/J48
FULL KITS FOR THE PW SANDBANKS METAL LOCATOR (should be ex stock)
FULL KITS FOR THE PW DORCHESTER

Radio ICs	
TDA1062	HF/VHF tunerhead 1.95
TDA1083	One chip AM/FM rx 1.95
TDA1090	One chip HiFi am/fm 3.35
TDA1220	One chip am/fm rx 1.75
HA1197W	HiFi AM tuner IC 1.40
CA3123E	AM tuner IC 1.40
TBA651	AM tuner IC 1.81
CA3089E	Famous FM IF system 1.94
CA3189E	As 3089+ deviation mute AF preamp, adj, agc 2.75
HA1137W	Improved S/N 3089 2.20
TBA120	limiting amp+detector 0.75
TBA120S	high gain 1.00
MC1350P	agc'd IF preamp 1.20
MC1330P	synch AM/video detector 1.35
KB4406	Cascade IF preamp 0.65
uA753	limiting FM preamp 1.95

Discrete devices: more than ever:	
BF960	800MHz/2.8dB nf mosfet 1.60*
BF961	200MHz/2.0dB nf ... 0.80*
40822	FM RF amp 0.43*
40823	FM mixer 0.51*
40673	Famous MOSFET 0.55*
2SJ49/2sK133	120v/100W MOSPOWER output devices 10.50*

LEDs: the best value today	
	3mm 5mm 2.5x5mm
Red	0.14 0.14 0.17
Green	0.18 0.16 0.20
Yellow	0.18 0.15 0.20
Orange	0.22 0.29 0.24

100 off mix, 25% discount. All are AEG first grade types - absolutely no junk. 5mm clips for panel mounting 0.03 each

Misc. ICs for radio/audio applications	
U237B	5 LED bargraph driver 0.80*
SAS6610	4 station touch tune IC 1.48*
SAS6710	adds 4 stations to 6610 1.48
MSM5523/4	LW,MW,SW and FM digital frequency readout plus clock, timers, stopwatch LW/MW/FM DFM with direct drive for LCO £14*
MSM5526	LW,MW,SW and FM digital frequency readout plus clock, timers, stopwatch LW/MW/FM DFM with direct drive for LCO £11*
TCA730	OC volume control 3.50
TCA740	OC tone control 3.50
TDA1028	DC input switch 3.50
TDA1029	OC mode switch 3.50

Radio and Tuner modules

We cannot really list all the details we would like to here - but with advent of the new mark 3 tuner system, the Dorchester and matching AF units, Ambit offers you the widest choice ever, plus hardware and styling that matches the very high standards we have set in this new range.

Communications circuits	
SD6000	DMOS RF/Mixer pair 3.75
KB4412	Bal mixers, IF+agc 2.55
KB4413	AM/SSB det, squelch,agc 2.75
KB4417	mic processor 2.55
MC3357	best thing in NBFM yet 3.12
MC1496P	popular double bal mixer 1.25

Multiplex decoders + noise blanker	
MC1310P	popular PLL decoder 2.20
uA758	buffered 1310 2.20
CA3090AQ	RCA PLL decoder 3.25
HA1196	improved PLL decoder with stereo preamps 3.95
HA11223	19kHz pilot cancel, low distortion, high S/N as HA11223 with remote VCO kill facility 4.35
KB4437	as HA11223 with remote VCO kill facility 4.55
KB4438	stereo MUTING preamp for post decoder mute 2.22
KB4423	impulse noise blanker 2.53

TERMS etc: CWO please, VAT on Ambit Items is generally 12%, except where marked (*). Catalogue part 1:45p, part 2 50p all inclusive. Postage 25p per order, carriage on tuner kits £3. Phone Brentwood (0277) 216029/227050 9am-7pm. Callers welcome inc. Saturdays.

At last, DIY HiFi which looks as if it isn't.

That's not to say it doesn't look like HiFi - just that it doesn't look like the usual sort of thing you have come to associate with DIY HiFi. The Mk3 outstrips and outperforms all British made HiFi tuners, and most imported ones too. Certainly at the price, there isn't one near it. But more than that, it looks superb. A small pic here would be an insult, so send an SAE for details on the kit that looks as if isn't. It's something else.....


- * Exceptionally high performance - exceptionally straightforward assembly
- * Baseboard and plug-in construction. Future circuit developments will readily plug in, to keep the MkIII at the forefront of technical achievement
- * Various options and module line-ups possible, to enable an installation approach to the system

and now previewing the matching 60W/channel VMOS amplifier:

- * Matching both the style and design concepts of the MkIII HiFi FM tuner
- * Hitachi VMOS power fets - characterized especially for HiFi applications
- * Power output readily multiplied by the addition of further MOSFETs
- * VU meters on the preamp - not simply dancing according to vol level
- * Backed with the usual Ambit expertise and technical capacity in audio

The PW Dorchester - LW, MW, SW, & FM stereo tuner

THE DIGITAL DORCHESTER ALL BAND TUNER

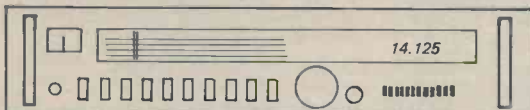

With styling and dimensions to fit in with the rest of AMBIT's new range of tuner & audio equipment.

When the new range of OKI digital frequency display ICs was announced, the original prototype of the Dorchester had been made - but since so many of you wanted to use the OKI frequency counterdisplay system with the Dorchester, we quickly designed a unit to incorporate the necessary facilities. The Digital Dorchester is designed in 19" inch form, and forms a perfect match for the other units in the range. If you don't want to go to the expense of the full Ambit DFM1 module, with AM/FM/Time/Timers, then the MA1023 clock module can be used instead.

The Dorchester has been described in PW Dec., Jan. and Feb. issues - but for those of you who may have missed it - it is an All Band broadcast tuner, covering LW/MW/SW and FM stereo in 6 switched ranges. Construction is very straightforward, with all the switching being PCB mounted - and the revolutionary TDA1090 IC used for AM/FM.

The electronics for the radio section of the Dorchester remain unchanged at £33.00, with 12.5% VAT. The hardware package, of case, meter, PSU now costs £33.00 + 8% with the MA1023 available for an extra £5 only.

For the fully digital version, with Ambit DFM1, the price is £56.50 + 8% VAT.

2 Gresham Road, Brentwood, Essex.

**SATISFACTION
OR YOUR MONEY
BACK IF GOODS
RETURNED
WITHIN
7 DAYS**

A BIG NEW DEAL

**STREAMLINED
RETURN-OF-POST
COMPONENT
ORDERS
SERVICE**

★
STUD DIODES
Rated 10amp 100V
Metal Brand New
Two for 35p

PANEL INDICATORS
Red 30p Amber 32p Green 32p
Clear lens red glow 22p

ALL BRAND NEW!

★
**AUDIBLE
WARNING DEVICE**
Transistorised 4-12v
Can be run from TTL
Brand New 74p each

ROTARY POTS
All modern types, carbon tracks. 60% long shafts, all new

10K Lin 18p
47K Lin 18p
50K Lin 18p
250K Lin 16p

DUAL
100K Lin 24p
100K Log 24p
22K Log 24p
1K+500K Lin 20p

WIREWOUND RESISTORS
All brand new modern types

1.5ohm 5w 5p
2.7ohm 2w 4p
30 ohm 5w 5p
51 ohm 5w 5p
56 ohm 5w 5p
500 ohm 5w 5p

560 ohm 5w 5p
1K 10w 5p
1K2 5w 5p
2K2 5w 5p
6K8 5w 5p

POLYSTYRENE CAPACITORS

47pF/400v
60pF/350V
163pF/125v
390pF/150v
395pF/350v
1000pF/350v
3070pF/125v
4000pF/125v

**ALL
AT
4p EACH**

TUNING CAPACITORS
250pF air spaced 40p
350pF + 350pF approx
double gang, slow tune, air spaced 60p
Both types are new

SUPER TESTED PAKS

30 Uncoded BC107 70p
30 Uncoded BC108 70p
30 Uncoded BC109 70p
30 AC128 branded 70p
20 Vari-Cap diodes uncoded 35p
40 Asstd transistors 70p
30 2W Zener diodes uncoded 42p
6 asstd pre-set pots 30p
20 wirewound resistors 42p
25 C280 Capacitors 30p
25 Polystyrene Capacitors 30p
25 Ceramic Capacitors 30p
25 asstd Capacitors 30p
6 P-channel FET's 60p
6 N-channel FET's 60p
6 Photo transistors uncoded 60p
10 Stud diodes asstd types 30p

SENSATIONAL SCOOP!

LED - DISPLAYS
Brand new devices, 7 segment, common anode and common cathode types, these are not full spec but are 100% functional. Data supplied, we cannot select display colours or c.a. or c.c. types.

0.3" single display 35p
0.6" single display 45p
0.5" double display 65p
0.5" Special +1 and 7 segment displays 70p

ONLY LIMITED STOCKS

PUSH BUTTON BANKS

All new, ratchet type switches
Single d.p. changeover 12p
Three banked all d.p. changeover 20p
Three banked, one d.p. changeover, two with four d.p. changeovers 24p
Three banked, one d.p. changeover, two d.p. changeovers 18p
Five banked, two d.p. changeovers, three single changeover 25p

POWER SUPPLY ELECTROLYTICS

32+32uF 275v wkg 20p
32+32uF 350v wkg 25p
100+200uF 275v wkg 25p
150+150+75uF 350v wkg 34p
200+200+100+32uF 325v 35p
All types brand new

TRIMMERS

Compression types, all brand new. 10pF, 30pF, 50pF, 1,000pF All 15p each
Tubular solder-in types, brand new. 3pF, 6pF, 8pF, 12pF All 10p each
Dau semi-air spaced 2 to 9pF 16p
6 to 45pF 16p
8 to 125pF 18p

I.C. TOOL

Insertion or extraction plastic, new 55p each

MAINS TRANSFORMERS

All primaries 240V:
24V tapped £1.80
14V lamp £2.00
22-0-22V 500ma £2.00
16V 2 amp £2.10
12V 1 amp £1.70
24V 1.75 amp £2.00
30V 1 amp £2.10
13-0-13V 1 amp £2.20
22V 500ma £1.40
32-0-32V 500ma £2.20
Please add P&P 40p on transformers

ELECTROLYTIC CAPACITORS

All brand new modern transistor types mostly, all values, voltages marked

1uF/75v 5p
2uF/40v 5p
4uF/300v 5p
6.8uF/25v 6p
12uF/25v 5p
25uF/12v 5p
25uF/30v 4p
32uF/40v 5p
32uF/160v 6p
40uF/16v 5p
47uF/25v 5p
56uF/25v 5p
64uF/10v 4p
64uF/70v 5p
75uF/9v 4p
100uF/6.3v 4p
100uF/40v 5p
125uF/10v 5p
125uF/10v 5p
150uF/6.3v 4p
150uF/16v 5p
150uF/25v 5p
200uF/10v 5p
250uF/16v 5p
300uF/9v 5p
300uF/25v 5p
320uF/18v 5p
320uF/18v 5p
330uF/25v 5p
400uF/10v 5p
400uF/25v 5p
470uF/6.3v 5p
470uF/16v 5p

TBA 120S FM DETECTOR

I.C.'s new with data but untested 18p each

LDR's

ORP 12 Equiv 50p
ORP61 60p
Both brand new

WIDEBAND AMPLIFIER

I.C.'s new with data but untested 18p each

35 amp FUSES

1 1/4" 51x for 20p

MULLARD TAA320

M.O.S.T. PRE-AMP I.C. with circuits brand new, tested 48p each

INFLATION BEATERS

I.C. SOCKETS

Low profile d.i.l. brand new types
8 pin 12p
14 pin 13p
16 pin 14p

13 AMP RUBBER Fly-lead

extension sockets. Black 40p

SUPER BUY

CARBON FILM RESISTORS
5% 1/4w and 1/2w
All brand new but with preformed leads
PAK OF 150
ONLY 60p

REED RELAYS

Small types 10p each

1/4" COIL FORMERS

With cores 9p

N-CHANNEL FET's

16p each

P-CHANNEL FET's

16p

PHOTO-TRANSISTORS

New, uncoded 18p each

INLINE FUSEHOLDERS

1 1/2" fuse type 16p each

13 amp PLUGS

Black rubber new 38p

TERMINAL BLOCKS

4-way 5A 12p

RELAYS

12v dc min new 70p

RELAYS

24v dc min. new. S/T 70p

PANEL FUSEHOLDERS

20mm type 30p each

BD187 TRANSISTORS

4 amp full spec 28p

STAR PACK

Twenty asstd I.C.'s. All sorts 8 pin, 14 pin, 16 pin all types. Many coded but all untested at only 24p

SLIDER POTS

All new smooth track plastic coded types

470R lin 1K lin 4.7K lin 5K lin 10k log 25K log 100K lin 250K lin

All 22p each

BARGAIN PAK

TEN POWER TRANSISTORS

All new and marked numbers, plastic and metal types, tested working Only £1.00

NUTS/BOLTS

6BA nuts 40 30p
6BA 1" Bolts 40 35p
4BA nuts 40 32p
4BA 1" bolts 40 36p
6BA solder tags 40 28p

PRESSIL SWITCH

Single/pole, new, 2 amp 18p

TO3 TRANSISTOR

Insulation Covers Nylon 4 for 24p

BATTERY HOLDERS

Takes 6 x HP7 24p each

MAGNETIC EARPIECES

8 ohm new 28p each

ROTARY SWITCH

Miniature 2 pole 4 way 30p each

DIODE PAK

50 Silicon types new only 35p

THYRISTOR

10 amp 100 PIV metal stud 35p each

TO3 WASHERS

Melinex for heat-sinks 4 for 16p

SUMMER OFFER

COMPRESSION TRIMMERS

10 to 100pF Only 12p each

TRANSISTORISED INVERTERS

All units ready assembled in blue rexine covered aluminium cases, plain bottoms, features include: on/off switch, output via 13A type rubber socket, silicon power transistors, all new components used throughout. 12v or 24v inputs as listed — output 240v AC off load, square wave, frequency between 45/54Hz approx

PLEASE ADD 15p post/packing. Minimum order £1.50. Payment by cheques, postal orders etc. Overseas postage at cost. It is very helpful if you print your name and address clearly.
Goods ordered now sent by return of post except where indicated.

12v in — 25 watts out. 6"x5"x4" £7.50
12v in — 40 watts out. 6"x5"x4" £10.80
12v in — 120 watts out. 11"x6"x5" £21.00
24v in — 25 watts out. 6"x5"x4" £8.80
24v in — 50 watts out. 6"x5"x4" £12.60
24v in — 100 watts out. 11"x6"x5" £21.00
24v in — 150 watts out. 11"x6"x5" £26.00
24v in — 200 watts out. 11"x6"x5" £34.00
24v in — 300 watts out. 11"x6"x5" £42.00

P&P
£2.00
Extra

ELECTROVANCE
TEL: 01-736 0685 MAIL ORDER ONLY
P.O. BOX 191 LONDON SW6 2LS

GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £57.35 inc. VAT. Crystals, if required: £2.50 each. All popular 2m. channels in stock. Marine band version (156-162MHz) £57.35 (xtals £2.79). Mains psu for above £11.25. Credit terms available, s.a.e. details.

Amplified Mobile Extn. Speaker boosts audio from small receivers. Single compact unit. 12vDC built-in 6W amplifier, with leads and jack plug. 4-8 Ω input £11.25. Amplifier only from above £2.70.

Neons min wire end 55p/10; £4/100 Slide switches min DPDT 18p ea; 5+ : 14p Resistor Kits E12 series, 22 Ω to 1M Ω 57 values. 5% carbon film, 1/4W or 1/2W Starter pack, 5 each value (285) £2.95 Mixed pack, 5 each 1/4W + 1/2W (570) £5.40 Standard pack, 10 each (570) £5.40 Giant pack, 25 each (1,425) £13.25 I.C.'s (new) 7410 25p CD4001AE 25p SN76660 75p NE555 55p 723(TO5) 75p 709 (TO5). 741 (DIL-8) Op.amps 30p; BNC Cable mtg socket 50 Ω 20p; 5+ : 15p PL259 UHF Plug & Reducer 68p; 5+ : 60p; SO239 UHF Socket panel mtd. 55p; 5+ : 45p Nicad rechargeables physically equiv. to zinc-carbon types: AAA (U16) £1.64; AA(U7) £1.20. C(U11) £3.15; D(U2) £4.94; PP3 £5.20 Any 5+ : less 10%. Any 10+ less 20%.

We stock V.H.F. mobile aerials, s.a.e. details.


Distributors for J. H. Associates Ltd. (switches and lamps)

PRICES INCLUDE UK POST, PACKING & VAT Mail order only Sole Address:

GAREX ELECTRONICS
7 NORVIC ROAD, MARSWORTH,
TRING, HERTS HP23 4LS
Cheddington (STD 0296) 688684

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 Silicon transistors plus 2 power out-put transistors in push-pull. Full wave rectification. Output approx 13 watts r.m.s. into 8 ohms. Frequency response 12Hz. 30KHz ±3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £18.00. P&P £1.20.

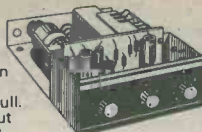


HARVERSONIC MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mv into 47k. input 2, 15mv into 47k (suitable for use with mic or guitar etc). Input 3, 200mv into 1 meg suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass and treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose-built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240v. Size approx 12 1/4" w x 5" h x 7 1/4" d. Special introductory price £28.00 + £2.50 carr & pkg.



HARVERSONIC STEREO 44

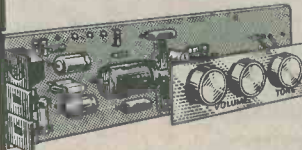

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated

circuit amplifiers with built-in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec/play socket are mounted on the printed circuit panel, size approx 9 1/2" x 2 3/4" x 1 1/2" max depth. Supplied brand new and tested, with knobs, brushed anodised aluminium, 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically), at only £10.00 plus 50p P&P. Mains transformer with an output of 17V a/c at 500 m/a can be supplied at £2.00 plus 40p P&P if required. Full connection details supplied.

STEREO DECODER SIZE 2" x 3" x 1/2"

Ready-built. Pre-aligned and tested. Sens. 20-580mV for 9-16V neg earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £8.00 plus 20p P&P. Stereo beacon light if required 40p extra.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State A/M F/M Stereo tuner. Covering MW AM 540-1605 KHZ, VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for MW. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built-in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600 mV RMS into 20K. Simulated teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w x 4" h x 9 1/2" d approx. LIMITED NUMBER ONLY at £28.00 plus £1.50 P&P.

SONOTONE 9TAHC COMPATIBLE STEREO CARTRIDGE

T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.80. P&P 20p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3.00 P&P 20p. LATEST CRYSTAL T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo 78, £2.20 P&P 20p. LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £2.20 P&P 20p. STEREO MAGNETIC PRE-AMP sens 3mVin for 100mV out 15 to 35V neg earth. Equ ± 1db. From 20Hz to 20KHz. input impedance 47k. Size 1 1/2 in x 2 1/2 in x 5 1/2 H. £3.00 plus 20p P&P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday.

Prices and specifications correct at time of press. Subject to alteration without notice

SPECIAL OFFERS

Mullard LP1159 RF-IF Double Tuned Amplifier Module for nominal 470KHz. Size approx 2 3/4" x 1 1/4" x 3/8" 7.6V + earth. Brand new pre-aligned. Full specification and connection details supplied. £2.25 + P&P 20p. Pye VHF/FM Tuner Head covering 88-108MHz/Hz. 10.7MHz IF output 7-8V + earth. Supplied pre-aligned with full circuit diagram. Connection details supplied. Beautifully made with precision-gear FM Gang and 323 Pf + 323 Pf AM Tuning Gang only £3.15 + P&P 35p.

SPECIAL OFFER Limited Number only!

New but very slightly shop soiled transistor radios by well known manufacturer. Very smart and attractive, vinyl covered with carrying handle. Size 7" H x 9 1/2" W x 4" D approx. Telescopic aerial for VHF/FM band and internal ferrite aerials for AM bands. AC mains or battery operated and covering VHF/FM and MW bands. Uses four HP11 or SP11 batteries (not supplied). £10.00 + £1.30 P&P

SPECIAL OFFER Limited Number only!

Goodmans speakers. 6 1/2" x 8 ohm, low throw, ceramic magnet, full range rated 10 watts RMS (when fitted in enclosure). £4.00 + 80p P&P (£P&P on two £1.20)

PRECISION MADE

Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p/c/o. Overall size 5" x 2 1/2" x 1". Supplied complete with chrome finished switch buttons 2 for £1.80 + 20p P&P

"POLY PLANAR" WAFER-TYPE, WIDE RANGE

ELECTRO-DYNAMIC SPEAKER. Size 11 1/2" x 14". 1 1/8" x 1 7/16" deep. Weight 19oz. Power handling 20W RMS (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, etc and used with or without baffle. Send SAE for details. Only £8.40 each. P&P 90p for one £1.10 for two. Now available in 8" round version. 10 watts RMS 60Hz-20KHz. £5.25 + P&P (one 65p, two 75p).

HARVERSONIC SUPER SOUND 10+10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge — instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts — no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts RMS per channel into 5 ohms. Frequency response ± 3dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M Ω Full power bandwidth: ±3dB 12-15,000 Hz. Bass, boost approx to ± 12dB. Treble cut approx to — 16dB. Negative feedback 18dB over main amp. Power requirements: 35v at 1.0 amp. Overall size 12" W x 8" D x 2 3/4" H. Fully detailed 7 page construction manual and parts list with kit or send 25p plus large SAE. AMPLIFIER KIT £14.50 P&P 80p (Magnetic input components 33p extra)

POWER PACK KIT £6.00 P&P 95p
CABINET £6.00 P&P 95p

SPECIAL OFFER — ONLY £25.00 IF ALL 3 UNITS ORDERED AT ONE TIME + £1.25 P&P

Full after sales service
Also available ready built and tested £31.25 P&P £1.50

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram. allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EC83, EF86 and E280 rectifier. Simple instruction booklet 25p x SAE (free with parts). All parts sold separately. ONLY £18.00 P&P £1.40. Also available ready-built and tested. £22.00 P&P £1.40.

OUR PRICES INCLUDE VAT AT CURRENT RATES


HARVERSON SURPLUS CO. LTD.

(Dept. REC) 170 MERTON HIGH ST. MERTON, LONDON, SW.19. Tel: 01-540 3985

A few minutes from South Wimbledon Tube Station

SEND SAE WITH ALL ENQUIRIES. FOR PERSONAL CALLERS ONLY: WE CAN NOW OFFER A FULL REPAIR SERVICE ON ALL HI-FI EQUIPMENT. DISCO, CASSETTES, CAR RADIO, ETC.

MORSE MADE EASY

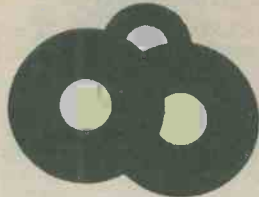

BY THE G3HSC RHYTHM METHOD!

These courses, which have been sold for over 23 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words.

Using scientifically prepared 3-speed records you automatically learn to recognise the code. RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 W P M in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books. For Complete Course send £5.00 plus part postage 50p (overseas surface mail £1 extra). Now available Shrouded Morse Keys £2.70 inc. UK postage

THE G3HSC MORSE CENTRE

Box 8, 45 Green Lane, Purley, Surrey. I enclose £5.50 or s.a.e. for explanatory booklet.


Name

Address

APEL POWER SUPPLIES

STABILIZED POWER SUPPLIES WITH ELECTRONIC SHORT CIRCUIT PROTECTION

AL.212 P

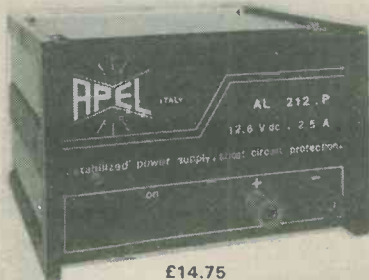

£14.75

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12.5 V dc
OUTPUT CURRENT MAX	2.5 Amp
LOAD REGULATION	<0.3% 0-2.2 Amp
RIPPLE	<5mV 2.2 Amp
DIMENSIONS (mm)	W140 x H90 x D140
WEIGHT	1,490 Kg.

AL.315 P



£29.50

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	1.7-15 V. dc
LOAD REGULATION	<0.2% 0-2.8 Amp
DIMENSIONS (mm)	W140 x H90 x D155
RIPPLE	3mV 2.8 Amp
WEIGHT	2,330 Kg.

AL.330 P



£46.50

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	3.4-30 V. dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 5% 0-2.8 Amp
RIPPLE	10mV 2.8 Amp
DIMENSIONS (mm)	W270 x H90 x D155
WEIGHT	4,250 Kg.

STOCKISTS

Alpha Sound Service,
50 Stuart Road, Waterloo, Liverpool L22 4QT.
England.

Anson Electronics,
1133 Hessle High Road, Hull, England.

Amateur Radio Shop,
13 Chapel Hill, Huddersfield, HD1 3ED.
England.

Brent Electronics,
Seaview Street, Cleethorpes,
Lincolnshire, England.

J. Birkett,
26 The Strait, Lincoln, England.

Bradford Consultants Limited,
25 Regent Parade, Harrogate,
Yorkshire, England.

F. Brown & Co. Ltd.,
44/46 George IV Bridge Street,
Edinburgh, Scotland.

N. R. Bardwell Limited,
Sellers Street, Sheffield, England.

Casey Brothers,
235 Boundary Road,
"Saint Helens,"
Lancashire, England.

Electronic Services Limited,
33 City Arcade, Coventry CU11 HX, England.

A. Fanthorpe Limited,
6 Hepworth Arcade, Silver Street,
Hull, England.

G. W. M. Radio,
Portland Road, Worthing, Sussex.

Leeds Amateur Radio,
27 Cookridge Street,
Leeds LS2 3AG, England.

Target Electric Limited
16 Cherry Lane, Bristol, England.

New Cross Radio,
6 Oldham Road, Manchester,
England.

Progressive Radio,
93 Dale Street, Liverpool L2 2JD,
England.

R. E. Pitt Electrical Services Limited,
60/64 Bath Buildings, Mont Pelier,
Bristol, England.

Peats Electronics,
Parnell Street, Dublin.

R. F. Potts,
68 Bobbington Lane, Derby, England.

Brian A. Pearson Limited,
66 Moncur Street, Glasgow, Scotland.

R M E Supplies Limited,
143 Stockwell Street, Glasgow, Scotland.

Stephan James Limited,
Warrington Road, Leigh, Lancashire.

Stewarts Radio,
4 Chance Street, Blackpool, England.

The Radio Shop,
16 Cherry Lane, Bristol BS 3NG,
England.

Q. C. Trading,
1 St. Michaels Terrace, Woodgreen M22 4FT,
England.

AL.1 P5



£78.00

INPUT VOLTAGE	220 \pm 10% 50 Hz
OUTPUT VOLTAGE RANGE	1 \pm 15 V. dc
OUTPUT CURRENT MAX	5 Amp
LOAD REGULATION	< 0.1% 0-4.5 Amp
RIPPLE	< 2mV 4.5 Amp
DIMENSIONS (mm)	W210 x H155 x D250
WEIGHT	5,100 Kg.

AL.212 PS



£18.00

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12.6 V dc
OUTPUT CURRENT MAX	2.5 Amp
LOAD REGULATION	<0.3% 0-2.2 Amp
RIPPLE	<5mV 2.2 Amp
DIMENSIONS (mm)	W140 x H90 x D140
WEIGHT	1,490 Kg.
AMPEROMETER	

AL.315 P2



£54.00

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	\pm 1.7 \pm 15 V dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 0.2% 0-2.8 Amp
RIPPLE	< 3mV 2.8 Amp
DIMENSIONS (mm)	W270 x H90 x D155
WEIGHT	4,140 Kg.

Stan Willets Limited,
37 High Street, West Bromwich.

M/S Waltons,
55a Worcester Street,
Wolverhampton WV2 4LL, England.

Distributed in the U.K.
and Ireland by:

PEAT'S WHOLESALE LTD.

Chapel Lane, Parnell St., Dublin 1, Ireland.

PHONE 741746-740678-722845. TELEX 31787.

STEVENSON

Electronic Components

REGULATORS

78L05 30p	7805 60p	79L05 70p	7912 80p
78L12 30p	7812 60p	79L12 70p	7915 80p
78L15 30p	7815 60p	7905 80p	LM723 35p


HARDWARE

MINIATURE TRANSFORMERS

240 Volt Primary

Secondary rated at 100mA.

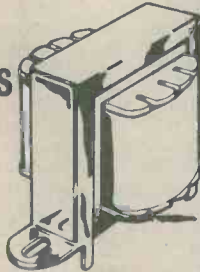Available with secondaries of:
6-0-6, 9-0-9 and
12-0-12. 92p. each.



LOUDSPEAKERS

56mm dia. 8 ohms	70p
64mm dia. 8 ohms	75p
64mm dia. 64 ohms	75p
70mm dia. 8 ohms	100p
70mm dia. 80 ohms	110p



TERMINALS

Rated at 10A. Accepts 4mm plug, black, blue, green, brown and red. 22p

SWITCHES

Subminiature toggle. Rated at 3A 250V.
SPDT 70p SPDT centre off 75p
DPDT 80p DPDT centre off 95p

Standard toggle

SPST 34p DPDT 48p

Wavechange switches.

1P12W, 2P6W, 3P4W or 4P3W all 43p ea.

Miniature switches (non-locking)

Push to make 15p Push to break 20p

Slide switches (DPDT)

Miniature 14p Standard 15p

CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p



TRANSISTORS

AC127 17p	BCY71 14p	ZTX109 14p
AC128 16p	BCY72 14p	ZTX300 16p
AC176 18p	BD131 35p	2N697 12p
AD161 38p	BD132 35p	3N1302 38p
AD162 38p	BD135 38p	2N2905 22p
BC107 8p	BD139 35p	2N2907 22p
BC108 8p	BD140 35p	2N3053 18p
BC109 8p	BF244B 36p	2N3055 50p
BC147 7p	BFY50 15p	2N3442 135p
BC148 7p	BFY51 15p	2N3702 8p
BC149 8p	BFY52 15p	2N3704 8p
BC148 8p	MJ2955 98p	2N3705 9p
BC177 14p	MPSA06 20p	2N3706 9p
BC178 14p	MPSA56 20p	2N3708 8p
BC179 14p	TIP29C 60p	2N3819 22p
BC182 10p	TIP30C 70p	2N3904 8p
BC182L 10p	TIP31C 65p	2N3905 8p
BC184 10p	TIP32C 80p	2N3906 8p
BC184L 10p	ZTX107 14p	2N4058 12p
BC212 10p	ZTX108 14p	2N5457 32p
BC212L 10p		2N5458 30p
BC214 10p		2N5459 32p
BC214L 10p		2N5777 50p
BC477 19p		
BC478 19p		
BC479 19p		
BC548 10p		
BCY70 14p		

DIODES

1N914 3p	1N5401 13p
1N4001 4p	BZY88ser 8p
Full spec. product.	
1N4148 £1.40/100. £11/1000	

LINEAR

THIS IS ONLY A SELECTION!	CA3140 38p	NE555 21p
709 28p	LM301AN 26p	NE556 50p
741 16p	LM318N 85p	NE565 85p
747 40p	LM324 45p	NE567 170p
748 30p	LM339 45p	SN76003 200p
CA3046 55p	LM380 75p	SN76013 140p
CA3080 70p	LM382 120p	SN76023 140p
CA3130 90p	LM1830 150p	SN76033 200p
	LM3900 50p	SN76477 220p
	LM3909 65p	TBA800 70p
	MC1496 60p	TDA1022 650p
	MC1458 32p	ZN414 75p

CAPACITORS

TANTALUM BEAD each
0.1, 0.15, 0.22, 0.33, 0.47, 0.68,
1 & 2.2uF @ 35V 8p
4.7, 6.8, 10uF @ 25V 13p
22 @ 16V, 47 @ 6V, 100 @ 3V 16p

MYLAR FILM
0.001, 0.01, 0.022, 0.033, 0.047
0.068, 0.1 3p
0.068, 0.1 4p

POLYESTER
Multilaid C280 series
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22
0.33, 0.47 10p
0.68 14p
1.0uF 17p

CERAMIC
Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF 2p

RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p
						7p
						13p
100						20p
			220			
25v	10	22	33	47		5p
						8p
						10p
				470		15p
						23p

CONNECTORS

JACK PLUGS AND SOCKETS

	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

DIN PLUGS AND SOCKETS

	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

1mm PLUGS AND SOCKETS
Suitable for low voltage circuits. Red & black Plugs 6p each Sockets 7p each.

4mm PLUGS AND SOCKETS
Available in blue, black, green, brown, red, white and yellow Plugs 11p each Sockets 12p each

PHONO PLUGS AND SOCKETS
Insulated plug in red or black 9p
Screened plug 13p
Single socket 7p Double socket 10p

VERO

Size in.	0.1in.	0.15in.	Veropins—
2.5 x 1	14p	13p	single sided
2.5 x 3.75	42p	40p	per 100
2.5 x 5	52p	50p	0.1in 35p
3.75 x 5	60p	60p	0.15in 40p
3.75 x 17	195p	180p	

BOXES



Aluminum boxes with lid and screws

	Length	width	height	
AL1	3	2	1	48p
AL2	4	3'	1 1/2	58p
AL3	4	3	2	65p
AL4	6	4	2	70p
AL5	6	4	3	85p
AL6	8	6	2	116p

THYRISTORS

Plastic-cased Thyristors Texas

	4A	8A	12A
100V	36p	45p	62p
200V	42p	53p	68p
400V	51p	66p	86p

TRIACS

Plastic-cased Triacs Texas. All rated at 400V.

4A	70p	12A	90p	20A	185p
8A	80p	16A	95p	25A	215p


CMOS

4001 12p	4018 55p	4050 25p
4002 12p	4023 12p	4066 35p
4007 12p	4024 40p	4068 18p
4011 12p	4026 90p	4069 12p
4013 28p	4027 30p	4071 12p
4015 50p	4028 48p	4081 13p
4016 30p	4029 50p	4093 45p
4017 48p	4040 60p	4510 65p
	4042 50p	4511 65p
	4046 90p	4518 65p
	4049 25p	4520 60p

FULL DETAILS IN CATALOGUE!

SKTS

Low profile by Texas

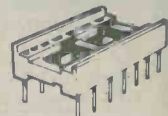

8 pin	8p	16 pin	11p	28 pin	22p
14 pin	10p	24 pin	18p	40 pin	32p
Soldercon pins 100 50p, 1000 370p					

OPTO

LED's

0.125in	0.2in	each	100+
Red	TIL209	TIL220	9p 8p
Green	TIL211	TIL221	13p 12p
Yellow	TIL213	TIL223	13p 12p
Clips	3p	3p	

DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

RESISTORS

Carbon film resistors. High stability, low noise 5%

E12 series, 4.7 ohms to 10M. Any mix

	each	100+	1000+
0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS
Very high stability, low noise rated at 1/2W 1%. Available from 51ohms to 330k in E24 series Any mix.

0.25W	each	100+	1000+
	4p	3.5p	3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 64 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER 2500 STOCK ITEMS.



WHY NOT VISIT OUR NEW SHOP

We welcome callers at our new premises at the address below (5 mins. from High St.) We are open Mon - Sat, 9am-6pm. Special offers available.

Express telephone order service. Orders received before 5pm, are shipped first class on that day. Contact our Sales Office now! Tel: 01-464 2951/5770.



Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.

BARCLAYCARD & ACCESS WELCOME.



Mail orders to: STEVENSON (Dept RE)

76 College Road, Bromley, Kent, England

TRADE COMPONENTS

PAY A VISIT — THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. CALLERS PAY LESS ON MANY ITEMS AS PRICES INCLUDE POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMERS RISKS UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST.

OFFERS CORRECT AT 23/4/79 APPLICABLE TO ORDERS RECEIVED DURING MAY.

VALVE BASES

Printed circuit B7G	7p
Chassis B7-B7G	11p
Shrouded Chassis B7G-B8A	13p
B12A tube. Chassis B9A	13p
Speaker 6" x 4" 5 ohm ideal for car radio	£1.55
4 1/4" diam. 30 Ω	£1.75
2 1/2" diam. 32 or 8 Ω	£1.07
TAG STRIP—6 way 5p	5 x 50pF or 1000 +
8 way 10p Single 2p	300pF trimmers 35p

Car type panel lock and key 65p

Transformer 9V 4A £3.78

Aluminium Knobs for 1/4" shaft. Approx. 5/8" x 7/8" with indicator Pack of 5 95p

JAP 4 gang min. sealed tuning condensers 40p

ELECTROLYTICS Many others in stock

Up to 10V 25V 50V 75V 100V 250V 350V 500V MFD	63-	200-	300-	450-
10 6p	7p	7p	10p	13p
25 6p	7p	7p	10p	13p
50 6p	7p	7p	12p	16p
100 7p	8p	13p	15p	24p
250 12p	13p	15p	22p	36p
500 13p	15p	22p	30p	55p
1000 16p	27p	50p	60p	—
2000 28p	47p	55p	93p	£1.20

As total values are too numerous to list, use this price guide to work out your actual requirements 8/20, 10/20, 12/20, 22/50, 47/25. Tub. Tant 24p each 16-32/275V, 100/150V, 100-100/275V 40p 50-50/385V, 2+2/200V non polar, 32-32-50/300V, 20-20-20/350V 0.1+0.1/500V AC 80p 200V, 100-200-60/300V £1.30 100-300-100-16/300V £1.85

RS 100-0-100 micro amp null indicator Approx. 2" x 1/2" x 1/2" £1.85

INDICATORS

Bulgin D676 red, takes M.E.S. bulb 38p
12 volt, or Mains neon, red pushfit 23p
R.S. Scale Print, pressure transfer sheet 12p

CAPACITOR GUIDE — maximum 500V
Up to .01 ceramic 4 1/2p. Up to .01 poly 6p .013 up to .1 poly etc. 7p. .12 up to .68 poly etc. 8p. Silver mica up to 360pF 10p, then to 2,200pF 13p; then to .01 mfd 21p.
1/750 13p. .01/1000, 8/20, .1/900, .22/900, 4/16, 25/250 AC (600V/DC), 3/600 15p.
5/150, 10/150, 40/150/50p.
Many others and high voltage in stock.

SONNENSCHNEIN/POWERSONIC DRI-FIT RECHARGEABLE SEALED GEL (Lead Antimony) BATTERY, 6V 1 amp.hr. (3 1/4" x 2" x 1 1/4") £3.70.
6 amp. hr. (4 1/2" x 2" x 3") £7.60
Ex-equipment, little used.

CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 9p each

1 1/2 glass fuses 250 m/a or 3 amp (box of 12) 20p
Bulgin 5mm Jack plug and switched socket (pair) 40p

Reed Switch 28mm, body length 11p

Aluminium circuit tape, 1/8 x 36 yards—self adhesive. For window alarms, circuits, etc. 95p

TV MAINS DROPPERS

5 assorted multiple units for 75p

100pF air-spaced tuning capacitor £1.30
5 1/4" x 2 1/4" Speaker, ex-equipment 3 ohm 65p
2 Amp Suppression Choke 10p
3 x 2 1/2 x 1 1/8" PAXOLINE 5 for 35p
4 1/2 x 1 1/2 x 1 1/8" 10 for 15p
PVC or metal clip on MES bulb Holder 5 for 30p
VALVE RETAINER CLIP, adjustable 5 for 15p

Sub-miniature Transistor Transformer 35p
Valve type output transformer 90p

POT CORES with adjuster
LA2508-LA2519 43p per pair

16 Watt Power Amp. Module
35v 1A power required, giving 16 watt RMS into 8 Ω £3.45

REGULATED TAPE MOTOR
Grundig 6V approx. 3" x 1 1/2", inc. shock absorbing carrier, or Jap 9V, 1 1/2" diam. £1.05

3.5mm metal stereo plug 30p
Fane 8 ohm 3" sq. heavy duty communications speaker £1.60

RS neg. volt regulator 103, 306-099 (equiv. MPC900) 10A, 100 watt 4-30 volt. Adjustable short circuit protection. Normally £12.50+. £6.65

BOXES — Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 57p clear perspex sliding lid, 46 x 39 x 24 mm 15p.

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 65p; 80 x 150 x 50mm black 97p; 109 x 185 x 60mm black £1.52.

DIECAST ALI superior heavy gauge with sealing gasket, approx 6 1/2" x 2 1/2" x 1 1/2" £1.50; 3 1/2" x 2 1/2" x 1 1/2" £1.25.

VARIABLE CAMM PROGRAMMER 10, 12 or 15 pole 2 way, 50VAC motor — series with 1mfd, or 3k 10W or 15W pygmy bulb for mains operation. Ex equipment £4.32

SWITCHES

Pole	Way	Type	Price
1	2	Slide	15p
6	2	Slide	24p
2	1	Rotary Mains	28p
2	Alternating	Micro with roller	30p
2	3	Minlature Slide	20p
2	1	Toggle	42p
1	2	Sub-Min Toggle	75p
2	Alternating	2A Mains Push (3/4" hole)	43p
2	Alternating	Slide	15p

S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 60p; 1 pole 2 way 10 amp oblong clip in mains rocker appliance switch 38p

Standard thumb-wheel switch 0-9 in 1248N or B.C.D., or Comp. 1242 also 2p co. £1.20
Standard Lever Key Switch D.P.D.T. locking plus D.P.D.T. and S.P.S.T. Heavy Duty non latching 82p

AUDIO LEADS

3 pin din to open end, 1 1/2yd, twin screened 45p
5 pin din 180° to 2-phono 70p
3 pole jack plug to tag ends, 4ft 45p

COMPUTER & AUDIO BOARDS/ASSEMBLIES
VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAMP RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES, INTEGRATED CIRCUITS, ETC.

3lb for £2 7lb for £3.70

1k horizontal preset with knob 10 for 40p	3" Tape Spools 5p
	1" Terry Clips 5p
	12 Volt Solenoid 40p

ENM Ltd. cased 7-digit counter 2 1/4 x 1 1/4 x 1 1/4" approx. 12V d.c. (48 a.c.) or mains £1.10

Auto charger for 12v Nicads, ex-new equipment £5.19

Miniature 0 to 5mA d.c. meter approx 1/8" diameter £1.25
RS Yellow Wander Plug Box of 12 40p
18 SWG multicore solder 3 1/2p foot

SAPPHIRE STYLII, 15 different; dual and single point, current and hard to get types. My mix £2.

BRIAN J. REED

161 ST. JOHNS HILL, BATTERSEA, LONDON SW11 1TO
Open 10 a.m. till 7 p.m. Tuesday to Saturday. VAT receipts on request.
Terms: Payment with order Telephone: 01-223 5016

Digital count unit. Counts in steps of 1, 2, 5 or 10 with total limit switch (2 x D.I.L. BCD), reed relay remote output. Mains power supply, relay and delay unit. UNUSED. £5.40
Displays on 2 Minitron. 7 segments sold separately.

£1.10
£3.25

RELAY 6 amp changeover. Mains coil 200µA F.S.D. level Meter 1 1/8" x 1 1/2"

DEAC rechargeable NICAD 450K. Capacity 6V 450 m.a.h. at 10 hour rate. Ex-new equipment £4.11

2.5A r.f. thermo-couple and meter 2 1/4" square £3.80

Crouzet 30-minute timer-programmer, multi-variable contacts £7.56

ACOS DUST JOCKEY Automatic record cleaner £1.30

Mail Order Over £50 deduct 10% Over £100 deduct 20%

McMurdo 4 or 8 way plug and socket ex-equipment 50p

"Makswitch" 1p 10-way wafer 15p Wood cased 8-12V buzzer £2.50

100 Capacitors £3.00
 100 Resistors 1W £2.00
 100 Resistors up to 1/2W £1.00
 100 Resistors 2-5W £3.00
 100 Wirewound Resistors £4.50
 Well mixed values and voltages

Mullard +12-0-12V 1A, 4A stabilized, regulated, power supply. £12.00
 27V 5A Double section bobbin transformer £4.32

UK — Postal Orders for same day service. Cheques require 8 days from a Tuesday banking to ensure clearance: export — banker's draft (sterling) same day service. Foreign currency money orders etc. can lose value and take 4-6 weeks to clear.

SEMICONDUCTORS Full spec. by Mullard etc. Many others in stock

AC126/128/176 20p	BD113 57p	BFX84/88.89 20p
ACY29 22p	BD115 36p	BFY51 16p
AD161/2 match pr. 85p	BD116(BRC116T) £1.15	BFY90 57p
ADZ12 £4.00p	BD130Y £1.50	BR101 34p
AF116 20p	BD131/2/3 40p	BR39/56 29p
AF124/6/7 28p	BD135/6/7/8/9 35p	BSV64 36p
AF139 23p	BD137/138 match pr 82p	BSV79/80 F.E.T.s 90p
AF178/80/81 36p	BD140/142 35p	BSV81 Mosfet £1.00
AF239 35p	BD201/2/3/4 92p	BSX20/21/78 16p
ASU27/73 35p	BD232/3/4/5/8 65p	BSY40 30p
AY110/113 £2.50	BDX77 £1.16	BSY95A 14p
BC107/8/9 + A/B/C 8p	BD437 58p	BU204+Mount Kit £1.85
BC147/8/9 + A/B/C 8p	BF/115/167/173 18p	BU208 £2.26
BC157/8/9 + A/B/C 8p	BF178/9 23p	CV7042 (OC41/44 ASY63) 12p
BC173 8p	BF180/1/2/3/4/5 18p	GET111/E112 45p
BC178A/B 179B 14p	BF194/5/6/7 8p	OC45(ME2) 13p
BC182/184/LC 11p	BF194A, 195C 8p	ON222 23p
BC186/7 23p	BF200 258 324 23p	R2008B/2010B £2.30
BC213L/214B/238 13p	BF262/3 35p	TIP30 50p
BC327/8 337/8 10p	BF336/274 31p	TIS43 (2N2646) 39p
BC547/8+A/B/C 13p	BF525 Dual Mosfet £1.15	uA7805 £1.85
BC556/7/7B/8/9 11p	BFT61 40p	ZT1486 £1.15
BCX32/36 16p	BFW10/11 F.E.T. 46p	ZTX300/341 9p
BCY31 90p	BFW30 £1.15	2N393 (MA393) 35p
BCY70/1/2 14p	BFW57/58 21p	2N456A 67p
BCZ11 32p	BFX12/29/30 23p	2N706A 18p

Amp	Volt	BRIDGE RECTIFIERS
1	1,600	BYX10 34p
1	140	OSH01-200 30p
5	100	Ex Equip 73p
0.6	110	EC433 20p
5	400	Texas £1.10
2 1/2	100	I.R. 48p
3 1/2	100	B40C 3200 58p

RECTIFIERS		
Amp	Volt	
M1 1/2	68	5p
1N4005/6 1	6/800	8p
1N4007/BYX94 1	1250	8p
BY103 1	1,500	21p
SR100 1.5	100	9p
SR400 1.5	400	10p
REC53A 1.5	1,250	16p
LT102 2	30	15p
BYX22-200 1 1/2	300	25p
BYX38-300R 2.5	300	48p
BYX38-600 2.5	600	52p
BYX38-900 2.5	900	60p
BYX38-1200 2.5	1,200	65p
BYX49-300R 3	300	35p
BYX49-600 3	600	42p
BYX49-900 3	900	47p
BYX49-1200 3	1,200	60p
BYX48-300R 6	300	47p
BYX48-600 6	600	60p
BYX48-900 6	900	70p
BYX48-1200R 6	1,200	92p
BYX72-150R 10	150	42p
BYX72-300R 10	300	52p
BYX72-600R 10	600	65p
BYX42-300 10	300	36p
1N5401 3	100	16p
1N5402 3	200	18p
MR866 3	600	24p
BYX42-900 10	900	92p
BYX42-1200 10	1,200	£1.07
BYX46-300R* 15	300	£1.19
BYX46-400R* 15	400	£1.75
BYX46-500R* 15	500	£2.00
BYX46-600* 15	600	£2.30
BYX20-200 25	200	72p
BYX52-300 40	300	£2.05
BYX52-1200 40	1,200	£2.90
RAS310AF* 1.25	1,250	48p

*Avalanche type

Amp	Volt	TRIACS	
25	900	BTX94-900	£4.50
25	1200	BTX49-1200	£6.75

Diode Characteristic, Equiv., and Substitution Book 82p

Transistor equivalents and substitution Book 1 38p Book 2 82p

Chrome Car Radio fascia 28p

Rubber Car Radio gasket 10p

DLI Pal Delayline 80p

Relay Socket miniature 2PCO 20p

28 pin d.i.l. socket low profile 38p

Colour EHT Tray 3000/3500 £6.50

Nylon self-locking, 3 1/2" tie clips 1.5, 10, 22 or 750 µh choke 12p

0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive 4 1/2" dia. 13p

Mullard Semiconductor, Valve & Component Data Book 1976-78 50p

OPTO ELECTRONICS		
Diodes	Photo transistor	
BPX40 57p	BPX29 92p	
BPX42 92p	OCF71 75p	
BPY10 92p		
(VOLIAC)		
BPY68 .2" Red 16p		
BPY69 92p	TIL209 .125" Red 14p	
BPY77 92p	Green 16p	
Wire end neons 9p		

PHOTO SILICON CONTROLLED SWITCH

BPX66 PNP 10 amp £1.15
3" red 7 segment L.E.D. 14 D.I.L. 0-9 + D.P. display 1.9v 19m/a segment, common anode .95p
RS 0.6in. green £2.25
Minित्रon 0.3in 3015F filament £1.25
CQY11B L.E.D. Infra red transmitter £1.15 One fifth of trade
R.S. Battery Holder for 4 x HP/SP 1130p

McMurdo PP108 8 way edge plug 12p
Multicore Solder 1/2kg. 16 or 18 or 20 s.w.g. 60/40£5.00
3 inch 8 Ω speaker£1.15

New unmarked, or marked ample lead ex new equipment

ACY17-20 10p	TIC44 28p
ASZ20 10p	2G240 £1.17
ASZ21 35p	2G302 6p
BC186 13p	2G401 6p
BCY30-34 24p	2N711 28p
BCY70/1/2 10p	2N2926 8p
BY126/7 5p	2N598/9 8p
HG1005 12p	2N1091 10p
HG5009 4p	2N1302 10p
HG5079 4p	1N1907 £1.17
L78/9 4p	Germ. diode 2p
M3 12p	2N3055 5p
OA81 4p	Motorola 36p
OA47 4p	GET120 (AC128 in 1" sq. heat sink 22p
OA200-2 4p	GET872 15p
OC23 27p	2S320 34p
OC200-5 24p	TIS43 25p
C106 THY 38p	

MINIATURE EDGE METERS

100uA f.s.d., scaled 0.5, 12V illuminated blue perspex front, 35mm x 14mm £3.45
200uA level meter, clear front. 10 x 18mm £1.20

2N2142 80p
2N2483 28p
2N2904/5/6/7/7A 18p
2N3053 16p
2N3065 R.C.A. 60p
2N3133/4062 24p
2N3553 56p
2N4037 39p
2N5484 FET 39p
2N5956 87p
2SA141/2/360 36p
2SB135/6/457 24p
2SC372/644/735 15p
2SC853 30p
40250 (2N3054) 35p

CATALOGUE
 38, 11 x 8 ins illustrated sheets, listing approx. 5,250 items, photo printed on day requested, from constantly updated masters, to ensure latest stock position, 75p (refundable with orders) plus large 24p s.a.e. or label.

TRANSFORMERS
 Ferromag C core. Screens 95-105-115-125-200-220-240v input output 17v 1/2A x 2 + 24-0-24v 1.04A+20v 1mA. these current ratings can be safely exceeded by 50%. £4.90
 Cassette Dynamic Micro phone with switch and twin plug £1.80
 Telephone Pickup, sucker with lead and 3.5 plug.70p

Amp	Volt	THYRISTORS	
1	240	BTX18-200	.35p
1	400	BTX18-300	.41p
1	240	BTX30-200	.35p
4	500	40506	.80p
1.5	500	BT107	£1.14
6.5	500	BT109-500R/SCR957/BRC4444	£1.14
20	600	BTW92-600RM	£3.40
15	800	BTX95-800R Pulse Modulated	£8.75

PAPER BLOCK CONDENSER

0.25MFD 800 volt 87p
1MFD 250 volt 54p
1MFD 400 volt 65p

TV KNOB
 Dark grey plastic for recessed shaft (quarter inch) with free shaft extension 8p

CHASSIS SOCKETS
 Car Aerial 11p, Coax 8p, 5 pin 180° 11p, 5 or 6 pin 240° din 8p, speaker din switched 13p, 3.5 mm switched 7p, stereo 1/2" jack enclosed 20p.

SPECIAL OFFERS

2500 mfd. 40v 56p
0.1 mfd. 350/500v 10 for 50p
10000 mfd. 15v 3 for £1.16
6800 mfd. 10v 3 for 90p
32+32/275v 3 for 90p
16 + 32/275v 3 for 80p
8+8 mfd. 375v/4 for 90p
1 mfd. non-polar 350v 10 for £1.19
25000 mfd. 25v 66p
12000/12v 3 for £1.16
G.E.C. 5% HI-stab capacitors 013 061, 066, 069, 075, 08 10 for 65p
AY5 8300 10 for £6
BC548B 500 for £28.50
BC556 500 for £28.50
BCY71 500 for £43.50
BD437 50 for £13.75
2N2906 500 for £43.50
TBA920 10 for £11.50
Vero card handle 10 for 65p
62 Ω 1/2W Resistor 2,000 for £6.75
ON222 (superior matched BF181) 10 for £1.20
68 Volt 10 Watt Zener Diodes.5 for £2.50

OTHER DIODES

1N916 8p
1N4009 9p
1N4148 4p
BA145 29p
Centercol 29p
BZV61/BA148/OA81 12p
BB103/110 Varicap 24p
BB113 Triple Varicap 43p
BA182 15p
OA57/10 17p
BZY88 up to 43 volt 10p
bZX61 11 volt 17p
AA133 10p
BZY96C 10V 34p
BZY95C 33V or 15V.34p

RS Irvinc high temperature wire, 19/0,16, minus 55° to 105°C, 600V 3A, white, black or red. Half trade price at 54p 10M coil.

PVC QUALITY TAPE
 Lasso 10m x 15mm grey 38p
 33m x 33mm green £1.13p

Trimmer: Post stamp type 3-30pF 16p
 10-80pF 19p
 30-140pF 23p

GARRARD
 GCS23T Crystal Stereo Cartridge £1.20
 Mono (Stereo compatible) Ceramic or crystal £1

INTEGRATED CIRCUITS

TBA920 TCA270 £2.20
TAA700 £2.40
TBA800 £1.24
7417/7490/7473 28p
uA702 op amp 53p
721709 38p
74107/74122 52p
SN76228N £2.03
SN76131/75110 £1.55
SN76013N/ND £1.40
TAD100 AMRF £1.22
CA3001 R.F. Amp £1.58
CA3132 £2.22
74151 45p
CD4069 24p
TAA300 1 wt Amp £1.15
TAA550 Y or G 26p
TAA263/74LS192 70p
TAA320 £1.15
7400/7401 16p
7402/4/10/20/30 18p
7414/74132N 64p
7438/7474/7432 27p
AY5 8300 £1.00
7483/74S20 79p
7493/CD4013 41p
LM300 2/20V reg £1.16
LM1303N £1.15
74154/TBA810 £1.02
TBA6500/74S112 £1.80
ZN414 £1

HANDLES
 Rigid light blue nylon 6 1/2" with secret fitting screws 11p

Belling Lee white plastic surface coax outlet box 40p

Miniature Axial Lead Ferrite Choke formers 5 for 13p

RS 10 Turn pot 1% 250 500 Ω 1K, 50K £1.70

Copper coated board 18 1/2" x 2 1/2" 40p

Geared Knob 8-1 ratio. 1 1/2" diam., black 93p

KLIPPON 25A 440v TERMINAL BLOCKS
 Professional leaf spring clamp, twin with clip-over cover 11p
 Strip of 4, 40A 440V 16p

VAT & POST PAID

MINIMUM ORDER £3 OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS (UNDER £1.00 TOTAL ALSO INCLUDE 9p S.A.E.)

NO MORE TO ADD — Prices INCLUDE UK VAT and Post/Packing
 ALL ENQUIRIES, ETC., MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

<p>MOTORS I-5 to 6VDC Model Motors, 20p. Sub. Min. 'Big Inch' Precision motors, 115VAC 3 rpm, 30p. 12VDC 5 Pole Modle Motors 35p. 8 track 12VDC motors, new £1.25. Cassette Motors 6VDC ex. equip., 65p. Crouze geared motor, 115VAC 4 rpm new 95p. Smiths clock motor, synchronous 240VAC 1 rev per hour £1.75.</p>	<p>TRANSFORMERS All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 73p each (15p). 12-0-12V 100mA 90p (15p). 0-6V, 0-6V, 280mA £1.10 (20p). 0-4-6-9V 200mA these have no mounting bracket, 65p (15p). 12V 500mA 95p (22p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.50 (54p). 30-0-30V 1 amp £2.75 (54p). 20-0-20V 2 amp £3.50 (54p). 0-12-15-20-24-30V 2 amp £4.50 (54p). 20V 2.5 amp £2.20 (54p).</p>	<p>FETS/SCRS ETC Union carbide N channel FET similar to 2n3819 15p each. 3N140 or BFW61 types 40p each. M203 dual matched pair of single gate mosfets in one can 40p. 2N5062 plastic (TO92) SCR 100V 800mA 18p each. BX504 Opto isolators, 4 lead infra red led to photocell 25p each.</p>	<p>AEROSOL SERVICE AIDS, SERVISOL Switch Cleaner 226gm 54p. Freezer 226gm 65p. Silicone Grease 226gm 68p. Foam Cleanser 370gm 55p. Plastic Seal 145gm 55p. Excel Polish 240gm 40p. Aero Klene 170gm 45p. Aero Duster 200gm 58p.</p>	<p>TOOLS SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.75 (spare nozzles 65p each). Good Quality side cutters, insulated handles, 5" £1.35. Good Quality snub nosed pliers, insulated handles, 5" £1.35. Antex Model C 15 watt soldering irons, 240VAC £3.60. Antex Model CX 17 watt soldering irons, 240VAC £3.60. Antex Model X25 25 watt soldering irons, 240VAC £3.60. Antex ST3 iron stands, suits all above models £1.40. Antex heat shunts 12p each. Servisol Solder Mop 45p each. Neon Tester Screwdrivers 8" long 40p each. Miyama IC test clips 16 pin £1.75.</p>
<p>SEMICONDUCTORS All full spec. devices. 741 8 pin 6 for £1. No. 555 Timers 22p each. TBA800 audio IC's 50p. 741S (wide bandwidth) 35p. LM380 80p. ZN414 Radio IC 75p. LM3900 40p each. TIL305 alpha numerical displays £2.50. Miniature LDR's (same spec. as ORP12) 30p.</p>	<p>TRIAC/XENON PULSE TRANSFORMERS 1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.</p>	<p>DIODES IN4001 10 for 35p. IN4004 10 for 45p. IN4007 10 for 50p. BY127 10 for 75p. IN914 (numbered) 100 for £2.50. IN4148 (numbered) 100 for £2.25.</p>	<p>SURPLUS BOARDS No. 1, has 14 encapsulated 12V reed relays easily removable £1.95. No. 2, this has at least 11 C106 (50V 2.5A) plastic SCR's, one relay a unijunction transistor and tantalum capacitors £1.95. No. 3, I.F. Boards, these are a complete I.F. board assembly made for car radios, 465Khz, full set of IF's and oscillator coils, trimmers etc., 40p each. No. 4, Lamp flasher board, suitable for low load 240VAC applications, approx. 1 flash per second but can be varied via preset pot. 38p each.</p>	<p>SWITCHES Sub. miniature toggles; SPST (8 x 5 x 7mm) 45p. DPDT 8 x 7 x 7mm 50p. DPDT centre off 12 x 11 x 9mm 75p. PUSH SWITCHES, 16 x 6mm, red top, push to make 14p each, push to break version (black top) 16p each. SLIDE SWITCHES, all DPDT; 15 x 8 x 12mm 12p. 16 x 11 x 9mm 12p. 22 x 13 x 8mm centre off 13p. Multipole slider, double action 12 tags 29 x 9 x 11mm 24p.</p>
<p>PROJECT BOXES Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 43p. 95 x 71 x 35mm 50p. 115 x 95 x 37mm 58p.</p>	<p>MICROPHONES ECM105 Condenser, Omni Directional, 600 ohms, on/off switch £2.95. EM506 Condenser Cardioid, Uni directional, 600 or 50K ohms 30-18Khz, heavy chromed copper case £12.95. DYNAMIC Stick mike, 5,000 ohms, on/off switch, fitted with std. jack £2.95. EM104 Sub. miniature tie pin condenser microphone, 1,000 ohms imp., 50-16Khz., uses deaf aid battery (supplied) £5.25. STANDARD CASSETTE MIKES, 200 ohms, fitted with 2.5/3.5mm jacks, on/off switch £1.25.</p>	<p>MURATA MA401 40kHz Transducers. Rec./Sender £3.25 pair.</p>	<p>POWER SUPPLIES 9 volt DC 120mA regulated supply, will replace PP9 etc. £2.25. SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 400mA, switchable £3.25. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £5.25</p>	<p>MICRO SWITCHES Standard button operated 28 x 25 x 8mm make or break, new 15p each. Roller operated version of the latter, New 19p each. Light action micro, 3 amp make or break 35 x 20 x 7mm, 12p each. Cherry plunger operated micro, 2 normally open, 2 normally closed, plunger 20mm long (40 x 30 x 18mm) 25p each.</p>
<p>VERO POTTING BOXES 49 x 71 x 24mm, available in black or white with lid and 4 screws 39p each.</p>	<p>REPLACEMENT CRYSTAL INSERTS 35mm diam. x 10mm deep 45p each</p>	<p>ELECTRICAL ITEMS 12 way Choc Blocks 2 amp or 5 amp 18p per strip. 13 amp Rubber Extension Sockets, white 38p each. 13 amp Plastic Fused Plugs (foreign) 25p each.</p>	<p>TOSHIBA LEDS TLG113 0.2" Green 13p. TLG115 0.2" Green diffused lens 14p. TLG1070 0.2" Green Flat top 14p. TLR120 0.2" Clear 17p. MAN3A min. (3MM) 7 segment LED displays Comm. anode 40p.</p>	<p>ROCKER SWITCHES 2 amp SPST, single nut mounting, various colours (red, green, white, blue, yellow, black) 19p each. 250VAC 6amp rocker (all white) 21 x 15 x 13mm 17p each.</p>
<p>VERO 'HAND HELD BOX' White ABS, 2.4" x 3.7" tapered, with screws 65p each.</p>	<p>RIBBON CABLE 8 way single strand miniature 20p per metre.</p>	<p>PUSH BUTTON TV TUNERS UHF, not varicap, transistorised new £2.25</p>	<p>BUZZERS MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, four voltage types available, 6-9-12 or 24VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam x 30mm high 60p. GPO OPEN TYPE BUZZER, adjustable, works 5-12VDC 25p each. SIRENS 125mm diameter gold coloured horn, high pitched wailing note of varying frequency, 12VDC £7.45.</p>	<p>TAPE HEADS Mono cassette £1.35. Stereo cassette £3.00. Standard 8 track stereo £1.75. BSR MNI330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly — 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20.</p>
<p>MULTIMETERS Big price reductions on pocket size testers. Model KRT100, 1,000 ohms per volt, mirror scale, range selector switch 1,000 volts AC/DC, 100K resistance, 150ma DC current £4.65. Model KRT101, same spec. as the KRT100 but range selection is via prod insertion £3.75.</p>	<p>SPECIAL OFFER SEMICONDUCTORS Plastic voltage regulators, 1 amp all now reduced in price, 7805, 7812, 7815, 7824 all 75p each. 7905, 7912, 7915, 7924 all 99p each. LM340T 6 volt 1 amp regulator 40p each. 723 14 pin regulators 40p each.</p>	<p>TELEPHONE PICK UP COIL Sucker type with lead and 3.5mm plug 55p</p>	<p>RELAYS Clare Elliot sub. min. sealed relay 10 x 10mm 2 pole C/O. 1.250 ohm coil, new 75p. Miniature encapsulated reed relay 0.1 matrix mounting, single pole make, operates on 12VDC 50p each. Continental series, sealed plastic case relays, 24VDC 3pole change over 5 amp contacts, new 65p. 12VDC (130 ohm) 1 C/O, 3 make and 1 break contacts, new 65p each. Metal Casced Reed Relay, 50 x 45 x 17mm, has 4 heavy duty make reed inserts, operates on 12VDC 35p each.</p>	<p>DECON DALO ETCHING PEN With spare tip 72p.</p>
<p>CONTINUITY TESTERS Tubular with probe and croc. fly lead £1.35, with batts.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>
<p>MORSE KEYS Beginners practise key 95p. All metal fully adjustable type £2.45.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>
<p>MINIATURE LEVEL METERS 1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>
<p>JUMPER TEST LEAD SETS 10 pairs of leads with various coloured croc clips each end (20 clips) 80p per set.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>
<p>New arrivals, 12 volt car stereo motors with pulley 55p. Car radio RF/IF and audio preamp boards 2 transistors, LM382 IC trimmers IF's etc., no info 65p each.</p>	<p>8 track stereo playback heads only 75p each. Car radio boards, complete with 6 transistors, IF's choke etc., these are new but no info available 75p each.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.


BUILD TWO FREE PROJECTS ON CSC

ELECTRONICS BY NUMBERS
FREE PROJECTS
NO 1 & NO 2

ELECTRONICS BY NUMBERS FISH'N'CLIKS

Now using **EXPERIMENTOR BREAD-BOARDS** and following the Instructions in "Electronics by Numbers" ANYBODY can build electronic projects. Look at the diagram, this has the same letter/number system as all **EXP BOARDS**. Look at the "YOU WILL NEED" list and select Q1 this is PNP transistor type HEP-230. This plugs into hole X9, A7 and C9. NOW take C1, a 50 uF capacitor, and put into holes J6 and J14 and do the same with all the components.

NOW YOU HAVE FISH'N'CLIKS

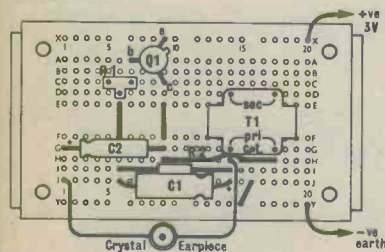

YOU WILL NEED

- B1, B2 - 2x1.5V AAA batteries
- C1, C2 - 50 uF, 12-VDC electrolytic capacitor
- E1 - Crystal earphone
- Q1 - Motorola HEP-230 pnp transistor
- R1 - 5000-ohm pot
- R2 - 27000-ohm, 1/4 watt resistor
- S1 - Spst switch part of R1
- T1 - Mini transistor output transformer; 500-ohm center tapped primary to 8-ohm secondary
- EXP - ANY EXP. BREADBOARD.


The anglers dream come true. This electronic marvel emits a CLIK-CLIK sound that makes fish really hungry. Shove the whole works in a watertight container lower it over the side and wait for the fish to grab the hook.

FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE A COPY OF THE FULL PROJECT FISH'N'CLIKS, AND A COPY OF PROJECT No 1 "TWO TRANSISTOR RADIO".

PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.

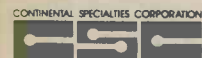- PC - 16 pin. £2.75.
- PC - 16 pin with cable. £6.00.
- PC - 16 with cable and 16 pin clips at both ends. £10.25.



Europe, Africa, Mid-East: CSC UK LTD.
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: SAFFRON WALDEN 21682.
Telex: 817477.

EXPERIMENTOR BREADBOARDS.

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.

EXP.325. The ideal breadboard for 1 chip circuits.
Accepts 8,14,16 and up to 22 pin IC's.
ONLY £1.60.



EXP.350. £3.15.
270 contact points with two 20-point bus-bars.




EXP. 300.
550 contacts with two 40-point bus-bars.
£5.75.



EXP. 650 for Micro-processors. £3.60.




EXP 4B.
More bus-bars.
£2.30.

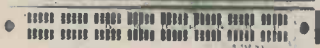

ALL EXP.300 Breadboards mix and match with 600 series.

PROTO-BOARDS.

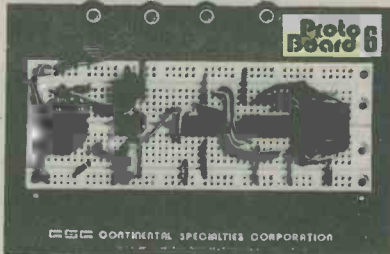THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST.
TWO EASILY ASSEMBLED KITS.



PB.6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

PROTO-BOARD 6 KIT. £9.20.



PB.100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

PROTO-BOARD 100 KIT £11.80.

HOW TO ORDER AND RECEIVE FREE COPY OF FISH'N'CLIKS PROJECT WITH BONUS OF FREE TWO TRANSISTOR RADIO PROJECT.

CSC UK LTD. Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T.
EXP. 325	130	1	£ 2.53
EXP. 350	270	3	£ 4.21
EXP. 300	550	6	£ 7.29
EXP. 650	270	use with 0.6 pitch Dip's Bus-Bar Strip	£ 4.69
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.29
TEST CLIPS			
PC. 16.			£ 3.78
PC.16-18.			£ 7.56
PC. 16-18 Dual Clip.			£12.15
PROTO-BOARDS.			
PB. 6.	630	6	£11.01
PB. 100.	760	10	£13.82

NAME
ADDRESS

Dept.16P

FILL IN COUPON & RECEIVE FREE COPY OF
ELECTRONICS BY NUMBERS PROJECTS No 1 AND No 2

PICK-A-PAK

ZENER DIODES

2 watt metal types
Asstd., untested but
about 80% good.
PAK of 40 for 70p

ROTARY POTS

Various types, singles,
and doubles, new and
coded.
PAK of six for 60p

BD187

Full spec transistors
new and coded
PAK of four — 98p

WIREWOUND RESISTORS

All new and coded,
modern types.
PAK of 50 for 95p

C280 CAPACITORS

Asstd. Pak, new and
coded types.
PAK of 40 for 70p

ELECTROLYTIC CAPACITORS

All new asstd., modern
transistor types.
PAK of 50 for 90p

TIP33

Full spec transistors
new and coded.
PAK of three — 85p

VARI-CAP DIODES

New, approx. 500pf,
untested but 80%
good, uncoded.
PAK of 40 for 70p

THYRISTORS

All new, some coded,
untested but 80%
good.
PAK of 25 for 70p

L.D.R.'s

Similar to ORP12
new, full spec.
PAK of two — 80p

AC128

Coded transistors
untested — approx. 80%
good.
PAK of 40 for 70p

ASSTD. RESISTORS

Pak of modern $\frac{1}{8}$ W
and $\frac{1}{4}$ Watt types.
PAK of 100 for 60p

E112 FETS

N-channel, new, full spec
similar to 2N3819's.
Coded.
PAK of four — 60p

POLYSTYRENE CAPACITORS

Pak of all new types,
coded.
PAK of 50 for 70p

CERAMIC CAPACITORS

Asstd. Pak, all new and
coded types.
PAK of 40 for 70p

ASSTD. TRANSISTORS

All new and most coded
90% good.
PAK of 50 for 95p

BC107/8/9's

Uncoded, untested but
approx. 80% good.
PAK of 40 for 70p

ASSTD. I.C.'s

All new, some coded
but all untested.
PAK of 30 for 40p

Please add 20p extra for post/packing U.K.,
overseas at cost. Minimum order value £1.00.
Cheques need 8 days to clear.

MAIL ORDER ONLY

We do not have any retail facilities.

M. CUTLER
125 HAZLEBURY ROAD,
LONDON SW6 2LX

LATEST BOUND VOLUME No. 31 of "Radio & Electronics Constructor"

NEW LARGER FORMAT



AUGUST 1977 to JULY 1978

Comprising
768 pages
inc. index

PRICE £5.20 P&P 90p

BOUND VOLUME No. 27
(August 1973 to July 1974)
Price £3.00 P&P 90p

BOUND VOLUME No. 28
(August 1974 to July 1975)
Price £3.20 P&P 90p

BOUND VOLUME No. 29
(August 1975 to July 1976)
Price £3.50 P&P 90p

BOUND VOLUME No. 30
(August 1976 to July 1977)
Price £3.70 P&P 90p

Limited number of these
volumes still available.

We regret all earlier volumes are now
completely sold out.

Available only from
DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN

RADIO AND ELECTRONICS CONSTRUCTOR

Come to the Great British Electronics Bazaar

"ALLY PALLY"
Thursday-Saturday
28th-30th June.

FREE!

(AND WAIT TILL YOU SEE OUR SEMINAR PROGRAMME)

The Great Big 'Bazaar' for the hobbyist, amateur, and small buyer.

There's never been an event like this before.

First, the very scale of the exhibition is huge. Virtually all the companies you're used to hearing about (and buying from) will be there. Companies like Fluke and Gould showing off their low cost multimeters; smaller but important manufacturers like Lektrokit and Chromasonics; and even the R.S.G.B. who will have a station 'on the air' throughout the 'Bazaar.'

Then there are the suppliers of low-cost components and equipment. Plus almost all the journals in the business. Plus, oh, so many more interesting people catering for your needs (including computer kits!).

And you get in FREE if you send an s.a.e. (see alongside).

The Seminars.

If you would like to hear just what the experts have to tell you, a season ticket for three whole days can be yours for only £1.50.

Send an s.a.e. and we'll give you all the information (just use the coupon).



Our home for three days - Alexandra Palace, where it all began. (Our seminars are sited alongside the organ - for those who know this unique hall.)

SEMINAR TICKETS

£1.50.

I'd like to sit in at your seminars. (And like a free ticket to the exhibition.) Send me full details, please, and I enclose a large-ish s.a.e.

Name:

Address:

.....

.....

Post to: The Bazaar, 34/36 High Street, Saffron Walden, Essex.

When?

Between Thursday to Saturday 28th-30th June.

You'll be in very good company; some ten thousand enthusiasts - and over a hundred stands displaying all that you want to see.

You'll come?

Eyes down for the appropriate coupon.

ADMISSION FREE

(or 50p on the door).

I'd like to see 'The Bazaar' FREE. I enclose a large-ish s.a.e. and will receive by return a ticket and full information.

Name:

Address:

.....

.....

Post to: 'The Bazaar,' 34-36 High Street, Saffron Walden, Essex. If you'd rather just pay 50p, go to Wood Green Tube Station and take a bus (every 3 minutes) to Alexandra Palace. We're open 10 am-6 pm daily, Thursday to Saturday, 28th-30th June.



Our Symbol.
We think it tells
you just what the
Bazaar is all about.

PP9 ELIMINATOR UNIT

By M. V. Hastings

- Supplies current up to 100mA
- Fully regulated
- Fantastic savings in running costs

This simple and inexpensive eliminator unit is designed to fit into the battery compartment of a transistor radio which normally employs a PP9 battery, thereby enabling the radio to run from the mains supply. When the portability given by battery operation is not required, or is required only occasionally, the eliminator unit offers far lower running costs, these being of the order of 300 to 400 hours of use for one penny! The initial price of the eliminator is obviously higher than that of a replacement battery, but the extra expense involved will soon be recovered in saved battery costs. Fitting the eliminator does not preclude future battery operation; the unit is built in a case slightly smaller than a PP9 battery, and it can be fitted and removed as easily as can a battery.

A power supply of this type is also very useful to have in the electronics workshop when building, testing and servicing small items of equipment intended for 9 volt operation. The unit gives a nominal output of 9 volts at currents up to 100mA maximum. It incorporates output current limiting which prevents the current from rising much above 100mA even if the output is short-circuited. The output is well stabilized and the voltage drop between zero load and full output current is only about 100mV. The output is also well smoothed, with hum and noise level being a fraction of a millivolt at low load currents and only a few millivolts at full load.

THE CIRCUIT

Fig. 1 gives the complete circuit of the PP9 battery eliminator.

The mains supply is applied via the fuse FS1 and on-off switch S1 to the primary of the isolating and step-down transformer T1. The fuse and the on-off switch are not included with the other circuitry of the unit. The fuse is fitted in the 13 amp 3-way mains plug which supplies the eliminator, and the switch is inserted in the mains lead at any convenient point. It is, of course, desirable to have the mains on-off switch separate from the eliminator

as, otherwise, it would in most instances be necessary to open the back of the receiver to switch the unit on and off. The receiver on-off switch may be left turned on all the time, the set being switched on and off by the eliminator mains switch. This is preferable to having the eliminator permanently running and switching on and off at the receiver switch.

T1 is a sub-miniature mains transformer having a secondary rated at 12-0-12 volts at 100mA. Transformers with these secondary ratings are available from a number of suppliers, including Home Radio. The secondary connects to the full-wave rectifier circuit given by diodes D1 and D2, and reservoir capacitor C1.

The voltage regulator circuit incorporates TR1, TR2 and TR3, and employs a well-known configuration. TR1 is conducting all the time, and its


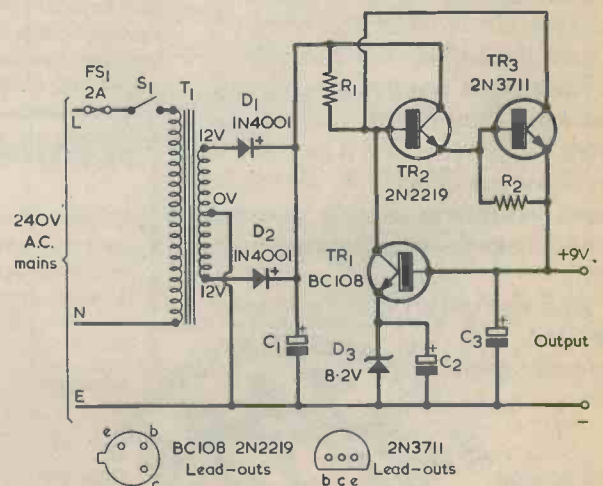


Fig. 1. The circuit of the PP9 battery eliminator. This offers a stabilized output at slightly less than 9 volts with a current limit of 100mA

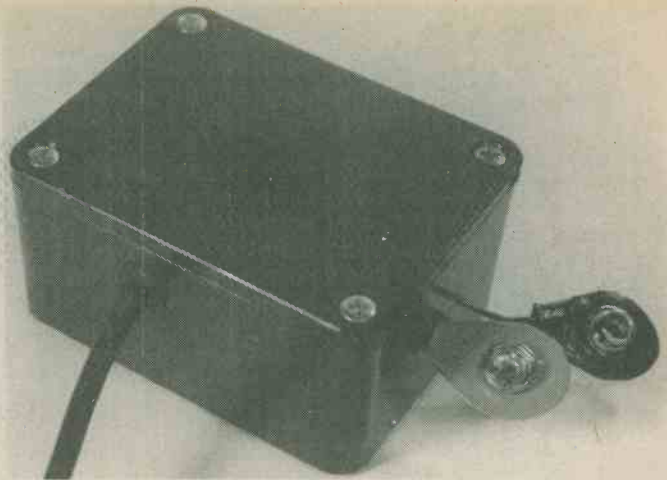The eliminator unit is housed in a plastic case having approximately the same dimensions as a PP9 battery



emitter is held at about 8.2 volts above the negative rail by zener diode D3. TR2 is an emitter follower and its emitter couples via R2 (part of the current overload circuit, which is described shortly) to the base of TR1. After switch-on, the voltage at the emitter of TR2 rises until it reaches 8.85 volts, whereupon the consequent 0.65 volt across the base-emitter junction of TR1 causes this transistor to pass collector current. If the voltage at TR1 base attempts to rise higher it causes TR1 to pass a heavier collector current, thereby reducing the voltage at TR2 base and counteracting the rise in voltage at TR1 base. As can be seen, a negative feedback loop is set up as soon as TR1 commences to pass collector current, and this stabilizes the output voltage at the zener diode voltage of 8.2 volts plus the 0.65 volt in the base-emitter junction of TR1.

If a load current is now drawn from the output, it will attempt to take TR1 base negative. The collector current of TR1 will then reduce and allow more current to flow into TR2 base via R1, whereupon the output current available from TR1 emitter increases and brings the output voltage back to the stabilized level.

C2 smoothes any noise or hum present across D3 and its presence gives a lower noise and hum level on the output. The final smoothing capacitor, C3, also reduces noise and hum. C3 is beneficial when the eliminator is supplying a receiver having a Class B a.f. output stage since it enables brief current peaks in excess of the output current limit to be supplied. The stabilizing action of TR1 and TR2 gives further electronic smoothing of the output voltage and is, indeed, largely responsible for the very low noise and hum levels.

The output current flows through R2, and this has no effect on circuit operation until the current rises to around 100mA. The voltage dropped across R2 then exceeds 0.65 volt, causing TR3 to turn on and draw a collector current through R1. It then becomes impossible to draw on increased output current, since this merely results in TR3 reducing the voltage at TR2 base with the consequence that the output voltage falls. Even if the output is short-circuited the output current will still only be typically a little in excess of 100mA, with TR3 conducting sufficiently to bring the output voltage down to zero.

The unit cannot then be damaged due to temporary overloading, although an output short-

circuit cannot be maintained indefinitely unless TR2 is provided with adequate heatsinking. TR2 would otherwise overheat and be damaged. In practice it is as unlikely that a continual short-circuit would be put on the output of the unit as it would be on the terminals of the PP9 battery it replaces, and it was considered not worth-while equipping TR2 with a heatsink.

CONSTRUCTION

The prototype eliminator is housed in a black A.B.S. plastic box measuring 75 by 56 by 35mm, which is available from Progressive Radio, 31 Cheapside, Liverpool 2. This box fitted comfort-

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5%)

R1 1.5k Ω

R2 6.8 Ω

Capacitors

C1 680 μ F electrolytic, 25V Wkg.

C2 10 μ F electrolytic, 25V Wkg

C3 100 μ F electrolytic, 10V Wkg

Transformer

T1 Mains transformer, secondary 12-0-12V at 100mA

Semiconductors

TR1 BC108 D1 1N4001

TR2 2N2219 D2 1N4001

TR3 2N3711 D3 BZY88C8V2

Switch

S1 s.p.s.t. "pressil" (see text)

Fuse

FS1 2A (see text)

Miscellaneous

A.B.S. plastic case (see text)

Verobox type 75-1469-L

Veroboard, 0.01 in. matrix

13A mains plug

PP9 battery connectors

Connection block (see text)

3-core mains lead

Nuts, bolts, wire, solder, etc

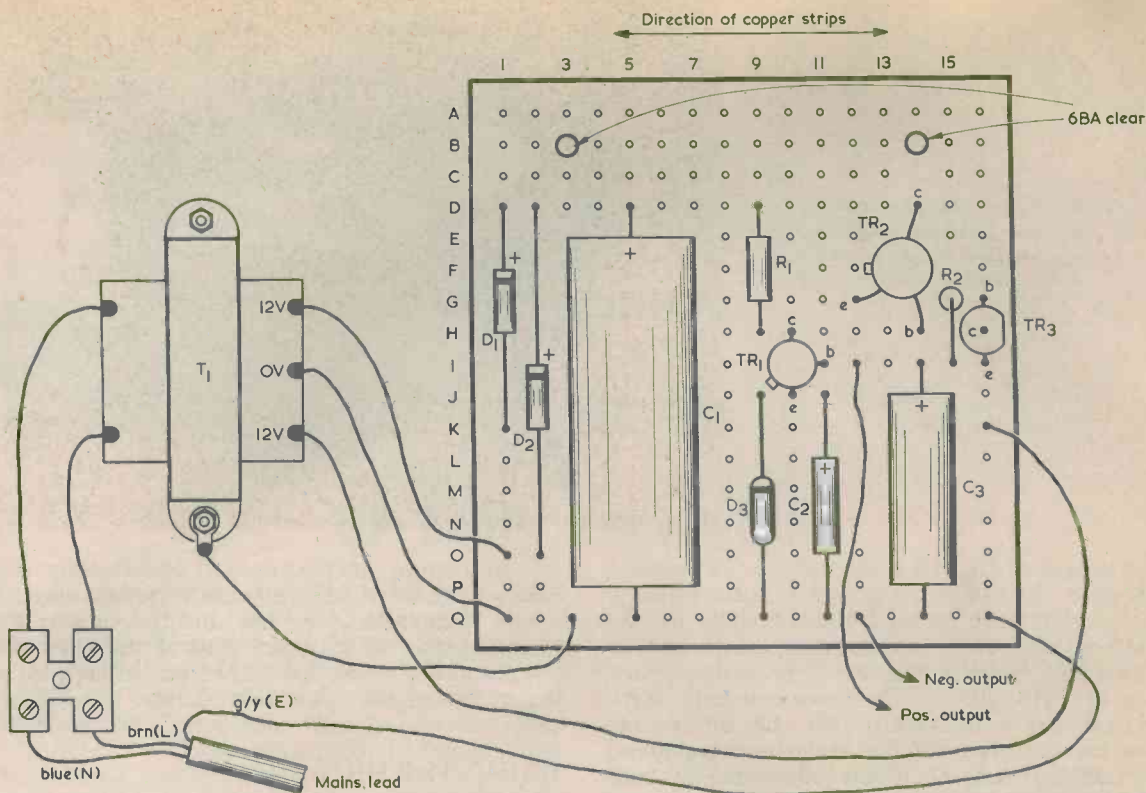


Fig. 2. Wiring up the eliminator unit. All the small components are assembled on a Veroboard module

tably into the battery compartment of the author's Fidelity RAD15 set, for which it was intended. Presumably, the same case should be of a suitable size for installation in other receivers designed to take a PP9 battery.


The mains transformer is mounted at one end of the case, being secured by two short 4BA screws and nuts. A solder tag is held under one of the nuts to allow the transformer frame and core to be earthed. It must be mounted as close to the end of the case as possible to allow sufficient space for the component board. An entrance hole for the mains lead is made high up on one of the long sides of the box and is fitted with a grommet. The mains lead should be secured inside the case with a plastic or plastic-faced clip. Two small holes for the output leads are drilled at roughly the centre of the short

side of the box adjacent to the component panel.


The component board consists of a piece of 0.1 in. matrix Veroboard having 16 holes by 17 copper strips, as shown in Fig. 2. This diagram gives details of the wiring on the board and also the other wiring in the unit. There are no breaks in the copper strips. The board is mounted in the case by means of two 6BA bolts and nuts, the board being oriented so that these are furthest away from the mains transformer. Spacing washers or several 6BA nuts, are fitted over the bolts between the case and the underside of the board to prevent strain on the latter when the mounting nuts are tightened.

The two connections between the mains lead and the primary of T1 are made via a plastic connector block of the type intended for mains wiring. These are normally sold in 12-way lengths, and it is

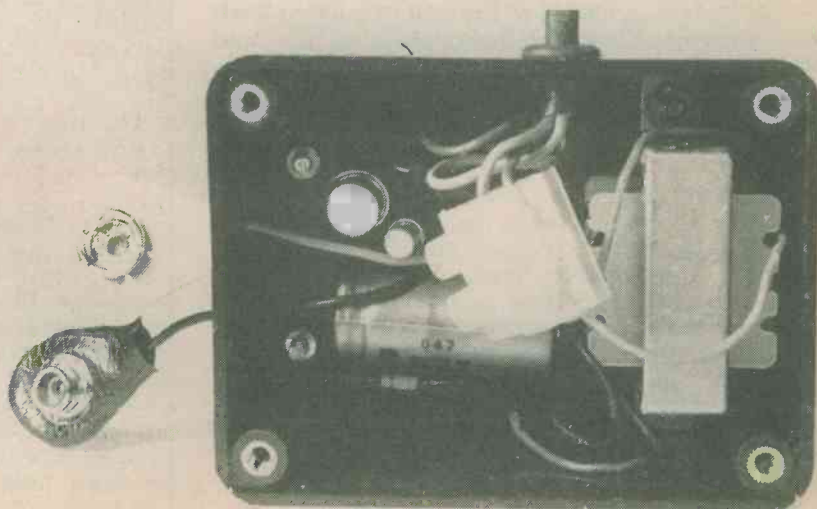Removing the lid of the eliminator case. The 2-way connector block provides connection between the transformer primary and the live and neutral wires of the mains lead



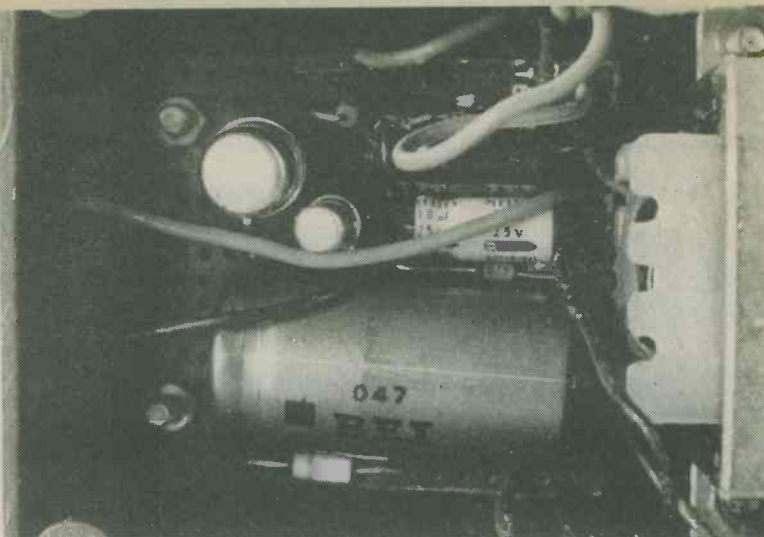The component board. The larger transistor here is TR2



necessary to cut off a 2-way block with a sharp knife. It is advisable to cover the connector block, after wiring, with two or three layers of insulating tape to ensure that the mains wiring cannot come into contact with any of the other wiring. Alternatively, a panel of s.r.b.p. can be interposed between the connector block and the component board to prevent any accidental electrical contact between the two.

The output of the eliminator is connected to the receiver by way of two PP9 battery connectors. What would normally be a negative connector now becomes the positive eliminator output clip, and what would normally be a positive connector now becomes the negative eliminator output clip. This situation can be readily visualised when the connector clips are compared with the terminals of a PP9 battery. It is necessary to connect the eliminator output to the receiver with correct polarity.

If desired, the output clips could be glued with Araldite to the outside of the short end of the case through which the output leads pass. The clips would then be presented to the receiver in a similar manner to the terminals on a PP9 battery.

As already mentioned, the mains on-off switch is inserted at any convenient point in the mains leads. The author employed a "pressil" switch of the type in which successive pressing of the button closes and then opens the switch. These switches are available from most electrical stores, as well as from Maplin Electronic Supplies. The switch is mounted in a small plastic Verobox type 75-1469-L having dimensions of 71.5 by 49 by 24.5 mm. A hole fitted with a grommet, is drilled at each short side to allow the mains lead to pass through. The

mains lead should be suitably clamped inside the box at both ends. If the lead has to be cut to allow access to the live wire, the neutral and earth wires at the cut ends may be connected through by way of a further 2-way connector block.

USING THE UNIT

Before connecting the eliminator to the radio, its output voltage should be checked by means of a multimeter switched to a suitable range. The output voltage will probably be slightly less than 9 volts but, since the actual voltage provided by a 9 volt battery varies from about 9.5 volts to less than 8 volts during its working life, this is not of any great practical importance.

It is also a good idea to check that the current limit circuit is functioning correctly. This can be achieved by connecting a multimeter set to a high current range to the output terminals with a 47Ω resistor in series, as shown in Fig. 3. If all is well the meter should give an indication of about 100mA. The resistor limits the current which can flow to a safe level of around 200mA if the current limit circuit is not working. The eliminator should be switched off without delay if the meter reading is well in excess of 100mA.

It should not be necessary to carry out any modification to the radio except, perhaps, to make a notch in the battery compartment door to accommodate the mains lead. Some battery compartments have a sliding door, and it will then simply be necessary to have the door not fully closed.

The negative output of the eliminator is at mains earth potential. Quite a few receivers have their chassis and some of the exposed metalwork connected to the positive supply rail, and this point should be borne in mind if the receiver is connected to any equipment, such as a tape recorder, having a chassis which is also at mains earth potential. No problems will arise when the receiver is used on its own.

Finally, it should be noted that the eliminator is only intended for use with items of equipment, such as radio receivers, which have a fairly modest current consumption. It cannot be used to power cassette recorders and similar items requiring a relatively high current. ■


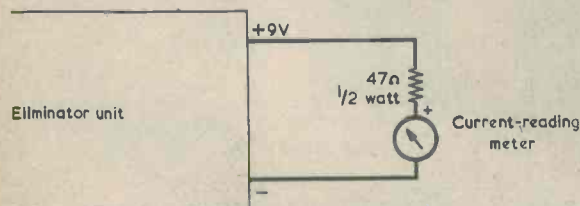


Fig. 3. Checking the current limit operation. The 47Ω resistor prevents excessive current flow if there is a current limit malfunction

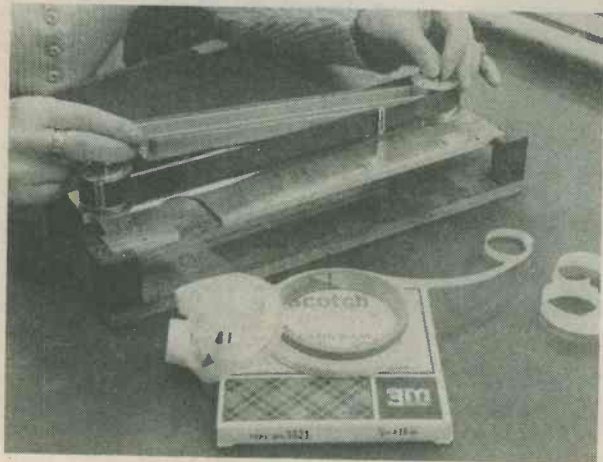HIGH DENSITY POLYTHENE TAPE SOLVES FRICTION PROBLEM



A strip of Scotch 5421 high density polythene tape mounted on foam rubber is installed behind the belt on the writing plate assembly of a Mufax document facsimile machine.

Linear movement, such as is found on recording, scanning and tracking devices can cause excessive friction and wear between components, resulting in early failure of equipment if it is not frequently maintained. A simple and effective solution to this

problem, in the form of a high density polythene tape, has been adopted by Muirhead Data Communications Limited, manufacturers of document facsimile machines.

The company's Mufax equipment will transmit and receive documents, charts and pictures over a telephone line or radio link, the image being reproduced by means of an electrostatic charge which is applied to the paper through a travelling stylus. This stylus is carried on a rubber belt and traverses the paper up to 600 times a minute.

Stability for the stylus throughout its travel is provided by a $\frac{1}{4}$ in wide strip of high density polythene tape mounted on foam rubber and positioned behind the belt. The tape used is Scotch 5421 from 3M, which features an ultra high molecular weight polythene backing. Its low friction properties and resistance to wear make it an ideal bearing surface which gives long, trouble-free performance. Being self-adhesive, it can be applied to almost any material without time-consuming mechanical fixing.

Users of Mufax machines include government departments and the police, so reliable operation is of prime importance. A marine version of the equipment, a weather chart recorder for shipboard applications, is also manufactured by Muirhead at their Beckenham factory.

ECONOMICAL ENCLOSURES

The latest range of enclosures from OK Machine & Tool (UK) Ltd., of 48a The Avenue, Southampton, Hants., the 'C' Series, is extremely versatile and has been designed to provide a purpose-built package for electronic instruments while offering substantial savings in assembly cost. This is achieved by building the case up from single components — top, bottom, sides and ends — rather than forming a one-piece unit.


Assemblies are available in over 25 sizes and numerous variations to accommodate printers, terminals, calculators, clocks, indicators, battery packs, timers, receivers, power supplies, radios and many other electronic or electro-mechanical components.

Moulded from tough, durable ABS, 3mm thick, the cases are dust and splashproof when assembled and can be supplied in beige, black or blue textured colours requiring no additional external furnishing. Standard width is 212mm and depth is 232mm with height ranging from

62mm to 88mm in 6mm increments. Inside, vertical circuit board guides are fitted in eleven places. Additionally a Mini Series is offered starting at 37mm high X

130mm wide X 144mm deep.

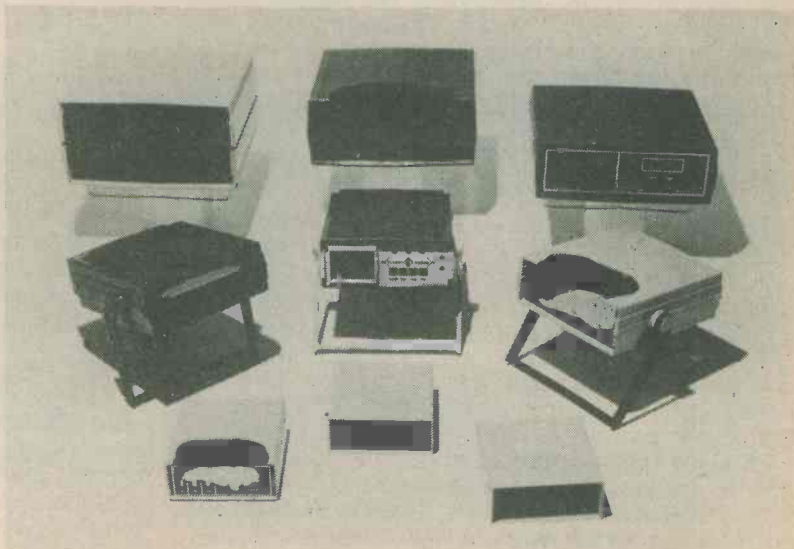Options include rail and card slide adaptors, standard and special front and rear panels, RFI/EMI shielding, handles and tilt stands.



COMMENT

AWARD FOR OUTSTANDING WORK ON COMMUNICATIONS BY SATELLITE

In May 1979 The President of the Italian Republic will present the Fifth Marconi International Fellowship worth \$25,000 to Dr John R. Pierce, Professor of Engineering at the California Institute of Technology, for his outstanding work in satellite and space technology directed especially towards improving world communications.

Dr Pierce retired in 1971 from the Bell Laboratories where he was Executive Director, Research, of the Communication Sciences Division. His work covered research into radio, electronics, acoustics and vision, mathematics, economic analysis and psychology. Dr Pierce has been granted more than 80 patents for inventions in electron tubes and communication circuits. In 1955, two years before the first satellite, Dr Pierce offered his first concrete proposals for satellite communications.

The Marconi International Fellowship was established in 1974 on the 100th anniversary of the birth of Guglielmo Marconi to commemorate his contributions to science, engineering and technology and is administered by the Aspen Institute for Humanistic Studies, Boulder, Colorado, U.S.A.

EXTENSIONS TO SERVICE

Sigtronic Electronics of 27 Malvern Street, Stapenhill, Burton-on-Trent, Staffs DE15 9DY, have informed us of a new, and rather unique, service which they will be operating from the beginning of May onwards.

They will accept orders by telephone, number 0283-46868, from 6.00pm to 10.30pm every evening from Monday to Friday inclusive, and they are also prepared to advise on the components readers may need without charge. They undertake to despatch orders within 48 hours of receipt of written confirmation, cash to be enclosed. All items are new, and guaranteed for six months, and there is no extra charge for the service.


PROPOSED NOVICE LICENCE

There is, of course, considerable controversy in the radio amateur world as to the desirability of a Novice Licence.

The European CW Association, who favour such a licence, suggest one with the following conditions. 1. A simple examination covering regulations and radio theory. 2. A 5wpm morse test. 3. Crystal control only in defined segments of amateur bands (hf and vhf). 4. Maximum power input 10 watts. 5. Holders of an RAE certificate need only to pass the morse test. 6. The licence to be held for 2 years in any 5 year period.

To ascertain support for the proposal would readers in favour send a postcard giving name and address to A. D. Taylor, G8PG, 37 Pickerill Road, Greasby, Merseyside L49 3ND.

NEW I. C. SOCKET RANGE

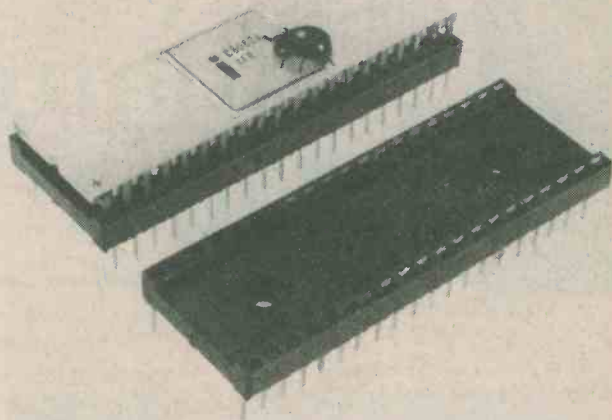

Winslow Component Systems Limited, the Kent based Semiconductor Accessory Manufacturer, announce the launch of a brand new range of I.C. Sockets.


Featuring low profile, glass reinforced polyester bodies — they have been designed to exceed the most stringent criteria demanded by today's high technology microprocessor user and yet are manufactured to be price attractive, even in consumer markets.

Technical Data available from: Winslow Component Systems Limited, Southern House, Edenbridge, Kent.

MODIFICATIONS TO A POPULAR DESIGN

A those of our regular readers who have followed Sir Douglas Hall's receiver designs will be aware, one of the most successful of these has been the "Spontaflex S. A. 5" medium and long wave radio, which was described in the June 1971 issue. Sir Douglas has had the prototype in constant use since the article appeared and has evolved several worth-while modifications which improve its performance.

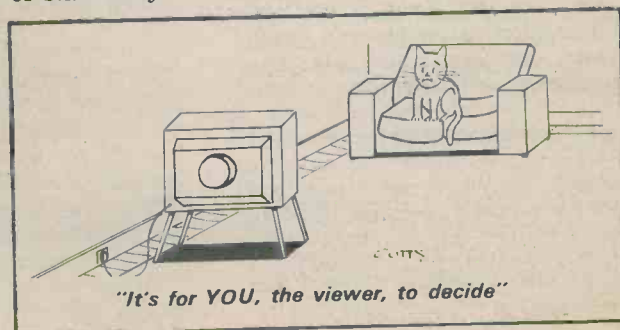Readers who are still using this receiver can obtain details of the modifications direct from Sir Douglas Hall at Barnford, Ringmore, Kingsbridge, Devon, and should send a stamped addressed envelope together with a 7p stamp towards the cost of stationery.





Remote Control Garage Light

by G. A. French

One of the minor irritations of life for the motorist is given when, on a cold night, he drives his car into his garage and then has to fumble around in the dark to find the switch for the garage light. This article describes a device which causes a garage light to be switched on for a timed period, being controlled entirely from within the car. The light is turned on simply by flashing the car headlights on and off, one of the headlights being directed against a photoconductive cell installed permanently in the garage. The timing period commences when the headlamps are turned off and can be extended by flashing them on and off again. The period over which the garage light is turned on is about one and a half minutes, which should be more than adequate to enable the driver to get out of the car and turn on the normal garage light switch.

This idea is not new and the author used it some years ago in the project "Automatic Garage Light", which appeared in *Radio & Electronics Constructor* for September 1975. The previous design employed rather a complex approach which necessitated the use of two relays, and the writer decided it would be of advantage to return to the subject with a circuit which had simpler electronics and required one relay only. The present article describes the result of his work.

RELAY OPERATION

An electronic circuit can, in general, control a mains powered lamp by means of a triac or a relay. The triac has the advantage that there are no moving parts to wear out and the disadvantage that, un-

less some form of isolating device is incorporated, the electronic circuit which controls it has to be connected to one side of the mains supply. The relay has the disadvantage of having moving parts, and the advantage that it enables the electronics to be completely isolated from the mains without any additional isolating components or circuitry. It is for this reason that a relay is employed in the design featured here. An incidental factor is that a very suitable small relay is available from Maplin Electronic Supplies, this being described as a "6 volt Open Relay". The relay has a 410Ω coil, an operate voltage range of 4.8 to 35 volts and changeover contacts rated at 5 amps at a maximum voltage of 240 volts a.c.

The same relay was employed in the previous circuit, which provided a slowly decreasing relay coil voltage near the end of the timing period, the voltage eventually falling below the release voltage level for the relay. Light-weight relays do not, however, always take kindly to slowly reducing coil voltages and tend to suffer from contact chatter. For this reason, a second heavier low voltage relay was included in the earlier design to control, in its turn, the Open Relay.

The present circuit appears in Fig. 1. In this diagram the photoconductive device is an ORP12 cadmium sulphide cell, the resistance of which decreases as the intensity of light falling on it increases. At very high light levels its resistance may be as low as 75 to 300Ω . It couples via R1 to the preset potentiometer VR1, the slider of which connects to the base of TR1.

Under normal ambient light conditions the ORP12 will have a fairly

high resistance, and this will fall to a low value when it is brightly illuminated by a car headlamp. The slider of VR1 is adjusted such that, with ambient light, the voltage applied to TR1 base is significantly less than the 1.2 volts needed to cause forward current to flow in the base-emitter junction of TR1 and D1. TR1 is, in consequence, turned off. In this circuit state C1 becomes charged via R3 to as high a voltage as the circuitry around TR2, TR3 and TR4 will allow. When the ORP12 is brightly illuminated by the car headlight the voltage at VR1 slider rises sufficiently to allow a forward bias current to flow in the base-emitter junction of TR1 and in D1. TR1 turns on. Capacitor C1 is rapidly discharged, with the voltage across it falling to around 0.8 volt (given by 0.6 volt across D1 and 0.2 volt across the bottomed TR1). When the car headlight is turned off, PCC1 exhibits its previous high resistance, the voltage at the base of TR1 drops and the transistor turns off. Capacitor C1 commences to charge via R3.

Thus, illuminating the ORP12 with the car headlight causes C1 to quickly discharge. Turning off the headlight allows C1 to slowly charge again.

SCHMITT TRIGGER

To avoid relay chatter it is necessary for its coil voltage to cease abruptly at the end of the timing period rather than reduce slowly, whereupon it is necessary to employ a voltage comparator which has an inherent regenerative action. An excellent choice for the present application is a Schmitt trigger and this is made up of TR3, TR4 and the associated resistors. When TR3

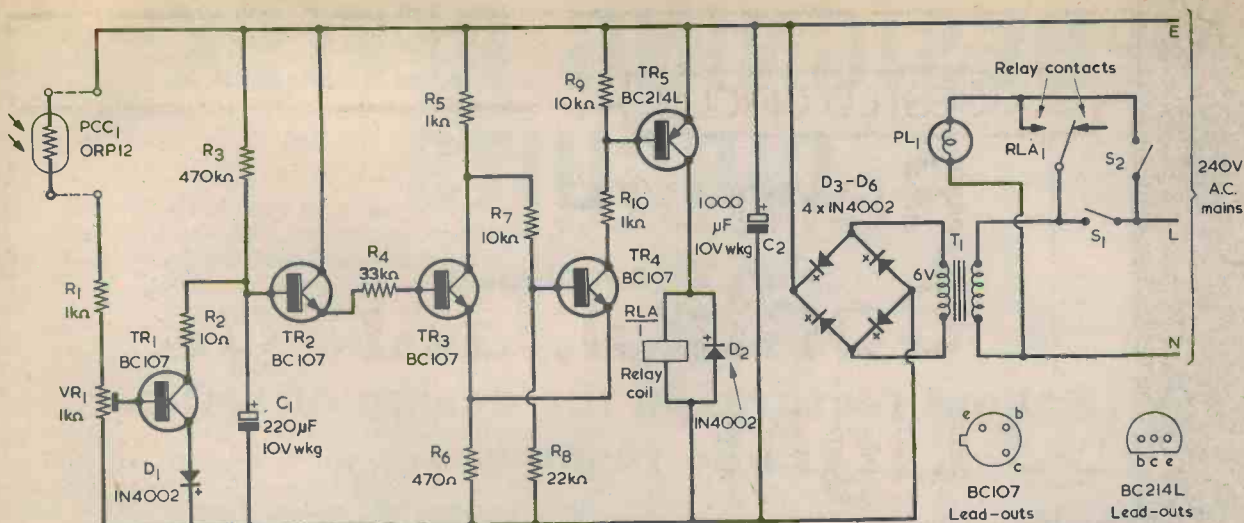


Fig. 1. The circuit of the remote control garage light. Switching on the car headlamps illuminates the photoconductive cell and causes lamp PL1 to be turned on for a period of about one and a half minutes

base is at a low voltage, with respect to the negative supply rail, this transistor is turned off and current flows to the base of TR4 via R5 and R7. TR4 is then turned on. If the base of TR3 is slowly taken positive a level is reached at which the transistor starts to conduct, thereby diverting to itself some of the base current for TR4 which flowed through R5 and causing additional current to pass through R6. The latter effect takes TR4 emitter positive and there is a regenerative action which results in TR3 turning fully on with TR4 cut off. The transistors remain in this state should TR3 base go further positive.

The reverse changeover will occur equally abruptly if the base of TR3 is taken slowly negative but, due to the hysteresis inherent in a Schmitt trigger, will take place at a more negative voltage at TR3 base than that which instigated the first changeover. The hysteresis is of no importance in the present circuit.

Under normal conditions, with only ambient light falling on the, ORP12, C1 is charged, the positive voltage on its upper terminal being passed via emitter follower TR2 and R4 to the base of TR3. TR3 is, in consequence, turned on and TR4 is turned off. The voltage across C1 is then held at around 3.5 to 4 volts by the current flowing through the base-emitter junctions of TR2 and TR3 and through R4 and R6. Since TR4 is turned off, so also is the p.n.p. transistor, TR5, which is connected in its collector circuit. No current flows through the relay coil and the relay is de-energised. The relay contacts are identified in the circuit as RLA1, and the make pair are open. The lamp, PL1, is therefore extinguished.

When the car headlight is flashed onto the ORP12, capacitor C1 discharges, TR3 turns off and TR4 turns on. So also does TR5, energising the relay and switching on PL1. C1 now commences to charge. Until it approaches the end of the timing period the charging current for C1 is that which flows through R3, because the base-emitter junctions of both TR2 and TR3 are reverse-biased. Near the end of the period current starts to flow into the base of TR2 also, and only a small further positive excursion is needed at TR2 base for the Schmitt trigger to go through its abrupt changeover, with TR3 turning on and TR4 turning off. The relay releases and PL1 is switched off.

If, during the timing period, the car headlight is turned on and off again C1 becomes discharged and the period commences once more. Using the component values shown, the prototype circuit gave a period of almost exactly 90

seconds. Divergencies from this time will be found in other assembled circuits due to component tolerances, particularly in C1 itself, but in general the period should be well in excess of 1 minute and shorter than 2 minutes.

The power supply consists of mains transformer T1, diodes D3 to D6 and smoothing capacitor C2. The rectified supply should be well smoothed, this being achieved by giving C2 the rather large value of 1,000μF. S1 is the on-off switch, whilst S2 is an override switch which can turn on PL1 regardless of the state of the timing circuit.

COMPONENTS

The components are all standard types. All the resistors may be ¼ watt 5% or 10% components. Switch S2 should be a type suitable for switching a mains lamp. The quiescent current drawn by the circuit from the smoothed supply is about 6mA only, this rising to some 14mA when the relay is energised. Despite these low currents it will be preferable to avoid employing a subminiature transformer for T1 and to use instead a transformer whose secondary is rated at at least 100mA, or even quite considerably more. The latter will give good supply voltage regulation, and there is also the fact that many sub-miniature mains transformers tend to run warm if left switched on for very long periods, as can happen with the present circuit.

The ORP12 may, if desired, be mounted away from the main cir-

Continued on Page 609

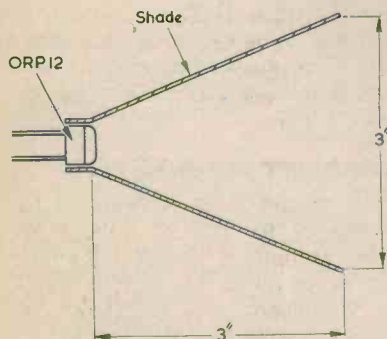



Fig. 2. The intensity of ambient light falling on the photoconductive cell can be reduced by fitting it with a simple shade, as shown here

Fig. 6(a). The "D.R.C.2" short wave reflex circuit. Audio instability problems do not occur at short waves due to the very low impedance at a.f. of the short wave tuning coil


(b). The circuit can be adapted for v.h.f. reception on both a.m. and f.m. A different reaction control circuit, illustrated here, is required at these frequencies

circuit the output at TR2 is in phase with the input of TR1 but, because of the very small a.f. impedance offered by a short wave tuned coil, the base of TR2 is virtually at the potential of the negative rail for audio frequencies. It is thus easier to maintain audio stability with reflexed short wave receivers than it is with medium and long wave receivers.

The circuit can be used for v.h.f., at which frequencies it is highly suitable both for a.m. and f.m. signals. With f.m. signals the synchronous method of detection is employed. The coupling capacitor should be reduced from 22pF to 2.2pF and the tuning capacitor from 150pF to 15pF. A suitable coil for Band II can consist of 6 to 8 turns of 34 s.w.g. wire space-wound on a former consisting of a length of the barrel of a "Bic" ball-point pen, the exact number of turns depending on layout design. Variable capacitor reaction is not suitable for v.h.f. and the circuit shown in Fig. 6(b) is recommended. The 1k Ω potentiometer varies the forward current flowing through the germanium diode and thus its impedance and the consequent damping effect of the tuned circuit. Maximum oscillation occurs with the potentiometer slider at the negative end of its track. The 33k Ω load for TR2 is replaced by a 100k Ω pre-set variable resistor which is adjusted so that the 1k Ω reaction potentiometer gives good control. The silicon diode and the zener diode

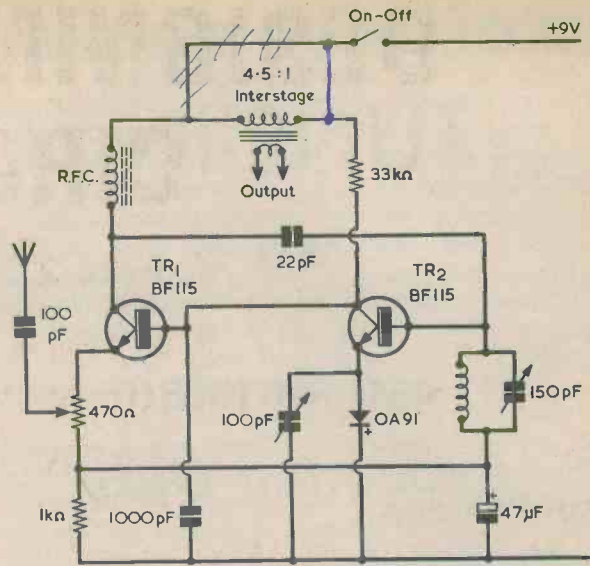

(a).

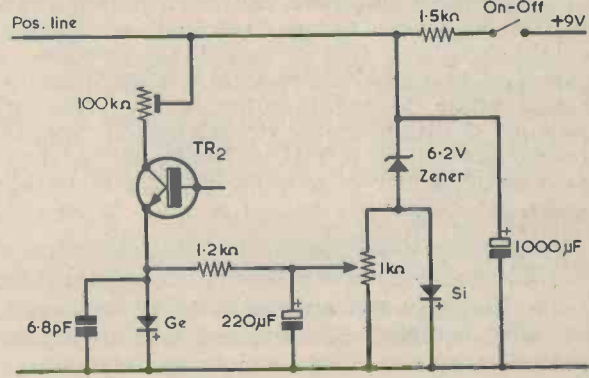

(b)

Fig. 6

maintain stable voltages in the circuit as the battery runs down. The two transistors should be changed from BF115 to BF167 or 2N3663.

(Concluded)

Remote Control Garage Light

continued from page 606

cuitry, being coupled to it by a twin lead which should be kept well away from unscreened mains wiring. It is mounted on a wall directly facing one of the car headlamps when the car is parked in its usual position. To reduce illumination by ambient light it can be fitted with a simple shade along the lines indicated in Fig. 2. It is of course extremely unlikely, to say the least, that the ambient illumination at day or night on the ORP12 inside a garage will even approach that offered by a car headlamp positioned a few feet away from it.

The switching part of the circuit may be coupled to the main light switch for the garage, although

some constructors may prefer that the circuit switch on its own lamp, the existing garage wiring then unaltered. **It is of the utmost importance that the unit be installed in a proper housing which allows no access to circuit points at mains potential and that all external metalwork be reliably connected to the mains earth.** It will be seen in Fig. 1 that the mains earth connects to the positive rectified supply rail, thereby allowing one of the leads to the ORP12 to be at earth potential. Precautions against shock from the mains must always be fully observed in a garage, which normally has a concrete floor offering a high shock hazard.

When the unit is connected to the mains and is then switched on, C1 will be discharged and the circuit will go through a timing period before it becomes set for use.

After completion and installation, it is necessary for VR1 to be set up. This potentiometer is initially adjusted so that its slider is at the negative end of its track. The car headlamp illuminating the ORP12 is then turned on and the slider of VR1 gradually advanced towards the positive end of the track. A setting will be found at which PL1 lights up and the circuit goes through a timing period. The final position for VR1 slider is just slightly beyond that setting. ■

EXCLUSIVE SERIES

TUNE-IN TO PROGRAMS

Part 5

by
Ian Sinclair

Becoming Dszy


One of the most important features of a programmable calculator is its ability to keep churning round a program loop, displaying results or storing quantities into memories. In Part 4 we noted one method of stopping such a loop by making use of the [x=t] unconditional branch key. This time, we're going to look at another way of limiting the number of times a loop is traced. This involves the [Dsz] key of the TI-57, which is operated by the sequence [2nd] [GTO].

SKIP ON ZERO

The key title [Dsz] comes from the description of what this key does in a program: "Decrement and Skip on Zero". Decrement means count down by 1, and what is being decremented is any number stored in memory 0. If, for example, before running a program we key in [12] [STO] [0], then on the first loop the [Dsz] operation will result in 1 being subtracted from the number in memory 0, leaving 11. On the next loop the [Dsz] operation will subtract 1 again, leaving 10 stored in memory 0, and so on. Eventually, when there is only 1 stored in memory 0, the [Dsz] operation will reduce this to 0, and *then* the program will skip one step so that the skip takes the program out of its loop.

This operation could, of course, be done by using the [x=t] operation, but some steps are saved in the program when a straight count-down is needed by the use of the [Dsz] key. We do not, for example, have to program the steps [INV] [SUM] to arrange the decrement, nor the [x=t] for the skip step.

Let's look at an example of this count-down in use. The average value of a wave over a cycle is a quantity which is rather important. If this average value is 0 then the wave is pure a.c., but if there is an average value which is not 0 then there must be more flow in one direction than in the other, so that some d.c. is present. Now this can be calculated by the mathematical process called integral calculus, but the programmable calculator can do the same job in an equivalent way by adding up the amplitudes of a wave at a number of points in the cycle. Suppose we decide to sample a sine wave every 5 degrees. Now, a complete cycle is 360 degrees, so that we will have a total of 72 sample points — a rather tedious business to do using tables or even a conventional calculator.

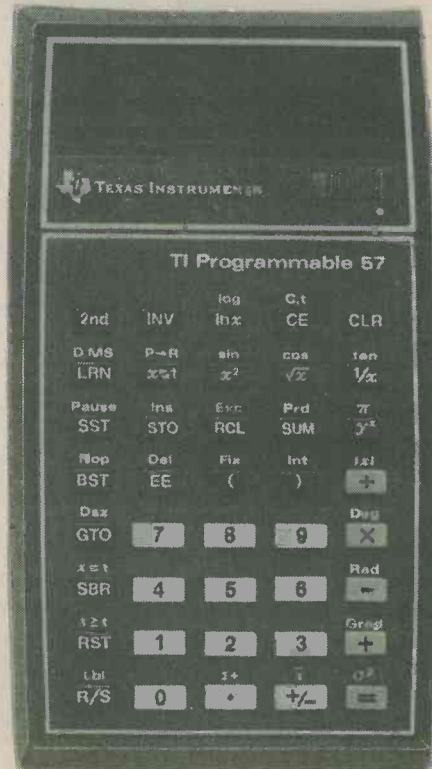

The keyboard of the Texas Instruments TI-57 programmable calculator. Most keys have a second function, whereupon facilities are nearly double the number of keys provided

In our program we will start by setting the content of memory 0 at 72 and decrement by 1 using [Dsz] on each run through. We could, of course, do this by counting up angles, 0,5,10, and so on. It is easier to use the contents of memory 0 to generate the angle, however. If we start with the number 72 stored in memory 0, then multiplying this by 5 will give 360, which is the first angle to be calculated. If we use the number in memory 0, and multiply it by 5 on each loop, then the result will be the angle we want to use. For example, on the second loop, the number in memory 0 will be 71, and the angle will be $71 \times 5 = 355$ degrees.

The program, shown in Fig. 1, starts by setting the contents of memory 1 at 0, and memory 0 at 72. These steps are *not* repeated during the loop because we want to count down the figure in memory 0, and to add up the answers that we get into memory 1. After the [72] [STO] [0] step, then,

Program	Procedure
LRN 0 STO 1 72 STO 0	Fix 2 RST R/S
Lbl 0 RCL 0 X 5 =	After 71 loops the result
sin SUM 1 Dsz GTO 0	(zero) is shown.
RCL 1 R/S LRN	

Fig. 1.

For a calculation of the average value of $\sin \theta \times \sin (\theta + 30^\circ)$, such as might be wanted for calculating power dissipation, the program would read:

Program	Procedure
LRN 0 STO 1 72 STO 0	Fix 2 RST R/S
Lbl 0 RCL 0 X 5 =	After 71 loops the result
STO 2 sin X (RCL 2	(31.17) is displayed. (Note
+ 30) sin = SUM 1	that this program will take
Dsz GTO 0 RCL 1 R/S LRN	about twice as long to run
	as that of Fig. 1.)

Fig. 2.

the program has [Lb] [0], indicating where the loop starts. Remember that memory 0 and label 0 are quite different. Within the loop the number stored in memory 0 is pulled out and its value multiplied by 5 to give the angle we need for the wave amplitude calculation. The step [sin] now calculates the sine of the angle, and this value is added into memory 1, which stores the sum of the amplitudes of the wave, a sine wave. For other calculations some other expression will replace the [sin] step, as in Fig. 2.

The next step in the program of Fig. 1 is [Dsz] for the count-down, and this is followed by [GTO] [0] so that the loop repeats. When the loop repeats, however, the number stored in memory 0 has been made 1 less by the action of the [Dsz] step, so that the angle whose sine is being calculated is 5 degrees smaller. On the last loop, with figure 1 stored in memory 0, the angle is 5 degrees, and this is the final amplitude calculated. At the [Dsz] step, subtracting 1 gives 0, so that the program skips the [GTO] [0] step and lands on [RCL] [1]. This puts into display the total amount (sum of amplitudes) stored in memory 1, and the [R/S] step then stops the program so that the final figure is visible in the display. Note that the angle 0 degrees is not calculated, because 5 degrees is the last run and the counter skips when the [Dsz] step is used. The value of a sine wave is the same at 360 degrees as it is at 0 degrees, so that we do not have to include the latter in the program. If, in some other program, we had to include the value at 0 degrees (or 0 of whatever quantity we used) we would have to amend the program by starting with a number 1 higher in memory 0 (73 in this example) and then subtracting 1 after this number is out of memory. Such a step sequence is shown in Fig. 3.

Program
LRN 0 STO 1 73 STO 0
Lbl 0 (RCL 0 - 1)
X 5 = STO 2
remainder as before

Fig. 3.

INVERTED STEP

Like most of the keys on the TI-57, the action of the [Dsz] key can be inverted by using the sequence [INV] [Dsz]. With this instruction in a program, the sequence that takes place is that 1 is subtracted from the number which is stored in memory 0. Then if the number stored in memory 0 is *not* 0 the program skips a step. If the number left in memory is 0, then the next step of the program is used. This 0 facility is nice to have, but we seldom need to use it because it's difficult to think of anything which can be done using [INV] [Dsz] which could not equally easily be done by using [Dsz] by itself.

There are a few points to look out for when we program in the [Dsz] type of instruction. The first and most important point is that we cannot use memory 0 for anything else. In part 8 of this series, we shall be looking at methods of keeping records of programs, but it's not revealing any secrets to say now that we should always keep a note of what each memory is used for when we write or record a program.

Because the [Dsz] instruction counts the number of times round a loop, it doesn't necessarily follow that the number stored in memory 0 must be the number of times that a loop is traced in the course of one program. It's possible to use the [Dsz] instruction in two different loops — counting down in one loop, then reloading another number into memory 0, switching to another loop and using the [Dsz] step all over again. How do we do it? Fig. 4 shows one method but you'll have to wait until we start dealing with subroutines next month for other methods.

Program	Procedure
LRN 4 STO 0 Lbl 0	Load resistor value into
RCL 1 + (RCL 0 X	STO 1.
.05 X RCL 1) =	CLR RST R/S
Pause Pause Dsz GTO 0	Display shows values for
4 +/- STO 0 GTO 0	positive tolerances from
LRN	20% down to 5%, then
	negative tolerance values
	from -20% upwards —
	negative values then
	repeat. To avoid repeats,
	see next month's issue.

Fig. 4.

A few more assorted points on the [Dsz] key are useful to know. One is that a fraction stored in memory 0 is taken for the purposes of the count down as the next whole number up. 0.6 is taken as 1, 5.5 as 6, 14.2 as 15, and so on. This is ocy for the purpose of the "skip-on-zero" step; the number stored in the memory is not rounded up. For example, if we place 4.65 in memory 0 then use the [Dsz] step in a loop, the number will be counted down as 3.65, 2.65, 1.65, 0.65 (which still counts as 1, so that there is no skip yet) and then the next [Dsz] step makes the count 0, *not* -0.35. If the number which is placed in memory 0 is a negative number, the [Dsz] operation *increments* by 1, so that 1 is *added* on each loop. This ensures that the count always ends in 0, causing the skip.

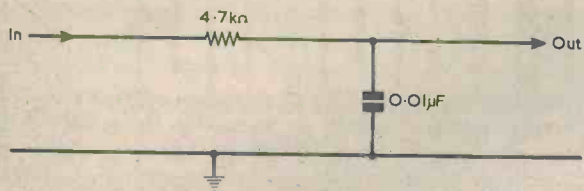


Fig. 5. Simple RC low-pass filter. Gain and phase angles at different frequencies are calculated by the program of Fig. 6. The program will, of course, operate with other values of resistance and capacitance than those shown here

This program calculates the gain (output voltage divided by input voltage) and phase angle (in degrees) for a simple RC low pass filter.

Program

```
LRN RCL 1 STO 4 RCL 2
Prd 4 RCL 3 Prd 4 Lbl 0
RCL 0 X RCL 4 = STO 5 x2
+ 1 = √x 1/x Pause Pause
RCL 5 INV tan +/-
Pause Pause Dsz GTO 0 GTO 1
LRN
```

Procedure

Load value of starting frequency (in kHz) into store 0, value of R (in kΩ) into store 1, value of C (in μF) into store 2
 2 X π = STO 3
 Fix 2 CLR RST

Pressing [R/S] will give displays of gain, then phase angle for the starting frequency, and then for each 1kHz less until 1kHz. The end of the cycle is signalled by a flashing display caused by the impossible instruction [GTO] [1] (Label 1 is not used).

Fig. 6

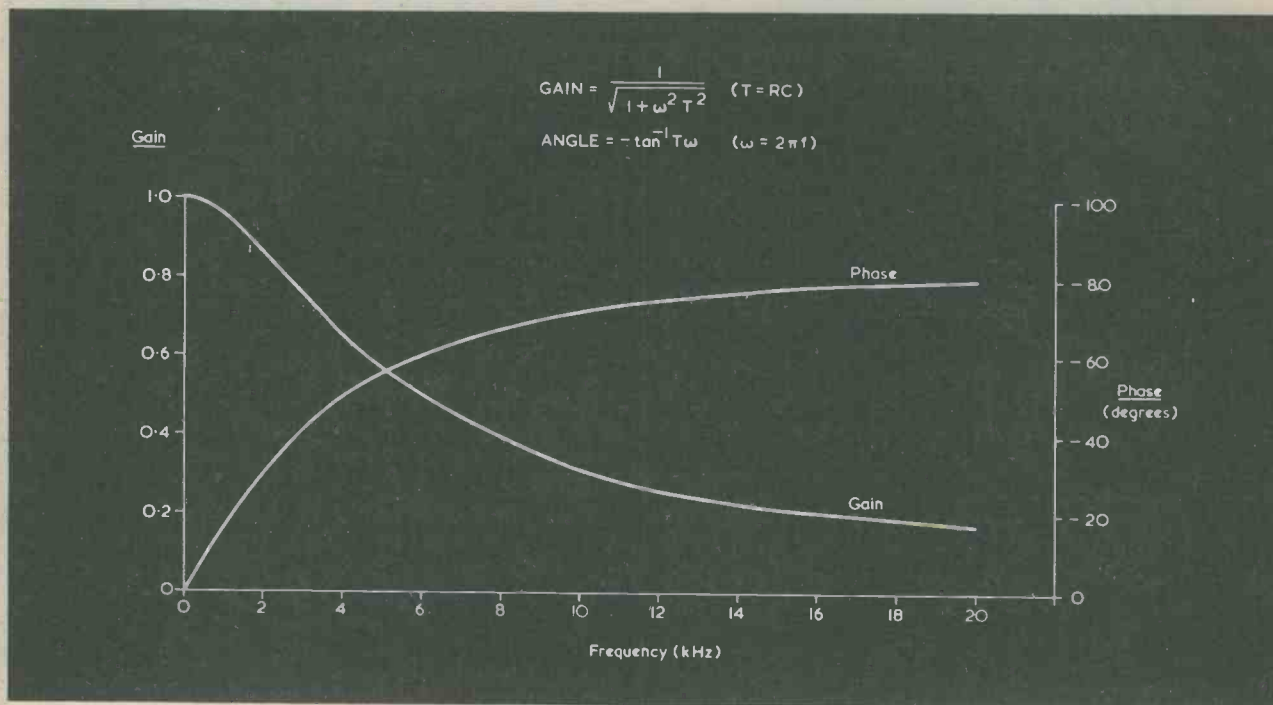


Fig. 7. Graph showing gain and phase angles of the low pass filter of Fig. 5 at a starting frequency of 20kHz. The curves are plotted from the read-out of the Fig. 6 program

PROGRAM STEPS

Just a short note here while you pause for breath. An important difference between the TI-57 and the PR-100 is the use of what are called merged codes on the TI-57. When, for example, we program [Lbl] [4], [STO] [3], [RCL] [2] on the TI-57, each of these, the instruction and the reference number, counts as just one program step. On the PR-100 each key-stroke counts as a program step. Because of this it is difficult to compare the program handling capacity of these two calculators. Another important point which applies to both calculators is that each digit of a number which is entered into a program is counted as a program step. For example if we need the steps [RCL] [2] [X] [15] [÷] [65], then the

number steps [15] [÷] [65] amount to 5 program steps. When constants like these have to be used, it's better to calculate the result first (15÷65=0.23) to insert into the program or, even better, to place the full result (0.2307692) in another memory. If we use memory 3 for this result, then the program steps become [RCL] [2] [X] [RCL] [3], which is only 3 steps on the TI-57, 5 on the PR-100.

Next month — subroutines, allowing us to use more program steps than we believed possible. As a tail-piece, though, Fig. 6 shows a program for the gain and phase angle of the low-pass filter of Fig. 5, and Fig. 7 shows the graph produced from the read-out of the TI-57.

RADIO & ELECTRONICS CONSTRUCTOR

IN OUR NEXT ISSUE —




AUDIO CONTINUITY TESTER

Signals continuity by audible tone

PHASE LOCKED 200kHz CALIBRATOR

A calibrator with BBC Radio 4 accuracy

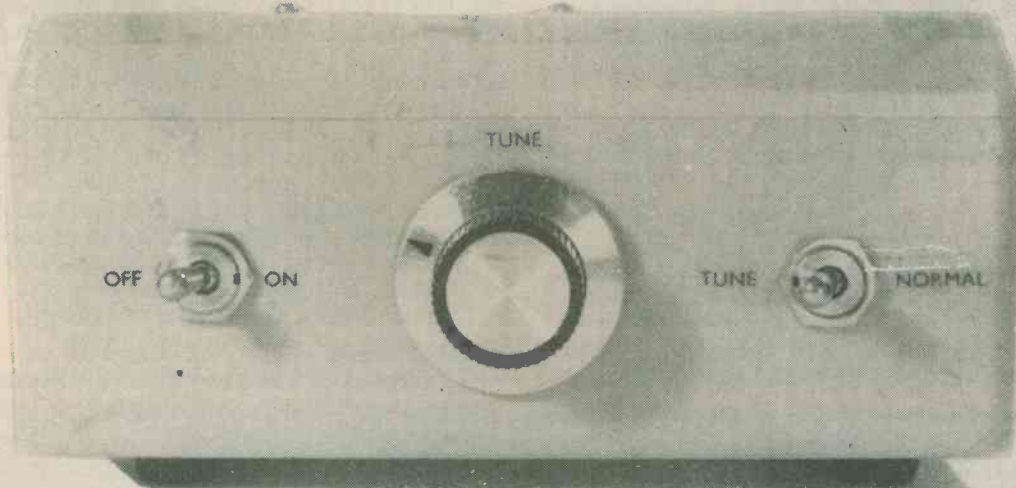

Car Voltage Monitor
Suggested Circuit

Prevent a.m. image interference
In Your Workshop

MANY OTHER ARTICLES

ON SALE 4th JUNE

Avoid disappointment. ORDER NOW

SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

● U.S.S.R. WORLD SERVICE

This service commenced last year and has been in operation for some time now, it commences at 0400 and is on the air continuously until 2300 on a wide range of frequencies. Entirely in the English language, the programmes are intended for a wide range of consumption — worldwide in fact — hence the title 'World Service'.

The many frequencies used throughout the period are complex, we present only a few below:

From 1000 to 1030 on 7300, 9600, 9640, 9720, 9780, 11705, 11740, 11810, 11820, 11835, 11960, 11975, 12055, 15110, 15150, 15305, 15350, 15360, 15440, 15460, 15510, 17700, 17730, 17775, 17825, 17870, 17900, 21615 and on 21645.

Massive coverage such as the above goes on throughout the day on various channels but it is helpful to remember that from 0400 to 1230 21645 is in constant use.

Another listening period could be from 2000 to 2030, in which case the channels in use are 5920, 6010, 6020, 6030, 6130, 6200, 7150, 7175, 7300, 7320, 7330, 7440, 9490, 9550, 9630, 9745, 9760, 9785, 9795, 9810, 9845 and on 12050. The latter frequency is in use throughout the period 2000 to 2300.

AROUND THE DIAL

In which recent loggings, made in the village of Holbrook in the county of Suffolk — the gem of East Anglia — (the county not the village!) are featured.

● SPAIN

Radio Nacional Espana, Madrid, on 11920 at 1534, a round-table discussion on Spanish internal affairs.

RNE Madrid on 11930 at 1530, OM with announcements in Spanish amid recordings of local pops.

● KUWAIT

Radio Kuwait on 21605 at 1050, Arabic music, YL (young lady) with songs in the Domestic Service, scheduled on this channel from 0815 through to 1305.

● MALTA

Duetche Welle, Cologne, with a relay from Cyclops, Malta, on 17825 at 1123, OM (Old Man — male announcer) with the Japanese programme for Asia, scheduled here from 1115 to 1215.

● ISRAEL

Jerusalem on 17630 at 1147, OM with a

newscast in Hebrew in a relay of the Domestic Network B to Europe and the Middle East, scheduled here from 0610 to 1740.

Jerusalem on 11655 at 1210, OM with a newscast in the English programme to Europe, Middle East, S & E Asia, N. America, Australia & N. Zealand, scheduled from 1200 to 1230.

● CYPRUS

BBC Limassol on 21660 at 1040, religious service in English to Singapore and Malaysia from the East Mediterranean relay station, the English programme being scheduled from 0900 to 1130.

● USSR

Radio Moscow on 21645 at 1043, YL with the English World Service, featuring at this time some Georgian folk songs and music. Also logged in parallel on 21615. The recently innovated World Service is entirely in English, see opening paragraph.

● PAKISTAN

Radio Pakistan on a measured 21728.5 at 0735, OM with religious chants, YL with identification in the World Service to South Asia, Middle East and Africa scheduled from 0700 and to the U.K. additionally from 0715. Nominal frequency is 21730. Also logged in parallel on 21625.

Radio Pakistan on a measured 11642 at 1805, OM with local songs in the Turkish Service to Europe, scheduled from 1800 to 1900 except for the news in English from 1815 to 1820.

Radio Pakistan on 21625 at 1100, YL with identification and a news bulletin of local affairs read at slow-speed in English in the World Service to Western Europe, scheduled here from 1100 to 1115. Also logged in parallel on 17665.

● SOUTH KOREA

KBS Seoul on 7550 at 2050, YL with the French programme to Europe, scheduled here from 2030 to 2100 (the English programme is from 2000 to 2030). This channel is probably your best chance to log S. Korea.

● CHINA

Radio Peking on 11445 at 1311, YL with the Laotian programme to Laos, scheduled here from 1300 to 1400.

Radio Peking on 11685 at 1308, YL with the programme for Indonesia, scheduled from 1300 to 1330.

Radio Peking on 15060 at 1320, YL with the programme for Burma, scheduled here from 1300 to 1330.

Radio Peking on **7480** at 2045, Chinese classical music; YL with songs in the Standard Chinese programme intended for Europe and North West Africa, scheduled from 2000 to 2100.

● CHINA — REGIONAL

Chinese regional stations broadcast programmes intended for local consumption. Dxing these stations not only provides a lot of interest but also imparts a sense of achievement — providing one logs them!

CPBS Harbin, Heilongjiang, on **4840** at 2215, OM and YL alternate in Chinese. The schedule of this one is from 2040 to 0635 and from 0825 to 1430 and is in parallel on **4924**.

Urumchi (in the new Romanised form Urumqi), Sinjiang, on **4220** at 1543, YL with song in Chinese in a relay of the Peking Home Service. This channel carries the Home Service in Mongolian and also relays Peking (Romanised=Beijing), the schedule being from 2300 to 0555, 1100 and 1730 and also relays the Peking Foreign Service in Russian from 1800 to 2055.

Urumchi, Singjiang, on **4500** at 1540, YL in Chinese in the Home Service, scheduled here from 2300 to 0710, 1000 to 1730 and also relaying the Peking Foreign Service in Russian from 1800 to 2100.

CPBS Peking on **6345** at 1430, Chinese orchestral music in the Domestic Service 2, scheduled here from 2100 to 0030, from 0950 to 1700 Wednesday & Friday, other days from 1033 through to 1700.

CPBS Peking on **11610** at 1115, Chinese music, YL announcer in the Domestic Service 1, scheduled here from 0743 to 1300 and from 2333 to 0300.

CPBS Qinghai on **6260** at 2304, YL in Chinese, choral music, also logged in parallel on **6500**. Schedule unknown.

● EGYPT

Cairo on **17920** at 1150, YL with news of local affairs in the Arabic programme for South and South East Asia, scheduled here from 1115 to 1215.

● SWITZERLAND

Berne on **21520** at 1055, typical Swiss music in the Entertainment Programme for Africa, scheduled from 1030 to 1100. Also logged in parallel on **21630**.

● ALBANIA

Tirana on **7065** at 1530, OM with the Arabic programme to the Near and Middle East, scheduled from 1530 to 1600.

● BULGARIA

Sofia on **7670** at 1535, YL announcer with recordings of local-type music in the Serbo-Croat

programme for Europe, scheduled from 1530 to 1600.

● POLAND

Warsaw on **7125** at 1545, YL and OM with the Danish programme for Europe, scheduled from 1530 to 1600.

Warsaw on **7285** at 1540, YL with a talk in Finnish in the programme for Europe, scheduled from 1530 to 1600.

● SOUTH AFRICA

RSA Johannesburg on **21535** at 1335, sports commentary in the English programme for Central and East Africa, Europe and the Middle East, scheduled from 1300 to 1600 (1500 to 1600 Sunday).

● AUSTRALIA

Melbourne on **9570** at 0759, YL with frequency details after station identification, 6 pips time-check at 0800 followed by a newscast in English.

Melbourne on **11740** at 0750, OM with the English programme for Europe (answering listeners letters). The English programme is scheduled here (at the time of writing) from 0700 to 0900.

● ITALY

Rome on **7275** at 1548, OM and YL with the German programme for Austria, scheduled from 1535 to 1550.

● WEST GERMANY

Deutsche Welle, Cologne, on **21600** at 1047. OM with identification followed by a newscast in the English programme to Central and East Africa, scheduled here from 1045 to 1115.

● NETHERLANDS

Hilversum on **9895** at 1335, OM with a talk about the prevailing weather in Holland in the English programme for Europe, scheduled from 1330 to 1420.

● VATICAN

Vatican City on a measured **6221.5** at 1050, OM and YL with announcements in English, classical music followed by announcements in various European languages.

● CLANDESTINE

Voice of the People of Thailand on a measured **9423** at 1512, local-type music, YL with songs in Thai.

● NOW HEAR THIS

Malabo, Equatorial Guinea, on **6250** at 2245, YL announcer, local-style music, songs with female chorus. The clock time quoted is just right for reception of this station, Radio Pyongyang is off channel, allowing the signal from Malabo to get through to the U.K. — we hope!

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 63p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

BASIC SHORT WAVE

By R. A. Pe



Uncomplicated
design covers
1.2 to 24

Five simple controls, of which one, for aerial attenuation, is only required occasionally, make this neat little short wave receiver easy to operate

For the enthusiast seriously interested in short wave Dx reception (i.e. the reception of distant, rare or otherwise difficult stations) the ideal receiver is, of course, a high quality superhet with good i.f. filters, a b.f.o. and a host of other specialised features. However, even a fairly modest short wave superhet receiver can be quite expensive to buy, whilst the less expensive approach of building one's own receiver is only open to the more experienced constructor.

Fortunately, it is possible to obtain quite good results from considerably simpler equipment, such as the short wave radio which forms the subject of this article. This is a t.r.f. (tuned radio frequency) design, and it differs from a superhet in that it detects the received signal at radio frequency rather than converting it first to an intermediate frequency which is fed to an i.f. amplifier. The t.r.f. receiver cannot have the same sensitivity and selectivity as has the superhet but it employs much simpler and cheaper circuitry, and it requires no complicated alignment after it has been completed. Dx signals may be readily picked up with a t.r.f. set provided that the operator exercises the requisite skill and patience.

THREE TRANSISTORS

The present receiver incorporates three transistors, one of which is a field-effect type. It is powered from its own internal 9 volt battery and has an output which is suitable for high, medium or low impedance headphones. It will also work well with a single crystal earphone, but proper

headphones are to be preferred for long periods of comfortable listening.

Three ranges are covered, the frequencies being approximately 1.2 to 4.2MHz in Range 1, 3.5 to 13.5 MHz in Range 2 and 7.0 to 24.0 MHz in Range 3. The set requires an external aerial of the long wire type, but it is still capable of receiving a great many stations with a short indoor aerial if, for any reason, a proper outdoor aerial cannot be provided.

The circuit of the receiver is given in Fig. 1. TR1 and TR2 provide r.f. amplification and detection, and appear in a hybrid cascode configuration which provides high gain and a low noise level at all the frequencies received. TR3 is a straightforward a.f. amplifier which also offers a high degree of gain.

The field-effect transistor, TR1, is used as a common source amplifier with source bias provided by R1 and R2 in series. R1 is adjusted to give optimum bias with the particular f.e.t. employed. The electrolytic capacitor C7 bypasses audio frequencies but, since it is not entirely effective at radio frequencies, the r.f. bypass is provided by the parallel capacitor, C2. The gate of TR1 is biased to the negative rail by the tuned winding of whichever r.f. transformer is switched into circuit by the range switch. There are three r.f. transformers, L1, L2 and L3, these corresponding to the similarly numbered ranges. For simplicity only L2 is shown in Fig. 1, the switch connections to L1 and L3 being identical.

VC1 is the main tuning, or "Bandset" control, whilst the lower value VC2 is the "Bandspread"

WAVE RADIO

Penfold

ated t.r.f.
covering
4 MHz.

control. The manner in which these controls are operated is described later. The aerial is coupled to a tap in the r.f. transformer tuned winding by way of S1(b) and VR2. The potentiometer acts as a simple aerial attenuator and may be needed to reduce the input signal strength if the detector becomes overloaded, or if the loading effect of the aerial prevents correct regeneration being obtained.

TR2 is connected in the common base mode, its emitter being driven directly from the drain of TR1. Bias is provided by R4 and R5, with C3 bypassing the base to the negative rail. The choke L4 offers a high impedance at r.f., and a proportion of the r.f. signal at TR2 collector is fed back, via C1, VR1, S1(a) and a coupling winding on the r.f. transformer selected, to the aerial input tuned winding. This feedback is positive and provides regeneration, or reaction, the level of feedback being controlled by VR1. When VR1 is adjusted so that the circuit is just below the threshold of oscillation, or is just beyond it, the effective Q of the tuned circuit is increased very many times, allowing the receiver to exhibit high sensitivity and selectivity. With the present circuit the regeneration also increases the detection efficiency.

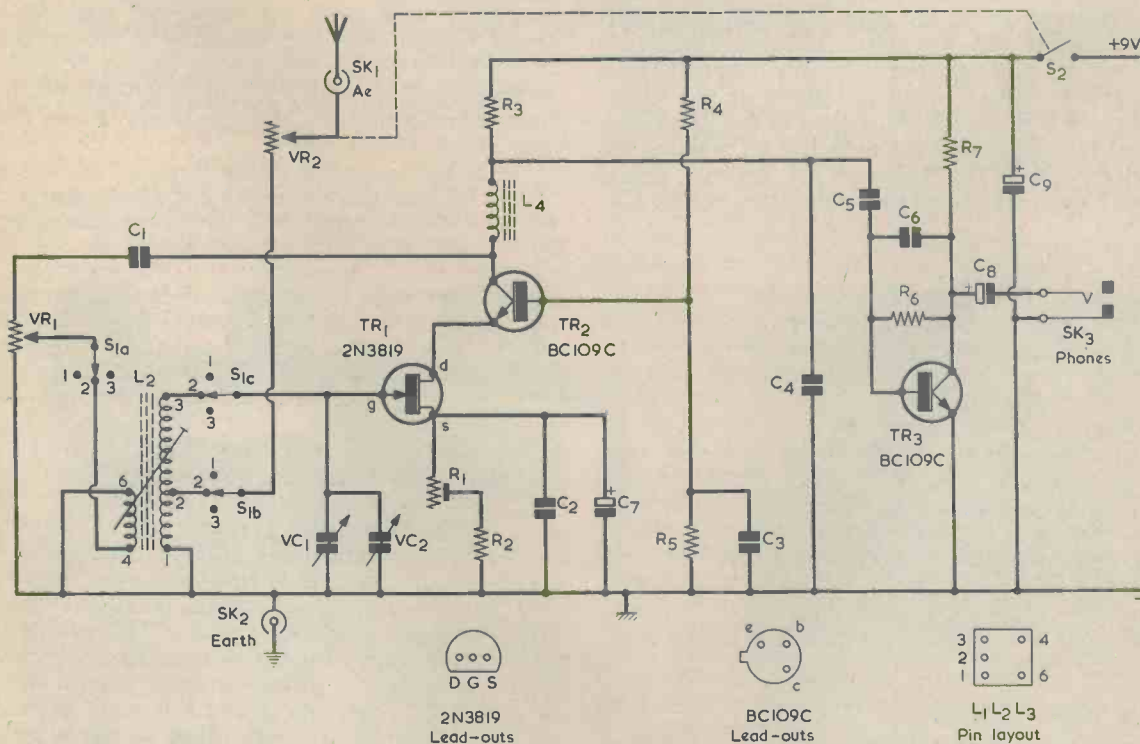


Fig. 1. The circuit of the short wave receiver. One of its attractive features is a very low battery current of 2.5mA only

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

- R1 2.2k Ω pre-set potentiometer, 0.1 watt, horizontal
- R2 470 Ω
- R3 1k Ω
- R4 6.8k Ω
- R5 6.8k Ω
- R6 1.8M Ω
- R7 5.6k Ω
- VR1 1k Ω potentiometer, linear
- VR2 5k Ω potentiometer, log, with switch S2

Capacitors

- C1 100pF ceramic plate
- C2 0.01 μ F type C280
- C3 0.1 μ F type C280
- C4 0.015 μ F type C280
- C5 0.1 μ F type C280
- C6 270pF ceramic plate
- C7 47 μ F electrolytic, 10V. Wkg.
- C8 47 μ F electrolytic, 10V. Wkg.
- C9 100 μ F electrolytic, 10V. Wkg.
- VC1 365pF variable, type 01 (Jackson)
- VC2 25pF variable, type C804 (Jackson)

Semiconductors

- TR1 2N3819
- TR2 BC109C
- TR3 BC109C

Inductors

- L1 R.F. transformer type KANK 3333R (Toko-Ambit)
- L2 R.F. transformer type KANK 3334R (Toko-Ambit)
- L3 R.F. transformer type KANK 3335R (Toko-Ambit)
- L4 10mH r.f. choke type 8RB 187LY103 (Toko-Ambit)

Switches

- S1 3-pole 4-way rotary with adjustable end stop (see text)
- S2 s.p.s.t. toggle, part of VR2

Sockets

- SK1 insulated wander plug socket, red
- SK2 insulated wander plug socket, black
- SK3 3.5mm. jack socket (see text)

Miscellaneous

- Metal instrument case (see text)
- Headphones with 3.5mm. jack plug (see text)
- 9-volt battery type PP3
- Battery connector
- 1 large control knob
- 4 medium size control knobs
- Materials for printed board
- Nuts, bolts, wire, etc.


Detection is achieved due to non-linearity in TR2. Negative-going half-cycles at its emitter cause TR2 to conduct more heavily, with a consequent increase in current gain. Positive-going half-cycles have the opposite effect. The non-linearity is enhanced by the regeneration and it results in a detected a.f. signal being produced at the upper end of the r.f. choke. R3 functions as the a.f. collector load for TR2, and the detected a.f. signals are passed via C5 to the base of TR3. Any r.f. signal present here is bypassed to the negative rail by C4.


TR3 is a standard common emitter a.f. amplifier, with R7 as its collector load and R6 providing bias. C6 rolls off the higher audio frequencies and gives an improved signal-to-noise ratio. C8 provides d.c. blocking at the output.

C9 is the supply decoupling capacitor whilst S2, which is ganged with VR2, is the on-off switch. The current consumption of the receiver is very low, being about 2.5mA only.



With the exception of the three r.f. transformers, L1 to L3, and the r.f. choke L4, all the components

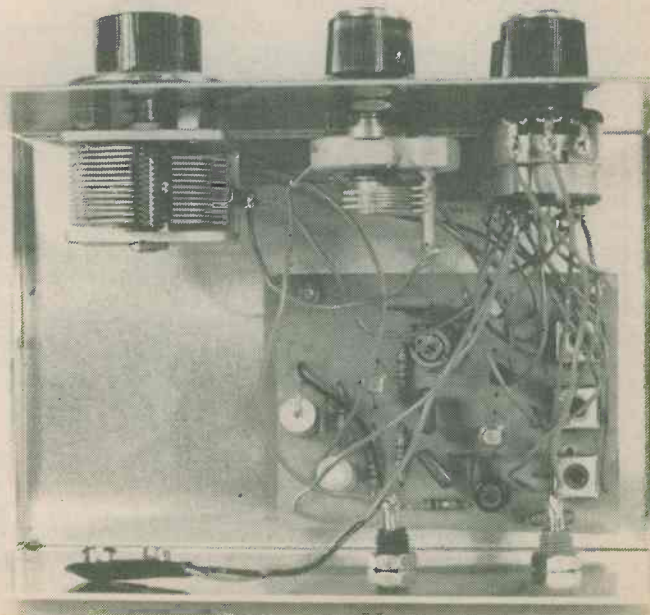Most of the components are assembled on a printed board with wire interconnections to the front panel controls



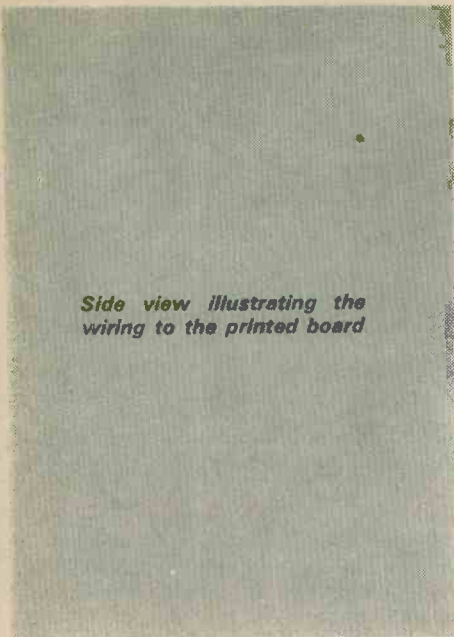

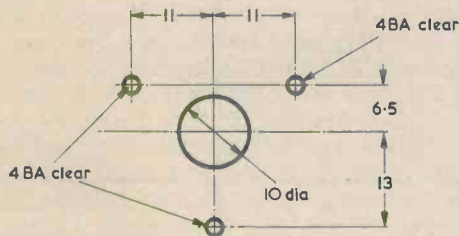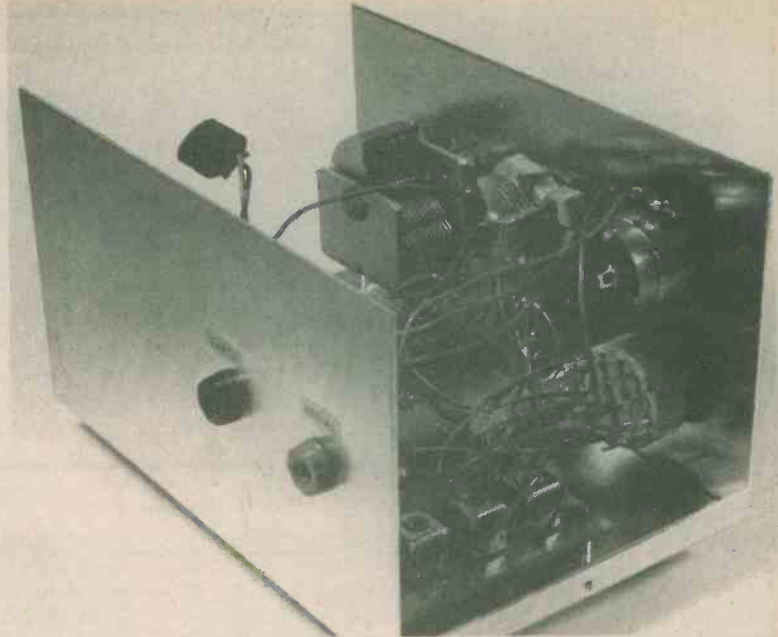Side view illustrating the wiring to the printed board



All dimensions in mm

Fig. 2. The variable capacitor VC1 is mounted by means of three 4BA bolts passing through holes in the front panel. These appear round the central hole for the spindle in the manner shown here

are generally available. The transformers and the choke are all manufactured by Toko, and can be obtained from Ambit International. The receiver is housed in a metal instrument case type BC2, available from Harrison Bros., P.O. Box 55, Westcliff-on-Sea, Essex SS0 7LQ. It has dimensions of 6 by 4 by 3½ ins.

ASSEMBLY

The controls and output socket SK3 are mounted on the front panel, using the layout shown in the photographs. At the upper left is VR2/S2, with VC2 to its right. Below VR2/S2 is S1(a)(b)(c), and below VC2 is VR1. To the right, with the larger knob, is VC1, with SK3 below it. The precise positioning of the front panel components is not important, although the two pairs of controls to the left should be centred on the same horizontal and vertical lines for the sake of appearance. The output jack socket should be of open construction (i.e. not insulated) since it takes up its sleeve connection to chassis from its mounting bush and nut.

VC1 is mounted by three short 4BA countersunk bolts passing through 4BA clear holes laid out in the manner shown in Fig. 2. The bolts fit into tapped 4BA holes in the front plate of the tuning

capacitor, and it is important to ensure that the bolt ends do not pass more than marginally past the capacitor front plate as they could then damage the fixed or moving vanes. Spacing washers are fitted over the bolts between the inside surface of the front panel and the capacitor front plate. The capacitor takes up its chassis connection via these mounting bolts. The chassis connection to VC2 is made by way of its mounting bush and nut.

SK1 and SK2 are mounted on the rear panel of the case, with SK1 roughly opposite VR2/S2 and SK2 roughly opposite VC2.

All the smaller components are assembled on a printed circuit board which is reproduced full size in Fig. 3. This is produced and wired up in conventional manner, and it should be noted that the holes for the mounting lugs of L1, L2 and L3 need to be slightly larger than the other component mounting holes. For maximum accuracy, the mounting lug and coil pin holes may be marked out with the aid of the r.f. transformers themselves.

As can be seen from Figs. 3 and 4, there is quite a lot of interwiring between the printed board and the front panel components. The board is finally positioned in the manner shown in the photograph of the receiver interior, with L3 closest to S1(a)(b)(c), and two 6BA clear holes are required in the bottom of the case for securing it in position. The wiring should be as short and direct as possible, including in particular that to VC1, VC2 and S1(a)(b)(c). An unconventional approach, but one which will probably prove easiest for many constructors, is to complete the wiring from the printed board to S1(a)(b)(c), VR1 and VR2/S2 with the board and the controls *outside* the case. Include a lead from the arm of S1(c) for later connection to VC2 fixed vanes. The board and the panel components are then finally mounted in place. Note, incidentally, that S1(a)(b)(c) is a 3-pole 4-way rotary switch with adjustable end stop set for 3-way operation. The underside of the printed board is held clear of the case bottom by short metal spacing washers. A chassis connection to the board is made via the copper print to these washers. There is also a wired chassis connection from one tag of VR1 to the moving vanes tag of VC2.

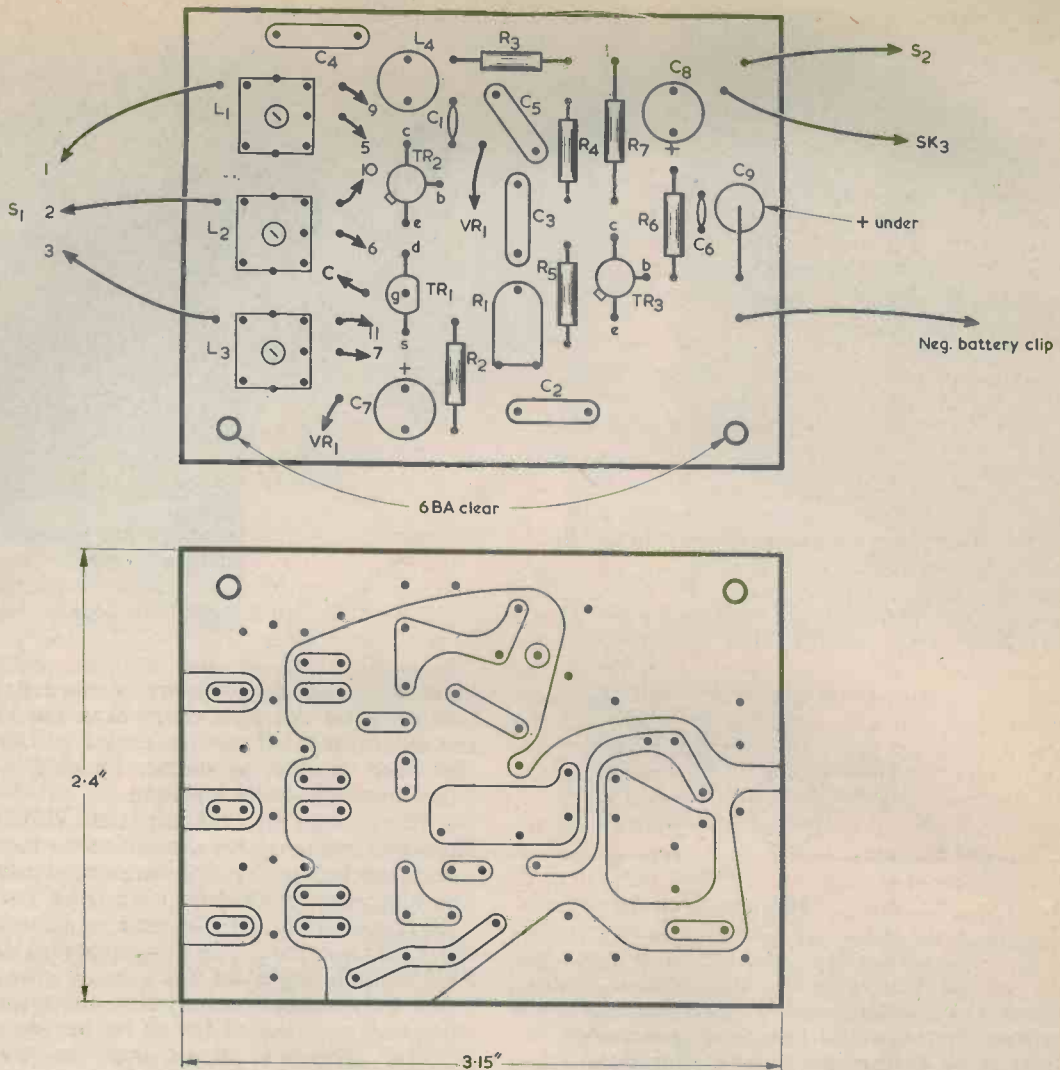


Fig. 3. The printed circuit board, reproduced actual size. The letter and number references indicate connections to the front panel components shown in Fig. 4

Shortening as necessary, the lead from S1(c) arm may be connected to the fixed vanes of VC2, which connect in turn to the fixed vanes of VC1. The lead from the board to SK3 may now also be connected. The only remaining connections should be to SK1 (from VR2 slider) and to SK2 (from the moving vanes tag of VC2).

AERIAL AND EARTH

Quite good results can be obtained by simply using a few metres of wire strung around the room as an aerial. With the prototype, even a telescopic aerial little more than a metre long produced good reception of a surprisingly large number of stations. However, as with any short wave receiver, a better aerial system gives improved results. This is especially the case with the lowest frequency Range 1, and here an earth connection will also result in a considerable increase in the number of stations which can be picked up.


An acceptable outside aerial will normally be about 10 to 30 metres in overall length, hung as high as possible and well away from buildings, walls and other earthed objects. The earth connection can consist of a metal spike or pipe pushed into

the ground at any convenient point and connected to the receiver by way of a lead which should be as short as possible. Apart from increasing signal strengths at low frequencies, the earth connection will also eliminate the otherwise inevitable hand capacitance effects which may be apparent when tuning in high frequency s.s.b. and c.w. signals.

USING THE SET

The receiver is switched on by rotating VR2/S2 knob clockwise until S2 closes. Normally, the potentiometer need not be advanced clockwise any further than is needed to operate the switch. Advancing the potentiometer further causes the aerial signal to be attenuated, and such attenuation is only needed if the detector is being overloaded by strong signals or if aerial loading effects prevent adequate regeneration from being obtained. Overloading will manifest itself in the form of a high background noise level and an almost total loss of selectivity. Aerial loading effects are only likely to be given with very long aeriels and they prevent VR1 from taking the detector to the oscillation point at certain bands of frequencies.

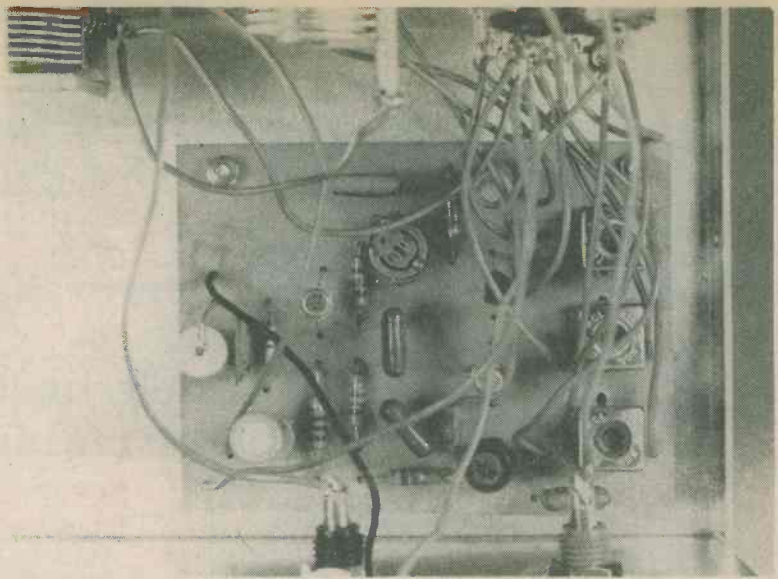Close-up view of the component board. This is secured to the chassis by two 6BA bolts and nuts, with spacing washers



When initially testing the receiver it is advisable to set S1(a)(b)(c) to Range 2, as there will be a large number of strong transmissions in this range at virtually any time. If VR1 is set fully anti-clockwise it is probable that few, if any, stations will be received. Advancing VR1 clockwise will increase the number of stations received, as well as their strengths, and will also improve the ability of the receiver to pick out just one of several closely spaced transmissions. However, VR1 is a regeneration control and not an a.f. or r.f. gain control, and if it is advanced too far the detector will go into oscillation. This will be heard as a tone of varying pitch as the receiver is tuned across an a.m. station and will make the proper reception of a.m. signals impossible. For optimum a.m. reception, both in terms of sensitivity and selectivity, VR1 should be adjusted so that the detector is just below the threshold of oscillation. The setting of VR1 varies at different frequencies, and it should be readjusted when the tuning control settings are altered significantly.

C.W. (morse) and s.s.b. (single sideband) are the

transmission modes which are mainly used on the amateur bands, and these signals can be resolved by adjusting VR1 so that the detector is just beyond the threshold of oscillation. With an s.s.b. signal the tuning must be adjusted to produce an audio signal of the correct pitch and very careful and accurate adjustment is needed in order to achieve this. Strong s.s.b. signals may be rather distorted unless VR1 is advanced a little further to produce stronger oscillation or VR2 is adjusted to decrease the signal strength.

Tuning will be difficult with VC1, particularly on Ranges 2 and 3, as a small movement of its knob will take the receiver through many stations. This problem is overcome by setting VC1 to the part of the range which is to be searched for stations, and then carrying out the actual tuning by means of VC2. Since the latter has a much lower value than VC1 it covers only a very limited range of frequencies and enables tuning to be far easier.

The required adjustment in pre-set potentiometer R1 will not normally be very critical, and the best setting is found by trial and error. It is necessary to include this potentiometer in the circuit due to variations in bias requirements between different 2N3819 transistors. If R1 is set too high in value (adjusted too far in a clockwise direction) it is likely that there will be a lack of gain and regeneration, with consequently poor results. On the other hand, too low a value may make the set difficult to operate and, with some samples of the 2N3819 in the TR1 position, could even result in the receiver ceasing to operate. It is really just a matter of experimenting with R1 at various settings to find the one which gives the best all-round results.

The r.f. transformers, L1, L2 and L3 are fitted with adjustable tuning cores but, in the absence of a suitable signal generator to set specific frequency coverages, these should be left at the settings they have when the transformers are purchased. The receiver should then cover approximately the frequency ranges stated earlier.

Finally it should be borne in mind that short wave propagation conditions vary throughout the day. In general, the low frequency bands produce the greatest number of stations during the hours of darkness, whereas the high frequency bands provide good long distance reception during daylight hours and tend to fade out completely after dark. There are no hard and fast rules here, however, and propagation can also be affected by seasonal and other variations.

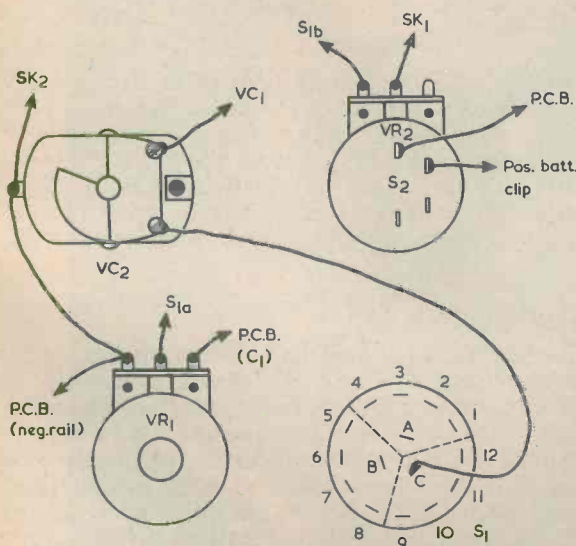


Fig. 4. Connections to VC2, VR2/S2, VR1 and S1(a)(b)(c). Confirm with a continuity tester the outer tags corresponding to the inner tags of S1(a)(b)(c) before wiring to this switch, as relative tag positioning may differ with some components

WORKSHOP POWER SUPPLY — Part 2

By R. A. Penfold

The concluding article on this high performance multi-option mains power supply

In last month's issue we dealt with the circuit design of this comprehensive power supply and commenced its construction. We now conclude with the remaining constructional details.

HEATSINK


TR1 and TR2 are mounted on the large heatsink using mica washers and insulating bushes. A solder tag is fitted under one mounting nut for each transistor to provide connection to the collector. Insulated leads about 200mm. long are then connected to the emitter and base and the collector tag of each transistor and these are led through two holes in the rear of the case, the holes being fitted with grommets. The leads should have different colours, which are noted down so that the transistor connections can be correctly identified later. The heatsink is bolted to the rear of the case, near the mains transformer end, in the position shown in the photographs. It may be used as a template for

marking out its six mounting holes. Before finishing with this part of the assembly, check with an ohmmeter that the transistor bodies are fully insulated from the heatsink. Confirm also that the connections to the transistor base and emitter pins, and to the collector tag, are well clear of the rear surface of the metal case.



A hole for the mains lead is drilled to the left of the heatsink (as viewed from the rear). This is fitted with a grommet. A plastic or plastic-faced clamp will be required to secure the mains lead on the inside of the case.

COMPONENT BOARD

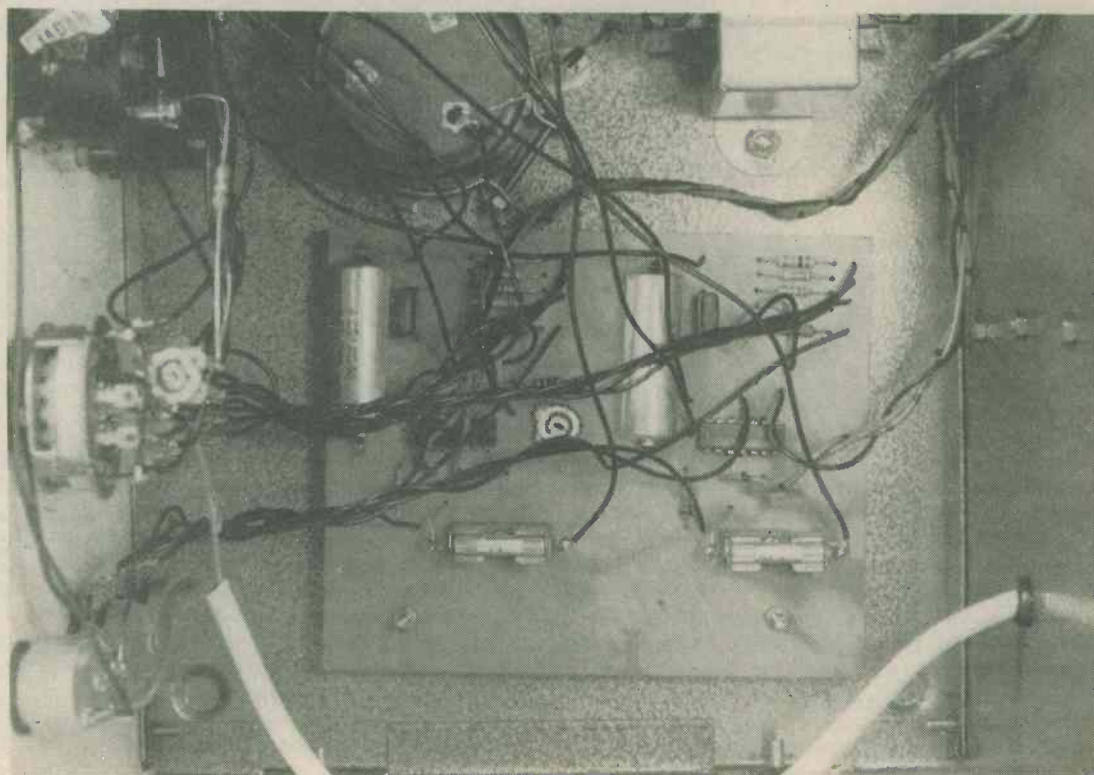Many of the small components are assembled on a printed circuit board which measures 100mm. by 120mm. The copper backing pattern of the board is reproduced actual size in Fig. 5. The two fuseholders are each fixed in position by means of a short 6BA bolt and nut. Mounting holes are not



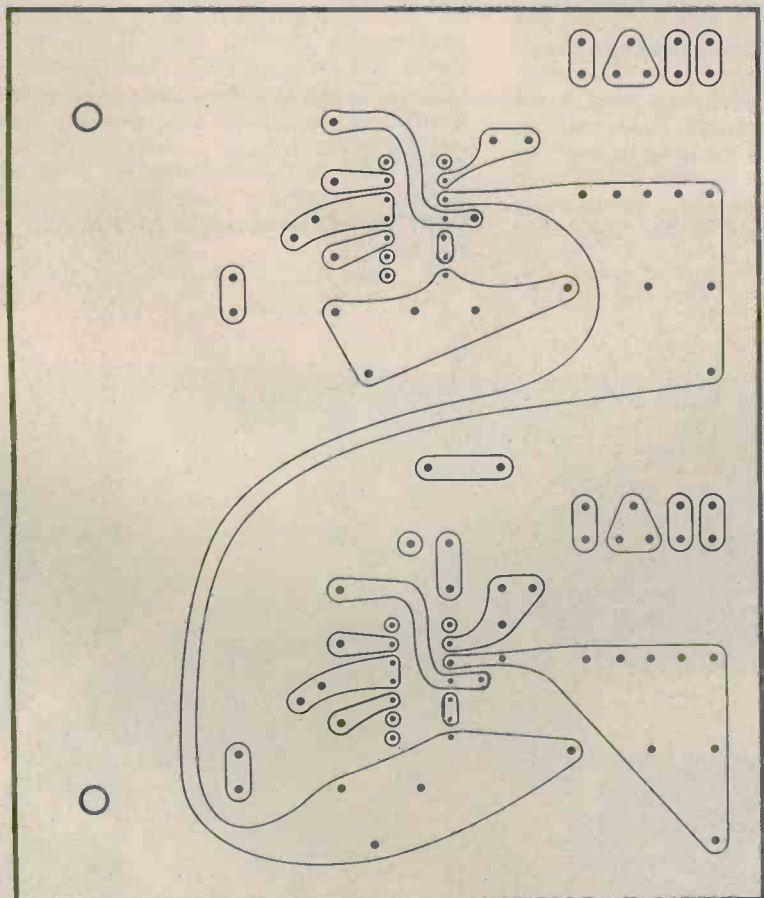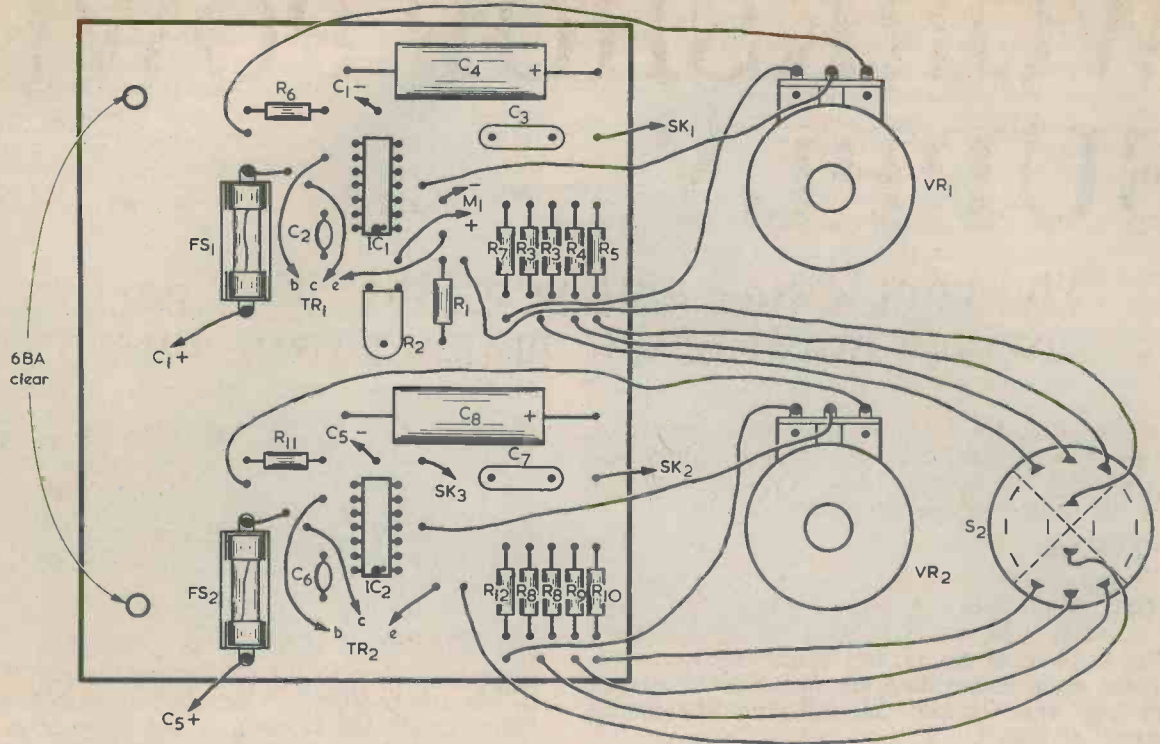Many of the small components are assembled on a printed circuit module. This is secured to the base plate of the power supply instrument case



Printed board
100 x 120 mm
shown full size

Fig. 5. The printed circuit board for the workshop power supply is shown here actual size. It will be noted that there are two resistors marked R3 and two resistors marked R8. This is because R3 and R8 each consist of two resistors in parallel

shown in Fig. 5 and these should be marked out with the aid of the fuseholders themselves. The fuseholders may have a locating pip on the underside; a second hole is then required for this.

It will be seen that there are two resistors marked "R3", and two resistors marked "R8". This is because R3 and R8 each consist of a 1.2 Ω resistor and a 1.5 Ω resistor in parallel.

The completed component board is mounted on the base of the case behind the controls with C4 at the front. In the prototype, the board was mounted with 6BA screws about 25mm. long, spacing washers about 10mm. long keeping the underside connections clear of the case. It is essential that the board underside be well clear of the case metalwork; longer screws and spacing washers can be used if the constructor wishes to provide a really good clearance here. The board cannot be finally mounted in position until all the external wiring to it has been completed.

OTHER WIRING

The eight rectifiers, D1 to D8, are wired in point-to-point fashion between the transformer secondary tags and C1 and C5, following the circuit diagram of Fig. 2.


The wiring associated with the front panel components is illustrated in Figs. 5 and 6. When the wiring in Fig. 5 has been completed, the component board may be finally bolted in position. The leads from TR1 and TR2 to the board may need to be shortened in the interests of neatness. Before wiring to the rotary switches, confirm visually or with an ohmmeter the outer tags which correspond to each inner tag. With some switches their positioning with respect to each other may differ from that shown in Figs. 5 and 6.

The wiring in Fig. 6 is point-to-point, with R14 and R13 being soldered to the tags of S4 and meter M2 as indicated. In practice, the slider tag of R14 is soldered direct to the tag of S4, the potentiometer body being horizontal so that it may be easily adjusted. R13 is then positioned laterally between R14 track tag and the positive meter tag. The result is an adequately firm mounting for these two components.


ADJUSTMENT

When the construction has been completed, all the wiring should be carefully checked to make certain that there are no errors. A wiring fault could cause damage to components when the supply is switched on. At this stage the lid of the case will not be fitted, whereupon mains connections are accessible at the on-off switch, the mains transformer primary tags and at the tags of the neon indicator if this is a type which does not have flying leads. Due care must be observed to avoid accidental shock. At this stage R2 and R14 should be adjusted to insert maximum resistance into circuit.

A multimeter switched to a suitable voltage range can be employed for the first tests on the unit. The power supply is switched on and the multimeter connected to each of the outputs in turn, checking that the range of output voltages provided by the appropriate control potentiometer is approximately correct. Next R14 is set up so that meter M2 gives an f.s.d. reading at 25 volts. To do this, S4 is set to select one of the outputs and the multimeter is applied to the output terminals. The control potentiometer is then adjusted for a reading of 20 volts in the multimeter, after which R14 is adjusted to give a corresponding reading in M2. With the original scale calibration, this will be 80 μ A.

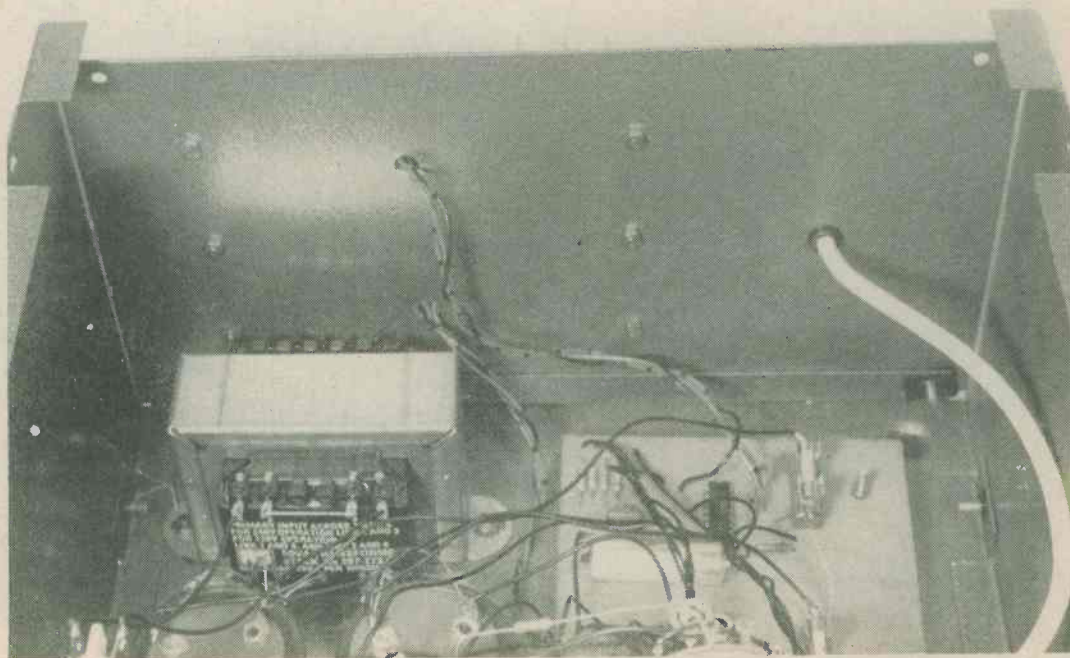

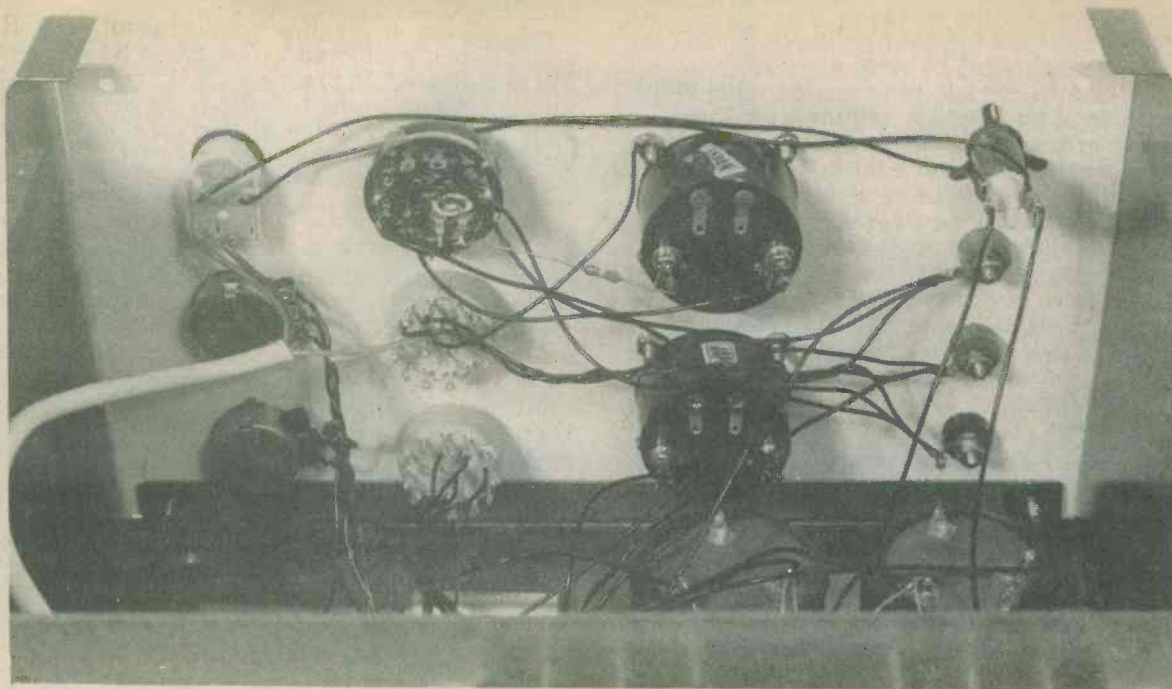Detail illustrating the mains transformer and the rear of the case. The eight bridge rectifier diodes are wired between the secondary tags on the mains transformer and the tags of C1 and C5



Behind the front panel of the power supply. Point-to-point wiring couples the panel components to the remainder of the circuit

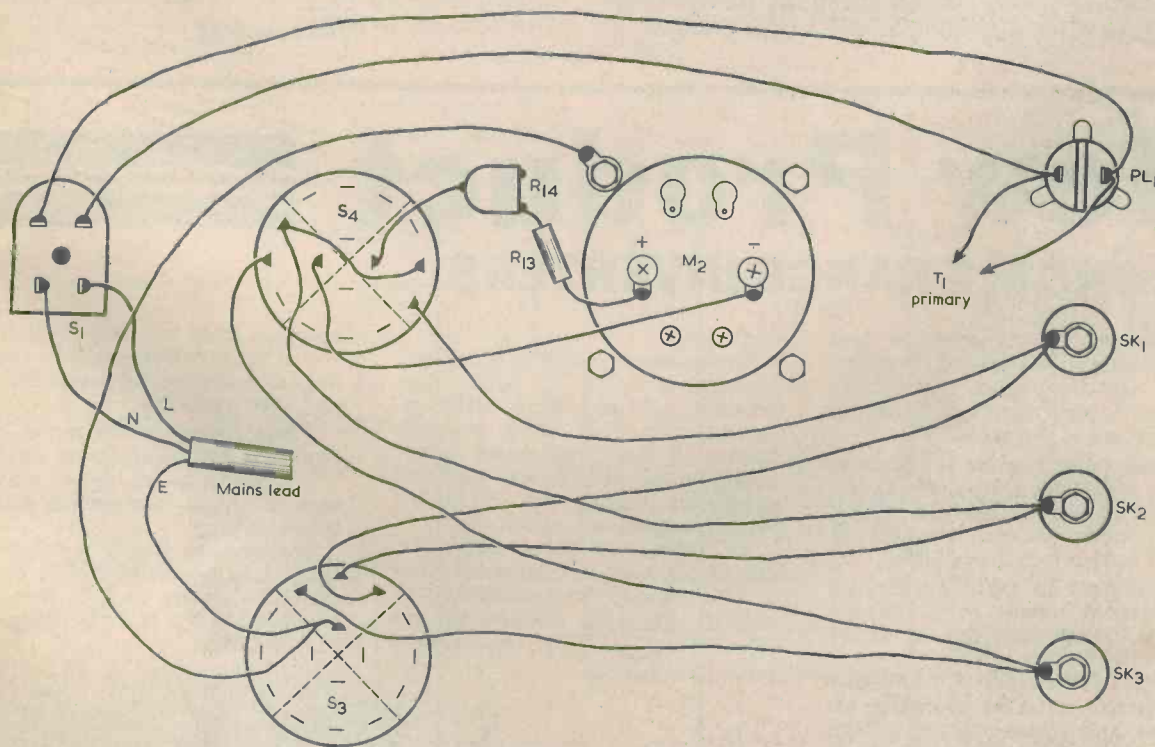


Fig. 6. The remaining wiring behind the front panel. The mains earth wire connects first to the arm of S3 and then to chassis by way of the solder tag secured under one of the mounting nuts of M2

It is next advisable to check that the current limiting circuits are functioning correctly. The two outputs are adjusted to 10 volts, after which each is tested in turn in the following manner. Switch the testmeter to a range which will allow it to give an indication of 1 amp, set S2 to the 1 amp position, and connect the testmeter to the output terminals with a 4.7Ω 5 watt resistor in series. If the current limit circuit is functioning correctly, the testmeter should give a reading of approximately 1 amp. Should there be a fault then the maximum current which can flow in the testmeter is limited to approximately 2 amps. Repeat the procedure with the 100mA limit, but this time inserting a 47Ω 1 watt resistor in series with the testmeter. The latter should indicate about 100mA if all is well. Finally carry out the check at the 10mA limit using a 470Ω $\frac{1}{4}$ watt resistor in series with the testmeter, whereupon the testmeter should indicate approximately the current limit value. As with the 1 amp test, the series resistors of 47Ω and 470Ω limit the current which can flow in the testmeter to about twice the current limit value. These checks must be carried out very carefully to ensure that there is no risk of damage to the testmeter.

When both outputs have been tested in this manner, S2 is set for the 100mA current limit and the testmeter is connected once more to the positive output with the 47Ω 1 watt resistor in series. Once again the testmeter should give an indication of 100mA. R2 is then adjusted so that meter M1 gives the same reading as that given by the testmeter. If the latter should be slightly in excess of 100mA, VR1 is adjusted to reduce the output voltage so that the testmeter reading is just at 100mA. R2 can then be adjusted for a reading of 100 in meter M1.

METER CALIBRATION

Perfectionists may wish to alter the meter scales so that they represent more accurately the currents and voltages that they measure. It is possible to remove the front covers of the meters and unscrew the scale plates for modification, but it must be strongly emphasised that this operation should only be carried out by constructors who have had experience in this type of work and who feel competent to carry out this task. The meters have very delicate mechanical movements which can be easily damaged by careless handling or by the entry of particles of dirt or dust.

In the case of meter M1, the legend "Microamperes" should be removed or covered, being replaced by the term "mA". The 0-100 scale does not need to be altered. With meter M2, the term "Microamperes" is replaced by "Volts". Also its scale is altered from "0-100" to read "0-25". The existing "0" is replaced by a "0" in the new figure type. "20" is changed for "5", "40" for "10", "60" for "15", "80" for "20" and, of course, "100" for "25". The new legends and figures may be cut out from "Panel-Signs" Set No. 4, which is obtainable from the publishers of this magazine.

The unwanted existing letters and figures can be gently scraped off, or they may be covered with thin white paint. Again, it must be reiterated that the process of altering the scales should not be attempted unless the constructor is fully confident that he can carry it out without damaging the meters.

(Concluded)

New Product

ECONOMY RANGE INVERTERS

Messrs. Electro Vance are specialising in the sale of inverters. They say they find particularly popular is their range of Economy Transistorised Inverters.

These units convert low voltage d.c. to 200/240v a.c. power simply, and they are suitable for many applications where a domestic mains source is not available.

Assembled in plain aluminium instrument cases with rexine material cover, they use an off the shelf transformer to form the main circuitry. Silicon power transistors are used to form the switching oscillator and instead of using high class branded famous name transistor, these economy inverters use cheaper but similar transistors. The transistors are new, numbered and not rejects.

These inverters are not suitable for absolute continuous use, as the housing cases do not have any ventilation slots and inverters can run fairly warm — all units are d.c. in-

put fused.

Operation is easy to complete, clip onto a normal car battery two polarity coloured leads with attached croc/clips, plug into the rubber 13 amp type mains output socket on the inverter any electrical appliance within the rated inverters wattage and switch on.

DC inputs available are 12v, 24v, 48v, as per models AC output is rated at 240v off load (no equipment connected) dropping on-load to approximately 200/220v AC. These

economy units will only keep within 8% of 50Hz when the full wattage output is drawn. Square wave output only available.

These inverters will power most domestic electrical items such as TV's, radios, razors, record players, tape recorders, hair curlers, electric blankets etc.

Electro Vance supply a substantial range and enquiries should be addressed to them at P.O. Box 191, London SW6 2LS or by telephone 01-736 0685.




How to control a lamp — or a relay — by successive sound signals.

This is the seventh in the series of articles describing projects which can be built up on two S-DeCs and it deals with a circuit which is activated by sound signals to operate a low voltage light bulb. The circuit is a development of the switching circuit featured last month in "Double Deccer" No. 6. A sharp intense sound such as is obtained from breaking glass or snapping wood will switch the light on, after which another similar sound will switch it off again. Alternatively, the reset switch can be used. The effective range depends very much on the sensitivity of the microphone employed; it is better to place an insensitive microphone near the source of sound than it is to have a sensitive microphone remote from the sound. This is because a sensitive microphone will trigger the circuit too easily on stray sounds. For burglar alarm use (when the lamp would probably be replaced by a relay operating a bell) an insensitive microphone placed near a window or a door is better than a sensitive microphone in the centre of the room being protected.

The circuit can be divided into sound amplifier, pulse former, bistable and lamp driver stages. Since the lamp driving stage has a relatively high current capability, the lamp can be replaced by a relay coil (with parallel protective diode) using the circuit which was shown in "Double Deccer" No. 6.

MICROPHONE

The microphone connects to points 30 and 21 of DeC 1, coupling to the base of TR1 through C1. TR1 and TR2 form a Darlington input circuit with a fairly high input resistance. Bias is provided by R1 which, because of the large current gain in the Darlington pair, has the high value of 1MΩ. The voltage gain of the two transistors is no greater than that of a single transistor fed from a low resistance signal source, but the Darlington circuit has the advantage of offering an input resistance which is high enough to avoid excessive losses when a medium impedance or high impedance microphone is used.

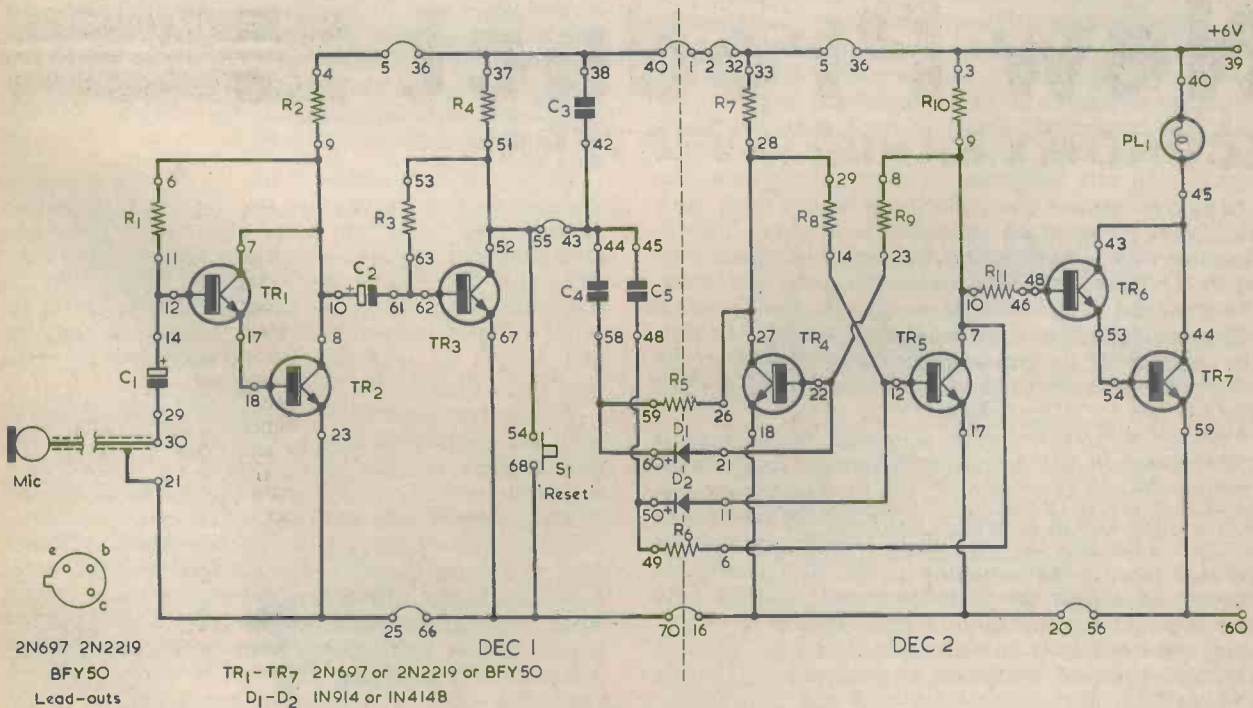

The circuit of the sound-operated light switch. The lamp is alternately turned on and off as the microphone picks up consecutive sounds

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5%)

R1 1M Ω	R7 1.8k Ω
R2 12k Ω	R8 22k Ω
R3 150k Ω	R9 22k Ω
R4 22k Ω	R10 1.8k Ω
R5 150k Ω	R11 56k Ω
R6 150k Ω	

Capacitors

C1 10 μ F electrolytic, 16 V. Wkg.
C2 10 μ F electrolytic, 16 V. Wkg.
C3 0.001 μ F polyester or mylar
C4 0.001 μ F polyester or mylar
C5 0.001 μ F polyester or mylar

Semiconductors

TR1-TR7 2N697 or 2N2219 or BFY50
D1, D2 1N914 or 1N4148

Lamp

PL1 6V, 60mA, m.e.s.

Switch

S1 push-button, press to make

Miscellaneous

2-off S-DeC
6V battery
Lampholder, m.e.s.
Microphone (see text)
Jack socket (see text)

The second stage, TR3, functions as an amplifier and pulse former. The transistor has a fairly large value collector load resistor, and is deliberately overbiased so that its collector voltage is only just over 1 volt above the negative supply rail. Incidentally, this voltage can only be measured accurately with a high resistance meter, such as a 50k Ω per volt meter switched to a 10 volt range. TR3 operates at full gain, so that the signal applied to its base becomes clipped at its collector. The signal at the collector will have a low voltage limit of about 0.2 volt (the bottomed voltage of the transistor) and a high voltage limit approaching the 6 volts of the supply. In the presence of signal, therefore, the average voltage at the collector is higher than the 1 volt level given when no signal is applied. This is another way of saying that the signal has been partially rectified by TR3 (a linear amplifier transistor would never bottom or cut off). C3 acts as a reservoir capacitor for this rise in voltage, so that the action of a few sound waves reaching the microphone is to make the voltage at point 42 of DeC 1 rise by a few volts.

When the sound ceases, however, the voltage at TR3 collector will return to its normal level, causing the voltage at point 42 to fall in similar manner. The rate of fall of voltage is governed by the rate at which C3 charges through TR3. The drop in voltage constitutes a negative-going pulse, and it will be enough to trigger the bistable circuit around TR4 and TR5. The operation of a bistable circuit of this type has been fully explained in previous "Double Deccer" articles, including in particular "Double Deccer" No. 3.

The reset push-button connects the collector of TR3 to the negative rail, causing a negative-going pulse to be transmitted through C4 and C5 when it is pressed. This will trigger the bistable so that if the lamp were illuminated it goes out. The bistable

is then in the ready condition with TR5 conducting fully and TR4 cut off. A sound pulse from the microphone will, as just described, cause the bistable to switch over, so that TR4 conducts fully and TR5 cuts off. Current now flows through R10 and R11 into the base of TR6, whereupon an amplified emitter current passes into the base of TR7 which turns on and lights the lamp in its collector circuit. Due to the high combined current amplification provided by TR6 and TR7 the lamp can if desired be replaced by a relay coil requiring a considerably higher current.

CONSTRUCTION

Clip the two S-DeCs together to form one long DeC. A panel may be fitted to DeC 1 to take the reset switch and the lampholder. The microphone can be connected by way of screened cable, the braiding of which connects to the negative rail of the circuit at point 21 of DeC 1. If the microphone is already fitted with a screened cable terminated in a jack plug, the best method of coupling to DeC 1 is to use a matching jack socket with two short lengths of wire soldered to its connection tags and inserted into points 21 and 30 of the DeC. The microphone plug is then fitted into this socket. This approach is preferable to dismantling the jack plug or soldering wires to it. If a new microphone cable is made up, however, remember to solder its ends to short lengths of single strand wire, which will plug much more easily into the S-DeC. Stranded wire should never be inserted into the S-DeC as the strands have a nasty habit of separating and catching in the internal springs.

Connect up the switch and the lamp, using single strand wires, then plug in the eight wire links which bridge the DeCs and the sections of each DeC. At this stage, insert R5, R6, D1 and D2, because these components also bridge the two DeCs. Make certain that the diodes are inserted right way round. The fact that both diode cathodes are on DeC 1 is a good aid for quick checking. The cathode end of the component will be identified by a band, usually white, around the diode body.

Next plug in the capacitors. C1 and C2 are electrolytic, so these must also be connected right way round. The capacitors are followed by the transistors, which are the same n.p.n. silicon types used in all the "Double Deccer" circuits. Check that the transistor lead-outs are fitted correctly; the transistor plug-in points have been chosen so that the full length of lead-out is unnecessary in most positions. Finally fit the resistors.

An electret capacitor microphone was employed with the prototype, and a crystal microphone will give similar results. A dynamic, or moving-coil, microphone with an output impedance of around 50k Ω (as employed with many cassette recorders) could also be employed, but in this case it is important to ensure that C1 is a modern component in good condition, since leakage current here could upset the bias conditions for TR1 and TR2. In practice, any difficulties here can be completely avoided by changing C1 for a 1 μ F polyester capacitor if a dynamic microphone is to be employed.

When all has been completed it only remains to insert two leads for connection to the battery, and the sound-operated switch is ready to go at the clap of a hand. ■



By E. A. Parr

● ● ●

Concluding article describing this exciting electronic rifle game

● ● ●

GUN CIRCUIT

The internal connections in the gun are shown in Fig. 3.

IC22 is the 15V LAS photo-electric cell. The image of the target light is focused onto the p.e.c. by a lens. The mechanics of setting up the optics will be described later. The sensitivity of the p.e.c. can be adjusted by VR1, but in practice this potentiometer has never had to be moved from its centre setting. The output of the p.e.c. is monitored by LED2 to simplify aligning the optics. This l.e.d. should not, of course, be visible to the budding marksman!

The trigger switch is a simple limit microswitch. LED1 gives the gun fire flashes. In the prototype it was mounted in the breech mechanism. The gun speaker was an ex-transistor radio 75Ω speaker. It was mounted in the gun butt to be just by the marksman's ear.

GUN CONSTRUCTION

The following is a description of how the prototype gun was made. It is intended as a guide, not a rigid set of instructions.

The machine gun was based on a child's toy. The original toy as purchased was made of two plastic pressings joined down the centre line of the gun. These were easily separated with a sharp knife. A small convex (magnifying) lens was obtained from a Christmas cracker (other sources would do, of course!). A bit of experimentation focusing a distant light onto a piece of paper gave the focal length, about 100mm.

The lens was now glued onto one half of the barrel with Araldite (having first checked that the two halves of the gun would fit round the lens). The lens was positioned as near the centre line of the

gun as possible, although this is not critical. Next, a proper foresight and backsight were made from the aluminium and attached to the gun. Exact positioning is not important, as the p.e.c. was positioned later to take account of errors.

Now comes the tricky bit. A single light was set up and the half of the gun with the lens in set up in vice at the distance from the light at which the gun would be used (about 3 metres with the prototype). The gun was aimed at the light using the sights. A

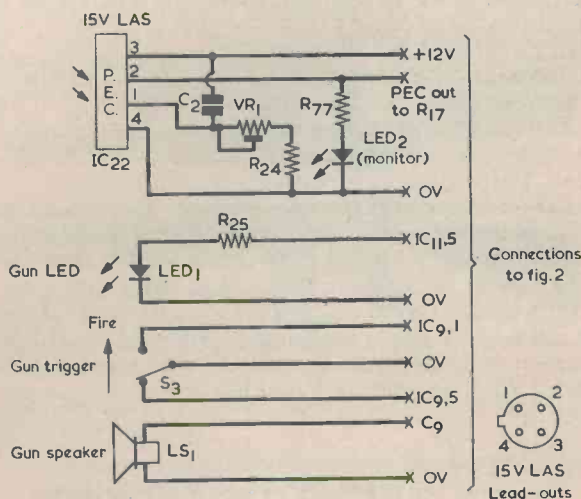


Fig. 3. The internal circuitry in the gun



The gun employed in the rifle game. It connects to the control logic by way of a 12-core cable

piece of paper was then put in the barrel with adhesive tape at the focal distance from the lens, and "spotted" where the light image fell.

The p.e.c. was set up on a small piece of Veroboard with flying leads for connection to R24, C2, etc. The Veroboard was then embedded in Araldite and manoeuvred so that the active area of the p.e.c. lay behind the spot. It is advisable to leave the leads of the p.e.c. long to allow it to be moved by a few millimetres for fine tuning.

When the Araldite had set, R24, VR1, C2, R77 and LED2 were mounted in the gun and connected to the p.e.c. The gun was again set up in the vice and aimed at the fixed light. The supply to the p.e.c. was turned on and the p.e.c. moved on its leads until LED2 came on, checking the aim all the time in case the gun had been moved. Care is essential here if shouts of "cheat" by peeved marksmen are to be avoided later.

By comparison, the mounting of the gun flash i.e.d., LED1, the trigger limit switch and the loudspeaker was simplicity. In mounting the limit switch it is better to have the trigger held back onto the switch by a spring, and the trigger pulling the striker off the switch rather than the trigger pushing a striker onto the limit switch. This prevents an over-strong trigger finger breaking the limit switch mounting, as happened in the development of the prototype.

The gun is connected to the control circuit by a 12 core cable. In the prototype this was about 1.2



The gun can be divided into two halves. The electronics and lens system is fitted into the half which will normally be held against the right hand side of the marksman's face

metres long. Note that the OV lines are separated out to prevent noise problems. The cable should be firmly anchored where it enters the gun, for obvious reasons.

When all is correct, the two halves of the gun can be fastened together again. To allow repairs and re-alignment of the optics, the prototype was simply bound with black tape, which was surprisingly effective and neat.

OTHER NOTES

The control circuit was wired up on an RS Components stripboard No. 433-911. No layout is given as the wiring is simply point-to-point. Layout is not critical, although the OV return from TR1 to TR16 was separated from the logic OV. To aid transportation the gun and target cables connect into the control box by way of plugs and sockets.

The power supply uses two transformers. An 8 volt transformer gives the 12 volt supply for the lamps and a 5 volt supply for the logic. A second 6 volt transformer provides the supply for the seven-segment displays. This separate supply was used to reduce the current through the 5 volt regulator. The circuit for the power supply is shown in Fig. 4.



The miniature speaker is fitted in the butt of the gun. The gun flash i.e.d. LED1, is mounted on the top of the gun housing, slightly forward of the butt, so that it can be seen by the marksman. The 12-core lead has an anchorage at the "magazine", and in the area above this is fitted the electronics, apart from the trigger switch and the photo-electric cell

Construction of the target was simple. Ten batten lampholders were fastened to a piece of chipboard, and connected back to the control box by 4 metres of 12 core cable (ten signal, one 12 volts and one spare).

VARIATIONS ON A THEME

In the development of the prototype a few ideas were tried out and rejected. They may be of interest to readers who might like to develop them further.

The first idea was based on a pistol, with IC10(a) and edge-triggered 100mS monostable fired off the bounce removing flip-flop IC9(a)(b). It was found that this was a more skilful game, but people preferred to loose off with a machine

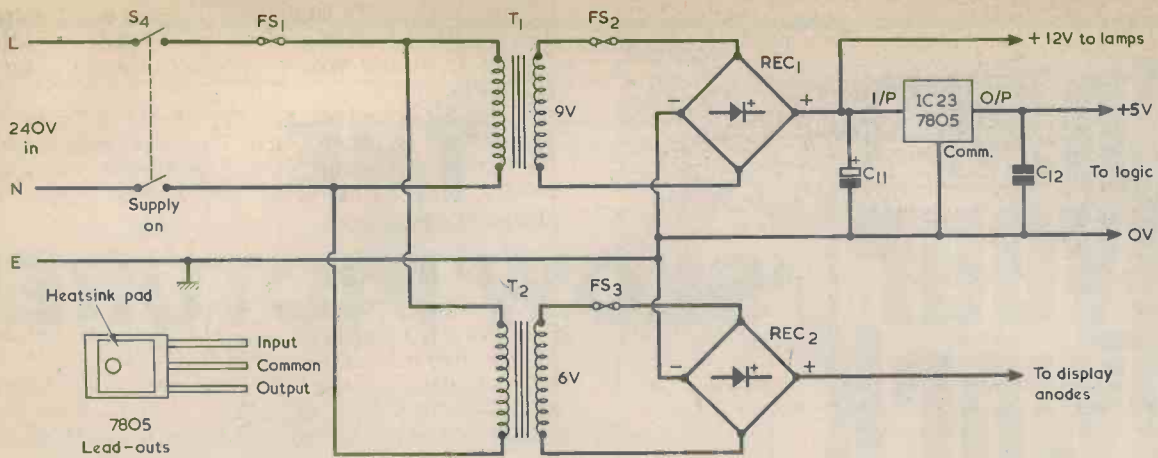


Fig. 4. The power supply. This provides separate outputs for the logic, the lamps and the display anodes

gun. Presumably they are working off their frustrations; there's a PhD thesis subject there for a psychologist!

The second idea was to give the gun a kick. A slot car motor had a lead weight fastened off centre onto the shaft, and the motor mounted at an angle into the gun. A relay was driven off IC9(b), causing the motor to run whenever the trigger was pulled. The effect was startling; the gun kicked worse than the notorious Thompson gun (which was reputed to be more dangerous to your friends than to your enemy). The gun proved impossible to aim and the motorised kick was shelved, although it probably could be made to work with a tamer motor.

Finally, the design proved to have a feature not designed in. With a good marksman it proved possible to "single shot" the gun by lifting off the trigger when a hit was recorded. The record score to date, in fact, is 85 bullets for 80 hits. The game was designed to take 2 minutes at most. With a needle match and a marksman firing single shots the game can take up to ten minutes. This is good fun, but bad for funds in a side show as it slows the income down. It would be easy to overcome the problem, and an obvious method would be a time-out of, say, two minutes. A second method would be a triggerable monostable added to keep the bullets coming for 1 second after the trigger was released.



The convex lens is positioned along the barrel slightly behind the foresight. The photoelectric cell is one focal length behind it and, in the prototype, was just behind the forward grip

This would force the marksman to hurry on and not single shoot. Finally, the bullets counter could be easily changed to a seconds timer, and the result based on hits/time rather than hits/bullets. ■

Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who fail to supply goods or refund money and who have become the subject of liquidation or bankruptcy proceedings. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

In your Work -Shop



THE 'SLOW PICTURE'

The TV with a fault in time

Smithy placed the 12 inch black and white television receiver on his bench and examined it briefly. He recognised it as one of the earlier fully solid-state sets capable of running from the mains or from a 12 volt accumulator. A small label was tied to the carrying handle at the top of its cabinet and, without much expectation, Smithy bent down to look at it. It was rarely that customer descriptions of fault symptoms, even when they were forthcoming, proved to be of any great assistance. This particular fault description was almost frightening in its incomprehensibility.

The label stated: "SLOW PICTURE".

A sudden eldritch vision of a television scene sluggishly trying to keep pace with the transmitter rose in his mind, and he shivered involuntarily. He shook his head irritably and turned to practical matters. After connecting the receiver to the mains, he plugged in an aerial and switched it on. The sound from one of the local channels became audible from the receiver speaker. After a short period the picture appeared, and Smithy examined it carefully. It had excellent brightness and contrast, was locked as firmly as the Rock of Gibraltar to the transmitter sync pulses, and gave no evidence of any serious non-linearity in either the vertical or the horizontal direction. Smithy checked for any conceivable attribute which could merit the adjective "slow", but had to admit himself baffled.

He scratched his sparse locks, then checked reception on the other local channels. Vision and sound continued to be perfect, with no obvious shortcomings in performance whatsoever.

ENTER DICK

"What's up, Smithy?" called out Dick from his bench at the other side of the Workshop. "Got a problem?"

"I certainly have," replied Smithy. "If what the label on this set says is true, it's got the weirdest snag I've ever heard of."

"D'you mean the label which says 'slow picture'?"

"You've seen it, too?"

Dick grinned.

"I always look at any label there is on a set before I take it off the rack for servicing. When I read *that* label I decided I'd leave that set for you!"

"Well, thank you very much," replied Smithy caustically. "But what the dickens does 'slow picture' mean? I've tried the set out and it's working perfectly."

"There's nothing in it that's slowing the action, is there? Like people in the picture moving more slowly than they should?"

"Of course there isn't," retorted Smithy shortly. "I suppose the best thing I can do is to leave the set running for a bit and see if anything happens."

On a sudden impulse, Dick rose from his stool and walked over to the filing cabinet. After a little searching, he pulled out a service

manual and took it over to the Serviceman's bench.

"These mains-battery sets fascinate me rather," he said. "In the old days a TV set ran off the mains and that was all there was to it."

"The 12 volt battery idea was a logical outcome of receiver development," remarked Smithy. "Or at least it was, so far as simple small monochrome TV's like this one were concerned. When the set-makers started manufacturing receivers with semiconductors in all the stages it became obvious that a complete set could run with a common supply rail of around 11 volts positive. The few high supply voltages which are needed for the picture tube circuits could then be taken from the line output transformer. Hey, is that the service manual for this mysterious set I've got here?"

Dick nodded in agreement, whereupon Smithy took the manual from him and opened it at the circuit diagram. He stabbed his finger at the power supply section of the circuit. (Fig. 1).

"There you are," he remarked. "Now, to continue my argument, here's a set in which all the stages work basically from a stabilized supply rail of around 11 volts. After a suitable mains supply has been provided, only a little extra circuitry is needed to make the set capable of working from a battery as well. It can, for instance, run from a 12 volt car battery."

'Blimey,' protested Dick, "that's

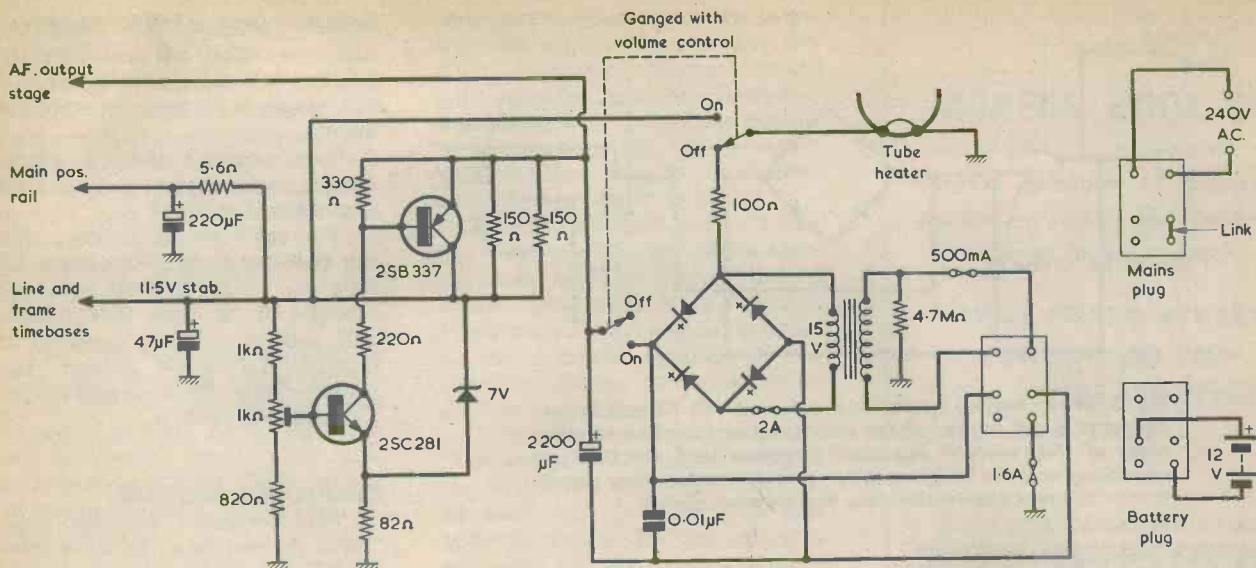


Fig. 1. A mains-battery power supply for a monochrome television receiver. Mains or battery operation is selected by inserting the appropriate plug. This is a slightly simplified version of the power supply section of the I.T.T. "Featherlight 12"

asking rather a lot, isn't it? Car battery voltages vary all over the place according to the state of charge they have."

"That's true," agreed Smithy. "In fact, you can expect a nominal 12 volt car battery in good condition to offer anything between say, 12 and 17 volts or so. But all that means is that there has to be a voltage stabilizing circuit in the power supply of the receiver which can handle these changes in voltage. Since a voltage stabilizing circuit is very desirable just for ordinary mains running, there's no serious extra expense incurred in using the same stabilizing circuit for battery operation."

MAINS-BATTERY SELECTION

"How do you select mains or battery supply?"

"Different manufacturers have different ideas here," said Smithy. "With this present set, the selection is done by having the power input plug wired up differently for mains and battery operation. Let's look at mains operation first. As you can see, the a.c. mains input goes to the top two pins of the 6-way power plug." (Fig. 2.)

"There's a shorting link," put in Dick quickly, "between the middle and bottom right hand pins of that plug."

"There is, indeed. Now the top two pins of the plug go to the mains transformer primary via a fuse. Although the set has got a mains

isolating transformer, a 4.7M Ω resistor couples one side of the mains to chassis. This is to prevent the chassis from assuming an excessively high static voltage, which it could do if it were completely floating. The 15 volt secondary of the transformer connects by way of another fuse to a standard bridge rectifier. An unusual aspect of the design is that one section of the receiver on-off switch appears *after* the rectifier. When the switch section closes, it connects the positive side of the rectifier output to the 2,200 μ F reservoir electrolytic. The negative electrolytic terminal connects to the negative output of the bridge rectifier, and these two circuit points then go to chassis through the link in the power input plug and another fuse. Got it?"

"Yes, it's all quite easy if you take the circuit one step at a time. Where does the positive voltage on the reservoir capacitor go?"

"To the voltage stabilizer."

"Right. Let's do battery operation next."

"Fair enough," said Smithy, pointing to the battery plug in the diagram (Fig. 3).

He paused to collect his thoughts.

"Well now," he continued, "the 12 volt battery connects to two different points in the power plug, and this time there are no links between any of the pins. So, when the battery plug is fitted there is, first, no mains going to the transformer primary and, second, no connection to chassis for the negative bridge rectifier output

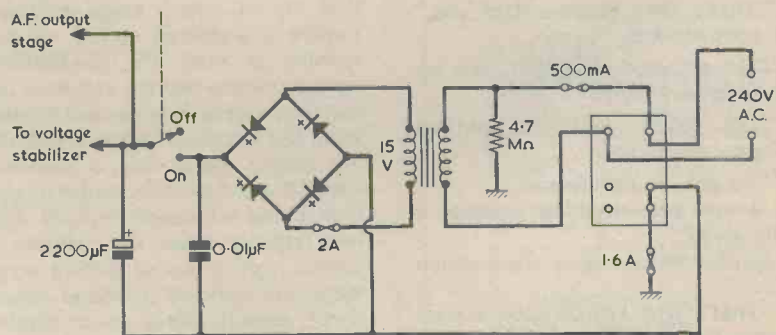


Fig. 2. Power supply circuit conditions for mains operation

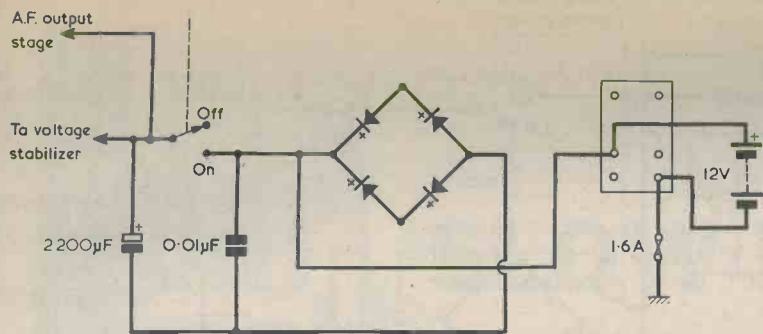


Fig. 3. When battery operation is selected, the 12 volt battery connects direct to the voltage stabilizing section. The negative sides of the reservoir capacitor (together with the 0.01 μ F capacitor) and the bridge rectifier do not now have any significant connection into the receiver circuit

point or the negative side of the 2,200 μ F electrolytic. You don't need the reservoir capacitor when the power is obtained from a low impedance source such as a car battery, and there's no point in having the bridge rectifier fully in circuit. What happens now is that the negative battery input goes to chassis through the same fuse which was in the rectifier output circuit, whilst the positive battery input goes to the same on-off switch section as did the positive output of the bridge rectifier."

"And from there it goes to the voltage stabilizer?"

"It goes to the voltage stabilizer."

"Just a minute," remarked Dick suddenly. "Didn't you say that all the stages in the receiver work basically from the stabilized voltage rail?"

"I did."

"Well in this circuit, one doesn't," returned Dick triumphantly. "The audio output stage runs from the unstabilized positive supply both with mains and battery operation."

Smithy looked down at the circuit, then turned to his assistant.

"That's very observant of you," he commended.

Dick polished his finger nails on an imaginary lapel.

"I'm pretty good at spotting things, you know."

"As you so rightly say..."

"I can see anything unusual a mile away."

"Well, this supply connection to..."

"That's why I'm so good at servicing. I've got this talent for..."

"Will you flaming well belt up?" roared Smithy. "Darn it all, I've only got to give you a bit of praise and

you spend the rest of the day playing it up. Come to think of it, why on earth *am* I giving you all this gen when I'm supposed to be working?"

"Well, you aren't doing any work while you're waiting for something to happen with this 'slow picture' TV."

Smithy looked down at the television receiver, which continued to reproduce an excellent picture. He reached over to its volume control and turned its knob anti-clockwise whereupon, with a click, the receiver became switched off. The sound ceased and the picture collapsed.

"I'll turn it on again after a while," he remarked. "Perhaps the fault will come on if the set is switched on and off a few times in a short period."

"Why," asked Dick, "does the a.f. output stage take its supply from the unstabilized positive voltage?"

Smithy sighed. When Dick was in search of information any hopes of peace were impossible until his curiosity was fully satisfied.

"There are two reasons for this," replied Smithy. "A minor reason is that the a.f. output stage does not require a stabilized supply so that running it from the unstabilized voltage means that the stabilizer circuit has a little less current to deal with. But the main reason is that the a.f. output stage has a standard Class B configuration which draws high peaks of supply current with loud signals when the volume is turned high. If the a.f. output stage were run from the stabilized supply these current peaks could slightly modulate the stabilized supply voltage, giving picture judder and things like that. One answer to this problem would be to have an ex-

tremely efficient and fast-acting stabilizer circuit, but a much easier solution is to simply run the a.f. output stage from the non-stabilized supply."

"But wouldn't the a.f. output current peaks tend to modulate the unstabilized voltage?"

"Oh yes," agreed Smithy. "But the stabilizer circuit deals more efficiently with sudden voltage changes at its input than it does with sudden current changes at its output. To some extent, the stabilizer pass transistor acts also as a decoupling resistor."

STABILIZER SECTION

"Pass transistor," repeated Dick. "What do you mean by pass transistor?"

"A voltage stabilizer circuit incorporating one or more transistors normally has one transistor which passes all the supply current," explained Smithy. "That's the pass transistor. If you look at the stabilizer section of this power supply, you'll see that there is a p.n.p. transistor which functions as the pass transistor." (Fig. 4.)

Dick looked at the part of the circuit at which Smithy was pointing, and groaned.

"Blow me," he complained, "the transistors here are those fiendish '2SB' and '2SC' types."

"They're no problem," retorted Smithy, reaching up to the shelf over his bench for a book. "What do you think we've got *Tower's* in here for?"

Smithy handed the Workshop copy of *Tower's International Transistor Selector* to his assistant, who proceeded to turn the pages quickly.

"Here we are," he said, running his finger down the columns in the *Selector*. "Now, the 2SB337 is a germanium p.n.p. power transistor in a TO3 case, and it's got a maximum collector current rating of 7 amps. Let's have a look next for the 2SC281."

He turned a few more pages.

"And the 2SC281," he went on, "is an n.p.n. silicon transistor in a TO1 case. This is quite a small job, with a maximum collector current of 100mA. Well, that's got the transistors sorted out. Let's now have a look at that stabilizing circuit."

He concentrated on the circuit and then started to frown in puzzlement.

"What's up?" asked Smithy.

"There's something queer here," stated Dick. "For a start, the base of the small n.p.n. transistor goes to a potential divider across the stabiliz-

ed supply. Right?"
"Right."

"Which means that if, for any reason, the stabilized supply rail goes negative, so also does the base of the transistor. This in turn will mean that it passes less collector current, with the result that less base current is available for the base of the p.n.p. pass transistor. But that's crazy!"

"Why?"

"Because that pass transistor is supposed to pass *more* current when the stabilized voltage goes negative, to bring the voltage back to its proper level. With this arrangement the stabilized voltage is actually *encouraged* to go negative!"

"You haven't got the full picture," admonished Smithy. "You're forgetting the 7 volt zener diode between the stabilized supply rail and the emitter of the n.p.n. transistor. Now, there's a good fat current flowing through that zener diode and the 82Ω resistor going down to chassis below it. Judging from the resistor value and the voltages concerned, the current in the 82Ω resistor will be around 50mA, part of which will flow through the zener diode and part of which will flow through the n.p.n. transistor. For the sake of argument, let's say that the pre-set pot is adjusted so that half the stabilized voltage appears at the base of the p.n.p. transistor. Let's also say that, for some reason, the stabilized voltage goes negative by a small voltage. Half that negative excursion will be applied to the base of the n.p.n. transistor, whilst the *whole* of the excursion will be applied to its emitter because of the

zener diode. Since its emitter is going more negative than its base, the n.p.n. transistor collector current will increase, and not decrease, thereby increasing the base current of the pass transistor. The pass transistor will then bring up the stabilized voltage to its correct level."

"Gosh," breathed Dick, "I can see it all now. The base of the n.p.n. transistor goes negative, but the emitter goes even more negative. You'll get a similar stabilizing effect in the opposite direction if the stabilized voltage attempted to go positive, won't you?"

"You will," confirmed Smithy. "The emitter of the n.p.n. transistor would be taken more positive than its base and it would pass less collector current. The pre-set pot is adjusted so that the stabilized voltage is just at the right level. Incidentally, you should never adjust the pre-set potentiometer in any TV stabilized supply without following the instructions in its service manual *exactly*. With some sets, too high a stabilized supply voltage can result in disproportionately increased voltages in the line output stage, and these could increase the possibility of component breakdown in the long term."

He consulted the service manual.

"I see that, with this set," he continued, "the pot should be set up for 11.5 volts at the collector of the pass transistor. This 11.5 volts goes direct to the line and frame timebases, and via a 5.6Ω decoupling resistor to all the remaining receiver stages."

"Except the a.f. output stage."

"Except," repeated a mildly exasperated Smithy, "the a.f. output stage."

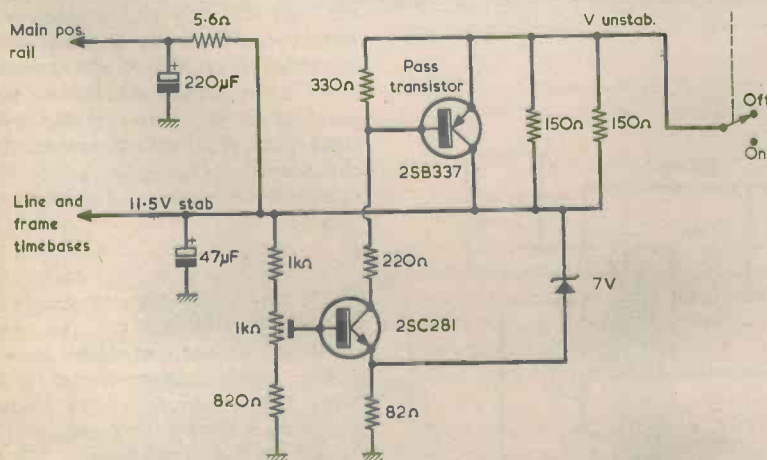


Fig. 4. The voltage stabilizing section of the power supply. The 1kΩ pre-set potentiometer is adjusted for a voltage of 11.5 volts at the collector of the pass transistor under operating conditions specified in the receiver service manual

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country

19-21 PRAED STREET
LONDON W2 1NP
Tel: 01-723 4185/2926

ELECTRONIC CONSTRUCTORS

SAVE MONEY!

With our BARGAIN PARCEL . . .

Contains:
10 x BC107, 10 x BC108, 10 x BC109, 3 x BFY51, 3 x 2N3819, 3 x 2N2926 and 10 Mixed Values - ELECTROLYTICS; 10 Mixed Values - CERAMIC CAPS; 20 Mixed Values - FIXED CAPS; 10 DIODES GERMANIUM - Sim. OA91; 10 DIODES SILICON - Sim. IN914; 2 x 741 IC's, 1 2grm PHIAL CYNOACRYLATE ADHESIVE, VAT inc. in price (all items are brand new).

Plus a Free Gift worth 75p
Send £5 plus 50p p&p
(Cheque, Postal Order, Money Order) to

SIGTRONIC ELECTRONICS
27 Malvern Street, Stapenhill
Burton-on-Trent, Staffs. DE15 9DY
Tel: (0283) 46868 special orders

PEATS for PARTS ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs
Transfers

Also a postal service

PEATS
the world of electronics
25 Parnell Street, Dublin 1. Telephone 749972

MORSE IMPROVEMENT

C90 Cassettes (A) 1-12 w.p.m. with simple exercises. Suitable for R.A.E. preparation. (B) 12-24 w.p.m. computer produced professional level operator material including International symbols.

Price each: complete with instruction and exercise booklets £4.50 including postage. Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price £4.50 including postage.
Overseas Airmail £1 extra.

MHEL ELECTRONICS (Dept. R)
12 Longshore Way, Milton;
Portsmouth (UK), PO4 8LS

MYSTERY UNCOVERED

He reached out and turned the volume control knob on the television receiver in order to switch it on. Once more the sound channel was heard from the speaker. After a period the irritatingly faultless picture appeared on the screen. Smithy watched it abstractedly and then glanced down at the service manual circuit. Suddenly his eyes narrowed as he surveyed the power supply section more closely.

"Eureka!"

"Hey?"

"Eureka!"

"Blimey," complained Dick, "what's got into you? And why on earth are you raving on about resistance wire?"

"I've just realised what this 'slow picture' business is all about," replied Smithy. "Seeing that you've wished yourself onto me for the moment you might as well make yourself useful. Get the back off that set, dig out the power supply section and locate the 100Ω resistor which connects between the bridge rectifier and the second part of the receiver on-off switch. This is the one."

Smithy pointed to the resistor in question. (Fig.5.)

Puzzled, Dick unplugged the receiver from the mains, removed the aerial and took off the cabinet back. After some minutes' work he was able to locate the 100Ω resistor.

"Right," said Smithy briskly, "put the set switch to the 'on' position, so as to break any external circuit to that resistor. Then measure its value."

Dick took up Smithy's testmeter and proceeded to carry out his in-

structions. The needle of the testmeter, switched to an ohms range, was hardly deflected from its left-hand end stop as Dick applied the test prods to the resistor.

"Stap me, Smithy," he said admiringly. "That was an inspired guess. This resistor's completely open-circuit."

"Good," grinned Smithy. "I was lucky; it could have been a bad contact in the on-off switch or a wire come adrift or something fiddling like that. Anyway, put in a new 100Ω resistor and then we'll see how this set performs."

After a trip to the spares cupboard Dick soon had a new 100Ω resistor soldered into circuit. He returned the power supply section to its correct place on the receiver chassis, put the receiver switch to the "off" position and looked expectantly at the Serviceman.

"Plug that set back into the mains again," said Smithy, "pop in an aerial and switch it on."

Obediently, Dick did as he was told. Once again, there was an immediate appearance of the sound at switching on with, after a delay, the production of a picture. Smithy beamed at the set cheerfully.

"I don't see what you're looking so pleased about," commented Dick. "The set's working just the same as it did before."

But Smithy's obvious mood of euphoria could not be shaken. He gazed happily at the picture on the TV screen for another minute or so then leaned over and turned the set off at the volume control switch.

"What the heck," asked Dick, "happens now?"

"Nothing," replied Smithy airily. "We just sit and wait for a few minutes."

Smithy looked at his watch and, despite Dick's growing impatience, sat impassively on his stool. Much to Dick's irritation, he refused to answer any further queries but merely kept glancing at his watch.

"Now," he remarked suddenly, "that set has been turned off for all of five minutes. Let's find out what it does when I switch it on again."

He once more operated the volume control switch and, yet again, the local sound channel was heard from the speaker.

But, this time, it was accompanied by the virtually immediate appearance of the picture on the screen.

"I'm beginning," said Dick thoughtfully, "to see what you're driving at now."

"We've cured the 'slow picture' fault," chortled Smithy. "This set is wired up so that, when it operates from the mains, the picture appears almost immediately at switch-on. When the set is turned on by means of its own on-off switch the picture tube heater is powered by the stabilized 11.5 volt supply. Putting the receiver switch to the 'off' position connects the tube heater via that 100Ω resistor you changed to the bridge rectifier, whereupon the heater continues to run at reduced power, ready to give a picture again when the set is next switched on. Now, the set-owner had got used to the picture coming on straightaway at switch-on so that when, after that 100Ω resistor had gone open-circuit, the picture took some time to appear he considered that he had a 'slow picture'. A very good customer diagnosis, that!"

"Come off it, Smithy," snorted Dick, "it had you baffled all along."

"Well, it did for a bit," confessed Smithy. "Anyway, to round things off, let's just see what power does actually get to the tube heater in the switched off condition. The only rectifier in the bridge which can then conduct is the one in the lower right-hand arm, with the result that the heater is being supplied with rectified alternate half-cycles." (Fig.6.)

CLOSING LINES

"This has certainly been an unusual fault," commented Dick. "Hey, just a minute; I think I could make up a little rhyme about it!"

"Oh no," groaned Smithy. "Don't say you're back at your old game of dreaming up limericks."

But Dick was not to be forestalled, and he held up a finger for silence.

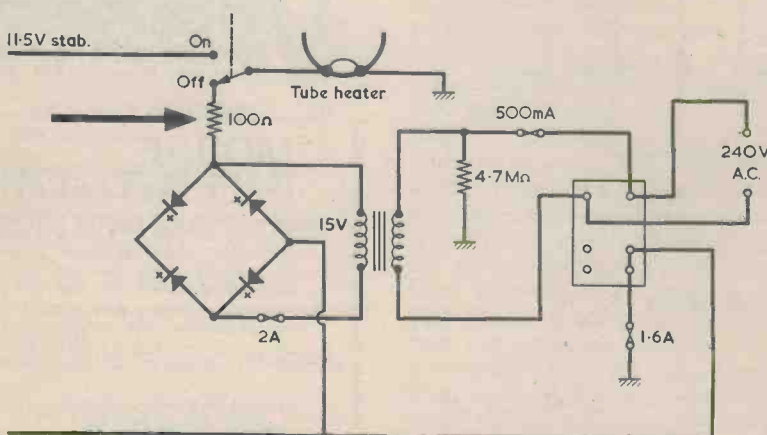


Fig. 5. Tube heater switching circuit. The arrow points at the 100Ω resistor which Smithy asked Dick to check

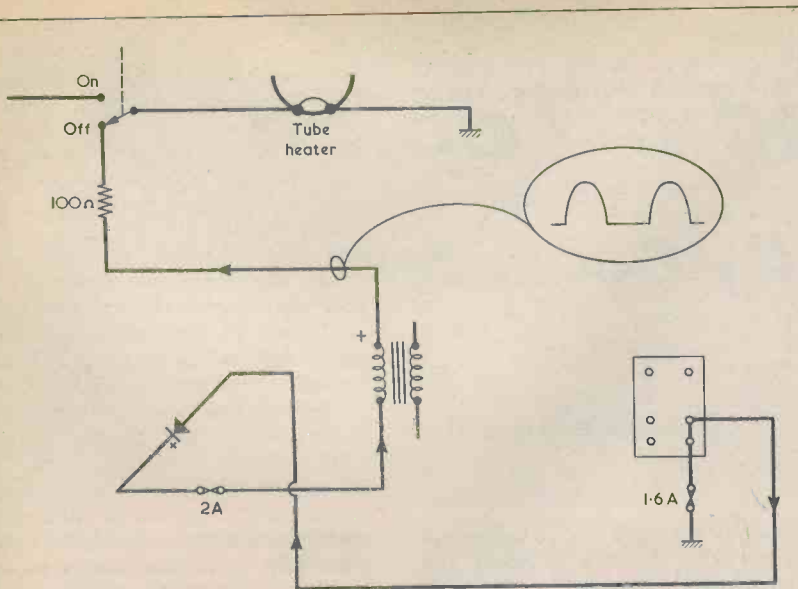


Fig. 6. When the receiver is switched off, alternate half-cycles from the transformer secondary pass through the tube heater, following the circuit path shown here. The current (assumed to flow from positive to negative) appears when the upper end of the secondary is positive

*"A slow picture is no real disaster.
And it's easy to make it come
faster.
Don't change a transistor
But just a resistor,
And you'll get an immediate
raster!"*

UNDERSTANDING TELEVISION



by

J. R. DAVIES

Over 500 pages
300 diagrams

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Introduction to Colour TV

£3.95 P. & P. 70p

To: DATA PUBLICATIONS Ltd., 57 Maida Vale London W9

Please supply copy(ies) of "Understanding Television" Data Book No. 17. I enclose cheque/crossed postal order for

Name

Address

BLOCK LETTERS PLEASE



"No, No, I said get me some crocodile clips — not crocodile and chips"

Radio Topics

By Recorder



Resistance in ohms is equal to voltage divided by current in amps. So runs the Law of the good Georg Simon Ohm, who lived over the years 1787 to 1854. One hundred and twenty-five years later we can still put Ohm's Law to good use in the constructional design work that we carry out.

To start off with, let's indulge in a little algebraic re-shuffling so that we can express the Law in its other two forms: voltage is current multiplied by resistance and, perhaps the most useful form of all, current is voltage divided by resistance.

EASIER UNITS

Since we don't frequently bump into amps in much of the electronics we deal with, it is usually easier for us to think of Ohm's Law in terms of milliamps, whereupon we can say that current, in milliamps, is equal to voltage divided by resistance in kilohms. If we find that 1 volt is dropped across a $1k\Omega$ resistor, then the current flowing through that resistor is 1mA. Should there be 2 volts across the $1k\Omega$ resistor, then the current is 2mA. Similarly, 1 volt across a 200Ω resistor denotes a current of 5mA in the resistor, and so on.

When we want to find the current flowing in a resistor it is normally much simpler to check the voltage across it than it is to measure the actual current itself. This is because we can easily obtain a voltage reading by applying our testmeter prods across the resistor. To measure current we would in most instances have to break the circuit in which the current flows and insert the current-reading meter in series. Determining current by measuring voltage is particularly of advantage in checking circuits such as transistor amplifier stages. These often have series emitter or

collector resistors whose values are of the order of 500Ω to $20k\Omega$. The mathematics involved in determining the current in these resistors from the voltages dropped across them is, in consequence, not too difficult at all.

OUTPUT POWER

Power, in watts, is equal to voltage multiplied by current in amps. Since, from Ohm's Law, current is voltage divided by resistance we can reach the conclusion that the power dissipated in a resistor is equal to voltage squared divided by the resistance. One useful application for this equation is in determining, roughly, the maximum r.m.s. output power which can be obtained from an audio amplifier in the mid-fi category. Nearly all a.f. amplifiers these days have an output voltage which, under no-signal conditions, sits at approximately half the supply voltage. When handling a signal the output voltage can then swing very nearly to the positive rail on positive audio half-cycle peaks and very nearly to the negative rail on the negative half-cycle peaks. The output of the amplifier normally couples to the speaker via a high value electrolytic capacitor.

To take a nice easy example of how to assess amplifier power, let's imagine that the amplifier supply voltage is 20 volts. The amplifier output can then swing up to 10 volts positive and negative and, as a result, has a peak value of 10 volts. This corresponds to an r.m.s. voltage of 0.7 times 10, or 7 volts. And when we square that r.m.s. value of 7 volts we get a figure of 49.

If we couple the amplifier to a speaker having an impedance of 50Ω (which we will treat as a

resistance of that value) then the maximum r.m.s. audio power we will get from the amplifier and speaker combination is 49 divided by 50 (voltage squared divided by resistance). This is just under 1 watt. With a 15Ω speaker the audio power is 49 divided by 15, or, near as dammit, 3.3 watts. An 8Ω speaker will give 49 divided by 8, which is 6.1 watts. And a 5Ω speaker produces a maximum r.m.s. output power of 49 divided by 5, or nearly 10 watts.

All these figures are very approximate because, in practice, the amplifier output swing won't be right up to the supply rails and the impedance offered by the speaker is pretty nominal anyway. But they give us a good guideline as to what can be expected from a particular amplifier and speaker. To be practical, it would be prudent to assume that the actual maximum r.m.s. output power is, say, some 70% to 80% of the calculated figure.

With a given amplifier, as speaker impedance goes down output power goes up. So also, unfortunately, does the amplifier output current. There will be a limit to the output current which the amplifier can produce, this being expressed normally in terms of the minimum speaker impedance which may be connected to its output. Connecting a speaker of lower impedance could then cause damage to the amplifier if it does not have automatic overload protection.

COMPONENT ANALYSER

For many years H. W. Sullivan Limited have been well known in the precision measurement field as manufacturers of bridges, potentiometers, detectors and measurement standards. The company now announces a completely new automatic instrument, the AC5555 Automatic Component Analyser,

designed and manufactured at their premises at Archcliffe Road, Dover, Kent, CT17 9EN. This instrument is suitable for production and goods inwards inspection as well as for laboratory applications. What is more, it has some almost spectacular capabilities, as the following description shows.

The Sullivan AC5555 accepts a wide range of components, whether they be resistors, capacitors or inductors. It automatically selects the range *and function*, and displays the value and unit on two digital displays. When the instrument is switched on, it is in the fully automatic mode and no setting-up procedure is required. This is the normal mode of operation and to test a component it is only necessary to connect it to the instrument, whereupon the value is displayed irrespective of the component type. The method of operation is thus so simple that it is virtually impossible to make mistakes. The auto-function facility makes the instrument particularly useful for the identification of unknown components in laboratory or production areas.

With some applications, such as the testing of a batch of components which have nominally the same value, the operator can if required lock the instrument into a particular range. This manual mode of operation gives a shorter display response time than is given with the automatic mode.

The mains operated fourteen-range AC5555 measures the parallel capacitance and conductance or the series inductance and resistance of the test component at a frequency of 1kHz. The maximum reading on each display is 19999, and the instrument measures capacitance up to 200 μ F with an ultimate resolution of 0.01pF, while inductance may be measured up to 200 henrys with a resolution of 10 nanohenrys. Resistors can be measured either as resistance up to 2M Ω or as conductance. With the resistance and conductance ranges, resistance values of 100 millionths of an ohms to 10,000M Ω may be discriminated.

Five terminals are provided on the front panel for connection to the component under test. With such a sophisticated piece of measurement equipment, a simple robust connection system is essential. H. W. Sullivan have designed a special Test Jig, the AC5556, and a lead set, both available as optional extras for use with the AC5555. The Test Jig is extremely easy to use and accepts discrete components with axial or radial leads and having a body length up to 95mm. For other applications, such as the testing of transformers or printed circuit boards, the screened test lead is used.

The AC5555 is suitable for rack mounting and has dimensions of 430 by 195 by 275mm, and you can obtain an idea of its appearance from the accompanying photograph.

BREAKDOWN TESTER

The second photograph illustrates another comprehensive item of test equipment, this originating from Avo Limited, also of Archcliffe Road, Dover, Kent. This new instrument is a Leakage and Breakdown Tester and has the type number RM215-F/3. It performs a particularly important role in factory applications, especially now that the Health and Safety at Work Act lays down rigid requirements for the safety of electrical installations.

The RM215-F/3 is portable and compact, and can be used for general flash testing work as well as the measurement of breakdown voltage. It will also detect leakage current in the testing of electrical components and systems.

The instrument operates from a standard supply voltage of 120 or 240 volts at 50Hz and will provide a continuously variable a.c. test voltage between the limits of 50 volts and 4 kilovolts. It is sensitive to current passed by a component under test and can be adjusted to operate in either leakage or breakdown operational mode.

A failure interlock ensures that when a component fails under test the test voltage is automatically switched off. The design of the instrument ensures that the output current is limited to a safe value, even with the test leads short-circuited together. The tester has a low internal resistance, a very important requirement when testing

Apply any component to the H. W. Sullivan AC5555 Analyser and it will automatically determine whether it is a resistor, a capacitor or an inductor, and then display its value! It is shown here in use with the AC5556 Test Jig



New Leakage and Breakdown Tester, introduced by Avo Limited. This provides an alternating test voltage which is continuously variable from 50 volts to 4 kilovolts



components possessing high capacitance.

The instrument is housed in a durable plastic case with a detachable lid containing a compartment into which the test leads and the power supply cable can be stored when these are not in use. It is available through Avo distributors in the U.K. and in other countries throughout the world.

RADIO CONTROL

Radio controlled model aircraft buffs have much to occupy themselves at present with the extremely sophisticated transmitting and receiving equipment which is currently available to them. I am

sure that their mouths will water, nevertheless, at the thought of the remote-piloted helicopter employing the "Supervisor" system which has been successfully developed by Marconi Avionics in association with Westland Helicopters.

The purpose of the Supervisor system is to enable a remote-piloted helicopter to be controlled from the ground so that a battlefield commander can keep the forward edge of a battlefield under constant surveillance.

The "Wideye" helicopter employed in the Supervisor system is manufactured by Westland Helicopters Limited of Yeovil, whilst its very advanced electronic control payload, as well as the ground con-

trol vehicle, is provided by Marconi Avionics Electro-Optical Surveillance Division at Basildon. The helicopter, with its twin coaxial rotors, stands about as high as an average man, and its payload comprises a small stabilized camera sensor and 2-way radio link to convey command data from the ground to the helicopter and video data from the aircraft to the ground vehicle. The latter is fitted with tracking antennas, data processors, video monitors and a control console.

This is yet another achievement for Marconi Avionics Limited, a company which is very energetic in the field of airborne electronic equipment.

A BOOK FOR THE RADIO AMATEUR

TELEVISION INTERFERENCE MANUAL, 2nd Edition. By B. Priestley, B.Sc., C.Eng., M.I.E.R.E. 80 pages, 210 x 145mm. (8¼ x 5½in.) Published by the Radio Society of Great Britain. Price £1.35.

This book is primarily intended for the amateur radio transmitter who seeks to avoid neighbourly friction and annoyance by ensuring that his signals do not break through on nearby television receivers. In crowded localities the problems of TVI can be difficult to solve, especially as the breakthrough may be due to shortcomings in design or operation of the television receiver itself.

"Television Interference Manual" covers the whole field of TVI, and the information and advice it gives can be assumed to be virtually the entirety available at the time of its publication. Also dealt with are break-through problems with audio equipment. Audio break-through has become much more difficult to solve owing to the current widespread use of expensive solid-state audio systems which are more prone to interference than earlier cross-modulation-free valve equipments.

THE MODERN BOOK CO

WORLD RADIO TV HANDBOOK 1979 £9.15

THE RADIO AMATEUR HANDBOOK 1979
by ARRL Price £7.86

UNDERSTANDING AMATEUR RADIO
by J. Rusgrove Price £4.25

SOLID STATE DESIGN FOR THE RADIO AMATEUR
by ARRL Price £6.00

THE A.R.R.L. ANTENNA BOOK
by ARRL Price £4.25

FM AND REPEATERS FOR THE RADIO AMATEUR
by ARRL Price £3.50

REPAIRING POCKET TRANSISTOR RADIOS
by I. R. Sinclair Price £2.50

BEGINNER'S GUIDE TO RADIO
by G. J. King Price £3.00

BUILDING & DESIGNING TRANSISTOR RADIOS - A BEGINNER'S GUIDE
by R. H. Warring Price £3.30

OP-AMPS - THEIR PRINCIPLES AND APPLICATIONS
by J. B. Dance Price £2.50

ELECTRONICS FAULT DIAGNOSIS
by I. R. Sinclair Price £3.00

UNDERSTANDING DIGITAL ELECTRONICS
by Texas Instruments Price £3.90

NEWNES RADIO & ELECTRONICS ENGINEER'S POCKET BOOK
by Newnes Price £2.80

BEGINNER'S GUIDE TO TAPE RECORDING
by I. R. Sinclair Price £3.20

BEGINNER'S GUIDE TO AUDIO
by I. R. Sinclair Price £3.00

BEGINNER'S GUIDE TO INTEGRATED CIRCUITS
by I. R. Sinclair Price £3.00

BEGINNER'S GUIDE TO COLOUR TV
by G. J. King Price £2.50

BEGINNER'S GUIDE TO ELECTRIC WIRING
by F. Guillou Price £2.50

THE OSCILLOSCOPE IN USE
by I. R. Sinclair Price £2.75

THE CATHODE-RAY OSCILLOSCOPE AND ITS USE
by G. N. Patchett Price £4.00

INTRODUCING AMATEUR ELECTRONICS
by I. R. Sinclair Price £1.50

* PRICES INCLUDE POSTAGE *

ABC'S OF ELECTRONICS
by F. J. Waters Price £4.15

BEGINNER'S GUIDE TO HOME COMPUTERS
by M. Grosswirth Price £3.20

ADVENTURES WITH ELECTRONICS
by T. Duncan Price £2.85

PROJECT PLANNING & BUILDING
by M. A. Colwell Price £2.20

110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR
by R. M. Marston Price £3.00

110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR
by R. M. Marston Price £2.75

TESTING METHODS AND RELIABILITY ELECTRONICS
by A. Simpson Price £4.30

DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS
by N. M. Morris Price £4.30

BEGINNER'S GUIDE TO MICROPROCESSORS
by C. M. Gilmore Price £4.75

GETTING ACQUAINTED WITH MICROCOMPUTERS
by L. Frenzel Price £7.00

We have the Finest Selection of English and American Radio Books in the Country
19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176



Wilmslow Audio

THE firm for speakers!


SEND 15p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX • AUDIOMASTER • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL • COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUSS • GOODMANS • I.M.F. • ISOPON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER • MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • STAG • TANNOY • VIDEOTONE • WARFEDALE • YAMAHA • SHACKMAN • TANGENT

WILMSLOW AUDIO DEPT REC

SWAN WORKS, BANK SQUARE, WILMSLOW CHESHIRE SK9 1HF

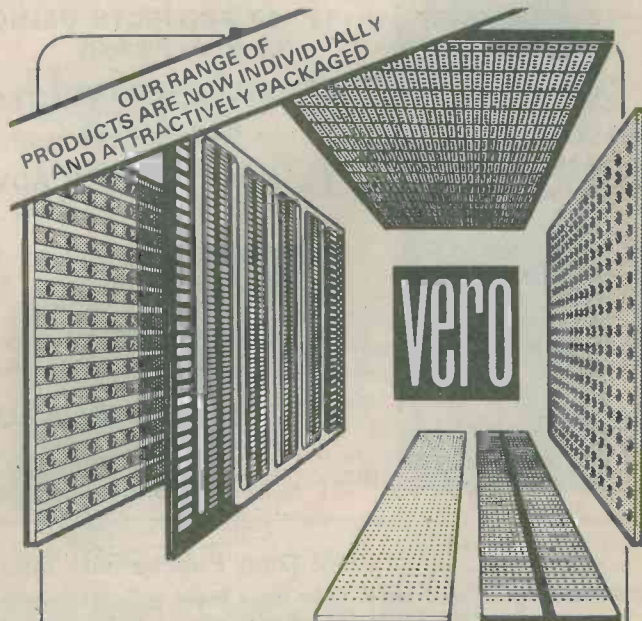Discount HiFi Etc. at 5 Swan Street and 10 Swan Street
Tel: 0625-529599 for Speakers, 0625-526213 for HiFi



Our new catalogue lists circuit boards for all your projects, from good old Veroboard through to specialised boards for ICs. And we've got accessories, module systems, cases and boxes - everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.




VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

DIRECT READER SERVICE

RADIO & ELECTRONICS BOOKS

1. **50 PROJECTS USING RELAYS, SCR's & TRIACS**
by F. G. Rayer £1.25
2. **FUN & GAMES WITH YOUR ELECTRONIC CALCULATOR** by J. Vine 90p
3. **50 (FET) FIELD EFFECT TRANSISTOR PROJECTS**
by F. G. Rayer £1.40
4. **DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS**
by Adrian Michaels £2.70
5. **50 SIMPLE L.E.D. CIRCUITS**
by R. N. Soar 90p
7. **THE COMPLETE CAR RADIO MANUAL**
by F. C. Palmer 90p
8. **SOLID STATE NOVELTY PROJECTS**
by M. H. Babani £1.00
9. **28 TESTED TRANSISTOR PROJECTS**
by R. Torrens £1.10
10. **SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS** by R. A. Penfold £1.10
11. **50 PROJECTS USING IC CA3130**
by R. A. Penfold £1.10
12. **50 CMOS IC PROJECTS**
by R. A. Penfold £1.10
13. **HOW TO BUILD ADVANCED SHORT WAVE RECEIVERS** by R. A. Penfold £1.35
14. **BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS** by R. A. Penfold £1.40
15. **50 CIRCUITS USING GERMANIUM SILICON & ZENER DIODES** by R. N. Soar 90p
16. **LINEAR I.C. EQUIVALENTS AND PIN CONNECTIONS**
by Adrian Michaels £3.00

all prices include postage & packing

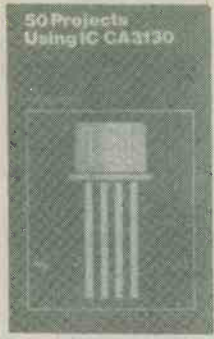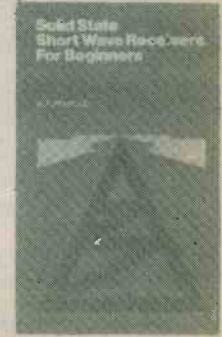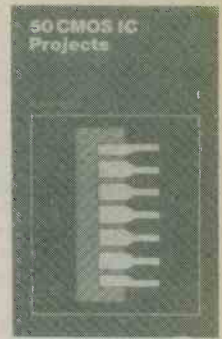

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies of

.....

..... No.

I enclose Postal Order/Cheque for £.....

Name

Address

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

SMALL ADVERTISEMENTS

Rate: 10p per word. Minimum charge £1.50

Box No. 25p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN.

A FAST INTRODUCTION TO COMPUTING £3.95. Introduction to Microprocessors and Computing £2.75. Both ordered together £6.20. S.A.E. for list of computing books. Dept. RC, Industrial Training Press, 3 Ringwood Way, Winchmore Hill, London N21 2RA.

SUPPLIERS OF ANY SERVICE SHEET or manual. S.A.E. with enquiries. Easy to follow repair instructions for any TV — send £5.00 and details of set. Circuit diagram £1 extra. AUSREC, 76 Church Street, Larkhall, Lanarkshire.

FOR SALE: Viscount X125 electronic organ, with separate Leslie speaker, 2-manual foot pedals, percussion, rhythm box. Matching stool, £450 o.n.o. T. F. Weatherley, 16 Beverley Court, Carlton Colville, Lowestoft, Suffolk. Telephone: Lowestoft 63216.

TIRRO'S NEW MAIL ORDER price list of electronic components now available on receipt of S.A.E. — TIRRO Electronics, Grenfell Place, Maidenhead, Berkshire.

FOR SALE: Inverter, 12V d.c. to 240V a.c. Suitable running electric shaver, camping, boating, etc. £5.50. Box No. G355.

WANTED: Large and small quantities of transistors, I.C.'s displays, etc., etc. Call any Saturday to: 306 St. Paul's Road, London N.1. Telephone: 01-359 4224.

88-108MHz TRANSMITTERS, built-in battery, mere 25 x 49 x 70mm. £13. 15 x 18 x 40mm. £25. Range up to 500 yards. Transmitter modules £8. Unlicensable U.K. Mail Order. Micro Electronics, 15 New Oxford Street, London W.C.1.

SOLAR CELLS: Bits, books and bargains. Send 95p for Solar Cell booklet and Data Sheets or stamp for list. — Edencombe Ltd., 34 Nathans Road, North Wembley, Middlesex HA0 3RX.

FOR SALE: Ex-A.M. rotary motor generator, 12V d.c. at 3.8 amps to 480V at 0.04 amps. £2.00 plus carriage. Box No. G356.

FOR SALE: Commodore PET Computer £65.00. S.A.E. for booklet. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

CAR BATTERY GIVING TROUBLE? Try our all electronic battery monitor. IC & PCB, £2.75 inc. S.A.E. for details. Tritch Electronics, 190 Roding Road, Loughton, Essex.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

FOR SALE: *Fundamentals of Radio Servicing* by B. W. Hicks, published by Hutchinsons Educational, £2.20 post paid. *Handbook of Satellites and Space Vehicles* by R. P. Haviland, £3.50 post paid. — Box No. G366.

NEW SHOP IN EAST KENT. Vast range of electronic components, equipment, hardware. Technocraft, 143 Tankerton Road, Whitstable, Kent. Telephone: 265097. Open Tuesday to Saturday. Easy parking.

(Continued on page 644)

CHESTER ELECTRONICS

TRANSFORMERS

6-0.6 @ 100mA £1.00 9-0.9 @ 75ma £1.00 12-0.12 @ 1A £3.00
6-0.6 @ 1 1/4 £2.00 9-0.9 @ 1A £2.44 25-0.25 @ 2A £5.00

SPECIAL SPECIAL OFFER

Brand new, boxed, manual car radios. Incredible price £10.00 each. Please hurry, this offer is only valid as long as stocks last. In the event that we are unable to supply we will refund your payment. NO EXTRA TO PAY.

BZY88 (400m/w) Zener diodes: 2V7 to 33V available @ 7p each. 100 mix £5.00

CAR AERIALS: 4 section type, chrome: only £2.00 each

CAR SHELF TYPE SPEAKERS: 5 watt, only £5.00 per pair. (All boxed, new etc)

SUB MINIATURE TOGGLE SWITCHES **PUSH SWITCHES**
250V 2A, 15mm x 12mm (diameter)
SPDT 250V 2A 48p each Push to make. Red top, 20p each.
(Available in red, yellow, black,
green and blue)

DPDT 250V 2A 65p each

240V SOLDERING IRONS (ALL NEW)

Antex Model C15W £3.60
Antex Model C17W £3.75

Antex Model X25 25W £4.00
DG 25W only £4.20 each

TRANSISTORS/DIODES

AC187K 25p	BC125 10p	BC301 25p	1N914 2p
AD161 35p	BC126 10p	BD135 25p	OA47 8p
AD162 35p	BC147B 7p	BD136 25p	1N4001 4p
AD149 45p	BC184C 7p	BDX32 £1.20	1N4006 6p
AU110 90p	BC182 8p	BRY39 25p	1N4007 7p
BC107 8p	BC183 8p	BFY51 14p	Silicon Rectifiers
BC109 8p	BC212 8p	OA200 5p	1 1/4 400v 10p each

CURLY LEADS: 4 core unscreened, stretch from 3in to 8in 30p each

ELECTROLYTICS

1 63V Axial 5p	2.2 25VA 5p	10 150V Tag Ended 10p
100 10V Radial 5p	220 16V A 5p	470 16V Radial 10p
640 25V Axial 8p	1000 35V R 15p	10,000 25V Tag 40p

PP3 Battery Snap-on Connectors 6p each. PP9 Snap-on Connectors 15p

KNOBES: Grey in colour but no clips. Push-on type. Special clearance price 5p each.


(NO CALLERS PLEASE AS WE HAVE NO RETAIL FACILITIES)

Send your order to:

CHESTER ELECTRONICS
6 HUNTER STREET CHESTER, CH1 2AU

Understand electronics

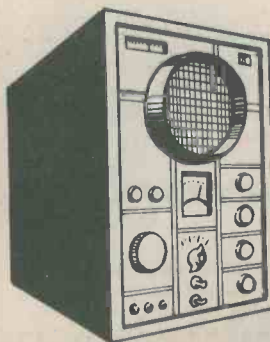Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Learn-a-Kit Course.



- (1) Build an oscilloscope
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

FREE

Brochure without obligation to

REF 6/79

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL!

P.O. Box 156, Jersey, Channel Islands.


NAME _____
ADDRESS _____

Self-Binder

for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

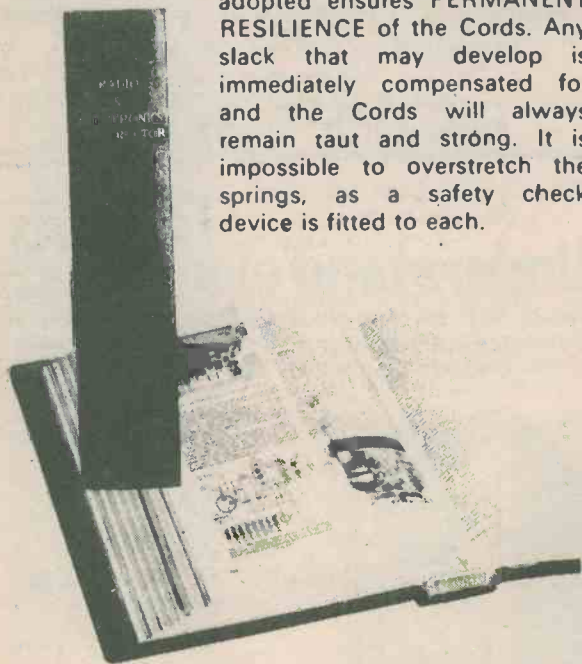

PRICE **£1.80** P.&P. 40p

including V.A.T.

Available only from:—

Data Publications Ltd.

57 Maida Vale London W9 ISN

SMALL ADVERTISEMENTS

(Continued from page 643)

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mr. H. R. Boutle, 14 Queens Drive, Bedford.

FOR SALE: Automatic car aerial £7.50. 25 2W zeners 75p. 100 1N914 50p. Miniature hearing aid amplifiers £1.00. Damaged video tape recorders £100. Closed circuit cameras £25-£50. S.A.E. for details. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

VHF—FM Micro-transmitter. I.C. design. Range 100 yds. 88-110MHz. Built £3.95. Kit £2.95. Both P.&P. 25p. P. Faherty, 4 Angus Drive, South Ruislip, Middlesex.

FOR SALE: Bush cassette tape recorder, battery driven. Microphone, etc. Excellent condition. £10 plus postage. Box No. G375.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £3.75 per annum. (U.K. and British Commonwealth), overseas \$10.00 or £4.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

FOR SALE: Mains transformer, 240V Pri., 2 separate secs. each 7V at 500mA, £1.10 each + 35p P.&P. NEW p.c.b. with 1 amp 200 p.i.v. bridge rect., 200k pot. 10k preset, 2 x 0.1µF 250V a.c. cap., 4 for £1 + 25p P.&P. NEW p.c.b. with 4 x BC108, 1 x BFY50, 4 x 0.1µF 160V, 2 x 1µF 160V caps. + zeners, diodes, resistors, 3 for £1 + 15p P.&P. D. Nicholls, Lyndale, Church Lane, Flax Bourton, Bristol.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

FOR SALE: "Experiments with Operational Amplifiers" — Learning by Doing. George B. Clayton £2.50. "Challenge of the Stars" by Patrick Moore and David A. Hardy £2.00. "Destroyers" by Antony Preston £4.00. Box No. G376.

VINTAGE VALVES, RADIOS, components, literature, service sheets, etc., 1920-1955. S.A.E. please with enquiries and for sample Antique Wireless Newsheet. Tudor Rees, 64 Broad Street, Staple Hill, Bristol. Telephone: 0272-565472.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

COLLECTORS' ITEMS. Nearly 50 copies of Radio Society of Great Britain's *Bulletins* covering period 1945 to 1949. In reasonable condition. Offers to: Box No. G377.

(Continued on page 645)

MAGENTA ELECTRONICS LTD

REC4 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS DE13 0UL
PHONE 02 83 65435. 9 a.m.-12, 2 p.m.-5. MON.-FRI. Mail Order only

All prices include VAT & First Class Post. Add 25p to orders under £5

R.E.C. PROJECT KITS

Make us YOUR No. 1 SUPPLIER of KITS and COMPONENTS for REC Projects. We supply carefully selected sets of parts to enable you to construct REC projects. Appropriate hardware — nuts, screws, I.C. sockets are included. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply — You construct.
PRICES INCLUDE CASES UNLESS OTHERWISE STATED.
Project Instructions only supplied as extra 39p each.

CONSTANT CURRENT TRANSISTOR TESTER, Mar. 79 £11.93.

I.C. MORSE PRACTICE OSCILLATOR, Mar. 79 £4.94.
Morse key extra £3.40.

2-TONE DOOR BUZZER, Feb. 79 £5.15.

3-BAND SHORT WAVE PRE-SELECTOR, Feb. 79 £13.33

ULTRA SENSITIVE ULTRASONIC REMOTE CONTROL, Feb. 79 £13.44. Doppler shift add-on unit, Mar 79 £3.61.

RADIO 4 CONVERTER, Jan 79, £5.99.

BRY39 METRONOME, Jan. 79 £4.21.

BRY39 TOUGH SWITCH, Dec. 78 £1.31. Relay extra £1.83.

BRY39 PILOT LIGHT, Dec. 78 £1.15.

LIGHT CHANGE ALARM UNIT, Dec. 78 £9.31.

SWINGING METRONOME, Nov. 78 £11.38.

REMOTE READ-OUT THERMOMETER, Oct. 78 £13.60.

DIGITAL DICE, Sept. 78 £9.13.

VARIABLE — 'C' A.F. GENERATOR, Aug. Sept. 78 £14.59.

PHOTOCELL PROPERTY PROTECTOR, Aug. 78 £8.07. Bell extra £1.46.

1979 ELECTRONICS CONSTRUCTORS CATALOGUE

HAVE YOU GOT YOUR COPY YET? MAGENTA'S NEW CATALOGUE INCLUDES MANY NEW PRODUCTS — CAREFULLY CHOSEN FOR EVERYDAY ELECTRONICS READERS, PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR CONSTRUCTORS. FULLY INCLUSIVE PRICES RIGHT NEXT TO THE PRODUCTS MAKE ORDERING EASY. NO MINIMUM ORDER — ALL PRODUCTS STOCK LINES. FIRST CLASS DELIVERY OF FIRST CLASS COMPONENTS. SEND FOR YOUR COPY AND SEE HOW EASY IT IS TO USE THE MAGENTA CATALOGUE!
WRITE TODAY ENCLOSING 4 x 9p STAMPS.

REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536

£14.91

POST
FREE


4" dia. lens

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE,
PRECISION GROUND AND
POLISHED LENS, CHROME PLATED
FRAME AND FLEXIBLE TUBE.
IDEAL FOR HOBBIES, AND
DETAILED WORK WHICH REQUIRES
BOTH HANDS FREE.

CALLERS WELCOME

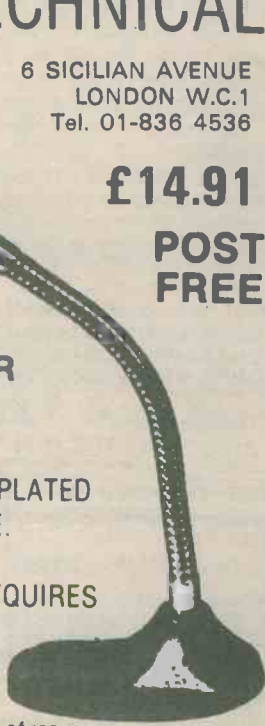(Subject to price ruling at the time of issue)



PLAIN-BACKED SELF-BINDERS

for your other magazines

(Maximum Format 11 $\frac{1}{4}$ " x 8 $\frac{1}{4}$ ")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE **£1.80** p. & p. 40p

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

TRANSISTORS	P	DIODES	P	SARGAIN PACKS
AC178	18	*AF117/9	28	*AA117/9
AC187	18	*BA13	28	*BA13
AD18	30	*BB105A	29	*BB105A
AO182	30	*BB197	10	*BB127
AL13	120	*BY199	36	*BY199
AS18	8	*OA47/79	7	*OA47/79
AU110	175	*OA95	9	*OA95
AU113	210	*OA200	9	*OA200
BC105	8	IB45N	9	IB45N
BC108	8	IN4001/2	9	IN4001/2
BC109	8	IN4004/5	9	IN4004/5
*BC117/8	14	IS920	8	IS920
*BC125	14	*S44	4	*S44
*BC132	14	*S20	8	*S20
*BC147	8	*S95	8	*S95
*BC148	8	BSX19/20	18	BSX19/20
*BC149	8	*BT106	110	*BT106
*BC154	18	*BU205	180	*BU205
*BC156	18	*BU208	175	*BU208
*BC158	18	*C100D	44	*C100D
*BC168	12	*MEJ340	43	*MEJ340
*BC172	9	MJE220	105	MJE220
*BC182/L	9	MJE255	80	MJE255
*BC183/L	9	MJE3055	80	MJE3055
*BC187	24	OC28	88	OC28
*BC207B	10	OC140	82	OC140
*BC212/L	9	*OC200	70	*OC200
*BC213/L	9	OC202	82	OC202
*BC214/L	9	*R2008B	170	*R2008B
BC301	27	*R2010B	170	*R2010B
*BC307	12	*TIP29	39	*TIP29
*BC337	10	*TIP30	39	*TIP30
BC348	10	*TIP31A	39	*TIP31A
BC361	10	*TIP32A	46	*TIP32A
*BC367/8	10	*TIP32B	65	*TIP32B
*BC368	10	*TIP33B	66	*TIP33B
*BC369	12	*TIP34B	94	*TIP34B
*BC370	14	*TIP41A	81	*TIP41A
*BC371/2	14	*TIP42A	62	*TIP42A
BD115	43	*TIX212	18	*TIX212
*BD121	34	*TIX301	12	*TIX301
BD132	34	*TIX302	12	*TIX302
BD136	34	*TIX302	16	*TIX302
BD139	35	*TIX303	16	*TIX303
BD137	35	2N1708	18	2N1708
BD138	35	2N1930	40	2N1930
BD139	35	2N1304	40	2N1304
BD140	36	2N1305	40	2N1305
BD161	64	2N2847	66	2N2847
BD236	66	2N3053	40	2N3053
BD895A	65	2N3054	40	2N3054
BD995A	65	2N3055	40	2N3055
BF115	18	*2N302/3	40	*2N302/3
*BF167	23	*2N3704/5	8	*2N3704/5
BF178	25	*2N4443	80	*2N4443
		*2N4443	80	

W/W RESISTORS	P	VOLTAGE REGS	P
2.5W Axial	10	Plastic TO-220 case	28
5W Radial	10	1.5A+VE	80
10W Axial	10	1A+VE	80
15W Radial	10	1A+VE90	80

TRANSISTORS	P	DIODES	P
AC178	18	*AF117/9	28
AC187	18	*BA13	28
AD18	30	*BB105A	29
AO182	30	*BB197	10
AL13	120	*BY199	36
AS18	8	*OA47/79	7
AU110	175	*OA95	9
AU113	210	*OA200	9
BC105	8	IB45N	9
BC108	8	IN4001/2	9
BC109	8	IN4004/5	9
*BC117/8	14	IS920	8
*BC125	14	*S44	4
*BC132	14	*S20	8
*BC147	8	*S95	8
*BC148	8	BSX19/20	18
*BC149	8	*BT106	110
*BC154	18	*BU205	180
*BC156	18	*BU208	175
*BC158	18	*C100D	44
*BC168	12	*MEJ340	43
*BC172	9	MJE220	105
*BC182/L	9	MJE255	80
*BC183/L	9	MJE3055	80
*BC187	24	OC28	88
*BC207B	10	OC140	82
*BC212/L	9	*OC200	70
*BC213/L	9	OC202	82
*BC214/L	9	*R2008B	170
BC301	27	*R2010B	170
*BC307	12	*TIP29	39
*BC337	10	*TIP30	39
BC348	10	*TIP31A	39
BC361	10	*TIP32A	46
*BC367/8	10	*TIP32B	65
*BC368	10	*TIP33B	66
*BC369	12	*TIP34B	94
*BC370	14	*TIP41A	81
*BC371/2	14	*TIP42A	62
BD115	43	*TIX212	18
*BD121	34	*TIX301	12
BD132	34	*TIX302	12
BD136	34	*TIX302	16
BD139	35	2N1708	18
BD137	35	2N1930	40
BD138	35	2N1304	40
BD139	35	2N1305	40
BD140	36	2N2847	66
BD161	64	2N3053	40
BD236	66	2N3054	40
BD895A	65	2N3055	40
BD995A	65	*2N302/3	40
BF115	18	*2N3704/5	8
*BF167	23	*2N4443	80
BF178	25	*2N4443	80

W/W RESISTORS	P	VOLTAGE REGS	P
2.5W Axial	10	Plastic TO-220 case	28
5W Radial	10	1.5A+VE	80
10W Axial	10	1A+VE	80
15W Radial	10	1A+VE90	80

TRANSISTORS	P	DIODES	P
AC178	18	*AF117/9	28
AC187	18	*BA13	28
AD18	30	*BB105A	29
AO182	30	*BB197	10
AL13	120	*BY199	36
AS18	8	*OA47/79	7
AU110	175	*OA95	9
AU113	210	*OA200	9
BC105	8	IB45N	9
BC108	8	IN4001/2	9
BC109	8	IN4004/5	9
*BC117/8	14	IS920	8
*BC125	14	*S44	4
*BC132	14	*S20	8
*BC147	8	*S95	8
*BC148	8	BSX19/20	18
*BC149	8	*BT106	110
*BC154	18	*BU205	180
*BC156	18	*BU208	175
*BC158	18	*C100D	44
*BC168	12	*MEJ340	43
*BC172	9	MJE220	105
*BC182/L	9	MJE255	80
*BC183/L	9	MJE3055	80
*BC187	24	OC28	88
*BC207B	10	OC140	82
*BC212/L	9	*OC200	70
*BC213/L	9	OC202	82
*BC214/L	9	*R2008B	170
BC301	27	*R2010B	170
*BC307	12	*TIP29	39
*BC337	10	*TIP30	39
BC348	10	*TIP31A	39
BC361	10	*TIP32A	46
*BC367/8	10	*TIP32B	65
*BC368	10	*TIP33B	66
*BC369	12	*TIP34B	94
*BC370	14	*TIP41A	81
*BC371/2	14	*TIP42A	62
BD115	43	*TIX212	18
*BD121	34	*TIX301	12
BD132	34	*TIX302	12
BD136	34	*TIX302	16
BD139	35	2N1708	18
BD137	35	2N1930	40
BD138	35	2N1304	40
BD139	35	2N1305	40
BD140	36	2N2847	66
BD161	64	2N3053	40
BD236	66	2N3054	40
BD895A	65	2N3055	40
BD995A	65	*2N302/3	40
BF115	18	*2N3704/5	8
*BF167	23	*2N4443	80
BF178	25	*2N4443	80

W/W RESISTORS	P	VOLTAGE REGS	P
2.5W Axial	10	Plastic TO-220 case	28
5W Radial	10	1.5A+VE	80
10W Axial	10	1A+VE	80
15W Radial	10	1A+VE90	80

P&P add 30c. VAT — Please add 8% except those marked * which are 12.8%
 Export — postage at cost. Wholesale and Industrial enquiries welcome. S.A.E. for lists
K & A DISTRIBUTORS
 52 Barkby Road, Syston, Leicester LE7 8AF — Tel: 0533 609391

TRANSISTORS	P	DIODES	P
AC178	18	*AF117/9	28
AC187	18	*BA13	28
AD18	30	*BB105A	29
AO182	30	*BB197	10
AL13	120	*BY199	36
AS18	8	*OA47/79	7
AU110	175	*OA95	9
AU113	210	*OA200	9
BC105	8	IB45N	9
BC108	8	IN4001/2	9
BC109	8	IN4004/5	9
*BC117/8	14	IS920	8
*BC125	14	*S44	4
*BC132	14	*S20	8
*BC147	8	*S95	8
*BC148	8	BSX19/20	18
*BC149	8	*BT106	110
*BC154	18	*BU205	180
*BC156	18	*BU208	175
*BC158	18	*C100D	44
*BC168	12	*MEJ340	43
*BC172	9	MJE220	105
*BC182/L	9	MJE255	80
*BC183/L	9	MJE3055	80
*BC187	24	OC28	88
*BC207B	10	OC140	82
*BC212/L	9	*OC200	70
*BC213/L	9	OC202	82
*BC214/L	9	*R2008B	170
BC301	27	*R2010B	170
*BC307	12	*TIP29	39
*BC337	10	*TIP30	39
BC348	10	*TIP31A	39
BC361	10	*TIP32A	46
*BC367/8	10	*TIP32B	65
*BC368	10	*TIP33B	66
*BC369	12	*TIP34B	94
*BC370	14	*TIP41A	81
*BC371/2	14	*TIP42A	62
BD115	43	*TIX212	18
*BD121	34	*TIX301	12
BD132	34	*TIX302	12
BD136	34	*TIX302	16
BD139	35	2N1708	18
BD137	35	2N1930	40
BD138	35	2N1304	40
BD139	35	2N1305	40
BD140	36	2N2847	66
BD161	64	2N3053	40
BD236	66	2N3054	40
BD895A	65	2N3055	40
BD995A	65	*2N302/3	40
BF115	18	*2N3704/5	8
*BF167	23	*2N4443	80
BF178	25	*2N4443	80

W/W RESISTORS	P	VOLTAGE REGS	P
2.5W Axial	10	Plastic TO-220 case	28
5W Radial	10	1.5A+VE	80
10W Axial	10	1A+VE	80
15W Radial	10	1A+VE90	80

Send 40p for New Autumn 1978 Fully Illustrated Catalogue.

BUILD YOUR OWN
P.A., GROUP & DISCO SPEAKERS by R. F. C. Stephens
 Save money with this practical guide. Plans for 17 different designs. Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman
 (full constructional details for versions using 15", 12" and 10" drive units.) £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BDK by R. F. C. Stephens
 This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING
 5 Swan Street, Wilmslow, Cheshire

PRINTED CIRCUITS AND HARDWARE

Comprehensive range Constructors' hardware and accessories. Selected range of popular components. Printed circuit boards for individual designs. Drawing materials for printed circuits. Resist coated laminate, epoxy glass for the d.i.y. man. Full processing instructions, no unusual chemicals required.

Send 15p for catalogue

Ramar Constructor Services
 Masons Road · Stratford-on-Avon · Warwks CV37 9NF

WHAT DO YOU DO WHEN YOU FIND YOU NEED A:

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 50p each, p&p 13p

Issue(s) required

Annual Subscription

Price **£7.50** inland, **£8.50** overseas

post free, commence with issue

Bound Volumes:

Vol. 27. August 1973 to July 1974	Price £3.00 , post & pkg 90p
Vol. 28. August 1974 to July 1975	Price £3.20 , post & pkg 90p
Vol. 29. August 1975 to July 1976	Price £3.50 , post & pkg 90p
Vol. 30. August 1976 to July 1977	Price £3.70 , post & pkg 90p
Vol. 31. August 1977 to July 1978	Price £5.20 , post & pkg 90p

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price **£1.80**, post & pkg 40p

With no title on spine, maroon

Price **£1.80**, post & pkg 40p

With no title on spine, green

Price **£1.80**, post & pkg 40p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages	Price £1.20 , P. & P. 20p
DB6 Radio Amateur Operator's Handbook, New edition in course of preparation	
DB17 Understanding Television, 504 pages	Price £3.95 , P. & P. 70p
DB19 Simple Short Wave Receivers 140 pages	Price 80p , P. & P. 20p

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White	— 6 sheets	Price £1.00 , P. & P. 8p
Set 4: Wording — Black	— 6 sheets	Price £1.00 , P. & P. 8p
Set 5: Dials	— 6 sheets	Price £1.00 , P. & P. 8p

Prices include V.A.T.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS