

**Circuit ideas: Class-A power buffer**

# ELECTRONICS WORLD

ISSN 0959-8332



9 770959 833066

A REED BUSINESS PUBLICATION SOR DISTRIBUTION

INCORPORATING WIRELESS WORLD

MAY 2000 £2.65

## Battery health monitor

High-performance inductance meter

New mobile phone services

Speaker environment effects

Tools for PLL design

Designing IF filters

JLH's first audio power amps

What is Bluetooth?





# Telnet

Tel: 02476 650702

## Quality second-user test & measurement equipment

### NEW PHONE CODE FOR COVENTRY 02476

#### Radio Communications Test Sets

Marconi 2955	£2000
Marconi 2958/2960	£2250
Anritsu MS55A2	£1200
Hewlett Packard 8922B (GSM)	£6950
Schlumberger Stabilock 4031	£3995
Schlumberger Stabilock 4040	£1500
Racal 6111 (GSM)	£1750
Racal 6115 (GSM)	£3995
Rhode & Schwarz CMTA 94 (GSM)	£5950
IFR 1200S	£2995



### Fax 02476 650 773

Wandel & Goltermann TSA-1 system analyser (100Hz-180MHz)	£2750
Wiltron 6409 - 10-2000MHz R/F Analyser	£1750

#### MISCELLANEOUS

Eaton 2075-2A - Noise Gain Analyser	at £2750
Fluke 5100A/5100B/5200A - Calibration Units (various available)	from £1000
Fluke 2620 Data Buckets	£500
Fluke 8842A - Digital Multimeter	£600
Hewlett Packard 339A Distortion measuring set	£1200
Hewlett Packard 435A + 435B Power meters	from £100
Hewlett Packard 778D Dual-Directional Couplers	£650
Hewlett Packard 3488A - Switch/Control unit	£475
Hewlett Packard 3784A - Digital Transmission Analyser	£4500
Hewlett Packard 3785A - Jitter Generator & Receiver	£1250
Hewlett Packard 5343A - Frequency counter 26.5GHz	£2000
Hewlett Packard 5385A - 1 GHz Frequency counter	£650
Hewlett Packard 6033A - Autoranging System PSU (20v-30a)	£750
Hewlett Packard 6622A - Dual O/P system p.s.u.	£1250
Hewlett Packard 6623A - Triple o/p system p.s.u.	£1300
Hewlett Packard 6624A - Quad Output Power Supply	£2000
Hewlett Packard 6632A - System Power Supply (20v-5A)	£800
Hewlett Packard 6652A - 20V-25A System PSU	£750
Hewlett Packard 8112A - 50MHz Pulse Generator	£2250
Hewlett Packard 8350B - Sweep Generator Mainframe	£2000
Hewlett Packard 8656A Synthesised signal generator	£850
Hewlett Packard 8656B Synthesised signal generator	£1450
Hewlett Packard 8660D - Synth'd Sig. Gen (10 KHz-2600MHz)	£3250
Hewlett Packard 8903A, B and E - Distortion Analyser	£2750
Hewlett Packard 16500A + B - Logic Analyser Mainframes	from £1000
Hewlett Packard 16500C - Logic Analyser Mainframe	£3250
Hewlett Packard 16501A/B & C - Logic Analyser System Expander Frame from	£2000
Hewlett Packard 37900D - Signalling test set	£3750
Hewlett Packard 75000 VXI Bus Controllers	£700
Hewlett Packard 4193A - Vector Impedance Meter	£4750
Hewlett Packard 5350B - 20Hz Frequency Counter	£1950
Hewlett Packard 8657B - 100KHz-2060 MHz Sig Gen	£3995
Hewlett Packard 8657D - XX DQPSK Sig Gen	£4500
Hewlett Packard 8130A - 300 MHz High speed pulse generator	£5250
Hewlett Packard 8116A - 50MHz Pulse/Function generator	£2250
Hewlett Packard 1660A-136 channel Logic Analyser	£3995
Keytek MZ-15/EC Minizap ESD Simulator (15kv - hand held)	£1750
Marconi 1066B - Demultiplexer & Frame Alignment Monitor (140MBIT to 64KBIT)	NEW
Marconi 2610 True RMS Voltmeter	£550
Marconi 6950/6960/6960B Power Meters & Sensors	from £400
Philips 5515 - TN - Colour TV pattern generator	£1400
Philips PM 5193 - 50MHz Function generator	£1500
Leader 3216 Signal generator 100KHz - 140MHz - AM/FM/CW with built in FM stereo modulator (as new) a snip at	£795
Racal 1992 - 1.3GHz Frequency Counter	£500
Rohde & Schwarz SMY-01 Signal Generator (9KHz-1040MHz)	£2250
Rohde & Schwarz NRV dual channel power meter & NAV Z2 Sensor	£1250
Syston Donner 6030 - 26.5GHz Microwave Freq Counter	£1995
Tektronix ASG100 - Audio Signal Generator	£750
Wayne Kerr 3245 - Precision Inductance Analyser	£1995
Wiltron 6474A-20 - 10MHz-20GHz - Swept Frequency Synthesiser	£4950

Hewlett Packard 8642A - high performance R/F synthesiser (0-1-1050MHz)	£4750
3335A - synthesiser (200Hz-81MHz)	£2400
Hewlett Packard 436A power meter and sensor (various)	from £750
437B power meter and sensor (various)	from £1100
Hewlett Packard 8753A network analyser (3GHz)	from £2500
8753B network analyser (3GHz)	from £3250
'S' parameter test sets 85046A and 85047A available at	£2000 & £3000

#### Wandel & Goltermann

##### SPECIAL OFFER

PCM-4 PCM Channel measurement set (various options available)	from £5500
Marconi 2305 - modulation meter	£999
Marconi 6310 - programmable sweep generator (2 to 20GHz) - new	£3250
Hewlett Packard 5342A - microwave frequency counter (500MHz-18GHz) ops 1 & 3	£700
5370B - universal time interval counter	£1500

#### OSCILLOSCOPES

Gould 4068 150MHz 4 channel DSO	£1500
Hewlett Packard 54201A - 300MHz Digitizing	£1250
Hewlett Packard 54600A - 100MHz - 2 channel	£750
Hitachi V152/V12/V22/V302B/V302F/V353F/V550B/V650F	from £125
Hitachi VI 100A - 100MHz - 4 channel	£900
Intron 2020 - 20MHz - Dual channel D.S.O. (new)	£450
Iwatsu SS 5710/SS 5702 -	from £125
Kikusui COS 5100 - 100MHz - Dual channel	£350
Lecroy 9450A - 300MHz/400 MS/s D.S.O. 2 channel	£2250
Meguro M50 1270A - 20MHz - D.S.O. (new)	£450
Philips PM3094 - 200MHz - 4 channel	£1750
Philips 3295A - 400MHz - Dual channel	£1600
Philips PM3392 - 200MHz-200MS/s - 4 channel	£1995
Tektronix 465 - 100MHz - Dual channel	£350
Tektronix 464/466 - 100MHz - (with AN. storage)	£350
Tektronix 475/475A - 200MHz/250MHz -	from £450
Tektronix 468 - 100MHz - D.S.O.	£650
Tektronix 2213/2215 - 60MHz - Dual channel	£350
Tektronix 2220 - 60MHz - Dual channel D.S.O.	£1250
Tektronix 2235 - 100MHz - Dual channel	£900
Tektronix 2221 - 60MHz - Dual channel D.S.O.	£1250
Tektronix 2245A - 100MHz - 4 channel	£900
Tektronix 2440 - 300MHz/500 MS/s D.S.O.	£2950
Tektronix 2445A - 150MHz - 4 channel	£1250
Tektronix 2445 - 150MHz - 4 channel + DMM	£1200
Tektronix TAS 475 - 100MHz - 4 channel	£995
Tektronix 7000 Series (100MHz to 500MHz)	from £200
Tektronix 7104 - 1GHz Real Time	from £2500
Tektronix 2465/2465A/2465B - 300MHz/350MHz 4 channel	from £1250
Tektronix 2430/2430A - Digital storage - 150MHz	from £1250
Tektronix 2467B - 400MHz - 4 channel high writing speed	£4750
Tektronix TDS 320 100MHz 2 channel	£850
Tektronix TDS 540 500MHz 4 channel	£4500
Tektronix 544A 500MHz 4 channel	£4950

#### SPECTRUM ANALYSERS

Ando AC 8211 - 1.7GHz	£1500
Avcom PSA-65A - 2 to 1000MHz	£850
Anritsu MS 2663A - 9KHz - 8.1GHz	£7000
Anritsu MS 62B - 50Hz to 1700MHz	£1450
Anritsu MS 610B 10KHz - 2GHz - as new	£3500
Anritsu MS 710F - 100KHz - 23GHz	£5250
Advantest/TAKEEDA RIKEN - 4132 - 100KHz - 1000MHz	£1500
Hewlett Packard 3562A Dual channel dynamic signal analyser 64µHz - 100KHz	£5500
Hewlett Packard 8505A - 1.3GHz - Network Analyser	£1995
Hewlett Packard 8756A/8757A Scalar Network Analyser	from £1000
Hewlett Packard 853A Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£2750
Hewlett Packard 182T Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£2250
Hewlett Packard 8568B - 100Hz - 1500MHz	£5250
Hewlett Packard 8567A - 100Hz - 1500MHz	£3995
Hewlett Packard 8754A - Network Analyser 4MHz-1300MHz	£1500
Hewlett Packard 8591E 9KHz-1.8GHz	£4250
Hewlett Packard 8594E 9KHz-2.9GHz	£6,750
Hewlett Packard 3561A Dynamic signal analyser	£3,995
Hewlett Packard 35660A Dynamic signal analyser	£3250
IFR A7550 - 10KHz-1GHz - Portable	£1950
Meguro - MSA 4901 - 30MHz - Spec. Analyser	£700
Meguro - MSA 4912 - 1 MHz - 1GHz Spec. Analyser	£995
Tektronix 2712 9KHz-1.8GHz (with tracking generator and video monitor mode)	£5500

## CONTENTS

### 355 COMMENT

Mobile Internet - who wants it?

### 357 NEWS

- Athlon or Pentium III?
- New substrate for high-speed processing
- Chip transistors shrink to 50nm
- Electronic tagging for consumer goods
- Self-assembling micro-wires for MCMs
- Digital watermarking for OS maps

### 362 VERIFY BATTERIES TO 7AH

This micro-controlled load tester for 12V sealed lead-acid and NiCd batteries covers twenty of the most popular capacities from 0.8 to 7Ah. Designed by Dave Sawford and Ken Duggan.

### 373 THIRD-GENERATION MOBILE PHONES

What exactly will be on offer when the new third-generation mobile phone services are rolled out? Richard Wilson reports, revealing that we may have to wait two or three years to find out.



Mobile video - just one new feature that the new third-generation mobile phone technology makes possible. But when? Read Richard Wilson's report on page 373.

### 378 CIRCUIT IDEAS

- RS232-to-parallel data conversion
- FDNCs using current conveyors
- Efficient battery auto-charger
- 30W Class-A power follower

### 384 GETTING THE MOST FROM YOUR SCOPE

Oscilloscope noise, and making measurements in noisy environments are the topics of Les Green's third article.

### 388 SPEAKERS' CORNER

Your listening environment has a surprisingly significant effect on what you hear from your loudspeakers. John Watkinson explains why.

### 392 PHASE-LOCKED LOOPS

Revealing useful web sites along the way, Cyril Bateman explains the phase-locked loop and the options and design tools available for those involved with this invaluable building block.

### 396 AN RF INITIATIVE

Ian Hickman introduces you to an important initiative aimed at encouraging a greater number of promising electronics engineering undergraduates to aim for a career in the fascinating field of RF engineering.

### 399 NEW PRODUCTS

New product outlines, selected and edited by Richard Wilson.

### 410 IF FILTER OPTIONS

Joe Carr looks at the variety of IF filtering techniques available and discusses their individual merits.

### 417 JLH - A LIFETIME IN ELECTRONICS

The coming of the transistor - this month John remembers the emergence and evolution of early transistor audio power amplifiers including the Lin design and his own 75 watter.

### 421 WHAT IS BLUETOOTH?

Soon it will be possible to connect peripherals to your PC via an rf link using a wireless local network technology called Bluetooth. Geoff Lewis outlines how it works.

### 424 A NOVEL INDUCTANCE METER

Michael Slifkin and Alexander Gornstein have developed a micro-controlled inductance meter capable of displaying accurate measurements from 20µH to 200mH on an LCD module.

### 430 EVERYTHING BUT THE SINK

Using synchronous rectification, SynQor has designed a DC-to-DC converter for distributed power systems that is so efficient that it doesn't need a heat sink.

### 432 WEB DIRECTIONS

Useful web addresses for the electronics designer.

### 435 LETTERS


TID: RIP? • Knee, mice • Free PCB layout tool • Early radar • Dangerous protection • Drum recordings • Defective colour vision



Photography: Mark Swallow



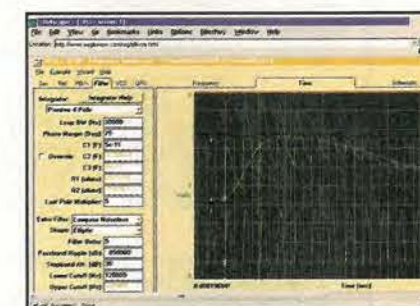Michael Slifkin's novel micro-controlled inductance meter measures from 20µH to 200mH with minimal errors due to ohmic loss - page 424.



A phase-locked loop simulator especially for rf design designers. If you are involved with PLLs, have a look at page 392.



When you're using an oscilloscope, there's a right way and a wrong way to probe a circuit like this. Find out how to do it properly on page 384.

All equipment is used - with 30 days guarantee and 90 days in some cases

Add carriage and VAT to all goods.

Telnet, 8 Cavans Way, Binley Industrial Estate, Coventry CV3 2SF.

CIRCLE NO. 101 ON REPLY CARD

Tel: 02476 650 702  
Fax: 02476 650 773

June issue on sale 5 May



# PIC Basic

Write your PIC programs in BASIC! - No STAMP REQUIRED!

## PIC Basic - £49.95

Quicker and easier than 'C' or assembler. PIC BASIC is a true compiler providing faster execution and shorter programs than BASIC Stamp interpreters, built in 12C routines and serial comms upto 115K Baud and full BASIC STAMP compatibility makes writing for the Microchip PICmicro's easy! PIC BASIC compiles your basic language programs to Microchip Hex format for use with in-circuit emulators or for programming directly into the PIC CHIP. Supports PIC12C67x, PIC14Cxxx, PIC16C55x, 6xx, &xx, 84, 92x and 16F87x. Full documentation with syntax examples are provided in the 168 page user manual. A technical support mailing list is provided for life time support.

## PIC Basic Pro - £149.95

The PIC BASIC Pro compiler instruction set is compatible with the Basic Stamp II providing additional functionality over PIC BASIC. feature like LCD read/Write, fully customisable Serial in / out. (Create a serial LCD display driver in minutes). Full de-bug facilities, compile with debug to produce assembly commented with your Basic commands. PIC BASIC and PIC BASIC PRO compile tight efficient code without the use of a basic interpreter. Supplied with a 168Page manual, explaining each command and worked examples. FREE PIC Macro compiler, FREE Programmers File Editor, FREE Windows Front End. PIC BASIC PRO includes samples programs and code to support Smart card read/write.

Download the full 168 page PIC BASIC MANUAL and sample programs  
<http://www.picbasic.co.uk>  
 Order Online via our secure server  
<http://www.crownhill.co.uk>

- Low cost programmer for PIC12Cxxx, PIC12Cxxx, PIC14Cxxx, PIC16C505, 55x, 6xx, 7xx, 84, 9xx/PIC 16C62x and PIC16F87x
- ZIF adaptors are available for 8/18 in 40/28Pin DIL, 8, 18 and 28 SOIC, 44 Pin MQFP, 44 and 68 Pin PLCC
- Powered by 2x 9V batteries or AC adapter.
- Connects to PC parallel port.
- Upgradable software is supplied for future PIC Micro's
- FREE 8051 style PIC Macro compiler

**£35** When purchased with PIC BASIC

Parallel port extension cable - £5.95

40Pin ZIF socket - £22.50

8/18Pin ZIF Socket - £22.50

PIC8 Prototype board - £4.50

PIC18 Prototype board - £5.50

PIC64 Prototype board - £8.50

All prices are subject to VAT@17.5%

## PIC Real-time 'Emulator' and Programmer



- For PIC16F87x (emulates most PIC16C6x/7x devices)
- In-Circuit run time debugging
- Real Time code execution 32KHz to 20MHz real time operation
- High Speed Parallel port interface
- 2.5V to 6.V operating range
- Built in device programmer
- Run, Step, Run to Cursor etc
- Conditional Animation Break
- Software animation trace captures 3 user defined variables in addition to opcode, W, Status, FSR registers and corresponding instructions.
- Source Level and symbolic debugging
- Runs under PICICD IDE (win95/98 or NT) or MPLAB
- Supplied with ICD debug module, Proto board, 40Pin and 28Pin emulator headers, Cables IDE software and user guide

All prices are subject to VAT@17.5%

## PIC Micro CD-ROM

over 1.2Gb of info **£10 inc P&P and VAT**

Packed with information, data sheets, application notes, programs diagrams and tutorials. Includes TETRIS and PING PONG with sound and video out of a single PIC 16F84. Basic language assembly routines and macros for hundreds of commands. Data sheets on thousands of devices, micro's, memory and support chips.

## LCD DISPLAYS

16x2 line super twist displays - **£7.50 ea**

## Xtals and Resonators

4Mhz and 20Mhz from **45p**



## PIC16x84 programmer Kit

WINDOWS Driver - **£15.00 inc P&P + VAT**

Programs the popular PIC1684 and 24 series serial memory devices. Connects to the serial port of PC upto pentium (not P2 or P3) and requires NO External power supply. The KIT includes Diagram, layout, High Quality PCB and all components, software on 3.5" FD

## SMARTCARD DEVELOPMENT SYSTEM



ChipDrive StarterKit + Windows Software  
 Read and Write data on Smart Cards and Memory cards  
 Microsoft PCSC compatible!  
 Package Includes:  
 Professional card Reader Writer (ChipDrive Micro),  
 Assorted Smart Cards (3 pairs),  
 Samples of source code in VB3,4,5+6, C and Delphi.  
 Examples Apps to Read and Write to Smart Cards and GSM cards  
 Documentation and detailed Windows DLL description.

**£69.95**

[www.towitoko.co.uk](http://www.towitoko.co.uk)

## LabProg 48LV

Low Cost - High Performance

Intelligent Universal Device Programmer

Includes:

- Connection cable
- Diagnostic POD
- User Manual
- PC Software Driver
- 240VAC/12V adaptor

CE certified

Plugs into parallel port of your PC  
 Adaptors for TSOP, PSOP, QFP, SOIC, PLCC  
 True No Adapter Programming upto 48 Pins  
 Programs and Verifies 2,2,7,3,3,3 & 5V devices  
 FREE software updates 3 Year Warranty

Universal Serial Eeprom programmer



**£49.95**

All prices are subject to VAT@17.5%

PreProm UNIVERSAL Eeprom Programmer  
 Adaptors for TSOP, PSOP, QFP, SOIC, PLCC  
 Adaptors for Microprocessors  
 Adaptors for Eeprom  
 Emulator adaptor

**£132.00**

## Crownhill Associates Limited

32 Broad Street Ely Cambridge Cb7 4PW  
 Tel: 01353 666709 Fax: 01353 666710

ORDER ON-LINE

[www.crownhill.co.uk](http://www.crownhill.co.uk)

CIRCLE NO. 104 ON REPLY CARD

## Mobile Internet - who wants it?

As the tortuous auction for 3G licences went on and the prices rose into the billions, did anyone ask themselves: "Who wants mobile Internet?" Already people talk about 'm-commerce', meaning mobile commerce, as the successor to e-commerce.

Will people really transact business deals and compose messages using the tiny keypads of mobile phones? Will people access the Internet using wireless connections which frequently cut off?

Many wonder. Not least Sir Alan Sugar, chairman of Amstrad/Viglen, at one time the parent company of the Danish mobile phone company DanCall. "Who wants to send e-mails from the middle of a field?", asks Sir Alan.

Many agree with Sugar that fiddling around with tiny buttons is not going to be a popular pastime. Those who say speech recognition, not tiny buttons, will be the input mechanism for portable Internet access aren't familiar with the inaccuracies of speech recognition. These require the frequent intervention of buttons for correcting the many errors.

With the technology at its current state of development, is Mobile Internet feasible?

Undoubtedly billions are being spent pursuing it. Marketing 'data' - often pretty spurious - abounds for supporting the proposition that 'by 2003 or 4 or even 5 more half the people accessing the Internet will be doing it from mobile terminals'.

How can these projections be believed? How can the people spending the billions sleep at nights? The reason could be that a very large number of people have a vested interest in making mobile datacommunications catch on. Not least the mobile phone manufacturers. How else can they escape the fate of the four-function calculator?

Back in the 1970s, the four-function calculator became a commodity. Its price tumbled from hundreds of dollars to ten dollars in a few years. The technical reason for that was the effect of the IC - the integrated circuit - then a ten-year old invention but doubling in transistor count every year.

The mobile telephone could easily go the same way as the four-function calculator. The technical reason for that happening is the effect of SOC, or system-on-chip, which is fast becoming possible in most types of consumer product. When you can put the electronic innards of a mobile phone on one chip, the cost of a mobile phone will plummet.

There is, of course, a way of avoiding the nightmare. You can add functionality to the mobile phone. When the makers of calculators were threatened by commoditisation, they added a host of



increasingly sophisticated and exotic functions ending up with such esoteric capabilities as div, grad and factorial.

So complicated were some of HP's calculators that, it was said, even PhDs only used 30 per cent of their functionality.

And PhDs do not make a mass market. The mass market wanted only the original four functions: add, subtract, multiply and divide. The attempt to move the mass market to accept - and pay for - more sophisticated functions failed.

The PC fared better. Terrified that commoditisation would happen to it, the PC industry succeeded for a couple of decades in avoiding price declines by having Microsoft produce ever more code-heavy operating systems. These required Intel to produce faster and faster processors and the DRAM-makers to produce denser and denser DRAMs.

Those strategies ensured that, for 20 years, the PC industry successfully averted the commoditisation process as the consumer bought more and more of this increasingly sophisticated - and sometimes functionally superfluous - kit. Mainstream PCs were \$1000 twenty years ago and are \$1000 now. That's a very clever trick to have pulled off.

Now it is the mobile phone that stands at the crossroads. One road leads to simplicity, commoditisation and declining profits, the other to complication, added value and high profitability. I wonder which will it be?

David Manners

### EDITOR

Martin Eccles  
 020 8652 3614

### CONSULTANTS

Ian Hickman  
 Philip Darrington  
 Frank Ogden

### EDITORIAL ADMINISTRATION

Jackie Lowe  
 020 8652 3614

### EDITORIAL E-MAILS

jackie.lowe@rbi.co.uk

### GROUP SALES EXECUTIVE

Pat Bunce  
 020 8652 8339

### ADVERTISEMENT E-MAILS

pat.bunce@rbi.co.uk

### ADVERTISING PRODUCTION

020 8652 8339

### PUBLISHER

Mick Elliott

### EDITORIAL FAX

020 8652 8111

### CLASSIFIED FAX

020 8652 8938

### NEWSTRADE ENQUIRIES

020 8261 7704

### ISSN 0959-8332

For a full listing of  
 RBI magazines:  
<http://www.reedbusiness.com>



### SUBSCRIPTION HOTLINE

Tel, (0) 1444 475662  
 Fax, (0) 1444 445447

### SUBSCRIPTION QUERIES

rbp.subscriptions@rbi.co.uk  
 Tel 01444 445566  
 Fax 01444 445447

**Electronics World** is published monthly. By post, current issue £2.65, back issues (if available) £3.00. Orders, payments and general correspondence to **L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**. Tlx: 892984 REED BP G. Cheques should be made payable to Reed Business Information Ltd

**Newstrade:** Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108.  
**Subscriptions:** Quadrant Subscription Services, Oakfield House Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address.  
 Subscription rates 1 year UK £36.00 2 years £58.00 3 years £72.00. Europe/Eu 1 year £51.00 2 years £82.00 3 years £103.00. ROW 1 year £61.00 2 years £98.00 3 years £123

**Overseas advertising agents:** France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Roy Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel; (212) 679 8888 Fax; (212) 679 9455

**USA mailing agents:** Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

**Printed by** Polestar (Colchester) Ltd, **Filmsetting by** JJ Typographics Ltd, Unit 4 Baron Court, Chandlers Way, Southend-on-Sea, Essex SS2 5SE.

© Reed Business Information Ltd 1997 ISSN 0959 8332



Over 50%  
Discount

Professional Electronics Design

EDWIN NC


Over 50%  
Discount

- Genuine, professional EDA software *with no limitations!* - and **YOU** can afford it!
- EDWin NC comes from Visionics: one of the *longest established, most experienced* producers of professional EDA systems, so it's fully proven in professional work.
- Now you can have this best-selling non-commercial version of the software at less than **50% of the normal price**, with no limits in its capabilities.
  - *It does just about everything you could want!*

Schematics, simulation, PCB layout, autorouting, manufacturing outputs, EMC and Thermal Analysis.

Many more advanced features are available and it runs in Windows 3.x, 95, 98 or NT.

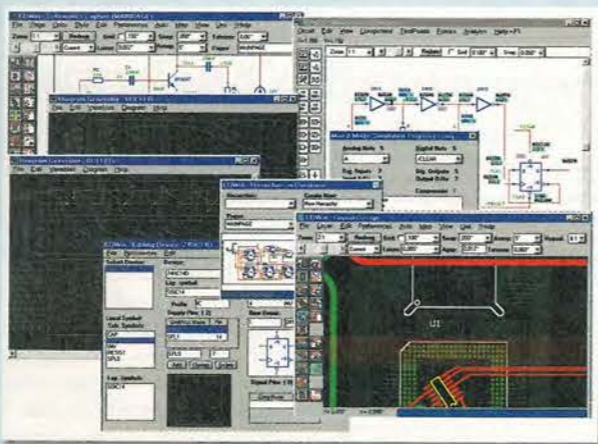- **Where's the catch?** It's for non-commercial use, but companies may order for evaluation purposes. Prices start from just £59.00 for the basic system!



**New**  
Super Powerful 32 bit  
version for Windows 95,  
98 & NT!



Don't forget - Phone Today for Your 50% Discount!

- **EDWin NC Basic:** Schematics, PCB Layout, Manufacturing Outputs, Max. 100 Component Database, 500 Device Library.
- **EDWin NC De Luxe 1:** Basic + Professional Database and Libraries, Arizona Autorouter.
- **EDWin NC De Luxe 2:** De Luxe 1 + Mix-Mode Simulation, Thermal Analyser.
- **EDWin NC De Luxe 3:** De Luxe 2 + EDSpice Simulation, EDCoMX Spice Model Generator, EMC and Signal Integrity Analysers.

Plus Postage & Packing UK £5.00; Rest of World £10.00 (only one charge per order)

Order hotline: +44 (0)1992 570006 Fax +44 (0)1992 570220 E-mail: [swift.eu@dial.pipex.com](mailto:swift.eu@dial.pipex.com)

Please Visit Our Web Site <http://www.swiftdesigns.co.uk>



I enclose: £.....total.

We aim to dispatch as soon as we receive payment, but please allow 28 days for delivery. Subject Unsold.

Cheque/PO/Credit Card:

Visa/Mastercard/Eurocard: No.

\_\_\_\_\_

Issue Date: \_\_\_\_\_ Expiry Date: \_\_\_\_\_

Date: \_\_\_\_\_ Signature: \_\_\_\_\_

Name: \_\_\_\_\_

Address: \_\_\_\_\_

\_\_\_\_\_

Postcode: \_\_\_\_\_

Tel.: \_\_\_\_\_ Evenings: \_\_\_\_\_

I wish to order:

- EDWin NC BASIC: £59.00 16 bit / £119.00 32 bit
- EDWin NC De Luxe 1: £119.00 16 bit / £177.00 32 bit
- EDWin NC De Luxe 2: £155.00 16 bit / £212.00 32 bit
- EDWin NC De Luxe 3: £285.00 16 bit / £340.00 32 bit

Postage & Packing UK

£5.00

Rest of World

£10.00

(only one P&P charge per order) Total £

Qty.	Total (£)
16 bit/32bit	



Swift Eurotech Ltd.,  
Twankhams Alley, 160 High Street,  
Epping, Essex, CM16 4AQ, UK.

CIRCLE NO. 105 ON REPLY CARD

# UPDATE

## Athlon outdoes Pentium III in 800MHz benchmark tests

The processor war between AMD and Intel has intensified following benchmark results that claim AMD's Athlon is up to twice as fast as Intel's Pentium III in certain situations.

The tests on 800MHz processors, carried out by Bert McComas of Inquest Market Research in the US, also show that virtual-channel DRAM is far better in many cases than standard synchronous or Rambus DRAM.

McComas tested several system configurations based on AMD's and Intel's 800MHz processors. Chip sets were from either Intel or VIA Technologies, the former supporting Rambus, 133MHz SDRAM (PC133) or virtual channel (VC133), the latter PC133 or VC133.

Using LinPack (see diagram) and StreamD benchmarks, McComas showed Athlon to be 50 per cent or more faster than Pentium III.

"Athlon's consistently high DRAM throughput is related to its CPU bus characteristics. At 200MHz it is much more capable of extracting the untapped performance (headroom) of PC133 and Virtual Channel SDRAM," the report stated.

Rambus and PC133 showed little difference on those metrics.

The Inquest report also examined the bottleneck caused by the graphics accelerator.

In his report, McComas said: "As 3D benchmarks are used to

evaluate CPU, chipset and DRAM performance, it has become common practice to crank down the screen resolution, colour depth and image quality features to their minimum. On the surface, this may seem logical, but in effect the hottest, fastest PCs on earth are being benchmarked at 1997 screen resolutions."

Therefore he tested the different systems using a high-end Creative Labs board based on nVidia's GeForce graphics chip.


The 3D tests used a Quake3 test program, setting resolution and image qualities to both their highest and lowest settings.

At the lowest settings, AMD comes out worst, due said McComas to its lower speed level two cache. At the highest resolution though, there was no difference between the various systems. Why? Because the bottleneck that is the graphics card completely chokes the system, says McComas.

Indeed, clocking either processor at just 400MHz caused graphics frame rates to drop by just two per cent. Overclocking the graphics chip - up to 140MHz from 120MHz - saw performance rise by 15 per cent, even though the CPUs were running at half speed, proof that graphics is a bottleneck.

The moral of this story - spend your cash on the graphics card and chipset, not the processor.

Richard Ball *Electronics Weekly*

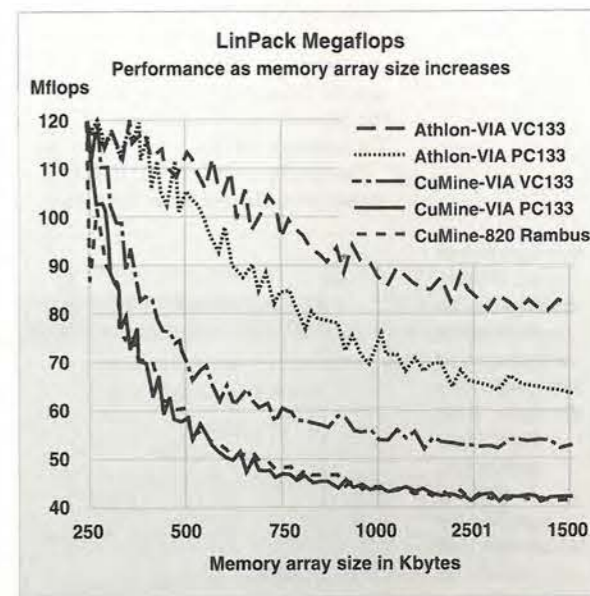

In the LinPack benchmark, which tests the combination of floating point performance, bus bandwidth and memory performance, Athlon outdoes Pentium III (CuMine) by a considerable margin - a factor of nearly 2x for larger data sets. Virtual-channel memory, on either processor, outperforms PC133 and Rambus. Intel's speed drops quickly as data array sizes increase, AMD is less affected.



## New substrate for high-speed processing

A group of ex-Intel workers has developed a method of reducing problems with electrical noise, clock skew, bus speed, and soft errors in high speed microprocessors.

Their start-up firm, Primarion, plans to split a processor's power grid into small independent sections. The die is then bonded to another silicon substrate which provides power regulators for each section of the circuit.

Such a system would improve the quality of the power supply, reducing problems such as ground bounce. Response times to current changes could improve by a factor of 100, the firm claims.

Clocks would also be sent to the processor chip via the substrate, reducing clock skew, noise and crosstalk. Noise could also improve by 100.

Circuits on the substrate will be

built using heterojunction bipolar transistors (HBTs) to improve the quality of power and clocks, which are essentially analogue.

Primarion expects its technology will be in widespread use within five years.

In order to develop the technology it has garnered \$13m in venture funding, mainly from Intel's \$8bn venture fund. The firm has also bought a bipolar fab from Lansdale in Arizona.



## Chip transistors shrink to 50nm in the bid for faster, cheaper silicon

The incredible shrinking transistor has done it again, this time at the hands of Silicon Valley firm Numerical Technologies (NumeriTech) which has produced 50nm (0.05µm) transistors using conventional 248nm optical lithography.

The devices, claimed to be the smallest ever fabricated using optical lithography, were made at the Massachusetts Institute of Technology (MIT).

Using phase-shift mask (PSM) techniques, the previous limit for

248nm lasers was thought to be 100nm feature sizes. Getting to 70nm and below was the realm of 157nm lasers.

"People have been predicting the end of optical lithography for several years, saying that it can't extend beyond 100 nanometers," said Y.C. Pati, president and CEO of NumeriTech. "The MIT Lincoln Laboratory results prove that with prudent use of phase shifting, optical lithography can be extended much further than anyone ever thought was possible."

Beyond the 100nm mark, it was expected that new techniques such as ion-beam lithography would be used to pattern silicon wafers.

If NumeriTech's 50nm technique can be commercialised, it could lead to faster and cheaper chips without the need for developing advanced chip manufacturing techniques to create smaller transistors.

However, PSM cannot get features much closer together because of the interference fringes close to the desired transistor, so you get fast, but not necessarily compact, devices.


PSM relies on the fact that a coherent imaging system will create interference as the laser is diffracted as it passes through the mask. The effect can be used to reduce the spatial frequency of a given object or to enhance its edge contrast.

Both resolution and depth of field of the image can be improved.

To shift the light phase, an extra layer of transmissive material with a different refractive index is needed on the mask.

NumeriTech designs the software that modifies the chip layouts to make use of optical proximity correction and PSM. It is already being used by firms such as Lucent and Motorola to produce features down to 120nm, or 0.12µm.

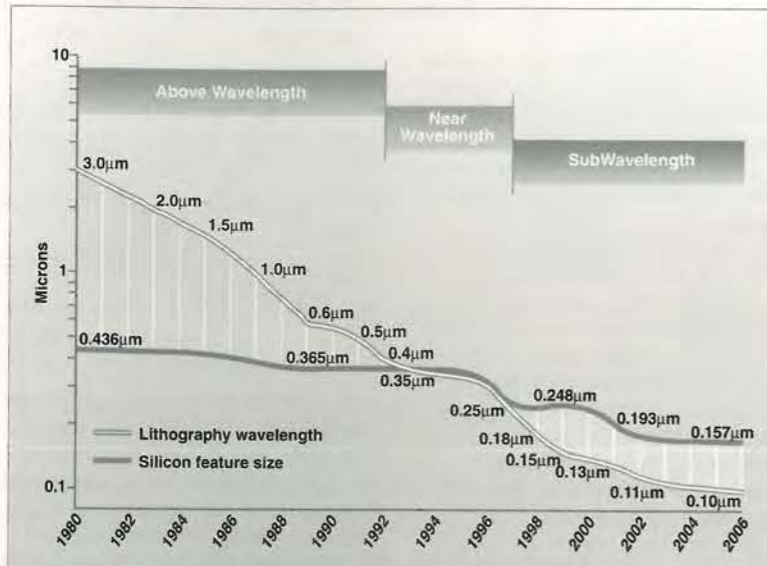Sub-wavelength era... Feature sizes used to be larger than the wavelength of light patterning the wafer. With the 0.35µm generation, features equalled the wavelength, but today, at 0.18µm, features are smaller than the 248nm laser light used.



## Electronic tagging for consumer goods?

RF tagging chips will be taking an active part in the fight against crime if a government Home Office initiative takes off.

"We must use every means at our disposal, including the latest technology, to see how it can best be used or developed to cut crime and make our communities safer," said Home Office minister Charles Clarke at the recent 'Chipping the Goods' seminar.

The plan is to electronically tag equipment by embedding a passive RF tagging device into consumer goods such as TVs, computers and cameras. The chip would carry information about the equipment and its owner. The information stored in the device can be changed in situ using RF technology and can be read remotely when required.

The technology is referred to as RF ID and devices are being developed by several companies including Texas Instruments, Philips, Oxley


and Gemplus of France.

The technology should also allow companies to track goods more effectively and so reduce stock losses as the information written to it will specify its last official location. "This is new technology which the Home Office is looking to encourage industry to make use of in protecting its property," said Martin Swedlow, chief executive of IT consultants Integrated Product Intelligence which is involved in organising trials of the tagging.

● The first UK licence for spectrum for an Asset-Tracking Mobile Data Network has been awarded by the Radiocommunications Agency to QNL (UK).

The licence is for the 866-868MHz range, which is causing concern to industry body The Low Power Radio Association, which fears it may cause interference with equipment offered by its members.

Melanie Reynolds *Electronics Weekly*

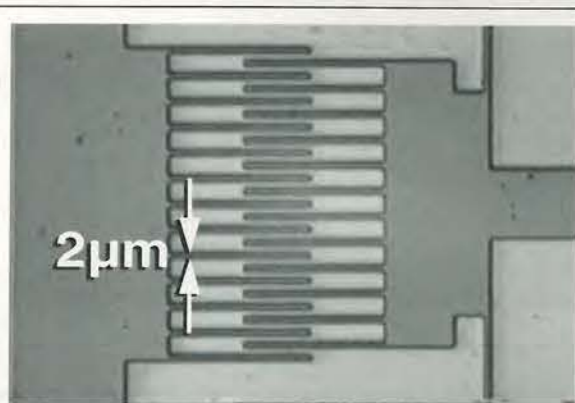

**Diamond micromachines:** Sandia National Laboratories in the US has created what it believes are the world's first diamond micromachines. The comb drive is constructed from etched amorphous diamond – the second hardest substance behind crystalline diamond. It is a better material than silicon because it is wear resistant. In addition, it is not rejected by the human body so it could be used for medical biochips. "Micromachines, for their marvellously tiny size, are still machines. They're subject to wear, even if it's only at the micro level," said researcher Tom Friedmann. He believes diamond MEMS could last 10 000 times longer than silicon devices.

## TiePieScope HS801 PORTABLE MOST



ARBITRARY WAVEFORM GENERATOR-  
STORAGE OSCILLOSCOPE-  
SPECTRUM ANALYZER-  
MULTIMETER-  
TRANSIENT RECORDER-

# Reliability

- The sophisticated cursor read outs have 21 possible read outs. Besides the usual read outs, like voltage and time, also quantities like rise time and frequency are displayed.
- Measured signals and instrument settings can be saved on disk. This enables the creation of a library of measured signals. Text balloons can be added to a signal, for special comments. The (colour) print outs can be supplied with three common text lines (e.g. company info) on three lines with measurement specific information.
- The HS801: the first 100 Mega samples per second measuring instrument that consists of a MOST (Multimeter, Oscilloscope, Spectrum analyzer and Transient recorder) and an AWG (arbitrary waveform generator). This new MOST portable and compact measuring instrument can solve almost every measurement problem. With the integrated AWG you can generate every signal you want.
- The versatile software has a user-defined toolbar with which over 50 instrument settings quick and easy can be accessed. An intelligent auto setup allows the inexperienced user to perform measurements immediately. Through the use of a setting file, the user has the possibility to save an instrument setup and recall it at a later moment. The setup time of the instrument is hereby reduced to a minimum.
- The minimum system requirement is a PC with a 486 processor and 8 Mbyte RAM available. The software runs in Windows 3.xx / 95 / 98 or Windows NT and DOS 3.3 or higher.
- TiePie engineering (UK), 28 Stephenson Road, Industrial Estate, St. Ives, Cambridgeshire, PE17 4WJ, UK Tel: 01480-460028; Fax: 01480-460340
- TiePie engineering (NL), Koperslagersstraat 37, 8601 WL SNEEK The Netherlands Tel: +31 515 415 416; Fax +31 515 418 819
- When a quick indication of the input signal is required, a simple click on the auto setup button will immediately give a good overview of the signal. The auto setup function ensures a proper setup of the time base, the trigger levels and the input sensitivities.



CIRCLE NO. 106 ON REPLY CARD



## Researchers develop self-assembling micro-wires for multi-chip modules

Self-assembling micro-wires could form the basis of a new interconnection system for multi-chip modules.

Researchers at Leeds University formed the wires from stacks of disc-shaped molecules in a 'discotic' liquid crystal. These stack themselves under certain conditions to form columns like piles of plates, as in the diagram below

Stacking on any flat surface can be provoked predictably, forming a

forest of independently-conducting wires like bristles on a brush. "The molecules will generally orient on anything," said Professor Richard Bushby of the Leeds team developing the technology.

Conductivity along the wires comes from a graphite-like six-atom carbon ring in the centre of each molecule. These can lose an electron leaving a hole which, once the molecules are stacked, can migrate up the centre of the column. Surrounding polythene-

like hydrocarbon chains form the wire's insulator.


If two chips are positioned face to face with a small gap between them, any conducting pad on one chip will be connected to a corresponding conducting pad on the other once the space is filled with the liquid crystal. Insulating layers on the chip surface prevent conduction where it is not wanted.

At the moment, pads 10µm across have been connected. Bushby expects this to be reduced to sub-micrometre levels in the future.

Resistance is a problem. "We have improved it by a couple of powers of ten over the last two years and need a couple more powers of ten," said Bushby.

The Leeds team is to receive a share of a £1.5m grant from the EU as part of a 3D-chip programme. Other members are: the University of Delft, which is developing ways to produce conducting vias through chips, CNRS in Paris, which is working on a conductive polymer interconnection system to achieve the same ends as Leeds, and University College London which is looking at some related visual image processing techniques.

Steve Bush *Electronics Weekly*

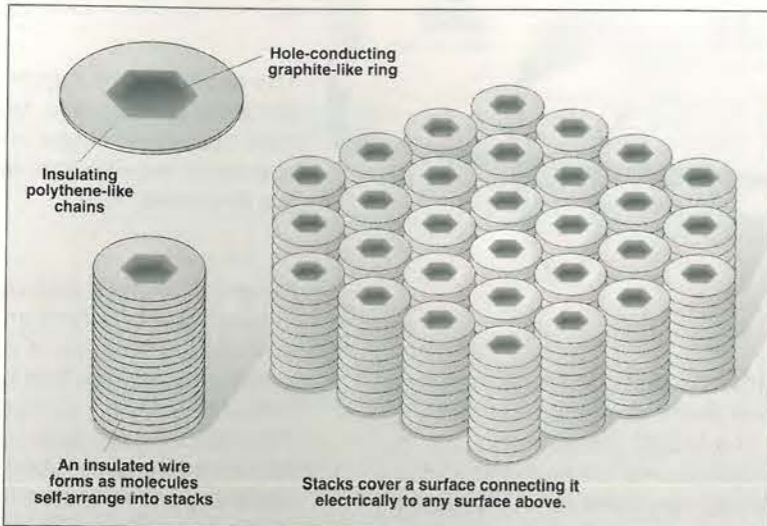

## Digital watermarking finds its way into maps

Signum Technologies has done a deal with Ordnance Survey to apply its digital watermarking technology to the OS's library of digital maps.

"Some people think they can just copy a map, use it commercially and get away with it," said Carl

Calvert, from the OS's intellectual property division.

While the OS is self funded, any shortfall in revenue if made up from taxpayer's money.

"It's one thing to photocopy a map so someone can find you easily. It is quite another to use the

information that costs us millions of pounds every year to provide and then use it commercially and unlicensed," said Calvert.

Signum's 'watermarks' can show when an image has been copied, even if all the colours are changed and content is removed or added. ■



Now you see it... Similar technology from Signum to the one it is using in the Ordnance Survey watermarking technology is seen above being applied to a speeding biker (allegedly). The left-hand image shows how changes to the bike's registration plate and speed, and removal of the car to the left have been spotted by the software.

## PROFESSIONAL Development Tools

from Milford Instruments

Milford Instruments Tel 01977 683665, Fax 01977 681465  
www.milinst.demon.co.uk info@milinst.demon.co.uk  
Milford House, 120 High Street, South Milford, LEEDS LS25 5AQ



### PIC Emulators from Tech Tools

Mathias In-Circuit Emulator  
● 16C5X to 20MHz  
● 16CXX to 25MHz and data breakpoints  
● Modular design  
● True Integrated Windows Environment  
● Supports standard assemblers and compilers  
● True Bondout Chip set based  
● Programmers and adaptors also available  
Full details at [www.tech-tools.com](http://www.tech-tools.com)

### BASIC Stamps

Still the easiest and fastest way to get your project up and going. 8 or 16 I/O pins, easy-to-read BASIC instructions plus on-board comms and simple interfacing to peripheral chips.



### ROM Emulators from TechTools



EconoROM, FlexROM and UniROM

- Fast ROMs - 45ns and 35ns access times
- Fast download (up to 2.5Mbit/sec)
- Readback, Verify and Selftest modes
- Full editor and utilities included
- Full details and demo software at [www.techtools.com](http://www.techtools.com)
- Live editing (UniROM only)
- 8bit & 16bit up to 32Mbit
- EPROM, FLASH and SRAM emulation

### Scenix Emulators from Parallax



### SX-Key Emulator

SX chips are EEPROM based, PIC16C5x pin compatible micros with up to 100mips performance.  
● Full speed debugging on production chips  
● Integrated Windows environment  
● Software configured oscillator  
● 18 to 52 pin reprogrammable devices  
● SX Blitz low cost programmer also available. Full details and software at [www.parallaxinc.com](http://www.parallaxinc.com)



**New to PICs or just wanting to learn new tricks?**  
We stock the excellent Square1 series of PIC primers. See our web site for contents.



**SERIAL LCDs reduce display hassle.**  
We stock a range of alphanumeric and graphic displays all fitted with serial RS232 interface boards - 2x16 to 4x40 and up to 128x64 graphics size.  
**RS232 data entry terminal unit also available**

CIRCLE NO.107 ON REPLY CARD

## GET EXPERT HELP!

### IAN HICKMAN TITLES 3-FOR-2 OFFER FROM NEWNES!

With a lifetime's experience in industry and as a leading technical writer, Ian Hickman is well known for his practical and useful advice. Having his books on the shelf is like having an expert at your side.



To celebrate Ian Hickman's long association with Newnes and Electronics World magazine we are delighted to offer **3 of Ian's books for the price of 2.**

**You will always find it easier to stay ahead of the rest if you rely on Hickman and Newnes!**

- Hickman's Analog and RF Circuits: 0 7506 3742 0 £25.00
- Analog Circuits Cookbook 2/e: 0 7506 42343 £24.99
- Practical Radio Frequency Handbook 2/e: 0 7506 3447 2 £19.99
- Analog Electronics 2/e: 0 7506 4416 8 £24.99
- Digital Storage Oscilloscopes: 0 7506 2856 1 £25.00
- Oscilloscopes 4/e: 0 7506 2282 2 £18.99
- EDN Designers Companion: 0 7506 1721 7 £30.00

Order your books by any of these 4 easy ways specifying the 2 books you would like to buy and the one you would like for FREE.  
Please make cheques payable to: Heinemann Publishers Oxford

By E-mail: email us on [bhuk.orders@repp.co.uk](mailto:bhuk.orders@repp.co.uk) quoting reference: T002TXAA01

By Phone: call us on 01865 888180 quoting reference: T002TXAA01

By Fax: fax us on 01865 314572 quoting reference: T002TXAA01

By Mail: write to Emma Hales, Butterworth-Heinemann, Linacre House, Jordan Hill, Oxford OX2 8DP

Visit us at [www.newnespress.com](http://www.newnespress.com) for a complete online catalogue

CIRCLE NO.108 ON REPLY CARD





**This programmable load tester for 12V sealed lead-acid and NiCd batteries covers twenty of the most popular capacities from 0.8 to 7Ah. Designed by Dave Sawford and Ken Duggan, it features an automatic test procedure, it has a load tolerance of better than 2% and it includes a DVM function with 0.3% measurement error.**

# Verify batteries to 7Ah

The function of backup batteries is to provide power to the system in the event of mains supply failure. In UPS, telecomms and alarm systems, sealed lead-acid batteries are the most popular because they offer good combinations of size, energy density per unit volume and cost.

However, batteries and related charging circuits remain common sources of failure – especially in alarm systems. Charging circuits are statistically more reliable than sealed lead-acid batteries, as correctly applied modern semiconductors typically last at least three times longer than even the most advanced batteries.

Testing such batteries gives multiple benefits, especially in the alarm industry; fewer call-outs for the installer,

police, site owners' etc., and fewer claims for the insurers. Testing identifies both weak and healthy batteries, reducing the chances of failure. It also allows you to make the best use of what is both a resource and, at the end of its service life, a source of pollution. Most batteries now being classified as special waste.

There are only two methods of testing sealed lead-acid batteries. Firstly you can measure the battery's internal resistance. By inference, a battery with a high internal resistance cannot deliver power.

Alternatively, you can evaluate a lead-acid battery using load testing. Here, the battery delivers power to a load and the voltage is monitored. Demonstrating that a battery can deliver

power for the required time increases confidence that it can perform to an almost identical level in the immediate future.

## A testing problem

Taking the example of a 12V, 7Ah battery, such a battery could theoretically be tested by connecting a  $12 \div 7 = 1.71\Omega$  resistor, which would allow 7A to flow; the 1C rate of this battery, hence a '1C' load test. If the battery voltage fell below 12V during the test, the battery would be failed.

Any size of sealed lead-acid battery can be tested in this manner, the load resistor value simply being calculated by Ohm's law. However, for each capacity of battery, a different resistor is required. Also, a nominal '12V' bat-

tery may have a start-of-test voltage of 13.8V causing, in this example, an initial current flow of  $13.8 \div 1.71 = 8.07A$ .

Taking in to account the 5-10% tolerance of the power resistor, the result is a worst case figure of 8.97A.

## A PIC based solution

The tester described here enables twenty of the most popular capacities of sealed lead-acid battery to be tested by applying an accurate constant current load. Yuasa recommends a minimum test of 1 minute at a 1C rate, and specify that the voltage should not drop below 12V.

The circuit is based on the cheap and versatile Microchip PIC16C74A. This device allows you to build a sophisticated but easy to use test instrument using very few components, thanks to features such as the on-board five-channel eight-bit analogue to digital converter. The block diagram of the tester is shown in Fig. 1.

As well as controlling the load, the PIC also directly controls four 7-seg-

## Important safety issues

There are safety concerns that influenced the design of the circuit, and these are due to the nature of the batteries being tested. Although they might be tested at currents of up to 7A, the batteries involved here can deliver many times more.

Uncontrolled current flow could cause arcing, which might damage the test lead clips. In a worst-case scenario, the power dissipated could be a fire hazard.

For these reasons, three considerations were taken into account. Whenever the unit is switched off, the load must be inactive. This applies whether the test lead clips are connected before the unit is turned on, or if the unit is turned off during a test.

At the first sign of a bad connection to the battery under test, the load must be swiftly de-activated.

Accidentally connecting the test leads with the wrong polarity must not cause any damage to either the tester or the battery under test.

## Specifications of the battery monitor

Battery types tested	12V sealed lead-acid and NiCd
Battery capacities tested (C)	0.8, 1.0, 1.1, 1.2, 1.8, 2.0, 2.1, 2.3, 2.5, 2.8, 3.0, 3.2, 3.5, 4.0, 4.5, 5.0, 5.7, 6.0, 6.5, 7.0 Ah
Test type	60s partial discharge at 1C
Fail threshold	11.75V
Voltage measurement tolerance	0.3%
Voltmeter range	3-13.8V
Voltmeter resolution	0.054V
Load voltage range	9-13.8V
Load tolerance	Better than 1.7% @ 7A, typically $\pm 5-15mA$
Power consumption, typical	40mA, approx.
Internal battery low level warning	7.6V

ment multiplexed displays and three indicator LEDs to show what is being displayed – current, voltage or time. The controller also responds to select, stop and start controls, and monitors the voltage of the battery under test. In addition it checks its own battery and keeps an eye on the load temperature while it is active.

The adjustment links allow a 2.5% increase or decrease in the load current to counteract inaccuracies in the current measuring circuit. A buzzer gives an audible indication of the end of a test, or a problem with the load temperature. It is also used to make a click when a control key is pressed or if a held down key is auto-repeating.


## Constant-current loading

The principle of the constant current load used for the tester is shown in Fig. 2.

Resistor  $R_1$  is the main load resistor, and  $T_{r1}$  actively controls current drawn from the battery. The comparator shown represents the way the PIC interacts with the circuit and is not physically present. Switch  $S_1$  is electronic, controlled by the PIC.

Voltage across  $R_1$ , namely  $V_1$ , is directly proportional to the current flowing through it. This allows the PIC software to make a comparison with a reference value, corresponding to the desired  $V_1$ , hence the desired current load.

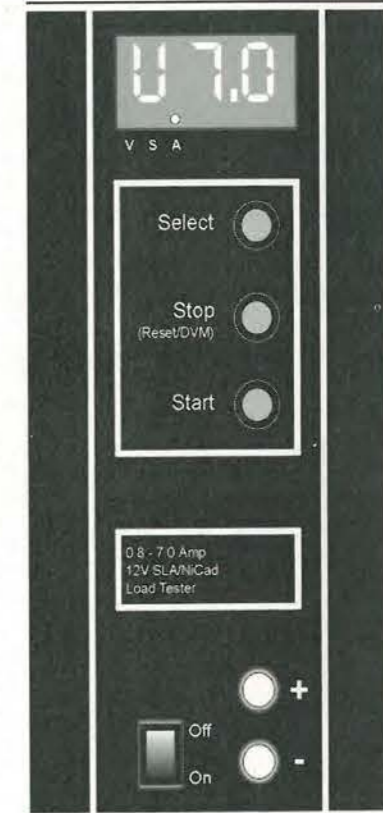By simply closing  $S_1$  if  $V_1$  is below



Front panel of the prototype battery tester.

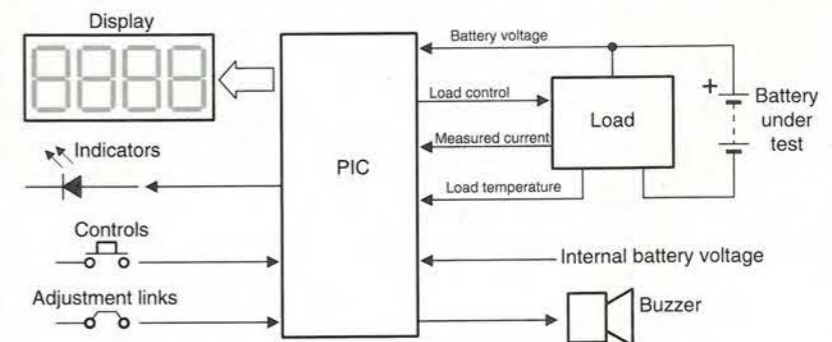


Fig. 1. At the heart of the tester is a PIC microcontroller, which evaluates the battery being tested. Having a five-channel analogue-to-digital converter built in, this controller greatly simplifies the monitor's design.







Table 1. The i/o pins of the PIC controller are designated as follows.

Pin	Name	Description
<b>Port A</b> All used pins configured as analogue inputs		
2	RA0	Load current. Voltage is 0.47 x the load current.
3	RA1	Voltage of the battery under test.
4	RA2	Internal battery voltage monitor.
5	RA3	The voltage reference for the PIC's a-to-d module.
6	RA4	Not used
7	RA5	Load temperature monitor.
<b>Port B</b> All used pins configured as digital inputs with pull-up resistor enabled		
33	RB0	'Start' key
34	RB1	'Stop / Reset / DVM' key
35	RB2	'Select' key
36	RB3	Not used
37	RB4	+2.5% Load current adjustment
38	RB5	-2.5% Load current adjustment
39	RB6	Not used
40	RB7	Not used
<b>Port C</b> All pins configured as TTL outputs		
15	RC0	Display segment 'a'
16	RC1	Display segment 'b'
17	RC2	Display segment 'c'
18	RC3	Display segment 'd'
23	RC4	Display segment 'e'
24	RC5	Display segment 'f'
25	RC6	Display segment 'g'
26	RC7	Display segment decimal point
<b>Port D</b> All pins configured as TTL outputs		
19	RD0	'Current' indicator LED
20	RD1	'Time' indicator LED
21	RD2	'Voltage' indicator LED
22	RD3	Buzzer
27	RD4	'Units' LED display
28	RD5	'Tens' LED display
29	RD6	'Hundreds' LED display
30	RD7	'Thousands' LED display
<b>Port E</b> All pins configured as TTL outputs		
8	RE0	Load PWM output
9	RE1	Input enable
10	RE2	Not used

itself. The system clock is a 4.096MHz crystal, chosen so the processor executes 1024 instructions a millisecond. This means that timings can be calculated reasonably easily using binary arithmetic. The MCLR pin is the reset pin and should be kept high.

**The software**

The software can be broken down into four main areas.

**The 'pre-test' routine.** Referring to Fig. 4, this routine is where the interrupts and ports on the PIC are set up, variables initialised and the program goes into a loop where it waits for the user to press a key. Pressing the 'Select' key changes the test current, the 'Stop' key toggles to the 'DVM'

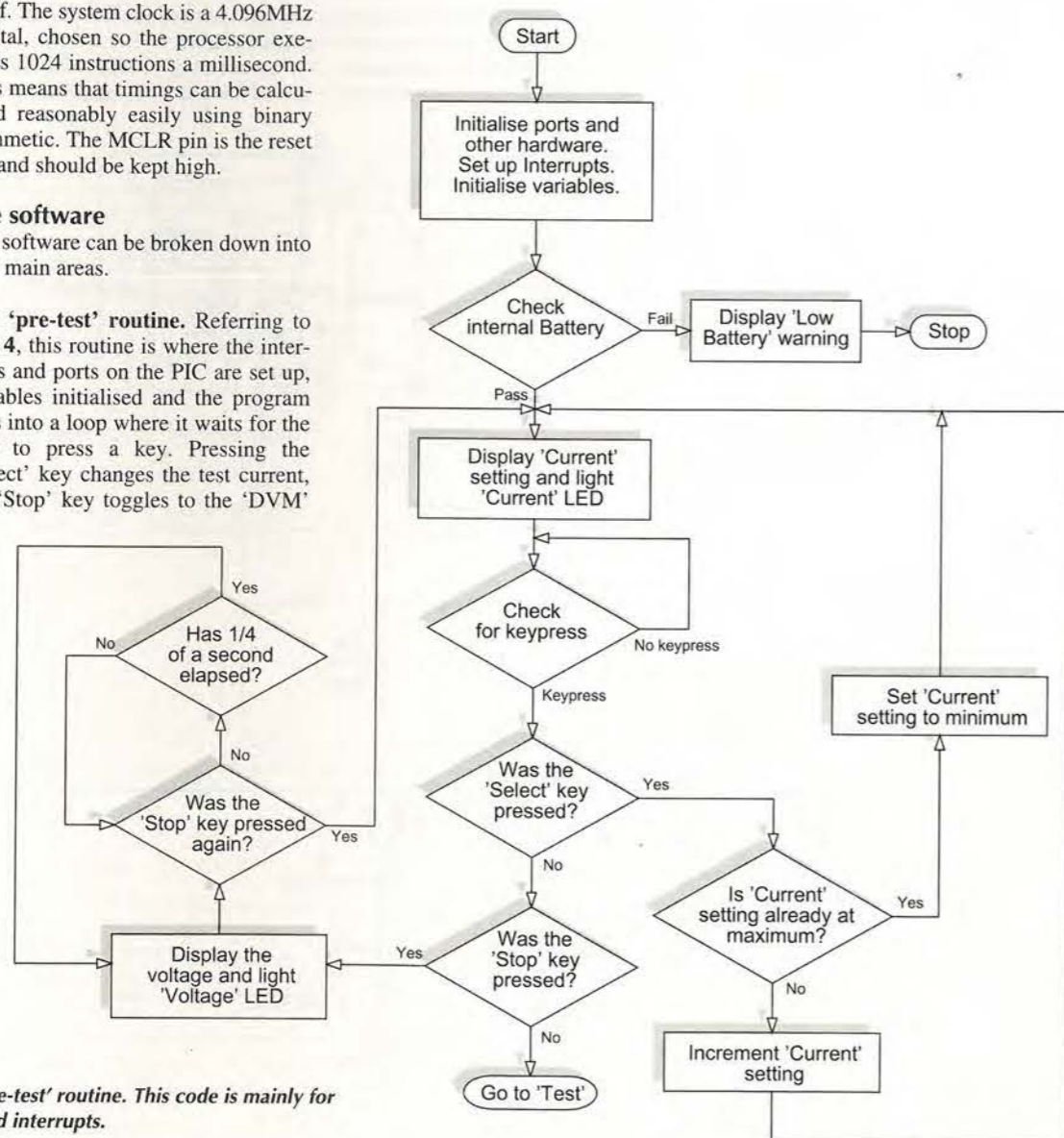


Fig. 4. Flow chart for the 'pre-test' routine. This code is mainly for setting up the PIC's ports and interrupts.

Table 2. ISR timing functions. The main program can use the bits of the interrupt register for its own timing requirements. 'Astable' bits toggle between 0 and 1 while 'monostable' bits need resetting by the main program routines.

Bit	7	6	5	4	3	2	1	0
Function	S	a	b	c	R1	R2	R3	R4

s: 1 second astable  
 a: 0.25 second astable  
 b: 0.25 second monostable 1  
 c: 0.25 second monostable 2  
 R1-R4: 0.25s bit rotation in the sequence R1 → R2 → R3 → R4 → R1...

mode where the voltage measured is continuously displayed and updated every quarter of a second, and the 'Start' key starts the test. The internal battery is also tested at this point.

**The 'test' routine.** This is the actual test, where the current specified by the user in the 'pre test' routine is drawn from the battery, Fig. 5. While this is happening the voltage, load temperature, time and keys are monitored. The user can change the display between 'battery save' mode where the only thing displayed is a moving dot (resulting in the internal battery drain of about 15 mA), display the elapsed time, the voltage of the battery under test (updated every quarter of a second), and the load current (set in the 'pre-test' routine) by pressing the 'Select' key.

**The 'post-test' routine.** The result of the test - 'PASS' or 'FAIL' - is displayed and the user can recall the time the test took for the battery to pass or fail, the final voltage measured before the battery passed or failed, and the load current, Fig. 6.

**The interrupt-service routine.** This routine, Fig. 7, provides time-critical routines. These allow other routines to operate without worrying how they will affect factors such as the load PWM signal or the overall timing of the test.

A 'clock' is provided by the interrupt-service routine. Routines in the main program can access this clock through a register, individual bits of that register making 0.25s and 1s monostables, a 0.25s astable and four bits that have a '1' rotated through them every second, Table 2.

The seven-segment displays are also driven by the interrupt-service routine. It switches between them 62 times a second, outputting the correct digit to each of the four displays in turn. The interrupt-service routine is also responsible for controlling the load.

Interrupts come from the PIC's internal TMR0 timer. This increments a register every instruction cycle (without pre-scaler). It produces an interrupt when it overflows from FF<sub>16</sub> to 00<sub>16</sub>.

The pre-scaler can be programmed so that the increments only happen every 2, 4, 8... 256 instruction cycles.

Communication between the interrupt-service routine and the main program is done through registers which the routine checks each time it is executed.

**Ancillary routines.** There are other

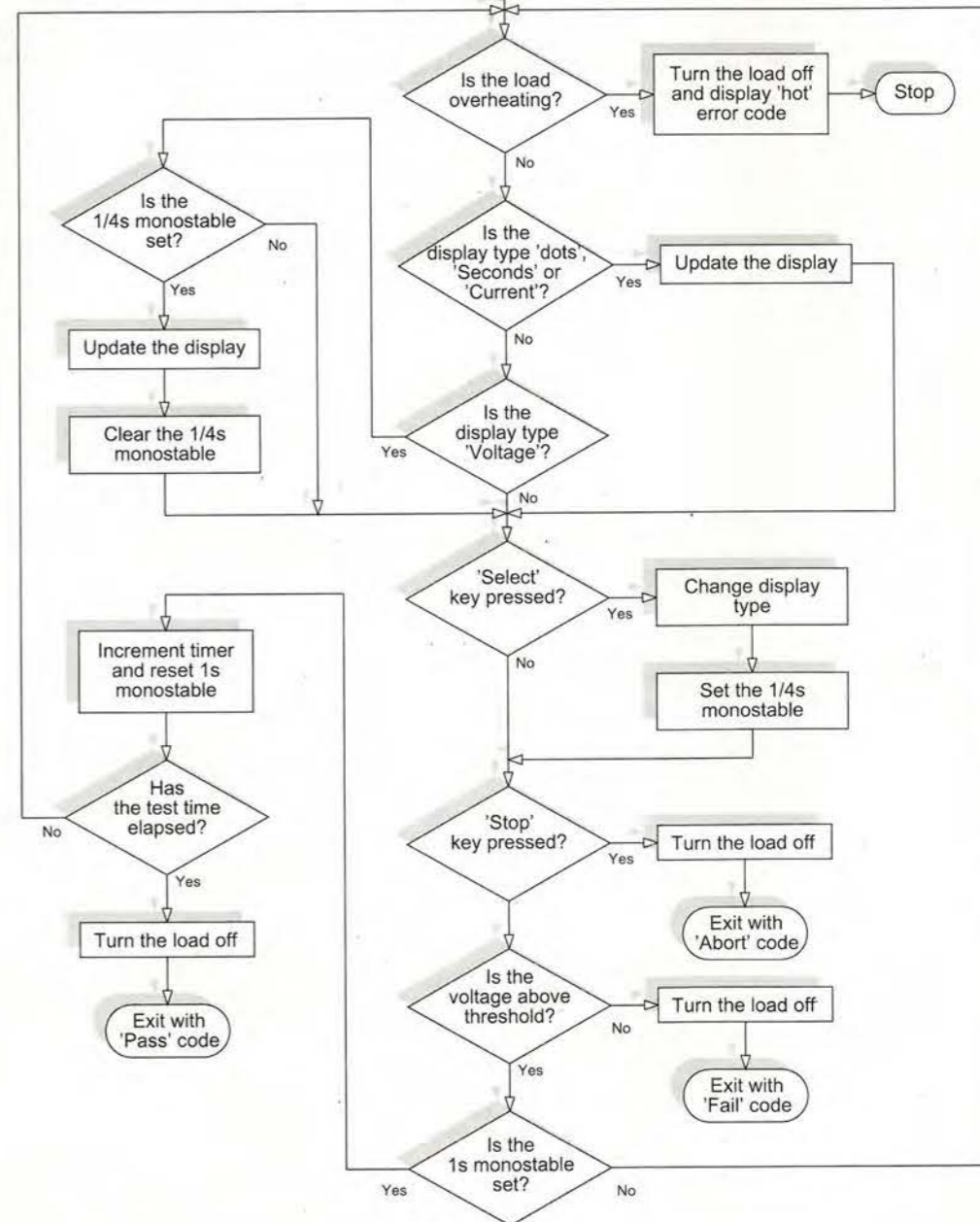


Fig. 5. The 'Test' routine puts the battery under load at a current specified by the user. During loading, voltage and temperature are measured and the keypad is checked.



common routines used by different parts of the main program. These perform tasks such as doing the a-to-d conversion, List 1, and reading the keys, Fig. 8.

The complete code for the tester is too large to reproduce here, but is available on the internet from

<http://www.the-shed.demon.co.uk/tester>

or by post as a hard copy or on floppy disk. Details of how to obtain technical support are given at the end of the article.

At just over 1500 lines of assembly code, the program is fairly large. When writing programs of this size there can be problems which do not occur in smaller programs.

**Controller usage notes**

**Stack depth.** The stack of the PIC 16C74A is only eight levels 'deep'. Each time a 'CALL' instruction is executed one of these levels is used up,

meaning that calls can only be nested seven times before things start going wrong.

Bear in mind that an interrupt uses the stack to store its return address. Also, if the interrupt-service routine performs an a-to-d conversion another stack level is used when the a-to-d subroutine is called.

These factors reduce the maximum number of nested calls the main program can use to five. It is very easy to accidentally go beyond this without noticing.

**Page boundaries.** Although the PIC 16C74A has a 13-bit wide address bus, only the lower 8 bits can be addressed when using computed look-up tables via the 'ADDWF PCL, F' command. This command adds the contents of the W register to the program counter.

The other 5 bits are loaded in from the PCLATH register when the 'ADDWF PCL, F' command is executed. For look-up tables, this effectively divides the memory into 256-byte pages, which they must not cross.

Probably the easiest way to avoid

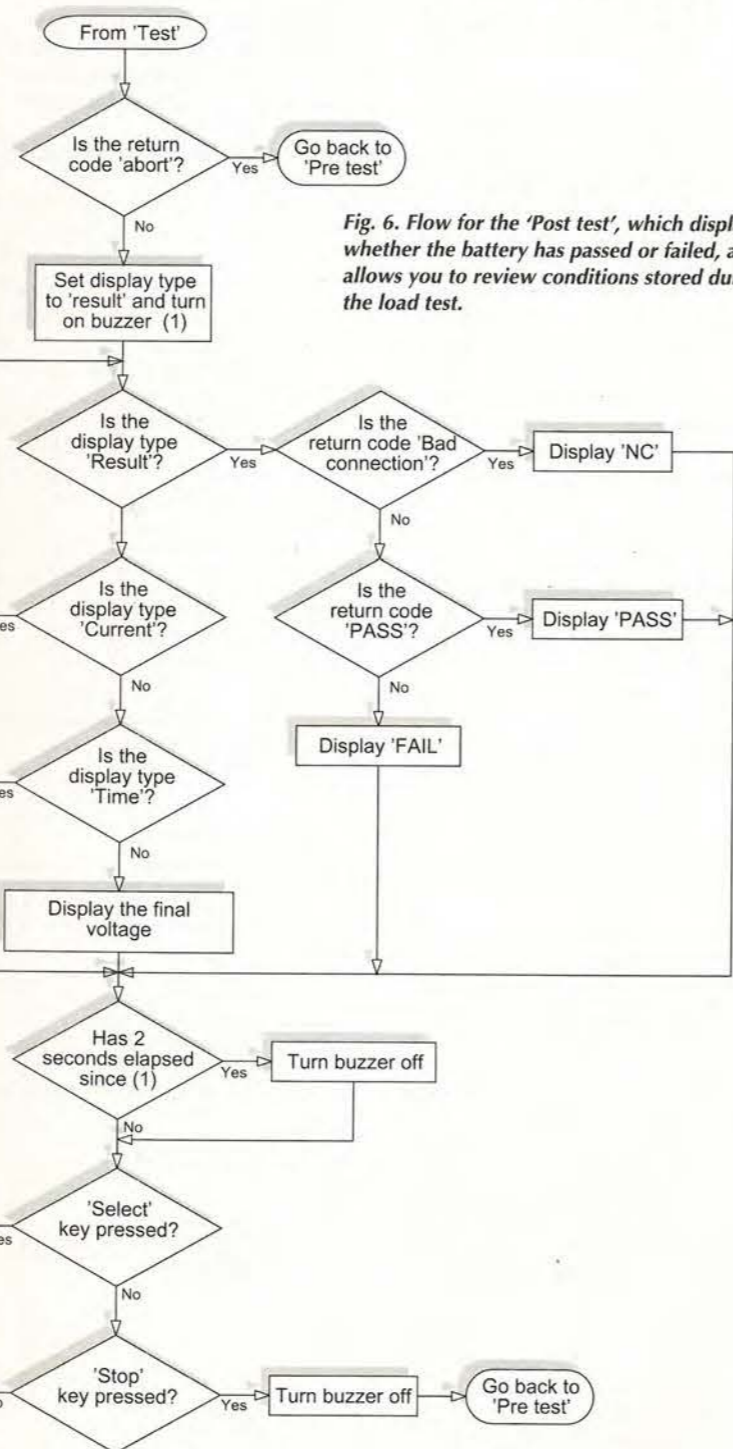


Fig. 6. Flow for the 'Post test', which displays whether the battery has passed or failed, and allows you to review conditions stored during the load test.

Table 3. The ADCON0 register is used to manage a-to-d conversion.

Bit	7	6	5	4	3	2	1	0
Function	ADCS1	ADCS0	CHS2	CHS1	CHS0	GO/DONE	-	ADON
Mnemonic	ADCS1, ADCS0							
Description	A-to-d clock select							
Mnemonic	CHS2, CHS1, CHS0							
Description	Analogue channel select							
Mnemonic	GO/DONE							
Description	A-to-d conversion status bit. Setting this bit starts the A-to-d conversion. On completion this bit is cleared by the a-to-d module.							
Mnemonic	-							
Description	Not used							
Mnemonic	ADON							
Description	Setting this bit turns on the a-to-d conversion module							

crossing these boundaries is to put all the look-up tables at the beginning of the code, before the main program. This makes it easier to check that no boundaries are crossed.

For look-up tables that are after the first 256 bytes of program memory, the PCLATH register must be used to set the upper 5 bytes of the program counter.

**More page boundaries.** A 'GOTO' or 'CALL' in the program only loads the program counter with the lower 11 bits of the address, meaning that calls only have a 1024-byte range. The other two bits needed to complete the 13-bit address are loaded from bits 3 and 4 of the PCLATH register.

If your program is over 1024 bytes long and uses calls to routines that are beyond the 1024/2046/3069 boundaries you must set the PCLATH 4:3 bits accordingly. The Microchip application note AN556 - available from the Microchip web site - has more details about these problems.

**The analogue to digital converter**

One of the most useful features of the 16C74A is the on-board a-to-d converter. Although it only has a resolution of 8 bits, used in conjunction with a precision voltage reference it allows accurate monitoring of many different parts of the circuit.

The reference voltage for the a-to-d - i.e. the voltage that a digital value of 255 from the a-to-d converter represents - can either be set up in software as the V<sub>SS</sub> supply voltage to the PIC or an external source.

As the tolerance of most 5V regulators is only 5%, an external 4.096V, 0.2% tolerance voltage reference, namely D<sub>2</sub>, is used in this circuit for improved accuracy in voltage measurements.

To convert a voltage to its corresponding digital value the following can be used,

$$D = \frac{V_{sample}}{V_{ref}} \times (2^n - 1)$$

where D is the digital value, V<sub>sample</sub> is the sampled voltage and n is the number

of bits of resolution of the a-to-d converter.

For the PIC 16C74A in this application,

$$D = \frac{V_{sample}}{4.096} \times 255$$

This circuit uses four of the PIC's a-to-d channels to monitor the following parameters:

**RA0:** Current flow through the load. For example, at 7A the voltage at RA0 is,

$$7A \times 0.47\Omega = 3.29V$$

So the value returned by the a-to-d conversion will be,

$$\frac{3.29}{4.096} \times 255 = 204.8$$

Note that as the PIC can only use integers, the actual value returned would be 204.

**RA1:** The voltage of the battery under

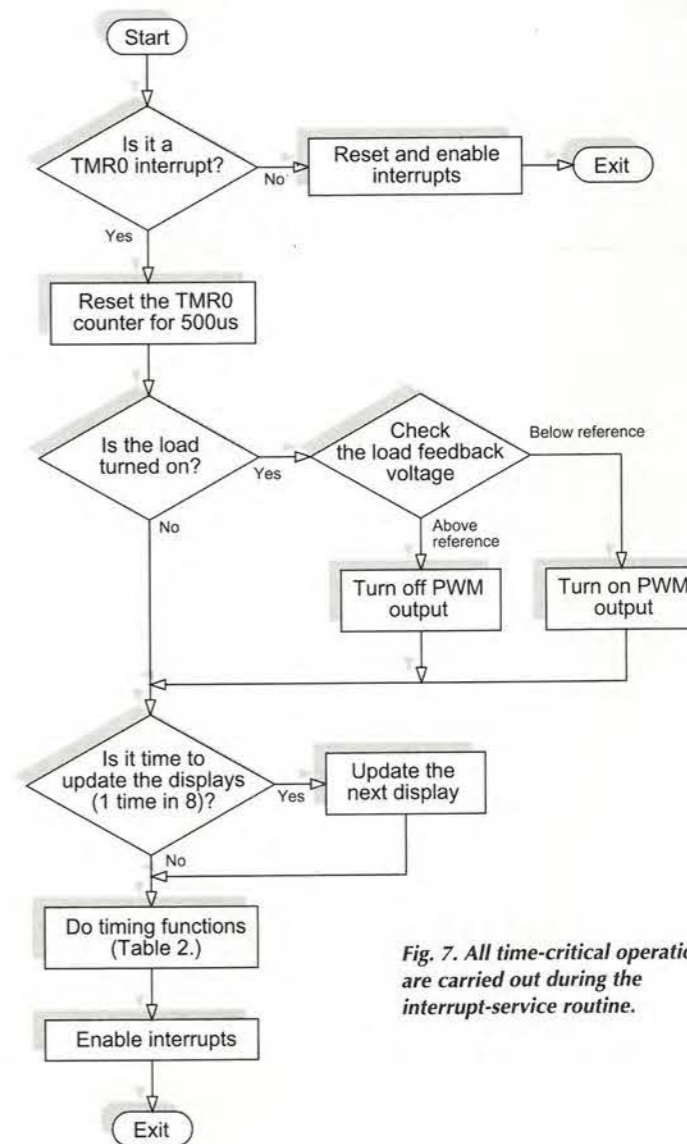


Fig. 7. All time-critical operations are carried out during the interrupt-service routine.



test. To provide a measuring voltage range of up to 13.8V,  $R_{19}$  and  $R_{20}$  (precision 0.1% tolerance components) are used as a potential divider,

$$13.8V \times \frac{10k\Omega}{23.7k\Omega + 10k\Omega} = 4.095V$$

at RA1.

**RA2:** The voltage of the tester's own battery. Resistors  $R_{14}$  and  $R_{15}$  are used to give a measured voltage range of up to 9V.

**RA5:** Drive-transistor temperature. The LM335 used here provides a voltage output of 10mV multiplied by its temperature in kelvin, so for a temperature of 55°C there would be a voltage of,

$$(273+55) \times 0.01 = 3.28V$$

present at RA5. Line RA3 is the input for the external voltage reference.

Code for the a-to-d conversion routine used by this application is shown in List 1. On entry to this routine, the W register contains the details needed by the converter. These details specify which port to read and which conversion clock to use – either a division of the clock frequency or an internal RC oscillator. They also specify whether the a-to-d module should be turned on. If a conversion is about to be initiated, it must be turned on.

Information from the W register is loaded into the ADCON0 register, Table 3. On exit from this routine the value returned by the a-to-d conversion – from the ADRES register – is copied into the W register.

Flags ADCS1 and ADCS0 select which clock is to be used by the a-to-d module. This clock may be the main clock frequency,  $F_{OSC}$ , divided by 2, 8 or 32, or an internal RC oscillator.

Using  $F_{OSC}$  means that the time taken by the successive approximation

a-to-d module can be calculated and minimised. But it also means that changing the clock speed necessitates changing the software to bring the a-to-d clock into the required range of values.

Although the RC clock option means we cannot predict the time that an a-to-d conversion will take, this does not matter so much if timing functions are performed by an interrupt-service register.

After the a-to-d unit has been set up, a 24µs delay is needed. This delay makes sure that the voltage on the pin to be read has stabilised and that the capacitor in the sample-and-hold circuit of the a-to-d unit has been fully charged.

The lines following the delay subroutine start the conversion and then loop round until the conversion status bit is cleared, indicating that the conversion is complete.

As the program uses a-to-d conver-

**Technical support**

A complete set of instructions on how to use the tester is available from <http://www.the-shed.demon.co.uk/tester>, where the complete code is also available. The instructions are also distributed with hard copies of the code, pre-programmed PICs and kits of parts.

To obtain details about how to get the code sent by mail, buy a pre-programmed PIC or a complete kit of parts (excluding case and heat sink), send a stamped self-addressed envelope to:

David Sawford,  
177 Sturton Street,  
Cambridge CB1 2QH.

Or email: [david.sawford@the-shed.demon.co.uk](mailto:david.sawford@the-shed.demon.co.uk)

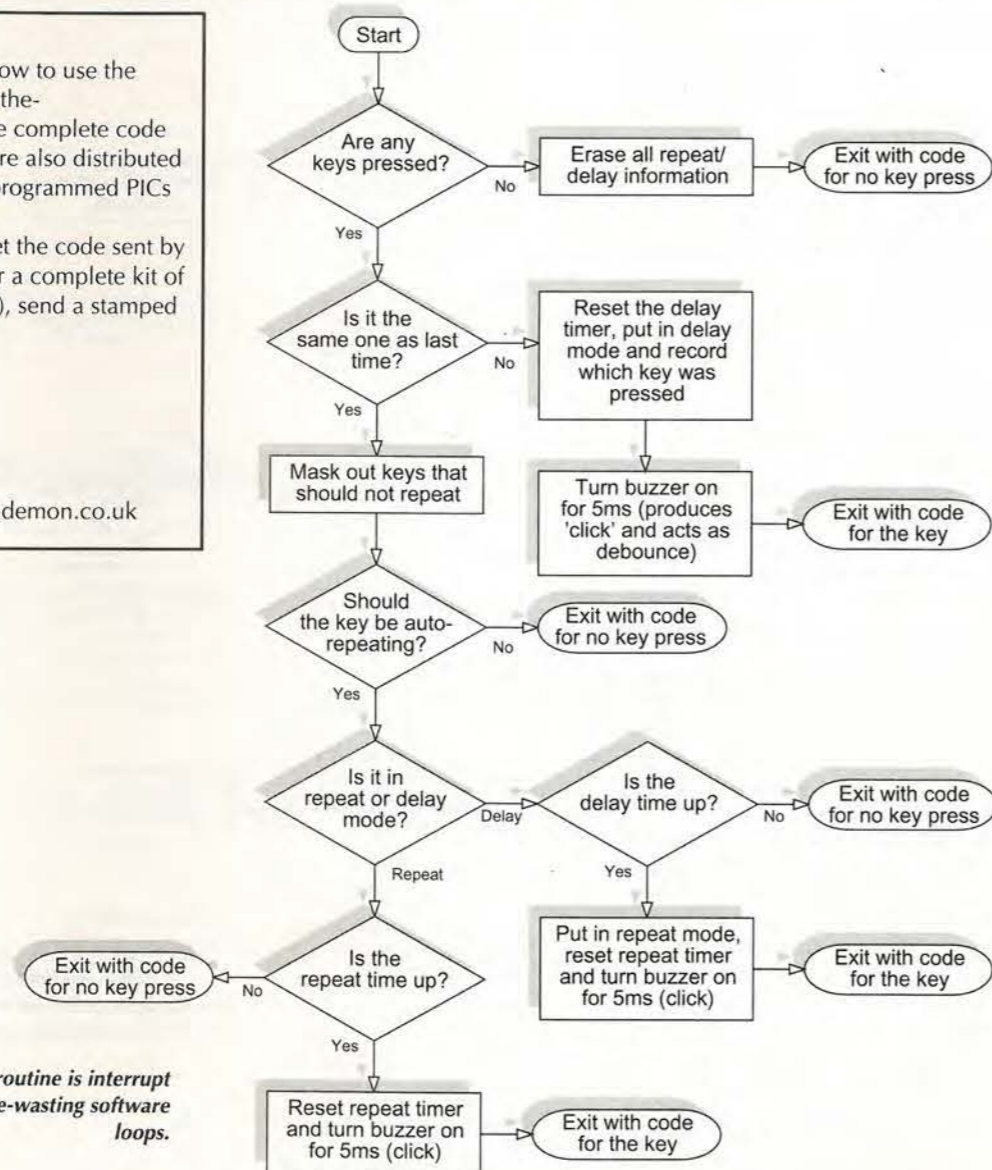


Fig. 8. The keypad interface routine is interrupt based so there are no time-wasting software loops.

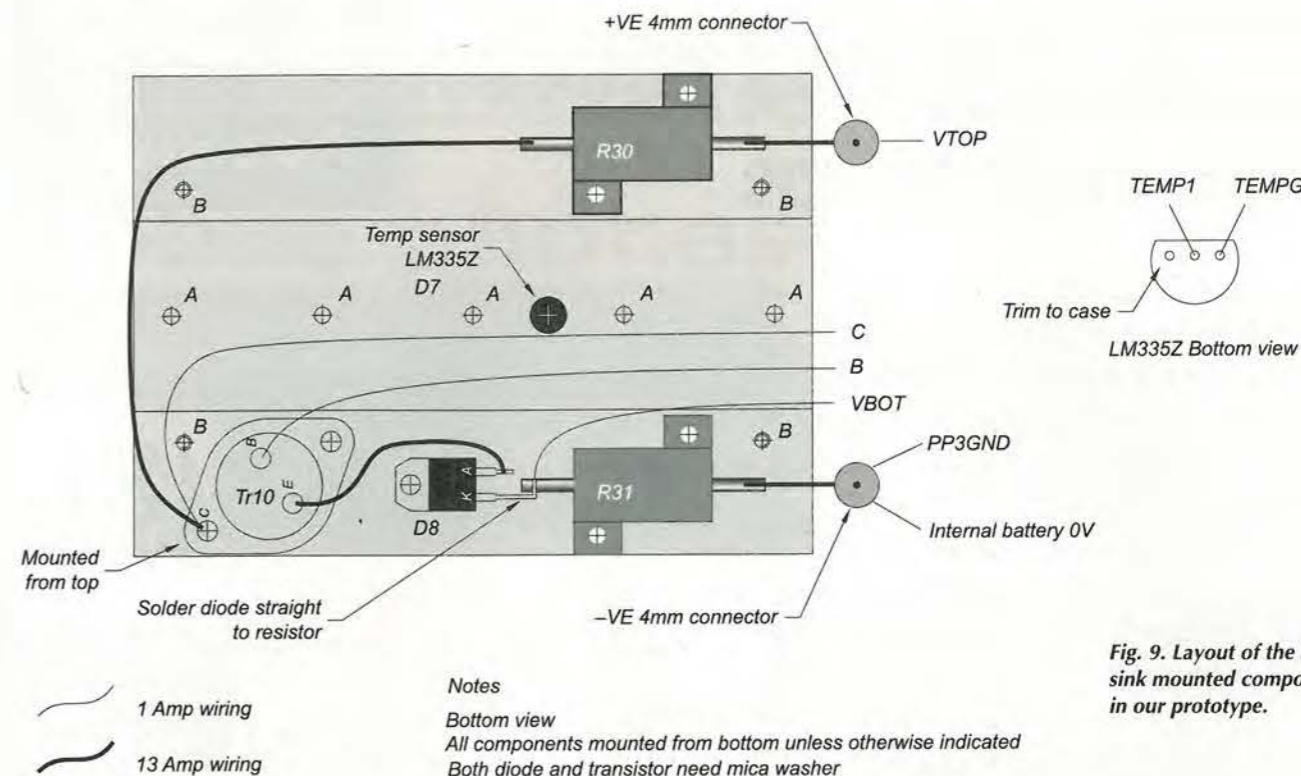


Fig. 9. Layout of the heat-sink mounted components in our prototype.

sion routines within interrupts, it is vital that an interrupt does not occur while this routine is being executed.

For example, an interrupt routine that used the a-to-d converter while the conversion program was acquiring a reading would over-write the value being read. Similarly, an interrupt during the set-up and delay sections could change which channel is read by the code that follows. For these reasons, interrupts are disabled at the start of the conversion routine and re-enabled at the end.

**The keypad interface**

In order to create a tactile 'feel' to the tester, the keypad reading routine does a bit more than just report which keys are being pressed.

Although the physical keys are no more than connections from the pins on the PIC to 0V, using software makes it possible to implement debouncing, auto-repeat of held-down keys with adjustable delay and repeat speed and an audible click when a key is pressed. Audible clicks are also produced while a held-down key is auto-repeating.

Figure 8 is the flowchart for the keypad interface routine. Timing functions, such as incrementing the counters for the delay/repeat of keys that are held down, are performed by the interrupt-service routine.

Using interrupts means that the routine does not have to have any loops in it to detect key statuses. As a result, a minimum of time is spent in the routine, allowing the calling routine to attend to more time-critical matters such as monitoring voltages and updating the display.

**Implementing the tester**

Our prototype battery tester was constructed in an extruded aluminium case, with the heat-producing components mounted on a piece of sheet aluminium, Fig. 9. They were bolted to the case using the holes marked 'A' via an aluminium block, shown in dotted lines, to form an effective heat sink.

Because there was a direct thermal path from the heat sink to the case, we chose 55°C as the temperature at which to suspend the test with an error message. The components on the heat sink can stand higher temperatures, but the operator holding the case might not be able to!

In this configuration, we found that three successive 7A tests could be performed before the unit started giving the 'too hot' error message. If a different build technique was used to allow a higher running temperature, the maximum test temperature could be raised by changing a value in the PIC code.

We stuck the temperature sensor into a hole in the heat-sink block using high-temperature epoxy to give a good thermal contact. All other components were mounted on a PCB that was bolted via the 'B' holes to the heat sink with insulating pillars.

There's a rectangular slot in the front of the case for the display. The keys, 4mm test-lead sockets and on/off switch were also mounted on the front. The battery compartment was in the base of the unit.

The choice of test leads is an important factor when it comes to accuracy. Not only must they be rated at 7A or more, but they must also have a known resistance.

Our tester has leads with a resistance of

0.054Ω/m, which made for a total resistance of 0.027Ω with 250cm lengths for both positive and negative connections.

In the code there is a look-up table of the voltage drops across the leads for each test current. This is subtracted from the 'fail' voltage digital equivalent by the software. For different leads, a different set of values will need to be calculated using,

$$value = \left( \frac{R \times I \times 10k}{10k + 23.7k} + 4.096 \right) \times 255$$

Good quality test clips are essential to minimise the voltage drop across them, and hence the voltage measurement error.

**Setting up**

The only adjustment that needs to be carried out is via the two links that add or subtract 2.5% from the load current. This is due to the fact that power resistors such as those used for the current sensor,  $R_{31}$ , typically have a tolerance of 5%.

Cutting link 1 adds 2.5% via a look-up table to the reference voltage that the pulse-width-modulated load signal generating routine will use for each current setting. Cutting link 2 subtracts 2.5%, and if both are cut there will be no net change.


Unless you have a way to accurately measure the resistance of  $R_{31}$  directly, the easiest way is to use a current of, say 2A from a power supply through the resistor and measure the voltage across it. As the resistance is voltage divided by current, it is easy to calculate  $R_{31}$  and cut the appropriate link if need be.

On a final note, it should be easy to apply the loading method to other current ranges and voltages. ■


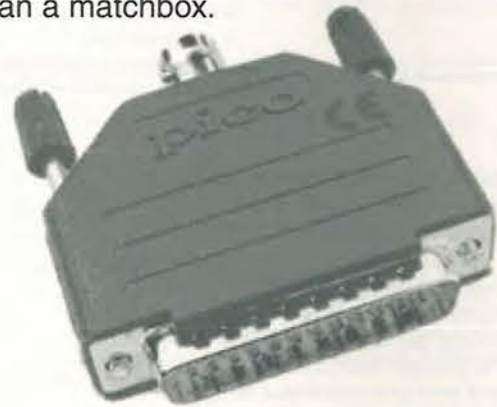
# Save 15% Pico ADC42 Virtual oscilloscope

Featuring 12-bit resolution and 1MΩ input impedance, the ADC42 samples at up to 15kS/s and includes software for spectrum analysis, oscilloscope functions and frequency display. Plugging into a PC's LPT port, the unit provides large, colourful displays and all the usual timebases and trigger options – all in a case slightly larger than a matchbox.



### ADC42 single channel oscilloscope

- Low cost and easy to use
- No power supply required
- Ultra compact design
- Oscilloscope and data logging software included
- Write-to-disk on trigger function standard

The ADC42 is a single-channel pc based virtual instrument. Simply plug the unit into the parallel port of your pc and run the software. Designed for analysing low-frequency signals, it provide all the functionality of a conventional scope at a fraction of the price.


The ADC42 has 12-bit resolution making it suitable for applications where detection of small signal changes is needed.

### Specifications

Scope timebases	500µs/div to 50s/div
Spectrum analysis	100Hz to 10kHz
Max sampling	15ksample/s
Voltage range	±5V
Resolution	12 bit
Channels	1 BNC
I/P impedance	1MΩ, dc coupled
Accuracy	1%
PC connection	D25 to PC parallel port
Power supply	Not required

**£98**  
inclusive of VAT  
and postage\*

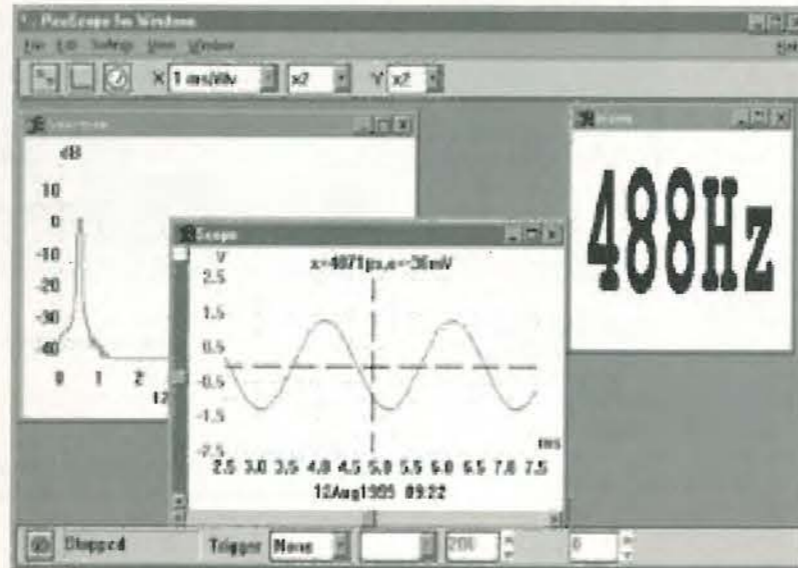\*UK only. Overseas readers please fax or e-mail for a quote including delivery charges.



### Use this coupon to order your ADC42

Please send me ..... ADC-42(s) at the special offer price of £98 fully inclusive of VAT and recorded UK delivery, normal selling price £111.63 excluding postage.

Name \_\_\_\_\_

Address \_\_\_\_\_

Phone number/fax \_\_\_\_\_

Total amount £.....

I enclose a cheque \_\_\_\_\_

Please charge to my credit/debit card.

Card type (Master/Visa/Switch etc)

Card No \_\_\_\_\_

Expiry date \_\_\_\_ / \_\_\_\_

Please mail this coupon to *Electronics World*, together with payment. Alternatively fax credit card details with order on **0181 652 8111**.

Address orders and all correspondence relating to this order to Pico Offer, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

email [jackie.lowe@rbi.co.uk](mailto:jackie.lowe@rbi.co.uk)

Make cheques payable to Reed Business Information Group.

# Third-generation mobile phones

The consumer will probably not get the benefits of 3G mobile phones for another two or three years, but what exactly will be on offer when the services are rolled out?  
**Richard Wilson takes a look**

As you can see from the table on the right, the UK, like the rest of Europe, is about to get its first third-generation mobile phone operators. But if like me you're wondering what third-generation mobile communications will offer in sexy new services then we should start to find out before the end of the year.

By Christmas 2000 each of the new third-generation (3G) operators will only be starting to build their network infrastructure. True 3G services are probably two years away at the earliest.

Some even suggest 3G will not happen in a significant way until 2002/3. One reason for this is that mobile-phone users will not have to wait until 3G is ready to get some of the anticipated new services like wireless Web browsers and video.

If GSM is second generation and UMTS is third generation mobile

communications, then somewhere in between comes the 2.5 generation system known as general packet radio service (GPRS). This is more than a half-way house mobile technology to full 3G. In fact its capability to carry packet-switched data at aggregated rates up to 384kbit/s may even persuade operators to put off investment in full-blown and expensive 3G networks a little longer.

Evidence suggests that UK operators are racing to upgrade their GSM networks to support GPRS and we could see first commercial general packet radio services by the end of the year.

"There is a strong desire for the rollout of GPRS," says Lance Hiley, a strategic marketing manager for wireless at Lucent Technologies. Microelectronics. "Every operator will have commercial GPRS services in 2000 – most likely the

### 3G licences in Europe

Country	Number of licences being awarded	Scheduled award date
Finland	4	awarded March 1999
UK	5	March 2000
Spain	4	March 2000
Netherlands	4-6	Q1 2000
Germany	4-6	Q2 2000
Norway	3-4	Q2 2000
Switzerland	3-4	?
Portugal	4	?
Denmark	4-5	?
France	4	Q3 2000
Belgium	3-4	Q3 2000
Sweden	?	Q3 2000
Italy	5	Q3 2000
Austria	4	Q4 2000
Ireland	3-4	Q4 2000
Greece	4	Q1 2002

Source: Netcom Consultants, UK



second half of the year."


But how does GPRS improve on existing GSM mobile systems? The key is data transmission.

The GSM mobile phone is essentially a voice communicator. GSM data transfers are literally in the dark ages being limited to 9600bit/s. This is less than 20 per cent of the rate of the modem in your PC, or 1000 times slower than the slowest office LAN.

The experts tell us that the 3G mobile phone will be defined as a

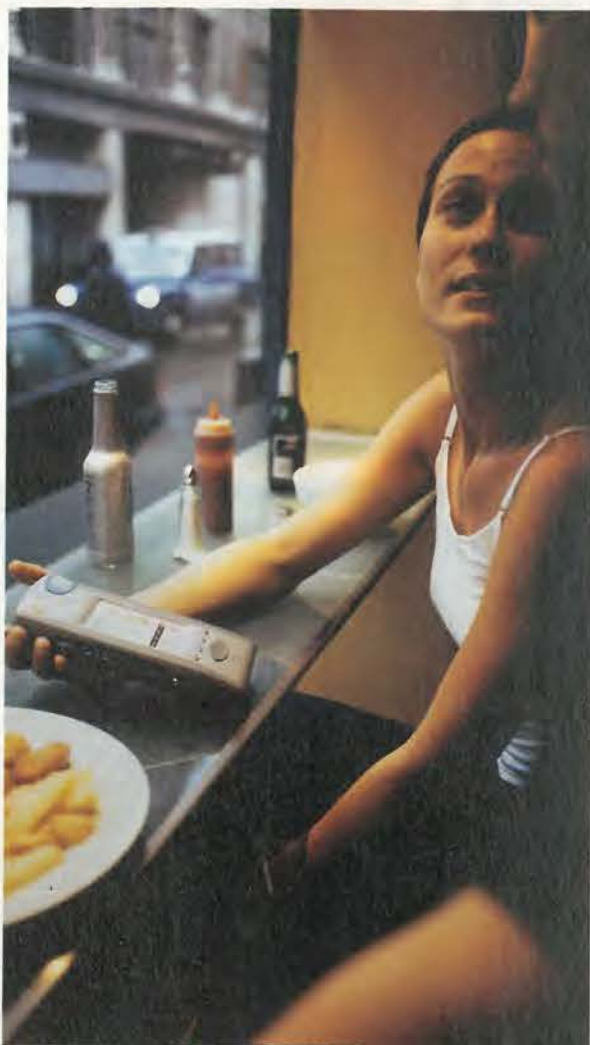Mobile video. Samsung shows what a 3G handset will look like.





Mobile phone operator Orange has already shown us what a 3G video phone could look like

mobile data terminal, with voice communications thrown in, perhaps for free.

"If 3G is only deployed for voice it will be like killing a bee with an F-14 fighter plane," asserts Thierry Laurent from Philips Semiconductors.

Never mind the technology, this will change the nature of mobile communications and present the mobile firms with a new concept to sell. "We must remember that on GSM mobile 99 per cent of the traffic is voice," says Stephen Wall, technical director of The Smith Group. "That is a straightforward sell for the operator; you sell two phones and you talk."

For this switch away from voice to happen, the radio network must be able to handle high-speed data channels. UMTS, the technology behind 3G, will do this. But GPRS will also be able to extend the data rates on GSM networks.

GPRS works by transmitting data

in packets. Each packet has an 'address' for where it is being sent so that all the data packets that make up a particular message do not necessarily have to be transmitted in sequence on one radio channel, as is the case with GSM at present.

With GPRS, data transmission can be increased above the capability of a single radio channel because packets can be sent on any of a number of different radio channels set up by the network.

A GPRS system allows a data rate of up to 14.4kbit/s to be transmitted in each of GSM's eight time slots. This gives an aggregated system data rate of 115.2kbit/s. A ten-fold increase on today's GSM modems.

However we as users are only starting out on the 3G road, despite how quickly manufacturers may wish to push us along. A full 115kbit/s GPRS mobile data terminal requires eight radio slots, for both transmit and receive. That requires a minimum of 16 slots and is known as a Class 18 GPRS system.

Class 18 mobiles offering 115kbit/s

data rates will not be available until next year. The first GPRS mobile we will see on the market this summer will be Class 8. This class uses four 14.4kbit/s channels so should offer the radio equivalent of a 56k modem.

So if you want to use your mobile to transmit data files to the office, or even to download information from the Internet, the data rates you can expect are as follows - 56kbit/s by the end of the year - 115kbit/s by the summer of 2001. And it does not stop there.

A further GSM data enhancement technology known as EDGE is being developed by Nokia and Ericsson amongst others. This could potentially extend mobile data rates to 384kbit/s. But it will not happen until late 2001 or early 2002.

And that should be just in time to get the market ready for the first full 3G services in 2002/3. The data capabilities of 3G will stretch up to 2Mbit/s by which time the mobile phone will be seen as a mobile data terminal and not simply a voice communicator. ■

## WAP

Wireless Web browsing will complicate considerably the business of selling mobile communications so operators and manufacturers have come up with the wireless applications protocol (WAP) standard to help companies through the minefield of the wireless Internet.

WAP defines a set of hardware and software interfaces which when implemented on mobile handsets and Web site servers should allow mobile phones to be used much like a PC, to send and receive e-mail messages and even to browse the Internet.

But the performance of the WAP applications will inevitably put demands on the bandwidth of the mobile's radio channel. So the development of WAP-based services will coincide with the rollout later this year of higher bandwidth radio systems like GPRS (general packet radio service) which theoretically offers data rates up to 115kbit/s.

WAP itself incorporates data compression to make the most of the lowly data transfer rate of today's GSM networks. It also uses error correction techniques to ensure that browsing and data transmissions are not severely affected by changes in the quality of the radio link.

The other important feature of the WAP is it is designed to run applications on different radio network architectures, such as GSM, CDMA, DECT and even TETRA.

The telecoms industry is notorious for its use of acronyms, so when third generation mobile systems became known as 3G systems hardly an eyebrow was raised in disbelief. However, 3G is just the start. Already there are 2G+, 3GPP and 3GPP2 to tax our powers of understanding. To help the inquisitive and perhaps confused amongst you Steve Bush presents a listing of some of the more useful acronyms associated with the next generation of mobile phone technology. Perhaps it will give you a chance to impress someone in the office but don't bank on using the knowledge at the local pub quiz night.

**2G+** Second generation mobile communications with enhancements to add high speed data capability. See EDGE, HSCSD and GPRS.

**3G** Third generation. 3G is used as a collective noun for the forthcoming generation of mobile phone systems. These are characterised by high speed data capability alongside voice services.

**3GPP** Third Generation Partnership Project. An organisation producing technical specifications for third generation mobile system based on GSM core networks. ARIB (Japan), CWTS (China), ETSI (Europe), T1 (USA), TTA (Korea) and TTC (Japan) are members. According to 3GPP, the 3GPP standards will be forwarded to the ITU and will support inter-working between IMT-2000 family members. The project is expected to accelerate IMT-2000 standardisation. [www.3gpp.org](http://www.3gpp.org)

**3GPP2** CDMA2000 equivalent to 3GPP, members are ARIB (Japan), CWTS (China), TTA (Korea) and TTC (Japan). [www.3gpp2.org](http://www.3gpp2.org)

**ARIB** Association of Radio Industries and Businesses. Japanese radio standards body. ARIB and the European UMTS specifications were developed to be interoperable at an early stage. [www.arib.or.jp](http://www.arib.or.jp)

**CDMA** Code division multiple access. A spread spectrum communication technique, the basis of most 3G systems.

**CDMA2000** 3G air interface standard, a Qualcomm trade name. Comes in 1X (1.25MHz channel) and 3X (3 x 1.25MHz channel) types.

**CWTS** Chinese Wireless Telecommunications Standards organisation. [www.cwts.org](http://www.cwts.org)

**EDGE** Enhanced Data-rates for GSM Evolution. GSM with a different modulation scheme boosting data throughput up to 384kbit/s using existing GSM infrastructure. Was known as 2G+ in Europe, now officially part of 3G and known as IMT-SC.

**EFR** Enhanced Full Rate. A speech codec for better speech quality code, also said to be more tolerant to interference.

**ETSI** European Telecommunications Standards Institute.

**FPLMTS** Future Public Land Mobile Telecommunication System, the ITU's single global 3G standard, abandoned when no agreement could be found, replaced by the IMT-2000 family of standards.

**FDD** frequency division duplex, part of 3G W-CDMA with separate Tx and Rx frequencies for up to 2Mbit/s short range data services. Will be implemented after TDD.

**GCF** GSM Certification Forum. An industry body defining a set of tests to supplement European self-certification type-approval tests to ensure functional compatibility to GSM networks. A 3G equivalent of this is expected to be formed.

**GPRS** General Packet Radio Services. Part of the GSM Phase 2+ extension. Packet switching on GSM with data rates of up to 115kbit/s carrying Internet Protocol, TCP/IP and X.25 Generalised Packet Radio Service.

**GSM** Global System for Mobile Communications, formerly Group Systeme Mobile

**GSM Phase 2+** GSM with high speed data capability.

**H.323** Real-time audio and video and data over packet switched network - multimedia over IP.

**HSCSD** High-speed circuit switched data, data over GSM up to 57.6kbit/s by concatenating up to four consecutive GSM time slots. Part of GSM Phase 2 development.

**IMT-2000** International Mobile Telecommunications for the year 2000. The ITU's family of 3G mobile phone systems. Replaced ITU's original concept of one single 3G system called FPLMTS which was abandoned when none of the vested interests could have it their own way. See: IMT-DS, IMT-MC, IMT-TC, IMT-SC and IMT-FT

**IMT-DS** Frequency division duplex version of UMTS.

**IMT-MC** CDMA2000, narrow-band CDMA for the USA. 3X CDMA 2000 using three 1.25MHz channels.

**IMT-TC** Time division duplex version of UMTS and time division SCDMA (TD-SCDMA).

**IMT-SC** The successor to IS-136 mobile standard. This is EDGE [the GSM phase 2+ standard].

**IMT-FT** The DECT cordless standard.

**IP** Internet Protocol

**IPv6 Forum** An organisation promoting Internet access on 3G mobile networks.

**IS-95** Second generation narrow-band CDMS system, used predominantly in the USA.

**IS-136** Enhanced IS-95

**IS-2000** CDMA2000 air interface standard. A successor to standard TIA/EIA-95-B

**ITU** International Telecommunication Union. Officially the final arbiter of telecommunications standards, but its power lies only in the agreement of its members. Has finally approved the radio interfaces for IMT-2000 third generation mobile phones. [www.itu.int](http://www.itu.int)

**NTT DoCoMo** Japanese company, similar to BT in the UK, implementing a 3G system in Japan, due in April 2001, it will be the first third generation system.

### Packet switching

Communication using a channel shared by multiple users, silent periods between a sender and receiver are filled with data from other user pairs. Very efficient use of system resources leads to more data through a given network, but it is difficult to guarantee the arrival time of time-critical data (voice, music or video) during busy periods. Highly suitable for time-tolerant data like Internet pages.

**PDH** Pleisynchronous Digital Hierarchy, here only because it includes the word pleisynchronous.

**T1** Industry body that creates network interconnection and interoperability standards for the United States. [www.t1.org](http://www.t1.org)

**TAA** Korean telecommunications standards body. [www.tta.or.kr](http://www.tta.or.kr)

**TCC** Japanese telecommunications standards body. [www.ttc.or.jp](http://www.ttc.or.jp)

**TCP/IP** Transmission Control Protocol/Internet Protocol. Protocol necessary for Internet data transmissions.

**TDD** time division duplex, part of 3G W-CDMA. Transmission and reception are at the same frequency, at different times. Data rates will be lower than FDD, but TDD has a longer range. TDD is planned to be operating before FDD.

**TDMA** Time division multiple access.

**TD-SCDMA** Time-Division Synchronous CDMA

**TIA** The Telecommunications Industry Association, a US standards development organisation. [www.tiaonline.org](http://www.tiaonline.org)

**TIA/EIA-95-B** Third generation CDMA air interface standard. Replaces IS-95

**TIA/EIA-136** ANSI version of the TDMA air interface standard. Replaces IS-136, second generation TDMA air interface standard

**TIPHON** Telecommunications and Internet Protocol Harmonisation over Networks

**TSG** Technical Specification Group. Part of the 3GPP and 3GPP2 processes.

**UMTS** Universal Mobile Telecommunications Systems. The 3G initiative for Europe. Promising to increase bandwidth to between 384kbit/s and 2Mbit/s, depending on the distance to base stations and whether user is travelling or not. Uses W-CDMA. The UMTS specifications and the Japanese ARIB specifications were developed to be interoperable at an early stage.

**VoIP** Voice over Internet Protocol.

**WAP** Wireless Application Protocol. If you write your Web site in WAP, it can be read on a suitable mobile phone.

**W-CDMA** Wideband code division multiple access.

**X.25** An ITU defined general purpose packet switching protocol



# You Can't Buy Better!

## TEST EQUIPMENT PRICE BLITZ

### MARCONI 2019A Synthesised Signal Generators

80kHz to 1040MHz AM-FM-CW LCD Displays  
Complete with Lids etc. FULLY TESTED and Warranted

**NOW ONLY £475.00**

### MARCONI 2022E Synthesised Signal Generators

10kHz to 1010MHz LCD Display Fitted IEEE with covers  
Small and Lightweight FULLY TESTED and Warranted

**NOW ONLY £495.00**

### Frequency Counters

**Racal Dana 9918**  
9 segment 560Mhz £75

### Signal Generators

**Marconi 6311**  
Programmable Sweep Generator.  
10Mhz to 20Ghz £3,250

**Rohde and Schwarz APN62**  
1hz to 260kHz with LCD display £750

**Farnell DSG2**  
Synthesised 0.1mhz to 110kHz £195

**Wavetek 155**  
Programmable VCG 0.01hz to 1Mhz sine,  
square, triangle £195

### Oscilloscopes

### TEK 2445

150Mhz Four Trace/2 Time base  
with Cursors, etc. Now Only £495

**TEK 2445A** 150Mhz Four Trace/  
2 Time bases  
with Cursors, etc. Now Only £595

**TEK 2465** 300Mhz Four Trace/2 Timebases  
Now Only £750

**TEK T922R** Dual trace rack mount 20Mhz  
scopes £150

**GOULD OS3500 with**  
DM3010 DMM fitted, 60Mhz  
Dual trace, Dual Timebase  
Was £350 . . . Reduced, Now ONLY £250

**HP 1741A** 100Mhz Storage.  
Dual Time base  
Was £350 . . . Reduced, Now ONLY £250

**TEK 465B** 100Mhz Dual Trace/  
Timebase Now Only £295

**TEK 465M** scope as 465B but built only  
for Military. Only £350

**TEK 475** 200Mhz Dual Trace/Timebase  
Now Only £395

**PHILIPS PM3217**  
DC-50Mhz 2 Trace 2 Timebase  
Only £275

**GOULD OS300** DC-20Mhz 2 Trace  
Special ONLY £150

### THIS MONTH'S SPECIALS

**TEK 2753P** Programmable Spectrum  
Analyser 100hz - 1.8Ghz OSD's  
Cursors etc £3,750

**HP141T + 8552B + 8554B**  
RF to 1250Mhz £850

**Philips PM3217** Scopes  
DC-50Mhz 2 Trace/2 Timebase  
A REAL Anchor Special ONLY £275



**GOULD OS300** Scopes  
DC-20Mhz 2 Trace  
SPECIAL NOW ONLY £150



### Regulated Power Supplies

**Thorn Automation**  
Variable power supply giving 0-40 volts at  
0-50 amps DC. V and I limiting (advise  
calling... these are heavy). 2 ONLY £125

**Lambda Labs**  
LME5V 5V at 40A DC... ONLY £20  
LMD12YV 12V at 10A DC... ONLY £20  
LMB24V 24V at 1.4A DC... ONLY £7.50  
LP523 variable 0-60V at 0.9A... ONLY £45  
Regulated + Stabilised Power supply. 0-30V  
@10A £60

### Miscellaneous

**Rolleiflex T** twin lens reflex csmersas,  
leather case £175

**Olympus LS-10 OES** lecture scopes (fibre  
scope) cased, un-issued £75

42 channel, 8 speeds from 15/16ips to  
120ips, 1in tape complete with SE7000  
patch panel... 1 ONLY £500

**GIGA** Pulse internal counter  
2-8Ghz ONLY £150

### Miscellaneous

**Fluke 80-40K**  
High Voltage probe for DMM's 40kv.  
Cased. NEW £45

**Beckman Industrial HD110**  
LCD Multimeters in Leather case,  
1000V, 10A  
ONLY £50

**Nere Saturn compact T**  
portable satellite uplink telephone  
system including case and dish £1,000

**GIGA GR1128AD**  
pulse interval counters 2 - 8GHZ £150

### HIGH POWER RF ATTENUATORS

A pair of 10db oil-filled attenuators.  
Mounted in a comon heat sink  
assy. Each rated at 100w 50 Ohms.  
BNC connectors. OK well into  
UHF range.

As new condition  
ONLY £25

**AVO Model 8**  
**Mk 5/Mk 6**  
Multimeters . . . THE Standard  
ONLY £85

### NEW EQUIPMENT

**DTA20 Oscilloscope 20Mhz**  
Twin trace incl probes ONLY £225

**DTS40 Oscilloscope 40Mhz**  
Digital Storage twin channel  
Cursors + readouts Incl. Probes.  
ONLY £399

**NEW SCOPE PROBES**  
X1/X10 switchable to 100Mhz  
Complete with adaptors  
Limit 2 sets per customer  
ONLY £9.95

## ANCHOR SUPPLIES LTD

All prices are EX VAT and Carriage

MAIL ORDER A PLEASURE


The Cattle Market Depot, Nottingham NG2 3GY, UK

Tel: (0115) 986 4902 Fax: (0115) 986 4667

Also at Ripley, Derbys (01773) 570137 and Coalville, Leicestershire (01530) 811800

Visit our Web Site: [www.anchor-supplies.ltd.uk](http://www.anchor-supplies.ltd.uk) email: [sales@anchor-supplies.ltd.uk](mailto:sales@anchor-supplies.ltd.uk)

# RESISTANCE IS FUTILE

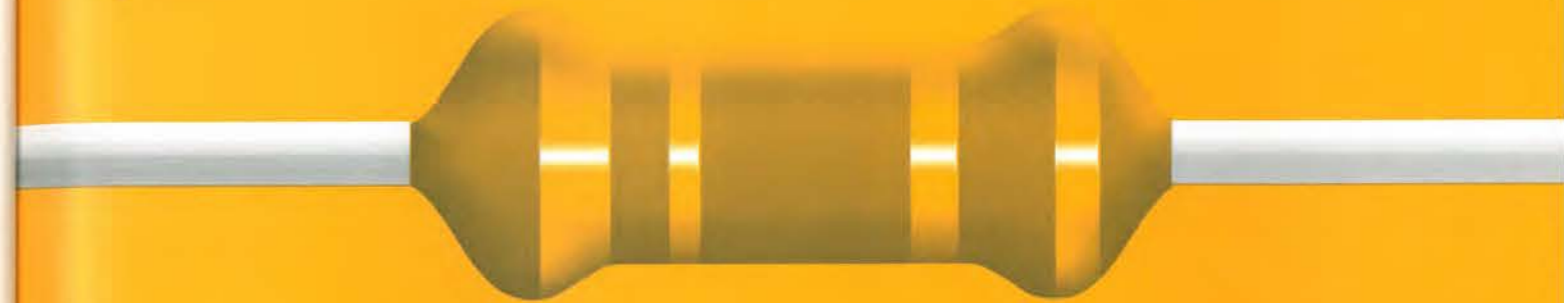

Subscribe for 3 years, pay for just 2

**ELECTRONICS  
WORLD**  
INCORPORATING WIRELESS WORLD

**HP86290A+B** Sweep PI-2 - 18GHz - £1000 - £1250.  
**HP8620C** Mainframe - £250. IEEE £350.  
**HP165A** Programmable signal source - 1MHz - 50Mc/s - £1k.  
**HP3455/3456A** Digital voltmeter - £400.  
**HP5370A** Universal time interval counter - £1k.  
**HP5335A** Universal counter - 200Mc/s-£1000.  
**HP3552A** Transmission test set - £350.  
**TEKTRONIX 577** Curve tracer + adaptors - £900.  
**TEKTRONIX 1502/1503** TDR cable test set - £400.  
**HP8699B** Sweep PI YIG oscillator .01 - 4GHz - £300. 8690B MF-  
£250. Both £500.  
**Dummy Loads & Power** att up to 2.5 kilowatts FX up to 18GHz -  
microwave parts new and ex equipt - relays - attenuators -  
switches - waveguides - Yigs - SMA - APC7 plugs - adaptors  
etc. qty. in stock.  
**B&K Items** in stock - ask for list.  
**Power Supplies** Heavy duty + bench in stock - Farnell - HP -  
Weir - Thurlby - Racal etc. Ask for list. Large quantity in stock,  
all types to 400 amp - 100Kv.  
**HP8405A** Vector voltmeter - late colour - £400.  
**HP8508A** Vector voltmeter - £2500.  
**HP8505A** Network Anz 500KHz-1.3GHz - £1000.  
**HP8505A + 8502A** or 8503A test sets- £1200 - £1500.  
**HP8505A + 8502A** or 8503A + 8501A normalizer - £1750-£2000.  
**Phillips 3217** 50Mc/s oscilloscopes - £150-£250.  
**Wavetek-Schlumberger 4031** Radio communication test set

**LIGHT AND OPTICAL EQUIPMENT**  
**Anritsu ML93A & Optical Lead Power Meter** - £250.  
**Anritsu ML93B & Optical Lead Power Meter** - £350.  
Power Sensors for above **MA96A - MA98A - MA913A** - Battery  
Pack MZ95A.  
**Anritsu MW97A** Pulse Echo Tester.  
Pl available - **MH914C 1.3 - MH915B 1.3 - MH913B 0.85 -**  
**MH925A 1.3 - MH929A 1.55 - MH925A 1.3GI - MH914C 1.3SM -**  
**£500 + one Pl.**  
**Anritsu MW98A** Time Domain Reflector.  
Pl available - **MH914C 1.3 - MH915B 1.3 - MH913B 0.85 -**  
**MH925A 1.3 - MH929A 1.55 - MH925A 1.3GI - MH914C 1.3SM -**  
**£500 + one Pl.**  
**Anritsu MZ100A** E/O Converter.  
**+ MG912B (LD 1.35) Light Source + MG92B (LD 0.85)**  
Light Source £350.  
**Anritsu MZ118A** O/E Converter.  
**+MH922A 0.8 O/E unit + MH923 A1.3 O/E unit** £350.  
**Anritsu ML96B** Power Meter & Charger £450.  
**Anritsu MN95B** Variable Att. 1300 £100.  
**Photo Dyne 1950 XR** Continuous Att. 1300 - 1500 £100.  
**Photo Dyne 1800 FA** Att £100.  
**Cossor-Raytheon 108L** Optical Cable Fault Locator  
0-1000M 0-10K £200.  
**TEK P6701** Optical Converter 700 MC/S-850 £250.  
**TEK OF150** Fibre Optic TDR - £750.  
**HP81512A** Head 150MC/S 950-1700 £250.  
**HP84801A** Fibre Power Sensor 600-1200 £250.

**TEKTRONIX MAINFRAMES - 1MHz-1502-300-300-3000-  
TM5003-5006.**  
**TEK PI 5010-M1** - Prog Multi Interface - £250. **FG** Prog 20MC/S  
Function Gen - £400 - **S1** Prog Scanner - £250 - **DM** Prog  
DMM - £400.  
**TEK 7000 OSCILLOSCOPE MAINFRAMES** - 7603-7623-7633-  
7834-7854-7904-7904A-7104 - £150-£1,000.  
**TEK 7000 PIs** - 7A11-7A12-7A13-7A18-7A19-7A22-7A24-7A26-  
7A29-7A42-7B10-7B15-7B53A-7B80-7B85-7B92A-7D15-7D20.  
**TEK 7000** - 7S11-7S12-7S14-7M11-S1-S2-S3A-S4-S5-S6-S51-  
S53-S54.  
**HP POWER SUPPLIES** - 6621A-6623A-6624A-6632A-6652A.  
Qty's available. Also 6000 types EPOA.

**RADIO COMMUNICATION TEST SETS**  
**BULK PURCHASE ONLY FROM JOHNS RADIO**  
**HP 8920A** RF Communication Test Sets - Opts available 001-3-  
4-5-7-11-12-14-H13-K13. £1,500-£1,750.  
**HP8920A** with opt 002 Spectrum anz plus tracking generator  
plus opts. 001-3-4-5-11-12-014 available in part includes syn sig  
generator - digital oscilloscope distortion meter - mod meter -  
RF power meter etc. £2,500.

**SPECIAL OFFERS**  
**MOTOROLA R2600A** plus **RLN4260A** RF Test Set - £1,800.  
**MARCONI 2955** RF Test Sets-1000MC/S - £1,000 each.  
**MARCONI 2956** RF Test Sets-1000MC/S - £1,250 each.  
**MARCONI 2955A** RF Test Sets-1000MC/S - £1,500 each.  
**MARCONI 2960A** RF Test Sets-1000MC/S - £1,500 each.  
**ANRITSU MS555A2** Radio Comm Anz-1000M/Cs - £750  
each.  
**MARCONI 2019A SYNTHESIZED SIGNAL GENERATORS** -  
80KC/S-1040MC/S - AM-FM - £400 inc. instruction book -  
tested.  
**MARCONI 2022E SYNTHESIZED SIGNAL GENERATOR** -  
10KC/S-1.01GHZ AM-FM - £500 inc. instruction book -  
tested.  
**R&S APN 62** LF Sig Gen 0.1Hz - 260KHz c/w book - £250.

**WE KEEP IN STOCK** HP and other makes of RF Frequency  
doublers which when fitted to the RF output socket of a  
S/Generator doubles the output frequency EG.50-1300MC/S to  
50-2600MC/S price from £250 - £450 each.

**SPECTRUM ANALYZERS**  
**HP 3580A** 5HZ-50KHZ - £750.  
**HP 3582A** Dual 0.2HZ-25.5KHZ - £1,500.  
**HP 3585A** 20HZ-40MC/S - £3,500.  
**HP 3588A** 10HZ-150MC/S - £7,500.  
**HP 8568A** 100HZ-1.5GHZ - £3,500.  
**HP 8568B** 100HZ-1.5GHZ - £4,500.  
**HP 8590B** 9KC/S-1.8GHZ - £4,500.  
**HP 8569B** 10MC/S (0.01-22GHZ) - £3,500.  
**HP 3581A** Signal Analyzer 15HZ-50KHZ - £400.

**SIGNAL GENERATORS**  
**HP8640A** - AM-FM 0.5-512-1024MC/S - £200-£400.  
**HP8640B** - Phase locked - AM-FM 0.5-512-1024MC/S - £500-  
£1.2K. Opts 1-2-3 available.  
**HP8654A** - B AM-FM 10MC/S-520MC/S - £300.  
**HP8656A** SYN AM-FM 0.1-990MC/S - £900.  
**HP8656B** SYN AM-FM 0.1-990MC/S - £1.5K.  
**HP8657A** SYN AM-FM 0.1-1040MC/S - £2K.  
**HP8657B** SYN AM-FM 0.1-2060MC/S - £3K.  
**HP8660C** SYN AM-FM-PM-0.01-1300MC/S-2600MC/S - £2K.  
**HP8660D** SYN AM-FM-PM-0.01-1300MC/S-2600MC/S - £3K.  
**HP8673D** SYN AM-FM-PM-0.01-26.5 GHz - £12K.  
**HP3312A** Function Generator AM-FM 13MC/S-Dual - £300.  
**HP3314A** Function Generator AM-FM-VCO-20MC/S - £600.  
**HP3325A** SYN Function Generator 21MC/S - £800.  
**HP3325B** SYN Function Generator 21MC/S - £2K.  
**HP8673-B** SYN AM-FM-PH 2-26.5 GHz - £6.5K.  
**HP3326A** SYN 2CH Function Generator 13MC/S-IEEE - £1.4K.  
**HP3336A-B-C** SYN Func/Level Gen 21MC/S - £400-£300-£500.  
**Racal/Dana 9081** SYN S/G AM-FM-PH-5-520MC/S - £300.  
**Racal/Dana 9082** SYN S/G AM-FM-PH-1.5-520MC/S - £400.  
**Racal/Dana 9084** SYN S/G AM-FM-PH-.001-104MC/S - £300.  
**Racal/Dana 9087** SYN S/G AM-FM-PH-.001-1300MC/S - £1K.  
**Marconi TF2008** AM-FM-Sweep 10KC/S-510MC/S - £200 Fully  
Tested to £300, as new + book + probe kit in wooden box.  
**Marconi TF2015** AM-FM-10-520MC/S - £100.  
**Marconi TF2016A** AM-FM 10KC/S-120MC/S - £100.  
**Marconi TF2171/3** Digital Synchronizer for 2015/2016A - £50.  
**Marconi TF2018A** AM-FM SYN 80KC/S-520MC/S - £500.  
**Marconi TF2019A** AM-FM SYN 80KC/S-1040MC/S - £650-£1K.  
**Marconi TF2022E** AM-FM SYN 10KC/S-1.01GHZ - £1K-£1.2K.  
**R & S SMPD** AM-FM-PH 5KHz-2720MC/S - £3K.  
**Anritsu MG3601A** SYN AM-FM 0.1-1040MC/S - £1.2K.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE.  
VAT AND CARRIAGE EXTRA. ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCRS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel: (01274) 684007. Fax: 651160

CIRCLE NO. 110 ON REPLY CARD







# CIRCUIT IDEAS

## Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly.

## RS232-to-parallel data conversion

Convert RS232 format data to 8-bit parallel data cheaper than with a UART.

Here, standard ICs convert RS232 format to eight-bit parallel data with one start and stop bit. Total cost and power consumption is less than that of any standard chip available.

The circuit can be used as part of a PC-based serial interface through the COM1 or COM2 port.

A general purpose timer, IC<sub>1</sub> is used as the clock generator, producing

clock pulses only on receipt of serial data. Data is shifted into a serial to parallel shift register, and along with each data byte (DATA) a latch pulse (LATCH) is generated for the parallel destination port.

No initialisation other than the bit-rate setting from the PC is required. The rate is equal to the clock, CL, generated by timer IC<sub>1</sub>. Setting the divisor value for bit rate 'B' sets the baud value of the PC.

$$CL = \frac{1.4}{(R_A + 2R_B) \times C}$$


The divisor value for the PC is,  $\frac{1843200}{16B}$

It is possible to program the PC for any bit rate by putting the corresponding divisor value in 16-bit format using statements in turbo-C as given below, for COM1,


```
output (0x2FB, 131)
/*2F8 for Baud setting*/
output (0x2F8, 0xLSB)
/* LSB byte of divisor*/
output (0x2F9, 0xMSB)
/* MSB of divisor*/
output (0x2FB, 3)
/* 2F8 for transmission */
```

Any data in eight-bit format can be sent to pin 3 of the nine-pin D-type connector using statement 'output (0x2F8, word)'. For COM2 use 3F8, 3F9 and 3FB.

S. Vijayan Pillai  
Kerala  
India  
C74

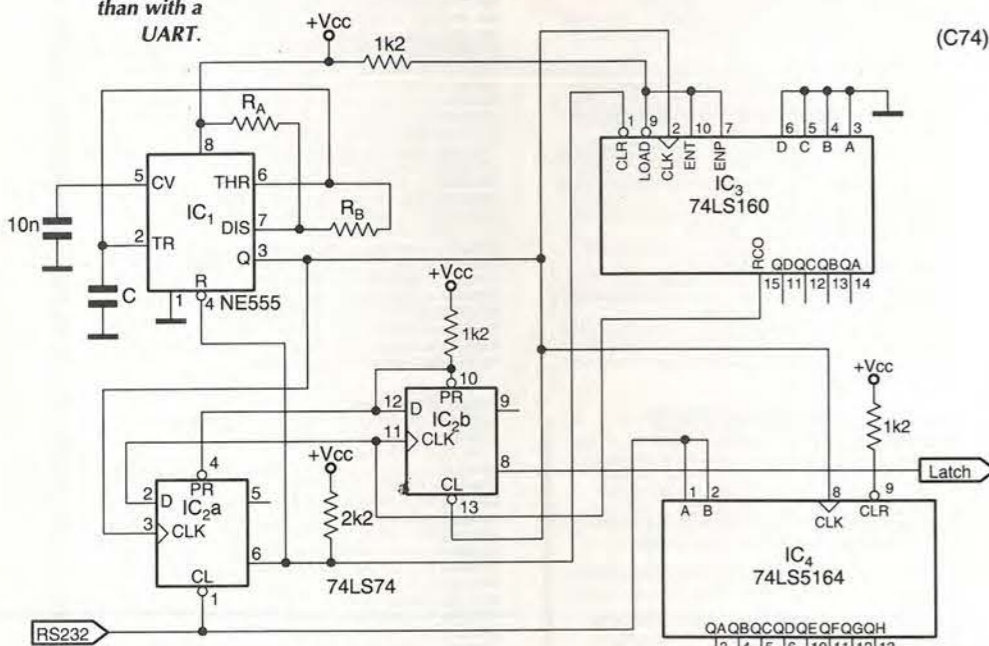

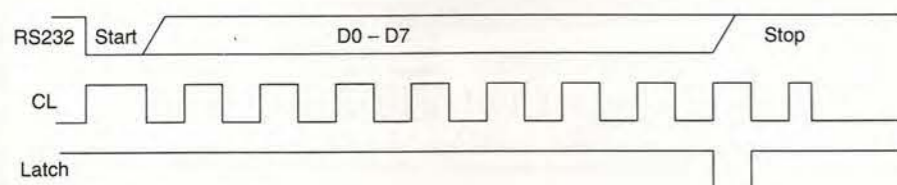
- 1 Decouple Vcc pin of all ICs with 100n
- 2 Vcc pin of IC<sub>4</sub> and IC<sub>2</sub> is pin14
- 3 GND of IC<sub>4</sub> and IC<sub>2</sub> is pin7
- 4 Pin16 and pin8 of IC<sub>3</sub> are VCC and GND respectively


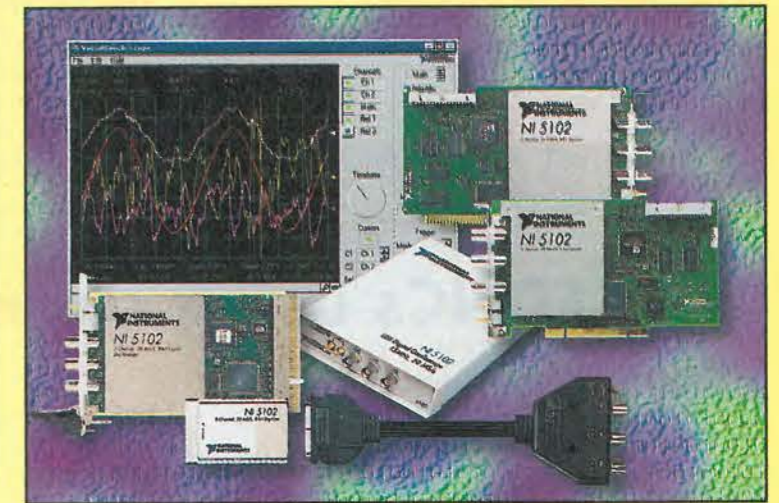
## National Instruments sponsors Circuit Ideas

Over the next 12 months, National Instruments is awarding over £3500 worth of equipment for the best circuit ideas.

Once every two months throughout 2000, National Instruments is awarding an NI4050 digital multimeter worth over £500 each for the best circuit idea published over each two-month period. At the end of the 12 months, National is awarding a LabVIEW package worth over £700 to the best circuit idea of the year.\*



### About National Instruments

National Instruments offers hundreds of software and hardware products for data acquisition and control, data analysis, and presentation. By utilising industry-standard computers, our virtual instrument products empower users in a wide variety of industries to easily automate their test, measurement, and industrial processes at a fraction of the cost of traditional approaches.

### Software

Our company is best known for our innovative software products. The National Instruments charter is to offer a software solution for every application, ranging from very simple to very sophisticated. We also span the needs of users, from advanced research to development, production, and service. Our flagship LabVIEW product, with its revolutionary, patented graphical programming technology, continues to be an industry leader. Additional software products, such as LabWindows/CVI, ComponentWorks, Measure and VirtualBench, are chosen by users who prefer C programming, Visual Basic, Excel spreadsheets, and no programming at all, respectively.

### Hardware

Our software products are complemented by our broad selection of hardware to connect computers to real-world signals and devices. We manufacture data acquisition hardware for portable, notebook, desktop, and industrial computers. These products, when combined with our software, can directly replace a wide variety of traditional instruments at a fraction of the cost. In 1996 we expanded our high-performance E Series product line in PCI, ISA and PCMCIA form factors, shipped our first VXI data acquisition products, and added remote (long-distance) capabilities to our SCXI signal conditioning and data acquisition product line.

Our virtual instrumentation vision keeps us at the forefront of computer and instrumentation technology. National Instruments staff works actively with industry to promote international technological standards such as IEEE 488, PCMCIA, PCI, VXI plug&play, Windows 95/NT, and the Internet. More importantly, we integrate these technologies into innovative new products for our users.

\*All published circuit ideas that are not eligible for the prizes detailed here will earn their authors a minimum of £35 and up to £100.

### National Instruments – computer-based measurement and automation

National Instruments, 21 Kingfisher Court, Hambridge Road, Newbury, Berkshire, RG14 5SJ. Tel (01635 523545), Fax (01635) 524395 info.uk@ni.com www.ni.com

### NI4050

The NI 4050 is a full-feature digital multimeter (DMM) for hand-held and notebook computers with a Type II PC Card (PCMCIA) slot. The NI 4050 features accurate 5<sup>1</sup>/<sub>2</sub> digit DC voltage, true-rms AC voltage, and resistance (ohms) measurements. Its size, weight, and low power consumption make it ideal for portable measurements and data logging with hand-held and notebook computers.

- DC Measurements: 20mV to 250V DC; 20mA to 10A
- AC Measurements: 20mV rms to 250V rms; 20mA rms to 10A rms;
- True rms, 20Hz to 25kHz
- Up to 60 readings/s
- UL Listed
- 5<sup>1</sup>/<sub>2</sub> Digit Multimeter for PCMCIA

### LabVIEW

LabVIEW is a highly productive graphical programming environment that combines easy-to-use graphical development with the flexibility of a powerful programming language. It offers an intuitive environment, tightly integrated with measurement hardware, for engineers and scientists to quickly produce solutions for data acquisition, data analysis, and data presentation.

- Graphical programming development environment
- Rapid application development
- Seamless integration with DAQ, GPIB, RS-232, and VXI
- Full, open network connectivity
- Built-in display and file I/O





# FDNCs using current conveyors

Using two current conveyors, the circuit of Fig. 1, realises the function  $Y_{1-1}(s) = s^2 D$ , where  $D = C_1 C_2 R_1$ . The equivalent circuit consists of a parallel connection of the ideal frequency-dependent negative conductance,  $D$ , capacitance  $C$  and conductance  $G$ .

Parasitic components  $C$  and  $G$  are due to the non-ideal nature of the current conveyors. The stable condition of the circuit requires positive signs for  $C$  and  $G$ . Figure 2 shows computer simulations of the negative conductance  $-\omega^2 D$  and  $C$  dependencies versus frequency. These were carried out for current conveyors constructed according to the Huertas concept<sup>1</sup> using two TL081s, four 100kΩ resistors and two 1kΩ resistors for each conveyor. Component values used were  $C_1 = 0.1\mu\text{F}$ ,  $1\mu\text{F}$ ,  $10\mu\text{F}$ ;  $C_2 = 1\mu\text{F}$  and  $R_1 = 1\text{k}\Omega$ .

In Fig. 2, the stable operation region of the circuit is marked by continuous lines. If capacitance  $C$  is negative the circuit becomes unstable.

The frequency-dependent negative conductance circuit forms a resonant circuit with resistance and can be used in resonant bridges capable of measuring capacitance with high losses, like the frequency-dependent negative resistance circuit used for measuring inductances with high losses<sup>2</sup>.

L. Tomawski, M. Manka, M. Slawiec  
Katowice  
Poland  
C75

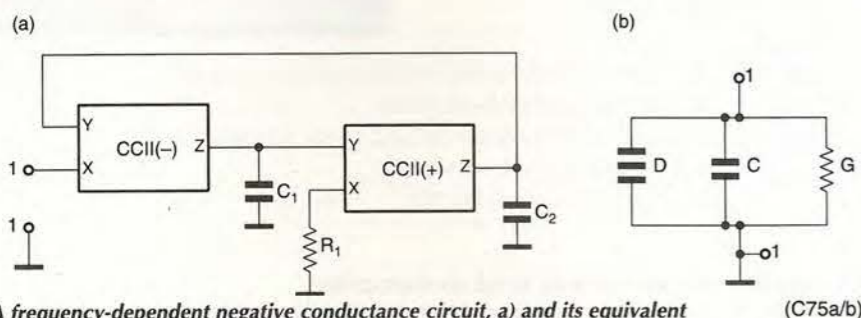


Fig. 1. A frequency-dependent negative conductance circuit, a) and its equivalent circuit, b).

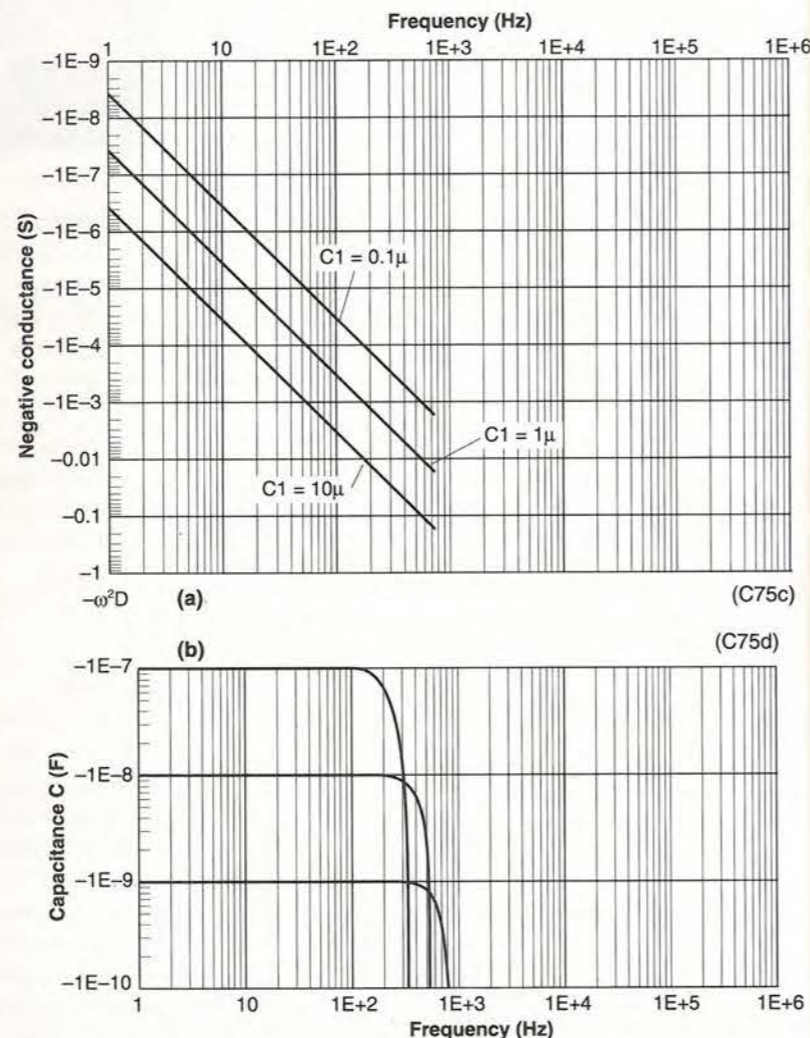


Fig. 2. Computer simulations versus frequency of a) negative conductance  $-\omega^2 D$  and b) capacitance  $C$ .

### References

- Huertas, J L, 'Circuit implementation of current conveyor,' *Electronic Letters* No. 16, 1980, pp. 225-226.
- Tomawski, L, 'Resonant bridge with Frequency Dependent Negative Resistance,' *IEEE Trans. On Instrum. and Meas.* No. 37 March 1988, pp. 45 - 48.

# Efficient battery auto-charger

This efficient automatic battery charger commences charging when the battery voltage reaches the set lower limit and ceases charging when the upper level is reached.

Adjustments are provided for both limits, which are best set up using a variable dc power supply. With the mains supply disconnected, the 'fully charged' voltage of 14.5V dc is applied at the circuit's battery terminals, and  $VR_1$  adjusted so that the relay is energised, cutting off the charging supply.


Next, the variable dc power supply is set to the lower limit of 12.5V dc, and  $VR_2$  adjusted so that the relay de-energises, reconnecting the charging supply. Settings for  $VR_1$  and  $VR_2$  interact, so the adjustments should be iterated as necessary.

An op-amp forms a pseudo window comparator. Its supply is stabilised at 9.1V and a 3.9V reference is applied to its inverting input.

Battery voltage is sensed by divider chain  $R_1, VR_1, R_2$  and applied to the non-inverting terminal. Positive feedback to the non-inverting terminal sets the lower limit at which charging recommences. The circuit can be used for charging various battery types.

Ejaz Ur Rehman  
Islamabad  
Pakistan  
E5

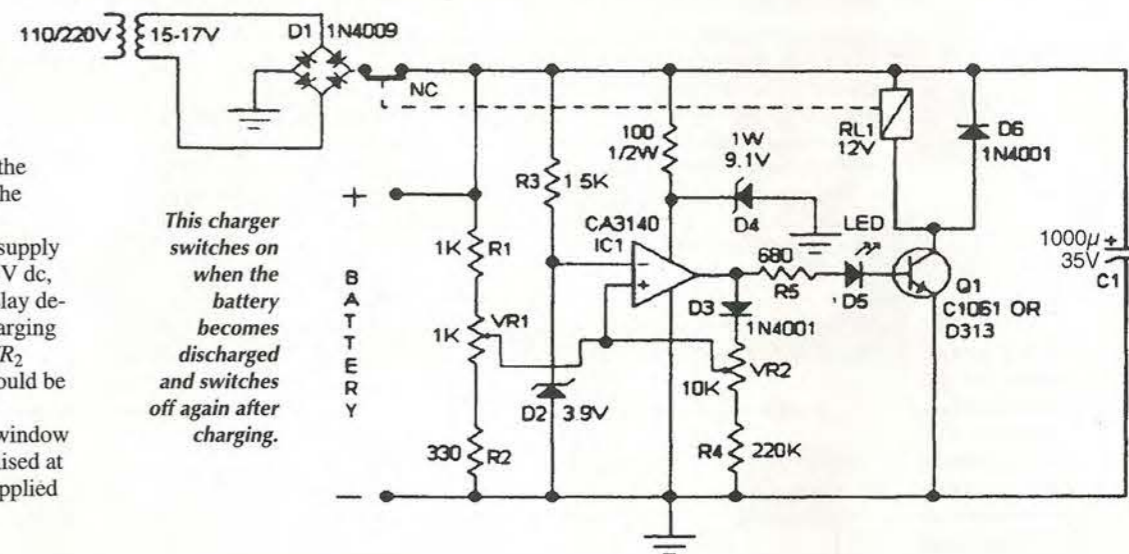Check the charge rate after implementation as it depends on output voltage and regulation of the transformer - Ed.



This charger switches on when the battery becomes discharged and switches off again after charging.

# Ten year index: new update

## Hard copies and floppy-disk databases both available

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past nine years.

The computerised index of *Electronics World* magazine covers the nine years from 1988 to 1996, volumes 94 to 102 inclusive and is available now. It contains almost 2000 references to articles, circuit ideas and applications - including a synopsis for each.

The EW index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512K ram and a hard disk.

The disk-based index price is still only £20 inclusive. Please specify whether you need 5.25in, 3.5in DD or 3.5in HD format. Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

Photo copies of *Electronics World* articles from back issues are available at a flat rate of £3.50 per article, £1 per circuit idea, excluding postage.

Hard copy *Electronics World* indexes on paper for volumes 100, 101, and 102 are available at £2 each, excluding postage.

TABLE OF CONTENTS	
Applications	The Electronics World SoftIndex runs from January 1988 to May 1998 and contains references to 1300 articles and 800 circuit ideas. There is a separate author index with full cross references. Reprints can be obtained for all the articles in this index - see the Information section for more details. For up to date information about Electronics World see our website at <a href="http://www.softcopy.co.uk">http://www.softcopy.co.uk</a> .
Applications by description	
Applications by part numbers	
Company addresses	
Author Index	
Books	
Circuit Ideas	
Information	
Subject Index	
Analogue Design	
Audio	
Avionics	
Broadcast	
Communications	
Components	
Computing	
Consumer Electronics	
Control Electronics	
Digital & DSP Design	
History	
Instrumentation & Test	

Search Report Note About Exit

[www.softcopy.co.uk](http://www.softcopy.co.uk)

### Ordering details

The EW index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders. Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide. For enquires about photocopies etc please send an sae to SoftCopy Ltd. Send your orders to SoftCopy Ltd, 1 Vineries Close, Cheltenham GL53 0NU. Cheques payable to SoftCopy Ltd, please allow 28 days for delivery.

e-mail at [SoftCopy@compuserve.com](mailto:SoftCopy@compuserve.com), tel 01242 241455



# £75 Winner!

## 30W Class-A power follower

At first glance, this circuit may seem familiar. Essentially, it is a typical source follower working in pure Class-A with a constant-current generator forming the load. Features that differentiate it are its negative power supply and small power supply reservoir capacitor.

The current generator has a DC feedback through the BD139 to prevent thermal effects on quiescent

current. Note that this circuit works only in class A, so it needs enough bias current for the required output power.

To keep the power dissipated under static and dynamic conditions the same, I have used identical devices for the follower and current source.



Class-A power amplifiers normally involve a large reservoir capacitor. This causes very high current peaks

in the diodes, which is undesirable.



My circuit has a relatively small capacitor after the bridge. It is followed by a MOSFET voltage regulator featuring a very low frequency CR filter of 220µF/100kΩ.

Components used in the power supply have been simulated and optimised for a 3A quiescent current and with a capacitor value of 3300µF. The 500Ω trimmer should be set to

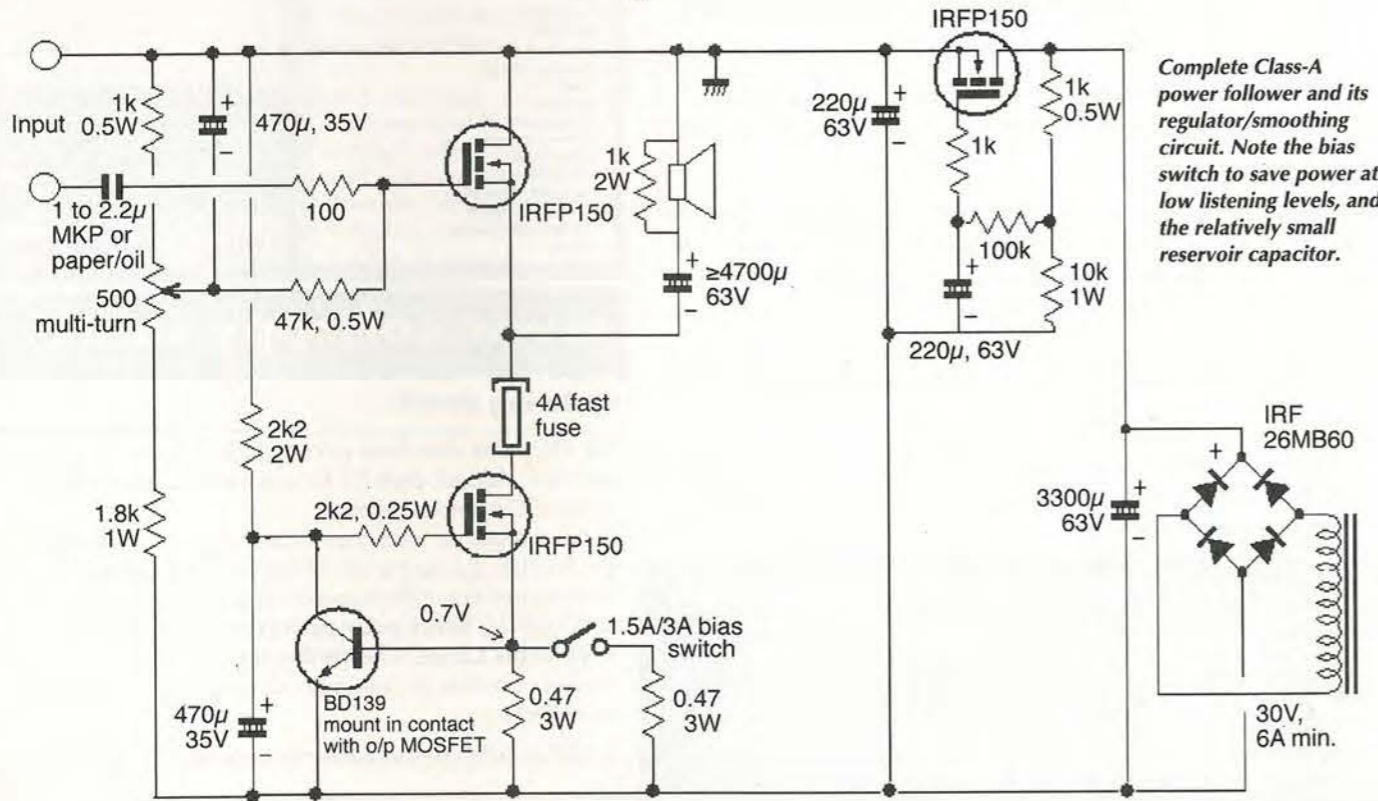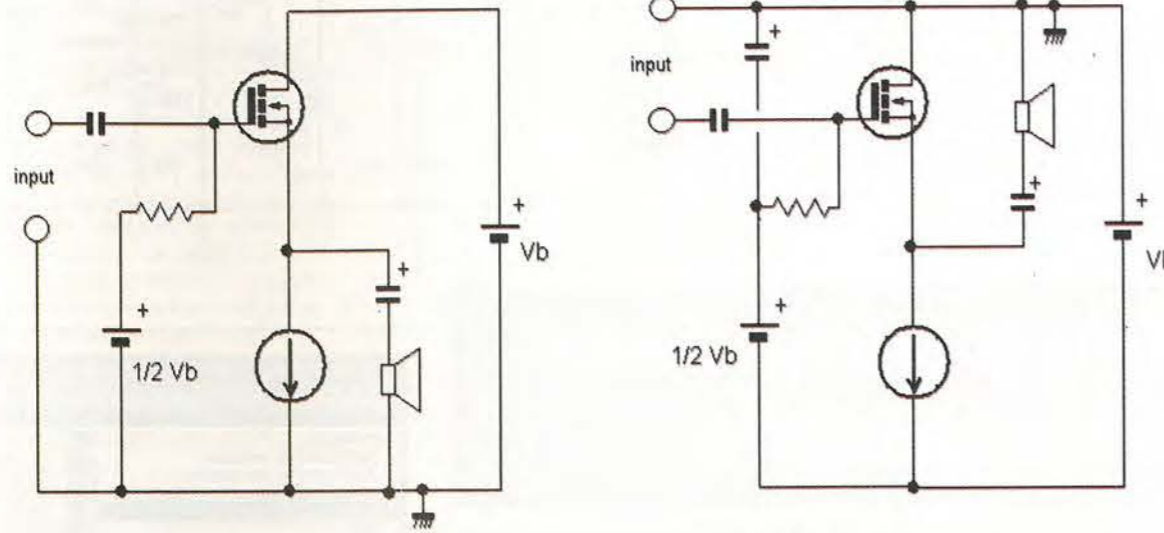Class-A amplifiers normally use the configuration on the left. This power follower uses a negative power supply, as in the right-hand diagram, and the speaker is in parallel with the driving mosfet instead of the current source.



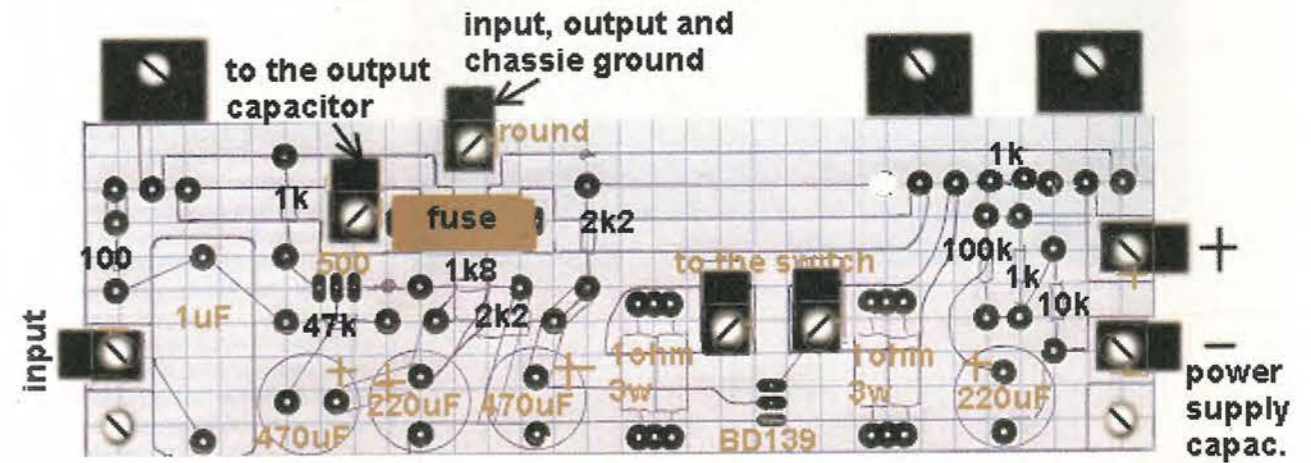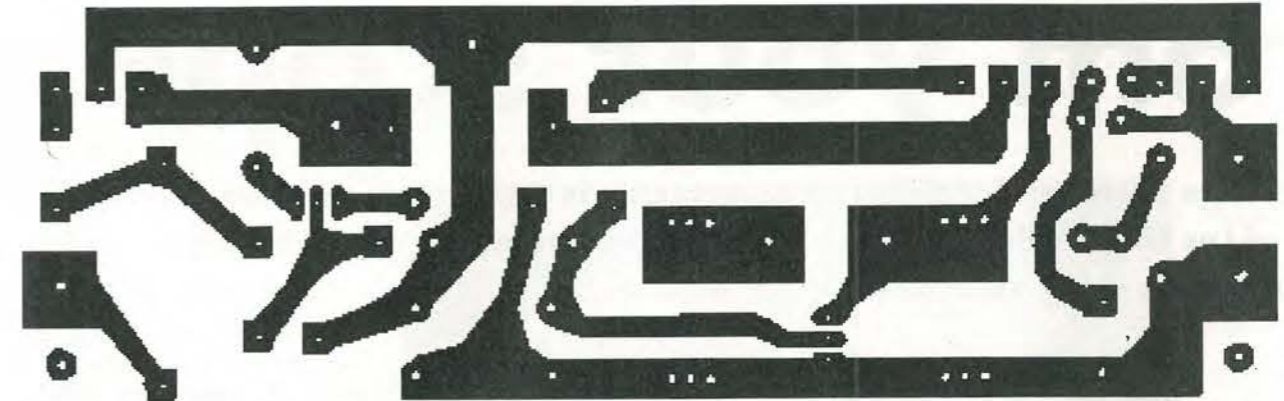Complete Class-A power follower and its regulator/smoothing circuit. Note the bias switch to save power at low listening levels, and the relatively small reservoir capacitor.



balance the output fuse voltage to half the regulator output. This single trim could be done after the switch-on; it simply allows you to get the maximum available output swing.


Quiescent current is set by the resistor at the current generator FET's source. It can be changed using  $I_q = 0.7/R$  where 0.7 is the base-emitter voltage of the BD139.

I added a switch that allows the bias current to be changed. Sometimes I listen to music at low volume so the switch can be used to save power dissipation.

The power supply transformer can have a secondary of anything between 24V and 33V, but you need at least 250VA per channel. If you use a smaller transformer, you will have to reduce the bias current.

With a bias current of 3A you can get about 30W continuous into a 6Ω load. Power can be increased within the limits of the heat sink and power devices.

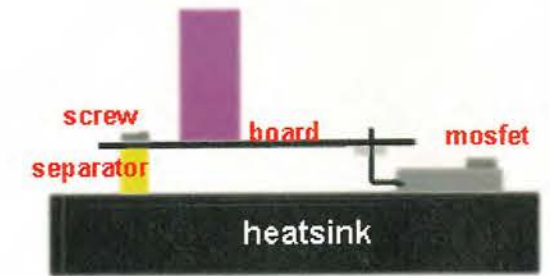My prototype's PCB foil pattern, its layout, and a suggestion for mounting the circuit board on the heat sink.



I suggest using a heat sink of at least 30 by 42 by 16cm, or a smaller one in conjunction with a fan.

In my view, the input capacitor, the 470µF input bypass and the output capacitor affect the sound quality. I prefer to use ELNA Cerafine whenever possible.

Since the circuit has no voltage gain it has to be preceded by a voltage amplifier with an output swing not lower than 10V rms. It should also have an output impedance of less than 1kΩ.

Input impedance of the buffer is

47kΩ/1450pF. Its resistive value can be adjusted over a pretty wide range by just using a different input resistor.

The input capacitance of 1450pF may seem high but a gain stage with a 1kΩ output resistance gives a cutoff frequency of more than 100kHz.

A TO3 equivalent or other similar MOSFETs, such as IRF250s, IRFP250s, IRF240s or IRFP240s, can be used to replace the IRFP150s with a minimal impact.

Andrea Ciuffoli  
Italy  
by e-mail



# Getting the most from your scope

Oscilloscope noise, and making measurements in noisy environments are the topics of Les Green's third article explaining how to make more reliable measurements using your scope.

The noise levels of DSOs and real-time oscilloscopes are not easy for the user to compare. All else being equal, one could reasonably expect a basic

real-time scope to be quieter than a DSO because there are no noisy microprocessors and a-to-d converters to corrupt the trace. So how do you measure the noise

of your scope? If it is a DSO, it is really easy; select a slow time-base, turn on the max-min function and measure the noise band.

If you are the unlucky owner of one of those bandwidth-reducing scopes that I mentioned in my last article, make sure that you compare the noise level with a scope of the reduced bandwidth.

To measure the noise of your real-time scope you can use the Tektronix 'tangential noise' measurement technique. This involves putting the oscilloscope in add-mode and applying a small amplitude quiet square wave to the other channel. The trigger is set to auto so that the untriggered square-wave-plus-noise pattern causes two bright bands to appear on the screen.

By adjusting the square wave amplitude the two bands can be made to merge in a very repeatable manner - when the dark band in the middle just disappears - and the square-wave amplitude is a measure of the noise of the first channel.

At first glance, anyone would complain that the DSO was very noisy compared to the real-time scope; the trace is much narrower on the real-time instrument. The problem here is the conversion from rms to peak-to-peak.

Estimating the peak-to-peak value of a real-time scope trace by eye you may well obtain a value that is twice the rms value. This is  $\pm 2\sigma$  as far as statistical tables are concerned.

Now look at the DSO result: it may be taking 100MS/s over a one-second measurement period and displaying the max-min values. Tables of the Normal/Gaussian distribution do not generally go

above  $5\sigma$ . However, even for this value the tabulated answer is 0.9999997133.

This says that on average 1 acquisition in 3.5 million will exceed the  $5\sigma$  positive peak. I have used MathCad to generate a graph of rms to peak-to-peak conversion factors for Gaussian noise, Fig. 1. In the case of 100MS/s for 1 second the number of samples is  $1E8$ . Reading the graph it says that 95% of the time the peak-to-peak noise level will be greater than  $11\sigma$  and less than  $12.7\sigma$ :  $\sigma$  being the rms value.

Clearly, for a DSO running at this speed a more reasonable conversion factor from rms to peak-to-peak is 12 - a conversion factor of x6 for general purpose work is often used, i.e.  $\pm 3\sigma$ .

Conclusion: a DSO with the same rms noise level as an equal bandwidth real-time scope can have a max-min trace width six times as large!

## Noisy measurements

Regardless of the type of scope used, there is often a problem measuring the actual noise of the circuit. This is due to the connection between the scope and the equipment being probed.

Unless you are using an isolated-input scope, the BNC connectors on the front panel have to be earthed. In order to meet safety standards like EN61010-1 the BNC outers have to be able to take 25A at the supply frequency and present an impedance of less than  $0.1\Omega$ .

As soon as you connect your scope probe earth-lead to the system being tested, a common-mode current flows down the outer braid of the coaxial cable. If the circuit being probed has much high speed logic on it, or a switched-mode power supply, there will be a significant high-frequency content to this common-mode current.

Before connecting your probe to an actual circuit node, try this simple test; clip the probe tip to the earthing crocodile-clip and touch the pair onto a convenient 0V point in the circuit to be probed.

If the noise measured on the scope becomes too large for comfort then you have a noise problem to resolve. This could be due to common-mode current alone or there could be an element of magnetic pickup, as the path from the coaxial cable screen via the probe earth-lead back to the probe tip has quite a large area.

Fortunately both pickup

mechanisms are handled by the same technique. Removing the probe signal clip reveals the probe tip and a metal earthing ring. If the probe earth-lead can be unclipped, do so. If not then just clip it to the probe lead out of the way, so that it does not dangle around and short-out parts of the circuit.

Wind several turns of tinned copper wire - 6 turns of 22SWG for example - around the metal earthing ring of the probe and leave a short tail at the end - not

more than an inch ideally. You can now solder the free tail to a signal earth and probe nearby points, Fig. 2.

It is also possible to use a finer coil of wire to contact the probe tip in order to make a hands-free connection to the circuit. Oscilloscope manufacturers know all about this but the information does not always get through to the user. Tektronix actually sells a little socket to plug probes into, which makes a nice semi-

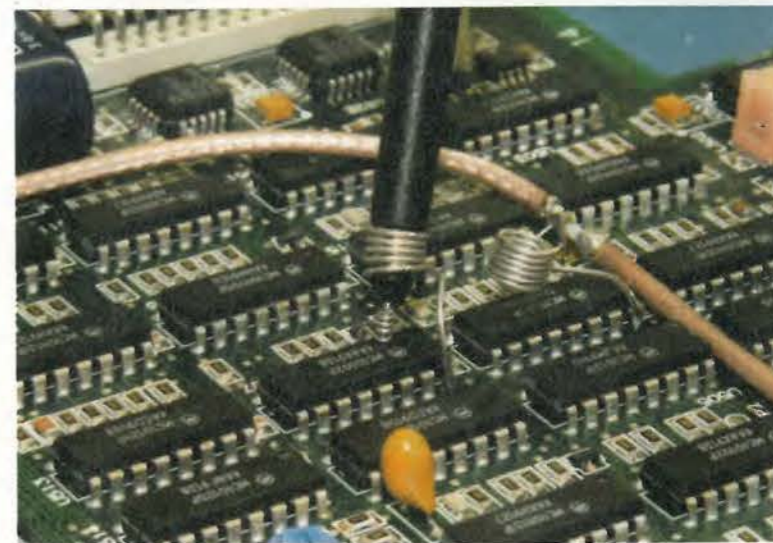


Fig. 2. Measurement technique for high-speed logic and for low-noise measurements. Note the other earthing coil so that pins on the other IC can be manually probed. Use 24SWG for the probe tip coil and 22SWG for the earth coil.


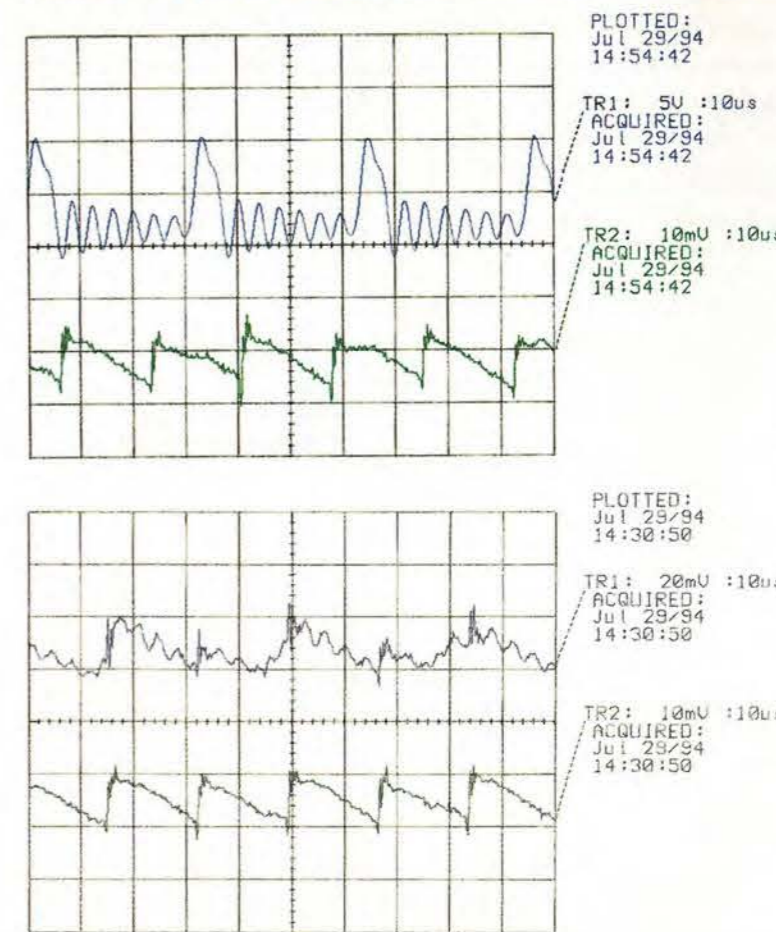


Fig. 3. Two readings of the same signal. Trace TR1 is the measurement with a 10:1 probe negligently placed near a line-output transformer, as in Fig. 5b). Trace TR2 is the same point measured with a coax cable soldered to the underside of the PCB, as in Fig. 5c). Measurements and plots were made on a Gould 475 with 20MHz bandwidth limit selected.

Fig. 4. Trace TR1 is measured with a 10:1 probe in its optimum position, as in Fig. 5a). The second trace is the same point measured with a coaxial cable soldered on the underside of the PCB, as in Fig. 5c). Measurements and plots were made on a Gould 475 with 20MHz bandwidth limit selected.

ptp := 6.046.06. 14

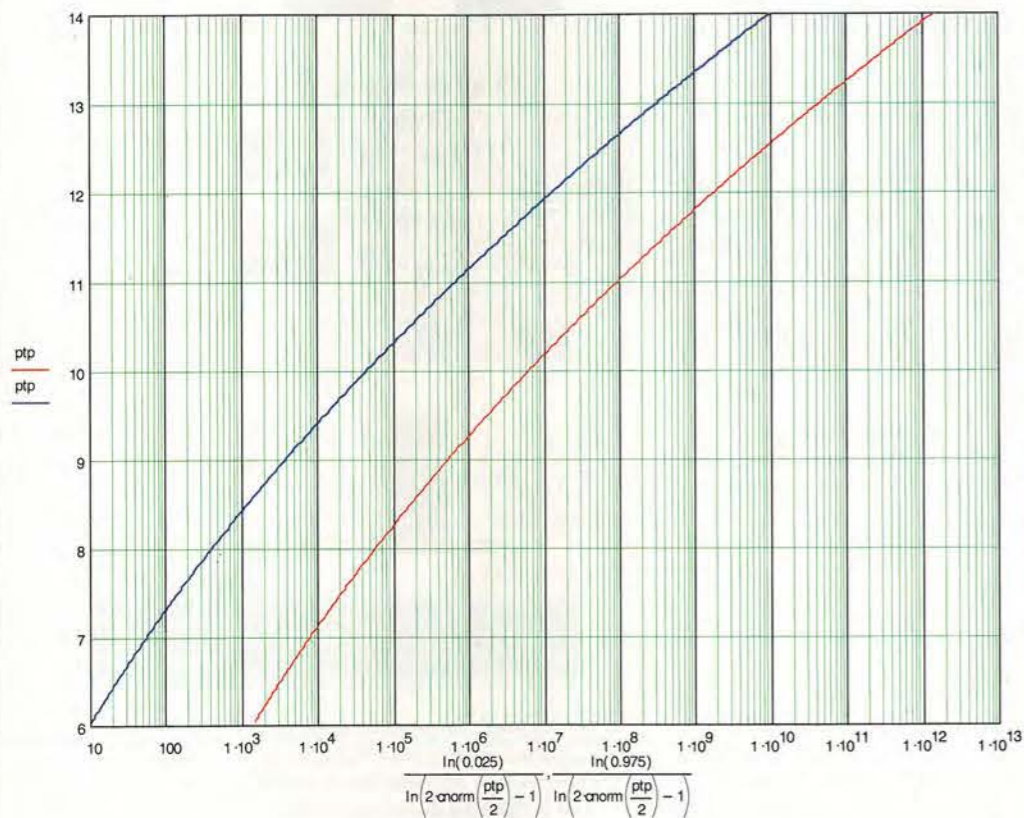

Number of samples required to exceed ptp noise value 2.5% and 97.5% of the time Hence for 95% of the time the ptp value will lie between the two curves.

CNORM is the MathCad cumulative Normal distribution function.  
 Probability of being less than +x is  $cnorm(x)$   
 Probability of being greater than +x is  $(1 - cnorm(x))$   
 Probability of being greater than +x or less than -x is  $2(1 - cnorm(x))$   
 Probability of being less than +x and greater than -x is  $1 - 2(1 - cnorm(x)) = 2 * cnorm(x) - 1$   
 Probability of being <+x and >-x after n trys is  $p = (2 * cnorm(x) - 1) ^ n$   
 Re-arrange in terms of n;  $n = \log(p) / \log(2 * cnorm(x) - 1)$

Fig. 1. MathCad generated graph of rms to peak-to-peak conversion factors for Gaussian noise.





Fig. 5. Power supply and video drive assembly under test. The supply is a flyback converter and the line-output transformer in the centre of the picture is another flyback converter. In a), the 10:1 probe is reasonably well positioned, but in b) it is too close to the line-output transformer. The best solution is to solder a coaxial cable on the underside of the board, c).



permanent probing point for development work. It is manufactured by Specialty Connector Co., of Franklin, Indiana.

There is also such a thing as a spring-loaded probe head that plugs onto the end of a probe with an ATE type of sprung pin for the earth contact.

Even connecting between pieces of equipment via BNC-BNC leads can cause additional noise. Different types of BNC cable can significantly affect common-mode noise performance; the only answer is to try a few different

ones and see which is the best in your application.

Another trick is to use a connection to an unused scope input – or even that funny earthed terminal on the front/back of the scope whose purpose eludes mortal man – as a parallel common-mode current path. The idea is to reduce the common-mode current flowing in the signal coaxial cable, to reduce the measured noise.

For low-noise measurements below 1MHz it is often convenient to do away with the probe entirely and just wire a piece of coaxial cable from your circuit to the scope, Figs 3, 4 and 5.

Use a proper BNC plug to connect to the oscilloscope and at the circuit end make sure that the connection to the coax braided screen is kept short, at less than an inch.

Note that the input capacitance of this arrangement may be around 100pF, depending on the length of the coaxial lead, so it may be necessary to put a 1kΩ resistor in series with the signal input to the coaxial cable. Do *not* put a resistor in series with the screen connection. The 1kΩ resistor will only give an attenuation of 0.1% into a 1MΩ input and the bandwidth will be nicely rolled off to around the 1MHz area.

There is another point to be made about measurements made in the presence of significant amounts of radiated field; it is not necessarily correct to move the probe to the position of minimum noise displayed on the scope screen. It is possible that the radiated noise can be made to cancel out some of the actual noise that exists on the point being measured. The measurement technique should be such that this type of cancellation is avoided. ■



**Unique reader offer:**  
**x1, x10 switchable**  
**oscilloscope probes,**  
**only £21.74 a pair,**  
**fully inclusive\***

\*Additional pairs as part of the same order, only £19.24 each pair.

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.


To order your pair of probes, send the coupon together with £21.74 UK/Europe to Probe Offer, Electronics World Editorial, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Readers outside Europe, please add £2.50 to your order.

**Specifications**

<b>Switch position 1</b>	
Bandwidth	DC to 10MHz
Input resistance	1MΩ – i.e. oscilloscope i/p
Input capacitance	40pF+oscilloscope capacitance
Working voltage	600V DC or pk-pk AC
<b>Switch position 2</b>	
Bandwidth	DC to 150MHz
Rise time	2.4ns
Input resistance	10MΩ ±1% if oscilloscope i/p is 1MΩ
Input capacitance	12pF if oscilloscope i/p is 20pF
Compensation range	10-60pF
Working voltage	600V DC or pk-pk AC
<b>Switch position 'Ref'</b>	
Probe tip grounded via 9MΩ, scope i/p grounded	

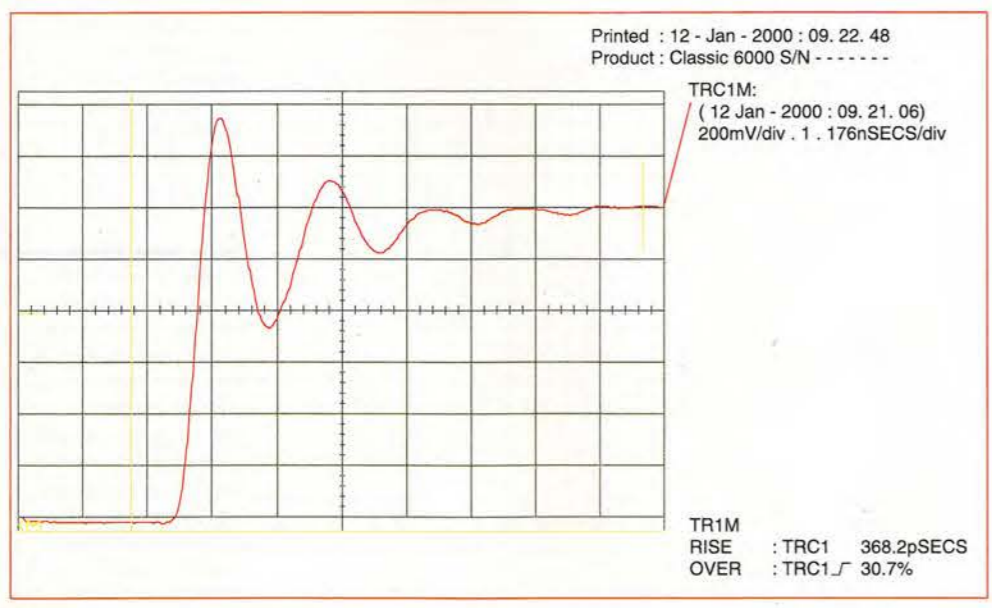**The best of both worlds**

This is the pulse response of an amplifier in development. It is being driven with a 200ps edge and being measured on an analogue sampling oscilloscope system, namely a Tektronix S-2 sampling head in a 7S11 sampling unit. To get cursor readouts and a stored trace, the analogue output of the 7S11 is fed into a Gould 6100 storage oscilloscope. Using averaging and measurement scaling, the 6100 is calibrated to give the correct rise time.



Please supply the following:

**Probes** \_\_\_\_\_ Total \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_ Telephone \_\_\_\_\_

Method of payment (please circle)

**Cheques should be made payable to Reed Business Information**

Access/Mastercard/Visa/Cheque/PO \_\_\_\_\_

Credit card no \_\_\_\_\_

Card expiry date \_\_\_\_\_ Signed \_\_\_\_\_

**Please allow up to 28 days for delivery**





## Room for improvement II

The listening room has a surprisingly significant effect on the loudspeaker. Last month, John Watkinson considered its effects at low frequencies. Here, he discusses how the room affects the rest of the spectrum.

# SPEAKERS' CORNER

A real sound source in a real environment produces a combination of direct sound and reflected sound.

The human hearing mechanism has evolved to locate the sound source accurately, despite the reflections, and to assess the nature of the environment from the reflections. If either the source or its reflection is absent, there will be a lack of realism.

In principle, a stereo recording can capture sound from any direction,

but the conventional stereo pair of speakers can only create virtual sound sources over an arc between the speakers. The 360° sound field will be mapped into that arc in the way the recording engineer thought best.

Clearly, listening to a sound field of restricted angle is not the same as listening to a 360° sound field. Fortunately the reverberation of the listening room can to some extent make up for the loss. Thus reverberation is essential in the

listening room to create a natural result.

Note that the listening room can never create the same reverberant field as the original venue with only a stereo signal pair; but then this is not the goal. Reverberation is chaotic and provided it comes from all around the listener and has no gross defects, it will be accepted as plausible by the ear and the reproduction will appear more realistic.

In the case of surround sound,

more channels are available. In principle, sound can be reproduced from any number of directions. But the argument still applies that with a finite number of channels, reverberation in the listening room is still necessary to create a continuous sound field from a set of discrete sources.

### See for yourself

In a domestic listening environment it is surprising how much of the sound we hear is reverberant. This is very easily demonstrated with any dipole loudspeaker – a Quad electrostatic for example.

In Fig. 1a) the speakers are in a normal listening position. In Fig. 1b) a large pair of cushions has been placed in front of the speakers and in Fig. 1c), they have been placed behind the speakers.

The results are non-intuitive. In practice position Fig. 1b) sounds better than position Fig. 1c). This is because blocking the front radiation allows the rear radiation to excite the reverberation in the room. Blocking the rear radiation makes the speaker sound dull.

One of the great advantages of the electrostatic speaker is that it is inherently a dipole and the excitation of the room comes free. However, the same results will be obtained if the speaker contains moving-coil units facing forward and backward. Certain Bose satellite speakers contain two tweeters that can be swivelled into such an arrangement.

### Tweeters fore and aft

For experimentation, the moving coil speaker with tweeters facing

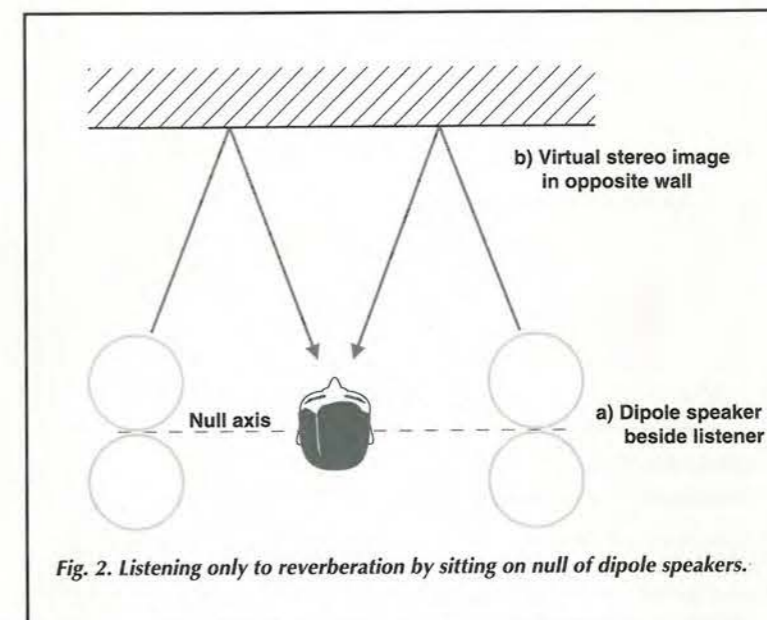


Fig. 2. Listening only to reverberation by sitting on null of dipole speakers.

forwards and backwards has the advantage that it is very easy to switch between a dipole and an omnidirectional radiation pattern simply by swapping the wires on the rear driver.

Despite the theories put forward about the massive differences in the excitation of the room between these two configurations, the simple fact is that in practice the skilled listener is hard pressed to tell which configuration is in use. There is no effect at all on the stereo image heard between the speakers; in fact this is still retained if one of the rear speakers is anti-phase and the other is in-phase.

For a moving coil system, having the tweeters working in phase as an omnidirectional source has the advantage that the low-frequency

roll off due to cancellation is avoided. This means that a lower and less audible crossover frequency can be used.

Another surprising result using dipole speakers is shown in Fig. 2a). Here, a pair of dipoles has been placed at either side of the listening position and adjusted so the listener's ears are in a null.

No direct sound at all reaches the listener from the speakers. A virtual stereo image will be heard in the opposite wall as shown in Fig. 2b).

Both of these examples illustrate just how much of the sound we hear is reverberant. As a result, it follows that an additional criterion for a precision loudspeaker is that as well as creating an accurate waveform on a direct path to the ear, it must also create a sufficiently accurate reverberant field.

This critical aspect of loudspeaker design has been obvious from psychoacoustic considerations for many years but the traditional loudspeaker industry, with a few notable exceptions, has passed it by.

### Why do loudspeakers sound so different?

It is well known that loudspeakers with identical specifications sound different. There is only one conclusion to be drawn from that, which is that the specifications are incomplete.

In short, the traditional ways of testing loudspeakers only give part of the picture. It's like testing cars in a straight line and then wondering



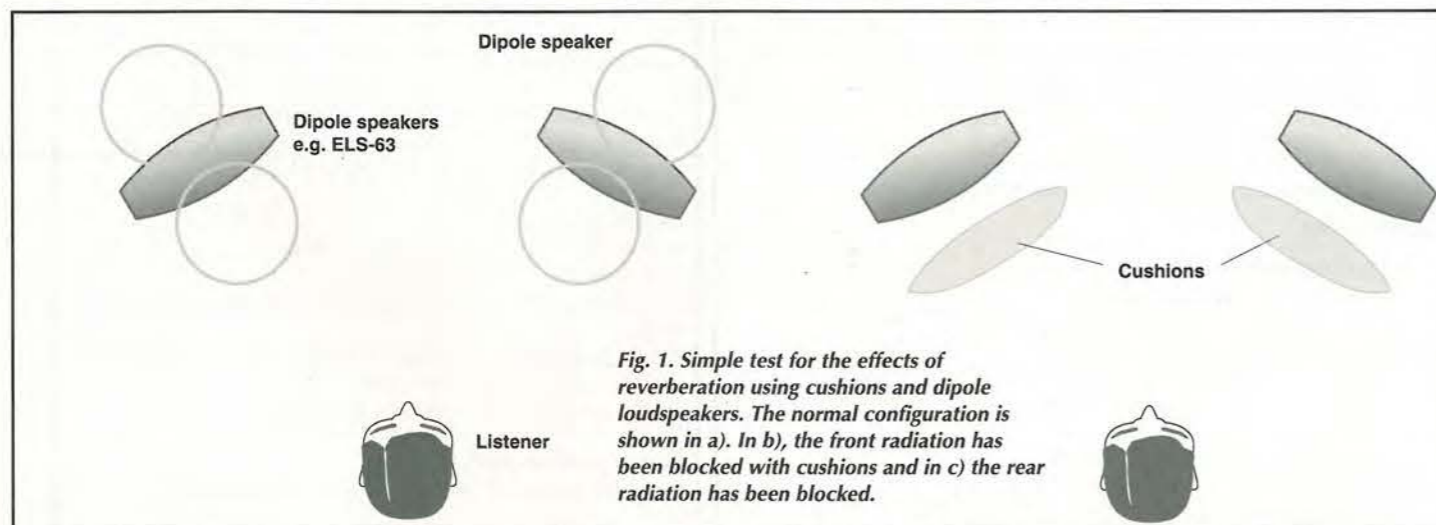


Fig. 1. Simple test for the effects of reverberation using cushions and dipole loudspeakers. The normal configuration is shown in a). In b), the front radiation has been blocked with cushions and in c) the rear radiation has been blocked.

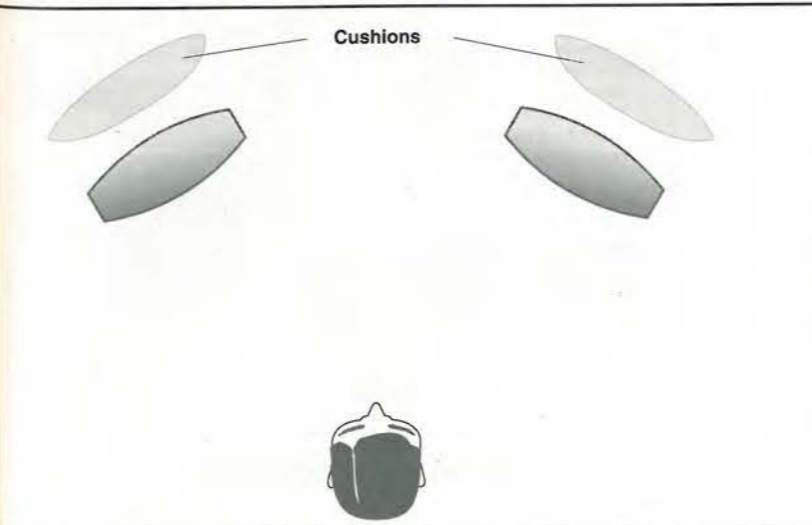

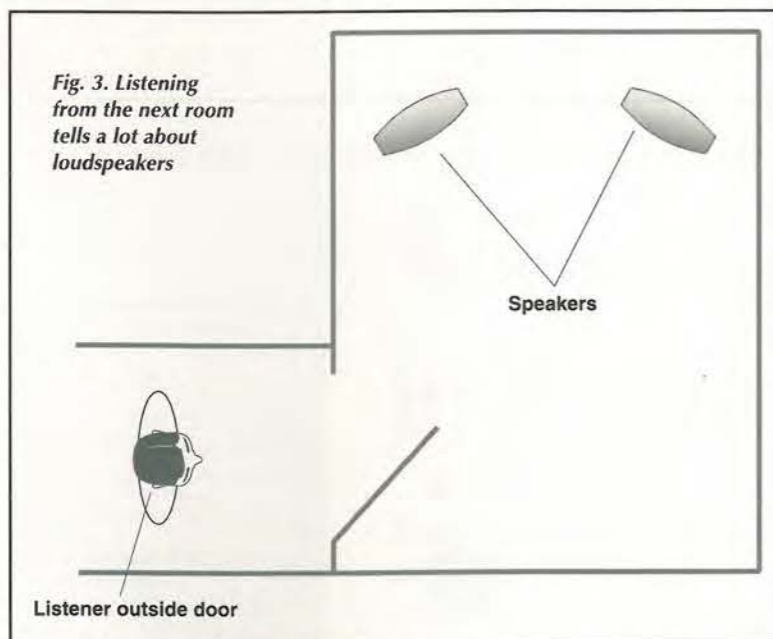



why they corner differently.

In any other industry, a disparity between theory and practice results in research to advance the theory

and close the gap. Why the audio industry should make itself a conspicuous exception could be the subject of a long discussion.

There is a trivially easy way of demonstrating the aspect of loudspeakers which makes them sound different. This is to listen from the next room via an open door and compare the tonal quality or timbre outside the room with that at the ideal listening position. Figure 3 shows the principle.

Without exception, the loudspeakers that sound the most tonally balanced in the next room are the ones that sound most realistic in the ideal listening position. Also, without exception, the loudspeakers that perform best are those that have had some thought given to the quality of the off-axis sound that they produce.

The constructional philosophy of the speaker seems to be more important here than the amount spent or the transduction principle.

The importance of off-axis sound quality in a loudspeaker cannot be underestimated. In my next article, I will explore the consequences of getting it wrong ■

## ADVANCED ACTIVE AERIAL



The aerial consists of an outdoor head unit with a control and power unit and offers exceptional intermodulation performance: SOIP +90dBm, TOIP +55dBm. For the first time this permits full use of an active system around the lf and mf broadcast bands where products found are only those radiated from transmitter sites

- General purpose professional reception 4kHz-30MHz.
- -10dB gain, field strength in volts/metre to 50 Ohms.
- Preselector and attenuators allow full dynamic range to be realised on practical receivers and spectrum analysers.
- Noise - 150dBm in 1Hz. Clipping 16 volts/metre. Also 50 volts/metre version.
- ★ Broadcast Monitor Receiver 150kHz-30MHz. ★ Stabilizer and Frequency Shifters for Howl Reduction ★ Stereo Variable Emphasis Limiter 3 ★ PPM10 In-vision PPM and chart recorder ★ Twin PPM Rack and Box Units. ★ PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and meter movements ★ Broadcast stereo coders ★

### SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh, Surrey GU6 7BG.  
Telephone: 01483 275997. Fax: 276477.

## The Source for Electrical Professionals

### MULTIMETERS

Models with True RMS, Datalogging, Graphical display, and PC interface & software. Measurements include Temperature, Capacitance, Duty Cycle, Power, and Phase.

### CLAMP-ONS

Models with True RMS, Datalogging, and PC interface & software. Measure to 2500 Amps, V, Ohms, Power, Temperature and more.

### INSULATION TESTERS

Measure to 2000Mohm, Test Voltages of 250, 500, 1000V. Features include voltage and resistance measurements.

## EXTECH INSTRUMENTS


For information on the range of products contact:

Technical & General Ltd.,  
Parkway House 101, Sheen Lane, London SW14 8LS  
Phone: 020 8392 6980 Fax: 020 8392 6999 Technical-General@Cableinet.co.uk



CIRCLE NO.111 ON REPLY CARD

# BOOK TO BUY

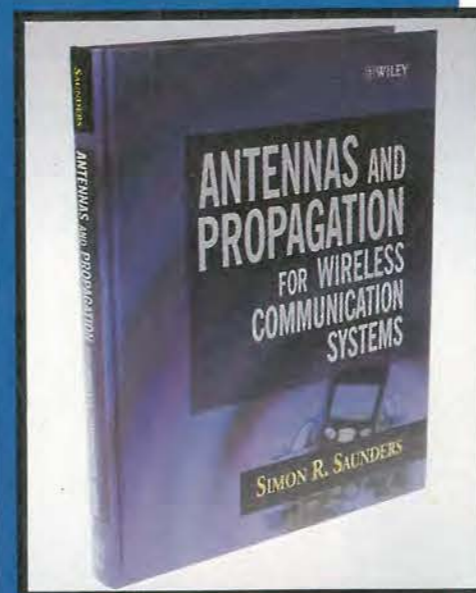

## Antennas and Propagation for Wireless Communication Systems

Antennas and propagation are the key factors influencing the robustness and quality of the wireless communication channel. This book introduces the basic concepts and specific applications of antennas and propagation to wireless systems, covering terrestrial and satellite radio systems in both mobile fixed contexts.

Including:

- Illustrations of the significance and effect of the wireless propagation channel
- Overview of the fundamental electromagnetic principles underlying propagation and antennas
- Basic concepts of antennas and their application to specific wireless systems
- Propagation measurement modelling and prediction for fixed links, macrocells, microcells, picocells and megacells
- Narrowband and wideband channel modelling and the effect of the channel on communication system performance
- Methods that overcome and transform channel impairments to enhance performance using diversity, adaptive antennas and equalisers.

*Antennas and propagation* is a vital source of information for wireless communication engineers as well as for students at postgraduate or senior undergraduate levels.

Distinctive features of this book are:

- Examples of real world practical system problems of communication system design and operation
- Extensive worked examples
- End of chapter questions
- Topical and relevant information for and about the wireless industry

### CONTENTS

Introduction: The Wireless Communication Channel • Properties of Electromagnetic Waves • Propagation Mechanisms • Basic Propagation Models • Terrestrial Fixed Links • Satellite Fixed Links • Macrocells • Shadowing • Narrowband Fast Fading • Wideband Fast Fading • Microcells • Picocells • Megacells • Diversity • Equalisers • Adaptive Antennas • Future Developments in the Wireless Communications Channel • Appendices

416pp £39.95

### How to pay

I enclose a cheque/bank draft for £ \_\_\_\_\_ (payable to Reed Business Information)

Please charge my credit/charge card

Mastercard  American Express  Visa  Diners Club

Credit Card No: \_\_\_\_\_

Expiry Date: \_\_\_\_\_

Signature of Cardholder \_\_\_\_\_

Send my order to: (please use capitals)

Name \_\_\_\_\_

Address \_\_\_\_\_

Post Code \_\_\_\_\_ Tel: \_\_\_\_\_

Fax: \_\_\_\_\_ Date \_\_\_\_\_

Please allow up to 28 days for delivery

Post your completed order form to:  
Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Phone your credit card order:  
020 8652 3614

Fax your completed order form to  
020 8652 8111

email: jackie.lowe@rbi.co.uk

POSTAGE FREE

For air delivery add £5.50 postage



# Hands-on Internet



# Phase-locked loops

Revealing useful web sites along the way, **Cyril Bateman** explains the phase-locked loop and discusses the options and design tools available for those involved with this invaluable building block.

Three years ago while researching for a phase-meter design, I surveyed the Internet for information on phase-locked loops. Since then, the drive to provide ever faster computer systems<sup>1</sup> has resulted in an explosion in the use of phase-locked loop integrated circuits. This is reflected in the much increased amount of phase-locked loop information and design aids now available for downloading.

A search of the Philips Semiconductors site alone brought up

407 matches for the phrase 'PLL'. But why search Philips first? Perhaps a brief look at the history of phase-locked loops will explain.

### Phase-locked loop roots

The phase-locked loop concept was first proposed in 1922.

Probably the first ever general use of a phase-locked loop was in a 'homodyne' radio receiver in the 1930s. It was in the 1950s though that the rapid expansion of television receivers saw the universal adoption

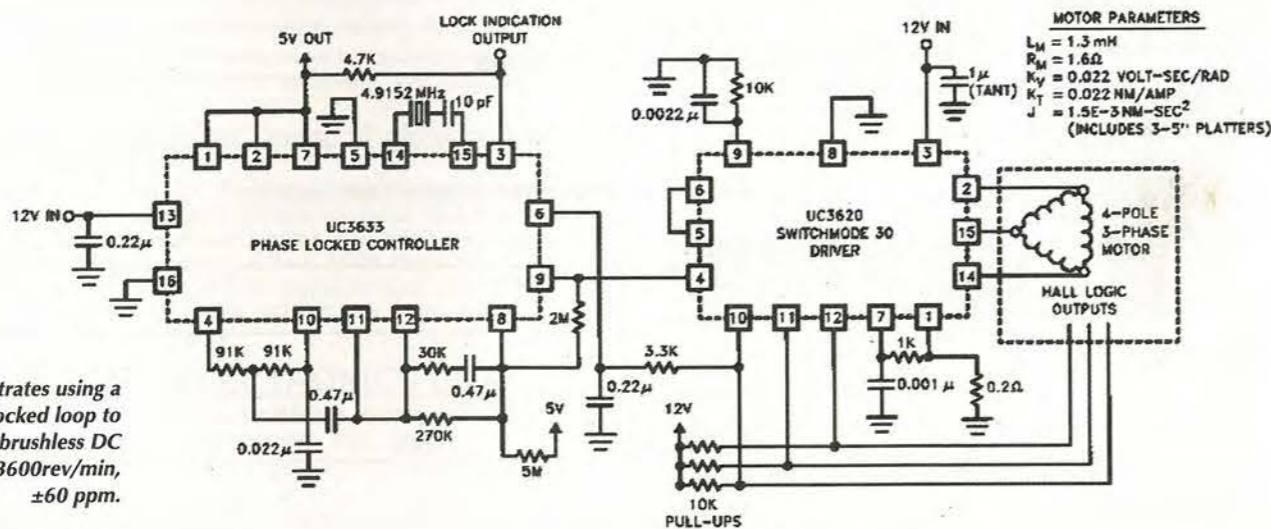


Fig. 1. Illustrates using a phase-locked loop to spin a brushless DC motor at 3600rev/min, ±60 ppm.

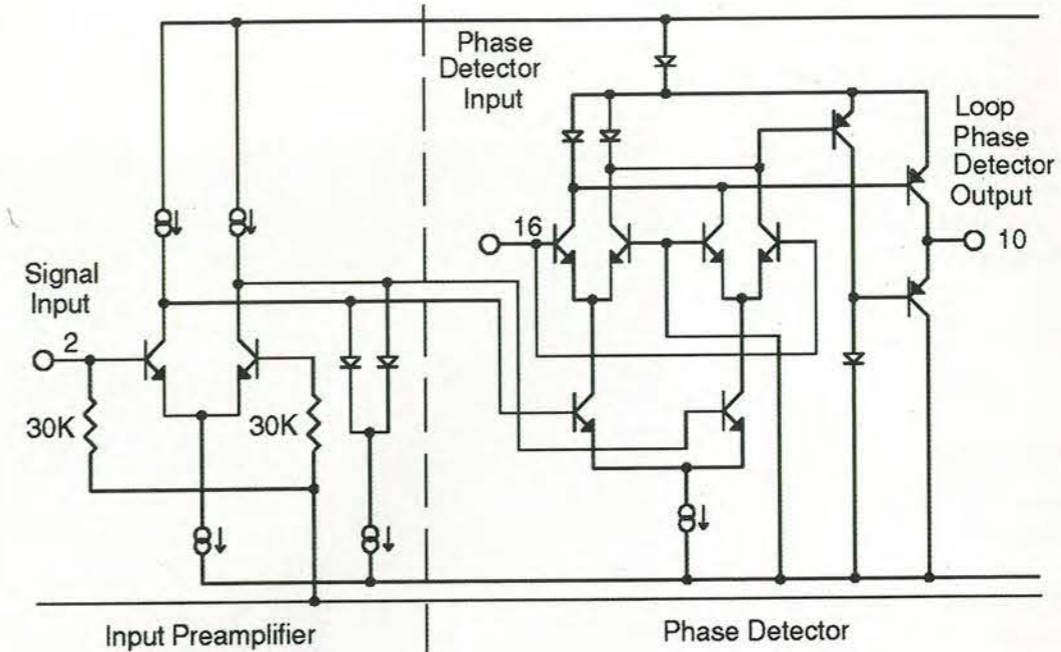


Fig. 2. Preamplifier and phase-locked loop schematics as used in the EXAR XR-2212 precision PLL integrated circuit. This illustrates use of a double-balanced mixer, or analogue phase locked loop.

of phase-locked loops. PLLs were used in tv sets to synchronise the 'frame' and 'line' oscillators to the incoming signals – the so-called 'fly-wheel sync' circuit.

Signetics claims to have produced the first ever dedicated phase-locked loop integrated circuits in the spring of 1970. These were selected as one of the hundred most significant technical products by the Industrial Research Institute in 1971.

Two other notable firsts that I recall were a phase-locked stereo decoder<sup>2</sup> and a phase-locked-loop fm tuner.<sup>3</sup> Both were published by *Wireless World*.

Today, phase-locked loops can be used to modulate and demodulate AM, FM, FSK and BPSK signals. They can detect the presence of specific frequencies buried in noise and produce voltage controlled frequencies or precise clock signals.

Phase-locked loops can also restore signal waveforms that have been distorted using fibre optic links and they can precisely control the speed of electric motors. In addition, PLLs are useful for restoring the timing waveforms when reading floppy and hard disk drives... the list is endless. Figure 1 is an example of a precise motor drive.

### Designing with PLLs

The 'flywheel' analogy is used to explain phase-locked loop behaviour

in application note AN177. Entitled 'An overview of the phase-locked loop,' this note downloads relatively quickly.<sup>4</sup> I commend this as a first read for those of you wanting a simple, readable introduction to the topic.

A much longer 123 page technical article, which is complete with all needed equations and called 'Dean's Book', can be downloaded from National's web site.<sup>5</sup>

The phase detector used in the original Signetics phase-locked loop designs was based on the double balanced mixer circuit. When this method of phase detection is used, the complete integrated circuit is labelled as an 'analogue' phase locked loop, even though it may also include many digital stages.

Analogue phase detectors can be used with both small and large input signals and at very high frequencies. A good detailed description of the analogue phase detector, entitled 'Modelling the PLL double-balanced mixer' can be downloaded as application note AN178.<sup>4</sup> Figure 2 is an example of an analogue phase-locked loop from inside an Exar XR2212.

Many of the most popular integrated phase-locked loops use a digital phase detector. For this reason, they are labelled as 'digital' phase-locked loops, even though analogue stages may be included.

Perhaps the best known and widely used is the CMOS 4000 series 4046

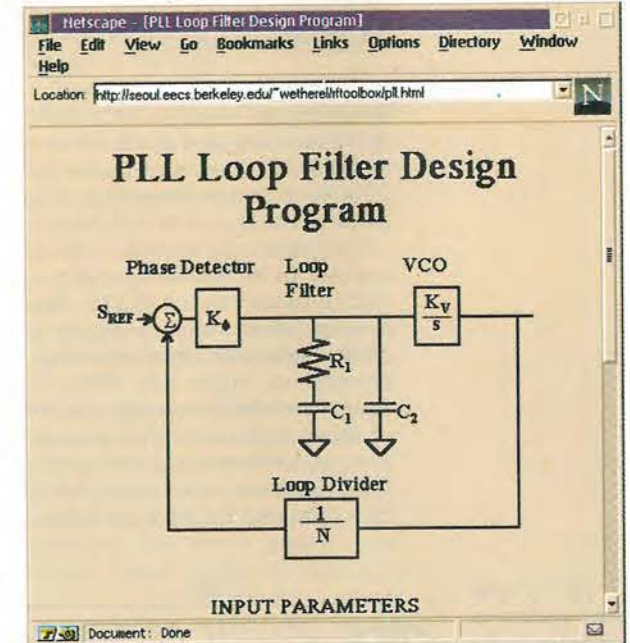


Fig. 3. An easy to use, on-line design aid that designs the loop filter for you, in response to your required parameters.


integrated circuit. While the maximum operating frequency of this particular circuit is restricted, other designs can be used at 100MHz and above.

### Three types of digital phase detector

Three common types of 'digital' phase detector circuits are in use.



Fig. 4. A screen shot of the phase-lock-loop simulator, one module in the EagleWare Genesys software package.

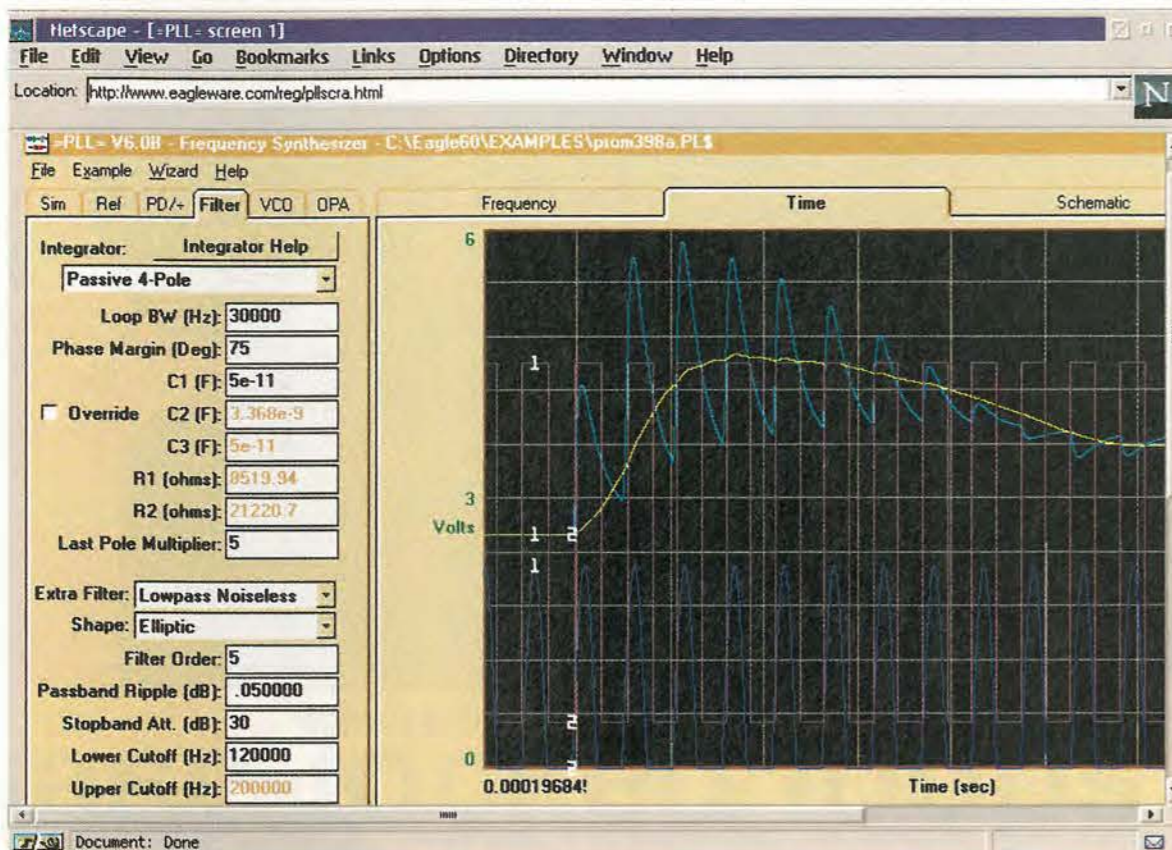

Sometimes all three types are included in the one integrated circuit. Since it includes all three, I will use the 74HC4046 as an example here. This device is usable to some 15MHz.

The simplest digital phase detector is based on the exclusive-or circuit, and is similar to a 74HC86. This detector, which should be driven by 50-50 mark-space input waveforms, provides an output zero when the input waveforms are exactly 90° out of phase. Its output is then a square wave at double the frequency of the input signal and with a duty cycle of 50%. The actual duty cycle of this

output waveform varies according to the phase difference of the input signals.

The second style of phase detector is effectively a digital memory network comprising four bistable devices, some gate logic and a tri-state output. These bistable devices act only on the rising edges of the input signals, so this detector works independently of the input signal's duty cycle.

When both input signals have the same phase, the tri-state output becomes a high impedance. Its output becomes a logic high or logic low only while the signal phases differ.

The third type of phase detector is again positive-edge triggered, so is also independent of the input signal duty cycles. Based on an RS flip-flop, it outputs a square wave at the input signal frequency with a duty cycle that varies with phase difference.

When the input signals have a 180° phase difference, this detector output waveform has a 50% duty cycle.

#### Designing loop filters

You can see from the above that for most applications, the phase detector output must be filtered. This filter may be active, or more simply can be

#### Where to browse

1. High-speed PLL chips ease transition to faster processors. <http://devel.penton.com/ed/Pages/magpages/sept0198/analog/0901ao2.htm>
2. Phase-locked Stereo Decoder, R.Portus & A.Haywood, 'High fidelity designs,' pub. *Wireless World* 1974
3. A phase-locked loop fm tuner, J. Linsley-Hood, *Wireless World* annual 1975.
4. Philips Semiconductors <http://www-us.semiconductors.philips.com>
5. National Semiconductors <http://www.national.com>
6. Electronic Design/Development Software <http://mypage.uniserve.ca/~gludwig/electron/software.htm>
7. Electronic Design <http://www-inst.eecs.berkeley.edu/~wetherel/rftoolbox/rfdesign.html>
8. PLL Loop Filter Design Program <http://seoul.eecs.berkeley.edu/~wetherel/rftoolbox/pll.html>
9. Interactive Digital Phase Locked Loop Design <http://www-users.cs.york.ac.uk/~fisher/mkpll>
10. Eagleware Corporation <http://www.eagleware.com>
11. SPICE Tools Provide Behavioral Modeling of PLL. <http://sites.penton.com/mwrf/libraypenton/archives/mrf/November1997/501.htm>
12. MC145170 PSpice Modeling Kit <http://www.mot-sps.com/lit/html/PLL.html>

based only on passive components.

Correct filter design however is most important for successful circuit operation. Filter design can prove time consuming if done iteratively. Solving the mathematical design equations can prove tedious.

Three years ago I found only one design aid available for downloading. This was version 2 of the 'HCMOS phase-locked loop design program,' which I downloaded from the Philips site.

When I looked again this January, I was unable to locate it, but I did manage to find an earlier version.<sup>6</sup> This is a DOS-based program that allows you to explore 'what if' designs for the Philips HC/HCT4046/7046 and HCT9046 phase locked loops by answering a few simple questions.

With little effort, I managed to find several other design and simulation aids. One particularly helpful page I found was on a university site.<sup>7</sup> It covered many other topics besides phase locked loops. In fact, it was so useful that I bookmarked it.

When I looked again this January, I was unable to locate it, but I did manage to find an earlier version.<sup>6</sup> This is a DOS-based program that allows you to explore 'what if' designs for the Philips HC/HCT4046/7046 and HCT9046 phase locked loops by answering a few simple questions.

#### On-line design aids

Some sites now offer on-line design aids for phase-locked loops. I found the first one on the Berkeley site. It provided an easy to use on-screen representation of a phase-locked loop, especially suited to first time users, Fig. 3.<sup>8</sup>

I also found an interesting and interactive on-line package on the UK's University of York web page. Written in Java code, this provides performance graphs in addition to calculating design values.<sup>9</sup> Many designers though will prefer the convenience of having their design tools stored within their own computer.

National Semiconductor<sup>5</sup> offers three software packages as part of its series of application notes for the design of wireless systems. The first

is a Windows program, titled 'Windows Loop Filter Design'. This 3Mbyte download helps with the design of loop filters.

The second is a smaller DOS program, entitled EasyPLL, which assists with component selection and designs and simulates the loop filter performance.

National's final offering is a number of miscellaneous phase-locked loop models to aid loop design and simulation. Many of these can only be run via Mathcad 7. Since I only have an older version of Mathcad, I was unable to try these out.

#### High-frequency applications

While the various Spice time-domain based simulators are extremely popular, many have restricted capability when performing analysis of high-frequency circuits. Historically high-frequency design has been based on frequency domain and harmonic balance simulators.

One phase-locked loop design module dedicated to rf design is Genesys from the EagleWare Corporation<sup>10</sup>. The EagleWare system is a complete system of design tools, targeted to RF designers' needs. These can be purchased either as separate modules or a package.

There are eleven modules in the full Genesys package. These include schematic entry, simulation, RF and conventional layout, filter synthesis, as well as the dedicated PLL module.<sup>4</sup>

Using PSpice analogue behavioural modelling techniques, a method of simulating the performance of digital phase-locked loop systems running at several hundred megahertz has been devised by Spanish RF engineer Orlando Pena.<sup>11</sup> This routine was developed using the PSpice simulator in version 7.1 of the Microsim DesignLab.

I have found this version of PSpice is particularly useful. While aimed at Windows 95 or Windows NT, provided the Win32S v1.3 extensions have been installed, it will run on a modest 486PC with Windows 3.1x operating systems.

The particular phase-locked loop he modelled was based on a digital phase-frequency detector, as used in the Motorola MC4044 integrated circuit. It has an analogue charge pump, which Orlando based on the Spice models for 2N222 and 2N2907 transistors, as the output.


Potentially even more useful is the 'MC145170 PSpice Modelling Kit' because the full Spice models used have been included. This is described in application note AN1671, which can be downloaded from the Motorola web site.<sup>12</sup> While the models included in this note are specific to this Motorola part, it does include sufficient background information to help you develop models for other integrated circuits.

#### Frequency synthesis

The MC145170 is a PLL frequency synthesiser integrated circuit complete with serial communications, reference oscillator, phase detector and counters. The phase detector and charge pump circuits are similar to those assumed for the Pena article, except for the models used for the charge pump. These simulate the actual devices used in the MC145170, Fig. 5.

The note also includes details of model changes needed to enable these simulations to be made using only the evaluation version libraries supplied with PSpice. I particularly liked the section that advised on providing for component and circuit board parasitics. When these parasitics have been overlooked, the measured results of a practical circuit and its Spice simulations will not agree. ■

Fig. 5. Digital phase detector as modelled for the 'MC145170 PSpice modelling kit'. This detector can be assembled and simulated using only standard PSpice model elements.

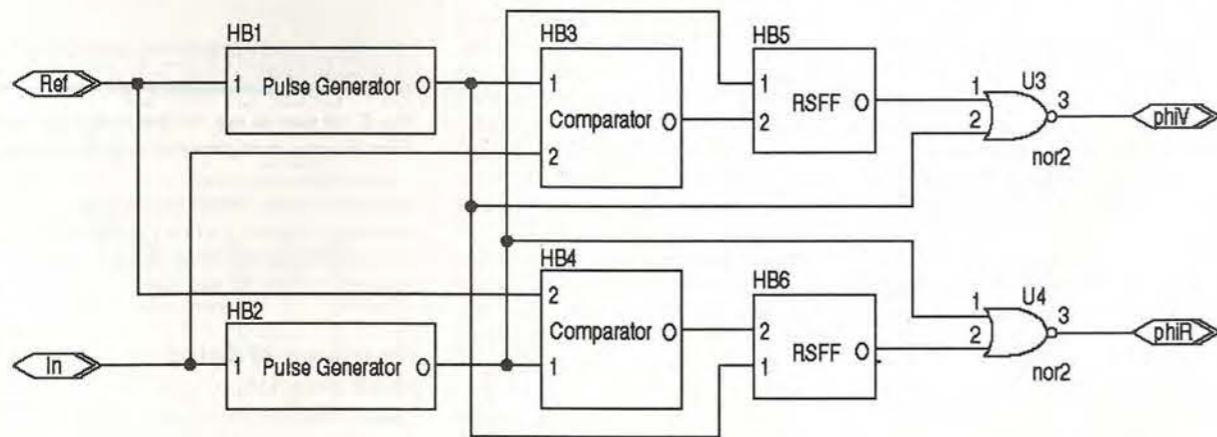



# An RF initiative

Ian Hickman introduces you to an important initiative aimed at encouraging a greater number of promising electronic engineering undergraduates to aim for a career in the fascinating – and burgeoning – field of radio-frequency engineering.

The Institution of Electrical Engineers started life in 1871 as the Institution of Telegraph Engineers. What must they have thought, I wonder, when along came others, pioneering the transmission and reception of messages without wires?

Naturally, this new technique was called Wireless Telegraphy, WT or just wireless; *télégraphie sans fil* in France, or just TSF. Later the term 'wireless' was used also for wireless telephony and later still broadcasting, as also TSF – *téléphonie sans fil*.

But the term wireless, used regularly by my grandparents, fell into

disuse, probably in the 1930s. It was replaced by 'radio' in both English and French, and even sometimes in German, in place of the more common word, 'rundfunk'.

Now, the term 'wireless' has been unearthed, dusted off and pressed back into service, in its most literal sense. Short-range UHF or microwave links are in vogue for the exchange of digital traffic such as data, for example the Bluetooth standard. What term could be more appropriate than 'wireless'?

Applications of wireless communication are booming in a dozen other fields – telemetry, remote meter reading, etc., and of course, most notably, mobile phones.

## Radio engineering

All these current applications, together with others forthcoming, such as UMTS – universal mobile telephone system – are creating an ever increasing demand for engineers skilled in radio frequency engineering. This is a demand that at present cannot be filled. The situation can only get worse, unless suitable steps are taken.

It is with this need in mind that the Department of Trade and Industry has launched the RF Engineering

Education Initiative, or RFEEL.

Under this, the electronic-engineering departments of universities receive a three year award aimed at encouraging interest in a career in RF engineering.

The scheme is being sponsored by a number of companies and Government departments.

## Ride the wave

Organisers of the RFEEL have produced a pack of literature called 'Ride the wave'. It contains a booklet about careers in radio engineering and leaflets describing the activities of the various companies supporting the Initiative are included.

I am privileged to be assisting with the Initiative at one of the participating universities, the University of Portsmouth, just a dozen miles from my home. The university has made a room in one of the Electronic Engineering labs available for use by a 'radio club'. This is an informal arrangement whereby interested students meet one evening a week in their spare time.

My spot is on a Monday evening with second year students, a colleague running a similar arrangement for the first year students on another evening. The club even lays on snacks

for the delectation of the students (and yours truly).

Starting with meetings late last autumn, the usual arrangement has been for me to think up a simple but interesting project for the students each week. Working alone or in small groups, they construct, complete and get the project working in a single session of a couple of hours or so, with a little help and advice if need be.

Initially, the projects were very simple. Few of the students had much experience of constructing circuits from the ground up. They had of course done lab work as part of their courses, but this tends to be very structured. Few opportunities had arisen for them to encounter the problems that arise in development work of any sort. These problems are often trivial, but baffling until you have learned how to sort them out.

Most of the students had no active engagement in electronics prior to embarking upon their degree course. This is in contrast to young electrical engineering students of my generation, who had mostly been exposed to wireless or radar servicing during National Service, or had constructed amateur radio kit from the copious amounts of ex-government electronic gear on the post-war surplus market.

## Expanding the scheme?



To date, five universities are the lucky recipients of funding under the scheme. It is to be hoped that it is successful – and seen to be so – leading to its future extension.

In the mean time, there is nothing to stop other universities starting their own home-grown version of the scheme. In fact, I know that one or two have already done so, but at least one such scheme has fallen by the wayside. This was due to lack of enthusiasm, *not* on the part of the students or of the organisers, but of their superiors.

A university wishing to start such a home-grown scheme need not incur any great expense. While a bespoke club room is a nice luxury, the after-hours activity can always be accommodated in one of the electronic engineering labs. And the projects can use inexpensive commonly available parts, many of which will in any case already be in stock.

As an assistance to any department wanting to run such a scheme, I hope – given the Editor's welcome enthusiasm for the Initiative – to publish simple projects, suitable for such a venture, in these pages in the forthcoming months. ■
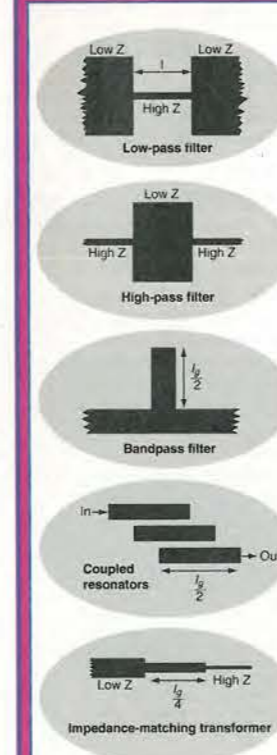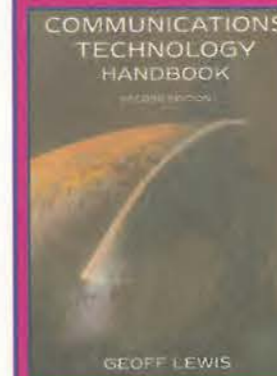
## COMMUNICATIONS TECHNOLOGY HANDBOOK Second Edition



*Microstrip – an example of RF design technique. Using microstrip allows you to make components and even circuits using nothing more than profiles etched on laminated PCB material. These diagrams are extracted from Geoff Lewis's Communications Technology Handbook.*

Geoff Lewis's comprehensive book provides a basic understanding of a wide range of topics. It offers a flexible approach for beginners and specialists alike. In addition, the work addresses an international audience by referring to all systems and standards throughout.

This is the first point of reference for the communications industries. It offers an introduction to a wide range of topics and concepts encountered in the field of communications technology. Whether you are looking for a simple explanation, or need to go into a subject in more depth, the Communications Technology Handbook provides all the information you need in one single volume.

This second edition has been updated to include the latest technology including:

- Video on demand
- Wire-less distribution systems
- High speed data transmission over telephone lines
- Smart cards and batteries
- Global positioning systems

The contents are ordered initially by communications systems. This is followed by an introduction to each topic and goes on to provide more detailed information in alphabetical order. Every section contains an explanation of common terminology, and further references are provided. This approach offers flexible access to information for a variety of readers. Those who know little about communications professionals, the book constitutes a handy reference source and a way of finding out about related technologies. The book addresses an international audience by referring to all systems and standards throughout.

**CONTENTS:** Analog systems and concepts; Antennae or aerials; Audio signal processing; Bar code technology; Codes and coding formats; Computers in communications; Digital communication systems; Digital pulse code modulation; Electromagnetic compatibility/interference; Encryption and decryption; Error control; Facsimile systems; Filters; Frequency bands in use; Image processing; Information theory; Logic; Measurement of systems parameters; Memories; Microwave devices; Mixer signal processing; Modulation and demodulation; Networks; Noise; Optical communications, devices and systems; Photo detector/receivers; Power supplies; Propagation; Quality and reliability; Radar and navigation systems; Radio frequency receivers; Satellite systems; Semiconductor devices and technology; Signals; Spread spectrum techniques; Standards organisations and associated bodies; Telephony and associated systems; Television signal processing and systems; Transmission lines and waveguides; Videotex; CCITT recommendations; Abbreviations and acronyms; Index

This work is written for communications and network managers, engineers, researchers, technicians and students. In hardback form, the book has 488 pp. and 100 line illustrations its price is £47.50 plus £3 carriage.

### Use this coupon to order

Please send me ..... copies of Communications Technology Handbook

Name  
Address

Phone number/fax

Total amount £.....

Make cheques payable to Reed Business Information  
Or, please debit my Master/Visa/other card.

Expiry date

Card No

Please post this coupon to Jackie Lowe, Electronics World, Quadrant House, Sutton, Surrey SM2 5AS or Fax 0208 652 8111

Table 1. Organisations participating in the RFEEL.

Aerial Group	International
Cellnet	Motorola
Defence Evaluation Research Agency	NEC
Department of Trade and Industry	Nokia
Ericsson	Nortel Networks
Hewlett Packard	NTL Telecommunications
IFR	Orange
Lucent Technologies	Plextek
Metaph Software	Racal
	Radio Communications
	Agency
	Simoco
	Sony
	Vodafone



Visit our website  
www.distel.co.uk

# THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always  
wanted for cash!

## THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND &  
VIDEO TUNER  
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers\* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95  
TELEBOX STL as ST but fitted with integral speaker £39.50  
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95  
For overseas PAL versions state 5.5 or 6 mHz sound specification.  
\*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

**NEW** State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**  
See www.distel.co.uk/data\_my00.htm for picture + full details

## FLOPPY DISK DRIVES 2 1/2" - 8"

All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 unlisted drives for spares or repair.

- 3 1/2" Mitsubishi MF355C-L, 1.4 Meg. Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D, 1.4 Meg. Non laptop £18.95(B)
- 5 1/4" Teac FD-55GFR 1.2 Meg (for IBM pc's) RFE £18.95(B)
- 5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE £25.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £25.95(B)
- Table top case with integral PSU for HH 5 1/4" Floppy / HD £210.00(E)
- 8" Shugart 800/801 8" SS refurbished & tested £210.00(E)
- 8" Shugart 810 8" SS HH Brand New £195.00(E)
- 8" Shugart 851 8" double sided refurbished & tested £260.00(E)
- 8" Mitsubishi M2894-63 double sided NEW £295.00(E)
- 8" Mitsubishi M2896-63-02U DS slimline NEW £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

## HARD DISK DRIVES 2 1/2" - 14"

- 2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) New £79.95
- 2 1/2" TOSHIBA MK2101TAN 2.18 Gb laptop (19 mm H) New £89.50
- 2 1/2" TOSHIBA MK4309MAT 4.3Gb laptop (8.2 mm H) New £105.00
- 2 1/2" TOSHIBA MK6409MAV 6.1Gb laptop (12.7 mm H) New £190.00
- 2 1/2" to 3 1/2" conversion kit for Pc's, complete with connectors £14.95
- 3 1/2" FUJI FK-309-26 20mb MFM I/F RFE £59.95
- 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95
- 3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE £69.00
- 3 1/2" QUANTUM 40S Prodriv ve 42mb SCSI I/F, New RFE £49.00
- 5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE £49.95
- 5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb £69.95
- 5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested £69.95
- 5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00
- 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
- 8" NEC D2246 85 Mb SMD interface. New £199.00
- 8" FUJITSU M2322K 160Mb SMD I/F RFE tested £195.00
- 8" FUJITSU M2322K 2 Gb SMD I/F RFE tested £345.00

Many other drives in stock - Shipping on all drives is code (C1)

## TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- MITS. FA3445ETKL 14" Industrial spec SVGA monitors £245
- FARNELL 0-60V DC @ 50 Amps, bench Power Supplies £995
- FARNELL AP3080 0-30V DC @ 80 Amps, bench Suppy £1850
- 1kW to 400 kW - 400 Hz 3 phase power sources - ex stock EPOA
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- IBM 53F5501 Token Ring ICS 20 port lobe modules £750
- IBM MAU Token ring distribution panel 8228-23-5050N £95
- AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE £550
- ALLGON 8360, 11805-1880 MHz hybrid power combiners £250
- Trend DSA 274 Data Analyser with 703(2M) 64 I/O EPOA
- Marconi 6310 Programmable 2 to 22 GHz sweep generator £6500
- Marconi 2022C 10KHz-1GHz RF signal generator £1550
- Marconi 2030 opt 03 10KHz-1.3 GHz signal generator, New £4995
- HP1650B Logic Analyser £3750
- HP3781A Pattern generator & HP3782A Error Detector EPOA
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP6264 Rack mount variable 0-20V @ 20A metered PSU £675
- HP54121A DC to 22 GHz 40 channel test set EPOA
- HP8130A opt 020 300 MHz pulse generator, GPIB etc £7900
- HP A1, A0 8 pen HPGL high speed drum plotters - from £550
- HP DRAFTMASTER 1 8 pen high speed plotter £750
- EG+G Brookdeal 9035C Precision lock in amp £1800
- View Eng. Med 1200 computerised inspection system EPOA
- Sony DXC-3000A High quality CCD colour TV camera £995
- Keithley 590 CV capacitor / voltage analyser EPOA
- Racal IC490 dual 40 channel voice recorder system £2750
- Fiskers 45KVA 3 ph On Line UPS - New batteries £9500
- Emerson A130 2.5KVA industrial spec UPS £2100
- Mann Tally MT645 High speed line printer £2200
- Intel SBC 486/133SE Multibus 486 system, 8Mb Ram £945
- Siemens K4400 64Kb to 140Mb demux analyser £2950

**DISTEL on the web !! - Over 16,000,000 items from stock - www.distel.co.uk**



**ALL MAIL TO**  
Dept ww, 29/35 Osborne Rd  
Thornton Heath  
Surrey CR7 8PD  
Open Mon - Fri 9.00 - 5:30

**LONDON SHOP**  
Open Mon - Sat 9:00 - 5:30  
215 Whitehorse Lane  
South Norwood  
On 68A Bus Route  
N. Thornton Heath &  
Selhurst Park SR Rail Stations

**NEW DISTEL ©**  
Visit our web site  
www.distel.co.uk  
email = admin@distel.co.uk

**ALL ENQUIRIES**  
**0208 653 3333**  
FAX 0208 653 8888


All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (C1)=£12.50, (D)=£15.00, (E)=£18.00, (F)=£20.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 1999. E & O.E. 07/99.

CIRCLE NO. 112 ON REPLY CARD
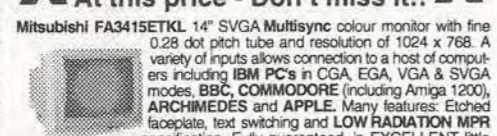
## IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK  
**10,000,000 items EX STOCK**  
For MAJOR SAVINGS  
CALL OR SEE OUR WEB SITE www.distel.co.uk  
**VIDEO MONITOR SPECIALS**

One of the highest specification  
monitors you will ever see -  
At this price - Don't miss it!!



Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT little used condition.

Tilt & Swivel Base £4.75  
VGA cable for IBM PC included.  
**Only £119 (E) MITS-SVGA**

External cables for other types of computers available - CALL  
**Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multisync etc. Full 90 day guarantee. Only £199.00 (E)**

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for Info  
PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed  
Dimensions: W14" x H12 1/2" x 15 1/2" D.  
**Only £99.00 (E)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 1 3/16" D. 240 V AC mains powered.  
**Only £79.00 (D)**  
KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.  
**Only £125 (E)**

## 20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.


20"....£135 22"....£155 26"....£185 (F)  
We probably have the largest range of video monitors in Europe. All sizes and types from 4" to 42" call for info.

## DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock  
Call or see our web site.
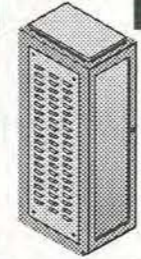
## 19" RACK CABINETS

Superb quality 6 foot 40U  
Virtually New, Ultra Smart  
Less than Half Price!




Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting, plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels. £345.00 (G)  
OPT Rack 2 Rack. Less side panels. £245.00 (G)

Over 1000 racks, shelves, accessories  
19" 22" & 24" wide 3 to 46 U high.  
Available from stock !!
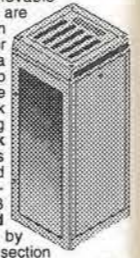
## 32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)



Sold at LESS than a third of makers price !!  
**A superb buy at only £245.00 (G)**  
**42U version of the above only £345 - CALL**

## 12V BATTERY SCOOP - 60% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12V DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SBS15 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each.  
**Our Price £35 each (C) or 4 for £99 (E)**

## RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££'s

## COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available. Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc, etc.  
Web ref = LK33 **ONLY £99.00 or 2 for £180.00 (B)**

## SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. **ONLY £89.00 (B)**  
ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95  
DOS 5.0 on 3 1/2" disks with concise books o/w OBASIC £14.95  
Windows for Workgroups 3.114 Dos 6.22 on 3 1/2" disks £55.00  
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95 shipping charges for software is code B

# NEW PRODUCTS

Please quote *Electronics World* when seeking further information



## 2mm extender

The Robinson Nugent Metpak Two range of 2mm connectors includes an extender board option that allows but mating (edge-to-edge facing) of PCBs. The 2mm interface and footprint comply with IEC1076-4-001, 48B and EIA/SP-3179 specifications. The design enables inverse female modules with integral guide pin to interface with standard male modules. When mated the connector bodies are 23mm long including the shroud and guide pin. PCB tails are available in press fit and solder, and plastic force fit pegs ensure retention of the PCB during soldering. Available pin counts are 30, 150 and 210 but other multiples of 30-position five row mono-blocks are possible.

Robinson Nugent  
Tel: 01227 794495  
Enquiry No 501

## 622MHz VCXO

A voltage-controlled crystal oscillator for time-multiplexing applications in SDH STM-4 and Sonet STS-12 synchronous digital trunk lines has

## Multi-rate Ethernet transceiver

National Semiconductor claims to have the industry's first single-chip 10/100/1000Mbit/s Ethernet transceiver, which is backward compatible to existing Ethernet infrastructures. The DP83891 Gig PHYter is a full-feature physical layer transceiver with integrated PMD sublayers to support 10BASE-TX, 100BASE-TX and 1000BASE-T Ethernet protocols, and is compliant with IEEE 802.3 specifications, including: IEEE 802.3ab, IEEE 802.3u, IEEE 802.3 compliant Auto-Negotiation, IEEE 802.3u MII and IEEE 802.3z GMI. Gig PHYTER is designed for implementation of 10/100/1000Mbit/s Ethernet LANs. It uses standard single Quad TX-Transformer interface and performs error-free operations at over 140m, 40m greater than IEEE specifications. The intention is to support deployment of the Gigabit technology within an existing 10/100Mbit/s environment using Cat. 5 cabling. Other features include fully IEEE 802.3u-compliant Auto-negotiation at all three speeds of 10, 100 and 1000Mbit/s.  
National Semiconductor  
Tel: 00 49 870 24 0 2171  
Enquiry No 502

been launched by C-Mac. The 622.08MHz CFPV-2365 uses bulk-acoustic-wave crystal technology. Frequency stability is ±20ppm from 0 to +70°C or ±30ppm from -25 to +85°C, with frequency pullability between ±80 and ±120ppm. Frequency pulling locks the oscillator onto an incoming signal at variance with the output frequency. The oscillator circuit runs at 155.52MHz, but its fourth harmonic is selected and amplified to provide the 622.08MHz output frequency. It operates from a 3.3V power supply. A sine-wave output is provided.  
C-Mac Frequency Products  
Tel: 01460 74433  
Enquiry No 504

## 1.1W transistors

Zetex's ZXT13 transistors use the firm's Supersot4 technology in a SOT23-6 package. Power dissipation is 1.1W and continuous collector current up to 5A. There are six devices - three n-p-n and three p-n-p - with ratings from 12 to 50V. To allow switching with low base currents, the current gain of each device is from 300 to 900. Typical



## Synchronous rectification IC

International Rectifier has introduced the IR1175 synchronous rectification IC (SRIC) which is designed to provide optimised gate drive for the MOSFETs configured as synchronous rectifiers in the secondary side of an isolated DC-to-DC converter. The IC programs the gate drives to ensure that the losses through the synchronous rectifiers are minimised and the parasitic diodes do not conduct. The IR1175 SRIC boosts converter efficiency to 90% at 3.3V output, claims the supplier.  
International Rectifier  
Tel: 01883 732020  
Enquiry No 506

saturation voltages are down to 45mV at a collector current of 1A, with a base current of 10mA.  
Zetex  
Tel: 0161 622 4422  
Enquiry No 503

## Programmable SLIC

Mitel Semiconductor has launched the MT91600 programmable subscriber-line-interface circuit. It provides the interface between a switching system and a subscriber loop for short-range applications. The device provides the normal interface functions between the codec or switching system and the analogue telephone line, including battery feed, programmable constant pulse detection, user-definable line and network balance impedance, and off-chip audio gain programming. It can accommodate a programmable current range between 18 and 32mA.  
Mitel Semiconductor  
Tel: 01793 518000  
Enquiry No 505

## Audio DSPs

Toshiba Electronics has released digital signal processors supporting audio compression formats in silicon audio players, DVD players and TVs. The TC9446F-004 single-chip DSP supports decoding AAC (two channel) and MP3 compression formats and

## 16-bit d-to-a converter

The LTC1657 from Linear Technology is a parallel 16-bit voltage output d-to-a converter for 5V single supply systems. It includes a rail-to-rail output buffer and an internal 2.048V reference. This device includes a 16-bit or 2-byte double-buffered architecture that allows glueless interface to micros and DSPs. Differential non-linearity is ±1LSB maximum. The device consumes 650µA typical and includes an internal reference and rail-to-rail output buffer that can drive capacitive loads. Power-on reset clears the output to zero. The package is a 28-pin SSSOP or PDIP.  
Linear Technology  
Tel: 01276 677676  
Enquiry No 507



the TC9446F-003 supports decoding for Dolby Digital, Dolby Prologic and other audio-visual systems including DVD. Using a 24-bit by 24-bit processor, which incorporates 12k word data RAM and 12k word program ROM, both have a 128 word program RAM. Up to 1Mbit external SRAM can be used as data RAM. Operating at 3.3V, they come in a 100-pin QFP.  
Toshiba Electronic  
Tel: 00 49 211 52960  
Enquiry No 508

## LCD card for PII/III

An LCD CPU board from Anders comes in a half-size format supporting Pentium II and III processors. Using industrial specification LCDs, these boards have applications in information kiosks, PoS advertising, games machines, medical equipment



Please quote *Electronics World* when seeking further information



and avionics. The HS-6200 supports CPU speeds above 650MHz and data bus speeds of 100MHz. Able to drive TFT, DSTN or EL LCDs up to 800 x 600, with 2Mbyte video memory, the product includes a power connector. The board can be used without a backplane. Although the single board computer is available as a component, the firm can also supply a fully configured product with display, touch screen, bios and cabling. Able to support 100Mbit/s Ethernet, it has USB, IrDA and two serial ports. There are also a bidirectional parallel port, two IDE ports and Dimm support for SDRAM up to 1Gbyte. The device can be configured with two floppy drives. Disc-on-chip to 144Mbyte is possible. The board includes a PISA (PCI+ISA) connector for backplane expansion.  
*Anders Electronics*  
 Tel: 0207 388 7171  
 Enquiry No 509

**RF power transistor**


Ericsson has introduced the PTF10149 RF transistor for the 920 to 960MHz band. It uses Goldmos technology. With an output power of 70W, it is suitable for GSM mobile phone base station transmitters. Gain is 16dB, linearity  $\pm 0.25$ dB and efficiency 50 per cent. It operates from a 28V supply and has a minimum drain-source breakdown voltage of 65V. The n-channel enhancement mode FET has a load mismatch tolerance of 5:1. Class AB two-tone third order intermodular distortion is -37dBc at 20W peak envelope power. It uses gold metallisation, ion implantation and surface passivation.  
*Ericsson*  
 Tel: 00 46 8 757 4700  
 Enquiry No 511

**LCD controller boards**

DM Electronics produces two controller boards for character and graphics LCD modules. The DM4-2120 character controller interfaces with character modules based on Hitachi's HD44780. It can be used with popular display formats up to four lines of 40 characters through an RS232 9600 or 19 200baud input device. Features include input buffer, constant current source for LED backlighting, contrast adjustment potentiometer and patch panel to allow LCD connector

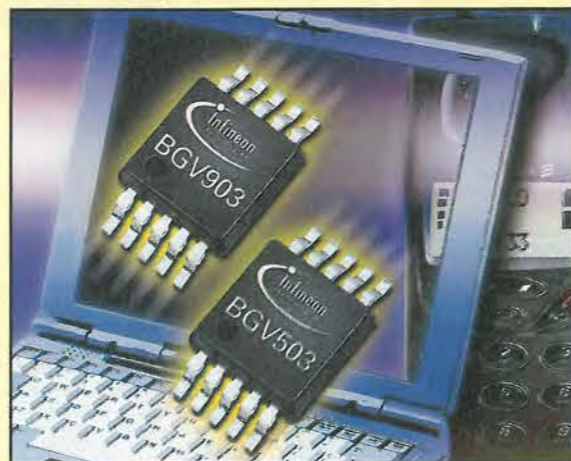**Two-stage voltage inverters**

The BGV503 and BGV903 are one and two-stage voltage inverters from Infineon. They convert a positive supply voltage between +2.7 and +5.0V to a typically corresponding negative output voltage of -2.1 to -4.6V and -4.4 to -9.6V, respectively. The BGV503 has an integrated regulator for biasing GaAs FETs and depletion high electron mobility transistors. An integrated oscillator has a typical frequency of 230kHz. The p-p output voltage ripple is typically 25mV at output currents of 3mA ( $C_{out}=1\mu F$ ). Shutdown input supply current is less than 5 $\mu A$  between -25 and +100°C. Both come in TSSOP-10-1 packages.  
*Infineon Technologies*  
 Tel: 00 49 89 234 22762  
 Enquiry No 110



reconfiguration. The DM4-2140 graphics controller interfaces with graphics modules based on the Toshiba T6963C. It caters for 128 x 64, 128 x 128, 240 x 64 and 240 x 128 display formats through an RS232 9600 or 19,200baud device.  
*DM Electronics*  
 Tel: 01235 811880  
 Enquiry No 512

**Time up to 3 hours**

With a three hour timing range, the S1DX timer from Matsushita has four operating modes - power on-delay, flicker, one-shot and one-cycle. Status is shown by colour LEDs on the front



face. The timer comes in five relay output and solid-state output versions. Relay output versions cover AC and DC operation, and the solid-state alternatives as transistor and triac types. Accessories include mounting frames, leaf holding clips, protective covers, sockets, caps and DIN terminal sockets in various configurations. This UL and CSA approved timer is suitable for timer control panels, production machinery and sequence operations.  
*Matsushita*  
 Tel: 01908 231555  
 Enquiry No 513

**Power supply IGBT**


Intersil has announced a 600V IGBT for switch-mode power applications requiring off-line power conversion at frequencies of 100kHz or more. It delivers currents to 20A and has a current fall time of 70ns typical at

125°C. They are for use in computers and other switch-mode power applications, including AC-to-DC supplies, DC-to-DC conversion and power factor correction in uninterruptible supplies. The

HGTG20N60A4 has a collector-to-emitter saturation voltage of 1.6V typical at 125°C. It is MOS gated.  
*Intersil*  
 Tel: 01344 350250  
 Enquiry No 514

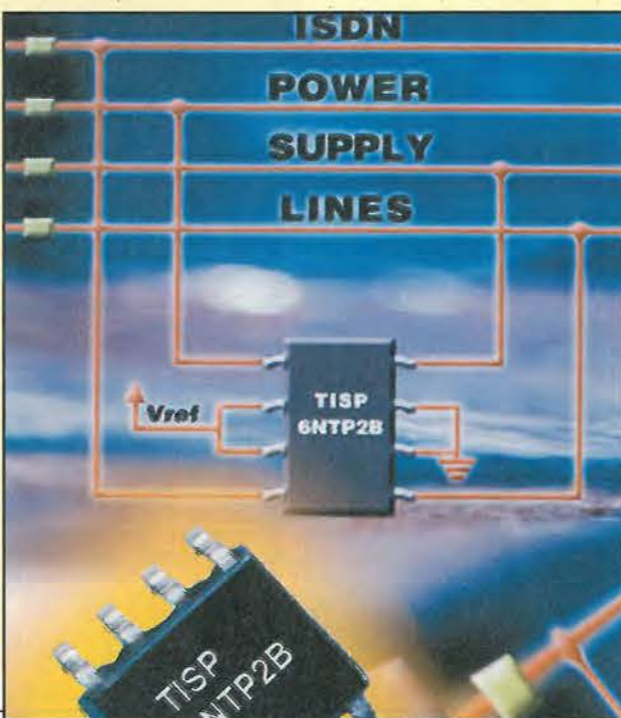**120V ISDN/Slic protector**

Power Innovations has introduced the TISP6NTP2B surface-mount ISDN protector. The 120V maximum rating makes it suitable for providing overvoltage protection on up to four ISDN DC power supply lines or two Slics. It combines four programmable and independently triggered protectors in a SOIC package, with each protector having international protection ratings including 25A ITU-T K20/K21 10/700 and 20A GR-1089-Core 10/1000. The trigger voltage is automatically programmed by reference to the system main supply voltage. In operation, negative surges are initially clamped close to the power supply rail, followed by a fast crowbar action, reducing voltage stress for downstream electronics. Positive surges are clamped to ground by an integrated inverse parallel diode for each line. It comes in tube or tape-and-reel format. Offstate capacitance is 60pF at -50V to ensure transparency in normal use and it has a 150mA holding current. Trigger current is 5mA.  
*Power Innovations*  
 Tel: 01234 223022  
 Enquiry No 515



# Number One Systems

From £97

Professional PCB Layout for Windows at Computer Store Prices!!

## Easy-PC For Windows

Version 3.0 of this outstanding product is the latest evolution of one of the most popular affordable CAD systems available. With powerful new features and a true Windows graphical user interface, it is also one of the easiest to learn and use.

With full manufacturing outputs using Gerber, Windows printers, N.C. Drill and pen plotters it is one of the most complete systems for the casual to the professional user.

Run multisheet Schematics, PCB layouts and library manager all at the same time in the same interface. Switching between each is simply case of selecting the window with the mouse without running a new program.

Now with our new autorouter option.

Runs under Windows 95/98™ and NT™



## Number One Systems

Call 01684 773662 or Fax 01684 773664

Email info@numberone.com

For a free demo disk, visit our web site [www.numberone.com](http://www.numberone.com)

Number One Systems, Oak Lane, Bredon, Tewkesbury, Glos, GL20 7LR, UK

CIRCLE NO.113 ON REPLY CARD


## The science lab in a PC



**Experiments ideas for DrDAQ**

- Flickering Lights. Use a PicoScope for Windows. (Dynamic experiments)
- Dawn Chorus. Use Light
- Sound waveforms. Use a microphone, scaling or sine wave to find the highest level
- Sound Decay. Use a box
- Sound insulation. Use a materials
- Sound waveforms of musical instruments
- Light decay inverse sq
- Light insulation. Sprinkle bits of insulation have been
- Acid Base Titration. Mor
- Acid Rain. Measure the p
- Exothermic Reactions
- Endothermic Reactions
- Day and Night. Plot tem
- Fermentation of Grass
- Fruit Power. Make a tuft
- Capacitor chargedisch
- Infra red remote control
- Output of a solar cell. In
- Heat insulation. Wrap t
- Global Warming. Show t and the other CO2
- Heat Loss Throu

**Only £59!**  
+VAT

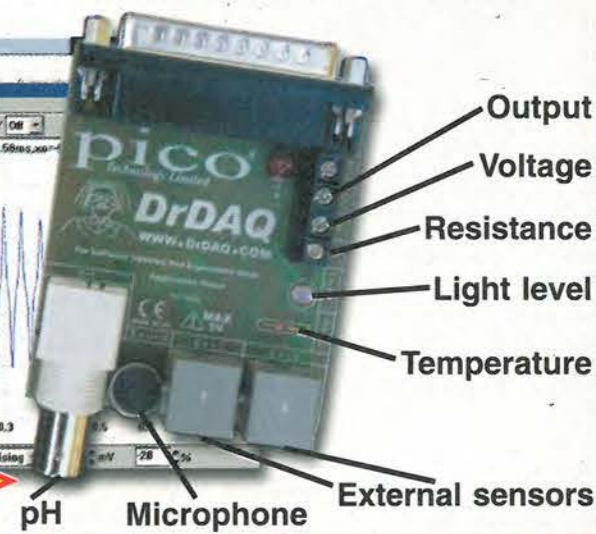

The DrDAQ is a low cost data logger from Pico Technology. It is supplied ready to use with all cables, software and example science experiments.

**DrDAQ represents a breakthrough in data logging.** Simply plug DrDAQ into any Windows PC, run the supplied software and you are ready to collect and display data. DrDAQ draws its power from the parallel port, so no batteries or power supplies are required.

- ✓ Very low cost
- ✓ Built in sensors for light, sound (level and waveforms) and temperature
- ✓ Use DrDAQ to capture fast signals (eg sound waveforms)
- ✓ Outputs for control experiments
- ✓ Supplied with both PicoScope (oscilloscope) and PicoLog (data logging) software

Tel: 01480 396395, Fax: 01480 396296, E:mail: post@picotech.com, Web: www.drdaq.com

CIRCLE NO.114 ON REPLY CARD

**PICO**  
Technology Limited



Please quote **Electronics World** when seeking further information

**Piezoelectric actuators**

Tokin piezoelectric actuators are available from Semicom. Using the piezoelectric longitudinal effect to transform electrical energy into mechanical energy, these devices are suitable for mechatronic systems with movement in increments down to 1µm. The AE resin-coated components deliver a typical clamping stress of 3500N/cm<sup>2</sup>. They can be driven to a third of the self-resonant frequency and have solid-state construction. A metal-sealed variant, the ASB, has also been introduced. Applications include pickup and tracking control of magnetic heads for hard disc drives and positioning of mirrors or prisms in laser systems. Semicom Tel: 01279 422224 Enquiry No 516

**SVGA colour STN display**

Hitachi has announced an SVGA colour STN display for PC and internet browsing. The 25.4cm display has a contrast ratio of 50:1, brightness of 200cd/m<sup>2</sup> and power



consumption of 2W. It is suitable for point-of-sale, point-of-information and internet terminals. The SX25S003 uses multi-line drivers. The transmissive CSTN display has a resolution of 800 by 600 pixels with 265 000 colours and operates from a +3.3V supply. Response time is 270ms. The CFL is enclosed in an evacuated glass flask, which ensures the heat generated is used to raise the temperature of the fluorescent tube. This means less power is needed to operate the display and backlighting. Hitachi Tel: 01628 585163 Enquiry No 517

**Security processor**

Philips has introduced the VMS747 single-chip security processor that can handle higher than 256Mbit/s Ipsec processing (3DES and MD5/SHA-1 hashing). It is based on transportable IP blocks that are part of the company's Velocity RSP7 security tool set. Applications include virtual private networks for OC3 and higher and cryptographic security in financial servers and point-of-sale terminals. It has an integrated Arm7 32-bit Risc microprocessor subsystem. Security features include a dual-state processor architecture,


encrypted program code execution, anti-spoofing technology and an integrated Ipsec accelerator. The processor integrates bulk data encryption, hashing, public key acceleration, random number generation and battery backed memory. A software development kit will be available in the spring. Philips Semiconductor Tel: 00 31 40 272 2091 Enquiry No 518

**Inverse multiplexer**

The Mitel MT90220 is an eight-port ATM physical layer inverse multiplexer providing a multi-vendor PCM interface and is for systems that implement ATM access over existing trunk interfaces, such as central office access concentrators and edge switches. It lets users set up multiple ATM multiplexing groups and can handle eight T1 and E1 interfaces. In mixed mode, T1 and E1 lines can be programmed to operate as inverse multiplexed or Uni lines for ATM over T1 and E1 IMA and Uni services operating simultaneously. It can be used for asymmetrical applications, such as internet access, where more bandwidth is required in one direction. The ability to route clocks from T1 and E1 lines allows the use of various phase lock loops. Supplied in a 208-pin PQFP, it provides a Utopia level two phy interface that lets up to four devices be cascaded, delivering up to 32 T1 and E1 interfaces. Dip International Tel: 01223 462244 Enquiry No 519

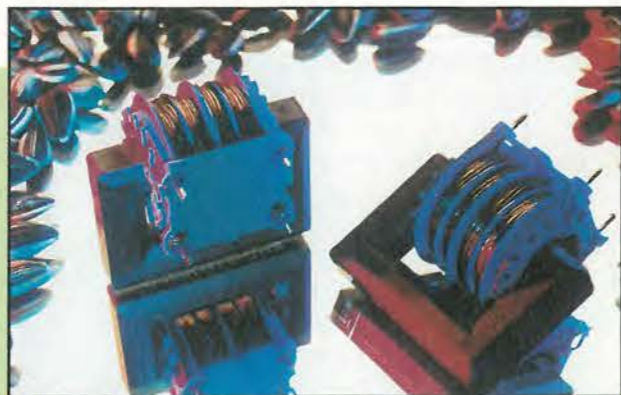**Enclosures**

APW has introduced the VEcase 700 EMC-screened desktop, 19in rack-mount and tower enclosures for CPCI and VMEbus systems, with applications in networking, traffic, transportation and industrial control. There are 18 versions - 3 and 6U heights in 42, 60 and 84HP widths and depths of 240, 280 and 340mm. They have an extrusion-based design. For CPCI systems, the front tiebars are compatible with IEEE1101.10, letting the injector and extractor handles operate correctly. For CPCI computer telephony, versions compatible with the IEEE1101.10 rear-plug module are available. The deepest 340mm standard unit will accept two 160mm deep cards back-to-back in the same slot position. For VME and general-purpose use, IEC297-3 tie bars let cards be mounted vertically or horizontally. RFI attenuation is typically greater than 45dB at 100MHz for the standard version. A further 10dB attenuation can be gained by fitting an optional EMC upgrade kit. Thermal management options include rear panels fitted with extractor fans, ventilated covers and sides and, in the extended height units, slim-line fans in the base below the active card area. The units are stackable. APW Electronics Tel: 01489 780078 Enquiry No 520



**D-core choke**

Epcos has introduced the B82731-M D core choke, a current-compensated double choke for interference suppression in electronic power supplies for lighting ballasts and TV sets. Inductance is between 3.3 and 47mH. Pin grid size is 12.5 by 10.0 ±0.2mm. Pin size is 0.6mm. With rated voltages of 250V AC or DC, the EMC component covers rated currents from 0.5 to 1.8A. Weight is about 8g and the device incorporates a closed rectangular ferrite core and a closed polycarbonate coil former with four sections. The coil former is flame-retardant to UL94V-0. The choke is made without encapsulation or adhesive materials. Epcos Tel: 01344 396689 Enquiry No 521

**The Distributor with 20,000 hard-to-find lines EX STOCK!!!**

**Semiconductors**

We have one of the largest ranges of discrete parts in the UK, both new and obsolete types and, if we do not have it in stock, we can usually source it for you.

Call or fax for our latest Semiconductor stock list

**Computer products**

We carry in stock everything to make a Personal Computer. CPUs - Memory - Motherboards - Cards - Scanners - Modems - Sound Cards - Speakers - All types of Drives - Cases - PSUs - Monitors etc

Call or fax for our latest Semiconductor stock list

**Components & equipment**

Capacitors - Resistors - Connectors - Potentiometers - Cables - Batteries - Speakers - Amplifiers - Lamps - Microphones - Fans - Power supplies - Transformers - Buzzers - Sirens - Fuses and Holders - LEDs - LCDs - Relays - PA Systems - Tools - Test Equipment - etc

Fax or write to us for our latest catalogue

Semiconductor Supplies International Ltd




Semiconductor Supplies International Ltd  
Sutton, Surrey, England, UK. SM1 4TW  
020-8643 1126 (Sales and Technical Queries)  
Daxton House, 128-130 Castleton Road  
Sutton, Surrey, England, UK. Tel: 01883-4420  
020-8643 1126 (Sales and Technical Queries)  
Web: ssi-uk.com  
Fax: 020-8643 3937 (For international use +4420)  
e-mail: sales@ssi-uk.com Web: ssi-uk.com

**Packed with new features:** • Uses the latest xspice engine for guaranteed accurate mixed mode simulation • Parameterised ac sweep • Monte carlo analyses • Parameterised transient sweep • New xspice simulations • New noise and distortion analyses • Improved features for processing plot families as units • New menu items to show local maxima, minima, and zero crossings **and much more!**

**ONLY £199 ex VAT\* - UPGRADES £99\*\***  
No hidden extras. All libraries included.

Not just a pretty interface...

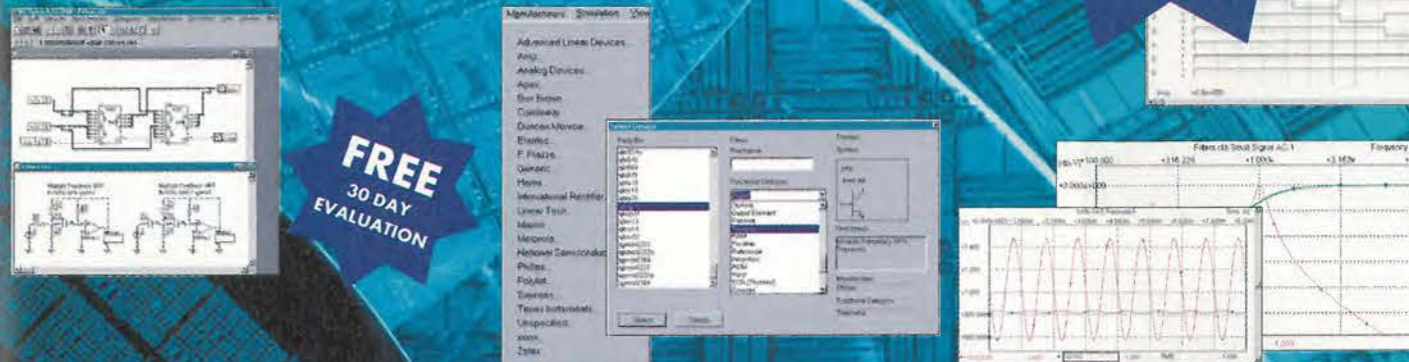


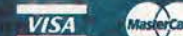**FREE 30 DAY EVALUATION**

... Accurate results that can be relied on



RD Research, Research House, Norwich Road, Eastgate, Norwich NR10 4HA  
Tel: 01603 872331 Email: rd.research@paston.co.uk www.looking.co.uk/spice  
\* Please add £5.00 postage and packing. \*\* applies to users of B<sup>2</sup> Spice & B<sup>2</sup> Logic  
All trademarks acknowledged.



CIRCLE NO.115 ON REPLY CARD

**30% discount for EW readers digital multimeter for just £8**



**Features**

- 3.5 digit 0.5inch Lcd display
- AC & DC voltage
- DC current to 10A
- Resistance
- Diode & transistor hFE test
- Basic accuracy of 0.5%
- Overload protection
- Supplied with battery & probes
- Optional soft carrying case



**Vann Draper Electronics Ltd**  
The test & measurement specialists  
www.vanndraper.co.uk

New & ex-demonstration instruments from Grundig, Kenwood, Hameg, Tektronix, Hitachi, Fluke, Avo, .....

For a limited period Vann Draper is offering the compact DT830B digital multimeter to readers of **Electronics World** at over 30% discount.

The DT830B normally sells at an already low price of £12.56 but is available to readers of **EW** for the amazing price of only **£8** fully inclusive of vat & delivery.

Ideal as a first meter or as a back up meter, the DT830B is supplied ready to use complete with test probes, battery, operating instructions and a 1 year guarantee. An optional soft vinyl carrying case is available at £3.50 including vat and delivery.

To order simply post the coupon to **Vann Draper Electronics Ltd at Stenson House, Stenson, Derby DE73 1HL.** Alternatively tel 01283 704706, fax 01283 704707, email sales@vanndraper.co.uk

**Key Specifications**

DC volts	:	200m, 2V, 20V, 200V, 1000V basic accuracy 0.5%
AC volts	:	200V, 750V basic accuracy 1.2%
DC current	:	200uA, 2mA, 20mA, 200mA, 10A
Resistance	:	200, 2k, 20k, 200k, 2Mohm basic accuracy 0.8%
Transistor hFE	:	0 to 1000
Size	:	70 x 126 x 24mm,
Weight	:	170g

CIRCLE NO.116 ON REPLY CARD

Use this coupon for your order

Please supply me .....

.....DT830B multimeter(s) at £8.00 inc vat and del

.....Soft carrying case(s) at £3.50 inc vat and del

Name .....

Address .....

.....

.....

Tel No .....

Total £ .....

Cheques payable to Vann Draper Electronics Ltd or debit my Visa, Mastercard or Switch card.

Card type .....

Card No .....


Expiry date ..... Switch iss No .....

Signature .....

Overseas readers can still obtain this discount but carriage charges vary according to country. Please telephone, fax, email or write to Vann Draper.



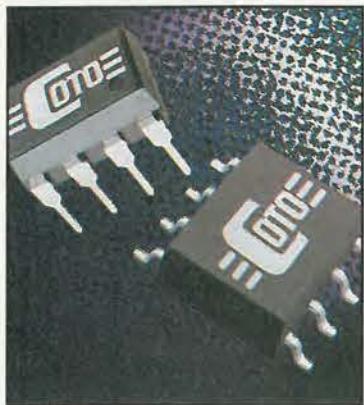Please quote *Electronics World* when seeking further information



#### SM relay

Rhopoint Components has introduced a solid-state relay in a surface mount package for modems and data communications applications. The G2-DA06 is a dual-form A device with 18Ω maximum on resistance – 10Ω typically – that can handle continuous load current of 180mA and peak load voltages of 250V. Input to output isolation is 3750V RMS. Maximum height is 0.22cm. No EMI or RFI is generated by the relay and its solid state construction eliminates arcing and contact bounce. No snubbing

circuits are needed. UL and CSA recognised, the relay is certified to BABT and VDE.  
Rhopoint Components  
Tel: 01883 717988  
Enquiry No 526

#### PCB applicator

Donprint has developed a device for printing and applying PCB labels. The Apply-Mark 610 uses the Zebra 90x11 printer with 600dot/in resolution. It can be linked or retrofitted to most production line equipment such as conveyors. It can also be combined with the firm's barcode software, data capture products and customised programming services for work in progress tracking. Cycle times are less than 3s and accuracy repeatability 0.5mm. The firm is developing three and four-axis applicators for multiple label pick-and-place application in one pass.  
Donprint  
Tel: 01355 249191  
Enquiry No 524

#### Flash for GPS

Unique Memec is sampling three silicon storage x16 flash products. The 8Mbit 39VF800A, 4Mbit 39VF400A and 2Mbit 39VF200A have

read access times of 45ns and use a 2.7 to 3.6V voltage supply for read, program and erase. They are suitable for program code storage in GPS navigation systems, MP3 players, PDAs, DSL, DVD, CD-RW, modems and disk drives. They use a uniform sector architecture of 4kbyte or 2kword and have a uniform block erase capability of 32kword or 64kbyte. Erase speed is 20μs per word for programming, 25ms for sector and block erase and 100ms for chip erase. They come in 48-pin TSOP and 48-ball TFBGA packages.  
Unique Memec  
Tel: 01296 397396  
Enquiry No 522

#### Application specific tools

Engineers and scientists can create measurement applications in Microsoft Visual C++, Visual Basic, and Labwindows/CVI using Measurement Studio from National Instruments. The set of integrated measurement tools includes acquisition, analysis and visualisation for text-based programming languages. The package includes user interface controls, mathematical analysis, signal processing routines and high-level data acquisition and instrument control I/O libraries for Visual C++ and Visual Basic. It integrates tools for data acquisition, data analysis and data visualisation directly into Visual C++.  
National Instruments  
Tel: 01635 523545  
Enquiry No 523

#### Instrument catalogue

A new test and measurement catalogue is available from Professional Instrument Distributors. 100 pages describe equipment for electrical, electronic, safety and environmental testing. Recorders, data loggers and analysers are among the 1000 items in the catalogue. There are five regional sources of the catalogue covering the whole of the UK. Ask for your regional outlet via the number below.  
Professional Instrument Distributors  
Tel: 01756 799737  
Enquiry No 527

#### USB protector

A dual-channel, high-side switched LSI IC measuring 5.0 by 6.2 by 1.5mm provides power system protection for equipment with a built-in USB hub. Rohm's BD6510F is for PCs, scanners, monitors, printers, disc drives and cameras. Features include under-voltage lockout, overcurrent protection and thermal shutdown circuitry that incorporates an output latch to ensure complete power shutdown. Typical on resistance is 100mΩ and it can operate with voltages from 3.0 to 5.5V making it suitable for notebook computers and other applications with mixed 3.3 and 5V power circuits.  
Rohm Electronics  
Tel: 01908 282666  
Enquiry No 528

#### 24-port 1U patch panels

Series 500 ITT Networks 24-port 1U patch panels from AX Distribution provide 96 outlets in 4U cabinet space. They use Link 5E (cat 5E) RJ45 data jacks and come with shielded or unshielded 808 connectors, cable ties and fixing kits. The panels can be mounted into the rack or cabinet first, letting the terminated 808 mark-two connectors be individually located and secured. Also available are cord management




panels and clips for routing patch cords within cabinets  
AX Distribution  
Enquiry No 529

#### Electrolytic capacitors

The GY electrolytic capacitors from Nichicon are for industrial power supplies in ballast applications. Working voltage is 160 to 250V (-40 to +105°C) and 315 to 450V (-25 to +105°C) and capacitance 39 to 2200μF. Tolerance is ±20 per cent. Ripple current covers 0.65 to 2.9A RMS. They have snap-in terminals, diameters of 22, 25, 30 and 35mm and lengths from 25 to 50mm.  
Nichicon  
Tel: 01276 685393  
Enquiry No 530
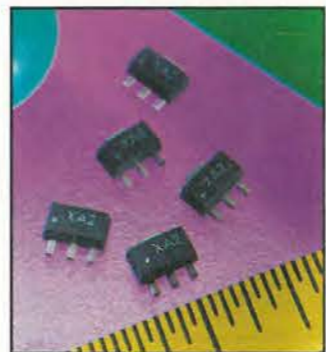
#### GaAs amplifier

The SXA-289 monolithic GaAs power amplifier from Link Microtek is for use as a driver stage in base station equipment for cellular, ISM and narrowband PCS applications. Made by Stanford Microdevices, it uses Darlington pair topology to provide broadband performance from 50MHz to 2GHz, while drawing 110mA from a +5V DC supply. Typical third-order intercept point is 42dBm across the full frequency



# KELLY'S

For 200 years the definitive source of UK products & services



www.kellys.co.uk

CALL NOW FOR FURTHER INFORMATION

FREE PHONE 0800 521393

## Test & Measurement Instruments

The NEW HF-08 Analog to Serial Converter



- ✓ 8 bit resolution
- ✓ Windows and DOS software available: DVM, Scope, Spectrum, Logging
- ✓ 7 ranges: +1.25V to +5.0V, -2.5V and ±2.5V
- ✓ Crystal controlled timing for accurate DSP
- ✓ Simple to interface to your own software
- ✓ Low Cost - just £69.33 incl vat.

12 bit module coming soon ...

RF Instruments  
EMC Equipment

**HF**  
Instruments

Data Logging & Acquisition

Phone: 01420 590000  
e-mail: sales@hf-inst.co.uk

Metered bench power supplies  
Up to 60V and 6A  
Prices from £127 inc. VAT



Handy DMM / Scope Counter/Timer  
TTL Sig. Gen.  
£199 inc. VAT



Visit our Web Site for full details:

www.hf-inst.co.uk

CIRCLE NO.117 ON REPLY CARD

## FM Embedded Controllers at a ground breaking price!

WEB SITE  
http://www.cms.uk.com

£95 each  
PER 100 UNITS



The range of 'FM-Controllers' provide most of the features required for embedded control at a very low cost

#### FEATURES FM-200 Controller

- ◆ 68K Micro-Controller 14 MHz clock
- ◆ 512 Kbytes Flash EEPROM
- ◆ 512 Kbytes SRAM Battery Backed
- ◆ 2 RS232 Serial Ports
- ◆ 1 RS232/RS485 Serial Port
- ◆ Real Time Calendar Clock (Y2K Compliant)
- ◆ Watchdog & Power fail detect
- ◆ 10 Digital I/O Lines
- ◆ 2-16 bit Counter/Timers
- ◆ I<sup>2</sup>C Bus or M-Bus
- ◆ Expansion Bus
- ◆ Size 100 x 80 mm

#### OTHER FEATURES

- ◆ Up/Download removable card for data logging and/or re-programming
- ◆ STE I/O Bus, 68000 and PC Interface
- ◆ Designed, Manufactured and supported in the UK

#### OPTIONAL EXTRAS

- Additional extra features to the FM 200
- ◆ LCD Port Graphics or Alphanumeric
  - ◆ Key Pad Port 64 Keys 8 x 8
  - ◆ 8 Channels 8 bit analogue in
  - ◆ 2 Channels 8 bit analogue out
  - ◆ 8 Channels 13 bit analogue in
  - ◆ Up to 32 Digital I/O Channels
  - ◆ Up to 8 Mbytes of SRAM Battery Backed
  - ◆ Up to 512 Kbytes of Flash EEPROM
  - ◆ 1 Mbyte EPROM Space



CAMBRIDGE  
MICROPROCESSOR  
SYSTEMS LIMITED

Units 17-18, Zone D Chelmsford Road Industrial Estate, Great Dunmow, Essex UK CM6 1XG Tel: +44 (0) 1371 875644 Fax: +44 (0) 1371 876077

#### DEVELOPMENT

The PC Starter Pack provides the quickest method to get your application up and running

#### Operating System

- ◆ Real Time Multi Tasking
- ◆ Unlimited copy licence

#### Languages

- ◆ 'C', Modula-2 and Assembler
- ◆ Full libraries & device drivers provided

#### Expansion

- ◆ Easy to expand to a wide range of peripheral and I/O cards

#### Support

- ◆ Free unlimited telephone, FAX, email and Internet support

#### Custom Design

- ◆ CMS will design and manufacture to customers requirements

CIRCLE NO.118 ON REPLY CARD




# BOOK TO BUY
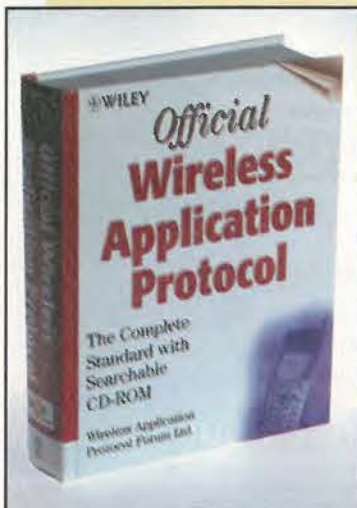
## Official Wireless Application Protocol: The Complete Standard with Searchable CD-ROM

Available for the first time in book and CD form, the complete, unabridged standard of the breakthrough wireless technology standard. The Wireless Application Protocol (WAP) is the first open, licence-free standard which allows for the first time any brand of wireless device to talk to another

across all networks worldwide. The potential for new applications using this protocol is enormous. Unwired Planet is the firm that developed WAP with AT&T Wireless, Motorola, Nokia, and Ericsson. In this, the first of a three-book series on WAP, they provide the definitive reference of the standard. CD-ROM provides the unabridged specification for quick reference



UK Price: £45.50 Europe £47.00 ROW £49.50

\*\* Price includes delivery and package \*\*

Return to Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following title:

Official Wireless Application Protocol

Total \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Telephone \_\_\_\_\_

Method of payment (please circle)

Access/Mastercard/Visa/Cheque/PO  
**Cheques should be made payable to Reed Business Information**

Credit card no \_\_\_\_\_

Card expiry date \_\_\_\_\_

Signed \_\_\_\_\_

## NEW PRODUCTS

range. Noise is 5dB in the 800 to 900MHz and 1800 to 2000MHz bands. Power gain is typically 20dB in the cellular band and more than 14dB in the PCS band. Fabricated using GaAs heterojunction bipolar transistor technology, it is housed in a SOT-89 surface-mount plastic package. Evaluation boards, development kits and application circuits are available.

Link Microtek  
 Tel: 01256 356771  
 Enquiry No 531

### 66W switching regulator

UR has available the STR-G6651 offline quasi-resonant flyback switching regulator from Allegro Sanken. The switch-mode power-supply regulator is for industrial, telecoms, datacomms, white goods, lighting, metering, charger and security applications. Capable of handling up to 66W, the device comes in a five-pin over-moulded isolated TO-220 package and incorporates the primary control and drive circuit with a discrete avalanche rated power MOSFET. The MOSFET has a Vds of 650V and is constant voltage soft gate driven. It can be used at switching frequencies of 20 to 300kHz and has built in cycle by cycle programmable current protection, latched overvoltage protection, latched thermal shutdown, internally programmed soft start and under voltage lock out.

Ultimate Renaissance  
 Tel: 01793 439310  
 Enquiry No 532

### 3U Eurocard controller

HM Computing has launched a 3U Eurocard combining a Pentium processor with functions and interfaces for real-time embedded systems. The card may be expanded using CompactPCI or PC/104 implemented as a mezzanine bus. It provides a foundation for controlling machinery and instrumentation and will run any PC operating system, as well as real-time operating systems including QNX, PSOS, VxWorks, Linux and Pharlap. The CPU-7310 card uses a Pentium or K6 processor operating at up to 400MHz. Also onboard is 64Mbit DRAM, 0.5Mbit synchronous L2



cache, 1Mbyte solid-state disk, watchdog and real-time clock and floppy disk and keyboard controllers.  
 HM Computing  
 Tel: 01299 250997  
 Enquiry No 533

### 60mm square fan

The San Ace 60L fan is available from EAO. The fan measures 60mm diameter by 25mm thick, and has a claimed operating life of 100,000 hours at 60°C ambient temperature. The unit is available in 5, 12 and 24V versions. Nominal acoustic noise level is 28dB(A). Alarm functions are available for remote



monitoring, and locked-rotor protection is provided by an overcurrent limiting circuit.  
 EAO  
 Tel: 01444 236000  
 Enquiry No 534

### Configurable memory device

A wafer-scale integration Easyflash programmable system device from Insight Memec provides in-system programmability of blank devices via a four-pin ISP port, based on the JTag standard, which lets code bypass the MCU blank and flow directly into the device's memory banks. The WSI PSD9xx can be soldered onto the circuit board and programmed at the end of the assembly line. The device provides concurrent memory arrays to support in-application

# Too good for words

# RANGER XL

The Complete Integrated Schematic PCB Layout Package



## The New Ranger XL Series

Ranger 2 for Windows £170  
**NEW** Ranger 2XL £500  
**NEW** Ranger XL from £950  
**FREE** Website Download Demo



Old Buriton Lime Works, Buriton, Petersfield, Hants. UK GU31 5SJ  
 Tel: (44) 01730 260062 Fax: (44) 01730 267273

Email: sales@seetrax.com Website: www.seetrax.com

CIRCLE NO.119 ON REPLY CARD

## LOW COST Embedded Control

...with extra BYTE!



Low cost Embedded Control Control Systems Custom Design Micro-Controllers Logic Controllers Data Loggers Analogue & Digital I/O

CAMBRIDGE MICRO PROCESSOR SYSTEMS LIMITED

Units 17-18, Zone 'D', Chelmsford Road Industrial Estate, Great Dunmow, Essex UK CM6 1XG  
 Tel: +44 (0) 1371 875644  
 Fax: +44 (0) 1371 876077

http://www.cms.uk.com

CIRCLE NO.120 ON REPLY CARD

## WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES (using a video capture card)



"Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use.....£91.91+ vat = £108.00  
 Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12V DC 150mA.  
 47MIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye).....£37.00 + vat = £43.48  
 30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole.....£35.00 + vat = £41.13  
 40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses.....£32.00 + vat = £37.60  
 Economy C mount lenses all fixed focus & fixed iris  
 VSL1220F 12mm F1.6 12x15 degrees viewing angle.....£15.97 + vat = £18.76  
 VSL4022F 4mm F1.22 63x47 degrees viewing angle.....£17.65 + vat = £20.74  
 VSL6022F 6mm F1.22 42x32 degrees viewing angle.....£19.05 + vat = £22.38  
 VSL8020F 8mm F1.22 32x24 degrees viewing angle.....£19.90 + vat = £23.38  
 Better quality C Mount lenses  
 VSL1614F 16mm F1.6 30x24 degrees viewing angle.....£26.43 + vat = £31.06  
 VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle.....£77.45 + vat = £91.00  
 1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat 1000 of 1 value £5.00 + vat  
 866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily.....£7.46+vat = £8.77

Please add 1.66 + vat = £1.95 postage & packing per order

**JPG ELECTRONICS**  
 276-278 Chatsworth Road, Chesterfield, S40 2BH.  
 Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch  
 Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

CIRCLE NO.121 ON REPLY CARD




# BOOK TO BUY
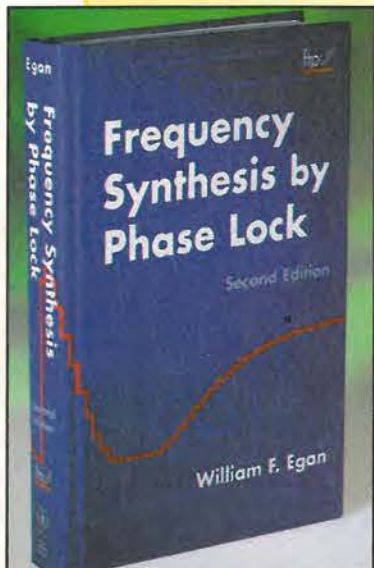
## Frequency Synthesis by Phase Lock

Frequency synthesis is an important element in the design of all communications equipment, but has taken on new life recently with the advent of new hand-held wireless devices. This technology not only allows wireless transmitters to change frequencies quickly, but also gives high reliability and security in transmissions. Thus, mobile devices such as cell phones can utilise this technology to change frequencies until a suitable one is found for the location in which it is being used.

- Emphasises the fundamentals of frequency synthesis
  - Based on a course that Dr. Egan has been teaching for over 20 years at Santa Clara University
  - Provides a link to the Wiley ftp site for the use of associated MATLAB exercises
  - Taken together with Phase Lock Basics by the same author, the two books provide readers with complete coverage of the field.
- CONTENTS** Introduction; The Elementary Phase-Locked Synthesiser; Modulation, Sidebands and Noise Spectrums; Frequency Dividers; Phase Detectors; Higher Order Loops; Sampling Effects; Architectures; Large-Signal Performance, Natural Acquisition; Acquisition Aids; Spectral Purity; Computer Aided Engineering.



UK Price: £64.00 Europe £66.50 ROW £69.00

\*\* Price includes delivery and package \*\*

# NEW PRODUCTS

re-programmability, which allows execution out of one memory array while the other is being updated. It integrates up to 2Mbit of flash, 256kbit of concurrent flash or EEPROM, up to 64kbit of SRAM, additional i/o, power management and security. PSDsoft Express software lets external memory and accompanying logic be added to the designs without logic design effort or expertise. It is programmable via the ISP port, the MCU's serial port or a third party device programmer.  
*Insight Memec*  
Tel: 01296 330061  
Enquiry No 535

### Piezo speakers

Megacera's piezo speakers are available from Deltron Roxburgh. The speakers house a 50µm thick ceramic resonator in a stainless package. The driving voltage is less than 6V. They have an operating frequency band up to 20kHz. The largest model, the MS-4048U, measures 40 by 48 by 2.5mm and develops 85dB (1m) sound pressure. The smallest measures 19 by 23 by 2.5mm, weighs 2.3g and achieves a sound pressure of 76dB (1m).  
*Deltron Roxburgh Electronics*  
Tel: 01724 281770  
Enquiry No 538

### Rad-hardened MOSFET

Intersil has introduced a radiation hardened MOSFET for protecting against single-effect effects in satellite and aerospace applications. The 60V p-channel MOSFET

delivers power conditioning and control in satellite applications, and has a typical on resistance of 16mΩ. The device is suitable for applications exposed to radiation environments, such as switching regulation, switching converters, motor drives, relay drivers and drivers for high-power bipolar switching transistors. The FST9055 acts as a switch to control or supply power to an entire system or to a single object such as a solenoid or motor. The device is an enhancement-mode silicon-gate power field effect transistor with a vertical double-diffused metal-oxide semiconductor structure.  
*Insight Intersil*  
Tel: 01344 350250  
Enquiry No 537

### LCD controller with SRAM

The SED1375 from Epson is a colour or monochrome LCD graphics controller with an embedded 80kbyte SRAM display buffer. Applications include office automation equipment, mobile communications devices and palm-sized PCs. Features include hardware portrait mode and virtual and split screen. It is aimed at Windows CE applications but works with other CPUs and operating systems. Resolution is 640 by 480 at a colour depth of 2bits/pixel, 640 by 240 at 4bits/pixel or 320 by 240 at 8bits/pixel.  
*Epson Electronics*  
Tel: 00 49 89 14005 363  
Enquiry No 539



### DC-to-DC converter with 12V inputs


Ginsbury has launched a dc-to-dc converter with 12V inputs for battery power architectures in portable equipment. The Powercube TD is available in half-brick 30, 50, 75, 100 and 150W units and full-brick 250 and 300W devices. It meets standards for distributed and board mounting power systems in telecoms and server applications. Features include over-temperature shutdown, overvoltage protection, power-good signal output, built-in current monitor, case ground pin and positive or negative logic shutdown (remote on-off). Other inputs are 300, 150, 48 and 24V.  
*Ginsbury Electronics*  
Tel: 01634 298900  
Enquiry No 536

# BOOK TO BUY

Without an engineering degree, a pile of money, or an infinite amount of time, the revised 289-page *Interfacing with C* is worth serious consideration by anyone interested in controlling equipment via the PC. Featuring extra chapters on Z transforms, audio processing and standard programming structures, the new *Interfacing with C* will be especially useful to students and engineers interested in ports, transducer interfacing, analogue-to-digital conversion, convolution, digital filters, Fourier transforms and Kalman filtering. Full of tried and tested interfacing routines.  
Price £14.99.

Listings on disk – over 50k of C source code dedicated to interfacing. This 3.5in PC format disk includes all the listings mentioned in the book *Interfacing with C*. Note that this is an upgraded disk containing the original *Interfacing with C* routines rewritten for Turbo C++ Ver.3  
Price £15, or £7.50 when purchased with the above book.

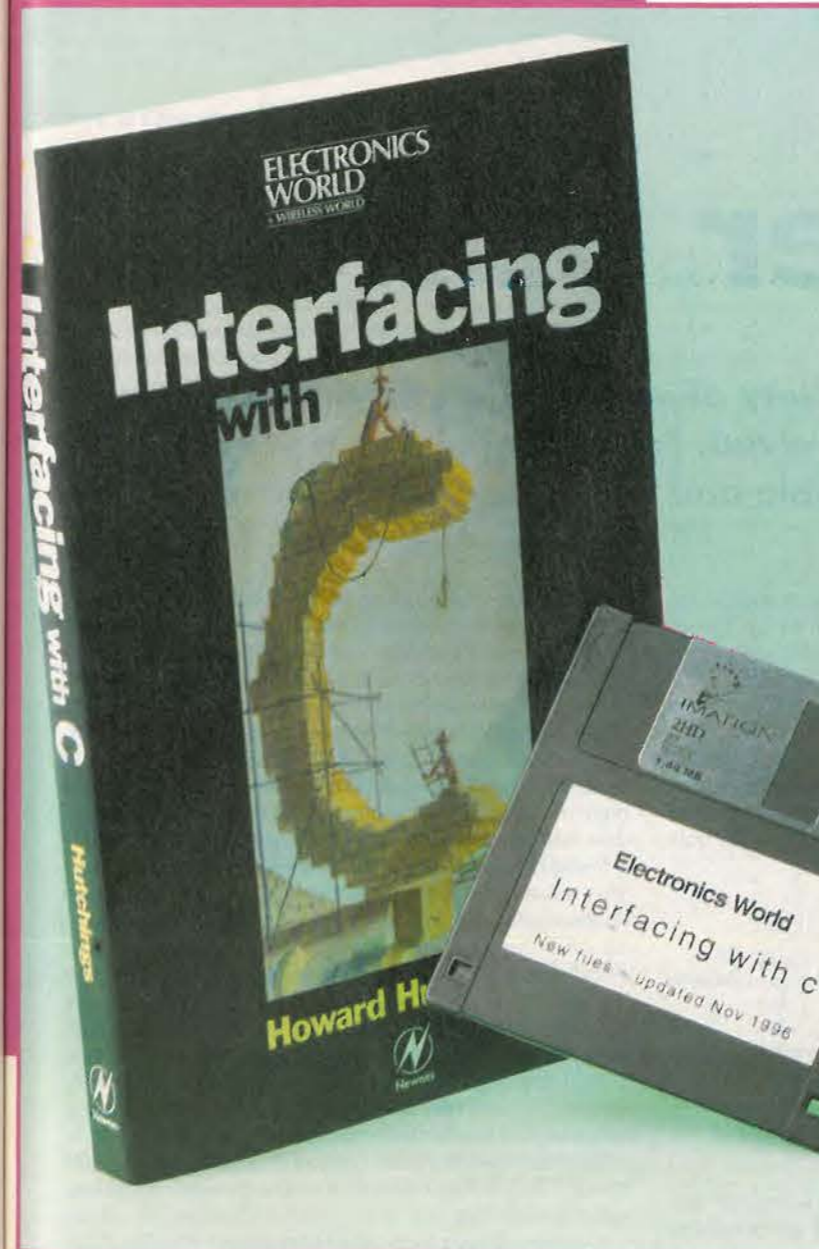Especially useful for students, the original *Interfacing with C*, written for Microsoft C Version 5.1, is still available at the price of £7.50. Phone 0181 652 3614 for bulk purchase price.



Post your completed order form to:-  
Jackie Lowe, Electronics World, Room L333,  
Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please send me	Price	Qty	Total
Enhanced Interfacing with C book @	£14.99	.....	£.....
Enh. Interfacing with C book @ + disk	£22.49	.....	£.....
Interfacing with C disk @	£15.00	.....	£.....
Original Interfacing with C book @	£7.50	.....	£.....
Postage + Packing per order UK	£3.50	.....	£.....
Postage + Packing per order Eur	£7.00	.....	£.....
Postage + Packing per order UK	£12.00	.....	£.....
		<b>Total</b>	<b>£.....</b>

### How to pay

I enclose a cheque/bank draft for £.....  
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard  American Express  Visa  Diners Club

Credit Card No: \_\_\_\_\_ Expiry Date: \_\_\_\_\_

Signature of Cardholder \_\_\_\_\_

**Send my order to:** (please use capitals)

Name \_\_\_\_\_

Address \_\_\_\_\_

Post Code \_\_\_\_\_ Tel: \_\_\_\_\_

Fax: \_\_\_\_\_ Date \_\_\_\_\_

Please allow up to 28 days for delivery



# IF filter options

Over the years, a variety of intermediate-frequency filter arrangements has evolved. Joe Carr looks at a variety of the techniques available and discusses their merits.

A number of different types of IF filters are used in radio receivers today. In addition to LC filters, there are various types of crystal filter, monolithic ceramic filters, and mechanical filters to consider. In this article, I take a look at the various types of IF filter, their characteristics and their applications.

Before delving into the topic, it is helpful to consider how these filters are used. Figure 1 shows a generic IF amplifier with the filters in place. The IF amplifier provides most of the gain in a superheterodyne receiver, as well as the bulk of the selectivity of the receiver.



Fig. 1. Intermediate-frequency filtering arrangement, as used in a typical superheterodyne receiver.

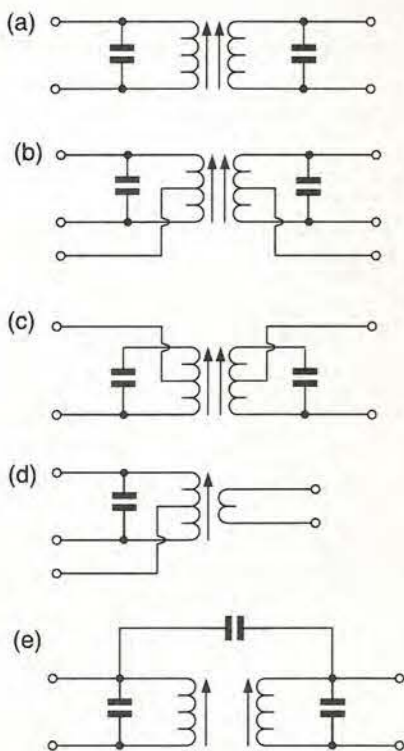


Fig. 2. Various LC IF filter circuits. Filters a) to c) are all tuned on either side of the transformer and vary primarily in drive impedance. Filter a) used to be the conventional IF filter, but it is no longer widely used. Filter b) has low-impedance taps on both sides to increase its usefulness in solid-state circuits; filter c) is identical, except that the high-impedance taps are no longer available to the outside world. Filter d) is single-tuned and its low-impedance output is used for impedance matching. In filter e), the filter coils are not magnetically coupled. Instead, the signal is transferred by common reactance. Here, the reactance is a capacitor, but it could equally well be an inductor.

Selectivity is the function of the IF filter. It has the narrowest bandpass of all the filters in the receiver. Its main function is to supply the selectivity of the receiver by narrowing the bandpass down to accommodate the type of modulation being used.

The IF amplifier may or may not use two – or more – filters, depending on the type of design. In cases where only one filter is used, then the filter will usually be placed at the input of the amplifier in order to eliminate the mixer products that can affect the IF amplifier performance.

Noise produced by the IF amplifier can be significant. This means that an output IF filter is indicated in order to eliminate that noise.

### LC IF filters

The basic type of filter, and once the most common, is the LC filter, which comes in various types Fig. 2. The type shown in Fig. 2a) contains two parallel tuned LC sections. Although it is not apparent here, the input and output sides of the LC network need not be the same impedance, although that is usually the case.

Once the most common form of IF amplifier filter, this type has largely been eclipsed by other types, except in certain IC amplifiers.

A more common form today is shown in Fig. 2b). This form has a low impedance tap for transistor or IC applications, with the high impedance portions still available. In Fig. 2c) is a common form of IF filter in which the low impedance tap is available to both input and output sides, but one side of the high impedance portions of the transformer is not.

In Fig. 2d) you can see a single-tuned IF filter. It has a standard IF filter input side, but it has only a low impedance link on the output side. The IF filtering is performed by the tuned LC circuit, whereas the low impedance link is for impedance matching.

In Fig. 2e) you can see a double-tuned IF filter that is not magnetically coupled (so it is not a transformer), but rather is coupled through a common impedance. In this case a small value capacitor is used as the common impedance, but inductors can also be used as well.

### Crystal filters

The quartz piezoelectric crystal resonator is ideal for IF filtering because it offers high Q – resulting in narrow bandwidth – and it behaves as an LC circuit. Because of this feature, it can be used for high quality receiver design as

well as filter type single-sideband transmitters.

Quartz has a dielectric constant of about 3.8. A schematic symbol for a crystal is shown in Fig. 3a), while the equivalent LCR circuit and the device's impedance curve are shown in Figs 3b,c). The equivalent circuit shows that there is a series inductance,  $L_s$ , and capacitance,  $C_s$ , as well as a series resistance  $R_s$ .

Series inductance and capacitance of a crystal are sometimes called the motional reactance values. There is also a parallel capacitance,  $C_p$ . The parallel capacitance resonates with the inductor to form a parallel resonance, while the series capacitance resonates with the inductor to form a series resonance.

Figure 3c) shows capacitive and inductive reactance against frequency. The frequency marked  $F_s$  is the series resonance point. The anti-resonance is 'officially' the parallel resonance, but in practical terms there is a range of parallel resonance.

Figure 4 shows a typical crystal package and its mounting on a printed circuit board. The basic package is shown in Fig. 4a). Note that the pins might be actual pins, or they may be wires. A cut-away view is shown in Fig. 4b). This gives you a better idea of how the crystal works.

Figure 4c) shows how the crystal is usually mounted on a double-sided printed circuit board. An insulator is placed on the board to prevent short circuiting the board tracks with the crystal package.

Figure 5a) shows a simple crystal filter that has been around since the 1930s in one form or another. Figure 5b) shows the attenuation graph for this filter.

There is a 'crystal phasing' capacitor, adjustable from the front panel, that cancels the parallel capacitance. This cancels the parallel resonance, leaving the series resonance of the crystal.

Although the 1930s vintage filters did not use it, this filter is built in trifilar form. This means that the windings of  $T_1$  are wound together, interlaced with each other.

Figure 6a) shows the circuit for a half-lattice crystal filter, while Fig. 6b) shows its attenuation curve. This type of crystal filter is used in lower cost radios. Like the simple crystal filter described above, this version uses a trifilar coil for  $T_1$ . But instead of the phasing capacitor there is a second crystal in the circuit.

The frequency relationship between the two crystals, Fig. 6b) shows that they have overlapping parallel and series resonance points. This makes the parallel resonance of crystal No 1 is the same as the series resonance of crystal No 2.

You can use the half-lattice filter to build a cascade half-lattice filter, Fig. 7, and a full-lattice crystal filter, Fig. 8. The cascade half-lattice filter has increased skirt selectivity. It also gives fewer spurious responses compared with the same passband in the half lattice type of filter. It is a back-to-back arrangement on a bifilar transformer,  $T_1$ . In practice, close matching is needed to make the cascaded half lattice filter work properly.

The full lattice crystal filter of Fig. 8 uses four crystals like the cascade half-lattice, but the circuit is built on a different basis. It uses two tuned transformers,  $T_1$  and  $T_2$ , with the two pairs of crystals that are cross-connected across the tuned sections of the transformers. Crystals  $Y_1$  and  $Y_3$  are of one frequency, while  $Y_2$  and  $Y_4$  are the other frequency in the pair.

The principal advantage of the full-lattice filter is the use of two different frequencies instead of one frequency for the crystals. It is more difficult to match four crystals than two.

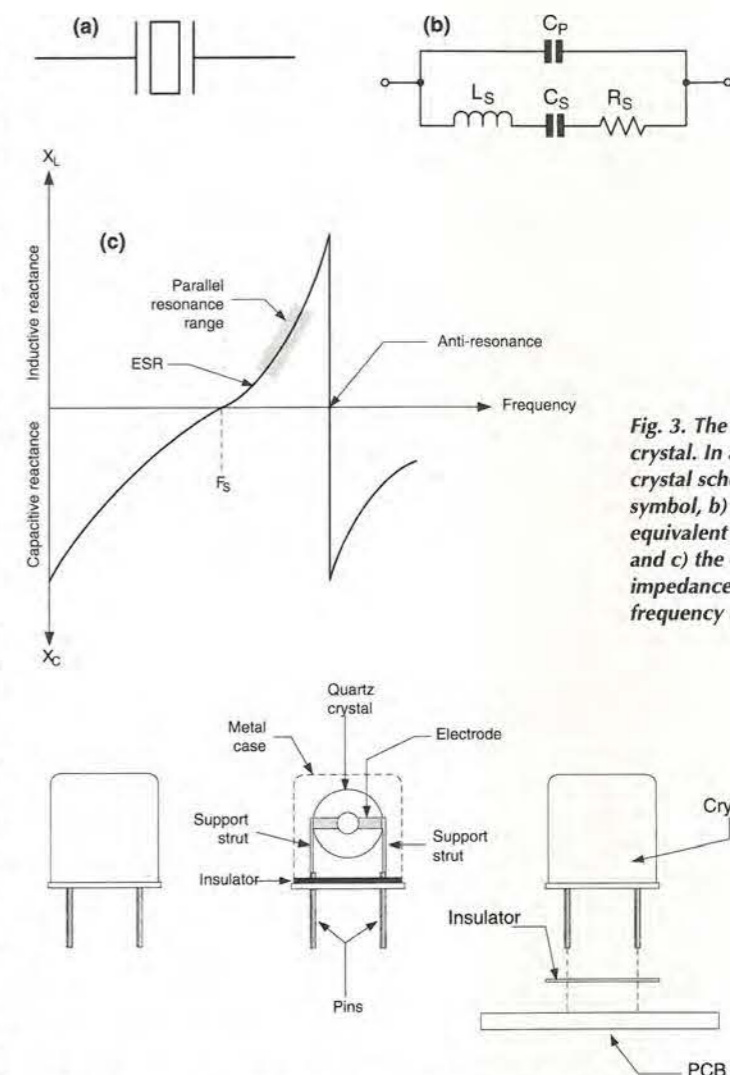


Fig. 3. The quartz crystal. In a) is a crystal schematic symbol, b) an equivalent circuit and c) the crystal's impedance-versus-frequency curve.

Fig. 4a) Crystal package; b) in cut-away form showing inside; c) Mounting on a printed wiring board.

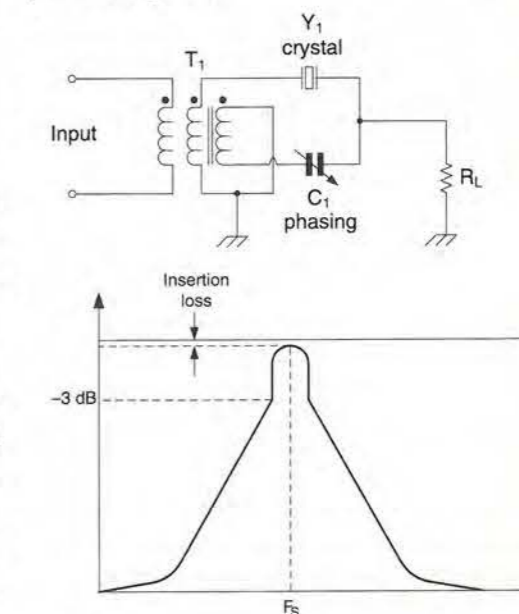


Fig. 5a). Simple crystal intermediate filter and b), its resonance curve. The transformer is trifilar. Capacitor  $C_1$  is for cancelling parallel capacitance.



Fig. 6. Half-lattice crystal filter, a), and its resonance curve, b). This type of filter is used in low-cost radios.

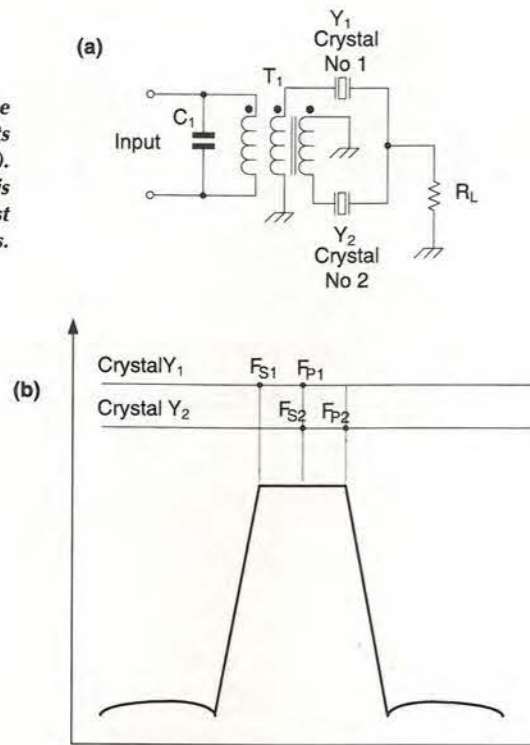


Fig. 7. Cascade half-lattice crystal filter has increased skirt selectivity over the standard half lattice.

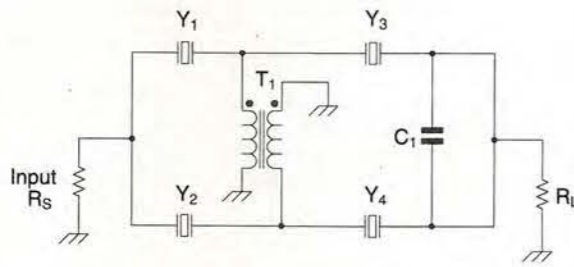


Fig. 8. Full lattice crystal filter involves two tuned transformers.


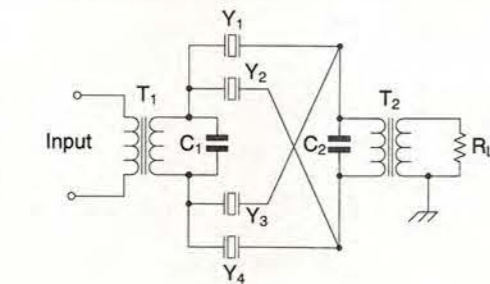


Fig. 9a). This type of filter, a), uses two crystals of the same frequency and results in a pass curve with asymmetrical slopes, as is evident in resonance curve b).

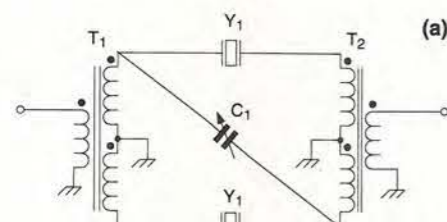

A different sort of filter is shown in Fig. 9a), with its asymmetrical attenuation curve shown in Fig. 9b). This filter has a more gradual fall-off on one side than on the other, Fig. 9b).

The filter has the advantage that the frequencies of crystals Y1 and Y2 are the same frequency. Capacitor C1 is included in the circuit to allow tuning of the desired pass band. The bandwidth of this filter is only half what is expected from the half-lattice crystal filter above.

**Crystal ladder filters**

Figure 10 shows a crystal ladder filter. This filter has several advantages over the other types.

- All crystals are the same frequency – no matching is required.
- Filters may be constructed using an odd or even number of crystals.
- Spurious responses are not harmful – especially for filters over four or more sections.
- Insertion loss is very low.

Both Butterworth and the equi-ripple or Chebyshev responses can be created using this design. Ideally, in Chebyshev designs the number of positive peaks should be the same as the number of crystals. Response should also be of equal amplitude over the passband of the filter.

In reality, fewer peaks than that are found, some being merged with each other. Additionally, the amplitude of the ripple increases towards the edges of the band.

Designing this filter can be simplified by using a test fixture to dope out the problem first. The value of the end capacitors is,

$$C_{END} = \left[ \frac{1.59 \times 10^5}{R_s F_o} \right] \times \left[ \sqrt{\frac{R_s}{R_{END}}} - 1 \right] - 5$$

The value of the coupling capacitors is,


$$C_{JK} = 1326 \left[ \frac{\Delta f}{B k_{JK} F_o} \right] - 10$$

And the value of R<sub>END</sub> is,

$$R_{END} = \left[ \frac{120B}{q \Delta f} \right] - R_s$$

Where:

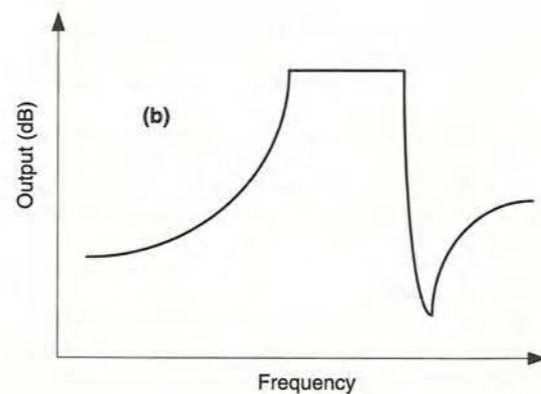- B is the bandwidth in hertz.
- C<sub>END</sub> is the end capacitance in picofarads.
- C<sub>JK</sub> are the shunt capacitors in picofarads.



- F<sub>O</sub> is the crystal centre frequency.
- Δf is the bandwidth measured in a test fixture.
- k<sub>JK</sub> is the normalised values given in tables 1 and 2.
- q is normalised end section Q given in tables 1 and 2.
- R<sub>S</sub> is the end termination of the filter, R<sub>S</sub> > R<sub>END</sub>.
- R<sub>END</sub> is the end termination to be used without matching capacitors.

A special version of the crystal ladder filter is the Cohn filter or 'minimum-loss' filter of Fig. 11.

This filter rotates the end capacitors, and makes the shunt capacitors equal value. It preserves a reasonable shape factor, while minimising loss when built with practical resonators.

Like the crystal ladder filter, the Cohn filter uses same frequency crystals throughout. The error in frequency between the crystals, ΔF<sub>O</sub>, should be less than 10% of the desired bandwidth of the filter.

The design procedure given by Hayward (1987) is simplified:

- Pick a crystal frequency in the range 2 to 12MHz. Hayward used 3.579MHz colour burst crystals.
- Pick a capacitance for the filter. A good start is 200pF – higher capacitance yields narrower bandwidth but higher insertion loss.
- Vary the end termination impedance to obtain a ripple-free pass band while providing sufficient stop band attenuation.

Table 3 gives various Cohn filter bandwidths, termination impedances and capacitor values for a three-crystal filter.

**Monolithic ceramic crystal filters**

Figure 12 represents a monolithic crystal filter. The principal benefit of this type of filter is its price, which is low enough to allow its use in low-cost consumer radios. Only a few monolithic filters have the shape factor needed for high-performance receivers though.

These filters are often made with synthetic piezoelectric resonators, rather than quartz. They are made in small packages, with some being made in crystal packages and some being made in special packages. Some of the special packages are smaller than crystals, and some are larger.

**Mechanical filters**

Considerable improvement in filter action is possible with the use of the mechanical filter. These filters were once

Table 1. Normalised k and q values for Butterworth response.

N	q	k <sub>12</sub>	k <sub>23</sub>	k <sub>34</sub>	k <sub>45</sub>
2	1.414	0.7071	–	–	–
3	1.0	0.7071	0.7071	–	–
4	0.785	0.8409	0.4512	0.8409	–
5	0.618	1.000	0.5559	0.5559	1.0

Table 2. Normalised k and q values for Chebyshev response.

N	q	k <sub>12</sub>	k <sub>23</sub>	k <sub>34</sub>	k <sub>45</sub>
2	1.638	1.6362	0.7016	–	–
3	1.433	0.6618	0.6618	–	–
4	1.345	0.685	0.5421	0.685	–
5	1.301	0.7028	0.5355	0.5355	0.7028

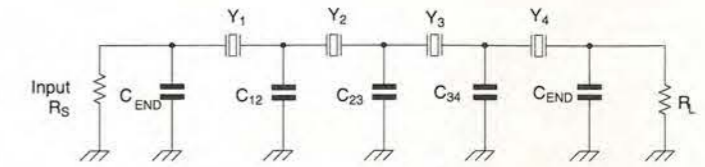


Fig. 10. Crystal ladder filter has a number of advantages over the other types, one of them being that its spurious are not problematical.

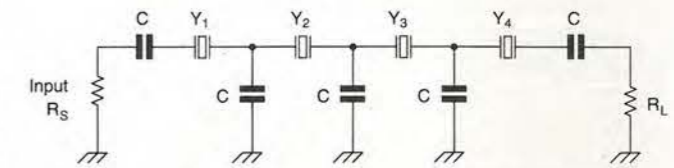


Fig. 11. Cohn ladder filter, also known as minimum-loss filter.

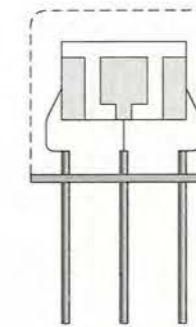


Fig. 12. Outline of a monolithic crystal filter's construction.

Table 3. Cohn three-crystal filter.

Bandwidth	C (pF)	R <sub>END</sub> (Ω)
380	200	150
600	130	238
1000	70	431
1800	30	1500
2500	17	3300

used in Collins high-end radio receivers and SSB transmitters. They are now more widespread, although the Rockwell/Collins company still makes the filters.

The basic principle of operation is the phenomenon of magnetostriction, that is the length or circumference of a piece of material will change when it is magnetised. Nickel changes in this way when magnetised, but only by about one part in about 20000.

Other materials, such as ferrites or powdered-irons (types 61, Q1 or 4C4), provide much stronger magnetostriction effects. In addition, these materials have a high electrical resistivity, so eddy current losses are minimised, and they

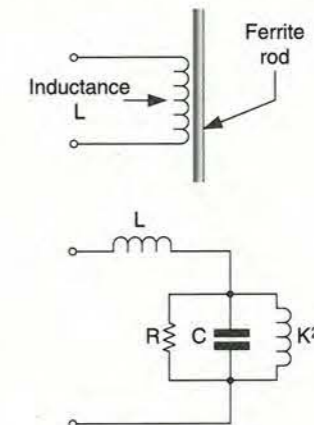


Fig. 13. Mechanical resonator, a), and its equivalent circuit, b). The coil is wound on the rod in such a way that it is free to slip, allowing the rod to expand and contract when subjected to a magnetic field.



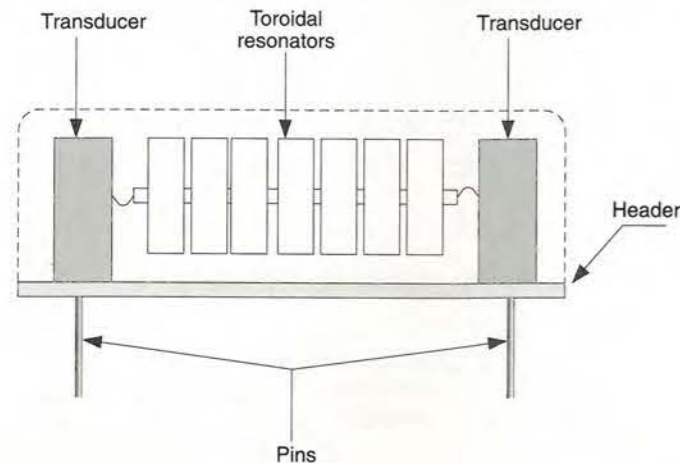


Fig. 14. Mechanical filter structure built using toroidal resonators.

have a mechanical Q on the order of several thousand. They make far better filters than nickel!

The typical ferrite material is formed at 1300 to 1400 degrees Celsius, and has a Q determined by the proportions of oxides used in the formation of the ferrite material.

Figure 13a) shows a magnetostrictive resonator, while Fig. 13b) shows the equivalent circuit. The ferrite rod is wound with a coil such that it is a slip fit. It is biased magnetically with either a permanent magnet or a DC component to the electrical signal applied to coil L.

When alternating current flows in the coil, it adds to or subtracts from the magnetic field of the bias, causing the ferrite length to oscillate. But with the parallel resonant component, Fig. 13b), there's a sharp peak in the response at a frequency equal to the mechanical resonance frequency. When the ferrite rod is wound into a toroidal shape the circumference, hence the radius, of the toroid shape varies as it is magnetised.

Figure 14 shows a mechanical filter built using toroidal resonators. Various mechanical filters are available in frequencies between 60kHz and 600kHz. A pair of transducers are located at either end of the filter to translate electrical energy to mechanical energy, and vice versa.

The resonators supply a sharp shape factor of up to 1.2:1 (60-to-6dB), with Qs of 8000 to 12000. This is up to 150 times the Q of crystal filters.

Over a temperature range of  $-25^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$ , the change of resonant frequency is as little as 1.5 parts per million. In one test, the frequency shift for eight months was one part per million.

The mechanical filter consists of three basic parts: a) the transducers, b) the mechanically resonant discs, and c) disc coupling rods. The transducer is a magnetostrictive device that converts electrical energy to mechanical vibrations, and vice versa. The resonant discs form parallel resonant circuits, so increasing the number of discs decreases the bandwidth of the circuit. ■



#### Further reading

- The ARRL Handbook for Radio Amateurs 1998 (CD-ROM Version), Chapter 16.
- Bottom, V E, (1982), 'Introduction to Quartz Crystal Unit Design', New York: Van Nostrand Reinhold Co.
- Carver, Bill, (1993), 'High-Performance Crystal Filter Design', *Communications Quarterly*, Winter 1993.
- Colin (1958), 'Narrow Bandpass Filters Using Identical Crystals Design by the Image Parameter Method' (in French), *Cables and Transmission*, Vol. 21, April 1967.
- Cohn, S. (1957), 'Direct Coupled Resonator Filters', *Proceedings of IRE*, February 1957.
- Cohn, S. (1959), 'Dissipation Loss in Multiple Coupled Resonators', *Proceedings of IRE*, August 1959.
- Dishal, 'Modern Network Theory Design of Single Sideband Crystal Ladder Filters', *Proceedings of IEEE*, Vol. 53, September 1965.
- Gottfried, Hugh L. (1958), 'An Inexpensive Crystal-Filter I.F. Amplifier', *QST*, February 1958.
- Hamish, (1962), 'An Introduction to Crystal Filters', *RSGB Bulletin*, January and February 1962.
- Hardcastle, J A, (1978), 'Some Experiments with High-Frequency Ladder Crystal Filters', *QST*, December 1978, and *Radio Communications* (RSGB) January, February, and September 1977.
- Hardcastle, J A, (1980), 'Ladder Crystal Filter Design', *QST*, November 1980, pp. 22-23.
- Hayward, W. (1982), 'A Unified Approach to the Design of Crystal Ladder Filters', *QST*, May 1982, pp. 21-27.
- Hayward, W. (1987), 'Designing and Building Simple Crystal Filters', *QST*, July 1987, pp. 24-29.
- Makhinson, Jacob, (1995), 'Designing and Building High-Performance Crystal Ladder Filters', *QEX*, No. 155, January 1995.
- Pochet, 'Crystal Ladder Filters,' *Technical Topics, Radio Communications*, September 1976, and *Wireless World* July 1977.
- 'Refinements in Crystal Ladder Filter Design,' *QEX*, No. 160, June 1995 (CD-ROM version).
- Sabin, William E, (1996), 'The Mechanical Filter in HF Receiver Design,' *QEX*, March 1996.
- Sykes, 'A New Approach to the Design of High-Frequency Crystal Filters', *Bell System Monograph* 3180. n.d.
- Van Roberts, Walter B, (1953), 'Magnetostriction Devices and Mechanical Filters for Radio Frequencies Part I: Magnetostriction Resonators', *QST*, June 1953.
- Van Roberts, Walter B, (1953), 'Magnetostriction Devices and Mechanical Filters for Radio Frequencies Part II: Filter Applications', *QST*, July 1953.
- Van Roberts, Walter B, (1953), 'Magnetostriction Devices and Mechanical Filters for Radio Frequencies Part III: Mechanical Filters', *QST*, August 1953.
- Vester, Benjamin H, (1959), 'Surplus-Crystal High-Frequency Filters: Selectivity at Low Cost', *QST*, January 1959, pp. 24-27.
- Zverev, A L, (1967), *Handbook of Filter Synthesis*, New York, pub. John Wiley & Sons.
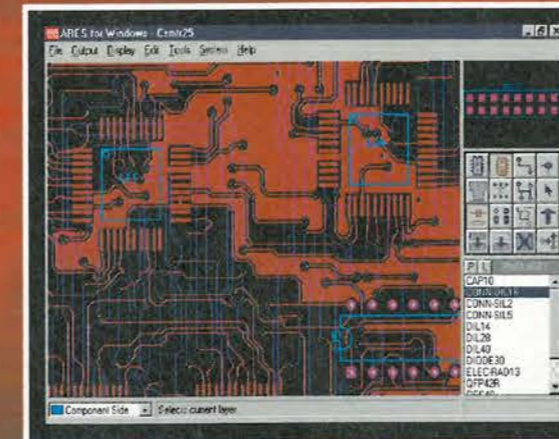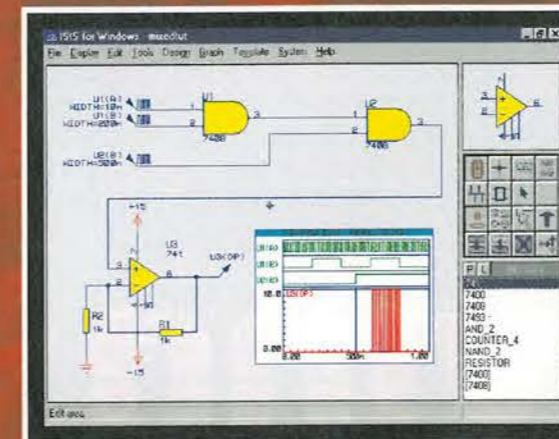
# PROTEUS

including **NEW SIMULATOR**  
**PRO SPICE 3F5**

**NEW**  
NOW WITH  
Interactive Circuit  
Animation



SHAREWARE VERSIONS  
NOW WITH INTERACTIVE CIRCUIT ANIMATION  
DOWNLOAD YOUR COPY NOW  
<http://www.labcenter.co.uk>

"the  
**BEST all-round  
PROGRAM"**  
EWW CAD Review Round Up September 1998

labcenter  
Electronics

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.  
Tel: 01756 753440. Fax: 01756 752857. EMAIL: [info@labcenter.co.uk](mailto:info@labcenter.co.uk)  
53-55 Main St, Grassington. BD23 5AA. WWW: <http://www.labcenter.co.uk>

Fully interactive demo versions available for download from our WWW site.  
Call for educational, multi-user and dealer pricing - new dealers always wanted.  
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

#### Simulation

- Berkeley SPICE3F5 analogue simulation kernel.
- True mixed mode simulation.
- New analysis types include multi-plot sweeps, transfer curves, distortion and impedance plots.
- Active Components: Switches, Pots etc.
- Over 1000 new library parts with SPICE models.
- Greater ease of use.

"a constant high level  
of capability throughout"

EWW CAD Review Round Up September 1998

#### Schematic Capture

- Produces attractive schematics like in the magazines.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Full support for buses including bus pins.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.

#### PCB Design

- Automatic Component Placement.
- Rip-Up & Retry Autorouter with tidy pass.
- Pinswap/Gateswap Optimizer & Back-Annotation.
- 32 bit high resolution database.
- Full DRC and Connectivity Checking.
- Shape based gridless power planes.
- Gerber and DXF Import capability.

Available in 5 levels - prices from £295 to £1625 + VAT.  
Call now for further information & upgrade prices.



# Don't get mad.

# Get leaving.

totally change your life



totaljobs.com

If you're unhappy at work, totaljobs.com can put a smile on your face. We've thousands of interesting jobs and we're adding vacancies all the time, to make us the UK's leading recruitment website. You can post your CV on the site, apply for jobs online, and even be notified of any new jobs that might suit you. So, if you want to leave your troubles behind you, you'd be mad not to visit totaljobs.com

IN ASSOCIATION WITH  
**ELECTRONICS  
WORLD**

# John

## a lifetime in electronics

**The coming of the transistor – this month John remembers the emergence and evolution of early transistor audio power amplifiers including the Lin design and his own 75 watter.**

**D**uring the 1950s, a new type of amplifying device emerged in fits and starts – and in some strange shapes – from the semiconductor manufacturers' laboratories. By the end of the decade, reasonably reliable and workmanlike components were readily available.

I had begun to introduce low-power dual-transistor gain blocks of the type shown in Fig. 6 in my domestic 'hi-fi'. These blocks were low-noise small-signal circuits with a low distortion of typically less than 0.01% at 1kHz and 1V RMS.

In this application, the freedom from heater-circuit wiring, the relatively low noise and the almost complete absence of mains-frequency hum in filter and frequency-correction circuits was welcome. Also, due to the fact that the devices gave off little heat in low-power use, one could, at last, make drift-free FM tuners.

However, there was no doubt that many reasonably competent electronics engineers found it difficult to come to terms with the 'solid-state' revolution.

### The transition to transistors

Junction temperatures in excess of about 200°C for silicon devices – and even less for germanium ones – could cause permanent damage to a transistor, even after brief overheating. This snag was made worse because the devices were polarity sensitive. Excessive currents could flow if they were inadvertently connected the wrong way round.

By comparison, valves mostly didn't object to even severe overloads – pro-

vided that they were brief. Nor, for that matter, did valves mind being connected the wrong way round. They just didn't work.

If one complicates the issue by noting that transistors could also burst into unexpected – and sometimes damaging – parasitic oscillation, and consequently expire before your eyes, it is easy to understand why many would-be users retired hurt after their first encounters with solid-state components.

From a design point of view, the transistor differed from the valve because it was a current, rather than a

voltage, operated device. All its electrodes presented internal conductive paths, whereas in a valve such inter-electrode paths were usually virtually open-circuit.

However, there were electronic circuit design engineers who were at home with these components, and they soon turned their attention to audio applications.

### Transistor audio amplifiers

From the late 1950s, circuit designs for transformer-coupled audio amplifiers, based on germanium p-n-p diffused

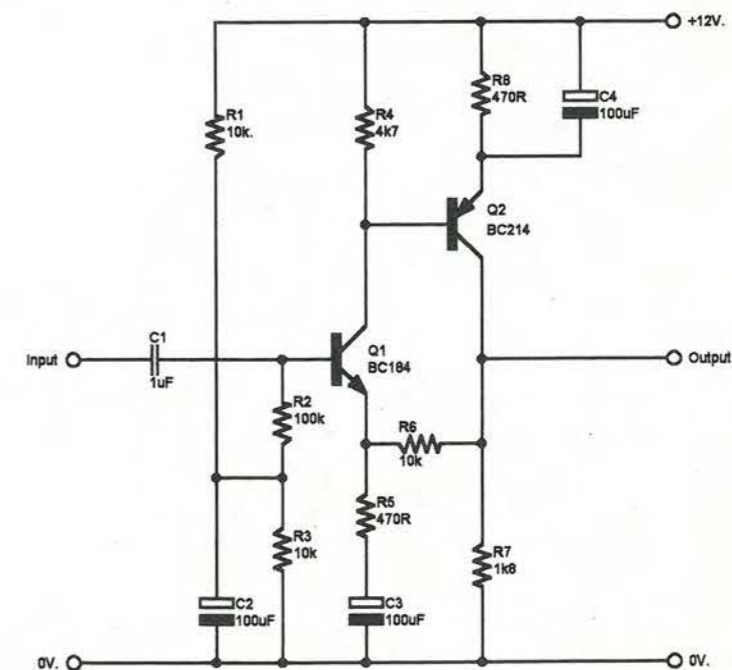


Fig. 6. Low distortion gain block.



junction transistors had been presented by transistor manufacturers. These germanium devices were the only ones commercially available at the time.

However, as in the case of valve-operated audio output stages, the challenge that remained was to eliminate the inter-stage coupling transformers.

These transformers were sources of distortion and they limited the frequency and phase linearity of the system. Moreover, even loudspeaker coupling output transformers shouldn't be needed with low impedance output loads such as a loudspeaker.

**The Lin design**

An almost complete answer to the demand for a transformerless audio power amplifier was proposed by H C Lin in 1956. At that time the only available power transistors were p-n-p by the way.

Lin's design is principally remembered for the introduction of the 'quasi-complementary' output stage layout. This involves a p-n-p/p-n-p and n-p-n/p-n-p arrangement used to simulate a symmetrical polarity pair of emitter-followers as the output group.

However, Lin's real contribution to amplifier design lay in his use of a low-power voltage amplifying stage followed by a low or unity-gain impedance conversion stage. This layout has been adopted for almost every power output stage design since then - not forgetting some thousands of op-amps. Lin's design is shown in Fig. 7.

This circuit gave some 6W output with around 1% distortion, and covered the audio range of 30Hz-15kHz within  $\pm 1$ dB. At that time, for reference, the better high power valve amplifiers could give 25 watts at less than 0.05% and with a 5Hz-50kHz bandwidth. However, these were early days, and I was quite content with my Williamson mono set up - the snag lying in the 'mono' bit.

**Turntable trauma**

When my old friend, the Seascale carpenter, made the cabinets for our two radiograms, he fitted each with a Decca turntable and its XMS sapphire-stylus pick-up. This seemed quite a good choice in 1952, before the advent of stereophonic LPs, even though the playing weight of the spring counter-balanced head was 40g or thereabouts.

Sadly though, there was no way that the Decca system would play a 'stereo' disc without jumping up and down during the loud bits.

Replacing the turntable and pick-up would have presented little difficulty, though any new system would probably not have fitted as snugly as the original joiners installation.

The real problem was what to do about the single Williamson power amplifier. Quite apart from the cost and difficulty of buying and installing another Williamson, with its separate 450V power supply, there simply wasn't room in the cabinet to accommodate it.

So my thoughts turned to constructing two equivalent transistor power amplifiers. This solution would certainly save space, but it had to sound as good too.

Fig. 7. Audio amplifier due to Lin.


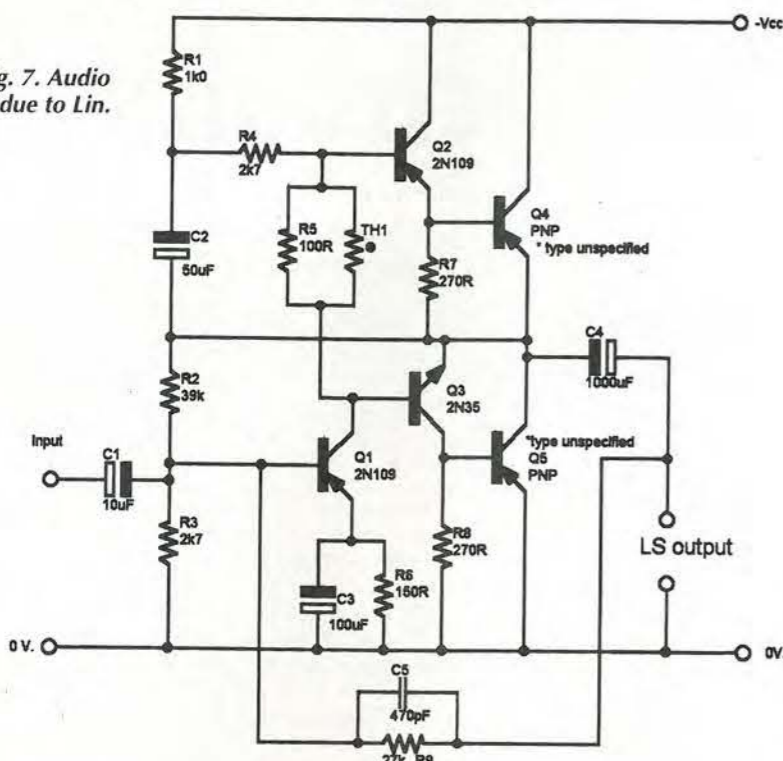


Fig. 8. The 10W class A design.

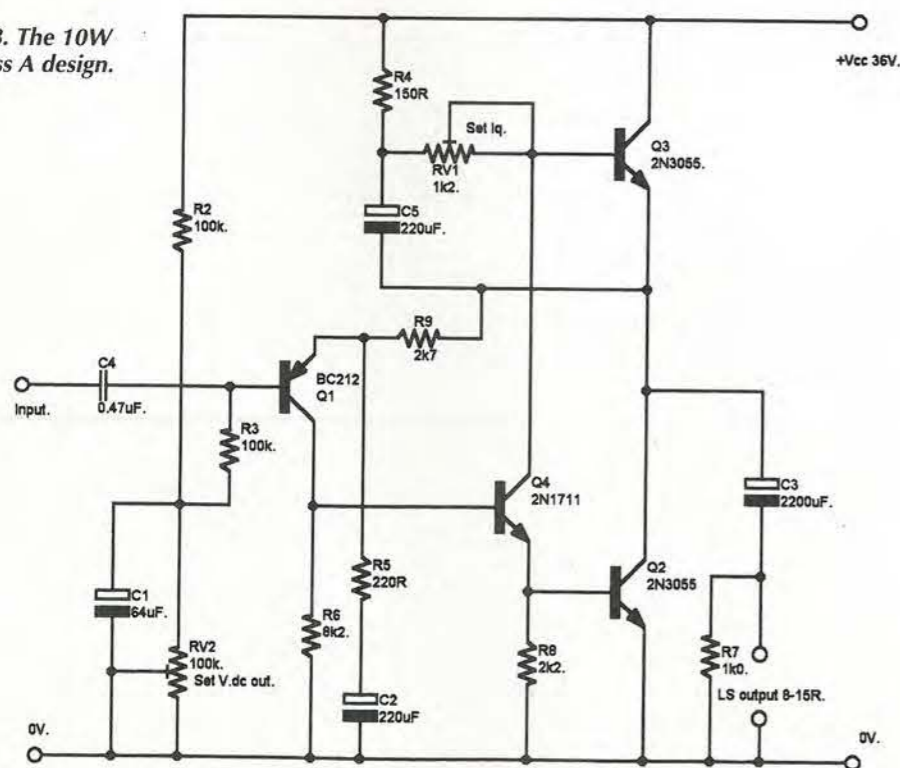

I treated the requirement as if it were for a typical industrial control system. The emphasis would be on simplicity - on the premise that 'what you don't put in won't go wrong'. I designed and made up the experimental four transistor power amplifier circuit shown in Fig. 8.

**Why was it n-p-n throughout?**

At that time, 1965, silicon p-n-p transistors were not very good, so the design used only n-p-n power devices. The opposite was the case with germanium devices, where it was the n-p-n ones which were relatively poor in performance.

This design operated in class A, which removed any problems which might arise with class 'AB' output bias level settings.

On being tested with a 35V supply line, this amplifier worked very well. It had an output power of a little over 10W, a THD figure rather better than 0.1%, and a bandwidth of 10Hz to 100kHz,  $\pm 0.5$ dB. This was very encouraging - especially when I compared its sound quality against the Williamson, and concluded that it was at least as good.

On seeing these results, I built a tidied-up stereo version as a Christmas present to myself in 1967. Some time later, I replaced the output transistors with Motorola 'epitaxial base' 2N3055s.

With an increase in the supply voltage

to 45V, the new transistors allowed an output power of more than 15W. This was equivalent to the Williamson,

though I am unconvinced that I ever needed or used more than two watts.

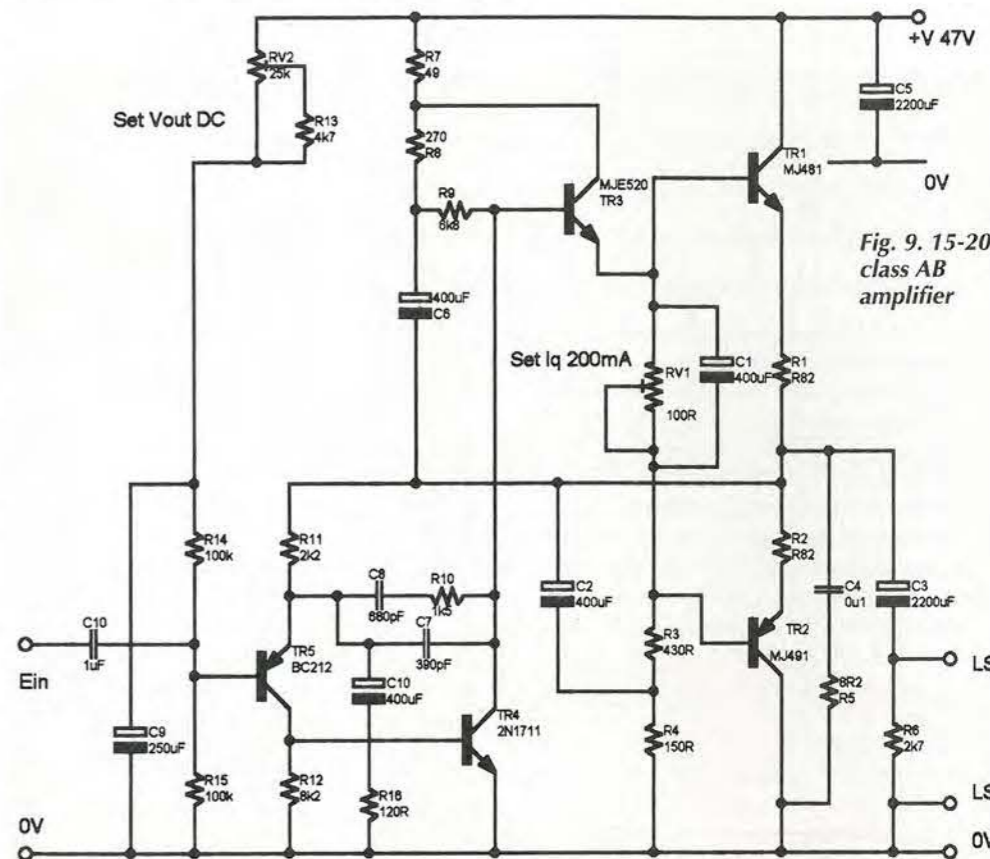


Fig. 9. 15-20W class AB amplifier

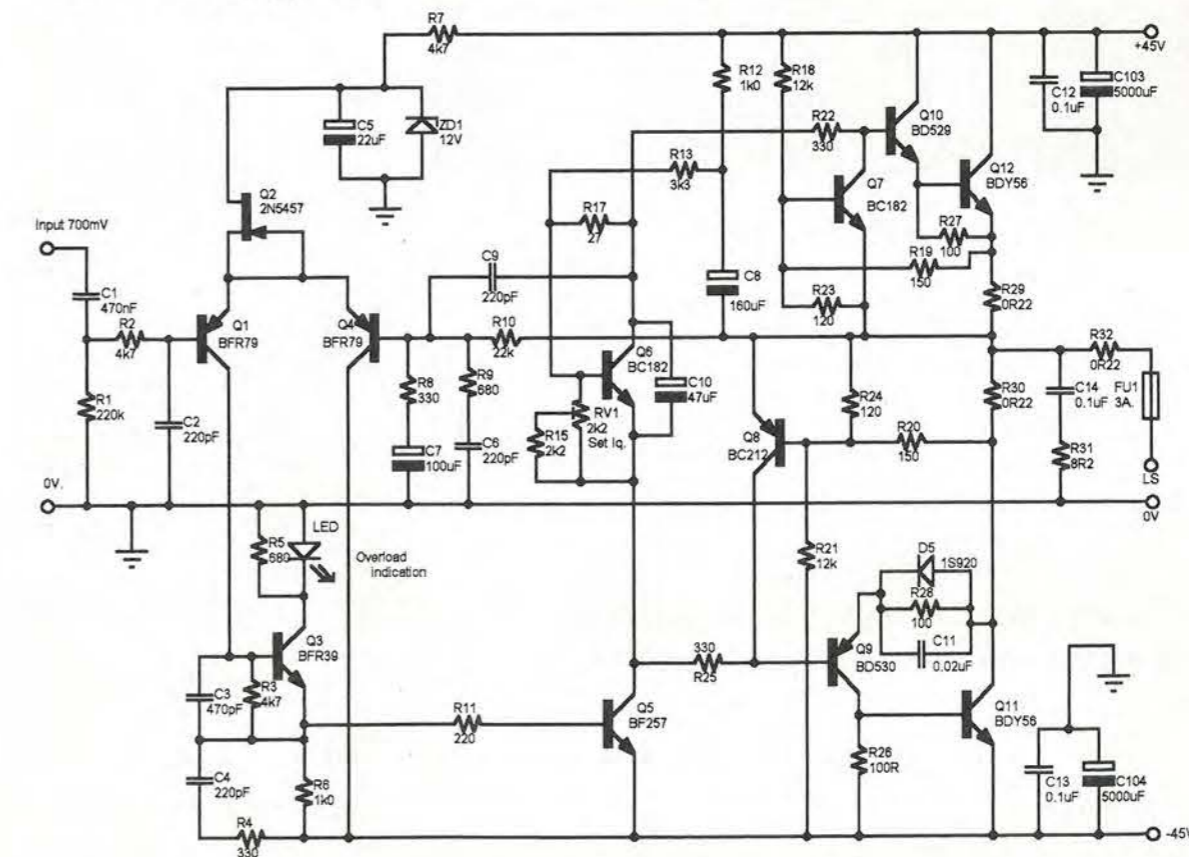


Fig. 10. 75 watt amplifier



Unlike the Lin design, my 10W Class-A circuit did not use a push-pull pair of output devices to provide the required low output impedance. Instead it used a 'Darlington pair' connected amplifier stage, comprising  $Q_1$  and  $Q_3$ , driving  $Q_2$  as an active load. Transistor

$Q_4$  gave increased loop gain for the AC and DC feedback loops.

**My first audio article**

It had not occurred to me to seek to publish my design. But two of my friends urged me to do so.

John Greenbank, an assistant editor on *Wireless World* at the time, greeted my contribution with enthusiasm. Unknown to me, the topic of Class-A versus Class-AB was one of current hi-fi debate. As a result of this publication, I suddenly found myself to be a hi-fi guru.

I was urged to offer more audio circuit designs. Two worthy of recalling were the simple 15-20W class AB circuit shown in Fig. 9 and a 75W design subsequently published in *Hi-Fi News* in 1972.

Of these designs, the 15-20W was aimed to give the same quality as the original 10W amplifier, but with more power at a much lower heat dissipation.

An unexpected tribute to its performance came at a lecture from a representative of a most eminent loudspeaker manufacturer. He mentioned that the company liked my design a lot – so much in fact that it had been adopted as an 'in-house' design.

The 75W design did not owe its inception to any feeling on my part that I needed more output power. It arose from a chance discussion with the managing director of a large speaker manufacturing company at one of the then popular annual Olympia or Earls Court Hi-Fi shows, where I had given a lecture.

The subject of our discussion was the incorporation of power amplifiers into the body of the speaker cabinet. This idea would allow the frequency response equalisation and cross-over networks to be provided at low power and high impedance – an arrangement which we both felt to be a good thing.

The question I then asked was what amplifier power should be provided. I was told '75W into 8Ω at 0.01% THD'. This was an interesting challenge, and I spent the next few months of my spare time trying out various likely circuit arrangements.

**High-power audio**

The final amplifier circuit, shown in Fig. 10, was demonstrated at a BKSTS lecture in London. The chairman was Mike Jones, technical editor of *Hi-Fi News*, where the circuit design subsequently appeared.

This design was offered in kit form by several manufacturers and proved enormously popular. At that point I resolved I would do no more audio amplifier designs. They took up too much time.

Alas, I did not keep to my resolve. There were two reasons for this – technical curiosity and requests from friends.

In the next article, John looks at the coming of the IC.



**GET EXPERT HELP!  
BUY TWO OF JOHN LINSLEY HOOD'S BOOKS FOR THE FANTASTIC PRICE OF JUST £38.99 – fully inclusive!**

Leading expert in the audio field John Linsley-Hood presents the wisdom of his lifetime in electronics in two excellent books.

Priced at £25.00, *Audio Electronics* covers audio techniques and equipment and explains the role that electronics plays in sound reproduction. This book is a must for anyone involved in designing, adapting and using digital and analogue audio equipment.

*Valve & Transistor Audio Amplifiers* normally costs £19.99. This work covers everything from classic amplifiers to new designs using the latest components.

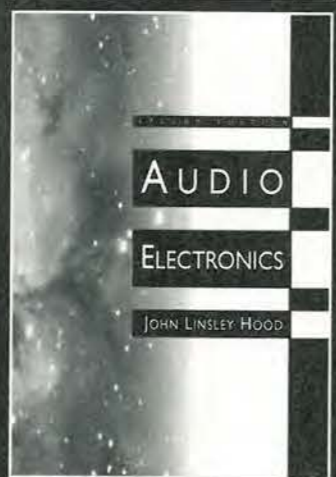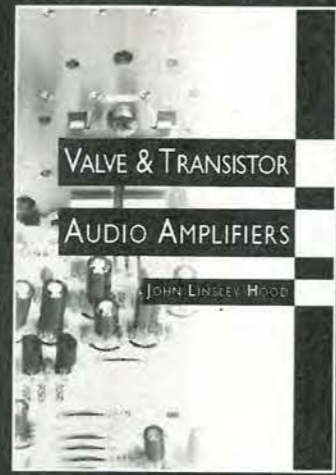Offer closes 31 December 2000 so order now and rely on John Linsley Hood to keep you ahead of the rest!  
Return to Jackie Lowe, Room L514, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS



Please supply the following titles:

**Audio Electronics/Valve & Transistor Audio Amplifiers**

Total \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Telephone \_\_\_\_\_

Method of payment (please circle) Access/Mastercard/Visa/Cheque/PO

**Cheques should be made payable to Reed Business Information**

Credit card no \_\_\_\_\_

Card expiry date \_\_\_\_\_

Signed \_\_\_\_\_

# What is Bluetooth?

Soon it will be possible to connect peripherals to your PC via an rf link using a wireless local network technology called Bluetooth. Geoff Lewis outlines how it works.

**B**luetooth is the title used for an open-specification system designed to provide a fast and secure short range radio interconnection between portable devices and a local area network (LAN) through the use of spread spectrum techniques. The services provided for include internet, e-mail, image and data transmission together with voice applications extending to three simultaneous 64kbit/s PCM channels.

The concept has been adopted by about 2000 diverse user organisations and is supported by many of the major semiconductor chip manufacturers. These include Intel, Toshiba, VLSI, Nokia, Texas Instruments, Ericsson, Thomson (ST), Lucent and Siemens. In addition, the Bluetooth standards have gained the approval of the FCC (Federal Communications Commission), ETSI (European Telecommunications Standards), the IEEE (Institute of Electrical and Electronic Engineers) and the IrDA (Infrared Data Association) for global use.

The 'user portable terminal devices' involved can include mobile phones, headsets, printers, digital cameras, PDAs (personal digital assistants) and lap/palm top and notebook computers. The emphasis is to provide a robust worldwide system capable of acting as a cable type of replacement at low cost with plug and play capabilities.

**The transmission system**

The system operates in the license-free Industrial, Scientific and Medical, or ISM, band from 2.4GHz to 2.5GHz and employs frequency-hopping spread-spectrum (FHSS) technology.

For this application, FHSS is preferred to the more common direct-sequence spread-spectrum (DSSS) system.

While FHSS is somewhat slower in operation, it is much simpler to implement through the use of a frequency synthesiser. The power output of the transmitters ranges from 1 to 2.5mW (0 to 4dBm) to provide a

coverage of at least 10 metres – a range that can be increased to 100 metres by the use a radio-frequency power amplifier.

A prime number (79) of sub-carriers, spaced by 1MHz, occupies the band 2.402MHz to 2.480MHz. Each sub-carrier is frequency modulated with a deviation of either -140kHz to -175kHz for binary 0 or +140kHz to +175kHz for binary 1. This modulation method is referred to as Gaussian frequency-shift keying (GFSK) because the base-band digital signal is filtered to provide a Gaussian bell-shaped response with at least 90% of the pulse energy contained within the 3dB bandwidth. The resulting signal has a good spectrum efficiency and resilience to co-channel interference (CCI).

Each sub-carrier can be switched at the rate of 1600 frequency hops per second to provide a spread spectrum signal with a hop period of 625µs. The maximum bit rate is currently set to 1Mbit/s but because each sub-carrier can carry multiple bits during

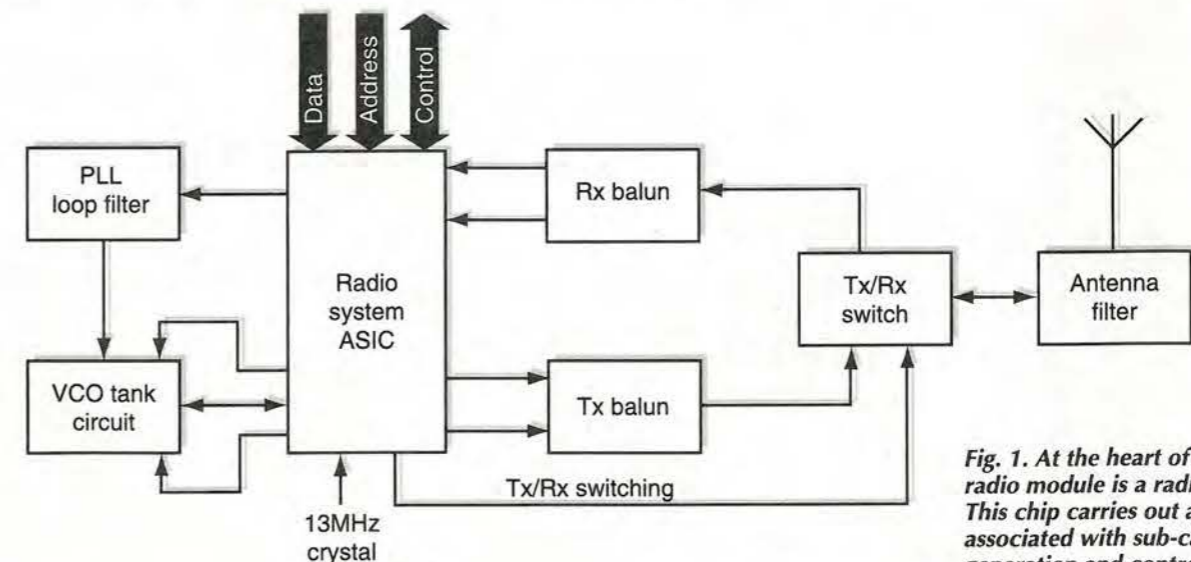


Fig. 1. At the heart of a Bluetooth radio module is a radio-system ASIC. This chip carries out all functions associated with sub-carrier generation and control.



each time slot, this figure might be doubled in the near future.

A bandwidth bit period ( $Bw \cdot T_{bit}$ ) product of 0.5 has been set for Bluetooth. For a maximum bit rate of 1Mbit/s, this yields a signal bandwidth of  $0.5 \times 10^6$ , which is 500kHz. Under these conditions, the system has an adjacent carrier interference (ACI) ratio of better than -20dBm. If the bit rate is increased to 2Mbit/s then this ACI protection ratio will be reduced.

### Bluetooth's radio module

As currently configured, each Bluetooth terminal is constructed around two highly integrated modules. Each contains an application-specific integrated circuit (ASIC) designed to handle the radio functions and the baseband signal processing.

The basic module is constructed on a laminated substrate consisting of seven layers of metal interleaved by six layers of ceramic. This is then connected to a PCB via ball grid array (BGA) mounts.

The lower metal layer acts as a ground plane while the component side carries a pair of metal screens to complete the electromagnetic shielding. In order to maintain good interference rejection, the various earths points are distributed around the ground plane.

As Fig. 1 illustrates, the radio system ASIC carries out all the functions associated with the generation and control of the sub-carrier frequencies. This is achieved through the use of a voltage-controlled oscillator, or VCO, linked to a phase-locked loop circuit. In turn, the PLL is locked to the output of a 13MHz

crystal oscillator.

A VCO tank circuit forms part of the PLL circuit. Its tuned load is laser trimmed for accuracy. A loop filter is used to remove any ripple from the output of the PLL circuit. For receive purposes, this IC employs a heterodyne technique to generate a low IF at 3MHz.

Spread-spectrum frequency-hopping modulation is performed directly on the VCO. A pair of balun circuits convert the balanced signals used within the ASIC into the unbalanced form used externally for transmission and reception.

An antenna switch diverts the signals between the baluns and the antenna input/outputs for the transmit/receive functions. The antenna filter reduces the harmonic radiation from the terminal device during transmit and helps to minimise the unwanted interference effects during receive. The antenna feed is designed to match a 50Ω impedance load.

### Baseband signal processing module

Figure 2 is a simplified block diagram of the baseband signal processor. The ASIC in this stage contains an embedded reduced instruction-set computer core that controls the operation of the radio section and the inputs from either of the input/output interfaces.

A flash reprogrammable memory carries the software that provides the overall control of the system. The supply voltage is well regulated and filtered to provide power for both the signal interfaces and the transceiver. The 13MHz clock signal from the radio section is used to synchronise

the action of the processor ASIC.

The universal asynchronous receiver transmitter, or UART, interface operates as a 'data circuit equipment', or DCE, device under the control of the request to send or clear to send signals RTS and CTS. In turn, these handshaking signals control the data flow lines TxD (transmit data) and RxD (receive data). This interface can handle all the standard data rates from 300bit/s up to 460.8kbit/s.

Apart from the universal serial bus standard bi-directional ports D+ and D-, two additional inputs are provided for the control of a lap/notebook computer. The 'wake-up' signal advises the host computer that the terminal has become operative and the 'detach' signal indicates a suspend operation mode. While the USB port is capable of running at 12Mbit/s, the Bluetooth operation is limited to 1Mbit/s.

The PCM interface operates at the standard sample rate of 8kHz and can handle linear PCM from 13 to 16 bits, plus both  $\mu$ -law and A-law 8-bit companded samples.

### Software and protocol

The code stored within the flash memory provides control for both host controller interface and the local link manager for the USB, UART and PCM ports. The operational protocol provides for link set up and configuration together with authentication.

To maintain a secure transmission system and a high data rate in what might well be a noisy environment, Bluetooth operates with a packet switching protocol that includes both forward error control and encryption.

### Networking Bluetooth

Bluetooth terminals are organised into small groups referred to as 'piconets'. These contain up to eight peer devices with one acting as a master for the group. The simplest network is just two devices linked by a virtual cable.


Piconets may be linked together via a terminal device that is common to two groups, but this must not be one of the masters. Each piconet has a different frequency hopping sequence and a collection of piconets is known as a 'scatternet'.

Finally, I should like to acknowledge the help received from Ericsson Components AB in preparing this article. The company's Bluetooth data sheets and extensive information on the web site,

[WWW.ericsson.com/bluetooth](http://WWW.ericsson.com/bluetooth)

have been particularly helpful. ■

Fig. 2. Baseband signal module controls operation of the radio section and inputs from either of the i/o interfaces using a RISC or DSP core.

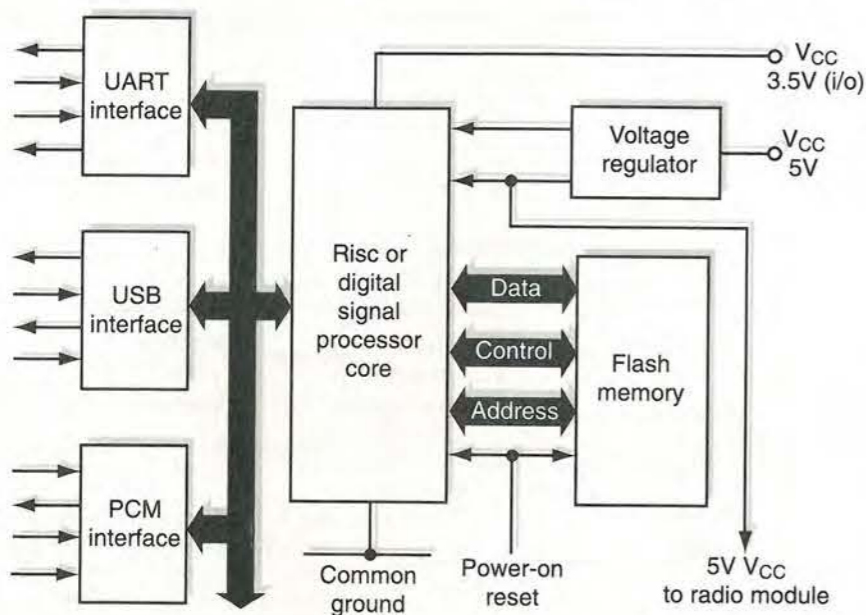

**£9.99**  
+ postage & packaging

Your Complete Guide to Car Maintenance

# The LP Is Back!

35 articles!

ISBN 1-85250-214-4  
9 781852 580217

Please send me \_\_\_\_\_ copies of The LP is Back!

Name \_\_\_\_\_

Address \_\_\_\_\_

Post code \_\_\_\_\_

Daytime phone number \_\_\_\_\_

I enclose a cheque for £ \_\_\_\_\_

Or debit my Visa \_\_\_\_\_ Master Card \_\_\_\_\_ (tick one)

Card number \_\_\_\_\_

Expiry date \_\_\_\_ / \_\_\_\_

Card-holder's signature: \_\_\_\_\_

# Love vinyl?

If you treasure your vinyl collection, this book is for you. Featuring articles from the pages of the US magazine *Audio Amateur* and other sources, it contains absolutely everything the serious LP music collector needs to get the most out of both vintage records and the highest quality new pressings.

## Articles feature:

- Cleaning discs
- How to build a cleaning machine
- Calibrating and maintaining your tonearm and cartridge
- Equipment that will improve the quality of long-play record listening

Collected from the high point of this old-new again technology, 'The LP is Back!' brings a wealth of information to help you keep your existing equipment in top form and help you understand and appreciate the best in new products available from cartridges to turntables. Published 1999, 160 pp., 8in by 10<sup>1</sup>/<sub>2</sub>in, softbound.

## Fully inclusive prices:

UK	£11.49
Europe	£11.99
ROW	£13.98

## How to order:

Post the coupon to:  
The LP is back, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, or fax 0208 652 8111,

or e-mail [jackie.lowe@rbi.co.uk](mailto:jackie.lowe@rbi.co.uk)

Please make cheques payable to Reed Business Information



# A novel inductance meter

Combining high-speed phase detection circuitry with microcontroller data processing, Michael Slifkin and Alexander Gornstein have developed an inductance meter capable of displaying accurate measurements from 20µH to 200mH on an LCD module.

There are many different ways of measuring reactance. Before the era of digital techniques, the usual methods were to use bridge circuits and to find the null point by adjusting resistors. Often the null point was very broad and it could take some time and manipulation to find the reactance value.

Reactance differs from resistance in that it is frequency dependent. Furthermore, inductance will contain some resistance, known as ohmic loss, and this will affect the measurements.

Nowadays reactance measurements can be made automatically, digitally and accurately. There are different options for carrying out such measurements and it is not always possible to say which is the best general method. Among the methods for measuring reactance are:

- Via a bridge. This method is outdated now, but you could automate the technique using a quasi bridge method to bring it up to date. This involves measuring the out-of-balance voltage or current rather than looking for a null, as is normally the case.

- Phase-shifting. Here you would use the reactance as the variable element in a phase-shifting circuit and then measure the change in phase of an oscillator working at fixed frequency. There are different ways of measuring phase change. You could use a pulse-counting technique as described in our article on a power factor meter in the February issue. Alternatively you could use the phase detector described in the April 1999 issue on page 312. It would be possible to devise a range of methods for such measurements.

- You could use the reactance as a frequency determining element in a tuned circuit and obtain the new frequency or change in frequency caused by the reactance. If the change in frequency were very small, you would probably find a linear relationship between the change and the value of the reactance.

Methods exist that are specific to the type of reactance being measured. You could measure capacitance by charging it to a known voltage and then find the discharge time. Or you could try to measure inductance by finding the back EMF when a pulse is applied to it.

Standard radio techniques can be used to measure reactance. This is not as far-fetched as it sounds. For example, a radio receiver with a BFO would detect the shifting of a carrier wave due to reactance added to the tuned circuit. You would not need to use an actual radio receiver to do this, although I once saw a radio receiver used in this manner about 45 years ago.

Nowadays you can buy chip sets comprising a transmitter and receiver in frequency and phase modulation modes that can be readily adapted to reactance measurements. This is not the subject of this article, but perhaps of one in the future.

Finally, you could try to measure the reactance directly by finding the current through the reactance at some voltage. This is the method we chose.

Although this would appear to be an obvious method, it does not seem to have been used before, probably because of the 90° phase shift between the current and the voltage introduced by the reactance. The ohmic loss also causes phase shifts of unknown value.

## The instrument in detail

Figure 1 is a block diagram of our instrument and Fig. 2 is its full circuit diagram.

The meter involves a simple analogue circuit in which the inductance to be measured is placed in series with an alternating constant current generator at the input to a high impedance FET op-amp. A voltage is produced across the inductance. This voltage is amplified. By using suitable values of gain, the amplified voltage is found to be numerically equal to the inductance.

At this point, the voltage is converted to a digital form. A processor now calculates the value of inductance according to the range and sends the reading to a 16-character by 2-line liquid-crystal display module.

The best form of detection of a sinusoidal voltage signal is the phase-sensitive detector, as mentioned above. As explained in the earlier article, the phase-sensitive detector is just a multiplier and a low-pass filter.

Our implementation of the phase-sensitive detector here is very different from that described in the previous article. In this case, we need only a fixed frequency but at the higher value of 1MHz as compared to a low frequency but variable over a wide range. The reason for using this high frequency is that the inductor has a small inherent resistance – ohmic loss – but as the reactance is given by  $\omega L$ , this can be swamped by using a relatively high value of  $\omega$ . Inductance of the component in henries is  $L$ , and  $\omega$  is the angular frequency, i.e.  $2\pi \times f$  where  $f$  is the frequency in hertz.

## Phase-sensitive detector

Digital switches together with a high quality op-amp form the phase-sensitive detector. To understand how it works, have a look at Fig. 3, which is taken from our 1999 article. The effect of the inductor is to add a 90° phase shift between the current and the voltage. Adding a 90° phase shift in the reference channel compensates for this.

In this design, the 90° phase shifter is the

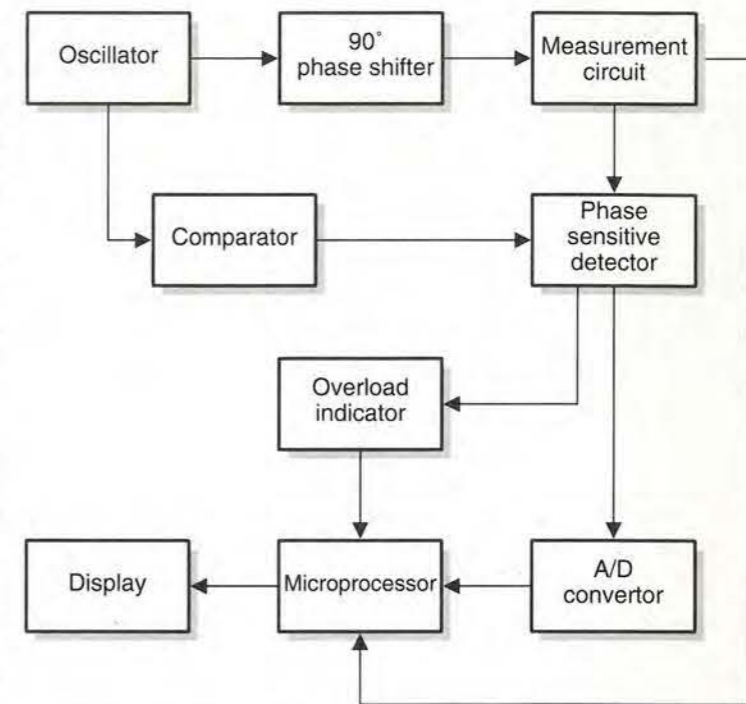


Fig. 1. Combining analogue and digital circuitry, the inductance meter. This design applies a constant-current sine-wave to the inductor under test and measures the resulting voltage.

Hexadecimal listing of 8051 code for the inductance meter. Locations not shown are filled with zeros.

```

000000 02 00 03 75 81 50 12 01 50 79 00 12 00 25 12 02 37 80 f8 e5 90 54 ...u.P..Py...8..7..Ä.T
000016 08 60 0b 12 01 68 90 05 4c 12 01 8b 80 ef 22 e5 90 b2 e4 54 10 60 ...h.L...Ö*Ä.S.T.
00002c 05 78 01 12 00 5a e5 90 b2 e5 54 20 60 05 78 02 12 00 95 e5 90 b2 ...x..zÄ.SÄT`x...Ä.S
000042 e6 54 40 60 05 78 03 12 00 d5 e5 90 b2 e7 54 80 60 05 78 04 12 01 Ètè`x...Ä.SÄT.`x...
000058 15 22 e9 98 60 0b e8 f9 12 01 5b 90 05 00 12 01 8b 11 13 e5 a0 75 ..È..E`.[.....Ätu
00006e f0 64 84 12 01 58 12 01 68 12 01 7f e5 f0 75 f0 0a 84 12 01 58 12 äd...X..h...Äuä...X.
000084 01 7f e5 f0 12 01 58 12 01 7f 90 05 35 12 01 8b 22 e9 98 60 0b e8 ..Ä.X...5...È..E
00009a f9 12 01 5b 90 05 0d 12 01 8b 11 13 e5 a0 75 f0 64 84 12 01 58 12 ...[.....Ätuä...X.
0000b0 01 68 12 01 7f e5 f0 75 f0 0a 84 12 01 58 12 01 7f 74 2e 12 01 7f .h...Äuä...X...t...
0000c6 e5 f0 12 01 58 12 01 7f 90 05 35 12 01 8b 22 e9 98 60 0b e8 f9 12 Ä.X...5...È..E.
0000dc 01 5b 90 05 19 12 01 8b 11 13 e5 a0 75 f0 64 84 12 01 58 12 01 68 .[.....Ätuä...X.h
0000f2 12 01 7f 74 2e 12 01 7f e5 f0 75 f0 0a 84 12 01 58 12 01 7f e5 f0 ...t...Äuä...X..Ä
000108 12 01 58 12 01 7f 90 05 35 12 01 8b 22 e9 98 60 0b e8 f9 12 01 5b ..X...5...È..E`.[
00011e 90 05 24 12 01 8b 11 13 e5 a0 75 f0 64 84 12 01 58 12 01 68 12 01 ..$.Ätuä...X...h
000134 7f e5 f0 75 f0 0a 84 12 01 58 12 01 7f e5 f0 12 01 58 12 01 7f 90 ..Äuä...X..Ä.X...
00014a 05 40 12 01 8b 22 c2 92 d2 92 12 01 c7 22 24 30 22 c2 90 75 80 01 .@...~if`x`$0`u..
000160 d2 91 12 02 2e c2 91 22 75 80 c0 c2 90 d2 91 12 02 2e c2 91 22 c2 "è...è"u.ç.~è...è"~
000176 90 d2 91 12 02 2e c2 91 22 75 80 d2 90 d2 91 12 02 2e c2 91 22 e4 ."è...è"1..~è...è"è%
00018c 93 b4 24 01 22 f5 80 d2 90 d2 91 12 02 2e c2 91 a3 80 ec 22 75 80 .¥$.~1..~è...èf.I`u.
0001a2 80 c2 90 d2 91 12 02 2e c2 91 22 75 80 0c c2 90 d2 91 12 02 2e c2 ~.~è...è"u..~è...~
0001b8 91 22 75 80 0f c2 90 d2 91 12 02 2e c2 91 22 c2 90 7f 20 7e ff de è"u..~è...è"~.~f
0001ce fe df fa 75 80 38 d2 91 12 02 2e c2 91 7f 14 7e ff de fe df fa 75 .fi"u.8"è...è...~fi,fi"
0001e4 80 38 d2 91 12 02 2e c2 91 7e 64 de fe 75 80 38 d2 91 12 02 2e c2 .8"è...è-dfi,u.8"è...~
0001fa 91 75 80 38 d2 91 12 02 2e c2 91 75 80 08 d2 91 12 02 2e c2 91 75 eu.8"è...èu..~è...èu
000210 80 01 d2 91 12 02 2e c2 91 75 80 06 d2 91 12 02 2e c2 91 75 80 0c .."è...èu..~è...èu..
000226 d2 91 12 02 2e c2 91 22 7f 28 7e ff de fe df fa 22 7f ff 7e ff de "è...è".(-~fi,fi".~f
00023c fe df fa 22 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 .fi".....
000252 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 .....
...
0004e6 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 .....
0004fc 00 00 00 00 55 70 20 74 6f 20 32 30 30 20 6d 48 24 55 70 20 74 6f ....Up to 200 mH$Up to
000512 20 32 30 20 6d 48 24 55 70 20 74 6f 20 32 20 6d 48 24 55 70 20 74 20 mH$Up to 2 mH$Up to
000528 6f 20 32 30 20 6d 69 63 72 6f 48 24 20 6d 48 65 6e 72 79 20 20 o 200 microH$ mHenry
00053e 20 24 20 6d 69 63 72 6f 48 65 6e 72 79 24 4f 75 74 20 6f 66 20 72 $ microHenry$Out of r
000554 61 6e 67 65 24 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 ange$.
00056a 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 .....
...
000fe6 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 .....
000ffc 00 00 00 00 .....
  
```

Michael Slifkin and Alexander Gornstein, Jerusalem College of Technology, Israel.

## Specifications

Displays three digits together with units. Overload message shown. The display is continuously updated

Measurement from 20µH to 200mH in four switchable ranges:

- Range 1 20µH to 200µH
- Range 2 200µH to 2mH
- Range 3 2mH to 20mH
- Range 4 20mH to 200mH
- Accuracy ±(1.5%+single digit)
- Voltage (V<sub>C</sub>) 8V





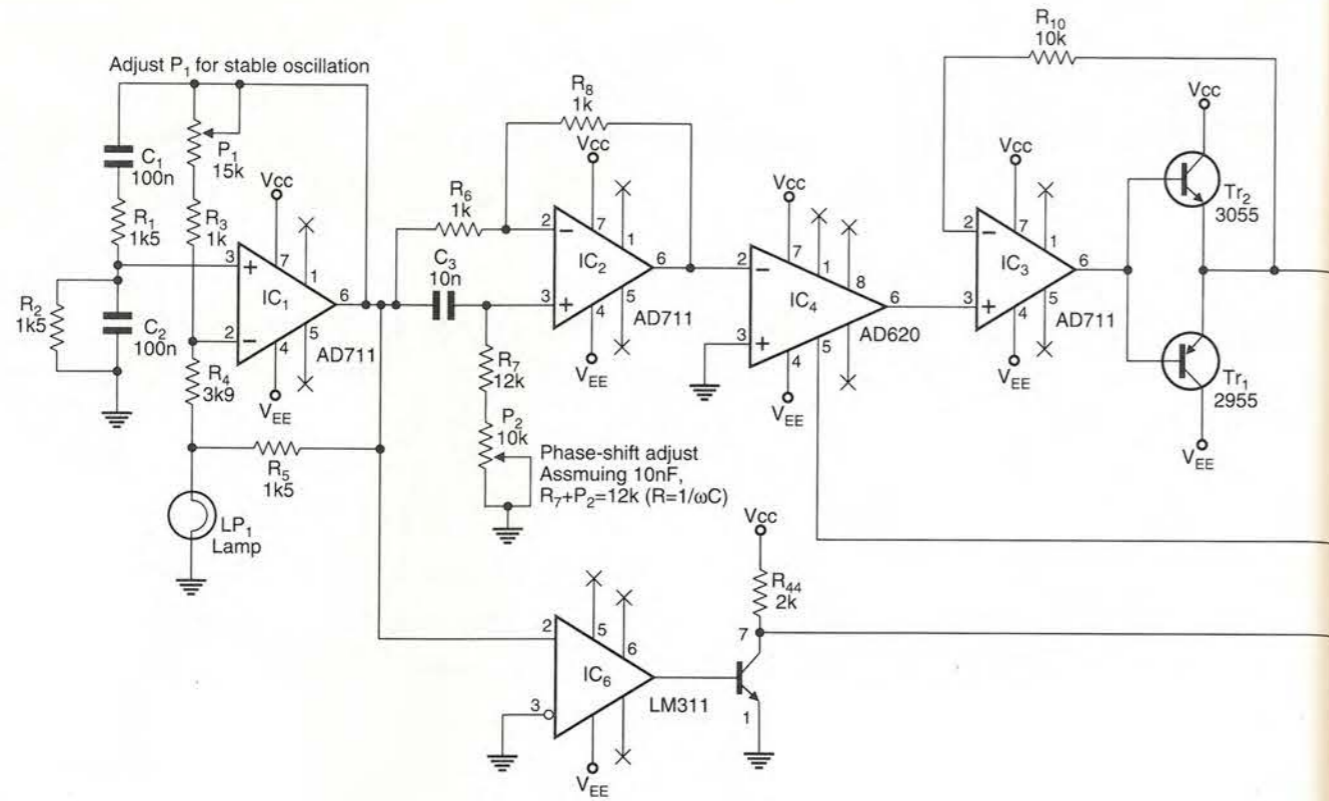
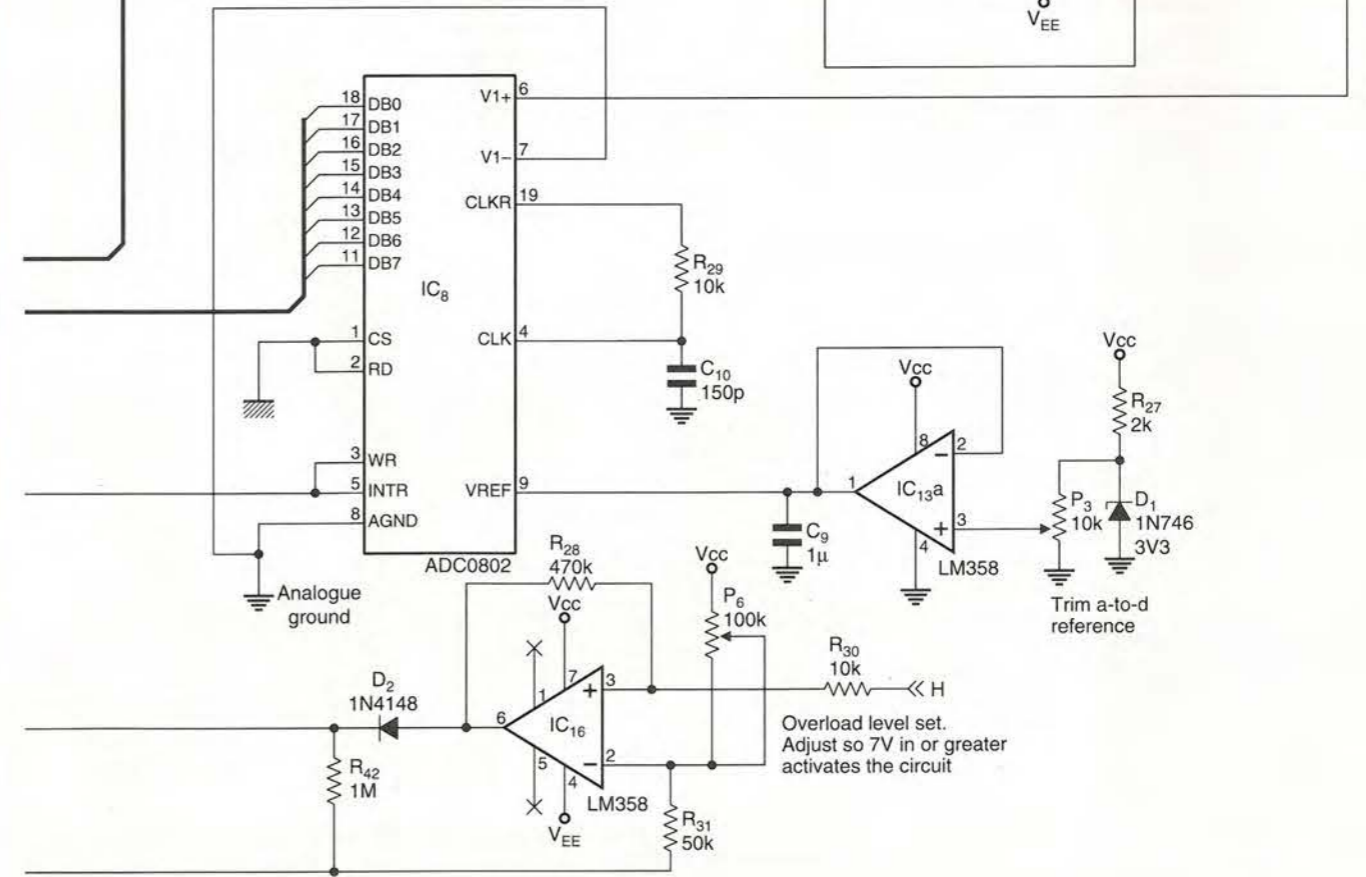


Fig. 2. Complete circuit of the four range inductance meter, with the Wien-bridge oscillator upper left, the switches of the phase-sensitive detector upper right and the microcontroller bottom left. The display is a generic 1620 matrix type with 16-by-2 characters such as the Sanyo C1620S.

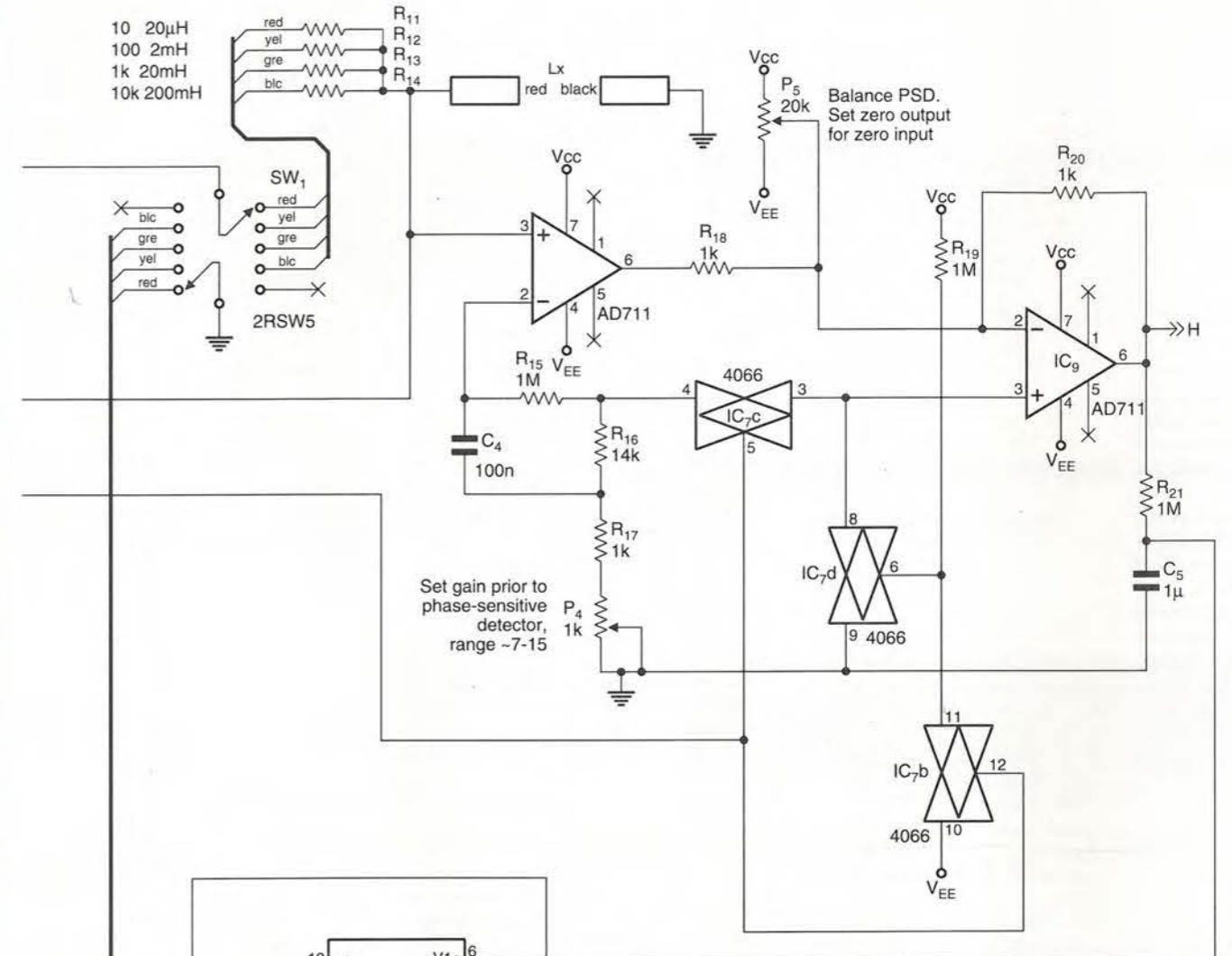

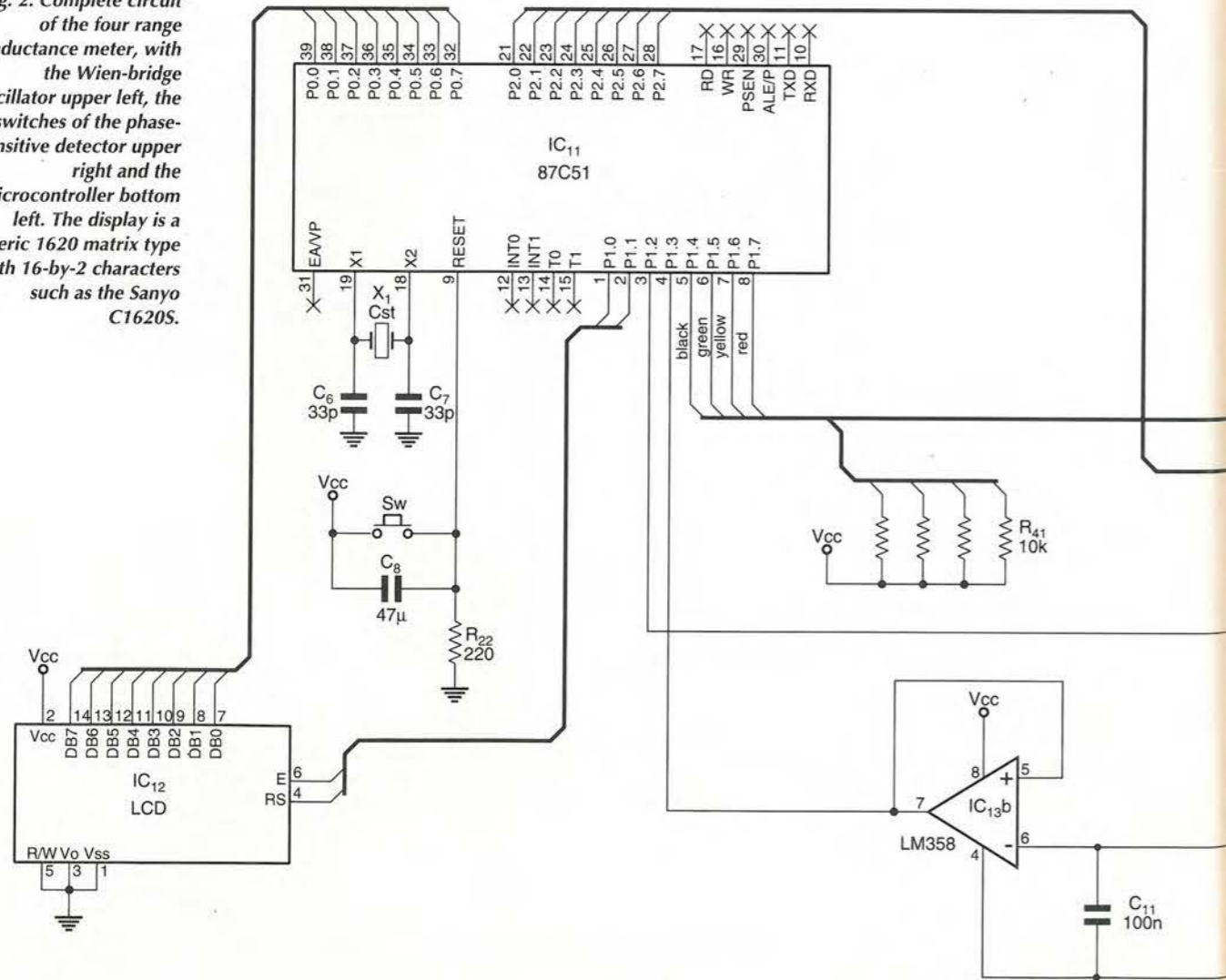

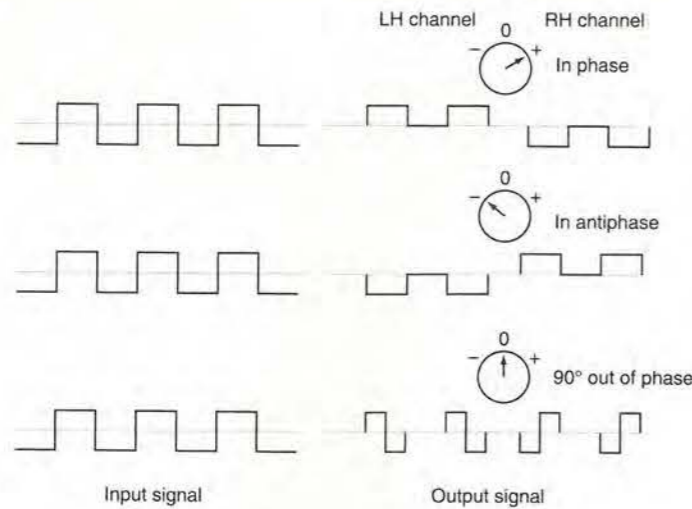


Fig. 3. Phase-sensitive detector concept. Taken from the April 1999 issue, this diagram shows how a switch operated by a reference signal feeds the signal being detected to two RC networks alternately.

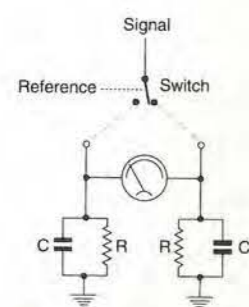


Fig. 4. Using a Sanyo 16-character by 2-line LCD module greatly simplifies the inductance meter.

built around IC<sub>2</sub>, and associated. In practice the overall phase shift will be slightly less than 90° due to the ohmic loss. However, as the reactance should be very much higher than the resistance, the difference will not be great. A phase shift error of as much as 10° will cause an amplitude error of only 1.5%. Modern inductors are most unlikely to introduce any greater error due to the ohmic loss, except for those

specially made for high-loss applications. You can always do a separate measurement on the ohmic loss as discussed later. Op-amp IC<sub>1</sub> and components around it form a Wien bridge oscillator. Such oscillators are very popular in situations such as this, as they are stable and cheap to build. The small light bulb is a non-linear element in the feedback loop used to stabilise the oscillator. Resistance of the bulb increases with heat, i.e. current through it. A crystal-controlled oscillator would be easier to implement than the Wien bridge, albeit not as cheaply. However, the stability of the Wien bridge is perfectly adequate in this application. Comparator IC<sub>6</sub> converts the sine wave produced by the Wien bridge oscillator into a square wave suitable for driving the phase-sensitive detector. This instrument has four manually-selected ranges. Each range is indicated to the microprocessor on a unique i/o pin. Overload indication involves IC<sub>16</sub> and IC<sub>13B</sub> and a separate pin on the

microprocessor. The display is a 16 by 2 alphanumeric LCD display made by Sanyo. Figure 4 details its connections. The microprocessor is an 87C51. It has an on-board EPROM into which the control program is loaded. We provided the 8V V<sub>cc</sub> supply rail using a separate power supply. Power drain is rather high for battery operation. Programming for this instrument is not particularly difficult and only occupies a small amount of memory. The object code is given and the source code in assembler is available from *Electronics World*.

**Enhancements**

Only a small portion of the EPROM in the microprocessor is used, so there's plenty of scope for enhancements. For example, you could add autoranging by monitoring the measurements and then switching in the appropriate range using electronic relays. You would not need to get the gain exactly right in the instrument; it should be possible to provide a scaling factor in software. You could easily make a very accurate instrument by also measuring the ohmic loss, *r*, under software control. This would be done by evaluating the DC voltage across the inductance for a given DC current or *vice-versa*.

If *X* is the apparent inductance value then the true value is given by  $L = X \sin \theta$  with  $\cos^{-1} \theta = r / \omega X$ . Of course you could measure the ohmic loss with a simple voltmeter and then apply the correction.

**In summary**

This instrument allows you to measure a wide range of inductance to a good accuracy without the problem of ohmic loss errors. Extra programming space is available to upgrade the instrument. You could improve accuracy even further by measuring the ohmic loss separately.

**The Stereo Headphone Amplifier Box**

Balanced or unbalanced line inputs to stereo headphone output  
Professional portable units operating from an internal PP3 battery or external mains adaptor



- \*Precision transformerless differential left and right inputs
- \*Wide range of headphone drive impedances
- \*High common mode rejection
- \*Low noise and distortion
- \*Low quiescent power consumption for extended battery life
- \*Extensive RFI protection

**The Balance Box (mic/line amplifier) - The Phantom Power Box - The OneStop** DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphook Hants GU30 7QW  
Information line 01428 751469 Fax 751223  
E-mail contact@confordelec.co.uk  
Web http://www.confordelec.co.uk/catalogue/

CIRCLE NO. 123 ON REPLY CARD

**CVC CHELMER VALVE COMPANY**

*for High Quality Audio Tubes*  
The CVC Premium range offers continuity of supply of high grade audio valves. Based on the best from world-wide sources, processed by us to suit audio applications. Pre-amp types tested/selected for LOW NOISE, HUM and MICROPHONY. Power valves are given controlled BURN-IN to improve stability and to select-out those with weaknesses. MAJOR BRANDS also supplied as available.

A selection of CVC PREMIUM Audio Tubes					
PRE-AMP TUBES	POWER TUBES	POWER TUBES	POWER TUBES	SOCKETS ETC.	
ECC81 5.00	EL34G 7.50	(Continued)	6336A 8.00	B9A (Glass or PCB) 3.00	
ECC82 5.00	EL34 (RESLA) 8.00	6550A 11.00	6550A 11.00	Octal (Ch or PCB) 1.80	
ECC83 5.00	EL34 (large Dia) 8.50	6550WA or WB 13.50	6550WA or WB 13.50	Octal (Ch or PCB) 4.20	
ECC85 6.00	EL84/85 4.70	7581A 11.00	7581A 11.00	4 Pin (for 2AL 300B etc.) 3.30	
ECC88 5.00	EL509/519 13.00	807 9.00	807 9.00	4 Pin (for 2A3 300B etc.) 5.00	
ECF82 5.00	E84L/7189A 6.50	811A 11.00	811A 11.00	4 Pin (for 211 etc.) 11.00	
ECL82 5.00	KT66 9.50	812A 34.00	812A 34.00	4 Pin (for 211 etc.) 15.00	
ECL86 5.00	KT77 12.00	845 30.00	845 30.00	5 Pin (for 6X5) 3.00	
EF85 5.00	KT88 (standard) 12.50	9A5 21.00	9A5 21.00	7 Pin (for 6X4) 4.50	
EF86 10.00	KT88 (gold plated) 21.00	9X4 14.50	9X4 14.50	9 Pin (for EL, 6X6, Ch or PCB) 5.00	
EF87 Gold Pl. 6.80	KT88 (gold plated) 21.00	E280 4.00	E280 4.00	Screening Can 2.00	
E81CC Gold Pl. 8.00	PL509/519 9.00	E281 4.50	E281 4.50	Anode Connector 1.50	
E82 CC Gold Pl. 7.50	2A3 (H or B Pin) 14.50	GZ32 11.00	GZ32 11.00	Anode Connector 1.70	
E83CC Gold Pl. 8.00	2A3 (H or B Pin) 14.50	GZ33 9.50	GZ33 9.50	Retainer (for 6X6 etc.) 2.00	
E88CC Gold Pl. 8.00	211 22.00	GZ34 6.50	GZ34 6.50		
6EU7 6.00	300B 50.00	GZ37 7.50	GZ37 7.50		
6SL7GT 4.50	6C33C-B 27.00	GZ37A 5.00	GZ37A 5.00		
6SN7GT 4.50	6L6GC 6.50	5U4G 5.00	5U4G 5.00		
6922 5.20	6L6WC/6881 8.00	5V4GT 4.50	5V4GT 4.50		
6V6GT 6.50	6V6GT 5.00	5Y3GT 4.50	5Y3GT 4.50		
6080 10.00	6080 11.50	5Z4GT 4.50	5Z4GT 4.50		
7025 6.50	6146B 10.50				

...and a few "Other Brands" (inc. Scarce types).

5AR4/GZ34 MULLARD 20.00	6B4G MATHIEW 27.00	6SN7GT BRIMAR 5.50	13E1 STC 110.00
5R4GY RCA STC 7.00	6BW6 BRIMAR 5.00	12A17WA MULLARD 5.00	805 CTRON 50.00
5U4WG OHTHAM USA 10.00	6BX7 GT SIVANNA 8.50	12AV7 GE SIVANNA 7.75	5842A GE 15.00
5U4GB RCA or GE 12.00	6C7/6F07 SIVANNA 7.50	12AZ7 GE 7.50	680WV TUNGSO 12.50
5Y3WGT SIVANNA 5.00	6CL6 RCA or GE 5.00	12B17A GE or RCA 13.00	6550A GE 22.00
6AS7G RCA or SORRENZ 12.00	6CW6 RCA 11.00	12BY7A GE 9.00	6146B GE 17.00
6ALW6C SIVANNA 3.50	6SL7GT STC 5.50	12E1 STC 12.50	

ASK ABOUT ANY TYPES NOT ON THIS LIST. ALL PRICES IN U.K. POUNDS £.  
Please note carriage extra + VAT (EEC only) - When ordering state if matching required (add £1.00 per tube).  
Payment by CREDIT CARD (ACCESS, VISA, MASTERCARD) or BANKERS' DRAFT, TRANSFER or CHEQUE (UK ONLY).  
FAX or POST your ORDER - We shall send PROFORMA INVOICE if necessary.

Value Amplifiers sound better still fitted with CVC PREMIUM Values!  
Chelmer Valve Company, 130 New London Road, Chelmsford, Essex CM2 0RG, England.  
T 44 (0)1245 355296/265865 Fax: 44 (0)1245 490064

CIRCLE NO. 124 ON REPLY CARD

**Technical support**

Michael Slifkin is in the Department of Electronics at the Jerusalem College of Technology. Alexander Gornstein is a former student at JCT. The authors have opened a web site at: <http://optics.jct.ac.il/~slifkin/nim.htm>. It contains URLs to all the devices used in this instrument. If you want the object code in electronic form, e-mail jackie.love@rbi.co.uk and it will be forwarded to you as text embedded in an e-mail. Please use L meter as the subject heading. If you want the object code on disk, again free of charge, send us a PC formatted 3.5in floppy with a protective self-addressed envelope and enough stamps to allow us to return the disk to you. Post it to the Quadrant House address below. The source code is available on disk for £15, or as an e-mail attachment for £10 fully inclusive. E-mail the above address with your credit card number, expiry date and card-holder address or fax 020 8652 8555 with the details. Alternatively, send your order to L meter, Electronics World Editorial, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

**SPECIAL OFFERS**

**TEKTRONIX 2445A** 4 Channel 150MHz delay sweep, cursors/readout **£750**

**TEKTRONIX 475** Dual Trace 200MHz delay sweep **£400**

**MARCONI 2610 TRUE RMS VOLTMETER** Digital LCD + analogue meter 5Hz - 25MHz + DC autoranging **£195**

**AVO 8 Mk 6 MULTIMETER** In Ever Ready case with leads and batteries **£80**  
Other AVOS from **£50**

**RACAL TRUE RMS VOLTMETERS** 9300 5Hz-20MHz usable to 60MHz 10 volts 316V **£95**  
9300B version **£150**

**GODDWIN GVT427 DUAL CHANNEL AC MILLIVOLTMETER** 10uV 300V in 12 ranges Frequency 10Hz-1MHz Used **£100** Unused **£125**

**SINAD MEASUREMENTS** for only **£60**  
MARCONI 893C AF POWER METER 300watts-30 watts; 20Hz-35KHz; 2.5 Ohm - 20k Ohms  
Marconi 893C unused, boxed **£100**  
Marconi 893B - to 10 watts max. NO SINAD **£30**

**GOULD J3B SINE/SQ OSCILLATOR** 10Hz-1200KHz. Low distortion. Balanced metered output. Attenuator **£75-£125**

**SOLARTRON 7150** DMM 6 1/2 digit. TRUE RMS. High accuracy IEEE **£95-£150**

**HIGH QUALITY RACAL COUNTERS**  
9904 Universal timer counter 50MHz **£50**  
9916 Counter 10Hz-520MHz **£75**  
9918 Counter 10Hz-560MHz. 9 digit. **£50**

**FARNELL AMM255** Automatic Mod Meter AM/FM 1.5MHz-2GHz 3.5 digit LCD Display. Unused **£400**  
Also available: FARNELL AMM2000 Automatic Mod Meter 10Hz-2.4GHz. Unused **£950**  
MARCONI 2305 Mod Meter 500KHz-2GHz from **£750**

**STEWART of READING**  
110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
Telephone: (0118) 9268041 Fax: (0118) 9351696  
Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

CIRCLE NO. 125 ON REPLY CARD

**SPECTRUM ANALYSERS**

H.P. 8562A 1KHz-22GHz	£9000
ADVANTEST R3261A 9KHz-2.6GHz Synthesised	£4000
EATON/ALTECH 757 0.001-22GHz	£2500
TEKTRONIX 492 50KHz-18GHz	£3500
H.P. 8558B with Main frame 100KHz-1500MHz	£1250
H.P. 853A (Dig Frame) with 8559A 100KHz-21GHz	£2750
MARCONI 2382 100Hz-400MHz High Resolution	£2000
B & K 2033R Signal Analyser	£1500
ADVANTEST TR4131 10KHz-3.5GHz	£2750
MARCONI 2370 30Hz-110MHz	from £500
HP141 Systems 8553 1KHz-110MHz	from £500
8554 500KHz-1250MHz	from £750
8555 10MHz-18GHz	from £1000

**UNUSED OSCILLOSCOPES**

TEKTRONIX TDS350 Dual Trace 200MHz 1GS/Sec	£1500
TEKTRONIX TAS485 4 Channel 200MHz etc	£1100
H.P. 54600B Dual Trace 100MHz 20MS/s	£1000
<b>OSCILLOSCOPES</b>	
PHILIPS PM3092 2+2 Ch 200MHz Delay TB etc	£950
PHILIPS PM3082 2+2 Ch 100MHz Delay etc	£800
TEKTRONIX TAS465 Dual Trace 100MHz Delay etc	£800
TEKTRONIX 2465 4 Ch 300MHz Delay Sweep Cursors	£1250
TEKTRONIX 2430 Dual Trace 150MHz 100MS/s Cursors etc	£800
TEKTRONIX 2232 Dual Trace 100MHz 100MS/s Cursors etc	£800
TEKTRONIX 2210 Dual Trace 60MHz 20MS/s Cursors etc	£650
TEKTRONIX 2210 Dual Trace 500MHz 20MS/s	£450
H.P. 54200A Digitising 50MHz 20MS/s	£800

**PHILIPS PM3217** - Very good oscilloscope including 2 probes. Pouch and Front Cover **£250-£300**

**GOULD OS1100** Dual trace, 30MHz delay, very bright. Supplied with manual and 2 probes. **£200**

**THIS IS THE BEST CHEAP SCOPE YOU WILL EVER BUY!!!**

**USED EQUIPMENT - GUARANTEED.** Manuals supplied. This is VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.



# Everything but the sink

Two significant breakthroughs in isolated modular dc-to-dc converters have been made by a relative newcomer in this field. The company, SynQor, has introduced synchronous rectification – increasing efficiency to such an extent that the new converters are the first of their kind to do away with heat sinking. Secondly, planar magnetics have been used, reducing weight and lowering board height.

Derating is another important issue in DC-to-DC converter design. As ambient temperature increases, the amount of power you can get out of a DC-to-DC converter falls. These curves show the new SynQor 40A product against some of its competitors for a 200 linear feet-per-minute air flow.

In the interests of increasing reliability, and to ease the problem of conveying power to electronic equipment in racking, it's common to have regulators on cards distributed throughout the racking system. Each individual regulator is fed by a relatively high voltage, allowing the cross section of power-distributing buses to be reduced.

Distributing the power supply in this way means that heat lost through regulator inefficiency is spread around the cabinet. This is a great advantage relative to having one large central regulator, but it does mean that valuable card space is lost to accommodate the

individual regulators.


There has been little innovation in the design of such regulators over the past few years. Almost all the inefficiency in modern regulators is still caused by the voltage drop of a Schottky diode – evidence that current products are making the most of traditional switching circuitry.

A typical 5V, 30A regulator will have an efficiency of 83%. At full output, it would dissipate just over 25W. Clearly, such a regulator needs some form of heat sink on top of it, increasing the amount of valuable inter-board space needed for the card, its regulator and the regulator's heat sink.

While 5V regulators have been the norm, and alternatives to Schottky diodes have been impracticable, designers have had to tolerate regulators that need additional heat-sinking. But now that supplies lower than 5V are becoming common, the dissipation problem is compounded.

Efficiency of a traditional 3.3V Schottky-diode-based regulator drops to 79% at 30A – an equivalent 1.5V product is only 64% efficient. This fall in efficiency is mainly due to the fact that the diode's voltage drop is becoming a greater proportion of the output voltage.

So when everything else is

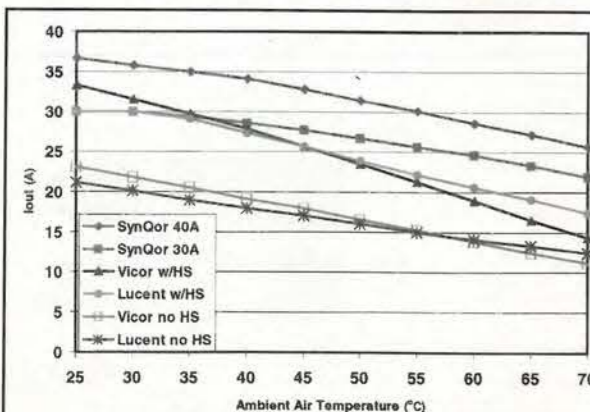

Output	Full load	Conventional converter	New converter	Heat reduction
15V	10A	88%	90%	1.2x
12V	12.5A	86%	90%	1.5x
5V	30A	83%	89%	1.7x
3.3V	30A	79%	89%	2.2x
2.5V	30A	74%	87%	2.4x
2.0V	30A	68%	85%	2.7x
1.5V	30A	62%	83%	3.0x

Reduction in dissipated heat offered by SynQor's DC-to-DC converters over conventional Schottky-diode based converters.


shrinking, the regulator assembly is actually increasing in size.

## So efficient they don't need a heat sink

Now, a new player in the DC-to-DC converter market, SynQor, has developed a range of products that need no heat sinking. Being more efficient, these regulators output more power for a given volume. And needing no potting compound or heat sink, they are significantly lighter. Eliminating the heat sink also removes the unreliability of the thermal interface between the traditional converter and its heat sink.

The company has replaced the traditional Schottky diodes with synchronous rectifiers, which has made a significant impact on efficiency. In addition, planar transformers are being used, offering benefits in both weight and board height. Windings of these transformers are actually pcb tracks, and their ferrite 'core' passes through the pcb, wrapping around heavy copper tracks.

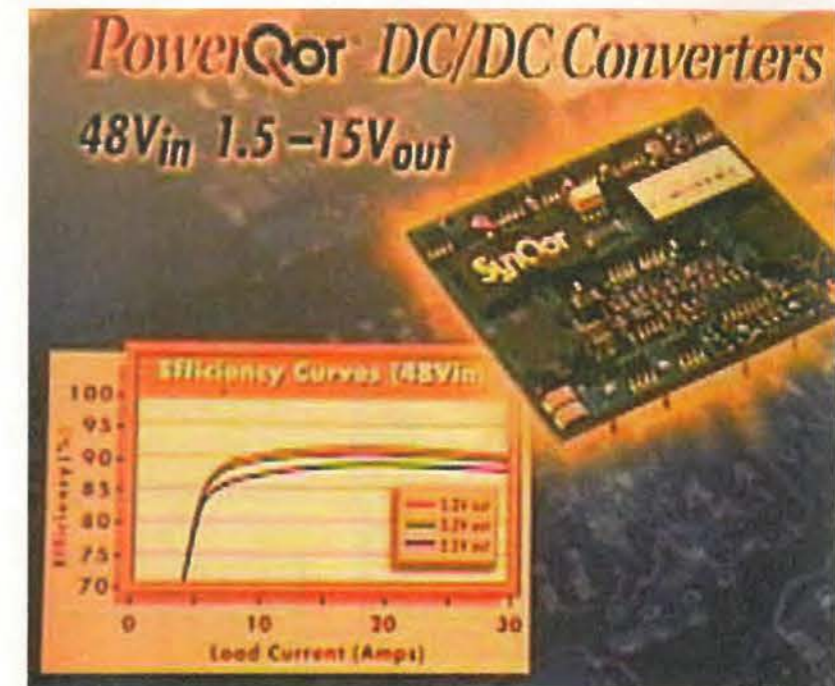These are not the first designs to be based on synchronous rectification, but they are the first to incorporate a patented method of improving rectifier efficiency. The rectifiers in this case are MOSFETs. To achieve a low 'on' resistance, these FETs have to be



large-area types. But large area is synonymous with large gate capacitance.

Normally, driving a high gate capacitance at a few hundred kilohertz would waste considerable power, but SynQor is using a patented method of re-using the gate driving energy.

Resulting efficiency improvements are good at 5V, rising from

83% for a typical conventional converter, to 89% for the new products. But at 1.5V and 30A, the efficiency is 83% against 62% for a conventional converter. Work this out in watts at 30A and you will get an idea of what a difference the efficiency gain makes.

For more information, see [www.synqor.com](http://www.synqor.com)

## See for yourself...


An evaluation kit for these new converters comprising:

- One regulator of any of the available voltages
- An evaluation board
- An evaluation procedure manual
- Carrying case

is available to *Electronics World* readers at a special 17.5% introductory discount price of £125. Simply mention *Electronics World* and this advertisement when ordering. Call SynQor on 01753 860276 or fax 01753 840332 for further ordering details and see [www.synqor.com/synqor/synqor.nsf/EvaluationKitsMain](http://www.synqor.com/synqor/synqor.nsf/EvaluationKitsMain) for more information on the kit.

Voltages available are 2, 2.5, 3.3, 5, 12 and 15V in the 30A series and 1.5, 1.8, 2, 2.5 and 3.3 in the 40A series. The 12-page manual and evaluation board allow you to thoroughly check out the performance of the module and to compare it against what you are currently using.

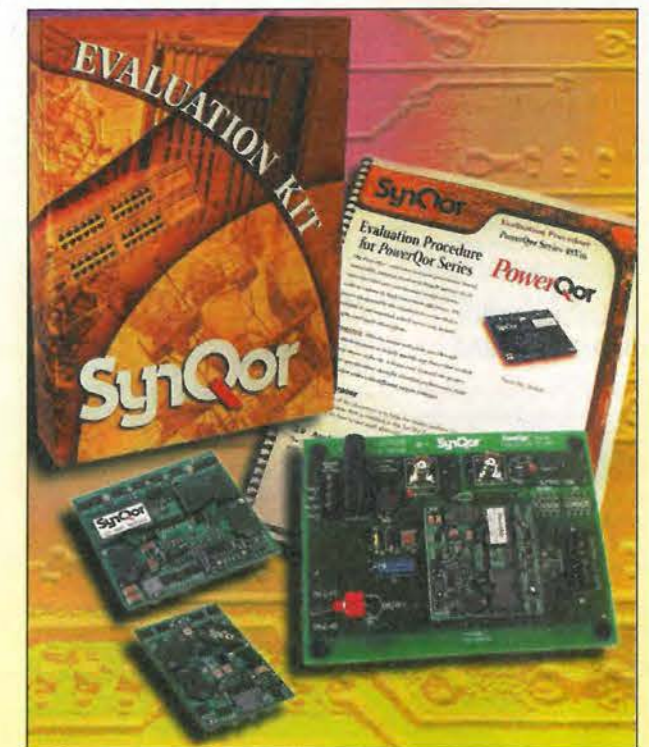The kit is also the basis of an educational tool for anyone wanting to find out more about the characteristics of DC-to-DC converter modules.





# WEB DIRECTIONS

## AQUILA VISION

<http://www.aquila-vision.co.uk>

Aquila Vision specialises in supplying and supporting Embedded Microprocessor Development products from PICs to DSPs. We also stock robotics boards, Linux and general interest CD-ROM's.



## ALCATEL COMPONENTS

<http://www.components@alcatel.de>

## ASHWELL ELECTRONICS

<http://www.ashwell-hq.com>

Ashwell provide technical support for Apex Microtechnology op-amps and DC/DC's; Aeroflex; EMP filtered connectors; M S Kennedy; Mintech obsolescence; NSC Mil/Aero; Teledyne Relays and isocom mil/optocouplers.

## ARCOM

<http://www.arcomcontrols.com/ev/>



A leading international supplier of communication and control technology to industry, Arcom provides leading edge solutions through a comprehensive range of market leading products.

## BROADCASTING COMMUNICATIONS SYSTEMS

[www.broadercasting.co.uk](http://www.broadercasting.co.uk)

WINRADIO now brings you a complete choice in personnel computer controlled radio scanning and reception solutions • Broadcast • Media • Monitoring • Professional Amateur Radio communications

## BEDFORD OPTO TECHNOLOGY LTD

<http://www.bot.co.uk>

Optoelectronic products UK design development manufacture standard and

custom, LED bargraphs, circuit board indicators, stand offs, transmissive/reflective switches, baseface optocouplers tubular and surface mount, pannel mount LED assemblies.

## CONCEPT ELECTRONICS

<http://www.conceptkey.co.uk>

Concept Keyboards are specialists in the design and manufacture of customer specified membrane panels and keyboards, and electronic design. Concept's membrane manufacture is supported by a full electronic production facility to provide a complete turnkey keyboard and electronics service, fully accredited to ISO9001.

## CONTROL SOLUTIONS

[www.controlsolutions.co.uk](http://www.controlsolutions.co.uk)

Data acquisition and control for beginners, hobbyists, and professionals. Perform mathematical and logical operations on data in real time. Email: [info@controlsolutions.co.uk](mailto:info@controlsolutions.co.uk).

## COOKE INTERNATIONAL

<http://www.cooke-int.com>

e-mail: [info@cooke-int.com](mailto:info@cooke-int.com)



Stockists of Quality Used Electronic Test Instruments and Operating & Service Manuals.

## CROWNHILL ASSOCIATES LTD

<http://www.crownhill.co.uk>

Crownhill supply low cost development tools for use with Micro-Controllers and Smart Cards. Products include Smart Card development tools, Smart cards, Micro Development tools and Bespoke Design Services.



## DANIEL MCBREARTY

<http://www.danmcb.demon.co.uk/eng.html>

Experienced engineer based in London, specialist in audio and control systems. Available for design, project engineering or general consultancy. Background of high-quality work.

## EQUINOX TECHNOLOGIES UK LTD

<http://www.equinox-tech.com>



Equinox Technologies UK Ltd., specialise in development tools for the embedded microcontroller market.

## ELECTRONICS WEEKLY HYPERACTIVE


<http://www.electronicweekly.co.uk/>


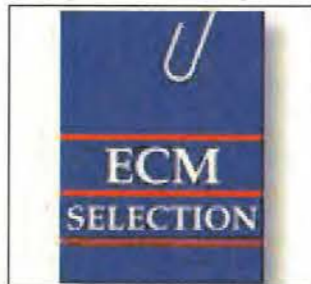
## ECM SELECTION

<http://www.ecmsel.co.uk>

For the pick of the UK's Top High-Tech Software and Hardware career opportunities - from fresh Grad/PhD to Senior Engineer/Manager -- £22,000 - £70,000



## ELECTRONICS PRINCIPLES FREE ONLINE

<http://www.eptsoft.com>

This popular electronics educational title now available to engineers, students and hobbyists absolutely free. A huge 'virtual textbook' of electronics information, from DC to PIC's.

## FELLER UK

<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

## FLASH DESIGNS LTD

<http://www.flash.co.uk>

Flash supply low cost AVR ISP programmers (£39), MINI-ICE starter kits (from £69), Portable Easy-ICE emulators (from £199), ICE Adapters & 'C' compilers for any ATMEL AVR, MCS51, Dallas, Hitachi H8 microcontroller. Download FLASH NEWS now, Watch out for Special Offers'. ARE YOU developing code in a Flash?

## HSPS LTD

<http://dSPACE.dial.pipex.com/hsp/>

FILTER DESIGNER - Advanced analog and digital filter design software for the PC. - Standard and Professional versions. - Free download of Evaluation version.

## LOW POWER RADIO SOLUTIONS

<http://www.lprs.co.uk>

LPRS markets low power radio transmitters, receivers and transceiver modules manufactured by ourselves, Radiometrix, Circuit Designs, RDT and Micrel. Applications for telemetry, video and remote control.

## MATTHEY MICROFILTERS

<http://www.microfilters.net>




30 years experience in the design and manufacture of high quality passive filters and delay lines. Used in Broadcast, Telecommunications, Medical, Multimedia, and Computer industries.
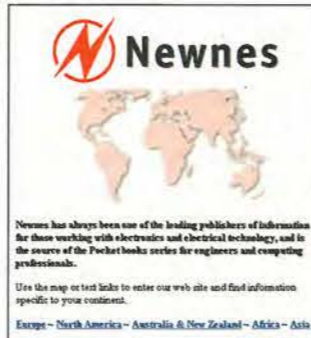
## NEWNES - BOOKS FOR THE ELECTRONICS WORLD

<http://www.newnespress.com>

Over 300 books and information packages for those working with electronics and engineering technology. Visit our site for a free catalogue and downloads



To reserve your web site space contact Pat Bunce

Tel: 020 8652 8339 Fax: 020 8652 3981

To reserve your web site space contact Pat Bunce  
Tel: 020 8652 8339  
Fax: 020 8652 3981

## PCA:PHILIP COLLINS & ASSOCIATES PTY. LTD

<http://www.pca.cc>

PCA manufactures Radphone 2000DX remote control systems for shortwave broadcasters and government agencies wanting worldwide control of communications receivers and transceivers from any tone phone.

## POLY-FLEX CIRCUITS LTD

<http://www.polyflex.com>

Design, manufacture and population of printed polyester flexible circuits, including Flip Chip on Flex providing practical, low cost, reliable solutions for today's small lightweight products.

## QUILLER ELECTRONICS

<http://www.quiller.com>

100+ pages of detailed technical information on Schrack Relays, MEC Switches, Hirose Connections.

## RADIOMETRIX

<http://www.radiometrix.co.uk>

Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use.

## RADIO-TECH LIMITED

<http://www.radio-tech.co.uk>

Radio modules, modems, telemetry, audio transmitters, pagers, antenna, remote controls and much more. All UK designed and manufactured.



## RALFE ELECTRONICS

professional test & measurement  
[www.ralfe-electronics.co.uk](http://www.ralfe-electronics.co.uk)

## RD RESEARCH

<http://www.looking.co.uk/spice>



Analogue and digital SPICE modelling software. Full details available on this site. Available on a 30 day evaluation basis.

## RS COMPONENTS LTD

<http://rswww.com>

The award winning on-line service from RS - 110,000+ products available  
- Technical data library  
- Stock availability check  
- Integrated on-line purchasing  
- Order by 8pm - with you tomorrow.



## SOFTCOPY

<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.

## SESCOM, INC.

<http://www.sescom.com>



SESCOM, INC. is a 30-year manufacturer of audio "problem solvers" and transformers. We also offer easily-fabricated aluminum enclosures for small production runs and prototypes.

## STAFFORDSHIRE WIRELESS COMPANY

<http://www.staffs-wireless.com>

Wireless, communication, test equipment, bought and sold for very competitive prices visit our web site or telephone John on 01899 569928 or 0973 296461.



## SUPRA AUDIO CABLES

<http://www.jenving.se>

Jenving Technology AB is the manufacturer of Supra Audio Cables. OEM productions are also accepted.

## TEMWELL CORPORATION

<http://www.temwell.com.tw>

Manufacturer & Exporter of Heical BPF Filter, 30 Watts BPF Power Filter and Handset/Base Station Duplexers

## THERMOSPEED

<http://www.thermospeed.co.uk>



ThermoSpeed  
The catalogue sales company of the  
MAYCO Group

We offer CE-Test-Shelf Temperature, pressure  
humidity & electrical instrumentation for  
sensing, measurement and control



Temperature and pressure, control and instrumentation. Full on-line purchasing.  
\* Overnight ex-stock delivery  
\* Create your own hotlist  
\* Download datasheets  
\* Full technical support

Continued over page

Put your web address in front of 21 000 electronics enthusiasts and experts. *Electronics World* acknowledges your company's need to promote its web site, which is why we are now dedicating pages in every issue to announce your WEB ADDRESS. This gives other readers the opportunity to look up your company's name, to find your web address and to browse the magazine page to find new sites.

We understand that cost is an important factor, as web sites are an added drain on budgets. But we are sure you will agree that the following rates make all the difference:

**FOR 12 ISSUES:**  
Lineage only will cost £150 for a full year just £12.50 per month.  
This includes your company's name, web address and a 25-word description.  
Lineage with colour screen shot costs £350 for


a full year, which equates to just £29.17 per month.  
This price includes the above mentioned information, plus a 3cm screen shot of your site, which we can produce if required.

To take up this offer or for more information ring:

Pat Bunce on 020 8652 8339  
or fax on 020 8652 3981.  
or e-mail: [pat.bunce@rbi.co.uk](mailto:pat.bunce@rbi.co.uk)

Company name	Web address



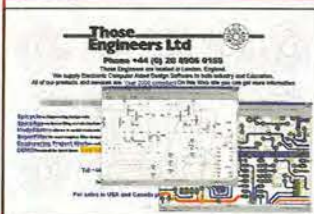

**THOSE ENGINEERS LTD**  
http://www.spiceage.com

Working evaluations of SpiceAge mixed-mode simulator, Spicycle PCB design tools and Superfilter demo (synthesises passive, active, digital filters). Tech support, sales links and price list.

**TEST EQUIPMENT SOLUTIONS**

http://www.TestEquipmentHQ.com  
Quality second user test equipment with full warranty and support. All types of

Specialists in the supply of quality refurbished Test Equipment.  
Phone: +44 (0)1753 596000  
Email: info@TestEquipmentHQ.com

equipment from all leading manufacturers including general purpose, communications and industrial test.

**TRIDENT MICROSYSTEMS LTD**  
http://www.trident-uk.co.uk

Visit the Trident website for details and datasheets on their entire LCD and printer product range. Download data and subscribe for our regularly updated newsletter.

**TOWER HILL TECHNICAL SERVICES**

http://www.towerhillaerials.com  
Everything you need for DIY Satellite & TV aerial installation. The one stop



shop for TV, FM, Satellite, Amateur Radio PMR Aerials, Distribution Equipment, Cable & Accessories.

**TECHNICAL AND SCIENTIFIC SUPPLIES**

http://www.technicalscientific.com

Suppliers of pre-1985 equipment and components.

- Test/Measurement equipment
- Valves and semiconductors
- Transducers and pressure gauges
- Scientific books and catalogues
- Manuals and data sheets

**VANN DRAPER ELECTRONICS LTD**

http://www.vanndraper.co.uk

Test equipment from Grundig, Kenwood, Hitachi, Fluke, Avo, Glassman, Advance in a comprehensive site including oscilloscopes, multimeters, power supplies, generators, counters, soldering, digital tv etc.

To reserve your web site space contact

Pat Bunce  
Tel: 020 8652 8339  
Fax: 020 8652 3981



**VUTRAX PCB DESIGN SOFTWARE**

http://www.vutrax.co.uk

VUTRAX electronic schematic and pcb design system for Windows 95, 98 and NT. Limited Capacity FREE version downloads available, all upgradeable to various customised levels.

**WOOD & DOUGLAS**

http://www.woodanddouglas.co.uk

Wood & Douglas Ltd is the leading independent British designer and manufacturer of quality radio products for International telemetry, data, voice & video wireless communications.

## Letters to the editor

Letters to "Electronics World" Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS  
e-mail jackie.lowe@rbi.co.uk using subject heading 'Letters'.

### TID: RIP?

Over the last thirty years there has been a continuing debate as to what might affect the sound quality of transistor power amplifiers.

In the early seventies, the argument was fired up by Lohstroh and Otala's transient intermodulation distortion (TID) theory<sup>1</sup> but over the last few years this appears to have been slowly falling out of favour.

Self has argued strongly for the Miller capacitor as a means to solve amplifier stability and distortion problems.<sup>2</sup> On the face of it, this seems to be a useful way forward. However, this Miller capacitor causes slew-rate overloading when the input signal exceeds the slew-rate limit.

I thought it useful to determine this limit so that it need not be exceeded. The calculations I have made contained a surprise that does indeed link the amount of feedback to the maximum acceptable input rate of change of voltage as I will now explain.

Consider a typical transistor stage in the diagram on the right. The input differential pair operate at a nominal current of  $i_s$  and the current source supplying them is  $2i_s$ . The voltage-amplifier stage, or VAS as Self calls it, shares any current between the base current,  $i_b$ , and the Miller capacitor current

$i_m$ . The Miller current is proportional to the collector voltage,

$$i_m = i_b + i_m \quad (1)$$

where,

$$i_m = C_m \frac{dV_c}{dt} \quad (2)$$

This Miller-capacitor current would have appeared as a voltage across the emitter resistors of the input transistors, which are usually used to linearise the input stage to reduce distortion (see Self, *op. cit.*). In order to determine the maximum drive to this capacitor to prevent the input stage from hard switching, and thus cause a high level of distortion, it is necessary to consider what the limit might be.

### Limited-slew criterion

I propose that the worst-case limit should be where the input transistors are able to respond to an input, and thus retain control of the amplifier. If the input-pair currents are altered by up to half their DC levels, this would leave a current of a further 50% still available to them. But with such a change this would already be 'large signal' and the distortion levels would be rising. However, it seems to be a reasonable starting point.

In this circumstance,  $i_1$  might be  $1.5i_s$ , while  $i_2=0.5i_s$ . Note that the emitter-base

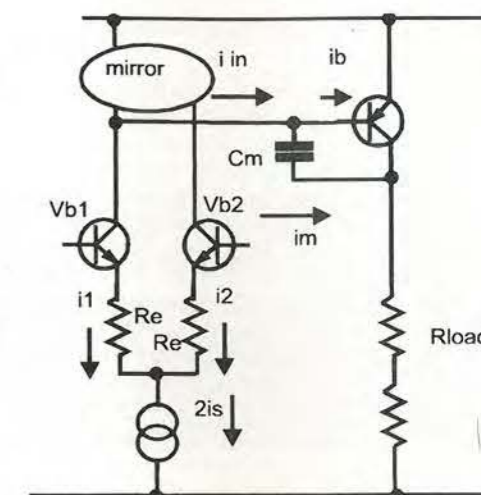


Fig. 1. Input stage of an audio amplifier in which current through each device of the input pair is  $i_s$ .

voltages are quite different, and are,

$$dV_b = V_{th} (\log(1.5) - \log(0.5)) \quad (3)$$

where  $V_{th}$  is the thermal voltage, 25.3mV at 20°C, and the logs are natural. (I prefer the programmer's 'log' rather than the mathematician's 'ln').  $dV_b$  is 27.8mV here.

With rather low values, in my opinion, of 22Ω emitter resistors, as Self originally suggested, there is an additional increase of 22mV where  $i_s=1mA$ . This gives a total margin between the bases of about 50mV. It would be 130mV for 100Ω resistors.

When the output voltage is limited by the slew rate to,

$$\frac{dV_c}{dt} = \frac{i_s}{C_m} \quad (4)$$

where the feedback point ( $V_{b2}$  the base of the second output transistor) rises at a rate of,

$$\frac{dV_{b2}}{dt} = \frac{i_s}{C_m} \alpha \quad (5)$$

where  $\alpha$  is the feedback attenuation factor, assuming that the output stage follows the VAS voltage closely.

If you plot this rising voltage with time, a straight line is observed as shown by (1) in the graph on the next page, where the maximum voltage reached corresponds to the maximum input voltage after the rise time  $t_r$ , as observed at the feedback point.

I said earlier that to achieve this voltage, the input must not exceed the 50mV drive

## ADVERTISE FREE OF CHARGE

Subscribers\* to *Electronics World* can advertise their electronics and electrical equipment completely free of charge

Simply write your ad in the form below, using one word per box, up to a maximum of twenty words.

Remember to include your telephone number as one word.

You must include your latest mailing label with your form.

\* This free offer applies to private subscribers only. Your ad will be placed in the first available issue.

This offer applies to private sales of electrical and electronic equipment only.

Trade advertisers - call Pat Bunce on 020 8652 3620

All adverts will be placed as soon as possible. However, we are unable to guarantee insertion dates. We regret that we are unable to enter into correspondence with readers using this service, we also reserve the right to reject adverts which do not fulfil the terms of this offer.


Please send your completed forms to:

Free Classified Offer: Electronics World, L333, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS



### There's a mouse on my knee

In the article 'Mouse holes' in the May 1999 issue, I mentioned the use of a proprietary pad on the upper leg for working the mouse. Using it there reduces muscular strain.

At the time, although these things were being used in the USA, there was no product available in the UK, so I was unable to nominate a supplier or give a review. Now a firm called NMI in Newcastle-upon-Tyne is making a rather good design that has won an Innovation 99 award. I have tried it out and it seems fine. You have to adapt your technique somewhat, but it certainly relieves the aches and pains of continuous mousing.

Rod Cooper  
Sutton Coldfield  
West Midlands



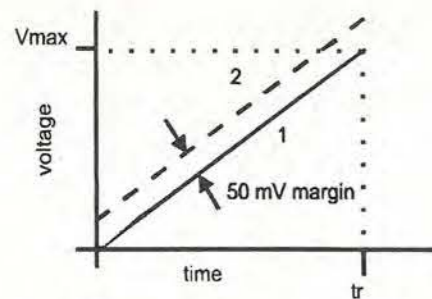


Fig. 2. Voltage curve up to rise time  $t_r$ .

margin, or the currents in the transistors will be in danger of cuffing off. This margin is shown by the dotted line on the graph.

Input voltage,  $V_{b1}$ , can be drawn to drive  $V_{b2}+0.05$  by line (2). This allows the input transition to change very slightly faster than the feedback, but is in essence virtually the same.

For a typical amplifier operating with  $i_c=1\text{mA}$ , a Miller capacitor of 100pF, and 50W 'rms' output, the peak output voltage is 28.3V for 8Ω, the maximum slew rate guideline is  $10\text{V}\cdot\mu\text{s}^{-1}$ .

With a feedback factor of 0.033, i.e. a gain of 30, the input slew limit is  $0.33\text{V}\mu\text{s}^{-1}$ . This corresponds to a frequency of

$$\frac{333 \times 10^3}{2\pi \cdot 0.7} \text{ Hz}$$

or 75kHz, where the input voltage is now a sine wave of 700mV, which has a peak of 1V.

This slew rate can be ensured by including an input filter in series with the input of, say, 10kΩ and 220pF shunt to ground.

If the situation is ever likely to occur where a square wave input of 1V is applied, the input time constant should be the slew limit, requiring the capacitor to be increased to 330pF.

If the input resistors are made much larger, such that the differential margin becomes equal to the maximum input voltage, then the margin is not exceeded even for a square wave, Fig. 3. Here, 1kΩ resistors have been used as these will give a 1V margin at 1mA.

This is the reason why I recommend much larger resistors than Self – even at the expense of reducing the open loop gain and worsening the overall distortion figures. Of course, a different slew-rate criterion could

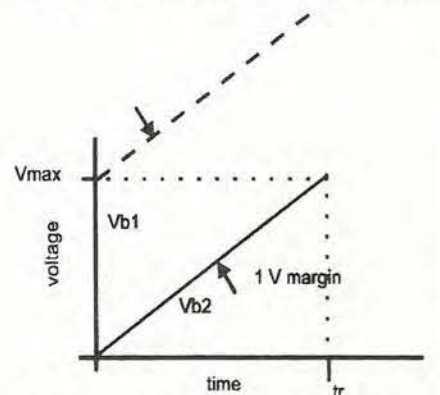


Fig. 3. Input margin for 1kΩ resistors.

be applied other than the 50% change in current, perhaps based on a certain increase in distortion figure.

Now for the surprise. In equation 5, the amplifier feedback attenuation ratio was included. Otala *et al.* (*op. cit.*) conjectured that a high level of feedback may increase transient intermodulation distortion. Equation 5 shows a simple but significant result – that for more feedback, where  $\alpha$  is greater, corresponding to a lower gain, a faster input signal can be tolerated.

Perhaps I was slow to appreciate this point before, because this is really just another way of saying that for more feedback, the bandwidth is greater! This would appear then to agree with Cherry's comments about TID<sup>3</sup>.

The sound of a power amplifier might have been affected by high-speed preamplifiers, which would undoubtedly influence low slew-margin amplifiers. If a simple input filter is used, it might, with the power amplifier limit, have adversely affect the overall frequency response of the system.

The simplest way out of this would be to use a faster amplifier. Another approach might be to use a two or three-order filter, to try to leave more of the upper audio frequencies untouched before the cut-off point.

It is not a new idea to include a low-pass filter on the input of an amplifier to prevent slew-rate limiting, but I hope this has shown a method for determining the optimum.

Alternatively, large input resistors solve the problem, admittedly with some other drawbacks. Perhaps, though, with either approach, we can lay the ghost of TID to rest.

J.N. Ellis  
Tavistock  
Devon

#### References

- Otala, M, 'Transient Intermodulation Distortion In Transistor Audio Power Amplifiers', IEEE transactions, AU-IS, Sept. 1970, pp. 234-239. (See also Lohstroh and Otala, 'Audio Power Amplifier for Ultimate Quality Requirements', IEEE Transactions on Audio and Electroacoustics, AU-21, Dec. 1973, pp. 546-651.)
- Self, D, 'Distortion in Audio Amplifiers,' series, E&WW, August 1993-March 1994
- Cherry, EM, 'Ironing out Distortion', EW+WW, January 1995, pp. 14-20.

#### Free PCB layout tool

A 'lite' version of the Eagle layout tool from Cadsoft is available off the web for free. Its limitation is that it can produce a maximum board size of 4in by 3in, double sided. I've successfully built a board for the 'Five-chip logic analyser' from EW February 1999 using the package.

I printed the layout for both sides on a laser printer and used blue 'iron-on' transfer material to make the board.

I succeeded first time and easily produced line thicknesses down to 0.016in with many tracks passing between IC pads – particularly at the FPGA.

Rob Graham  
Via e-mail

#### Early radar

In the very interesting history article on Blumlein in the March issue of *Electronics World*, mention is made of 'chain-home' radio direction finding, later to be called radar. Apart from the later airborne aircraft interception, or AI, fitted to Beaufighter night fighters, from the earliest days there were 'chain-home low-flying', or CHLF, stations and later the ground-controlled interception, or GCI, version.

Chain-home low flying worked at 200MHz with 25kV on the transmitter valve anodes. The range was up to 20 miles, if the open feeder wire SWR could be reduced to around 1.01:1, but on occasions of temperature inversion, second-trace reception was possible with ships plotted at up to 400 miles.

#### Domestic thermocouples?

Can someone tell me how thermocouples work? From time to time I change our domestic ones, but I do wonder how the minuscule voltage of around 12mV can do the work of opening and holding open a gas valve?

I have asked a couple of professional installers of heating equipment. One said he didn't know the other that it transmitted heat.

Graham Cox  
Bexhill-on-Sea  
West Sussex

*I'm not an expert on this, but the 'thermocouples' you find used to control gas appliances, etc., are not thermoelectric. I've always assumed that they rely on expansion, or state change, of some material within their copper tubing. The only ones I've seen have a plunger that activates an electrical push switch or displaces a mechanical valve. Does anyone know how they work? Are thermocouples ever found in domestic appliances? Ed.*

#### Dangerous protection

On page 776 of the September 1999 issue, the 'Overvoltage load protection' circuit betrays a fundamental and dangerous lack of knowledge of MOSFETs.

Including  $D_1$  in the gate circuit of the MOSFET ostensibly to provide 'protection' against reverse voltage is totally wrong. Firstly, MOSFETs of the type shown are characterised for 20V on the gate. There is no restriction as to polarity – only voltage magnitude – making the diode redundant.

More importantly, the inclusion of the diode ensures that the MOSFET cannot be turned off quickly as the charge cannot be

removed from the gate except via the leakage current of  $D_1$ : this may take hours.

Another point is that in higher voltage circuits, there is nothing to prevent the gate being charged via the drain-gate capacitance to very high voltages – enough to puncture the very thin insulation layer. MOSFET gates must have a resistive gate-source path under all conditions and should be clamped at  $\pm 18\text{V}$ .

Come to think of it, I have never seen anything in your journal that describes in detail the behaviour of switching MOSFETs.

Are you lot totally besotted with ancient linear bipolar circuitry and endless rehashes of low-noise amplifiers and such? How about something that is relevant to modern power electronics?

Dale Butler  
Dir. Research and Development.  
EnerTec Pty Ltd

Not quite sure who "you lot" are Dale, but I would like to say that the topic of power electronics is well covered by power electronics magazines. You're obviously not a long-term reader either, otherwise you would have seen the numerous articles we have carried on power mosfets since their introduction. I am on the look-out though for someone to do an in-depth piece on how the latest generation mosfets perform though. They are quite remarkable relative to the early devices for both linear and switching applications. Ed.

#### Can anyone throw light on this?

I believe I have managed to overcome some of the problems associated with the electrical replay of cylinders, but I would like to achieve better quality replay by the use of a light beam.

To this end, I am looking for a Philco photo-electric reproduction pickup head, model 41429, produced around 1946 for the replay of 78rev/min discs. It was a light-beam device in a 78 pickup head reflecting off the recording groove back into a mirror also in the pickup head. A jewel stylus was used for the purpose of guiding the pickup.

Does any reader have such a pickup lying on a shelf somewhere? Alternatively, is there anyone out there working on light beam replay? Allied to the feed-screw drive on cylinder machiners, such a device could well give surprising results.

Joe Pengelly  
Plymouth

#### On 'defective colour vision'

In Letters, February 2000, R N Soar asks if 'colour-blind' males find it easier to read the time on a (green fluorescent display) video recorder than a (red LED display) clock-radio. Could the answer depend on

the nature of their deficiency?

While it is true that approximately 8% of men suffer from 'defective colour vision' – often incorrectly called 'colour blindness' – these statistics are made up from 2% who suffer from abnormal 'red' perception, and 6% who suffer from abnormal 'green' perception. By comparison only about 0.5% of women are affected by red/green perception problems.

Most colour deficiency is congenital, following the male line. Abnormal 'Blue' perception is very rare, affecting only about 0.01% of the population, both men and women equally.

My son has green perception difficulties, inherited from my father-in-law, but we

reckon that the colour is not the main factor. He doesn't see the 'greenness', only the 'brightness' of the green display. Many of these are blue-green anyway, and he can perceive blue OK.


The over-riding factors that determine clarity are the brightness, contrast and character-shape of the display. Colour does not seem to present him with a major problem either way.

A more telling question would have been 'how many people can manage to programme a video-recorder', which in my experience seems to be linked to 'age' and 'gender' rather than colour perception?

Graham Field  
London E7

## Free capacitor pack\*

\*UK readers only

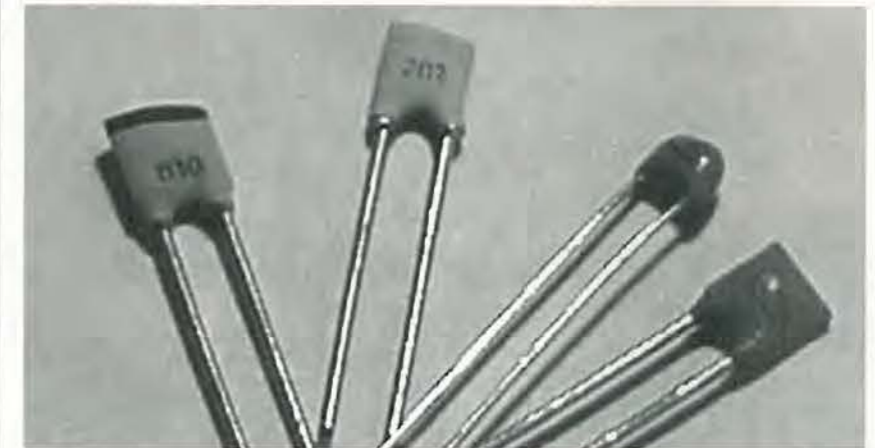

Free with this issue is a pack of four miniature ceramic capacitors with 0.1in lead spacing. Pictured above, their values are 100pF, 2.2nF, 1nF and 10nF from left to right. With a voltage rating of 63V, these devices are suitable for a wide range of filtering to decoupling applications at all frequencies to RF. Three of the capacitors are ceramic disk types while the fourth, the blue 1nF device, is a multilayer type.

Sponsored by:




Semiconductor Supplies International Ltd

Dawson House, 128 - 130 Carshalton Road,  
Sutton, Surrey, England, UK. SM1 4TW  
020-8643 1126 (Sales and Technical Queries)  
Fax: 020-8643 3937 (For International use +4420)  
e-mail: sales@ssi-uk.com Web: ssi-uk.com





### OPERATING & SERVICE MANUALS

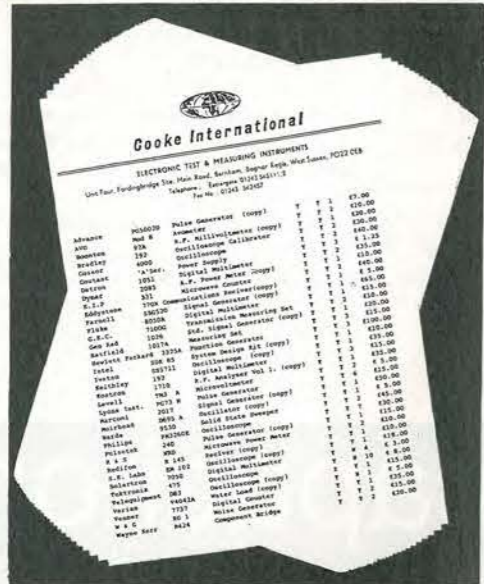

### Cooke International

Unit Four, Fordingbridge Site, Barnham, Bognor Regis, West Sussex, PO22 0HD, U.K.  
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

Web: <http://www.cooke-int.com>  
E-mail: [info@cooke-int.com](mailto:info@cooke-int.com)  
catalogue available

CIRCLE NO.126 ON REPLY CARD



### SUPPLIER OF QUALITY USED TEST INSTRUMENTS



### Cooke International

Unit Four, Fordingbridge Site, Barnham, Bognor Regis, West Sussex, PO22 0HD, U.K.  
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

Web: <http://www.cooke-int.com>  
E-mail: [info@cooke-int.com](mailto:info@cooke-int.com)  
catalogue available

CIRCLE NO.127 ON REPLY CARD

## ADVERTISERS' INDEX

ANCHOR.....	376	MILFORD INSTRUMENTS.....	361
BUTTERWORTH.....	361	PICO.....	401
CHELMER VALVE.....	429	PS CONSULTANTS.....	IBC
CONFORD ELECTRICAL.....	429	RD RESEARCH.....	403
CMS.....	405 & 407	SEETRAX.....	407
COOKE INTERNATIONAL.....	438	SIGHTMAGIC.....	401
CROWNHILL.....	354	STEWART OF READING.....	429
DISPLAY ELECTRONICS.....	398	SURREY ELECTRONICS.....	390
H F INSTRUMENTS.....	405	SWIFT EUROTECH.....	356
ICE TECHNOLOGY.....	OBC	TECHNICAL & GENERAL.....	390
JOHNS RADIO.....	377	TOTAL JOBS.....	416
JPG ELECTRONICS.....	407	TELNET.....	IFC
LABCENTER ELECTRONICS.....	415	TIE PIE.....	359

Contact Pat Bunce on  
0208 652 8339

# ELECTRONICUPDATE

A regular advertising feature  
enabling readers to obtain more  
information on companies'  
products or services.

### DAQ Designer 2000



National Instruments new DAQ Designer™ 2000 is a FREE CD that helps engineers and scientists interactively configure custom measurement systems. DAQ Designer 2000 includes the new capability to recommend real-time data acquisition and motion control hardware and software.

Phone 01635 523545 Fax: 01635 524395  
e-mail [info.uk@ni.com](mailto:info.uk@ni.com) web [www.ni.com/uk](http://www.ni.com/uk)

CIRCLE NO.128 ON REPLY CARD




### Video On-Screen Display Products

LSdesigns supply a range of simple-to-use and cost-effective On-Screen Display devices that superimpose text and graphics directly onto composite video signals. These products offer new possibilities for designers looking for a simple method of displaying data and information in conjunction with a video image.

For the simple solution to your On-Screen Display requirements call LSdesigns today

Tel: 0115 932 4488

CIRCLE NO.129 ON REPLY CARD

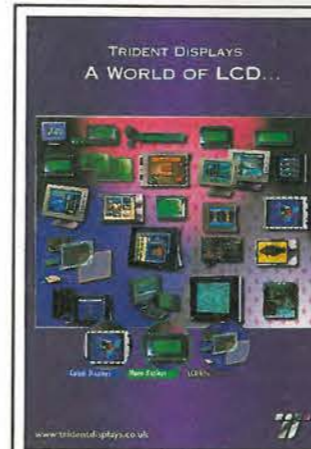

### TRIDENT DISPLAYS A WORLD OF LCD...

The widest range of colour LCDs, LCD monitors and plug and play kits available in the UK, all in one easy to use brochure, is now available FREE!

It includes information on products ranging from 2.9" monitors to 16.1" colour LCD screens, mono/colour STN TFTs and touch screen technology from the world's leading manufacturers.

Phone TRIDENT today for your free copy.

TEL: 01737 780790  
FAX: 01737 771908

OR VISIT OUR WEBSITE:  
[www.tridentdisplays.co.uk](http://www.tridentdisplays.co.uk)

CIRCLE NO.130 ON REPLY CARD



### TOOLWORLD

### Toolworld Ltd

Call now for the TW Catalogue featuring thousands of quality brand name products.

- Adhesives, Aerosols & Cleaning Supplies
- Datacom/Telecom, Cables & Connectors
- Test & Measurement
- Cutting & Polishing Tools
- Toolkits, Cases & Bags

TW Ltd

Tel: 01249 822100  
Fax: 01249 821919

CIRCLE NO.131 ON REPLY CARD



### ELECTRONICS WORLD

INCORPORATING WIRELESS WORLD  
FEBRUARY 2000 £3.55

Adaptable active loudspeaker  
Measure power factor  
Get more from your RF generator  
Quantifying EMC  
Make better notch filters  
Using oscilloscopes  
DSP for hearing aids

ELECTRONICS WORLD is the longest established magazine in the industry, with a history of over 80 years.

The editorial is the most respected in the industry, presenting ideas to innovate and improve products.

For all your advertising needs  
Call Pat 0208 652 8339  
E-mail: [Patbunce@rbi.co.uk](mailto:Patbunce@rbi.co.uk)

CIRCLE NO.132 ON REPLY CARD



### SMART COMMUNICATIONS

### PROGRAMMERS

- Hand held and bench top
- Single socket to 16 gang
- Stand alone and PC based
- DOS and Windows 3.1/95/NT
- Fast algorithms
- Vast range of adaptors:-  
-PLCC, QFP, SOIC,  
-SSOP, BGA, etc...

Tel: +44(0) 181 953 9292  
Email: [sales@smartcom.co.uk](mailto:sales@smartcom.co.uk)  
Web: [www.smartcom.co.uk](http://www.smartcom.co.uk)

CIRCLE NO.133 ON REPLY CARD

**TO ADVERTISE  
YOUR CURRENT  
CATALOGUE /  
CD ROM  
CONTACT  
PAT BUNCE FOR  
DETAILS**

**TEL: 0181 652 8339  
FAX: 0181 652 3981**



As an advertiser you can be certain that your sales message is going to be read by decision-making electronics professionals with the power to purchase your products.

## Service Link

The pre-paid rate for semi-display setting is £17 per single column centimetre (maximum 4cm). Box number £22 extra. All prices plus 17½% VAT. All cheques, postal orders etc to be made payable to Reed Business Information. Advertisements together with remittance should be sent to Electronics World Classified, 12th Floor, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.  
**Fax: 0208 652 3981. Tel: 0208 652 8339**

### ARTICLES WANTED

#### WANTED

Valves & Semiconductors  
 All types e.g. Discrete & IC's  
 Good Rates Paid  
**CHELMER VALVE CO.**  
 130 New London Road, Chelmsford, Essex  
 Tel: 01245 265865 Fax: 01245 490064

#### Rack Enclosures

New and Used most sizes  
 16U to 50U side and rear panels  
 mains distribution 19" Panel mounts  
 optima eurocraft. Prices from £45 +vat  
**M&B Radio**  
 86 Bishopsgate Street Leeds LS1 4BB  
 Tel. 0113 2702114 Fax. 0113 2426881

#### TOP PRICES PAID

For all your valves,  
 tubes, semi conductors  
 and IC's.  
**Langrex Supplies Limited**  
 1 Mayo Road, Croydon, Surrey CR0 2QP  
 TEL: 020 8684 1166 FAX: 020 8684 3056

Please Mention Electronics World  
 When Replying to advertisements

**PRINTED CIRCUIT BOARDS** - Quick Service. Design and Manufacture for Prototypes or Production. Agar Circuits, Unit 5, 308 Albertbridge Road, Belfast BT5 4GX. Tel: 02890 738897. Fax: 02890 731802. E-mail: agar@argonet.co.uk

Need schematics or service manuals, Fluke 887A differential Voltmeter, B&K 2203 sound level meter; your costs reimbursed. Mueller (Germany) (49) 2461 61 4259.

Jog/Shuttle System as fitted to high grade video recorders with plastic wheels. Lee 01705 467700. Garrard Zero 100SB turntable for sale with Shure M55E cartridge and new (genuine Shure) N55E stylus. Tel: 0780 336 6894.

CIRSIM. Circuit simulation program for Windows. Circuits up to 100 nodes. Graphical output. Many examples. £10. Tel: 01753 643384.

### SERVICES

**From Concept To Production** 98 HOUR SERVICE

Electronic design and engineering services for the new millennium.

- Embedded control
- Telecommunication products
- Datacommunication products
- SM PSU and battery management
- Wireless transmission systems
- Audio and Video processing
- DVD control systems
- Internet site and graphics authoring
- PCB design
- Schematic layout and re-drawing
- Technical documentation & translation

Tel/Fax: +44 (0) 1872 223306  
 Email: designer.systems@btinternet.com

see our web site @ <http://designersystems.co-td.net>

**Designer Systems**  
 Microchip Consultant Program Member

#### Total Service

Analogue and digital, mechatronics, EMC, Low voltage and Machineries Directives Compliance, Industrial design, microprocessor, software, PCB layout, machining, sheet metal, ASIC design, draughting, CAD and CAE, technical authoring, model making, Fluid and Thermodynamics, production, consultancy.  
**Cyber Developments Ltd**  
 Tel: 020 8940 1676 Fax: 020 8948 7258  
 E-Mail: papawhisky@zetnet.co.uk

### ARTICLES FOR SALE

#### RF DESIGN SERVICES

All aspects of RF hardware development considered from concept to production.

**WATERBEACH ELECTRONICS**

**TEL: 01223 862550  
 FAX: 01223 440853**

### ARTICLES FOR SALE

**DYNAPERT 318 HR**  
 High speed/high resolution head, fiducial correction, linear bearing tweezers, manual load, 60 feeder positions, 100 x 8mm feeders, 2 x 12mm feeders, 2 x 16mm feeders all late type. Sold and serviced by Dynapert. 5500 hours.  
**£6,900**

**IEMME 750**  
 Reflow oven, PC control (included) four heating zones plus two forced air convection zones, mesh belt. Low hours.  
**£2,900**

The pair, £8,800, both available last week in March - contact Ray Malkowski, Fringe Electronics Ltd., 4 Highfield Road, Clipstone, Mansfield, Notts NG21 9ER.  
**Tel: 01623 643802  
 Fax: 01623 625407**

Please Mention Electronics World  
 When Replying to advertisements

#### POWER SUPPLY DESIGN

Switched Mode PSU  
 Power Factor Correction  
*designed to your specification*  
**Tel/Fax: 01243 842520  
 e-mail: eugen\_kus@cix.co.uk  
 Lomond Electronic Services**

#### D.S.G. SPEDITION LIMITED

In co-operation with our partner in Belgium ECU TRANS Antwerp we offer daily services between Brentwood and Antwerp opening up  
**EAST EUROPE, BALTIC STATES, GERMANY**  
 For further information please contact  
**TERRY MURPHY or JOHN OVERLAND**  
 Tel: 01277 812337  
 Fax: 01277 812359  
 Email: DSGSPED@aol.com

As an advertiser you can be certain that your advertisement is going to be read by **DECISION-MAKING ELECTRONIC PROFESSIONALS** with the **POWER TO PURCHASE** your products.

**Why not let Electronics World help you?**

Call Pat Bunce  
**Tel: 020 8652 8339  
 Fax: 020 8652 3981  
 E-mail: patbunce@rbi.co.uk**

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD

**READER INFORMATION SERVICE**

For more information about any of the products or services in this issue of **ELECTRONICS WORLD**, simply ring the relevant enquiry number.  
 Enquiry numbers may be found at the bottom of each individual advertisement.

101	102	103	104	105	106	107	108	109	110	111
112	113	114	115	116	117	118	119	120	121	122
123	124	125	126	127	128	129	130	131	132	133
134	135	136	137	138	139	140	141	142	143	144
145	146	147	148	149	150					

					500	501	502	503	504	
505	506	507	508	509	510	511	512	513	514	515
516	517	518	519	520	521	522	523	524	525	526
527	528	529	530	531	532	533	534	535	536	537
538	539	540	541	542	543	544	545	546	547	548
549	550	551	552	553	554	555	556	557	558	559
560	561	562	563	564	565	566	567	568	569	570
571	572	573	574	575	576	577	578	579	580	581
582	583	584	585	586	587	588	589	590	591	592
593	594	595	596	597	598	599	600			

Name \_\_\_\_\_  
 Job title \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_  
 Company Address \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_  
 Telephone \_\_\_\_\_ MAY 2000

Only tick here if you do not wish to receive direct marketing promotions from other companies.

# Subscribe today!

Guarantee your own personal copy each month

## Save on a 2 year subscription

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD

## Newsagent order form

Pass this order form to your newsagent to ensure you don't miss the next issue of **EW**.

To .....  
 (name of Newsagent)

Please reserve me the June issue of *Electronics World* and continue to order every month's issue until further notice

Name.....

Address.....

Thank you

# Subscribe today!

Guarantee your own personal copy each month

## Save on a 2 year subscription

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD



Postage will be paid by licensee

Do not affix postage stamps if posted in Gt Britain, Channel Islands, N Ireland or the Isle of Man.

Business Reply Service  
Licence No. CY711

**ELECTRONICS WORLD**  
Reader Information Service  
Reed Business Information  
Oakfield House  
Perrymount Road  
Haywards Heath  
Sussex RH16 3BR

SEE OVER!

211

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD

**SUBSCRIPTION CARD**

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ \_\_\_\_\_ made payable to **Reed Business Information**  
Please charge my Mastercard/Visa/Amex account

Mastercard/Visa/Amex account

With £ \_\_\_\_\_ Expiry Date \_\_\_\_\_

Signature \_\_\_\_\_

Name \_\_\_\_\_

Job Title \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Tel: \_\_\_\_\_ Country \_\_\_\_\_

**SUBSCRIPTION RATES**

UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
<b>Airmail</b>	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

Post to:  
**ELECTRONICS WORLD**  
P.O. Box 302  
Haywards Heath,  
West Sussex RH16 3DH UK.

**CREDIT CARD HOTLINE**  
Tel: +44 01444 445566  
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing-promotion from other companies

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD

**SUBSCRIPTION CARD**

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ \_\_\_\_\_ made payable to **Reed Business Information**  
Please charge my Mastercard/Visa/Amex account

Mastercard/Visa/Amex account

With £ \_\_\_\_\_ Expiry Date \_\_\_\_\_

Signature \_\_\_\_\_

Name \_\_\_\_\_

Job Title \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Tel: \_\_\_\_\_ Country \_\_\_\_\_

**SUBSCRIPTION RATES**

UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
<b>Airmail</b>	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

Post to:  
**ELECTRONICS WORLD**  
P.O. Box 302  
Haywards Heath,  
West Sussex RH16 3DH UK.

**CREDIT CARD HOTLINE**  
Tel: +44 01444 445566  
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing-promotion from other companies

# WINRADIO

**TAKING THE EUROPEAN RADIO MARKET BY STORM**

TAKE A LOOK AT WINRADIO'S DIGITAL SUITE SOFTWARE (AWARDED 5 STARS BY WRTH)

1. WEFAX / HF Fax
2. Packet Radio for HF and VHF
3. Aircraft Addressing and Reporting System (ACARS)
4. Audio Oscilloscope, real time Spectrum Analyzer with calibration cursors
5. Squelch-controlled AF Recorder
6. DTMF, CTSS decode and analyse

The DSP applet provided with the WR3100i spectrum monitor ISA card (£995+VAT) allows continuous control of audio bandwidth and other signal conditioning functions.

**ONLY £81.07 inc vat**  
(requires SoundBlaster 16 compatible sound card)



**WINADIO™ PC RECEIVERS**

Available as either an internal ISA card that slips inside your PC, or as an external (portable) unit. WINRADIO combines the power of your PC with the very latest, and greatest, synthesised receivers.

**YOU CAN USE WINRADIO™ SCANNING PC COMMUNICATION RECEIVERS FOR:**

Broadcast, media monitoring, professional & amateur radio communications, scanning, spot frequency, whole spectrum monitoring, instrumentation surveillance and recording.

If you're after the ultimate receiver-in-a-PC with full DSP then smile and say, "Hello" to the new **WR31000i-DSP** with its hardware for real-time recording, signal conditioning and decoding applications. It's all you need.

**NEW EXTERNAL MODELS**

**EXTERNAL WINRADIO™**  
We are now able to offer you a complete range of stand-alone WINRADIO comms systems:

- **WR1000e - £359 inc vat**
- **WR1500e - £429 inc vat**
- **WR3100e - £1169 inc vat**

Each stand-alone unit connects to your PC through either the basic RS232, or through an optional PCMCIA adapter (for high speed control).

The units are powered through either your existing 12v supply, or through an (entirely optional) NiMH rechargeable 12v battery pack.

"It's software is excellent.. more versatile and less idiosyncratic than that of the Icom IC-PCR1000"  
**WRTH 1999 Review**

"Five stars for its mechanical design"  
**WRTH 1999 Review**

"Most Innovative Receiver"  
**WRTH 1998 Awards**



**Model Name/Number**

**Construction of internals**  
**Construction of externals**  
**Frequency range**  
**Modes**  
**Tuning step size**  
**IF bandwidths**

**Receiver type**  
**Scanning speed**  
**Audio output on card**  
**Max on one motherboard**  
**Dynamic range**  
**IF shift (passband tuning)**  
**DSP in hardware**  
**IRQ required**  
**Spectrum Scope**  
**Visitune**  
**Published software API**  
**Internal ISA cards**  
**External units**

	<b>WR-1000</b>	<b>WR-1500</b>	<b>WR-3100</b>
<b>Construction of internals</b>	WR-1000i/WR-1500i-3100i-DSP- Internal full length ISA cards		
<b>Construction of externals</b>	WR-1000e/WR-1500e - 3100e - external RS232/PCMCIA (optional)		
<b>Frequency range</b>	0.5-1300 MHz	0.15-1500 MHz	0.15-1500 MHz
<b>Modes</b>	AM,SSB/CW,FM-N,FM-W	AM,LSB,USB,CW,FM-N,FM-W	AM,LSB,USB,CW,FM-N,FM-W
<b>Tuning step size</b>	100 Hz (5 Hz BFO)	100 Hz (1 Hz for SSB and CW)	100 Hz (1 Hz for SSB and CW)
<b>IF bandwidths</b>	6 kHz (AM/SSB), 17 kHz (FM-N), 230 kHz (W)	2.5 kHz(SSB/CW), 9 kHz (AM) 17 kHz (FM-N), 230 kHz (W)	2.5 kHz(SSB/CW), 9 kHz (AM) 17 kHz (FM-N), 230 kHz (W)
<b>Receiver type</b>	PLL-based triple-conv. superhet		
<b>Scanning speed</b>	10 ch/sec (AM), 50 ch/sec (FM)		
<b>Audio output on card</b>	200mW	200mW	200mW
<b>Max on one motherboard</b>	8 cards	8 cards	3-8 cards (pse ask)
<b>Dynamic range</b>	65 dB	65 dB	85dB
<b>IF shift (passband tuning)</b>	no	±2 kHz	±2 kHz
<b>DSP in hardware</b>	no - use optional DS software		YES (ISA card ONLY)
<b>IRQ required</b>	no	no	yes (for ISA card)
<b>Spectrum Scope</b>	yes	yes	yes
<b>Visitune</b>	yes	yes	yes
<b>Published software API</b>	yes	yes	yes (also DSP)
<b>Internal ISA cards</b>	£299 inc vat	£369 inc vat	£1169.13 inc
<b>External units</b>	£359 inc vat	£429 inc vat	£1169.13 inc (hardware DSP only internal)

**PCMCIA Adapter (external):** £69.00 inc when bought with 'e' series unit (otherwise: £99 inc)  
**PPS NiMH 12v Battery Pack and Charger:** £99 inc when purchased with 'e' series unit (otherwise: £139 inc)  
**The WINRADIO Digital Suite:** £74.99 inc when purchased with a WINRADIO receiver (otherwise: £81.05 inc)

To receive your completely free (no obligation) info pack and WINRADIO software emulation demo disk all you have to do is get on the internet and go to our website at <http://www.broadercasting.com>. If you don't yet have easy access to the internet then by all means feel free to telephone us or send a fax. Please send all your enquiries to: [info@broadercasting.com](mailto:info@broadercasting.com) or Telephone: 0800 0746 263 or +44 (0)1245 348000 - Fax: +44 (0)1245 287057  
Enformatica Limited, Unit B, Chelford Court, Robjohns Road, Chelmsford, Essex, CM1 3AG, United Kingdom

E&OE WINRADIO and Visitune are trademarks of WINRADIO Communications - copyright Broadercasting Communications Systems



# For development or production...

A range of truly portable, Universal and EPROM/Flash programmers for every need

- Support for all types of devices including 8 and 16-bit memory, up to 128Mbit, PLDs, CPLDs, and over 300 microcontrollers
- Uses the parallel port of any PC or laptop
- Program and verify low voltage devices down to 1.8V
- Low cost package adapters available for PLCC, PSOP, TSOP, QFP, SDIP, SOIC and BGA
- No additional modules or adapters required for any DIP device
- Compatible with DOS, Windows® 95/98, Windows® NT
- Powerful and comprehensive software interface is easy to use
- Uses PSU/Recharger supplied, or batteries for real portability
- Includes Chiptester for TTL/CMOS, DRAM and SRAM devices
- Optional EPROM/RAM emulators also available

Model	Supports	Price
EPMaster LV48	48-pin support for EPROM, EEPROM, Flash & Serial PROM	£295
Speedmaster LV48	As EPMaster LV48, plus BPROMs, PALs, GALs, CPLDs and 8748/51 microcontrollers	£495
Micromaster LV48	As Speedmaster LV48, plus over 300 microcontrollers including 87C48/51/196, PICs, AVR's, 89Cxxxx, S16, MC7057/11, SAB-Cxxx, TMS320/370, Z86, COP etc... FULLY UNIVERSAL	£695
LV48 Portable	40-pin version of Micromaster LV48 + LCD & keypad	£995



## ...the best programmers are here...

The new Matrix Programming System offers the most complete, flexible gang programmer you will ever need for production applications at an extremely competitive price from £1,995

- Two levels of device support: Memory only, or Universal support for memory devices up to 128Mbit, PLDs, CPLDs and over 300 Microcontrollers
- 4 or 8 independent programming sites per box
- Daisy-chaining allows up to 48 centrally controlled sites
- Very high throughput (program/verify time in seconds): 28F400 = 4/2.5, 28F160B3 = 18/12, 28F640J5 = 155/60
- Low cost passive socket modules give support for DIP, PLCC, PSOP, TSOP, QFP etc.
- Modules are not device specific giving major savings in cost of ownership
- True low voltage support down to 1.8V, plus marginal verification
- Intelligent auto-sensing of sockets eliminates need to continually access keyboard
- Powerful and comprehensive software, with easy-to-use interface
- Manufacturer approved algorithms for accurate programming and maximum yield
- Full on-board diagnostics
- Compatible with Windows® 95/98 and Windows® NT
- Universal input power supply - 90-260V, 50/60Hz

All ICE Technology programmers come with lifetime FREE software updates† and technical support, 12 month warranty and 30-day money-back guarantee. For complete Device Support lists, FREE software updates, Demo software and full product information, just visit our website at [www.icetech.com](http://www.icetech.com)

# ...and here, [www.icetech.com](http://www.icetech.com)

ICE Technology Ltd Penistone Court, Sheffield Road, Penistone, Sheffield. S36 6HP. UK  
tel: +44 (0)1226 767404 • fax: +44 (0)1226 370434 • email: [sales@icetech.com](mailto:sales@icetech.com)

ICE Technology Inc 5370 Gulf of Mexico Drive, Suite 204B, Longboat Key, FL 34228. USA  
tel: 1 (941) 387 8166 • fax: 1 (941) 387 9305 • email: [icetechusa@icetech.com](mailto:icetechusa@icetech.com)

**ORDER NOW VIA OUR CREDIT CARD HOTLINE : +44 (0) 1226 767404  
ALL PRODUCTS IN STOCK**

† Custom software and enhanced priority device support is also available for all programmer platforms. All prices are exclusive of carriage and VAT. All trademarks are recognised as belonging to their respective owners.

CIRCLE NO. 103 ON REPLY CARD

