

Unique reader offer; universal programmer – 15% discount

ELECTRONICS WORLD



INCORPORATING WIRELESS WORLD

A REED BUSINESS PUBLICATION SOR DISTRIBUTION

JULY 2000 £2.65

Big brother technology

Adjustable PLL

Variable-gain
circuits

Tini Java

Windows
2000 review

EEPROM
programmer


Circuit ideas:

Phase noise meter

Log sweep generator

Low-power mains SMPS

Drive for valve amps

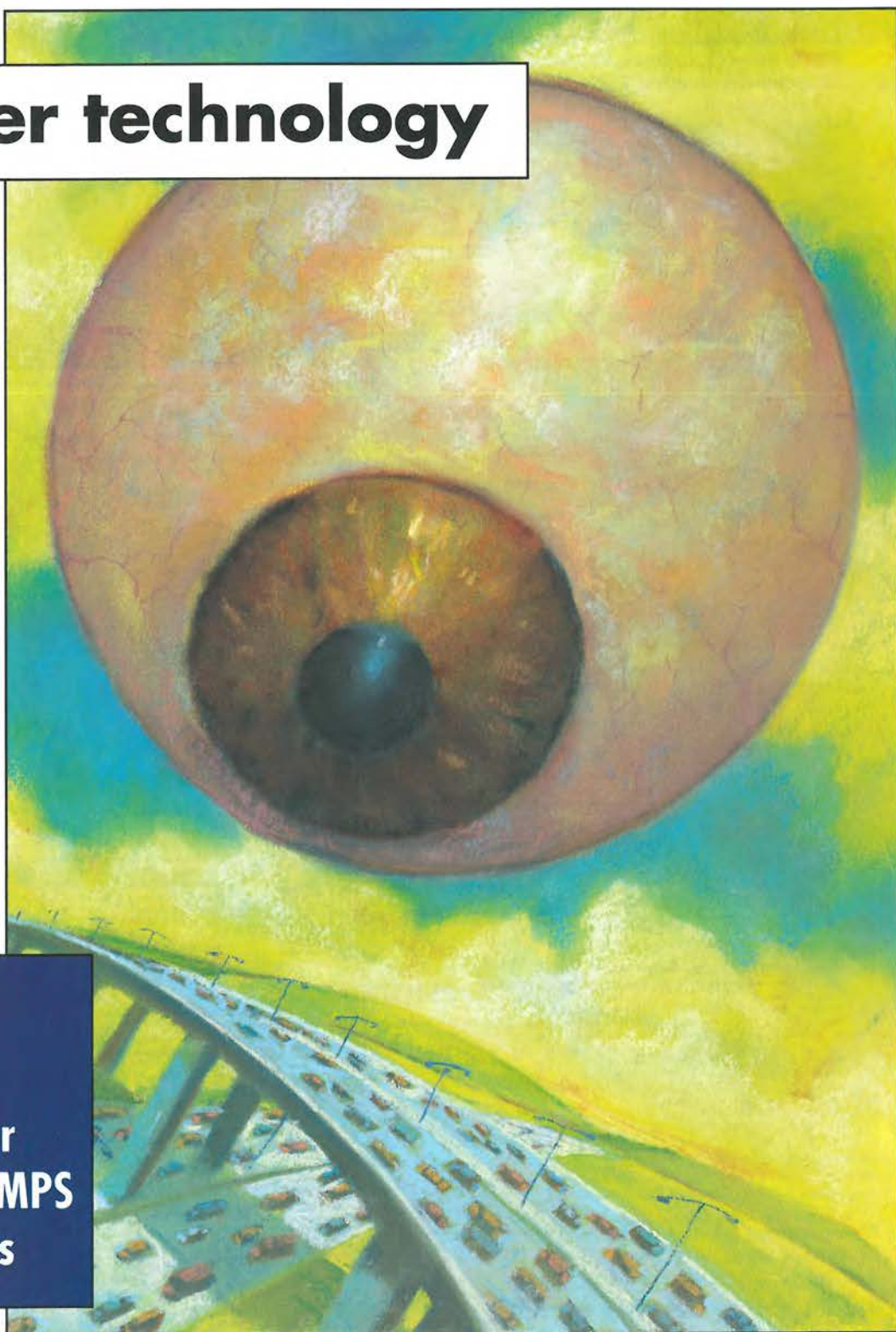

Telnet

Tel: 02476 650702

Hewlett Packard	
8642A - high performance R/F synthesiser (0-1.1050MHz)	£4750
3335A - synthesiser (200Hz-81MHz)	£2400
Hewlett Packard	
436A power meter and sensor (various)	from £750
437B power meter and sensor (various)	from £1100
Hewlett Packard	
8753A network analyser (3GHz)	from £2500
8753B network analyser (3GHz)	from £3250
'S' parameter test sets 85046A and 85047A available at	£2000 & £3000
Wandel & Goltermann	
SPECIAL OFFER	
PCM-4 PCM Channel measurement set (various options available)	from £5500
Marconi 2305 - modulation meter	£999
Marconi 6310 - programmable sweep generator (2 to 20GHz) - new	£3250
Hewlett Packard	
5342A - microwave frequency counter (500MHz-18GHz) ops 1 & 3	£700
5370B - universal time interval counter	£1500

OSCILLOSCOPES	
Gould 4068 150MHz 4 channel DSO	£1500
Hewlett Packard 54201A - 300MHz Digitizing	£1250
Hewlett Packard 54600A - 100MHz - 2 channel	£750
Hitachi V152/V212/V222/V302B/V302F/V353F/V550B/V650F	from £1125
Hitachi VI 100A - 100MHz - 4 channel	£900
Intron 2020 - 20MHz. Dual channel D.S.O. (new)	£450
Iwatsu SS 5710/SS 5702 -	from £125
Kikusui COS 5100 - 100MHz - Dual channel	£350
Leeroy 9450A - 300MHz/400 MS/s D.S.O. 2 channel	£2250
Meguro MISO 1270A - 20MHz - D.S.O. (new)	£450
Philips PM3094 - 200MHz - 4 channel	£1750
Philips 3295A - 400MHz - Dual channel	£1600
Philips PM3392 - 200MHz-200MS/s - 4 channel	£1995
Tektronix 465 - 100MHz - Dual channel	£350
Tektronix 464/466 - 100MHz - (with AN. storage)	£350
Tektronix 475/475A - 200MHz/250MHz -	from £450
Tektronix 468 - 100MHz - D.S.O.	£650
Tektronix 2213/2215 - 60MHz - Dual channel	£350
Tektronix 2220 - 60MHz - Dual channel D.S.O	£1250
Tektronix 2235 - 100MHz - Dual channel	£600
Tektronix 2221 - 60MHz - Dual channel D.S.O	£1250
Tektronix 2245A - 100MHz - 4 channel	£900
Tektronix 2440 - 300MHz/500 MS/s D.S.O.	£2950
Tektronix 2445A - 150MHz - 4 channel	£1250
Tektronix 2445 - 150MHz - 4 channel + DMM	£1200
Tektronix TAS 475 - 100MHz - 4 channel	£995
Tektronix 7000 Series (100MHz to 500MHz)	from £2000
Tektronix 7104 - 1GHz Real Time	£2500
Tektronix 2462/2465A/2465B - 300MHz/350MHz 4 channel	from £1250
Tektronix 2430/2430A - Digital storage - 150MHz	from £1250
Tektronix 2467B - 400MHz - 4 channel high writing speed	£4750
Tektronix TDS 320 100MHz 2 channel	£850
Tektronix TDS 540 500MHz 4 channel	£4500
Tektronix 544A 500MHz 4 channel	£4950

SPECTRUM ANALYSERS	
Ando AC 8211 - 1.7GHz	£1500
Avcom PSA-65A - 2 to 1000MHz	£850
Anritsu MS 2663A - 9KHz - 8.1GHz	£7000
Anritsu MS 62B - 50Hz to 1700MHz	£1450
Anritsu MS 610B 10KHz - 2GHz - as new	£3500
Anritsu MS 710F - 100KHz - 23GHz	£5250
Advantest/TAKEDA RIKEN - 4132 - 100KHz - 1000MHz	£1500
Hewlett Packard 3562A Dual channel dynamic signal analyser 64µHz - 100KHz	£5500
Hewlett Packard 8505A - 1.3GHz - Network Analyser	£1995
Hewlett Packard 8756A/8757A Scalar Network Analyser	from £1000
Hewlett Packard 853A Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£2750
Hewlett Packard 182T Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£2250
Hewlett Packard 8568B - 100Hz - 1500MHz	£5250
Hewlett Packard 8567A - 100Hz - 1500MHz	£3995
Hewlett Packard 8754A - Network Analyser 4MHz-1300MHz	£1500
Hewlett Packard 8591E 9KHz-1.8GHz	£4250
Hewlett Packard 8594E 9KHz-2.9GHz	£6,750
Hewlett Packard 3561A Dynamic signal analyser	£3,995
Hewlett Packard 35660A Dynamic signal analyser	£3250
IFR A7550 - 10KHz-1GHz - Portable	£1950
Meguro - MSA 4901 - 30MHz - Spec. Analyser	£700
Meguro - MSA 4912 - 1 MHz - 1GHz Spec. Analyser	£995
Tektronix 2712 9KHz-1.8GHz (with tracking generator and video monitor mode)	£5500

Quality second-user test & measurement equipment

NEW PHONE CODE FOR COVENTRY 02476

Radio Communications Test Sets

Marconi 2955	£2000
Marconi 2958/2960	£2250
Anritsu MS555A2	£1200
Hewlett Packard 8922B (GSM)	£6950
Schlumberger Stabilock 4031	£3995
Schlumberger Stabilock 4040	£1500
Racal 6111 (GSM)	£1750
Racal 6115 (GSM)	£3995
Rhode & Schwarz CMTA 94 (GSM)	£5950
IFR 1200S	£2995



Fax 02476 650 773

Wandel & Goltermann TSA-1 system analyser (100Hz-180MHz)	£2750
Wiltron 6409 - 10-2000MHz R/F Analyser	£1750

MISCELLANEOUS

Eaton 2075-2A - Noise Gain Analyser	at £2750
Fluke 5100A/5100B/5200A - Calibration Units (various available)	from £1000
Fluke 2620 Data Buckets	£500
Fluke 8842A - Digital Multimeter	£800
Hewlett Packard 339A Distortion measuring set	£1200
Hewlett Packard 435A + 435B Power meters	from £100
Hewlett Packard 778D Dual-Directional Couplers	£650
Hewlett Packard 3488A - Switch/Control unit	£475
Hewlett Packard 3784A - Digital Transmission Analyser	£4500
Hewlett Packard 3785A - Jitter Generator & Receiver	£1250
Hewlett Packard 5343A - Frequency counter 26.5GHz	£2000
Hewlett Packard 5385A - 1 GHz Frequency counter	£650
Hewlett Packard 6033A - Autoranging System PSU (20v-30a)	£750
Hewlett Packard 6622A - Dual O/P system p.s.u.	£1250
Hewlett Packard 6623A - Triple o/p system p.s.u.	£1300
Hewlett Packard 6624A - Quad Output Power Supply	£2000
Hewlett Packard 6632A - System Power Supply (20v-5A)	£800
Hewlett Packard 6652A - 20V-25A System PSU	£750
Hewlett Packard 8112A - 50MHz Pulse Generator	£2250
Hewlett Packard 8350B - Sweep Generator Mainframe	£2000
Hewlett Packard 8656A Synthesised signal generator	£850
Hewlett Packard 8656B Synthesised signal generator	£1450
Hewlett Packard 8660D - Synth'd Sig. Gen (10 KHz-2600MHz)	£3250
Hewlett Packard 8901B - Modulation Analyser	£2750
Hewlett Packard 8903A - B and E - Distortion Analyser	from £1250
Hewlett Packard 16500A - B - Logic Analyser Mainframes	from £1000
Hewlett Packard 16500C - Logic Analyser Mainframe	£3250
Hewlett Packard 16501A/B & C - Logic Analyser System Expander Frame from	£2000
Hewlett Packard 37900D - Signalling test set	£3750
Hewlett Packard 75000 VXI Bus Controllers	£POA
Hewlett Packard 4193A - Vector Impedence Meter	£4750
Hewlett Packard 5350B - 20Hz Frequency Counter	£1950
Hewlett Packard 8657B - 100KHz-2060 MHz Sig Gen	£3995
Hewlett Packard 8657D - XX DQPSK Sig Gen	£4500
Hewlett Packard 8130A - 300 MHz high speed pulse generator	£5250
Hewlett Packard 8116A - 50MHz Pulse/Function generator	£2250
Hewlett Packard 1660A-136 channel Logic Analyser	£3995
Keytek MZ-15/EC Minizap ESD Simulator (15kv - hand held)	£1750
Marconi 1066B - Demultiplexer & Frame Alignment Monitor (140MBIT to 64KBIT)	NEW
Marconi 2610 True RMS Voltmeter	£550
Marconi 6950/6960/6960B Power Meters & Sensors	from £400
Philips 5515 - TN - Colour TV pattern generator	£1400
Philips PM 5193 - 50MHz Function generator	£1500
Leader 3216 Signal generator 100KHz - 140MHz - AM/FM/CW with built in FM stereo modulator (as new) a snap at	£795
Racal 1992 - 1.3GHz Frequency Counter	£500
Rohde & Schwarz SMY-01 Signal Generator (9KHz-1040MHz)	£2250
Rohde & Schwarz NRV dual channel power meter & NAV Z2 Sensor	£1250
Systrom Donner 6030 - 26.5GHz Microwave Freq Counter	£1995
Tektronix ASG100 - Audio Signal Generator	£750
Wayne Kerr 3245 - Precision Inductance Analyser	£1995
Wiltron 6747A-20 - 10MHz-20GHz - Swept Frequency Synthesiser	£4950

CONTENTS

513 COMMENT

High-tech pretenders

515 NEWS

- Industry warned on environmental policy
- Video-link data tapping
- Auction for broadband wireless licences
- Mobile licence costs - who pays the bill?
- Electronics engineers in big demand
- Mobile phone health risks
- Tool eliminates chip noise error
- Trainee engineers jam military satellite

520 BEHIND BIG BROTHER

Never before has the British public been monitored so closely - or so willingly. Unblinking eyes now scan the trunk roads and city centres of Britain but with differing aims and using different technologies. **Andrew Emmerson** takes a closer look at who's zooming whom.

524 E-PROPHECY

Will the revolution in communications enhance all our lives? Not necessarily. **Melanie Reynolds** explains how it



could lead to a breakdown in society.

526 BEGINNERS' CORNER

Ian Hickman's circuit for beginners this month is suitable for those with little or no prior experience of constructing and trouble-shooting hardware.

531 TINI JAVA

Java expert **Les Hughes** has been experimenting with a tiny controller designed for Internet connection. Although only \$50, this controller is a complete computer with Internet, network and serial i/o capabilities, giving it huge potential for remote i/o and telemetry applications.

536 CIRCUIT IDEAS

- Low-power mains SMPS
- Phase-noise meter
- Solid-state drive circuit for valves
- Log-frequency sweep generator

542 GET THE MOST FROM YOUR SCOPE

Leslie Green presents an overview of useful oscilloscope features. He also highlights areas where errors can occur in this final article describing how to use your oscilloscope to the full.

549 NEW PRODUCTS

New product outlines, edited by **Richard Wilson**

560 SPEAKERS' CORNER

John Watkinson explains the importance of a loudspeaker's off-axis response

562 PROGRAMMING EPROMS

If you are still using UV-erasable EPROMs, this programmer should save you an inordinate amount of time. Designed to interface with anything from a 386 PC upwards, **Guo-yin Xu's** parallel port programmer handles popular electrically-erasable PROMs ranging from the 2804 to 28256.



Illustration: Jamel Akib



Unique reader offer - 15% discount on a range of programmers for programming anything from PICs to serial eeproms - page 571.

566 VARIABLE-GAIN CIRCUITS

Cyril Bateman has been using the internet to see what he could find on variable gain circuits, including those featuring in Dolby-B, companders and automatic gain and level controllers.

574 WINDOWS 2000

Rod Cooper investigates Windows 2000 from the CAD user's viewpoint. He's found that this new NT-based operating system offers major benefits, but it will mean new hardware and software for many users.

578 ADJUSTABLE PLL FOR RECEIVERS


Darren Heywood's 46 to 76MHz phase-locked loop module is tuned by simply turning a ten-turn potentiometer. It was originally designed to form the master oscillator of a short-wave receiver, but is easily adapted for other applications.

582 WEB DIRECTIONS

Useful web addresses for everyone involved in electronics.

586 LETTERS

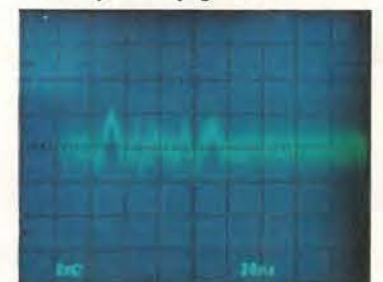
New mobile phone health risk, fuel-starved diesels, RF initiative, Class-T...



Is this a signal, or random noise? Find out how to tell the difference on page 542.



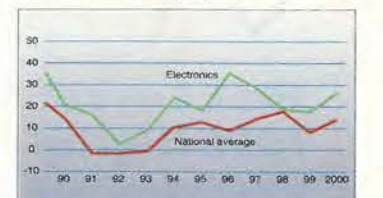Java on a stick. This tiny Java controller with networking and Internet capability costs just \$50. **Les Hughes** describes how to use it on page 531.



Electronics engineers are in demand again, with a third of electronics companies looking to recruit in the second quarter of this year. This, and much more news on pages 515-518.

All equipment is used - with 30 days guarantee and 90 days in some cases

Add carriage and VAT to all goods.

Telnet, 8 Cavans Way, Binley Industrial Estate, Coventry CV3 2SF.

CIRCLE NO. 101 ON REPLY CARD


Tel: 02476 650 702

Fax: 02476 650 773

Packed with new features:

- Uses the latest **xspice** engine for guaranteed accurate mixed mode simulation
- Parameterised ac sweep
- Monte carlo analyses
- Parameterised transient sweep
- New **xspice** simulations
- New noise and distortion analyses
- Improved features for processing plot families as units
- New menu items to show local maxima, minima, and zero crossings **and much more!**

Not just a pretty interface...

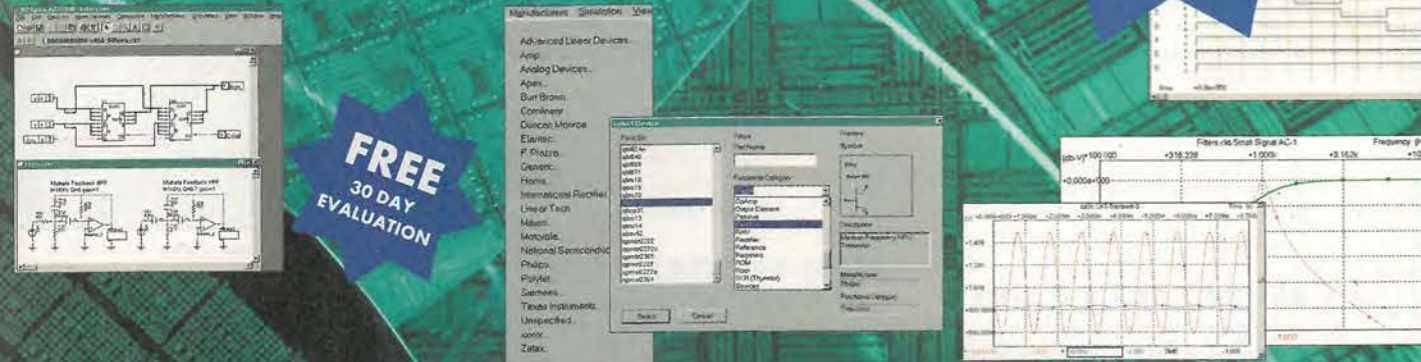

**FREE
30 DAY
EVALUATION**

...Accurate results that can be relied on



RD Research, Research House, Norwich Road, Eastgate, Norwich NR10 4HA
 Tel: 01603 872331 Email: rd.research@paston.co.uk www.looking.co.uk/spice
 *Please add £5.00 postage and packing. *applies to users of B² Spice & B² Logic.
 All trademarks acknowledged.



CIRCLE NO. 104 ON REPLY CARD

**ONLY
£199 ex VAT* -
UPGRADES £99**†**
No hidden extras.
All libraries
included.

High-tech pretenders

The so-called 'New Economy' has been having a bad time lately with over-greedy backers and bankers pushing their luck too far, and eroding the credibility of the money men behind these ventures.

One of the backers of two, recent, ill-fated dot.com IPOs, was Intel. The company backed both the Dutch WorldOnline and the UK's lastminute.com public offerings. Its PR initiatives had helped create lastminute's high public profile in the months preceding the launch.

Both offerings fell below their initial offer price losing the small investors money - though the original backers profited greatly.

The chairman of World Online sold most of her shares before the IPO even occurred, and US investment bankers Goldman Sachs who managed the launch were warned by Japan's Ministry of Finance that its record in the WorldOnline and other launches had made it consider debaring the bank from advising on Japanese government privatisations.

Suddenly the authorities woke up to the fact that the dot.com boom could get out of hand and bring down the whole house of cards. To most of us it was difficult to take seriously the valuations put by banks, stockbrokers and investors on dot.com companies. Now the credibility of the financial sector is being questioned by the authorities.

The same thing is happening with the credibility of the founders of dot.com companies. At one time we were encouraged to think that dot.com companies were started by sparky young people with nothing except a 'good idea': the truth is often very far from that. Dot.com founders are not the innocent young techies operating from a garage of an earlier generation but sharp-eyed marketing men looking for a kill.

Venture capital - once something to be jealously hoarded by high-tech start-up companies for innovative product development - tends to be spent by dot.coms mostly on publicity rather than on developing a service or a product.

Some of the dot.com companies are spending on publicity at the rate of £1m a month - the money coming from venture capitalists wanting to make a quick killing through an early public offering on the stock market.

Now there is a more realistic attitude emerging but the hangover from the dot.com frenzy is affecting the whole of the high technology

industry. That's because, very often, dot.coms are regarded as high-tech by newspapers, analysts and television programmes - even though they may be purveying cooking recipes. That means the sharp swings of their share prices can affect the whole high-tech sector.

For instance, some of this year's fall of the US NASDAQ high technology stock exchange - from over 5000 in March to under 3400 by mid-May - is attributable to the excessive expectations generated by the dot.coms. It was then dissipated by the reality of collapsing share prices and even, in some cases, scandal.

It seems very hard on real technology companies to have their shares hit by a general disillusionment with 'high-tech' brought on by some lack-lustre performance from the so-called dot.com companies. Most of these dot.commers have nothing to do with high technology at all.

For instance lastminute.com is basically a travel agency with some add-on shopping opportunities. Internet-based activities like job agencies or even Internet service providers are not high-tech companies; they simply rely on the technology in order to distribute their product.

You wouldn't say Harrods is in the transportation business because it uses vans to deliver its goods to customers would you?

Real high-tech companies are those that develop and sell high-tech products: semiconductor companies, computer firms, networking companies, software companies, manufacturers of printers, mobile phones, scanners, camcorders, smart missiles, radars and the like.

Anyone making the broadband switches, high-speed optical fibre transmission network systems like dense-wavelength division multiplexers, or making the terminals and appliances that hang off the network, is facing a bright future. But these real high-tech companies don't want their shares jerked around by association with commercially unproven dot.com companies purveying dubiously useful services over the Internet.

While real engineers may be entering a golden age - able to make money on a scale which earlier generations never dreamed of - they face the threat of being devalued and tarnished by the dot.com community

David Manners

EDITOR

Martin Eccles
020 8652 3614

CONSULTANTS

Ian Hickman
Philip Darrington
Frank Ogden

EDITORIAL ADMINISTRATION

Jackie Lowe
020 8652 3614

EDITORIAL E-MAILS

jackie.lowe@rbi.co.uk

GROUP SALES EXECUTIVE

Pat Bunce
020 8652 8339

ADVERTISEMENT E-MAILS

pat.bunce@rbi.co.uk

ADVERTISING PRODUCTION

020 8652 8339

PUBLISHER

Mick Elliott

EDITORIAL FAX

020 8652 8111

CLASSIFIED FAX

020 8652 8938

NEWSTRADE ENQUIRIES

020 7907 7777

ISSN 0959-8332

For a full listing of
RBI magazines:
<http://www.reedbusiness.com>



SUBSCRIPTION HOTLINE

Tel (0) 1444 475662
Fax (0) 1444 445447

SUBSCRIPTION QUERIES

rbp.subscriptions@rbi.co.uk
Tel (0) 1444 445566
Fax (0) 1444 445447

Electronics World is published monthly. By post, current issue £2.65, back issues (if available) £3.00. Orders, payments and general correspondence to **L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**. Tlx: 892984 REED BP G. Cheques should be made payable to Reed Business Information Ltd **Newstrade**: Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108. **Subscriptions**: Quadrant Subscription Services, Oakfield House Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year UK £36.00 2 years £58.00 3 years £72.00. Europe/Eu 1 year £51.00 2 years £82.00 3 years £103.00. ROW 1 year £61.00 2 years £98.00 3 years £123

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel: (212) 679 8888 Fax: (212) 679 9455

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

Printed by Polestar (Colchester) Ltd, **Filmsetting by** JJ Typographics Ltd, Unit 4 Baron Court, Chandlers Way, Southend-on-Sea, Essex SS2 5SE.

© Reed Business Information Ltd 1997 ISSN 0959 8332



WWW.PCB-POOL.COM

Prototype PCBs
from your usual manufacturer for a
fraction of the cost

1 Eurocard as / pm
+ TOOLING
+ PHOTOPLOTS
+ V.A.T.
= **£49**


FREE Layout Software
FREE Digital-Multimeter
FREE PHONE 0800 389 8560



+353 (0)61 701170
FAX 701164

KELLY'S

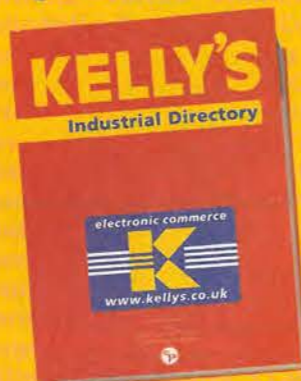For 200 years the
definitive source of UK
products & services



www.kellys.co.uk

CALL NOW FOR FURTHER INFORMATION
FREE PHONE 0800 521393

CIRCLE NO. 123 ON REPLY CARD

CIRCLE NO. 105 ON REPLY CARD

Number One Systems

From
£97

Professional PCB Layout for Windows at Computer Store Prices!!

Easy-PC For Windows

Version 3.0 of this outstanding product is the latest evolution of one of the most popular affordable CAD systems available. With powerful new features and a true Windows graphical user interface, it is also one of the easiest to learn and use.

With full manufacturing outputs using Gerber, Windows printers, N.C. Drill and pen plotters it is one of the most complete systems for the casual to the professional user.

Run multisheet Schematics, PCB layouts and library manager all at the same time in the same interface. Switching between each is simply case of selecting the window with the mouse without running a new program.

Now with our new autorouter option.

Runs under Windows 95/98™ and NT™



Available Now

Number One Systems

Call 01684 773662 or Fax 01684 773664

Email info@numberone.com

For a free demo disk, visit our web site www.numberone.com

Number One Systems, Oak Lane, Bredon, Tewkesbury, Glos, GL20 7LR, UK

CIRCLE NO.106 ON REPLY CARD

WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES (using a video capture card)



"Liesegang diav" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use.....£91.91 + vat = £108.00

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye).....£37.00 + vat = £43.48

30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole.....£35.00 + vat = £41.13

40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses.....£32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed iris

VSL1220F 12mm F1.6 12x15 degrees viewing angle.....£15.97 + vat = £18.76

VSL4022F 4mm F1.22 63x47 degrees viewing angle.....£17.65 + vat = £20.74

VSL6022F 6mm F1.22 42x32 degrees viewing angle.....£19.05 + vat = £22.38

VSL8020F 8mm F1.22 32x24 degrees viewing angle.....£19.90 + vat = £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30x24 degrees viewing angle.....£26.43 + vat = £31.06

VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle.....£77.45 + vat = £91.00

1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat 1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily.....£7.46 + vat = £8.77

Please add 1.66 + vat = £1.95 postage & packing per order

JPG ELECTRONICS

276-278 Chatsworth Road, Chesterfield, S40 2BH.
Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch
Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

CIRCLE NO.107 ON REPLY CARD

Test & Measurement Instruments

The NEW HF-08 Analog to Serial Converter



- ✓ 8 bit resolution
- ✓ Windows and DOS software available DVM, Scope, Spectrum, Logging
- ✓ 7 ranges: +1.25V to +5.0V, -2.5V and ±2.5V
- ✓ Crystal controlled timing for accurate DSP
- ✓ Simple to interface to your own software
- ✓ Low Cost - just £69.33 incl vat

12 bit module coming soon ...

RF
Instruments
EMC
Equipment

HF
Instruments

Data Logging
& Acquisition

Phone: 01420 590000
e-mail: sales@hf-inst.co.uk

Metered bench power supplies
Up to 60V and 6A
Prices from £127 inc. VAT



Handy DMM / Scope
Counter/Timer
TTL Sig. Gen.
£199 inc. VAT



Visit our Web Site for full details:

www.hf-inst.co.uk

CIRCLE NO.108 ON REPLY CARD

UPDATE

Industry warned on environmental policy

The electronics and IT industries have been warned that ignoring their environmental responsibility could have a serious impact on long term growth.

"Environmental responsibility is increasingly recognised as one of the key factors sustaining long-term growth," said Dr Belinda Howell, director of Business in the Environment (BiE).

BiE, the business campaign for environmental responsibility, only received a response from six out of the 28 IT and electronics companies invited to participate in its 'Index of

Corporate Environmental Engagement.' These were Racal Electronics, Marconi, STMicroelectronics, Fujitsu, IBM and Sema Group.

The survey assesses performance in five areas: energy, transport, global warming emissions, waste and water consumption.

Set-top box manufacturer Pace Micro Technology was one of the companies which did not participate.

When questioned, a spokeswoman said she was unaware of the survey but Pace definitely had an environmental policy. "It's something

we're very, very aware of," said the spokeswoman. "We have some things to be proud of as far as handling the environment is concerned."

Chip design firm ARM also did not participate because it felt the survey was geared towards manufacturing whereas it is an intellectual property company.

"We try to make sure our facilities operate in an energy efficient manner," said John Cornish, ARM's director of product marketing. "We don't regard ourselves as being exceptional but we try to be good citizens where we operate."

Protection against video-link data tapping could become mandatory

Companies handling personal information over video links may have to protect against data path tapping, according to Basingstoke-based videocommunications company AuDeo Systems. This could affect those discussing matters including health, government, defence and legal issues.

"The 1998 Data Protection Act coming into force in March has placed the issue of data security at the top of the business agenda," said AuDeo in a statement.

"Videoconferencing comes under the act, which stipulates that businesses handling personal data must take appropriate technical and organisational measures to prevent

hacking and data loss through system crashes."

AuDeo is predicting a large growth in the used of video-meeting technology. "As the costs of such technology reduce, videoconferencing products can be used daily throughout any organisation," said Kevin Wilson, MD of AuDeo.

The statement was made at the launch of a secure videoconferencing system, claimed to be the first, which has come out of a deal between AuDeo and security specialist Biodata Information Technology.

The system is based on Biodata's BabylonMETA encryption units and is claimed to be able to secure ISDN lines against tapping.

Government prepares to auction broadband wireless licences


An auction of the airwaves for broadband fixed wireless access services will follow the success of the £22bn auction for 3rd generation (3G) mobile phone licences.

The government will auction the spectrum at 28GHz in September for services which will allow fast Internet and multimedia access via radio links.

Three licences will be awarded in each coverage area which will be defined in May. Each licence will contain a forward and return channel to send and receive data.

At the time of writing the 3G auction had raised £22bn for the government although it is doubtful this second radio frequency auction will be quite so popular.

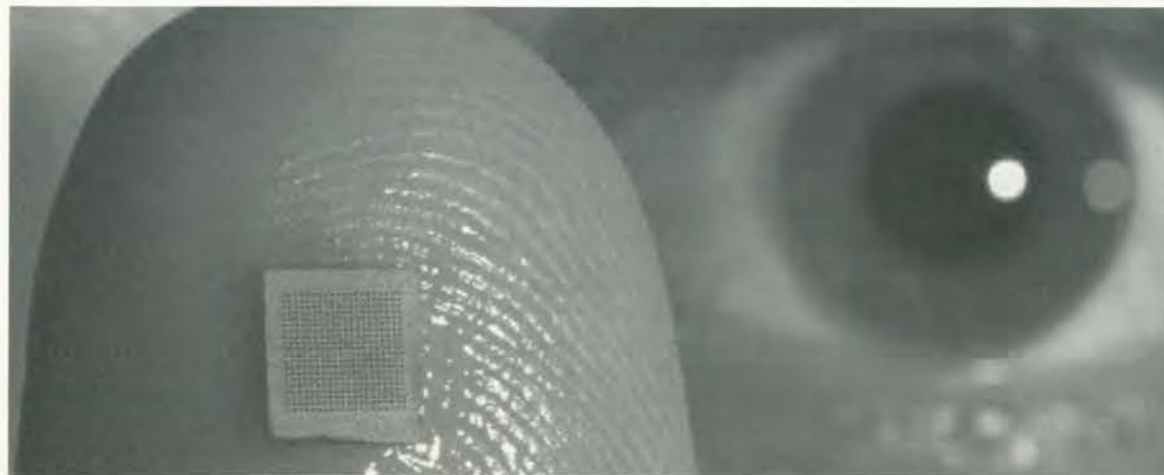"Awarding licences by auction will ensure that they are taken up by those operators best placed to develop services most efficiently," said Patricia Hewitt, e-commerce minister. "The licence package is designed to encourage new entrants and the development of a competitive market."



You won't feel a thing...

Microneedles could be the basis for a new drug delivery technique. Under development at the Georgia Institute of technology, the needles are short enough not to hit nerves, but big enough to enable large molecules - including insulin - to penetrate the skin.

Excessive mobile licence costs – who will pay the bill?

The multi-billion pound sums generated by bids for third-generation mobile phone licences cannot be justified by the business cases made for the technology before the auction began, according to an analyst involved.

"The licences are now costing more than the business plans will allow," said Andrew Parkin-White, an analyst at Ovum. "They are costing more than the infrastructure."

Ovum worked with several companies on their business case

before the auction. Using a conservative estimate, Parkin-White believed all five licences would go for £3.2bn. Infrastructure costs were estimated at £2 to £3bn.

The worry is the prices will result in high costs for the user. "Someone's going to have to pick up the tab," said Parkin-White, "and new entrants won't want to see prices fall too much."

BT refused to be drawn on the subject of the auction in which it is bidding as BT3G. "I'm not going to

tell you my bidding strategy," commented Sir Peter Bonfield, BT's chief executive. The company was the first to raise the bid for a licence over £5bn.

Parkin-White's other worry is that the mobile market is being fuelled by the current dot.com mentality as the mobile and Internet worlds converge. "The question is whether the bubble will burst and affect mobile Internet," said Parkin-White.

The five successful bids were, TIW 4.4bn, Vodaphone 6bn, BT 4bn, One2One 4bn and Orange 4bn.

Electronics engineers are in big demand

Electronics engineers are in demand like never before, with job prospects in the sector predicted to be strong over the next few months, according to Manpower's latest Quarterly Survey of Employment Prospects.

Year-on-year figures for electronics show improvements in the forecast for job increases. A third of electronics companies are looking to recruit in the second quarter of this year – 33 per cent up from 28 per

cent. Companies looking to shed staff are down from ten to six per cent.

"As one of the few sectors not to suffer downsizing in the second quarter of 1999, it has had a strong base from which to build a lead that keeps it well ahead of the national average," said a Manpower spokesperson.

Unfortunately for the industry – but good for individual engineers – the high demand is not matched by the supply of suitably qualified staff.

"It is exceptionally difficult to find people at the moment: silicon designers, anyone to do with ICs and embedded software engineers are in particularly short supply," said Geoffrey King, managing director of electronics recruitment firm Cambridge Recruitment Specialists. "People are being offered crazy amounts of money to do jobs that aren't worth that much."

King sees the problem as fundamental. "You can only go on so far

by stealing from your competitors. The problem is that the supply chain is not keeping pace. The number of people reading relevant subjects at university is shrinking.


"It is a huge educational issue. Kids need to be tuned in to this much earlier," he added.

Competition for design engineers is as bad or even greater in Silicon Valley and other US electronics centres. As a result some companies are looking to developing design groups in new electronics areas around the world like Bangalore in India.

"There are some excellent engineers there, but it is a slow process to bring engineers from India," said King.

With recruitment so competitive, companies are having to work to keep staff.

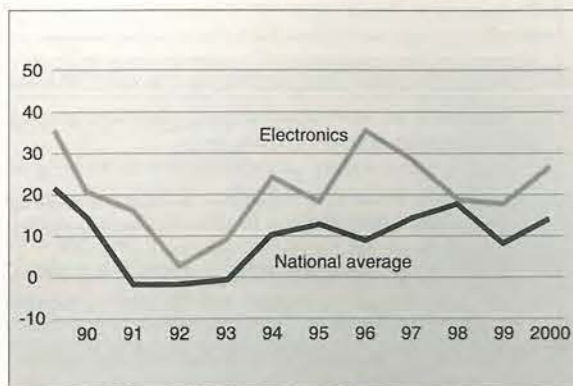"It is not necessarily the money, it is the way people are utilised," said King. "Give them interesting things to do and listen to them."



Experts play down mobile phone health risk claims

A government-sponsored report is set to dismiss claims that mobile phones are a proven health risk.

The Stewart Inquiry, due to report on 11 May, is expected to conclude that allegations that they cause illnesses ranging from memory loss to tumours appear to be unfounded.

The committee of 12 experts is understood to accept evidence that while mobiles tend to heat up the brain, the heating is not enough to affect people's health.

The maximum rise in temperature is just one tenth of a degree, the team were told, while the normal body temperature varies by a full degree over the course of a day.

But as a precaution, the committee is

expected to call for tighter controls on microwave radiation emissions bringing them in line with European levels.

The committee will also say there must be more research by the Department of Health into the "non-thermal" effects, which some other studies have suggested can pose a health risk.

But the committee, chaired by Tayside University Hospital Sir William Stewart, does accept that the children, who own 300 000 of the 24 million mobiles in Britain, could be at greater risk if there is any risk.


The report follows 10 months of research and is expected to call for tighter planning controls on the siting of mobile phone masts and urges the National Radiological

Protection Board (NRPB) to conduct regular spot checks on the 500 masts sited near schools. It seems that the committee was struck by the strength of public opposition to the masts.

But as the final drafts of the report are prepared, some critics said the committee had been "captured" by the NRPB and recently doubts have been cast on the safety of the hands-free mobiles introduced in response to the health concerns over mobiles.

● According to a BBC on-line news report, Sir William says that he would discourage his grandchildren from using mobile phones until further research is completed.

TiePieScope HS801 PORTABLE MOST

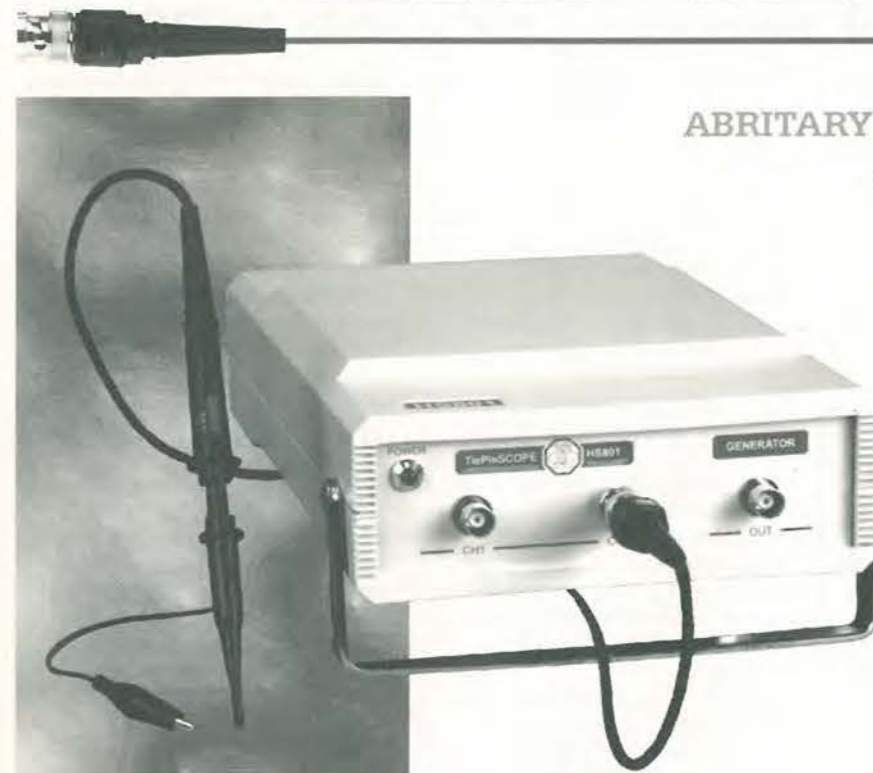

ARBITRARY WAVEFORM GENERATOR-
STORAGE OSCILLOSCOPE-
SPECTRUM ANALYZER-
MULTIMETER-
TRANSIENT RECORDER-

Reliability

- The sophisticated cursor read outs have 21 possible read outs. Besides the usual read outs, like voltage and time, also quantities like rise time and frequency are displayed.
- Measured signals and instrument settings can be saved on disk. This enables the creation of a library of measured signals. Text balloons can be added to a signal, for special comments. The (colour) print outs can be supplied with three common text lines (e.g. company info) on three lines with measurement specific information.
- The HS801: the first 100 Mega samples per second measuring instrument that consists of a MOST (Multimeter, Oscilloscope, Spectrum analyzer and Transient recorder) and an AWG (arbitrary waveform generator). This new MOST portable and compact measuring instrument can solve almost every measurement problem. With the integrated AWG you can generate every signal you want.
- The versatile software has a user-defined toolbar with which over 50 instrument settings quick and easy can be accessed. An intelligent auto setup allows the inexperienced user to perform measurements immediately. Through the use of a setting file, the user has the possibility to save an instrument setup and recall it at a later moment. The setup time of the instrument is hereby reduced to a minimum.
- The minimum system requirement is a PC with a 486 processor and 8 Mbyte RAM available. The software runs in Windows 3.xx / 95 / 98 or Windows NT and DOS 3.3 or higher.
- TiePie engineering (UK), 28 Stephenson Road, Industrial Estate, St. Ives, Cambridgeshire, PE17 4WJ, UK
Tel: 01480-460028; Fax: 01480-460340
- TiePie engineering (NL), Koperslagersstraat 37, 8601 WL SNEEK The Netherlands
Tel: +31 515 415 416; Fax +31 515 418 819
- When a quick indication of the input signal is required, a simple click on the auto setup button will immediately give a good overview of the signal. The auto setup function ensures a proper setup of the time base, the trigger levels and the input sensitivities.



CIRCLE NO. 109 ON REPLY CARD

Conventional chips may be viable to 2005

US researchers are claiming that performance limits on conventional transistors might not be reached as quickly as first thought.

A transistor's gate oxide layer was thought to reach a limit at nine or ten atoms thick, but Bell Labs researchers think it could work down to six atoms, or 1.5nm, thick. "Achieving such thin dimensions with the required intrinsic

reliability was previously thought to be impossible," said Ashraf Alam, the Bell Labs' scientist that led the research.

Alam's team showed that a 1.5nm gate could, in theory at least, run at 1V for up to ten years. Another Bell Labs team proved the result experimentally.

The life extension to silicon dioxide (SiO₂) as a gate material,

perhaps until 2005, gives engineers more time to develop alternative materials.

These include group IVB oxides such as hafnium oxide and zirconium oxide which have leakages up to 10⁴ times less than SiO₂. These can match the performance of SiO₂, but can be deposited in layers around three times as thick.

Trainee engineers jam military satellite with ham radio gear


Military satellites can be jammed with easily-bought material using information from the Internet. A report in *New Scientist* magazine, describes how the US Air Force tasked two "rookie" engineers to build a UHF satellite jammer. They succeeded using materials from high street stores and radio ham swap meets. The total cost of the jammer, which runs from a simple petrol generator and can be transported on the back of a pick-up truck, was \$7500.

Stress claims triple in six months

Increasing workplace stress is boosting compensation claims on employers - says the Engineering Employers Federation.

Stress related enquires to the Federation have tripled in the last six months. "There is also no doubt that, in the UK, employees are increasingly aware of their rights and are now routinely looking to litigation rather than using it as a last resort," said Sandra Howard, head of legal affairs at the Federation's north west association.

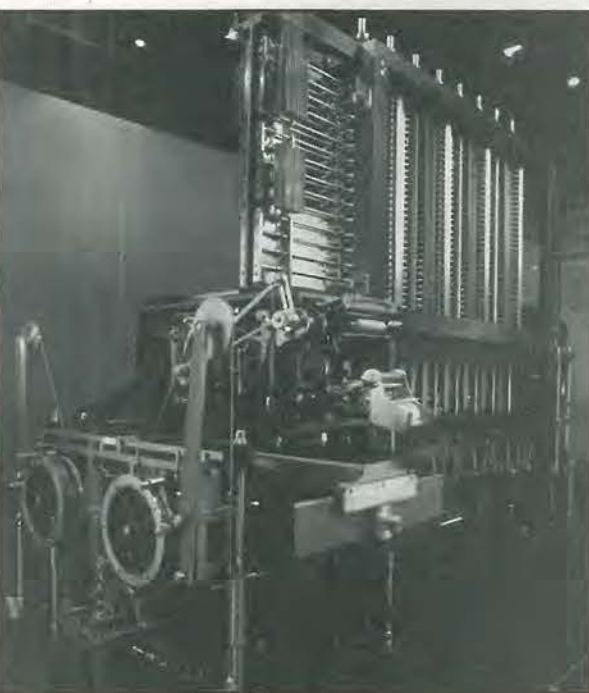"There is no doubt that we still have a 'long hours' culture in the UK and that can add to pressures," said Howard.



Tool eliminates chip noise errors

EDA start-up Moscape has a tool it claims can eliminate chip design errors due to noise.

Called GateScope, the tool can identify and correct noise problems caused by cross-coupling, being found more as designs move to 0.18µm.

"The devastating effects of noise on functionality and timing are typically unrecognised until test chips are produced. Silencing this noise prior to tapeout is possible only with the new analytical and corrective approach embodied in GateScope," said Fuad Musa,

Moscape's president and CEO.

Smaller design rules and more advanced processes are bringing noise problems as cross-coupling between the narrow pitched metal interconnect increases. Logic simulation and static timing analysis fail to isolate these problems, Moscape claimed.

The tool, it said, has the precision to find the smaller errors, reducing the chance that the design fails to meet its timing specification.

GateScope runs on Unix, Solaris and Linux operating systems and costs \$75 000 per seat, per year.

Tory presses labour on e-government issue

A former Tory science minister is launching a Parliamentary campaign to force the government to deliver on its 'Information Age' pledge.

Robert Jackson believes the government is falling behind in the drive to put its services on line. The Wantage backbencher has tabled a series of questions aimed at discovering exactly how far each Whitehall Department has got in bringing in e-government.

"The UK's strategy for on-line government is flawed," said Jackson. "They have produced a 34-page book

that took a year to write but says nothing."

According to Jackson, none of the Inland Revenue's dealings with citizens or business involved the Internet in 1999, and it will rise by four per cent by 2002. No dealings at the DSS will be Internet deliverable by 2002.

"Ministers make grand promises to have services on line by 2002 and all suitable services electronically available by 2005 but they haven't given any indication of how they will do it," added Jackson.

Babbage gets printer after 150 year wait

Engineers worried about shorter development cycles should spare a thought for Charles Babbage whose printer has just been built, over 150 years since it was designed.

Built by the Science Museum, the mechanical printer can output results of calculations with programmable line width, margins and number of columns.

The printer can also produce

stereotype plates for use in a printing press.

The computing part of the system, Babbage's Difference Engine No 2, was built in 1991, but the printer had to wait a few years more.

Both devices weigh in over 2.5 tonnes and contain more than 4000 parts. They were designed to produce tables used in navigation, engineering, banking and insurance.

SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK

HP New Colour Spectrum Analysers LAST FEW ONLY
 HP141T+ 8552B IF + 8553B RF - 1KHz - 110Mc/s - £500.
 HP141T+ 8552B IF + 8554B RF - 100KHz - 1250M - £600.
 HP141T+ 8552B IF + 8556A RF - 20Hz-300KHz - £400.
 HP141T+ 8552B IF + 8555A 10 MC/S-18GHz - £1000.
 HP8443A Tracking Gen Counter 100KHz-110Mc/s - £200
 HP8445B Tracking Prescaler DC to 18GHz - £250.
 HP8444A Tracking Generator 5-1300Mc/s - £450.
 HP8444A OPT 058 Tracking Gen 5-1500Mc/s - £650.
 HP35601A Spectrum Anz Interface - £300.
 HP4953A Protocol Anz - £400.
 HP8970A Noise Figure Meter + 346B Noise Head - £3k.
 HP8755A+B+C Scalar Network Anz PI - £250 + MF 180C - Heads 11664 Extra - £150 each.
 HP3709B Constellation ANZ £1,000.
 HP11715A AM-FM Test Source - £350.
 FARNELL TVS70MKII PU 0-70V 10 amps - £150.
 MARCONI 6500 Network Scalar Anz - £500. Heads available to 40GHz many types in stock.
 Mixers are available for ANZs to 60GHz.
 HP6131C Digital Voltage Source - 100V/5 Amp.
 HP5316A Universal Counter A+B.
 Marconi TF2374 Zero Loss Probe - £200.
 Rascal/Dana 2101 Microwave Counter - 10Hz-20GHz - with book as new £2k.
 Rascal/Dana 1250-1261 Universal Switch Controller + 200Mc/s PI Cards and other types.
 Rascal/Dana 9303 True RMS Levelmeter + Head - £450.
 TEKA6902A also A6902B Isolator - £300-£400.
 TEK CT-5 High Current Transformer Probe - £250.
 HP Frequency comb generator type 8406 - £400.
 HP Sweep Oscillators type 8690 A+B - plug-ins from 20Mc/s to 18GHz also 18-40GHz.
 HP Network Analyser type 8407A + 8412A - 8654A - 300Kcs - 110Mc/s - £500 - £1000.
 HP 8410-A-B-C Network Analyser 110Mc/s to 12GHz or 18 GHz - plus most other units and displays used in this kit-up - 8411A-8412-8413-8414-8418-8419-8420-8421-8422-8423-8424-8425-8426-8427-8428-8429-8430-8431-8432-8433-8434-8435-8436-8437-8438-8439-8440-8441-8442-8443-8444-8445-8446-8447-8448-8449-8450-8451-8452-8453-8454-8455-8456-8457-8458-8459-8460-8461-8462-8463-8464-8465-8466-8467-8468-8469-8470-8471-8472-8473-8474-8475-8476-8477-8478-8479-8480-8481-8482-8483-8484-8485-8486-8487-8488-8489-8490-8491-8492-8493-8494-8495-8496-8497-8498-8499-8500-8501-8502-8503-8504-8505-8506-8507-8508-8509-8510-8511-8512-8513-8514-8515-8516-8517-8518-8519-8520-8521-8522-8523-8524-8525-8526-8527-8528-8529-8530-8531-8532-8533-8534-8535-8536-8537-8538-8539-8540-8541-8542-8543-8544-8545-8546-8547-8548-8549-8550-8551-8552-8553-8554-8555-8556-8557-8558-8559-8560-8561-8562-8563-8564-8565-8566-8567-8568-8569-8570-8571-8572-8573-8574-8575-8576-8577-8578-8579-8580-8581-8582-8583-8584-8585-8586-8587-8588-8589-8590-8591-8592-8593-8594-8595-8596-8597-8598-8599-8600-8601-8602-8603-8604-8605-8606-8607-8608-8609-8610-8611-8612-8613-8614-8615-8616-8617-8618-8619-8620-8621-8622-8623-8624-8625-8626-8627-8628-8629-8630-8631-8632-8633-8634-8635-8636-8637-8638-8639-8640-8641-8642-8643-8644-8645-8646-8647-8648-8649-8650-8651-8652-8653-8654-8655-8656-8657-8658-8659-8660-8661-8662-8663-8664-8665-8666-8667-8668-8669-8670-8671-8672-8673-8674-8675-8676-8677-8678-8679-8680-8681-8682-8683-8684-8685-8686-8687-8688-8689-8690-8691-8692-8693-8694-8695-8696-8697-8698-8699-8700-8701-8702-8703-8704-8705-8706-8707-8708-8709-8710-8711-8712-8713-8714-8715-8716-8717-8718-8719-8720-8721-8722-8723-8724-8725-8726-8727-8728-8729-8730-8731-8732-8733-8734-8735-8736-8737-8738-8739-8740-8741-8742-8743-8744-8745-8746-8747-8748-8749-8750-8751-8752-8753-8754-8755-8756-8757-8758-8759-8760-8761-8762-8763-8764-8765-8766-8767-8768-8769-8770-8771-8772-8773-8774-8775-8776-8777-8778-8779-8780-8781-8782-8783-8784-8785-8786-8787-8788-8789-8790-8791-8792-8793-8794-8795-8796-8797-8798-8799-8800-8801-8802-8803-8804-8805-8806-8807-8808-8809-8810-8811-8812-8813-8814-8815-8816-8817-8818-8819-8820-8821-8822-8823-8824-8825-8826-8827-8828-8829-8830-8831-8832-8833-8834-8835-8836-8837-8838-8839-8840-8841-8842-8843-8844-8845-8846-8847-8848-8849-8850-8851-8852-8853-8854-8855-8856-8857-8858-8859-8860-8861-8862-8863-8864-8865-8866-8867-8868-8869-8870-8871-8872-8873-8874-8875-8876-8877-8878-8879-8880-8881-8882-8883-8884-8885-8886-8887-8888-8889-8890-8891-8892-8893-8894-8895-8896-8897-8898-8899-8900-8901-8902-8903-8904-8905-8906-8907-8908-8909-8910-8911-8912-8913-8914-8915-8916-8917-8918-8919-8920-8921-8922-8923-8924-8925-8926-8927-8928-8929-8930-8931-8932-8933-8934-8935-8936-8937-8938-8939-8940-8941-8942-8943-8944-8945-8946-8947-8948-8949-8950-8951-8952-8953-8954-8955-8956-8957-8958-8959-8960-8961-8962-8963-8964-8965-8966-8967-8968-8969-8970-8971-8972-8973-8974-8975-8976-8977-8978-8979-8980-8981-8982-8983-8984-8985-8986-8987-8988-8989-8990-8991-8992-8993-8994-8995-8996-8997-8998-8999-9000-9001-9002-9003-9004-9005-9006-9007-9008-9009-9010-9011-9012-9013-9014-9015-9016-9017-9018-9019-9020-9021-9022-9023-9024-9025-9026-9027-9028-9029-9030-9031-9032-9033-9034-9035-9036-9037-9038-9039-9040-9041-9042-9043-9044-9045-9046-9047-9048-9049-9050-9051-9052-9053-9054-9055-9056-9057-9058-9059-9060-9061-9062-9063-9064-9065-9066-9067-9068-9069-9070-9071-9072-9073-9074-9075-9076-9077-9078-9079-9080-9081-9082-9083-9084-9085-9086-9087-9088-9089-9090-9091-9092-9093-9094-9095-9096-9097-9098-9099-9100-9101-9102-9103-9104-9105-9106-9107-9108-9109-9110-9111-9112-9113-9114-9115-9116-9117-9118-9119-9120-9121-9122-9123-9124-9125-9126-9127-9128-9129-9130-9131-9132-9133-9134-9135-9136-9137-9138-9139-9140-9141-9142-9143-9144-9145-9146-9147-9148-9149-9150-9151-9152-9153-9154-9155-9156-9157-9158-9159-9160-9161-9162-9163-9164-9165-9166-9167-9168-9169-9170-9171-9172-9173-9174-9175-9176-9177-9178-9179-9180-9181-9182-9183-9184-9185-9186-9187-9188-9189-9190-9191-9192-9193-9194-9195-9196-9197-9198-9199-9200-9201-9202-9203-9204-9205-9206-9207-9208-9209-9210-9211-9212-9213-9214-9215-9216-9217-9218-9219-9220-9221-9222-9223-9224-9225-9226-9227-9228-9229-9230-9231-9232-9233-9234-9235-9236-9237-9238-9239-9240-9241-9242-9243-9244-9245-9246-9247-9248-9249-9250-9251-9252-9253-9254-9255-9256-9257-9258-9259-9260-9261-9262-9263-9264-9265-9266-9267-9268-9269-9270-9271-9272-9273-9274-9275-9276-9277-9278-9279-9280-9281-9282-9283-9284-9285-9286-9287-9288-9289-9290-9291-9292-9293-9294-9295-9296-9297-9298-9299-9300-9301-9302-9303-9304-9305-9306-9307-9308-9309-9310-9311-9312-9313-9314-9315-9316-9317-9318-9319-9320-9321-9322-9323-9324-9325-9326-9327-9328-9329-9330-9331-9332-9333-9334-9335-9336-9337-9338-9339-9340-9341-9342-9343-9344-9345-9346-9347-9348-9349-9350-9351-9352-9353-9354-9355-9356-9357-9358-9359-9360-9361-9362-9363-9364-9365-9366-9367-9368-9369-9370-9371-9372-9373-9374-9375-9376-9377-9378-9379-9380-9381-9382-9383-9384-9385-9386-9387-9388-9389-9390-9391-9392-9393-9394-9395-9396-9397-9398-9399-9400-9401-9402-9403-9404-9405-9406-9407-9408-9409-9410-9411-9412-9413-9414-9415-9416-9417-9418-9419-9420-9421-9422-9423-9424-9425-9426-9427-9428-9429-9430-9431-9432-9433-9434-9435-9436-9437-9438-9439-9440-9441-9442-9443-9444-9445-9446-9447-9448-9449-9450-9451-9452-9453-9454-9455-9456-9457-9458-9459-9460-9461-9462-9463-9464-9465-9466-9467-9468-9469-9470-9471-9472-9473-9474-9475-9476-9477-9478-9479-9480-9481-9482-9483-9484-9485-9486-9487-9488-9489-9490-9491-9492-9493-9494-9495-9496-9497-9498-9499-9500-9501-9502-9503-9504-9505-9506-9507-9508-9509-9510-9511-9512-9513-9514-9515-9516-9517-9518-9519-9520-9521-9522-9523-9524-9525-9526-9527-9528-9529-9530-9531-9532-9533-9534-9535-9536-9537-9538-9539-9540-9541-9542-9543-9544-9545-9546-9547-9548-9549-9550-9551-9552-9553-9554-9555-9556-9557-9558-9559-9560-9561-9562-9563-9564-9565-9566-9567-9568-9569-9570-9571-9572-9573-9574-9575-9576-9577-9578-9579-9580-9581-9582-9583-9584-9585-9586-9587-9588-9589-9590-9591-9592-9593-9594-9595-9596-9597-9598-9599-9600-9601-9602-9603-9604-9605-9606-9607-9608-9609-9610-9611-9612-9613-9614-9615-9616-9617-9618-9619-9620-9621-9622-9623-9624-9625-9626-9627-9628-9629-9630-9631-9632-9633-9634-9635-9636-9637-9638-9639-9640-9641-9642-9643-9644-9645-9646-9647-9648-9649-9650-9651-9652-9653-9654-9655-9656-9657-9658-9659-9660-9661-9662-9663-9664-9665-9666-9667-9668-9669-9670-9671-9672-9673-9674-9675-9676-9677-9678-9679-9680-9681-9682-9683-9684-9685-9686-9687-9688-9689-9690-9691-9692-9693-9694-9695-9696-9697-9698-9699-9700-9701-9702-9703-9704-9705-9706-9707-9708-9709-9710-9711-9712-9713-9714-9715-9716-9717-9718-9719-9720-9721-9722-9723-9724-9725-9726-9727-9728-9729-9730-9731-9732-9733-9734-9735-9736-9737-9738-9739-9740-9741-9742-9743-9744-9745-9746-9747-9748-9749-9750-9751-9752-9753-9754-9755-9756-9757-9758-9759-9760-9761-9762-9763-9764-9765-9766-9767-9768-9769-9770-9771-9772-9773-9774-9775-9776-9777-9778-9779-9780-9781-9782-9783-9784-9785-9786-9787-9788-9789-9790-9791-9792-9793-9794-9795-9796-9797-9798-9799-9800-9801-9802-9803-9804-9805-9806-9807-9808-9809-9810-9811-9812-9813-9814-9815-9816-9817-9818-9819-9820-9821-9822-9823-9824-9825-9826-9827-9828-9829-9830-9831-9832-9833-9834-9835-9836-9837-9838-9839-9840-9841-9842-9843-9844-9845-9846-9847-9848-9849-9850-9851-9852-9853-9854-9855-9856-9857-9858-9859-9860-9861-9862-9863-9864-9865-9866-9867-9868-9869-9870-9871-9872-9873-9874-9875-9876-9877-9878-9879-9880-9881-9882-9883-9884-9885-9886-9887-9888-9889-9890-9891-9892-9893-9894-9895-9896-9897-9898-9899-9900-9901-9902-9903-9904-9905-9906-9907-9908-9909-9910-9911-9912-9913-9914-9915-9916-9917-9918-9919-9920-9921-9922-9923-9924-9925-9926-9927-9928-9929-9930-9931-9932-9933-9934-9935-9936-9937-9938-9939-9940-9941-9942-9943-9944-9945-9946-9947-9948-9949-9950-9951-9952-9953-9954-9955-9956-9957-9958-9959-9960-9961-9962-9963-9964-9965-9966-9967-9968-9969-9970-9971-9972-9973-9974-9975-9976-9977-9978-9979-9980-9981-9982-9983-9984-9985-9986-9987-9988-9989-9990-9991-9992-9993-9994-9995-9996-9997-9998-9999-10000-10001-10002-10003-10004-10005-10006-10007-10008-10009-10010-10011-10012-10013-10014-10015-10016-10017-10018-10019-10020-10021-10022-10023-10024-10025-10026-10027-10028-10029-10030-10031-10032-10033-10034-10035-10036-10037-10038-10039-10040-10041-10042-10043-10044-10045-10046-10047-10048-10049-10050-10051-10052-10053-10054-10055-10056-10057-10058-10059-10060-10061-10062-10063-10064-10065-10066-10067-10068-10069-10070-10071-10072-10073-10074-10075-10076-10077-10078-10079-10080-10081-10082-10083-10084-10085-10086-10087-10088-10089-10090-10091-10092-10093-10094-10095-10096-10097-10098-10099-10100-10101-10102-10103-10104-10105-10106-10107-10108-10109-10110-10111-10112-10113-10114-10115-10116-10117-10118-10119-10120-10121-10122-10123-10124-10125-10126-10127-10128-10129-10130-10131-10132-10133-10134-10135-10136-10137-10138-10139-10140-10141-10142-10143-10144-10145-10146-10147-10148-10149-10150-10151-10152-10153-10154-10155-10156-10157-10158-10159-10160-10161-10162-10163-10

Never before has the British public been monitored so closely or, it would appear, so willingly. Unblinking eyes now scan the trunk roads and city centres of Britain but with differing aims and using different technologies. Andrew Emmerson takes a closer look at who's zooming whom.



Illustration: Jamel Akib

Behind big brother

In theory, Trafficmaster's number plate cameras could be used to report speeding vehicles, but the company insists its data is not passed on to any outside agencies.

That prickly feeling on the back of your neck that you are being watched is generally put down to paranoia. Scientific tests at the University of Hertfordshire to measure skin resistance certainly failed to detect any change when hidden video cameras were trained on them.

For the public at large though – and motorists in particular – this suspicion may well be justified. Their movements are coming under increasing surveillance. The UK is now said to have Europe's largest market for CCTV equipment, valued at over £385 million per year.

With most city centres, banks, shops, airports and main railway stations under 24-hour watch by closed circuit television (CCTV) the suggestion is now made that British citizens – 'subjects' may be a better word – may be snapped 14 times a day.

Headlines are no longer made when news reports state that crime suspects were caught on camera, while the

police acknowledge that it takes just four seconds now to alert them if a vehicle caught on their cameras is on the wanted file. Crime rates in CCTV zones have fallen by up to 50 per cent, driving wrongdoers out of town centres and into the suburbs.

Initial concern over civil liberties has now subsided into widespread acceptance of these high-profile installations. Indeed, according to Strathclyde Police, the public has now become so accustomed to CCTV cameras that they now view them as "simply part of the street furniture".

But what about the not-so-obvious systems and what are the technologies involved?

Steady as you go


By now, most motorists in Britain will have spotted the distinctive cobalt blue poles carrying cameras and radio antennas that adorn the majority of trunk roads. Many people give them a careful berth, assuming they are a new generation of speed camera but in fact

their purpose is PTFM, or passive target-flow monitoring.

The cameras belong to Trafficmaster plc – a company that first made its name by providing information about traffic jams using a network of sensors along main motorways in Britain. PTFM takes the concept much further by measuring the time taken by individual vehicles to cover the known distances between sensors.

These specially developed infra-red sensors, installed approximately four miles apart, 'snap' the number plates of passing vehicles. Computers at each site transmit this information back to Trafficmaster's national control centre in Milton Keynes.

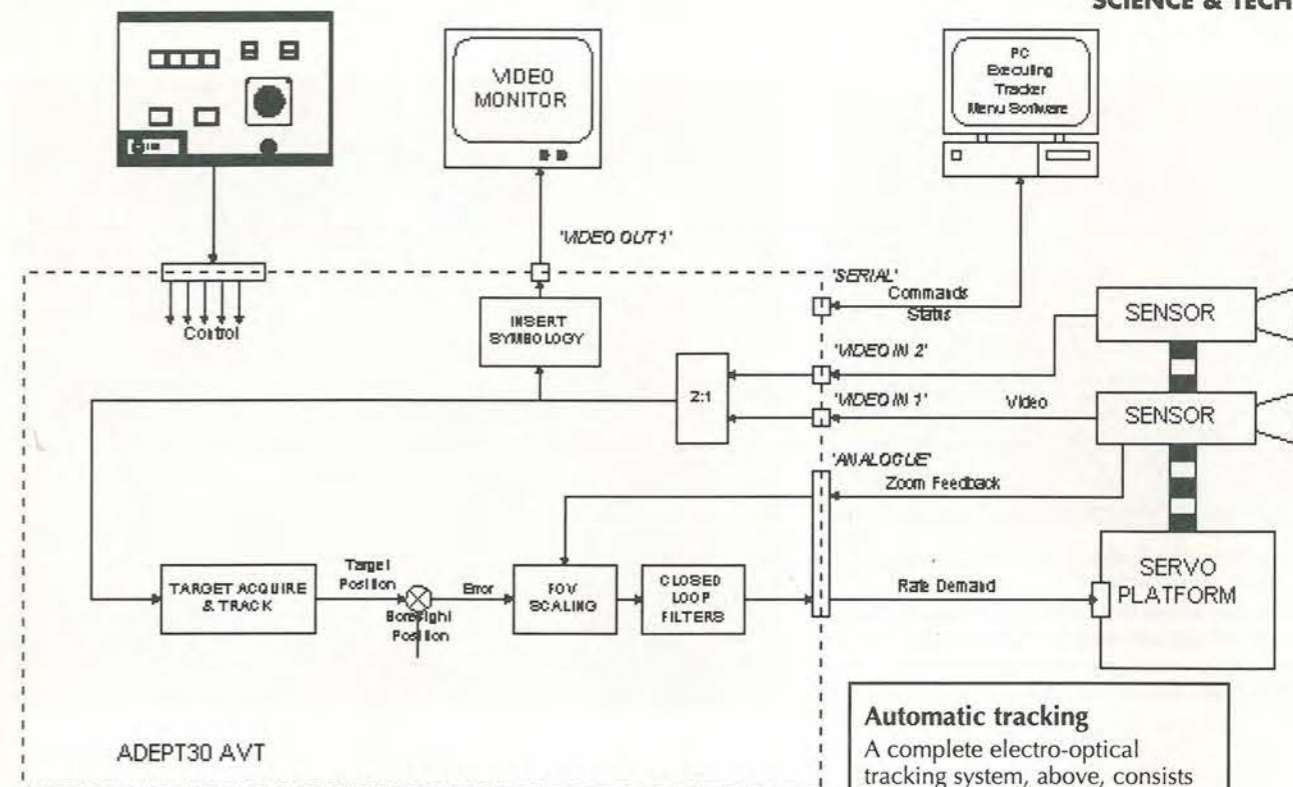The time taken for a vehicle to travel between each sensor site is calculated. Then, odd spurious results are rejected – for example, drivers who have turned off or stopped along the way – and a pattern is thus built up of the average speed along the stretch of road. This information is then trans-



Automatic tracking

A complete electro-optical tracking system, above, consists of an imaging sensor – typically TV or IR – mounted on a two-axis servo platform and a tracker controlling the position of the platform based on the scene observed through the imaging sensor.

The automatic tracking system processes video images directly in real-time to ascertain the position of a designated object with respect to the sensor boresight. An error signal derived by the system from the image is then used to control the platform such that the platform and attached sensors accurately follow the target.

An Octec video tracker is designed to be integrated with a servo platform and video sensor. The video tracker automatically detects and tracks a single target in the video picture from the sensor mounted on the servo platform. From this picture, it provides an 'output demand' that controls the position of the servo platform such that the platform and attached sensors follow the target.

Serial or VMEbus interfaces can be used in place of the discrete interfaces (Controller, Analogue etc.)

mitted directly to vehicles fitted with Trafficmaster receivers when they pass the next sensor site.

A potential speed trap

In theory, the system could be used for identifying speeding drivers or for tracking individuals but the company insists the data is not passed on to any other agency. Indeed, to avoid falling foul of data-protection legislation, the first and last characters of each vehicle number taken is discarded. The remaining character string, or 'tag', is still sufficiently unique for processing purposes.

The system is also being developed to use neural networks. This is a form of computer intelligence that allows the software to predict the movement of traffic flows, and recognise when traffic congestion is building up or starting to disperse.

Concern over misuse of data collected is dismissed by a Trafficmaster spokesperson, who told me, "Under

the terms of Trafficmaster's licence agreement with the Department of Transport, we must dump the information gathered immediately it has been processed. We only read the central four digits of a car's number plate. In addition, we only read a small percentage of those vehicles that pass by each site. A 100 per cent sample is not only unnecessary, but also not desirable—the equipment needed to process that amount of data would be extremely expensive, and totally unnecessary."

Expanding rapidly...

Trafficmaster's expanded network now covers approximately 8000 miles of motorways and trunk roads in England, with some 5000 cameras in use. The service is being extended to motorists in Scotland and Wales shortly. It provides the most comprehensive, near-nationwide, live traffic-monitoring network in the world.

A further enhancement of the sys-

Information on-line

CAATS	http://www.octec.co.uk/trackers/caats2.html
Mandrake	http://www.tssi.co.uk/
Trafficmaster	http://www.gifford.co.uk/i-contact/tash/tash20.html
Visionics face recognition	http://www.trafficmaster.co.uk
Conspiracy theories	http://www.faceit.co.uk
	http://www.spy.org.uk/trafficmaster.htm
	http://www.ultranet.com/~bevanr/saab/trafficmaster.html
	http://www.geocities.com/MotorCity/2195/speedtrap_notatrap.html#traffic2



Frames from two videos taken from a helicopter fitted with CAATS to illustrate electro-optical tracking, left, and 'scenelock', right, where the camera automatically tracks a particular picture, regardless of the helicopter's movement. The demonstration video samples are available for downloading from Octec's web site.



Mandrake is a face recognition system that automatically monitors live images from closed-circuit tv cameras and captures people's faces as they pass through the field of view. Captured images are analysed and compared to a data base of known, wanted people. On identifying a wanted individual, Mandrake raises an alarm.

tem's software will enable it to predict when traffic is at its worst and hence the best time to travel. The accurate journey time data can be produced in formats that can be integrated into any on-board electronic information system, for example, GPS navigation systems.

Plans are in hand to extend the system to France, Germany and Italy. And the company has recently announced the development of a new patented 'mobile' sensor technology. This will use specially equipped vehicles to actively measure journey times between two points.

The resulting traffic information will appear 'seamless' to the end user. It has been designed to be fully integrated with data collected from Trafficmaster's fixed networks.

Eye in the sky

An engaging feature of the numerous

'Police Stop' programmes on television is the aerial view footage of fast-moving felons taken from helicopters. Curious minds may wonder how the cameraman manages to keep the vehicle in shot so successfully and avoid judder on the images. The answer is of course a robot and the technology is significantly more sophisticated than the first 'heli-tele' systems.

Giro stabilisation was all that was available when helicopter-mounted video cameras were first used for public surveillance. That occasion was in 1979, when London's Metropolitan Police observed the Notting Hill Carnival.

Many of today's crime helicopters use the compact airborne automatic-tracking system (CAATS) developed originally for missile guidance and other defence purposes. Infra-red technology tracks vehicle movement through streets and even behind buildings to drive the camera pod and maintain visibility.

How electro-optical tracking works

CAATS is made by Octec Ltd, based in Bracknell and one of the leading independent suppliers of digital video tracking and image processing systems to the defence market worldwide. The company's electro-optical tracking system consists of an imaging sensor – either video or infra-red – mounted on a two-axis servo platform. There's also a tracker that controls the position of the platform based on the scene observed through the imaging sensor.

Automatic tracking is achieved by an electronic system that processes video images directly in real-time to

ascertain the position of a designated object with respect to the sensor bore-sight. This error is then used to control the platform such that the platform and attached sensors accurately follow the target.

Pre-processing, using image enhancement algorithms, is also possible. This allows the target to be enhanced prior to the 'tracking process' and rejecting unwanted elements in the picture, or 'clutter'. A number of selectable options are also available to allow the operator to select 'positive contrast', 'negative contrast', or 'polarity independent' modes of operation.

Thanks to Octec for helping with this description.

Just a face in the crowd?

Even more remarkable to non-specialists is the face recognition capabilities that can be used to enhance CCTV surveillance systems. Notable in this connection is the Mandrake system developed in the UK by Software and Systems International. It is based on neural-network face recognition technology from Visionics in the USA.

The software automatically detects, locates and identifies human faces from live video or static images, using sophisticated algorithms for pattern recognition that mimic how the human brain recognises faces. This is carried out continuously and in real time. Results are tagged with a percentage score of how confident the computer is that the person spotted is one of the individuals in the database.

A high-profile system went live in the London borough of Newham in October 1998, linked to Newham's

CCTV street cameras – now 240 in number – and a database of suspects supplied by the Metropolitan Police. At the launch, Newham's chief of security Bob Lack stated bullishly: "We have ten or so active muggers in and around our shopping centres," says. "As the system develops, facial images of known paedophiles may also be added to the automated watch list." He added that the computer had distinct advantages over humans. "If you stare at a screen for hours, you tend to glaze over," he said. "But never forget the need for the human element. None of our cameras has got down off a pole and arrested anyone yet," he added.

Applied responsibly, biometrics can be used in this way to combat crime, although civil liberties campaigners have voiced concern over the system's accuracy and what is done with discarded recordings. According to the council, the system does not need registration under the Data Protection Act since personal information is not held on the face recognition system; only photographs and police reference numbers are held.

Digital does it better

New-generation digital video recording systems have rendered older analogue CCTV systems obsolete, with their ability to monitor, archive and retrieve video data captured on camera. NiceVision, a system designed for organisations using multiple CCTV cameras in one or more locations, is a good exemplar of the new breed, providing 'high-motion' digital video and audio recording along with simultaneous playback.

Operated from a rack-mounted platform of NT-based PC computers, NiceVision offers a high number of camera and channel capacities. Each of the 32 channels can be configured independently to record up to 12 frames a second from each PAL colour camera connected, with pre- and post-alarm, and event-triggered recording options. This allows for optimal recording methods for both event and personal identification and offers enhanced security management capabilities.

NiceVision permits password-authorized users to search and find video segments for playback quickly from a desktop computer. In this way security managers and officers can review, analyse and respond to events immediately while continuing to record.

The system's open architecture allows it to be integrated with existing access control, alarms and other intrusion detection systems where users

can set different recording modes for each independent camera. Modular and scalable, the system also allows for multi-user control via local-area network (LAN), remote access via wide area network (WAN), and data transmission over fibre optics or ISDN lines.

George Orwell was right...

Where all this takes us is anyone's guess. Law-abiding citizens clearly have nothing to fear from enhanced levels of surveillance. Many indeed welcome any device that secures greater levels of law and order.

In any case, Orwell's prediction from his book '1984' may already be fulfilled – *There was of course no way of knowing whether you were being watched at any given moment; it was conceivable that they watched everybody all the time.*

Old news?

Spying on motorists goes back a lot further than most people would imagine. Doubtless few Automobile Association members are aware that their organisation's origins lie in a club that posted 'scouts' on main roads to warn motorists of speed traps back in 1905.

Setting that aside and confining our attention to electronic surveillance, the first introduction of CCTV for road traffic control was in Durham back in 1959 – a world first. The installation was by Pye of Cambridge, by the way.


By 1970, wide-area computerised traffic control with traffic signals linked to sensors in the roadway had been introduced in major British cities, enhanced with CCTV for visual observation of traffic flows.

Use of these cameras for surveillance of individual vehicles – and persons – dawned a little later. It was in the early 1980s that CCTV cameras were first linked to computers specifically for scanning and capturing vehicle registration numbers. The first experimental installations were on a bridge overlooking the M1 motorway in Hertfordshire near Junction 9 and at the Dartford Tunnel. While the latter's stated purpose was to catch stolen or suspect vehicles, it

Honey pot for perverts

"The cameras are already intruding into our private lives. Diana Sampson, who monitors CCTV for the London Borough of Sutton says, 'I know for a fact that one leisure centre has cameras in its women's changing room, monitored by men and they can do anything with those tapes.' CCTV is a honey pot for perverts.

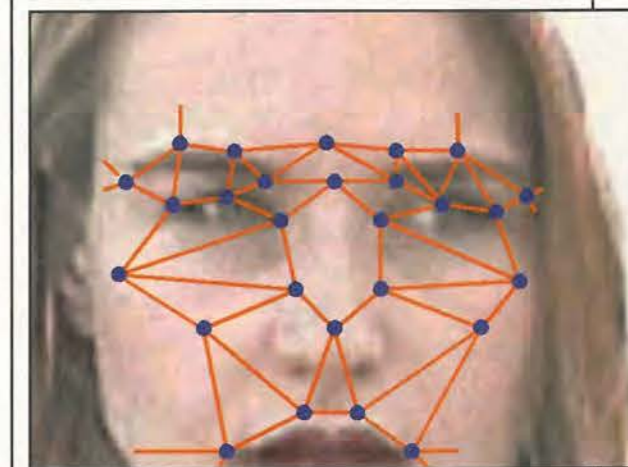One camera operator in Mid Glamorgan has been convicted on more than 200 counts of using cameras to spy on women, and making obscene phone calls from the control room." www.videonetwork.org



How faces are recognised

Fundamental to any face recognition system is the way in which faces are coded. Visionics' Facelt uses Local Feature Analysis, or LFA, to represent facial images in terms of local statistically derived building blocks.

LFA is a mathematical technique based on the realisation that all facial images – or for that matter all complex patterns – can be synthesised from an irreducible set of building elements.

These elements are derived from a representative ensemble of faces using sophisticated statistical techniques. They span multiple pixels – but are still local – and represent universal facial shapes, but are not exactly the commonly known facial features. In fact, there are many more facial building elements than there are facial parts.

However, it turns out that synthesising a given facial image to a high degree of precision requires only a small subset – 12-40 characteristic elements – of the total available set.

Identity is determined not only by which elements are characteristic, but also by the manner in which they are geometrically combined – i.e. their relative positions. In this manner Facelt maps an individual's identity into a complex mathematical formula that can be matched and compared to others.

proved of great value for monitoring the movements of striking coal miners travelling north from Kent during the pit strike of 1984/85.

Public surveillance systems have grown considerably in sophistication, coverage and geographical extent since then. Roadways are no longer the sole targets of coverage. In many towns and cities entirely separate networks have been established for road

Continued on page 525...

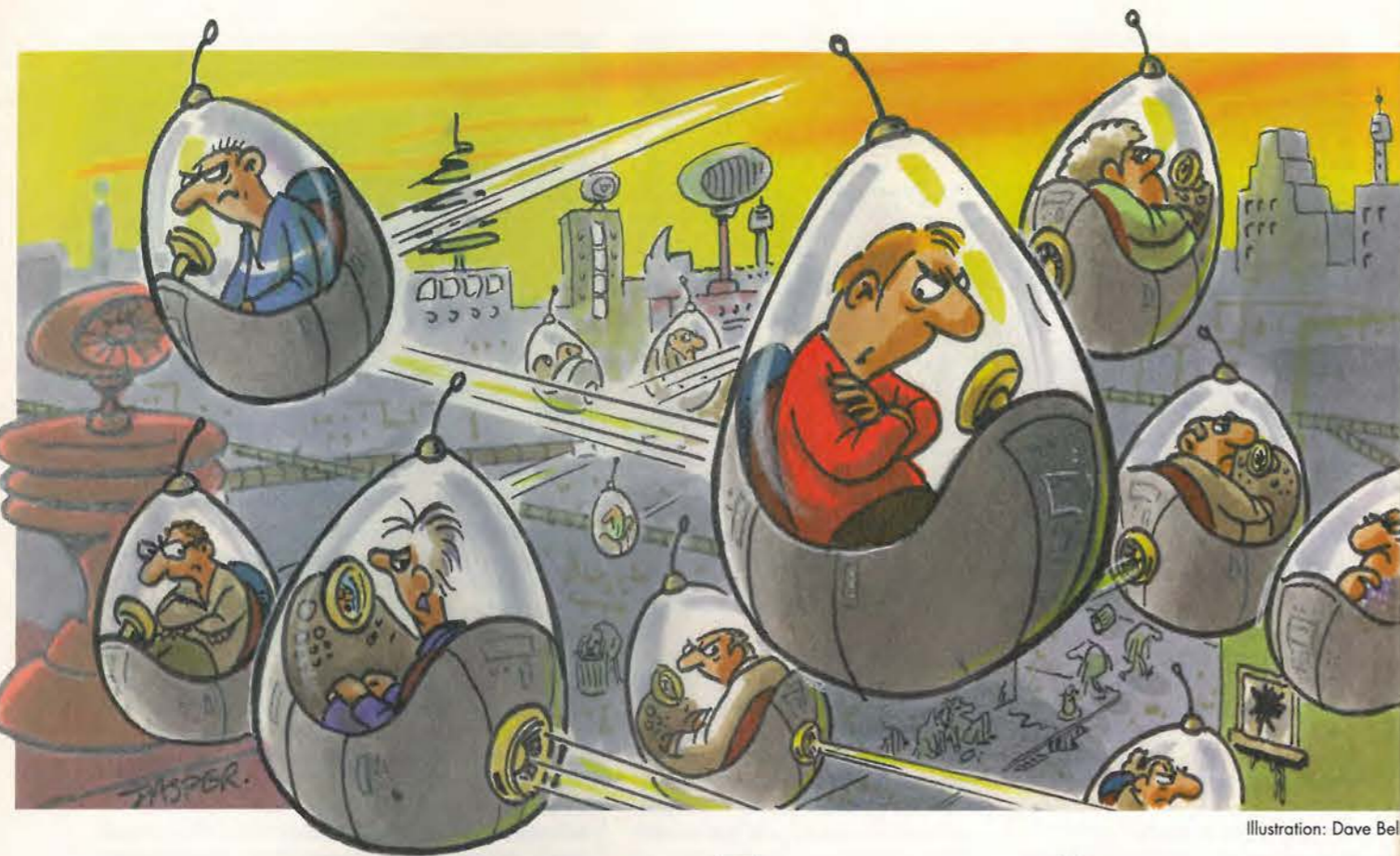


Illustration: Dave Bell

e-prophecies

So the revolution in communications has enhanced all our lives has it? Not necessarily so. It could lead to a breakdown in society. Melanie Reynolds explains.

Hollywood has always had a penchant for portraying future civilisation as being a mad, bad, dangerous place to be. Just consider 'The Terminator' and 'Mad Max'.

The movies always seem dark, portraying an existence full of menace where the fight is for survival. But it is, after all, just the movies we think. It will never really be like that. But could it be?

The advance of technology is

usually regarded as improving the quality of our lives, but what if it is a catalyst for the deterioration of it instead? Technology does have the capability to increase the gap between the haves and the have-nots that already exists and with the increasing divide comes trouble – for all of us.

With the breakdown in relationships and family life, and the rise in single person households, the way we live our lives is already changing. Adding the buffer zone effect that communications technology can bring to this change gives you a society where people are isolated and personal interaction is made more difficult.

As society becomes more insular, the social pressures that tend to limit anti-social behaviour will be eroded, leading to a breakdown in society and perhaps the post-apocalyptic world of the movies will seem a bit too close for comfort.

Maybe this scenario seems a bit far-

fetched and we will never live in a 'Mad Max' world, but it is a possibility the government is considering in a consultation paper called 'Just Around the Corner' by the DTI's Foresight crime prevention panel.

The report is seeking to provoke people into thinking about the next 20 years where society has evolved along these lines and crime and crime prevention are more technology based.

One of its theories is that technology allows people to choose to be isolated in public places. You can already see this happening with people using mobile phones.

Although surrounded by others they are detached from the environment and even from their immediate group.

Where meetings would once be social and static, the progress of technology means they can now be personal and mobile, meaning people have a greater choice about who they

meet and how. The down side of this means there is less social interaction.

The report says this could result in physical society becoming a more hostile place which people pass through and do not interact with. In this dehumanised environment, people seem less real to each other, which leads to 'more extreme reactions, interactions and a reluctance to intervene in conflict' when they happen.

Although technology will empower people, it could also further divide society into those who have the technology and those who do not. This technologically devoid underclass would have limited access to mainstream society and be a breeding ground for dissent and crime.

The Foresight report offers extreme scenarios of the future as food for thought. One involves us aspiring to live in safe ghettos, where we view strangers with suspicion and feel deeply unsafe when we venture beyond the walls. The outside world is full of danger – the result of the division of society

Crime in the e-world

Technology will result in crime taking on a different face. The theft of physical property could pretty much be stopped by technology, for example, by electronic tagging or by tying the operation of an item to an individual or a location. The item then has no value to a thief.

However, if property has no value, that does not mean crime will go away. Technology will be the facilitator of crimes instead.

Fraud is one crime ideally suited to the Internet. It could simply be for financial gain or to get information to facilitate this. False websites could record credit card details or personal and financial details which could be used for identity theft – identity and the way we prove it will become increasingly important in the future.

As individuals become more adept at using the technology, but less knowledgeable about how it works, there is a danger of being at the mercy of a small knowledgeable elite and those criminals without the knowledge may turn to violence or disorder.

The Internet being global also means that crime can go global, making traditional law enforcement unsuitable for policing it.

The speed at which technology crimes can be committed also makes catching the culprits far harder. To stand any chance against the criminals, the police will have to acquire suitable skills.



due in part to technology.

It all sounds pretty dire. But, although technology will undoubtedly change our lives it does not have to change things for the worse. The

answer lies with us and how we choose to manage the technology.

Being aware of what can go wrong is half the battle in preventing it from happening. ■

Behind big brother

...continued from page 523

traffic observation on one hand and for crowd and security control on the other.

The trigger for security surveillance was the terrorist threat; in 1994 a network of more than 100 street cameras were installed in the City of London for anti-terrorist surveillance purposes. Installations established since then have targeted theft and public disorder in shopping centres, car parks and in the streets at large.

Northampton: CCTV centre of excellence

Unlikely as it may sound, the otherwise unexceptional Midlands town of Northampton is the most densely surveyed town of Britain. Its streets and car parks are scanned by 200 cameras – rising to 250 within 12 months – outnumbering those of any other town in Britain and making it the largest urban system outside London.

Car park cameras are interfaced to the Police National Computer for detecting stolen or wanted vehicles. Public reaction is positive – the system is responsible for an average of 100 arrests a month. And study teams have come from the USA, Canada and

Italy to see this remarkable centre of CCTV excellence.

CCTV evidence is legally conclusive

Legal history was made in March of this year when confirmation was given that digital CCTV recordings had provided the crucial evidence that secured the conviction of three killers. The case concerned Bradley Bolton, murdered in July 1999 in High Wycombe town centre. This is one of the first times that footage from a local authority-run digital CCTV system has been used as evidence in a major prosecution case.

Wycombe District Council installed the equipment from NiceVision in 1998 to record a number of public areas. Detective Inspector Ashley Smith, who led the murder investigation, commented, "CCTV recordings are a crucial weapon in criminal investigation, and we always view them immediately whenever they are available. These digital CCTV recordings provided excellent evidence and some of the clearest CCTV images we have seen. They allowed the jury to have clear sight of the incident itself,

providing a brutal, yet conclusive picture of the event."

The government's view on CCTV

CCTV works as an effective crime reduction and detection tool – particularly when used as part of a wider crime reduction strategy. It has helped to reduce crime in many parts of the country and the current CCTV initiative will bring the benefits of CCTV to a wider community.

Under the Crime Reduction Programme, some £153million is available for schemes in England and Wales for the period up to March 2002, with another £17 million available for Scotland and Northern Ireland. Initial priorities are tackling crime problems in housing areas and measures to improve the security of public car parks.

Closed-circuit tv must also retain public confidence, operating under detailed codes of practice to protect individual rights to privacy and adhere to the principles of the Data Protection Act 1998. It must also meet the requirements of the Human Rights Act 1998. ■

Beginners' corner

Ian Hickman has produced a number of circuits for electronics undergraduates – or anyone – to build, troubleshoot and test. Biased towards rf applications, the circuits become gradually more complex and are chosen to be interesting, as well as instructive. This month's circuit is simple and suitable for those with little or no prior experience of constructing and trouble-shooting hardware. Apart from the components themselves, all that is needed is a dual power supply or batteries, and an oscilloscope – the electronic engineer's magic lantern.

This month's project is an audio oscillator. Oscillators of one sort or another are key components in so many electronic applications, from PCs to mobile 'phones to a simple superhet radio such as the humble pocket 'trannie'. Traditionally, an oscillator used a single active device, such as a single transistor, or in earlier times, a valve.

The following circuit uses an operational amplifier or 'op-amp', resulting in an audio oscillator of good performance but low circuit complexity. A typical op-amp contains a dozen or more transistors, plus a handful of other components such as resistors and the odd capacitor, all implemented in the same tiny slice of silicon.

With semiconductor manufacture and testing so highly automated, an op-amp, while still more expensive than a single transistor, really costs very little. And four op-amps in a

'quad' package cost little, if any, more than four individual transistors.

The integrated circuit

Op-amps were produced originally as modules built up from discrete components. The first readily available integrated circuit op-amp was the 709, produced in bipolar technology.

I remember pouncing on it with glee in the 1960s, when it first became available. It provided me with a replacement for a discrete op-amp, in a 75Ω, 140Ω and 600Ω standard milliwatt test set I had designed and that was bought by the Post Office in large quantities.

Subsequently, the IC became avail-

able from many manufacturers as the LM709, the μA709, and various other type numbers. It was widely used, despite various shortcomings, such as its tendency to 'latch-up'.

With this device, the sign of the gain reverses if the limited common-mode input voltage range is exceeded, turning negative feedback into positive! The later 741 op-amp was also bipolar, but unlike the 709 was latch-up free, making it very useful. It was also internally compensated for unity gain, unlike the 709. This was useful, but non-optimum for use at higher gains.

Later still, CMOS devices, such as the CA3130 and others, became available, offering very much higher input

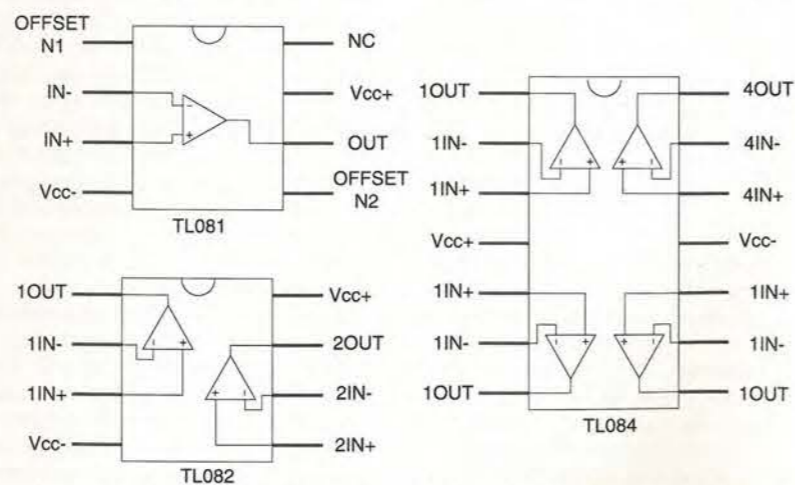


Fig. 1. Showing the pin connections of the TL08x series op-amps. Most op-amps will suffice in this application, and most op-amps have the same pin-out as the TL08x series.

Op-amp alternatives

This circuit was designed to use a TL084 JFET-input quad op-amp integrated circuits, but the TL081 single op-amp version, or the TL082 dual op-amp would do equally well. Pin connections of all three are shown in Fig. 1; there is even a TL084x2 octal op-amp in a 30-pin package, though I have never actually seen one.

The connections shown are almost universally standard for singles, duals and quads, and almost any internally compensated op-amp, from the 741 onwards, should work in this circuit.

resistance than bipolar types.

The circuit described below was used as one of the mini-projects for the RF Club mentioned in an earlier article.

How the circuit works

The following describes how the circuit works. But you may want to get started straight away, build the circuit and get it working before reading further. That's fine, but I hope that at some point, you will take the trouble to understand just what makes it all work.

And you might find you need to understand, in order to help you trouble-shoot your circuit if it doesn't work. Even if it works first time, you should still want to know just how, for such is the inquisitive nature of an innovative circuit designer.

Figure 2 shows the Wien bridge, invented not surprisingly by a certain Herr Wien. Mr Vienna's bridge was designed not for making audio oscillators, but for measuring audio frequencies, in the days before frequency counters.

At the frequency f Hz, where the reactance of C in ohms, is numerically equal to the resistance R , the voltage across the earpiece detector is zero. Adjusting the value of the two resistors, R , keeping them always equal, thus gives a null at the frequency where $f=1/(2\pi CR)$. How this comes about is explained in a little more detail later on.

Figure 3 shows the circuit of an audio oscillator based on the Wien bridge. With the component values shown, it produces a sine wave output of 1.59kHz. This frequency is nominal, the actual value depending upon the tolerances of the components.

Typical tolerance values are $\pm 1\%$ for metal film resistors, $\pm 2\%$ or $\pm 5\%$ for carbon film types. But for capacitors, $\pm 1\%$ tolerance is rare and usually only available in polystyrene- or mica-dielectric capacitors. A tolerance of $\pm 5\%$, $\pm 10\%$ or $\pm 20\%$ is more typical for the common metallised film types, and worse still for electrolytics.

The circuit oscillates because there is positive feedback from the output, in the form of a potential divider network. The upper arm of this network consists of a resistor and a capacitor in series, and the lower arm of a resistor and a capacitor in parallel.

Analysing the circuit

Figure 4 shows the relationship between the voltages across the arms and the current through the components, at the frequency where the reactance of $1nF$, in ohms, is numerically equal to the resistance $100k\Omega$.

At this frequency, the voltage drop across C_2 must numerically equal that across R_2 . But whereas the drop across the resistor is in phase with the current, the voltage drop across C_2 will lag the current through it – and the voltage across R_1 – by 90° .

The impedance of the R_2+C_2 series arm will be the sum of the resistance and the reactance. Although these have the same magnitude, being in quadrature, they must be added root sum of squares-wise (RSS), giving the value $141.4k\Omega$, i.e. $100k\Omega \times \sqrt{2}$.

For the C_1/R_1 parallel arm, the admittance is given by RSS adding the conductance and susceptance, here both equal to $1/100k\Omega$. Converting the answer back to impedance gives $70.7k\Omega$, or just half that of the series arm. So, since the same total current flows through each arm, the voltage drop across the shunt arm is just half

that across the series arm.

Furthermore, since both arms present a phase angle of 45° , the voltage at their junction will be in phase with the applied voltage. Thus assuming there is a sine wave of 1.59kHz at the op-


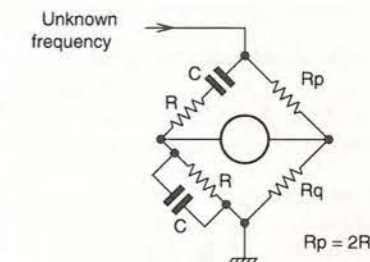


Fig. 2. The Wien bridge is at the heart of this design, but it was originally invented for measuring audio frequencies. Source and detector may be interchanged.

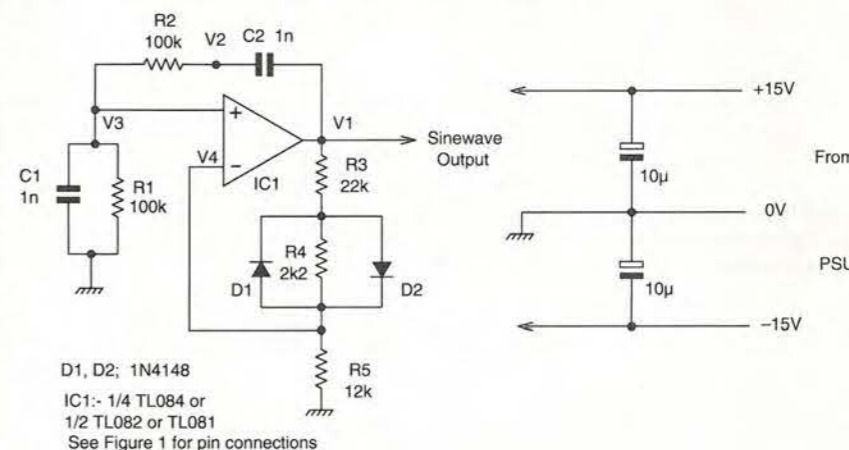

D1, D2: 1N4148
IC1: 1/4 TL084 or 1/2 TL082 or TL081
See Figure 1 for pin connections

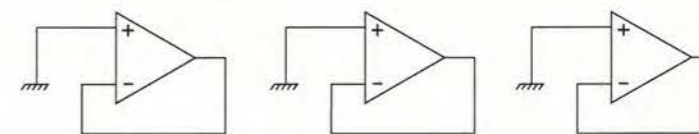


Fig. 3. An audio frequency oscillator circuit together with power supply decoupling, top right, and wiring for the unused sections of a quad op-amp.

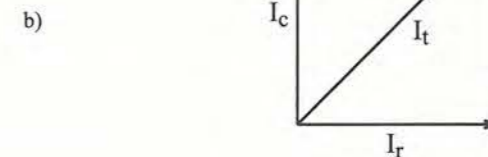
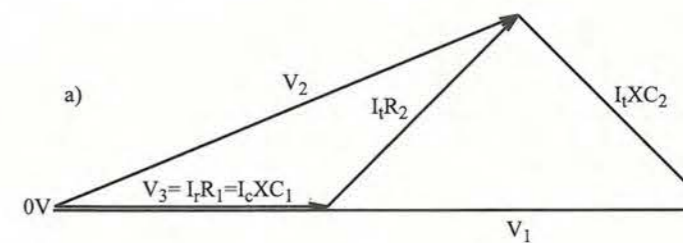


Fig. 4. Vector diagram showing the currents and voltages in the frequency determining arm of the circuit, Fig. 3.

amp's output, there will be a one third size replica at its non-inverting input. All this is actually much clearer from Fig. 4.

An alternative safe start-up method

If the PSU does not have an adjustable current limit, and like some units, is not adjustable right down to zero output voltage, an alternative strategy can be used.

Simply connect a 470Ω resistor in series with the +15V supply lead, and similarly for the -15V supply. The circuit should draw not more than about 12mA if using a TL084, or a half or quarter of this if using a dual or single op-amp. Use 1kΩ resistors for a dual, 1.8kΩ for a single op-amp. If the current drawn is as expected, the resistors can then be removed.

Creating a vector diagram

When drawing a vector diagram such as Fig. 4, to analyse the action of a circuit, the secret is to start at the right place.

In this case, V_1 is definitely the wrong place. Start with a voltage that is simply related to 0V ground, in this case, V_3 in Fig. 4a). Immediately, the currents I_r and I_c through R_1 and C_1 can be marked in, as in 4b), giving also the total current I_t . This flows through R_2 and C_2 , so the voltage drop $I_r R_2$ across R_2 and $I_t X_{C_2}$ across C_2 - where X_{C_2} is the reactance of C_2 at f Hz, namely,

$$\frac{1}{2\pi f C_2} = R$$

can now be marked in, in 4a).

The vector sum of these three voltage drops equals V_1 , which has been

shown slightly offset in 4a), for clarity. You can see that while V_1 and V_3 are in phase, a little third- $^{\circ}$ form geometry shows that V_2 actually leads them by 22.5 $^{\circ}$.

If the resistive potential divider at the op-amp's inverting input also results in a one third size replica there, the signals at the two inputs will be identical, the Wien Bridge is balanced. Thus the op-amp sees only a 'common-mode' input, and op-amps have - ideally - zero response to common mode inputs.

If however the voltage at the non-inverting input is slightly less than a third of that at the op-amp's output, then there is a net input in phase with the output. In view of the op-amp's very large gain, this is more than enough to produce an output at the said frequency.

where the voltage drop across R_4 , and hence across the diodes, reaches something like 600mV. Thus the diodes start to conduct, one on each alternate polarity swing.

When the diodes conduct, their low incremental or 'slope' resistance effectively shorts out R_4 . Thus for part of each half cycle, the resistive arm attenuation factor becomes approximately,

$$\frac{22k\Omega + 12k\Omega}{12k\Omega}$$

which is 2.833. Now, the negative feedback exceeds the positive, and the amplitude of the oscillation cannot build up much further. In fact, the amplitude will settle at that level where the negative feedback attenuation at the fundamental frequency component of the output is very close to, but marginally greater than three, averaged over the course of a complete cycle.

Note that the attenuation is only as low as a factor of 3 at the frequency f Hz. At this point, the reactance of C_1 , C_2 equals the resistance R_1 , R_2 , namely where,

$$\frac{1}{2\pi f C} = R$$

It increases as you move away from f , either up or down in frequency. In fact, the attenuation of the $R_1 C_1 R_2 C_2$ arm is infinite at 0Hz, due to C_2 , and also at infinite frequency, due to C_1 . So with the attenuation to the inverting input marginally in excess of 3, f is the only frequency at which the circuit can possibly oscillate.

The circuit is thus a 'slightly-out-of-balance' Wien bridge, the out of balance voltage being amplified for driving the input to the bridge.

Now try making one...

The circuit can be built up in various ways. A scrap of 0.1 inch matrix copper strip-board, cut from RS stock number 433-595 or 433-602 can be used; the same material, in different size sheets, is available from all the usual electronic components catalogues. Alternatively, you can produce a dedicated printed circuit board, assuming you have the necessary facilities.

But probably the most convenient way is to make the circuit up on 0.1in matrix plug-type prototyping board, after the style of RS 488-618 or 488-933. This has the advantage that the component leads do not need to be cut. They can therefore be straightened out again after use, and the components returned to stock to live another day.

With a circuit operating at low fre-

quencies such as this, layout is completely unimportant, and component leads can be simply bent as required, to plug in wherever convenient.

...and getting it to work

The circuit may not work first time, due to an accidental misconnection, and this could conceivably damage the IC. The first-time power-up can be safely achieved in various ways. For example, a twin power supply unit, or PSU, having an output voltage adjustable right down to zero, and an adjustable current limit is ideal.

First select output tracking - also called master/slave operation - where a single knob controls both the +15V and the -15V output with the prototype circuit disconnected.

Now set the variable current-limit control to minimum, fully anticlockwise. This will cause the output voltage to collapse to zero.

The circuit is then connected and the PSU's output switched on, advancing the current limit control cautiously while keeping a close eye on the current meter. If the current does not exceed the expected ten milliamps or so as the voltage rises to the preset $\pm 15V$ levels, then all is well.

Even if the circuit is not actually working, at least it is safe to leave on while trouble-shooting. If on the other hand, the current increases alarmingly while the supply voltage is still only a volt or so, it is wise to switch off and recheck the circuit.

If you don't have a suitable power supply, then use the procedure outlined in the separate panel entitled, 'An alternative safe start-up method'.

And if it doesn't

An oscilloscope should reveal a sinewave at about 1600Hz, centred about 0V ground, at the output of the section of the TL084 op-amp in use.

If the dc or average level at the output is not 0V - if it is 'stuck high' or 'low' at near supply rail level - then the circuit is probably wrongly connected. Alternatively, the op-amp is dud, but this is exceedingly unlikely if the device is new.

If the dc level is 0V, but there is no oscillation, then either there is a misconnection, or component tolerances have conspired to result in more negative feedback than positive.

The resistors should preferably be 1% metal film types. Even so, in the worst case, the resistive arm attenuation could be less than 3:1. Swapping over C_1 and C_2 may do the trick; if not then it will be necessary to connect a high value resistor of around 100kΩ in

parallel with R_5 . The resistor's value can then be increased until the output amplitude is, say, 10V peak-to-peak.

On the other hand, should the oscillation build up to nearly 30V peak-to-peak, with the peaks clipped, then a high value resistor should be connected in parallel with R_3 .

Add-ons

When using a TL084, it is good practice to look after any unused sections properly, as indicated in Fig. 3.

But once you have got the oscillator section working, the spare sections can usefully be employed in one or two extensions to the circuit.

Such enhancements are shown in Fig. 5, and include a squarewave output stage, and a buffered passive integrator giving a triangular output.

The triangular wave provided by this is only an approximation to the ideal, albeit a good one. But this arrangement does not have the disadvantage of an active integrator - namely a propensity to integrate any offset or asymmetry, resulting in its output becoming stuck at one or other supply rail.

A stage providing a variable output voltage at 600Ω output impedance completes the design. ■



In this series

As explained in a preliminary article in the May 2000 issue, this series is intended to help students - and anyone interested in getting to grips with RF design - a background in practical electronic circuitry and troubleshooting.

The series was originally developed as a response to the government's RF Engineering Education Initiative. Below is a list of the two tutorials that have already appeared, together with my plans for future articles in the series - 'Beginners' corner'.

- 1 Timer circuit using the 555, June issue
- 2 Audio oscillator - Wien bridge based, this issue
- 3 h_{fe} tester
- 4 Radio-frequency oscillator, Colpitts type
- 5 Audio frequency filter/oscillator - state variable based
- 6 Capacitance meter
- 7 Radio-frequency oscillator/receiver involving negative resistance

Fig. 5. Spare op-amp sections can be used to produce a variety of other waveforms.

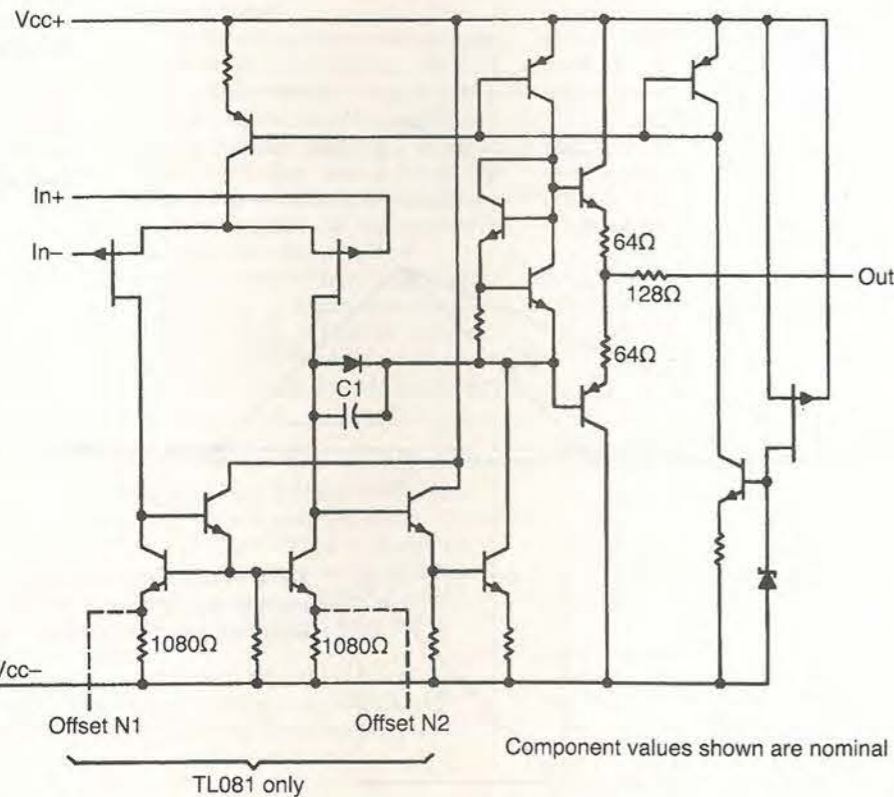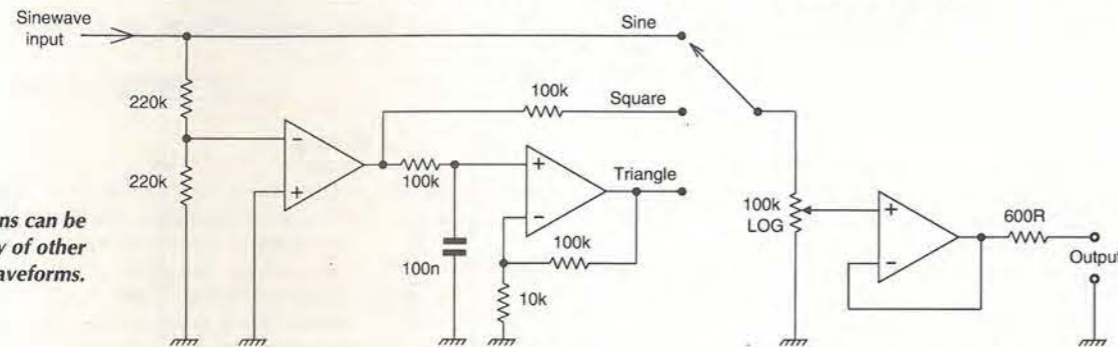

The trick therefore, to provide just enough net drive to give a modest, stable value of output voltage, is to make the attenuation of the resistive arm adjust itself to a value marginally in excess of $\times 3$.

When the circuit is first switched on, before it has a chance to start oscillating, the resistive arm attenuation factor is,

$$\frac{22k\Omega + 2.2k\Omega + 12k\Omega}{12k\Omega}$$

which is 3.0167. Thus the positive feedback exceeds the negative, and the circuit will start to oscillate. But as the oscillation builds up, a point is reached

Fig. 6. The long-established and widely used TL081/82/84 series op-amps feature very low input bias and offset currents, thanks to their P-channel JFET input stages. A bipolar output stage contributes high drive capability and the overall design, shown here, results in a 13V/ms slew rate and a total harmonic distortion figure of just 0.003%. (Reproduced courtesy of Texas Instruments)

Visit our website
www.distel.co.uk

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND &
VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 mHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**
See www.distel.co.uk/data_my00.htm for picture & full details

FLOPPY DISK DRIVES 2 1/2" - 8"

All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 unlisted drives for spares or repair.

3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only	£25.95(B)
3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop	£18.95(B)
5 1/4" Teac FD-55GFR 1.2 Meg (for IBM pc's) RFE	£18.95(B)
5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE	£29.95(B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95(B)
Table top case with integral PSU for HH 5 1/4" Floppy / HD	£29.95(B)
8" Shugart 800/801 8" SS refurbished & tested	£210.00(E)
8" Shugart 810 8" SS HH Brand New	£195.00(E)
8" Shugart 851 8" double sided refurbished & tested	£260.00(E)
8" Mitsubishi M2894-63 double sided NEW	£295.00(E)
8" Mitsubishi M2896-63-02U DS slimline NEW	£295.00(E)
Dual 8" cased drives with integral power supply 2 Mb	£499.00(E)

HARD DISK DRIVES 2 1/2" - 14"

2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H)	New £79.95
2 1/2" TOSHIBA MK2101MAN 2.16 Gb laptop (19 mm H)	New £89.50
2 1/2" TOSHIBA MK4309MAT 4.3Gb laptop (8.2 mm H)	New £105.00
2 1/2" TOSHIBA MK6409MAV 3.1Gb laptop (12.7 mm H)	New £190.00
2 1/2" to 3 1/2" conversion kit for Pc's, complete with connectors	£14.95
3 1/2" FUJIK FK-309-26 20mb MFM I/F RFE	£59.95
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE	£59.95
3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE	£69.00
3 1/2" QUANTUM 40S Prodriv ve 42mb SCSI I/F, New RFE	£49.00
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE	£49.95
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95
5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested	£69.95
5 1/4" HP 97548 850 Mb SCSI RFE tested	£99.00
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested	£195.00
8" NEC D2246 85 Mb SMD I/F Refurb New	£195.00
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00
8" FUJITSU M2392K 2 Gb SMD I/F RFE tested	£345.00

Many other drives in stock - Shipping on all drives is code (C1)

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

MITS. FA3445ETKL 14" Industrial spec SVGA monitors	£245
FARNELL 0-60V DC @ 50 Amps, bench Power Supplies	£995
FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply	£1850
1kW to 400 kW - 400 Hz 3 phase power sources - ex stock	EPOA
IBM 8230 Type 1, Token ring base unit driver	£760
Wayne Kerr RA200 Audio frequency response analyser	£2500
IBM 53F5501 Token Ring ICS 20 port fibre modules	£795
IBM MAU Token ring distribution panel 8228-23-5050N	£995
AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE	£550
ALLGON 8360.11805-1880 MHz hybrid power combiners	£250
Trend DSA 274 Data Analyser with G703(2M) 64 I/O	EPOA
Marconi 6310 Programmable 2 to 22 GHz sweep generator	£6500
Marconi 2022C 10KHz-1GHz RF signal generator	£1550
Marconi 2030 opt 03 10KHz-1.3 GHz signal generator, New	£4995
HP1650B Logic Analyser	£3750
HP3781A Pattern generator & HP3782A Error Detector	EPOA
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts	£1800
HP6264 Rack mount variable 0-20V @ 20A metered PSU	£675
HP54121A DC to 22 GHz four channel test set	EPOA
HP8130A opt 020 300 MHz pulse generator, GPIB etc	£7900
HP A1, A0 8 pen HPGL high speed drum plotters - from	£550
HP DRAFTMASTER 1 8 pen high speed plotter	£750
EG-G Brookdeal 9503C Precision lock in amp	£800
Viewing Mod 1200 computerised inspection microscope	EPOA
Sony DXC-3000A High quality CCD colour TV camera	£995
Keithley 590 CV capacitor / voltage analyser	EPOA
Riscal ICRA40 dual 40 channel video recorder system	£3750
Fascals 45KVA 3 ph On Line UPS - New batteries	£9500
Emerson AP130 2.5KVA industrial spec UPS	£2100
Mann Tally MT645 High speed line printer	£2200
Intel SBC 486/133SE Multibus 486 system, 8Mb Ram	£945
Siemens K4400 64Kb to 140Mb demux analyser	£2950

DISTEL on the web !! - Over 16,000,000 items from stock - www.distel.co.uk



ALL MAIL TO
Dept ww, 29/35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5.30

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath &
Selhurst Park SR Rail Stations

NEW DISTEL
Visit our web site
www.distel.co.uk
email = admin@distel.co.uk

ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges: (A)=£3.00, (At)=£4.00, (B)=£5.50, (C)=£8.50, (C1)=£12.50, (D)=£15.00, (E)=£18.00, (F)=£20.00, (G)=CALL. Allow approx 5 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 1999. E & O.E. 07/99.



CIRCLE NO. 111 ON REPLY CARD

IC's - TRANSISTORS - DIODES

OBsolete - SHORT SUPPLY - BULK
10,000,000 items EX STOCK
For MAJOR SAVINGS
CALL OR SEE OUR WEB SITE www.distel.co.uk
VIDEO MONITOR SPECIALS

One of the highest specification
monitors you will ever see -
At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPPR specification. Fully guaranteed, in EXCELLENT little

used condition.
Tilt & Swivel Base £475
VGA cable for IBM PC included.
External cables for other types of computers available - CALL

Only £119 (E) Order as MITS-SVGA
Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multisync etc.
Full 90 day guarantee. Only £199.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for Info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 3/4" x 15 1/2" D.
Only £99.00 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.
Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 KHz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.
Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive test style case. Perfect for Schools, Shops, Disco, Clubs, etc. in EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)
We probably have the largest range of video monitors in Europe. All sizes and types from 4" to 42" call for info.

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock
Call or see our web site.

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting, plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:
OPT Rack 1 Complete with removable side panels. £345.00 (G)
OPT Rack 2 Rack, Less side panels. £245.00 (G)

Over 1000 racks, shelves, accessories
19" 22" & 24" wide 3 to 46 U high.
Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)

Sold at LESS than a third of makers price !!
A superb buy at only £245.00 (G)
42U version of the above only £345 - CALL

12V BATTERY SCOOP - 60% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12V DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SBS15 featuring pure lead plates which offer a far superior life & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each.
Our Price £35 each (C) or 4 for £99 (E)

RELAYS - 200,000 FROM STOCK

Save EEEE's by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Watted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save EEEE's

COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available.
Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc, etc.
Web ref = LK33 ONLY £99.00 or 2 for £180.00 (E)

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (E)
ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95
DOS 5.0 on 3 1/2" disks with concise books c/w QBasic. £14.95
Windows for Workgroups 3.11+ Dos 6.22 on 3.5" disks £55.00
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
shipping charges for software is code B



Tini Java

Java expert Les Hughes has been experimenting with a tiny controller designed for Internet connection. Although very low cost, this controller is a complete computer with Internet, network and serial i/o capabilities, giving it huge potential for remote i/o and telemetry applications.

Much noise has been made concerning Java. Although originally conceived as a technology capable of powering embedded systems, it is only recently that Java devices have appeared on the market. One of the most interesting of these is the Tiny InterNet Interface - or TINi - from Dallas Semiconductors.

custom i/o. That's quite a few features for a device that is no bigger than a normal PC SIMM and only costs \$50.00!

Les is a Technical Architect with Rubus.com - a fast growing e-Business Consultancy, currently working with a number of dot-com clients.

TINI executes a Java Virtual Machine, which in turn executes Java 'bytecodes' - in a similar manner to any other Java platform. However, although TINi runs Java, it is not a hardware implementation of a VM. Instead, the current TINi hardware is based on the Dallas 80C390 micro controller.

Of course, as with any beta product, revisions often occur and APIs and specifications change, based on

Free software

The TINi VM, operating system and various user programs are loaded into flash memory. This enables simple updates, which are freely downloadable from the project web site - www.ibutton.com/TINI.

All of the software required to develop applications for TINi is available free of charge from various Internet sites. Installing and configuring your environment in order to get TINi up and running consists of a number of tasks. Guillaume Fournier's excellent guide at <http://www3.sympatico.ca/guillaume.fournier/> describes in detail the process that you should follow in order to be able to boot your TINi.


describes in detail the process that you should follow in order to be able to boot your TINi.

The current TINi board incorporates a plethora of external interfaces: 10baseT ethernet, Dallas one-wire, I²C and RS232. Besides the processor, the TINi board also contains 512Kbyte of flash memory, 512Kbyte of NVRAM and an RTC. Processor address, data and control busses are brought out to the edge of the board for custom expansion - e.g. memory expansion or

describes in detail the process that you should follow in order to be able to boot your TINi.

describes in detail the process that you should follow in order to be able to boot your TINi.

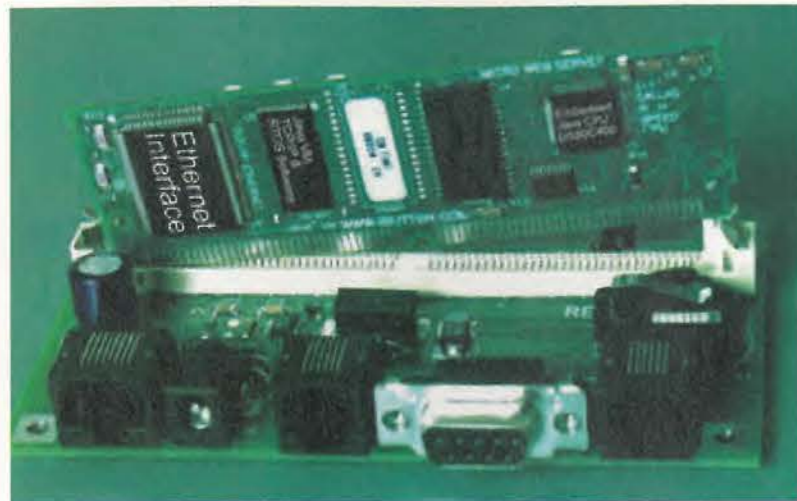user feedback. In a similar manner to open-source software development, TINI has been subject to the input of a large community. This has enhanced the end product in a way that is not possible within a closed environment. Perhaps this open development is the most unusual aspect of the project.



TINI – for around \$50, you get 10baseT ethernet, Dallas one-wire, I²C and RS232 interfaces, a processor, 512Kbyte of flash memory, 512Kbyte of NVRAM and an RTC. At its core is a soft Java virtual machine that's easy to update.

Establishing a network

While it is not actually necessary to network TINI in order to start experimenting, you'll be missing out on the whole idea that makes TINI so special – an embedded network node that runs Java.

Networking hardware has reduced in price dramatically in recent years. Browsing any of the monthly PC magazines shows a whole host of network cards for less than £15.00 and small 'micro' hubs – i.e. those with somewhere between 3 and 10 ports – for less than £30.00.

While it is beyond the scope of this article to delve into the intricacies of network engineering and the selection of networking hardware, we can examine the steps required to establish a simple TCP/IP network at home.

Of course you'll need a network card for your PC. I use a £10 NE2000 clone. Any 10baseT card should do, as long as it's supported by your chosen operating system.

You have two basic hardware options for connecting TINI to your personal computer. You can either use a crossover network cable or buy a small network hub and patch leads.* The crossover network cable has the advantage of being the cheapest but a small network hub offers far greater flexibility for not much more outlay.

Setting up your network

First, you'll need to ensure that you have TCP/IP networking installed for your chosen development platform – but this is the easy part as most systems come pre-configured with this option. If you dial into the Internet, you almost certainly have TCP/IP installed. If not, for a Windows platform, you can add this option in Control Panel -> Network -> Protocols.

Once you have all of the hardware installed and connected, you will need to configure each of the machines on the network with an address. If you use your PC for surfing the net then you should assign a network address from the range 192.168.0.0 to 192.168.255.255. These are from a range of special addresses that, if they 'escape' from your private network onto the Internet, can't cause any damage.

Addresses ending in '.0', '.1' and '.255' should not be used as they have special meaning on the network. For the rest of this article, I'll assume that you've chosen 192.168.0.50 for your PC and 192.168.0.100 for TINI.

Addresses are assigned to PCs in Control Panel -> Network. Find the TCP/IP protocol that maps to your network card – not to your dial-up network adapter! Select properties and then the IP address tab. Enter your chosen IP address in the box provided and 255.255.255.0 into the 'subnet

Getting started with TINI

In order to take full advantage of TINI's network abilities – it is the tiny Internet interface after all – you will need to connect TINI to a LAN. Many home users won't have their own IP network but this need not put you off. The box 'Establishing a network' shows how simple and cheap it is now to 'get wired'.

As has become traditional in the world of computing, our first TINI program is a network server version of the 'Hello World' classic. Groans aside, this simple application serves a number of purposes.

Firstly, the procedure to compile, build and load an application onto TINI is somewhat different from that of a normal Java application. A simple application can help with establishing that all is working correctly before we attempt something more extravagant.

Secondly, the program demonstrates a standard way of writing a multi-threaded network server. Next time, we'll be looking at something far more interesting but until then...

Listing 1 is the source code for our Hello Server. As mentioned, this program simply waits for a network connection, says Hello to the connecting machine, then closes the connection. Most Internet services such as web servers, etc., operate in a similar way.

Back to the example. Since this program uses Java's network and input/output libraries, these are imported at the top of the file. Next, define the name of the application – i.e. HelloServer. The main method forms the entry point to the program; this method is called by the

mask'. You can leave all of the other boxes empty. You can check your settings by using the commands winipcfg on windows 9x and ipconfig on NT.

TINI's IP address is set using the ipconfig command thus:

```
TINI /> ipconfig -a
192.168.0.100
```

You will need to login to your TINI board using JavaKit over a serial line in order to run ipconfig. Of course, you should have installed the firmware and booted TINI first!

Once you have two devices configured on the network, try pinging each one in turn from the other, e.g.,

```
C:\> ping 192.168.0.100
Pinging 192.168.0.100 with 32
bytes of data
Reply from 192.168.0.100:
bytes=32 time<10ms TTL=64
```

```
TINI /> ping 192.168.0.50
Got a reply from node
192.168.0.50/192.168.0.50
Sent 1 request(s), got 1
reply(s)
```

This shows that all's OK between the PC and TINI and vice versa.

*The author means a UTP crossover cable. Note that there are NE2000 clones that only have BNC connectors. Ed.

Java virtual machine when it starts our program.

Our main method defines a `Socket` field called `client`, which is used for incoming connections. However, in order to receive these connect requests from clients, we have to use a 'ServerSocket' to manage the process.

A `ServerSocket` 'binds' to a particular 'port' and listens for connections. When a `ServerSocket` accepts a connect request from a distant client, it passes the connection on, in the form of a `Socket` object, and goes back to listening. In this way, you don't have to wait for a client to finish using the Server program before others can connect.

It's a bit like phoning your bank's call centre. You dial a single number and your call is routed through to any available operator, allowing more calls to come in.

In order to be able to process multiple connections simultaneously, you can take advantage of Java 'threads' and make our server multithreaded. This is what's happening in the statement new

```
HelloServer(client). Our main
method takes the Socket returned by the
ServerSocket and creates a new
HelloServer object to handle the
connection. This object automatically
starts a new thread upon creation and
starts talking to the client.
```

This action can be seen in the constructor methods,

```
serverThread = new
Thread(this);
serverThread.start();
```

method calls.

The `start()` method eventually calls `run()` method. The `run` method first asks the `Socket` for something to write to – the `OutputStream` – and then turns this into something that can be printed to. You then simply print a message to this `Writer`.

Once we've sent our message we wait for a second, to allow you to read the message and then, rather rudely, we close our output channel and the socket, thus cutting off the client before they can respond to our Hello.

Building the application

Once you have entered the `HelloServer` code, you will need to turn it into a format suitable for the TINI.

First, compile the `HelloServer.java` file using,

```
javac -bootclasspath
<TINIPATH>/tiniclasses.jar
HelloServer.java
```

replacing the `<TINIPATH>` tag with the location of your TINI installation, for example, `C:\tini`.

The `-bootclasspath` directive allows the compiler, which is written in Java, to use a different set of core classes (`java.lang`, `java.io`, `java.net`, etc.,) from those compiled into the application. You won't be running under the standard JVM

So what can I do with it?

Interestingly, Tina's manufacturer, Dallas Semiconductor, is still a technology driven company. From the outsider's view – and this is often reflected in Dallas engineers' posts to the TINI mail list – it seems as if the company produces numerous clever solutions just waiting for a problem to come along.

TINI is more than just a rather cool toy though; it is a near-complete implementation of the J2ME platform albeit in pre-production, beta form.

At present, judging from the 'TINI-users' list, real-world TINI applications range from data loggers, security systems and network server monitors to GPS-aware systems and simple dial-up gateways. TINI could be applied in almost any scenario requiring a networked controller; from remote surveillance with an off-the-shelf webcam and wireless LAN technology to home automation using a DS1920 and Tesco Direct to ensure that you always have a good supply of cold beer!

Listing 1. HelloServer.java. This is a simple server that says 'Hello' to any clients.

```
/* HelloServer.java
*/
import java.io.*;
import java.net.*;

public class HelloServer implements Runnable {
    public static void main(String args[]) {
        Socket client;
        try {
            //Create a new server listening on port 1234
            ServerSocket server = new ServerSocket(1234);
            while(true){
                //wait for a call from a client
                client = server.accept();

                //start a new HelloServer for this client
                new HelloServer(client);
            }
        } catch(Exception e) {
            //No error handling - it's only an example ;- )
        }
    }

    Thread serverThread;
    Socket sock;

    public HelloServer(Socket sock) {
        this.sock = sock;
        serverThread = new Thread(this);
        serverThread.start();
    }

    public void run() {
        try {
            //Say hello, wait a bit and then disconnect
            PrintWriter out =
                new PrintWriter(sock.getOutputStream());

            out.println("Hello from Tini!");
            Thread.currentThread().sleep(1000);
            out.close();
            sock.close();
        } catch(Exception e) {
            //No error handling - it's only an example ;- )
        }
    }
}
```

remember; you'll be using the special TINI VM so special core libraries are needed.

This should produce a file called HelloServer.class. Now we need to convert this class file into a .tini file,

```
java -classpath <TINIPATH>\tini.jar
TINIConvertor -f HelloServer.class -o
HelloServer.tini -d
<TINIPATH>\firmware\tini.db
```

again replacing the <TINIPATH> tag with the location of your TINI installation.

This command should produce a HelloServer.tini file. You will now need to FTP this class onto your TINI board. Windows and Linux both include command-line FTP clients, or you might like to use something like CuteFTP. Nearly there! Telnet to your TINI board:

```
C:\>telnet 192.168.0.100
```

(use the standard username root and the password tini)

After logging in, start the HelloServer with the command
java HelloServer.tini &

Now open another telnet window and connect to your TINI on port 1234:

```
C:\>telnet 192.168.0.100 1234
```

TINI should say Hello and then, after a second or so, disconnect you.

Until next time

That's all for now. Next time, I'll be looking at some of the more useful features of TINI, including the various web-enabling technologies available. I will be showing how to hook up the one-wire iButton interface to a web-server, an RS232 terminal and an i/o port to create a simple web-enabled security system.

Resources

- http://www.ibutton.com/TINI
- http://www3.sympatico.ca/guillaume.fournier/
- http://java.sun.com/
- http://www.apms.com.au/tini/

- TINI homepage - hardware, firmware, mail lists etc.
- Excellent 'Getting Started' resource
- Source of all things Java inc. JDK, javax.comm. required for use with TINI
- Another good TINI resource site

BOOK TO BUY


The definitive biography of the century's godfather of invention-from the pre-eminent Edison scholar "Israel's meticulous research and refusal to shy away from the dodgier aspects of Edison's personality offers a fresh glimpse into the life of the inventor."-
New Scientist

"Remarkable."- **Nature**

"An authoritative look into Edison's working methods, here leavened by enough personal detail to give the achievements shape."-**Publishers Weekly**

"Israel's book should go a long way toward taking Edison out of the shadows and placing him in the proper light."-**Atlanta Journal-Constitution**

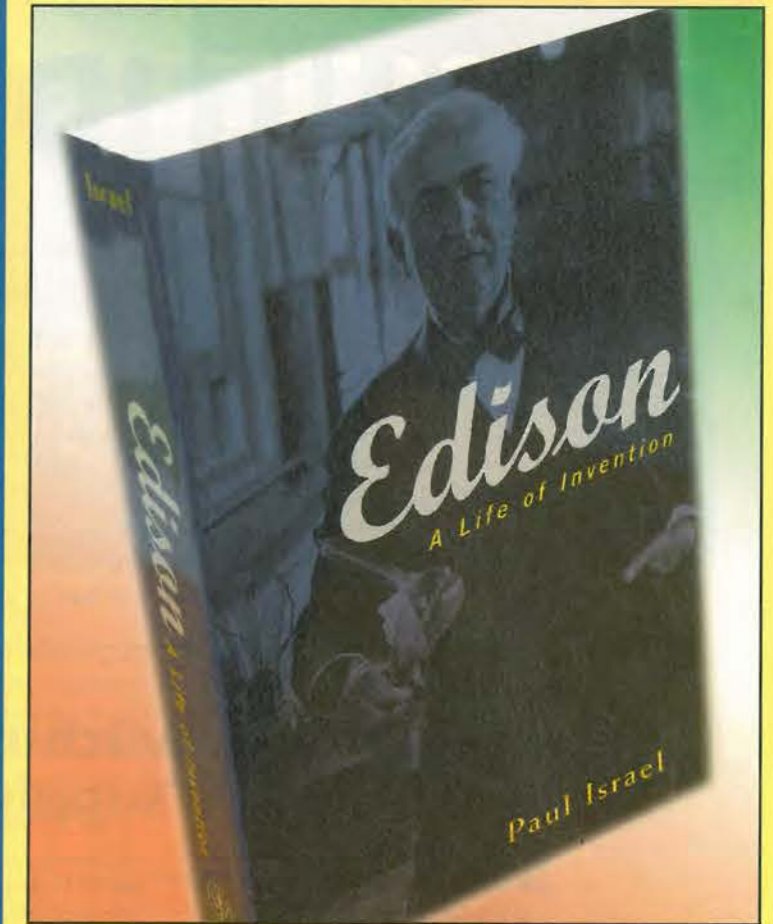"Exhaustively researched, with strong emphasis on Edison's methods and achievements."-**Kirkus Reviews**



Post your completed order form to:-
Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS

Fax your completed order form to 020 8652 8111
UK Price: £15.00 Europe £17.00 ROW £19.00
Price includes delivery

How to pay (Edison) paperback

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card
 Mastercard American Express Visa Diners Club

Credit Card No: _____ Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals) _____

Name _____

Address _____

Post Code _____ Tel: _____

The conventional story of Thomas Edison reads more like myth than history: With only three months of formal education, a hardworking young man overcomes the odds and becomes one of the greatest inventors in history.

But the portrait that emerges from Edison: A Life of Invention reveals a man of genius and astonishing foresight whose career was actually a product of his fast-changing era. In this peerless biography, Paul Israel exposes for the first time the man behind the inventions, expertly situating his subject within a thoroughly realized portrait of a burgeoning country on the brink of massive change. Informed by Israel's unprecedented access to workshop diaries, notebooks, letters, and more than five million pages of archives, this definitive biography brings fresh insights to a singularly influential and triumphant career in science.

SPECIAL OFFERS

TEKTRONIX 2445A
4 Channel 150MHz delay sweep; cursors/ readout
£750

TEKTRONIX 475
Dual Trace 200MHz delay sweep
£400

MARCONI 2610 TRUE RMS VOLTMETER
Digital LCD + analogue meter 5Hz - 25MHz + DC autoranging
£195

AVO 8 Mk 6 MULTIMETER
In Ever Ready case with leads and batteries
£80
Other AVOSs from **£50**

RACAL/AIM 9343M LCR Databridge. Digital. Auto measurements of R, C, L, Q, D.
HUNTRON TRACKER Model 1000. £125
H.P. 5315A Universal Counter 1GHz 2Ch. £80
FLUKE 8050A DMM 4 1/2 digit 2A True RMS. £75
FLUKE 8010A DMM 3 1/2 digit 10A. £50
FLUKE 8012A DMM 3 1/2 digit 2A. £40

RACAL TRUE RMS VOLTMETERS
9300 5Hz-20MHz usable to 60MHz. 10 volts 316V. **£95**
9300B version **£150**

GOODWILL GVT427 DUAL CHANNEL AC MILLIVOLTMETER
10µV 300V in 12 ranges. Frequency 10Hz-1MHz. Used **£100** Unused **£125**

STEWART of READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: (0118) 9268041 Fax: (0118) 9351696
Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

SINAD MEASUREMENTS
for only
MARCONI 893C AF POWER METER
300µ watts-30 watts; 20Hz-35KHz; 2.5 Ohm - 20K Ohms **£60**
Marconi 893C unused, boxed **£100**
Marconi 893B - to 10 watts max. NO SINAD **£30**

GOULD J3B SINE/SQ OSCILLATOR
10Hz-120KHz. Low distortion. Balanced metered output. Attenuator **£75-£125**

SOLARTRON 7150
DMM 6 1/2 digit. TRUE RMS. High accuracy IEE **£95-£150**

HIGH QUALITY RACAL COUNTERS
9904 Universal timer counter 50MHz **£50**
9916 Counter 10Hz-520MHz **£75**
9918 Counter 10Hz-560MHz. 9 digit. **£50**

FARNELL AMM255
Automatic Mod Meter AM/FM 1.5MHz-2GHz 3.5 digit LCD Display. Unused **£400**
Also available:
FARNELL AMM2000 Automatic Mod Meter 10Hz-2.4GHz. Unused **£950**
MARCONI 2305 Mod Meter 500KHz-2GHz from **£750**

MARCONI 2022E SYN AM/FM SIG GEN 10KHz - 1.01GHz
Up to +10dBm output, phase mod, LCD display, keyboard entry etc. Small, lightweight
£525-£600-£750

RADIO COMMUNICATIONS TEST SETS
MARCONI 2555. £2000
MARCONI 2555A. £2500
MARCONI 2019 Synth AM/FM Sig Gen 80KHz-104MHz. £475
H.P. 8657A Synth Sig Gen 100KHz-104MHz. £2500
H.P. 8656B Synth Sig Gen 100KHz-990MHz. £1350
H.P. 8656A Synth Sig Gen 100KHz-990MHz. £965
GIGATRONIC 7100 Synth Sig Gen 10MHz-20GHz. £5000
MARCONI 2017 AM/FM Phase Locked Sig Gen 10KHz-1024MHz. £1200

Good Signal Purity
H.P. 8640A AM/FM Sig Gen 500KHz-1024MHz. £400
H.P. 8640A AM/FM Sig Gen 500KHz-512MHz. £250
PHILIPS PMS328 Sig Gen 100KHz-180MHz with 200MHz Freq Counter IEE. £650

RACAL 9081 Synth AM/FM Sig Gen 5-520MHz. £350
H.P. 3325A Synth Function Gen 21MHz. £600
MARCONI 6500 Amplitude Analyser. £1500
H.P. 4275A LCR Meter 10KHz-10MHz. £2750
H.P. 8903E Distortion Analyser. £750
WAYNE KERR Inductance Analyser 3245. £2000
H.P. 8112A Pulse Generator 50MHz. £1250
DAITRON AutoCal Multimeter 5 1/2-7 1/2 digit. 1065/1061A/ 1071. from £300-£600

MARCONI 2440 Frequency Counter 20GHz. £1000
H.P. 5350B Frequency Counter 20GHz. £2000
H.P. 5342A 10Hz-18GHz Freq Counter. £800
FARNELL AP10030 Power Supply. £1000
FARNELL AP10030 Power Supply. £800
PHILIPS PM5418TV Colour TV Pattern Generator. £1750
PHILIPS PM5418TV Colour TV Pattern Generator. £2000
B&K Accelerometer type 4066. £300
H.P. 11892D Dual Directional Coupler 2MHz-18GHz. £1600
H.P. 11891D Dual Directional Coupler 2MHz-18GHz. £1250
TEKTRONIX P6108B Probe 100MHz Readout. Unused. £90
TEKTRONIX P6106A Probe 250MHz Readout. Unused. £85

SPECTRUM ANALYSERS
H.P. 8562A 1KHz-22GHz. £9000
ADVANTEST R3261A 9KHz-2.6GHz Synthesised. £4000
EATON/AILTECH 757 0.001-22GHz. £2500
TEKTRONIX 492 50KHz-18GHz. £3500
H.P. 8558B with Main frame 100KHz-1500MHz. £1250
H.P. 853A (Dig Frame) with 8559A 100KHz-21GHz. £2750
MARCONI 2382 100Hz-400MHz High Resolution. £2000
B & K 2033R Signal Analyser. £1500
ADVANTEST TR4131 10KHz-3.5GHz. £2750
MARCONI 2370 30Hz-110MHz. from £500
HP141 Systems 8553 1KHz-110MHz. £500
8554 500KHz-1250MHz. £750; 8555 10MHz-18GHz. £1000

UNUSED OSCILLOSCOPES
TEKTRONIX TDS350 Dual Trace 200MHz 1GS/Sec. £1500
TEKTRONIX TAS465 4 Channel 200MHz etc. £1100
H.P. 54600B Dual Trace 100MHz 20MS/s. £1000


OSCILLOSCOPES
PHILIPS PM3092 2-2 Ch 200MHz Delay TB etc. £950
PHILIPS PM3082 2-2 Ch 100MHz Delay etc. £800
TEKTRONIX TAS465 Dual Trace 100MHz Delay etc. £800
TEKTRONIX 2465 4 Ch 300MHz Delay Sweep Cursors. £1250
TEKTRONIX 2430 Dual Trace 150MHz 100MS/s Cursors etc. £800
TEKTRONIX 2232 Dual Trace 100MHz 100MS/s Cursors etc. £900
TEKTRONIX 2212 Dual Trace 60MHz 20MS/s Cursors etc. £650
TEKTRONIX 2210 Dual Trace 50MHz 20MS/s. £450
H.P. 54200A Digitising 50MHz 20MS/s. £600

PHILIPS PM3217 - Very good oscilloscope including 2 probes Pouch and Front Cover **£250-£300**
Dual Trace 50MHz Delay

GOULD OS1100 Dual trace, 30MHz delay, very bright. Supplied with manual and 2 probes. **£200**

USED EQUIPMENT - GUARANTEED. Manuals supplied
This is VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.

CIRCLE NO.112 ON REPLY CARD

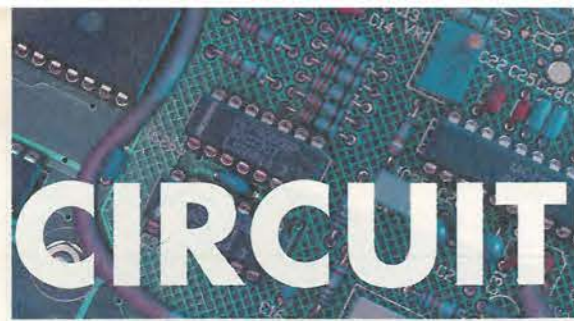

CIRCUIT IDEAS

Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly.

Low-power switch-mode mains power supply

Small mains transformers of about 1W rating tend to run hot and produce a large external hum field. This switching power supply provides an alternative.

Keeping the pulse length very short in the output device allows the use of a low inductance toroid normally found in low voltage

regulators. Obtaining a suitable output is simply a case of winding a few turns of insulated wire over the top of the original winding. Thus this circuit is especially suitable where an output with a very high degree of isolation is required, perhaps up to several kilovolts.

Omitting the high-voltage smoothing capacitor after the bridge rectifier saves one somewhat undesirable component and increases efficiency – although reducing output; however this means the low-voltage outputs will need smoothing to low-frequency standard.

About one watt can be expected with the values shown, but output can be increased to the point where heating of the toroid becomes a problem by increasing the value of the capacitor coupling the Schmidt oscillator to the tripled buffer.


If supplying low power – perhaps

as a built-in battery eliminator or nickel-cadmium battery charger – the circuit can easily be built into a 35mm film container. The 4093 was used because several were to hand. More logical choices might be 40106 or 74C14 hex Schmidt inverters.

A surprisingly small ferrite toroid of the type normally used in supply filters proved perfectly adequate, with a primary of 60 turns and a secondary of 7 turns.

A small load should always be connected to this type of circuit. The original circuit had a second diode in place of the 2mH inductor. If the circuit does not work, reverse the connections from the toroid secondary, as only one way round is correct.

A Ziemacki
Rotherham
C83

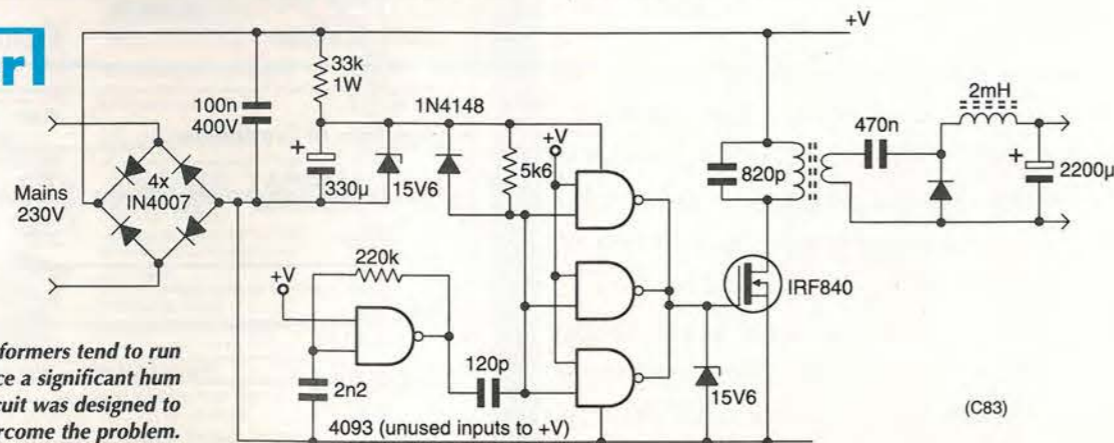

Very small mains transformers tend to run hot, and they produce a significant hum field. This circuit was designed to overcome the problem.

£50 Winner!

Warning

If you are not fully conversant with the requirements for, and practices relating to, designing circuits that connect directly to the mains, do not attempt to replicate this circuit. Explosion, lethal electric shock or fire could result from the simplest of oversights. Ed.

National Instruments sponsors Circuit Ideas

National Instruments is awarding over £3500 worth of equipment for the best circuit ideas.

Once every two months throughout 2000, National Instruments is awarding an NI4050 digital multimeter worth over £500 each for the best circuit idea published over each two-month period. At the end of the 12 months, National is awarding a LabVIEW package worth over £700 to the best circuit idea of the year.*



About National Instruments

National Instruments offers hundreds of software and hardware products for data acquisition and control, data analysis, and presentation. By utilising industry-standard computers, our virtual instrument products empower users in a wide variety of industries to easily automate their test, measurement, and industrial processes at a fraction of the cost of traditional approaches.

Software

Our company is best known for our innovative software products. The National Instruments charter is to offer a software solution for every application, ranging from very simple to very sophisticated. We also span the needs of users, from advanced research to development, production, and service. Our flagship LabVIEW product, with its revolutionary, patented graphical programming technology, continues to be an industry leader. Additional software products, such as LabWindows/CVI, ComponentWorks, Measure and VirtualBench, are chosen by users who prefer C programming, Visual Basic, Excel spreadsheets, and no programming at all, respectively.

Hardware

Our software products are complemented by our broad selection of hardware to connect computers to real-world signals and devices. We manufacture data acquisition hardware for portable, notebook, desktop, and industrial computers. These products, when combined with our software, can directly replace a wide variety of traditional instruments at a fraction of the cost. In 1996 we expanded our high-performance E Series product line in PCI, ISA and PCMCIA form factors, shipped our first VXI data acquisition products, and added remote (long-distance) capabilities to our SCXI signal conditioning and data acquisition product line.

Our virtual instrumentation vision keeps us at the forefront of computer and instrumentation technology. National Instruments staff works actively with industry to promote international technological standards such as IEEE 488, PCMCIA, PCI, VXI plug&play, Windows 95/NT, and the Internet. More importantly, we integrate these technologies into innovative new products for our users.

*All published circuit ideas that are not eligible for the prizes detailed here will earn their authors a minimum of £35 and up to £100.

National Instruments – computer-based measurement and automation

National Instruments, 21 Kingfisher Court, Hambridge Road, Newbury, Berkshire, RG14 5SJ. Tel (01635 523545), Fax (01635) 524395 info.uk@ni.com www.ni.com.

NI4050

The NI 4050 is a full-feature digital multimeter (DMM) for hand-held and notebook computers with a Type II PC Card (PCMCIA) slot. The NI 4050 features accurate 5½ digit DC voltage, true-rms AC voltage, and resistance (ohms) measurements. Its size, weight, and low power consumption make it ideal for portable measurements and data logging with hand-held and notebook computers.

- DC Measurements: 20mV to 250V DC; 20mA to 10A
- AC Measurements: 20mV rms to 250V rms; 20mA rms to 10A rms;
- True rms, 20Hz to 25kHz
- Up to 60 readings/s
- UL Listed
- 5½ Digit Multimeter for PCMCIA

LabVIEW

LabVIEW is a highly productive graphical programming environment that combines easy-to-use graphical development with the flexibility of a powerful programming language. It offers an intuitive environment, tightly integrated with measurement hardware, for engineers and scientists to quickly produce solutions for data acquisition, data analysis, and data presentation.

- Graphical programming development environment
- Rapid application development
- Seamless integration with DAQ, GPIB, RS-232, and VXI
- Full, open network connectivity
- Built-in display and file I/O



£9.99

+ postage & packaging



Please send me _____ copies of The LP is Back!

Name _____

Address _____

Post code _____

Daytime phone number _____

I enclose a cheque for £ _____

Or debit my Visa _____ Master Card _____ (tick one)

Card number _____

Expiry date ____ / ____

Card-holder's signature: _____

Love vinyl?

If you treasure your vinyl collection, this book is for you. Featuring articles from the pages of the US magazine *Audio Amateur* and other sources, it contains absolutely everything the serious LP music collector needs to get the most out of both vintage records and the highest quality new pressings.

Articles feature:

- Cleaning discs
- How to build a cleaning machine
- Calibrating and maintaining your tonearm and cartridge
- Equipment that will improve the quality of long-play record listening

Collected from the high point of this old-new again technology, 'The LP is Back!' brings a wealth of information to help you keep your existing equipment in top form and help you understand and appreciate the best in new products available from cartridges to turntables. Published 1999, 160 pp., 8in by 10¹/₂in, softbound.

Fully inclusive prices:

UK	£11.49
Europe	£11.99
ROW	£13.98

How to order:

Post the coupon to:
The LP is back, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, or fax 0208 652 8111,

or e-mail jackie.love@rbi.co.uk

Please make cheques payable to Reed Business Information

Log frequency sweep generator

£50 Winner!

Swept frequency responses are usually displayed as log amplitude against a log frequency baseline. This circuit generates an exponential waveform to control a generator whose frequency is proportional to an input control voltage. It does so without relying on the transfer function of a semiconductor device.

In addition to the exponential waveform, the circuit generates a linear sawtooth voltage for horizontal deflection of an oscilloscope, giving effectively a log frequency base, and a blanking waveform for the oscilloscope's Z modulation input.

An exponential voltage is developed across a capacitor, $C_{1.4}$, the transfer function being,



$$U_o = U_i \times e^{\frac{t}{R_1 C_1}}$$

The voltage is exponential since the current through R_8 is proportional to the voltage across C_1 , so that the rate of increase of voltage is proportional to its present value. The capacitor voltage is amplified by a factor of 2 by IC_{1a} , and applied via R_8 back to the capacitor. Schmitt trigger IC_{1b} discharges capacitor C_1 and also generates the blanking signal. Op-amp IC_{2a} amplifies the exponential sweep, and 220kΩ potentiometers P_1 , P_2 permit adjustment of the centre frequency and sweep width respectively, the sweep voltage being buffered by IC_{2c} .

The horizontal sawtooth sweep output is generated across $C_{5,6,7}$ or C_8 by constant current generator Tr_4 , giving sweep times of 10ms to 10s, approximately. The sawtooth waveform is reset by Tr_3 at the same

time as the exponential waveform is reset by Tr_2 . Sawtooth amplitude is adjusted by $P_{2.6}$ (10kΩ).

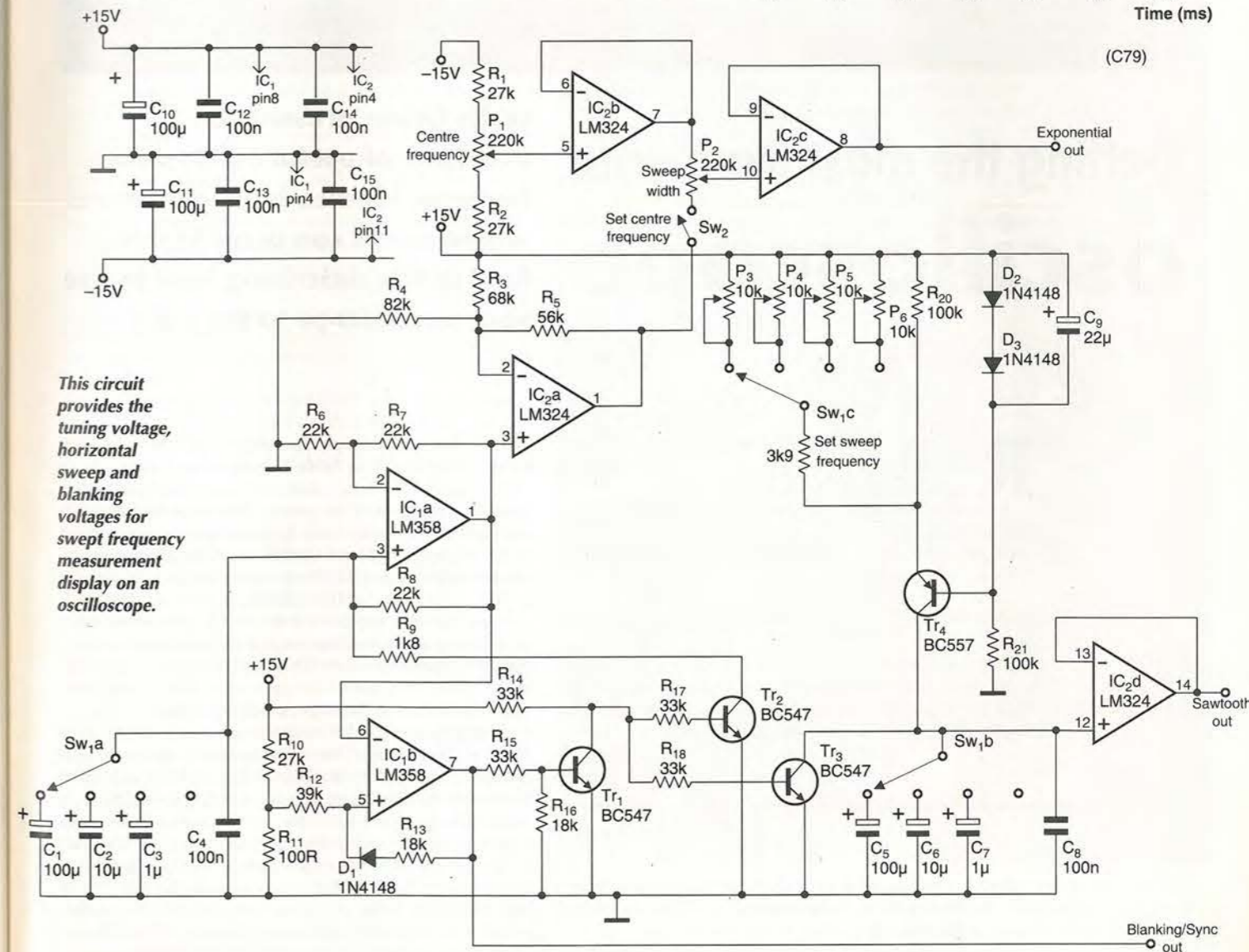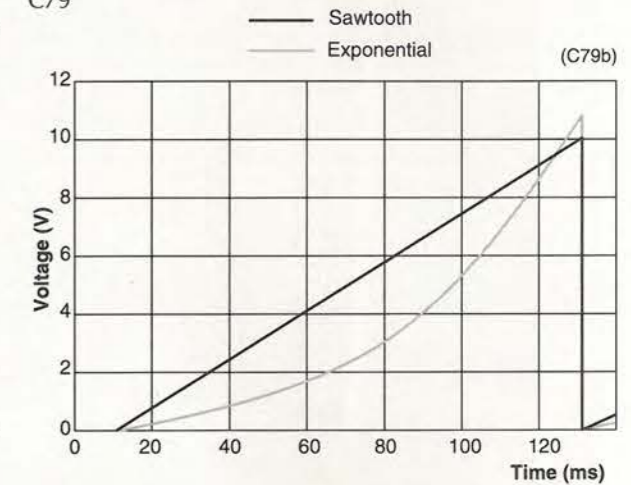Bernard Van den Abeele
Evergem
Belgium
C79



This circuit provides the tuning voltage, horizontal sweep and blanking voltages for swept frequency measurement display on an oscilloscope.



Getting the most from your oscilloscope

Leslie Green presents an overview of useful oscilloscope features. He also highlights areas where errors can occur in this final article describing how to use your oscilloscope to the full.

Regardless of the type of oscilloscope you are using, there will be an error as the measured signal approaches the bandwidth/rise-time of the scope.

A convenient number to remember is that a 100MHz scope has a rise time of 3.5ns. All other bandwidths can be scaled from this; for example a 50MHz scope has a rise time of 7ns. This is expressed by,

$$\text{Rise time} = \frac{350\text{ns}}{\text{bandwidth}}$$

where *bandwidth* is in megahertz.

If you can believe the bandwidth of your oscilloscope, then you can get an idea of the possible error at any frequency by using the normalised amplitude factor,

$$\text{Normalised amplitude factor} = \left| \frac{1}{1 + j \times \frac{f}{B}} \right| = \left| \frac{1}{1 + j \times F} \right| = \frac{1}{\sqrt{1 + F^2}}$$

where *f* is the operating frequency and *B* is the oscilloscope bandwidth and normalised frequency *f/B*. This factor was used to plot the graph of Fig. 1.

What this means is that at a frequency equal to the band-

width of the oscilloscope, the factor is 0.7071 – a 29.3% error. Values shown in Table 1 illustrate the point.

Note that values below about 1% are probably an unreasonable expectation of the general flatness of the frequency response of the oscilloscope. An even more important point is that the scope badge of 100MHz says that the bandwidth should not be below 100MHz; it is possible that you have got a 'good' one with 150MHz bandwidth, or even 200MHz.

There is another way to view the measurement errors introduced by using an oscilloscope and a probe, each having a finite bandwidth/rise-time. The measured value of rise time is the root-of-the-sum-of-the-squares, or RSS, of the individual rise-times of the scope, probe and signal.

Using this theory, a 1ns edge measured on a 350MHz/1ns scope will read 1.4ns. This is not always a good approximation though, as the formula relies on the overshoot on each of the individual step responses not exceeding about 3%.

It is often possible to evaluate the response of your system using this formula and decide that your circuit has more than infinite bandwidth. For example, your scope has a measured rise-time of 3.5ns (100MHz). You measure the rise-time of your circuit as 3.4ns. And you conclude from the mathematics that your circuit's rise time is therefore j0.8ns; the real answer is that your circuit is overshooting heavily.

There is not much point in going too mad specifying a high bandwidth conventional probe for your scope; a 250MHz probe may be adequate for a 200MHz scope. The probe is adjusted to optimise the response of the pair and the result is adequate, within the limitations of measurement with this type of probe.

High-speed measurements

It is not easy to say when a measurement becomes 'high speed'. Certainly, 500MHz/700ps signals are high speed and 1MHz/350ns signals are not – as far as measuring them with a scope is concerned.

Note that the technique of using a probe socket, or tinned copper wire coil, to connect to the circuit is also appropriate for high-frequency measurements, Fig. 2. Trying to use the probe hook and long earth-lead supplied with the probe is just not workable at high frequency.

A normal 1:1 scope probe has an input impedance of typically 1MΩ/60pF. The capacitance is so high because it contains the capacitance of the scope input, which is generally 10-30pF, and a long length of coaxial cable. This is no use at all at even modest frequencies.

People generally use 10:1 probes, which have input capacitances in the range of 10-18pF. These capacitances do not depend strongly on the scope input capacitance because of the long coaxial lead. But these probes can not be used to very high frequencies either. The problem is that the 15pF of the probe is too low an impedance at high frequency and it lowers the perceived bandwidth.

The probe may be displaying an accurate representation of what is occurring at its tip, but it has caused the edge to be much slower than it would be in its unloaded condition.

It is important to bear in mind that modern high-speed logic systems can not be considered 'verified' until the logic transitions have been viewed on a high-speed scope and the timings have been measured and tolerated; it is not sufficient just to verify that the prototype works.

Modern CMOS technology can easily produce 1ns edge speeds. These can be a real liability. If they are not correctly terminated, and have to travel more than a couple of inches, then the reflection can cause logic failure. This is a particularly pernicious problem as the logic may work most of the time, but then fall over at high temperatures once every two weeks or so.

The source impedance of a CMOS gate may be around 100Ω so the 15pF probe gives a time constant of 1.5ns and a rise-time of 3.3ns. All the wriggles, bumps and foldbacks on the edge become invisible and you can no longer find the problem in your circuit.

The answer is to use a probe with a much lower capacitance. It is possible to obtain 100:1 probes that have a low input capacitance of around 6pF. But then it becomes difficult to look at low-level signals and the probe bandwidth itself may be a limiting factor.

Conventional 1:1, 10:1 and 100:1 probes are 'passive' probes. A better answer is to use an 'active' probe. This way you can get plenty of bandwidth at a high signal sensitivity.

There are only two drawbacks with active probes. Firstly they cost anything from £100 to £1500 each. Secondly their output voltage is generally limited to around ±0.6V.

The maximum input voltage to the probe is therefore calculated from the probe attenuation. Typically a 1:1 active probe can handle ±0.6V, a 10:1 active probe can handle ±6V and a 100:1 active probe can handle ±60V. Clearly, to look at a 5V logic swing you need to use a 10:1 active probe; this may have an input capacitance in the 1-2pF region.

Because of this source impedance loading problem, active probes may be necessary to make accurate measurements below 100MHz and/or signal levels below 1V. Passive 10:1

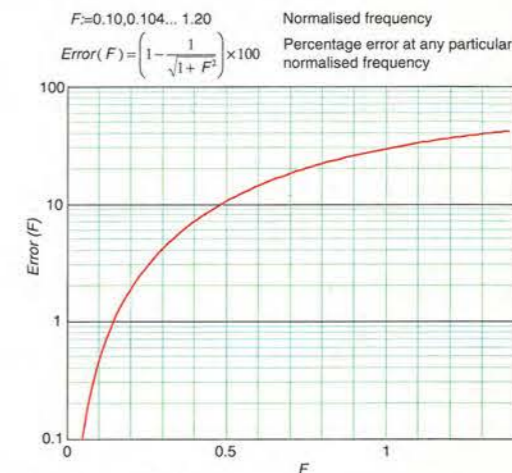


Fig. 1. Error caused by finite bandwidth/rise-time. *F* is normalised frequency, i.e. the signal frequency divided by the instrument bandwidth. It can also be considered as the inverse of normalised rise time.

500Ω probes with bandwidths up to 3GHz are also available and can be of use on low impedance circuits. In their simplest form, they consist of a 450Ω resistor in series with a 50Ω coaxial cable, terminated in the 50Ω input resistance of the scope.

Table 1. Errors due to bandwidth limitation.

Normalised frequency (<i>f/B</i>)	Error
0.1	0.5%
0.2	1.9%
0.5	10.6%
0.7	18.1%
1.0	29.3%

Floating inputs

Engineers sometimes want to measure circuits that are mains referenced. This would occur in off-line power supplies, for example.

Some people have a 'solution' for this; they remove the earth from the scope. But manufacturers clearly state that this is not an acceptable connection mode. Also, considering that a manager could be sued from a health and safety viewpoint for allowing this activity, removing the earth connection is out of the question.

In order to meet rf emission limits, it is common for scopes

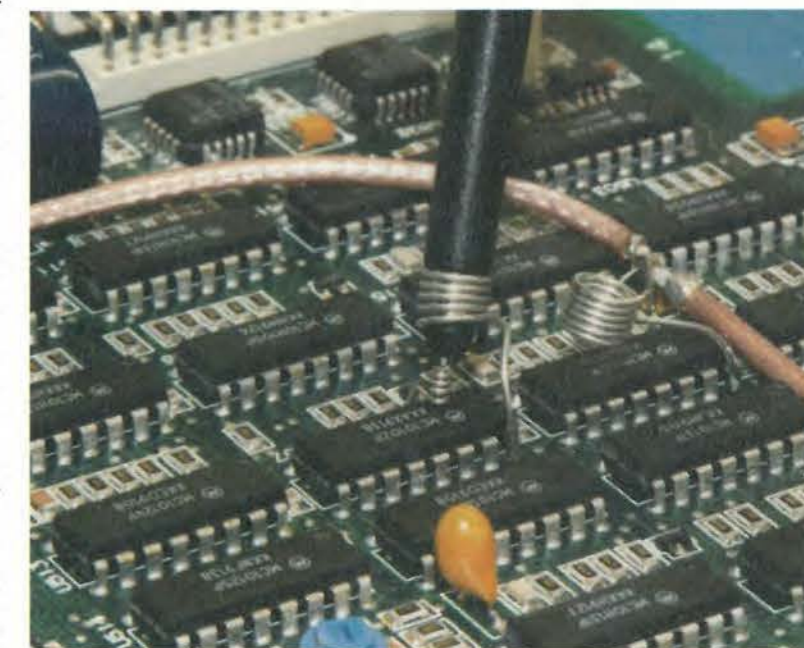


Fig. 2. Discussed in the May issue, this low-noise probing technique lends itself to measuring high speed logic. Note the other earthing coil so that pins on the other IC can be manually probed. Use 24SWG for the probe tip coil and 22SWG for the earth coil.

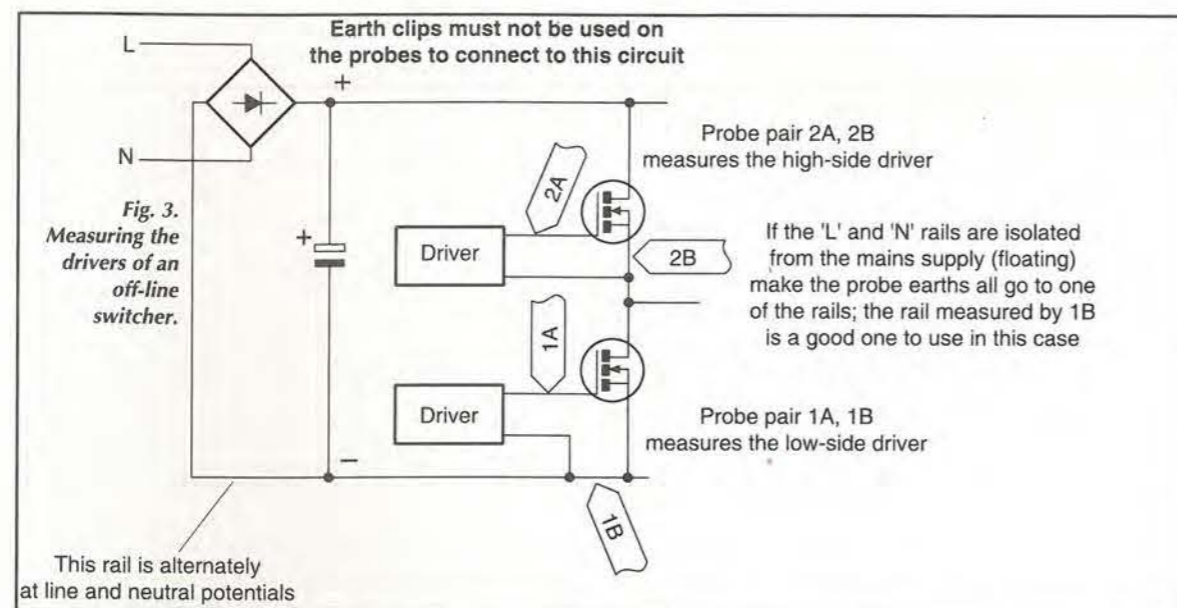


Fig. 3. Measuring the drivers of an off-line switcher.

to have mains filters on them. These have capacitors to earth to meet the filtering requirements. They may also have bleed resistors to earth to stop you getting zapped when you touch the plug pins after unplugging it from the mains. Pull the earth off the scope and the instrument's case floats to some unpleasant potential, due to the earth leakage current having no place to go.

Now the unwise might think that this problem can be overcome by using an isolation transformer. The scope can now be hung onto the output of a mains bridge rectifier – taking the scope's case alternately to neutral and live potentials. Such a set-up is great, provided you don't need to touch the scope to change range and you don't need to connect it to a computer or external plotter – and provided you don't mind hanging a vast capacitance on your circuit.

You see the case has a very large metal area and there is always some earthy material nearby to which it will have capacitance. This capacitance will be charged by drawing a current from the circuit under test. Of course having gone to the trouble of risking life, limb and legislation by removing the scope's earth, it is rather disappointing to find out that it is still not possible to measure both the low-side and high-side drivers of the off-line switcher at the same time.

Running the circuit rather than the oscilloscope from an isolating transformer would help with the safety aspects, but you would still have problems with charging currents. The isolation transformer would then need to swing in potential if the output of the bridge were to be earthed by the scope. Also, systems involving large motors would need the mother of all isolation transformers to power them!

Fortunately there are such things as scopes with individually floating inputs; there are also floating-input converter boxes that take a floating input and transfer the signal across

an isolation barrier to the measuring equipment. This is OK at low frequencies, but there is still a common-mode charging current. Fortunately this current is much less than for a whole scope as the input guard boxes are physically quite small.

Note that if the isolated scope input's 0V – i.e. the one connected to the scope's internal guard box – is connected to a high impedance point in the circuit under test then the common-mode current will have a much greater adverse effect.

Differential inputs

Another solution to the same problem is to use a scope with differential inputs; a probe with differential inputs is virtually the same thing as far as its use is concerned.

Using this type of equipment, both the high-side and low-side drivers of an off-line switcher can be viewed at the same time; this is vitally necessary to make sure that the timing is set up correctly.

Differential probes are available that convert conventional scope inputs into differential inputs. These cost anything from around £150 to well over £1000, depending both on the performance and the name badge.

Differential technology can require 3 or 4 connections per measurement rather than the conventional 2, the number used depending on the system being probed. When measuring an earthed system, it is not at all obvious whether or not one should use the earth clips of the probes, as the resulting earth loop may cause more trouble than it is worth. Try it and see which works best on your system.

It is essential that the circuit being probed has an earth reference. On a floating system, the scope itself can be used to provide the earth reference via the earth leads on the probes.

Continuing with the task of measuring the drivers of an off-line switcher, Fig. 3 shows the connections necessary if the switcher is driven direct off-line. Note that the earth clips are not used at all.

If the system is powered from an isolating transformer and there is no defined earth path then it is essential that the earth clips are used; a power rail would be the most sensible place to tie the system to earth.

Two extra terms are necessary for you to see if the differential system you are considering is suitable for your use; these are common-mode input voltage range and common-mode rejection ratio (CMRR).

The common-mode input voltage is the average voltage, measured with respect to earth, of the two differential inputs. If this exceeds the common-mode input voltage range of the

CMRR versus frequency

Caution is needed with isolated inputs. CMRR versus frequency may well not be given as a parameter of the equipment but this does not mean that it is invariant with frequency. In fact it is highly frequency dependent as the common-mode current increases linearly with frequency. This is because the admittance of the guard-box to earth capacitance increases linearly with frequency. It is therefore quite likely that an isolated measurement system will give a worse effective CMRR than a differential system at even moderate frequencies – perhaps as low as a few kilohertz.

Buyers' tips

I have often seen test gear left on the shelf because nobody wants to use it. Some manager or accountant bought it because it had a good banner specification and looked like good value. On a real-time scope this banner specification might just be bandwidth; on a DSO it would include sampling rate.

But when it comes down to using the instrument, you find out why it's so cheap. Try to move the traces and change the range and you need to fight your way through the maze of the user interface. Or how about something simple like changing the trigger level? Having once used a scope that has trigger level markers on the screen, I can assure you that you would not want to go back to randomly wiggling the trigger control about, trying to get

the scope to trigger.

This is especially true when you want to set the scope up to capture a transient event; you have to set the trigger level half way between where the trace is now and where you expect it to go – a hideous task without trigger level markers.

Try before you buy is the key here. If the manufacturer is too mean to give you a decent demonstration of the equipment, then you can always rent one for a week to ensure that the scope is suitable for your application. The banner specifications don't tell you much about how a scope really performs or whether it is user friendly.

It is necessary to convince managers and accountants that the cost of a piece of equipment does not stop at the initial purchase. A new scope should last for years; this is so much the case that several manufacturers will

give you a five-year warranty.

The total cost of the equipment has to be considered. This definitely includes servicing costs and total down-time. When checking out a supplier it is wise to see what their service facilities are like; service costs and turn-around times should affect purchasing decisions.

Another rising consideration in purchasing considerations is the law. With health and safety legislation becoming more significant to employers, there are growing concerns about test equipment sold without the relevant UL/CSA/IEC/EN safety specifications.

Managers purchasing equipment that is not certified as 'safe' to some international safety standard may get prosecuted if something nasty happens. Within Europe, it is illegal to buy equipment unless it is CE marked.

differential equipment, then overload and malfunction can be expected.

Common-mode rejection ratio is a measure of how much output you get for a given common-mode input voltage. Reading a few specifications will reveal that CMRR is strongly dependent on frequency, getting dramatically worse at high frequencies. CMRR is usually given in decibels; this can obscure the problem for those not so familiar with the decibel. Remember that 40dB is a factor of 100 whereas 80dB is a factor of 10000.

I will continue with the example of a high-side driver directly connected to the mains live, which is also known as the 'line' or the 'phase' connection. Clearly this live line is ultimately referenced to earth and the common-mode voltage is roughly $240\sqrt{2}=339V$ peak. Always use peak voltages for common-mode input levels.

With 80dB CMRR, the output voltage, referred to the input, is $339/10000$, which is 34mV peak. This is a fairly low noise level for the measurement of a 15V gate drive waveform.

Clearly the situation gets a lot messier when probing after a bridge rectifier. The common-mode voltage is now a half-wave rectified sine wave and therefore contains significant high frequency harmonic content.

Calculating the resultant output voltage is not possible because the relative phases of the harmonics are not specified by a plot of CMRR versus frequency alone. A worst-case analysis would add the harmonics, assuming them to be in-phase.

Bandwidth-resolution trade-off

Most designers realise that there is such a thing as a speed-accuracy product. If the fastest available a-to-d converter is 500MS/s at 8-bits, then you tend to expect that there will be 125MS/s 10-bit converters around as well.

The same thing is true in scopes; if you want a greater number of bits or a more sensitive input then you tend to find that the bandwidth is lower as a result. Thus you either buy an accurate relatively low-frequency scope or a less accurate high-frequency scope. What would be really nice would be to trade off bandwidth against resolution in the same box. Some DMMs and timer/counters trade off number of digits against update rate, which is a similar concept.

A new generation of DSOs can now perform this feat using a combination of ultra-fast digital signal processing and ana-

logue jiggery-pokery. If these are applied effectively, the basic differential non-linearity of the converter is significantly reduced – a factor of four improvement is easily achieved. Small-signal accuracy of the converter is genuinely enhanced. You really have to see this to believe it.

This is in stark contrast to the scopes previously mentioned, whose bandwidth can not be relied on. In these resolution-changing scopes the bandwidth is clearly announced as it is reduced and you get something in exchange for the loss. Note that large-signal accuracy is not improved by this technique on its own.

One particular use of this type of scope is to zoom-in on fine detail in a waveform without overloading the amplifiers. When a waveform fills the screen from top to bottom, that is the limit of fully guaranteed operation on many scopes. A good scope would allow you to click the sensitivity up a notch, so that the signal is 2 or 2.5 times larger than the screen. You would still be able to shift the trace around and see the signal with reasonable accuracy.

Note that this feature is only workable at low frequencies. It definitely does not apply at the upper frequency end of the scope's range. This sort of operation of a scope is not at all well specified and some scopes are much better at it than others. The higher resolution of these scopes allows you to zoom-in on the signal without overloading the amplifiers at all.

Given that the data is stored in high-resolution form, it is then also possible to zoom in on fine detail after the signal has been acquired. This is useful for some transient events – particularly where the expected signal size is relatively unknown.

By setting the amplifiers to a less-sensitive range, the higher resolution means that there is a better chance of capturing the desired transient event and seeing something useful. Another use of this type of scope is that the usual 2mV/div sensitivity can be usefully increased to 125µV/div, albeit for bandwidths below 1MHz.

DSO store length

The question that should be on your lips is "Why would anyone want more data acquired than they can see on the screen?" As screens tend to display only about 500 to 1000 points, why acquire more? In fact there are many different applications where a longer store length is useful, although it is also probably true that many users don't take full advantage of the longer stores.


One advantage of a long store is that you can acquire a screen full of data then zoom-in on a particular area to look at some of the fine detail. This is only particularly useful if the event is difficult to reproduce. If you can just re-run the test with the timebase and trigger delay set to a different position then this is the easiest way to view detail. If, however, your test is to blow up an ocean liner then you may want the acquisition system running for an hour before the test until an hour after the test to make absolutely certain that you get the data you need.

Elusive noise spike with no definite repetition rate

Random noise will produce the leading pulse shown. Adjusting the trigger level seems to show that there is a spike of both polarities present. This is a characteristic of random noise, a rising or falling edge will always occur somewhere and the scope will trigger on it.

In this case the random noise was obtained by setting channel 2 at 2mV/div and feeding the CH2 output (10mV/div) into channel 1. Channel 2 is acting as a wideband amplifier with a gain of 5, so that the noise level is more easily viewable.

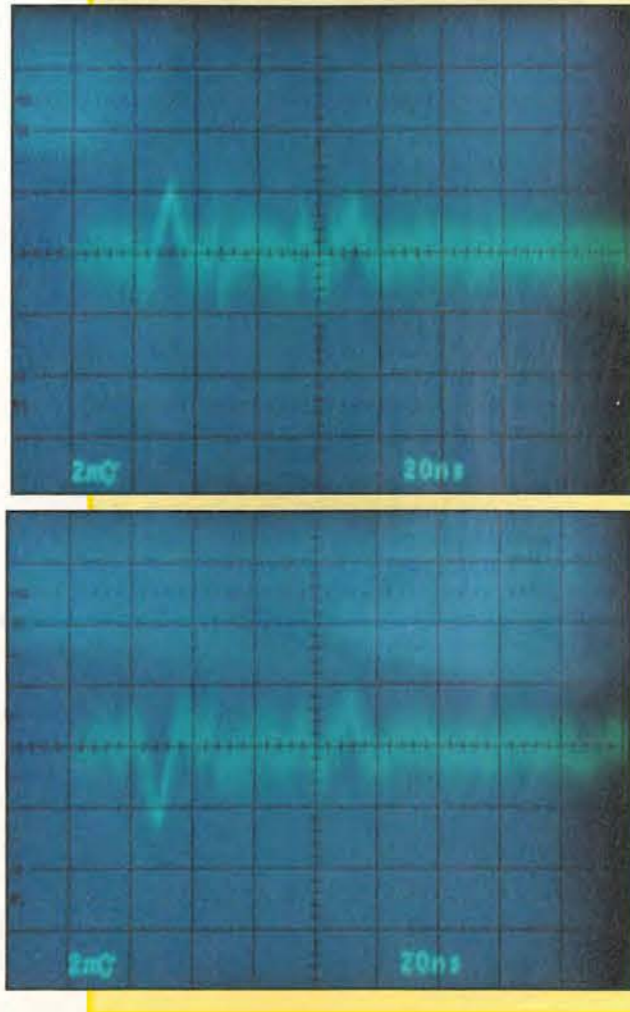Note that the rubbish after the leading pulse is constant between the two traces. This is usually indicative of either a start of sweep or trigger-breakthrough effect on the scope.



Another use of long stores is for signal processing applications. The longer the acquisition length, the lower the potential noise floor in an FFT. Fast Fourier transforms allow you to convert a time-related signal that you have acquired to a frequency-related signal, of the kind seen on a spectrum analyser.

Note that even if your scope does not handle FFTs itself, it is often possible to down-load the data to a pc to get some serious processing power on the job.

Digital games

I have described certain basic measurement situations and illustrated which ones are best made on a real-time scope as opposed to a DSO. In summary, the point is that with a real-time scope all you can do is look at the waveform. The most you can do by way of signal processing is to invert the trace and/or perhaps add it to another trace that is occurring at the same time on another channel.

However, the possibilities of data manipulation, once the data has been digitised using a DSO, are limited only by your imagination. Automatic measurements of rise-time, overshoot, pulse width, frequency and production limit-testing are just the obvious, everyday ones. The conversion of the time-domain data to a spectral response using an FFT is likewise common place.

Having downloaded the data into a computer, however, you are then free to apply the most hideously obscure filtering algorithms to convert the complete pile of unintelligible rubbish that you acquired into some meaningful result. It is this ability to play digital games, with what was once a real signal, that will inevitably mean that the market for the DSO will increase with time, while that of the real-time scope will fall.

There is also no doubt that more enlightened purchasers of DSOs do so to buy a ready-made acquisition system for measuring whatever it is they really want to be doing. This is a very cheap way of buying decades of experience in acquisition system design, encapsulated in a single box.

Less fortunate engineers, unable to convince their managers/accountants, may struggle for weeks to create a one-off acquisition system to plot widget production, not realising that two weeks of lost production of widgets and three weeks of engineering effort costs more than the DSO would have cost!

Round-up

In this short series of articles, I hope that I have given you some hints about making better and more meaningful measurements – with or without an oscilloscope. Sometimes a scope is not the correct measuring device, but always the method of connection of the scope to the circuit is crucial.

In this modern world, an engineer who cannot use an oscilloscope is effectively like an adult without a driving licence. If you feel that this applies to you, then you should read your scope manual carefully and play with the instrument until you are comfortable and competent with it.

Once you master the basics of measuring using a DSO, you can go on to more advanced measurements. Did you realise that it is useful to deliberately under-sample (alias) signals on a pair of DSO inputs? The DSO then acts as a frequency transfer standard with sub-ppm accuracy, regardless of the absolute timebase accuracy of the DSO.

Understanding the basics means that you will be able to devise your own tricky ways of getting the most from your oscilloscope.

'Electronics, Electrical & Mathematics Principles V6'

If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics then this is the software for you.

CD-ROM
 Students and Hobbyists the complete package for **£49.95* (\$82.17) normally £99.95***
 Colleges and universities including unlimited user site licence. **£299.95* normally £595.95***
 * +VAT if applicable
Postage FREE

Features.

- Analogue.
- Digital.
- Electrical.
- Microprocessors.
- PIC Microcontrollers.
- Mathematics.
- Electronics Toolbox.
- Components and Equipment Dictionary.
- Fully interactive graphics, graphs and calculations.
- Single page colour printing.

Full Windows integration. Explanatory text. Hundreds of Electronics & Maths formulae with worked examples using your inputs. All calculations are shown. Default values on startup. Easy to use, no prior knowledge assumed. Comprehensive menu and indexing. Covers college courses from entry to university level.

"Electronics Principles is a well thought out and comprehensive program that is also easy to install and stable in operation. It can be wholeheartedly recommended."
 Robert Penfold. Everyday Practical Electronics magazine.

www.eptsoft.com

Please telephone or visit our web site for a list of over 900 topics from Ohm's Law to PIC' microcontrollers.

eptsoft limited. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.
 Tel: 01376 514008. Fax: 0870 0509660 info@eptsoft.com
 Switch, Delta, Visa and MasterCard payments accepted - please give card number and expiry date.
 Cheques and P.O. made payable to eptsoft limited.

PROFESSIONAL Development Tools

from Milford Instruments

Milford Instruments Tel 01977 683665, Fax 01977 681465
www.milinst.demon.co.uk info@milinst.demon.co.uk
Milford House, 120 High Street, South Milford, LEEDS LS25 5AQ



PIC Emulators from Tech Tools

Mathias In-Circuit Emulator

- 16C5X to 20MHz
- 16CXX to 25MHz and data breakpoints
- Modular design
- True Integrated Windows Environment
- Supports standard assemblers and compilers
- True Bandout Chip set based
- Programmers and adaptors also available

Full details at www.tech-tools.com



New to PICs or just wanting to learn new tricks?
We stock the excellent Square 1 series of PIC primers. See our web site for contents.

BASIC Stamps

Still the easiest and fastest way to get your project up and going. 8 or 16 I/O pins, easy-to-read BASIC instructions plus on-board comms and simple interfacing to peripheral chips.



ROM Emulators from TechTools




EconoROM, FlexROM and UniROM

- Fast 90ns, 40ns and 30ns access times
- Fast download (up to 2.5Mbit/second)
- Read-back, Verify and Software mode
- Full editor and utilities included
- Low editing (UniROM only)
- 8bit & 16bit up to 32Kbit
- EPROM, FLASH and SRAM emulation

Full details and firm software at www.tech-tools.com

Scenix Emulators from Parallax

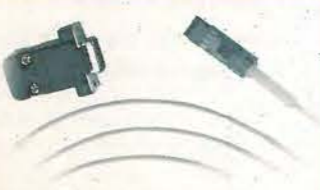

SX-Key Emulator

SX chips are EEPROM based, PIC16C5x pin compatible micros with up to 100mips performance.

- Full speed debugging on production chips
- Integrated Windows environment
- Software configured oscillator
- 18 to 52 pin reprogrammable devices
- SX Blitz low cost programmer also available. Full details and software at www.parallaxinc.com



SERIAL LCDs reduce display hassle

We stock a range of alphanumeric and graphic displays all fitted with serial RS232 interface boards: 2x16 to 4x40 and up to 128x64 graphics size

RS232 data entry terminal unit also available

CIRCLE NO.114 ON REPLY CARD


The science lab in a PC



Experiments Ideas for DrDAQ

- Flickering Lights. Use a...
- Dawn Chorus. Use light...
- Sound waveforms. Use...
- Sound insulation. Use a...
- Sound insulation. Use a...
- Sound waveforms of m...
- Light decay (inverse sq...
- Light insulation. Expan...
- Sound insulation. Use a...
- Acid Base Titration. Mor...
- Acid Rain. Measure the p...
- Exothermic Reactions. I...
- Endothermic Reactions...
- Day and Night. Plot temp...
- Fermentation of Grass (...
- Fruit Power. Make a fruit...
- Heat insulation. Wrap te...
- Capacitor charge/disch...
- Infra red remote control...
- Output of a solar cell. V...
- Heat insulation. Wrap te...
- Global Warming. Show t...
- Heat Loss Through...

Only £59!
+VAT

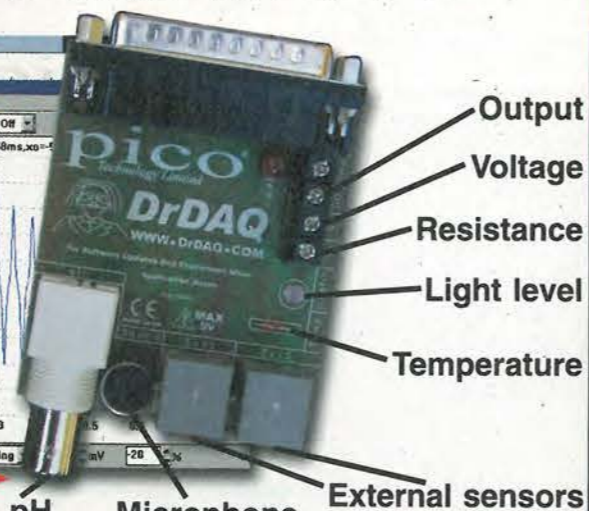

pH Microphone External sensors

- ✓ Very low cost
- ✓ Built in sensors for light, sound (level and waveforms) and temperature
- ✓ Use DrDAQ to capture fast signals (eg sound waveforms)
- ✓ Outputs for control experiments
- ✓ Supplied with both PicoScope (oscilloscope) and PicoLog (data logging) software

The DrDAQ is a low cost data logger from Pico Technology. It is supplied ready to use with all cables, software and example science experiments.

DrDAQ represents a breakthrough in data logging. Simply plug DrDAQ into any Windows PC, run the supplied software and you are ready to collect and display data. DrDAQ draws its power from the parallel port, so no batteries or power supplies are required.

Tel: 01480 396395, Fax: 01480 396296, E-mail: post@picotech.com, Web: www.drdaq.com

CIRCLE NO.115 ON REPLY CARD

pico
Technology Limited

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

Development system for CPCI

The Vanguard is an off-the-shelf CPCI development system from APW Electronics. The thermally-managed, EMC screened, wired and powered modular unit lets the system integrator specify the combination of components needed. Conforming to IEEE1101.10, the 19in. unit can be fitted with a centrally-mounted eight-slot backplane, allowing for left and right-hand system slots. It can also have a 16-slot CPCI monolithic backplane, in which two eight-slot backplanes share power and ground planes and can be linked by a bridge module to give a system with 14 useable slots. It conforms to PICMG CPCI 2.1 rev 3.0 or, for telecoms, to H110. It is compatible with 32 and 64-bit data transfers and supports 33 and 66MHz operation with 3.3 and 5V signalling.

APW Electronics
Tel: 01489 780078

VDSL transformer

Two VDSL transformers from Pulse, for use with Broadcom's BCM6010 scaleable DSL transceiver chip, support data transfers up to 25.92Mbit/s. The transformers are available as surface mount devices (B4025) or in through-hole packages (B4008) and are used in Broadcom's VDSL transceiver reference design (BCM96011).

Pulse
Tel: 01483 401700



150MHz digital oscilloscope

Four true channels and acquisition speed up to 50GS/s on the Metrix OX2000 digital oscilloscope from Chauvin Arnoux enable testing of complex signals up to 150MHz bandwidth. Measuring four signals at once, it has autoselect and undo functions, extended memory, analysis capacity, including FFT function, and a 17.8cm hi-lite fast-scan display. A VGA output provides the full display on a colour computer screen. A dual-time base function allows zooming in on part of the reference signal while displaying the whole recording and up to eight curves on the screen.



There can be up to 16 automatic and cursor measurements. Self-calibrating for offset

takes 5 minutes without measuring instruments. Chauvin Arnoux
Tel: 01628 788888

Single board computer

The MAT915 PICMG processor card supports flip-chip PGA Pentium III processors in speeds from 500 to 750MHz. It also supports multimedia AGP video, flat panel and analogue video, Ethernet, SCSI and Compactflash disk. Features include a parallel port, two serial ports, infra-red port, keyboard, mouse, USB, IDE and floppy. Support of AGP video allows dual independent display outputs - TV, flat panel or CRT - with video input and capture. Options include 8 or 16Mbit video memory and Panalink for digital flat panels. The video input channel supports composite or S-video input as NTSC or Pal, with a Samsung decoder. It can also be used with the Celeron 300 to 566MHz processor and suits OEM and embedded applications. Features include best effort boot, automatic recovery and a customisable

Award bios. There is a choice of Adaptec or Symbios SCSI, both providing Ultra2 LVD SCSI. Converters to 50-way connections are also available. Microbus
Tel: 01628 537333

Synchronous buck converter

An integrated synchronous buck converter IC for powering baseband and PA circuitry in satellite phones and other mobile communications handsets is available from



Visay. Capable of delivering up to 600mA output, the Si9167BQ will serve multi-cell and multiple battery chemistry configured cell phones, smart phones, communicators, web phones, PDAs and other systems powered by two-cell lithium ion batteries. It operates at up to 2MHz. Efficiency is typically 95 per cent under full-load conditions. Vishay Intertechnology
Tel: 001 610 644 1300

24-bit a-to-d converter

Linear Technology has introduced the LTC2402 two-channel 24-bit no latency delta-sigma A/D converter in a 10-pin MSOP. It is for applications where an extra channel is needed for sensor compensation, cold junction compensation and measuring ambient temperature in pressure sensors. The extra channel also allows sensing and compensating for voltage drops in remote RTD connections. It provides automatic channel

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

selection (ping-pong) for continuous monitoring of two inputs such as thermocouple temperature probe and a cold junction temperature sensor. Two or three wire i/o allows two channels of 24-bit data over two wires for isolated measurements such as smart sensors. It includes an on-chip oscillator.

Linear Technology
Tel: 01276 677676

2Mbit ternary CAM

Sibercore Technologies has introduced a packet forwarding engine, the Sibercam Ultra-2M. Based on a ternary content addressable memory (CAM) architecture, it performs up to 100 million multilayer, multi-protocol look-ups per second and can support OC-768 (40Gbit/s), OC-192 (10Gbit/s) and OC-48 (2.4Gbit/s) transmission systems. Sibercore Technologies
Tel: 001 613 271 8100

Logic analyser software

Tektronix has added Dragonfly Software Development LLC and Synapticad to its embedded systems tools partners programme, bringing the number of partners to 26. Also several embedded systems tools partners announced products at the recent Embedded Systems Conference. These support vari-

ous applications on the TLA logic analyser family. Tektronix
Tel: 01344 392243

RJ45 connector

A thinner version of the RJ45 single-line data socket has been introduced by Honda. The MOD connector is 10.2mm deep. With a mating plug, it can be used for connecting a modem, printer or data PBX at up to 19.2kbit/s with untwisted wire. Faster transmission protocols, such as Ethernet, can be



handled via twisted pair wire. It has a standard eight-pin interface with gold plated contacts. Honda Connectors
Tel: 01793 523388

MOSFETs

Fairchild has announced Powertrench MOSFETs at 60, 80, 100, 150 and 200V. For use in dc-to-dc converters, servers and PC power supplies, they are suitable for 48V input dc-to-dc modules, such as those used in telecoms. They come in SO-8 and DPAK packages with

different on resistances. They are also available in TO-220 and TO-263 packages. The 60, 80 and 100V units are in production and the 150 and 200V models are sampling. Fairchild Semiconductor
Tel: 01793 856819

Brushless dc motor

An EMA brushless motor from Papst, the 933 7032 100 EMA, provides an output of 400W and measures 90mm diameter by 68.5mm long. Efficiency is 74 per cent and weight less than 1.8kg. The motor is also available as an OEM platform supplied in basic or custom form including different shaft configurations, application specific performances, connection options and factory fitted gearboxes. Drive electronics allow speed control from 300 to 5000rev/min,



variable direction of rotation, and active braking using an external resistor network. Papst
Tel: 01264 333388

Power supply

Lambda has introduced a 300W version of its JWS power supply for use in process control, industrial ATE,



telecoms and industrial computer applications. It accepts an input of 85 to 265V ac or 120 to 330V dc and comes in seven versions from 2 to 48V dc with 60 to 6.5A respectively. Power factor correction is fitted and is rated at 0.99 typical at 100V ac full load and 0.95 at 200V ac. Able to support parallel operation, it has an output current balance circuit for multiple unit designs. Features include overcurrent and overvoltage protection, thermal shutdown, remote sensing and remote on-off control. Fan cooled, it operates between -10 and +60°C and measures 120 by 92 by 190mm. Lambda
Tel: 01271 856666

Digital multimeter

The 2700 digital multimeter from Thurlby Thandar also works as a data acquisition system or data logger for an IEEE488, RS232, PC-based or stand-alone system. It allows temperature characterisation, data logging, precision measurement and control and mixed-signal data acquisition. There are 13 measurement functions including signal conditioning and mx+b scaling. The unit has up to 80 differential analogue input channels, each individually configurable, in one half-rack system with built-in i/o and

PIC Basic

Write your PIC programs in BASIC! - No STAMP REQUIRED!

PIC Basic - £49.95

Quicker and easier than 'C' or assembler. PIC BASIC is a true compiler providing faster execution and shorter programs than BASIC stamp interpreters, built in I2C routines and serial comms upto 115K Baud and full BASIC STAMP compatibility make writing for the Microchip PICmicro's easy! PIC BASIC compiles your basic language programs to Microchip Hex format for use with in-circuit emulators or for programming directly into the PIC CHIP. Supports PIC12C67x, PIC14Cxxx, PIC16C55x, 6xx, 8xx, 84, 92 and 16F87x. Full documentation with syntax examples are provided in the 168 page user manual. A technical support mailing list is provided for life time support.

PIC Basic Pro - £149.95

The PIC BASIC Pro compiler instruction set is compatible with the Basic Stamp II providing additional functionality over PIC BASIC, feature like LCD read Write, fully customisable Serial in / out. (Create a serial LCD display driver in minutes). Full de-bug facilities, compile with debug to produce assembly commented with your Basic commands PIC BASIC and PIC BASIC PRO compile light efficient code without the use of a basic interpreter. Supplied with a 168Page manual, explaining each command and worked examples FREE PIC Macro compiler, FREE Programmers File Editor, FREE Windows Front End. PIC BASIC PRO includes samples programs and code to support Smart card read/write.

Download the full 168 page PIC BASIC MANUAL and sample programs
<http://www.picbasic.co.uk>
Order Online via our secure server
<http://www.crownhill.co.uk>

- ◆ Low cost programmer for PIC12Cxxx, PIC12CExxx, PIC14Cxxx, PIC16C505, 55x, 6xx, 7xx, 84, 9xx PIC 16CE82x and PIC16F87x
- ◆ ZIF adaptors are available for 8/18 in 40/28Pin DIL, 8, 18 and 28 SOIC, 44 Pin MQFP, 44 and 68 Pin PLCC
- ◆ Powered by 2x 9V batteries or AC adapter.
- ◆ Connects to PC parallel port
- ◆ Upgradable software is supplied for future PIC Micro's
- ◆ FREE 8051 style PIC Macro compiler

£35 When purchased with PIC BASIC

- Parallel port extension cable - £5.95
- 40Pin ZIF socket - £22.50
- 8/18Pin ZIF Socket - £22.50
- PIC8 Prototype board - £4.50
- PIC18 Prototype board - £5.50
- PIC64 Prototype board - £8.50

All prices are subject to VAT@17.5%

PIC Real-time 'Emulator' and Programmer



- NEW! £149.95
- For PIC16F87x (emulates most PIC16C6x/7x devices)
- In-Circuit run time debugging
- Real Time code execution 32KHz to 20MHz real time operation
- High Speed Parallel port interface
- 2.5V to 6.0V operating range
- Built in device programmer
- Run, Step, Run to Cursor etc
- Conditional Animation Break
- Software animation trace captures 3 user defined variables in addition to opcode, W, Status, FSR registers and corresponding instructions.
- Source Level and symbolic debugging
- Runs under PIC16C IDE (win95/98 or NT) or MPLAB
- Supplied with ICD debug module, Proto board, 40Pin and 28Pin emulator headers, Cables IDE software and user guide

All prices are subject to VAT@17.5%



PIC 16F84 / 04n - £1.90	PIC 12C508A - £0.63
PIC 16F84 / 04so - £2.00	PIC 12C509A - £0.63
PIC 16F84 / 10n - £3.95	24LC16 - £0.75
PIC 16C622 / 04n - £2.50	24LC16 so - £0.95
PIC 16F877 / 04n - £5.50	24LC32 - £1.50
PIC 16F877 / 20n - £6.00	24LC64 - £1.50
PIC 16F876 / 04n - £4.50	24LC65 - £1.50
PIC 16F874 / 04n - £4.50	
PIC 16F873 / 04n - £4.50	

All prices are subject to VAT@17.5%

PIC Micro CD-ROM

over 1.2Gb of info **£10 inc P&P and VAT**

Packed with information, data sheets, application notes, programs diagrams and tutorials. Includes TETRIS and PING PONG with sound and video out of a single PIC 16F84. Basic language assembly routines and macros for hundreds of commands. Data sheets on thousands of devices, micro's, memory and support chips.

LCD DISPLAYS

16x2 line super twist displays - £7.50 ea

Xtals and Resonators

4Mhz and 20Mhz from 45p



PIC16x84 programmer Kit

WINDOWS Driver - £15.00 inc P&P + VAT
Programs the popular PIC1684 and 24 series serial memory devices. Connects to the serial port of PC upto pentium (not P2 or P3) and requires NO External power supply. The KIT includes Diagram, layout, High Quality PCB and all components, software on 3.5" FD

SMARTCARD DEVELOPMENT SYSTEM

ChipDrive StarterKit + Windows Software
Read and Write data on Smart Cards and Memory cards
Microsoft PCSC compatible!
Package includes:
Professional card Reader/Writer (ChipDrive Micro),
Assorted Smart Cards (3 pairs),
Samples of source code in VB3,4,5+6, C and Delphi.
Examples Apps to Read and Write to Smart Cards and GSM cards
Documentation and detailed Windows DLL description.
£69.95
www.towitoko.co.uk

LabProg 48LV

Low Cost - High Performance
Intelligent Universal Device Programmer

Includes:
Connection cable
Diagnostic POD
User Manual
PC Software Driver
240VAC/12V adaptor

Universal Serial Eeprom programmer

£49.95



PreProm UNIVERSAL Eeprom Programmer
Adaptors for TSOP, PSOP, QFP, SOIC, PLCC
Adaptors for Microprocessors
Adaptors for Eeprom
Emulator adaptor

£132.00

All prices are subject to VAT@17.5%

Crownhill Associates Limited



32 Broad Street Ely Cambridge Cb7 4PW
Tel: 01353 666709 Fax: 01353 666710



ORDER ON-LINE www.crownhill.co.uk


Right-angle backplane connector

Molex has added a right-angle version to its

Omnigrid connector range for backplanes in

automation and telecoms applications. Contacts, size and configuration can be specified to suit each application. Power and signal contacts can be mixed in the same housing. The right-angle version is based on Chicklet V tails press fit contacts for board extension and front i/o. The 2.5mm grid is adapted for high speed i/o systems. Combined with the Omnigrid Coaxial cable connectors, the 90° Omnigrid front i/o is a suitable interface for single ended transmission up to 622Mbit/s.

Molex
Tel: 01252 720720

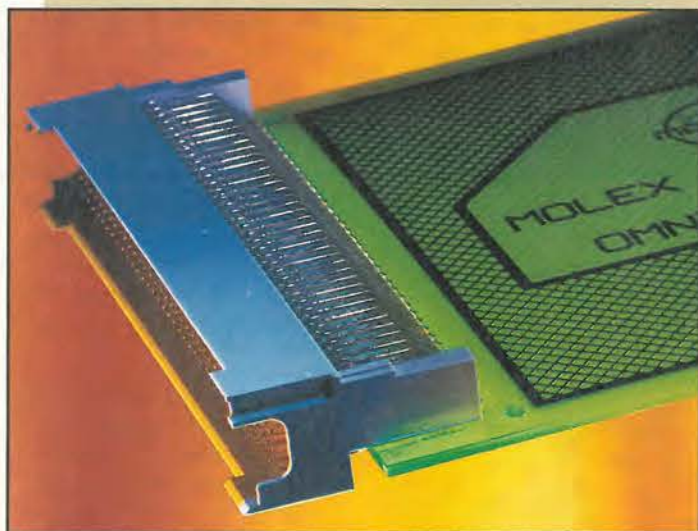

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

isolated switching. Including two slots for plug-in cards, it has the accuracy and traceability of a 6.5-digit 22-bit DMM. A button allows switching between front and rear measurement inputs. Five plug-in cards are available: the 7700 20-channel differential multiplexer with automatic

cold-junction compensation; 7702 40-channel differential multiplexer; 7703 32-channel differential multiplexer; 7705 40-channel, single-pole control and actuator module; and 7706 multifunction i/o module. It comes with Windows-based application software to configure the DMM and



display, analyse and archive test data to a PC. Testpoint and Labview are also supported. *Thurlby Thandar Instruments*
Tel: 01480 412451

TFT colour LCD module

Sunrise Electronics has announced an NEC 46cm colour TFT LCD module with a digital interface and 170° horizontal and vertical viewing angles. The NL128102AC28-04 provides 8-bit RGB in 256 steps for 16.7 million colours at up to SXGA resolution of 1280 by 1024 pixels. It is mechanically compatible with the NL128102AC28-01/01A analogue interface 46cm module that provides electrical compatibility with existing CRT monitors. It uses an analogue signal processing technique that ensures



compatibility with CRT displays without an additional analogue-to-digital converter. *Sunrise Electronics*
Tel: 01908 263999


Audio power amplifier

Designers of audio systems for portable and desktop applications can use a filterless Class-D audio power amplifier announced by Texas Instruments. The TPA2000D2 is a stereo amplifier with an

Board-to-cable connector

The Hirose MQ172 board-to-cable system from Flint is for making power connections to handheld systems. The three-contact PCB receptacle is 3.9mm high with dimensions of 6.4 by 6.0mm. Current capacity is 3A. It is also available in a four-pin version and both have a two-point contact design and a lead construction that provides shock and vibration resistant connection to the PCB. The use of a snap lock system and keyways helps ensure positive, error-free insertion. Plugs have solder bucket contacts, so they can be used with various cable types. The plug case and cable bushing are integrated into a one-piece body, so assembly is a matter of pressing the case into position once harness work is complete. The receptacles come in embossed tape-and-reel for automatic pick-and-place installation.

Flint SMD
Tel: 01530 510333

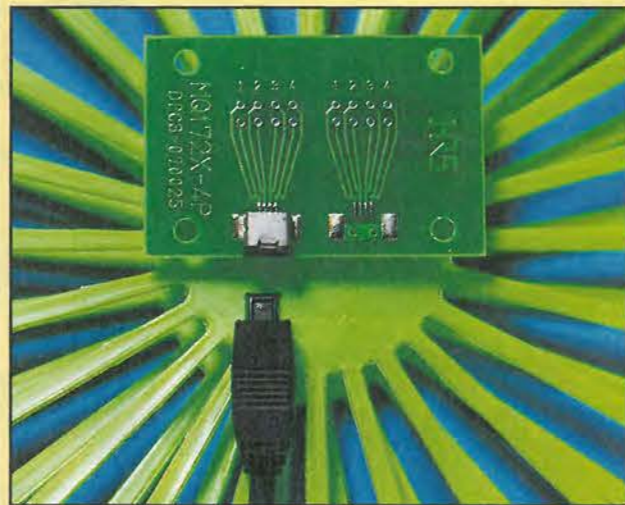

The Distributor with 20,000 hard-to-find lines EX STOCK!!!

Semiconductors

We have one of the largest ranges of discrete parts in the UK, both new and obsolete types and, if we do not have it in stock, we can usually source it for you.

Call or fax for our latest Semiconductor stock list.

Computer products

We carry in stock everything to make a Personal Computer. CPUs - Memory - Motherboards - Cards - Scanners - Modems - Sound Cards - Speakers - All types of Drives - Cases - PSUs - Monitors etc

Call or fax for our latest Semiconductor stock list.

Components & equipment

Capacitors - Resistors - Connectors - Potentiometers - Cables - Batteries - Speakers - Amplifiers - Lamps - Microphones - Fans - Power supplies - Transformers - Buzzers - Sirens - Fuses and Holders - LEDs - LCDs - Relays - PA Systems - Tools - Test Equipment - etc

Fax or write to us for our latest catalogue



Semiconductor Supplies International Ltd

Dawson House, 128 - 130 Carshalton Road, Sutton, Surrey, England, UK. SM1 4TW
020-8643 1126 (Sales and Technical Queries)
Fax: 020-8643 3937 (For International use +4420)
e-mail: sales@ssi-uk.com Web: ssi-uk.com

from **£60 (inc)**
Shareware Version
Download & Order Online!

PROTEUS VSM

Virtual System Modelling


Build It In Cyberspace

www.labcenter.co.uk

CIRCLE NO. 117 ON REPLY CARD

Develop and test complete micro-controller designs without building a physical prototype. **PROTEUS VSM** simulates the **CPU and any additional electronics used in your designs. And it does so in real time.***

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.

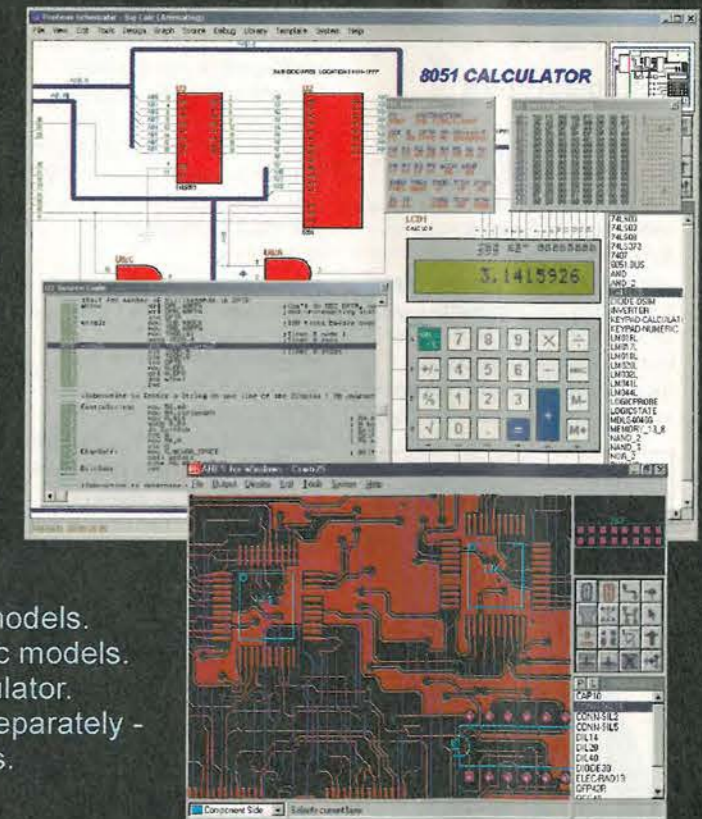

*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium II.

labcenter
Electronics

Write, phone or fax for your free demo CD - or email info@labcenter.co.uk.
Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington. BD23 5AA.

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

output power of 2W rms or 4W peak into 4Ω speakers. The 5V amplifier provides four internal gain settings. Shutdown control helps prolong battery charge life by limiting total supply current to less than 1μA. Using PWM, it samples the input audio signal at a rate of 12 times the audio band and then recreates the audio signal at the speaker.

Texas Instruments
Tel: 01604 663000

Touch-screen controller

Burr-Brown's ADS7846 is a single-chip touch-screen controller for battery-operated systems such as PDAs, pagers and mobile phones. It provides onboard voltage reference, temperature sensing, battery monitoring and touch-pressure measurement. It measures a change in resistance as the screen is touched. The resistive change is then used to determine where contact was made. Power consumption is less than 0.6mW with power-down control and single-supply operation of 2.7 to 5.25V.

Burr Brown
Tel: 001 520 746 1111

Voltage/current calibrator

The Yokogawa CA11 is a battery operated voltage and current calibrator for the field calibration of process measurement and control instruments. The unit combines source and measurement facilities, so it can be used for testing control loops that include measurement functions and transmission outputs. These



outputs can include current loops and voltage outputs to devices such as recorders and data-acquisition systems. A one-touch function causes the output to step up or down in five equal steps on the 4 to 20mA or 1 to 5V ranges. For loop checks, it has a sink function in which the loop voltage is used to simulate a two-wire transmitter and a sweep function increases or decreases the output level at a constant rate. Measurement ranges are from 10μV to 30V and 10μA to 24mA. Accuracy is ±0.05 per cent for measurement and source functions.

Yokogawa
Tel: 01494 459200

Temperature sensor

A temperature sensor on a 1206-sized surface mount chip has been developed by Heraeus. For -50 to +130°C use, the sensor can replace a thermistor in temperature measurement or temperature compensation applications. Based on thin-film platinum technology, it is available as a 100 or 1000Ω device in two tolerance classes. Temperature coefficient is positive and complies with Din EN60751. Maximum drift over 1000 hours at 130°C is 0.06 per cent. Sensors come in blister reels that are compatible with automated assembly techniques.

Heraeus
Tel: 01246 454849

Subscriber line IC

Mitel has launched the MT91610 programmable subscriber line IC that provides a line card interface between a switching system and a telephone line. The device uses sine wave ringing above 70V rms to reduce the risk of crosstalk on adjacent lines. It supports battery feed, user-definable line and network balance impedance, and off-chip audio gain programming. The device goes into power-down mode when not in use to reduce power consumption in short-loop applications such as pair gain and wireless local loop. With on-hook transmission and top



ring reversal, it accommodates DID signalling in PBX and CLID applications. The device also has unbalanced detection for applications requiring ground start. It can take a programmable current range between 20 and 30mA, and loop lengths above 1800Ω in voltage foldover mode.
Mitel Semiconductor
Tel: 01793 518000

30V and 20V trench MOSFETs

Intersil has announced trench MOSFETs to provide power management in notebook PCs, mobile phones and lithium-ion battery pack protection applications. The 30V ITF861xx and 20V ITF870xx come in TSSOP8 and TSOP6 packages. The ITF861xx logic-level MOSFETs are either single p channel, single n channel or dual n channel devices. The p-channel devices

perform high-side load control switching in ACPI circuits and notebook PCs, such as battery disconnect switching and battery charge switching. The n channel devices perform low-side load control switching and can be used in switching regulator circuits such as power control circuits in notebook




PCs. The 7.8mΩ on-resistance single n-channel version is for 5 and 3.3V supply rail switching in hotplug applications such as servers and Raid. The ITF870xx sub logic-level range includes single and dual p and n channel devices.

Intersil
Tel: 01344 350250

Java virtual machine

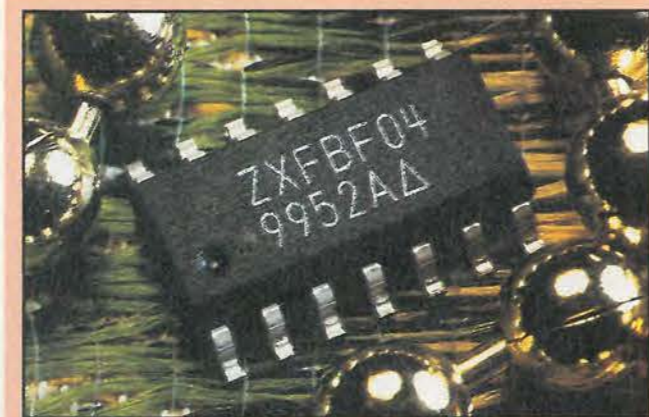Scenix has introduced a virtual machine (VM) for embedded applications that is programmable in Java. For use with the company's SX communications controller



Four-channel analogue video buffer

From Zetex, the ZXFBF04 provides four channels of analogue video buffering for multi-channel applications where broadcast quality is not required. These include video switching matrixes and multi-channel a-to-d input buffers in instrumentation, signal acquisition and security. Small signal bandwidth is above 100MHz, while 1V peak-to-peak bandwidth is more than 20MHz. Slew rate is typically 40V/μs. Each channel draws 1.9mA and the buffer is powered from a ±5V supply. It comes in a 14-pin SOIC package.

Zetex
Tel: 0161 622 4560

electronic design STUDIO



New Version 1.2


The new fully integrated electronics CAD system with schematic, simulation, PCB, autorouting and CAD/CAM modules as standard.

- Brings the power of desk top publishing to EDA.
- Publication quality feature rich schematic production.
- New generation dynamic netlist navigator with project management.
- Superb quality CAD/CAM output, including R-274X and Excellon.
- Wizards automate key features.
- Compatible with TINA Pro 5.5.
- No pin limits!

Electronic Design Studio from £199
Price excludes VAT and P&P where applicable.
30 DAY MONEY BACK GUARANTEE
Copyright © 2000. Prices & specifications subject to change without notice.



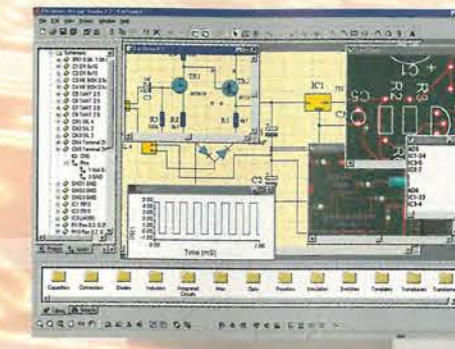Quickroute Systems Ltd,
Regent House, Heaton Lane,
Stockport SK4 1BS UK
Tel 0161 476 0202 Fax 0161 476 0505
Email info@quickroute.co.uk
WEB www.quickroute.co.uk



Tailor made to suit you

CIRCLE NO.118 ON REPLY CARD

30% discount for *EW* readers
on dmm with frequency, capacitance & inductance



Features

3.5 digit 43 ranges 0.25%
AC & DC voltage & current
Resistance to 20Mohm
Capacitance to 2000uF
Frequency to 20MHz
Inductance to 20H
Diode, continuity & logic test
Auto pwr off, data & peak hold
Overload protection
Input warning beeper
Rubber holster

Vann Draper is offering the professional quality LP300 digital multimeter to readers of *Electronics World* at a 30% discount. The LP300 normally sells at an already low price of £81.08 but is available to readers for only £59 fully inclusive of vat & delivery.

The meter is supplied ready to use complete with test leads, rubber holster, battery, operating instructions and a 12 month guarantee.

Data sheets for all products are published on our web site at www.vanndraper.co.uk including the new pc based 20MHz 40Ms/s digital scope & spectrum analyser for £159

To order your meter simply post the coupon to:

Vann Draper Electronics Ltd, Stenson House, Stenson, Derby DE73 1HL.
Or Tel 01283 704706 Fax 01283 704707 Email sales@vanndraper.co.uk

Key Specifications

DC volts	:	200m, 2V, 20V, 200V, 1000V - basic accuracy 0.25%
AC volts	:	200m, 2V, 20V, 200V, 750V - basic accuracy 1.0%
DC current	:	200uA, 2mA, 200mA, 10A - 200mA & 10A fuse protection
AC current	:	200uA, 2mA, 200mA, 10A - 200mA & 10A fuse protection
Resistance	:	200ohm, 2k, 20k, 200k, 2M, 20M - protection to 500Vrms
Capacitance	:	20nF, 200nF, 2uF, 20uF, 2000uF - by test leads or socket
Inductance	:	2mH, 20mH, 200mH, 2H, 20H - by test leads or socket
Frequency	:	2kHz, 20kHz, 200kHz, 2MHz, 20MHz - auto ranging
Size and weight	:	200 x 95 x 55mm, 500g (with holster)



Vann Draper Electronics Ltd

The test & measurement specialists

www.vanndraper.co.uk

Equipment from Grundig, Kenwood, Hameg, Tektronix, Hitachi, Fluke, Avo and many more.

Use this coupon for your order

Please supply me:

..... LP300 multimeter(s) at £59.00 inc vat & del

Name:

Address:

Tel No:

Total £

Cheques payable to Vann Draper Electronics Ltd or debit my visa, mastercard or switch card:

Card type:

Card No:

Expiry date:

Switch iss No:

Signature:

Overseas readers can still obtain this discount but carriage charges vary according to country. Please telephone, fax, email or write to Vann Draper.

CIRCLE NO.119 ON REPLY CARD

Please quote *Electronics World* when seeking further information

chips, it occupies 3k 12-bit words of on-chip program memory. It can be stored in the on-chip flash memory of an SX chip and executed as needed to run compiled Java code. The PC-based integrated development environment lets the designer communicate with a VM resident on an SX chip for source-level debugging, variable inspection and setting multiple user-defined breakpoints. It is based on the Java card specification with modifications to improve performance in memory-constrained embedded applications. For example, strings have been added so operations do not need to be done serially, and native methods have been included that can call routines written in assembly language. It runs on a

50MHz, 50Mips Scenix controller, which has 256byte of SRAM and 4k 12-bit words of flash program memory on chip. The controller lets the VM execute Java byte code at up to 1Mips, and the 1k remaining memory can be used for other functions.

Scenix
Tel: 001 650 210 1500

Coaxial connector

Radiall has launched the UMP surface mount coaxial connector comprising a board-to-board link and adaptor. Footprint is 4.4 by 3.6mm and height 2mm when mated. The receptacle and plug weigh 0.03 and 0.08g respectively and mating can take place after the PCB has been installed. Frequency range is dc to 6GHz. Applications include 900 and



1900MHz mobile phones and portable computing devices. VSWR is 1.02:1 at 900MHz, 1.06:1 at 1800MHz and 1.16:1 at 5GHz. It can be mounted on the PCB or used as an edge connector. An extraction tool is provided to disengage the connector. The tool, when inserted, eases up the retaining clip letting the receptacle be

withdrawn without damaging the retaining mechanism or the connector.

Radiall
Tel: 020 8997 8880

1.8V micros

Hitachi has announced the H8/3847R microcontroller with a 16MHz 8 and 16-bit CPU core that operates from 1.8 to 5.5V. Applications include domestic and industrial electricity meters and battery powered data loggers and sensors. It is pin compatible with the H8/3847 but can execute a 16-bit addition in 250ns and an 8-bit multiply in 1.75µs. Its LCD controller can display up to 160 segments and its asynchronous event counter counts external pulses while the device continues at low power operation. The 32kHz sub-

BOOK TO BUY

Low-Power CMOS VLSI Circuit Design

A comprehensive look at the rapidly growing field of low-power VLSI design



Low-power VLSI circuit design is a dynamic research area driven by the growing reliance on battery-powered portable computing and wireless communications products. In addition, it has become critical to the continued progress of high-performance and reliable microelectronic systems. This self-contained volume clearly introduces each topic, incorporates dozens of illustrations, and concludes chapters with summaries and references. VLSI circuit and CAD engineers as well as researchers in universities and industry will find ample information on tools and techniques for design and optimization of low-power electronic systems.

Topics include:

- Fundamentals of power dissipation in microelectronic devices
- Estimation of power dissipation due to switching, short circuit, subthreshold leakage, and diode leakage currents
- Design and test of low-voltage CMOS circuits
- Power-conscious logic and high-level synthesis
- Low-power static RAM architecture
- Energy recovery techniques
- Software power estimation and optimization

UK Price: £54.50 Europe £55.50 ROW £57.50

** Price includes delivery and package **

Return to Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following title:

Low-Power CMOS VLSI Circuit Design

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Access/Mastercard/Visa/Cheque/PO

Cheques should be made payable to Reed Business Information

Credit card no _____

Card expiry date _____

Signed _____

Give your career a medical.

totally change your life



totaljobs.com

You're amazing. We want you to stay that way, and perhaps get even better. Visit totaljobs.com, use our free Career Health Check and discover your true vocation. With a new path prescribed, you'll be able to find thousands of interesting jobs. Indeed, we're adding vacancies all the time, to make us the UK's leading recruitment website. You can post your CV on site, apply for jobs online, and even be notified of any new jobs that might suit you. So, for a career booster, take a look at totaljobs.com

IN ASSOCIATION WITH
**ELECTRONICS
WORLD**


BOOK TO BUY

Frequency Synthesis by Phase Lock

Frequency synthesis is an important element in the design of all communications equipment, but has taken on new life recently with the advent of new hand-held wireless devices. This technology not only allows wireless transmitters to change frequencies quickly, but also gives high reliability and security in transmissions. Thus, mobile devices such as cell phones can utilise this technology to change frequencies until a suitable one is found for the location in which it is being used.

- Emphasises the fundamentals of frequency synthesis
- Based on a course that Dr. Egan has been teaching for over 20 years at Santa Clara University
- Provides a link to the Wiley ftp site for the use of associated MATLAB exercises
- Taken together with Phase Lock Basics by the same author, the two books provide readers with complete coverage of the field.

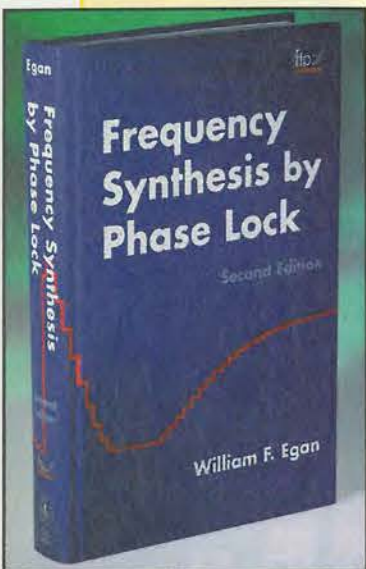CONTENTS Introduction; The Elementary Phase-Locked Synthesizer; Modulation, Sidebands and Noise Spectrums; Frequency Dividers; Phase Detectors; Higher Order Loops; Sampling Effects; Architectures; Large-Signal Performance, Natural Acquisition; Acquisition Aids; Spectral Purity; Computer Aided Engineering.



UK Price: £64.00 Europe £66.50 ROW £69.00

** Price includes delivery and package **

Return to Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following title:

Frequency Synthesis by Phase Lock

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Access/Mastercard/Visa/Cheque/PO

Cheques should be made payable to Reed Business Information

Credit card no. _____

Card expiry date _____

Signed _____

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

oscillator allows the use of various operating modes, including module standby and watch mode, where the oscillator can be used to provide the timebase for a real time clock. It comes in a 100-pin QFP or TQFP.

Hitachi
Tel: 01628 585163

Single-chip modem

Insight Memec has launched a single-chip modem semiconductor that provides one interface for connection to any telephone network in the world. Developed by Conexant Systems, the SmartSCM combines a modem controller, data pump, ROM, RAM and a universal silicon DAA telephone-network interface. It includes the functions needed to incorporate global internet connectivity into internet appliances such as game consoles and handheld devices. Versions support V.32 bis, V.34 and V.90 modem modulations. Because the devices are pin-compatible, users can start with a lower-speed modem modulation and migrate to a higher speed without changing the hardware design. It comes in a 128-pin TQFP.

Insight Memec
Tel: 01296 330061

20MHz function generator

Kenwood has introduced a 20MHz microprocessor controlled programmable function generator. The FGE 1202 has a frequency range of 0.2Hz to 20MHz in eight decade ranges with an accuracy of 0.05 per cent in frequency lock mode. Wave shapes include sine, square, triangle and dc. Output level is variable up to 20V with additional attenuation of -20 and -40dB. Internal and external sweep are standard. Microprocessor control lets the start and stop frequencies



be digitally set and run in logarithmic or linear modes sweeping positively or negatively as selected. An integral 16 by 2 backlit LCD provides frequency, parameters, set up and operational information. A nonvolatile memory lets up to 30 setups be retained or can be used to cycle test conditions for repetitive applications. An RS232 interface lets the unit be controlled and data saved to and loaded from a PC. An optional Windows software package supports the interface. Features include TTL output, AM and FM modulation modes, symmetry and dc offset.

Kenwood Electronics
Tel: 01923 655292

Safety supplies

Acal has developed two metal-cased power supplies for safety-critical applications. The VLT100 is in an enclosure measuring 97 by 146 by 36mm. Power density is 0.37W/cm³ and typical efficiency at full load 86%. Weight is less than 340g and it can be convection cooled up to full rated output at 50°C. Single output supplies have outputs of 3.3, 5, 12, 15, 24 or 48V, while multiple output units have ±3.3, ±5, ±12, ±15 and ±24V. All accept inputs from 90 to 264V ac. The VLT130 comes in the same size case. Power density is 0.43W/cm³ and typical efficiency at full load 82%. Weight is 355g. Quad-output supplies come with 3.3 and 5V outputs as standard, and options of ±12, ±15 and 24V dc outputs. The 3.3V output provides up to 16A and the 5V output up to 14A. Single-wire current sharing is available across V₁ and V₂ outputs for dual-redundant or power sharing applications. The single-output version has dc outputs of 3.3, 5, 12, 15, 24 or 48V.

Acal
Tel: 01252 858585

BOOK TO BUY

THE INVENTOR OF STEREO The Life and Works of Alan Dower Blumlein



Robert Charles Alexander

Post your completed order form to:-

Jackie Lowe, Room L514, Quadrant House,

The Quadrant, Sutton, Surrey, SM2 5AS

Phone your credit card order: 020 8652 3614

Fax your completed order form to 020 8652 8111

UK Price: £17.50 Europe £20.00 ROW £22.00

Paperback price includes delivery

How to pay

(Blumlein) paperback

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____ Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

This book is the definitive study of the life and works of one of Britain's most important inventors who, due to a cruel set of circumstances, has all but been overlooked by history.

Alan Dower Blumlein led an extraordinary life in which his inventive output rate easily surpassed that of Edison, but whose early death during the darkest days of World War Two led to a shroud of secrecy which has covered his life and achievements ever since.


His 1931 Patent for a Binaural Recording System was so revolutionary that most of his contemporaries regarded it as more than 20 years ahead of its time. Even years after his death, the full magnitude of its detail had not been fully utilized. Among his 128 patents are the principal electronic circuits critical to the development of the world's first electronic television system. During his short working life, Blumlein produced patent after patent breaking entirely new ground in electronic and audio engineering.

During the Second World War, Alan Blumlein was deeply engaged in the very secret work of radar development and contributed enormously to the system eventually to become 'H2S' - blind-bombing radar. Tragically, during an experimental H2S flight in June 1942, the Halifax bomber in which Blumlein and several colleagues were flying, crashed and all aboard were killed. He was just days short of his thirty-ninth birthday.

For many years there have been rumours about a biography of Alan Blumlein, yet none has been forthcoming. This is the world's first study of a man whose achievements should rank among those of the greatest Britain has produced. This book provides detailed knowledge of every one of his patents and the process behind them, while giving an in-depth study of the life and times of this quite extraordinary man.

Contents

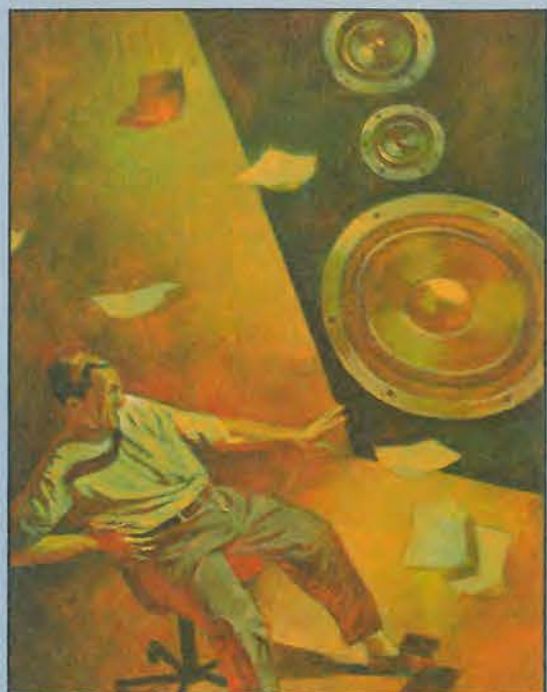- Earliest days
- Telegraphy and telephony
- The audio patents
- Television
- EMI and the Television Commission
- The high-definition television period
- From television to radar
- The story of radar development
- H2S - The coming of centimetric radar
- The loss of Halifax V9977
- Legacy
- To Goodrich Castle and beyond



In this third article on the topic of room acoustics, John Watkinson explains the importance of a loudspeaker's off-axis response.

SPEAKERS' CORNER

In the first two parts of this debate, I showed that the room and the speaker are inseparable and ideally should be considered as a system. This is not always possible – especially in domestic installations where the speaker designer has little control. However, there are certain criteria that loudspeakers need to meet. Whatever the domestic acoustic may be, meeting these will improve results.

In a stereo system, two speakers

can only give spatial accuracy for virtual sound sources located between them. Reverberation in the listening room then provides ambient sound from all remaining directions.

The resulting reverberant sound field can never be a replica of that at the microphone, but a plausible substitute is essential for realism and its absence results in an unsatisfactory result. Clearly the traditional use of heavily damped rooms for monitoring is suspect.

Achieving reality

If realism is to be achieved the direct sound and the reverberant sound must both be uncoloured. Figure 1 shows that most of the reverberant sound in a listening room is due to excitation by sound radiated in directions other than the central axis of the loudspeakers.

It is thus clear that the quality of the off-axis sound is just as important as the quality of the on-axis sound. Concentrating on the on-axis performance to the detriment of the off-axis performance produces a coloured reverberant field.

An uncoloured reverberant field requires that the loudspeaker should produce the same level and have the same frequency response over a wide range of directions. The output may fall as the off-axis angle increases, but it must do so gradually.

Figure 2 shows that the directivity function or polar response should be broad and independent of frequency. If the directivity varies with frequency, the frequency response off-axis will not be the same as it is on-axis.

It follows that for realistic results the polar diagram of the loudspeaker and its stability with frequency is

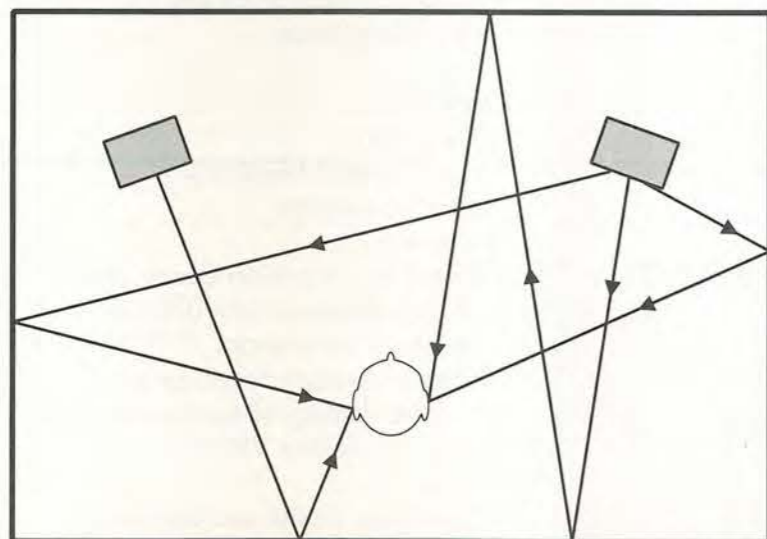


Fig. 1. Reverberant sound is produced off the axis of the speakers.

extremely important. The necessary accuracy is difficult to achieve. The most accurate commercially available units in this respect are the Quad ESL-63 which use an electrostatic phased array and the Manger planar speaker (produced in Germany) which achieves the same result using propagation delays in the diaphragm.

Crossover problems

A common shortcoming with most loudspeaker drive units is that output becomes more directional with increasing frequency. This is the reason for the multi-way speaker with a frequency-dividing crossover between the units. Unfortunately if the individual drive units are not appropriately specified, crossing over between them produces a step in the directivity.

Figure 3a) shows that although the frequency response on-axis may be ruler flat, giving a good-quality direct sound, the frequency response off-axis may be quite badly impaired as at Fig. 3b). In the case of a multiple drive unit speaker, if the crossover frequency is too high, the LF unit will have started beaming before it crosses over to the tweeter which widens the directivity again. Figure 3c) shows that the off-axis response is then highly irregular. As the off-axis output excites the essential reverberant field, the tonal balance of the reverberation will not match that of the direct sound.

The skilled listener can determine the crossover frequency, which by definition ought not to be possible in a good loudspeaker. Figure 3 also shows why the listening-from-the-next-room test, mentioned last month, works. The radiation leaving through the open door of the listening room will have the frequency response of Fig. 3c) and the colouration will be audible.

Subconscious effects

In the listening room, the resultant conflict between on- and off-axis tonality may only be perceived

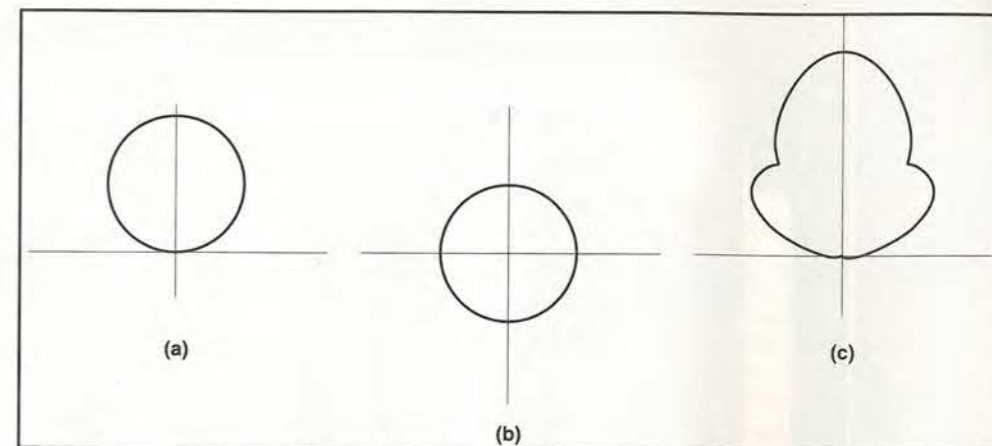


Fig. 2. Directivity functions for loudspeakers. a) cosine – good, b) omni – good, c) typical speaker with lobes – poor.

subconsciously. It may cause listening fatigue where the initial impression of the loudspeaker is quite good, but after a while one starts looking for excuses to stop listening. The hallmark of a good loudspeaker installation is that you can listen to it indefinitely and that of an excellent installation is where one does not want to stop.

Unfortunately such instances are rare. More often loudspeakers are used having such poor off-axis frequency response that the only remedy is to make the room highly absorbent so that the off-axis sound never reaches the listener. This has led to the well-established myth that reflections are bad and that extensive treatment to make a room dead is necessary for good monitoring.

The dead-room approach has no psychoacoustic basis and has simply evolved as a practical way of using loudspeakers having poor directivity. The problem is compounded by the fact that an absorbent room requires more sound power to obtain a given SPL. Consequently heavily treated rooms require high power loudspeakers, which have high distortion and often further sacrifice polar response in order to achieve that high power.

Coloured ears

A worse consequence of monitoring


using speakers with a poor off-axis response is that the user's ears become first accustomed and then imprinted with the coloured reverberant sound. In other words prolonged exposure to a poor speaker actually distorts one's ability to assess the quality of another speaker.


I discovered this the hard way when a prototype speaker with a ruler-flat frequency response was loaned to an experienced audio engineer who had worked for years with the same pair of nameless speakers.

The loaned speaker was returned because it was said to have a peak in its response – which it did not have. After a polite enquiry, the frequency of the peak was estimated. This turned out to be exactly the crossover frequency of the loudspeakers to which this engineer was accustomed. He was using a two-way speaker having a small dome tweeter. This requires a high crossover frequency at which the woofer is beaming badly. The resultant is a serious notch in the off-axis power response.

I haven't named the speaker concerned because there are any number of speakers like it and they all sound pretty much the same. These are called 'bookshelf loudspeakers' because by putting a plank across a pair of them a useful bookshelf can be made. The transducers are best left disconnected. ■

Fig. 3. In a), directivity may be narrower at high frequency, F_H , than low, F_L . b) Frequency response off-axis is then impaired. c) Directivity will improve as the speaker crosses over to the tweeter, but this will put a dip in the off-axis response.

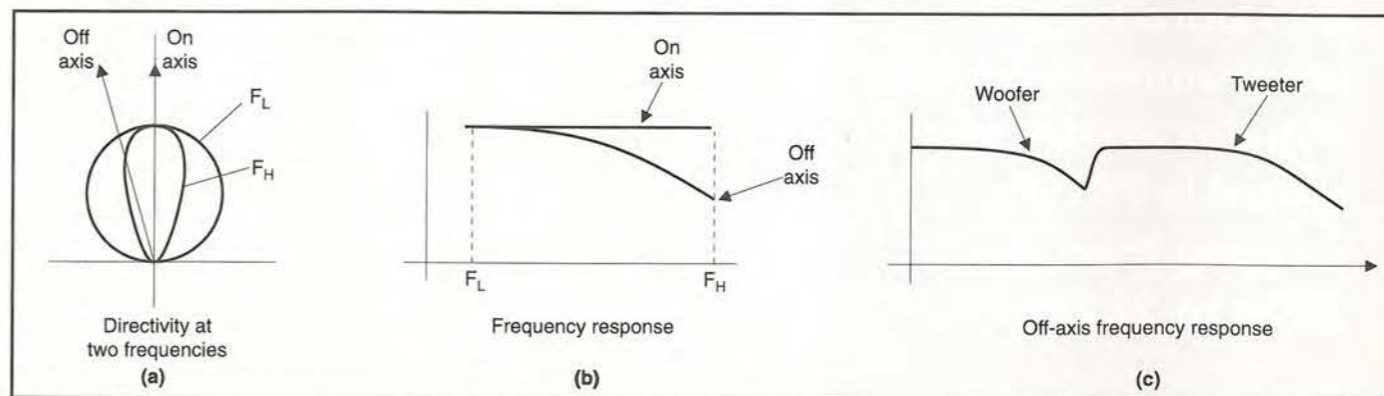

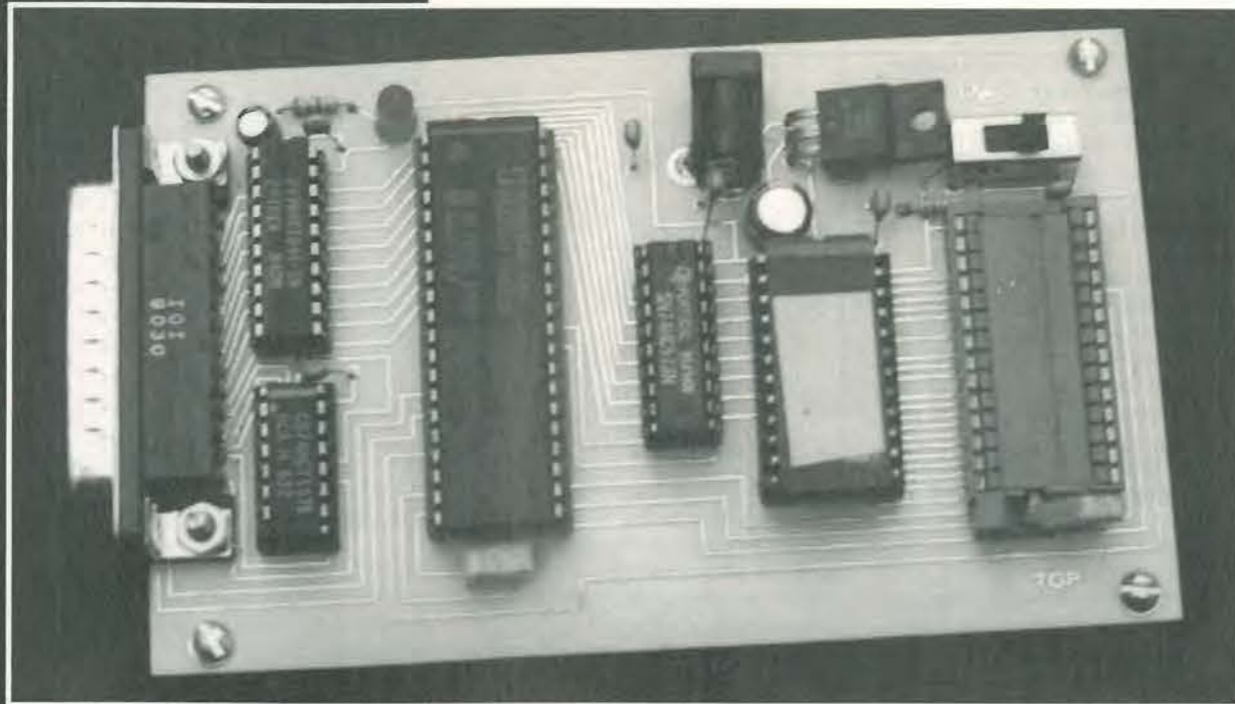

Programming EPROMs?

If you are still using UV-erasable EPROMs, this programmer should save you an inordinate amount of time. Designed to interface with anything from a 386 PC upwards, Guo-yin Xu's parallel port programmer handles popular electrically-erasable PROMs ranging from the 2804 to 28256.

When developing microprocessor and microcontroller systems, you usually need external memory ICs. Ultra-violet erasable PROMs and electrically-erasable and programmable PROMs, i.e. EPROMs and EEPROMs, are two major non-volatile memory alternatives used for storing data or control code in a digital system. They hold what is referred to as the 'firmware.'

The main advantages of EEPROM over EPROM are that it requires no erasure before reprogramming, and it requires only one 5V, or lower, rail. The only disadvantage is that EEPROMs still cost more than their equivalent EPROMs. But the price gaps are becoming narrower or insignificant, especially for the low capacity components.

When you begin developing a project, you might have to modify your code frequently. If that is the case, then you would be better off using EEPROM rather than EPROM. If you opt for EPROM, although the device may

be slightly cheaper, you will have to buy an ultra-violet EPROM eraser and wait 15 minutes for erasure. During such a design phase, an EEPROM programmer is invaluable as a quick and economical project development tool.

Programmer for electrically erasables

The PEE-1 parallel port EEPROM programmer described here, and shown in the photograph, is just for that purpose. It programs the most popular,

28(C)04
28(C)16
28(C)64
28(C)256

EEPROMs, and it accepts both binary and Intel hex format files.

The programmer also contains a unique feature that lets you demonstrate some of your programming results using the programmer itself, so you won't have to build a lot of prototypes. This is particularly helpful to the beginning user.

It works with early computers too

The PEE-1 programmer was designed to be used with most existing PCs with original or standard parallel ports. It has been successfully tested on a number of PCs, ranging from turbo XT to 386, 486, and Pentium PCs.

At the circuit's heart is the Intel 8031/8051 microcontroller. The entire circuit comprises five ICs. Octal buffer IC₁ is a 74LS541 with three-state outputs. It acts as an interface between the PC's parallel port data register and the programmer.

When the control-voltage level at IC₁ pin 1G and 2G, which are tied together, goes 'low', the buffers are enabled and 8-bit data from the PC is transferred through it to the 8031's port P1, that is pin 1 to pin 8. If the control level is set 'high', then the 3-state outputs are in high-impedance and so the data is completely blocked. The control voltage is applied by the 8031's port 3 bit 0, marked as P3.0.

A 74LS157 quad 2-to-1 data selector, IC₂, is responsible for transferring data from the 8031 to the PC via the parallel port's status register, pins S4-S7. Because the status register is not completely available to the outside world, a byte of data input to the PC is divided into two steps.

First the low-order four-bit data D0, D1, D2 and D3 – called the low-nibble – are transferred. Then the high-order four bits D4, D5, D6 and D7 – the high-nibble – are transferred. Select pin S on IC₂ controls these two steps. When S is in logical '1' level, the low-nibble is selected; when S is logical '0', the high-nibble is selected. It is easy to write software to combine the two nibbles into a byte, including the inversion of bit S7.

Microcontroller IC₃ is an 8031 type. It controls the programmer operations and communications with the PC. As you may know, the 8031 has four 8-bit registers, called ports. Port 0 includes pins 32-39 and carries both data and the low-byte address in multiplexed form. Port 2 includes pin 21-28 and forms the high-byte address register. In this application, port 1 on pins 1-8 is used as a data i/o port between the PC and the programmer, and port 3 on pins 10-17 is used for status and control functions.

Capacitor C₄ connected to 8031's reset pin provides reset operation to put the chip in known state after power up. The LED showing the system status connects to port P3, bit 5 on pin 15. Port P3, bit 0 connects to IC₁ pin 1G and 2G to control the tri-state buffers as discussed above.


PC parallel ports, old and new

This diagram shows the pin-out of the original IBM PC parallel port's DB-25 female connector. This port's hardware consisted of three 8-bit registers: the data register, D₀₋₇, the status register, S₀₋₇, and the control register, C₀₋₇. Each register was accessed using a unique address.

Originally, the data register was designed to output data to printer, so it was unidirectional and has only output capability; the status register was designed to flag the printer's status, providing signals such as 'paper empty', so it has input only capability. But the control register has input and output capability.

A few bits in the status and control registers were not used, so these bits, or more precisely the pin that represent them, are not seen on the connector. Furthermore, some bits are inverted for convenience.

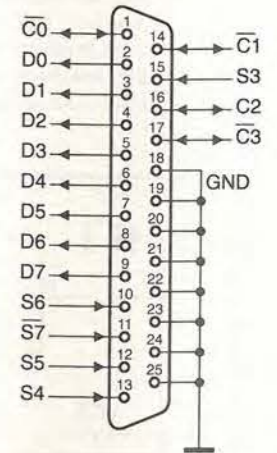Mnemonics indicating inverted signals are often shown with an 'overscore', as opposed to an underscore, or prefixed with a slash character by the way.



Talking to each other

How do the PC and the programmer communicate each other? One solution involves a special control/status signal line between the PC and the programmer that operates a 'polling' scheme. This special line on the programmer side is connected to port 3, bit 4. On the PC's side it connects to the parallel-port control register bit C0, which is pin 1 on the DB-25 connector shown in the separate panel.

The line has a special property in that if, and only if, both sides are held in logical high, state then the line is logic 'high'; otherwise, if any side becomes 'low', the entire wire will be 'low'. Such a property is usually implemented using inverter gates with open-collector outputs.

Another scheme for data communication between a PC and a programmer is achieved through the 8031's external interrupt sources. The 8031 has two external interrupt pins: /INT0 on pin 12, or P3.2, and /INT1 on pin 13, or P3.3.

When a low external signal is applied to either pin for some period of time, the 8031 suspends its current instruction execution and jumps to execute the instructions written for that specific interrupt service routine. Data transfer between a PC and programmer under such an 'interrupt-driven' scheme can take place much faster than the normal polling scheme, so this is what I've implemented here for EEPROM programming.

Specifically, interrupt 0 is employed for EEPROM writing and erasing routines, while interrupt 1 is used for EEPROM reading routine.

Interruptions

When using interrupt 1 to read EEPROM contents, a typical session would be as follows. First, the PC sends a 'high' level signal to the parallel-port control register bit /C1, on pin 14, where it is inverted to a 'low' level signal to activate the 8031's /INT1.


It will take several machine cycles for the 8031 to respond to the interrupt, so, the PC cannot immediately read the data. Rather it needs to wait for that short period of time. The 8031's P3.1 pin, which connects to the parallel-port status register bit S3, signifies whether data is actually available.

When the 8031 enters the interrupt service routine, it first puts this pin 'low'. Only after it has read the data from EEPROM and put the data to port 1 does it pull this pin 'high' to signify that data is available. So the PC keeps checking pin S3 until it becomes 'high', then it reads in the data from the status port.

A polling scheme is used for the housekeeping, such as sending a command from the PC to the programmer, or sending the number of bytes to be written to the programmer. I use the polling scheme here because in such cases the number of data bytes to be sent is only one or two, so the speed is not important. Furthermore, human speed to touch the keyboard is still much slower than that.

An 8MHz ceramic resonator instead of a crystal provides the system clock signal. The resonator has its own built-in capacitors so no external capacitors are needed.

Hands-on Internet

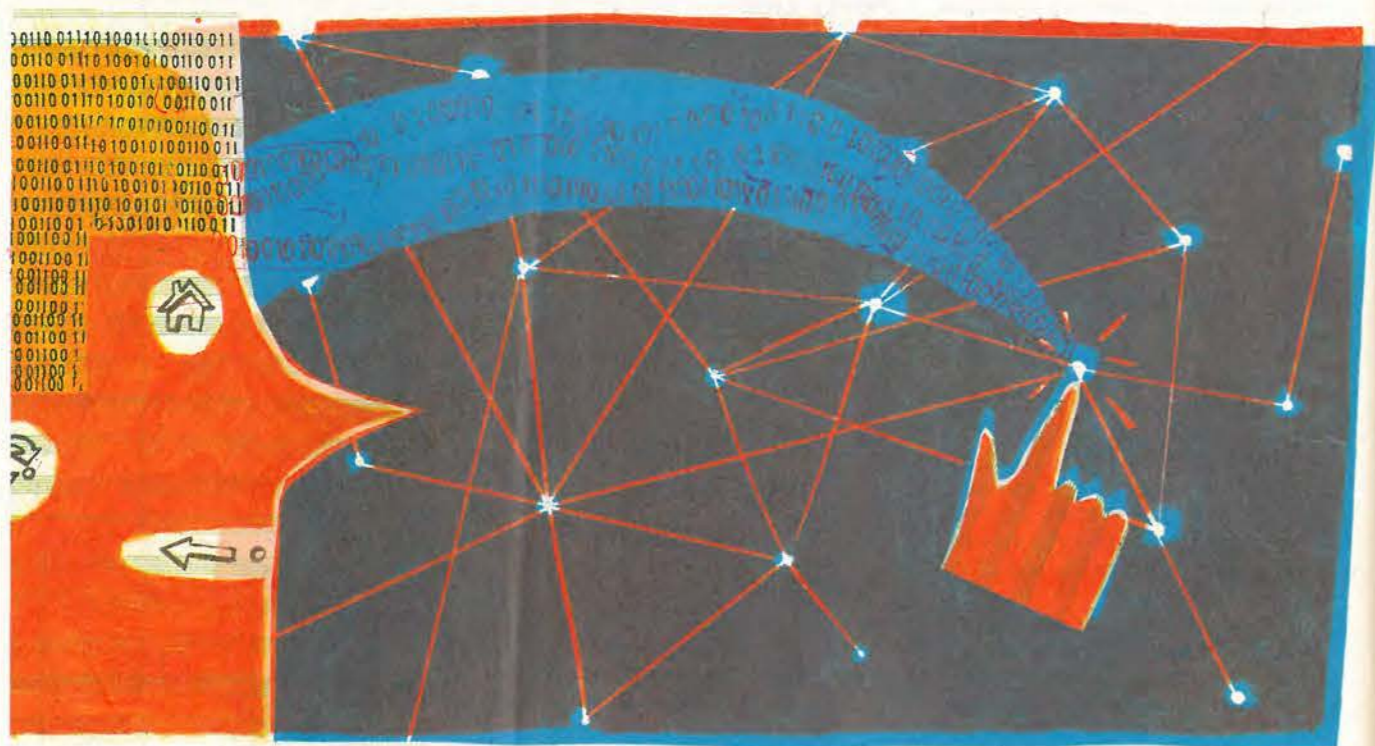

Variable-gain circuits

Cyril Bateman has been using the internet to see what he could find on variable gain circuits, including those that feature in Dolby B, compressors and automatic gain and level controllers.

In the December 1999 issue, I introduced a wide-bandwidth AGC circuit based on the OPA660 IC from Burr Brown. This circuit provided a constant output voltage when presented with a varying input. Other circuits provide a similar automatic gain-control mechanism to dramatically boost low-level input signals. Some also reduce high-level inputs, to allow a steadily increasing output voltage with input increase. When a known input signal is to be processed, a gating circuit can be

used to 'clamp' or 'key' the circuit's output voltage levels to a reference in the signal being processed. One early widely used IC that I recall, the Motorola MC1352, was used to key the video IF stages of domestic colour television receivers almost 30 years ago. This circuit effectively eliminated 'aircraft flutter', which plagued early receivers. Today, similar specialised functions are common for a range of RF signal processing applications. A simple search for AGC on the Global

Semiconductor Data sheet site¹ produced 43 application notes available for download. These covered both specialised and general purpose functions.

Dolby B
Another early variable gain circuit was used to reduce noise levels rather than control circuit gain. The ubiquitous 'Dolby B' circuit was responsible for the universal acceptance of the compact audio cassette.

During recording, loud signals were recorded unchanged, but lesser signal levels received a degree of high frequency boost. A sliding band filter was used to control the frequency and degree of boost. Both varied depending on the immediate spectrum being processed, Fig. 1.

This system's success resulted from a perceived quality improvement playing 'Dolby B' processed tapes on all cassette systems – even those not incorporating the Dolby B playback circuits.

Commencing May 1975, *Wireless World* published in a three part article a Dolby-B design, suitable for home construction by the way.

Compressors

For professional recording systems, an alternative system called DBX was often used. This compressor-expander, or compander, system achieved significant noise reduction without needing frequency boost or cut. Using compression techniques, it reduced the dynamic range of signals recorded to tape in a controlled manner. The DBX system used the rms rectified input signal as its control voltage.

Tape recordings suffer from two dynamic-range restrictions. Tape can overload when presented with high-level signals. Secondly, tape noise becomes intrusive with low level signals. These combine to restrict the usable dynamic range.

On playback, DBX control circuits were used to reverse the process, expanding signals back to their original levels, offering a much increased dynamic range. The system could produce a 110dB dynamic range, subjectively free from noise.

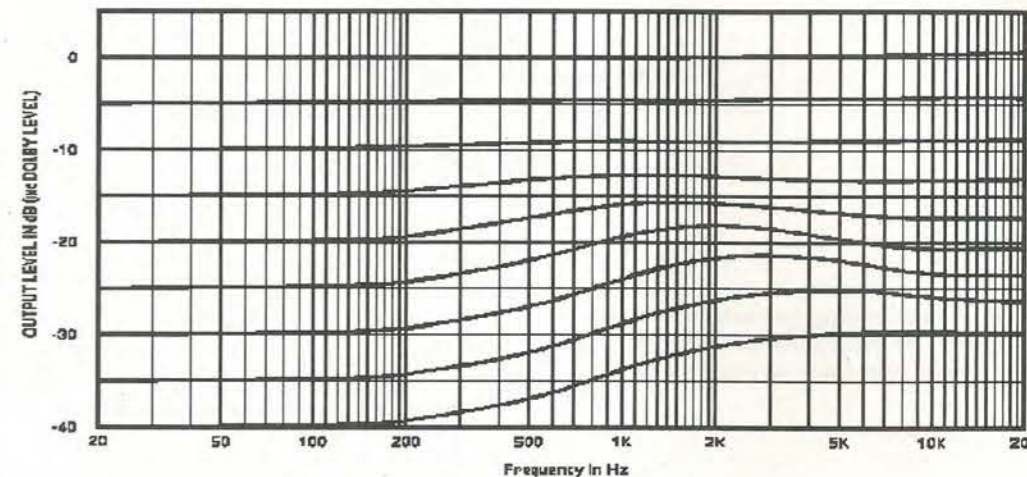


Fig. 1. Depicting the frequency and amplitude of selective boost, applied during the Dolby-B recording processing.

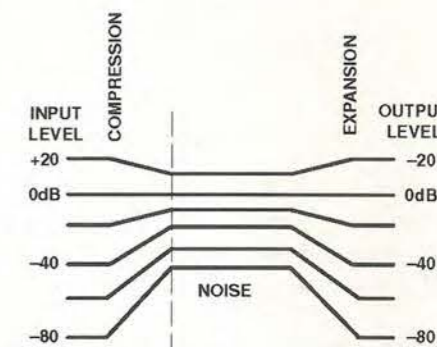


Fig. 2. A 100dB dynamic-range signal compressed to 50dB for transmission (recording), then expanded back to its original dynamic range when received (playback).

A low cost IC, the Signetics NE570/571², was developed to improve the signal-to-noise ratio on crowded telephone circuits. It used exactly this same companding approach, providing a 2:1 compression/expansion of signals. This allows an original dynamic range of 100dB to be transmitted as a 50dB range signal. Reversing this control, it is expanded back to the 100dB range of the original signal, in the process attaining up to 45dB of noise reduction, Fig. 2.

The 570 and 571 each comprise two channels containing a full-wave averaging rectifier, a variable gain cell and a summing node operational amplifier. While this variable-gain function could be provided using conventional OTA circuits, gain of an OTA varies with temperature. Philips designed a low noise, low distortion

and temperature independent, linearised transconductance multiplier gain cell.

Capable of operating well above audio frequencies and introducing little distortion, this IC became

Bugs

As I write, Microsoft has just released a patch to eliminate yet another security weakness in its Windows 95, Windows 98 and Windows 98 SE operating systems. This most recent bug is called 'DOS Device in Path Name'. It is so called because it has been found that when the operating system attempts to read or write to a file which contains certain reserved DOS keywords within its name, it crashes, showing the 'Blue screen of death'.

This file access can be maliciously triggered when you download a Web page that has been embedded with malicious code, when you open an e-mail message on Hotmail, or similar Web-based e-mail service, or simply when you type the code at a DOS prompt. When the computer encounters the sequence of characters and tries to process them, it crashes.


Internet users with the above operating systems – especially those who use a Web based e-mail service – are advised to download this security patch from Microsoft.

Web E-mail breach - 'Dos Device in Path Name'
<http://www.microsoft.com/technet/security/bulletin/MS00-17.asp>



A new twist on web e-mail based bugs. If a Windows computer is forced into processing certain reserved DOS keywords, it crashes displaying a blue screen.

Fig. 3. The NE572 – a compander suitable for use in hi-fi systems – offers high-quality and substantial noise reduction. Its gain-control components have many other uses. Shown here together with an NE5532, it produces a high-performance levelling system.

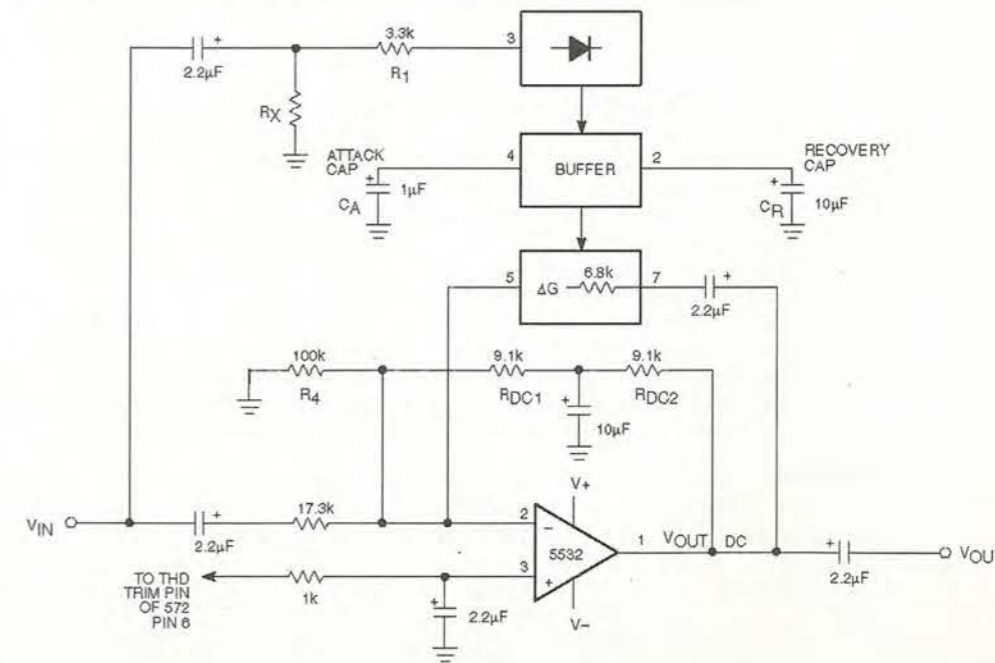

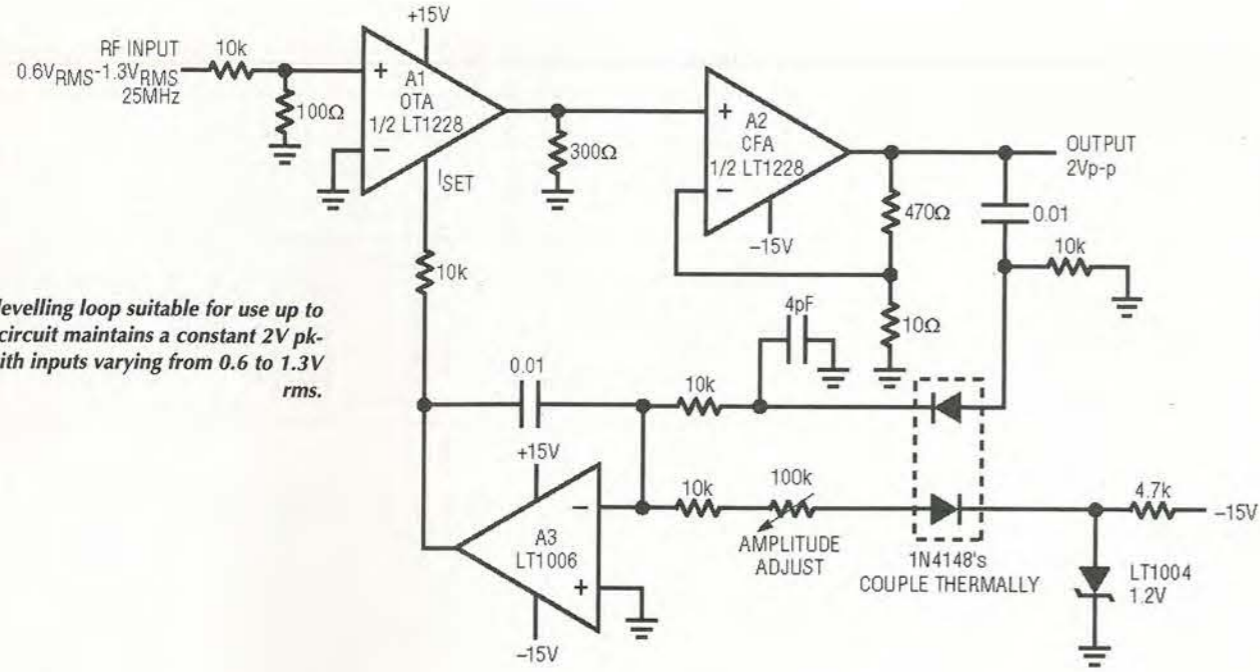


Fig. 4. An RF levelling loop suitable for use up to 25MHz. The circuit maintains a constant 2V pk-pk output, with inputs varying from 0.6 to 1.3V rms.

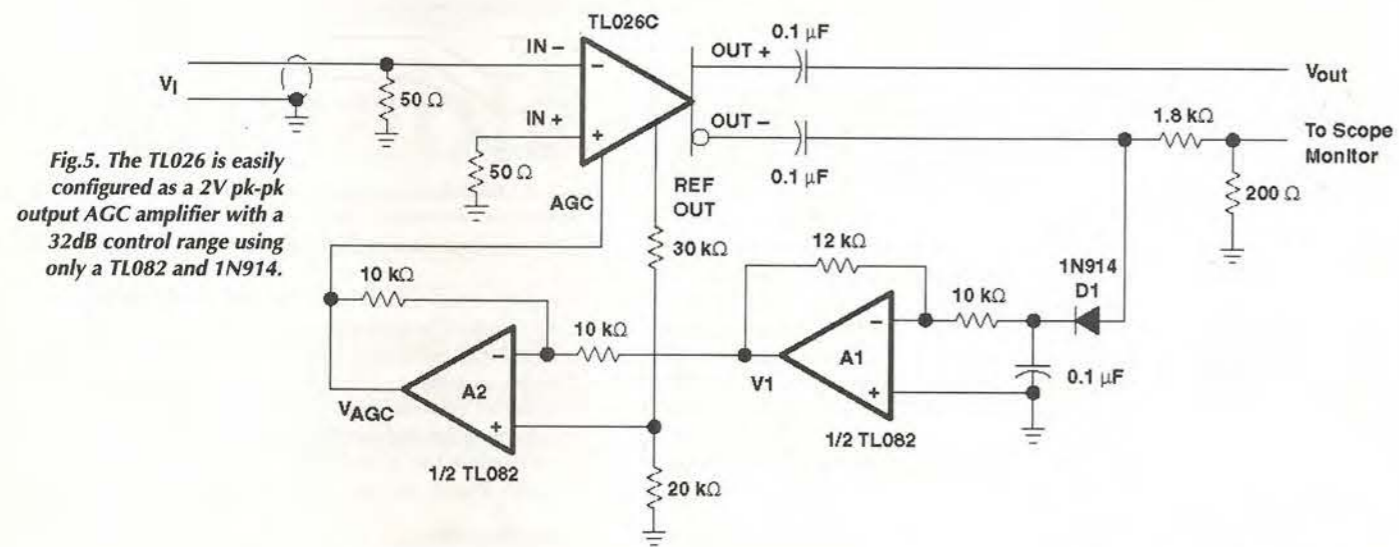


Fig. 5. The TL026 is easily configured as a 2V pk-pk output AGC amplifier with a 32dB control range using only a TL082 and 1N914.

popular for high-fidelity home tape recordings. In November 1978, *Wireless World* published a circuit by D. Harrison using the NE570, which claimed to reduce cassette tape recorder noise by 30dB.

The NE570/571 provides three useful building blocks usable to 1MHz. These can be configured to provide a number of functions other than the simple compander shown in the current data sheet. The original

Signetics Consumer Circuits handbook for the NE570/571 included 12 pages of application circuits. These included a fast-attack, slow-release limiter, a voltage-controlled attenuator, a variable-slope compander and an automatic level-control circuit.

Other variants on these ICs have since been introduced, including the NE572 which has its 0dB reference set at 100mV. This device is intended

for hi-fi studio-quality systems. The SA577/578 provide a resistor-programmable 0dB reference level, adjustable between 10mV and 1V, Fig. 3.

A number of application notes on this topic are available for downloading. But perhaps AN1762, which includes an overview of seven Philips compander chips, provides the best introduction. AN1762 can be downloaded as 8020.PDF from Philips' site².

As discussed in the January issue, many designs rely on the gain control, made possible using a transconductance amplifier. Essentially a variable-gain amplifier, with its gain control driven from a rectified voltage derived from the amplifier's output signal, can be used

More information...

1. Global Data sheet Library <http://www.semi.com.tw>
2. Philips Semiconductors <http://www-us.semiconductors.philips.com>
3. Texas Instruments <http://www.ti.com>
4. National Semiconductor <http://www.national.com>
5. Mitel Semiconductor <http://www.mitel.com>

to provide automatic gain or level control.

Automatic level control

The basic automatic level-control circuit, Fig. 2 from the January 2000 issue, provided performance to 10MHz and 20dB gain control. Addition of an output-driven, half-wave rectifier and gain-control buffer, produces a low-cost, RF levelling stage. This simple circuit features low output drift and distortion. Usable to 25MHz, it produces a constant 2V pk-pk output, with inputs from 0.6V to 1.3V rms, Fig. 4.

For higher frequencies, a number of dedicated, variable-gain-amplifier devices are available. Two that caught my attention, the TL026³ and the CLC520R⁴, offer a large AGC range, wide bandwidth and low phase shift, combined with easy control of gain.

Automatic gain control

The TL026 provides differential inputs and outputs in an eight-pin package. It has a 50MHz bandwidth, peak gain of 38dB, and an AGC range of 50dB. A change in voltage of ±180mV on its AGC pin relative to its reference pin voltage will send its gain from minimum to maximum Fig. 5.

The CLC520 offers an increased bandwidth of 160MHz, a 40dB AGC range and differential input to single-ended output, all in a 14-pin package. Maximum gain of the device is preset using one external resistor. Preset gain can range from +6dB to a maximum of +40dB. Set to +6dB, voltage-controlled gain ranges from +6dB to less than -34dB. Set to +40dB it ranges from +40dB to less than 0dB.

The CLC520 provides high impedance, differential voltage inputs with better than 0.5° linear phase deviation up to 60MHz, and 0.04% signal non-linearity at 4V pk-pk output.

With a gain-control bandwidth of 100MHz, the CLC520 simplifies AGC/ALC loop stabilisation. It can also be used for amplitude modulation and voltage-controlled filters. Gain is minimum with zero volts applied to the gain control input, and maximum with +2V applied. An evaluation board is available both for DIP and SOIC package versions⁴ Fig. 6.

400MHz-bandwidth gain control

The SL6140 integrated circuit was designed by GEC-Plessey Semiconductors, now part of Mitel

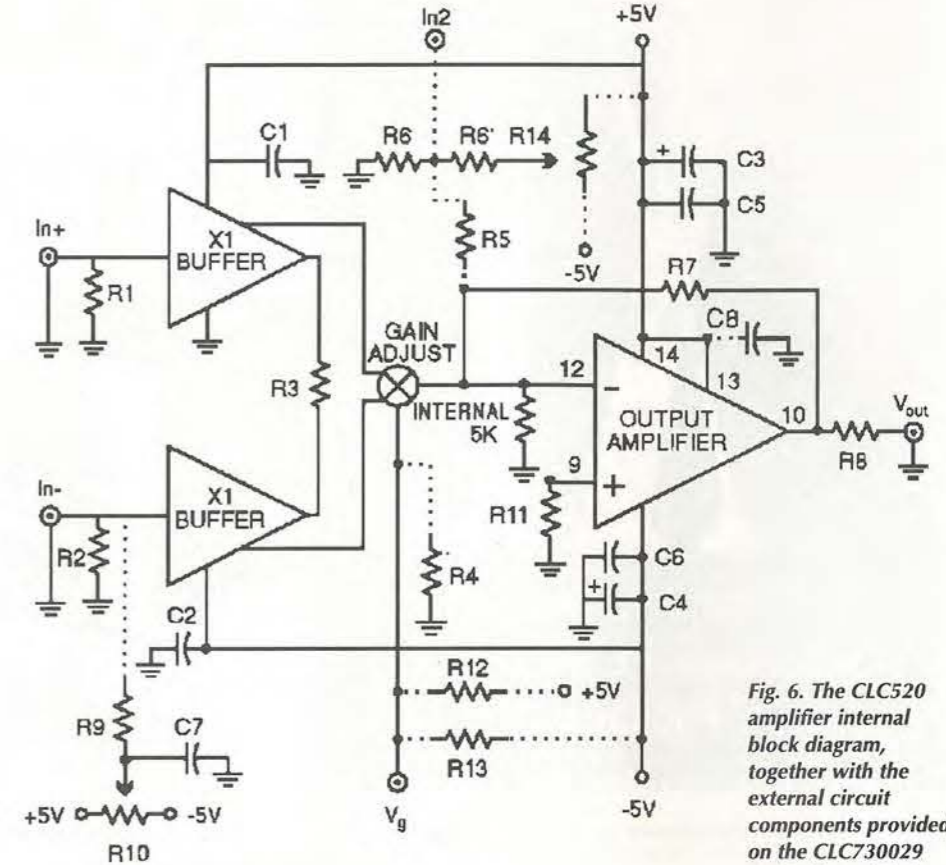


Fig. 6. The CLC520 amplifier internal block diagram, together with the external circuit components provided on the CLC730029 evaluation printed circuit board.

Semiconductor⁵. Housed in an eight-pin package, this design offers a 70dB gain control range with a 400MHz bandwidth when loaded with 50Ω.

Its open-collector outputs allow you to trade off gain against bandwidth. Loaded with 50Ω, the device provides 15dB gain and 400MHz bandwidth. With a 1kΩ load, gain increases to 45dB but bandwidth reduces to 25MHz.

By tuning, or matching, the inputs

and outputs of the device to a 50Ω system, gain can be increased. The SL6140 circuit can be used as a high-frequency, tuned AGC amplifier with narrow-bandwidth and high gain. As described in AN45, with input and output stages tuned and matched to a 50Ω system, the circuit can provide a 35dB power gain at 100MHz, Fig. 7.

My next Internet article will explore other, non-standard methods that can be used to control signal amplitudes. ■

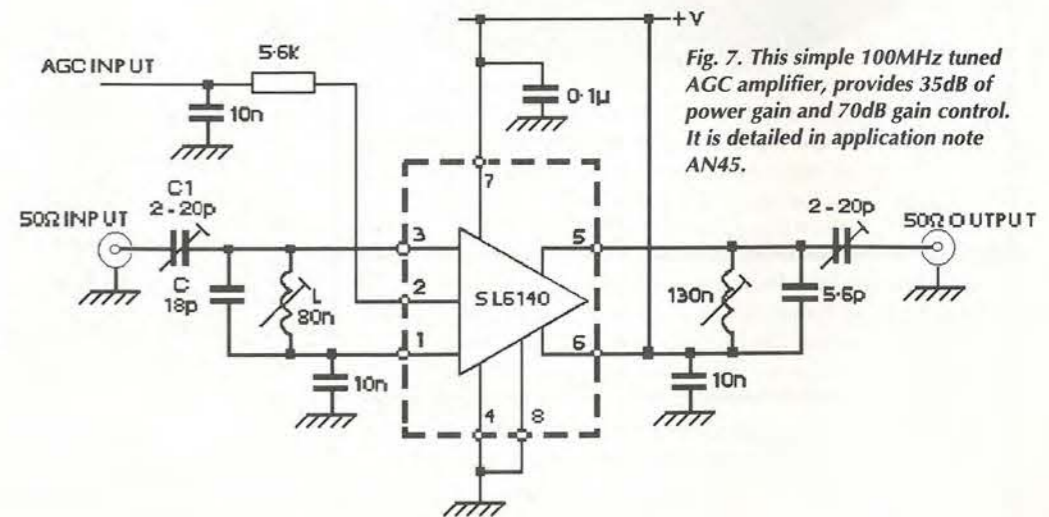


Fig. 7. This simple 100MHz tuned AGC amplifier, provides 35dB of power gain and 70dB gain control. It is detailed in application note AN45.

RANGER XL

The Complete Integrated Schematic PCB Layout Package

Email: sales@seetrax.com Website: www.seetrax.com

Too good for words



The New Ranger XL Series

Ranger 2 for Windows £170
NEW Ranger 2XL £500
NEW Ranger XL from £950
FREE Website Download Demo



Old Buriton Lime Works, Buriton, Petersfield, Hants. UK GU31 5SJ
 Tel: (44) 01730 260062 Fax: (44) 01730 267273

CIRCLE NO.120 ON REPLY CARD

The Headphone Amplifier Box

Balanced or unbalanced microphone or line input to headphone output

Professional portable units operating from an internal PP3 battery or external mains adaptor



- * Precision transformerless balanced input
- * Bridged headphones output drive
- * Sensitivity selectable over a wide range of input levels
- * Low noise and distortion
- * High common mode rejection
- * Loop through facility
- * Extensive RFI protection

The Balance Box (precision mic/line amplifier) –
The Phantom Power Box – **The OneStop** DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphook Hants GU30 7QW
 Information line 01428 751469 Fax 751223
 E-mail contact@confordelec.co.uk
 Web <http://www.confordelec.co.uk/catalogue/>

CIRCLE NO.121 ON REPLY CARD

STEREO STABILIZER 5



- Rack mounting frequency shifter for howl reduction in public address and sound reinforcement.
- Mono box types
- 5Hz Fixed Shift Boards for constructors and equipment manufacturers



- ★ Broadcast Monitor Receiver 150kHz-30MHz.
- ★ Advanced Active Aerial 4kHz-30MHz.
- ★ Stereo Variable Emphasis Limiter 3.
- ★ PPM10 In-vision PPM and chart recorder.
- ★ Twin Twin PPM rack and Box Units.
- ★ PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and movements.

SURREY ELECTRONICS LTD
 The Forge, Luicks Green Cranleigh GU6 7BG
 Telephone: 01483 275997 Fax: 01483 276477

CIRCLE NO.122 ON REPLY CARD

Unique 15% reader discount on Crownhill's range of versatile programmers

LabProg 48

Flagship universal programmer, for Microprocessors, EEproms, Eproms, Flash memory etc.

Normal selling price exclusive of VAT and delivery £356.00, discount price £302.60.

UK delivery £15.00 – next day courier

EC delivery £45 – DHL or UPS normally 1-2 working days

Delivery outside EC £55 – DHL or UPS 2-3 working days

VAT @17.5% is applicable only to UK and EC orders.



Company orders in EC (not UK) where the company is VAT registered and the VAT number is produced at the time of order, can be shipped exclusive of VAT.

SEE PROG

Serial EEprom programmer with enhanced facilities.

Normal selling price exclusive of VAT and delivery £49.95, discount price £42.46.

UK delivery £7.00 (Royal Mail special next day delivery)

EC delivery £10.00 (Swift Registered air mail 5-7 working days)

Delivery outside EC £12 (Swift Registered air mail 5-7 working days)

USA £45 (DHL or UPS 2-3 working days)

VAT @17.5% is applicable only to UK and EC orders.



Company orders in EC (NOT UK) where the company is VAT registered and the VAT number is produced at the time of order, can be shipped exclusive of VAT.

PIC Prog

Universal Pic Programmer

Normal selling price exclusive of VAT and delivery £99.95, discount price £84.96.

UK delivery £7.00 (Royal Mail special next day delivery)

EC delivery £10.00 (Swift Registered air mail 5-7 working days)

Delivery outside EC £12 (Swift Registered air mail 5-7 working days)

USA £45 (DHL or UPS 2-3 working days)

VAT @17.5% is applicable only to UK and EC orders.



Company orders in EC (not UK) where the company is VAT registered and the VAT number is produced at the time of order, can be shipped exclusive of VAT.

Programmers for all occasions

Crownhill Associates is offering an exclusive 15% discount on any product in the company's programmer range to any reader of *Electronics World* until 31 August 2000. This unique reader discount is of particular interest in that the range of programmers on offer is competitively priced even without the discount.

For more details on the of range programmers, see Crownhill's web site, detailed below, and the company's advertisement on page 551 of this issue.

Crownhill Associates Limited, 32 Broad Street, Ely, Cambridge CB7 4AH England, UK.

Tel: +44 (0) 1353 66 67 09 Fax +44 (0) 1353 66 67 10

sales@crownhill.co.uk

<http://www.crownhill.co.uk>

<http://www.edsim2000.com> <http://www.picbasic.co.uk>

<http://www.cambsnet.co.uk> for your FREE Internet account

Order coupon

Please send me:

LabProg 48

SEE Prog

PIC Prog

For which I enclose a a cheque made payable to Crownhill

Associates Limited for £_____ or my credit card details as follows:

Card type (please tick) Visa Master

Card number _____

Expiry date ___/___/___

Name of cardholder _____

Address of cardholder _____

Please post this coupon to Crownhill Associates Limited 32 Broad Street Ely, Cambridge CB7 4AH England, UK.

HyperACTIVE

electronicsWEEKLYonline

“Your passport to a better future”

“What a partnership!”



HyperACTIVE
electronicsWEEKLYonline

A science lab in your PC

Measure:


- Light
- Sound
- Temperature
- Voltage
- Resistance

Via your PC for just £59, excluding VAT – but postage free* and including Pico Technology's renowned PicoScope virtual-instrument package and PicoLog data logging software.

Add:

- pH
- two external temperature probes for an extra £40.

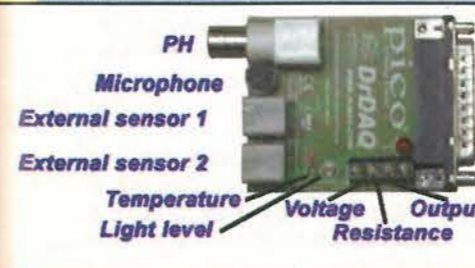*UK postage only; please contact us for o/s carriage prices




General specifications

Connection to PC	Parallel port D type
Input channels	7 internal, 2 internal
Sampling rate	10 to 15kS/s
Overload protection	±30V
Digital outputs	1 ttl, 1-3kΩ Z _{out}
Dimensions	55 by 70 by 20mm

Key features

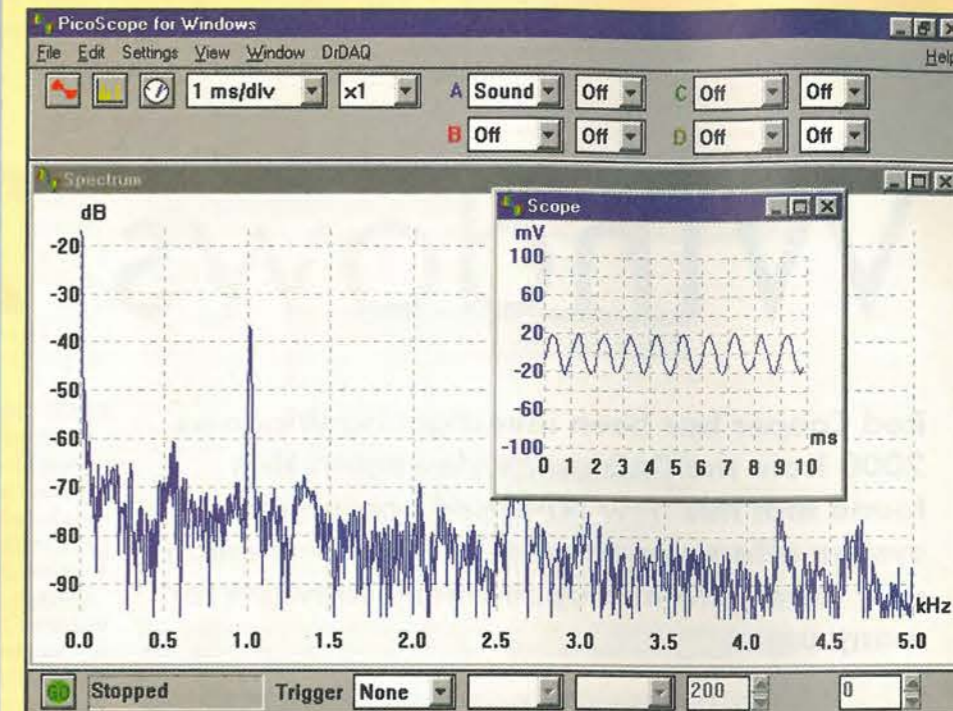- Built-in sensors for light, sound and temperature
- Measures pH
- Complete and ready to use at a fraction of the cost of other data loggers
- Output for control experiments
- PicoLog data logging software included
- PicoScope software included providing virtual oscilloscope, spectrum analyser and more
- Teacher and student software library of science available at www.picotech.com/experiments



DrDAQ samples fast enough to capture audio frequencies. This is a someone whistling measured via DrDAQ's built-in microphone using PicoScope running on a PC under Windows 3.1, 95, 98, NT or 2000.

Built-in sensors

Channel	Range	Resolution	Accuracy
Sound waveform	±100	0.2	Not calibrated
Sound level	55 to 100dBA	1dBA	
Voltage	0-5V	5mV	3% fsd
Resistance	0-1MΩ	100Ω @ 10kΩ 400Ω @ 100kΩ	2% @ 100kΩ 2% @ 100kΩ
Temperature	0 to 70°C	0.1°C	2°C @ 25°C
Light	0 to 100	0.1	Not calibrated

External sensors

pH	0-14	0.02pH	Calibration dependent
Temperature	-10 to 105°C	0.1°C @ 25°C	0.3°C @ 25°C

To obtain your DrDAQ, please fill in and post the coupon below to DrDAQ, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, or fax 020 8652 8111. E-mail jackie.lowe@rbi.co.uk for details of postage-free prices for extra sensors, extension cables and the book, 'Data logging in practice'.

Please send me:

Quantity?	Product	1-off fully-inclusive price
_____	DrDAQ	£69.33
_____	DrDAQ+2 extra temperature sensors	£92.83
_____	DrDAQ+2 extra temperature sensors + pH electrode	£116.33

Total

For which I enclose (please tick if cheque): A cheque payable to Reed Business Information

My credit-card details: Name _____

Card-holder statement address _____

Post code _____

Card type Master Visa Switch Delta

Card number _____ Expiry date ____/____

Signature _____

Please post this coupon to DrDAQ, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, or fax 020 8652 8111.

Windows 2000

Rod Cooper has been investigating Windows 2000 from the CAD user's viewpoint. He's found that this new NT-based operating system offers major benefits, but it will mean new hardware and applications software for many users.

Now that all the hype and commotion surrounding the launch of Windows 2000 is over, it is a good time for a measured examination of what this OS offers those in the field of CAD/CAM.

As most potential purchasers will already know, there are two versions of Windows 2000, one for servers to challenge Linux, Unix and the like, and the other for general business use.

The business version is called Windows 2000 Professional, and is the topic of this review. Of the huge amount of money spent on developing this system, I think it likely that much of it has gone towards the Server version and the new and much talked about Active Directory. A lot of investment seems to have gone into networking generally, and into administration tools, Fig. 1.

The Professional version is an updated version of NT, with most of the best features of Windows 98 fused in to create what amounts to a hybrid NT5.

The concept of using the existing Windows 95/98 interface with the more robust NT kernel is an excellent one, but Windows 2000 is clearly not the all-purpose definitive version of Windows that the pundits were predicting. It is aimed squarely at the business sector, with many features only a business would be interested in. These include control of individual users on multi-user machines, and other similar tasks you would expect only an administrator to perform.

Indeed, on the side of the Windows 2000 box, it makes this perfectly clear in a section labelled "Which Windows is right for you?" by directing certain potential purchasers away from Windows 2000 and back towards Windows 98 as the platform for consumer software, internet access, music, multimedia, games, video, etc. This is a telling statement, but in fact Windows 2000 does have features like

the CD player, sound recorder and media player.

Comments in the computer press centre on the lack of support for such things as 3D hardware. This may be important for certain categories of CAD/CAM user. And there have been comments that some popular high-end AGP graphics cards may give only basic functionality under Windows 2000.

Contrary to what was expected prior to the launch of Windows 2000, Windows 98 is to be developed further with another version currently under development, code-named Millennium. It is scheduled to appear later this year. But Windows launch schedules are, as everyone realises by now, variable quantities.

What hardware will you need?

The absolute minimum for Windows 2000 Pro is a 133MHz Pentium with 32Mbyte of RAM, and a 2Gbyte hard disk with at least 650Mbyte free.

I initially tried loading the system using somewhere near the minimum requirement, but performance was poor. Using the recommended minimum increases the amount of RAM to 64 Mbyte. At this level, Microsoft claims that Windows 2000 is 25 to 30% faster than Windows 98.

However, there are reports that if you use 128Mbyte or 256Mbyte of RAM there are further significant increases in performance, so this indicates the real amount of RAM you should aim for in order to take full advantage of the operating system's potential. There's no point in buying a high performance car and then running it on paraffin.

This increase in speed is offset by the longer boot-up times though. It is interesting to compare boot-up times, as in the Table. This is not a definitive table, but shows a snapshot of the general situation.

Typically, Windows 2000 takes up about 600 to 650Mbyte of hard disk space. There is less opportunity to lighten the load by omitting components with this version of Windows. For example, I always left out screen savers, Paint, the accessibility tools for the disabled, the games, and a few other things when installing Windows 95/98, but with Windows 2000 you get them whether you want them or not. It is possible to leave out some Internet and networking tools. You can also retrospectively delete some of the things you do not want.

If you have 64Mbyte of RAM, don't be surprised if Windows 2000 consumes 50Mbyte or more. This doesn't leave much memory for heavy-duty applications like CAD. Autorouters, for example, like plenty of memory.

Hard disk space and RAM are cheap. But for a small business with a few machines to upgrade and staff to retrain, the costs can mount rapidly. In this case you will do well to assess the benefits of Windows 2000 carefully and weigh them against the real overall cost.

Human requirements

If you use Windows 95 or 98 regularly, then you will take to Windows 2000 easily. Although several changes have been made to the interface, most of the familiar aspects are still there, albeit in an upgraded and altered state.

If you are trained in NT4 with no experience of Windows 95/98 then no doubt you have some catching up to do.

Table. Comparison of boot-up times from various systems.

PC	Op. system	Time
Pentium, 133MHz 32 Mbyte RAM	WIN3.11	40 seconds
	WIN95	1 minute 20 seconds
	WIN98	1 minute 35 seconds
	WIN2000	4 minutes 30 seconds
AMD K6-2-500 128Mbyte RAM, Dual Pentium 400MHz, 256Mbyte RAM	WIN2000	1 minute 30 seconds
Apple Mac G4 450MHz, 128Mbyte RAM	NT4, SP6	2 minutes 50 seconds
	Mac OS 8.6	1 minute

Installation

Windows 2000 comes on a single CD which gives you the choice of upgrading your existing system, if it is based on Windows 95/98 or NT 3.51 or 4.0, or performing a new installation from scratch. It is not possible to upgrade from Windows 3.x.

If you upgrade an existing Windows installation, the procedure is straightforward. It is very similar to setting up Windows 95 or 98.

If you are sitting in front of a PC with an empty formatted hard disk, then you must have a working CD-ROM, preferably one you can boot from, as most modern ones are. The CD is bootable. You may have to alter the bios to include the CD-ROM drive in the boot sequence.

You could have problems if you are without a CD-ROM drive that is bootable, as I was. In this case, the first part of a fresh installation requires four floppy disks to initiate the setup, and these must be downloaded from the CD. These disks did not come with the shrink-wrapped box. This presupposes you have a working CD-ROM drive, but of course if you have a blank hard disk you don't. You could mess around getting it up and running, download the floppy disks and then install, but this is time-wasting.

Happily, I had access to a second PC already running Windows 95 and this did the trick. However, without this second PC, I would have had much more work to do to download these files. I think these four floppies should be included in the box as part of the package.

Before installation you have to decide whether you want to run the FAT32 disk filing system or Windows NT's own specific NTFS system. The advantages of FAT32 over FAT16 were explored in my Windows 98 review in the August 1998 issue.

NTFS has further advantages over FAT32. For example, if you decide to use NTFS you will not find Scandisk in the system tools, because NTFS already does the job of Scandisk as it goes along, i.e. finding disk faults, marking them down and rescuing data.

This is a much superior system because the inevitable hard-disk faults that crop up will be found by NTFS long before you would find them yourself in the normal course of events using Scandisk. Consequently there is less risk of loss of data.

The other advantages consist of a batch of small improvements rather than any large single step. Amongst these are better file integrity, better use of disk space, and support for very large drives up to 2Tbyte, without the loss of performance you would get with FAT.


Like FAT, NTFS still fragments with time, probably more slowly than FAT, so you will still need to defragment on a regular basis. A fragmented NTFS hard disk eventually becomes just as slow. The defragmenter used is from Executive Software, Fig. 2.

However, if you drop FAT in favour of NTFS, you will lose compatibility with systems using FAT. This may be important if you use dual-booting with another operating system and want access to common files.

Also, you will not be able to boot to a plain Dos prompt, which is so useful when things start to go wrong. But if you intend making a clean break with the legacy of the past, the best advice may be to burn your boats and use the demonstrably better NTFS.

Installation takes over an hour, during which time you are asked questions. Earlier versions halted installation until you had answered the questions, which meant that it was not possible to do an unattended installation. This was a particular bind if several machines had to be upgraded.

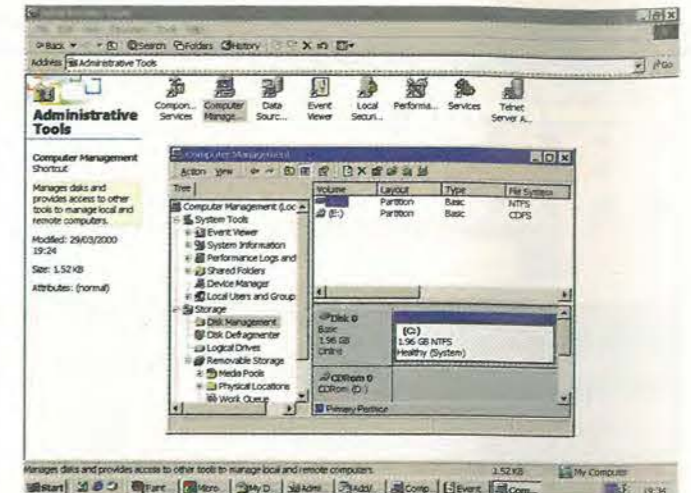An interesting feature in WIN2000 is that you can use a template, answering the questions in advance, so you can start the install and then walk away. If you have several



machines to set up, I recommend this method. It is not difficult to use, and works well provided all the machines are to be set up with an identical configuration.

If you envisage re-installing on a regular basis, or if you use several removable hard disks on one machine, it is also worth considering this method.

It is wise to check your hardware before starting to install 2000. This can be done from the 'Hardware Compatibility List' on the CD, or you can get a more up-to-date list from Microsoft at www.microsoft.com/hcl.

There is a utility called SysPrep that you can use to check if your system will run Windows 2000.

Compatibility issues

Windows 95/98 had a dual-purpose nature in that it was a 32-bit system that had to accommodate existing 16-bit software. Windows 2000 is not dual purpose so it will not run many Windows 95/98 applications and drivers.

For example, I discovered that my Logitech mouse driver would not work. But I found that Logitech was already offering a new driver for Windows 2000, available for free download on its web site. Logitech advises though that you must remove the old mouse driver before installing Windows 2000 over a copy of Windows 95/98.

It seems there is no clear-cut way of finding out which existing products will work and which will not. From what I can deduce from experiments with various programs, those labelled 'WIN95/98 compliant' are unlikely to run, as they may have some 16-bit code. Those labelled 'for WIN95/98' with no mention of NT have a small chance of

Fig. 1. Windows 2000 provides much more information about the system as a whole and the means to configure and adjust, like these 'administration tools'. But as you may be able to see from the lower screen shot, the operating system can use a lot of memory. Compare the total physical memory with that available. Paint Shop Pro V3.11 was used to do the screen capture and it seems to run fine by the way.

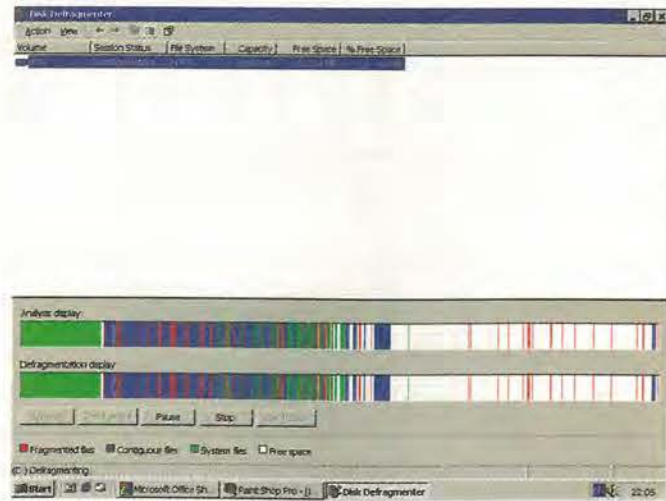


Fig. 2. Windows 2000's defragmenter works with both disk filing system options, i.e. FAT32 or NTFS. Windows NT users will be pleased to see that the defragmenter is now supplied with the operating system.

running, and those with NT in the title will probably run. Adaptec's Easy CD Creator 3.5c – designed for WIN95/98 and NT – is an example of an application that may cause you significant problems. If you succeed in installing this using the Adaptec self-starting installation procedure, it will subsequently prevent Windows 2000 from even starting. If you use the Install Software utility in Control Panel, it will give you a message that the installation cannot proceed.

Adaptec has issued a patch to enable Easy CD Creator 3.5c to be used with WIN2000, and this can be downloaded from their website. However it is only a partial cure because it does not fix the very useful Direct CD part of the Creator suite. To get a working version of Direct CD you are obliged to buy the complete new Easy CD Creator Suite.

Although I have picked Adaptec's software as an example, many other applications fall into the same category. There may or may not be a patch, and the patch may or not do all you require from it. The process of approving applications to run on Windows 2000 is under way but progress seems slow.

It is still possible to run Dos programs in a 'Dos box', even if you have NTFS, provided they don't try to seize control of the machine as some are prone to do. For example, I ran the XTREE Dos utility successfully.

Reading matter

You get two booklets in the box. One is a slim 'Quick Start Guide', about installation, and also describing the setting-up of the system after installation. There is plenty of essential advice in this little guide; how to decide on installation choices, a brief section on the FAT versus NTFS option, a section on improved security against unauthorised users, on creating user/administrator accounts if you are in control of a firm's computer system, configuring passwords, setting up dialling rules, shared resources like printers, etc., and all the other paraphernalia of typical business use. The information is packed tight; skip a sentence and you'll miss something vital.

The other, larger booklet is a 107-page guide which expands on the installation procedure, the use of dual-boot systems, partitioning, and gives a little more information on the differences between FAT and NTFS. It also delves into the basics of working the WIN98-style desktop – essential reading if you are a NT4 convert – the basics of LANs and Internet connections, and adding hardware.

In the appendix are the most important Stop Error Codes, and what to do about them. In the WIN98 manual there was very little in this respect. Including these codes with

Windows 2000 is a useful addition – especially if you are looking at a frozen screen with just an error code on it. It should forestall some calls to technical support.

General view

If you come from a Windows 95/98 background then the desktop will seem instantly familiar. You could be forgiven for thinking you were in Windows 98, but on closer inspection you will find many small changes.

In transferring the Windows 98 interface, almost every aspect has been given an overhaul, generally for the better. Strangely though, small things that were criticised in Windows 95/98, are still there. These may be minor gripes, but they have a tendency of becoming major irritations when they are encountered every working day.

For example, the sheer illogicality of using the 'start' button on the taskbar for shutting down the PC, is anathema to logically-minded people – i.e. most engineers – and has become something of a joke. But it remains. It's as though Microsoft is thumbing its nose at the critics.

Another one is the close/minimise/restore buttons at the top right-hand corner, which are still too close together for some people to click on easily. The 'My Computer' logo which many found rather childish – I admit I renamed this immediately – still persists, as well as 'my documents'. Now, for good measure, there's also 'my network'.

Strangely for a business-oriented operating system, four games are included, and the rather elementary Paint program, as well as a splendid choice of wallpapers. Will the average business user welcome these? On the other hand, most of the changes to the Windows 98 interface that have been made are clearly improvements.

Improved driver handling

Although plug-and-play is a feature carried over from Windows 98 that NT4 users will welcome, there are bound to be times when a third-party driver will still be needed.

In the past, drivers for add-on cards such as modems, video cards, etc., tended to be a bit of a mixed bag. Some were excellent, but others were a source of built-in instability unfairly blamed on the operating system. Of course, you could say that a well-designed operating system would fend off these badly-written third-party drivers, and in a sense this is what Windows 2000 does.

Third-party manufacturers can now have their software approved for use in Windows 2000 by being given a digital signature. With this system, approved drivers are installed easily. The system administrator can set the system so that non-approved drivers can be halted on installation, or a warning message displayed to the effect that, if you go ahead and install, it is at your risk.

What a shame this simple system for sorting the sheep from the goats was not introduced years ago. It would have enhanced the reliability and the reputation of the previous versions of Windows no end. Perhaps the obstacle was one of cost, as a fee is charged for this approval.

Help?

The help files are much improved and expanded, with better and longer explanations, better links, and more detail. Some of the help text is written with the assumption of a certain level of Windows know-how and appears to be directed at experts, but the beginner is also well catered for. I think most *Electronics World* readers will welcome this expansion and increased depth.

Stability issues

One of the major causes of unreliability of Windows in the past has come from installing and then removing applications. This type of instability was blamed on so-

called 'power users' but in effect we are all in this category, as over a period of time everyone puts on and takes off applications of one sort or another.

I have noticed that Windows 95/98 systems that are left undisturbed, and their applications consistently used in a routine way, run for a much long time without crashing.

The recent review of pcb-CAD and simulators gave me some first-hand experience of this, as Windows 98 would first wobble and then crash as the review programs were installed and removed one after the other.

Even using one of the many uninstaller utilities that are on the market did not provide a dependable cure. I tested Windows 2000 out with a few installs/uninstalls which I knew would have unsettled Windows 98, and the system seemed to carry on unaffected. Also, it seems that if a badly-written application crashes, Windows 2000 will soldier on. This is impressive!

Part of the new reliability comes from Windows File Protection, which runs in the background and guards critical system files from being overwritten. If a file gets corrupted, the most likely source being a badly compiled third-party application, WFP replaces it with a clean file, either from a back-up copy or from the Windows 2000 CD. This throws the responsibility for any shortcoming in this particular respect back on to the originator of the third-party application. File protection works well. You can try it yourself by altering a system file, then checking for its restoration.

Secondly, the Windows installer/uninstaller is also said to be better at its job, leaving less in the way of debris after a program has been uninstalled, or if an install has misfired and collapsed.

It has been suggested that the Registry was one of the main causes of unreliability. Third party programs would insert Registry entries on being installed but not remove them completely on removal. This resulted in a much-enlarged Registry – so-called 'Registry bloat', with many irrelevant and potentially trouble-causing entries. Also, other files such as DLLs would be left lying around at random.

Installation failure

Having an installation fail to complete is common experience. It leaves everything in a state of limbo.

The Windows Installer in Windows 2000 is designed to return the system to a clean state if the install fails. Moreover, it can prevent conflicts between applications using shared resources. It can repair applications by replacing files that are found to be bad, and do a few other unexpected things as well.


More importantly, uninstalls are more thorough. Registry entries are removed, and there's better control over DLLs and other application files.

The message here is, if you want the increased reliability of Windows 2000, let the operating system handle all the application installs and uninstalls.

In summary

Critics of Windows 2000 will see it as an oversized operating system that promotes yet more technology churn – i.e. a large increase in resources and total cost with not much to show for it. Here is the law of diminishing returns operating with a vengeance.

But in mitigation of this argument, the price of new PCs has fallen considerably, as has the cost per megabyte of hard disk drive space and memory. Given that some improvement to the reliability of the existing product was really needed, it is difficult to see what could be done to Windows and at the same time avoiding the creation of a certain amount of technology churn – without starting again from scratch that is.

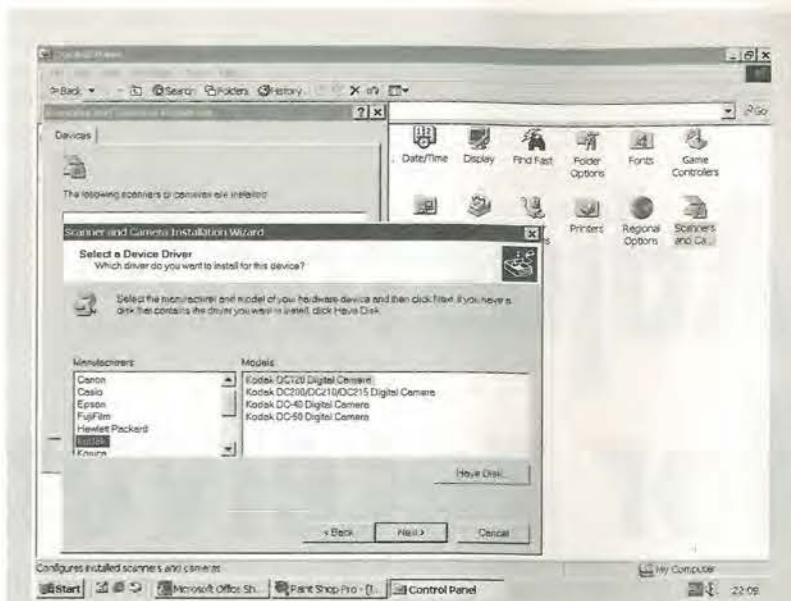

Relative to NT, Windows 2000 has improved support for digital imaging devices like cameras.

Cameras and scanners

Support for digital cameras and scanners is much improved. Now that digital cameras with high resolutions have made an appearance, they have become more a part of the technical scene, so engineers will welcome their easier implementation in Windows.

The number of devices catered for is not large, as the screen shot shows, but then the digital camera and scanner world is awash with products. New models appear and old models are discontinued at an amazing rate, so it would be unreasonable to expect an operating system to keep pace.

Also included is a basic image-manipulation program.

Certainly, the extra checks and balances introduced to combat the known instability of Windows 95/98 are to be welcomed, as is the more reliable NT kernel. However, if you are already an experienced user of Windows 95 or 98 and are having no particular problems it is not easy to justify a move to Windows 2000.

The deterrents to adopting Windows 2000 are firstly the incompatibilities with existing systems introduced by the superior NTFS – although you can drop down a notch and adopt FAT on installation if you really want. Secondly, the 32-bit operation may make some of your current Windows 95/98 applications unusable. Thirdly, the increased hardware requirement may make your existing PC redundant. Certain stand-alone CAD/CAM users may find the administrator tools get in the way.

However, if you are running Windows 95/98 and you are suffering persistent and debilitating instability, then Windows 2000 Professional is an attractive proposition, provided you have a machine that can be easily upgraded, or you are prepared to buy a new PC.

If you are running NT4 and you find it unfriendly, then Windows 2000, alias NT5, is a natural progression. By following this route, you will not have the dilemmas listed above that Windows 95/98 users have to face, apart from some staff retraining to cope with the new interface.

For those who have clung on to Windows 3.x waiting for something better than Windows 95/98 to appear – and I have observed many smaller businesses doing exactly that – then Windows 2000 will have considerable appeal. For these users, a clean sweep of hardware and software may make good sense.

Adjustable PLL for receivers

Darren Heywood's 46 to 76MHz phase-locked loop module is tuned by simply turning a ten-turn potentiometer. It was originally designed to form the master oscillator of a short-wave receiver, but it is easy to adapt it for other applications.

This phase-locked-loop module was designed to be the master oscillator in a short-wave receiver. The most common method of overcoming image channel interference is to up-convert the first IF to 45MHz. This PLL spans 46 to 76MHz in 500kHz steps or increments and so covers the entire HF band. It can easily be adapted to cover other frequency ranges simply by adjusting the zero/span potentiometers and/or changing L_7 . Assuming correct set-up, stepping through the frequency range involves the user simply turning a ten-turn potentiometer.

Circuit overview

The module accepts an unregulated 12V supply, regulating it to 8.3V via IC_2 in conjunction with Tr_1 , Tr_2 , and Tr_{16} . It is capable of delivering up to 300mA. A 5V regulator, IC_1 , supplies 5V to the various TTL chips. A 74HC4060 oscillator/divider produces the reference frequency, outputting a very stable 125kHz on pin 4. There's a 250kHz signal available at pin 5. This feeds a Class-C amplifier, Tr_3 , that generates about 60V. Regulation by ZD_2 limits the output across C_{14} to about 33V. This voltage is needed to drive the BB909B varicap diode.

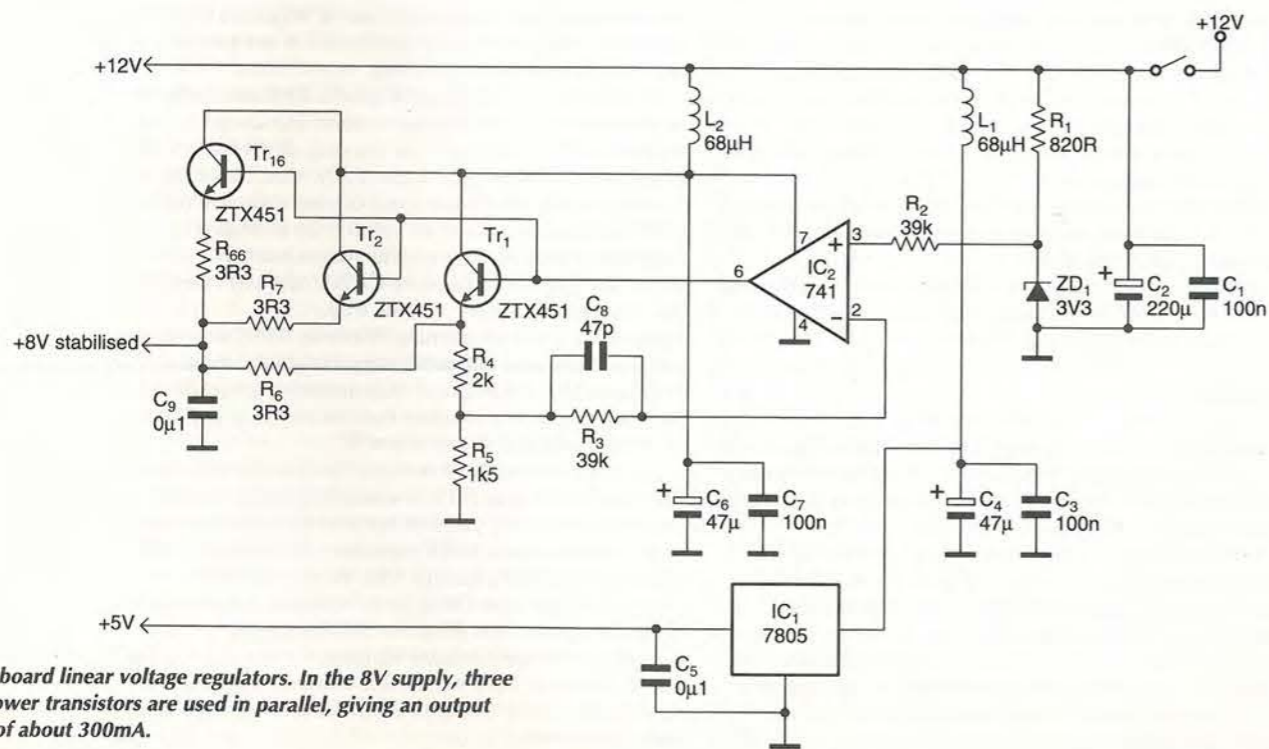



Fig. 1. PLL board linear voltage regulators. In the 8V supply, three medium-power transistors are used in parallel, giving an output capability of about 300mA.

Transistor pair Tr_5 and Tr_6 are designed to have a voltage gain of about 6. As a result, output from the linear phase 74HC4046 detector, IC_4 is 0 to 5V. When amplified by a factor of 6, the 0-5V signal produces a linear 0 to 30V dc error voltage for the varicap diode. This arrangement allows the module to

produce very wide span ranges. Resistors R_{25}/R_{24} and C_{24} make up the loop filter, which in this case is a single-order lag/lead filter type. A FET, Tr_7 , is at the heart of the free-running voltage-controlled oscillator, or VCO, which is a Hartley variant. Where L_6 and L_7 are concerned, it is easier to talk of wire lengths than

inductance values, so L_6 and L_7 are 180mm and 190mm respectively. To make these two inductors, simply cut two lengths as stated from ordinary single-core hook-up wire and wind them around a pen, etc. Output from the VCO is lightly coupled to Tr_8 which amplifies the signal. Further amplification takes place in

Fig. 2. Main PLL board includes a step-up voltage converter for supplying the 33V needed to operate the varicap over its full range.

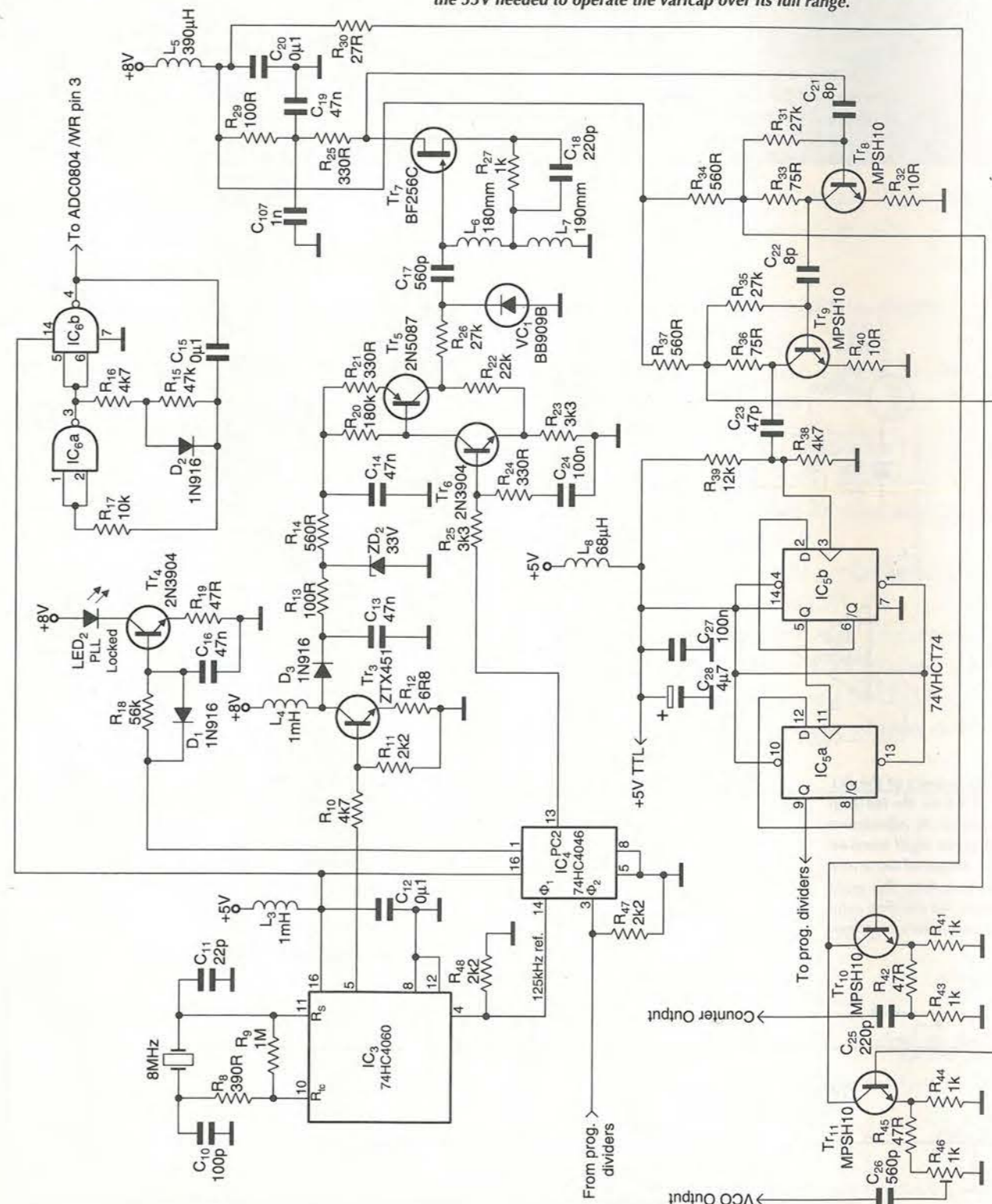

Tr_9 . Resistors R_{39} and R_{38} bias IC_5 just on its switching threshold. Note that IC_5 is actually used as a divide-by-four prescaler; the 'VHCT' TTL family is capable of working up to 160MHz.

Transistor Tr_{10} provides an output to a frequency meter while Tr_{11} 's output can be fed directly into a mixer, such as the NE602.

Output from pin 9 of IC_5 is then fed into IC_{10} . This device, together with IC_9 , makes up the programmable dividers. The output of IC_9 at pin 13 is fed back to IC_4 pin 3 for comparison.

Transistor Tr_{15} , combined with ZD_3 , generates a stable 3.3V reference. This reference is buffered by IC_{7b}/Tr_{13} and then fed into pin 9 ($V_{ref}/2$) of the ADC0804 analogue-to-digital con-

verter. Potentiometer VR_1 affords span adjustment while VR_2 adjusts zero.

Setting up

To calibrate this PLL, connect a frequency meter to the counter output. Rotate VR_3 to its earthy end and adjust zero, via VR_2 , as required. Then rotate VR_3 for maximum and adjust the span, VR_1 for the upper frequency limit. Repeat this procedure a few times until you obtain the correct lower and upper frequencies.

Since the ADC0804 is a successive-approximation type a-to-d converter, it requires continuous active-low strobe pulses on its pin 3. This is achieved by IC_6 .

As the circuit stands, it is possible to have a total of 255 500kHz steps. In

my application though, I only needed 60 steps of 500kHz to cover a 30MHz range. This covers the entire HF band.

Output frequency of the PLL circuit is found using,

$$f_{out} = 4 \times 125 \text{kHz} \times N$$

where N is the eight-bit binary byte generated by a-to-d converter. As a result of this, the PLL should span 500kHz to 127.5MHz, but the VCO, Tr_7 , would probably run out of range. As shown, with L_6 180mm and L_7 190mm, 46MHz to 76MHz is achieved with plenty of spare capacity.

Capacitors C_{108} and C_{35} should be mounted as close to the ADC0804 as possible.



Unique reader offer:
x1, x10 switchable
oscilloscope probes,
only £21.74 a pair,
fully inclusive*

*Additional pairs as part of the same order, only £19.24 each pair.

Please supply the following:

Probes

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Cheques should be made payable to Reed Business

Information

Access/Mastercard/Visa/Cheque/PO

Credit card no _____

Card expiry date _____

Signed _____

Please allow up to 28 days for delivery

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74 UK/Europe to Probe Offer, Electronics World Editorial, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Readers outside Europe, please add £2.50 to your order.

Specifications

Switch position 1
 Bandwidth DC to 10MHz
 Input resistance 1MΩ - i.e. oscilloscope i/p
 Input capacitance 40pF+oscilloscope capacitance
 Working voltage 600V DC or pk-pk AC

Switch position 2
 Bandwidth DC to 150MHz
 Rise time 2.4ns
 Input resistance 10MΩ ±1% if oscilloscope i/p is 1MΩ
 Input capacitance 12pF if oscilloscope i/p is 20pF
 Compensation range 10-60pF
 Working voltage 600V DC or pk-pk AC

Switch position 'Ref'
 Probe tip grounded via 9MΩ, scope i/p grounded

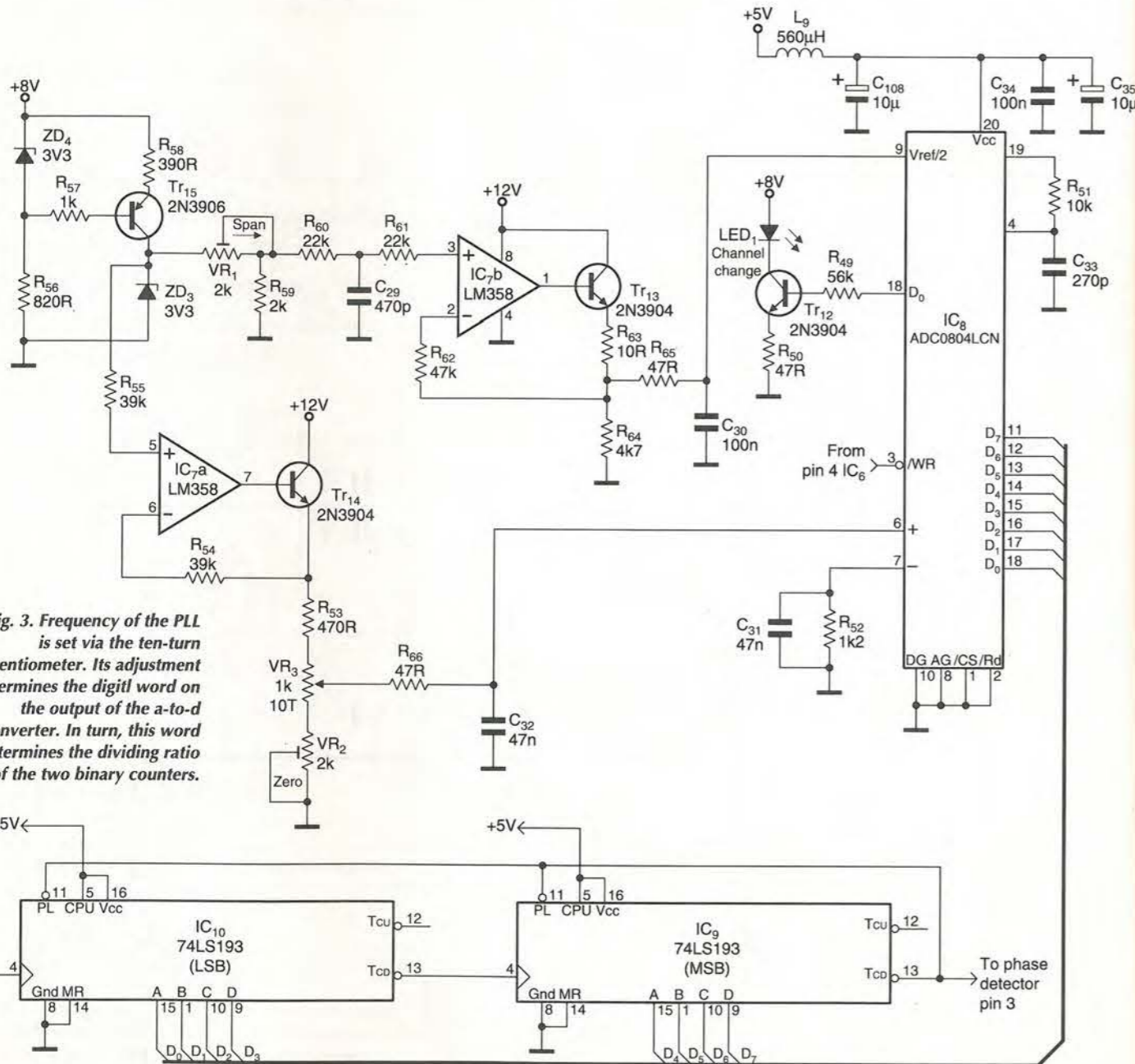


Fig. 3. Frequency of the PLL is set via the ten-turn potentiometer. Its adjustment determines the digit word on the output of the a-to-d converter. In turn, this word determines the dividing ratio of the two binary counters.

AQUILA VISION

<http://www.aquila-vision.co.uk>

Aquila Vision specialises in supplying and supporting Embedded Microprocessor Development products from PICs to DSPs. We also stock robotics boards, Linux and general interest CD-ROM's.



ALCATEL COMPONENTS

<http://www.components.alcatel.de>

ASHWELL ELECTRONICS

<http://www.ashwell-hq.com>

Ashwell provide technical support for Apex Microtechnology op-amps and DC/DC'S; Aeroflex; EMP filtered connectors; M S Kennedy; Mintech obsolescence; NSC Mil/Aero; Teledyne Relays and isocom mil/optocouplers.

ARCOM

<http://www.arcomcontrols.com/ew/>



A leading international supplier of communication and control technology to industry, Arcom provides leading edge solutions through a comprehensive range of market leading products.

BROADCASTING COMMUNICATIONS SYSTEMS

www.broadercasting.co.uk

WINRADIO now brings you a complete choice in personnel computer controlled radio scanning and reception solutions • Broadcast • Media • Monitoring • Professional Amateur Radio communications

BEDFORD OPTO TECHNOLOGY LTD

<http://www.bot.co.uk>

Optoelectronic products UK design development manufacture standard and

custom, LED bargraphs, circuit board indicators, stand offs, transmissive/reflective switches, baseface optocouplers tubular and surface mount, panel mount LED assemblies.

CONCEPT ELECTRONICS

<http://www.conceptkey.co.uk>

Concept Keyboards are specialists in the design and manufacture of customer specified membrane panels and keyboards, and electronic design. Concept's membrane manufacture is supported by a full electronic production facility to provide a complete turnkey keyboard and electronics service, fully accredited to ISO9001.

CONTROL SOLUTIONS

www.controlsolutions.co.uk

Data acquisition and control for beginners, hobbyists, and professionals. Perform mathematical and logical operations on data in real time. Email: info@controlsolutions.co.uk

COOKE INTERNATIONAL

<http://www.cooke-int.com>

e-mail: info@cooke-int.com



Stockists of Quality Used Electronic Test Instruments and Operating & Service Manuals.

CROWN HILL ASSOCIATES LTD

<http://www.crownhill.co.uk>

Crownhill supply low cost development tools for use with Micro-Controllers and Smart Cards. Products include Smart Card development tools, Smart cards, Micro Development tools and Bespoke Design Services.



DANIEL MCBREARTY

<http://www.danmcb.demon.co.uk/keng.html>

Experienced engineer based in London, specialist in audio and control systems. Available for design, project engineering or general consultancy. Background of high-quality work.

EQUINOX TECHNOLOGIES UK LTD

<http://www.equinox-tech.com>



Equinox Technologies UK Ltd., specialise in development tools for the embedded microcontroller market.

ELECTRONICS WEEKLY HYPERACTIVE


<http://www.electronicweekly.co.uk/>



ECM SELECTION

<http://www.ecmsel.co.uk>

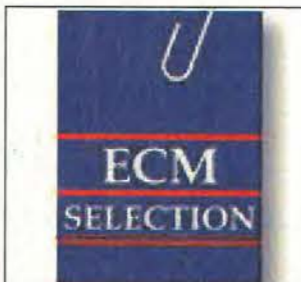For the pick of the UK's Top High-Tech Software and Hardware career opportunities - from fresh Grad/PhD to Senior Engineer/Manager -- £22,000 - £70,000



ELECTRONICS PRINCIPLES FREE ONLINE

<http://www.eptsoft.com>

This popular electronics educational title now available to engineers, students and hobbyists absolutely free. A huge 'virtual textbook' of electronics information, from DC to PIC's.

FELLER UK

<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

FLASH DESIGNS LTD

<http://www.flash.co.uk>

Flash supply low cost AVR ISP programmers (£39), MINI-ICE starter kits (from £69), Portable Easy-ICE emulators (from £199), ICE Adapters & 'C' compilers for any ATMEL AVR, MCS51, Dallas, Hitachi H8 microcontroller. Download FLASH NEWS now. Watch out for Special Offers'. ARE YOU developing code in a Flash?

HSPS LTD

<http://dspace.dial.pipex.com/hsp/>

FILTER DESIGNER - Advanced analog and digital filter design software for the PC. - Standard and Professional versions. - Free download of Evaluation version.

LOW POWER RADIO SOLUTIONS

<http://www.lprs.co.uk>

LPRS markets low power radio transmitters, receivers and transceiver modules manufactured by ourselves, Radiometrix, Circuit Designs, RDT and Micrel. Applications for telemetry, video and remote control.

MATTHEY MICROFILTERS

<http://www.microfilters.net>




30 years experience in the design and manufacture of high quality passive filters and delay lines. Used in Broadcast, Telecommunications, Medical, Multimedia, and Computer industries.

NEWNES - BOOKS FOR THE ELECTRONICS WORLD

<http://www.newnespress.com>

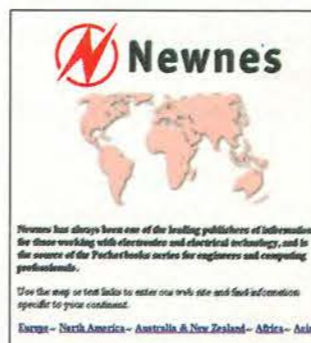Over 300 books and information packages for those working with electronics and engineering technology. Visit our site for a free catalogue and downloads



To reserve your web site space contact Pat Bunce
Tel: 020 8652 8339
Fax: 020 8652 3981

PCA: PHILIP COLLINS & ASSOCIATES PTY. LTD

<http://www.pca.cc>

PCA manufactures Radphone 2000DX remote control systems for shortwave broadcasters and government agencies wanting worldwide control of communications receivers and transceivers from any tone phone.

POLY-FLEX CIRCUITS LTD

<http://www.polyflex.com>

Design, manufacture and population of printed polyester flexible circuits, including Flip Chip on Flex providing practical, low cost, reliable solutions for today's small lightweight products.

QUILLER ELECTRONICS

<http://www.quiller.com>

100+ pages of detailed technical information on Schrack Relays, MEC Switches, Hirose Connections.

RADIOMETRIX

<http://www.radiometrix.co.uk>

Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use.

RADIO-TECH LIMITED

<http://www.radio-tech.co.uk>

Radio modules, modems, telemetry, audio transmitters, pagers, antenna, remote controls and much more. All UK designed and manufactured.

Put your web address in front of 21 000 electronics enthusiasts and experts.

Electronics World acknowledges your company's need to promote its web site, which is why we are now dedicating pages in every issue to announce your WEB ADDRESS.

This gives other readers the opportunity to look up your company's name, to find your web address and to browse the magazine page to find new sites.

We understand that cost is an important factor, as web sites are an added drain on budgets. But we are sure you will agree that the following rates make all the difference:

FOR 12 ISSUES:

Lineage only will cost £150 for a full year just £12.50 per month.

This includes your company's name, web address and a 25-word description. Lineage with colour screen shot costs £350 for




RALFE ELECTRONICS

professional test & measurement
www.ralfe-electronics.co.uk

RD RESEARCH

<http://www.looking.co.uk/spice>

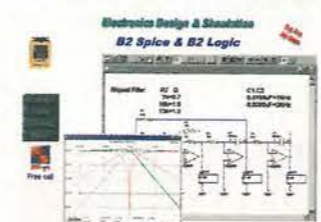

Analogue and digital SPICE modelling software. Full details available on this site. Available on a 30 day evaluation basis.

RS COMPONENTS LTD

<http://rswww.com>

The award winning on-line service from RS - 110,000+ products available - Technical data library - Stock availability check - Integrated on-line purchasing - Order by 8pm - with you tomorrow.



SOFTCOPY

<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.

SESCOM, INC.

<http://www.sescom.com>



SESCOM, INC. is a 30-year manufacturer of audio "problem solvers" and transformers. We also offer easily-fabricated aluminum enclosures for small production runs and prototypes.

STAFFORDSHIRE WIRELESS COMPANY

<http://www.staffs-wireless.com>

Wireless, communication, test equipment, bought and sold for very competitive prices visit our web site or telephone John on 01889 569928 or 0973 296461.

To reserve your web site space contact Pat Bunce

Tel: 020 8652 8339
Fax: 020 8652 3981



SUPRA AUDIO CABLES

<http://www.jerving.se>

Jerving Technology AB is the manufacturer of Supra Audio Cables. OEM productions are also accepted.

TEMWELL CORPORATION

<http://www.temwell.com.tw>

Manufacturer & Exporter of Heical BPF Filter, 30 Watts BPF Power Filter and Handset/Base Station Duplexers

THERMOSPEED

<http://www.thermospeed.co.uk>



ThermoSpeed the catalogue site company of the HAVCO Group

We offer Off-The-Shelf temperature, pressure, humidity and electrical instrumentation for sensing, measurement and control.

Temperature and pressure, control and instrumentation. Full on-line purchasing. • Overnight ex-stock delivery • Create your own hotlist • Download datasheets • Full technical support

Continued over page

Company name	Web address

WEB DIRECTIONS



THOSE ENGINEERS LTD
http://www.spiceage.com

Working evaluations of SpiceAge mixed-mode simulator, Spicycle PCB design tools and Superfilter demo (synthesises passive, active, digital filters). Tech support, sales links and price list.

TEST EQUIPMENT SOLUTIONS

http://www.TestEquipmentHQ.com

Quality second user test equipment with full warranty and support. All types of

TEST EQUIPMENT SOLUTIONS
Specialists in the supply of quality refurbished Test Equipment.
Phone: +44 (0)1753 596000
Email: info@TestEquipmentHQ.com

equipment from all leading manufacturers including general purpose, communications and industrial test.

TRIDENT MICROSYSTEMS LTD
http://www.trident-uk.co.uk

Visit the Trident website for details and datasheets on their entire LCD and printer product range. Download data and subscribe for our regularly updated newsletter.

TOWER HILL TECHNICAL SERVICES

http://www.towerhillaerials.com

Everything you need for DIY Satellite & TV aerial installation. The one stop

Tower Hill Technical Services
Specialists in the supply of quality refurbished Test Equipment.

shop for TV, FM, Satellite, Amateur Radio PMR Aerials, Distribution Equipment, Cable & Accessories.

TECHNICAL AND SCIENTIFIC SUPPLIES

http://www.technicalscientific.com

Suppliers of pre-1985 equipment and components.

- Test/Measurement equipment
- Valves and semiconductors
- Transducers and pressure gauges
- Scientific books and catalogues
- Manuals and data sheets

VANN DRAPER ELECTRONICS LTD

http://www.vanndraper.co.uk

Test equipment from Grundig, Kenwood, Hitachi, Fluke, Avo, Glassman, Advance in a comprehensive site including oscilloscopes, multimeters, power supplies, generators, counters, soldering, digital tv etc.

To reserve your web site space contact Pat Bunce
Tel: 020 8652 8339
Fax: 020 8652 3981



VUTRAX PCB DESIGN SOFTWARE

http://www.vutrax.co.uk

VUTRAX electronic schematic and pcb

design system for Windows 95, 98 and NT. Limited Capacity FREE version downloads available, all upgradeable to various customised levels.


WOOD & DOUGLAS

http://www.woodanddouglas.co.uk

Wood & Douglas Ltd is the leading independent British designer and manufacturer of quality radio products for International telemetry, data, voice & video wireless communications.

Save 15% Pico ADC42 Virtual oscilloscope

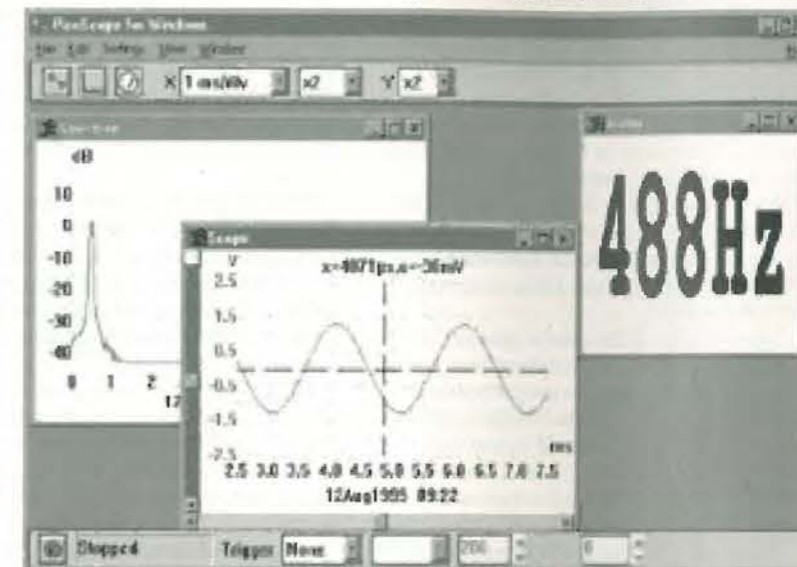Featuring 12-bit resolution and 1MΩ input impedance, the ADC42 samples at up to 15kS/s and includes software for spectrum analysis, oscilloscope functions and frequency display. Plugging into a PC's LPT port, the unit provides large, colourful displays and all the usual timebases and trigger options – all in a case slightly larger than a matchbox.



Use this coupon to order your ADC42

Please send me ADC-42(s) at the special offer price of £98 fully inclusive of VAT and recorded UK delivery, normal selling price £111.63 excluding postage.

Name _____

Address _____

Phone number/fax _____

Total amount £.....

I enclose a cheque _____

Please charge to my credit/debit card.

Card type (Master/Visa/Switch etc)

Card No _____

Expiry date ____ / ____

Please mail this coupon to *Electronics World*, together with payment. Alternatively fax credit card details with order on 0181 652 8111. Address orders and all correspondence relating to this order to Pico Offer, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. email jackie.lowe@rbi.co.uk

Make cheques payable to Reed Business Information Group.

ADVERTISE FREE OF CHARGE

Subscribers* to *Electronics World* can advertise their electronics and electrical equipment completely free of charge

Simply write your ad in the form below, using one word per box, up to a maximum of twenty words.

Remember to include your telephone number as one word.

You must include your latest mailing label with your form.

* This free offer applies to private subscribers only. Your ad will be placed in the first available issue.

This offer applies to private sales of electrical and electronic equipment only.

Trade advertisers – call Pat Bunce on 020 8652 3620

All adverts will be placed as soon as possible. However, we are unable to guarantee insertion dates. We regret that we are unable to enter into correspondence with readers using this service, we also reserve the right to reject adverts which do not fulfil the terms of this offer.

Please send your completed forms to:

Free Classified Offer: Electronics World, L333, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

Letters to the editor

Letters to "Electronics World" Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS
e-mail jackie.lowe@rbi.co.uk using subject heading 'Letters'.

New mobile phone health risk?

I have just read an article in the May issue regarding the new Blue Tooth wireless network system.

I note that the frequency at which it will operate is the same as that used by domestic microwave ovens, namely 2.45GHz.

Does anybody really think that, in light of the recent discussion over mobile phones, it is a good idea to introduce a network using the very frequency most likely to cause personal injury?

I do not know if the people who set out the specification realised what they were doing. Are we now going to have to have another expensive debate as to the merits or health hazards of this new piece of technology? Or will we get stuck with a system that is going to cause future problems for those who are taken in by all the glossy hype?

What sort of antenna will be used to radiate the energy and, how will it all work any way, when a real microwave oven swamps it out?

Some one will probably come up with some answers in the near future. Or will the topic be swept under the political carpet I wonder?

On another tack, I wrote in to ask if any reader could explain why cables are directional.

Ian Johnson
Kidderminster
Worcestershire

Sharing knowledge

I notice pieces such as Ian Hickman's 'An RF initiative' in the May 2000 issue plod along regularly in the electronics literature. Indeed, similar exhortations and initiatives appear in the scientific community's literature in general.

Lean and mean

I have a question regarding the electronic computer control system, or ECCS, of my car. Can anyone help please?

I would like to modify my ECCS and/or emission control module, ECM, to make the engine more compatible with driving conditions in my part of Australia.

The Nissan Patrol 2.8-litre turbo diesel that I bought last year was made for European and US markets, where emissions are tightly regulated. All our imported 4WD vehicles run far too lean.

In spite of this, I have noticed over many years that science and technology continues to be unattractive to many youths, who see it as 'boring' or even Frankensteinian. Many older people have a negative view of manipulative science and technology – while consuming the fruits of the enterprise, of course.

The dangers of 'radiation' from mobile 'phones is one of our bug-bears. Genetically modified foods is another. Electronic surveillance, genome projects, powerful technological states, all frighten many people and this fear gets communicated to the young.

My own efforts in youth leadership over many years helped to produce awareness of the subject in some hundreds of young people. Many gained examination passes and a good number went on to university degrees.

My approach operated within the non-selective school population more or less exclusively, the main reason being that selective and public school students do not find time to go the Youth Clubs for any purpose. Also, the democratic and eclectic nature of this work with youth had much wider ramifications for developing citizenship, self confidence; you name it, we did it. Remember, the youngsters were mainly working class.

An article I wrote in *Wireless World* – July 1985 issue, yes, that long ago – effectively told the same story. That article resulted in some interesting correspondence. Many readers offered obsolete or surplus apparatus.

One or two asked if a similar scheme existed in their region. One local employer asked if any youths were, 'really skilled, as I am looking for new junior staff'. But the main call I made in the article, i.e. for volunteer workers to set up clubs or

They are starved of fuel at low revs, and thus have very little torque.

Regulations for 4WD cars imported to Australia do not demand such a lean burn. I have approached Nissan but the company refuses to make any modifications.

Apparently a few replacement computers exist on the market in Australia and overseas. I would like to hear from anyone who has any experience of them.

Guy Dyson
Brisbane
Australia

schemes, went unheeded then and has been unheeded ever since. *You can't get leaders to work with kids at grassroots level.* No other Clubs were ever founded.

The TEC Group (as we called it) who met in a workshop that one early group of boys named *The Faraday Room*, went on to its ultimate peak of success in the decade after the article. Even that excellent work has now ceased because of radical changes in the Youth Service and impossibility of finding institutional support.

I still receive calls from youths or parents who say, 'I hear you have a science club...'. Although these calls are few and far between now, the response is always crestfallen when I say sorry, but no work is going on at present. Many young people would still flock to a caring, stimulating Club project, that they could help run themselves. As my ancient article says: 'Where are the teachers?'

I do not know whether the IEEE ever knew of the work. The Royal Institution was just aware. Certainly the Institute of Physics was well aware and supported me in the role of presenter in one of the 'Grand Schools Lecture Tours'. The Lecture-Demo in 1988 was called *From Whiskers to Walkman* and dealt with the history of Radio. *Electronics World* was an important supporter, as your records should show.

Mr Hickman is fairly on the ball, but still makes the inappropriate argument to 'rob Peter to pay Paul'. Yes, you might convert a few electronic engineers from this or that to RF work, but doing so is a zero sum game. The lack of awareness is overall, and ignorance in general about powerful manipulative subjects like technology, is dangerous for democracy.

Dr Ken Smith,
Canterbury
Kent

Mobile Internet – who wants it?

In the May 2000 issue of *EW*, Mr Manners quotes Sir Alan Sugar: "Who wants to send E-mails from the middle of a field?" – words spoken clearly by one who never has had to work there. Please try and poll opinion from minds with a bit larger perspective.

Thank you very much.
Alan Jeffrey Marcy
Phoenix
Arizona
USA

Misrepresented

I read Mr Ellis' letter on slew-limiting in the May 2000 issue with little enthusiasm. I take considerable exception to being misrepresented in print.

I have never suggested anywhere that 22Ω is the optimum value for input-stage degeneration resistors. It is certainly nothing of the kind. All the amplifier designs I have published use 100Ω

degeneration components.

Mr Ellis adopts what appears to be a completely arbitrary criterion that the input-pair currents should not alter by more than 50%, without reference to how much non-linearity this would generate. The rest of his analysis appears to offer no new insights, though it is interesting to note that the base current of the VAS transistor in Fig 1

appears to be flowing backwards.

The values for emitter degeneration resistors are actually chosen as follows:

The higher the resistor value, the more linear the input stage, the lower the open-loop gain, and the smaller the value of C_{dom} required for stability. On the other hand, the higher the value, the more Johnson noise is introduced just where it is

not wanted, increasing the amplifier noise output.

The choice of 100Ω reduces the input stage contribution to high-frequency distortion to negligible proportions compared with output stage non-linearities, without seriously degrading noise performance. The value is not critical.

Douglas Self
London

Hot headed drive

We have a Conner ST38410A hard-disk drive formatted in DOS 6.22 that has failed. It overheated, so we took it to a top specialist in Singapore but the problem was beyond the scope of the company's capability.

The diagnosis was probable failure of the head interface IC inside the platter compartment. I expect there are the skills in the UK that can handle this problem and would be much obliged if you could help in any way to contact these professionals.

Ray McKay
Via e-mail

Cadsoft? I met with a brick wall

Rob Graham shouted about his free download of the Eagle Lite software by Cadsoft but kept quite about the web address.

Anyone who logged on to cadsoft.com will have found that those folks are selling software to the brick and mortar industry – a waste of time thus.

Ray McKay
via email

Sorry Ray, and Rob, I should have included the contact details: www.cadsoft.de. The blue iron-on transfer Rob mentioned is from Maplin by the way. Ed.

Class-T

The April 2000 features Ian Hickman's article on the Tripath approach to switching amplifiers, 'Is Class-T hi-fi?' on pages 274-279.

Hickman properly applauds the Tripath scheme for exhibiting lower crossover and IM distortion than conventional class-D designs. But this is achieved at the cost of reduced efficiency due to higher switching-frequency components, albeit distributed in their proprietary fashion over a range of frequencies.

A method that involves none of these compromises has been around for a while now, but perhaps owing to its use in profes-

sional audio has received little attention by audiophiles. It is Crown International, Inc.'s 'Opposed current power converter'.

This patented topology – and associated pulse-width modulation scheme – uses two switches and two diodes in an 'opposed current half-bridge'. The bridge is intrinsically free of the shoot-through current fault path of the basic half bridge. As a result, zero dead-time operation – and the elimination of the finite dead-time crossover distortion mechanism – is possible.

Stanley and Bradshaw (IEEE Transactions on Power Electronics, Vol. 14, No 2, March 1999) describe performance results from a 2.5kW full-audio-bandwidth amplifier with 92% efficiency and an open-loop (!) full-scale output-stage THD of about 0.2%.

Appropriately applied feedback eliminates distortion arising from supply voltage fluctuations, as well as further improving linearity. It also yields THD less than 0.02% between 6W and 800W.

The authors use a 'total difference-frequency distortion' test (see A. N. Thiele, J. Audio Eng. Soc., vol. 31, No 6, pp. 443-445, June 1983) to demonstrate the ampli-

er's outstanding IM distortion performance.

Many other advantages to this approach are discussed too, including its extension to an interleaving approach which results in waveforms in which reduced amounts of ac content accompany increased PWM frequencies. This allows yet simpler output filtering. It also offers the opportunity to apply more global feedback, thereby reducing output impedance and hence better control of real loudspeaker loads.

About the only disadvantage that I can see occurs if the technique is applied to very low-power low-voltage applications, where the forward drops of the diodes entail a bit of power loss. Also, as noted by the authors, two output inductors are needed.

Stanley and Bradshaw conclude: "PWM amplifiers have traditionally been deemed unfit for studio-quality sound reproduction and other precision applications. Such a judgment has been premature. It is possible to have both efficiency and fidelity at the same time."

Brad Wood
Chatsworth
California

Two transistor FM broadcast receiver

Regarding the winning circuit in the June issue's circuit ideas, there doesn't seem to be any such transistor as a BF797. We still haven't managed to track down the circuit's designer so we cannot confirm what was intended to be used, but the circuit has been tested here using two BFR91s.

Ed.

The right spheres

In the article 'Adaptable active loudspeaker' in the February, 'Styropor' spheres were used as enclosures. The article's author, Christof, informs us that Styropor is the trade name used in

Germany for expanded polystyrene from the company BASF.

The same product is sold in the UK under the trade names of Montopor and Styrocell. In the USA it is soled as Dylite and Telastan, in France as Afcylene, in Italy as Restical and in Japan as Snowperl.


As to the drive units, many readers have written to ask for more information about the speakers used in Christof's article. Here are the contact details for his supplier:

Fa. Hifisound Lautsprechertrieb
Judefelderstrasse 35
D 48143 Munster Germany
Tel + 251 47828 Fax + 251 43956

E-mail: hifisound@t-online.de
Internet: http://www.hifisound.de
Ed.



OPERATING & SERVICE MANUALS

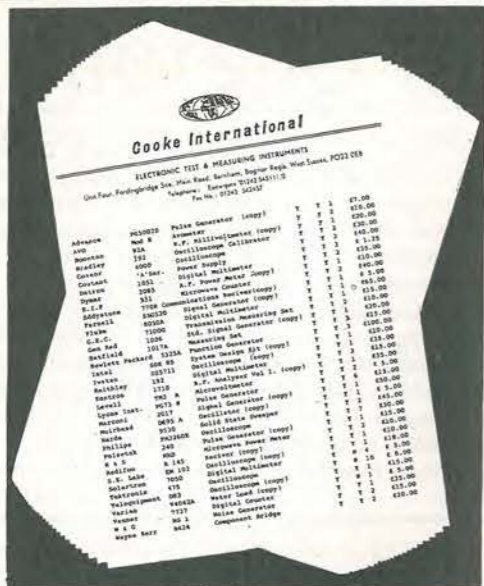

Cooke International
 Unit Four, Fordingbridge Site, Barnham,
 Bognor Regis, West Sussex, PO22 0HD, U.K.
 Tel: (+44)01243 545111/2 Fax: (+44)01243 542457
 Web: <http://www.cooke-int.com>
 E-mail: info@cooke-int.com
 catalogue available

CIRCLE NO.124 ON REPLY CARD



SUPPLIER OF QUALITY USED TEST INSTRUMENTS



Cooke International
 Unit Four, Fordingbridge Site, Barnham,
 Bognor Regis, West Sussex, PO22 0HD, U.K.
 Tel: (+44)01243 545111/2 Fax: (+44)01243 542457
 Web: <http://www.cooke-int.com>
 E-mail: info@cooke-int.com
 catalogue available

CIRCLE NO.125 ON REPLY CARD

As an advertiser you can be certain that your sales message is going to be read by decision-making electronics professionals with the power to purchase your products.

Service

Link

The pre-paid rate for semi-display setting is £17 per single column centimetre (maximum 4cm). Box number £22 extra. All prices plus 17½% VAT. All cheques, postal orders etc to be made payable to Reed Business Information. Advertisements together with remittance should be sent to Electronics World Classified, 12th Floor, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.
Fax: 0208 652 3981.
Tel: 0208 652 8339

SERVICES

From Concept To Production
 Electronic design and engineering services for the new millennium:
 • Embedded control
 • Telecommunication products
 • Datacommunication products
 • SM PSU and battery management
 • Wireless transmission systems
 • Audio and Video processing
 • DVD control systems
 • Internet site and graphics authoring
 • PCB design
 • Schematic layout and re-drawing
 • Technical documentation and translation
Tel/Fax: +44 (0) 1872 223306
Email: sales@designersystems.co.uk
 see our web site @ <http://www.designersystems.co.uk>

POWER SUPPLY DESIGN
 Switched Mode PSU
 Power Factor Correction
designed to your specification
Tel/Fax: 01243 842520
e-mail: eugen_kus@cix.co.uk
Lomond Electronic Services

RF DESIGN SERVICES
 All aspects of RF hardware development considered from concept to production.

WATERBEACH ELECTRONICS
TEL: 01223 862550
FAX: 01223 440853

PRINTED CIRCUIT BOARDS - Quick Service. Design and Manufacture for Prototypes or Production. Agar Circuits, Unit 5, 308 Albertbridge Road, Belfast BT5 4GX. Tel: 02890 738897. Fax: 02890 731802. E-mail: agar@argonet.co.uk
FARNELL GS600 SMPS 12V adjustable at 50A, unused, complete, £250 ono. Phone Leeds 0113 249 8661.
MSI 868 C-V plotter measures capacitance 2/20/200/2000pf over fixed or swept bias voltage between 199.9V at 1 MHz £400. 01476 550826.
P&P Electronics, design and analogue and digital systems, phone and fax: 01924 402931.
NICOLET 4094 DSO two independent plugins each with 12 bit twin channel differential amplifiers timebase 0.5µs-2000s/point user manual RS232/GPIB, £200. 01476 550826.
ANRITSU MS62D spectrum analyser with storage display two ranges 50Hz-1700kHz 10kHz-1700MHz with MH628A tracking generator 100kHz-1700MHz with manuals £900. 01476 550826.

ARTICLES WANTED

TOP PRICES PAID
 For all your valves, tubes, semi conductors and IC's.
Langrex Supplies Limited
 1 Mayo Road, Croydon, Surrey CR0 2QP
TEL: 020 8684 1166 FAX: 020 8684 3056

19" Rack Enclosures
 New and Used most sizes
 16U to 50U side and rear panels
 mains distribution 19" Panel mounts
 optima eurocraft. Prices from £45 +vat
M&B Radio
 86 Bishopsgate Street Leeds LS1 4BB
 Tel. 0113 2702114 Fax. 0113 2426881

MISCELLANEOUS

PSU PROBLEMS? HAVE AN IDEA!
 Talk to us first Centronics Power Limited can solve all your problems with one phone call.
So Don't Delay Call Today and Let us help solve your PSU problems, plus we can offer off the shelf products same day delivery
Mobile 07989 874960

ARTICLES FOR SALE

ADVANTEST 3261 B SPECTRUM ANALYSER
 9kHz to 3.6GHz.
 Calibrated, user manual.
 Private sale
£2000
 Tel: Southampton
0238 069 4515

Please Mention Electronics World When Replying to advertisements

APPOINTMENTS

SENNHEISER SERVICE ENGINEER

SENNHEISER UK Ltd is a market leader in the supply of audio equipment to the professional and consumer markets. Part of an International Group of companies, we currently have a vacancy for a Service Engineer. Candidates must have experience in professional radio equipment and generic electronics service and repair to component level.
Responsibilities will include:
 * Service and repair of the entire range of products distributed by Sennheiser
 * Client liaison
 * Provide technical expertise to assist customers
Attributes required:
 * 2-3 years experience in the audio or RF industries
 * Experience in the testing and repair of RF and audio systems
 * Good communication and interpersonal skills
 * Computer literate
 Remuneration subject to experience.
 If you think you have these attributes and feel you can achieve the requirements of the Job, please send your CV for the attention of:
 Dave Hawker
 SENNHEISER UK LTD
 3 Century Point, Halifax Road, High Wycombe, Bucks HP12 3SL
 e-mail your C.V. to: dhawker@sennheiser.co.uk
 or Fax: 01494 551521

ROLEC SERVICES

ROLEC Services is a company that specialises in the supply and installation of electric and water services to Marinas and Caravan Sites. Over the last 5 years we have developed various metering and control systems using "Microchip" processors and more recently "Hitachi" Microprocessors.
WANTED
 We are looking to appoint a company/person to assess, modify, produce full parts, product lists and manuals on these systems. You will ideally have experience with fine-tuning of circuit board design, programming and practical knowledge of installation of such systems.
ROLEC SERVICES LIMITED
 Algores Way, Wisbech, Cambridgeshire PE13 2TQ
Tel: 01945 475165 Fax: 01945 588045

ADVERTISERS' INDEX

CONFORD ELECTRICAL.....584	QUICK ROUTE.....555
COOKE INTERNATIONAL.....588	RD RESEARCH.....512
CROWNHILL.....551	RALFE ELEC.....590
DISPLAY ELECTRONICS.....530	SEETRAX.....512
EPTSOFT.....547	SIGHTMAGIC.....514
H F INSTRUMENTS.....514	STEWART OF READING.....534
DATAMANN.....OBC	SURREY ELECTRONICS.....584
JOHNS RADIO.....519	TOTAL JOBS.....557
JPG ELECTRONICS.....514	TELNET.....IFC
LABCENTER ELECTRONICS.....553	TIE PIE.....517
MILFORD INSTRUMENTS.....548	WANN DRAPER.....555
PICO.....548	WEB PAGES.....582-584
PS CONSULTANTS.....IBC	

T & M EQUIPMENT



ADVANTEST TR8407 ft spectrum analyser to 1MHz £2000
 ADVANTEST TR4133 100kHz-20GHz spectrum analyser £5000
 ANRITSU ML33A optical power meter with MA96A power sensor (0.75-1.8µm) £1000
 ANRITSU MN95D fibre-optic attenuator 0-65db £250
 BRADLEY 192 oscilloscope calibrator £250
 CHASE LFR1000 interference measuring receiver 9kHz-150kHz £200
 DATRON 1061A voltmeter /10/20/30/40/50 £1250
 DRANETZ 626-PA-6006 ac neutral monitor, c/w TR2018 clamp £250
 EIP 548B frequency counter 26GHz (+fx ext option) £1750
 FLANN MICROWAVE 27072 frequency meter 73-113GHz £275
 FLANN precision rotary waveguide attenuator 20110 0-80db 18-26 GHz £750
 FLANN precision rotary waveguide attenuator 22110 0-70db 26-40GHz £750

ralfe electronics *exclusively professional T&M*

• Unit 1 Olds Close • Olds Approach • Watford • Herts WD1 8RU • England •
 TEL (+44) 01923-721396 • FAX (+44) 01923-721402

EST 45 YRS

IFR A-7550 1GHz portable spectrum analyser with receiver options AM./FM/SSB £1500
 MARCONI 2022 signal generator 10kHz-1GHz INCLUDING FREE CALIBRATION £750
 PHILIPS PM5139 function generator 0.1mHz-20MHz £1500
 RACAL DANA 1992 frequency counter, GPIB opt £500
 SCHLUMBERGER 1250 frequency response analyser £3000
 RACAL 6102 GSM test set £2000
 TEKTRONIX 2430A digital oscilloscope £750
 TEKTRONIX 2432A 100MHz 250MSa/sec digital storage oscilloscope £1000
 TEKTRONIX 2236 100MHz analogue oscilloscope £500
 TAU-TRON MN302/MB302N bert transmitter/receiver £250
 WANDEL & GÖLTERMANN PCM4 test sets... call for details & options call
 WANDEL & GÖLTERMANN PF2 error ratio measuring set £400
 WANDEL & GÖLTERMANN DLM-20 data circuit test set £250
 WANDEL & GÖLTERMANN SPM31 level meter £500
 WANDEL & GÖLTERMANN WM30 level tracer £500
 WANDEL & GÖLTERMANN PF4 bit error rate tester (BN911/01, Opt 00.01) £2000
 WAVETEK 23 synthesized function generator 0.01Hz-12MHz £500
 WAVETEK 1080 sweep generator 1-1000MHz £750
 WAYNE KERR 3220 20A bias unit (for 3245 inductance analyser) £1000
 WAYNE KERR SR268 source and detector £250
 WILTRON 6637 sweeper generator 2-18GHz (option 03) £2000
 WILTRON 6640B sweep generator 26.5-40GHz (option 03) £3500

HEWLETT PACKARD



214B pulse generator £2000
 3336A level generator £1000
 1640B serial data generator £500
 10715A digital interferometer £1000
 4274A multi-frequency icr meter £2500
 3245A universal source with option 001 (2nd channel) £3250
 3335A level generator £2500
 3561A dynamics signal analyser £3000
 3586A selective level meter £1250
 37717A/U1A8/UKK/US1/URU (SDH/PDH) test set + optical £5000
 4083B protocol tester base (PT300) £3000
 5334B frequency counter, option 060 £1000
 54600A 2 channel 100MHz digital oscilloscope £600
 54601A 4 channel as above £750
 8018A serial data generator £1000
 83411C lightwave receiver 100/1550nm £1750
 83440C lightwave detector 20GHz 1300nm/1550nm £2000
 8350B sweep generator mainframe £1250
 83572B sweeper plug-in unit (for 8350B) 26.5-40GHz £5000
 85053B 3.5mm verification kit £2000
 85640A tracking generator to 2.9GHz £2000
 8672A synthesized signal generator 2-18GHz £4000
 8671A synthesized signal generator 2-6.2GHz £3000
 86222A 10MHz-2.4GHz sweep generator plug-in unit £1000
 86280B 2-18GHz sweep generator plug-in unit £1500
 8684B signal generator 5.4GHz-12.5GHz £1000
 8903B audio analyser with opts 10 and 051 £2500
 8904A/001/002 multifunction synthesizer DC-600kHz £2000
 8922E GSM test set £3000
 E5200A broadband service analyser (STM1 options) £9500
 J3458A fast ethernet Lanprobe £1500
 J2522B internet advisor £2000

PLEASE NOTE WE HAVE NOW MOVED TO LARGER PREMISES AS ABOVE...

We are situated just 5 Mins from J18 on the M25. Callers very welcome by appointment please.

THIS MONTH'S SPECIALS:
 GSM TEST SETS
 RACAL 6102 £2000
 HP8922F with spec an option (06) £3500

All equipment sold calibration-checked by independent laboratories and carries un-conditional refund and 90-day guarantees.
TEST EQUIPMENT WANTED.
 TOP PRICES PAID FOR PROFESSIONAL HIGH-END UNITS
AGILENT TECHNOLOGY SPECIALISTS.
 FOR COMPLETE STOCK LISTING PLEASE CHECK OUR WEBSITE
www.ralfe-electronics.co.uk

ISO9002 ACCREDITED STOCKIST MEASUREMENT & TEST EQUIPMENT

ELECTRONICS WORLD INCORPORATING WIRELESS WORLD

READER INFORMATION SERVICE

For more information about any of the products or services in this issue of **ELECTRONICS WORLD**, simply ring the relevant enquiry number. Enquiry numbers may be found at the bottom of each individual advertisement.

101	102	103	104	105	106	107	108	109	110	111
112	113	114	115	116	117	118	119	120	121	122
123	124	125	126	127	128	129	130	131	132	133
134	135	136	137	138	139	140	141	142	143	144
145	146	147	148	149	150					
						500	501	502	503	504
505	506	507	508	509	510	511	512	513	514	515
516	517	518	519	520	521	522	523	524	525	526
527	528	529	530	531	532	533	534	535	536	537
538	539	540	541	542	543	544	545	546	547	548
549	550	551	552	553	554	555	556	557	558	559
560	561	562	563	564	565	566	567	568	569	570
571	572	573	574	575	576	577	578	579	580	581
582	583	584	585	586	587	588	589	590	591	592
593	594	595	596	597	598	599	600			

Name _____
 Job title _____
 Company Address _____
 Telephone _____ JULY 2000

Only tick here if you do not wish to receive direct marketing promotions from other companies.

Newsagent order form

Pass this order form to your newsagent to ensure you don't miss the next issue of **EW**.

To
 (name of Newsagent)

Please reserve me the August issue of *Electronics World* and continue to order every month's issue until further notice

Name.....
 Address.....

Thank you

ELECTRONICUPDATE

A regular advertising feature enabling readers to obtain more information on companies' products or services.

Contact Joannah Cox on 0181 652 3620

DAQ Designer 2000

National Instruments new DAQ Designer™ 2000 is a **FREE CD** that helps engineers and scientists interactively configure custom measurement systems. DAQ Designer 2000 includes the new capability to recommend real-time data acquisition and motion control hardware and software.

Phone 01635 523545 Fax: 01635 524395
 e-mail info.uk@ni.com web www.ni.com/uk

A.C. POWER METERS

The latest Hioki Power Meters from Telonic. The 3332 can measure single phase power from below 1 Watt to 3kW and the 3331 measures 3 phase power up to 30kW. Features include inrush power measurement, consumptive and regenerative components, GPIB and RS232C interfaces as standard.

Further details from Telonic Instruments Ltd
 Tel: 0118 978 6911
 Fax: 0118 979 2338
 E-mail: info@telonic.co.uk

ELECTRONICS WORLD INCORPORATING WIRELESS WORLD

February 2000 £3.55

Adaptible active loudspeaker
 Measure power factor
 Get more from your RF generator
 Quantifying EMC
 Make better match filters
 Using striplines
 DSP for hearing aids

Exclusive reader offer - save 25% on B5Spice 2000

Richard's life and works - save 10% on the book

TRIDENT DISPLAYS
 A WORLD OF LCD...

The widest range of colour LCDs, LCD monitors and plug and play kits available in the UK, all in one easy to use brochure, is now available FREE!

It includes information on products ranging from 2.9" monitors to 16.1" colour LCD screens, mono/colour STN TFTs and touch screen technology from the world's leading manufacturers.

Phone TRIDENT today for your free copy.
 TEL: 01737 780790
 FAX: 01737 771908
 OR VISIT OUR WEBSITE: www.tridentdisplays.co.uk

Subscribe today!

Guarantee your own personal copy each month

Save on a 2 year subscription

ELECTRONICS WORLD
INCORPORATING WIRELESS WORLD

Subscribe today!

Guarantee your own personal copy each month

Save on a 2 year subscription

ELECTRONICS WORLD
INCORPORATING WIRELESS WORLD

WINRADIO®

TAKING THE EUROPEAN RADIO MARKET BY STORM

FREEPHONE 0800 0746263 TO PLACE A CREDITCARD ORDER

Receive a **FREE Mini-Cone Antenna** With Every WR-3100 order!*

JOIN THE TRUNKED RADIO REVOLUTION WITH YOUR WINRADIO RECEIVER!

1. Enjoy multiple, major trunk tracking modes
2. Automatic traffic following & sophisticated control panel
3. Take comfort in the automatic volume control
4. Single & dual receiver modes
5. Convenient inbuilt electronic logger and database
6. Comes complete with an inbuilt traffic recorder
7. Full XRS™ - compliant technology

The WINRADIO Trunking Option*

Trunking systems are used by public safety, transportation, business, law enforcement, government, military and other organisations. This software includes major trunking modes: Motorola SmartNet® and MPT1327.

ONLY £81.07 inc vat




TAKE A LOOK AT WINRADIO'S DIGITAL SUITE

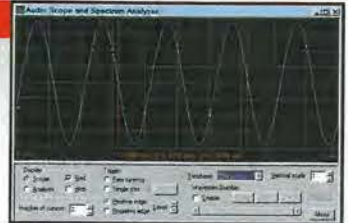1. WEFAX / HF Fax
2. Packet Radio for HF and VHF
3. Aircraft Addressing and Reporting System (ACARS)
4. Audio Oscilloscope, real time Spectrum Analyzer with calibration cursors
5. Squelch-controlled AF Recorder
6. DTMF CTSS decode and analyse

The DSP applet provided with the WR3100i spectrum monitor ISA card (£995+VAT) allows continuous control of audio bandwidth and other signal conditioning functions.

ONLY £81.07 inc vat
(requires SoundBlaster 16 compatible sound card)



WINRADIO® PC RECEIVERS

Available as either an internal ISA card that slips inside your PC, or as an external (portable) unit. WINRADIO combines the power of your PC with the very latest in synthesised receivers.

YOU CAN USE WINRADIO™ SCANNING PC COMMUNICATION RECEIVERS FOR:

Broadcast, media monitoring, professional & amateur radio communications, scanning, spot frequency, whole spectrum monitoring, instrumentation surveillance and recording.

If you're after the ultimate receiver-in-a-PC with full DSP then smile and say, "Hello" to the new **WR3100i-DSP** with its hardware for real-time recording, signal conditioning and decoding applications. It's all you need.

NEW EXTERNAL MODELS

EXTERNAL WINRADIO™

We are now able to offer you a complete range of stand-alone WINRADIO comms systems:

- WR1000e - £359 inc vat
- WR1550e - £429 inc vat
- WR3100e - £1169 inc vat

Each stand-alone unit connects to your PC through either the basic RS232, or through an optional PCMCIA adapter (for high speed control).

The units are powered through either your existing 12v supply, or through an (optional) NiMH rechargeable 12v battery pack.

"It's software is excellent.. more versatile and less idiosyncratic than that of the Icom IC-PCR1000"
WRTH 1999 Review

"Five stars for its mechanical design"
WRTH 1999 Review

"Most Innovative Receiver"
WRTH 1998 Awards



Model Name/Number	WR-1000i & WR-1000e	WR-1550i & WR-1550e	WR-3100i & WR-3100e
Construction of internals	WR-1000i/WR-1550i-3100iDSP- Internal full length ISA cards		
Construction of externals	WR-1000e/WR-1550e - 3100e - external RS232/PCMCIA (optional)		
Frequency range	0.5-1300 MHz	0.15-1500 MHz	0.15-1500 MHz
Modes	AM,SSB/CW,FM-N,FM-W	AM,LSB,USB,CW,FM-N,FM-W	AM,LSB,USB,CW,FM-N,FM-W
Tuning resolution	100 Hz (5 Hz BFO)	10 Hz (1Hz for SSB and CW)	10 Hz (1Hz for SSB and CW)
IF bandwidths	6 kHz (AM/SSB), 17 kHz (FM-N), 230 kHz (W)	2.5 kHz(SSB/CW), 6 kHz (AM) 17 kHz (FM-N), 230 kHz (W)	2.5 kHz(SSB/CW), 6 kHz (AM) 17 kHz (FM-N), 230 kHz (W)
Receiver type	PLL-based triple-conv. superhet		
Scanning speed	10 ch/sec (AM), 50 ch/sec (FM)		
Audio output on card	200mW	200mW	200mW
Max on one motherboard	8 cards	8 cards	6-8 cards (please ask)
Dynamic range	65 dB	70 dB	85dB
IF shift (passband tuning)	no	±2 kHz	±2 kHz
DSP in hardware	no - use optional DS software		YES (ISA card ONLY)
IRQ required	no	no	yes (for ISA card)
Spectrum Scope	yes	yes	yes
Visitune	yes	yes	yes
Published software API	yes	yes	yes (also DSP)
Internal ISA cards	£299 inc vat	£369 inc vat	£1169.13 inc
External units	£359 inc vat	£429 inc vat	£1169.13 inc (hardware DSP only internal)
PCMCIA Adapter (external):	£69.00 inc vat when bought with 'e' series unit (otherwise: £99 inc vat)		
PPS NiMH 12v Battery Pack & Chrg:	£99 inc vat when purchased with 'e' series unit (otherwise: £139 inc vat)		
The WINRADIO Digital Suite:	£74.99 inc vat when purchased with a WINRADIO receiver (otherwise: £81.05 inc vat)		

For your free (no obligation) info pack & WINRADIO demo disk go to: <http://www.broadercasting.com>. If you don't have access to the internet then by all means feel free to phone/fax us. *Trunked radio transmissions should only be received & decoded with permission of the originator of the transmission.

Please send all your enquiries to: info@broadercasting.com or Telephone: 0800 0746 263 or +44 (0)1245 348000 - Fax: +44 (0)1245 287057
Broadercasting Communication Systems, Unit B, Chelford Court, Robjohns Road, Chelmsford, Essex, CM1 3AG, United Kingdom

ES&OE WINRADIO and Visitune are trademarks of Rosetta Labs. Australia - copyright Broadercasting Communications Systems
Broadercasting Communication Systems is a trading name of USP Networks Ltd. *Free gifts are subject to availability
Registered trademarks are the property of their respective owners

Postage will be paid by licensee

Do not affix postage stamps if posted in Gt. Britain, Channel Islands, N. Ireland or the Isle of Man.

Business Reply Service
Licence No. CY711

ELECTRONICS WORLD
Reader Information Service
Reed Business Information
Oakfield House
Perrymount Road
Haywards Heath
Sussex RH16 3BR

SEE OVER!

211

ELECTRONICS WORLD

INCORPORATING WIRELESS WORLD

SUBSCRIPTION CARD

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ _____ made payable to **Reed Business Information**
Please charge my Mastercard/Visa/Amex account

With £ _____ Expiry Date _____

Signature _____

Name _____

Job Title _____

Address _____

Postcode _____

Tel: _____ Country _____

Post to:
ELECTRONICS WORLD
P.O. Box 302
Haywards Heath,
West Sussex RH16 3DH UK.

CREDIT CARD HOTLINE
Tel: +44 01444 445566
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing-promotion from other companies

SUBSCRIPTION RATES	
UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
Airmail	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

ELECTRONICS WORLD

INCORPORATING WIRELESS WORLD

SUBSCRIPTION CARD

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ _____ made payable to **Reed Business Information**
Please charge my Mastercard/Visa/Amex account

With £ _____ Expiry Date _____

Signature _____

Name _____

Job Title _____

Address _____

Postcode _____

Tel: _____ Country _____

Post to:
ELECTRONICS WORLD
P.O. Box 302
Haywards Heath,
West Sussex RH16 3DH UK.

CREDIT CARD HOTLINE
Tel: +44 01444 445566
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing-promotion from other companies

SUBSCRIPTION RATES	
UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
Airmail	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

Surely not. Surely someone somewhere has developed a portable programmer that has even more features, even greater flexibility and is even better value for money.

Actually, no. But don't take our word for it. Use the feature summary below to see how other manufacturers' products compare.

Dataman-48LV

- Plugs straight into parallel port of PC or laptop
- Programs and verifies at 2, 2.7, 3.3 and 5V
- True no-adaptor programming up to 48 pin DIL devices
- Free universal 44 pin PLCC adaptor
- Built-in world standard PSU - for go-anywhere programming
- Package adaptors available for TSOP, PSOP, QFP, SOIC and PLCC
- Optional EPROM emulator



Money-Back 30 day Trial

If you do not agree that these truly are the most powerful portable programmers you can buy, simply return your Dataman product within 30 days for a full refund

FREE
30 DAY TRIAL

powerful, portable programmers

still
the world's most

free software

upgrades +

technical support

for life

3
year
GUARANTEE

Support

- 3 year parts and labour guarantee
- Windows/DOS software included
- Free technical support for life
- Next day delivery - always in stock
- Dedicated UK supplier, established 1978

DATAMAN

Dataman Programmers Ltd, Station Road,
Maiden Newton, Dorchester, Dorset, DT2 0AE, UK

Telephone +44/0 1300 320719

Fax +44/0 1300 321012

BBS +44/0 1300 321095 (24hr)

Modem V.34/V.FCV.32bis

Home page: <http://www.dataman.com>

FTP: [ftp.dataman.com](ftp://ftp.dataman.com)

Email: sales@dataman.com

CE

£495
PLUS VRT

Dataman S4

- Programs 8 and 16 bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 microcontrollers and more
- EPROM emulation as standard
- Rechargeable battery power for total portability
- All-in-one price includes emulation leads, AC charger, PC software, spare library ROM, user-friendly manual
- Supplied fully charged and ready to use

S4 GAL module

- Programs wide range of 20 and 24 pin logic devices from the major GAL vendors
- Supports JEDEC files from all popular compilers

Still as unbeatable as ever!

Beware of cheap imitations. Beware of false promises. Beware of hidden extras.

If you want the best, there's still only one choice - Dataman.

Order via credit card hotline - phone today, use tomorrow.

Alternatively, request more detailed information on these and other market-leading programming solutions.

hotline
01300 320719



Orders received by 4pm will normally be despatched same day.

Order today, get it tomorrow!

CIRCLE NO. 10 ON REPLY CARD