


Reader competition see page 24

ELECTRONICS WORLD



OCTOBER 2003 £3.25


500W inverter project

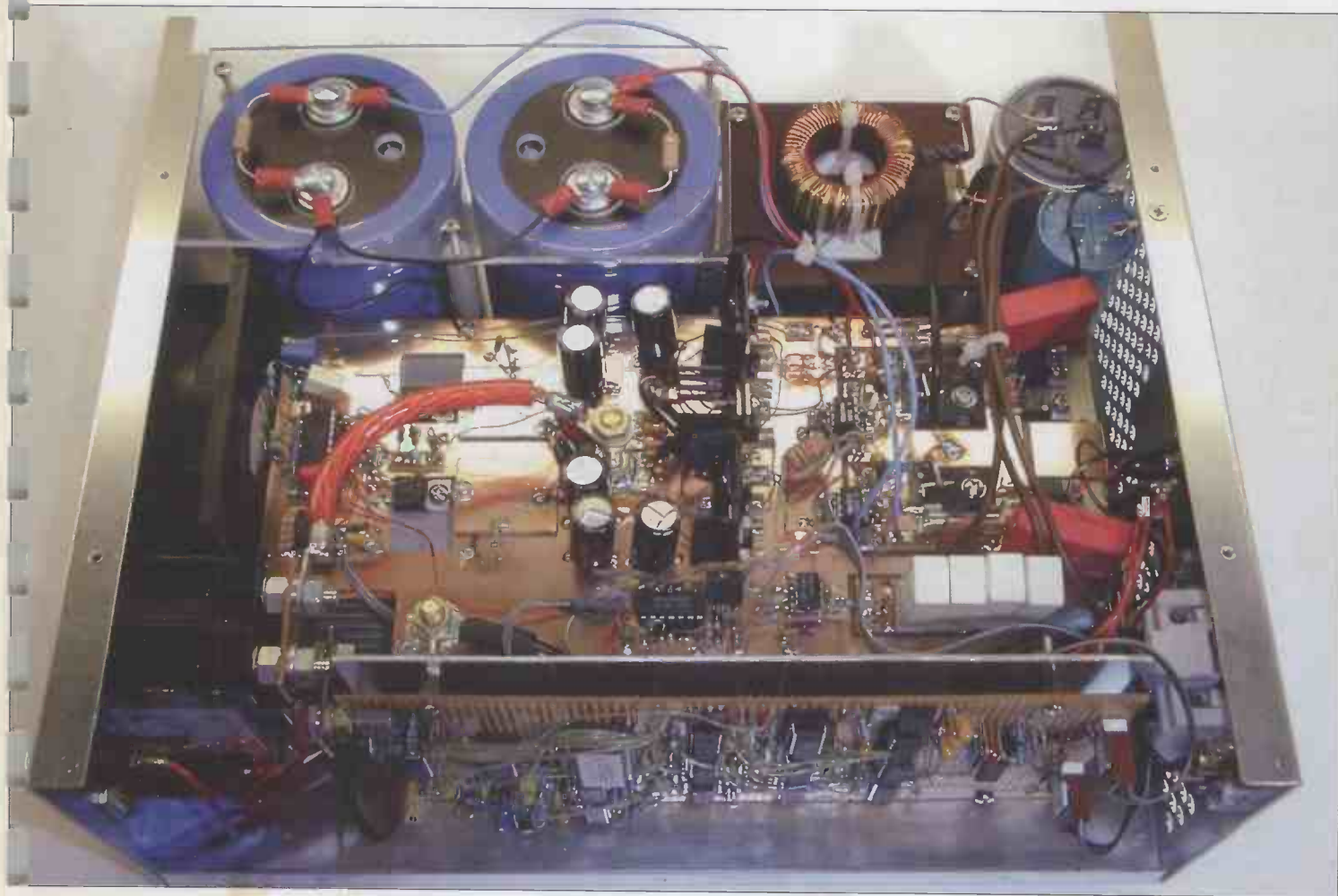

Noise and moving magnet cartridges

Wideband buffers

Win a serial I/O card

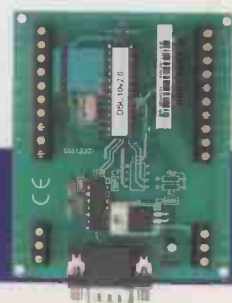



Hewlett Packard 3314A Function Generator 20MHz	£750
Hewlett Packard 3324A synth. function/sweep gen. (21MHz)	£1950
Hewlett Packard 3325B Synthesised Function Generator	£2500
Hewlett Packard 3326A Two-Channel Synthesiser	£2500
H.P. 4191A R/F Imp. Analyser (1GHz)	£3995
H.P. 4192A L.F. Imp. Analyser (13MHz)	£4000
Hewlett Packard 4193A Vector Impedance Meter (4-110MHz)	£2900
Hewlett Packard 4278A 1kHz/1MHz Capacitance Meter	£3500
H.P. 53310A Mod. Domain Analyser (opt 1/31)	£3950
Hewlett Packard 8349B (2 - 20 GHz) Microwave Amplifier	£2000
Hewlett Packard 8508A (with 85081B plug-in) Vector Voltmeter	£2500
Hewlett Packard 8904A Multifunction Synthesiser (opt 2+4)	£1750
H.P. ESG-D3000A 3GHz Signal Gen	£6995
Marconi 6310 - Prog'ble Sweep gen. (2 to 20GHz) - new	£2500
Marconi 6311 Prog'ble sig. gen. (10MHz to 20GHz)	£2995
Marconi 6313 Prog'ble sig. gen. (10MHz to 26.5GHz)	£3750
R&S SMG (0.1-1GHz) Sig. Generator (opts B1+2)	£2500
Fluke 5700A Multifunction Calibrator	£12500
Fluke 5800A Oscilloscope Calibrator	£9995

OSCILLOSCOPES

Gould 400 20MHz - DSO - 2 channel	£695
Gould 1421 20MHz - DSO - 2 channel	£425
Gould 4068 150MHz 4 channel DSO	£1250
Gould 4074 100MHz - 400 Ms/s - 4 channel	£1100
Hewlett Packard 54201A - 300MHz Digitizing	£750
Hewlett Packard 54502A - 400MHz - 400 MS/s 2 channel	£1600
Hewlett Packard 54520A 500MHz 2ch	£2750
Hewlett Packard 54600A - 100MHz - 2 channel	£675
Hewlett Packard 54810A 'Infinium' 500MHz 2ch	£2995
Hitachi V152/V212/V222/V302B/V302F/V353F/V550BV650F	from £100
Hitachi V1 100A - 100MHz - 4 channel	£750
Intron 2020 - 20MHz. Dual channel D.S.O (new)	£450
Iwatsu SS 5710/SS 5702 -	from £125
Kikusui COS 5100 - 100MHz - Dual channel	£350
Lecroy 9314L 300MHz - 4 channels	£2750
Meguro MSO 1270A - 20MHz - D.S.O. (new)	£450
Philips 3295A - 400MHz - Dual channel	£1400
Philips PM3070 - 100MHz - 2 channel - cursor readout	£650
Philips PM3392 - 200MHz - 200Ms/s - 4 channel	£1750
Philips PM3094 - 200MHz - 4 channel	£1500
Tektronix 468 - 100MHz D.S.O.	£500
Tektronix 2213/2215 - 60MHz - Dual channel	£900
Tektronix 2220 - 60MHz - Dual channel D.S.O	£850
Tektronix 2221 - 60MHz - Dual channel D.S.O	£850
Tektronix 2235 - 100MHz - Dual channel	£500
Tektronix 2245A - 100MHz - 4 channel	£700
Tektronix 2430/2430A - Digital storage - 150MHz	from £1250
Tektronix 2445 - 150MHz - 4 channel +DMM	£850
Tektronix 2445/2445B - 150MHz - 4 channel	£800
Tektronix 2465/2465A /2465B - 300MHz/350MHz 4 channel	from £1250
Tektronix 7104 - 1GHz Real Time - with 7A29 x2, 7B10 and 7B15	from £1950
Tektronix TAS 475 - 100MHz - 4 channel	£850
Tektronix TDS 310 50MHz DSO - 2 channel	£750
Tektronix TDS 520 - 500MHz Digital Oscilloscope	£2500

SPECTRUM ANALYSERS

Advantest 4131 (10kHz - 3.5GHz)	£3750
Advantest/TAKEDA RIKEN - 4132 - 100KHz - 1000MHz	£1350
Anritsu MS2613A 9kHz - 6.5GHz Spectrum Analyser	£4950
Ando AC 8211 - 1.7GHz	£1500
Avcom PSA-65A - 2 to 1000MHz	£750
Farnell SSA-1000A 9KHz-1GHz Spec. An.	£1250
Hewlett Packard 182T Mainframe + 8559A Spec.An. (0.01 to 21GHz)	£2000
Hewlett Packard 853A Mainframe + 8559A Spec.An. (0.01 to 21GHz)	£2500
Hewlett Packard 3582A (0.02Hz - 25.5kHz) dual channel	£1500
Hewlett Packard 3585A 40 MHz Spec Analyser	£3000
Hewlett Packard 3561A Dynamic Signal Analyser	£3500
Hewlett Packard 8568A -100kHz - 1.5GHz Spectrum Analyser	£3500
Hewlett Packard 8590A (opt 01, 021, 040) 1MHz-1.5MHz	£2500
Hewlett Packard 8596E (opt 41, 101, 105,130) 9KHz - 12.8GHz	£9950
Hewlett Packard 8713C (opt 1 E1) Network An. 3 GHz	£6000
Hewlett Packard 8713B 300kHz - 3GHz Network Analyser	£5000
Hewlett Packard 8752A - Network Analyser (1.3GHz)	£4995
Hewlett Packard 8753A (3000KHz - 3GHz) Network An.	£3250
Hewlett Packard 8753B+85046A Network An + S Param (3GHz)	£6500
Hewlett Packard 8754A - Network Analyser 4MHz -1300MHz	£1500
Hewlett Packard 8756A/8757A Scaler Network Analyser	from £900
Hewlett Packard 8757C Scaler Network Analyser	£3500
Hewlett Packard 70001A/70900A/70906A/70902A/70205A - 26.5 GHz Spectrum Analyser	£7000
IFR A7550 - 10KHz-GHz - Portable	£1750
Meguro - MSA 4901 - 30MHz - Spec Analyser	£600
Tektronix 492P (opt1,2,3) 50KHz - 21GHz	£3500
Willron 6409 - 10-2000MHz R/F Analyser	£1250
Tek 496 (9KHz-1.8GHz)	£2500

Radio Communications Test Sets

Hewlett Packard 8920B (opts 1,4,7,11,12)	£6750
Hewlett Packard 8922M + 83220E	£2000
Marconi 2955	£1250
Marconi 2955A	£1750
Marconi 2955B/60B	£3500
Marconi 2955R	£1995
Motorola R2600B	£2500
Racal 6111 (GSM)	£1250
Racal 6115 (GSM)	£1750
Racal 6103 (opts1, 2)	£5000
Rohde & Schwarz SMFP2	£1500
Rohde & Schwarz CMT 90 (2GHz) DECT	£3995
Rohde & Schwarz CMTA 94 (GSM)	£4500
Schlumberger Stabilock 4015	£3250
Schlumberger Stabilock 4031	£2750
Schlumberger Stabilock 4040	£1300
Wavetek 4103 (GSM 900) Mobile phone tester	£1500

MISCELLANEOUS

Ballantine 1620A 100Amp Transconductance Amplifier	£1250
EIP 545 Microwave Frequency Counter (18GHz)	£1000
EIP 548A and B 26.5GHz Frequency Counter	from £1500
EIP 575 Source Locking Freq.Counter (18GHz)	£1200
EIP 585 Pulse Freq.Counter (18GHz)	£1200
Fluke 6060A and B Signal Gen. 10kHz - 1050MHz	£950
Genrad 1657/1658/1693 LCR meters	from £500
Gigatronics 8541C Power Meter + 80350A Peak Power Sensor	£1250
Gigatronics 8542C Dual Power Meter + 2 sensors 80401A	£1995
Hewlett Packard 339A Distortion measuring set	£600
Hewlett Packard 436A power meter and sensor (various)	from £750
Hewlett Packard 438A power meter - dual channel	£1750
Hewlett Packard 3335A - synthesiser (200Hz-81MHz)	£1750
Hewlett Packard 3457A muli meter 6 1/2 digit	£850
Hewlett Packard 3784A - Digital Transmission Analyser	£2950
Hewlett Packard 37900D - Signalling test set	£2500
Hewlett Packard 34401A Multimeter	£500
Hewlett Packard 4274A LCR Meter	£1750
Hewlett Packard 4275A LCR Meter	£2750
Hewlett Packard 4276A LCR Meter (100MHz-20KHz)	£1400
Hewlett Packard 5342A Microwave Freq.Counter (18GHz)	£850
Hewlett Packard 5385A - 1 GHz Frequency counter	£495
Hewlett Packard 6033A - Autoranging System PSU (20v-30a)	£750
Hewlett Packard 6060A and B Electronic Load 300W	from £750
Hewlett Packard 6622A - Dual O/P system p.s.u	£950
Hewlett Packard 6624A - Quad Output Power Supply	£1750
Hewlett Packard 8350B - Sweep Generator Mainframe	£1500
Hewlett Packard 8642A - high performance R/F synthesiser (0.1-1050MHz)	£2500
Hewlett Packard 8656A - Synthesised signal generator	£750
Hewlett Packard 8656B - Synthesised signal generator	£995
Hewlett Packard 8657A - Synth. signal gen. (0.1-1040MHz)	£1500
Hewlett Packard 8657B - 100MHz Sig Gen - 2060 MHz	£3950
Hewlett Packard 8657D - XX DOPSK Sig Gen	£3950
Hewlett Packard 8901B - Modulation Analyser	£1750
Hewlett Packard 8903A, B and E - Distortion Analyser	from £1000
Hewlett Packard 11729B/C Carrier Noise Test Set	from £2500
Hewlett Packard 53131A Universal Frequency counter (3GHz)	£850
Hewlett Packard 85024A High Frequency Probe	£1000
Hewlett Packard 6032A Power Supply (0-60V)(0-50A)	£2000
Hewlett Packard 5351B Microwave Freq. Counter (26.5GHz)	£2750
Hewlett Packard 5352B Microwave Freq. Counter (40GHz)	£5250
Keithley 220 Programmable Current Source	£1750
Keithley 228A Prog'ble Voltage/Current Source IEEE.	£1950
Keithley 237 High Voltage - Source Measure Unit	£3950
Keithley 238 High Current - Source Measure Unit	£3750
Keithley 486/487 Picoammeter (+volt.source)	£1350/£1850
Keithley 617 Electrometer/source	£1950
Keithley 8006 Component Test Fixture	£1750
Marconi 2840A 2 Mbit/s Transmission Analyser	£1100
Marconi 6950/6960/6960A/6970A Power Meters & Sensors	from £400
Philips 5515 - TN - Colour TV pattern generator	£1400
Philips PM 5193 - 50 MHz Function generator	£1350
Philips PM 6654C System Timer Counter	£750
Panasonic VP 8175A Sig. Gen. (100KHz-140MHz) AM/FM/CW	as new £650
Rohde & Schwarz FAM (opts 2,6 and 8) Modulation Analyser	£2500
Rohde & Schwarz NRV/NRVD Power meters with sensors	from £1000
Tektronix 1720 Vectorscope	£950
Tektronix 1735 Waveform Monitor	£1100
Tektronix AM503 - AM503A - AM503B Current Amp's with M/F and probe	from £800
Wayne Kerr 3245 - Precision Inductance Analyser	£1750
Bias unit 3220 and 3225L Cal.Coil available if required.	(P.O.A)
Wayne Kerr 3260A + 3265A Precision Magnetics Analyser with Bias Unit	£5500
W&G PCM-4 PCM Channel measuring set	£3750

All equipment is used - with 30 days guarantee and 90 days in some cases.

Add carriage and VAT to all goods.

1 Stoney Court, Hotchkiss Way, Binley Industrial Estate
Coventry CV3 2RL ENGLAND

Tel: 02476 650 702

Fax: 02476 650 773

Web: www.telnet.uk.com

Email: sales@telnet.uk.com

3 COMMENT

On the turn

5 NEWS

- Fuel cell laptops in 2004
- Baby tags use wideband RF
- Silicon circuits top 100GHz
- Broadband meets expectations
- Keyboard gets virtual



- Amish lead in headlights
- Insurance costs to soar
- Secure satellite communications
- UK start-up improves infra-red comms



- Precision in CMOS voltage reference
- Power firm back in business
- micromachined switch sits on CMOS

12 HIGH PERFORMANCE 500W MAINS INVERTER

Paul Bennett shares his practical inverter design, especially for those who need a high surge performance.

19 FLAT, WIDEBAND BUFFERS

Many textbooks neatly sidestep the issue of stability in buffers – **Dewald de Lange** elucidates

24 COMPETITION

Win a software configurable serial I/O card, courtesy of Observant Electronics.

25 NEW PRODUCTS

The month's top new products.

34 CIRCUIT IDEAS

- RF power loader
- Simple triggered timer
- Electronic fluorescent lamp starter
- Simple fastest finger first circuit
- Oscilloscope DC offset adapter
- Missed call indicator

38 NOISE AND MOVING-MAGNET CARTRIDGES

Still close to the heart of serious audiophiles, MM cartridges and vinyl records are still a force to be reckoned with in this digital age.

Marcel van de Gevel investigates noise optimisation in preamps with a practical example.

44 SIMPLE FORMULAE FOR SKIN EFFECT

Leslie Green is back with some more equations, especially for wire lovers

48 CAPACITOR SOUNDS II

Cyril Bateman continues his design of the 'de facto' distortion analyser

53 LETTERS

- Self powered amp
- In circuit RF measurement
- Electronic Balun
- Illogicalities
- Hard times
- Measurements using slotted lines
- Technicians
- Easy job?
- Help Wanted

60 WEB DIRECTIONS

Useful web addresses for electronics engineers.

November issue on sale 2 October

FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
 ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
 BFR BFS BFT BFW BFX BFY BLY BLX BS BR BRX BRY BS
 BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUY
 BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS
 DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
 KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
 MC MDA J MJE MJF MM MN MPS MP5A MP5H MP5U
 MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
 SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
 STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB
 TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA
 UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN
 ZTX + many others

Please ask for our Free CD Rom STOCK LIST.
 WE STOCK A MASSIVE RANGE OF
 COMPONENTS!

Mail, phone, Fax, Credit Card orders & callers welcome.



Cricklewood Electronics Ltd

40-42 Cricklewood Broadway, London NW2 3ET
 Tel: 020 8452 0161 Fax: 020 8208 1441
 www.cricklewoodelectronics.co.uk
 E-mail: sales@cricklewoodelectronics.com

PCB-POOL®

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

- Prototypes at a fraction of the cost
- Industry standard quality
- Tooling and setup included
- Follow up series runs
- Any contour
- CAM / CAD consulting
- Fr4 1.6mm, 35µm Cu

PRICE EXAMPLE:
 1 EUROCARD 05/PTH

- + Tooling
- + Photoplots
- + VAT

= £ 29.89*

*Sterling rates may vary. Price = € 49



FREE with first order (while stocks last)

Tel: +353 (0)61 701170
 Fax: +353 (0)61 701164
 E-Mail: sales@beta-layout.com

Freephone
 0800-389 8560

Simply send your files and order ONLINE:

WWW.PCB-POOL.COM




Easy-PC for Windows

World Beating Value in PCB Design Software

from
£97

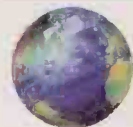High performance Windows based PCB Design Capture, Simulation and Layout software at prices you'd expect from your local computer store!



NEW! in Easy-PC 7


- Library Databook
- Step and repeat plotting
- Swap Connection Mode
- Dimensioning
- Copy to Metafile plus much more.....

Stop press... by customer demand, now with Tsien Boardmaker 2 design import...

Number One Systems delivers true 32 bit Windows software applications including features that a few short years ago would only have been available in software tools priced in the thousands!

Test drive Easy-PC and Easy-Spice for yourself and be prepared to be amazed at the super value...

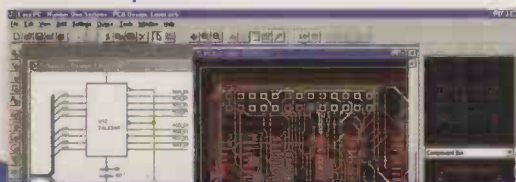Call for a brochure, price list and demo CD on +44 (0)1684 773662 or email sales@numberone.com



No1 Number One Systems

Number One Systems
 Oak Lane, Bredon
 Tewkesbury, Glos GL20 7LR
 United Kingdom

or download from
www.numberone.com

EDITOR**Phil Reed****p.reed@highburybiz.com****CONSULTANT****Ian Hickman****CONTRIBUTING EDITOR****Martin Eccles****EDITORIAL E-MAILS****EWeditor@highburybiz.com****EDITORIAL ADMINISTRATION****EWadmin@highburybiz.com****GROUP SALES****Reuben Gurunlian****01322 611292****ADVERTISEMENT****E-MAILS****r.gurunlian@highburybiz.com****CLASSIFIED FAX****01322 611292****PUBLISHING DIRECTOR****Tony Greville****ISSN 0959-8332****SUBSCRIPTION QUERIES**

Tel (0) 1353 654431

Fax (0) 1353 654400

Disclaimer

We work hard to ensure that the information presented in *Electronics World* is accurate. However, *Electronics World's* publisher - Highbury Business Communications - will not take responsibility for any injury or loss of earnings that may result from applying information presented in the magazine. It is your responsibility to familiarise yourself with the laws relating to dealing with your customers and suppliers, and with safety practices relating to working with electrical/electronic circuitry - particularly as regards electric shock, fire hazards and explosions.

On the turn

I keep getting reports lately that the industry is on the up. Whilst there is bound to be some PR 'hype' - reports are suggesting that recruitment is returning and capital spend in some quarters is definitely up. In a recent report commissioned by the IFC and produced by Booz Allen Hamilton, they reckon 16% of global electronics manufacturing, currently running at \$65Bn annually - is performed in emerging countries. More than half of the current emerging market production and 8% of total global production is already in China and \$46Bn or 77% of all emerging markets new production growth through 2005 will be in China, causing China to pass Europe as a source of electronics manufacturing. Food for thought.

I'm definitely getting more press releases about new products - that are genuinely new - and just some half-baked 'improvement'. One of which is the subject of our reader competition, courtesy of Observant Electronics. The product description will undoubtedly speak for itself - so good luck, but if you are not so lucky, we'll be running a reader discount offer in subsequent issues.

I've had few negative comments about Nigel Cook's leader in August. Whilst the piece may not have been quite up to the usual 'standard' (although I thought it was perfectly OK) I feel that some of your comments were extremely rude and not befitting of professionals. Rather than create an unholy slanging match, there will be no correspondence published on this subject. If however, you'd like to contribute a leader yourself - I am always happy to listen to any new ideas.

Housekeeping

Yet again, I have to report that EW has moved offices. I suppose it's a sign of the times that publishing is in a mess like the rest of industry and we are 'consolidating' to share resources with other similar magazines in the group. So, we've moved to sunny Swanley in Kent and because the extra journey

would have been too much - we've lost Jackie Lowe as well. While we look for a replacement her mail addresses remain active - but I'm doing her job as well - do not hold your breath for a reply - I'm going as fast I can! Thanks to Jackie for all the hard work she's put in over the years both with us (Highbury) and previously at Reed Publications.

I have also decided to make some new email boxes that will enable us to deal with you more efficiently. These new addresses are sprinkled around the magazine - but basically if you need me, use EWeditor, if you have an admin problem like we owe you money or an issue - use EWadmin if you have a letter for publication - use EWletters and finally if you've got a circuit idea - please use EWcircuit. All addresses are @highburybiz.com

There will undoubtedly be hiccoughs while mail of all types gets re-directed (and possibly lost) so please bear with us for a few months as we sort ourselves out.

Phil Reed

New editorial and advertising address

The Highbury Business Communications office previously at Cheam, Surrey has moved to Swanley in Kent. All correspondence intended for the editorial and advertising departments should be addressed to:

Electronics World,
Highbury Business Communications,
Nexus House,
Azalea Drive,
Swanley,
Kent, BR8 8HU

The switchboard phone no. is
01322 660 070
Advertising sales (Reuben Gurunlian)
Tel 01322 611292
Fax 01322 616 339

Electronics World is published monthly. Orders, payments and general correspondence to Jackie Lowe, Highbury Business Communications, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ.

Newstrade: Distributed by COMAG, Tavistock Road, West Drayton, Middlesex, UB7 7QE Tel 01895 444055.

Subscriptions: Wyvern Subscription Services, Link House, 8 Bartholomew's Walk, Ely Cambridge, CB7 4ZD. Telephone 01353 654431. Please notify change of address.

Subscription rates
1 year UK £38.95 O/S £64.50
US\$100.62 Euro 102.55

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

Printed by Polestar (Colchester) Ltd,
Filmsetting by Impress Repra by Design
A1 Parkway, Southgate Way, Orton Southgate,
Peterborough, PE2 6YN



HIGHBURY
Business Communications

A SUBSIDIARY OF HIGHBURY HOUSE COMMUNICATIONS PLC



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ

Prices Exclude Vat @17½%. UK Carriage £1.50 (less than 1kg) £3.50 greater than 1kg

Cheques / Postal orders payable to ESR Electronic Components. PLEASE ADD CARRIAGE & VAT TO ALL ORDERS



See Next / Last Months Ad. for COMPONENT ACCESSORIES

4000 Series	74HC32	£0.18	74LS107	£0.30
4000B	74HC42	£0.36	74LS109	£0.21
4001B	74HC73	£0.40	74LS112	£0.24
4002B	74HC74	£0.19	74LS113	£0.24
4007UB	74HC75	£0.31	74LS114	£0.36
4008B	74HC76	£0.20	74LS122	£0.31
4009UB	74HC85	£0.24	74LS123	£0.31
4010B	74HC86	£0.22	74LS125	£0.28
4011B	74HC107	£0.40	74LS126	£0.25
4012B	74HC123	£0.33	74LS132	£0.26
4013B	74HC125	£0.26	74LS133	£0.36
4014B	74HC126	£0.46	74LS136	£0.23
4015B	74HC132	£0.26	74LS139	£0.33
4016B	74HC133	£0.34	74LS138	£0.26
4017B	74HC137	£0.30	74LS145	£0.56
4018B	74HC138	£0.29	74LS148	£0.64
4019B	74HC158	£0.54	74LS151	£0.38
4020B	74HC159	£0.31	74LS153	£0.38
4021B	74HC151	£0.33	74LS156	£0.36
4022B	74HC153	£0.30	74LS157	£0.22
4023B	74HC154	£0.85	74LS158	£0.21
4024B	74HC157	£0.40	74LS160	£0.48
4025B	74HC158	£0.23	74LS161	£0.32
4026B	74HC160	£0.28	74LS162	£0.44
4027B	74HC161	£0.28	74LS163	£0.32
4028B	74HC162	£0.45	74LS164	£0.43
4029B	74HC163	£0.26	74LS165	£0.48
4030B	74HC164	£0.23	74LS173	£0.24
4035B	74HC165	£0.35	74LS174	£0.24
4040B	74HC173	£0.38	74LS175	£0.24
4041B	74HC174	£0.27	74LS190	£0.29
4042B	74HC175	£0.35	74LS191	£0.27
4043B	74HC192	£0.72	74LS192	£0.60
4044B	74HC193	£0.40	74LS193	£0.43
4046B	74HC195	£0.32	74LS195	£0.24
4047B	74HC240	£0.32	74LS196	£0.24
4048B	74HC241	£0.37	74LS221	£0.41
4049B	74HC244	£0.42	74LS220	£0.32
4049UB	74HC245	£0.42	74LS241	£0.32
4050B	74HC251	£0.30	74LS243	£0.30
4051B	74HC253	£0.25	74LS244	£0.38
4052B	74HC257	£0.25	74LS245	£0.38
4053B	74HC259	£0.57	74LS247	£0.60
4054B	74HC273	£0.32	74LS251	£0.24
4055B	74HC299	£0.61	74LS257	£0.24
4060B	74HC365	£0.28	74LS258	£0.24
4063B	74HC367	£0.38	74LS259	£0.45
4066B	74HC368	£0.25	74LS266	£0.14
4067B	74HC373	£0.35	74LS273	£0.32
4068B	74HC374	£0.40	74LS279	£0.24
4069UB	74HC390	£0.52	74LS283	£0.47
4070B	74HC393	£0.38	74LS365	£0.21
4071B	74HC541	£0.25	74LS367	£0.21
4072B	74HC563	£0.56	74LS368	£0.21
4073B	74HC564	£0.48	74LS373	£0.32
4075B	74HC573	£0.27	74LS374	£0.38
4076B	74HC574	£0.38	74LS377	£0.32
4077B	74HC594	£0.27	74LS390	£0.34
4078B	74HC588	£0.46	74LS393	£0.33
4081B	74HC4002	£0.31	74LS395	£0.26
4082B	74HC4017	£0.36		
4085B	74HC4020	£0.36		
4086B	74HC4040	£0.29		
4093B	74HC4049	£0.29		
4094B	74HC4051	£0.50		
4097B	74HC4052	£0.43		
4098B	74HC4053	£0.38		
4099B	74HC4060	£0.23		
4502B	74HC4075	£0.27		
4503B	74HC4078	£0.32		
4508B	74HC4511	£0.64		
4510B	74HC4514	£0.84		
4511B	74HC4538	£0.41		
4512B	74HC4543	£0.90		
4515B				
4516B				
4518B				
4521B				
4526B				
4527B				
4528B				
4529B				
4532B				
4536B				
4538B				
4541B				
4543B				
4555B				
4556B				
4558B				
4559B				
4724B				
40106B				
40109B				
40174B				
40175B				

ICM7556	£0.88	27C4001-120E5.84	£0.33
L165V	£2.36	93C46N	£0.33
L272M	£1.21		
L293E	£4.03		
L297	£5.12		
L298N	£6.67		
L4960	£2.81		
L6219	£4.48		
LF347N	£0.46		
LF351N	£0.42		
LF356	£0.40		
LF358	£0.38		
LF411CN	£0.40		
LM301AN	£0.25		
LM311N8	£0.25		
LM319N14	£0.90		
LM324	£0.21		
LM335Z	£1.00		
LM339N	£0.19		
LM348N	£0.36		
LM350Z	£1.90		
LM358N	£0.17		
LM380N	£0.81		
LM386	£0.45		
LM392N	£0.79		
LM393N	£0.21		
LM748CNB	£0.29		
LM1881	£0.36		
LM2901N	£0.15		
LM2917N8	£0.24		
LM3900N	£0.72		
LM3914	£1.97		
LM13700	£1.04		
LMC660CN	£1.26		
LMC6032IN	£1.55		
LP311N	£0.74		
LP324N	£0.72		
LT1013CNB	£0.56		
M34-1	£0.64		
M34-2	£0.38		
MAX202CPE	£1.97		
MAX208CN	£6.99		
MAX220CPE	£5.06		
MAX222CPE	£5.06		
MAX232CPE	£1.30		
MAX483CP	£3.13		
MAX485CP	£2.08		
MAX631ACP	£4.99		
MAX635ACP	£4.99		
MC1282CP	£2.80		
MC1488	£0.40		
MC1489	£0.40		
MC3302	£0.56		
MC4558P	£0.33		
MK484	£0.66		
NE521N	£6.39		
NE555N	£0.17		
NE556N	£0.29		
NE565N	£2.30		
NE567N	£0.39		
NE592	£0.62		
NE532N	£0.48		
NE533N	£0.38		
NE539N	£0.45		
OP07CN	£0.90		
OP27CN	£2.33		
OP90CP	£2.91		
OP97FP	£1.84		
OP113GP	£3.44		
OP176GP	£2.09		
OP177GP	£1.86		
OP200GP	£5.60		
OP213GP	£5.20		
OP275GP	£2.57		
OP283GP	£2.27		
OP290GP	£2.20		
OP297GP	£4.28		
OP400GP	£4.64		
OP495GP	£11.81		
RC4136	£8.69		
RC4136	£1.00		
SG3524N	£0.70		
SG3543	£6.88		
SSM2141P	£3.21		
SSM2142P	£6.16		
SSM2143P	£3.78		
TBA120S	£1.04		
TBA800	£0.75		
TBA810S	£0.65		
TBA820M	£0.58		
TDA1170S	£4.80		
TDA2004	£2.21		
TDA2030AV	£2.20		
TDA2050V	£2.28		
TDA2611A	£1.88		
TDA2822A	£0.86		
TDA2653A	£2.99		
TD7361N	£1.25		
TED9718DP	£5.03		
TEA5115	£0.67		
TLO61CP	£0.37		
TLO62CP	£0.60		
TLO64CN	£0.72		
TLO71CN	£0.32		
TLO72CN	£0.32		
TLO74CN	£0.40		
TLO81	£0.28		
TLO82CN	£0.32		
TLO84CN	£0.42		
TL7705ACP	£0.63		
TL7713	£0.60		
TL7722N	£0.60		
TS274CN	£0.50		
TS555CN	£0.35		
TMP01FP	£5.60		
UA741CN	£0.25		
ULN2003A	£0.38		
ULN2004A	£0.44		
ULN2803A	£0.44		
ULN2804A	£0.44		
ULN2805A	£0.44		
ULN2806A	£0.44		
ULN2807A	£0.44		
ULN2808A	£0.44		
ULN2809A	£0.44		
ULN2810A	£0.44		
ULN2811A	£0.44		
ULN2812A	£0.44		
ULN2813A	£0.44		
ULN2814A	£0.44		
ULN2815A	£0.44		
ULN2816A	£0.44		
ULN2817A	£0.44		
ULN2818A	£0.44		
ULN2819A	£0.44		
ULN2820A	£0.44		
ULN2821A	£0.44		
ULN2822A	£0.44		
ULN2823A	£0.44		
ULN2824A	£0.44		
ULN2825A	£0.44		
ULN2826A	£0.44		
ULN2827A	£0.44		
ULN2828A	£0.44		
ULN2829A	£0.44		
ULN2830A	£0.44		
ULN2831A	£0.44		
ULN2832A	£0.44		
ULN2833A	£0.44		
ULN2834A	£0.44		
ULN2835A	£0.44		
ULN2836A	£0.44		
ULN2837A	£0.44		
ULN2838A	£0.44		
ULN2839A	£0.44		
ULN2840A	£0.44		
ULN2841A	£0.44		
ULN2842A	£0.44		
ULN2843A	£0.44		
ULN2844A	£0.44		
ULN2845A	£0.44		
ULN2846A	£0.44		
ULN2847A	£0.44		
ULN2848A	£0.44		

Fuel cell laptops in 2004

NEC has unveiled a prototype notebook PC with an internal fuel cell.

The fuel cell boasts the world's best output density, claims NEC, of 40mW/cm, achieves an average output of 14W and a maximum output of 24W.

The firm aims to release a notebook PC with a built-in fuel cell on the market by end of 2004, and to make a notebook PC equipped with an internal fuel cell that has a battery life of 40 hours available within two years.

The cell employs carbon nano tubes, in the form of what NEC calls carbon-nano-horns.


"We use the carbon-nano-horn as an electrode covered by a catalyst using white gold. If carbon-nano-horn is used, the catalyst can be attached on the surface of an electrode evenly and in very small particles," said NEC. "If acetylene black is used in the electrode as usual, the catalyst cannot be attached evenly in very small particles."

How the catalyst is attached is the impact on the power of the battery.

"Because of the evenly attached catalyst and the small particles, our battery can generate bigger power with lower cost than other ways," said NEC



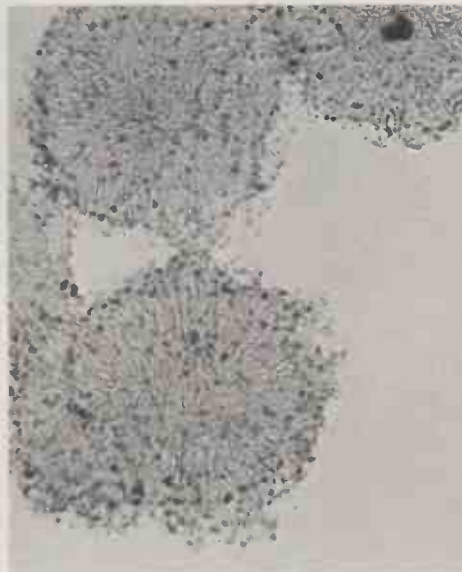The little black specs are white gold catalysts, small and evenly distributed (better) in one case, and clumpy and large in the other.



Fuel cell specification

Average output	14W
Maximum output	24W
Voltage	12V
Weight	900g
Fuel weight	300g (300cc)
Fuel concentration	10% methanol
PC weight incl. cell	2 kg
PC size	288 x 280 x 40mm
Operating time	5 hours aprox.

Academy recognises youth and experience

The Royal Academy of Engineering has elected its youngest ever fellows in Paul Westbury (33) and Professor Colin McInnes (35).

Westbury is a structural engineer at Buro Happold, and was project engineer for the Millennium Dome. McInnes is Professor of space systems engineering at the University of Glasgow with significant work on solar sails and autonomous guidance of space vehicles.

"Britain is privileged to be the home of some of the world's best engineers," said Sir Alec Broers, president of the RAE.

"The Academy is working hard to ensure that these people are recognised and that their skills are utilised for the greater good of the country."

Both engineers beat the RAE's previous age record held by Professor Polina Bayvel, of the department of electrical and electronic engineering at University

College London, who was 36 on election.

The RAE also elected Gordon Moore, chairman emeritus and co-founder of Intel, as a foreign member.

"Not only have Gordon's pioneering technological efforts revolutionised the design of virtually all modern products, but his business leadership and his philanthropic activities have had an enormously positive impact on society," said Broers.

Keyboard gets virtual

A chipset and optical components that project the image of a keyboard and then tracks a user's fingers has been developed by US firm Canesta.

The technology could be used with mobile phone and other handheld devices in lieu of a physical keyboard.

Three devices make up the system: A scanning projector to create the

'keyboard'; an infra-red LED and optics to create a beam; and a sensor which locates fingers in space, assessing when they touch the virtual keys.

By using IR light the system can work in any ambient light conditions. A wide angle lens in the projector allows the keyboard to be imaged from relatively low angles.

Other applications for the system include intelligent airbags that sense the size and position of a car's occupants, security systems that detect the difference between an intruder and pets, and virtual reality games with no mechanical input.



Silicon circuits top 100GHz

Researchers at Infineon Technologies in Germany have constructed silicon germanium (SiGe) circuits that run at up to 110GHz.

The firm made three devices; a 110GHz dynamic frequency divider, an 86GHz static frequency divider and a 95GHz voltage controlled oscillator.

The dynamic divider has a ratio of two, runs from a 5V supply and draws 62mA. The static design divides by 32, and consumes 180mA at 5V. The VCO circuit operates between 95 and 98GHz with a phase noise of -97dBc/Hz . Output power is -6dBm , said Infineon. At 5V it draws 12mA.

A 77GHz radar transceiver is also possible, said the firm. In the long term the firm said it could manufacture devices for 40Gbit/s wireline telecoms, microwave radio links, ultra wideband wireless up to 60GHz and automotive radar.

The basis for the circuits was Infineon's SiGe:C process, which produces transistors with cutoff frequencies of over 200GHz.

IBM has also done significant work in this area. It has produced SiGe transistors with transition frequencies of 350GHz, although it is yet to release details of circuits made with the devices.

In Brief

Baby tags use wideband RF

An RF tagging system that uses ultra wideband (UWB) technology to track documents and patients around hospitals in real time is being developed by two Cambridge companies.

Ubisense, which is developing the local positioning system (LPS) using UWB expertise from technology house Cambridge Consultants, said lost patient records are a major problem. Knowing immediately where records are means fewer patients arriving for surgery without their notes, fewer delays in treatment, and greater patient safety.

Precise applications are still being defined, but Ubisense said tracking

the location of babies would be a good trial subject.

Operating at 5.8GHz, a network of sensors distributed throughout a building can locate a credit card-sized tag to within 15cm in real time - an order of magnitude better than that available from wireless LAN or Bluetooth-based systems.

Depending on the composition of the hospital's walls, a network should need around 25 sensors for every 1000m².

"We're just getting these ready within the NHS," explained David Theriault, CEO of Ubisense. "It just literally has not been done before... We need details about the demand for applications and the cost."

The regulatory position over UWB is still unclear in the UK, although developers' licences are being granted by the

Radiocommunications Agency. The FCC in the US is leading the standardisation process for consumer systems.

Broadband meets expectations

A Website devoted to all things broadband has found that ADSL services can reach almost 90 per cent of their rated speed in downloads.

ADSLguide has tested all the UK's 512kbit/s ADSL operators, and found that the fastest, Eclipse Internet, reaches a download speed of 457.2kbit/s and an upload rate of 240.8kbit/s.

All the top ten services, which includes names such as Pipex, BT and Demon, exceed 430kbit/s in download and 225kbit/s in upload. www.adslguide.org.uk

Amish lead in headlights

The Amish of Pennsylvania, members of a religious sect known for rejecting modern conveniences including cars, are adopting LED headlights for their horse-drawn buggies to avoid being hit by cars at night.

“With conventional lighting systems, buggy owners have to drag a 60 or 70 pound (30kg) battery out of a carriage and lug it over to a charging station after roughly six hours of operation, which typically translates to every two weeks,” said Elam Beiler, president of Sunline Solar, a part-Amish-owned alternative energy firm in Pennsylvania. “With LEDs, the buggy battery stays charged for as much as 100 hours of run time, so

recharging is required only every six months.”

In addition, Beiler predicts that widespread adoption of LEDs in Amish buggies will make it possible to reduce weight of carriage batteries by half in coming years.

Sunline uses a single Lumileds Luxeon red LED in its tail light and eight whites in its headlamp.

“There is some irony in the fact that a culture that resists most of the ingredients of a modern lifestyle is embracing a Silicon Valley technology,” said Fran Douros, marketing manager at Lumileds. “In some sense the Amish are even ahead of the technology curve because LED-powered headlamps are available in Amish buggies



before they are available in cars.”

Amish charging stations are solar powered as they do not use mains electricity.

www.sunlinesolar.com

Insurance costs to soar

The bill for employers' liability insurance could go up by £150m under plans to recover NHS costs in all compensated workplace accidents.

The warning comes from the Engineering Employers' Federation

EEF, which added that UK manufacturing will be hit badly by the Health and Social Care Bill.

“The Department of Health expects the employers' liability insurance system to foot the bill but, as this is a compulsory insurance, the costs will simply be spread among all employers in the form of rising premiums,” said the EEF's

southern regional group.

Moreover, the proposals would unfairly penalise companies with the best safety records, pointed out David Seall, chief executive of EEF South: “Employers who take positive action to improve the health and safety of their employees will subsidise those who do not or who are negligent.”

Researchers pave way to completely secure satellite communications

Austrian researchers have used free-space links to successfully transmit a pair of quantum entangled photons to two independent receivers. The work could lead eventually to completely secure satellite-based communications.

Entangled particles exist in related states that remain undetermined until a measurement is made. Once a measurement is performed on one, the other instantaneously ‘knows’ what state it is in. In cryptography, the effect allows a key to be generated with complete security between receivers sharing the entanglement.

However, entanglement can break down due to interactions with the environment in a process known as decoherence. The scientists, from the Institute for Experimental Physics in Vienna, used free-space links to probe the distances over which decoherence occurs.

Their experiment used receivers spaced 150m and 500m respectively from the entangled photon source, with no clear line of sight between them - and the Danube river in between. The links had an attenuation of around 12dB, which the researchers said is similar to the performance currently available from satellite links, making a satellite-based secure communications system a feasible aim. The research was published in the August 1 issue


of the journal Science.

Brian Lowans, team leader in the Single Photon Optical Techniques group at QinetiQ in Malvern, said: “This is a significant achievement and is currently a world record for this technique. It is important because it is currently unknown over what distance entanglement can be maintained before decoherence affects the exchange.”

The instantaneous transfer of information between entangled particles when a

measurement is made is the so-called ‘spooky action at a distance’ identified by Einstein, Podolsky and Rosen in their famous 1935 thought experiment.

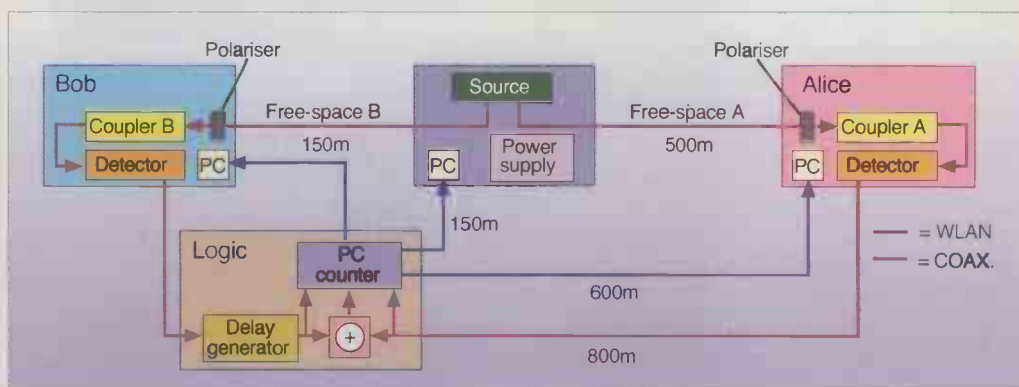QinetiQ itself, with Munich's Ludwig Maximilians University, set a world record of 23.4km for free-space quantum key distribution between two points in the Alps last year. Its system used attenuated laser pulses to achieve single photon exchange.



Antenova, Orange and Queen Mary University team up to increase spectrum efficiency

Cambridge-based antenna company Antenova, with Queen Mary University of London, has won a contract from the Radiocommunications Agency to look into MIMO (multi-input multi-output) antenna arrays for laptops, PDAs and phones.

"This forms part of a wider investigation commissioned by the Radiocommunications Agency into optimising spectrum efficiency to enable future expansion of wireless network systems by using MIMO technology with multiple antennas at the handset and basestations," said Antenova.

Rather than just pick the biggest signal from several antennas, MIMO techniques make use of normally-disruptive multi-path effects and combine the outputs of several receive channels in a constructive way using digital signal processing.

Coding such as variable time delays at multiple transmit antennas assist in signal recovery.

Antenova's specialist is its high dielectric antenna (HDA) technology which makes antennas compact, and less likely to interact than conventional antennas. Queen Mary will be providing a complementary technology known

as 'photonic band-gap surfaces', which can enhance isolation between antenna ground planes. Queen Mary will also investigate alternative antenna technologies which could provide both spatial and polarisation diversities for MIMO technology.

Phone company Orange is also involved, providing technical and commercial expertise from an operator's standpoint.

www.antenova.com
www.orange.com
www.qmul.ac.uk
www.radio.gov.uk

Micromachined switch sits on CMOS

STMicroelectronics has released details of a technique to integrate RF switches into circuits fabricated using standard CMOS technology.

"The switch promises to enhance the performance of mobile phones and similar portable terminals where efficient RF switching is required to minimise power consumption," said the company.

The 'Above IC' switch, as it is called, has been developed jointly by ST and long-term research partner CEA-LETI at ST's Crolles1 facility in France. "It meets the four key criteria of high reliability, low power consumption, low actuation voltage and compatibility with SoC

fabrication techniques," said ST.

The moving element in the switch consists of a $400 \times 50 \mu\text{m}$ beam made from silicon nitride and aluminium, and includes titanium nitride heating resistors and electrostatic holding electrodes. It is fixed at both ends.

Heating with 20mA at 2V bends the beam centre downwards through bi-metallic distortion to meet a gold contact $3 \mu\text{m}$ below.

Actuation takes around $200 \mu\text{s}$, an activation energy of $8 \mu\text{J}$.

Once the switch has been turned ON, a voltage is applied to the holding electrodes, producing an electrostatic force that retains the

beam in position, allowing the heating current to be turned off.

For the first prototypes, the voltage required to achieve electrostatic hold was 15V and with improved stress control for the beam material this is expected to be reduced to 10V.

More than 10^9 switching cycles have been demonstrated, claims ST, without any failure or contact degradation.

Insertion loss is 0.18dB and isolation is 57dB at 2GHz.

ST and CEA-LETI are now working to optimise the electrostatic hold, develop wafer-level packaging and to cut cost by reducing the number of masks required.

Power firm back in business

Custom power supply manufacturer VxI Power has been setup following a management buyout of Bulgin Power Source.

Bulgin Power Source called in the receivers last year, but has now been revived by former managers Grant Ashley and Tim McCann and 14 of the 70 employees made redundant.

"We are hoping to take on more, but it depends on how business grows," said Ashley, a director at VxI.

The firm is aiming its products at the fire protection, security and utilities markets. Typical products include 12/24V AC-DC converters up to several kilowatts.

VxI will also perform small scale contract manufacturing at its Lincoln plant.



UK start-up improves infra-red comms

Optical Antenna Solutions (OAS) of Coventry has produced its first technology demonstrator, an optical device which replaces the lens in optical TO18 packages to improve photodiode performance.

Optical antennas - see the cross section - capture light like normal lenses for rays near the axis. However off-axis rays, which would be wasted by a normal lens, are also directed to the output of an optical antenna by a single internal reflection. This means gain holds up further from the centre axis - out to the critical angle where a single bounce no-longer works.


The type of optical antenna the company is developing is more accurately described as a dielectric totally internally reflecting concentrator, or DTIRC, which was developed at Warwick University and which spun-out OAS.

OAS' partner for the technology demonstrator is German firm Silicon Sensors.

The demonstration DTIRC has a field of view of ± 25 degree - see graph - and was swapped into a PD2-6 from Silicon Sensors.

The graph shows the DTIRC performance as well as the maximum performance available from a conventional lens with the same field of view.

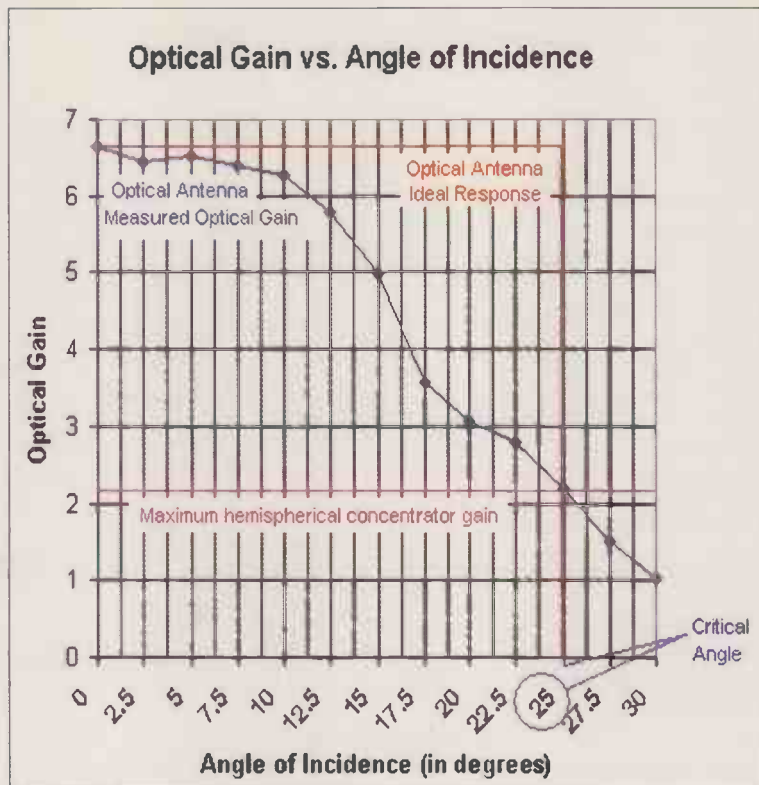Other versions have been produced for low light levels, using Silicon Sensor's series-6 chips, and for high bandwidth applications using high-speed epitaxial series-5 chips.



OAS is also working with members of the infra-red communications industry body IrDA to develop improved infra-red devices.

"We expect that opto-electronic components including IrDA devices will go through a period of enhancement to meet the demands and challenges associated with achieving more bandwidth and better


signal to noise," said OAS marketing director Alex Clarke.

As DTIRCs can be designed to squeeze light down to a small aperture, they can be designed to reduce the size of photodiode chip needed for a certain field of view. Smaller chips mean less capacitance, and therefore faster operation.

www.opticalantennasolutions.com

University of Warwick postgraduate Roberto Ramirez-Iniguez has earned his PhD for his work developing dielectric totally internally reflecting concentrators, the technology behind Optical Antenna Solutions (OAS).

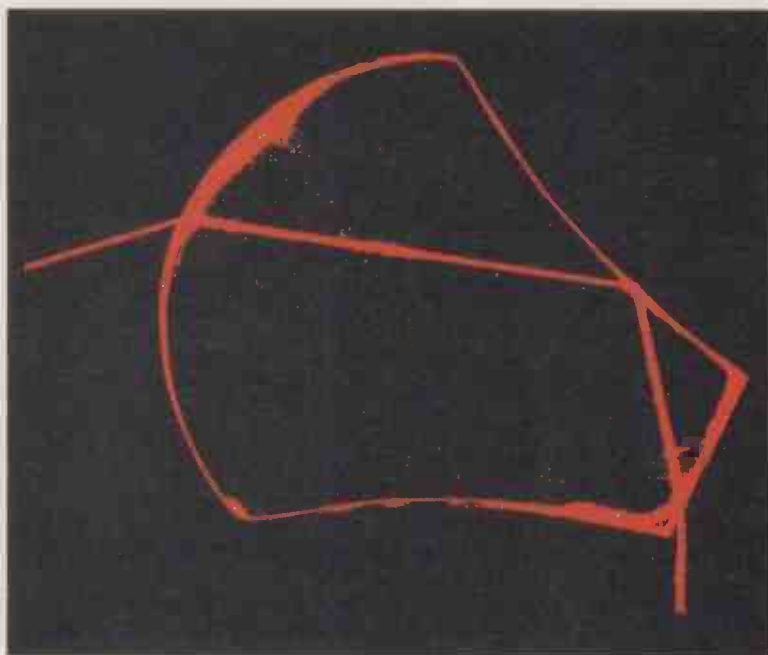He previously completed a master's degree in Communications and Real-Time Electronic Systems at Bradford University and started his PhD work there under the supervision of Professor Roger Green. Green moved to Warwick University to create the Communications and Signal Processing Research Group and Ramirez-Iniguez followed him. Together they founded OAS.



For on-axis light, the antenna acts like a lens. Off-axis light is internally reflected once, and still makes it to the output (right) - where a silicon sensor would collect it.

Floating gate puts precision in CMOS voltage reference

Xicor has introduced a floating gate-based precision voltage reference.

Floating gates, mosfet gates that are isolated on all sides, are used in flash and eeprom memory, but are seldom used in analogue applications.

The firm has used a floating gate as a means to fine-tune a CMOS voltage reference, whose output voltage is normally dependant on doping levels and is, as such, un-tunable.

The voltage reference is the middle four transistors of the diagram, ladled 'Reference Amp'. Its output is the sum of the threshold voltages of the two lower fets - with the left-hand fet being a depletion mode device which self-biases to

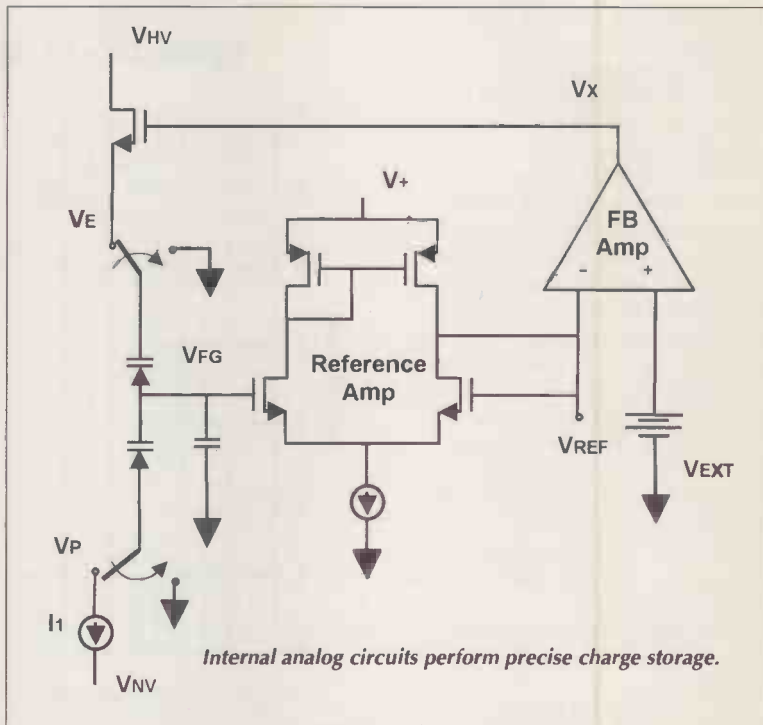


Table 1. Floating-gate voltage reference measured data

● Initial accuracy	<0.2mV
● Low TC	3ppm/°C
● Low drift	10ppm/1000hr
● Low power	500nA at 5V

have its threshold voltage on its source in this configuration.

Charging the floating gate through its isolating oxide - represented by the gate capacitor and two tunnel diodes respectively - sets the threshold voltage and would be a hit-and-miss affair if it wasn't for the rest of the circuit shown.

In it, a current sink draws electrons through the oxide from the bottom

of the floating gate while a controllable voltage source feeds electrons through the oxide into the top.

With a fixed voltage source, there are always a constant number of electrons in the gate, even if some are entering and some are leaving at all times.

The op-amp alters the voltage source until sufficient electrons are on the gate to make the reference output voltage (V_{REF}) equal the calibration voltage (V_{EXT}).

Once this happens, the switches are thrown and the right number of electrons are locked into the floating gate - "without loss for between 10 to 100 years," said the company.

Calibration is actually in two stages, with V_{EXT} slightly adjusted to allow for circuit offsets in the second phase.

Adjusted accuracy is better than 0.2mV.

The right hand lower transistor actually includes a buffer amplifier to reduce the output impedance of the reference.


The on-chip calibration circuit is disabled permanently after use to save power, leaving the overall current consumption at an astonishingly low 500nA.

Temperature coefficient can be inherently good in CMOS voltage references, and Xicor claims to have

pulled out all the stops with its latest design to get 5ppm/°C.

The first two devices are the X60008CIS8-50 ($\pm 0.5mV$) and X60008DIS8-50 ($\pm 1.0mV$).
www.xicor.com

Ideal tunnel diode characteristic.

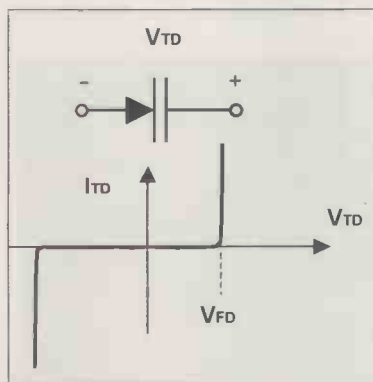

Xicor reference specification

- 5V output
- $\pm 0.5mV$ initial accuracy
- 5ppm/°C temperature coefficient
- 10ppm/1,000Hr stability
- 30 μV_{p-p} noise voltage (0.1 to 10Hz)
- $\pm 10mA$ output current
- 500nA supply current
- 40 to +85°C operating range

Give me Sunshine

Internet connections running at 54Mbit/s and costing just £10 per month should start soon in the east of England with a service called Sunshine.

The wireless service is aimed primarily at business users, but the operator said it would welcome residential subscribers. It promises no connection fees.

By the end of the year, the service will cover areas within 10km of Bingham, Bottesford, Bourne, Elton, Scalford, South Witham, Stamford, and Uppingham.

The firm behind the high speed access is planning further rollouts in Cambridgeshire, Essex, Leicestershire, Lincolnshire, Norfolk, North Lincolnshire, Rutland and Suffolk next year. By 2005 it hopes to have national coverage.

THERE IS INTERESTING NEWS



THE FIRST USB 2.0
100 MS/S, 12-16 bit
MEASURING INSTRUMENT
IN THE WORLD

PC CONTROLLED MEASURING INSTRUMENT
COMPLETE PACKAGE STARTING AT £ 435

OSCILLOSCOPE


FFT ANALYSER

VOLTMETER

RECORDER

The Handyscope 3 is a powerful and versatile two channel measuring instrument with an integrated function generator.

- USB 2.0 connection (USB 1.1 compatible)
- sample speed up to 100 MHz per channel
- 8 to 16 bit resolution (6 μ Volt resolution)
- 50 MHz bandwidth
- input sensitivity from 200 mV up to 80 Volt
- large memory up to 131060 samples per channel
- four integrated measuring devices
- spectrum analyser with a dynamic range of 95 dB
- fast transient recorder up to 10 kHz
- several trigger features
- auto start/stop triggering
- auto disk function up to 1000 files
- auto setup for amplitude axis and time base
- auto trigger level and hysteresis setting
- cursor measurements with 21 read-outs
- very extensive function generator (AWG) 0-2 MHz , 0-12 Volt

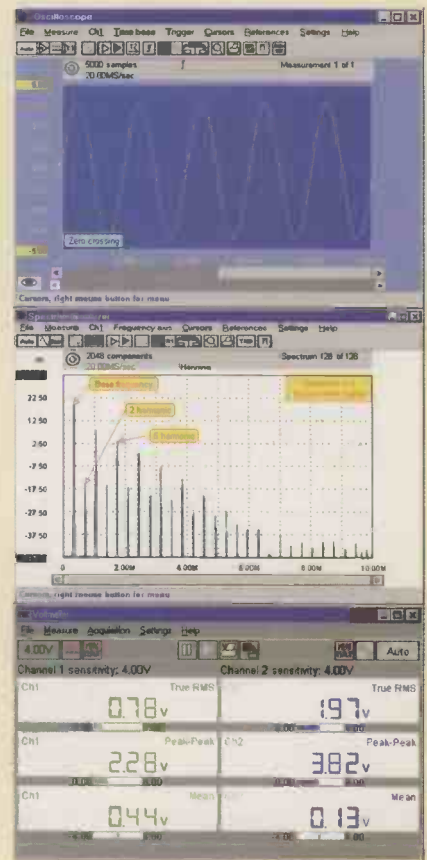

HANDYSCOPE HS3

WWW.TIEPIE.NL

for more information, demo software, software, source code and DLL's visit our internet page: <http://www.tiepie.nl>



TiePie engineering (NL)
Koperslagersstraat 37
8601 WL SNEEK
The Netherlands
Tel: +31 515 415 416
Fax: +31 515 418 819

TiePie engineering (UK)
28, Stephenson Road, St. Ives
Cambridgeshire, PE17 3WJ, UK
Tel: 01480-460028
Fax: 01480-460340

High performance 500W mains inverter

Do you think that commercially available power inverters are just not good enough? This design by Paul Bennett should bring many improvements over most commercial designs.

This project is similar to my design for a 400Hz inverter published in February 1999, but has a perhaps more useful output of 240V 50Hz. It is powered from 12V, and has been specifically designed to start and run a full size fridge.

Most refrigerators still use a traditional split phase induction motor, usually sealed inside the compressor casing. These motors have two windings, one for running and one for starting. Starting torque is provided by the starting winding having a different L/R ratio to the run winding and so generating the necessary phase shift. When the motor is up to speed the starting

winding is disconnected. This is accomplished by a current relay on the run winding or PTC thermister on the starting winding.

When the motor is at rest there is no back emf in the windings due to no rotor rotation. Current is therefore only limited by the winding inductance and resistance. The starting current is therefore very high and significantly lagging. Any inverter therefore has to support this reactive current long enough to get the motor started. Once running the current is much reduced but remains lagging. At rest all the true power ends up as heat in the winding. Once running this divides mainly into mechanical power output and some

remaining winding copper and iron loss. In-between there is a point of maximum power transfer, for a brief moment, as the motor accelerates through the point of maximum torque.

The starting and running conditions can be measured, to gauge what inverter rating is required. A low AC voltage can be applied to the motor, low enough so that the motor doesn't turn. The current can then be measured to give the stalled impedance. When running the inductance can be tuned out to give the lowest current using capacitors. Alternatively many DVMs these days can measure real and apparent power.

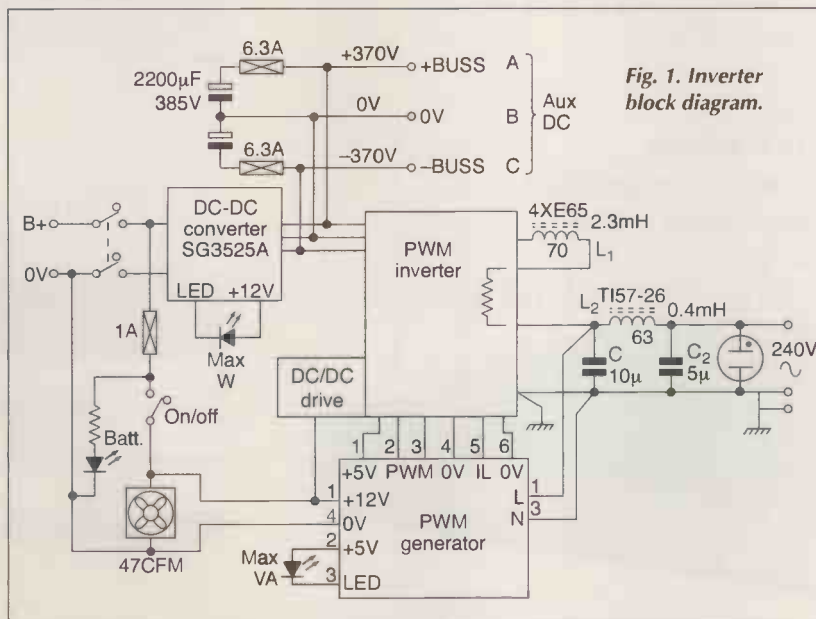


Fig. 1. Inverter block diagram.

Design choice

As we can see from the box on page 15, the typical 120W device requires 1500VA to start. With such a high VA to support during starting, a single stage design was ruled out. A simple 50Hz transformer square wave design would have to pass all the VA between the load and the battery/smoothing capacitors. This would lead to high copper losses unless very heavily engineered. Induction motors have reduced efficiency on square waves as harmonic currents produce torque at harmonic speeds which the rotor obviously cannot follow. PWM sine wave transformer designs are widely used in budget UPS addressing the harmonic problem but not the reactive current.

A two-stage design has been adopted with a DC-to-DC converter followed by a PWM half bridge.

tap current with a transformer and terminating the PWM pulse. The current limit effectively determines the true power (W) rating of the over all inverter. Fig. 2 shows the full circuit.

The author experimented with the possibility of a phase shift resonant design. These offer various advantages such as low loss switching, placing the inductor in the primary circuit and low diode stress. The main disadvantage is high circulating current in the primary leading to poor efficiency at low load. It also requires a full bridge with high side switches.

A half bridge is used for the output. This has to support the full VA, i.e. deliver 6A rms or so without any restriction. The current limit for this therefore determines the overall inverter VA rating. Current is sensed by a fast optocoupler placed in between the main filter inductor L1 and smoothing capacitor C1. In this position, rather than directly at the transistors, avoids the reverse recovery spike. The current at this point is continuous between PWM cycles so a transformer would have to have a frequency response down to 50Hz.

The DC - DC converter control loop needs to be chosen with care. The output load draw has a 50Hz ripple which alternates between the positive and negative buses. The loop is chosen quite slow to average this out, to avoid peak currents in the DC - DC converter which would otherwise reduce efficiency slightly. The slightly increased ripple on the busses is easily coped with by the PWM output control loop with negligible increase in distortion.

Component choice

Fuelled by automotive and portable IT needs, low voltage power MOSFETs have made great strides in recent years. The Infineon SPP80N06S2-05 used here provides $5m\Omega$ at 55V in a To220 package. And only cost a few pounds. The



Fig. 5. Completed unit external view.



Fig. 6. Completed unit internal view.

IRF1405 from International Rectifier offers a similar performance.

The output bridge uses two 1200V IGBTs, IR4GPH40U from IR. These are types for switch mode psu

applications, i.e. no specified short circuit withstand capability. Devices with this capability usually have inferior switching performance. The device's gain is designed to limit the short circuit current (i.e. come out

Typical measurement from a '120W' fridge freezer

Stalled $Z = 39\Omega$, so stalled current at 240V = 6.2A. Therefore equivalent to 1500VA.

Cold resistance 13.5Ω . Most loss is copper $I^2R = 520W$. Running current 0.93A.

Approx $8\mu F$ could tune this down to a minimum of 0.47A, 113W.

Inverter power and VA is therefore dominated by the starting conditions, requiring approx 1500VA, 500W.

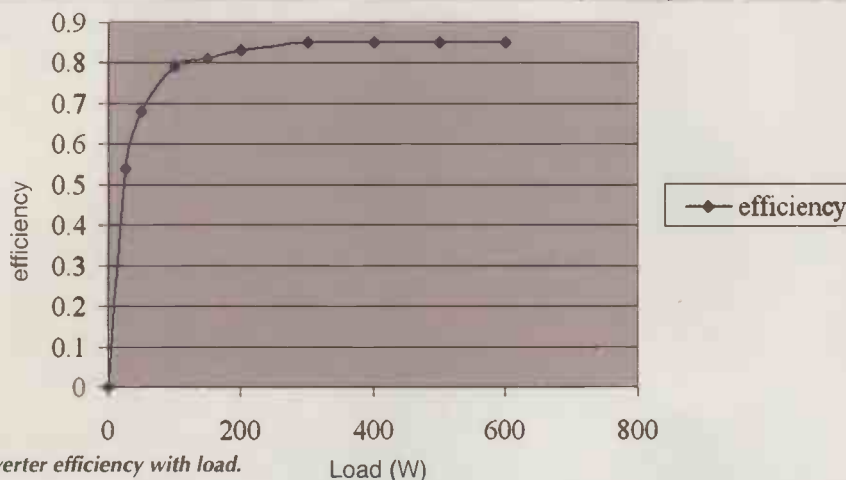


Fig. 7. Inverter efficiency with load.

of saturation), but still needs to be turned off within a few μs , to avoid the destruction by the very high instantaneous power dissipation. In this design current build up under short circuit conditions is limited by L1 to avoid desaturation, and long enough to turn the devices off.

Use of IGBTs allows the necessary fast recovery free wheeling diodes to be connected directly in parallel. Two 600V 8A STTi860 devices from ST are used. These incorporate two 300V die in series. Low voltage diodes have lower reverse recovery charge, and as they are in series, the same charge flows through both diodes. The penalty is higher forward voltage drop, although this also increases for single junction high voltage fast recovery diodes. The low charge reduces the IGBT turn on transient which reduces EMC problems and makes layout less critical.

Output filter

L1 is the main PWM filter choke. Its value needs to be high enough to reduce the 25.6KHz current ripple to an acceptable value. It should be low enough not to attenuate the 50Hz signal significantly and be an acceptable size and shape. It should not saturate under worst case current limit conditions. Four 3C85,

E65/32/27 cores were used with a 70 turn winding of 2mm enamelled copper wire. Rubber spacers gave an 'air gap' of approx 2mm for a value of 2.3mH.

C1 is the main output smoothing capacitor. Its value needs to be high enough to pass the remaining 25.6KHz ripple current to ground, minimising the resultant voltage ripple. It also supports some 50Hz inductive reactive current from the load. Any reactive current through C1 not taken by the load circulates through the half bridge, increasing losses, so C1 should not be too large. 10 μF is chosen here. Residual 25KHz ripple is approx 1V rms. This is further reduced by L2/C2. C2 also contributes to reactive current circulation. 0.4mH and 5 μF are used. Fig. 3.

PWM generation

The 50Hz reference signal is itself PWM coded in an EPROM. This is then clocked out and filtered to a high quality sine wave. All of a 512K EPROM clocked at 1.6384MHz stores one 50Hz cycle. Only one bit is used. The other bits could store other output frequencies providing they are an integer multiple of 50Hz. Non-multiples could be stored using an additional bit to reset the EPROM address divider. A reset bit after a count of 436906 approximates to 60.000092Hz. Additional bits could also provide additional phases. The shape of the stored waveform could be changed to more accurately mimic the typically flattop distorted mains. Fig. 4.

An error amplifier compares the

reference to a sample of the output waveform to generate the required PWM demand. A twin ramp and comparator arrangement is employed for the PWM generator. This fixes one of the PWM edges in time with respect to the master clock. This gives a defined dead time at the end of each PWM cycle to reset the current limit latch. Logic and monostables ensure there is always dead time between conduction of the bridge transistors. A current limit latch turns off both transistors in response to a current limit signal. This is reset during the dead time at the end of each PWM cycle.

Under current limit conditions significant distortion occurs as the threshold is a fixed value and doesn't follow a sine reference. Current limiting is therefore more likely at the peak of the 50Hz cycle. Under partial overload the waveform becomes flat topped. To reduce this distortion the pwm reference sine wave is reduced in response to repeated current limit by a multiplier gain stage.

Packaging

The prototype was built into a simple two-part aluminium case as shown in figures 5 & 6. A 12V 50cfm fan provides cooling. Indicators show battery connected, output on, max W and max VA. The battery indicator uses a high performance green LED. This draws just 1mA – comparable or less to the self discharge of a battery large enough to match the inverter's full output. Unfortunately these LEDs appear only available in clear packages with narrow viewing angle. An old diffused green LED was cut up and glued to the new one, the join being hidden by the chrome bezel.

Performance

The overall true power was checked using lamps. The output half bridge was also checked with lamps and a 1KW fan heater. A variac and transformer providing extra power. The graph shows the overall efficiency as a function of load. The acid test is the fridge, which started and ran fine. The thermostat cycle being a surprisingly long 1- hours. Inverter input started off at 143W but this fell to 133W just before the thermostat time out. ■

SAFETY WARNING

This project contains high DC voltages of relatively high energy. Exercise extreme care if recreating this project.



®

UK's NO.1 IEC CONNECTION

OLSON DISTRIBUTION PANELS WITH IEC 320 SOCKETS INDIVIDUALLY FUSED AND NEON INDICATORS

OLSON PANELS with 10AMP CEE22/IEC SHUTTERED SOCKETS FUSED, DOUBLE FUSED WITH MAINS FILTER AND RCD PROTECTION

OLSON DISTRIBUTION PANELS WITH IEC 320 SOCKETS INDIVIDUALLY FUSED

OLSON DISTRIBUTION PANELS FOR 19" RACK MOUNTING WITH R. F. FILTER AND TRANSIENT SUPPRESSOR

OLSON 'The Rack Range' CEE22/I.E.C. SOCKETS

OLSON POWER DISTRIBUTION UNITS with IEC 320 Sockets

OLSON SEQUENTIAL START POWER DISTRIBUTION PANELS FOR 19" RACK-MOUNT SYSTEMS

OLSON ELECTRONICS LIMITED

OLSON 'THE RACK RANGE' MAINS DISTRIBUTION PANELS FOR 19" RACK MOUNTING HORIZONTAL

OLSON ELECTRONICS LIMITED

OLSON 19" RACK MOUNTING DISTRIBUTION PANELS WITH IEC 320 SOCKETS AND REAR CABLE MANAGEMENT

OLSON ELECTRONICS LIMITED

CALL OUR SALES HOTLINE

020 8905 7273



24 HOUR DELIVERY SERVICE



OLSON ELECTRONICS LIMITED
 OLSON HOUSE, 490 HONEYPOT LANE, STANMORE, MIDDX HA7 1JX
 TEL: 020 8905 7273 FAX: 020 8952 1232
 e-mail: sales@olson.co.uk web site: http://www.olson.co.uk

ELECTRONICS WORLD



The world's leading electronics magazine, **Electronics World** is a technology- transfer magazine for the global electronics industry. It covers research, technology, applications, products and patents in areas such as audio, R.F., components, CAD design, circuit building, PC & Micro based products, tests & measurement, semiconductors, power sources and much, much more.....

A trustworthy source of reference each month for keeping ahead with the latest news and technical developments in the electronics industry.

As the longest established magazine in the industry - 80 years experience serving the electronics market, **Electronics World** is the leading technical journal for electronics professionals and high-level enthusiasts.



Make sure you receive your regular monthly copy by subscribing today.....

Complete and fax the coupon to: +44 (0) 1353 654400

I wish to subscribe for one year to **Electronics World** (12 Issues) 1 year

UK £38.95 O/S £64.50
 US\$100.62 Euro 102.55

Please tick preferred method of payment

- I enclose a cheque payable to Highbury Business Communications Ltd
 Please invoice me Purchase No
 (NB Purchase order must be included to validate invoice)
 Please charge my: Master Card/Visa/Amex/Diners
 Club/Switch/Delta (please circle)

Card No _____
 Expiry Date _____

(Switch/Delta Only) Valid from / Issue Number

Signature _____

Date _____

Name _____

Job Title _____

Company _____

Address _____

Postcode/Zip _____

Country _____

Telephone/ Fax _____

E-mail _____

Please tick here if you do not wish to be contacted by other businesses either by
 Mail Telephone Fax E-mail

Please return to: **Highbury Subscription Services, Link House,
 8 Bartholomew's Walk, Ely, Cambridgeshire CB7 4ZD, UK.
 Email: wss@wyvemcrest.co.uk (Quote Ref: EW1)**



HIGHBURY
 Business Communications
A SUBSIDIARY OF Highbury News Communications PLC

Flat, wideband buffers

Many textbooks cover the emitter-follower or common-collector transistor configuration as a buffer, but they usually don't mention a word about stability. In this article we will show that a buffer circuit can produce gain, and even oscillate under certain source and load conditions. We also look for ways of achieving a flat gain-frequency response. Dewald de Lange elucidates.

The idealised emitter-follower circuit of Fig. 1, driven by a source with zero impedance, and not reactively loaded, gives the theoretical transfer function in Fig. 2. It shows a flat response beyond 1GHz.

In practice, the source may have some resistance R_G , and stray inductance L_S due to a lead or PCB track; and the load, some capacitance C_L , due to subsequent circuitry – most circuits are capacitive over their normal operating frequency range. When these are added, as in Fig. 3, the simple buffer can deliver some unexpected surprises, such as gain or instability at higher frequencies, as a graph of the transfer function shows in Fig. 4.

The gain is caused by the transistor's internal base-emitter capacitance C_{be} , and the base transit time – a parameter used in more advanced transistor models, such as the Spice model used in many CAD (Computer Aided Design) software. Both cause a delay from the input to the output.

To understand what causes the gain peak, consider what happens when a step voltage is applied to the input in Fig. 5. Internal capacitance C_{be} must first be charged up for v_{be} to increase, and for i_e to increase. The difference between i_e and i_b charges up C_L . When v_{out} reaches the +0.1V target voltage, C_{be} is still charged higher, making v_{be} and i_e larger, and causing v_{out} to overshoot. It takes a finite time for C_{be} to discharge to the point where i_e equals i_b again, and v_{out} settles down to its final value.

By re-arranging the components as in Fig. 6, it will be recognised as a Colpitts oscillator. Therefore, given the right source and load impedances, a buffer will oscillate. It is useful to remember this undesirable circuit arrangement when implementing a buffer.

Flattening the response

The purpose of a buffer is to provide a replica of its input signal. Therefore we need to find ways of flattening the

gain. This can be achieved by slowing down the rate at which C_{be} is charged, i.e. limiting the bandwidth of the buffer.

For distortionless buffering of non-

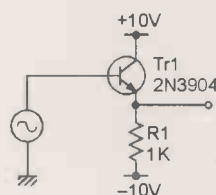


Fig. 1. Simple emitter follower.

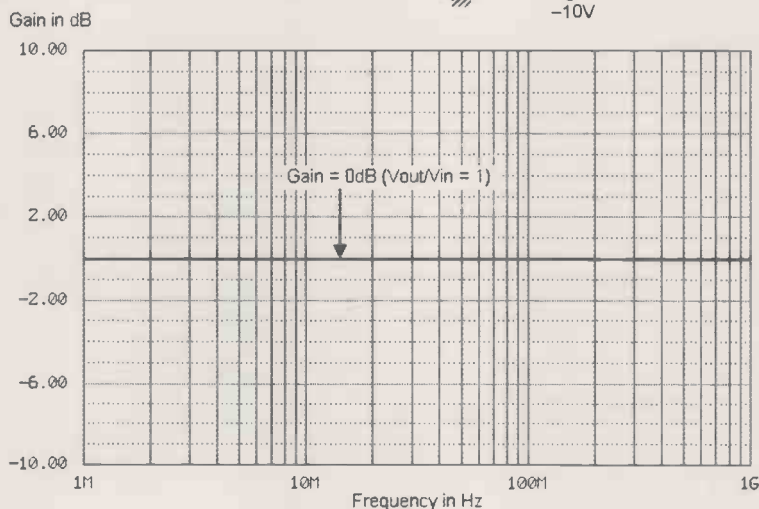


Fig. 2. Response of a simple emitter follower.

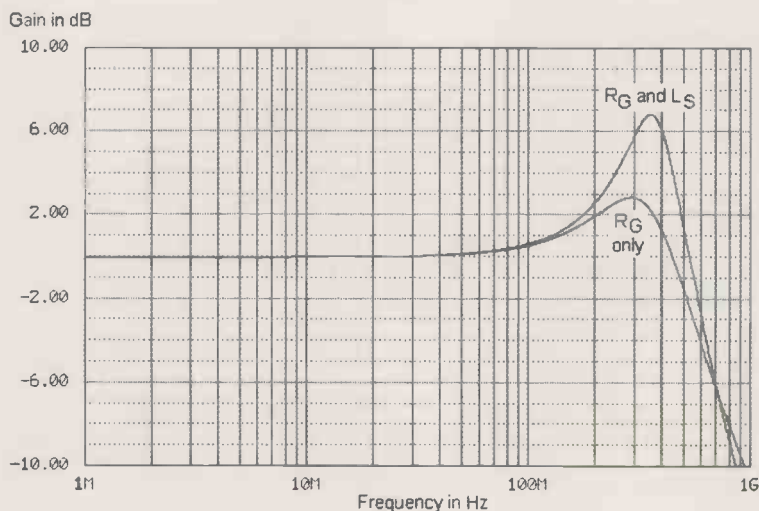


Fig. 4. Buffer response with a practical source and load.

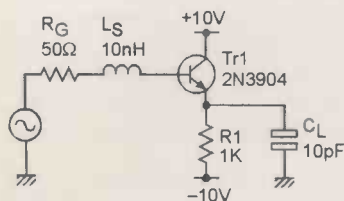


Fig. 3. Buffer with a practical source and load.

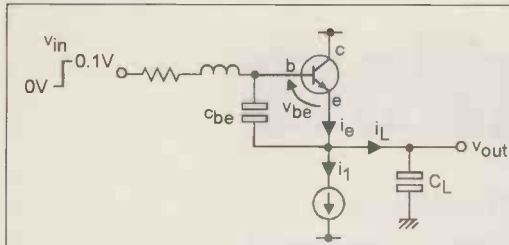


Fig. 5. Effect of internal base-emitter capacitance.

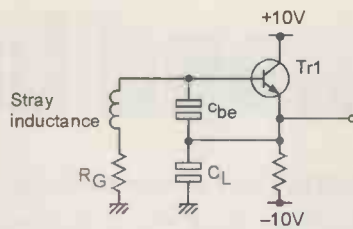


Fig. 6. A buffer can turn into an oscillator.

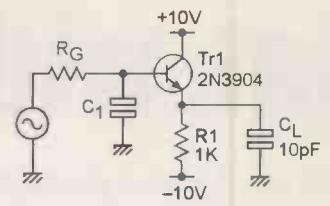


Fig. 7. Bandwidth limiting with RC filter.

Fig. 8. Response of circuit in Figure 7.

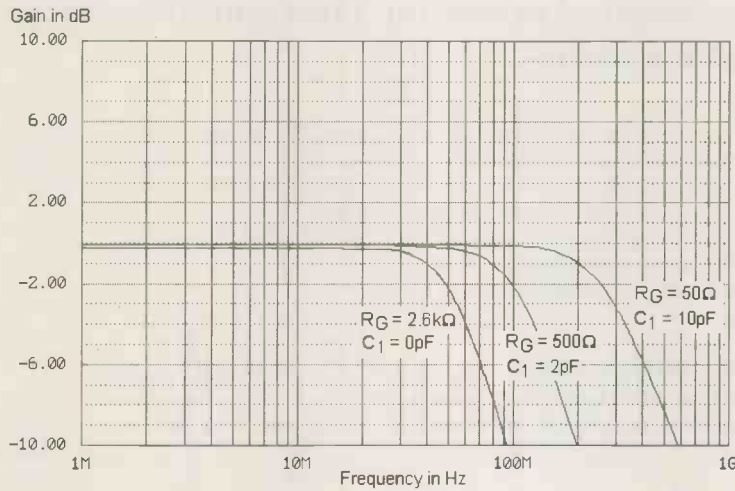


Fig. 9. Circuit in figure 7, with $R_G = 500\Omega$ and $C_1 = 2pF$.


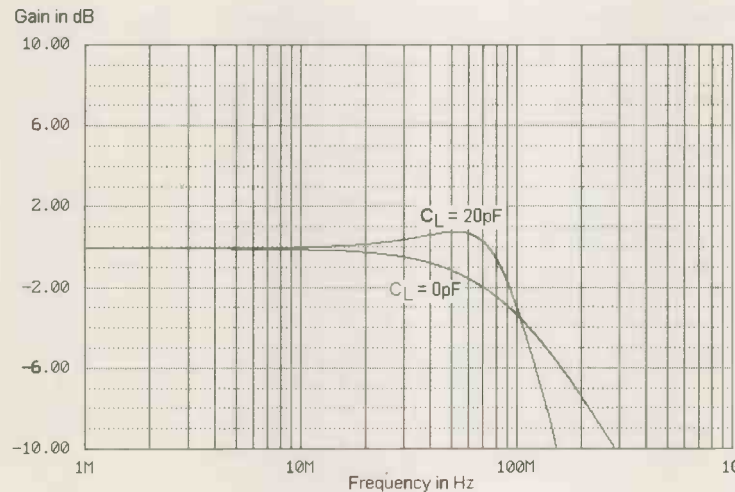


Fig. 10. Response of circuit in Figure 7, with transistor BFG67

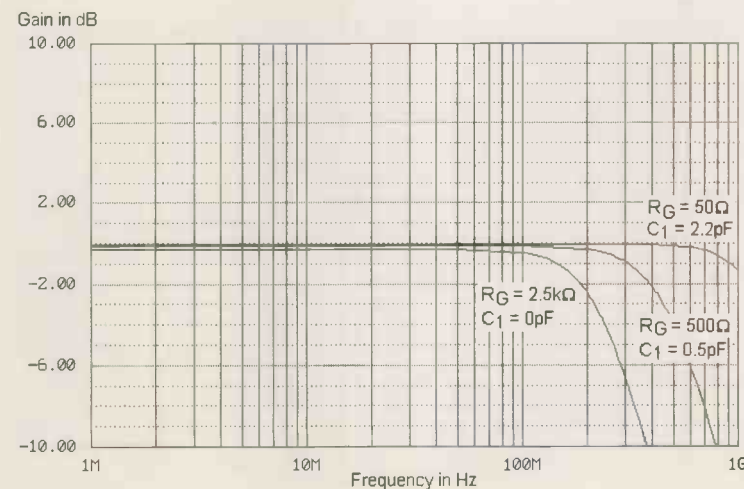

sinusoidal waveforms, all frequencies should also be delayed the same – the buffer should have a flat group delay (the change in phase relative to the change in frequency). In this application, it is a small factor compared to the gain.

RC filter

One way of flattening the gain is with a resistor-capacitor low-pass filter on the input, as in Fig. 7. Figure 8 shows the bandwidth for different combinations of R_G and C_1 . These graphs are for a capacitive load C_L of 10pF. Stray inductance is left out for simplicity.

The larger the source resistance R_G , the less the capacitive load C_1 presented to the source, but the lower the bandwidth. A filter capacitor C_1 of 10pF would equal the load capacitance C_L , and may make the buffer redundant, except for partially isolating the source from variations in the load.

A multi-order LC (inductor-capacitor) filter may in principle give a higher cut-off frequency, but achieving a flat gain is more difficult.

Figure 9 shows the effect of a change in load capacitance, away from the nominal 10pF. This is for $R_G = 500\Omega$ and $C_1 = 2pF$ in Fig 7.

The 2N3904 has a current gain bandwidth product f_T of 300MHz, which would limit its performance above 100MHz. What bandwidth could we achieve if we used a microwave transistor such as the BFG67, with a transition frequency f_T of about 8GHz? Fig. 10 shows the gain for different combinations of R_G and C_1 .

RRC filter

The bandwidth can be extended further with a series R_1 and C_1 as in Fig. 12. Component values are more critical, and a trimmer capacitor will be required for a really flat response.

Smaller load resistance

If the load has a smaller resistance, the response will also be flatter, as shown in Fig. 16. A drawback to the

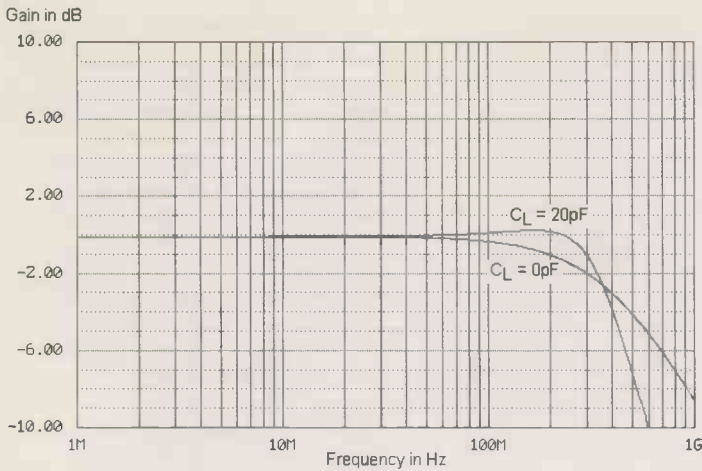


Fig. 11. Effect of load capacitance on microwave transistor.

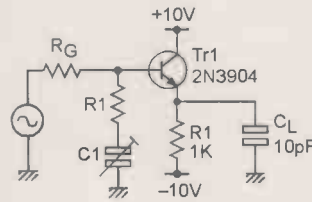


Fig. 12. Bandwidth limiting with RC filter.

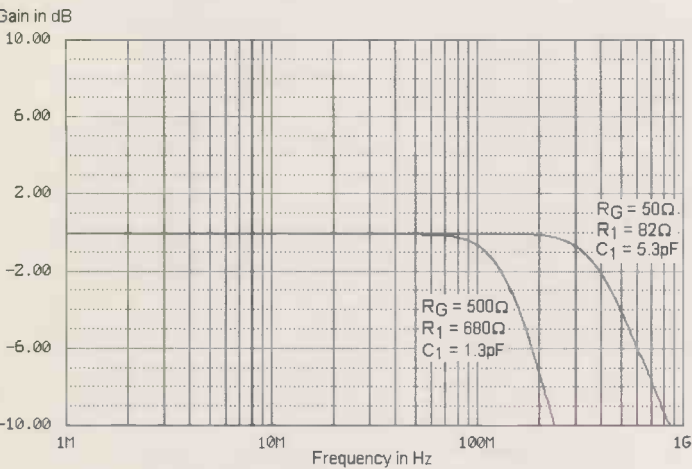


Fig. 13. Response of circuit in Figure 12

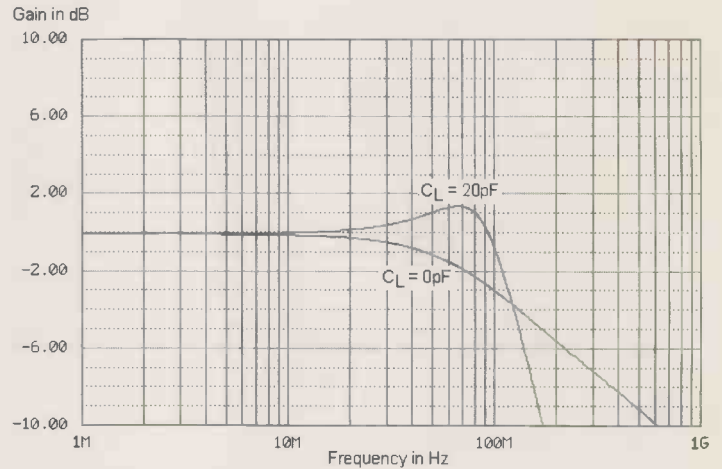


Fig. 14. Effect of change in load capacitance.

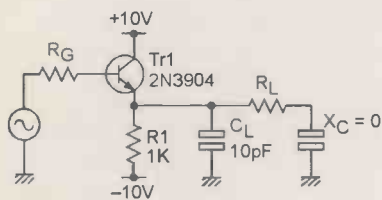


Fig. 15. Adding a load resistor.

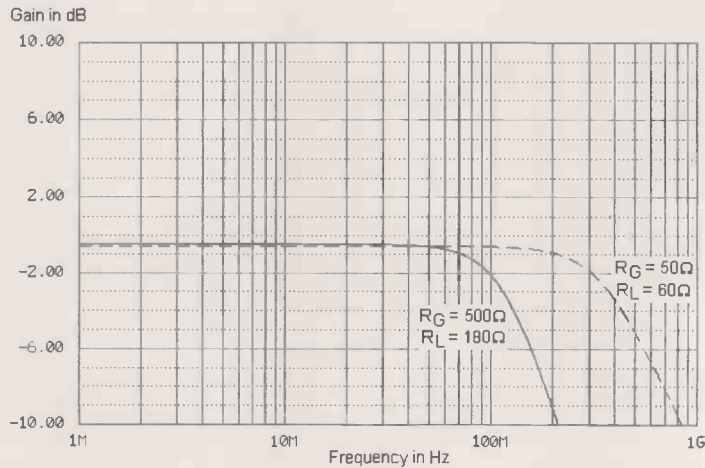


Fig. 16. Response with load resistor.

smaller load resistance is a reduced input resistance.

Other buffer circuits

The complementary compound emitter follower, or feedback pair, of Fig. 18 reduces the distortion of the single transistor buffer, by keeping v_{be1} , which determines the voltage drop from input to output, constant.

The current i_1 through resistor R2 remains fairly constant, as the voltage across it is set by v_{be2} . If i_1 is chosen at 5 to 10 times the varying base current i_{b2} , it provides a fairly constant current through Tr1 and a constant V_{be1} , when the input voltage and output load current changes.

Since the base current of Tr1 also remains constant, the input resistance is increased.

Due to the extra delay through the second transistor, it will be more prone to instability with a capacitive load, as the response in Fig. 20 of the circuit in Fig. 19 shows.

To flatten the gain of this circuit is difficult, even without any load. Fig. 21 shows one solution for a 10pF load. Gain flatness above 10MHz is dependent on component tolerances.

Large signals

If a buffer is to handle large signals, a current source in the place of an emitter resistor offers several advantages. Fig. 24 compares the current flows for an output signal that varies from -5V to +5V over a load resistance of 1k, within a $\pm 10V$ supply. Both circuits draw 20mA at $V_{out} = 0V$.

In the case of an emitter resistor, the transistor current i_c varies from 5 to 35mA, whilst with a current source, it

Fig. 17. Effect of change in load capacitance, for circuit in Figure 15 with $R_G = 500\Omega$ and $R_L = 180\Omega$.

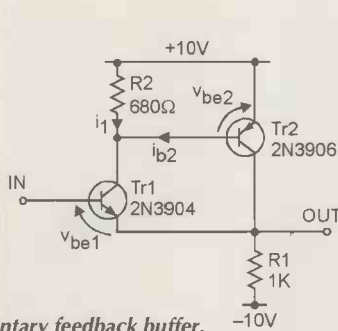
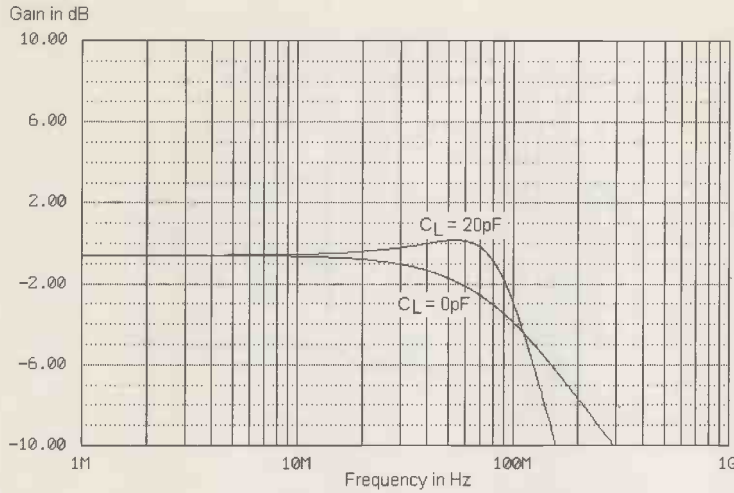


Fig. 18. Complementary feedback buffer.

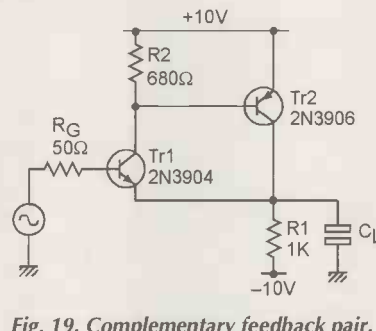


Fig. 19. Complementary feedback pair.

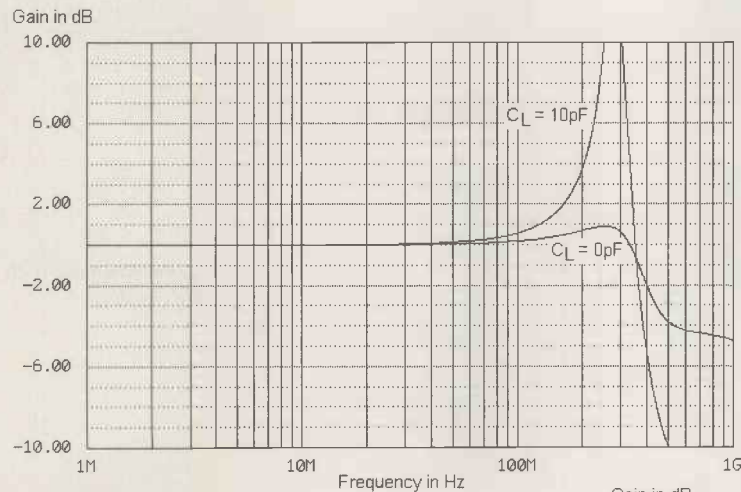


Fig. 20. Response of circuit in Figure 19.

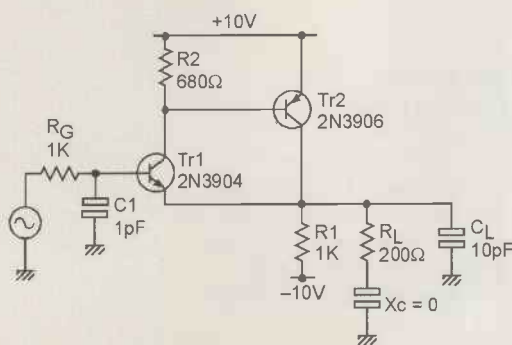


Fig. 21. Complementary feedback pair with flattened gain.

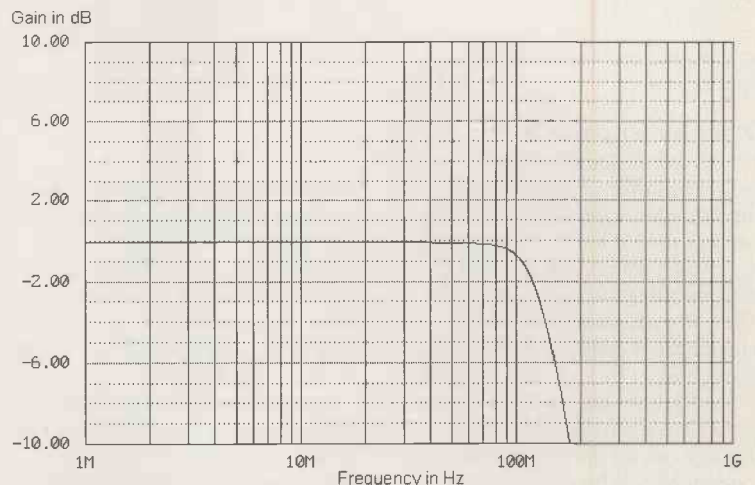


Fig. 22. Response of circuit in Figure 21.

varies from 15 to 25mA. A smaller change in i_e means less change in v_{be} , which reduces the distortion from input to output. Knowing the change in i_e , one can get an idea of the distortion at lower frequencies from a datasheet graph of the base-emitter voltage V_{BE} against collector current I_C .

A current source also allows the buffer to operate close to the supply rails. An emitter resistor limits the negative peak, e.g. in the example given, it is limited to $-6.7V$.

Current for capacitive load

The maximum current required to drive a capacitive load at a given frequency, can be determined as follows:

From the definition of a capacitor:

$$\text{Capacitance } C = \frac{\text{Electrical charge } Q}{\text{Voltage } V} = \frac{\text{Current } I \times \text{Time } t}{\text{Voltage } V}$$

from which follows the slew rate for a given current and capacitance as:

$$\frac{\Delta V}{\Delta t} = \frac{I}{C}$$

The maximum slew rate for a sinusoidal wave occurs at the zero crossing and is:

Combining the two equations: Current required $I = V_p \omega C$

Class B buffer

A class-B buffer is better than an emitter-follower with a current source, in that it can provide high source and sink currents when required, whilst drawing a low quiescent current. This makes it particularly suitable for driving a capacitive load at high frequencies. It also has the advantage of symmetrical distortion (positive and negative halves are attenuated the same), and the same DC level from input to output.

Figure 25 shows one example of such a circuit. The (small signal) frequency response is shown in Fig. 26.

Two current sources keep the voltage drop over the diodes constant, and the distortion down. For less critical applications, the current sources can be replaced with resistors, e.g. 4k7 values for large signals, but that would lower the

input resistance to half the resistor value, e.g. 2.3kΩ.

Schottky rectifier diodes D2 and D3 are used for a low voltage drop of about 0.2V. R7 and R8 determine the quiescent current through the transistors, and makes the output resistance of the buffer half of their value, namely 7.5Ω.

To reduce distortion, the class B stage is often combined with a

differential amplifier, as in Fig. 28.

The delay through four transistors does however severely limit the bandwidth, when stabilising components are added. Tr1 and Tr2 form a differential amplifier, D1 and Tr3 mirror the current from Tr1, which drives class B stage Tr4 and Tr5. The output is fed back to the base of Tr2. For gain, it is fed back via a resistive divider. ■

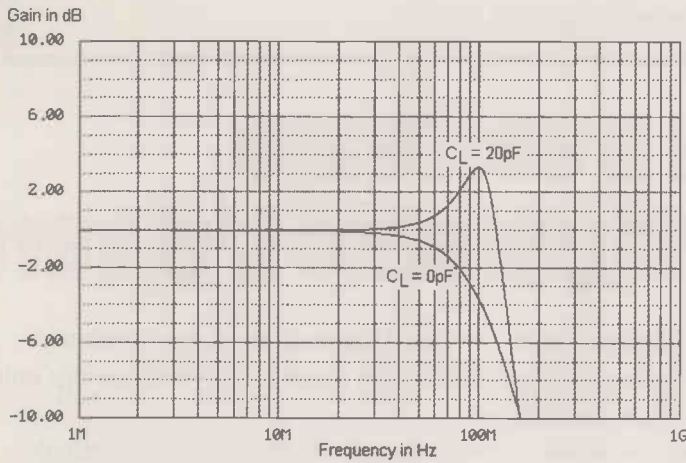


Fig. 23. Change in load capacitance.

Fig. 25 Class-B buffer.

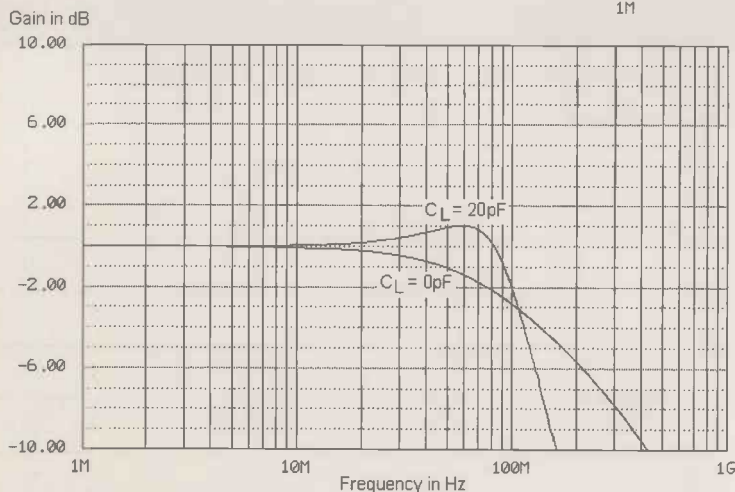
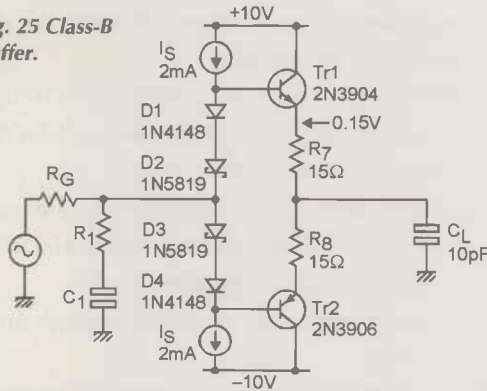


Fig. 27. Effect of load capacitance, with $R_G = 500\Omega$, $R_1 = 1k5$ and $C_1 = 0.73pF$.

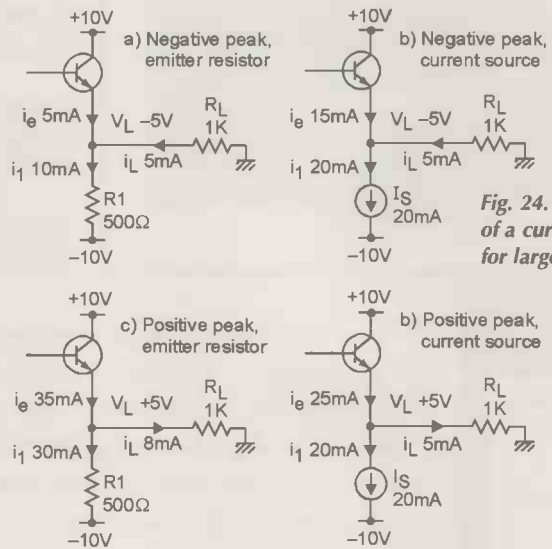


Fig. 24. Advantage of a current source for large signals.

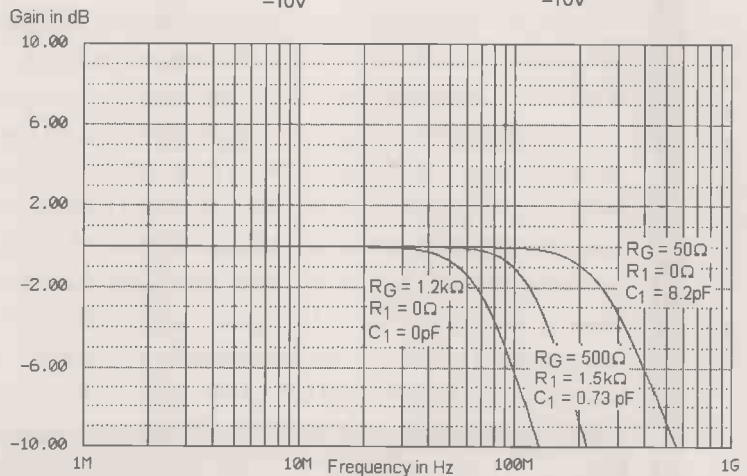


Fig. 26. Class-B buffer response.


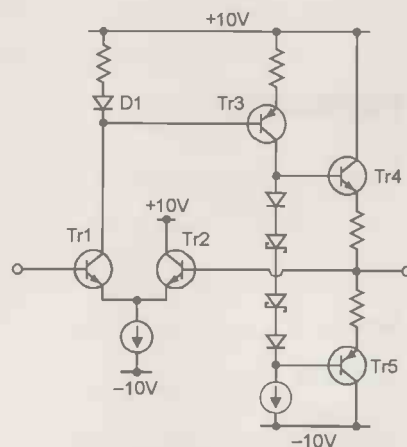


Fig. 28. Class B stage with feedback.

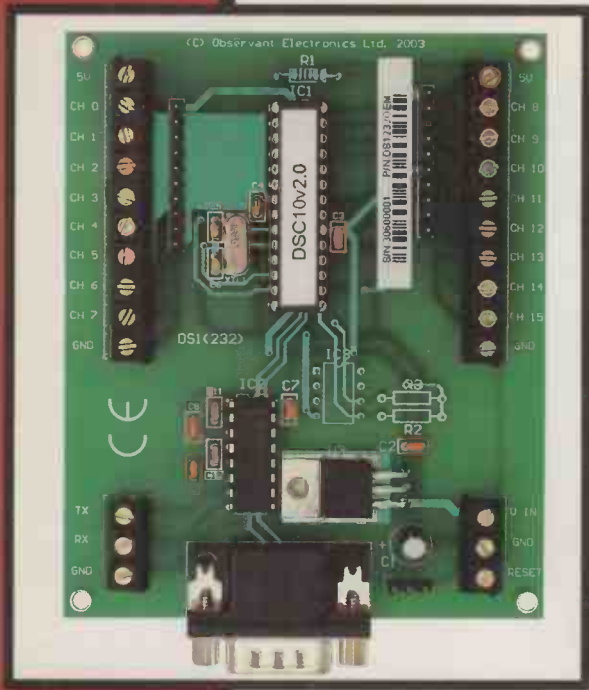

Want to win it? Simply answer the questions in the box below and send it together with your name and address and your entry will go into the hat. Post your answer to Electronics World, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU Please read the competition rules first though.

This competition is sponsored by **Observant Electronics**
www.ObservantWorld.com

Win a software configurable I/O card

Competition rules

No purchase is necessary. Strictly one entry per household. Competition closing date 20th November 2003. No entries will be accepted after that date. The draw will take place within the next working week following the 20th November. and the winner will be announced as soon as possible thereafter. The prize is not negotiable. No correspondence will be entered into regarding this competition. No employee of Highbury Business Communications or Observant Electronics may enter the competition.

By combining software-configurable channels with a compact instruction set, the Observant Electronics DataStation family of software-configurable, mixed signal I/O products brings unique flexibility to control and data acquisition applications.

The new product overcomes the two main problems of traditional serial I/O solutions: i) limited choice of channel configurations and ii) low sample rates.

Delivering a 12 bit sample rate of greater than 500 samples a second – a 50 times improvement over many other solutions – DataStation is suitable for applications as diverse as machine control, industrial automation, environmental monitoring and robotics. Making it possible for designers to meet the needs of virtually any application with just one software compatible family of products.

DataStation's 16 software-configurable channels can be configured to give any combination of up to 6 analogue inputs (with selectable 8 or 12 bit resolution), 2 PWM outputs, 16 digital inputs and 16 digital outputs; giving a total of 391 different I/O configurations from a single product.

The DataStation family is available as an OEM product and in an IP65 rated enclosure and will soon be extended to include an IP40 rated enclosure plus RS-485 and CAN-bus interfaces in addition to the current RS-232 interface. The winner will receive an Observant Electronics DataStation plus development board and cable (normally worth £119 + VAT). For those readers unlucky enough not to win there will be a special offer running from the November issue.

THE QUESTION

- 1: How many different I/O configurations are possible with the DataStation?
- 2: If you win the product, what use will you put it to?

THE ANSWER is

1: _____ 2: _____

Name _____

Address _____

Entries only accepted on an original or photo copy of this form

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

Digitally programmed capacitor

Designed to replace variable capacitors, Xicor has introduced the X90100 digitally programmable capacitor, which can be used to tune the frequency response of electronic systems up to 400MHz. The device can be set to 1 of 32 discrete capacitor steps ranging from 7.5pF to 14.5pF in 0.20pF increments. Once the desired capacitor value is selected via an up/down interface it is stored in the on-chip EEPROM.

Xicor

www.xicor.com

Tel: +44(0) 1993 700544

High power transistor cuts saturation voltage

Rohm's latest family of small transistors are available in high-power surface mount packages and feature reductions in saturation voltage $V_{CE(sat)}$ of up to 90 per cent when compared with previous technologies, according to the supplier. The low $V_{CE(sat)}$ transistors are designed to offer low energy consumption characteristics in switching and interface circuits without sacrificing current handling capabilities. Package options include 3-pin TSMT3 devices with power ratings of 0.5W, and 6-pin TSMT6 devices rated at up to 1.25W. These packages both have dimensions of 2.9 x 1.6 x 1.0mm. Available in both NPN and PNP versions, the surface mount parts are suitable for power management, load switch applications, and DC-DC conversion in portable

applications such as mobile phones, PDAs and camcorders. Collector currents for the transistors range from 1A to 6A, while voltage ratings are either 12V or 30V depending on device chosen. In addition, the company can supply further devices in three smaller packages of SC-70 SC-75A and VMT3 measuring just 1.2 x 0.8mm. Here the I_C capability ranges from 0.5A to 1.5A.

Rohm

www.rohm.com

Tel: +44(0) 1908 282666

Hall-effect sensor with snug-fitting back-biasing magnet

Allegro MicroSystems has developed a packaged Hall-effect sensor IC with a back-biasing magnet designed to achieve high air-gap performance. The SG package allows the magnet to sit closer to the IC than it does in conventional packaging, allowing it to work with a higher air gap and smaller magnet. The resultant package fits into the tight spacing

dictated by automotive applications such as ABS systems, said the company. The package is manufactured with a single-step moulding operation, which according to the supplier eliminates the possibility of voids caused by air entrapment during the potting process and results in improved heat dissipation. The lead configuration is suitable for PCB surface mounting and attachment of a bypass capacitor. The spacing provided between the two leads allows an axial-leaded capacitor to be welded across them. Attachment to the sensor can also be made with a lead frame to preclude the use of a costly PCB.

Allegro

www.allegromicro.com

Tel: +44(0) 33 450 512 359

Aluminium instrument housings in all shapes and sizes


Hammond Electronics has added an additional three sizes to its recently introduced 1455 family of extruded aluminium instrument cases, designed to



house PCBs mounted horizontally into internal slots in the body of the case or as an enclosure for any small electronic or pneumatic instrument. The recently introduced sizes are the 1455J160 at 160 x 78 x 27mm, the 1455L160 at 160 x 103 x 30.5mm. The two larger sizes accept a standard or extended depth Eurocard. The body of the enclosure is in either clear or black anodised finish. Hammond Electronics www.hammondmfg.com Tel: +44(0) 1256 812812

Ethernet connector

Harting has introduced a range of connectors for industrial Ethernet systems. The range of Ethernet products being offered covers all the relevant international standards being developed on both sides of the Atlantic by organisations such as Profibus Nutzer Organisation, Open DeviceNet Vendor Association, International Electrotechnical Commission and Industrial Automation Open Networking Alliance. For industrial Ethernet applications, the range includes the RJ industrial family which offers data-only types in IP67 and IP20 variants and a hybrid (data and power) version to IP67. Also available are Ethernet

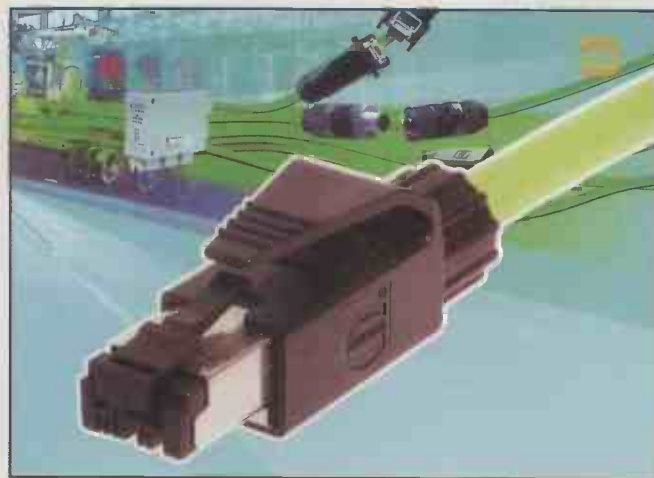

compatible shielded M12 connectors to IP67 and rectangular HanBrid 3A-RJ45 connectors to IP65. RJ Industrial connectors are the only RJ45 based connectors

that can accept 22 AWG gauge conductors, claimed the firm.

Harting

www.harting.co.uk

Tel: +44(0) 1604 766686



Please quote *Electronics World* when seeking further information

Power supplies for all weathers

Designed for environmentally demanding applications such as mobile radio base stations and roadside electronic cabinets, the BBC series of 200 to 400W AC-DC switching power supplies from XP is a range of rugged units that need no derating over a -20 to +70°C ambient temperature range. The power supplies use a 6mm thick aluminium baseplate to provide effective conduction cooling. All heat dissipating components are attached to the baseplate which in turn is attached to the equipment enclosure. The single output units comply with

international EMC and ETSI standards and the active power sharing feature allows simple parallel operation where higher output currents are needed. A version capable of operating at down to -40°C is also available and the power supplies can be conformally coated for use in environments with high humidity. The BCC family consists of 12 standard power supplies with universal AC inputs and outputs from 3.3V DC (50A) to 28V DC (14.5A). Output load regulation is 1.5 per cent for output voltages up to 7.5V DC and 1 per cent above this.

XP
www.xppic.com
Tel: +44(0) 118 984 5515

PCI/LPC embedded modules

Diamond Point is offering the X-board from Kontron, which is a family of high density PCI and LPC-compatible embedded PC modules. According to the supplier, it is intended to close the gap between the previous DIMM-PC and ETX embedded PC modules. The sub-miniature credit card size (68 x 49 x 8mm) modules integrate a host of interfaces including USB, LAN, and serial in addition to sound, LCD and CRT. The omission of

legacy interfaces such as PS/2, floppy and parallel enables the use of ARM and or other Risc processor architectures as well as X86. Powered by a single 3.3V supply, the first X-Board CPU has been developed based on a 266MHz National Geode processor. It comes complete with integrated LCD digital, CRT analogue and TV-composite graphics interfaces, three USB ports, 10/100Mbit Ethernet, AC97 digital audio and PCI/LPC bus expansion.

Diamond Point
Tel: +44(0) 1634 722390

Low ESR cylindrical SMT electrolytics

A series of cylindrical surface mount electrolytic capacitors from NIC Eurotech are designed to provide low ESR (equivalent series resistance) performance and long load life ratings. Capacitance values are between 3.3µF and 6,800µF with voltage ratings of 6.3V to 100V DC. ESR values at 20°C and 100kHz are down to 0.0033Ω. The load life rating at 105°C for 105°C for 4x10mm diameter parts is 2,000 hours, whilst for 12.5 x 18mm parts this increases to 5,000 hours. With an operating temperature range of -55 to +105°C, the capacitors called Nack can be used in electronic



equipment designed for use in harsh environments. All parts are designed for automatic mounting and reflow soldering. NIC Eurotech
www.niccomp.com
Tel: +44(0) 1634 722390

High frequency PLLs for WLANs

National Semiconductor is offering its first family of high frequency phase lock loop (PLL) devices. Aimed at applications operating at over 3GHz as well as wireless LANs and 5.8GHz cordless phones, the first products are the LMX2430, LMX2433 and LMX2434 PLLs. The devices feature a normalised phase noise contribution of -219.0dBc/Hz, which will increase radio sensitivity, extend base station range and improve voice quality, said the supplier. The LMX2434PLL has an operation frequency of 5.0GHz RF with 2.5GHz IF, which can eliminate



AC-DC supplies support world standards

Lambda has introduced a series of AC-DC power supplies that accept a continuous universal input from 85 to 265V AC (47-63Hz) and as such will support world standards. The supplies use soft-start circuitry, have an integral class B EMI filter and provide over voltage and over current protection. Other features include an output adjustment potentiometer (±10 per cent), integral power good LED indicator and screw terminals for input and output connections. Four models are available with nominal output power ratings of 50, 75, 100 and 150W. Each model can be supplied with a choice of 5, 12


or 24V output. The company will extend the SWS series soon to offer more output voltage selections between 3V and 48V. CE marked in accordance with the Low Voltage Directive, the new SWS series carries UL, CSA EN60950 and EN50178 safety approvals. All models conform to EN61000-3-2, the SWS100 and SWS150 being fitted with an integral active PFC filter. Other approvals include EN55011-B, FCC-B and EN-61000-4. Operating temperature range is -10 to +60°C

Lambda
www.lambda-gb.com
Tel: +44(0) 1271 856666



PROTEUS

The Complete Electronics Design System

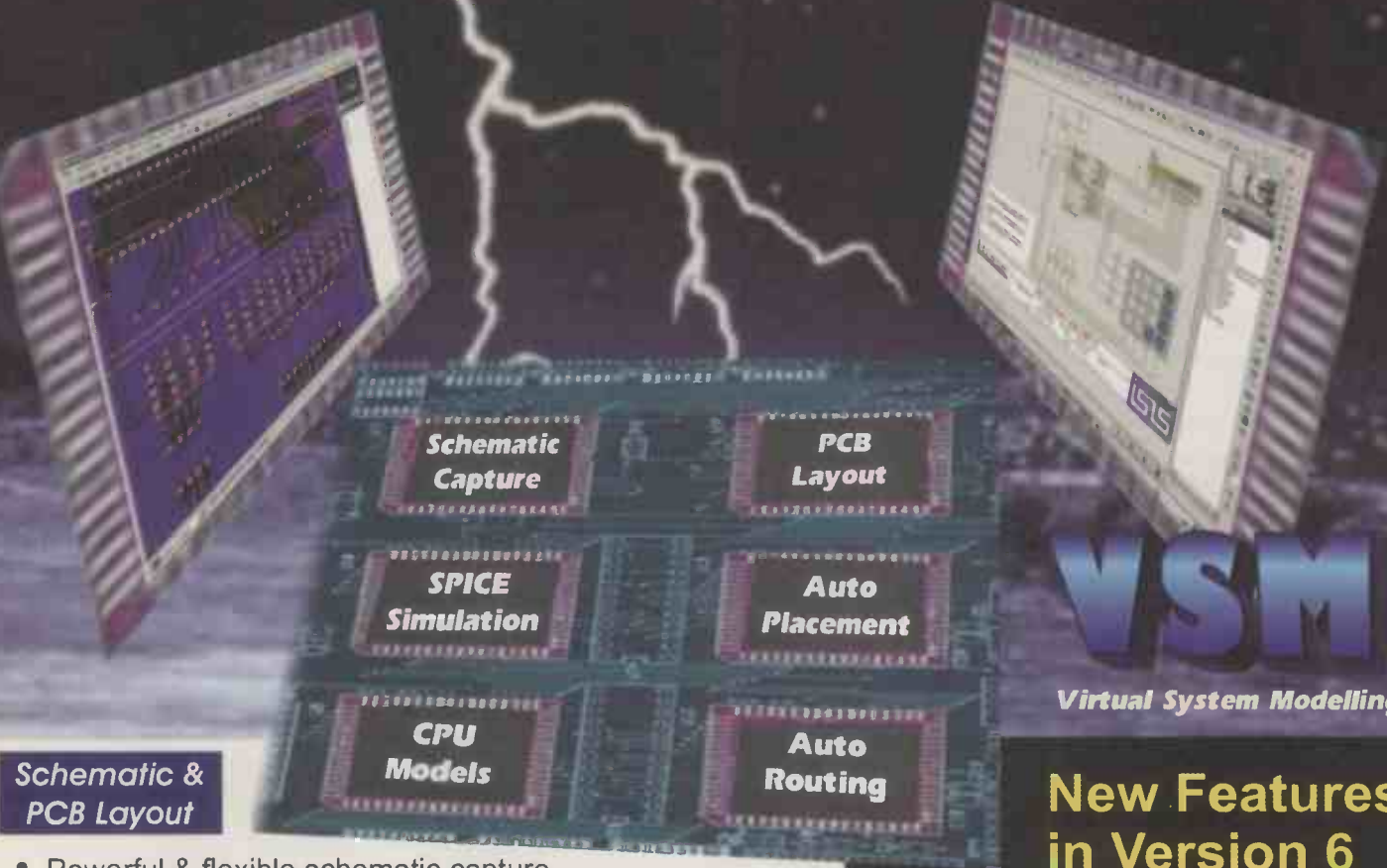

Schematic & PCB Layout

- Powerful & flexible schematic capture.
- Auto-component placement and rip-up/retry PCB routing.
- Polygonal gridless ground planes.
- Libraries of over 8000 schematic and 1000 PCB parts.
- Bill of materials, DRC reports and much more.

Mixed Mode SPICE Circuit Simulation

- Berkeley SPICE3F5 simulator with custom extensions for true mixed mode and interactive simulation.
- 6 virtual instruments and 14 graph based analysis types.
- 6000 models including TTL, CMOS and PLD digital parts.
- Fully compatible with manufacturers' SPICE models.

Proteus VSM - Co-simulation and debugging for popular Micro-controllers

- Supports PIC, AVR, 8051, HC11 and ARM micro-controllers.
- Co-simulate target firmware with your hardware design.
- Includes interactive peripheral models for LED and LCD displays, switches, keypads, virtual terminal and much, much more.
- Provides source level debugging for popular compilers and assemblers from Crownhill, IAR, Keil, and others.

New Features in Version 6

- Drag and drop toolbars.
- Visual PCB packaging tool.
- Improved route editing.
- Point and click DRC report.
- Multiple design rules (per net).
- Multiple undo/redo.

Call Now for Upgrade Pricing

**Works with
PIC Basic Plus
from Crownhill
Associates**

labcenter

Electronics

53-55 Main Street, Grassington. BD23 5AA

Tel: 01756 753440

Fax: 01756 752857

Contact us for

Free Demo CD

www.labcenter.co.uk

info@labcenter.co.uk

NEWPRODUCTS

Please quote *Electronics World* when seeking further information

the need for frequency multiplication in 5GHz ISM band applications. Power consumption is 7.0mA. The LMX2433 PLL has an operating frequency of 3.6GHz RF with 1.7GHz IF and a power supply current of 5.2mA.

National Semiconductor
www.national.com
Tel: +44(0) 870 242171

Low ESR cylindrical SMT electrolytics

Embedded PC specialist, DSP Design, has introduced a PC/104

application development kit that supports Linux, the open source operating system. Known as LaunchPad LP400LIN, this application development kit is supplied with a version of the Linux operating system configured to meet the user's needs. It includes a PC/104 processor board, a Compact flash card pre-loaded with the Linux operating system, full documentation and sample software plus necessary hardware accessories. The complete system is housed in a smart laptop carrying case.

DSP Design
www.dspdesign.com

Analyser tests amplifiers in mobile handsets

Anritsu has introduced the ME7840/4 handset power amplifier test system, that characterises the performance of next-generation handset power amplifiers. The device integrates the measurement capabilities of five instruments with a high power test set, said the supplier. The system handles 5W of power from 10MHz to 6GHz and includes measurement

software including the ability to tune for swept power gain compression and intermodulation distortion (IMD). Other single connection tests include S-parameters, harmonics, and noise figure from 50MHz to 6GHz.

Anritsu
Tel: +44(0) 1582 433200

Kits are ready to roll

Trident microsystems has added a series of 'ready-to-roll' kits for battery-operated systems designed for implementing handheld PC-based instrumentation and equipment. Each of the kits includes a single-board computer and TFT display, together with the associated inverter, cables, software drivers and optional power supply and hard disk drive. Microsoft Windows can be pre-loaded. The kits are based on Toshiba's low power poly silicon 8.4" 800x600 TFT LCD. Designers can opt to have one of three 3.5" FDD-format Evalue SBCs in the kit: the ECM3412 uses a National Geode GX1 processor at 300MHz offering fanless low power operation; The ECM3610 has a 667MHz VIA Eden processor; and the

ECM3615, with a Transmeta Crusoe TM5400, can run two displays simultaneously.

Trident Microsystems
www.tridentdisplays.co.uk
Tel: +44(0) 1737 780790

Chip inductor for 3GHz signals

The HPL range of thin film chip inductors, available from Rhopoint Components, operate



at frequencies as high as 3GHz and is designed for use in such applications as cellular phones, telecommunications networks, and filter circuits. These thin film inductors have a Q factor of up to 50 at 1.5GHz, which is higher than most multilayer devices. Available in the range 1.0nH to 15nH, this series of inductors has an inductance tolerance down to ± 0.1 nH. The temperature coefficient of inductance is from 0 to 125ppm/ $^{\circ}$ C. The inductors are available in 0201 and 0402 sizes.

Rhopoint
Tel: +44(0) 1883 717988

DC-DC outputs with independent regulation

SynQor has a line of dual output quarter brick DC-DC converters with independent regulation. Called the DualQor Giga series, the quarter bricks are designed to deliver 15A of total output current on each rail simultaneously, without a heatsink. Profile on a standard footprint and pin out is 8.5mm. The series operates from an input voltage of 35V to 75V and offers output voltage combinations of 3.3/2.5V, 3.3/1.8V, 3.3/1.5V and 3.3/1.2V with other voltages to follow.



Line protection thermistor withstands lightning

Epcos has launched two PTC thermistor designs for telecoms line protection,

which comply with ITU-T standards K20, K21 and K45 in the tripped (high-

resistance) state, they can even withstand continuous contact with power lines at 110/230VAC. The square PTC thermistor R212 is designed for the latest generation of main distribution frame modules. With overall dimensions of only 5.95 x 5.95 x 2.65mm, it is intended for vertical surface mounting which offers considerable space savings over conventional SMD solutions. Its electrodes are suitable for soldering as well as for clamping. Rated resistance is 12 Ω at 120mA and 25 $^{\circ}$ C. There is a telecoms pair protector (TPP) containing two PTC thermistors in a four-pin case. Epcos
www.epcos.com



AS PART OF OUR PLANNED DISPOSAL PROGRAMME

FINAL MASSIVE CLEARANCE SALE

ELECTRONIC TEST AND COMMUNICATION EQUIPMENT

TEKTRONIX – HEWLETT PACKARD – AGILENT – MARCONI – PHILIPS – RACAL – W&G – R&S – ETC

Due to retirement closure and sale of our main Whitehall Works Trading Site. All stock is being moved over the next few weeks to our large bulk storage site – Smithies Mill – where we will hold a combined massive total clearance sale over the rest of the year.

Starting now 20,000 sq ft full of electronics is being made ready over the coming weeks for complete disposal, either bulk or single item offers can be made by anyone – trade or private. The warehouse is being opened for callers all day on Saturdays 9.00am-5.00pm or weekdays by appointment.

Instructions have been given to start early September to help with this disposal by way of auction/tender sales on site and on line by:

www.teck-asset.co.uk

E-mail: info@teck-asset.co.uk

Details also of electronic items by

www.johnradio-electronics.com

www.johnradio-electronics.co.uk

www.johnradio.com

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER.

Tel: 01274 684007. Fax: 01274 651160


Smithies Mill

Location M62 Junction 27 A62 1 mile Birstall Smithies lights – under Smithies Mill chimney topped with aerials on left

Tel: 01924 442905. Fax: 01924 446170

Our normal workshop repairs and calibration checks – plus all sales are still on going contact Pat

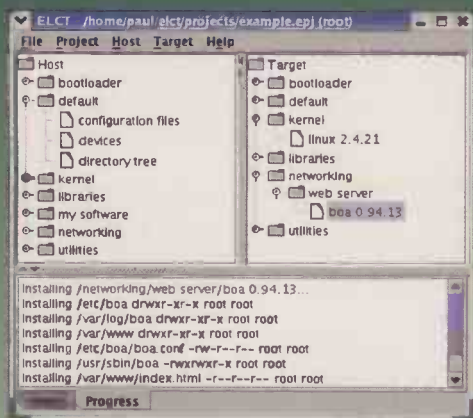ROLL-YOUR-OWN minimal embedded Linux system



Embedded Linux Configuration Tool

Select the software to include in your target project. Use ELCT to launch source configuration programs, compile source, check for library dependencies and install to the target.

Included on the ELCT CDROM is enough open source software for you to roll-your-own minimal Linux system.

See our website for more details.

£135

excl. VAT

Ashdown Electronics Ltd

www.ashdownelectronics.com

sales@ashdownelectronics.com

Telephone 01342 315656



A QUANTUM LEAP IN EMBEDDED CONTROLLERS

Quick FIRE

SUPERCONTROLLERS

Our range provides:-

- The fastest 68000 based Core up to 66 Mhz.
- Extensive I/O:- Serial, IrDA, SPI, I²C, Analogue, Timers/Counters, RTC, etc.
- Large Memory Capacity:- Flash, SRAM, DRAM.
- Supports:- Mono & Colour LCD's, Touch Panels & Keypads, Very Low Power.

ALSO LOW COST

DEVELOPMENT

- Target easily & quickly.
- Full ANSI 'C' compiler, assembler & linker all Windows32 based.
- Source Level Debug.
- Full Driver Support with Libraries.
- Real Time Multitasking OS with a free run time licence.
- Free Unlimited email support.

www.cms.uk.com

see our web site for full details

CAMBRIDGE MICROPROCESSOR SYSTEMS LTD



Unit 17-18 Zone 'D' Chelmsford Rd. Ind. Est. Great Dunmow, Essex CM6 1XG

Telephone: 01371 875644

email: sales@cms.uk.com

Please quote *Electronics World* when seeking further information



The unit measures 1.45 x 2.3 x 0.335in. All modules can deliver full load current of 15A on each rail at typical ambient environments of 55°C and 200 LFM airflow. The DualQor units essentially consist of two eight-brick modules placed in the space of a quarter-brick.

According to the supplier, this allows it to develop any output voltage combination required by customers.

SynQor
www.synqor.com
Tel: +44(0) 49 9621 60700

Chipset for cordless telephones

Atmel has available a 2.4GHz DCT chip set, consisting of the LNA/PA IC T 7026 and the transceiver ICT 2803. It is designed for cordless phones, while also being used for wireless data applications such as internet access, wireless headsets, games and home entertainment. The chipset enables an extended distance between the handset of a cordless phone and the base station, from 300m to 600m. The 2803's variable data transmit bit rate allows to adjust to any data transmit bit rate in a range of 9.6kbit/s to 1.152Mbit/s.

Atmel
www.atmel.com
Tel: 0033 442 53600

Module brings GPRS connectivity

Acte Components has available the WISMO Quik Q2406B module that is designed to bring voice, data, SMS and GPRS



class 10 connectivity to applications including mobile phones, industrial machine-to-machine and automotive applications. The ETSI compliant Q2406B is loaded with complete 2.5G GSM/GPRS class 10 capability. It is designed for dual band operation and is available in either 900MHz/1800MHz or 850MHz/1900MHz or CDMA/AMPS variants. With

overall dimensions of 58 x 32 x 3.9mm thick, the module includes an optional embedded TCP/IP. It also has 32k of RAM and 4k EEPROM that enables customers to embed their own applications (via MUSE Open AT) and reduces the need for additional software and hardware that is external to the module. The Q2406B draws less than 3.5mA in GSM idle mode, and an average 300mA when communicating (GSM900, 0 per cent DTX, Pmax). The module requires a 3.6V DC power supply and can be connected directly to a Li-ion battery pack. Acte Components
www.actecomponents.com
Tel: +44(0) 1256 84588

Analogue video signal analyser

Tektronix has an automated component analogue video signal analyser that is designed to measure high definition, progressive scan, and PC format signals for consumer video equipment manufacturers, video network

operators, and others that require fast and repeatable testing. Designated the VM5000HD, the automated video measurement set is designed to provide accurate, and repeatable video measurements in 1080i, 720p,

480p, and SXGA formats making use of multiple industry-standard video parameters, without the need for complicated instrument set-ups, algorithm selection, time-consuming manual measurements or tedious results correlation. With a single button push, the VM5000HD can make 100 different parametric measurements in eight specific test categories within 10 seconds so that product performance can be objectively and reliably assessed. It offers a high-definition matrix test signal set for the creation of standardised test signals including colour bars, multi-burst, sweep, and five other signal types, for testing in Y/Pb/Pr and RGB colour space.

Tektronix
www.tektronix.com
Tel: +44(0) 1344 392241

Test software for fast serial data

Test equipment and software aimed at compliance and validation testing for emerging serial data standards has been unveiled by Tektronix. The RT-Eye serial data compliance and analysis software (TDSRT-Eye) package works with the firm's TDS6000 and TDS/CSA7000 oscilloscopes and the P7350SMA 5GHz differential probe. It is capable of testing serial links up to 3.2Gbit/s. Option RTE provides software clock recover, eye diagrams, and standard specific parametric measurements in the amplitude, timing, and jitter domain, including total jitter at 10¹² BER. Beyond known standards, waveform masks, measurement





WELDEX 2003

WELDCOME. 11-14 November 2003
National Exhibition Centre Birmingham, UK

11-14/NOVEMBER/03

Join us at Weldex 2003

The international welding, joining, cutting and fabrication exhibition
co-located with Manufacturing Week INSPEX, Tooling and CIM (T.E.A.M)

Weld class event

At Weldex 2003 you will experience, first hand, the very latest products, services and technologies in welding, joining, cutting and fabrication. As the largest international show of its kind in the UK, Weldex 2003 represents a unique opportunity to make contact with some of the biggest and best names in the business, from all over the world.

Weldex 2003 is the event in the UK welding calendar

Whether you are selling, buying, learning, or just staying in touch, Weldex 2003 is the place to do good business in the UK. So make a date to join us at the NEC, Birmingham, 11 - 14 November 2003.

For tickets and early registration visit: www.weldexpo.com or call
Nichola Mitchell: +44(0)1322 660070 **NOW!**

To find out what's exhibiting at Weldex 2003 contact: Karin Allfree or Isobel Roberts:
+44(0)1322 660070

WEEX/VAD/HHC/IPG

Supported by:



American Welding Society



Official sponsoring publications:

ENGINEERING
DEFINITION

European Quality Today

iEM

Laboratory
SPECIAL

Quality Today

weldex news

NEWPRODUCTS

Please quote *Electronics World* when seeking further information




Dual comparator and reference for 6.5µA

Linear Technology's LT6700 dual micropower comparator has an integrated 400mV reference and is available in the 6-lead ThinSOT. Aimed at monitoring supply voltages in portable devices, the chip has 40mA outputs for driving LEDs, opto-isolators and relays directly. Operating over 1.4V to 18V supply range, the device draws 6.5µA, has built-in comparator hysteresis, and guaranteed plus two per cent threshold accuracy to ensure stable operation over temperature and in noisy environments. The device provides two external comparator inputs with the other two inputs connected internally to the on-chip reference. These high impedance inputs need less than 10nA input bias current. The comparator outputs are open collector and the output load can be referred to any voltage up to 18V, also independent of supply voltage.

Linear Technology
www.linear.com
Tel: +44(0) 1276 677676

limits, and reporting functions can be customised by the user, enabling companies and industry groups working on proprietary and emerging standards to develop their own internal and external compliance programs and reports.

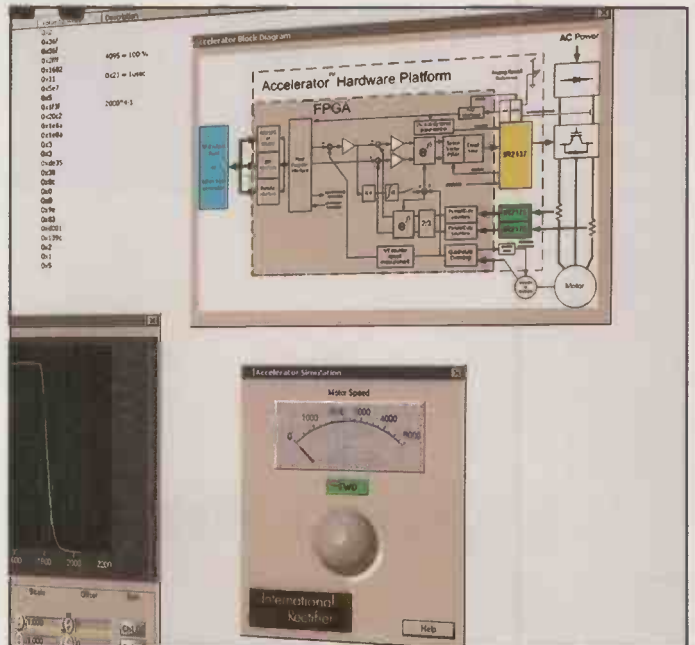Tektronix
measurement.uk@tektronix.com
Tel: +44(0) 118 984 5515



IP library for speedy motor control design

International Rectifier has announced the IRMCS203 development system and the IRMCO203 intellectual property (IP) library of motion

control algorithms. This development system and object code IP library support the firm's iMOTION integrated design platform for applications such as high-speed spindle motor control. The development system comes with proven analogue and power stage hardware designs as well as the software needed to achieve a design flow that requires no coding to configure motor control algorithms. The digital control section uses the firm's Accelerator configurable control engine system architecture using parallel processing and customisable peripherals. The analogue section uses high voltage ICs for the gate drive and current sensing functions. The power stage is based on the latest non-punch-through (NPT) IGBT and PlugNDrive integrated power module technologies. The algorithm is a licensable object code IP library for sensor-less control of permanent magnet motors featuring high starting torque and smooth ramp-up. It is targeted for low cost FPGA applications, and is designed to reduce the need for complicated programming processes.
International Rectifier
www.lambda.com
Tel: +44(0) 20 8645 8003

DIN-rail AC-DC supplies for industry go lead-free

Lambda has developed the DLP series, a family of DIN-rail mounted AC-DC supplies aimed specifically at factory

automated, industrial control and test and measurement applications. The 23V DLP series has a maximum efficiency

of 87 per cent and power density of up to 0.21W/cm³. Three models are being launched with output powers of 75, 120 and 240W. Output currents range from 3.1A on the DLP-75 to 10A on the DLP240-24. Input voltage covers the range 85 to 264AC. The supplies are fitted with a red alarm LED giving operators an immediate warning should a short circuit of the load occur. The units have a common height and depth of 97 x 110mm. They range in width from 50mm for the 75W unit to 120mm for the 240W supply. Operating temperature range is -10 to +50C at full load derating to 60 per cent at +60°C. From October 2003 the DLP will be manufactured as lead-free to satisfy emerging legislation.

Lambda
www.lambda.com
Tel: +44(0) 1271 856666





Quasar Electronics Limited
 PO Box 6936, Bishops Cleeve, Nottingham
 CM23 4WP
 Tel: 0870 246 1826
 Fax: 0870 460 1045
 E-mail: sales@quasarelectronics.com

Add £2.00 P&P to all UK orders. 1st Class Recorded - £4.
 Next day (insured £250) - £7. Europe - £5. Rest of World - £10.
 We accept all major credit/debit cards. Make cheques/PO's
 payable to Quasar Electronics Limited.
 Prices include 17.5% VAT. MAIL ORDER ONLY.
 Call now for our FREE CATALOGUE containing details of
 over 300 electronic kits, projects and modules.



QUASAR 0871 CREDIT CARD SALES 717 7168
 electronics

Motor Drivers/Controllers

Here are just a few of our controller and driver modules for AC, DC, unipolar/bipolar stepper motors and servo motors. See website for full details.

DC Motor Speed Controller (6A/100V)

Control the speed of almost any common DC motor rated up to 100V/5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15VDC. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£12.95**
 Assembled Order Code: AS3067 - **£19.95**

NEW! PC / Standalone Unipolar Stepper Motor Driver

Drives any 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps max. Provides speed and direction control. Operates in stand-alone or PC-controlled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9V DC. PCB: 80x50mm. Kit Order Code: 3179KT - **£9.95**
 Assembled Order Code: AS3179 - **£16.95**



PC Controlled Dual Stepper Motor Driver

Independently control two unipolar stepper motors (each rated up to 3 Amps max.) using PC parallel port and software interface provided. Four digital inputs available for monitoring external switches and other inputs. Software provides three run modes and will half-step, single-step or manual-step motors. Complete unit neatly housed in an extended D-shell case. All components, case, documentation and software are supplied (stepper motors are NOT provided). Dimensions (mm): 55Wx70Lx15H. Kit Order Code: 3113KT - **£16.95**
 Assembled Order Code: AS3113 - **£24.95**

NEW! Bi-Polar Stepper Motor Driver

Drive any bi-polar stepper motor using externally supplied 5V levels for stepping and direction control. These usually come from a software running on a computer. Supply: 8-30V DC. PCB: 75x85mm. Kit Order Code: 3158KT - **£12.95**
 Assembled Order Code: AS3158 - **£26.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU203 £9.95

Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12VDC/6mA (standby). Two and Ten channel versions also available. Kit Order Code: 3180KT - **£41.95**
 Assembled Order Code: AS3180 - **£49.95**



Computer Temperature Data Logger

4-channel temperature logger for serial port. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 38x38mm. Powered by PC. Includes one DS1820 sensor and four header cables. Kit Order Code: 3145KT - **£22.95**
 Assembled Order Code: AS3145 - **£29.95**
 Additional DS1820 Sensors - **£3.95 each**



NEW! DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130x110x30mm. Power: 12VDC. Kit Order Code: 3140KT - **£39.95**
 Assembled Order Code: AS3140 - **£69.95**




Serial Isolated I/O Module

PC controlled 8-Relay Board. 115/250V relay outputs and 4 isolated digital inputs. Useful in a variety of control and sensing applications. Uses PC serial port for programming (using our new Windows Interface or batch files). Once programmed unit can operate without PC. Includes plastic case 130x100x30mm. Power: 12VDC/500mA. Kit Order Code: 3108KT - **£64.95**
 Assembled Order Code: AS3108 - **£64.95**



Infrared RC Relay Board

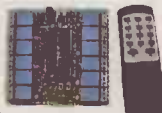Individually control 12 on-board relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112x122mm. Supply: 12VDC/0.5A
 Kit Order Code: 3142KT - **£41.95**
 Assembled Order Code: AS3142 - **£69.95**



PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) **£16.00**
 18V DC Power supply (PSU201) **£6.95**
 Leads: Parallel (LEAD108) **£4.95** / Serial (LEAD76) **£4.95** / USB (LEADUAA) **£4.95**

NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied complete with 40-pin wide-slot ZIF socket, box and Windows Software. Kit Order Code: 3128KT - **£49.95**
 Assembled Order Code: AS3128 - **£64.95**



Enhanced "PICALL" ISP PIC Programmer

Will program virtually ALL 8 to 40 pin PICs plus a range of ATMEL AVR, SCENIX SX and EEPROM 24C devices. Also supports In System Programming (ISP) for PIC and ATMEL AVRs. Free software. Blank chip auto detect for super fast bulk programming. Requires a 40-pin wide ZIF socket (not included). Kit Order Code: 3144KT - **£54.95**
 Assembled Order Code: AS3144 - **£69.95**



ATMEL 89xxx Programmer

Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16-18VDC. Kit Order Code: 3123KT - **£29.95**
 Assembled Order Code: AS3123 - **£34.95**



NEW! USB & Serial Port PIC Programmer

USB/Serial connection. Ideal for field use. Header cable for ICSP. Free Windows software. See website for PICs supported. ZIF socket not incl. Supply: 18VDC. Kit Order Code: 3149KT - **£29.95**
 Assembled Order Code: AS3149 - **£44.95**



www.quasarelectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads



Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process.

This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly. Where software or files are available from us, please email Jackie Lowe with the circuit idea name as the subject.

Send your ideas to: *Phil Reed, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU*


email ewcircuit@highburybiz.com

RF power loader

This circuit offers a symmetrical load for the 125W exciter. It is equally suited to driving one or two loads but power is increased when one or two loads is driven. The configuration is broadband and inexpensive.

When driving two loads, outputs of the circuits are connected in parallel. The diodes are very high speed SBYV27-200 types capable of handling an amp. Their reverse recovery time is 15ns. For lower powered and VHF circuits a suitably rated 'hot carrier/Shottky' diodes would be suitable.

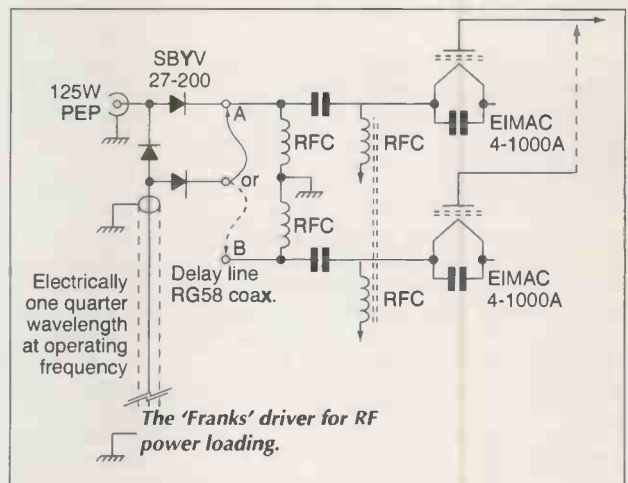Frank Shaw, VK6ALF
Ballajura
Western Australia




Simple triggered timer

A trigger pulse of 5V amplitude turns on the amplifier and pulls the non-inverting input high. Output from the amplifier is latched high until capacitor C charges to the voltage on the non-inverting input. It then switches low, turning off the amplifier and discharging the capacitor.

An advantage of this circuit is the high speed of the LMH6639. Also, the circuit draws almost no power supply current when not triggered.

Kamil Kraus,
Rokycany
Czech Republic

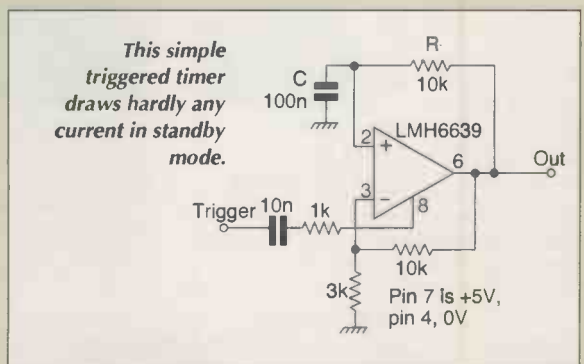

Electronic fluorescent lamp starter

I have found that conventional neon/bi-metal starters are not only a source of malfunction, but they can also cause tubes to suffer from heater failures. In this circuit, the heater pins are paralleled, effectively halving the current in the heaters during tube operation.

The circuit has been in operation for some years now and appears to extend tube life significantly. I adapted existing choke ballasts to permit the circuit shown to strike the tube repeatedly until sustained by normal choke action.

Resistor R_1 charges C_1 until, the transistor conducts and fires the SCR, discharging C_1 to provide a high voltage across the tube. Once the tube has ionised, the rectified AC voltage generated across the choke tap drives the transistor off, and turns the starter off.

Components R_1 , R_2 and P_3 are 350V rated. In addition, C_1 must be suitable for 400V DC.

In the case of one slim style choke, it was possible to remove the end cap from the connections

and solder a tap to the existing winding. In another case, a choke wound on E and I laminations was adapted by winding 50 turns of 36 SWG (0.2mm) wire over the outer layer without dismantling. The number of turns required should develop 6V when run as a transformer across 240V mains.


Observe safety precautions for mains operated equipment.

Henry Maidment
Salisbury Wiltshire UK

Warning

When powered up, this circuit must be considered live throughout and potentially lethal. Do not attempt to replicate it unless you are fully conversant with the regulations and safety guidelines associated with mains-rated circuitry.

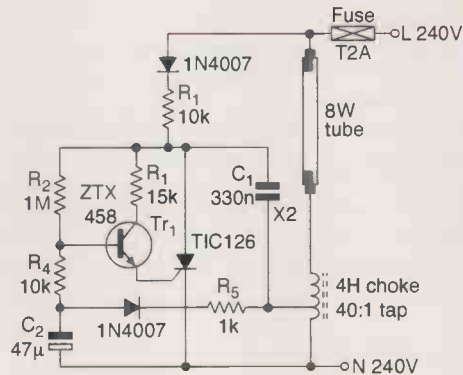Having found that conventional neon/bi-metal starters can cause tubes to suffer from heater failures I designed this electronic alternative, which effectively halves current in the heaters when the tube has fired.



Simple fastest finger first circuit


This simple circuit indicates the first switch closed and will inhibit others until re-set.

A number of identical circuits can be built, four are shown, there are no critical components, the lamps L1 are low voltage filament lamps, resistor values R_1 and R_2 are such to enable

the SCR trigger voltage to be available. The first switch of S_1 to be closed will turn on the related SCR, illuminate the associated lamp, maintaining current flow. This will cause the diode gating arrangement to reduce the available trigger voltage, inhibiting further SCRs from

being turned on. Momentary opening of S_2 removing power and turning off the activated SCR resets the system.

M J Nicholas
Bournemouth
Dorset
UK

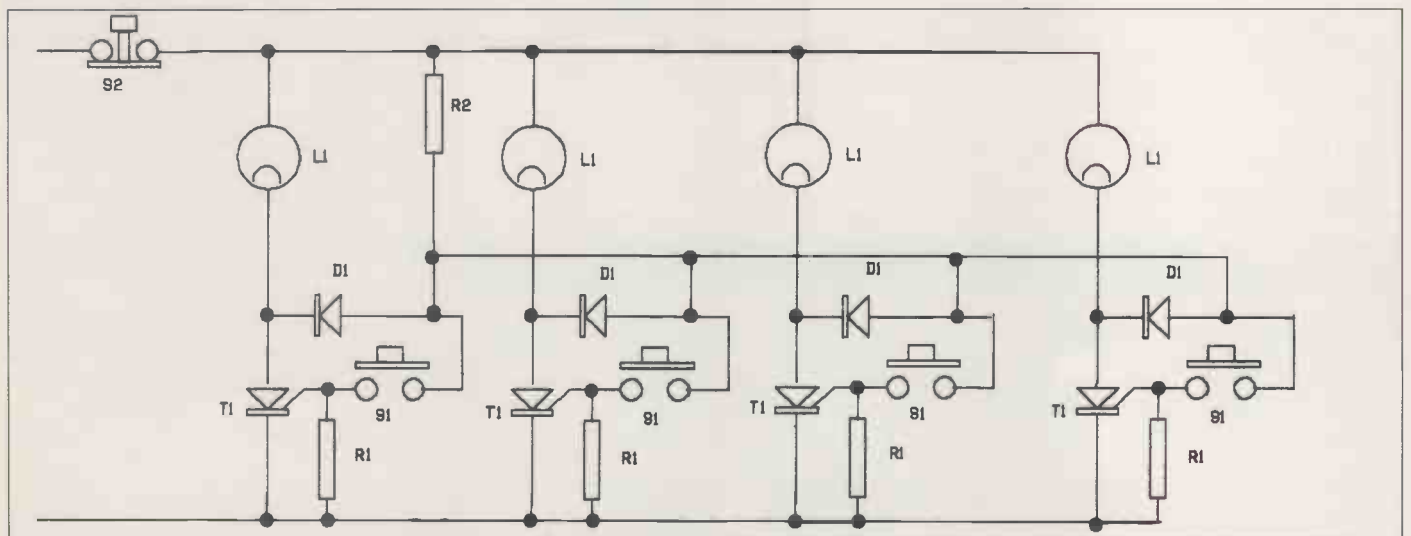

Simple oscilloscope DC offset adapter

This circuit was born out of nostalgia for some of the facilities available on my old Tektronix 535A oscilloscope, namely the 1A5 plug-in with its calibrated DC offset.

These and other useful functions are not available on my current CRO, a Tektronix 2213. I have found this adapter useful for monitoring CRT video driver waveforms and improved amplitude accuracy by measurement of the offset voltage, while using the CRO as a null indicator.

The adapter is a 20dB pad for a $1M\Omega$ system, with a DC injection point and frequency compensation. $R1+R2 = 1M22$; $R3+R4 = 4M95$ and $R5+R6+R7 = 1M22$

With these component ratings, the CRO adapter will have a maximum input rating of 250V (DC + AC peak). This being determined by the capacitor ratings, which can be increased by adding fixed 100V or

200V capacitors in series with C1 & C2. Select values about triple the total required value, this will give a total voltage rating approximately the sum of the two ratings.

Alternatively, C1 & C2 could be constructed from copper or brass wire or strip, but the resistors then will limit the input to about 500V.

The offset generator can be either a $10k\Omega$ 2W 10 turn pot connected across a $\pm 40V$ regulated supply. Or a 40V floating supply with polarity reversing switch. A 1 volt input to the DC offset terminal appears as a 1 volt input to the adapter. When used with a 10:1 probe this gives an offset of 400V at the probe tip.

Setting up

A 1kHz square wave generator with low output impedance is required. First connect a 10:1 probe to the CRO and adjust the compensation. Then remove the probe and connect

the adapter. Connect the generator to the input of the adapter via a suitable inline-terminating resistor and adjust C2 for optimum corners (the same as for probe compensation). Now connect the 10:1 probe to the adapter and adjust C1 for the correct waveform.

Operation

Use the adapter between the 10:1 probe and CRO to monitor signals with a high DC component. Set the CRO coupling switch to DC. And use the offset generator to bring the relevant part of the signal into view.

To measure a waveform

With the coupling switch set to ground centre the trace. Then set the V/div switch for the highest sensitivity without overload (distortion). Use the offset generator to bring the +ve peak to the centre and note the offset volts. Then do the same for the -ve peak, the pk - pk of the waveform equals the difference between the two readings.


It can also be used to closely examine a signal. I have used it to check the output of a simple digital sine wave generator. With the V/div set to maximum (2mV/div) giving 20mV at the adapter input, the synthesised sine wave, (at 8V pk-pk) could be examined in detail over the whole cycle.

Construction

This adapter is mounted in a small box with a BNC male at one end and BNC female at the other. Farnell have a suitable item, 309-801. The components should be kept away from the sides of the box and the 1M22 resistors should preferably be at right angles to the 4M95 resistor. For improved accuracy, either use a suitable ohmmeter to select the value (the MRS25 resistors have good stability) or higher accuracy components, although getting the values above $1M\Omega$ may be more difficult.

Caution: This unit will not increase the maximum input voltage rating of your oscilloscope or the probe

Rodger Bean
Watson
Australia

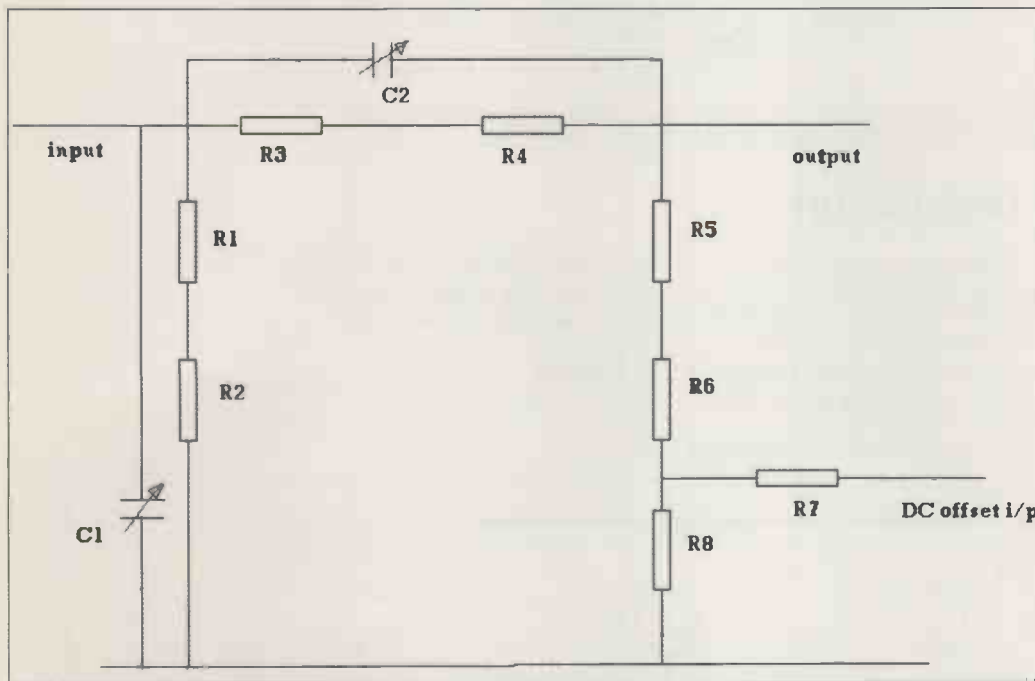

The resistors are all Philips MRS25 (0.6W, 250V max, 1%)

R1	698K	R5	681K
R2	523K	R6	536K
R3	2M2	R7	6K2
R4	2M7	R8	2K

C1 & 2 2 - 10pF trimming 25V, BC components 2222 808 11109, Farnell 303-811.

Missed call indicator

No answer phone or voice mail service? Need to be told you have been called? This handy missed call indicator will plug into a telephone socket and indicate if any calls have been received by a pulsing red LED and a unobtrusive chirp from the piezo sounder. All power is obtained from the telephone line.

Telephone systems can only supply a few milliamps without an unacceptable voltage drop so low power techniques are employed through out this design.

R5, D5,6,7,8,9 & C3 form a 5 Volt power supply. A bridge rectifier is employed to maintain supply when "ringing" is in progress and up to 100V AC is superimposed on the steady 50V DC line voltage.

R1, D1,2 R2, TR1, D3, & R3

detect the presence of the ringing voltage, D1 & 2 isolating C1 when off hook preventing dial tones from triggering the unit and any loading of the audio signal. When ringing is detected TR1 collector is pulled low on +ve going peaks, D3 providing AC continuity and protection for TR1.

R4, C2 & IC1a are coupled into TR1 via D4 and in effect form a low pass filter.

IC1a output goes high when "ringing" is first detected and does not go low until after ringing is finished, by when either the caller has rung off or voice mail has taken the call.



The output of IC1a is connected via R6 and C4, the time constant of which is approx. the delay before the

unit triggers, to the latch formed by IC1b and IC1c and associated feedback components R8 and D10. The unit remains active until it is reset by pressing the reset switch. R7 reduces contact erosion by limiting the discharge current from C4.

When the Latch output is high Oscillator IC1d is enabled this gives a 20ms pulse every second, this is passed via buffer IC1f which in turn drives a high brightness LED. This pulse also enables the oscillator IC1e that chirps the piezo sounder.

NOTE: This unit is not type approved for connection to a PSTN and as such should only be used on private telephone circuits.

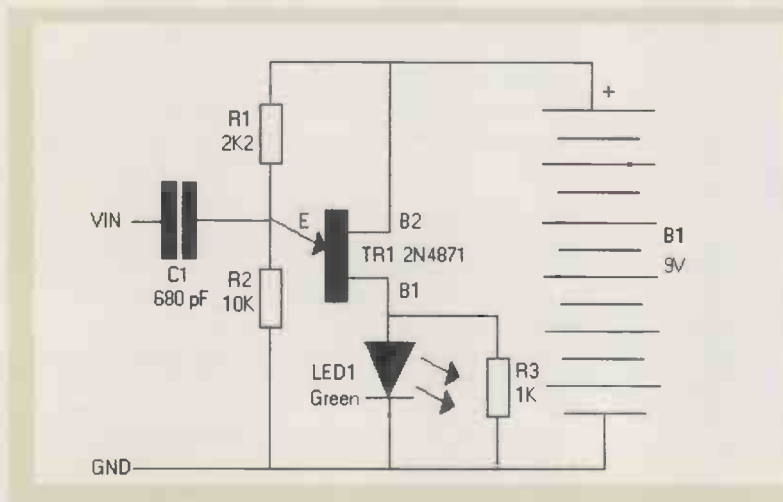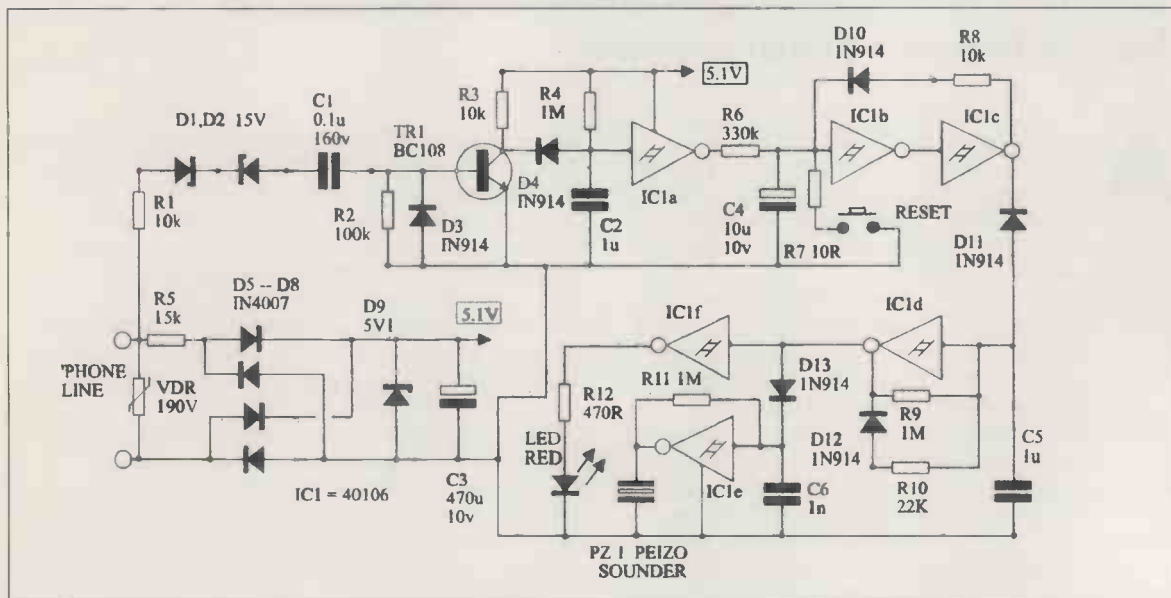*Nigel Goodman Eng tech MIIIE
St. Leonards on sea
East Sussex*



Unijunction memory

This circuit illustrates using a unijunction transistor as a bistable memory element. R1 and R2 set the DC bias at the emitter of TR1. If a positive pulse is applied to Vin, TR1 will switch to a low resistance state causing the LED to light. If a negative pulse is applied to Vin, TR1 will revert to a high resistance state. R3 prevents the LED glowing faintly when the transistor is in a high resistance state.

*André de Guérin
Vale
Guernsey*

Noise and moving-magnet cartridges

Marcel van de Gevel investigates noise optimisation in RIAA amplifiers for moving magnet cartridges and presents a high-performance design example.

As you can read in any textbook on low-noise design, the noise of an amplifier can be described with two equivalent input noise sources. These are an equivalent input noise voltage source in series with the input of the amplifier and an equivalent input noise current source shunted across its input¹.

Which of the two has the largest influence depends on the impedance of the signal source driving the input. For example, when the magnitude of the source impedance is $12\text{k}\Omega$, a noise current of $1\text{pA}/\sqrt{\text{Hz}}$ has the same influence as a noise voltage of $1\text{pA}/\sqrt{\text{Hz}} \times 12\text{k}\Omega = 12\text{nV}/\sqrt{\text{Hz}}$.

Unfortunately, some of the measures that a designer can take to reduce the equivalent input noise-voltage density lead to an increase of the equivalent input noise current density and vice versa. This applies especially to the selection of the input device and its biasing conditions.

It is important for a designer of low-noise electronics to know the source impedance, so that he or she can choose the device and biasing that gives the smallest total noise for that specific source impedance. Because noise optima are usually rather broad, there is no need to know the source impedance with a high accuracy; a reasonable estimate will do.

In the case of RIAA amplifiers for moving magnet (MM) cartridges, the source impedance varies enormously over the band of interest. A typical cartridge with $1\text{k}\Omega$ of

DC resistance and 0.5H of inductance has an impedance of $1\text{k}\Omega$ at low frequencies and almost $63\text{k}\Omega$ at 20kHz . The question is: for what impedance should a RIAA amplifier be optimised if we want to get the smallest amount of audible noise? It will be shown in this article that the cartridge impedance at 3852Hz is a good estimate. Also, an easy way to account for $1/f$ -noise will be given.

When the input stage and feedback network are properly designed, the thermal noise of the $47\text{k}\Omega$ resistor shunted across the input is usually the largest remaining noise contribution in the RIAA amplifier itself.

Just leaving this resistor out is not an option, as this would reduce the damping of the resonant circuit consisting of the cartridge inductance and the load capacitance, seriously affecting the response between 10kHz and 20kHz . However, a lower noise $47\text{k}\Omega$ input resistance can be realised by using combinations of series and parallel feedback.

This technique is also known as the active input impedance or 'electronic cooling' technique. Two examples of such RIAA amplifiers, one discrete circuit and one with op-amps, will be given.


Finally, the improvement which can be obtained by replacing the $47\text{k}\Omega$ resistor with an active input resistance will be estimated for a typical cartridge.

The 3852Hz rule

Figure 1 is a simple model of a cartridge connected to an RIAA amplifier, followed by an A-weighting filter. The L-R series network models the impedance of a moving magnet cartridge with inductance L and DC resistance R .

The noise of the RIAA amplifier is represented by the noise voltage source v_{noise} and the noise current source i_{noise} . These noise sources are assumed to be white and uncorrelated. The noise of the cartridge itself is not included in this model, because the amplifier designer cannot optimise this anyway. The voltage controlled

Fig. 1. Simple model of a cartridge connected to an RIAA amplifier.

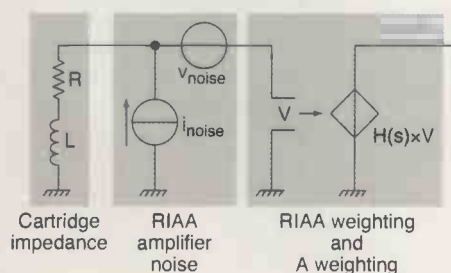

voltage source with transfer $H(s)$ models the RIAA- and the A-weighting.

Note that a real cartridge has a frequency-dependent effective series resistance, unlike a simple L-R series network. However, this mainly affects the phase of the cartridge impedance, while only the magnitude will be used in the following calculation.

The contribution of v_{noise} to the total integrated noise at the output is:

$$A = \int_0^{\infty} |H(j2\pi f)|^2 S(v_{noise}) df$$

$$= \int_0^{\infty} |H(j2\pi f)|^2 df \cdot S(v_{noise}) \tag{1}$$

The second equality sign applies when $S(v_{noise})$ is independent of frequency, that is, when the noise is white. $S(v_{noise})$ is the noise voltage spectral density, that is, the number of squared volts per hertz. A is the part of the mean-square noise voltage (square of the RMS noise voltage) at the output which is caused by v_{noise} . $|H(j2\pi f)|$ is the magnitude of the RIAA and A filter transfer at frequency f .

The contribution of i_{noise} equals:

$$B = \int_0^{\infty} |H(j2\pi f)|^2 (4\pi^2 f^2 L^2 + R^2) S(i_{noise}) df$$

$$= \int_0^{\infty} |H(j2\pi f)|^2 (4\pi^2 f^2 L^2 + R^2) df \cdot S(i_{noise}) \tag{2}$$

assuming the current noise to be white. $S(i_{noise})$ is the noise-current spectral density, that is, the number of squared amperes per hertz. B is the part of the mean-square noise voltage (square of the RMS noise voltage) at the output which is caused by i_{noise} .

Hence,

$$\frac{B}{A} = \frac{\int_0^{\infty} |H(j2\pi f)|^2 (4\pi^2 f^2 L^2 + R^2) df}{\int_0^{\infty} |H(j2\pi f)|^2 df} \cdot \frac{S(i_{noise})}{S(v_{noise})}$$

$$= \left(\frac{\int_0^{\infty} |H(j2\pi f)|^2 f^2 df}{\int_0^{\infty} |H(j2\pi f)|^2 df} \right) \cdot 4\pi^2 L^2 + R^2 \cdot \frac{S(i_{noise})}{S(v_{noise})} \tag{3}$$

At a single frequency $f=f_1$, the ratio of the contribution of i_{noise} to the contribution of v_{noise} equals:

$$\frac{D}{C} = (4\pi^2 f_1^2 L^2 + R^2) \cdot \frac{S(i_{noise})}{S(v_{noise})} \tag{4}$$

Here, D is the contribution of i_{noise} and C is the contribution of v_{noise} to the total noise density at f_1 .

Equations (3) and (4) are equal when:

$$f_1 = \pm \sqrt{\frac{\int_0^{\infty} |H(j2\pi f)|^2 f^2 df}{\int_0^{\infty} |H(j2\pi f)|^2 df}} \tag{5}$$

Equation (5) can be evaluated numerically. This can easily be done with PSpice and Probe, using an analogue behavioural model of an idealised RIAA amplifier with an A-weighting filter behind it.

You can first simulate the AC transfer and use Probe to evaluate the denominator integral. Then put a differentiator in the circuit with unity transfer at 1Hz, and do the same

for the numerator. The result is $f_1 \approx 3852\text{Hz}$. I used the IEC modified RIAA response, which has an extra roll-off below 20Hz, but this should make very little difference.

This proves that the total integrated weighted noise is a constant factor times the noise in a 1Hz bandwidth around 3852Hz. 'A constant factor' means that this factor is independent of $S(v_{noise})$ and $S(i_{noise})$. Hence, the combination of $S(v_{noise})$ and $S(i_{noise})$ which is optimal at 3852Hz is also optimal for the integrated weighted noise.

In other words, optimising the integrated A- and IEC modified RIAA-weighted noise is the same as optimising the noise at 3852Hz. When $R=1\text{k}\Omega$ and $L=494\text{mH}$, which are typical values for a MM cartridge, the impedance is about $12\text{k}\Omega$ at this frequency. We will therefore assume a $12\text{k}\Omega$ cartridge impedance in the remainder of this article, unless otherwise noted.

1/f-noise and noise densities relationships

The calculations above apply only to white noise, while many active devices produce substantial 1/f-noise in the audio frequency band. To what white noise level does a given amount of 1/f-noise correspond? Further, if you measure the total A-weighted noise level, how can you compare the results to the theoretical noise densities?

Calculations which are similar to those in the previous section show that 1/f voltage noise has the same influence on the total RIAA/IEC- and A-weighted noise level as white voltage noise with the same density at 1169Hz. In other words, if you determine the noise voltage density at 1169Hz, it doesn't matter what part is white and what part is 1/f noise.

The situation is a bit more complicated for 1/f current noise. If the cartridge impedance were constant, the same rule that applies to 1/f voltage noise would also apply to 1/f current noise. If the magnitude of the cartridge impedance were exactly proportional to frequency, a similar rule would apply, but at a frequency of 5398Hz instead of 1169Hz.

The frequency dependence of the magnitude of the impedance of a real cartridge is something in between these two cases, closer to being proportional to frequency than to being constant. Hence, the current noise density should be determined at a frequency of about 5kHz.

In order to be able to compare measured A- and RIAA/IEC-weighted RMS noise levels to theoretical noise voltage and current densities, one needs to know the noise bandwidth of the cascade of a RIAA/IEC and an A filter. Simulations show that this bandwidth is 3219Hz referred to the transfer at 1kHz. In other words, if one divides the A-weighted RMS output noise voltage by the voltage gain at 1kHz and by the square root of 3219Hz, one finds the average equivalent input number of volts per root Hz.

In order to find the equivalent input noise voltage and the equivalent input noise current, one can measure the output noise voltage twice, once with short-circuited and once with open input.

The equivalent input noise voltage per root hertz can then be calculated directly from the measurement with shorted input, as explained above. As long as the input capacitance is so small that the input impedance can be assumed to be $47\text{k}\Omega$ over the entire audio band, the equivalent input noise current is simply the input noise voltage measured with open input, divided by $47\text{k}\Omega$.

'Electronic cooling'

The thermal noise of a resistor can be modelled with a noise voltage source with a spectral density of $4kTR$ (RMS value $\sqrt{4kTR\Delta f}$ over a bandwidth Δf) in series with a noiseless resistor (the Thévenin equivalent). In this equation, T is the absolute temperature and k is


Boltzmann's constant ($1.38065 \times 10^{-23} \text{J/K}$).

Alternatively, the noise can be modelled with a noise current source with a spectral density $4kT/R$ (RMS value $\sqrt{(4kT/R)\Delta f}$) over a bandwidth Δf) in parallel with a noiseless resistor (the Norton equivalent). Both models behave in exactly the same way at their terminals. A designer can choose whichever model is the most convenient for his or her calculations.

Modelling the $47\text{k}\Omega$ resistor with its Norton equivalent, it becomes clear that this resistor contributes $4kT/47\text{k}\Omega \approx 3.445 \times 10^{-25} \text{A}^2/\text{Hz}$, or $0.5869 \text{pA}/\sqrt{\text{Hz}}$, to the equivalent input noise current, Fig. 2. With a typical effective cartridge impedance of $12\text{k}\Omega$, $0.5869 \text{pA}/\sqrt{\text{Hz}}$ has the same influence as $7.043 \text{nV}/\sqrt{\text{Hz}}$, which is substantial compared to a carefully optimised input stage.

Fortunately, there's a simple solution. Build an accurate and low-noise inverting amplifier with a high input impedance and a voltage gain of $-K$ times. Then connect a resistor with a value of $(K+1) \times 47\text{k}\Omega$ between the input and output of this amplifier, Fig. 3.

Fig. 2. RIAA amplifier with a noisy $47\text{k}\Omega$ resistor.

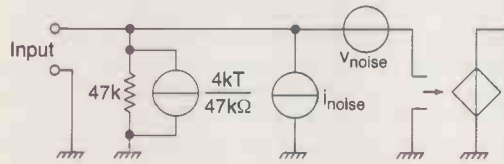

Note: i_{noise} is noise from the rest of the RIAA amplifier.

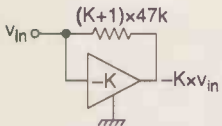


Fig. 3. Low-noise active input resistance.

The voltage across the resistor is $K+1$ times the input voltage and its value is $K+1$ times $47\text{k}\Omega$. Hence, the current flowing through the resistor equals the current that would flow through a $47\text{k}\Omega$ resistor connected between the input and ground.

If the noise of the inverting amplifier is negligible though, the noise current spectral density is $K+1$ times as small. This technique is known as the active input impedance technique or as 'electronic cooling', as it has the same influence on the thermal noise as cooling the resistor down to a $K+1$ times lower absolute temperature.

Both terms can cause confusion, the first because it has a completely different meaning in network theory and the second because the resistor is not really cooled down.

Discrete RIAA amplifier

Figure 4 depicts a circuit in which the inverting amplification and the RIAA equalised amplification are combined². Block N_1 is a two-port with very high voltage, current, transimpedance and transadmittance gain.

Because of the negative feedback around this high-gain block, the voltage v_{in} at the amplifier input also occurs at R_1 . As a result, a current $i = v_{in}/R_1$ flows through R_1 , through the RIAA equalising network R_2, C_2, R_3, C_3 and through the output port of the amplifying block. Resistors R_1 and R_4 are normally made much smaller than R_5 . Hence, the voltage on the upper side of R_4 becomes approximately,

$$-R_4 \times i = -\frac{R_4}{R_1} v_{in}$$

realising a negative voltage gain $-R_4/R_1$.

A more accurate analysis shows that if the amplifying block has infinite gain and if the current flowing into one output pin exactly equals the current coming out of the other, the input resistance equals:

$$R_{in} = \frac{R_4 + R_5}{\frac{R_4}{R_1} + 1} \quad (6)$$

Unfortunately, the input impedance changes when a load

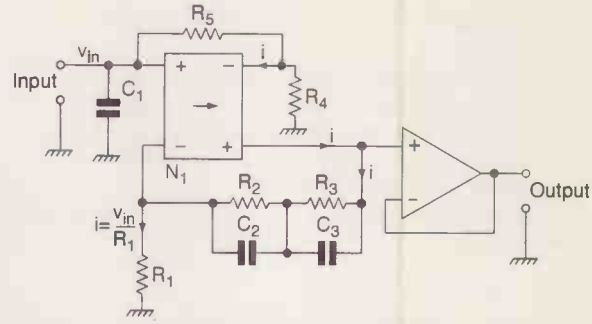


Fig. 4. RIAA equalised amplifier with active input resistance according to reference 2

is connected to the output of the two-port. That is why there is a voltage follower connected behind the RIAA equalising stage.

A discrete implementation is shown in Fig. 5. I use it as a part of a wholly discrete preamplifier with $\pm 14\text{V}$ regulated power supply voltages, but it should also work at the more usual $\pm 15\text{V}$. It has an IEC modified RIAA response, that is, it includes a first-order roll-off below 20Hz .

If desired, this corner frequency can be lowered by increasing the values of the bipolar electrolytic capacitors, although lowering it too much can make the start-up time rather long. The input resistance increases from $47\text{k}\Omega$ to $10\text{M}\Omega$ for subsonic frequencies. This is no problem, as the purpose of the $47\text{k}\Omega$ input resistance is to damp a resonance in the 10kHz to 20kHz frequency range.

The voltage follower at the output is a simple emitter follower. The high-gain block is made of two differential pairs. For reasons of noise optimisation, the input pair is asymmetrical, consisting of a JFET and a bipolar transistor.

It can be shown¹ that the optimal bias current for minimum noise is,

$$I_{C,opt} = \frac{kT}{q} \cdot \frac{\sqrt{h_{FE}}}{|Z_S + r_b|} \quad (7)$$

when a bipolar transistor is driven from a source impedance Z_S , assuming that $1/f$ noise is negligible and that the frequency lies well below $f_T/\sqrt{h_{FE}}$. In this equation, q is the electron charge ($1.6022 \times 10^{-19} \text{C}$), h_{FE} the DC current gain factor and r_b the parasitic base resistance of the transistor. The corresponding transconductance equals,

$$g_{m,opt} = \frac{\sqrt{h_{FE}}}{|Z_S + r_b|} \quad (8)$$

and the total contribution to the noise is,

$$S(v_{n,bip,inc,currentnoise}) \approx 4kT \left(\frac{|Z_S + r_b|}{\sqrt{h_{FE}}} + r_b \right) \quad (9)$$


This includes the current noise term, which has been transformed into an equivalent noise voltage across the given source impedance Z_S . The 2SC2545, 2SC2546 and 2SC2547, which are good low-noise low-frequency transistors, have $r_b \approx 14\Omega$ and $h_{FE} \approx 600$.

The input device is driven from a source impedance of about $12\text{k}\Omega$, which is largely reactive. If a 2SC2545 were used here, the resulting values would be:

$$\begin{aligned} I_{C,opt} &\approx 51.56 \mu\text{A} \\ g_{m,opt} &\approx 2.041 \text{mS} \\ S(v_{n,bip,inc,currentnoise}) &\approx 8.158 \times 10^{-18} \text{V}^2/\text{Hz} \text{ or } 2.856 \text{nV}/\sqrt{\text{Hz}} \end{aligned}$$

According to the graphs in reference 3, a high

Fig. 5. Discrete IEC/RIAA amplifier using a low-noise active input resistance. Note that all non-electrolytic capacitors are $\pm 2\%$ ceramic Class I or $\pm 2.5\%$ polystyrene unless otherwise noted. All $\pm 1\%$ capacitors are polystyrene. Don't use Class II ceramic capacitors.

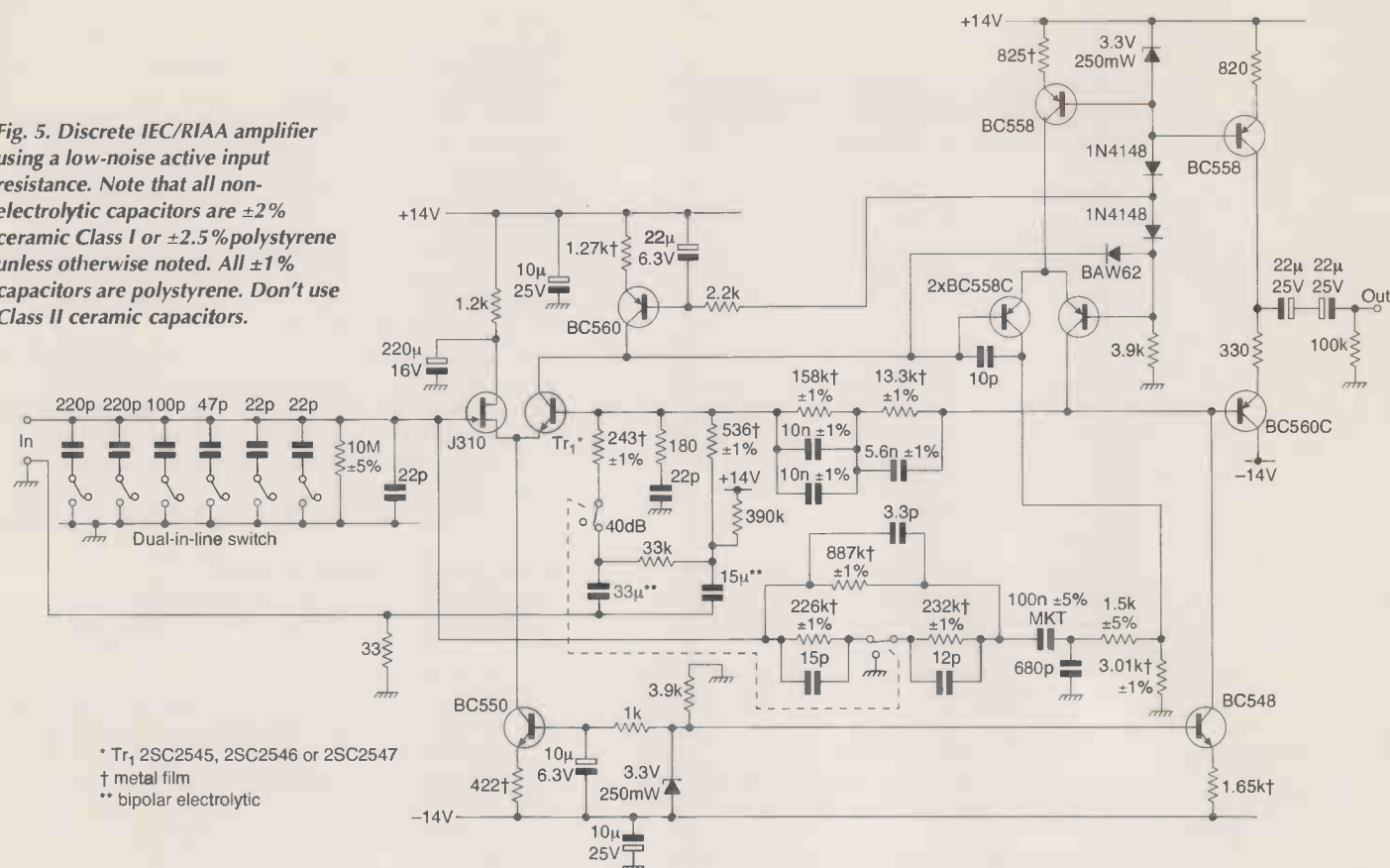

* Tr₁ 2SC2545, 2SC2546 or 2SC2547
 † metal film
 ** bipolar electrolytic

transconductance JFET such as the J310 biased at several milliamperes should be able to outperform this bipolar transistor, having a noise of about 2nV/√Hz at 1169Hz (for a large part 1/f).

At the same time, the JFET provides more transconductance and a better high-frequency behaviour than a 2SC2545 biased at about 52μA. The J310 in Fig. 5 is biased at about 3.3mA. A higher bias current (10mA to 15mA) would be somewhat better.

The situation is different for the transistor driven from the feedback network. In the 40dB gain position, its base is driven from a source impedance of about 165Ω, while its emitter 'sees' the output resistance of the source follower, about 145Ω. This results in a 1.913mA optimal bias current and a 0.6637nV/√Hz total noise contribution. This cannot be outperformed by a single J310 – although it should still be possible with a group of paralleled J310s.

The 887kΩ, 226kΩ and 232kΩ feedback resistors have been shunted with capacitors. This has been done to swamp the few tenths of a picofarad of capacitance associated with a discrete resistor.

The corner frequency lies at about 52kHz. The 680pF capacitor attenuates the voltage on the feedback resistors above 52kHz, eliminating the Miller effect which would otherwise multiply the influence of the capacitances across the feedback resistors.

Gain at 1kHz can be switched between about 30 and 40dB to account for different cartridge sensitivities. The input resistance is designed to be about 3% too low in the 30dB position. It should damp the resonance of the cartridge inductance and load capacitance a bit more than normal, resulting in a small high-frequency loss. This should more or less compensate for the error of +0.37dB at 20kHz caused by the fact that the gain drops to unity rather than zero at high frequencies.

At low frequencies, the maximum output signal level

without clipping is about 16.7V peak to peak, or 5.9V RMS in the case of a sine wave. The tail current of the output stage and the feedback network impedance determine the headroom at high signal frequencies.

The output stage can deliver about 1.33mA peak to the feedback network. In the 40dB position, the resistance between the base of the 2SC2545 and ground is about 167Ω, corresponding to 222mV maximum peak input voltage at high audio frequencies. This changes into 711mV peak in the 30dB position.

To put these figures in perspective: my record player produces peak signal levels of 30mV to 35mV when it plays popular music records with a large high-frequency content, but according to reference 4, peak signal levels up to 100mV can occur at the output of sensitive cartridges playing loud records.

Measured results

Several measurements have been made using an HM1505 oscilloscope with cursors and a $\pm 3\%$ vertical accuracy specification. A 1:1 probe has been used whenever this could be expected to give the most accurate results.

When possible, relative measurements have been made using the same oscilloscope channel to minimise inaccuracies. In most cases, the test signals have been generated with a CD player playing a test CD and with 0.01% accurate resistors to attenuate the signal or to convert it into a current (for the impedance measurements). For the noise measurements, a separate 100 times amplifier and A-weighting filter have been used.

Response when driven from a low source impedance has been measured at 15 different frequencies and compared to the theoretical IEC modified RIAA response. The voltage gain at 1kHz has been measured to be 30.17dB in the 30dB-mode and 40.27dB in the 40dB-mode.

Compared to 1kHz, the response was accurate to within

Table 1. Equivalent parallel resistances at various frequencies calculated from measurement of input impedance magnitude and phase.

Frequency	R _{in} , 30dB	R _{in} , 40dB
1kHz	46.64kΩ	48.85kΩ
10kHz	45.54kΩ	46.99kΩ
15kHz	45.5kΩ	46.76kΩ
20kHz	45.79kΩ	46.3kΩ

±0.1dB for frequencies between 30Hz and 20kHz in the 40dB-mode. With 30dB nominal gain, the response was accurate to within ±0.14dB between 30Hz and 10kHz, and at 20kHz, the measured error was +0.24dB. Theoretically, this should be +0.37dB. At 20Hz, the error was +0.18dB in the 30dB and +0.25dB in the 40dB position, probably due to the relatively large tolerances of the electrolytic capacitors.

The input impedance magnitude and phase have been measured at various frequencies and the equivalent parallel resistance has been calculated from the measurement results, see the Table 1.

Input capacitance is in the order of 30pF at the minimum input capacitance setting – i.e. just the RIAA amplifier, not including the probe capacitance.

A-weighted noise has been measured with a shorted input and with an open input with 30dB and 40dB mid-band gain, in all cases with the minimum input capacitance setting.

The measurements can be about 20% off, because I had to estimate the RMS noise from the quasi peak to peak values measured with the oscilloscope. Besides, the noise

current (open input) measurement has been affected by interference from the mains.

In the 30dB mode, the A-weighted noise at the RIAA amplifier output was – fortunately – 27.67μV RMS with open input and 9.85μV RMS with shorted input. This corresponds to 5.381nV/√Hz and 0.3216pA/√Hz at the input.

In the 40dB mode, the results were 26.83μV A-weighted RMS at the output with shorted input and 43.67μV RMS at the output with open input, corresponding to 4.729nV/√Hz and 0.1638pA/√Hz at the input.

All measured results are reasonably close to the expected values, except for the equivalent input noise voltage, which is higher than expected. With the source of the J310 AC shorted to the input ground, it drops to somewhere between 2.2 and 2.9nV/√Hz in the 40dB gain mode.

Most probably, the unexpectedly high noise voltage is due to the 1/f noise of the J310 being higher than expected.

RIAA amplifier using op-amps

The network in Fig. 4 is not very suitable for implementation with op-amps. After all, an op-amp does not have a pin carrying a current which is equal but opposite to the output (signal) current.

Although it is possible to use floating power supplies to solve this problem⁵, it is much simpler to use a different topology, Fig. 6. A $-R_2/R_1$ times amplified version of the input signal occurs at the output of A2, resulting in an input resistance of $R_3/(1+R_2/R_1)$. I have only subjected this circuit to a functional test, not to measurements. It seems to work fine.

Noise can be slightly reduced by replacing A2 with an ultra-low noise op-amp such as the LT1028, and adjusting its frequency compensation. The LT1028 may need a compensation capacitor between pin 5 and its output when the output signal is fully fed back to the inverting input at high frequencies. The data sheet is not very clear about the required value⁶.

On the other hand, replacing A1 with an ultra low noise op-amp would make the noise much worse. Ultra-low noise op-amps usually have a bipolar input stage biased at a high bias current. This results in a low input-noise voltage density, but also in a high input noise current density.

To make matters worse, they often feature a base current compensation circuit which injects large fully correlated noise currents in the inverting and non-inverting input terminals.

In the case of the LT1028, the input noise voltage is specified as 0.9nV/√Hz, with a noise current of 1pA/√Hz typical at 1kHz⁶. Carefully reading the small print and the applications information shows that the noise current value only applies when both inputs are driven from exactly the same impedance.

In the case of an RIAA amplifier, this would mean that a dummy cartridge would have to be included in the feedback network. Fortunately, there is also a graph of the total noise versus unmatched source impedance, which shows that the actual input noise current is about 3.25pA/√Hz.

With a source impedance of 12kΩ, 3.25pA/√Hz has the same influence as 39nV/√Hz, showing that even a 741 would be better suited for a moving-magnet RIAA amplifier.

How much improvement can be obtained?

As a best-case approximation for the improvement due to using an active input resistance, I'll compare the sum of

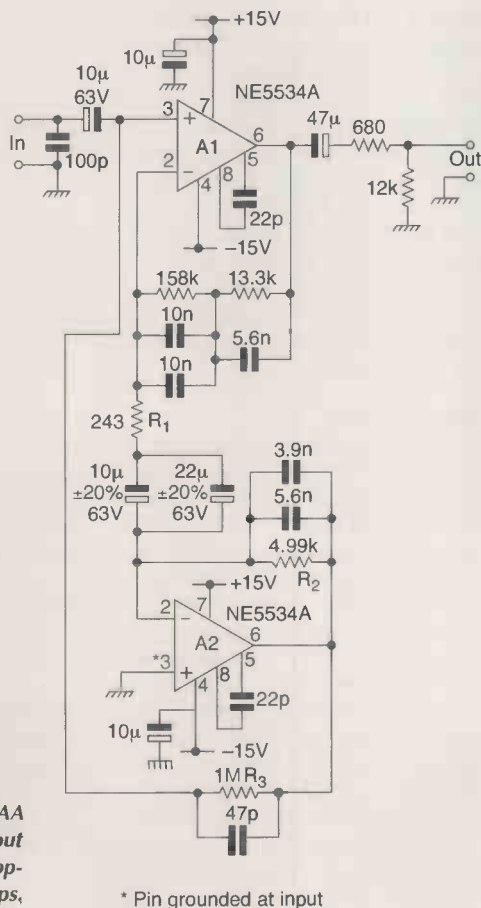


Fig. 6. IEC modified RIAA amplifier with an active input resistance made from op-amps,

* Pin grounded at input

Table 2. Impedance for a Shure V15 III cartridge and for an LR network.

f	Z _{measured}	Z _{theory}	$\varphi_{\text{measured}}$	φ_{theory}	R*	G*	F*	F _{theory}
2kHz	6k Ω	5934 Ω	72°	76.96°	1.85k Ω	51.5 μ S	1.5dB	1.93dB
5kHz	14k Ω	14513 Ω	72°	84.71°	4.33k Ω	22.1 μ S	2.93dB	6.38dB
7kHz	20k Ω	20276 Ω	70°	86.21°	6.84k Ω	17.1 μ S	3.51dB	8.77dB
10kHz	28k Ω	28934 Ω	66°	87.35°	11.4k Ω	14.5 μ S	3.92dB	11.55dB
14kHz	37k Ω	40486 Ω	61°	88.1°	17.9k Ω	13.1 μ S	4.19dB	14.32dB
20kHz	50k Ω	57821 Ω	53°	88.67°	30.1k Ω	12 μ S	4.42dB	17.33dB

*calculated from measured results

the cartridge noise and the amplifier noise for two cases.

The first case is with a RIAA amplifier with the 47k Ω resistor as its only noise source, the second with a RIAA amplifier which does not generate any noise at all.

In both cases, assume that the noise coming out of the cartridge is only thermal noise. This implies that the record player is not playing a record, otherwise there would also be record noise and rumble.

If the cartridge had a frequency-independent effective series resistance, calculating the difference in A-weighted integrated noise level would be easy. For the example of a cartridge with a 1k Ω effective series resistance and 12k Ω impedance at 3852Hz:

Cartridge noise: 4.024nV/ \sqrt Hz

Noise due to 47k Ω : 7.043nV/ \sqrt Hz

Total of the cartridge and resistor: 8.111nV/ \sqrt Hz

Difference between total and cartridge noise: 6.089dB.

However, the effective series resistance of a real cartridge rises with frequency. Richard Vis e⁷ measured the impedance of a Shure V15 III cartridge using an HP4194A impedance gain and phase analyser. The DC resistance and the inductance were 1.3388k Ω and 460mH, respectively. See Fig. 7 and Table 2.

In Table 2, the value |Z_{measured}| is the magnitude of the measured impedance, $\varphi_{\text{measured}}$ is its phase. R is the effective series resistance at a frequency f, while G is the effective parallel conductance. F is the ratio of the thermal noise of the cartridge and a 47k Ω load to the noise of the cartridge alone at a frequency f, expressed in dB.

For comparison, |Z|, φ and F have also been calculated

for a theoretical cartridge with 460mH of inductance and a constant 1.3388k Ω series resistance. Obviously, only the magnitude of the impedance can be reasonably modelled with a simple LR series network.

It is clear that the improvement averaged over the audio band lies somewhere around 3dB, rather than the 6.089dB calculated before.

Similar results have been found for a Marantz cartridge by measuring its A and IEC/RIAA weighted noise using the amplifier in Fig. 5. After correcting for the amplifier noise, this relatively low-impedance cartridge with 349mH inductance and 350 Ω DC resistance turned out to have a noise equivalent to roughly 2215 Ω weighted average effective series resistance. The noise of the cartridge and a passive 47k Ω resistor together would have been 2.27dB higher than the thermal noise of the cartridge itself.

Whether about 3dB best-case improvement is worth the effort depends on your point of view. It will not be immediately noticed by the average user. But then again, it is common practice to try to keep the distortion, frequency response errors and noise levels introduced by audio amplifiers well below the errors introduced in other parts of the audio signal chain or well below the threshold of audibility.

In this way, the final quality is determined by the parts of the audio chain which are the hardest to get right: microphones, loudspeakers, cartridges, the acoustics of the listening room and the bad habit of some recording and broadcasting people to use unnecessarily high amounts of dynamic compression. ■

References

- Ernst H. Nordholt, *Design of high-performance negative feedback amplifiers*, Elsevier, Amsterdam, 1983, republished by the Delftse Uitgevers Maatschappij, Delft, 1993
- Jean M. Hoeffelman and Rene P. Meys, "Improvement of the noise characteristics of amplifiers for magnetic transducers", *Journal of the Audio Engineering Society*, vol. 26, number 12, December 1978, pp. 935...939 and Ernst H. Nordholt, "Comments on 'Improvement of the noise characteristics of amplifiers for magnetic transducers'", *Journal of the Audio Engineering Society*, vol. 27, number 9, September 1979, p. 680.
- Siliconix, *FET data book*, November 1977
- Tomlinson Holman, "Phonograph preamplifier design criteria: an update", *Journal of the Audio Engineering Society*, vol. 28, number 5, May 1980, pp. 325...330
- Ernst H. Nordholt, "Extending op amp capabilities by using a current-source power supply", *IEEE Transactions on Circuits and Systems*, vol. 29, number 6, June 1982, pp. 411...414
- Linear Technology, *Linear databook supplement 1988*, Milpitas, 1987
- Richard Vis e, private communication, 1996 and 2001

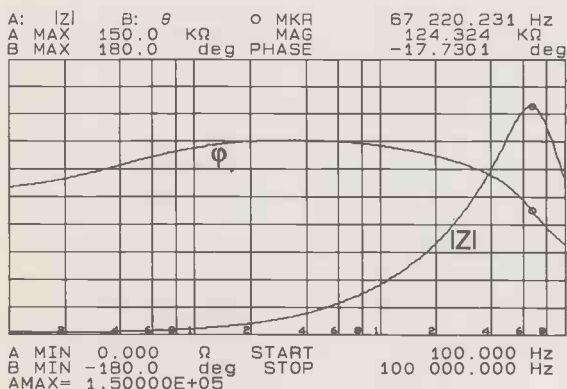


Fig. 7. Magnitude and phase of the impedance of a Shure V15 III cartridge. Frequency scale is 100Hz to 100kHz while the magnitude scale is 0 Ω to 150k Ω and the phase scale is -180° to +180°. The phase hardly exceeds 72° at any frequency.

Simple formulae for skin effect

As Leslie Green explains, although the exact formula for the AC resistance of an isolated piece of wire was developed over a century ago, a modern graduate electrical engineer is not equipped to calculate the resistance of a piece of copper wire to within a factor of three! This gap is filled by some new formulae.

Text books have mentioned the idea that alternating current preferentially flows on the outer surface of a conductor since at least as early as James Clerk Maxwell's 1864 essay 'A Dynamical Theory of the Electromagnetic Field'.

Joseph Henry provided early qualitative confirmation of this preferential current flow in 1876. Lord Kelvin eventually beat the mathematics into submission, solving the second order partial differential equation in terms of a

zero order Bessel function with a complex argument.

It turns out that a Bessel function of complex argument is itself too complicated to immediately evaluate, so Kelvin had to invent a new pair of functions to deal with the problem. The Kelvin-Bessel functions *ber* and *bei*, meaning the real and imaginary parts of a Bessel function, were the result.

A complete expression for the AC resistance of an isolated round wire could then be given in terms of *ber* and *bei*, and

Table 1. The formulae, together with their error limits and range of validity.

Formula	Region	Error — none — definition of skin depth
$\delta = \sqrt{\frac{\rho}{\pi f \mu}}$	all	— none — definition of skin depth
$R_{AC} = R_{DC} = \frac{4\rho \cdot L}{\pi \cdot d^2}$	$\left(\frac{d}{\delta}\right) \leq 0.93$	<0.1% always low
$R_{AC} = R_{DC} = \frac{4\rho \cdot L}{\pi \cdot d^2}$	$\left(\frac{d}{\delta}\right) \leq 1.66$	<1% always low
$R_{AC} = R_{DC} \cdot \left[1 + \frac{1}{772} \cdot \left(\frac{d}{\delta}\right)^4 \left(1 - \frac{1}{1079} \cdot \left(\frac{d}{\delta}\right)^4 \left[1 - \frac{1}{1687} \cdot \left(\frac{d}{\delta}\right)^4 \right] \right) \right]$	$\left(\frac{d}{\delta}\right) \leq 4.7$	<±0.04%
$R_{AC} = \frac{R_{DC}}{4} \cdot \left[1 + \left(\frac{d}{\delta}\right) + \ln \left[1 + \left(\frac{\delta}{d}\right) \right] \cdot \left(0.77 - 15 \cdot \exp \left[-0.645 \left(\frac{d}{\delta}\right) \right] \right) \right]$	$\left(\frac{d}{\delta}\right) > 4.7$	< ± 0.25%
Butterworth's approximation $R_{AC} = \frac{R_{DC}}{4} \left[1 + \left(\frac{d}{\delta}\right) \right]$	$\left(\frac{d}{\delta}\right) \geq 3.8$	< 2% always low
$R_{AC} = \frac{\rho \cdot L}{\pi \cdot (d - 0.955 \times \delta) \cdot \delta}$	$\left(\frac{d}{\delta}\right) \geq 6.8$	< ± 0.2%
$R_{AC} = \frac{\rho \cdot L}{\pi \cdot (d - \delta) \cdot \delta}$	$\left(\frac{d}{\delta}\right) \geq 6.8$	< 1% always high
Butterworth's approximation $R_{AC} = \frac{R_{DC}}{4} \left[1 + \left(\frac{d}{\delta}\right) \right]$	$\left(\frac{d}{\delta}\right) \geq 8.2$	< 1% always low
$R_{AC} = \frac{R_{DC}}{4} \cdot \left[1 + \left(\frac{d}{\delta}\right) + 0.77 \cdot \ln \left[1 + \left(\frac{\delta}{d}\right) \right] \right]$	$\left(\frac{d}{\delta}\right) > 8.6$	< ± 0.04%

*Leslie Green
CEng MIEE

their first derivatives, *ber'* and *bei'*.

$$R_{AC} = R_{DC} \times \frac{x}{2} \cdot \frac{ber(x) bei'(x) - bei(x) ber'(x)}{[ber'(x)]^2 + [bei'(x)]^2}$$

The *x* in the equation contains information about the operating frequency, the wire diameter, the conductivity of the material and the permeability of the material.

'Approximations'

Now Kelvin's formula was useful because the *ber* and *bei* functions, and their derivatives, were tabulated. Furthermore, the overall function was tabulated and graphed so engineers could look up the values and get immediate accurate answers.

Unfortunately all of these texts have been out of print for more than 50 years and are no longer readily available. Additionally, these old books necessarily use an old system of units; conversion from which allows plenty of opportunity for errors.

Kelvin's formula contains mathematics which is too advanced for undergraduate courses, which means that it is not taught. Instead, the graduating electrical engineer is equipped with two approximations, one for 'low frequency' and one for 'high frequency'.

At DC the resistance is given exactly by:

$$R_{DC} = \frac{4\rho \cdot L}{\pi \cdot d^2}$$

where ρ is the electrical resistivity, *L* is the length and *d* is the diameter.

The AC resistance is evaluated using a quantity called the *skin depth*. This skin depth is an *equivalent* depth in the material, where, for the purposes of calculation, one

can assume that the current is evenly distributed throughout this thin surface layer, being zero elsewhere. The skin depth is given by:

$$\delta = \sqrt{\frac{\rho}{\pi f \mu}}$$

where ρ is the electrical resistivity, *f* is the frequency and μ is the (absolute) permeability.

The 'high frequency' resistance of a piece of wire is then given as:

$$R_{HF} = \frac{\rho \cdot L}{\pi \cdot d \cdot \delta}$$

where it is stated that this approximation is only valid when the diameter is 'much greater' than the skin depth.

Suppose you wish to calculate the resistance of a 10mm diameter copper bus bar for use in a power system at 50Hz. Which formula should you use and what is the error in the approximation? The first step must be to calculate the skin depth. For copper we have 17nΩ/m resistivity and a skin depth at 50Hz of 9.3mm.

The DC resistance works out as 0.233Ω/km. The 'HF' resistance works out as 0.0582Ω/km, which is less than the DC value and therefore evidently completely wrong. Of course you could argue with my interpretation of the HF formula. I evaluated the effective cross-sectional area as the circumference times the skin depth. Perhaps it would have been more accurate to use the 'true' cross-sectional current path as:

$$\frac{\pi}{4} \cdot d^2 - \frac{\pi}{4} \cdot (d - 2\delta)^2 = \pi \cdot \delta(d - \delta)$$

giving,

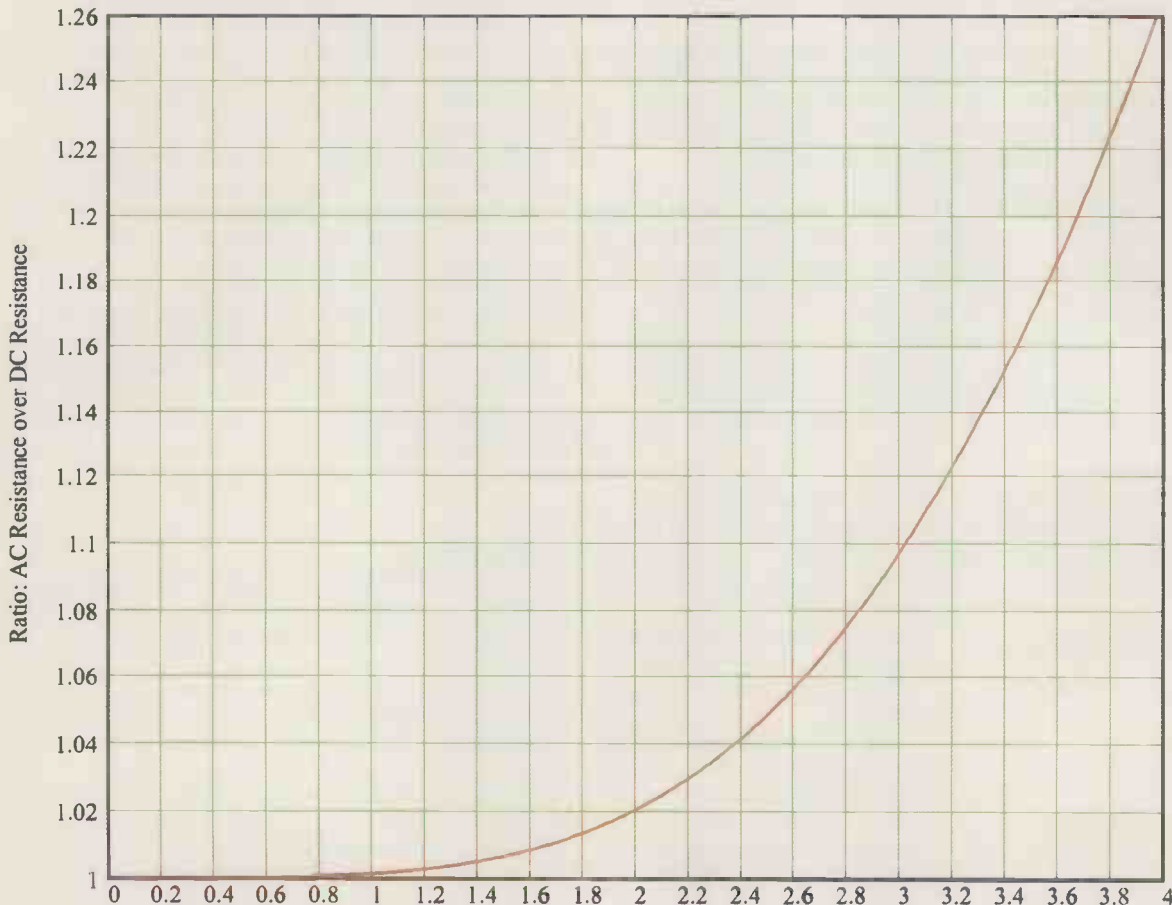


Fig. 1. Graph of the transition region between the low frequency and high frequency formulae.

$$R_{HF} = \frac{\rho \cdot L}{\pi \cdot (d - \delta) \cdot \delta}$$

This revised formula gives the HF resistance as 0.831Ω/km. Among these three 'approximations' we have a greater than 14:1 spread, and we have no way of knowing which one is the best approximation!

Accuracy

No engineering formula or approximation is useful unless its range of validity and error limits are given. Since we have an exact equation for this problem, it is only necessary to evaluate the function numerically and compare the approximations with the exact answer.

The formulae, error limits, and range of validity are best given in a table for ease of comparison and use. See Table 1. Butterworth's approximation, as given in the table, was published in 1921. The two complicated approximations, which between them cover the entire range of possible values, are new.

While the title of this article relates to 'simple' formulae, these two new formulae still qualify on the grounds that they use standard calculator functions, which are also found in mathematical libraries for compilers. This ease of calculation is in stark contrast to the Kelvin-Bessel function formula, which uses functions that can only be evaluated as power series solutions, and which have a nasty habit of causing overflows due to the large factorial numbers used.

If you happen across a table of values of the AC/DC resistance ratio of a cylindrical conductor it will probably be given as function of the variable x , as given in Kelvin's formula. The relationship to the present usage is:

$$x\sqrt{2} = \left(\frac{d}{\delta}\right)$$

It is very easy to make a typing mistake when applying a formula, so a few exact 'check values' of the function are useful. These are provided in Table 2. A graph of the transition region between the low frequency and high frequency formulae is also useful, see Fig. 1.

I have also included a short table of resistivity and skin depth, Table 3. The skin depth is given for 1Hz, so for any other frequency just divide the figure in the table by the square root of the actual frequency in Hertz. Note that all resistivity values are very approximate, since the purity of the specimen affects the resistivity.

The skin depth for iron is considerably more uncertain than for the rest however. The reason is that the relative permeability of iron changes by orders of magnitude according to its purity and its crystal structure.

Errors

It is important to note that when the approximation formulae state errors, these errors are mathematical values derived using the exact formula. Consider the case for the new formula giving errors of less than ±0.04% for $d/\delta \leq 4.7$. The error in the

approximation is so low that the approximation can be considered as exact for all practical purposes.

In a real situation, the tolerance on the resistivity of the conductor is likely to be of the order of several percent at least. Furthermore, the loss resistance will increase when other conductors are brought up close

to the ideal isolated conductor. This increased loss is attributed to further current crowding within the conductor, such additional current crowding being known as the *proximity effect*.

Text books love to simplify the theory of the skin effect in order to make it 'understandable' to mathematically challenged engineers. The problem with these simple explanations is that they can be grossly misleading.

One popular 'theory' for the skin effect says that current does not flow down the middle of a conductor at high frequency because of the increased inductance at the centre of the conductor. This theory is amplified by drawings showing concentric circles of flux around the conductor.

It is then evident that a current filament in the centre of the conductor links to more of these flux lines than a current filament at the perimeter.

It does not take much thought to shoot this 'increased inductance' theory down in flames. The internal inductance of a piece of wire, that is the inductance due to the flux within the wire, is a very small proportion of the total inductance.

The formula is given in all basic electromagnetics text books. And yet this miserably small difference in inductance is supposed to account for the *exponential* drop in current density which occurs in practice. Furthermore, an increased inductance would have the effect of merely reducing the current density.

In reality, any good electromagnetics text book shows that the current density actually reverses a small distance from the surface; that's right, there is a subsurface current flowing backwards! Some simple theories allow teachers to silence their student's questions, but fill the students with incorrect 'facts' that subsequently need to be unlearned.

It can only be hoped that future teachers present the facts, state that the maths is rather hard, and present a graph rather than a formula. Anyone can understand a graph. Showing that there is something more to learn is, to my way of thinking, better than stating that everything is exact and complete.

Earlier in this article the problem was posed as to the exact resistance of a copper bus bar 10mm in diameter at 50Hz. The ratio d/δ is 1.075, so it is clear from Fig. 1 that the increase from the DC resistance is certainly considerably less than one percent.

Using the appropriate new formula, the AC/DC resistance ratio is found to be 1.0017, so the resistance effectively remains unchanged at 0.233Ω/km. Of course 10mm copper bus bars are probably of little interest to you, but I trust that you have realised by now that the 3:1 uncertainty I mentioned when using the previous LF/HF approximations also applies for 1mm wires at 5kHz. ■

Table 2. It's easy to make a typing mistake when applying a formula, so a few exact 'check values' of the function are useful.

0	1.0000
1	1.0013
2	1.0205
5	1.5050
10	2.7681
20	5.2593

Table 3. resistivity versus skin depth.

Material	Resistivity	Skin depth @ 1Hz
Iron	97	10
Copper	17	65.6
Aluminium	26	81.2
Brass	39	99.4
Tin	115	171
Lead	220	236

Further reading

Circular No.74 of the Bureau of Standards: "Radio Instruments and Measurements", 1918.
Principles of Radio Communication by J.H. Morecroft (2nd edition), 1927.
Wireless: A treatise on the theory and practice of high-frequency electric signalling by L.B. Turner, 1931.
Radio Frequency Measurements by E.B. Moullin, (2nd edition), 1931.
Radio Engineer's Handbook by F.E. Terman, 1943.
A useful list of references and formulas for other situations is provided in:
H.A. Wheeler, 'Formulas for the Skin Effect', in *Proceedings of the Institute of Radio Engineers*, 30 (Sept 1942), pp. 412-424.



Electronics World reader offer:
x1, x10 switchable
oscilloscope probes,
only £21.74 a pair,
fully inclusive*

*Additional pairs as part of the same order, only £19.24 each pair.

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74 UK/Europe to **Probe Offer, Jackie Lowe, Highbury Business Communications, Nexus House, Azalea Drive, BR8 8HU**

Readers outside Europe, please add £2.50 to your order.

Please supply the following:

Probes

Total _____

Name _____

Address _____

Postcode _____ Telephone _____

Method of payment (please circle)

Cheques should be made payable to Electronics World

Access/Mastercard/Visa/Cheque/PO

Credit card no _____

Card expiry date _____ Signed _____

Please allow up to 28 days for delivery

Specifications

Switch position 1

Bandwidth DC to 10MHz
 Input resistance 1MΩ – i.e. oscilloscope i/p
 Input capacitance 40pF+oscilloscope capacitance
 Working voltage 600V DC or pk-pk AC

Switch position 2

Bandwidth DC to 150MHz
 Rise time 2.4ns
 Input resistance 10MΩ ±1% if oscilloscope i/p is 1MΩ
 Input capacitance 12pF if oscilloscope i/p is 20pF
 Compensation range 10-60pF
 Working voltage 600V DC or pk-pk AC

Switch position 'Ref'

Probe tip grounded via 9MΩ, scope i/p grounded

47

Measuring Amplifier Distortions

Cyril Bateman continues to describe his improved real-time hardware distortion measuring system

Pre-amplifier and power amplifier distortions, to a maximum of five volts RMS, can be measured directly using my Real Time second and third harmonic distortion analyser described in the July issue, together with my 1ppm low distortion 1kHz generator, buffer amplifier and notch filter preamplifier using a soundcard and FFT software or my ADC-100 AD converter¹. The addition of a simple resistive input attenuator in front of the notch filter, quickly extends this measurement capability to encompass even the highest output power amplifiers.

I seldom need to measure at powers exceeding 100 watts into an eight Ohm load so have assembled a simple, easily replicated dummy load complete with a built in attenuator matching the switchable input voltage ranges of my LC960² cased, Standalone Distortion Meter, which was described in my last article³.

Apart from being able to handle the amplifier output power without

overheating, a dummy load should be totally resistive, exhibiting no significant self-inductance at least for audio frequencies. Special non-inductive resistors are available but these are far too expensive for use by many enthusiasts, so I decided to examine whether a less expensive approach, based on low cost commercial 'aluminium clad' wirewound resistors would suffice. I already had a number of 25 watt 8.2Ω resistors and a 2°C/W heatsink. Mounting two series pairs of 8.2Ω resistors in parallel would reduce their self inductance and mounting on this heatsink would permit measurement to 50 watts which could then be extended up to my 100 watts maximum when needed by using a small 'snail' cooling fan to dissipate excess heat.

The attenuator included in this dummy load would easily connect to the 'V - in' and 'V - low' BNC sockets on my LC960 cased distortion meter, the 'I - out' and 'I -

low' sockets providing the test signal needed by the amplifier under test. Using an 8Ω dummy test load, 100 watts develops some 28.3 volts, 50 watts requires 20 volts and 25 watts just 14.14 volts. Using a simple fixed 7.075:1 attenuator and extending the 50 watts to just 56 watts (21.25 volts) reduces these load voltages to 4, 3 and 2 volts respectively, exactly matching my switchable test levels. Inclusion of one additional low value attenuator resistor would also allow measurements to be made at 50 watts when needed.


Exploratory measurements using one of my elderly laboratory workhorse Maplin Mosfet 100W amplifier modules confirmed this approach would be more than satisfactory, so I proceeded to build a permanent attenuator/dummy test load for routine use with my LC960 cased standalone distortion meter, described in my last article³. Fig. 1.

Experimental circuits

Measuring experimental low level circuits and pre-amplifiers requires a different approach. In the past I have used my uncased test generator and notch/filter assembly with the FFT software to measure experimental circuits assembled on plug in proto lab boards, but this arrangement poses considerable difficulties with mains pickup. Also the proto board circuit assemblies are easily and unwittingly disturbed. I decided to use a small die cast box to contain my circuits, which would solve the mains pickup problem. Mounting my designs on an easily re-configurable PCB would make for an easily adapted but stable test system.

Mounting four short BNC cables at 22mm centres, to match the front panel of my standalone distortion

Fig. 1. The Real Time hardware system assembled into the low cost LC960, a 250 x 180 x 100 mm case as described in the September issue, is shown using my dummy test load/attenuator to measure the distortions produced by my Maplin Mosfet 100W amplifier.

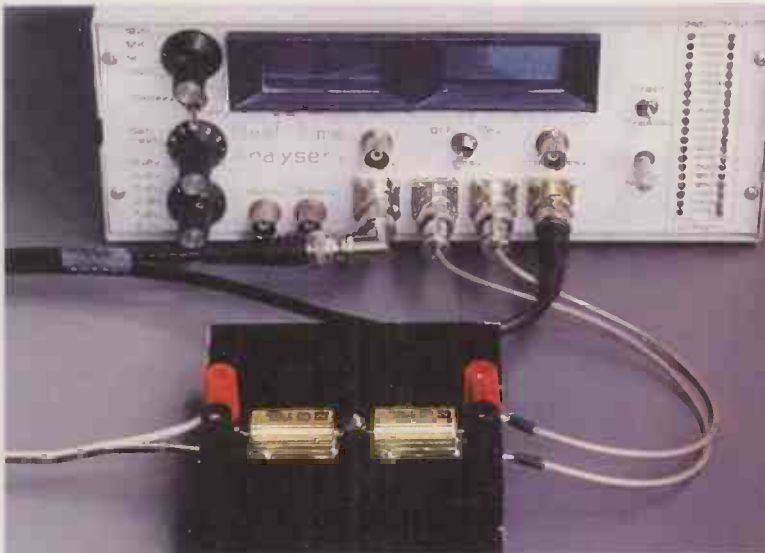

meter, along one side of a die-cast box, would facilitate the required connections and ensure a repeatable, consistent test method. This boxed PCB would include its own power supply three leg stabilisers and a power switch, disabling the circuit to allow change of components or integrated circuit. All ICs would be fitted in turned pin sockets and resistor and capacitor components which may need changing, would be soldered onto Vero pins, accessible without dismantling the PCB from the test box, facilitating experimental circuit changes. Fig. 2.

I decided to provide for two amplifier stages, similar to the two stage output buffer used in my test equipment, to allow experimental verification of performance especially when driving into low impedance loads. Replacing the second amplifier with a DIL header which has its pins three and six shorted together, would permit comparison measurements of single IC performance against the same amplifier with separate output buffer, all without changing this PCB layout. Fig. 3.

Because many readers prefer to use dual IC amplifiers to save space and cost, I provided a second similar two IC PCB which used a dual amplifier for the first stage. While this alternative board could be quickly exchanged in the box by unsoldering a few wires and removing six nuts, I decided it would be simpler and better to assemble this alternate PCB into a second die cast box, the small extra expense being quickly recouped by saving much time when comparing and designing just a couple of circuits. Fig. 4.

The input amplifier for both PCB variants can be arranged either in non-inverting or inverting mode simply by changing a couple of link wires and resistors. Additionally a capacitor-coupled input with variable level potentiometer can also be quickly linked into circuit when desired. This flexibility allows many different circuit configurations also performance comparisons between different ICs. For this reason space



Fig. 2. The four BNC connectors mounted at 22mm centres, provide true four terminal measurements, isolating the test current from the voltage being measured. These enable a quick change from measuring capacitor distortions to evaluating low power amplifier circuits, simply by change of test jig as shown, with no change of the distortion meter internal circuitry.

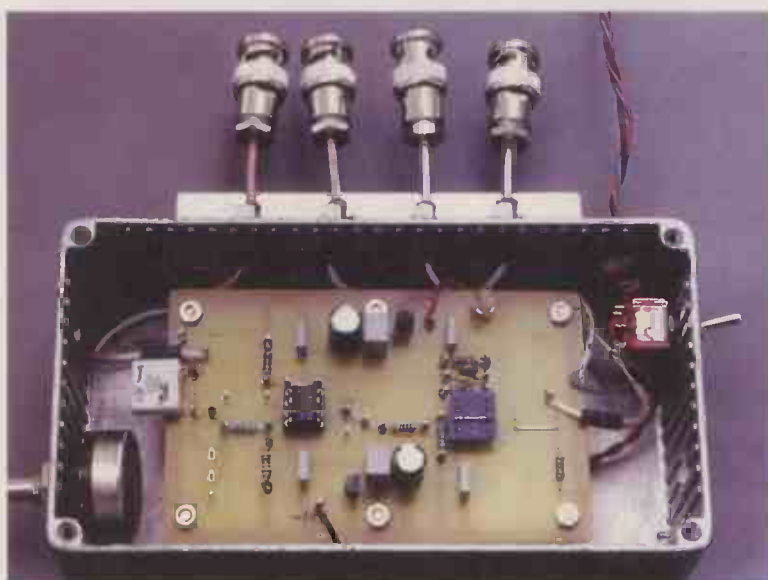


Fig. 3. Using a simple adaptable printed circuit board with components mounted on Vero pins permits change of circuit configuration as well as component values, without access to the track side of the PCB. The DIL header connecting pins three and six in the right hand op-amp position as shown, permits evaluation of single stage circuits, easily extended to two IC stages, by replacing the DIL header with an IC as in figure 4.

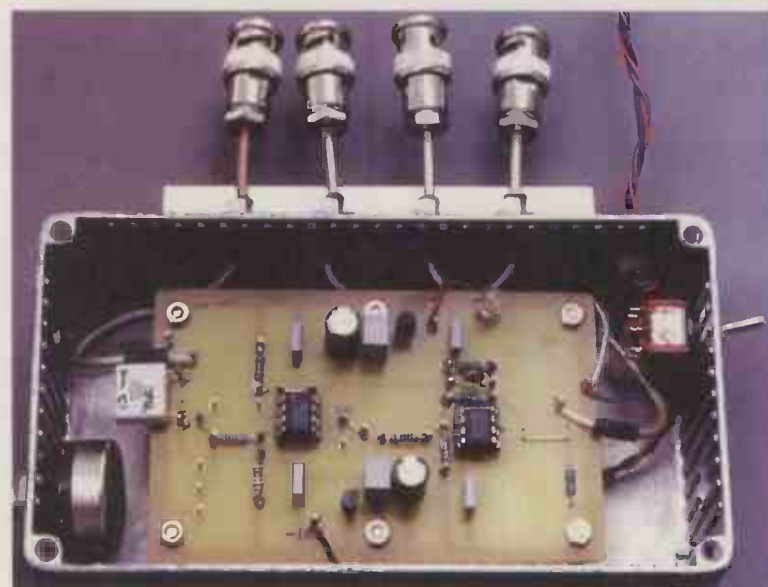


Fig. 4. The figure three PCB but now arranged as an amplifier with an output buffer IC. The potentiometer, bottom left allows measuring the differing distortions produced by both inverting and non-inverting variable level voltage followers.

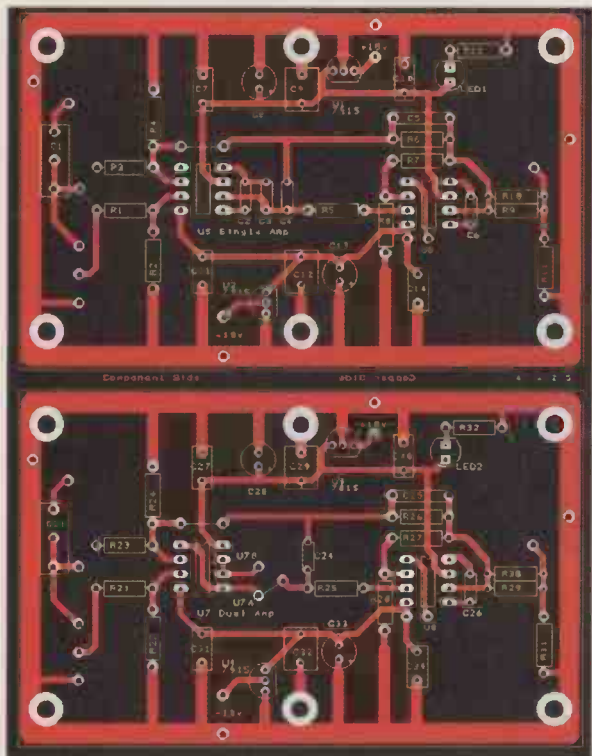


Fig. 5. I designed two PCB versions, the top version accepts a variety of single op-amps, and provides mounting positions for the 50pF capacitor needed for the AD797 also the 22pF needed to allow using an NE5534 at unity gain. The lower circuit board is similar but allows using a dual op-amp either as a single or two stage amplifier with or without a separate output buffer stage.

has been provided for the 22pF capacitor from pin 5 to pin 8, needed when using an NE5534 at unity gain, also the 50pF capacitor from pin 6 to pin 8 when using an AD797 IC. Other options allow using a BUF634P as the output stage as well as the AD811 used in my test oscillator output buffer. No doubt readers will think of many other variations they would like to incorporate for their own experiments. Fig. 5.


Use with Uncased test modules

Perhaps you are happy to use my test equipment as a number of uncased modules, assembled on your workbench, exactly as I did for all published measurements, prior to my September 2003 issue article. These test box methods and power amplifier dummy test load approaches are equally valid when using my uncased test modules.

The general procedure was described in earlier articles, the user manual supplied with my PCBs as well as in my CD ROM. When testing capacitors the test signal output from the buffer amplifier is connected to the notch filter input via the capacitor test jig. When measuring amplifiers this common connection must be broken, the test signal being sent to the amplifier input and the notch filter connected to the amplifier output.

This is easily arranged by turning the 'switch41' fully anticlockwise to the AOT position, having first removed any resistor from the R77 position. The test signal is sent to the test amplifier input using a short length of coax cable connected to the

Fig. 6. The test arrangements shown for my LC960 cased distortion tester can equally be applied to the original bench top assembly of discrete modules, as shown.

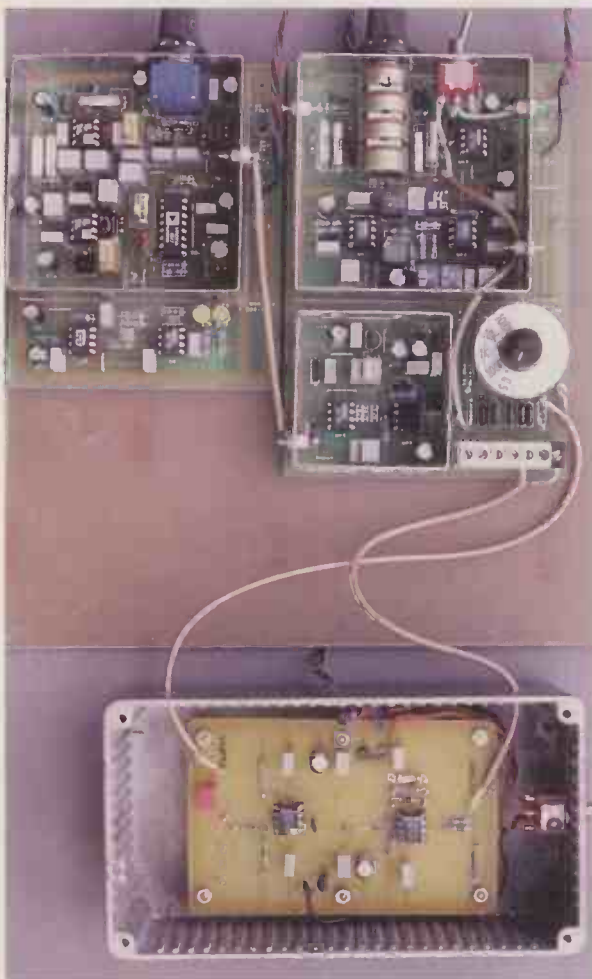

R77 resistor Vero pin nearest to 'switch41'. The test amplifier output, is connected to the capacitor test jig using a second coax cable. This general arrangement is clearly shown in Fig. 6.

Amplifier Dummy Load

Four 25 watt 8.2Ω aluminium clad power wirewound resistors were connected as two pairs in series and parallel to provide a 100 watt capable low inductance 8Ω dummy load. One pair of resistors was mounted above the heatsink using thermal paste as shown in the photo, the second pair beneath the heatsink, so are not visible. Also underneath the heatsink are fitted the attenuator resistors needed to reduce the test amplifier output to match the 0.5V, 1V through 4V test levels provided in my LC960 cased, standalone Real Time test system. For most purposes using a simple single stage attenuator to measure amplifier powers of 1.5W, 6.5W, 25W, 56W and 100W would suffice, however adding one extra attenuating resistor and output contact as in my photo, visible between the two 8.2Ω resistors, provides also for measurements at 50W. Fig. 7.

I said earlier that a dummy test load ideally should be non-inductive. To ascertain the behaviour using these two pairs of series/parallel 8.2Ω aluminium clad commercial 25W wirewound resistors, I made a series of impedance measurements by frequency using the method described in my SMPS capacitor article⁴. From 1kHz to 100kHz the impedance increased by less than one decimal place, from 8.02Ω to 8.06Ω, less than 0.5%. At 1MHz the impedance increased to 9.94Ω indicating my dummy test load's self inductance was slightly less than 1μH at audio frequencies.

A simple attenuator was assembled using three 1kΩ 1% 1W resistors in parallel to drop the excess voltage, then through the 2.7Ω compensation resistor needed when measuring amplifiers at 50W into a 56Ω tail resistor. The measurement voltage being taken across this 56Ω to earth for all measurement except for 50W, when the output is taken from the junction of the 2.7Ω and 1kΩ resistors. In this way we only need to adjust the test levels to match our 0.5V, 1, 2, 3 and 4V switchable test levels to measure at the desired

amplifier power. Fig. 8.

As can be seen, I have provided two ground returns into the standalone distortion tester, one for the test current input to the test amplifier, the second for the attenuated amplifier output voltage, both grounds are of course commoned inside the distortion meter. Depending on the earthing details used for the amplifier under test, lower distortion meter readings may be obtained if both grounds on the heatsink are commoned, and the I-low ground to the tester is not used. This has not been found necessary for my tests, both earths having been connected exactly as shown in figure 1.

How does this work in practise?

Using a conventional notch filter THD distortion meter requires a certain delicacy of touch to first set the correct gains or test voltage levels, then more importantly to ensure optimum nulling of the test fundamental, which using my HP331A distortion meter can take several minutes. During this time the amplifier must continue producing the desired power level. Even when testing at only 25W both amplifier and dummy load can become hot.

Because of the excellent stability of my test oscillator and notch filter after a short warm up, having once carefully matched the notch filter tuning to the test oscillator, further tuning adjustments are not needed. This notch filter tuning adjustment is easily performed when using the capacitor test jig. Simply monitor the AC voltage at the 'Harmonics out' front panel BNC socket and slowly adjust the notch filter tuning potentiometer so as to attain the lowest possible voltage.

With my Real Time second and third harmonic distortion method, measurements at a number of amplifier power levels can be performed very quickly, simply select the desired test voltage range and adjust the test level control. A matter of a few seconds only of amplifier power is needed for each measurement, reducing the possibility of amplifier damage through overheating, even when testing inadequately heatsinked amplifiers. Much quicker and far easier than when using my conventional Hewlett Packard distortion meter.

Bi-polar electrolytics

In my article about aluminium electrolytic capacitor distortions⁵. I recommended using bi-polar and even two bi-polar types in series, which for convenience I labelled as a 'double bi-polar series pair' (Patent application GB0227606.1), in place of a conventional polar capacitor to reduce distortion.

Using the workhorse Maplin Mosfet 100W amplifier mentioned above, I performed a quick experiment to confirm the improvements gained. Originally this amplifier was built using bi-polar aluminium electrolytic capacitors for both its 10 μ F input coupling and the 47 μ F in the negative feedback loop. I replaced these and both power supply rail decoupling capacitors with new polarised aluminium electrolytic capacitors, as originally specified in the parts list. With its bias current carefully reset to the recommended 100mA, I measured its distortion. Built using the Maplin capacitor types, its measured second harmonic was -81.5dB and -91.4dB third harmonic when tested at 25 watts, confirming the design did meet its claimed less than 0.01% distortion.

I then replaced these four polar aluminium electrolytics, with the same value and voltage bi-polar types and re-measured distortion at 25 watts. For both tests the power supply used was built using two 10,000 μ F 63V conventional polar aluminium electrolytic capacitors.

With bi-polar capacitors in the module only, second harmonic improved significantly to -92.1dB and third to -94.3dB, a three fold improvement in distortion gained by using four bi-polar capacitors, a total cost of £2.10, to now measure just 0.0031%. No doubt replacing the remaining capacitors, especially the metallised PET items specified for this design with better types and replacing the input bi-polar electrolytic with a good film capacitor would further reduce this amplifier's measured distortion. These additional changes require modifications to the printed board layout, so have yet to be tried. No doubt redesigning the power supply to also use bi-polar electrolytic capacitors would further reduce measured distortions.

Distortion measurements

The conventional notch filter style

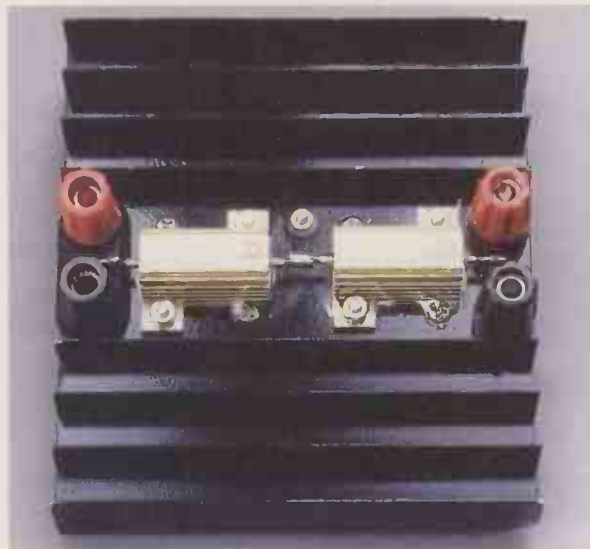


Fig. 7. The dummy load/attenuator shown was built to match my LC960 cased test meter's switched test levels, enabling distortion testing at 1.5, 6.5, 25, 50 and 100 watt amplifier powers. This attenuator and two of the four 8.2 Ω load resistors used are mounted on the underside of the heatsink, so not visible in this photo.

distortion meter provides a single measure of distortion, including circuit noise which can be significant when using a wide measurement bandwidth. To clarify whether second or third harmonic distortion is dominant requires using an oscilloscope to identify the distortion meter residuals. At best this can only

Technical support

Full details of this new hardware test method and my original Capacitor Sounds series 1ppm low distortion oscillator, buffer amplifier, notch filter/preamplifier and DC bias assemblies, together with parts lists, assembly manuals and full size printed circuit board drawings, all as .PDF files arranged for easy viewing on screen or hardcopy, are provided in my new 'Capacitor Sounds' CD.


This CD ROM includes updated and much expanded re-writes with very many more figures, of my recent series of six 'Capacitor Sounds' articles, supported now by some ninety capacitor distortion measurement plots. Also on the CD are PDF re-writes of my earlier 'Understand Capacitors' series together with articles on how to diagnose failed capacitors while still mounted on printed circuit boards and essential low cost capacitor measurement methods, more than twenty popular articles.

The CD is now available, cost £15 Sterling including post packing. Send cheques or postal/money orders in Pounds Sterling only to:-

C. Bateman.

'Nimrod' New Road. ACLE. Norfolk. NR13 3BD. England.

Fig. 8. Schematic of my non-inductive dummy test load and the resistive attenuator used with my LC960 cased distortion meter. The four 8.2Ω resistors are standard commercial 25W aluminium clad wirewound, the three 1kΩ were 1% 1W metal film types and the remaining resistors were 0.5W 1% metal film.

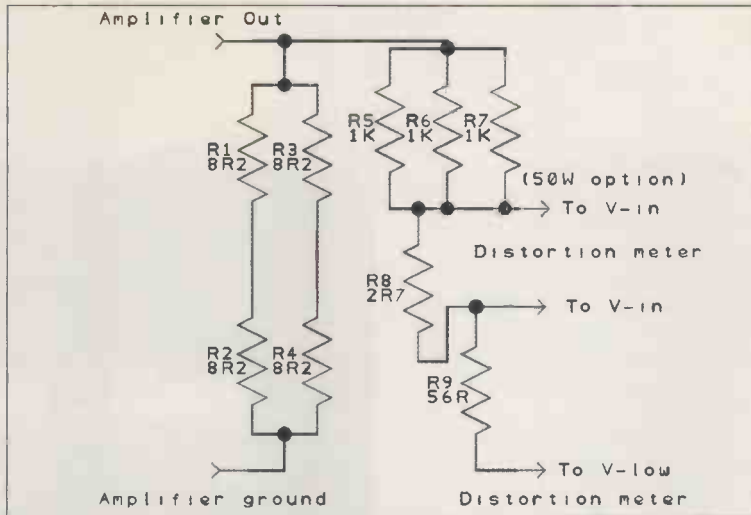

become an educated guess.

Using my Real Time method, the exact levels of second and third harmonic are directly indicated on the panel meters. By also using the ADC100 or computer soundcard and FFT software to monitor the front panel 'Harmonics out' BNC connector, other harmonics and intermodulation products can be measured together with total distortion with and without noise levels as desired.

The main disadvantage of my equipment may be seen as its fixed frequency when compared to some commercial instruments having comparable low distortion performance, but even second hand, these commercial distortion testers will be at least 25 times more expensive than building my published designs and vastly more complex in use.

I know of no commercial distortion measuring instruments that provides

similar DC bias facilities, usable when testing either amplifiers or capacitors. For this reason a number of amplifier designers of repute have recently replicated my test instruments.

In my next article I explore using this equipment to look more closely into capacitor implications in amplifiers and to measure distortions in I.C. amplifier circuits. ■

References.

1. Capacitor Sounds. C. Bateman, *Electronics World*, July, September, October 02.
2. DIL/C-1 Electronics, Holland. email to dil@euronet.nl
3. Capacitor SoundsII. C. Bateman, *Electronics World*, September 2003.
4. Evaluate capacitors for SMPS designs. C. Bateman, *Electronics World*, September 2000.
5. Capacitor Sounds. C. Bateman, *Electronics World*, January 2003.

High Resolution Oscilloscope


- High speed, 5GS/s dual channel oscilloscope
- 50MHz, 80dB dynamic range spectrum analyser
- PicoScope & PicoLog software supplied FREE
- Plug into any desktop or laptop PC
- High resolution - 12 bits
- Large 128K memory
- 1% DC accuracy

NEW
Product
Range



Request your FREE Test & Measurement catalogue and Software & Reference CD, or visit our web site:

www.picotech.com/scope123

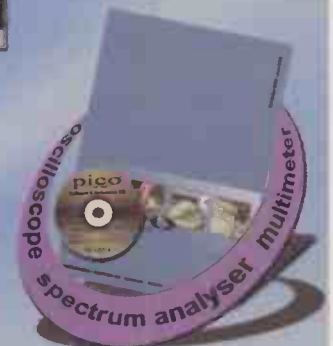

PICO
Technology Limited

Tel: +44 (0) 1480 396395 Fax: +44 (0) 1480 396296 E-mail: sales@picotech.com

LETTERS

to the editor

Letters to "Electronics World" Highbury Business Communications,
Nexus House, Azalea Drive, Swanley, Kent, BR8 8Hu
e-mail EWletters@highburybiz.com using subject heading 'Letters'.

Easy job?

I read with interest Ian Hickman's preface to the July edition of *Electronics World*, and being a contract electronic design engineer for the last 20 years, whose work environment was dealt a double death blow (GSM and 3G hit the buffers in 2001, followed by the aircraft industry after September 11th), I now work as a factory maintenance electrician for a local company.

My main criticism with Ian's piece is his assumption that his future son-in-law "given a few days study of the latest edition of the IEE Wiring Regulations, could probably make a comfortable living at the trade". This is, I feel, misleading at best and could have people who are out of work in the electronics and software industries thinking it will be an easy way to get a job. After spending the last two years collecting an armful of certificates and work experience, I am only now approaching the point where I can apply for a Joint Industries Board (JIB) card. Without this card, the majority of electrical contractors will not even interview you, let alone set you on. As an alternative, he could set up his own business as an electrician. Great, this works fine until he comes to the question of company and public liability insurance. The first question the insurance company asks is 'How much experience have you in this industry. (Are you getting my drift yet?) It is because of the (apparent) risk, the insurance will (of course) cost a large four figure sum, probably more than the work will generate - not a good position to be in. (exactly the same reason that the electrical contractors aren't interested!!). If he decides to work without insurance, then remember that the first time he makes a mistake, the 'no win, no fee' lawyers are always looking for clients, particularly with what they deem as a 'soft target' - hence the insurance.

Sorry if I seem to be discouraging what is probably a quite able and competent person from filling a gap in the skills shortage, but I think that it must be quite a few years since Ian last looked at the electrical trade. Like all other trades (plumbers, gas fitters, etc.) the electrical industry is trying to rid itself of 'cowboys'

and, as such, does not easily accept anyone who has not come the traditional route through a trade apprenticeship. In addition, I have found that you need to be able to do a great deal more than read and interpret the regulations, particularly when it comes to practical installation and trade tests. However, on the bright side, if you would like information on how you can get through the maze, let me know (Davev@davroengineering.co.uk) and I will forward you a list of requirements put out by the National Electro-technical Training Scheme (NETS). Also, if you can get any job in the electrical trade, this will help enormously when you need to start amassing an 'evidence' file to back up the qualifications.

Dave Wroe BA (Hons), C.Eng., MIEE, MIDiagE
By email

Technicians

I read with interest the critique by Bob Nelson (*Electronics World*, Letters - June 2003). He stated that not enough high-level technical articles are being published in *Electronics World*. Perhaps you should try to attract people at different levels, from hobbyist to professional. Also periodic tutorials on different topics could be included, such as op amp, digital, and industrial electronic controls. Many readers may want more articles on electronics in industrial automation, robotics, and interfacing with programmable logic controllers (PLCs). Automated inspection with lasers and electronic eyes, motor controllers, interface electronics for flow control (hydraulics and pneumatics), and computer numeric controlled (CNC) machining are especially important. I don't know what other publications in the UK or Europe cover this, but industrial machine automation is especially important to a nation's technical and economic standing. You should also cover the state of the electronics industry both in the UK and in other countries. Especially important are employment levels, different careers in electronics, and training programs. Such articles would be valuable for those with children at an age to decide on a career path. In the past, engineers

Hard times

With reference the article *Hard times* by Ian Hickman, he refers to the fact that software engineers are going through a black patch with regards to employment. He also suggests that his son-in-law who is a software engineer and finds himself in this position takes up employment as an electrician suggesting that his son-in-law has an appreciation of just dangerous 240V not to mention 415V three phase can be.

He also suggests after a few days study of the IEE regulations he could make a comfortable living at the trade. As a retired electrician he would require a little while longer than that.

He refers to the shortage of skilled men in various trades - electricians, plumbers and welders. He also refers to our unbalanced education system with politicians of all shades wanting everyone to finish with a degree resulting in many people finishing with 'Mickey-Mouse' degrees.

Another view is that not many young people today are willing to get their hands dirty doing something whichever way you look at it can be a dirty job!

Brian Corbett
Oldham
Lancashire UK

were usually the people emphasised.

Now technicians and technologists are assuming more of the high-level design and implementation traditionally done by engineers. In America, the two-year associate's degree from a community college or state technical school is becoming ever more important. Associate level programs are offered in a variety of technical options, including electronic engineering technology, robotics, advanced manufacturing, and quality control. Topics covered in great depth include analogue, digital and

Self powered amp

In Doug Self's article 'Power amplifier input currents and their troubles' he mentions using FETs instead of bi-polars to reduce input current non-linearities in the power amp. One way to use them is to cascode the difference amp with the base bias of the cascode transistors taken from a voltage divider between the output and a DC bias source, so as to track input and feedback. This might get rid of the main source of capacitive non-linearity in the difference amp stage.

William C. Cross
Denver
Colorado
USA

microprocessor systems, programmable logic controllers, fluid power control, and semiconductor manufacturing technology. When Congress passed the \$125 million TECH PREP training bill in the early 1990's, it stated that America's technical leadership depends more on technicians than engineers. As *Fortune* magazine (August 22, 1994) stated in the feature article "Technicians - The New Worker Elite", as companies rely on technology to improve product quality, technicians are the front-line workers they depend on. Also, some four year bachelor's degree programs in industrial technology cover industrial electronic controls, as well as robotics and computer aided design and manufacturing (CAD/CAM). Technicians and technologists serve as the important link between high-level design and world-class quality factory-floor manufacturing. Perhaps *Electronics World* could cover both the Associate's degree options in America and the HNC programs in the

Electronic Balun

Referring to Ian Hickman's "An Electronic Balun" article in the June 03 *EW*, putting in C3 (and C4) in Fig. 2 introduces an asymmetry that degrades the CMRR at high frequencies. Presumably it is introduced to limit the bandwidth and improve the stability margin. You can restore symmetry by bypassing R11 and R14 with 100pF caps.

David Hadaway

By email


With regards to Ian Hickman's electronic balun article, I have an alternative solution: It is well known that Ota's differential input is converted in single ended at the output with good common mode rejection without any need to carefully match resistors.

For example, adding two resistors to a circuit idea of September 2002 (2 channels one gain pot), you obtain a stereo balun with some 60 dB CMRR and a very low distortion. The gain of each LM13600 goes from 0 to 900 when the command voltage is varied from -15 to +15 volts.

Jean-Marc Brassart

SAINT-LAURENT-DU-VAR

France

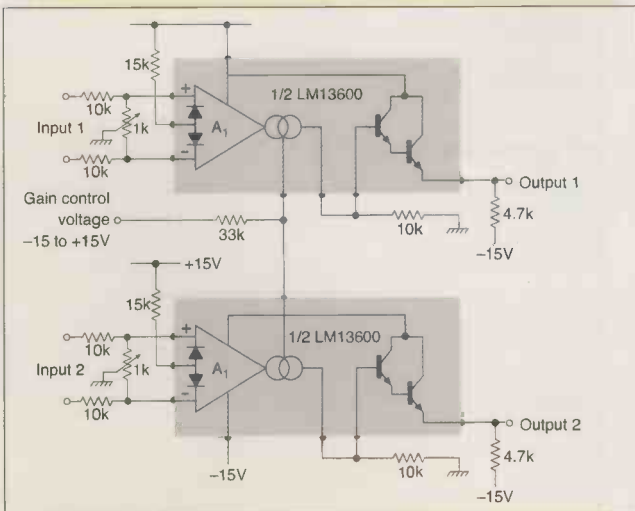

UK. Different specialties (computer, automation systems, communication) could be included. Some magazines are too oriented toward computers or internet technology. A broader coverage would attract more readers.

Glen W. Spielbauer

Dallas,
Texas
USA

Another pile of good ideas to put into my melting pot. Ed.

In circuit RF measurement

When I saw the third page of the article by Tuck Choy in *EW* July 2003, I was surprised at its low standard. I decided to write a proper article on capacitor-diode RF voltage measurement based on a correct mathematical solution to the relevant equations and a C-programming language program to calculate the correct DC output voltage, none of which I have seen published before.

I then noticed that Tuck Choy had used an incorrect equation taken from Wes Hayward's *Introduction to radio frequency design*. Wrong in Hayward and just copied in your issue; is this plagiarism any way one spells it?

Next I noticed that you ridicule 'hand written letters' on page 56 of the same issue. What now am I to do with hand written original work not wanted by you but technically useless printed work copied from Wes Hayward's mistake is acceptable to you?

William Coughlan

Dublin
Ireland

The point I was trying to make about hand-written material is that mistakes can and will occur. It also takes a lot longer to get a handwritten contribution on the printed page as it has to be typed in (usually by me). As regards accepting hand-written feature contributions - that's fine, but the remuneration will be less as it costs me more to get it in the magazine and it will take longer to get it published as rather than relying on fast email - the printed page and 'snail mail' will have to be used instead. But surely one could toddle off to the local library, type it into a computer and email it? In any case, send it in. Ed.

Tuck Choy replies:

Regarding the 'error' - I'm not sure what William means, if it's the factor (-1) then the exponential prevails. The diode equation at high frequencies contain much more of course. For details of an equivalent circuit, see S.M. Sze "Physics of semiconductor Devices".

The allegation of plagiarism is a very

serious one to be put in print. I happen to be acquainted with Hayward and he has not complained to me so far. In any case the formula and its related derivations are found in many standard texts. No one owns the diode equation nor any one equation for that matter. If Einstein owns $E=mc^2$, then many many more people would have been in trouble for plagiarism!

Measurements using Slotted Lines

Congratulations on the very fine July 2003 *EW* article! As both a professional engineer and a radio amateur since 1952, I passed the majority of my professional career, i.e. 37 years, at the laboratories of the Belgian state broadcasting institute, formerly NIR/INR later BRT and now VRT for the Dutch speaking part.

Although my lab occupations at the beginning were strictly low frequency (recording lab from which I became Laboratory Chief in 1963) as my interests as a radio amateur shifted in the early sixties away from the HF bands to VHF and UHF, I spent a lot of my spare time in the microwave labs of my friends at the institute. Later on as I became Laboratory Group Leader, I also had the responsibility over the radio studios and our mobile recording vans, in which VHF/UHF equipment was used for communication. So I could use my experience on VHF/UHF from my hobby for my professional job.

In the early seventies I had the opportunity to buy in a local Ghent surplus store a General Microwave Corporation (Farmingdale USA) coaxial slide screw tuner type N253. This serves normally to correct a high SWR by moving on a carriage along a slab type coaxial line a capacitive acting mass from which the distance to the centre conductor of the line can be varied with a micrometer-gauge.

The instrument is similar in construction to Hewlett-Packard slotted lines 805 C and General Microwave N200. This type of construction, side plates of approximately 115 mm wide, spaced at ± 20 mm, has many advantages over classic 'slotted lines' as the one described in the *EW* article. To quote an old HP catalogue "This configuration results in negligible slot radiation, minimum sensitivity to variation in probe depth or centering and greater structural stability" (as the backsides or outsides of the 'slabs' are reinforced by ribs.)

I soon modified my slide screw tuner into a real slotted line. The carriage travel is ± 350 mm, the vernier reads to 0.1mm, so the usable frequency range is about 400 to 4000MHz. I modified the set as follows: The micrometer drive serves for the capacitive probe penetration (a thin silver brazing rod passes through a slide

contact near the grounded edge in a half-wave resonator tuned at the centre by a capacitive plunger from about 1280 to 2500MHz. The probe is isolated for UHF from the micrometer gauge above it by some ferrite beads.) The other grounded side of the $\lambda/2$ line has a BNC socket on which a homemade Schottky-barrier diode detector is seated.

I do have much experience in mechanical engineering, as one of my uncles had a well equipped workshop nearby with six lathes, three milling machines, four planing machines, etc. etc. in which I spent great part of my summer holidays.

Later we had a small workshop at the recording lab including a Myford Super 7 Lathe and grinding machine, etc.

So the authors of the *EW* article must have had an very well equipped machine shop, far more sophisticated than my laboratory possibilities at the time. They chose for the construction of a very difficult project: drilling a very long precise hole in the axis of a 300mm long brass square and cutting a precise slot in it, etc. Sincere congratulations to their work! The slab type slotted line is much easier for home construction. I started constructing one for VHF (slabline with two large aluminium square U profiles) but never finished it because of its bulkiness and other measuring apparatus with more possibilities (antenna analysers from Bird and/or MFJ.)

Originally I made my 1296MHz measurements using a second hand General Radio 1021-AU HF generator (250 MHz -960 MHz, piston type attenuator < 0,5 micro volts to 2V) succeeded by a diode frequency tripler and a homemade coaxial cavity.

For the readout instrument I constructed along the lines of *Ham Radio Magazine* October 1970 "The SWR Meter" (p6 to 14 incl.) using European transistors instead of the original American, a square law reading peaked 1kHz microvoltmeter with a sensitivity of 0.15 microvolts, with attenuators seven steps of 10dB. This with the help of "DATA" publications and a Philips transistor curve tracer. I had also much help from a later *HR* article - May 1977 "How to use the slotted line for transmission line measurements".

Later I constructed a simpler SWR indicator in a small die-cast box ("Wide range power meter" *HR* April 1986) using some op-amps as a tuned amplifier with HSCH-3486 Schottky barrier diode.

I also constructed two small VCO units following another *HR* magazine article from July 1985. This uses a pair of BFR 93s in push-pull for 880 to 1350MHz and a pair of BFG 65s for the VCO for 1.6 to 2.5GHz. The VCOs are tuned by a variable emitter voltage from -1 to -11V. For the 2.5GHz unit I had to use thin Rogers RT duroid, the lower frequency unit uses ordinary G4-1.5mm epoxy. Each VCO is

followed by a MMIC amplifier from Minicircuits, which can be fed by +12V or a square-wave at 1kHz from a 555 timer-oscillator and a pass transistor. Both include small attenuators to isolate the VCOs proper, to stabilise the MMIC and also attenuators before the 'device under test'. Output from the small devices is 0.5 to 0.8mW at the lower tuning frequency and around 1.5 (1.3GHz VCO) to 4mW from the 2.5GHz one flat ± 1 dB between 1GHz and 1.3GHz respective 2 to 2.5GHz. The phase noise is high, about -40dB as seen on a spectrum analyser, but they are satisfactory for wide-band

measurements such as antenna-alignment, insertion loss of coaxial cables, isolation of coaxial switches, wideband preamps etc. The power and readout unit contains in a die-cast box fixed supplies for +12V, variable ones for -1 V to -12V for the VCOs (10 turn helipot plus LM337T), +2 to +30V for the tuning voltage of transistor GDO units tuned by vari-caps (10 turn helipot + LM317 T), a small DVM for readout of tuning voltages plus a small meter for GDOs with DC-amplifier, the 555 oscillator, etc. This construction from 1985 I baptised 'The UHF- tester'.

I used extensively the information of

Metal detection

In the article 'Metal detection' in the July issue, the author firstly experimented with a square loop measuring its inductance in presence of metal objects, and found that the iron object did not increase the inductance, the inductance being reduced both with iron objects and with metallic non ferromagnetic objects. The author attributes (rightly, I think) this behaviour to the eddy currents, "predominant in both materials". His point is confirmed by the experiments made with ferrite rods, where eddy currents are negligible and the increase in the inductance is effectively seen.

His tests with the assembled metal detector confirm all of that.

However, having done some consulting work for induction heaters, I know that the increase in the inductance, in a coil near iron objects, is a real word effect, as is introducing into the induction coil some iron to make the resonant frequency decrease.

So I started to think that the frequency makes the difference. At high frequencies, the eddy currents are strong enough to prevent the magnetic field effectively entering the metal object (be it iron or non ferrous), but at some lower frequency the inductance should increase in the presence of iron. The experiments of the article were made at 10kHz (with measuring bridge) and at 460kHz (with the assembled metal detector).

Having at hand a LCR bridge with selectable measuring frequency of 10, 1 and 0.1kHz and a big air-cored coil I normally use as dummy load for testing magnetotherapy devices, I made some measurements with them. Here are the results, for anybody that may be interested.

Coil: about 27 turns, 2.5mm², on a square 240x240mm cardboard box; resistance 0.29 ohm, inductance 618 μ H. Metal objects are placed about 80mm over the centre of the winding.

Measuring instrument: Wayne Kerr automatic LCR meter 4210, in 'series' mode measurement. All values are μ H.

Measurements on 100Hz show some variations, about 0.5 μ H around the mean value, presumably because of disturbances from 50Hz fields. The above table confirms that the iron can be distinguished from non-ferromagnetic metals, if the frequency is low enough. Besides, there is no 'magic' frequency; one needs to resort to lower and lower frequencies, as the iron sample becomes bigger.

Examining the table, the first line (free air) tells us that the inductance is about the same at all the three measuring frequencies. This should mean that the measuring instrument and the measuring mode (series inductance) are both adequate. The second line (aluminium) confirms, as we expected, that non-iron metals make the inductance decrease; but, too, it shows that at 100Hz the reduction is less, as presumably the eddy currents are less effective in keeping the magnetic field entirely out of the metal body.

The third line (iron can) shows what I suspected; at 10kHz the inductance decreases, as in the experiments of the article, but at 1kHz it increases (and at 100Hz even more).

The fourth line (iron nails) shows that, for objects as small as a nail, the inductance increases even at 10kHz (though less than at a lower frequency). This could well explain the claims of the capability to discriminate iron, made by some authors and not confirmed by other experiments. The difference could be in the dimension of the metal object. I had to test with a number of nails, because a single nail would be not detected by the resolution of the LCR bridge.

Incidentally, this test tells us another thing: it is the dimension of the single object (nail) that makes it detectable as iron at a given frequency, not the total weight; the total weight of the nails is well over the weight of the metal can of the preceding line.

The fifth line (large iron box) confirms that the discriminating frequency is lower for a bigger object; at 1kHz the inductance still decreases, only at 100Hz it increases.

Ezio Rizzo Italy

	10KHz	1KHz	100Hz
Free air	618.00	618.20	619.10
115x200mm aluminium heat sink	606.20	607.70	613.30
Iron tin-plated cylindrical can 65mm diam., 25mm length	615.70	620.60	622.30
Plastic box with iron nails	618.80	619.40	620.70
Large empty iron box 365x150x170mm	589.70	606.60	631.20

several other articles from the late *HR* magazine e.g. to align a homebuilt 1.2 meter diameter parabolic antenna with log periodic primary feed with the slotted line and the two UHF indicators (one for the slotted line, one for a remote field strength meter) to find a compromise position relative to the focus of the dish and the phase centre for 1296 and 2320MHz for the LPD. It is a pity that this fine magazine ceased publication in the late 80's.

I understand that *Ham Radio Magazine* is now available on several CD ROMs from the ARRL. Their own QEX is interesting but fails in being a valid substitute.

Ing Walter Empsten, ON4ZN
Chief of Service (retired)
External Radio Studios,
Recording and Outside Broadcasting
VRT
Brussels

Illogicalities

With Ian Johnson, I too feel most gratified that Ivor Catt is alive and well - as with his name, he should have at least nine goes at staying alive. On the other hand, though concurring with Ian's support of independent points of view and argument, I

found his letter, (July issue, *EW*) strangely pessimistic - amounting at the end to a feeling of depression!

Yes of course, the World, the Universe and Everything is imperfect (a human value judgement, and therefore subjective, by the way). We all know how boring a so-called perfect world would be. Everything would be done, it would all be designed, no free will - a perfect perpetual motion machine with not a single statistical variation or wear-out phenomenon. Those poor old capacitors in Ian's world, what have they done to be sooo evil and faulty? I have always found them remarkable, from my first Leyden Jar (which I thought was perfect - it gave me and pals a mighty shock when we held hands in series to 'test the possible charge', two days after charging it) to the extraordinary technology of the microwave surface mount caps we routinely solder onto our boards. Every time I open, say, a distant Radio Repeater with a little stub antenna radiating 2.5 watts (Oh, sorry, the little imperfect PA cannot be more than about 50% efficient - therefore about a watt may go out.), I marvel at those 'Laws of Physics' that Ian would like to be 'flexible', (what a mess we would be in if they were.) Just what does radiate all those miles - at that speed - to open the repeater? That mystery is what got me into musing for a lifetime about just what is out there, and how do 'waves' travel through nothing? (Don't mention the Ether - but...?) I find it no good to listen to the reply, "Well, when the electric field lines rapidly change their strength, (i.e. $\frac{dE}{dt}$) you get magnetic field lines at right angles - and they in turn give you more electric lines. You should know that!" I reply that I do, but just what are those 'lines'? Why, they're just made up models or pictures (and therefore completely false) that we have invented for our poor minds to see something. Then we believe it? But what does penetrate empty space - reach out over a distance to 'know' a lump of iron is there, for example, and pull on it, without losing any energy? (Even a child's little magnet has this deep mystery still taken for granted.) Oh, yes, we have Maxwell Equations (a tiny bit is that differential above) and we get surprisingly accurate design stuff from them - notwithstanding the depressingly imperfect world offered by Ian.

But though I mightily appreciate them, I cannot see an explanation from the equations of the real physical mystery of how and why all that design out there fits together so well, in spite of, er, imperfections. Of course, we could very easily slide into the Creationists' 'argument from design' stuff at this point, with all the illogicalities, wild assumptions, untestable assertions with which that bunch troubles certain areas of the United States. Nevertheless, it is the remarkable success of the discoveries of the givens in the

natural world that is so exhilarating, not allowing the imperfections to depress us (I suspect Ian is one of the closeted perfectionists at heart - and they are always most unhappy.). It would be a tonic for Ian and any other readers to peruse a lovely little book called *It Must Be Beautiful* Great Equations of Modern Science, ed. Graham Farmilo, Granta Publications. No bemoaning the imperfections there.

'Joules Watt'
By email

Self made project

Can I reply to Sébastien Veyrin-Forrer's letter in the July issue of *EW* as it criticises me? (The floor is yours - Ed.)

Seb's letter gives out the impression of arrogance; condescendence, snobbery and elitism, I can live with the first two, but I am totally against the last two. The equation for snobbery is: the more the snob, the lesser the intellect.

Subjective! "relating to the subject - existing in one's own consciousness" *Chamber's Dictionary*. A designer designs a power amp - a manufacturer makes the amp, the amp is sold to hi-fi shop and who do they sell it too? That's right, Mr. & Mrs. Joe Public. And how do they judge the amp? Right again - subjectively. It is played to them to judge it, specifications come second. We are not robots, cut us and we bleed, something funny we laugh - sad we cry. Modulated airwaves go down our ear and are converted to electrical pulses and sent to our brain, Seb - we are 100% analogue, not digital. All our actions on this planet are subjective. We marry "I love this woman", "I eat fish and chips because I love them", "Mr. X punched me - so I punched him back". Try telling a psychologist subjectivism isn't built into human beings and shouldn't be used as a means for us to judge other beings or things.

Don't get me wrong - in my last letter I acknowledged that I used two of D. Self's means to lower distortion in my amp, the man is a genius, nil distortion amps using cheap components - I hold my hand up to him as he well deserves world-wide praise and will go down in history books. But Seb, although he is your 'God' it does not necessarily follow that his amps will sound better than anyone else's.

Taking "a leaf out of your book" I will be 60 in a year and a half, and suspect that I have been building amps long before you were born and have repaired more than "you've had hot dinners".

You think the hi-fi industry is perfect? Eight months ago a friend gave me his amp to repair, it had already been to a Scottish hi-fi shop to repair. This amp had no output when the CD input was selected. The fault was that a square of plastic carrying four phono sockets had sheared the steel connectors to the PCB and also internally

Wireless networking

The Ian Poole article on 802.11 wireless networks explained how these networks offer many benefits over conventional wired networks but failed to explain how these benefits come with added risks for the unwary user.

As with many modern PC installations the default install does little to protect the user from prying eyes, even worse he can be open to hacking even stealing his data.

The August issues of both *Personal Computer World* and *PCPro* magazines include comparative performance reviews of many wireless kits, which might assist any reader wanting to install a wireless network.

A single page article "Turn on, tune in, get hacked" in *PCPro* p.11, by James Morris explains how he was able to obtain free broadband internet access using a nearby 'open' network without the owners permission. I paraphrase: "I turned on my notebook and found I'd magically acquired internet access. Someone in the vicinity had a wireless network connected to their broadband and it was completely insecure. One mouse click and I was able to connect for free."

This should present a sobering warning to all wireless network users. This default install lack of security problem is not exclusive to wireless networks. All internet users are commended to log on to the Gibson Research site: <http://grc.com> (note no www needed) This site provides a wealth of data about how easily most internet enabled computers can be accessed. In addition one can request a practical test to prove whether ones own computer is open or secure.

Gibson Research also offers a free for individual users local firewall software. Having once tested my computer using the Gibson site, I now personally never access the internet, using Windows, without first enabling his free firewall software.

Cyril Bateman
Acle
Norfolk
UK

due to the plastic not being rigid enough. I replaced the phono sockets and hard wired them back to the mode switch. Now this a bottom of the range amp costing about £200, I have no problem with cheap sockets or cheap ALPS volume controls due to the price, but coming to the power section, there sat a well known audio chip - not JLH's way of doing things, or mine, but again the amp was cheap, but there staring at me at the output were two power chips, not by any stretch of the imagination could a designer spend more than five minutes planning the amp. Page 8 of my "How to build a power amp for beginners" shows the same circuit. My friend said it was smooth, and so it was smooth in the bass, smooth in the mid-range and smooth in the top range, so smooth that the amp was flat as a pancake - no dynamics, no imaging, no emotion. Yes, it had a very low distortion and a nice square wave response, but the amp was a rip-off. If anybody recognises it, they should hang their heads in shame. What really made me angry was when I gave it back to my friend, he again said it was smooth and I had to bite my tongue rather than tell him the truth. I am a straight forward person, what you see is what you get and in then past I have been brutally honest - but have learned how to keep my mouth shut.

On another tack, I read Douglas Self's article on input impedance. Again, I hold my hand up and say that I measured the bandwidth and the state of the square wave at just over three quarters revolution of a 50k Ohm variable resistor, it gave me a flat bandwidth to 100kHz, putting it back to quarter revolution produced a square wave very badly rounded at the leading edges and solid verticals with the speed of a dead snail, so out they came after a check for output impedance on my CD player and preamp and the 2 volts (RMS) outputs. I fitted two (one each channel) 20k Ohm pots. I turned them to very near the end stops and adjusted the amp's input gain to correspond to full output. There I re-tested after adjustment of the 1950s 'beehive' air spaced trimmer also used as compensation capacitor, as per D. Self, I found the frequency response was flat to an amazing 1.116MHz. No wonder I had so much trouble with HF oscillations, although now cured, I thought I was dealing with a 100kHz band width - not over 1MHz. The square wave was now excellent, the verticals can only be seen if you press your nose up to the scope screen.

The mains transformer I put in for Class A operation was upright and I noticed some AC current due to leakage. I decided to take a leaf out of the top of the range model and build an outboard power supply. In the transformer space I grouped all eight 10,000µF capacitors around the star earth and commoned the earth returns

via a 30A cable, requiring run of only 3" to reach the star earth. I built the power unit into a small heavy gauge case with a 25A rectifier and two 4,000µF capacitors at its output (the regulation is still the amp case). As there is a very large RF pulse of approximately 2MHz in my area, I added very heavy current ferrite cored coils in series with the pos/neg output. Also 0V/earth, which is fully floating 12" of 30A cable connected by plug and socket to the stabilised section and to the bottom of the star earth. D. Self is quite correct about where you apply wires to. No mains earth is applied to the power supply, amp, or preamp earth fully floating, the AC current has now vanished. I took off the fan and fitted a very large heatsink, but was disappointed as noise has now doubled at the output. A previous amp design in *EW* had an output noise of 40µV, I now had 2mV. I then realised I wasn't judging like with like. I switched the amp off for two hours and on switching on I adjusted the quiescent current to 180mA, shorting the input, I put an 8Ω wirewound resistor and connecting up my millivolt meter and oscilloscope, did I feel good? You betcha - staring back at me was 90µV of noise, a world first for me. I then tested for distortion and another world first, 1kHz was 0.002% and 20kHz was 0.007%. Now I realise what was making the Class A distortion look bad.

Several points: I realise new regulations on earthing, i.e. mains isolated PCB/double insulation, but the amp has no longer any AC current running around it. Each channel now has six earth returns. No problem now with low frequency 'grunt' due the large storage capacity of 80,000µF. I admit that the circuit is now nothing JLH's original design, using the best points of D. Self and others in the amp, but the earth returns are totally down to me. Over the top? I refuse to accept that on two counts: firstly it works and secondly I was surprised at the large amount of audio designers who own Krell amplification equipment. An excellent amp, but it can cost £8000+. Just look inside one and tell me I've been OTT.

Personally, I think it's time *EW* got all the anti/pro subjectives together and hired a hall in London to thrash this out to a conclusion. D. Self and his disciples, JLH and his.

I now have my best ever imagery. It sounds like I am in large concert hall, it's pitch black and all of a sudden vocals and instruments come towards me in mid air, fast, clear and strong.

I want to thank *EW* for giving me my three minutes of fame. I will now die in peace.

D. Lucas
Pittenweem
Anstruther
Scotland
KY10 2lh

Help Wanted

Old radios

Having just read the article on the old German VE301 receivers in August edition, I write looking for help in trying to establish the origin of an old British broadcast receiver which I have recently revived.

Recently I was asked by a friend, (G0DKW) to attempt the restoration of a very old broadcast receiver which had apparently been languishing in a barn for unknown years. The set was a three valve TRF design and despite much dirt, nearly all of the components were in working order. After a week's work in cleaning and re-wiring it worked amazingly well bringing in 23 stations at loudspeaker level in the mid afternoon on medium wave. The aerial was a 20 metre wire.

Unfortunately, the receiver bears no identification marks apart from the component manufacturer's names and I would really like to know who made it and when. Perhaps someone with a grey beard that is somewhat longer than mine might be able to recognise the design.

The receiver is built on a half inch thick wooden base board of side 12 x 14". It has an ebonite panel, 14 x 7", with four controls, i.e. LT switch, reaction and twin edge-wise tuning controls with scales marked 0 to 180. The circuit is a 1V1 style using triode valves of the types 210LF, ???LF and 215P of Cossor manufacture. As a triode is used in the RF amplifier it has an internally set neutralising capacitor adjustable with a short ebonite rod. The plug-in tuning coils are 2.125" dia. and 2.4" in length, Litz wound and are labelled 'LEW - The London Electric Wire Company and Smiths Ltd.' The RF coil is type SP A5 and the detector SP T5. The three fixed capacitors are made by Dubilier, two are mica breadboard fixing types and the third a 2µF paper decoupler. The only resistor, the 2MΩ grid leak, is held in a clamp made by DUMETOHM. It has a single audio interstage coupling transformer made by Varley which is also inscribed Oliver Pell Manufacture. It has no audio output transformer and I guess it was intended to operate with a high impedance balanced reed loudspeaker. All external connections are via row of ten screw terminals along the rear edge of the board. The neutralising capacitor is by Igranic but the main tuning capacitors bear no inscription. Valve holders by LOTUS, and RF choke by RI Ltd.

Was it a kit? Certainly the front panel mounted tuning capacitors look factory prepared. As no cabinet or cover was recovered, I wonder if it was originally fitted as one shelf in a cabinet which may have also housed a phonograph. The battery supplies look as if they were fed from below. This receiver works very well but needs a fair bit of expertise in order to adjust it to best results, so I guess it must have come early in the broadcast reception era. Can anyone please cast any light on this old mystery? It certainly took me back to my first encounter with TRF b/c receivers in 1944 with I guess much the same pleasure when it worked.

Chas F Fletcher. G3DXZ
g3dxz@thersgb.net

HP Manual needed

I need a user manual for an HP Digitising Oscilloscope type 54501A. Photocopy would be very acceptable. Will cover costs.
Charles Coultas
0118-9785713 or email: charles@dataskil.com

Data sheet needed

I need a datasheet for an obsolete Philips IC TDA 2581 or source.

Stephen Tames
0118 9875123 ext7998 or email: s.r.tames@rdg.ac.uk

The Electronics World Book Service offers access to our team of specialist publishing experts. We can order any book or CD-ROM currently in print from *War And Peace* to the *Reference Data for Engineers*. All books are delivered free of charge within the UK unless otherwise stated. Contact us at the numbers below:

Telephone: **01737 812727** or **01737 812676**

Fax: 01737 813526

Email: salesteam@boffinbooks.demon.co.uk

HIGH SPEED DIGITAL DESIGN

Howard W Johnson & Graham Martin

Re-issue

Focusing on the field of knowledge lying between digital and analog circuit theory, this text sets out to help engineers working with digital systems shorten their product development cycles and help fix their latest design problems. It covers signal reflection and crosstalk.

820 pages ▲ HB

Code PEAR 0 13 395724 1

£44.99

RF CIRCUIT DESIGN: THEORY & APPLICATIONS

Reinhold Ludwig; Pavel Bretchko

This practical guide introduces RF circuit design fundamentals while emphasizing a circuit based approach. It provides MATLAB routines to carry out simple transmission line computations and uses a PC-based commercial RF circuit simulation tool to demonstrate actual circuit behaviour.

Oct 1999 ▲ 656 pages ▲ HB

Code PEA 0 13 095323 7

£35.99

THE ART OF ANALOG LAYOUT

Roy Alan Hastings

This text aims to provide students with a broad understanding of the issues involved in successfully laying out analog-integrated circuits - ranging from the mechanics of layout to essential information about many related areas, such as device physics, processing and failure modes and effects.

Oct 2000 ▲ 559 pages ▲ HB

Code PEAR 0 13 087061 7

£30.99

DESIGN-FOR-TEST: FOR DIGITAL INTEGRATED CIRCUITS AND EMBEDDED CORE

Alfred L Crouch

An introduction to the basic concepts of Design-For-Test, an area in chip design.

July 1999 ▲ 350 pages & CD-ROM

Code PEAR 0 13 084827 1

£59.99

ELECTRONIC PROJECTS FROM THE NEXT DIMENSION: PARANORMAL EXPERIMENTS FOR HOBBYISTS

Newton Braga

A guide to making and using paranormal research electronics. It describes practical electronic circuits to be used in experiments involving instrumental transcommunication (ITC), the electronic voice phenomenon (EVP), and paranormal experiments involving ESP, auras, and Kirlian photography. White and pink noise generators for use in instrumental transcommunication (ITC) experiments; Kirlian photography; plasma experiments; extrasensory perception testers; magnetic fields sensors.

Nov 2000 ▲ 256 pages ▲ PB

Code HBO 7506 7305 2

£28.50

BASIC AC CIRCUITS

Clay Rawlins

A step-by-step approach to AC circuits for beginners, providing thorough coverage of theory and practice. The text provides individualized learning goals covering electronics concepts, terms and the mathematics required to understand AC circuit problems.

2nd Edition ▲ Oct 2000 ▲ PB

Code HBO 7506 7173 4

£34.50

VERILOG DEVELOPER'S LIBRARY

Bob Zeidman

Verilog is one of the most used hardware description languages. This text contains a library of useful code for those users who do not want to recreate identical code for common tasks.

Jul 1999 ▲ 450 pages ▲ PB

Code PEA 0 13 081154 8

£79.99

PASSIVE COMPONENTS FOR CIRCUIT DESIGN

Ion Sinclair

Designed for technician engineers and anyone involved in circuit design, this text provides an introduction into a key area of analogue electronics. It covers all component types capable of power amplifications, including: resistors, capacitors, transformers, solenoids and motors.

Nov 2000 ▲ 301 pages ▲ PB

Code HBO 7506 4933 X

£23.50

ELECTRONIC PROJECTS FROM THE NEXT DIMENSION: PARANORMAL EXPERIMENTS FOR HOBBYISTS

Newton Braga

A guide to making and using paranormal research electronics. It describes practical electronic circuits to be used in experiments involving instrumental transcommunication (ITC), the electronic voice phenomenon (EVP), and paranormal experiments involving ESP, auras, and Kirlian photography. White and pink noise generators for use in instrumental transcommunication (ITC) experiments; Kirlian photography; plasma experiments; extrasensory perception testers; magnetic fields sensors.

Nov 2000 ▲ 256 pages ▲ PB

Code HBO 7506 7305 2

£28.50

BASIC AC CIRCUITS

Clay Rawlins

A step-by-step approach to AC circuits for beginners, providing thorough coverage of theory and practice. The text provides individualized learning goals covering electronics concepts, terms and the mathematics required to understand AC circuit problems.

2nd Edition ▲ Oct 2000 ▲ PB

Code HBO 7506 7173 4

£34.50

INTERFACING WITH C

Mike James & Howard Hutchings

An exploration of interfacing personal computers using C. An introduction to C; loops and data conversion; data acquisition using C; essential mathematics; convolution; digital filters; Fourier transforms; correlation; Kalman filters; data conversion; investigating the spectral and time-domain performance of z-transforms using computer-managed instruction; introducing audio signal processing using C; standard programming structures. Dewey: 005.71262

2nd edition ▲ Dec 2000 ▲ 308pages

Code HB 0 7506 4831 7

£20.50

SELF ON AUDIO

Douglas Self

This work offers a collection of *Electronics World* articles, including self-build projects. It aims to demystify amplifier design and establish empirical design techniques based on electronic design principles and experimental data.

Jul 2000 ▲ 256 pages ▲ PB

Code HBO 7506 4765 5

£28.50

BUILD AND UPGRADE YOUR OWN PC

Ion Sinclair

This third edition of *Build and Upgrade Your Own PC* is based around building and upgrading to the very latest systems running processors with speeds over 2.0 Ghz and ultrafast buses. It also covers upgrading to Windows XP and Windows Me.

3rd edition ▲ Jul 2002 ▲ 335 pages ▲ PB

Code HB 0 7506 5758 8

£22.50

PRACTICAL ELECTRONICS HANDBOOK

Ion Sinclair

A collection of all the key data, facts, practical guidance and circuit design basics needed by a spectrum of students, electronics enthusiasts, technicians and circuit designers. It provides explanations and practical guidance, and includes new sections on SHF techniques and intruder alarms.

5th edition ▲ Feb 2000 ▲ 571 pages ▲ PB

Code HB 0 7506 4585 7

£16.99

ANALOG CIRCUIT TECHNIQUES WITH DIGITAL INTERFACING

Trevor Wilmshurst

Aimed at junior undergraduates, this textbook offers comprehensive coverage of analogue electronic circuit design with two full chapters devoted to the use of SPICE in circuit simulations, programmes leading to Eng MSC Electronic conversion type courses.

Mar 2001 ▲ 320 pages ▲ PB

Code HBO 7506 5094 X

£19.99

ELECTRONICS FOR SERVICE ENGINEERS

Joe Cieszynski & Dave Fox

From simple mathematics and circuit theory to transmission theory and aerials, this text provides the range of knowledge required to service electronic and electrical equipment. Questions and worked examples illustrate the concepts described in each chapter.

Mar 1999 ▲ 294 pages ▲ PB

Code HBO 7506 3476 6

£20.99

FABRICATING PRINTED CIRCUIT BOARDS

Jon Varteresian

Engineers are often faced with the need for small quantities of a certain board design for construction of a small number of devices. This book describes the process of making a printed circuit board, from the conversion of a schematic diagram into a board layout to the making of the board itself.

Jul 2002 ▲ 251 pages ▲ PB

Code HB 1 878707 50 7

£21.99

REFERENCE DATA FOR ENGINEERS: RADIO, ELECTRONICS, COMPUTERS AND COMMUNICATIONS

Mac E Van Valkenburg

Written by professionals for professionals, this title is a complete reference for engineers, covering a broad range of topics. As well as addressing radio technology data, this reference volume covers digital electronics, computers and communications.

9th edition ▲ Aug 2001 ▲ 1568 pages
HB & CD-ROM

Code HBO 7506 7291 9

£90.00

PRACTICAL RF HANDBOOK

Ian Mickman

A hands-on-guide for engineers, technicians, students and enthusiasts working in RF design, this comprehensive text covers all the key topics in RF, including: analogue design principles; transmission lines; transformers; couplers; amplifiers; oscillators; modulation; and antennas.

3rd edition ▲ Feb 2002 ▲ 289 pages

150 line drawings ▲ PB

Code HB 0 7506 5369 8

£19.99

NEWNES TELEVISION AND VIDEO ENGINEER'S POCKET BOOK

Eugene Trundle

This text provides a pocket tool for service engineers. It presents a range of essential information in a compact form, covering television reception, satellite and cable television, video recorders, colour camera technology, teletext and fault-finding.

3rd edition ▲ Oct 1999 ▲ 512 pages ▲ HB

Code HB 0 7506 4194 0

£17.99

BEBOP TO THE BOOLEAN BOOGIE

Clive Maxfield

Comprehensive introduction to contemporary electronics - friendly, funny and quirky. Whether you're an engineer, hobbyist, or student who needs a thorough and up-to-date electronics reference or a non-technical person who wants to understand more about this electron dance that has seemingly taken over the world, this book is the answer. Hundreds of diagrams that clarify even the most difficult subjects.

2nd Edition ▲ Jan 2003
Code HB 0 7506 7543 8

£27.50



NEWNES GUIDE TO DIGITAL TV

Richard Brice

Covering all aspects of digital television (terrestrial, satellite and cable), this text has been updated with developments since the 2000 edition. Foundations of television; digital video and audio coding; digital signal processing; video data compression; audio data compression; digital audio production; digital video production; the MPEG multiplex; broadcasting digital video; consumer digital technology; the future.

2nd edition ▲ Sep 2002 ▲ 304 pages ▲ HB
Code HB 0 7506 5721 9

£24.99



NEWNES DICTIONARY OF ELECTRONICS

SW Amos & R S Amos

Aimed at engineers, technicians and students working in the field of electronics, this dictionary provides clear and concise definitions, including TV, radio and computing terms, with illustrations and circuit diagrams.

4th edition ▲ March 2002 ▲ 394 pages ▲ PB
Code HB 0 7506 5642 5

£12.99



RSGB RADIO AND ELECTRONICS COOKBOOK

Radio Society of Great Britain

Only a basic knowledge of electronics is assumed for this collection of electronics projects, and it is ideal for all electronics and DIY enthusiasts and experimenters. Designed by the RSGB, the UK radio amateurs federation, the projects are clearly explained step by step.

Nov 2000 ▲ 336 pages ▲ PB
Code HB 0 506 5214 4

£17.99



ELECTRONIC SERVICING AND REPAIRS

Trevor Linsley

Updates the previous text taking into account changes in the City and Guilds courses 2360 and 2240. Also features hardware topics, testing and fault diagnosis, PLCs and CAD software, and new chapters. Health and safety; electronic component recognition; electronic circuit assembly techniques; electronic semiconductor devices; electronic circuits in action; testing electronic circuits; digital electronics; electrical circle theory; electronic systems; communication systems; security systems; sensors and transducers.

3rd edition ▲ Aug 2000 ▲ 261 pages
Code HB 0 7506 5053 2

£18.99



DIGITAL LOGIC DESIGN

Brian Holdsworth & Woods

This undergraduate text on digital systems covers first and second year modules and HND units, and can also be used as a reference text in industry. Updated topics in the fourth edition include: EBCDIC, Grey code, practical applications of flip-flops, linear and shaft encoders and memory elements.

4th edition ▲ Aug 2002 ▲ 448 pages
Code HB 0 7506 4582 2

£19.99



NEWNES INTERFACING COMPANION: COMPUTERS, TRANSDUCERS, INSTRUMENTATION AND SIGNAL PROCESSING

Tony Fischer-Cripps

Provides the fundamentals of electronics, transducers, computer architecture and interfacing techniques needed to use a simple PC or PLC-based system for the collection of data previously only obtainable from expensive dedicated equipment.

Aug 2002 ▲ 320 pages ▲ HB
Code HB 0 7506 5720 0

£24.99




NEWNES RADIO AND RF ENGINEERING POCKET BOOK

Steve Winder & Joseph J Carr

With a mass of information and data for students, radio and telecommunications engineers, RF circuit designers, radio hobbyists and technicians, this guide covers all aspects of radio and communications engineering from low frequencies to microwaves, with an emphasis on mobile communications.

3rd edition ▲ Jul 2002 ▲ 352 pages ▲ HB
Code HB 0 7506 5608 5

£16.99

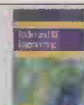

ROBOTICS, MECHATRONICS, AND ARTIFICIAL INTELLIGENCE: EXPERIMENTAL CIRCUIT BLOCKS FOR DESIGNERS

Newton C Braga

This work simplifies the process of finding basic circuits to perform simple tasks, such as how to control a DC or step motor, and provides instruction on creating moving robotic parts, such as an "eye" or an "ear".

Nov 2001 ▲ 317 pages ▲ PB
Code HB 0 7506 7389 3

£21.99



EMBEDDED MICROPROCESSOR SYSTEMS: REAL WORLD DESIGN

Stuart Ball

Providing an introduction to the design of embedded microprocessor systems, this edition covers everything from the initial concept through to debugging the final result. It also includes material on DMA, interrupts and an emphasis throughout on the real-time nature of embedded systems.

3rd edition ▲ Nov 2002 ▲ 368 pages ▲ PB
Code HB 0 7506 7534 9

£35.00



POWER SUPPLY COOKBOOK

Marty Brown

Providing an easy-to-follow, step-by-step design framework for a wide variety of power supplies, including linear, switching and quasi-resonant switching. There is also discussion of design topics such as magnetics, feedback loop compensation design and EMI/RFI control in straightforward terms.

2nd edition ▲ Jun 2001 ▲ 336 pages ▲ HB
Code HB 0 7506 7329 X

£24.99



MIXED-SIGNAL AND DSP DESIGN TECHNIQUES

Walt Kester

Mixed-signal processing implies the use of analog and digital in the same system; this is a specialized type of signal processing that requires a high level of experience and training. This book focuses primarily on signal processing hardware - how it works, how to interface it, and design it.

Oct 2002 ▲ 336 pages ▲ PB
Code HB 0 7506 7611 6

£39.99



UNDERSTANDING AUTOMOTIVE ELECTRONICS

W B Ribbens

Covering the most recent technological advances in operation and troubleshooting of electronic systems and components, including low-emission standards, on-board diagnostics and communications, digital instrumentation, and digital engine control. A practical text, suitable for the automotive technical, student, enthusiast, or professional who wants to upgrade his or her background in electronic systems found in the automotive.

6th ed. Dec 2002
Code HB 0 7506 7599 3

£24.99




DESIGNING EMBEDDED INTERNET DEVICES

Brian DeMuth & Eisenreich

This guide to designing internet access and communications capabilities into embedded systems takes an integrated hardware/software approach, using the Java programming language and industry-standard microcontrollers. The CD-ROM has Java source code and a version of the text.

Aug 2002 ▲ 320 pages
PB & CD-ROM
Code HB 1 878707 98 1

£35.00

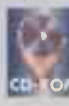

PIC IN PRACTICE: AN INTRODUCTION TO THE PIC MICROCONTROLLER

David W Smith

An exploration of the PIC microcontroller, designed to be used at a variety of levels. It introduces the reader to the range of tasks the PIC can perform and makes use of readily available components. The PIC used in the examples is the re-programmable EEPROM 16C84/16F84.

Apr 2002 ▲ 261 pages ▲ PB
Code HB 0 7506 4812 0

£14.99



If you are ordering by credit card, need further information, or would like to use our search facilities call
01737 812727 Fax 01737 813526.
The order/helpline is open from 9am to 5pm, or leave your order on our out of hours answerline or email us at
salesteam@boffinbooks.demon.co.uk.

When placing orders please quote
● Name ● Address (home & delivery) ● Daytime telephone number ● Debit/Credit card number ● Expiry date ● Details of order. Please note that prices may change, but are correct at time of going to press.

Boffin Books Ltd., 24 Walton Street,
Walton-on-the-Hill, Tadworth, Surrey KT20 7RT, UK

ELECTRONICS WORLD ORDER FORM

Please order or search the following:

Code	Description	Qty	Price
POSTAGE & PACKING FREE IN THE UK*		TOTAL	
Name	Daytime Tel		
Address			
	Postcode		
Delivery address (if different)			
	Postcode		

I enclose a cheque/postal order value £ payable to 'Boffin Books Ltd'

Please debit my Access/Visa/Switch/Delta card Issue number (Switch only)

Card Number Expiry Date

Signed emailsalesteam@boffinbooks.demon.co.uk

*Postage charges outside the UK available upon request or email to salesteam@boffinbooks.demon.co.uk

Send order form to: Boffin Books Ltd., 24 Walton Street, Walton-on-the-Hill, Tadworth, Surrey KT20 7RT, UK

Wilmslow Audio

View Cart Checkout




100 CABLES | SPECIAL OFFERS | 100% SATISFACTION GUARANTEE

WEB DIRECTIONS

VUTRAX

Beyond ordinary PCB CAD

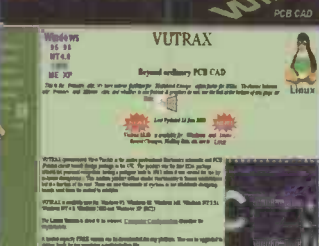

Put your web address in front of 18,000 electronic fanatics. Electronics World acknowledge your company's needs to promote your web site, which is why we are dedicating 2 pages in every issue to WEB ADDRESSES. Linage only will cost £150 + vat for a full year. Linage with colour screen shot will cost £350 + vat for a full year, this will include the above plus 3cm shot of your web site which we can produce if required. To take up this offer or for more information telephone Reuben Gurunlian Tel 0208 722 6028 E-mail r.gurunlian@highburybiz.com

in our extensive database covering Akai, Alba, Bush, Ferguson, Goldstar, Hitachi, LG, Marantz, Matsui, Nokia, Saisho, Sanyo, Sony, Sharp, Thomson, Panasonic, Philips, Samsung, Tascam, Teac, Toshiba, Yamaha and many more. In addition huge ranges of Lasers, Laptops, Remote controls and Semiconductors may be accessed.

CHYGWYN
<http://www.chygwyn.com>



Linux Consultants and Electronic Designers

Linux Services

System Design and Implementation

Electronic Design Services

ChyGwyn Limited offers electronic design and embedded software development for remote monitoring, embedded appliances, set-top boxes and similar devices. We are experts in customisation of Linux and write device drivers for custom hardware.

CONFORD ELECTRONICS
<http://www.confordelec.co.uk/index.shtml>



Welcome to our range of professional audio and process control products

Just select the products that interest you from the following description:

Lightweight portable battery/mains audio units offering the highest technical performance. Microphone, Phantom Power and Headphone Amplifiers. Balanced/unbalanced signal lines with extensive RFI protection.

Lightweight portable battery/mains audio units offering the highest technical performance. Microphone, Phantom Power and Headphone Amplifiers. Balanced/unbalanced signal lines with extensive RFI protection.

CRICKLEWOOD ELECTRONICS
<http://www.cricklewoodelectronic.co.uk>

Cricklewood Electronics stock one of the widest ranges of components, especially semiconductors including ICs, transistors, capacitors, all at competitive prices.

DB TECHNOLOGY
<http://www.dbtechnology.co.uk/>

EMC Testing and Consultancy. Anechoic chamber and open area test site.

- Compliance Tests
- Rapid, accurate pre-compliance tests.
- Fixes included. FCC Listed.



dB Technology

Taking the pain out of EMC


Experts in EMC Testing and Consultancy

Tel: +44 (0) 1964 261974
 E-Mail: mail@dbtechnology.co.uk

● Flexible hourly booking available.

DESIGNER SYSTEMS CO.
<http://www.designersystems.co.uk>

Electronic product design company with

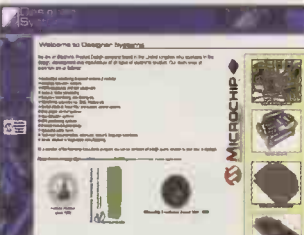

Welcome to Designer Systems

MicroCHIP

over a decade of experience promoting it's own product range and designing and manufacturing innovative products for client companies/individuals.

EAGLE PCB DESIGN SOFTWARE
<http://www.puresoft.co.uk>

● Professional PCB design made easy!



Professional PCB Design Made Easy

Introducing the New Eagle 6.0.0

Fully functional freeware download.


- Schematics, Layout & Autorouting.
- Free tech support

● Fully functional freeware download.

● Schematics, Layout & Autorouting.

● Free tech support

EasySync
<http://www.easysync.co.uk>

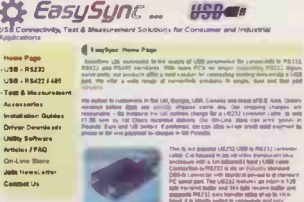

EasySync

USB Connectivity, Test & Measurement Solutions for Consumer and Industrial Applications

Home Page

USB-RS232

USB-RS422/485

Test & Measurement

Accessories

Installation Guides

Driver Downloads

Utility Software

Articles / FAQ

Contact Us

EasySync supplies a wide range of USB-RS232 and USB-RS422/485 converters. It also specialises in USB test and measurement devices.




FELLER

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

FELLER UK
<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

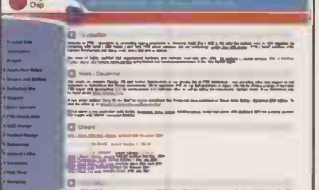FUTURE TECHNOLOGY DEVICES INTL. LTD.
<http://www.ftdichip.com>



FTDI

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s. Complete with PC drivers these devices simplify the task of designing or upgrading USB peripherals

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s. Complete with PC drivers these devices simplify the task of designing or upgrading USB peripherals

GREENWELD
<http://www.greenweld.co.uk>




GREENWELD

Audio ● Batteries & Chargers ● Books ● Communications ● Computer ● Cable ● Capacitors ● Car Equipment ● Craft Goods ● Disco Equipment ● Enclosures ● Electrical ● Fuses ● Graphic supplies ● Hardware ● Instrumentation ● Kits ● Lighting ● Mechanical ● Optical ● Photographic ● Power supplies ● Transformers ● Resistors ● Semiconductors ● Software ● Soldering Irons ● Surplus goods ● Switches ● Relays ● Telephone Accessories ● Tools ● Plus much more.

Audio ● Batteries & Chargers ● Books ● Communications ● Computer ● Cable ● Capacitors ● Car Equipment ● Craft Goods ● Disco Equipment ● Enclosures ● Electrical ● Fuses ● Graphic supplies ● Hardware ● Instrumentation ● Kits ● Lighting ● Mechanical ● Optical ● Photographic ● Power supplies ● Transformers ● Resistors ● Semiconductors ● Software ● Soldering Irons ● Surplus goods ● Switches ● Relays ● Telephone Accessories ● Tools ● Plus much more.

Whether your interest is in electronics, model engineering, audio, computer, robots or home and

ANASOFT LTD
<http://www.anasoft.co.uk>

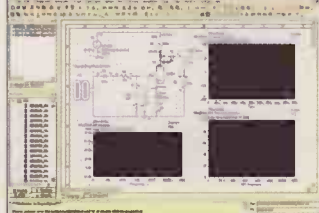

SuperSpice, the affordable, mixed-mode windows circuit simulator. Wrote by an analogue design engineer for those Teletubbies who like keeping things simple.

SuperSpice, the affordable, mixed-mode windows circuit simulator. Wrote by an analogue design engineer for those Teletubbies who like keeping things simple.

CHARLES HYDE & SON Ltd
<http://www.charleshyde.co.uk>

Search for both original and copy spare parts



CHARLES HYDE & SON LTD

Search for both original and copy spare parts

To reserve your web site space phone Reuben Gurunlian
 Tel: 020 8722 6028
 Fax: 020 8722 6096

TOTALROBOTS
 Robotics, Control & Electronics Technology

Range of OOIPs • 68000s • 80000s • 68000s • 68000s • 68000s • 68000s • 68000s • 68000s

Ordering Information: Find out what's new, pricing for our free NEWSLETTER. Useful Robot Links

This is factor is an exciting new robot that is easy to assemble and can be used in a variety of environments.

For more info and ordering visit our Programmable Robot page.

We sell high quality robot kits and components, and source products and accessories. Our customers are Educators, hobbyists and individuals, looking for innovative and exciting products.

leisure products (to name just a few) we have a wide range of new and surplus stock available.

J W HARDY COMMUNICATIONS

<http://www.jwhardy.co.uk>



R.F. Network Specialist. Shop online - for R.F. network components. We supply a full range of TV, radio reception equipment to receive analogue/digital signals from both terrestrial and satellite sources. We provide a free planning service for your R.F. networks, MATV and SMATV etc

LOW POWER RADIO SOLUTIONS

<http://www.lprs.co.uk>

LPRS produces radio modules with embedded "easy-Radio" software protocols for short range radio applications. We also represent Circuit Design narrow band modules in the UK.

MATRIX MULTIMEDIA LTD

www.matrixmultimedia.co.uk




Matrix Multimedia publishes a number of highly interactive CD ROMs for learning electronics including: Complete electronics course, Analogue filter design, and PICmicro(R) microcontroller programming (C and assembly).

NORCALL Ltd

<http://www.tetra-com.co.uk>

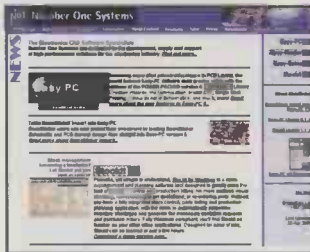e-mail Norcall@aol.com
 Suppliers programmers and repairers of new and refurbished two-way radio equipment. Retuning and recrystalling service available. All types of batteries chargers and aerials supplied.



EASY-PC PCB DESIGN SOFTWARE

<http://www.numberone.com>

UK's leading PCB design software Runs under 95/98/ME/NT4/2000 & XP Very easy to use ● Schematic, ● PCB, ● Autorouting, ● Simulation. Free professional UK based tech support 4 variants available to suit budget Demo CD available or download from web

QUASAR ELECTRONICS

www.QuasarElectronics.com



Over 300 electronic kits, projects and ready built units for hobby, education and industrial applications including PIC/ATMEL programming solutions. Online ordering facilities. Tel: +44 (0) 870 246 1826 Fax: +44 (0) 870 460 1045 Email: sales@QuasarElectronics.com

RADIOMETRIX

<http://www.radiometrix.co.uk>



Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use. They comply with European harmonised standards EN300 220-3 and EN301 489-3 and are CE certified by an independent Notified Body.


SOFTCOPY

<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.

TELNET

<http://www.telnet.uk.com>

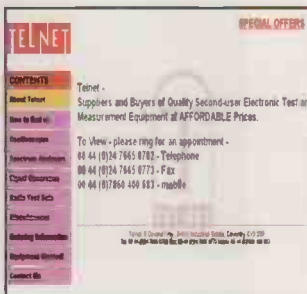

Top quality second-user Test and Measurement Equipment
 eMail sales@telnet.uk.com

TELEVES

<http://www.televes.com>

Tel: 44(0) 1633 875821
 email hbotas@televes.com
 Televes website was launched as an easier way to keep in contact with our World-wide Network of Subsidiaries and Clients. This site is constantly updated with useful information/news plus you can download info on our range: TV Aerials & accessories, Domestic and Distribution amplifiers, Systems Equipment for DTT and Analogue TV, Meters and much more.

TEST EQUIPMENT SOLUTIONS

<http://www.TestEquipmentHQ.com>



Test Equipment for rental or second user sale at the industry's lowest prices. All types of equipment from all leading manufacturers including general purpose, communications and industrial test. Items fully refurbished with 1 year warranty. Rental rebate given on purchases.

TELONIC

<http://www.telonic.co.uk>



Telonic specialists in laboratory AC & DC Power Supplies, Electronic AC & DC Loads, Electrical Safety Testing and complete test systems. Plus RF Filters, Attenuators, Diesel Engine Smoke Measurement, Quartz Crystal Microbalances.
 Tel +44 (0) 118 9786911


TECHNICAL AND SCIENTIFIC SUPPLIES

<http://www.technicalscientific.com>

- Suppliers of pre-1985 equipment and components.
- Test/Measurement equipment
- Valves and semiconductors
- Transducers and pressure gauges
- Scientific books and catalogues
- Manuals and data sheets

THOSE ENGINEERS LTD

<http://www.spiceage.com>

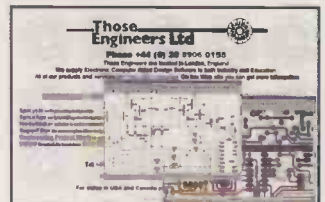

Working evaluations of SpiceAge mixed-mode simulator, Spicycle PCB design tools and Superfilter demo (synthesises passive, active, digital filters). Tech support, sales links and price list.

TOTAL ROBOTS

<http://www.totalrobots.co.uk>

Robot Kits and Control Technology products, including OOPIc the first Object-Oriented Programmable Integrated Circuit. Secure on-line ordering and fast delivery.

TOTALROBOTS
 Robotics, Control & Electronics Technology

Range of OOIPs • 68000s • 80000s • 68000s • 68000s • 68000s • 68000s • 68000s • 68000s

Ordering Information: Find out what's new, pricing for our free NEWSLETTER. Useful Robot Links

This is factor is an exciting new robot that is easy to assemble and can be used in a variety of environments.

For more info and ordering visit our Programmable Robot page.

We sell high quality robot kits and components, and source products and accessories. Our customers are Educators, hobbyists and individuals, looking for innovative and exciting products.

We offer our on-line ordering, rapid delivery and highly competitive prices. Please contact us for one of our special educational and bulk quantity discounts.

Find out what's new, sign up for our free NEWSLETTER.

ULTRA-CREA OY

<http://www.ultra-crea.fi>



Our business idea is to provide our customers complete service, i.e. design from the customer specification to the delivery of finished and tested products.

Our offerings are as follows:

- RF transmission line filters from 100MHz to 3GHz
- Special antennas to frequencies as above
- Transmitter and Receiver modules
- RF-subunits such as amplifiers, oscillators, directional couplers etc.

VUTRAX PCB DESIGN SOFTWARE

<http://www.vutrax.co.uk>



Vutrax electronic schematic and pcb design system for Windows 95/98, ME, NT, 2000, XP and Linux. Limited capacity FREE version downloads available, all upgradeable to various customised level.

WILMSLOW AUDIO

<http://www.wilmslow-audio.co.uk>



'Uk's largest supplier of high quality loudspeaker kits and drive units. Comprehensive range of components and accessories, including damping products, connectors and grilles materials. Demonstration facilities available.

Ten year index: new update



Photo copies of *Electronics World* articles from back issues are available at a flat rate of £3.50 per article, £1 per circuit idea, excluding postage.

Hard copy *Electronics World* index Indexes on paper for volumes 100,101, and 102 are available at £2 each, excluding postage.

www.softcopy.co.uk

Hard copies and floppy-disk databases both available

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past nine years.

The computerised index of *Electronics World* magazine covers the nine years from 1988 to 1996, volumes 94 to 102 inclusive and is available now. It contains almost 2000 references to articles, circuit ideas and applications - including a synopsis for each.

The *EW* index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512K ram and a hard disk.

The disk-based index price is still only £20 inclusive. Please specify whether you need 5.25in, 3.5in DD or 3.5in HD format.

Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

Ordering details

The *EW* index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders. Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide.

For enquires about photocopies etc please send an sae to SoftCopy Ltd.

**Send your orders to SoftCopy Ltd,
1 Vineries Close, Cheltenham GL53 0NU.**

Cheques payable to SoftCopy Ltd, please allow 28 days for delivery.

**WATCH SLIDES ON TV
MAKE VIDEOS OF
YOUR SLIDES
DIGITISE YOUR
SLIDES
(using a video capture card)**



"Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatv.co.uk £91.91+ vat = £108.00

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MIR size 60x36x27mm with 6 Infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye).....£37.00 + vat = £43.48

30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole.....£35.00 + vat = £41.19

40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses.....£32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed Iris

VSL1220F 12mm F1.6 12x15 degrees viewing angle.....£15.97 + vat = £18.76

VSL4022F 4mm F1.22 63x47 degrees viewing angle.....£17.65 + vat = £20.74

VSL6022F 6mm F1.22 42x32 degrees viewing angle.....£19.05 + vat = £22.38

VSL8020F 8mm F1.22 32x24 degrees viewing angle.....£19.90 + vat = £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30x24 degrees viewing angle.....£26.43 + vat = £31.06

VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle.....£77.45 + vat = £91.00

1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat 1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily.....£7.46+vat = £8.77




Please add 1.66 + vat = £1.95 postage & packing per order

JPG ELECTRONICS

Shaws Row, Old Road, Chesterfield, S40 2RB
Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch
Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

The Simple Solution!
FlexIt
AVR Controller Development System

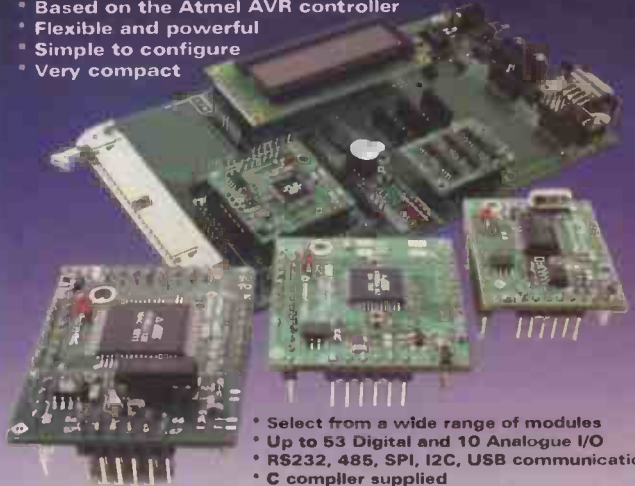- Based on the Atmel AVR controller
- Flexible and powerful
- Simple to configure
- Very compact



- Select from a wide range of modules
- Up to 53 Digital and 10 Analogue I/O
- RS232, 485, SPI, I2C, USB communication
- C compiler supplied
- Compatible with most AVR dev. tools
- In-system programmable
- Free Atmel debug simulator available
- Peripheral drivers and libraries supplied
- Increasing range of expansion modules
- Full website support

Check out FlexIt at www.ennovi.co.uk

ennovi ltd
Dynamic Design

+44 (0)1425 478884
sales@ennovi.co.uk

Precision measurement
Embedded control
Intrinsic safety
Internet embedded systems
USB interface

ADVERTISERS INDEX

Ashdown Electronics	pg 29
Beta Layout	pg 2
Cambridge Microprocessor Systems.....	pg 29
Cricklewood Electronics	pg 2
Ennovi	pg 63
ESR Electronic Components	pg 4
Johns Radio.....	pg 29
JPG Electronics.....	pg 63
Labcenter.....	pg 27
Number One Systems	pg 2
Observant Electronics	IBC
Olson.....	pg 17
Pico Technology	pg 52
Quasar Electronics.....	pg 9
Telnet Ltd.....	IFC
Test Equipment Solutions	OBC
Tie Pie Engineering	pg 11

Service Link

ARTICLES WANTED

BEST CASH PRICES PAID

FOR VALVES KT88,
PX4 AND MOST
AUDIO/OTHER
TYPES.

Tel: 01403 784961

Billington Export Ltd.
Sussex RH14 9EZ
Fax: 01403 783519
Email: sales@bel-tubes.co.uk
Visitors by appointment

TOP PRICES PAID

For all your valves,
tubes, semi conductors
and ICs.

Langrex Supplies Limited
1 Mayo Road, Croydon, Surrey CR0 2QP
TEL: 020 8684 1166 FAX: 020 8684 3056

FOR SALE

RF DESIGN SERVICES

All aspects of RF
hardware development
considered from
concept to production.

WATERBEACH ELECTRONICS

www.rlaver.dial.pipex.com
TEL: 01223 862550
FAX: 01223 440853

FOR SALE

PRINTED CIRCUIT BOARDS

DESIGNED & MANUFACTURED

- Prototype or production quantities
- Fast turnaround available
- PCBs designed from circuit diagrams
- Almost all computer files accepted
- PCB assembly - mechanical assembly
- Full product design-manufacture-test-repair

 agar
Circuits

Unit 5, East Belfast Enterprise Park
308 Albertbridge Rd, Belfast BT5 4GX
TEL 028 9073 8897 FAX 028 9073 1802
info@agarcircuits.com

AVO COIL WINDER WITH MC6 CONTROLLER

2 reels of wire.

Good working condition
Bench top mounting
£750 ono

sales@headwayelectronics.com
01295-721180/Fax: 01295-722916
Godswell House, Church St,
Bloxham, Oxon OX15 4ES

SERVICES

POWER SUPPLY DESIGN

Switched Mode PSU
Power Factor Correction
designed to your specification

Tel/Fax: 01243 842520
e-mail: eugen_kus@cix.co.uk

Lomond Electronic Services

WESTDALE ELECTRONICS

We would welcome the opportunity
of quoting for your requirements.

*If you have a problem with your
semiconductors or relays,
give us a call and we will locate
them for you.*

We also have access to inventory
Stateside ie
Current, Obsolete, MII, Spec

Call: Bryan on -
Tel/Fax:
0115 9402127



For a
FREE
consultation on
how best to
market your
products/services
to a
professional
audience ring
01322
611292

Service Link

A thousand applications ONE SOLUTION!

Introducing DataStation™ a 16 Channel, mixed-signal, software-configurable serial I/O controller.

Greater than 500 samples per second & 391 different I/O configurations from just one product!


With up to:

- 6 Analogue Inputs
- Selectable ADC resolution
- 2 PWM Outputs
- 16 Digital Inputs
- 16 Digital Outputs
- RS-232 interface

Typical Applications:

- Machine control
- Industrial automation
- Environmental monitoring
- Robotics

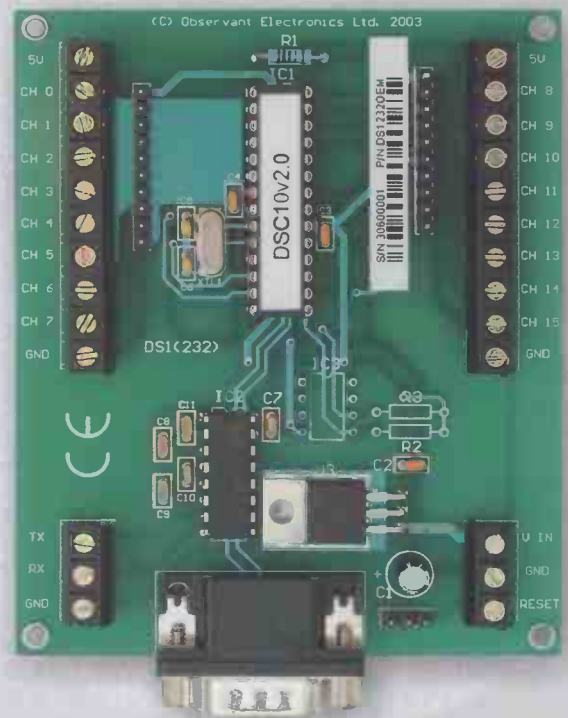This unrivalled flexibility allows designers to meet the needs of virtually any application with just one product, helping to reduce development costs and time-to-market significantly.



£89.00
plus VAT

(Significant discounts for higher volumes)

To find out more or buy online visit: www.ObservantWorld.com



Unit F2b, Avonside Enterprise Park,
New Broughton Road, Melksham,
Wiltshire. SN12 8BS. U.K.
Telephone: 01225 704631
Facsimile: 01225 708618
www.ObservantWorld.com
Email: enquiries@ObservantWorld.com

TEST EQUIPMENT SOLUTIONS

Quality Second User Test Equipment
With 12 Months Warranty

The Industry's Most Competitive Test Equipment Rental Rates

Sale (GBP) Rent (GBP)

Sale (GBP) Rent (GBP)

Sale (GBP) Rent (GBP)

AMPLIFIERS

Amplifier Research 10W1000B 1GHz 10W RF Amplifier 2950 89
Amplifier Research 1W1000 1GHz 1W RF Amplifier 950 48
HP 8348A 26.5GHz 25dB 25dBm Microwave Amplifier 7500 270
HP 8349B 2-20GHz 15dB +20dBm Amplifier 2950 89
Kalmus KMS737LC 25W 10KHz-1GHz Amplifier 4750 143

COMPONENT ANALYSERS

HP 4145B Semiconductor Parameter Analyser 14500 522
HP 4155B Semiconductor Parameter Analyser 24000 864
HP 4284A 1MHz Impedance Analyser 7950 399
HP 4285A 30MHz Precision LCR Meter 8500 425
HP 4286A 1MHz - 1GHz LCR Meter 5250 263
Tek 370A Curve Tracer 19500 702
Tek 371A Curve Tracer 17950 647

DATACOMMS

Microtest 2 W/ INJECTOR+ 2 Way Cat 5 Injector 350 18
Microtest MT340 LAN Cable Tester 750 50
Microtest PENTA SCANNER Cat 5 Cable Tester 975 50
Microtest PENTA SCANNER+ Cat 5 Cable Tester 975 50

ELECTRICAL POWER

Dranetz PP4300 Power Quality Analyser 4950 179
Dranetz TR2022 10-1000A Current Clamp For PP4300 595 25
Kikusui TOS8850 Insulation Tester 1250 45

EMC

Chase HFR2000 30MHz Measuring Receiver 750 38
Chase LFR1000 9KHz-150KHz Interference Meas Receiver 850 43
R&S EB100 20MHz-1GHz EMC Test Receiver 1950 59
R&S EP2100 Panoramic Display For EB100 695 28
Schaffner NSG1025 Fast Transient/Burst Generator 2950 89

FREQUENCY COUNTERS

HP 53131A/030 3GHz Universal Counter 1350 41
Philips PM6670 120MHz Frequency Counter/Timer 350 28
Philips PM6673 120MHz Frequency Counter/Timer 395 20
Racal 1992 1.3GHz Frequency Counter 1150 35

FUNCTION GENERATORS

HP 33120A 15MHz Function/Arbitrary Waveform Generator 950 38
HP 3325B 21MHz Function Generator 2950 89
Lecroy 9109/9100-CP Arb Waveform Gen With Controller 1950 59
Tek AWG2021 125MHz 250MS/s Arbitrary Waveform Gen 4950 149
Thandar TG1010 10MHz Function Generator 450 27

LOGIC ANALYSERS

HP 16500C Logic Analyser Mainframe 2350 71
HP 16510A 100MHz Timing/25MHz State 80Ch Card 975 36
HP 1662A 500MHz Timing/100MHz State 68Ch 2900 87
HP 1662AS 500MHz Timing/100MHz State 68Ch with DSO 4500 135

MULTIMETERS

Fluke 8010A 3.5 Digit Digital Multimeter 175 18
Fluke 8050A 4.5 Digit Digital Multimeter 250 20
HP 34401A 6.5 Digit Digital Multimeter 650 33
Keithley 2400 200V Digital SourceMeter 2500 75
Schlumberger 7150+ 6.5 Digit Precision Multimeter 395 29

NETWORK ANALYSERS

HP 35677A 200MHz 50 Ohm S Parameter Test Set 1895 56
HP 3577A 5Hz-200MHz Vector Network Analyser 4750 142
HP 4195A 500MHz Vector Network/Spectrum Analyser 9500 342
HP 8714C/1E1 300KHz-3GHz Vector Network Ana c/w TR 7250 218
HP 8753B/006 6GHz Vector Network Analyser 6500 195
HP 8753ES 3GHz Vector Network Analyser c/w S Parameter 16950 508
HP 89441A - Various options available - CALL prices from 14000 504

OSCILLOSCOPES

HP 54501A 4 Channel 100MHz 20MS/s Digitising Scope 1250 38
HP 54502A 2 Channel 400MHz 400MS/s Digitising Scope 1500 45
HP 54622D 2 + 16 Channel 100MHz 200MS/s Scope 2650 80
HP 54825A 4 Channel 500MHz 2GS/s Digitising Scope 7200 216
Lecroy LC534L 4 Channel 1GHz 1GS/s Digitising Oscilloscope 6750 203
Tek A6302 50MHz, 20A CURRENT CLAMP 700 35
Tek TDS320 2 Channel 100MHz 500MS/s Digitising Scope 1550 56
Tek TDS460A/XL 4 Channel 400MHz 100MS/s Digi Scope 3950 143
Tek TDS540 4 Channel 500MHz 1GS/s Digitising Scope 4400 132
Tek TDS754D 4 Channel 500MHz 2GS/s Digitising Scope 8750 315
Tek TDS794D 4 Channel 2GHz 4GS/s Digitising Scope 17500 630

Checkout our Latest 2003 Product Guide !!
Call Us Now for Your Copy



POWER METERS

HP 11722A 2.6GHz Power Sensor Module 1500 45
HP 437B RF Power Meter 1350 49
HP 437B/002 RF Power Meter 1350 49
HP 438A Dual Channel RF Power Meter 1550 49
HP 8481A 10MHz-18GHz 100mW Power Sensor 450 27
HP 8481D/11708A Power Sensor 10MHz-18GHz 695 35
HP 8481H 10MHz-18GHz 3W Power Sensor 650 33
HP 8484A 10MHz-18GHz 100pW Power Sensor 900 45
HP 8900C Peak Power Meter 1850 67
HP E4412A 10MHz-18GHz 100mW Power Sensor 695 35
HP E4418A Single Channel RF Power Meter 1650 60
HP E4418B Single Channel RF Power Meter 1750 63
HP E4419A Dual Channel RF Power Meter 2350 71

POWER SUPPLIES

Many units available Call us Prices from 85 9
Kikusui PLZ150W 150W Electronic Load 595 25
Tek 1101A Dual Probe Power Supply 150 15

PULSE GENERATORS

HP 8082A 250MHz Pulse Generator 1450 53
HP 8112A 50MHz Pulse Generator 2450 89
HP 8130A 300MHz Pulse Generator 5500 198
Leader LT1611 150MHz Prog. Analog RGB Video Generator 2250 81

SIGNAL & SPECTRUM ANALYSERS

Advantest R3361A 9KHz-2.6GHz Spectrum Analyser With TG 5750 173
Advantest R4131B 3.5GHz Spectrum Analyser 3950 143
Advantest R9211A 100KHz Dual Channel FFT Analyser 2950 89
Anritsu MS9710B/005 600-1750nm Optical Spec Analyser 6750 243
Anritsu MS2601A 2.2GHz Spectrum Analyser 2950 107
Anritsu MS2602A/01 100Hz-8.5GHz Spectrum Analyser 7750 233
Anritsu MS610B 2GHz Spectrum Analyser 2650 80
Anritsu MS710C 23GHz Spectrum Analyser 7500 225
HP 3339A 110KHz Distortion Analyser 1250 38
HP 3561A/001 100KHz Dynamic Signal Analyser (1 Channel) 2950 89
HP 3562A 100KHz Dual Channel Dynamic Signal Analyser 3650 110
HP 35660A 102.5KHz Dual Channel Dynamic Signal Analyser 3250 98
HP 3585A 40MHz Spectrum Analyser 3950 119

HP 53310A 200MHz Modulation Domain Analyser 3950
HP 7000 System with 100Hz-2.9GHz capability 4950
HP 85024A 3GHz Active Probe 1450 43
HP 8560E 50Hz-2.9GHz Synthesised Spectrum Analyser 8500
HP 8561E 6.5GHz Spectrum Analyser 10500
HP 8563A/103/104/M09 22GHz Spectrum Analyser 10950
HP 8565E 50GHz Spectrum Analyser 25500
HP 8591A/010/021 1.8GHz Spectrum Analyser With TG 3950
HP 8594E/41/130 2.9GHz Spectrum Analyser 5450
HP 8901A/001 1.3GHz Modulation Analyser 950
HP 8901B 1.3GHz Modulation Analyser 1950
HP 8903B/001/010/051 20Hz-100KHz Audio Analyser 1950
Marconi 2380/83/303G 4.2GHz Spectrum Analyser (no TG) 4500

SIGNAL GENERATORS

HP 8644B/002 2GHz High Performance Signal Generator 7500
HP 8648B 2GHz Synthesised Signal Generator 3750
HP 8648C 9KHz-3.2GHz Synthesised Signal Generator 5250
HP 8656B 1GHz Synthesised Signal Generator 1100
HP 8657A 1GHz Signal Generator 1600
HP 8657B/001 2GHz Synthesised Signal Generator 3500
HP 8657D/H01 1GHz DQPSK Synthesised Signal Generator 1350
HP E4421B 3GHz Signal Generator 5500
HP E4432B 3GHz Synthesised Signal Generator 7250
HP E4433B/100/UN5/UND 4GHz RF Signal Generator 8950
Marconi 2017 10KHz-1024MHz Low Noise Signal Generator 950

TELECOMS

HP 37717C/UKJ PDH Transmission Analyser 2450
HP 3788A/001 2MBPS Error Performance Analyser 1350
Trend AURORA DUET Basic & Primary Rate ISDN Tester 3250
Trend AURORA DUET Basic Rate ISDN Tester 995
Trend S BUS Wiring Tester 350
TTC 147 2MBPS Handheld Communications Analyser 3750
TTC Fireberd Interfaces prices from 395
TTC Fireberd 6000A Communication Analyser 4250
TTC Fireberd PR-45 Printer For Fireberd 6000 350
TTC TIMS-45 TIMS Test Set For Fireberd 4000/6000 750
W&G DST-1 Handheld E & M Signalling Tester 750
W&G PCM-5/BN984/00.01/02/BN958.24 PCM Measuring Set 2500
W&G PFA-35 2MB/s Digital Transmission Analyser 3850

TV & VIDEO

Minolta CA-100 CRT Colour Analyser 2500
Tek 1751 PAL Vectorscope 2500

WIRELESS

Anritsu ME4510B Digital Microwave System Analyser 10950
HP 11759C RF Channel Simulator 6950
HP 83220A DCS1800 (1710-1880) Test Set 1750
HP 8920A/1/4/7/13/14/103 1GHz Radio Comms Test Set 3950
HP 8920A/3/4/5/50 1GHz Radio Comms Test Set 4750
HP 8920B/1/4/7/13/14/51 1GHz Radio Comms Test Set 3950
HP 8922M/001/003/101 1GHz GSM MS Test Set 5950
IFR 1600S/16/20/21/22/35 1GHz Radio Comms Test Set 4950
Marconi 2965/11 1GHz Radio Communications Test Set 5950
R&S CMD55/B1/4/6/9/41/42/43/44/51/61/018/020 RCTS 6550
R&S CMU200/B11/21/41/52/021/22/23 Tri-Band RCTS 21250
Racal 6102/04E GSM MS Radio Comms Test Set 2950
Racal 6103/001/002/014 Digital Mobile Radio Test Set 6500
W&G 4202S/AM Triband Digital Mobile Radio Test Set 4500
WaveTek 4201S Triband Digital Mobile Radio Test Set 3950

If you don't see what you want, please CALL

See our extensive online catalogue at www.TestEquipmentHQ.com

Flexible commercial solutions available on all products

FREE
Palm Zire shipped with every order over £5K

Prices shown are for guidance in £UK and are exclusive of VAT. Rental prices are per week for a rental period of 4 weeks. Free carriage to UK mainland addresses for Sales. This is just a selection of the equipment we have available - If you don't see what you want, please call. All items supplied fully tested and refurbished. All manuals and accessories required for normal operation included. Certificate of Conformance supplied as standard; Certificate of Calibration available at additional cost. Test Equipment Solutions Terms apply. E&OE.

01753 596000
Fax: 01753 59 6004

www.TestEquipmentHQ.com
email: info@TestEquipmentHQ.com