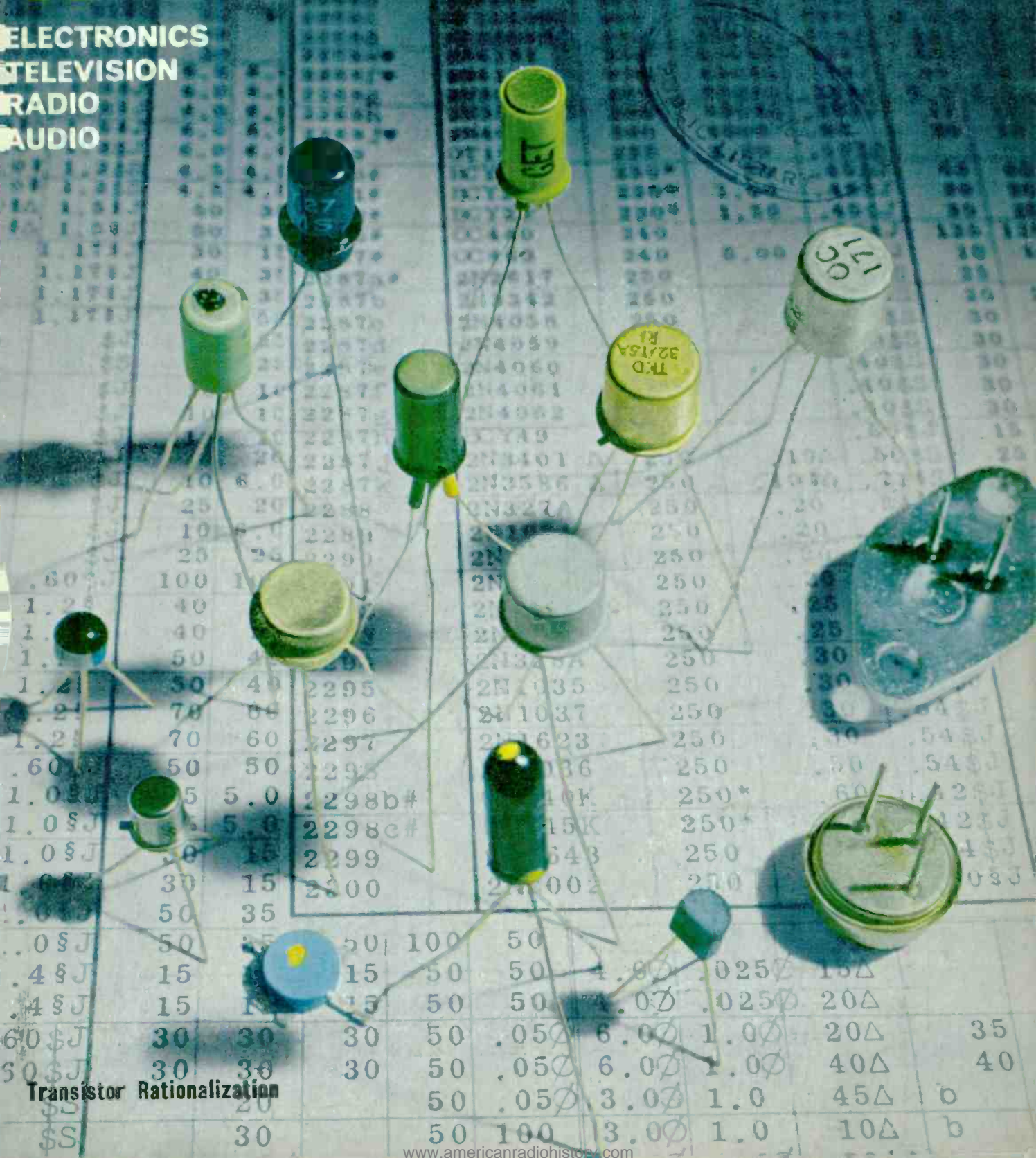


PORTABLE FREQUENCY STANDARD

FEBRUARY 1968
Three Shillings

Wireless World

ELECTRONICS
TELEVISION
RADIO
AUDIO



Transistor Rationalization

RELAYS

ex stock in 7 days

*C.S.A. APPROVED IN CANADA AND GREAT BRITAIN

*MK



- ★ 3 pole 7.5 amp
- ★ 5 million ops. min.
- ★ **12/4** each per 1000
- Single pole **9/7** each per 1000

- ★ 2 pole 5 amp
- ★ 5 million ops. min.
- ★ **14/8** each per 1000

*MM Contactor



- ★ 2 pole 15 amps
- ★ 5 million operations minimum
- ★ **17/8** each per 1000

MHP Plug-in relay



- ★ 4 pole, 1 amp
 - ★ 100 million operations
 - ★ **13/-** each per 1000
- SOLDER TERMS

2 pole **8/-** each per 1000

1051



- ★ Snap action microswitch relay
- ★ 7.5 amp. 1 million operations
- Also available in plug-in version

★ **7/5** each per 1000

*MKP Plug-in relay



*MK103

- ★ Single pole 3 amp
- ★ 1 million operations minimum
- ★ **5/11** each per 1000



MK403P NEW Plug-in relay



- ★ 4 pole 3 amp
 - ★ 5 million operations minimum
 - ★ **29/-** each per 1000
- SOLDER TERMS
- ★ **21/9** each per 1000


RELAYS

made to measure

APPROVALS: C.E.G.B. No. 131 & 92 · B.R. POST OFFICE KRL · U.K.A.E.A.

P.O. 3000 RELAY

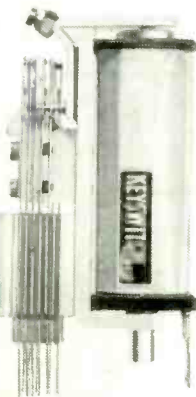- ★ Manufactured to full G.P.O. specification, also to Industrial Standards
- ★ Contacts up to 30 amp



P33 PLUG-IN RELAY

- ★ Plug-in version to BPO 3000 relay, made to measure for Industrial Applications
- ★ Contact ratings up to 10A/750V
- ★ Positive-lock retaining clip
- ★ 30 million operations minimum

P.O. 600 RELAY

- ★ Compact version of BPO 3000 relay
- ★ Contacts up to 10A
- ★ Sensitivities down to 30mW
- ★ Up to 18 contact springs




COMPONENT BOARD P304



- ★ Plug-in component board unit for low cost, easy chassis fabrication
 - ★ **15/-** each per 500
- FROM STOCK

CONTACTOR K700 RELAY

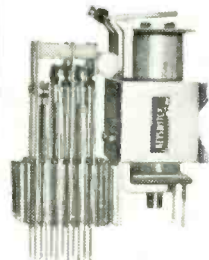- ★ High-current/high-voltage 3000-type relay
- ★ Contact up to 30A240V a.c.
- ★ Sensitivities down to 45mW
- ★ PTFE armature bar/lifting rods



KEYSWITCH RELAYS

KEYSWITCH RELAYS LIMITED

120/132 Cricklewood Lane · London · NW2 · Tel: 01-452 3344
Telex: 262754

WW-001 FOR FURTHER DETAILS

Wireless World

ELECTRONICS TELEVISION, RADIO, AUDIO

FEBRUARY 1968

Editor-in-chief:

W. T. COCKING, F.I.E.E

Editor:

H. W. BARNARD

Technical Editor:

T. E. IVALI

Editorial Assistant

B. S. CRANK

Drawing Office:

H. J. COOKE

Production:

D. R. BRAY

Advertisements:

G. BENTON ROWELL
(Manager)

J. R. EYTON-JONES

Iliffe Technical Publications Ltd.,
Managing Director: Kenneth Tett
Editorial Director: George H.
Mansell
Dorset House, Stamford Street,
London, S.E.1

Subscribers are requested to notify a change of address four weeks in advance and to return wrapper bearing previous address.

© Iliffe Technical Publications Ltd., 1968. Permission in writing from the Editor must first be obtained before letterpress or illustrations are reproduced from this journal. Brief extracts or comments are allowed provided acknowledgement to the journal is given.

VOLUME 73 No. 14

PRICE: 3s.

FIFTY-SEVENTH YEAR
OF PUBLICATION

- | | | |
|-----|---|--------------------|
| 665 | Technical Manpower | |
| 666 | Portable 1-MHz Frequency Standard | by L. Nelson-Jones |
| 672 | Distortions Inherent in P.W.M. | by K. C. Johnson |
| 677 | Log-Periodic Television Aerial | |
| 678 | Transistor Rationalization | by T. D. Towers |
| 682 | European Space Research | |
| 684 | GaAs Miniature Radar | |
| 685 | Acousto-electric V.H.F. Transmitter | |
| 693 | Emitter-coupled Emitter-timed
Multivibrators—2 | by G. B. Clayton |
| 696 | The Simple Transistor Equivalent Circuit and the
Impedance Transforming Node | by R. V. Leedham |
| 699 | Pin-board Construction | by G. W. Short |
| 701 | Ferrite Aerial Receivers | by R. S. Roberts |
| 702 | Miles-per-Gallon Meter | by D. J. Grover |
| 705 | Point-to-Point Review 1967 | by D. Wilkinson |
| 709 | Demonstrating Rectifier Action in Slow Motion | by T. Palmer |

SHORT ITEMS

- | | |
|-----|---|
| 671 | Further Notes on "V.H.F. Signal Generator" |
| 692 | Computer-aided Circuit Construction |
| 692 | Monolithic F.M. Discriminator |
| 692 | Picosecond Pulses Observed in Q-switched Lasers |
| 707 | Advice on Materials Technology |

REGULAR FEATURES

- | | | | |
|-----|-----------------------|-----|------------------------|
| 665 | Editorial Comment | 698 | World of Amateur Radio |
| 683 | Books Received | 700 | H.F. Predictions |
| 686 | World of Wireless | 706 | Literature Received |
| 688 | Personalities | 707 | News from Industry |
| 690 | Letters to the Editor | 710 | New Products |
| 692 | Technical Notebook | 718 | February Meetings |

PUBLISHED MONTHLY (3rd Monday of preceding month). Telephone: 01-928 3333 (70 lines), Telegrams/Telex: Wiworld Ilifepres 25137 London. Cables: "Ethaworld, London, S.E.1." Annual Subscriptions: Home: £2 6s Od. Overseas: £2 15s Od. Canada and U.S.A.: \$8.00. Second-Class mail privileges authorised at New York N.Y. BRANCH OFFICES: BIRMINGHAM: 401, Lynton House, Walsall Road, 22b. Telephone: Birchfields 4838. BRISTOL: 11 Marsh Street, 1, Telephone: Bristol 21491/2. COVENTRY: 8-10, Corporation Street. Telephone: Coventry 25210. GLASGOW: 123, Hope Street, C.2. Telephone: Central 1265-6. MANCHESTER: 260, Deansgate, 3. Telephone: Blackfriars 4412. NEW YORK OFFICE U.S.A.: 300 East 42nd Street, New York 10017. Telephone: 867-3900



**NO ONE OFFERS A
WIDER RANGE OF
MONITOR TUBES
THAN BRIMAR**

BRIMAR offers the most comprehensive range of monitor tubes in the country, together with the widest selection of phosphors.

The tubes range in size from 5" to 23". They can be used for television camera viewfinders, studio quality monitors, data displays and closed circuit television - twenty tubes in all! They have been designed to give maximum resolution under high ambient lighting conditions.

A variety of mounting and implosion protection methods, including self protection bonded glass faces are available from BRIMAR who are Britain's leaders in implosion protection.

Common features include magnetic deflection, electrostatic focus and aluminised screens.

The phosphors. In addition to the standard type for television, a wide selection of others is available offering varying degrees of persistence and colour.

**....OR A MORE
PERSONALISED
SERVICE!**

Every BRIMAR tube is backed by a first-class technical service and assistance on any type of problem involving its use in monitors - from special characteristics to circuit design. BRIMAR engineers are always available - contact is on a personal basis. Please telephone or write for full details.



Thorn-A.E.I. Radio Valves & Tubes Ltd.
7 Soho Square, London W1. Telephone: 01-437 5233

WW-097 FOR FURTHER DETAILS

1A 6759

Wireless World

ELECTRONICS, TELEVISION, RADIO, AUDIO

Technical Manpower

THE present shortage of scientists and technologists in the electronics industry, and the increasing demand for them, are highlighted in a recently issued study* by the Manpower Research Unit of the Ministry of Labour. This fact is widely known, of course, and is borne out by the enticingly worded display advertisements in the technical and lay press; indeed one company has said that it can cost a year's salary in advertisements to fill one vacancy!

This manpower study was conducted among 36 firms who, between them, have on their payrolls about 70% of the industry's 370,000 or more employees. The 72-page report covers the whole occupational structure of the industry and it is significant that scientists and technologists account for 6%, and technicians 6% of the industry's employees. In the capital goods sector the two categories each account for some 11%. (These figures contradict the usually quoted ratio of four technicians to each technologist.) Moreover, although the estimated total increase in staff over the five years from 1965 to 1970 is expected to be 28% the increase in scientists and technologists in the capital goods sector is foreseen as 49%.

It is obvious therefore that the present situation is unlikely to change for some time to come unless something can be done to encourage young people of both sexes to see a future in engineering. This note was struck forcefully by Major General Sir Leonard Atkinson in his recent I.E.R.E. presidential address. He said "If we [as a nation] are to survive and prosper we must reverse the accent on classical education and turn more to science and engineering. . . . The excitement of creating new tools . . . can only be engendered by stimulating a love of mathematics and physics—not by revering Latin and Greek, which, however commendable in humanistic studies, will never create . . . a transistor. . . . I believe that the newer places of learning should concentrate on courses and degrees in engineering and technology rather than trying to emulate the pattern of degrees in general science which suited the country's needs when older universities were established." This concern is also voiced in the Manpower report which records that several companies have expressed disquiet that some of the technological universities have been developing along more academic lines and losing, or loosening, their links with industry.


Little reference is made in the Manpower report to the question of the "brain drain" but Sir Leonard aphoristically sums up the present situation in the phrase "brains are like hearts—they go where they are appreciated"!

One large organization is quoted in the Ministry's study as saying "We cannot make use of arts graduates as scientists and technologists." However, the report adds, "it seems possible that there is scope for some replacement of scientific and technological manpower by suitable arts graduates, at least in some areas that are not 'technical'". Having elected to take an arts degree, is one to be debarred from making a contribution in a technological industry? After all, the ability to think analytically is not confined to science graduates. The arts graduate would obviously not want to take an engineering degree course, but could not postgraduate reorientation or conversion courses be devised by the colleges of technology which would help to equip the arts man for an engineering post? If this were done we might well find many of the long-standing vacancies in engineering filled.

* "Manpower Studies No. 5: Electronics" H.M.S.O.

Portable 1-MHz Frequency Standard

By L. NELSON-JONES, A.M.I.E.R.E.

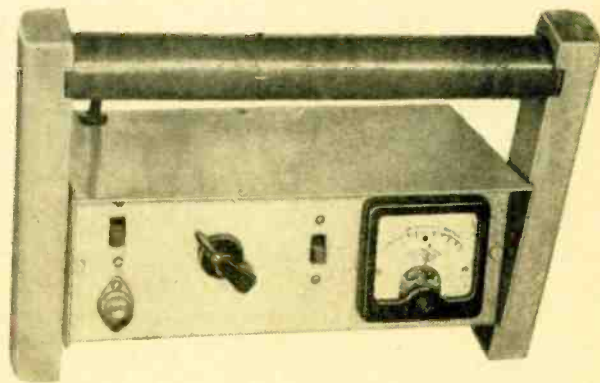

Uses crystal oscillator phase locked to 200 kHz B.B.C. Droitwich transmission

THE increasing accuracies being demanded in the generation and measurement of radio frequencies, together with the increasing use of digital frequency measuring instruments, make a frequency standard a necessary part of most laboratories today. The degree of accuracy required will naturally depend on the work in hand, and a number of types of standard are currently employed. These range from simple crystal or tuning fork oscillators to highly stable lenticular or Essen Ring crystal oscillators with elaborate temperature control, and for the very highest accuracies atomic standards are used. In addition, a number of transmitters radiate standard frequency transmissions throughout the radio spectrum, and for a very full treatment of this subject the author would refer readers to the excellent *Wireless World* article by J. McA. Steele*.

The l.f. and v.l.f. transmissions are most suitable for general use as frequency standards, and of these the 200 kHz transmission of the B.B.C. Radio 2 programme from the Droitwich transmitter is in many ways the most useful, since it is a continuous transmission and is not keyed or interrupted as many other transmissions are.

It is possible to use the 200 kHz transmission direct as a standard, with sufficient amplification and successive limiters to remove the amplitude modulation. The author has seen such a specially built receiver which

successfully used this method and which "piped" a standard 100 kHz signal through a group of laboratories.

An alternative for removing the modulation from the generated standard frequency is to compare the phase of the standard frequency transmission with the phase of a local oscillator and use the output of the phase comparator to control the local oscillator frequency so that it is locked to the standard transmission. The phase-lock system may then have a sufficiently long response time that it does not respond to the instantaneous phase modulation caused by the amplitude modulation of the transmitted carrier, and so the local oscillator will be free from the effects of this modulation.

The type of local oscillator used is of little importance so far as long term accuracy is concerned since the oscillator is locked to the transmission, but so far as short term accuracy is concerned a crystal oscillator is much to be preferred, for the following reasons: First, because of the narrow resonance bandwidth of the crystal, it will not respond to any but the slowest changes in the frequency control circuit, and it thus assists materially in removing the effects of carrier modulation. Secondly, because of the narrow "pull-in" range of such an oscillator, quite a good frequency standard is still available even if the standard frequency transmission should fail.

The portable frequency standard described uses a 1 MHz crystal oscillator, together with a variable capacitance diode and a blocking-oscillator divider ($\div 5$) in a phase-lock loop. A sampling technique is used rather than a phase sensitive detector. The frequency of the output is that of the crystal (1 MHz) but the output is provided by a non-saturating emitter coupled multivibrator locked to the crystal frequency. The output pulses are of 120 ns width, with fast rise and fall times. The instrument is battery operated. Fig. 1 is a block schematic showing the main functional units of the frequency standard. A complete circuit diagram is given in Fig. 2.

200 kHz receiver.—A ferrite rod aerial 8 inches long is contained in the paxolin tube forming the handle above the unit (see photo). This handle also contains the tuning capacitors for the ferrite rod, and the trimmer is accessible through a small hole in the rear of the tube.

The coupling coil of the aerial is connected to the receiver through a coaxial cable. The ferrite rod must, of course, be mounted clear of the case in this way in



Laurence Nelson-Jones, who is 38, is now a principal engineer with the Data Equipment Division of the Plessey Automation Group at Poole, Dorset, but he has spent the major part of his career (1953-65) with Kelvin Hughes which he joined after National Service in the R.A.F. At Plessey he is working on computer peripheral equipment, having previously spent a short time with S.T.C. at Basildon on p.c.m. repeater design.

order to avoid screening from the case, and instability caused by pick-up from the internal circuitry. The aerial rod used is the type made for the "Contessa" portable receiver, with the medium wave and car coupling coils discarded. (This item together with the other tuning coils, the crystal, etc., may be obtained from Henry's Radio Ltd.) It is important to ensure that, as the tuning and the coupling coils of the ferrite rod are wound over one another, the earthy ends of the two windings are adjacent, or the losses and stray capacitances of the coils will be very serious.

The first two stages of the receiver are conventional grounded-emitter r.f. amplifiers. These stages are,

however, run at only about 600-700 μ A of collector current, so that their gain is less than the maximum available from such a stage. This reduction of gain ensures a high margin of overall stability in the receiver, and avoids the necessity for neutralization. The 15k Ω damping resistors across the primary windings of both stages are required, not to damp the tuned windings themselves, but to prevent oscillation of the stages at the self-resonant frequency of the primary windings which are very loosely coupled to the main tuned winding. The damping resistors have little effect on the gain at 200kHz.

The third stage of the receiver (Tr3) is also of the

Fig. 1. Block schematic showing principle of operation of the frequency standard.


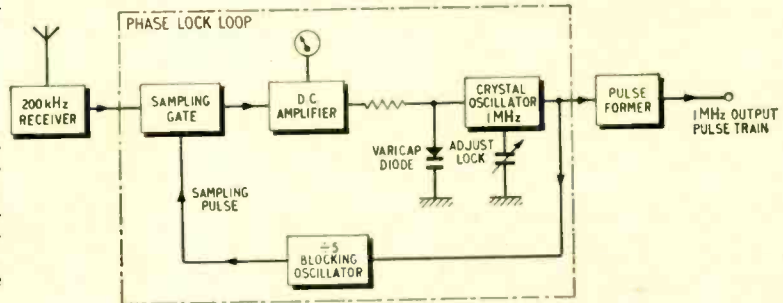


Fig. 2. Circuit diagram of the instrument. All resistors are $\frac{1}{2}$ W (10%, unless indicated). All tuning capacitors and 47 pF and 680 pF of 1-MHz oscillator and 820 pF capacitor of multivibrator are silvered mica. 2,200 pF of blocking oscillator is polyester. All other capacitors are ceramic. Values below 100 pF are N750; higher values are HI-K.

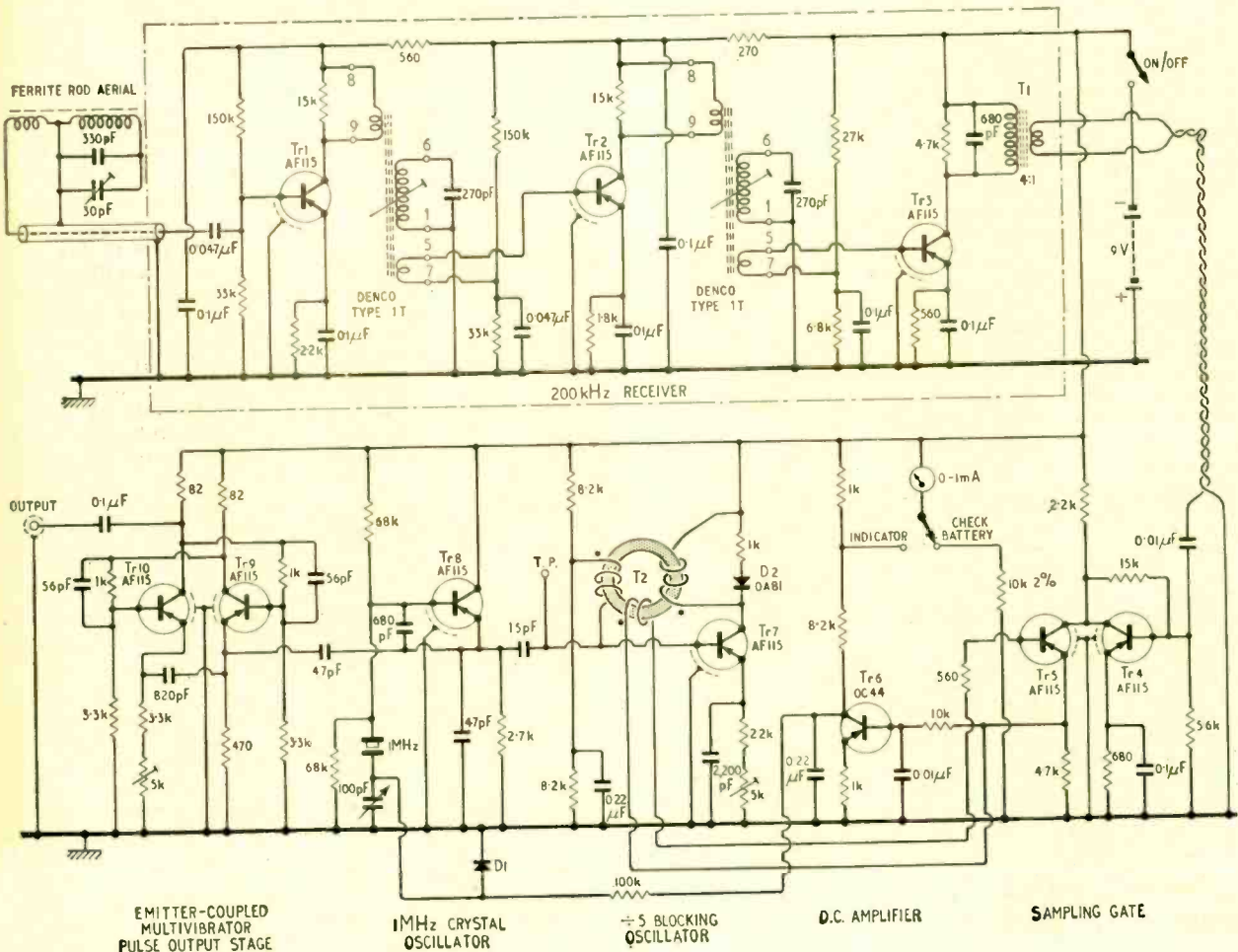

grounded-emitter type, but the load is a tightly coupled tuned transformer connected directly in the collector circuit. No adjustment of the tuning is provided as the working Q of the transformer is 3. The tolerances of the components therefore have little effect on the resonant impedance of the transformer. The secondary of the transformer is coupled by a twisted pair to the driver stage of the sampling gate.

The transformer (T1) is wound on a Denco iron-dust pot core assembly Type 10D. The primary winding,

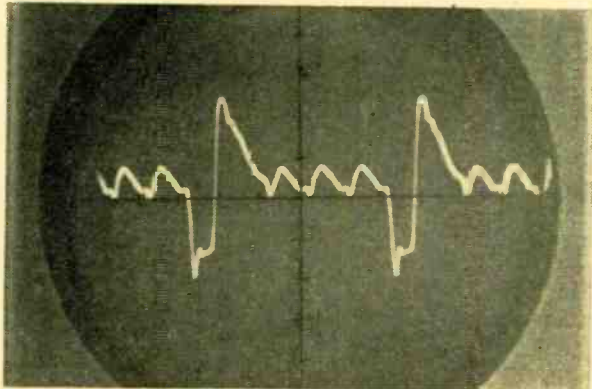


Fig. 3. Frequency divider waveform. $x = 1 \mu\text{s}/\text{div}$. $y = 1 \text{ V}/\text{div}$.

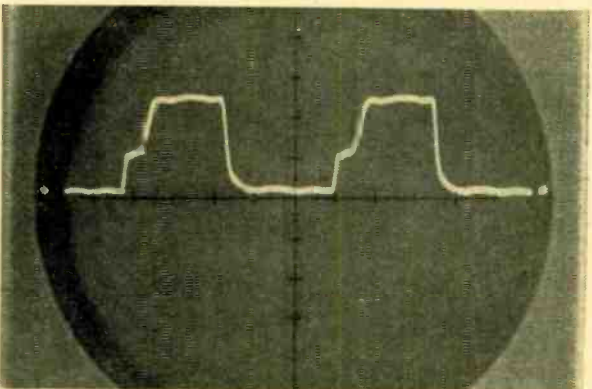


Fig. 4. Sampling gate waveform. $x = 1 \mu\text{s}/\text{div}$. $y = 2 \text{ V}/\text{div}$.

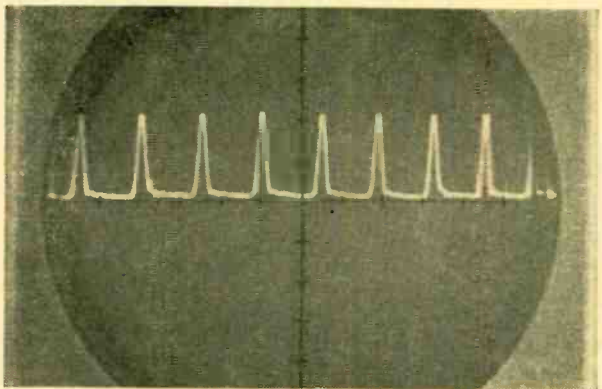


Fig. 5. Output pulse waveform. $x = 0.6 \mu\text{s}/\text{div}$. $y = 0.5 \text{ V}/\text{div}$.

(On above reproduced photos, $\text{div.} = 0.5 \text{ cm approx.}$)

of 160 turns of 40 s.w.g. enamelled copper single silk covered wire, is wound with 100 turns in one of the outer slots and 60 turns in the centre slot of the bobbin. The secondary is wound with 40 turns of 34 s.w.g. enamelled copper wire in the other outer slot. These windings give a primary inductance of 1mH. The iron dust adjusting core may be fitted if desired but, as has been said, it will have little or no effect on the gain due to the low working Q.

1 MHz crystal oscillator.—The circuit operates at the fundamental parallel resonance of the crystal, which is an S.T.C. Type 4044 (AT cut). An adjustable capacitor is included in series with the crystal so that the oscillation frequency may be pulled to exactly 1 MHz. The variable capacitance diode D1 is also connected at this point. The variable capacitance is mounted on the front panel so that the phase-lock may be adjusted.

A number of diode types were tried as reverse biased variable capacitance devices, since no diode specially selected for this purpose was available at the time. Standard diode types range in effective capacitance from the 200-500 pF of the 400 mW zener diodes to only 1-4 pF of such high speed diodes as 1N914 and 1N916. It was found that a diode with a suitable range of capacitance for this application could be found among the smaller rectifier diodes such as OA200, OA202, 1S120 series, and 1S130 series, CV7040, etc. An OA200 was used in the prototype. The electrical Q of such diodes is probably not high, but as the oscillator is fairly tightly coupled the effect of the diode being connected is negligible, nor is the amplitude greatly affected by the amount of reverse bias applied to the diode.

Blocking oscillator frequency divider.—A number of locked divider circuits were tried, but that used² was found most suitable on a number of counts: (1) It is very stable, and is relatively unaffected by temperature and voltage variations. (2) The variable resistor is at earth potential on one side, making it easier to bring this control out. (3) The use of a blocking oscillator enables a suitable sampling pulse to be generated directly.

The divider is coupled to the crystal oscillator through a small capacitor, and the waveform at the base is available on a socket on the rear panel for adjustment purposes together with the 5k Ω variable resistor of the divider circuit. The waveform is shown in Fig. 3, as it appears when set to the correct division ratio.

The transformer T2 is wound on a Mullard ring core Type FX1593 (obtainable from Henry's Radio Ltd.) or FX308, nylon coated. If the uncoated core FX1593 is used, it should first be covered with a layer of insulation, as the abrasive nature of the ferrite quickly strips the enamel from the wire in winding. In the prototype the core was first wound toroidally with very narrow strips of paper "masking" tape.

The primary (collector) winding is of 25 turns of 34 s.w.g. enamelled copper wire and occupies about a third of the periphery of the core, wound as a single layer.

The secondary (base) winding is of 12 turns of 34 s.w.g. enamelled copper wire, also wound as a single layer adjacent to the primary.

The coupling winding to the sampling gate is of 6 turns of 34 s.w.g. enamelled copper wire, wound in a single layer in the remaining space.

In the prototype a 4 B.A. nylon screw was then passed through the centre aperture and secured in place by a nylon nut. The whole assembly, except for the remaining thread, was then dipped in cellulose enamel to lock

the wires in position. (An equally suitable coating would be obtained with one of the polyurethane varnishes.) The excess thread was then used to mount the toroidal transformer onto the chassis with a second nut.

The phasing of the windings, together with the relative position of the windings, is indicated on the circuit diagram (Fig. 2).

Sampling gate and d.c. amplifier.—The driver stage of the sampling gate (Tr4) is a conventional grounded emitter stage, with a degree of d.c. feedback since the base bias potentiometer is connected to the collector. This configuration does not result in any great degree of a.c. feedback since the source impedance is low (around 300 Ω). In normal operation in the Bournemouth area, where the 200 kHz signal is none too strong, this stage is driven fully into limiting; indeed full limiting takes place in this stage over nearly the whole of the 360° of rotation of the receiving aerial. Only near the two nulls in the response is there any appreciable reduction in the signal fed to the sampling switch (Tr5).

At full signal the collector potential of Tr4 swings between -2.4 V and -7.4 V. The waveform at this point is shown in Fig. 4.

The notch in one side of the waveform is due to the loading effect of the sampling switch during the sampling period, and is typical of the waveform when phase-lock is established.


The sampling switch Tr5 is brought into conduction for approximately 1 μ s every 5 μ s by the sampling pulse generated in the blocking oscillator divider. This pulse is applied through a limiting resistor between the base and emitter of Tr5. During the sampling period, therefore, the emitter circuit of Tr5 is connected to the collector of Tr4. The average d.c. potential at the emitter of Tr5, after smoothing by the RC network feeding this level to Tr6, is approximately a fifth of the potential of the collector of Tr4, and will therefore vary between approximately -0.5 V and -1.5 V, depending on the relative phase of the sampling pulse and the 200 kHz signal at the collector of Tr4. The gain of the d.c. amplifier Tr6 is determined by the ratio of the collector load to the emitter resistor, and with the meter in circuit is approximately eight times. Thus the collector potential of Tr6 will vary from the "bottomed" state which is just reached when the collector is at -1 V up to about -6.5 V at minimum base input.

The potential at the collector of Tr6 is applied to the reverse biased diode D1 through a 100 k Ω resistor to afford isolation between the d.c. amplifier and the crystal oscillator, and to minimize the loading on the crystal oscillator.

Output pulse generator.—The output pulses are generated by a non-saturating emitter-coupled multivibrator locked to the crystal oscillator frequency through the small coupling capacitor between the emitters of Tr8 and Tr9. The lock-in of the stage is set by the variable emitter resistor of Tr10.

The output pulse at the collector of Tr10 is of approximately 1 V amplitude and is positive-going. An almost identical negative-going pulse is available at the collector of Tr9 if required. The output waveform as viewed on the author's oscilloscope (of 4.5 MHz bandwidth and 80 ns risetime) is shown in Fig. 5. The pulse has, however, been examined on an oscilloscope of 4.5 ns risetime, when the pulse was seen to be rectangular in shape. The risetime (10-90%) was 20 ns, and the falltime 30 ns. There was a slight overshoot on leading and trailing edges. Unfortunately no camera was available at the

Fig. 6. Modification to d.c. amplifier output circuit for obtaining higher short-term accuracy.

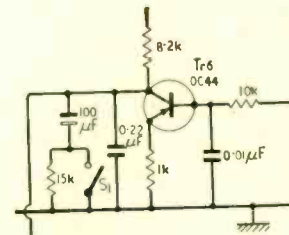

time to record the waveform. If this pulse is to be conveyed over any distance it should be coupled via 75-80 Ω coaxial cable terminated at the receiving end, or the waveform will be hopelessly mutilated, and the harmonic content greatly reduced.

An effect was observed on the wide-band oscilloscope which confirms the finding of appreciable though small harmonics in the output pulse waveform at 200 kHz intervals. It was observed that if the scope was triggered at a speed which was a multiple of 5 μ s then the trace was sharp, whereas if it was triggered at another speed the pulses were very slightly blurred due to a cyclical phase modulation of the 1 MHz crystal oscillator by the blocking oscillator divider operating at 200 kHz. Something of this effect is just about visible in Fig. 5 where the base of each fifth pulse is slightly different.

In practice the effect is of little consequence, the main effect being to give harmonics in the output at 200 kHz intervals in addition to the main ones at 1 MHz intervals. If, however, the effect were felt to be undesirable it could largely be eliminated by placing a buffer stage between the crystal oscillator and the blocking oscillator divider.

The choice of a narrow pulse for the output was made in the interests of equality of harmonic levels at the even and odd harmonics. A blocking capacitor is included in the output lead to prevent damage to the 82 Ω collector load from short circuiting of the output terminals.

Setting-up procedure.—As will be seen in the photograph on page 666, there are three controls on the front panel. An on/off switch is on the left. A meter switch adjacent to the meter permits a check of the battery voltage in the upper position and connects the meter as a phase-lock indicator in the lower position. (The meter used on the prototype had a right-hand zero.) The large dot on the meter scale merely indicates a suitable setting for the pointer when setting the phase-lock, it being the average of optimum settings at minimum (7 V) and maximum battery voltage. The third, rotary, control is the variable capacitor of the crystal oscillator used to set the phase-lock.

To set up the instrument correctly the knob is slowly turned from left to right when the beat seen on the meter will slowly drop in frequency until at about 1 Hz the beat will cease suddenly. Further movement of the knob moves the pointer of the meter over the scale until at the limit of the phase-lock range the meter suddenly starts beating again, the frequency rising as the knob is further turned. The correct setting is achieved by turning the knob to the position where the oscillations first cease, and then further adjusting the knob until the pointer of the meter is over the centre of the scale (at the dot mentioned above). Normally if this setting is not disturbed the unit can be switched off, and then on again, when it will drop back into correct lock within about 1 second.

Accuracy.—The $0.22\ \mu\text{F}$ capacitor at the collector of Tr6 provides additional smoothing of the voltage fed to variable capacitance diode D1, but it is of insufficient capacitance to eliminate any residual modulation present in the 200 kHz waveform of the collector of Tr4, and hence present in the voltage of the collector of Tr6. The effect of residual modulation is to cause short-term

phase modulation of the 1 MHz output and hence to reduce the short-term accuracy. Since the total pull-in range of the phase-lock loop is only about 2 Hz the effect of this residual modulation (usually less than 10 % peak-peak) is only a fraction of a hertz at the 200 kHz rate, or less than one hertz at 1 MHz.

The accuracy is thus better than one part in 10^6 over a period of one second (or about three parts in 10^6 if the signal does not produce full limiting at the collector of Tr4). Over a period of 10 seconds it is one part in 10^7 , over 100 seconds one in 10^8 , and so on. The long-term accuracy is, of course, the accuracy of the transmitted carrier, i.e., five parts in 10^{10} , with a drift rate of less than one in 10^{10} per day³.

The size of the capacitor at the collector of Tr6 cannot be greatly increased, or it will be found that it is not possible to set the phase-lock loop up initially. However, the circuit of Fig. 6 is suggested for those applications where higher short-term accuracy is needed. The phase-lock is set up with S1 open, when the circuit is similar to that of Fig. 2. After a period of some 30 seconds, to allow for the $100\ \mu\text{F}$ capacitor to charge up, S1 is closed, which may cause slight temporary disturbance of the phase lock. After a further 30 seconds or so the phase lock will be steady, and largely free from modulation effects, since the low frequency cut-off of the phase-lock loop is below the lowest modulation frequencies. Switch S1 must be opened again before switching on, or the phase-lock will not re-set. The $100\ \mu\text{F}$ capacitor should preferably be of a low leakage type, such as a solid dielectric tantalum or wet tantalum electrolytic. The working voltage of the capacitor should be greater than the supply voltage, which can be up to 10 V with a fresh battery. The majority of users will find that this modification is not necessary.

Power supply.—A standard 9 V dry battery has been used in the prototype, and stabilization of this supply has not been found necessary. The main effect of reduced battery voltage is loss of output pulse amplitude.

If desired it would be a simple matter to build in a mains supply circuit with stabilization (perhaps by a zener diode only). Care should be taken, however, to provide adequate suppression of the mains supply lead, both to avoid the introduction of interference to the unit and to avoid the radiation of interference from the internal circuits, especially as the harmonic content of the output pulses covers a very wide frequency spectrum.

Constructional notes.—Figs. 7, 8 and 9 show the construction used in the prototype unit. The packing density is rather high, and if the author were to make a second unit it would be of larger size and use a larger battery than the PP7 shown. Despite its small size this battery gives about 40 hours of intermittent use at the normal load current of 28 mA at 9 V, and is quite adequate for the purpose for which the standard was built, namely as a reference for the calibration of signal generators, digital frequency meters, etc.

Figs. 8 and 9 show the construction of the 200 kHz receiver, which is built in a standard Eddystone die-cast box, Type 896. Screening of the receiver in this way is essential for stability. The screening cans of the coils are the cans in which the coils are supplied, as suggested in the leaflet accompanying them. The numbers on the coils in the circuit diagram are the pin numbers of the coils.

Those readers wishing to modify the circuit to allow

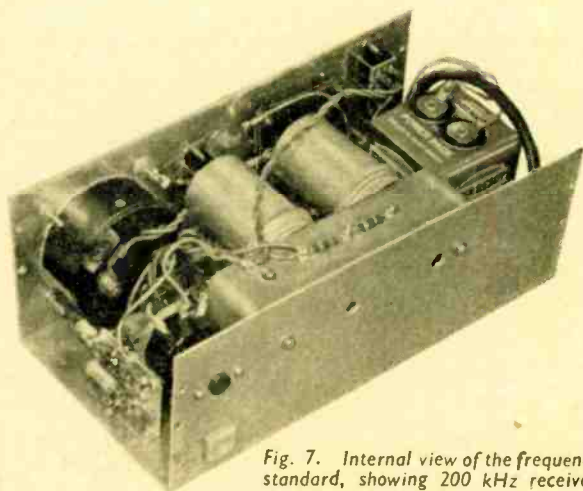


Fig. 7. Internal view of the frequency standard, showing 200 kHz receiver that also appears below (Fig. 8).

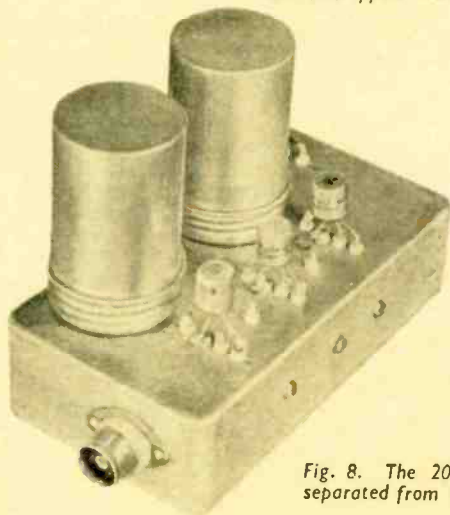


Fig. 8. The 200-kHz receiver separated from the instrument.

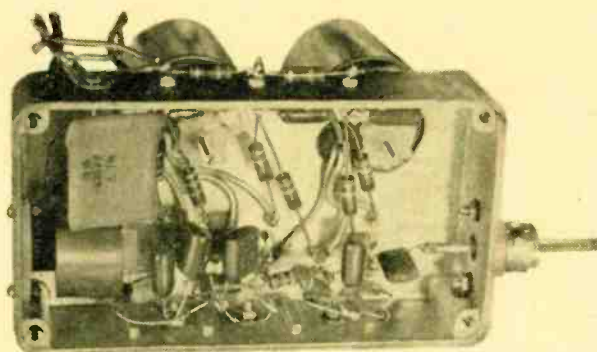


Fig. 9. Circuit wiring in the 200-kHz receiver.

use of silicon n-p-n devices should find that the BC108 is suitable, but slight changes of value may be necessary, for instance a reduction in the value of the emitter resistors of transistors 1, 2 and 3 to maintain the value of the collector currents of those stages. It may also be necessary to alter the values of the 56 pF capacitors in the output pulse generator stage Tr9 and Tr10 to obtain a satisfactory pulse shape. If this change is made it will be necessary to reverse the two diodes, the meter and the battery connections. In addition, if the modification of Fig. 6 is incorporated, the electrolytic must be reversed. The output pulse will be negative, but can be made positive by connecting the output capacitor to the collector of Tr9. It should be added that the author has not tried these modifications, but that since the circuit is in no way critical, he sees no reason why the change to n-p-n silicon devices should not be successful.

Layout is not critical, but leads should be kept short. In the unit shown the circuits (other than the receiver) are constructed on small aluminium plates using A.E.I.

Polytags Type PT23, which are p.t.f.e. feed-through insulators. The progression of the circuit as shown in Fig. 2 should be followed in the physical layout to avoid unnecessary stray couplings between different parts. The output pulse generator was built on a separate plate and is coupled to the output socket through a coaxial cable.

REFERENCES

1. Motorola "Switching Transistor Handbook," 2nd edition. Section 8.4, page 276.
2. Mullard Reference Manual of Transistor Circuits, 1st edition. Section 8.4, page 276.
3. *The Radio & Electronic Engineer*, the journal of the Institution of Electronic and Radio Engineers, publishes each month a record of the daily performance of the GBR (16 kHz) MSF (60 kHz), and Droitwich (200 kHz) standard frequency transmissions. (GBR is a standard time transmission and has at present the internationally agreed offset of -300 parts in 10^{10} . The MSF and Droitwich transmissions have no offset as referred to the basic standard caesium F m (4-0)—F m (3-0) transition at zero field of 9, 192, 631, 770.0 Hz.)

Further Notes on "VHF Signal Generator"

By G. W. SUTTON, on his article in the December 1967 issue

Attenuator piston.—Since the attenuator drawings were made available Mr. V. J. Cox has pointed out that there is no advantage, and a definite disadvantage, in making the perspex piston as much as $\frac{3}{8}$ inch in axial length. It is suggested that this dimension should be reduced to $\frac{1}{4}$ inch, thus reducing the inductance of each turn of the piston coil to about one third of its previous value. The number of turns on the coil may therefore be almost doubled for the same total coil-inductance as before. The limit to the number of turns is set by the necessity to keep the inductive reactance of the coil well below 75Ω at the highest frequency generated. As the maximum output voltage was already within the range of a valve-voltmeter there is no particular advantage in raising it by 6 dB or so, but the battery voltage can be reduced, for the same output, to 20 V or less.

Coaxial cable.—Good quality 75Ω cable should be used for the coaxial output of the piston attenuator. A cheap open-mesh braiding is now in almost universal use, but some readers may not be aware of its shortcomings.

Battery voltage.—The battery voltage suggested is above the transistor manufacturer's maximum rating. The load current, on the other hand, is only about 1/20th of the rated maximum. The author has carried out tests at considerably more than 36 V, and has used BFY18s and BSY26s in signal generators at 36 V for protracted periods during the past 18 months. At no time has any instability been detected, nor has the output varied. However, if doubt is felt at this point, or more especially, if a germanium alternative is used, the piston turns may be increased to 4 or 6 on the shorter piston mentioned above, and the battery voltage correspondingly reduced. This will still provide a maximum output voltage readable on a valve-voltmeter.

Additional output.—For some tests on television sets an r.f. voltage of 1 V or more is needed. An additional, higher voltage, output from the signal generator has been provided by incorporating a pick-up coil coupled to the r.f. oscillator coil. A strip of perspex 4 mm thick was mounted on the rear face of the oscillator coil (see photo on p.575 December issue, and piston attenuator drawings). Four small holes were drilled laterally through the strip and 2 turns of 30 s.w.g. wire were threaded through these holes, fixed in place by squeezing a little cement into each hole, and terminated on a 75Ω cable socket mounted on the top of the oscillator shield. Two to three volts r.f. are induced in this coil and, provided the leads to the receiver under test are short, can be applied undiminished to a valve grid. The lid of the outer shield has to be removed, but the resulting leakage is of no significance in tests at this level.

Better shielding.—The front end of the piston attenuator projects through a circular hole in the inner shield and is connected to it by phosphor-bronze springs. Somewhat better shielding is obtained if a slot of the same dimensions as that in the end of the attenuator is cut in the inner shield instead of a circular hole. The oscillator coil mounting should then be altered to bring the flat side of the coil to within 2 mm of this slot. The springs may be omitted and the attenuator face should be brought also to within 2 mm or so of the outer surface of the inner shield. The two slots should face one another accurately.

Corrections.—In the caption to Fig. 7 the reference to graph point 4/7 should read "e.g. 4/7 is the beat with the 7th harmonic of No. 4 crystal. . ."

In the last paragraph on p.573 the thickness of the coil turn spacing washers is incorrectly given as 0.400 in. This should be 0.040 in.

3: DISTORTIONS INHERENT IN P.W.M.

By K. C. JOHNSON, M.A.

THE two previous articles have described the possibility of making power amplifiers of high efficiency using components with wide tolerances by exploiting the class D principle. It has been pointed out that amplifiers of this type may suffer from serious distortion arising from two quite distinct causes. First there is the usual sort of trouble due to the non-linearity present in all electronic systems. This causes the amplitude of the final switching square-wave to have undesirable variations, and also degrades the precise timings of the edges as they pass through the several stages of amplification. These effects are analogous to those which are familiar in the more conventional types of amplifier and to a large extent they can be overcome in the same way—by the use of negative feedback. In a class D circuit this feedback has to be taken from the output of the switching stage and is used to modify the edge-timings at the square-wave generator, but the action is essentially the same as usual.

The second distortion effect is inherent in the class D principle itself. It comes from the fact that the output of a circuit of this type is taken from the powerful square-wave source to the loudspeaker through nothing more than a simple linear filter network. This means that the edge-timings of the square-wave should ideally possess the peculiar property that all its frequency components within the band to be amplified correspond exactly with those of the required signal; whilst the components at other frequencies must be such as to make the total form a square-wave. This very particular requirement is certainly not met by the square-wave from just any circuit that gives a variation of the mark-space ratio. It is true that moderately low levels of distortion can be obtained with a simple square-wave generator circuit if the average switching rate is made substantially higher than the highest output frequency required, and the maximum range of mark-space variation is severely restricted, as was the case in the circuit described last month, but the utilization of the output transistors in such an arrangement is very poor.

Alternatively we can consider more carefully what the exact mathematical requirements are and attempt to devise a generator principle that is nearer to the ideal but yet avoids being too complicated to be practical. This article is concerned with this approach, but, as the reader may suspect from the fact that it is appearing after the amplifier design, there is not going to be any clear conclusion and it seems that any real improvements in the performance of the square-wave generator are likely to be more trouble than they are worth. There is always the hope though, that this assertion will be proved false by some new development.

In order that an amplifier of the class D type shall behave sensibly for input signals of any nature, the switching square-wave cannot be allowed to stop or change dras-

tically in any way. In particular it must run steadily with a near 50:50 mark-space ratio when there is no input applied and change progressively in a smooth manner so as to give the required output when the input is varied. Clearly this is a process of modulation. The zero-input square-wave is an unmodulated carrier which must be generated within the circuit itself, whilst the change, when an input is applied, must follow some well defined modulation law.

Most readers will be familiar with the process of modulation as applied to sinusoidal carrier waveforms in radio practice, a.m., f.m., s.s.b. and so on. In every case appropriate demodulator circuits are necessarily incorporated in the receiver and it is normally possible so to design these that the original modulating waveform can be recovered without any distortion being introduced by the modulation process. The modulation technique that we require for the class D type of amplifier, on the other hand, must work without a demodulator of any sort. Thus if a distortionless output is to be obtained the modulation law must be such as to generate precisely that square-wave which contains the correct frequency components, and no other.

Suppose that we have a carrier square-wave of repetition frequency f_c under our control throughout an interval of time t during which it makes some exact number, $n=t/f_c$ of complete cycles. There will, of course, be $2n$ edges occurring during this time, since there are two per cycle, and in the modulation process each of these edges may be displaced independently by any required fraction of their separation. Thus the system has $2n-1$ degrees of freedom, since one of the edge positions must effectively be used as a reference to measure the displacements of the remainder. But it is well known that in this kind of process the only distinguishable frequency components in the modulation are those which make an exact integral number of cycles during the interval of time t (it is as if this interval were necessarily joined round on itself head-to-tail). These components have the frequencies $0, 1/t, 2/t, 3/t$ and so on. Now for the first of these, the d.c. term, there is an amplitude only, whilst the remainder have both amplitude and phase. Thus, provided that the amplitudes are not so excessive that the edges try to cross-over with their neighbours, we can use our $2n-1$ degrees of freedom to determine the values of all the frequency components from 0 to $(n-1)/t$ inclusive. But this upper frequency is $f_c - 1/t$ and, since the argument holds good as t increases to infinity, we therefore find that we can in principle so modulate the edge-timing of a square-wave as to make it have any frequency components of reasonable amplitude that we wish in the band between zero and just less than the carrier frequency itself.

Thus there is no theoretical objection to the use of a carrier which is only just above the highest frequency

that we wish to amplify. The edge-timings of such a carrier can be modulated so as to achieve the result we are seeking. In practice, though, there will have to be a decent margin left to allow for the attenuation change of the filter, which must pass the required signal whilst suppressing not only the carrier but also the mass of complicated components that will inevitably be present above it. So far then the prospect is quite encouraging and we have established that the modulation process we are seeking does at least exist. Let us next consider what the available modulation processes can in fact do.

Since a square-wave has both upward and downward edges there can be two distinct forms of modulation applied to it. The first is, of course, mark-space modulation, where the two types of edge are displaced in opposite directions in proportion to the magnitude of an applied signal. When the input signal changes, each displacement is proportional to the input at the instant that the edge is made, rather than to the value at the time from which the edge has been displaced. The magnitude of the modulation will be best measured in this case by the ratio of the displacement to the time of a quarter-cycle of the carrier and this will be called the modulation index, x . Clearly this index has strict limits and cannot go beyond the range from plus to minus unity without trouble due to the edges trying to cross over.

The second form of modulation is obtained by displacing all the edges in the same direction, regardless of type, by an amount which is again proportional to the input signal at the instant each edge is made. This is obviously a form of phase modulation and the magnitude can be measured in terms of the phase angle of the carrier that is equivalent to the displacement. This angle will be called θ and it will normally be convenient to measure it in radians. There is in principle no limit to the value that this angle can have, but as with sine-wave modulation, the value will not normally exceed a radian or so when the mechanism is of the nature of a "phase modulation," but can have vastly greater values when a "frequency modulation" is involved. The distinction between the two is not a rigid one but is convenient and we shall use it here in the usual way.

Now clearly it is possible to generate a square-wave which has either of these forms of modulation, or even both at the same time if required. An analogue computer type of circuit can determine when each edge ought to be formed and then some form of flip-flop can be triggered so as to produce the required square-wave. There is a slight oddity in that it is possible for a sufficiently rapid change of either kind of input to cause an edge to be first made, then reversed, and then made again within a single half-cycle of the carrier, so that a triplet results. But this is nothing to worry about because the input waveforms of practical amplifiers never change sharply enough for this effect to occur. In general these modulation processes work quite well and there is no ambiguity about the square-wave produced for given modulating waveforms.

This is not true in the reverse direction since, in contrast to a sine-wave, a square-wave carries modulation information only at the instants when edges occur rather than continuously. Thus it is not possible to say unambiguously what the modulating waveforms were from an examination of the square-wave produced, and, in particular the same resultant square-wave can be obtained from a variety of different modulating waveforms. But things are not as bad as they may seem, since the ambiguities all result from the effects of reflection of frequency components through the effective sampling frequency. They can thus be eliminated for practical purposes if we

consider modulating waveforms whose frequency components are strictly limited to values below the carrier and this limitation will be assumed for the remainder of this article.

It is not unduly difficult then to show that the amplitude A of a square-wave made from a carrier of angular frequency $\omega_c = 2\pi f_c$ by the application of both forms of modulation at the same time can be expressed as a mathematical series as follows:

$$\begin{aligned}
 A = & x + \frac{4}{\pi} \cos\left(\frac{\pi x}{2}\right) \cos(\omega_c t - \theta) \\
 & - \frac{4}{2\pi} \sin\left(\frac{2\pi x}{2}\right) \cos 2(\omega_c t - \theta) \\
 & - \frac{4}{3\pi} \cos\left(\frac{3\pi x}{2}\right) \cos 3(\omega_c t - \theta) \\
 & + \frac{4}{4\pi} \sin\left(\frac{4\pi x}{2}\right) \cos 4(\omega_c t - \theta) + \dots
 \end{aligned}$$

It will be seen that each term in this series consists of the product of an amplitude modulating factor, which is some function of the mark-space modulation index, and a cosine, which represents a sort of harmonic of the phase modulated carrier frequency. If both x and θ have steady values then the spectrum consists simply of a series of components on the harmonic frequencies. But if x and θ are made to vary in response to some applied input waveforms then each of these harmonic components becomes surrounded by a cluster of sidebands. Since the modulation laws involved are not simple even a single incoming tone will normally make each cluster an infinite series of sidebands spaced regularly at multiples of the modulation frequency with amplitudes which tend to decrease at greater distances from the harmonic, but which never actually become zero anywhere in the frequency range. When more than one input frequency is applied there will also be further sets of sidebands spaced from each harmonic by sum and difference frequencies, so that the pattern will be vastly more complicated.

IDEAL MODULATION SYSTEM

It will be noticed that the zero harmonic, or baseband, term at the start of this mathematical series is a plain unvarnished x . Thus if the index of the mark-space ratio modulation is made to follow the input waveform directly, this term alone will provide exactly the correct frequency components that we require for the proper reproduction of the signal. Since the later terms can only contribute components at frequencies which are of the nature of sidebands of the harmonics of the carrier frequency, it is inconceivable that these could also come at the wanted signal frequencies, since the carrier frequency is not in general related to the modulation in either its phase or its frequency. Thus we find that in the ideal system that we are seeking the mark-space modulation must have this simple proportionality to the input, and our problem is reduced to that of finding what function of the input voltage we must use for making phase modulation if we are to achieve the elimination of all the sidebands that fall within the band to be amplified as a result of this amount of modulation of the mark-space ratio.

Fig. 6 shows how this cancellation of the unwanted sidebands by the application of phase modulation can occur in a very simple case. The top diagram (a) shows a half-cycle of a low-frequency sine-wave applied to the amplifier input. Diagram (b) shows the square-wave

that corresponds to this if only the mark-space modulation is applied. The next diagram (c), indicates how we can extract an amplitude modulated fundamental component sine-wave from this square-wave, since a 50:50 square-wave plainly has a bigger fundamental component than one of the same amplitude but different mark-space ratio. It will be noticed that this modulated sine-wave is the second term of the mathematical series given previously. Diagram (d) illustrates how the amplitude modulation of this sine wave can be represented approximately by the addition of the two most important sidebands, which are at the frequencies $f_c - 2f_m$ and $f_c + 2f_m$ where f_m is, of course, the modulation repetition frequency and the usual "spinning vector" method of representation is used. But if we introduce also the amount of phase modulation of the square-wave represented by the "spinning vectors" shown in diagram (e), then the two sidebands at the lower frequency will cancel whilst the important modulation is almost unaffected and no serious extra sidebands are introduced.

It is not very difficult to show from these diagrams that if the original modulating waveform is a simple sine wave of such amplitude that the index for the mark-space ratio modulation is:

$$x = X \cos \omega_m t$$

where ω_m is the angular modulation frequency, and X is the peak amplitude of sine-wave modulation as a fraction of the limit of the system, then the phase modulation required to eliminate the sideband at $f_c - 2f_m$ will be very close to:

$$\theta = \left(\frac{1 - \cos(\pi x/2)}{1 + \cos(\pi x/2)} \right) \sin 2\omega_m t$$

But this phase modulation only gives approximate cancellation of one only of the sidebands for the very simple case of a single sine-wave at the input, and it is already most unpleasantly complicated. It seems hard to believe that there is not some other better approach

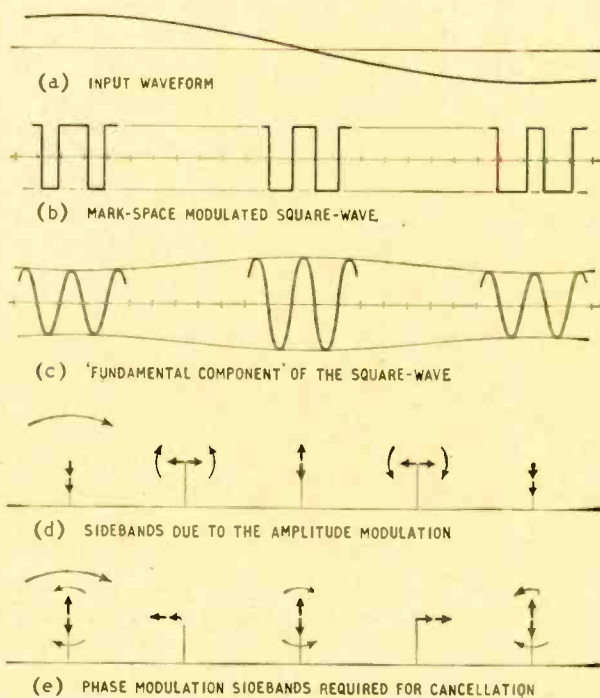


Fig. 6. Two forms of modulation combined to eliminate sidebands.

whereby the correct phase-modulation to eliminate all the unwanted sidebands for any modulation waveform can be derived, but the author has been unable to find it.

The problem is in many ways analogous to that of producing s.s.b. modulation of a sine-wave, and there are two respects in which the systems will certainly prove to be similar. The first of these is that the extra modulation that must be applied to give the elimination of the unwanted sidebands will be of the nature of a "phase" modulation rather than one of "frequency." Thus in an ideal system the average carrier frequency will be constant regardless of the modulation, and the phase displacements will, in fact, be limited to no more than 90° at the most. Secondly we must expect that in constructing an ideal system we shall have to use the quadrature function of the input waveform. This is a sort of half-way between the integral and the differential waveforms and is similar to them in that every frequency component is separately phase-shifted through a right-angle, but differs in that the amplitudes are left unchanged. It is well known in s.s.b. techniques that this waveform can be obtained only by the use of a filter network whose cost and complexity increases rapidly as the performance is made more accurate and maintained over a wider frequency range. To obtain an output with the phase-shift correct to within say $\pm 10^\circ$ throughout the audio-band would require a network costing more than most amplifiers, so that our ideal system is hardly likely to be an economic one.

We must never forget that it is not really the ideal that we are seeking but merely some system which is an appreciable improvement over those already known. We have been considering the perfect solution only as a guide to indicate how such an improvement might be obtained. Let us now consider just how serious these distortion effects are in the modulation systems that have been used in published designs of amplifier.

PRACTICAL MODULATION SYSTEMS

All the practical designs of class D amplifier of which the author is aware employ one or other of two quite distinct systems for the generation of the modulated square-wave. The system^{6,7} that we shall consider first uses a free-running multivibrator arrangement to form a regular triangular waveform which is then compared with the input in a circuit that generates a switching-edge whenever the two voltage levels cross over. The alternative system, which was described with references in the first of these articles and used in the circuit of the second, is the one where a feedback network is used to give a continuous measure of the error of the output of the switching stage and the square-wave is obtained from a flip-flop circuit that is triggered whenever the time-integral of this error reaches either end of a prescribed range. We shall call these two the "pure mark-space" and the "simple feedback" systems respectively.

As the name of the first would suggest the essential action of a circuit of this type is to generate a square-wave which is correctly modulated in its mark-space ratio but has no phase variation at all. In practice amplifiers based on this system suffer from serious distortion due to the absence of negative feedback, but if we assume that the design is so generous that we can ignore the non-linearity effects, then there will still be distortion due to the presence of the sidebands, since no attempt has been made to obtain their cancellation. Notice that with this system there is a well-defined limit to the modulation value that can be obtained. In the theory this is reached when the displacement of the edges is so large that they

Frequency at which distortion term occurs	MODULATION SYSTEM		
	Pure mark-space $f'_c = 1$	Simple feedback $f'_c = (1 - \frac{1}{2} X^2)$	Improved feedback $f'_c = 1$
f_m	100	$100 + 86 f_m^2$	$100 + 85 f_m^2$
$3f_m$	0	$78 X^2 f_m^2$	$190 X^2 f_m^2$
$5f_m$	0	$70 X^4 f_m^2$	—
$(f'_c - 2f_m)$	$38 X$	$36 X (2f_m)^{\frac{1}{2}} (f'_c - 2f_m)$	$38 X (f'_c - 2f_m)$
$(f'_c - 4f_m)$	$2 X^3$	$17.5 X^3 (4f_m)^{\frac{3}{2}} (f'_c - 4f_m)$	$2.4 X^3 (f'_c - 4f_m)$
$(f'_c - 6f_m)$	$0.04 X^5$	$9.5 X^5 (6f_m)^{\frac{5}{2}} (f'_c - 6f_m)$	$0.18 X^5 (f'_c - 6f_m)$
$(f'_c - 8f_m)$	—	$5.6 X^7 (8f_m)^{\frac{7}{2}} (f'_c - 8f_m)$	—
$(f'_c - 10f_m)$	—	$3.5 X^9 (10f_m)^{\frac{9}{2}} (f'_c - 10f_m)$	—

Table shows the percentage magnitude of various distortion terms introduced by the modulation of square waves

X Peak amplitude of sine-wave modulation as a fraction of the natural limit of the system.
 f_m Frequency of the modulation as a fraction of that of the unmodulated carrier.
 f'_c Frequency of the modulated carrier as a fraction of that of the unmodulated carrier.

meet and try to cross over, whilst in the actual circuit the corresponding limit is the point when the incoming voltage equals the peak value of the triangular wave. We shall as before refer to the depth of sine wave modulation by the symbol X , which is the ratio of the peak value of an applied sine-wave to this ultimate limiting value. With this system the carrier frequency is constant when modulation is applied, so that we need not worry about any change, but it will be convenient to measure the frequency of the applied modulation by the symbol f_m , which is the ratio of the value to that of the steady carrier.

The simple feedback system gives a more complicated action in which the amount of mark-space modulation produced is not, in fact, correct, whilst a degree of phase modulation is introduced. This is exactly right to cancel any sideband whose frequency happens to fall very close to zero, the negative feedback and integration ensure that such cancellation must be obtained, but unfortunately the phase modulation produced is incorrect at other frequencies and can even make the sidebands larger than they need have been. Again there is a well defined limit to the input voltage that can be accepted, when the error current from the feedback network falls to zero. In this form of modulator the carrier frequency does change when modulation is applied, so that we must define not only the modulation frequency, f_m , but also the actual carrier frequency, f'_c , and we can conveniently measure both by their ratios to the unmodulated carrier. It is not difficult to show that the relationship:

$$f'_c \approx 1 - \frac{1}{2} X^2$$

holds to sufficient accuracy for our purposes.

Naturally actual circuits working on either of these principles have their own peculiarities and only follow the modulation rules in an approximate manner. Nevertheless it is possible to formulate the rule which an ideal version of each circuit would follow in a purely mathematical form. From this it is possible, in principle, to calculate the exact times at which the switching-edges would be generated under any particular conditions and hence, by a process of Fourier transformation, to obtain the precise frequency spectrum of the square-wave and the magnitudes of all the sidebands.

CALCULATION OF THE DISTORTION TERMS

It seems that the actual calculation of the spectra by analytical methods, so as to obtain a generalized result, is impossibly difficult in the case of the simple feedback system, whilst it involves the Bessel Functions even in the more straightforward case of the pure mark-space system. Fortunately, though, there is an alternative

approach that holds good for any conceivable modulation process and allows different systems to be compared very conveniently. We can use a digital computer to produce both the timings of the edges and the spectrum of frequencies that they represent. The results obtained are necessarily only approximate and apply only to specific levels of modulation, however, it is possible to extract a useful general expression by the comparison of a sufficient number of individual cases. This is the method which has been employed in the production of the results shown in the Table.

There are restrictions in this method in that the modulation waveform used at each computation must not only be a single sine-wave but must also have a frequency related in some comparatively simple way to that of the carrier. This follows from the fact that the calculation must be performed over an interval which contains an exact whole number of cycles of each of the two frequencies, and the time required will become excessive if these numbers are made unduly large. The calculations from which the results given here are taken were made with an interval of 25 carrier cycles, so that modulation frequencies at multiples of 4% of the carrier could be tested.

There is a further restriction when the action is of a type where the average square-wave frequency changes with modulation, as in the simple feedback system, since it is then only possible to make a fair test at those amplitudes which bring the carrier to a frequency which is again related to that of the unmodulated carrier in this same way. Here the allowable amplitudes were those which reduced the carrier to 96%, 92%, 88% and so on of its initial frequency. This second restriction is much less serious than it might appear as these amplitudes are, in fact, reasonably convenient and the computer was able to work out the values to adequate accuracy very quickly. So far as it was possible to tell, these restrictions on the values that could be calculated have introduced no significant errors into the results. The errors arising in the computation itself were about one part in a million of the amplitude of the main carrier component.

The technique that was used to obtain the generalized form of the results shown in the Table consisted of finding the magnitude of a particular distortion term for a variety of values of modulation amplitude and frequency. These were so chosen that levels for the distortion in the range 0.1% to 1% were obtained at frequencies that would be likely to be important in actual use. An approximate expression was then derived for the term in question as a percentage of the modulation amplitude in the form of a constant factor and appropriate powers of the peak amplitude of the modulating sine-wave, the frequency of the modulation, and the frequency of the term itself.

At levels of distortion in the region of 1 % the error in assuming this simple sort of power relationship is not too serious, being perhaps $\pm 10\%$ of the term magnitude, but these results must not be extrapolated to higher levels of distortion where more complicated formulae are needed. Remember also that these results apply only to the rather artificial situation of modulation by a single steady sine-wave, and no estimate of the numerous possible forms of cross-modulation that will arise with more complicated input waveforms has been attempted.

The systems that are being considered have the property of giving the correct components at the output when the amplitude and the frequency of the modulation are both very low. At higher levels of input distortions of various kinds are generated. Since the pure mark-space system has errors only in its phase modulation, the distortion terms that it causes are just unwanted sidebands of which those at $(f_c - 2f_m)$, $(f_c - 4f_m)$ and $(f_c - 6f_m)$ will normally be the most important. Notice that the amplitude of these sidebands is not affected by the frequency at which they are made to occur. In contrast to this the simple feedback system not only generates these sidebands, but also has distortion of the fundamental and introduces harmonics, since its mark-space action is incorrect as well. These distortions rise with the square of the modulation frequency. Notice that the sidebands in this system change their amplitude in a relatively complicated manner with frequency falling to zero when their frequency is zero, and that they are centred on the modified carrier frequency, f_c , so that they will come into the band at lower modulation frequencies as the input amplitude increases.

Both the systems that we are considering have the property of being balanced, meaning that the treatment of positive and negative inputs and also of the upward and downward switching edges are symmetrical. This means that only the odd harmonics of the modulation will be generated, and also that only those sidebands at frequencies $(af_c \pm bf_m)$ where $(a + b)$ is odd will occur. Needless to say such systems are much to be preferred and unbalanced systems need not be seriously considered unless they have some quite exceptional advantage in another respect.

It will be seen from the table that there is no clear advantage in either of these systems. The freedom from harmonic generation and lower average levels of the sidebands with the pure mark-space modulation compares with the cancellation of sidebands at low frequencies when the Simple Feedback system is used. The choice in practice depends on such factors as the benefits to be obtained from the action of the negative feedback and the fact that the feedback system requires appreciably fewer components.

POSSIBILITIES FOR IMPROVED SYSTEMS

We now naturally come back to the question of whether it is possible to devise a system which would be a useful improvement over these two, since we have shown that there is no fundamental reason why a vastly better system should not be made. Clearly the principle of feedback should be retained, since it reduces the effects of imperfections in the circuit and also ensures the elimination of any sidebands that come at very low frequencies, but what other features ought we to change? One of the more hopeful possibilities is to say that it is wrong for the carrier frequency to be made to vary, and this leads to the idea of the improved feedback system.

This is similar in most respects to the simple feedback arrangement, but differs in that the triggering limits of

the flip-flop are brought closer together (in a symmetrical manner), in proportion to the quantity $(1 - x^2)$, where x is the instantaneous value of the input waveform measured as a fraction of the natural limiting value. This quantity will have to be made by some circuit of the type used in analogue computers, but remember that it is only required to obtain a refinement of the action of a system which already works comparatively well, and so it will not matter too much if the value is not precisely correct. This reduction of the triggering range has been chosen so that the carrier frequency is maintained at a substantially constant value when modulation is applied and thus the excessive sideband amplitudes should be usefully reduced. The actual amplitudes to be expected from such a system have, in fact, been computed, since there is no problem in getting a digital machine to follow such a process with high accuracy, and the results are presented in the third column of the Table.


It will be seen that the effect obtained is more or less as predicted. The amplitudes of the sidebands are indeed a substantial improvement over the values obtained with the two previous systems. The third harmonic generation, however, is considerably worse, though the reason for this increase is not at all clear particularly as the fifth harmonic appears to be much reduced. The overall impression seems to be that these improvements are not sufficient to justify the extra complexity of the circuitry and that if any real improvement is to be obtained some other type of modification to the circuit arrangement will be required to achieve it. They might, for example, be expected to include some rudimentary form of 'quadrature' generating network in addition to arrangements for keeping the carrier frequency at a constant value, since the theory suggested that both these features would be required. But the advantages of the class D system are so small already that any successful improved modulation generator would have to use almost no extra components if it were to remain economic and the chance of such an arrangement being devised seems, unfortunately, to be negligible.

REFERENCES

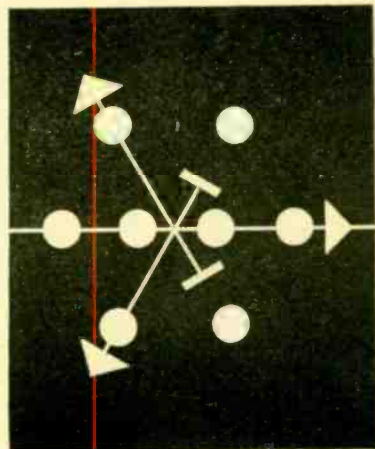6. D. R. Birt, *Wireless World*, Feb., 1963, p. 76.
7. C. Sinclair, X10 and X20 circuits as advertised 1965.

Physics Exhibition Symbol

The Institute of Physics and the Physical Society announces the adoption of this symbol for the annual Physics Exhibition. "Based on the weight diagram for the irreducible representation $D^8(1,1)$ that of the $SU(3)$ symmetry which has been so strikingly successful in bringing order to the classification of sub-atomic particles." The exhibition takes place on 11-14 March at Alexandra Palace, London. Tickets are obtainable free from the I.P.P.S., 47 Belgrave Square, London, S.W.1.



Log-periodic TV Aerial

A New look in Band III Arrays

JUST over ten years ago the first frequency-independent aerials were announced in America. The bandwidth of these aerials, which are basically conical or spiral, is limited only by the smallest and largest dimensions of the structure. Change of frequency merely moves the resonant region of the aerial within the structure but does not affect the impedance or radiation pattern. The advantages of the frequency-independent aerial have been combined with those of the Yagi in the logarithmic dipole. However, unlike the Yagi, which normally has only one driven element plus a number of parasitic elements, the log-periodic consists entirely of driven dipoles the lengths and spacings of which increase progressively.

Log-periodic aerials have, of course, been used for some time for h.f. communications and telemetry purposes. The principles were discussed and details given for a u.h.f. television aerial* in our September and October 1964 issues but log aerials for television have not been available commercially in the U.K. until now, although they were introduced in North America a year or more ago.

Antiference have now introduced a series of log-periodic dipole aerials for Band III, having in mind particularly those areas where both I.T.A. and BBC-1 transmissions are radiated on widely separated channels in this band.

To obtain a performance which is basically independent of frequency from a structure composed of a series of resonant dipoles, such resonances must "taper off" so that as the frequency is varied the function of the resonant dipole is smoothly transferred from one dipole to the next. This means that the physical dimensions of the dipoles must be scaled from one to the next in such a way that the desired frequency range is covered by a series of dipoles with

overlapping response characteristics. The degree of overlap of any one dipole to its immediate shorter neighbouring dipole must be constant throughout that part of the structure which is within the limits of the desired frequency range.


Since the characteristics of the elements are, to a certain degree also determined by their surroundings, such as relative spacing one to another, then these spacings must be scaled also.

The log-periodic dipole aerial is, then, an array of parallel linear dipoles arranged side by side, and both the "tapering off" of the


element lengths and the spacing between them, form a geometric progression with a fixed ratio throughout.

The elements are energized from a balanced, constant impedance transmission line. Adjacent elements are connected to this line in an alternate manner and the operation of the aerial is "end fire" in the direction of the shorter elements with the feeder connected at this end.

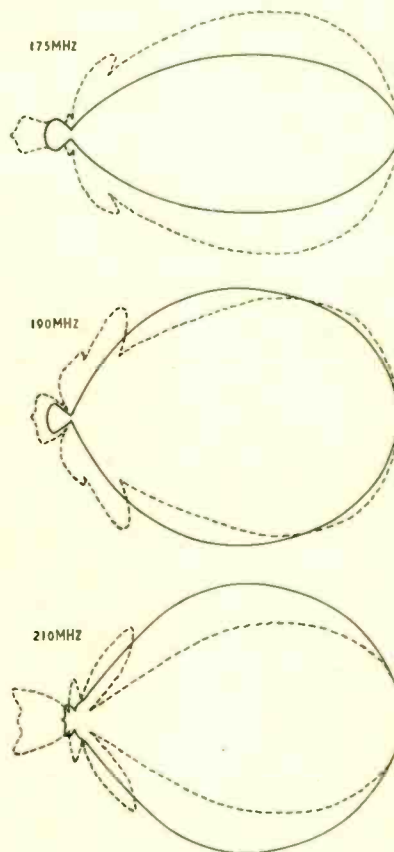In the Antiference log-periodic arrays a double rectangular cross-section boom performs the function of transmission line as well as the support for the elements.




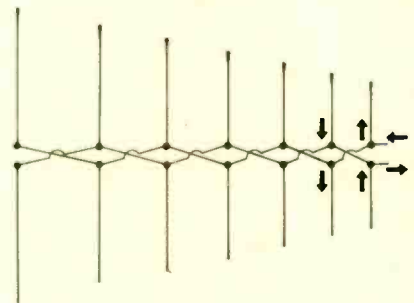Polar diagrams for a 7-element log-periodic aerial compared with those for a 5-element double driven Yagi (broken lines).



Schematic diagram of log-periodic dipole aerial showing the phasing.

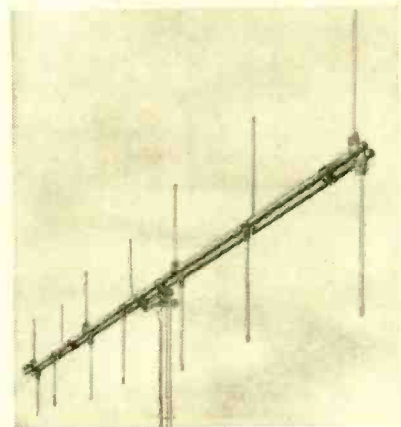The Antiference 7-element log-periodic aerial type LP7.



* "Logarithmic Aerials for Bands IV and V" by M. F. Radford.

Transistor Rationalization

How to standardize on a few, easily-available "work-horse" devices

By T. D. TOWERS,* M.B.E., M.A., C.Eng.

HAVING discussed last month semiconductor type numbering and how to find information on the many tens of thousands of device types on the market, we will now take a look at the rationalized selection of a few transistor families which many engineers have come to accept as standards for run-of-the-mill industrial circuit applications.

CHOOSING BETWEEN SILICON AND GERMANIUM

Every user of transistors is concerned with reliability, but the technique of transistor manufacture has reached a stage where there is little to choose on this score between germanium and silicon.

Semiconductor manufacturers tend to divide their products into three classes: "entertainment," "industrial," and "professional." In the past, reputable manufacturers have produced essentially professional transistors, these are reliable and are guaranteed to meet an exacting specification for Services use. The need for this close tolerancing, multiple testing and quality documentation of professional devices has meant that they are expensive. Semiconductors from the same production line but to a less rigorous specification are fed into the industrial market (high-quality instrumentation and communications field) where reliability is still a prime requirement but the reduced test costs result in lower prices. Finally, the entertainment field (which prudently designs for wide spreads of parameters) gets even more economical devices because with them much of the procedural and testing costs involved in the other fields are avoided.

Over recent years a new situation has emerged. Manufacturers are setting about designing transistors primarily for the entertainment field (in which users cannot afford to pay for even the economical offshoots of the high-quality professional-industrial transistor lines). Thus we see large numbers of plastic-encapsulated transistors at low prices on the market. These are silicon devices, because plastic encapsulations do not suit germanium. Despite some unresolved doubts on the long-term reliability of plastic encapsulated transistors, their low price means that they are finding their way even into the industrial field for less exacting requirements. But as yet they have not been accepted in the professional field.

L.F. TRANSISTORS

Transistors for low-frequency and d.c. use fall into three distinct groups: *low level*, operating in the region of 1 mA; *mid-level*, around 50 mA; and *high level*, around 500 mA. Each area has its different features.

L.F. low-level amplifiers.—The principal requirements in the low-level stages of low-frequency circuits are the

obvious ones of low noise and high gain at low currents. In general, in these respects, silicon tends to be superior to germanium and is largely replacing it. Even so, we still see many circuits using time-proved germanium p-n-p devices such as the AC107 and the NKT216. The OC71 and GET106 were progenitors of this breed. There are no germanium n-p-n transistors in common use in low-level circuits.

In silicon, on the other hand, low-noise low-level amplifier transistors tend to be n-p-n. The BC107/8/9 family has become almost a standard for this area. They are characterized by very low-noise levels and by high current-gain at collector currents of around 100 μ A. Many specialized devices in the same category, such as the 2N929/930 (for operation at high voltages and in the microamp current range), the 2N2483/4 and the 2N2604/5, are marketed.

As yet there is no widely accepted common device for p-n-p silicon low-level work. Users have not established any particular type as a standard. I myself design around the 2N3547/8/9/50, which is a good p-n-p complement to the BC107/8/9. Somewhat in the same category fall such devices as the increasingly used BCY70/1/2 and the 2N3250/1.

L.F. mid-level amplifiers.—In circuit stages operating from about 10-100 mA, the major requirement on the transistor is that it should have a fairly high and constant current gain over a wide range of current. In germanium, both n-p-n and p-n-p devices are common for mid-level amplifiers. Typical n-p-n units are the AC127 and NKT713 with voltage ratings around 30 V and current gains about 50. On the p-n-p side, there are many devices of which the OC75 and NKT213 are typical. These, too, are characterized by 30-V collector rating and current gains of around 100. Whatever the polarity, this style of transistor has an f_T of around 1 MHz.

When we turn to silicon, n-p-n mid-level amplifier transistors far outnumber p-n-p. Because so much American circuitry has been written around the 2N3053, it has become the best known device in this field. With a 60-V rating, a capability of handling up to 500 mA, and a current gain of around 75, this "maid of all work" still has many competitors such as the 2N696, 2N697, 2N718, 2N956, 2N1420, 2N1613, 2N1711 and 2N1893.

In mid-level n-p-n silicon transistors, the 2N1131/2 is fairly typical with characteristics not unlike the n-p-n 2N3053. It finds many alternatives in the market such as the BFX29/30 and BFX87/88.

L.F. high-level amplifiers.—When a stage is required to handle up to 1 A collector current, we have to turn to "beefier" larger-geometry devices. In germanium we find well-tried standards like the AC176 and NKT781 in

* Newmarket Transistors Limited.

n-p-n and the ACY17/8/9/20/1/2 and NKT237/8/9/40/1/2 families in p-n-p. Whatever the polarity, these transistors are basically 30-V transistors (with higher voltage selections), characterized primarily by a high current gain at currents up to 1 A.

In silicon for 1-A amplifications there is no widely used single device. However, the 2N2297 basic transistor, better known in this country under the family numbers BFY50/1/2, BFX84/5/6 and BSX60/1, is representative of n-p-n devices. It has an f_T around 100 MHz, is characterized by a voltage rating of around 60 V, low saturation voltage and a 1-A current gain of 15 minimum. There is as yet no universal 1-A p-n-p device available.

R.F. AND SWITCHING TRANSISTORS

R.F. amplifier transistors tend either to have a low C_{ob}^* for stable low-level amplifier operation or the high C_{ob} which goes with the larger junction for high current carrying capacity in later circuit stages.

R.F. "low- C_{ob} " amplifiers.—For many years now r.f. amplifier circuits requiring low feedback capacitance have standardized on the well-known germanium p-n-p AF114/5/6/7 (OC170/1) and NKT674/5/6/7 families of devices. These are a special type of post-alloy diffused transistor, which because of their high gain at low current, and low (2 pF) collector-base feedback capacitance permit gains of around 45 dB per stage in standard tuned 470 kHz i.f. amplifiers. There has been no germanium n-p-n equivalent device in common use.

By contrast, when we come to silicon, there has been no common low- C_{ob} p-n-p transistor. The n-p-n BF115, which can be regarded as a silicon equivalent of the p-n-p germanium AF115, has found many applications. Such devices are all characterized by very small collector-base junctions, but further improvements have been made by what is known as the "Faraday-shield diode" technique. In this, a diode diffused underneath the base overlay bonding pad is connected to the emitter, which is operated at a.c. ground. This diode region is diffused simultaneously with the base during the diffusion cycle. By using this technique the intrinsic feedback capacity of the transistor can be reduced to around 0.1 pF. This, together with the typically 0.4 pF interlead capacitance gives a C_{ob} of the order of 0.5 pF compared with the 2.0 pF of the AF114 family. Typical of this Faraday-shield type of transistor is the BF167.

R.F. "high- C_{ob} " amplifier.—For higher level r.f. stages, where the feedback capacitance is not so critical, we find several widely used transistor types. In germanium the most common are p-n-p polarity, such as the 2N1303/5/7/9, the 2N404 and the NKT135. All of these have a C_{ob} of the order of 20 pF, and typical f_T of the order of 5-15 MHz. Smaller geometry devices of the same character with $C_{ob}=10$ pF are the well-known OC44/5 and NKT11/12.

The best known n-p-n germanium devices of the same sort are the 2N1302/4/6/8 family which are direct n-p-n equivalents of the p-n-p 2N1303/5/7/9. All these high- C_{ob} germanium transistors are similar in other respects, with voltage ratings of around 20 V, an f_T of typically 7.5 MHz and current gains of 50-100.

Silicon transistors for high- C_{ob} r.f. applications are readily available in both n-p-n and p-n-p. The most commonly used device family is almost certainly the

n-p-n 2N2217/8/9/20/1/2 series. These have relatively flat current gain from a few mA to several hundred mA, with typical collector capacitances of 6 pF and f_T of around 350 MHz. Voltage ratings are typically 60 V, i.e., double the corresponding germanium devices mentioned above. Also 80-V versions are available, by contrast with germanium, for which even 30-V selections are rare.

In high-Cob r.f. transistors we also find a common p-n-p family, the 2N2904/5/6/7, which is a close equivalent to the 2N2217 family in its characteristics. Other common devices similar to the 2N2904 family are the 2N3133/4/5/6.

V.H.F. amplifiers.—Silicon diffusion techniques lend themselves particularly to u.h.f. transistors. Thus we find the n-p-n type 2N918 with a typical f_T of 900 MHz in everyday use. The 2N2475 and the BSY90, faster versions of the 2N918 with f_T of the order of 1.5 GHz, are tending to replace the 2N918. U.h.f. silicon transistors exhibit relatively low collector voltage ratings for silicon (around 30 V only) and low current gain (typically only 30). They do, however, have low collector capacity, typically 1.5 pF or less. U.h.f. germanium transistors, whether p-n-p or n-p-n, are not in common use industrially.

L.F. switches.—For low-frequency switching, manufacturers do not in general produce special families of devices, and we find slow-speed switching generally being done by transistors of the type described above under l.f. mid-level amplifiers or h.f. high-level amplifiers, depending on the current being switched. There is one exception in that the 2N2904 family described above under r.f. high-cob amplifiers is so widespread that it is often used for slow-speed switching in the absence of a common p-n-p equivalent to the BFY50-52 series.

R.F. switches.—For r.f. or medium-speed switching, the tendency in the past has been to use r.f. amplifier transistors. Thus with germanium we find the n-p-n 2N1302 family or the p-n-p 2N1303 family widely used, as also has been the OC42 (a selection of the OC44/45).

When we come to the new silicon r.f. switching transistors there is a vast array of transistors specially designed for switching rather than general purpose r.f. amplifier-cum-switching work. The commonest basic device is the famous 2N914, an n-p-n gold-doped switching transistor with a typical f_T of 300 MHz, a 500 mA current capability and a collector capacity of around 4 pF. Other well-known devices of a similar character are the 2N706, 2N708, 2N743/4, 2N753, 2N919/20, 2N2368/9/9A, BSY26/7, BSY38/9 and the ubiquitous BSY95A. Silicon p-n-p r.f. switching transistors are much less common, but the serviceable 2N2904 family again is often used.

V.H.F. switches.—For ultra-fast switching, there are no germanium devices in common use, but the last of the v.h.f. germanium switching transistors will still be found in equipment. Typical of these are the p-n-p 2N711B or NKT603F, with relatively low (20 V) collector voltage ratings, maximum currents of 100 mA, current gains of around 50, typical f_T of 125 MHz and C_{ob} of about 3 pF. On the n-p-n side in germanium there never have been any common ultra-fast switches.

In silicon the "daddy of them all" in ultra fast switches is the n-p-n 2N709, with switching times of less than 10 ns. This device has a low collector voltage rating

* C_{ob} (C_{ob})—output capacity with base open to a.c.

(15 V) and will handle up to 200 mA only. On the other hand it has an f_T of 800 MHz typically and a 2-pF Cob. Its current gain is about 50. The 2N709 has proved a very difficult transistor to manufacture and is still quite expensive. There are no p-n-p silicon ultra-fast switches widely available.

POWER TRANSISTORS

When you want to dissipate more than about a watt in a transistor, you have to leave the small flexible-lead devices described so far. Two main styles of case have become widely used, at least for low-frequency operation. These are the well-known standard TO3 large "diamond-shaped" outline and a miniature version of it. The miniature medium power transistor comes in three different cases: (1) TO66 small diamond; (2) "Continental" small diamond (as Mullard AD161/162); and (3) TO8 (with clamp that makes it similar to small diamond).

L.F. medium-power transistors.—In germanium there are only a few medium-power devices on the British market, but these are widely used. For p-n-p requirements, the international standard germanium unit is the 2N1183/4 or NKT302 in TO8 outline with typical voltage ratings of 60 V, current gains of around 50, maximum current around 3A and f_T about 1 MHz. In the

TABLE I
A SELECTION OF WIDELY USED TRANSISTOR TYPES AVAILABLE FROM MORE THAN ONE MANUFACTURER

	n-p-n		p-n-p	
	Ge	Si	Ge	Si
L.F. Low-level Amp.	*	BC109	AC107 NKT216	2N3548
L.F. Mid-level Amp.	{ AC127 NKT713	2N3053	{ OC75 NKT213	2N1132
L.F. High-level Amp.	{ AC176 NKT781	BFY52	ACY20	*
R.F. Low-Cob Amp.	*	BF115	{ AF117 NKT677F	*
R.F. High-Cob	2N1304	2N2221	{ OC45 NKT12	2N2906
V.H.F. Amp.	*	2N918	*	*
A.C./D.C. Switch	{ AC176 NKT781	BFY52	ACY20	*
R.F. Switch	2N1304	2N914	{ OC45 NKT12	2N2906
V.H.F. Switch	*	2N709	{ 2N711B NKT603F	*
A.C./D.C. Medium Power Amp.	{ AD161 NKT871	2N3054	{ 2N1183 NKT302	*
A.C./D.C. Power Amp.	*	2N3055	{ OC35 NKT404	*

*No "standard" device commonly available from several manufacturers.

n-p-n germanium category there is no corresponding TO8 standard, but the AD161 or NKT871 n-p-n small diamond power devices find wide use. These have a p-n-p exact counterpart in the AD162 or NKT371 (as an alternative in some applications to the 2N1183/4).

In silicon in the medium-power small diamond range there is no p-n-p commonly available, but in n-p-n the 2N3054 is a widely accepted standard device. This is in a TO66 encapsulation and features 90-V collector rating, 4-A maximum current, 25-W theoretical maximum dissipation, typical f_T of 1 MHz, and a current gain around 50.

L.F. power transistors.—When higher operating powers of the order of 10-25 W dissipation are called for, the larger TO3 outline is the common encapsulation. In germanium there is a family of TO3 p-n-p devices which has been virtually the standard power transistor for years now. These are the OC28/9/35/6 and NKT401/2/3/4. The most important features of these are current carrying capacities up to 10 A, typical voltage ratings of 60 V, typical current gains of 50 and f_T of around 300 kHz. In the main, germanium p-n-p power transistors of this type still carry the bulk of transistor power applications in this country. There are no n-p-n equivalent germanium power transistors commonly used.

In silicon the standard TO3 high-current power transistor is the n-p-n 2N3055. This features voltage ratings of 60-100 V, current ratings of 15 A, f_T of 1 MHz and theoretical maximum dissipation of 115 W, together with typical current gains of around 50 at 1 A. Whenever the standard p-n-p germanium power transistors described above are replaced by silicon in a redesign, the tendency is very largely to go over to the n-p-n 2N3055. The only major drawback in this silicon transistor is its 7-V emitter rating compared with the 20 V of the OC28 series.

Other special transistors.—So far, we have been dealing with "run-of-the-mill" devices. Limitations of space prevent any coverage of special devices such as r.f. power or field-effect transistors. Most semiconductor manufacturers have their own ranges of devices for these, but sufficient field experience has not yet accrued for any particular devices to become accepted as industry standards.

TABULAR INFORMATION SUMMARIES

To bring into focus all the information detailed above, Table I has been prepared setting out for each circuit function a typical device from the "standard" ranges discussed above, classified as germanium/silicon and n-p-n/p-n-p.

To give some idea of the special characteristic of the various families, Table II sets out critical information on the devices selected as examples in Table I. A study of Table II will reveal most of the differences between n-p-n and p-n-p and between germanium and silicon transistors. For example, you will note in the emitter voltage rating column (headed V_{eh}) that silicon diffused devices have ratings always below 10 V and germanium alloy always above 10 V.

PLASTIC vs METAL CASE TRANSISTORS

You cannot help but be aware that over the last two years plastic encapsulated silicon transistors at low prices have had a great impact on the transistor market,

but there has been controversy about them. Designed primarily for the entertainment market, their most obvious advantage is low cost, but the absence of a metal case can also be an advantage in that they can have lower parasitic capacitances than corresponding metal case units. Also in most silicon hermetically sealed transistors the collector is connected internally to the metal case, so that precautions have to be taken to isolate the case in equipment. With plastic encapsulated devices, no special care is required for this.

Plastic case transistors do have disadvantages, however. Generally the same transistor chip will have lower permissible dissipation than in the corresponding metal-can version. Also there has been much discussion about their long-term reliability when compared with true hermetically sealed devices. As yet, no plastic device has received "CV approval" in this country, and the final verdict on the long-term reliability problem will be given only if and when such approval is obtained.

Typical plastic-encapsulated transistors.—Table III sets out for l.f. amplifier applications a selection of fairly common types of roughly equivalent specification, in two classes—n-p-n and p-n-p. The table cross-refers types from several manufacturers to common equivalent metal-case devices.

There is as yet no uniformity in the outlines used for the plastic encapsulations. Difficulties arise because, while some manufacturers supply devices physically interchangeable with standard TO18 or TO5 cans, others produce completely new lead configurations, which are sometimes difficult to fit to boards drilled for standard metal-case devices. However, some manufacturers do provide their devices with the leads pre-dressed

TABLE III
REPRESENTATIVE COMPARATIVE SELECTION OF METAL-CASE AND RELATED PLASTIC ENCAPSULATED SILICON TRANSISTORS

Metal Case Device	Plastic Encapsulated			
	Texas	S.T.C.	Ferranti	Fairchild
(L.F. Low-level n-p-n)				
BC107 ..	BC182L	BC171	ZTX303	BC115
BC108 ..	BC183L	BC172	ZTX302	BC113
BC109 ..	BC184L	BC173	—	BC114
(L.F. Low-level p-n-p)				
BCY71 ..	2N3702	—	ZTX502	BC154
BCY72 ..	2N3703	—	ZTX503	BC153

to the required TO18 spacing. Also, you can get small plastic mounting pads which do the pre-dressing for you as you draw the transistor down to the board.

It is hoped that the analysis of the various transistor types given above will be helpful to the reader in his assessment of what transistor to use for a specific circuit application. He can find fuller information on details of devices in one of the various sources of information outlined in last month's article.

TABLE II
CRITICAL DATA ON TRANSISTORS IN TABLE I

	Polarity & Material	Fabrication	Case	V _{cb0}	V _{eb0}	I _c max (mA)	P _c max (mW)	h _{FE}	f _T (MHz)	C _{ob} (pF)
ACY20 ..	P-Ge	Alloy	T05	40	—	2A	260	100	1	—
AC107 (NKT216)	P-Ge	Alloy	T01	15	5	10	80	50	1.5	12
AC127 (NKT713)	N-Ge	Alloy	T01	32	10	500	340	100	2.5	—
AC176 (NKT781)	N-Ge	Alloy	T01	32	5	1A	700	200	1.5	—
AD161 (NKT871)	N-Ge	Alloy	Special	32	10	2A	4.5W	100	4	—
AF117 (NKT677F)	P-Ge	Alloy								
		diffused	T07	32	1	10	50	150	75	2
		Diffused	T018	20	5	100	300	400	250	4
BC109 ..	N-Si	Diffused	T018	20	5	100	300	400	250	4
BF115 ..	N-Si	Diffused	T072	50	5	30	160	100	270	—
BFY52 ..	N-Si	Diffused	T05	40	6	1A	800	125	100	—
NKT302 ..	P-Ge	Alloy	T08	60	15	2.5A	13W	100	1	—
NKT603F ..	P-Ge	Alloy								
		Diffused	T07	40	1	50	80	100	120	3
		Alloy	T03	60	20	10A	30W	50	0.4	—
OC35 (NKT404)	P-Ge	Alloy	T01	15	12	10	83	50	5	10
OC45 (NKT12)	P-Ge	Alloy	T01	30	12	50	125	100	0.5	—
OC75 (NKT213)	P-Ge	Alloy	T01	30	4	200	300	50	800	2
2N709 ..	N-Si	Diffused	T018	15	4	200	300	50	800	2
2N711B ..	P-Ge	Alloy								
		diffused	T018	18	2	100	150	50	150	3
		Diffused	T018	40	5	500	360	50	300	4
2N914 ..	N-Si	Diffused	T018	40	5	500	360	50	300	4
2N918 ..	N-Si	Diffused	T072	30	3	50	200	25	900	1.5
2N1132 ..	P-Si	Diffused	T05	50	5	600	600	50	200	30
2N1183 ..	P-Si	Diffused	T05	50	20	3A	7.5W	50	0.5	—
2N1304 ..	P-Ge	Alloy	T08	45	25	300	150	100	8	20
2N1304 ..	P-Ge	Alloy	T05	25	25	300	150	75	350	6
2N2221 ..	N-Si	Diffused	T018	60	5	600	400	75	350	6
2N2906 ..	P-Si	Diffused	T018	60	5	600	400	75	350	6
2N2906 ..	N-Si	Diffused	T05	60	5	700	1W	75	200	—
2N3053 ..	N-Si	Diffused	T05	60	5	700	1W	75	200	—
2N3054 ..	N-Si	Diffused	T066	90	7	4A	25W	50	1	—
2N3054 ..	N-Si	Diffused	T03	100	7	15A	115W	50	1	—
2N3055 ..	N-Si	Diffused	T03	100	7	15A	115W	50	1	—
2N3548 ..	P-Si	Diffused	T018	60	6	100	400	200	200	6

NOTE: Information generally extracted from "Transistor D.A.T.A. Book."

European Space Research



Setbacks encountered—current programme—satellite situation—uncertainty as to the future

THE satellite programme of the European Space Research Organisation (ESRO) has suffered two major setbacks since it was inaugurated in 1964, although the sounding rocket programme has proceeded very smoothly. The first of these occurred in October 1966 when the premises of the European Space Technology Centre (ESTEC) and the European Space Research Laboratory (ESLAB) situated at Noordwijk in Holland were destroyed by fire together with all equipment, test data and records. The second occurred last May when a failure of the third stage of the four-stage Scout launch vehicle resulted in the first flight model (F1) of the satellite ESRO 2 falling into the Pacific after failing to go into orbit. Telemetry data received from the satellite during the abortive launch showed that all the satellite systems functioned normally.

At the time of this launch the European satellite tracking and telemetry network (ESTRAC) was incomplete and full responsibility for tracking, attitude control, turn-on of experiments, and data acquisition from ESRO 2 (F1) would have been with the American National Aero-

navics and Space Administration (NASA). Now the ESTRAC facility is fully operational and the projected launch of F2, in April 1968, will result in a much larger ESRO participation. The design, integration, environmental and flight testing of the satellites is being carried by ESTEC and, apart from the early orbit determination that will be carried out by NASA as part of the launch service, full control of the satellite will be in the hands of ESTRAC.

Some uncertainty now exists as to the future programmes of ESRO following a meeting of member countries held in Rome last year. At this meeting no decision was taken as to the extent of future programmes on the grounds that insufficient information was available at that time. It was agreed, however, to form a programme advisory committee to look into the whole organization; their report is due to be presented shortly. It is envisaged that a further ministerial meeting will be held in late April or early May and a decision as to the magnitude of future programmes will be made, based on the Advisory Committee's Report.

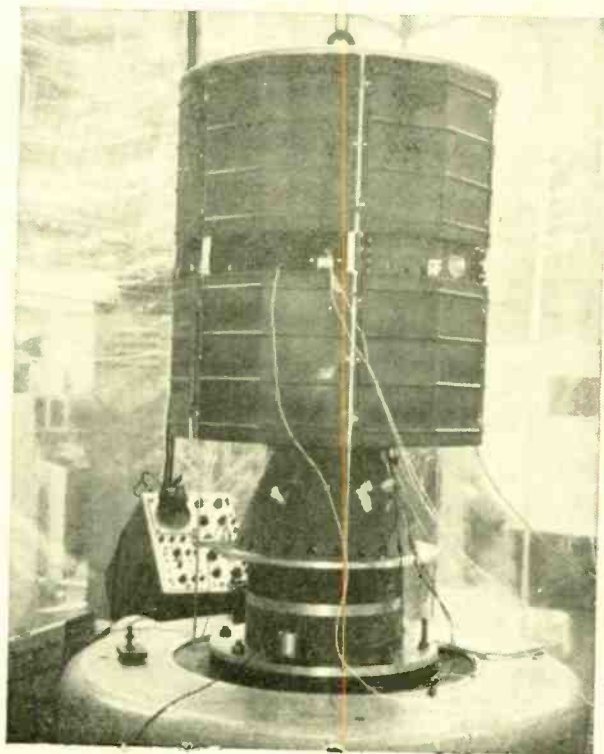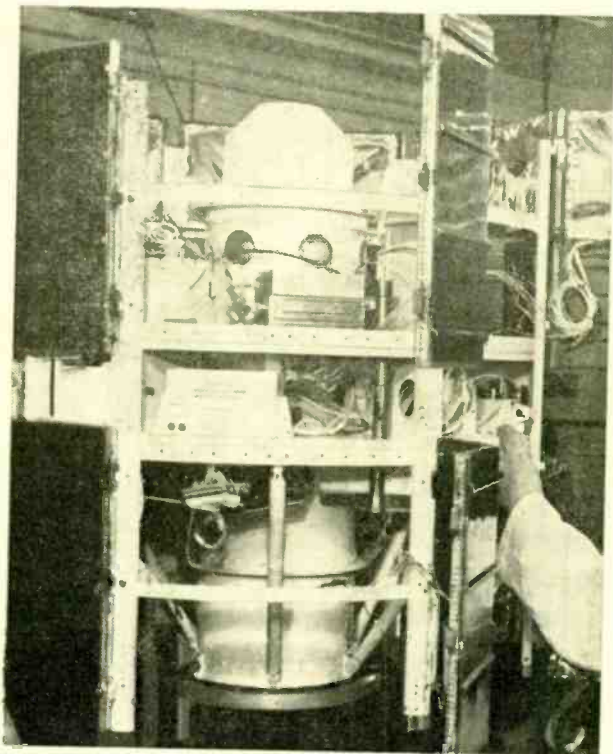

The left hand photograph shows an experimental unit being installed in ESRO 2 and the right hand photograph shows the same satellite undergoing vibration tests. The main contractor for the project was Hawker Siddeley Dynamics Ltd. with Société des Engins Matra (France) as principal sub-contractors, Ferranti supplying the solar cells. The satellite will be controlled in flight by 36 commands using a tone-digital system on a frequency of 148.25 MHz.

As has already been mentioned the ESTRAC facility is now ready and in addition ESLAB and ESTEC have been rebuilt and re-equipped forming a sophisticated tool for research, design, environmental testing and tracking of satellites. This has been an expensive process involving the purchase of large amounts of capital equipment; the danger of too small a programme being granted is that these facilities will be only partly utilized. The net result would be a very high unit cost per project and a danger would exist in that scientists may tend to drift away from European Space Research. It is the hope of the organization that the programme will include communication and navigation satellites as well as those carrying scientific experiments currently planned.

The design and development of a satellite or sounding rocket payload is carried out in three definite stages: materials and components, sub-systems and the integrated system. At ESTEC the main task is concerned with environmental testing during the first and third of these stages, the second stage being left in the hands of contractors. The equipment at ESTEC includes comprehensive vibration facilities and large chambers capable of simulating the space environment as far as temperature, vacuum, solar radiation and "blackness" are concerned.

Work is at present proceeding on five projects with the prospect of a sixth "on the horizon." Out of 41 scientific experiments to be carried in these craft, 17 are British. As far as contracts received by British industry are concerned the story is rather different; only a small percentage of the equipment comes from British sources. However, this situation is likely to improve. In the past the organization discovered that in many cases, "space approved" electronic components were not available from European sources and increasing reliance was placed on components of American manufacture, although some were obtained as by-products of the French national space programme.

Briefly the satellites planned by the organization are: **ESRO 1**, a polar ionosphere satellite which will measure energies and fluxes of particles at high altitudes and the effects of particles as manifested by auroral events and the composition of the ionosphere. Studies will also be made of solar proton events which are responsible for polar cap absorption phenomena. To assist in making these measurements, the satellite will be stabilized along the earth's magnetic field lines by incorporating permanent magnets in the structure.

ESRO 2 is designed to study solar astronomy and cosmic rays and as such its orbit is planned to keep the satellite in direct sunlight for the majority of its design lifetime (1 year). The equipment on board will measure the corpuscular radiation from the sun during solar flares, protons trapped in the inner Van Allen Belt, the electron component of primary cosmic radiation and the modulation mechanism of cosmic rays in interplanetary space.

The highly eccentric orbit satellite **HEOS A** is designed to study interplanetary physics, particularly magnetic fields, cosmic radiation and the solar wind during a period of large solar activity. The orbit apogee will be about 250,000 km and the perigee about 300 km. This orbit, a narrow ellipse, allows telemetry transmissions to be wholly in real time eliminating the need for an internal tape recorder and enabling the satellite to be "seen" for nearly 100% of the time (above 30,000 km) using only two ground stations. These will be the ESTRAC installations at Redu (Belgium) and Fairbanks (Alaska).

The main purpose of the satellite **TD1** will be to study stellar astronomy and cosmic rays and will to this end

carry seven experimental installations. It will have a circular orbit at an altitude of 500 km with an inclination of 97.4° to the equator.

TD2 will study solar-terrestrial relationships during a period of maximum solar activity. It is of similar construction to **TD1** but will be on an elliptical orbit with an apogee of 1200 km and a perigee of 350 km inclined at 90°.

The previously mentioned sixth satellite "on the horizon" is the **LAS** (Large Astronomical Satellite) on which work, although not suspended, has been reduced to a minimum for financial reasons. This is the largest and most complex of the projected satellites and is expected to be of high optical resolution 10^{-5} μm (0.1 \AA). Design of a three-axis simulator for the satellite was completed and various parts constructed up till the time of the fire at ESTEC; fortunately, some parts had not been delivered and escaped destruction. It has been estimated that some 7.5 man years and 232,000 French francs had been spent on this machine before the fire.

BOOKS RECEIVED

The BEAMA Directory 1967/1968. Compiled by The British Electrical & Allied Manufacturers' Association Incorporated, this directory starts with a pictorial review of the achievement of the British Electrical Industry, the rest of the book being divided into four sections. Section 1—Directory of Manufacturers—gives the names and addresses of manufacturers, a summary of the products manufactured, overseas branches, representatives and agents. Section 2—Technical Information. Section 3—Buyers' Guide—an alphabetical list of products and who makes them. Section 4—Foreign Languages—equivalent expressions in German, Spanish, French, Portuguese and Russian for the English headings found in the Buyers' Guide section. Pp. 556. Price 60s. Pergamon Press Ltd., Headington Hill Hall, Oxford.

Telecommunications for Technicians, Vol. 1, by D. Coatesworth. From the Penguin Library of Technology this paper back is the first of three volumes to be published in this series. It introduces some of the basic principles of electricity, magnetism and electronics in a clear and well defined manner without short-circuiting the necessary mathematics. Unusually, in a book of this nature, the properties of semiconductor materials, diodes and transistors are discussed as well as the principles of thermionic emission. Although by no means a full treatment of the subjects it covers, this book provides an excellent introduction to electronics either as a hobby or as an intended career. Pp. 136. Price 10s 6d. Penguin Books Ltd., Harmondsworth, Middlesex.

Television in Education and Training by D. A. de Korte from the Philips Technical Library. The object of this book is to provide a general review of the development and scope of television as well as other audio-visual aids in education. Following a discussion of television and the audio-visual concept in general the history and the basic principles of television are broadly outlined together with details of equipment in use. Teaching projects that have been carried out in various countries using television are examined. Final chapters cover film projection and television, teaching machines and television and the production of closed circuit television broadcasts. Pp. 175. Price 41s. Macmillan & Co. Ltd., Little Essex Street, London, W.C.2.

GaAs Miniature Radar

SMALL, simple and cheap radar sets for burglar alarms, automobile speed measurement, ship docking and other domestic and professional uses have become a practical possibility as a result of a development programme at the Royal Radar Establishment, Great Malvern. They are all based on the gallium arsenide (GaAs) Gunn-effect diode. As is well known, this is a piece of bulk semi-conductor which only requires a low voltage battery to be connected across it to produce oscillations in the microwave region. The diodes are mass-produced in a small plant at R.R.E. Their active part is a $10\ \mu\text{m}$ epitaxial layer of pure GaAs deposited on a substrate of highly conducting GaAs. This conducting substrate acts as the anode, while a silver contact evaporated on to the epitaxial layer forms the cathode. The completed dice, which are $400\ \mu\text{m}$ square, are mounted on molybdenum stubs and put into standard diode encapsulations.

R.R.E. were working on gallium arsenide in the early 1960s, before the Gunn effect was discovered. At that time it was thought that this material would be suitable for integrated circuits. A consortium of U.K. firms had been formed to explore the production possibilities of GaAs devices, and it was because of this early work, and successful co-operation between R.R.E. and the consortium, that the development of miniature radar went ahead so fast after the discovery of the Gunn effect. Incidentally the present leader of the R.R.E. team, Dr. Cyril Hilsum, is well known as the author of one of the first papers predicting the possibility of oscillations in GaAs and other bulk semiconductors*.

A further advantage of the Gunn oscillator over the klystrons and magnetrons normally used in radar trans-

* "Transferred Electron Amplifiers and Oscillators" by C. Hilsum. *Proc. I.R.E.*, vol. 50, No. 2, February 1962, pp. 185-189.

mitters is that it can be turned on and off more rapidly, to give extremely narrow pulses. In fact pulses as short as 3ns at 10 GHz have been obtained, and this means that a distance resolution of 0.5 metre is possible at ranges down to 2 metres—a useful facility in, say, the docking of ships.

The two devices illustrated are both Doppler radar systems. One is intended for use as a burglar alarm. The $6\text{in} \times 4\text{in} \times 4\text{in}$ box holds a transmitter, receiver and dry batteries, and the radar has a range (on a man) of about 50 yards. When it is operating in a room, any disturbance of stationary conditions, such as the entry of an intruder, causes the lamp on top to light—and, of course, an external alarm could be actuated. The other device is a hand-held, battery-operated Doppler radar for vehicle speed measurement. Its range is 50 yards on a man and 200 yards on a large vehicle, and the speed is read directly on a meter.

A third set, not illustrated, is a high resolution pulsed radar suitable for marine application and has a distance resolution of better than 1 m at ranges down to 2 m. The 10-GHz Gunn-diode oscillator is mounted across a waveguide in a straightforward radar transmitter-receiver system using a circulator, the receiver being blanked by a germanium diode switch during transmission. Switching of the Gunn diode is performed by an avalanche transistor circuit built into a coaxial structure. The best transmitter performance obtained has been pulses of 5 ns (half height) duration and peak power of 1 watt—that is, an energy of about 5 nJ per pulse. The receiver is a crystal video detector followed by a pulse amplifier with 1.2 ns risetime, and a sampling oscilloscope is used to give an A-scope display. It seems likely that this particular set will become available in commercial form.



(left) Portable radar speedometer being used to measure the speed of a car. The battery-operated microwave Doppler radar set has a range of about 200 yards on a large vehicle.


(below) Intruder alarm, showing warning lamp on top. The Doppler radar set inside uses a horn aerial giving a moderately wide beam, and has a range on a man of about 50 yards.



Acousto-electric V.H.F. Transmitter

THE simplest v.h.f./f.m. radio transmitter that one could hope to achieve was recently seen by *Wireless World* in operation at the Royal Radar Establishment, Malvern. Consisting of little more than a thin plate of cadmium sulphide with a voltage supply connected across it and an aerial attached, it was being used to transmit audio signals on a carrier frequency of 100 MHz across a room to an f.m. receiver. The power was only a few microwatts. This was in fact just a demonstration to illustrate some of the work of J. D. Maines and E. G. S. Paige at R.R.E. on acousto-electric oscillations in piezo-electric semiconductors, of which cadmium sulphide (CdS) is one. Nevertheless there are obvious practical uses for such a simple and cheap oscillator, which will operate between 30 MHz and 1 GHz, can be frequency modulated by a varying voltage and will generate oscillations in both electrical and mechanical form. In the transmitter, higher power could be obtained by more efficient crystal/aerial coupling.

Acousto-electric oscillations are the result of interaction between ultrasonic (mechanical pressure) waves set up spontaneously in the semiconductor by thermal effects, and the electrons which are caused to drift through the material by the voltage applied across it. Interaction occurs because the successive compressions and extensions of the ultrasonic waves, occurring as they do in a piezo-electric medium, produce electrical potentials within the material and these cause the drifting electrons to collect in bunches which travel with the waves (Fig. 1). If the electron stream is travelling in the same direction as the ultrasonic waves, and faster,

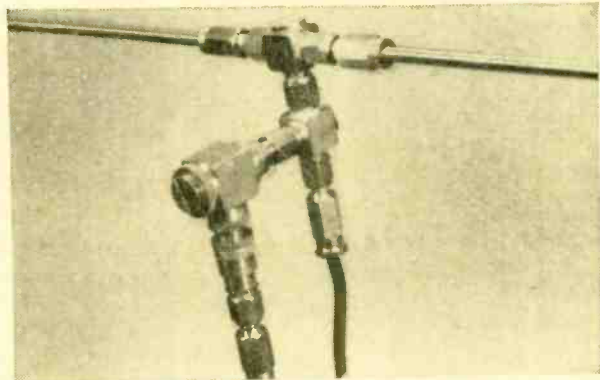

The transmitter, dipole aerial and light source assembly.

their interaction produces mechanical effects which augment the original waves—a phenomenon which has been used for acousto-electrical amplification in CdS. In the oscillator, however, when the ultrasonic waves strike an end face of the semiconductor they are reflected: the reflected waves are then travelling in the opposite direction to the electron stream and this causes them to be attenuated. After reflection at the opposite face the waves are once more travelling in the same direction as the electron stream, again being augmented by the effects of the electron-bunching, and by the time they have completed a "round trip" a net amplification has been obtained. Non-linear effects reduce the round-trip amplification to unity, and this, of course, is the condition necessary for self-sustaining oscillations.

After several hundred such round trips a steady-state acoustic oscillation on a single frequency is reached, and the electron bunching associated with this is sufficiently large to modulate the d.c. bias current. As a result electrical oscillations are produced in the supply circuit. The thickness of the CdS plate, t , determines which wavelengths can be supported ($2t=N\lambda$, where N is an integer) and, through the velocity of sound, which oscillation frequencies are possible ($f=v/\lambda$). If the piezo-electric plate were functioning as a crystal filter or transducer $N=1$, but in the demonstration transmitter $N=21$.

The velocity of the waves is determined by the applied voltage and the conductivity of the material. In CdS 0.2 mm thick, for example, frequencies between 20 and 500 MHz have been generated with applied voltages of 20 V to 100 V. For the 100 MHz demonstration transmitter a supply of 50 V is used. The conductivity of the CdS (typical resistivity $\approx 10^7$ ohm cm) is controlled by directing a light source of adjustable intensity on to the plate so that the incident photons liberate electrons in the material. As shown in Fig. 2 a small lamp is included in the v.h.f. transmitter for this purpose.

Since the frequency of oscillation can be varied by altering the CdS supply voltage, it is a simple matter to frequency modulate the transmitter by superimposing a modulating signal on the d.c. bias as shown in Fig. 2. The frequency shift obtained varies with supply voltage and material conductivity but a typical value is 10 kHz per modulating volt and in the demonstration transmitter the modulating voltage range is about 0–2 V.

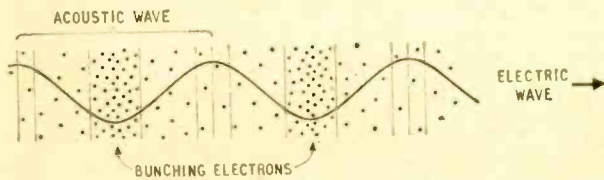


Fig. 1. Interaction of acoustic and electric waves.

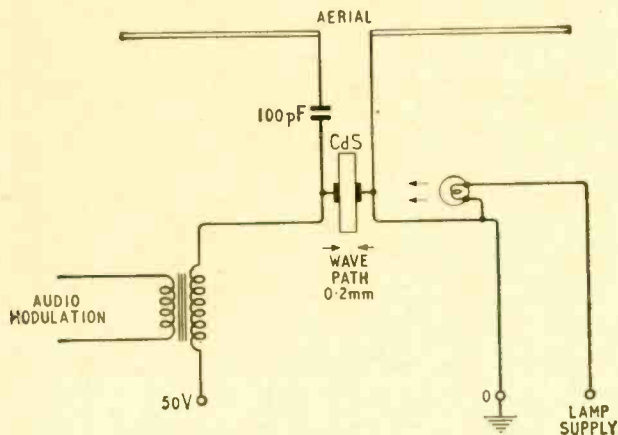


Fig. 2. Circuit of the v.h.f. transmitter, showing light control.

WORLD OF WIRELESS

Satellite vs Cable Communications

WHEN commercial telephone traffic via Early Bird commenced in 1965 the Scandinavian countries had three circuits with New York terminating in Oslo, Stockholm and Copenhagen, and routed via London. It was decided to make a subjective evaluation of whether calls via Early Bird were acceptable to the general public, the idea being to make as close a comparison as possible with existing cable circuits to New York. A total of 1,624 satellite calls were listened to by operators and notes made of the quality of the connections and subscribers' reactions and comments. The same process was repeated on 844 cable calls. In a second stage of these tests subscribers were interviewed immediately after calls, in accordance with an agreed questionnaire. Each of the three terminal stations in Scandinavia made interviews after 50 satellite calls and 50 cable calls, making a total of 300 calls in all. The subscribers had no idea which means of communication they had used and no

subscriber was interviewed more than once and, in addition, no publicity was given to the tests.

It is obvious from what has been said that the statistical material obtained was very limited, nevertheless it was thought that investigations over a longer period or with a greater number of circuits would not have produced substantially different results. The main conclusion of the tests is that calls via Early Bird have been generally satisfactory to the Scandinavian public and the results of the objective evaluation of such calls are very much the same as for the cable calls. The tabulated result showed that, based on the operators' report, 84.1% of the satellite calls were found to be very good as against 76.1% of the cable calls. Observations of echo, crosstalk and signal level variation showed little difference between systems. Of the interviewed subscribers 46.7% found the satellite and 54% found the cable very good.

Television-telephone Trials in America

FIELD trials on a visual telephone equipment suitable for use in the office or home will commence next September. Known as the Picturephone and developed by Bell Telephone Laboratories of America, the equipment will be built and evaluated by Westinghouse Electric Corporation. For the trials some 40 sets will be manufactured, 28 will be installed in Pittsburgh and 12 in New York so that the usefulness of the system for both inter- and intra-city communications can be gauged. Providing the trials are a success, the American Telephone and Telegraph Company, Bells' parent organization, said that it hopes to introduce a limited number of the sets into customer service in the early 1970s.

A silicon target camera tube is employed utilizing an electronic zoom system, adjustable focus and an automatic iris resulting in the production of good pictures over a wide range of ambient lighting conditions. A screen measuring 5.5in x 5in is incorporated and this, in conjunction with the

wide angle capability of the camera lens system, gives the user considerable latitude regarding side to side movement. To enable larger scenes to be transmitted the camera may be focused at 20ft. Printed matter may also be sent, and for this the camera is focused at 1ft. When this is done a built-in mirror swings to an angle of 45 degrees in front of the lens so that the material may be placed flat in front of the picturephone. When used for normal face-to-face conversation the depth of field is 16 inches centred on 32 inches. A typical installation comprises: dialling unit, control unit, display unit and a service unit. Four push buttons enable the user to initiate a video or voice-only call, to see the picture he is sending out, to prevent his picture from being transmitted—in this case a bar pattern is sent instead, and to select either a normal handset or a loudspeaker for the sound.

The camera tube employed is interesting in that the target consists of a small silicon slice containing over half a million photodiodes. An advantage of this tube is that its performance is not degraded or modified by exposure to bright light or by electron beam bombardment and it does not suffer from optical or raster "burn in."



Submarine Acoustics

ENGINEERS from Honeywell's Marine Systems Centre at Seattle have started a three-year research programme to study the underwater scattering of sound waves. The object of the programme is to discover whether any consistent patterns emerge so that future marine acoustics instruments may be programmed to take them into consideration. The scattering medium consists of micro-organisms and impurities suspended in the sea that distort the sound paths in such a way as to make signals unreliable or too weak to be detected at all; it is known that air bladders in fish are a real factor in sound deflection. It was formerly assumed that the scattering field could be modelled on the homogenous, densely populated impurities and could be averaged for practical purposes, but this approach is now considered to be insufficiently precise. A 1,600 pound acoustic sensing and transmitting instrument has been set up on the ocean bed in the Strait of Juan de Fuca, British Columbia, where

the Pacific Ocean penetrates a protected salt-water labyrinth. The eight-foot high unit will send signals from a depth of 325 ft to Honeywells' research vessel *Neper* and at the same time water current, salinity, dissolved oxygen and temperature will be measured. The experiment is claimed to be the largest company sponsored basic research programme on underwater acoustics ever carried out.


The formal opening of Heriot-Watt University's new Mountbatten Building by Earl Mountbatten of Burma took place on January 3rd. The opening ceremony followed a graduation ceremony at which Sir Alec Douglas-Home, Chancellor of the University, conferred honorary degrees upon a number of dignitaries including a doctorate of science on Earl Mountbatten. The new building was recently completed at a cost £650,000 and accommodates the Department of Electrical and Electronic Engineering and departments of the Faculty of Humanities. The building is T-shaped in plan and it includes a 250-seat conference theatre with adjacent conference rooms, a television suite (see "News from Industry," page 707), two main lecture theatres and a number of well-equipped laboratories—including a language laboratory. Every room is wired for closed circuit television and a comprehensive network connects the TV complex in the Mountbatten Building with the main University building providing direct two-way links.

To assist listeners in parts of Scotland who are having difficulty in receiving B.B.C. Radio 2 on 1,500 metres and who do not possess a v.h.f. receiver, low-power repeater stations have been installed in Glasgow and Edinburgh. These stations will provide local reinforcement of Radio 2 by making use of the international common wavelength of 202 metres. The range of stations using this wavelength is restricted by international regulations to only a few miles. In addition the useful range is further limited at night by interference from the other 150 European stations that share this wavelength. The possibility of operating additional transmitters on this wavelength in other parts of Scotland is being investigated.

The Eddystone Radio essay competition organized early in 1967 has been won by Bruce Taylor, a 25-year-old student who is engaged on Ph.D. work at Edinburgh University. For his essay describing a new approach to radio receiver design he wins an EA12 Eddystone communication receiver worth £185.

The Simon Memorial Prize for 1968 has been awarded by The Physical Society to Dr. K. A. G. Mendelssohn, F.R.S., Reader in Physics in the University of Oxford, in recognition of his distinguished work on superconductivity and the properties of liquid helium.

Professor J. Barraquer, an eminent Spanish eye surgeon, flew into London recently to see a demonstration of EMI's miniature television camera, type BC.930. Professor Barraquer, who specialises in anterior chamber surgery of the eye, required a high quality camera of small dimensions for use in the operating theatre at the Clinica Barraquer in Barcelona. The EMI BC.930 is 1.7 inches in diameter and about the size of a small pocket torch. Using a $\frac{1}{2}$ -inch vidicon camera tube, the BC.930 gives high resolution pictures with a very low noise level. After a test of the camera's capabilities, Professor Barraquer returned to Spain the following day with the camera. The picture shows Professor Barraquer using the camera during his evaluation.

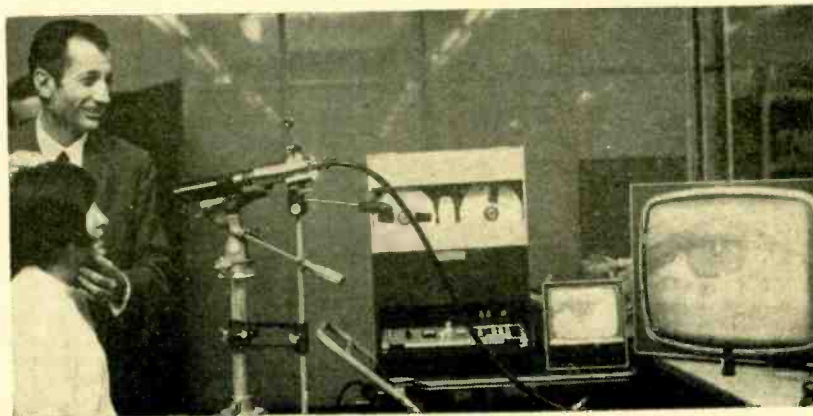

ANNOUNCEMENTS

The second International Broadcasting Convention is to be held in London from the 9th-13th September. Sponsored jointly by the Electronic Engineering Association, the I.E.E., I.E.R.E., I.E.E.E. and the Royal Television Society, it will include an exhibition and the television conference already announced by the learned Societies. Enquiries should be addressed to the International Broadcasting Convention, Savoy Place, Victoria Embankment, London, W.C.2.

A second conference on solid state devices is being arranged by the Institute of Physics and the Physical Society in collaboration with the I.E.E., I.E.R.E. and I.E.E.E. The conference will be held at the University of Manchester Institute of Science and Technology from 3rd to 6th September.

A 98-page prospectus giving details of full-time and sandwich courses to be held during 1968 and 1969 at the Borough Polytechnic, Borough Road, London, S.E.1, is now available.

A course on high-fidelity sound reproduction will be held each Wednesday evening during February and March at Hendon College of Technology, The Burroughs, London, N.W.4.

A course of three evening lectures on the science and engineering of elementary particle physics will be held at University College, Gower Street, London, W.C.1, on Mondays at 5.30 commencing February 26th.

Some 25 American manufacturers of miniature and micro-miniature components are collaborating with the U.S. Department of Commerce to stage an exhibition of the latest products at the United States Trade Center in London, between 14th and 22nd February.

Now available from G. A. Stanley Palmer Ltd. are Type KS 1 polystyrene film capacitors manufactured by the German company Ernst Roederstien. The capacitance values range from 5 pF to 0.022 μ F with working voltages of 25, 63, 160 and 630 V and tolerances vary from $\pm 2.5\%$ to $\pm 20\%$. The temperature range is -10 to $+70^\circ\text{C}$.

The telemetry system for Britain's satellite launching vehicle Black Arrow is to be supplied by E.M.I.

For the sum of £150 per day, a complete closed circuit colour television system can be hired, with a cameraman and engineer, from Closed Circuit Television Hire, 93 Greenfield Road, London, E.1.

A new service for independent testing of audio equipment is available from H. F. Engineering, 3 Willowbank, Sunbury-on-Thames, Middx.

PERSONALITIES

The B.B.C. has announced that **James Redmond, F.I.E.E.**, assistant director of engineering for the past year, is to become director of engineering when **Sir Francis McLean** retires in May. Mr. Redmond, who is 49, served as a marine radio officer before joining



J. Redmond

the B.B.C. in 1937 and also during the war. In his early days with the Corporation he was in the Television Service at Alexandra Palace. He became asst. superintendent engineer (film) in 1956; supt. engr. (television recording) in 1960; supt. engr. television (regions and O.Bs) in 1962; for the past year he has been responsible for the operational work of the Engineering Division.

S. N. Watson, F.I.E.E., head of the B.B.C. Designs Department for the past four years, is to become chief engineer, television, when **T. H. Bridgewater, O.B.E., F.I.E.E.**, retires in April. Mr. Watson joined the B.B.C. in 1933 and after serving at the Newcastle and Birmingham studios he became an engineer in the Lines Department in 1938. He transferred to the Designs Department in 1947 and became head of the television group in 1951.



S. N. Watson

L. A. A. Thomas, B.Sc., F.I.E.E., F.Inst.P., chief physicist at the G.E.C. Hirst Research Centre, Wembley, since 1961, has been appointed visiting professor in the School of Physics at Bath University of Technology. He will be lecturing to postgraduate students in solid-state physics and will advise the School of Physics on both undergraduate and postgraduate courses. Mr. Thomas joined the Research Laboratories of the G.E.C. in 1935, graduating at the University of London in 1938, and specializing later in the fields of crystallography and magnetism.

Gerald H. Askew, B.Sc., M.I.E.E., who has been with Peto Scott Ltd. for the past three years, has become chief engineer and will manage the development laboratory. After graduating at King's College, London University, he joined Kolster Brandes Ltd. in 1945 as a junior development engineer. Seven years later he went to Cinema Television (now Rank Cintel) where he



G. H. Askew

became section leader and was concerned mainly with the development of flying-spot teletext equipment. Mr. Askew, who is 42, left Rank Cintel in 1964 to join Peto Scott.

I. W. Dick, who resigned last October as managing director of the Marconi Marine Company's Norwegian associates, Norsk Marconikompani A/S, which he joined as general manager in 1962, has been appointed management executive with the parent company. Mr. Dick served as an instructor in air radio in the Royal Air Force during the war, and on leaving the Service in 1946 became an instructor at the Glasgow Wireless College. He later joined the seagoing radio officer staff of the Marconi Marine Company. In 1955 he was transferred to the company's technical shore staff.

G. C. Briggs, Grad.I.E.R.E., who joined Marconi Instruments in 1959 as a special trainee after 15 years' service in the Royal Navy from which he retired with the rank of lieutenant commander, has become manager, commercial administration. In 1960 he joined



G. C. Briggs

the company's technical sales department and has for some time been field sales manager. He is succeeded in this position by **T. L. Clarke, B.Sc.(Eng.), M.I.E.E.**, who has been with Marconi Instruments as senior representative in the Midland Area since 1963. A graduate of King's College, London University, he served his graduate apprenticeship with B.T.H. During his National Service with the R.E.M.E., he served as a staff instructor on radar equipment at the Army School of Electronics at Arborfield, leaving the Service with the rank of captain. He then joined Iso-



T. L. Clarke

tope Developments Ltd., as a senior development engineer, and from 1957 to 1963 was technical sales manager of I.D.M. Electronics Ltd. Marconi Instruments also announce the appointment of **J. H. Buying** to the newly created post of manager, overseas projects. He will be responsible for the

smooth running of the Company's overseas manufacturing operations (at present in the U.S.A., Italy and India), whilst also retaining his duties as an export regional manager. Mr. Buying joined Marconi Instruments as an X-ray development engineer in 1948, following service with Philips Electrical Ltd. In 1950 he became a service engineer with General Radiological Ltd. but rejoined Marconi Instruments, as a sales engineer in the Export Department in 1954.

Leonard T. Perriam, M.A., who joined Daystrom Ltd., of Gloucester, six years ago as technical sales and service manager of the Industrial Products Division, has been appointed managing director. He has succeeded **A. E. B. Perrigo, M.Sc., F.I.E.E.**, who has been managing director since the formation of the company in 1960, and recently took up the appointment of director of the Small Businesses Centre at the University of Aston, Birmingham. Mr. Perriam was for some fifteen years with I.C.I. Ltd., working on instrument development, before joining Daystrom.



L. T. Perriam

Kenneth L. Richardson, a technical systems supervisor at the London Air Traffic Control Centre, Heathrow Airport, has received a cheque for £500 "in recognition of his suggestion which has led to improvements in the performance of radar displays used by air traffic controllers." The Committee on Awards to Inventors considered that Mr. Richardson had provided an elegant solution to a long-standing problem and had made a significant contribution to safety. Mr. Richardson, who is 43, joined the National Air Traffic Control Service in 1947 and at the time he made the suggestion was engaged on radar maintenance at the London A.T.C. Centre. Now known as Selective Moving Target Indicator, the specification prepared by Mr. Richardson has been developed by Solartron Ltd. who have been asked by the Board of Trade to incorporate S.M.T.I. into five long-range radars at Ash (Kent), Ventnor (Isle of Wight), Clee Hill (Shropshire) and East and West Harrow on a trial basis and it will probably be incorporated in radars at ten civil airports.



J. Baldwin

John Baldwin, B.Sc., A.Inst.P., recently joined the I.T.A. as head of the video and colour section of the Experimental and Development Dept. Mr. Baldwin, who is 39, had been chief engineer and research and development manager of Peto Scott Ltd. since 1965. Prior to joining Peto Scott in 1964 he had been for 14 years with Rank Cintel.

Alfred Woods, who has joined the I.T.A. as contracts engineer in the Station Design and Construction Dept., was with E.M.I. Electronics from 1958, latterly as commercial contracts officer. Prior to joining E.M.I. he served with R.E.M.E. on a short-service commission.

Philip Darby, who joined the I.T.A. staff in 1955 as a senior shift engineer at the Caldbeck transmitting station,



A. Woods



P. Darby

is appointed head of the technical quality control section of the Authority's Operations and Maintenance Dept. Mr. Darby, who is 42, became assistant engineer-in-charge at the Emley Moor transmitting station in 1956 and has been engineer-in-charge of the Dover transmitting station since 1959.

G. Kaye, M.I.E.E., recently joined ATV Network Ltd. (I.T.A. programme contractors for London and the Midlands) as head of engineering. For the past eleven years he has been with Alpha Television Studios latterly as engineer-in-chief. Mr. Kaye was for two years with the B.B.C. before joining the R.A.F. as a radar mechanic in 1946. After the war he went to E.M.I. Research Laboratories and from 1954-6 was studio manager of High Definition Films Ltd.

NEW YEAR HONOURS

Among the recipients of awards in the New Year Honours list are the following:—

Oliver W. Humphreys, C.B.E., B.Sc., F.Inst.P., F.I.E.E., who was for many years director of the G.E.C. Hirst Research Centre, Wembley, and recently retired as vice-chairman of the General Electric Company and also as chairman of the Conference of the Electronics Industry, has been created a knight bachelor.

C.B.
Captain M. Hodges, O.B.E., M.I.E.R.E., Royal Navy (retired), lately Under Secretary, Cabinet Office.

Ieuan Maddock, O.B.E., F.R.S., M.I.E.R.E., Controller of Industrial Technology, Ministry of Technology.

C.B.E.
B. J. A. Bard, D.I.C., Ph.D., board member and chief executive (department of applied science), National Research Development Corporation.

E. L. T. Barton, O.B.E., M.I.R.E., chief of telecommunications (civil aviation) Board of Trade.

H. K. Robin, chief engineer, Diplomatic Wireless Service, Foreign Office.

O.B.E.
E. R. T. Ponsford, chairman and managing director of Solartron Electronic Group Ltd., for services to export.
W. H. Storey, managing director of Unicam Instruments Ltd., for services to export.

M.B.E.
E. A. Beaumont, superintendent engineer, B.B.C. External Broadcasting.
G. A. C. R. Britton, M.I.E.E., lately senior executive engineer, G.P.O. Radio Planning & Provision.
A. G. German, M.I.E.E., senior executive engineer, G.P.O.
C. E. Hutchings, assistant station radio officer, Government Communications Headquarters, Foreign Office and Commonwealth Office.

B. B. Learoyd, co-ordinator, colour familiarisation, B.B.C.

B.E.M.
H. E. Wall, receiver technician, B.B.C.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents

"A Genuine Reject?"

PUTTING spurious type numbers on transistors amounts to giving a false description of goods offered for sale. This is an offence. Unfortunately, unscrupulous vendors are likely to get away with it, because the victims are invariably buyers of small quantities, who cannot afford to go to law.

A reasoned complaint is sometimes effective, but if no redress is obtained the buyer should complain to the magazine in which the goods were advertised. The advertisement managers of reputable magazines always pay attention to reasonable complaints.

Magazine publishers do possess the ultimate sanction of refusing to accept further advertisements, thereby depriving a mail order firm of its "shop window", and while this sanction is seldom exercised (perhaps too seldom), a reminder that it exists can curb the excesses of some advertisers.

"Unmarked transistors are in quite a different category to "re-marks". The vendor does not often claim that they meet a standard specification, and in practice they range from straightforward factory rejects (including out-and-out duds) to perfectly genuine transistors which conform exactly to a standard specification. The trouble is that there is no way of distinguishing the sheep from the goats. Unless the supplier is prepared to quote a definite specification the description of such goods as "tested" or "guaranteed" is almost meaningless. Even if a specification is forthcoming, the things it leaves unsaid may be more significant than the things it says. A transistor with $h_{fe}=200$ at $I_c=1$ mA may appear to be suitable for use in low-level a.f. stages, but what about leakage and noise? It may have been rejected on these very counts. Testing transistors thoroughly calls for time and proper equipment, and as the specification of an unmarked transistor is made more rigid so the price rises towards that of the genuine article.

There is a third class of transistors: those marked with type numbers, but not type numbers which appear on any transistor maker's lists. They are sometimes peculiar to a large-scale user, such as a computer maker, who

arranges with the manufacturer for a supply of transistors which are a variant on some standard type, but there are other possible explanations, less attractive to the buyer. To my knowledge at least one big manufacturer has been known to mark his own rejects with both non-standard type numbers and the name of an obscure subsidiary company as a 'front' for marketing them.

GEORGE WAREHAM

London, W.C.2

AS ONE of the "home constructors" referred to in your January Editorial, I welcomed your remarks about "reject" transistors. But what can be done about it? A glance through the smaller display advertisements in that issue reveals the following descriptions:

1. "Genuine brand new products."
2. "100% tested transistors."
3. "Fully guaranteed devices."
4. "All guaranteed."
5. "Discount transistors."
6. "First grade, guaranteed."
7. "Transistors—not remakes."
8. "Best quality new semi-conductors."
9. "Brand new, first grade and guaranteed."
10. "No duds: uncoded devices."

And many, many more variations, including those that claim "unmarked" as if it were an advantage.

Nor are these the only snags into which the "home constructor" can run, particularly if components for high-quality audio equipment are needed. Even a simple piece of equipment can involve six suppliers. My efforts to obtain a series of small non-electrolytic capacitors produced an incredible series of replies ranging from "6s each but out of stock" to "£3 each and 26 weeks delivery."

I hate to be able to paint the U.S.A. in a better light, but there one can obtain massive catalogues free and obtain ALL your parts, post free, from one supplier.

GORDON B. NESS

Altrincham, Ches.

The Future of British Electronics

I DISAGREE with your Editorial in the December issue on two counts. First, electronics is now growing from the *black box* to the *systems* phase. So long as one was concerned with the production of individual "black boxes", the design of the detailed circuits (i.e. the connecting together of selected discrete components) was the aspect on which the designer exercised his skill. But surely the main concern of the equipment designer now is with systems, and he is not interested in the contents of a package provided it gives him the specification he wants. If an equipment designer can call for an i.c. linear amplifier, in terms of gain, bandwidth, distortion and peak-to-peak output voltage, or a logic circuit in terms of fan-in, fan-out, 0 and 1 levels, propagation, time and noise immunity, is not this better than being

obliged himself to assign a value to every individual component in such a circuit? L.S.I. might be thought to be a move to extend integrated-circuit techniques from the black-box to the systems phase. But the l.s.i. manufacturer could not sell his wares unless either he had engaged in vertical integration, in the economic sense, so that he had changed from being an i.c. manufacturer to being an equipment manufacturer, or he was manufacturing to the requirements of equipment manufacturers. Presumably it is the former alternative which equipment makers fear.

Secondly, I do not like the protectionist idea of a "Buy British Act." Apart from military projects (to which special strategic considerations apply) products should be bought on the basis not of brand image but of specifica-

tion, price and delivery. If British made components cannot compete on this basis, there is no hope for them in the long run. But if British purchasing executives place orders irresponsibly (as suggested in your Editorial), it is the business of the managements who employ them to see that they mend their ways. It must be rare for the merits of rival suppliers to be so finely balanced that they cannot be differentiated until one finds a difference in nationality. If the British component manufacturer is consistently inferior to the foreigner, then the British equipment maker cannot afford to buy British; because if he buys his components for non-commercial reasons the equipment he wishes to sell will not remain commercially competitive.

D. A. BELL

University of Hull.

Identification of Electronic Parts

WE were, of course, extremely interested in Dr. Stanton's letter in the January issue concerning identification of electronic parts under the BS 9000 scheme run by the Institution.

You, sir, have partially given the answer to Dr. Stanton in your Editorial, but it is worth adding a few more facts. The committee co-ordinating the implementation of the Burghard recommendations considered very carefully the question of parts identification. They decided that first priority was to get the specification system going and that it would be better to consider an identification code after some viable specifications were in being. It was felt that, when this stage was reached, the practical implications to which you yourself refer on page 619 would be more easily assessed.

It may be of interest that this co-ordinating committee is comprised of organizations representing the manufacturers of active and passive electronic parts and industrial and Government.

ROHN HOPPER


British Standards Institution,
London, W.1.

Semi-stabilized D.C. Supply

THE term "semi-stabilized" was used to describe my circuit (October 1967, p. 482) because the stabilization is obtained, not by comparing the output voltage with a reference voltage and then applying a correction, as in a conventional series stabilizer, but by recourse to a sort of "dead reckoning" process. With such a system, the degree of perfection attained in the stabilizing action cannot be made arbitrarily large as it can in theory in a series stabilizer by making the loop gain very high.

Nevertheless, the performance is quite good enough for many purposes. Even without load-current compensation the output voltage of my prototype stays within half a volt of 15 V over the range 0-150 mA. The variation can be reduced to less than 0.1 V by using load-current compensation, and improved still further by the methods kindly suggested by Mr. Peter Williams (November, p. 554). The only serious shortcoming is that if the circuit is set up to give optimum performance at one output voltage it does not necessarily provide optimum performance at other output voltages.

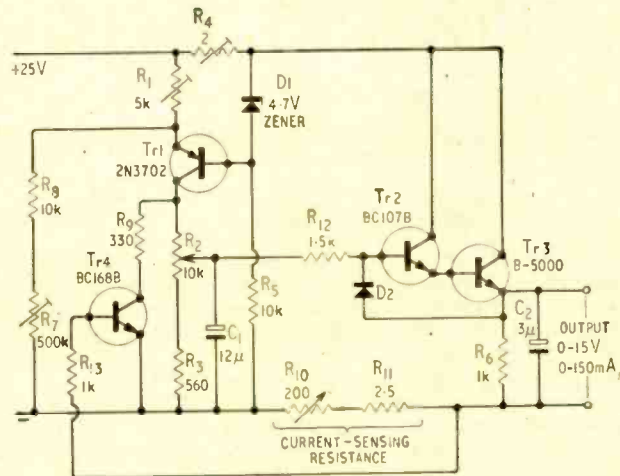In the revised circuit shown here, Mr. Williams' method of compensating for input-voltage variations by means of resistance R_7 is incorporated. With careful adjustment perfect compensation can be achieved at any chosen output voltage. A current-limiting circuit (Tr4,



R_{10} , R_{11} , etc.) has been substituted for the lamp used in the original version. The output current can be limited to anything between about 3 mA and 0.25 A with the values of current-sensing resistance shown. Smoothing capacitor C_1 has been retained because the optimum setting of R_7 for supply voltage compensation turned out to be different from the optimum value for hum cancellation. This is presumably an indication that the a.c. impedance of the Zener diode differs from its d.c. incremental resistance. With some output transistors a leakage current of several milliamps flows, and for this reason R_6 has been reduced to 1 k Ω so that the minimum output voltage off load is kept small.

G. W. SHORT

Croydon

Variants on the Ring-of-two Reference

FIRST may I apologize for a silly slip in my letter published in the November issue. The bridge action referred to for balancing out the effects of supply changes should not have included the combination $R_2 + R_3$, but rather the added compensating resistor R_7 .

The high performance of the single Zener diode form of the ring-of-two reference described by Mr. May (November "Letters") shows the flexibility of this circuit. I agree entirely with him on the self-starting problems that may exist, and in my original letter (September 1966) had described the circuit as "a complementary bistable with catching Zeners." The single diode circuit is a good example of how, even in these days of massively increasing publication, effort is duplicated. I, too, have used it for some time and referred to it in a letter published in June 1967 (p. 301) without knowing of Mr. May's design. Already I have come across half a dozen individuals who have devised variants on the ring-of-two reference quite independently.

It occurs to me that there may be other readers who have done so, or have seen some published information. Might I ask any such to get in touch with me, as it would help me considerably in a research project I have undertaken. In return I would gladly supply them with a complete list of information received should they wish it.

PETER WILLIAMS

Dept. of Elec. Engg.,
Paisley College of Technology,
Paisley, Renfrew.

TECHNICAL NOTEBOOK

Computer Aided Circuit Construction

MUCH design effort in electronics can be saved by using computers to work out problems which are solvable by a systematic, logical routine. At the Royal Radar Establishment, Great Malvern, experiments are being conducted in using a computer to decide the optimum placing of components on printed-circuit boards—in particular the placing of dual-in-line integrated circuit packages on a rectangular matrix. Ultimately the computer programmes will be used in conjunction with a conductor route running programme to provide a complete placing and interconnection diagram. So far, three programmes, based on two algorithms, have been evolved.

To determine the optimum placing of a package any one of a number of criteria can be used. Two programmes prepared at R.R.E. have as their aims: (1) the minimum number of through connections from one side of the board to the other; and (2) the minimum length of leads between packages. The first programme helps to reduce the number of plated-through holes required on double-sided boards. If two packages are electrically connected the programme will try to place them in either the same row or the same column of a matrix arrangement. The second programme will try to place packages which are electrically connected as close to each other as possible. An alternative version using a square law tries to reduce very long leads.

A random initial placing is assumed in each case, and then pairs of packages are exchanged in the matrix. At each stage all the possible exchanges are considered, then the


best one is selected. For practical boards the programmes take into account fixed devices such as plugs and sockets, and for a board containing twelve packages and an edge connector a layout can be produced, using about 3,000 words of computer storage, in approximately 15 seconds. Practical boards usually do not have very well defined "best arrangements," and it is sometimes difficult to decide which of two alternatives is really optimum.

R.R.E. are also using computers to design integrated circuits. In general, the computer does d.c. and transient analyses of a theoretical circuit design and from this produces information for the manufacture of the masks used in fabricating the i.c.s. A circuit analysis programme for use in the design of m.o.s. integrated circuits has been written. This can analyse any circuit made up of resistors, m.o.s. transistors and their associated capacitances, and has a simple but flexible input code so that it can be used by a circuit engineer with no knowledge of computer programming. The programme has been applied to the design of a four-stage binary counter, containing 84 transistors on a 0.06-in square silicon chip. Sample devices have been made by using the resulting mask master drawings in Plessey's i.c. manufacturing process. Work has now started on a language for describing integrated circuit layouts to the computer. The stored information will then be used for mask checking, calculation of circuit parameters for use by analysis programmes, and for control of an automatic mask making machine.

Monolithic F.M. Discriminator

A SMALL quartz plate carrying a simple electrode pattern that will detect narrow-band f.m. signals has been developed by Bell Telephone Laboratories, U.S.A. The device eliminates the need for the second stage converter used in many f.m. receivers and is superior to conventional crystal units with comparable bandpass limits. The discriminators can be produced to operate at frequencies in the range of 10 to 30 MHz with a passband ranging from 0.01%

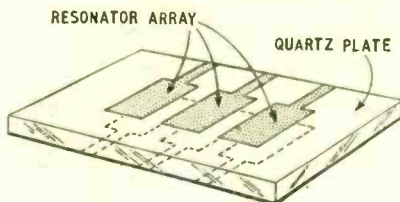to 0.02% of the desired midband frequency. The discriminator consists of an AT cut quartz plate 0.5in x



0.25in and a triple resonator array formed by depositing gold electrodes on the two major surfaces. The amount of gold deposited sets the frequency of each region; by this means the centre region is adjusted to resonate at the centre frequency and the outer regions above and below this to give the required passband. The resonant frequencies are determined partly by controlling the mass of the gold deposited and partly by the properties of the crystal. The device operates in a similar fashion to electric circuit discriminators except that the resonators and coupling are mechanical. Electro-mechanical conversion is carried out through the piezo-electric effect.

Picosecond Pulses Observed in Q-switched Lasers

TRAINS of light pulses with individual pulse lengths in the picosecond region have been discovered in the outputs of ruby and neodymium: glass lasers Q-switched by a rotating mirror. These pulse trains were previously thought to be a single pulse due to the resolution, or lack of it at these speeds, of oscilloscopes. The discovery, made at Bell Telephone Laboratories, U.S.A., made use of a phenomenon known as two-photon fluorescence to display the pulses. Using this method, pulses of less than a fraction of a picosecond may be seen. The train of light pulses to be observed is directed on to a mirror immersed in a fluorescent liquid and the pulses are reflected back on themselves. Two-photon fluorescence occurs at the points where two pulses overlap, causing bright luminous spots to appear. These are photographed and measured to determine their duration. Using this technique, pulses with a duration of about ten picoseconds in ruby lasers and less than one picosecond in neodymium: glass lasers have been observed. Pulses from two to eight microseconds in duration had previously been produced in a neodymium: glass laser Q-switched with a special dye. At the time it was generally believed that the dye was the agent responsible for the appearance of the short pulses. However, the new observations show clearly that the mechanism for the generation of these pulses is inherent in the laser itself.

Emitter-coupled, Emitter-timed Multivibrators

2: Monostable circuits


By G. B. CLAYTON, B.Sc., A.Inst. P.

LAST month the advantages of emitter-coupled emitter-timed circuits were discussed and the astable multivibrator was looked at in detail. An example of a monostable multivibrator that forms the basis of this month's article is shown in Fig. 13. In the permanently stable state Tr2 is conducting and Tr1 is off. The circuit loop—emitter Tr1—collector Tr1—base Tr2—emitter Tr2—emitter Tr1—is regenerative and if Tr1 is brought into conduction, by a positive pulse applied to its base, a regenerative switching action takes place which switches Tr2 off. The negative step at the emitter of Tr2 is communicated to the emitter of Tr1 by capacitor C, diode D2 is reverse biased. The emitter current I_e is transferred to Tr1 and C charges (Fig. 14) causing the potential at the emitter of Tr2 to fall towards earth. After a period t_p , Tr2 goes into conduction again and a regenerative action returns the circuit to its permanently stable state.

The waveforms observed in the circuit are shown in Fig. 15. At the end of the timing period the emitter of Tr1 is driven positive and the capacitor C has then to discharge. The discharging current, in addition to the current through R_4 , passes through Tr2 and is responsible for the overshoot in the collector waveform of Tr2. The overshoot decay and recovery time are governed by a time constant $C(R_3 + R_d + R_1)$. Where R_d is the effective resistance of diode D2 and R_1 is the input resistance at the emitter of Tr2. The run down in the emitter voltage of Tr2 during the timing period is non-linear accounting for the slope in the collector waveform of Tr1. The transistors do not saturate and the circuit is capable of producing narrow pulses, Fig. 15 (c) shows a 320 ns. pulse at the collector of Tr2.

A detailed design procedure will not be given since the circuit will operate satisfactorily with a fairly wide range of component values. Care must of course be taken to

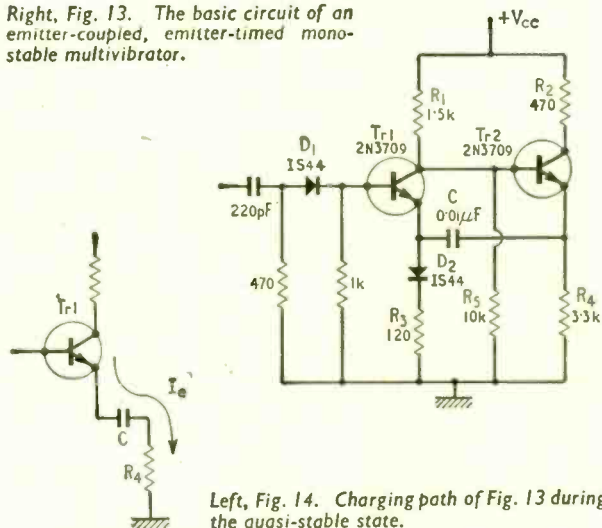Right, Fig. 13. The basic circuit of an emitter-coupled, emitter-timed monostable multivibrator.




Left, Fig. 14. Charging path of Fig. 13 during the quasi-stable state.

ensure that the transistor ratings are not exceeded. The following are some useful design equations; The pulse width is given by the approximate relationship $t_p = CR'(1 - R'/2R_4)$. Where $R' = R_1R_5/(R_1 + R_5)$.


The emitter current of Tr2 in the permanently stable state is given approximately by: $I_e = V_{c'}'/R_4$, where $V_{c'}' = V_{cc}R_5/(R_1 + R_5)$ is the potential at the base of Tr2 in the permanently stable state.

The output pulse height at the collector of Tr2 is equal


Fig. 15. Waveforms of Fig. 13. (a) The upper trace shows the waveform of the emitter and the lower trace the waveform at the collector of Tr1. (b) The collector (upper) and emitter (lower) waveforms of Tr2. (c) High speed performance of the monostable; a 320 ns pulse at the collector of Tr2 the timing capacitor reduced to 330 p.

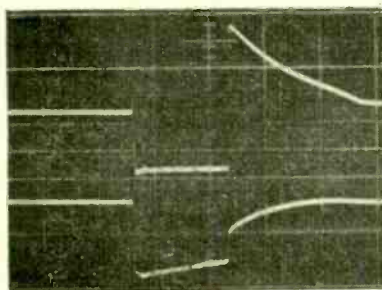

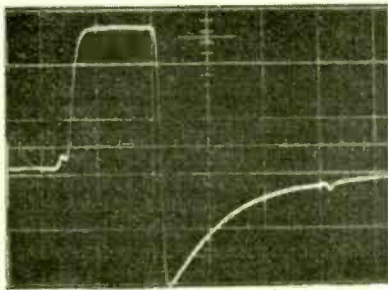(a) upper — 1 V/cm,
lower — 5 V/cm. 5 μs/cm.



(b) 2 V/cm. 5 μs/cm.

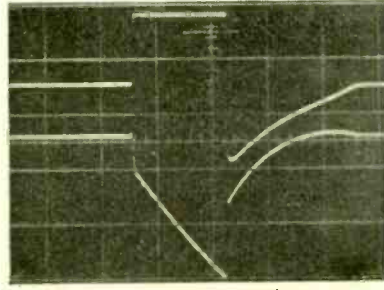

(c) upper — 2 V/cm. 5 μs/cm.
lower — 1 V/cm. 0.2 μs/cm.

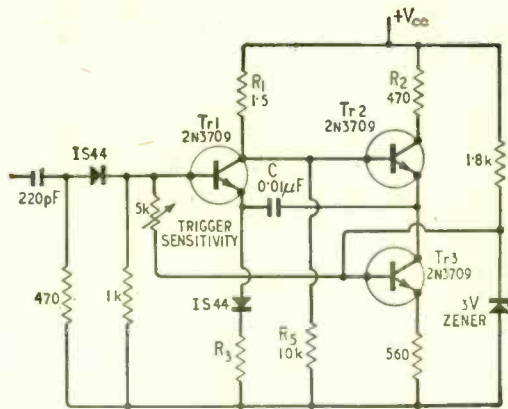



Fig. 16. An improved emitter timed monostable.

to (V_c'/R_4) . R_2 . The fastest switching is realised if the transistors are not allowed to saturate, in the case of Tr2 the output pulse height should be made less than $V_{cc} - V_c'$ and for Tr1 R' should be less than R_1 if saturation is to be avoided.


It is advantageous to make V_c' as large as possible in order that the pulse width should be reasonably stable against changes in the supply voltage V_{cc} . (See appendix). Using the component values shown in Fig. 13 a change in supply voltage from 20 to 30 V was found to change the pulse width by 10%. The trigger sensitivity of the circuit is low. This is to be expected since the triggering pulse has to supply a forward bias to three silicon p-n junctions (D1, D2 and the base emitter junction of Tr1) before any current can pass in Tr1. This situation can be improved by connecting a 5 kΩ variable resistor between the positive supply rail and the base of Tr1. When this resistance is reduced below a certain value the circuit free runs.

The performance of the circuit of Fig. 13, as far as the stability of the pulse width is concerned can be improved if the emitter resistance R_4 is replaced by a transistor acting as a constant current source.¹ An example of a practical circuit using this modification is shown in Fig. 16. This circuit incorporates a trigger sensitivity control in the form of a variable resistor connected between the base of Tr1 and the stabilized zener voltage supply. The waveforms obtained with this circuit are shown in Fig. 17. The run down in Tr2 emitter voltage

Fig. 17. Waveforms of Fig. 16 (a) Upper trace-collector, lower-trace emitter, Tr1 (b) upper trace-collector, lower trace emitter Tr2.

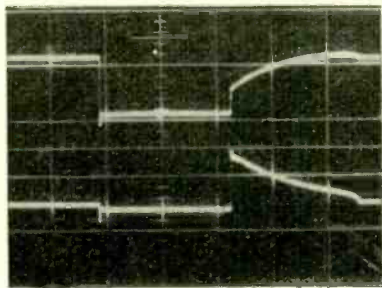

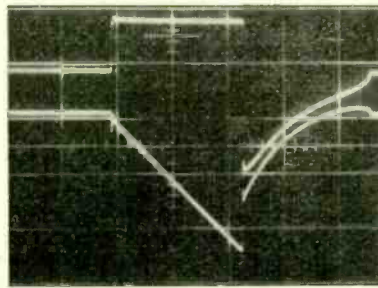(a) upper — 5 V/cm, lower 2 V/cm. 5 μs/cm.



(b) 2 V/cm. 5 μs/cm.

is seen to be linear and the bottom of the collector waveform of Tr1 is flat. The steps in the emitter waveforms occurring at the start of the timing period are smaller than those in Figs. 28 and 29. This fact arises from the small forward biasing of Tr1 by the trigger sensitivity control.

An expression for the pulse width may be readily obtained if it is assumed that transistor Tr3 takes a constant current I_c . The run down in Tr2 emitter voltage starts at a value $V_c' - V_{be2} - \delta V_{e2}$. $V_c' = V_{cc}R_6/(R_1 - R_5)$ is the voltage at the base of Tr2 in the permanently stable state, V_{be2} is the base emitter voltage of Tr2 in this state δV_{e2} is the step occurring in the emitter voltage of Tr2 as it switches off. The run down ends when Tr2 emitter voltage reaches a value $V_c' - I_cR' - V_{be'}$, $R' = R_1R_5/(R_1 + R_5)$, is the effective collector load resistance of Tr1 and $V_{be'}$ is the base emitter voltage of Tr2 when regenerative switching occurs. Capacitor C thus charges through a voltage, $\Delta V = I_cR' - [\delta V_{e2} + (V_{be2} - V_{be'})]$.

The pulse width,

$$t_p = (\Delta VC)/I_c = CR' - C/I_c [\delta V_{e2} + V_{be2} - (V_{be'})]$$

If the bracketed terms, which are small, are neglected $t_p = CR'$. Note that the power supply voltage does not occur in this expression for pulse width. In the case of the circuit shown in Fig. 16 a change in supply voltage from 15 to 30 V was found to produce only a 2% increase in pulse width.

A further modification to the basic circuit can be made in order to eliminate the overshoot in the pulse at the collector of Tr2. An example of a practical circuit in which this modification is incorporated, is shown in Fig. 18. The waveforms produced by the circuit are shown in Figs. 19 (a), (b) and (c).

SAWTOOTH GENERATOR

In the circuit of Fig. 16 the run down in the emitter voltage of transistor Tr2 is linear enabling the circuit to be used as the basis of a linear sawtooth generator. The collector load resistor of transistor Tr2 is not required and with it omitted from the circuit, the resistor R_5 is no longer needed to prevent Tr2 from saturating. A circuit for the saw tooth generator is shown in Fig. 20.



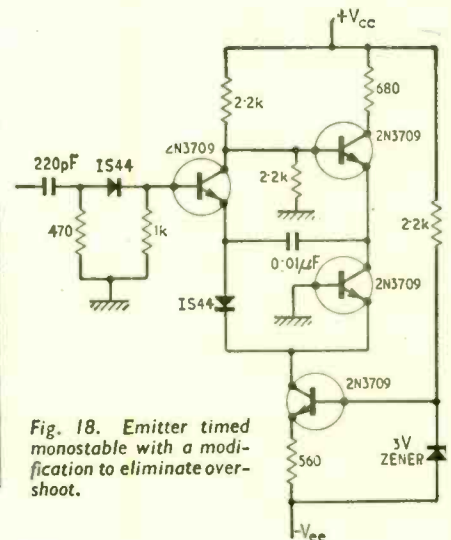



Fig. 18. Emitter timed monostable with a modification to eliminate overshoot.

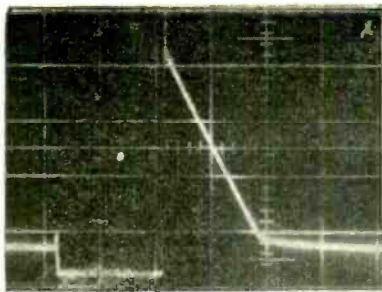

(a) 1 V/cm. 5 μs/cm.

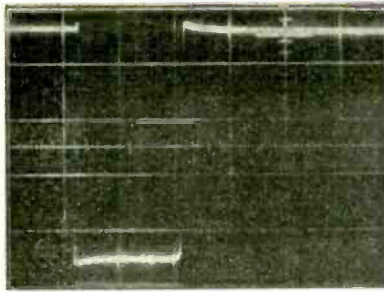

(b) 1 V/cm. 5 μs/cm.

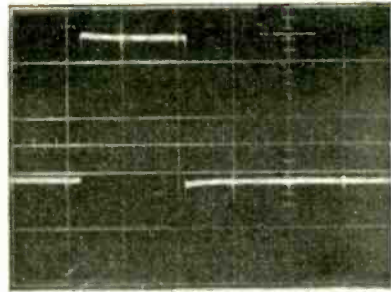

(c) 1 V/cm. 5 μs/cm.

Fig. 19. Waveforms encountered in the circuit of Fig. 18 (a) emitter Tr1 (b) collector Tr1 and (c) collector Tr2.

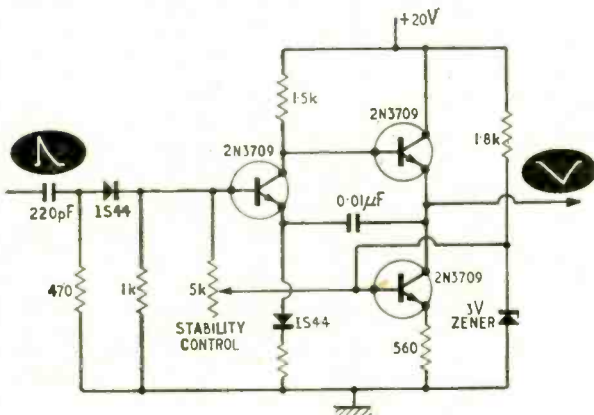


Fig. 20. A linear sawtooth generator circuit.

The measurements made on the practical circuits described would appear to confirm that emitter timed multivibrators possess the desirable features outlined in the introduction. Facilities were not available to test the stability of pulse widths against changes in temperature. The analyses given show that temperature changes may be expected to affect the timing periods because of the V_{be} terms that appear in the equations. These terms change by a few millivolts per °C change in temperature but the analysis shows that they only have a small effect on the timing periods. The astable circuits are useful as stable frequency pulse sources and the monostable circuits are suitable for use as high speed pulse generators.² The circuits are not really suitable when long timing periods are required as the timing capacitor would need to be excessively large. Base timed circuits are more suitable for low frequencies and long timing periods.

APPENDIX

Derivation of an expression for the pulse width produced by the circuit of Fig. 13. During the quasi-stable period the charging current into C starts at a value $I_i = (V_c' - V_{be2} - \delta V_{e2})/R_4$ and decays exponentially to a value $I_f = (V_c' - I_c R' - V_{be}')/R_4$ in a time t_p .

$V_c' = V_{cc} R_5 / (R_1 + R_5)$ is the potential at the base of Tr2 in the permanently stable state. V_{be2} is the base emitter voltage of Tr2 in this state. V_{be}' is the base emitter voltage of Tr2 when switching occurs. δV_{e2} is the step in the emitter voltage of Tr2 and $R' = R_1 R_5 / (R_1 + R_5)$ is the effective collector load resistor of Tr1. It is assumed that $\alpha_{cb1} + \alpha_{cb2}$.

Now $I_f = I_i \exp(-t_p) / CR_4$ so that $t_p = CR_4 \log_e I_i / I_f$.

Substitution for I_i and I_f gives:

$$t_p = CR_4 \log_e \frac{V_c' - V_{be2} - \delta V_{e2}}{V_c' - V_{be}'} \frac{R_4 + R'}{R_4}$$

If V_c' is considerably larger than the other voltage terms we may write an approximate expression for the pulse width.

$$t_p = CR_4 \log_e \frac{R_4 + R'}{R_4}$$

Expanding the log term gives:

$$t_p = CR_4 \left[\frac{R'}{R_4} - \frac{1}{2} \left(\frac{R'}{R_4} \right)^2 + \frac{1}{3} \left(\frac{R'}{R_4} \right)^3 \dots \right]$$

$$t_p = CR' \left[1 - \frac{1}{2} \left(\frac{R'}{R_4} \right) + \frac{1}{3} \left(\frac{R'}{R_4} \right)^2 \dots \right]$$

provided that $R_4 > R'$. If $R_4 \gg R'$ then $t_p \approx CR'$.

Correction: Amend caption of Fig. 2 to read "below" and caption of Fig. 3 to read "above" (not right and left). The lower end of R_1 (Fig. 6) should be connected to the base of Tr2.

Do you want a job in electronics that is something out of the ordinary? Would you like to be in daily contact with, and extending your knowledge of, the whole field of electronics and communications? Do you want to travel and meet people? Would you like the opportunity to develop your own interests, theoretical or practical, in this field? Do you enjoy doing something creative and working on your own initiative?

If so, and you have a flair for writing, you may not realize it but you are a potential technical journalist. So why not consider joining the editorial staff of **Wireless World**

(see advertisement on p.114)

The Simple Transistor Equivalent Circuit and the Impedance Transforming Node

By R. V. LEEDHAM,* B.Sc.Tech., M.Sc., C.Eng.

THE idea that a transistor may be used in a similar way to a transformer for the conversion of impedance levels in problems of matching loads to generators, and devices to one another, is familiar to circuit designers. This property of impedance transformation is due to a particular arrangement of one of the nodes in the T equivalent circuit of the transistor, and it will be shown how the effect occurs, and how the simple T circuit may be used for approximate circuit analysis by inspection, without the tedious algebra of an exact analysis.

The simple T equivalent circuit for the transistor is shown in Fig. 1. The element r_e has been omitted from the exact circuit, removing the internal feedback, and leaving the transforming node b' in its pure form. The

essential elements of the node are shown in Fig. 2 together with an impedance z which includes the emitter resistance r_e . The important property of this node is that one node current is a linear function of one of the other node currents. In this case, α_e is directly proportional to i_e . In order to determine the apparent impedance between the terminals shown, assume an input step δv ,

$$\text{then } \delta i = \delta i_e - \alpha \delta i_e = \delta i_e(1 - \alpha) = \frac{\delta i_e}{\alpha_{eb}}$$

where α_{eb} is the current gain between base and emitter, and is related to the current gain between base and collector by

$$\alpha_{eb} = \alpha_{cb} + 1$$

The test potential step may be equated to the circuit parameters

$$\delta v = \delta i_e z = \alpha_{eb} \delta i_e z$$

and the apparent impedance is given by

$$\frac{\delta v}{\delta i} = \alpha_{eb} z$$

i.e. the impedance z appears to be increased by the factor α_{eb} when seen from the base connection. This impedance transformation works both ways, and Fig. 3 illustrates the effect of an impedance z in the base lead (including $r_{bb'}$). In this case when we apply the test signal δv the current drawn from the generator is δi_e . The current through z however is

$$\delta i_e(1 - \alpha) = \frac{\delta i_e}{\alpha_{eb}}$$

and hence the potential difference produced across z is

$$\delta v = z \times \frac{\delta i_e}{\alpha_{eb}}$$

and the apparent impedance is

$$\frac{\delta v}{\delta i} = \frac{z}{\alpha_{eb}}$$

In this case the impedance z has been reduced by the factor α_{eb} . This impedance transformation effect is entirely due to the fact that two of the node currents are related by a constant factor. The effect is similar to that of the ideal transformer shown in Fig. 4, of ratio $1:n$. The relationships in this case are well known to be

$$\frac{v_2}{v_1} = \frac{n}{1} \quad \frac{i_2}{i_1} = \frac{1}{n}$$


and the apparent impedance

$$\frac{v_1}{i_1} = \frac{v_2}{i_2} \cdot \frac{1}{n} = \frac{z}{n^2}$$

a transformation ratio of n^2 .

The transformer is a more versatile component than

* University of Bradford.

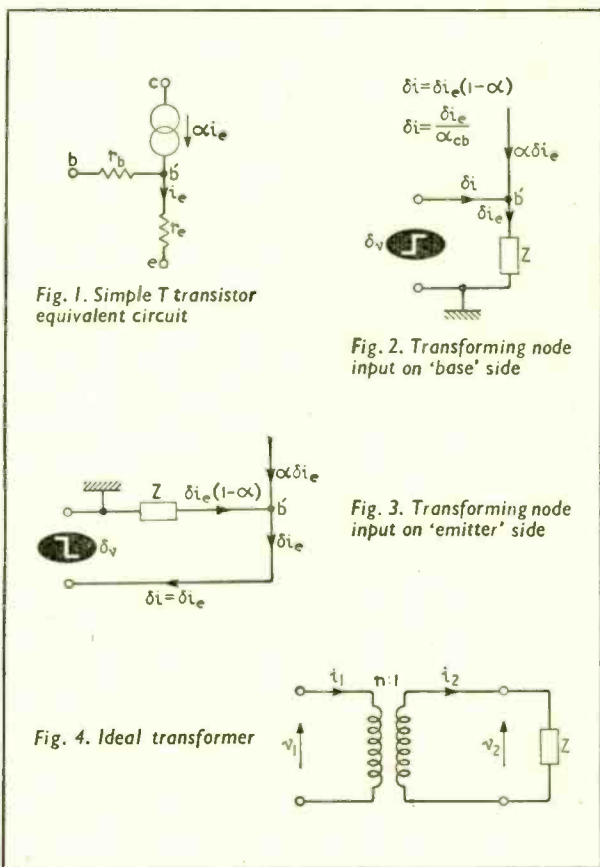

the transforming node, since both the current and voltage are transformed in the ratio n , whereas in the case of the node the current only is transformed. Using the idea of the transforming node, the input impedance and gain of a transistor circuit may be written by inspection. The method gives no indication of the output impedance of the transistor, but this is not very serious, since the output impedance is high, normally, compared with the load which shunts it. Examples of the method are given below.

COMMON COLLECTOR

The basic circuit is shown in Fig. 5. It may be seen that the input impedance is given by the sum of $r_{bb'}$ and the effect of the transforming node on r_e and R_L .

$$R_{in} = r_{bb'} + \alpha_{eb}(r_e + R_L)$$

Fig. 6 shows the circuit for the calculation of output impedance. The impedance is seen to be

$$R_{out} = r_e + \frac{(r_{bb'} + R_s)}{\alpha_{eb}}$$

The voltage gain is seen to be that of an attenuator, from Fig. 5, of

$$\text{gain} = \frac{\alpha_{eb} R_L}{r_{bb'} + \alpha_{eb}(r_e + R_L)}$$

COMMON EMITTER

The circuit is shown in Fig. 7 and the circuit parameters of interest may be written down as

$$R_{in} = r_{bb'} + \alpha_{eb}(r_e + z_e)$$

The gain is obtained as follows.

Consider the attenuator giving the potential at b' . The attenuation factor is

$$\frac{\alpha_{eb}(r_e + z_e)}{r_{bb'} + \alpha_{eb}(r_e + z_e)}$$

the current i_e is given by the attenuated signal at b' divided by the impedance $r_e + z_e$, and the output signal is αi_e .

$$\begin{aligned} \text{gain} &= \frac{\alpha_{eb}(r_e + z_e)}{r_{bb'} + \alpha_{eb}(r_e + z_e)} \cdot \frac{1}{(r_e + z_e)} \cdot \alpha R_L \\ &= \frac{\alpha_{cb} R_L}{r_{bb'} + \alpha_{eb}(r_e + z_e)} \end{aligned}$$

COMMON BASE

The circuit is shown in Fig. 8. The circuit parameters of interest are

$$R_{in} = r_e + \frac{r_{bb'}}{\alpha_{eb}}$$

and, by inspection, the voltage gain is

$$\text{gain} = \frac{\alpha R_L}{r_e + \frac{r_{bb'}}{\alpha_{eb}}}$$

In some cases it is possible to include the effect of the component r_{cs} , but the effect is often complex due to 'Miller effect' and other feedback aspects. The method is presented as a quick first approximation analysis to facilitate design synthesis, to be followed by exact analysis when the design is completed.

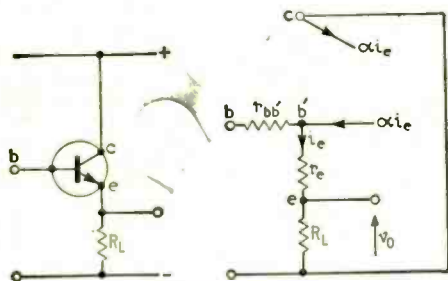


Fig. 5. Common collector

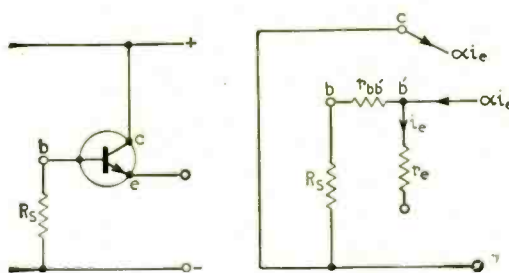


Fig. 6. Calculation of output impedance

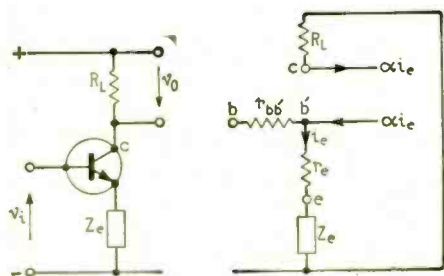


Fig. 7. Common emitter

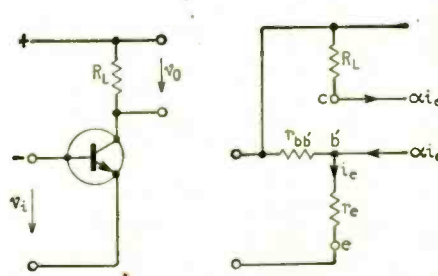


Fig. 8. Common base

WORLD OF AMATEUR RADIO

Antique Wireless Association

MRS. MARION ARMSTRONG, widow of Edwin H. Armstrong, the f.m. pioneer, was guest of honour at the fifth annual convention of the Antique Wireless Association held recently in the Henry Ford Museum, Dearborn, Michigan, U.S.A. Among the historical radio items on display in the Museum are the original rotary gap and condenser used at station NAA (Arlington, Va), the McMurdo-Silver historical collection of valves, early de Forest equipment (including a Syn-tonizer and a 1907 U.S. Navy "singing arc" radiophone), as well as much early amateur equipment. During the convention Mr. Henry Houck (Major Armstrong's assistant) demonstrated one of the first superheterodyne receivers developed by Major Armstrong. The receiver was later donated to the Museum by Mrs. Armstrong. The call sign of the Antique Wireless Association, an amateur radio organization interested in the history of early wireless, is W2AN. The Association maintains a museum of historical equipment at Holcolomb, New York, the earliest example on display being a replica of the spark transmitter and coherer used by Marconi in his initial tests. Secretary of the A.W.A. is Mr. Bruce Kelley (W2ICE ex-8ACY) of Main Street, Holcolomb, N.Y., who also edits *The Old Timers' Bulletin*, published quarterly. Is it not time a similar organization was established in the United Kingdom to document the history of wireless and the work of its pioneers?

Eye Bank Network.—Dr. Alson E. Braley (W0GET), Professor of Ophthalmology of the University of Iowa, received the first annual Achievement Award of the Medical Amateur Radio Council for founding the Eye Bank Network in December 1962. The purpose of the network, operated by radio amateurs, is to provide rapid, inexpensive and efficient communication once a day, to make known to participating eye banks throughout the United States of America any emergency requirements for eye tissue and where such tissue is available. The sight of scores of patients has been saved since the network was founded.

Australian Intruder Watch.—Nearly 20 years ago the R.S.G.B. set up an organization to report on the presence in "exclusive" amateur bands of broadcast and commercial stations. Known as an Intruder Watch the organization continues to submit regular reports to the G.P.O., who take action, when appropriate, to have the offending stations removed. Since that time Intruder Watch organizations have been established by national amateur radio societies in a number of countries including the U.S.A. Latest addition to the list is the Wireless Institute of Australia.

Belgium-Netherlands Amateur TV Contact.—Thanks to having been granted a temporary (three-day) licence by the Belgium authorities, Gaspard de Wilde (ON4ZK) in Dessel (Province of Antwerp) was able to achieve the first two-way amateur television contact on 70 cm between his country and the Netherlands when he worked A.H.M. Lambriex (PA0LAM) in Reethoven, on October 27th, at 19.30 G.M.T., over a distance of 24 km. M. de Wilde has also received amateur television from PA0COB (The Hague) and from G3NOX (Saffron Walden, Essex).

Reports on Two-metre German Beacon.—First U.K. reception reports of signals from the German beacon station DL0PR at the Lindau Ionospheric Observatory operating on 145.97 MHz, have reached the R.S.G.B. from R. A. Ham, of Storrington, Sussex. Signals were first heard on November 21st, at readability 5 and signal strength varying from 2 to 5 from 08.30 to 09.30 G.M.T. Further reports will be welcomed by the Society's Scientific Studies Committee, 28 Little Russell Street, London, W.C.1.

International DX Competition.—Amateurs throughout the world are invited to participate in the 34th A.R.R.L. International DX Competition for which special certificates of performance will be issued to the top telephony and telegraphy scorers in each country. In addition, plaques will be awarded to continental high scorers—single-operator, telephony and telegraphy. The competition will take place during the weekends February 3/4 and March 2/3 (telephony) and February 17/18 and March 16/17 (telegraphy). The object of the contest is for stations outside the U.S. and Canada to work as many of the 48 United States and Canadian call areas as possible. Further details and log forms can be obtained from A.R.R.L., 225 Main Street, Newington, Conn., 06111, U.S.A.

A.R.R.L. 1967 DX Contest.—The leading U.K. station in the 1967 A.R.R.L. Telegraphy Contest was D. Gibson (G13OQR), Co. Tyrone, N. Ireland, with a score of 1,886,304 points obtained from 2,807 transatlantic contacts made during an operating time of 70 hours. Leading English station was that of C. R. Perks (G4CP), Walsall, Staffs, whose score of 1,446,552 was obtained from 2,199 contacts in a 40-hour operating period. In the Telephony Section the leading U.K. entrant was L. F. Coursey (G4JZ), Birdlip, Glos, who had a score of 1,171,596, obtained from 2,194 contacts in an operating period of 53 hours.

Top European Memberships.—The German amateur radio society (D.A.R.C.) recently reported a total membership in excess of 18,000, of whom more than half hold a transmitting licence. As at June 30th, 1967, the total membership of the Radio Society of Great Britain stood at 13,400 (an increase of 115 since the same date in 1966) of whom 7,945 (including a large number of overseas members) held a transmitting licence. At the same date there were 12,308 Class A Sound Licences in force in the U.K. The rapid growth of the amateur radio movement in the Federal German Republic can be attributed, in full measure, to the efforts made by D.A.R.C. to cater for "Der Jungamateurl," a section of each issue of *DL-QTC*—the society's journal—being devoted especially to their interests.

R.S.G.B. President.—John C. Graham (G3TR), of Crawley, Sussex, was installed as the 34th president of the Radio Society of Great Britain at a recent informal meeting of members at the Kingsley Hotel, London, W.C.1. Mr. Graham has been a member of the Society for more than 30 years. Professionally he is senior air traffic controller at Gatwick Airport.

OSCAR News Bulletins about satellites designed to carry amateur radio equipment into orbit are transmitted by W6ASH on Fridays at 02.00 G.M.T. on 14.03 MHz and at 05.00 G.M.T. on 7.015 MHz. The European OSCAR constructed by the German amateur Karl Meinzer (DJ4ZC) and the Australian OSCAR, constructed by a team of radio amateurs associated with Melbourne University, are both in the U.S.A. waiting to be launched.

Change of Name.—The title of the *R.S.G.B. Bulletin*, known throughout the world of amateur radio as "The Bull," has been changed to *Radio Communication*. The official journal of the Radio Society of Great Britain first appeared in July 1925 as the *T & R Bulletin*. It remained the title until July 1942, although the Transmitter & Relay Section of the Society ceased in December 1926. The T & R Section came into being during September 1923 to safeguard the interests of the transmitting amateurs, many of whom considered too much attention was being given by the Society to broadcasting matters and to the interests of broadcast listeners; broadcasting having commenced in the United Kingdom in November 1922. JOHN CLARRICOATS, G6CL

Pin-board Construction

A simple, beginners' circuit-building technique employing a circuit diagram as a guide to layout By G. W. SHORT*

IT is very difficult for the beginner or young constructor to perform the mental contortions necessary to turn a theoretical circuit into a practical layout, and even if he manages this feat, or has it done for him, useful working concepts, such as the idea of signals flowing from left to right, or the positive line always being at the top, are destroyed, unless one uses an inordinate quantity of terminal blocks.

The practical difficulties are manifold. First, screw-down terminal blocks are not very reliable as a means of making connections, at least not in the hands of a young constructor. The actual connection is hidden away inside the block, and so cannot be inspected. Dimensions of the blocks impose limitations on the components which can be used with them. Epoxy-encapsulated transistors with half-inch leads have to be mauled in order to make them span three adjacent terminals. Short-lead second-hand resistors and capacitors are likewise awkward, and the assembled circuit often looks clumsy. Certain educational circuit-construction techniques were considered, but were rejected because of their high cost. However, from these, and demonstration circuits seen at exhibitions, the simple constructional technique discussed here was developed. The main problem was the method of making joints. If the ends of leads can first be wrapped round a fixed, rigid post even an eleven-year-old can then solder them. Suitable posts can be provided by hammering ordinary domestic electro-plated pins (which solder well) into a piece of wood and then cutting off their heads with wire snippers, leaving about a quarter of an inch of stem showing.

Suitable materials for the baseboard are hardboard, soft wood, and the "sandwich board" which has an inner core of softwood and outer skins of veneer, even plywood can be used if not too hard. Whatever is used, it must be dry. If thin materials such as hardboard are used, the points of the pins come through, and should be filed off to avoid scratching surfaces on which they are laid.

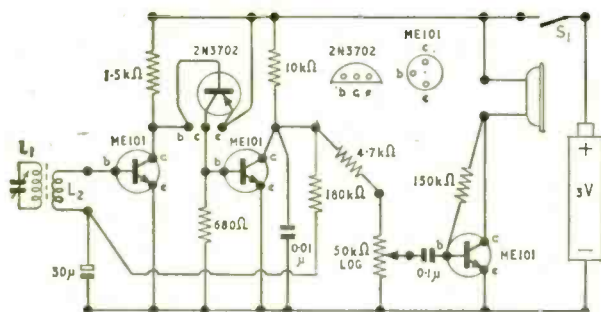


Fig. 1. The circuit diagram is drawn in the usual way, except that the transistor electrode connections are positioned so as to correspond with the transistor header. In this circuit the only transistor which requires special treatment is the 2N3702, which has its leads in a straight line with the collector in the middle.

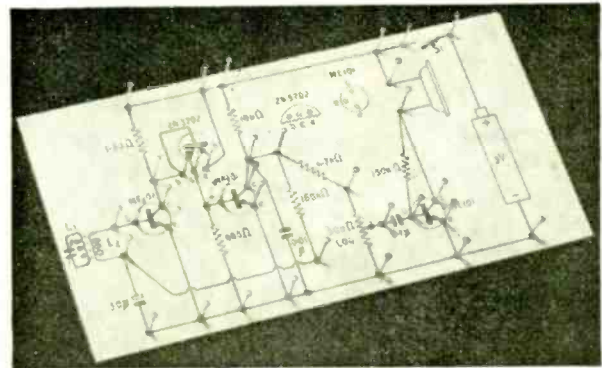


Fig. 2. Ordinary household pins are hammered in at every connecting point.

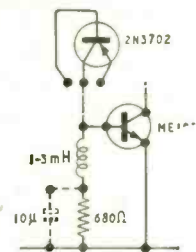


Fig. 3. Adding a choke increases r.f. gain. By-passing the 680-ohm resistor to a.f. reduces noise.

The layout problem is solved by working directly from a circuit diagram, drawn out large, so that the actual components can be laid over their symbols on the paper. Transistors are drawn both symbolically and physically, so that the connections are quite clear (Fig. 1). This circuit diagram is placed on the baseboard, and pins are knocked in at every junction point (Fig. 2). The lines and symbols then form a direct guide for wiring-up. Errors will be at a minimum, and are easily checked by inspection, and soldered joints can be inspected. Straight connections which do not cross other wires are first put in using bare wire, and soldered. Crossing-over wires are next put in, with insulated wire. The passive components come next, and finally the transistors. Variable capacitors, volume controls, and earphones are at first connected by long leads, then, when the equipment is working, they can be accommodated on a front panel.

Pinboard construction is very simple and adaptable. If for example, the leads of a resistor prove to be too short to span the gap between a pair of pins, it is a simple matter to drive in an extra pin and complete the connection with ordinary wire. Modifications are easily made, because the layout is necessarily open and accessible. Testing is likewise easy. Apart from its cheapness and simplicity, this method has the great advantage that the beginner is not tied to very elementary circuits. There is no reason, for example, why his first radio receiver should not be something more than a mere toy.

The accompanying diagrams show how the basic radio receiver of the pin-board (Fig. 1) can be gradually im-

*Amatronix Ltd.

proved. Adding a choke (Fig. 3) increases the r.f. gain substantially. It then becomes apparent that the signal-to-noise ratio is poor (because the wide-band r.f. amplifier generates a.f. noise). Adding an a.f. bypass capacitor across the resistive part of the load of 2N3702 takes care of this, but if its capacitance is too large, l.f. relaxation oscillations may occur, because of the phase shifts round the d.c. feedback path over the first three stages. The easiest way to add reaction (improving selectivity) is to connect a wire to the live side of the aerial tuned circuit, and place the other end somewhere near the collector load (680Ω) of the second transistor 2N3702 (Fig. 1). The audio output can be progressively increased by means of the amplifier circuits of Figs. 4 and 5.

Although the pin-board method was devised for the

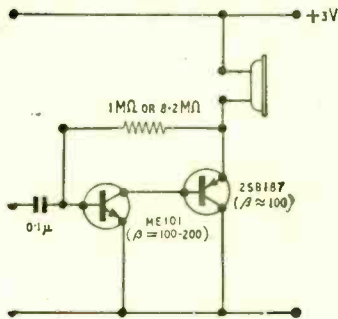


Fig. 4. Simple two-stage class A amplifier. The current drain is 8-35 mA, depending on the speaker impedance. A power output of about 10 mW is delivered to a load of 20-40Ω and loads up to 200Ω may be used without change of component values. For higher loads, or headphones, the bias resistor is 8.2 MΩ, and the current taken is 1.5 mA.


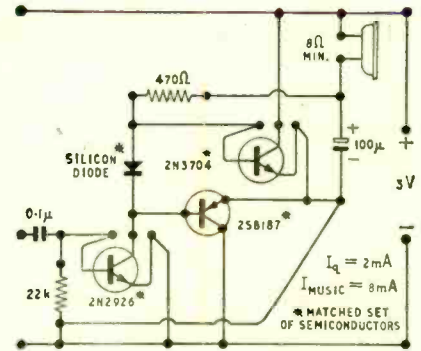
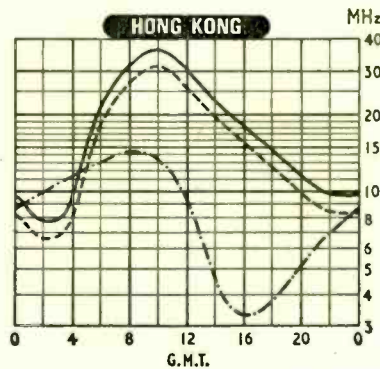
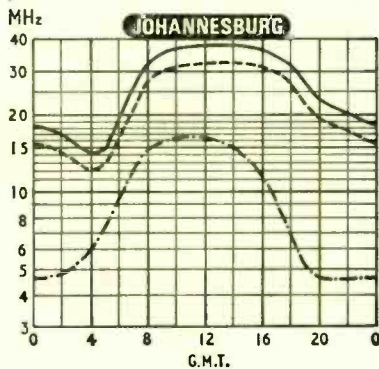
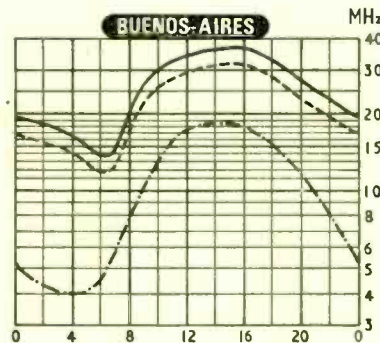


Fig. 5. Complementary a.f. amplifier. With sine-wave drive this delivers 60 mW to an 8Ω load. Speakers of any higher impedance may be connected.

beginner, it is also useful for experimental circuits, since it is very quick, and the chances of making a wiring error are small. Quite compact layouts are possible, and a number of circuit "cards" can be stacked in a complete equipment. The usual type of pin, known as a "standard short white," is one inch long, strong and easy to handle. The cut ends are rather sharp, however, and if this is considered a serious hazard it is better to use shorter pins and leave the heads on. The type known as "lills," which are half an inch long, are suitable.

H. F. PREDICTIONS — FEBRUARY

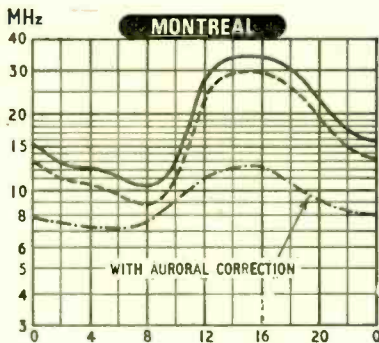

—	MEDIAN STANDARD MUF
- - -	OPTIMUM TRAFFIC FREQUENCY
· · ·	LOWEST USABLE HF

Daytime maximum usable frequencies continue to peak around 35 MHz. Duration and timing of these peaks depends on relative longitudes of the stations; high MUFs occurring when both ends of a path are in daylight. On the South African route conditions on frequencies between 23 and 30 MHz should be excellent. The South American route will be similar.

Hong Kong being a long-distance east-west route will be difficult due to the almost continuous change of MUF and probably be unworkable from midnight to dawn G.M.T.

The great-circle path to Montreal crosses the North Auroral zone. To allow for expected periods of high attenuation the curve for the lowest usable frequency has been amended.

LUFs shown are for reception in the U.K. of automatic telegraphy but serve as a guide for all types of service.

Ferrite Aerial Receivers

Setting up known fields in a loop aerial for receiver alignment

RECEIVERS designed for use with outdoor aerials are, of course, tested or aligned by injecting a modulated signal into the aerial terminal from a signal generator, and a suitable indicating device is used to measure the a.f. output.

However, receivers that use a built-in ferrite aerial pose two problems. How should the signal-generator voltage be injected, and how can the final sensitivity be assessed?

The first problem is usually overcome by using a little ingenuity in devising a loop of wire which, when connected to a signal-generator, can set up a field in the vicinity of the ferrite aerial. Such a field can be adjusted by varying the position of the loop with respect to the aerial rod, and alignment can be carried out quite satisfactorily using this method for injecting a test signal. But what of the final sensitivity? It is not possible to know whether the overall sensitivity of the aligned receiver is up to standard. The performance cannot be related in any way to the signal generator output setting.

Many transistor receivers that use a built-in ferrite aerial have provision for connecting an external aerial. It is a convenient way of using a portable receiver with, say, a car aerial. A signal generator test signal can be injected into the aerial socket of such a receiver, but the results will, generally, be meaningless in terms of receiver sensitivity. The coupling provided in the receiver between the ferrite tuned circuit and the aerial socket can be carried out in a number of possible ways, none of which provides a clear relationship between the signal generator output setting and the sensitivity of the receiver to a known field strength.

It is possible, however, to set up a known field by using a signal generator to drive a current round a suitable loop aerial. The resulting field in the vicinity of the loop can be determined, and the receiver aerial can be positioned in the field.

By passing a current through a loop, a magnetic field, H , is produced. This field can be related to an equivalent electric field component, E , by the relationship $E = ZH$, where Z is the impedance of free space ($Z = 377 \Omega$).


The magnitude of the field strength produced by a single-turn circular loop is given by

$$E = \frac{60 \pi r_1^2 I}{(d^2 + r_1^2 + r_2^2)^{3/2}} \sqrt{1 + \left(\frac{2 \pi d}{\lambda}\right)^2} \dots \dots (1) \dagger$$

where

- E = equivalent free-space field strength (V/m)
- r_1 = radius of transmitting loop (m)
- r_2 = radius of receiving loop (m)
- d = axial spacing between loops (m)
- I = transmitting loop current (A)
- λ = wavelength (m).

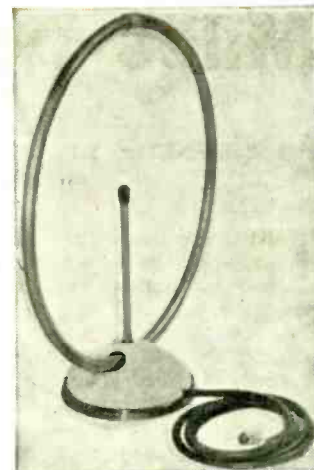The magnitude of the field is substantially independent of frequency up to about 10 MHz if the spacing, d , is kept low. Useful fields can be generated up to about 30 MHz.



The stub indicates the centre of the loop from which the receiver coil should be spaced axially 24 in.

By

R. S. ROBERTS*
M.I.E.R.E.

Examination of equation (1) suggests that a few simplifications and expedients can be adopted to assist in turning it into practical form:—

- (a) Making the transmitting loop 10 in (0.254 m) dia.
- (b) Determining d as 24 in (0.6 m).
- (c) Ignoring r_2 . The radius of most receiver aerial coils using ferrite rod cores is, generally, about 0.5 cm.
- (d) Ignoring the last part of the equation, under the root sign.

Re-writing equation (1) in these terms gives

$$E \approx 13.12 I \dots \dots (2)$$

Using a three-turn loop, equation (2) becomes

$$E \approx 39.36 I \dots \dots (3)$$

If this loop is driven from a signal generator, the current I is conveniently determined by placing in series with the loop a resistance which is large in value compared with the loop reactance. This resistance value is particularly useful if it is about 390 ohms. If the loop is then driven by, say, 1 V from a low-impedance generator, the current through the loop is then $\approx 1/390$ A and, from equation (3), the field E is 0.1 V/m. In other words, the generated field strength in V/m will be -20 dB on the signal-generator output voltage setting.

The loop requires screening in order to minimize "vertical effect" and is, preferably, driven from a balanced source. The device is easily constructed, and the photograph shows one version. The three turns of insulated wire are threaded into a loop which is made from 3/8 in diameter aluminium tube. The loop is split at the top by means of an insulating sleeve, and is secured in a suitable base that houses the 390- Ω series resistor and the end of the feeder cable.

The model shown is unbalanced, and the feed cable is a length of 75- Ω coaxial. The cable length is not very significant when the device is used in the m.f. and l.f. bands but, if it is to be used up to 30 MHz, the length should not be an appreciable fraction of a wavelength. Although the device is not a precision instrument the fields generated on the long- and medium-wave broadcast bands are surprisingly accurate, with increasing errors up to 30 MHz, where the error is about 2 dB.

The author thanks the directors of Antiference Ltd. for permission to publish this article.

† National Bureau of Standards Circular 517, December 1951.

* Northern Polytechnic, London.

Miles-per-Gallon Meter

An electronic motoring aid

By D. J. GROVER, B.Sc.

THE meter described here indicates continuously miles per gallon when installed in a car; it makes use of facilities already available to obtain the necessary information, namely, distance and fuel flow. The rate of petrol flow is measured by using pulses obtained from an electric petrol pump. Unfortunately the quantity obtained at each stroke varies with the rate of pumping due to inertia of the liquid, distortion of the diaphragm and valve leakage. However, over the practical operating range this variation is nearly linear with speed and may easily be compensated for electronically. A measure of distance is obtained from the odometer which contains a mechanism which reciprocates at the rate of one cycle per 32.5 yds. It is a simple matter to mount an insulated contact which is shorted for approximately half the cycle of this lever. It would have been preferable to have a contact which was shorted to ground for a very small time compared with the cycle time, but this was difficult to achieve in practice so as near a 50:50 ratio as possible was chosen.

The circuit generates a voltage which is proportional to the number of strokes of the petrol pump over the distance indicated by the odometer contactor. This voltage is stored and fed to a meter while the calculation for the next distance period is being carried out. The "working" stroke of the petrol pump generates a positive going 12 V pulse which is fed to a diode-transistor pump formed by C_1 , C_2 , Tr1, D2 via capacitor C_1 (Fig. 1). Capacitor C_2 therefore assumes a potential proportional to the number of pulses entering C_1 until it is reset to zero by switch P. Tr2 is an emitter-follower whose function is to buffer C_2 from the storage capacitors C_3 and C_4 . Assume that Q is in the position shown and that X is open and Y closed. The meter, M, will now be deflected if there is any charge in capacitor C_4 . C_3 will follow the potential on C_2 until a reset pulse is imminent. When this pulse arrives Q changes over and P momentarily shorts C_2 to earth. Y opens and X closes so that the voltage stored in C_3 now feeds the meter. C_2 again assumes a voltage proportional to the number of strokes of the petrol pump and Tr2 charges C_4 until a reset pulse is again imminent. When this occurs the

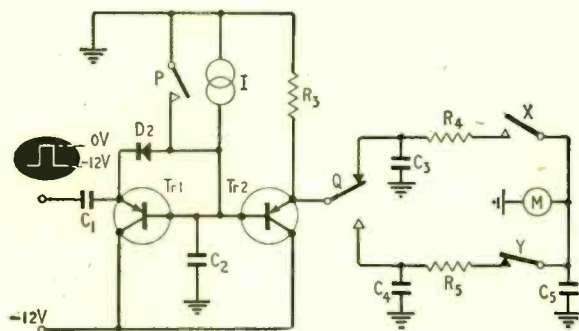


Fig. 1 Illustrating the computing method employed.

D. J. Grover graduated in physics and mathematics at University College, London, in 1953. After several years of circuit development work in this country he spent three years in the U.S.A. Returning to the U.K. in 1963 Mr. Grover joined Marconi Instruments and later went to Cossor Electronics as a senior systems engineer.

process repeats itself. It is evident that the meter deflection will be proportional to the number of strokes of the petrol pump between operations of the reset switch P. The current generator I compensates for leakage etc., in the petrol pump and capacitor C_5 smooths the drive to the meter.

Contact K of the petrol pump (Fig. 2) assumes earth potential during each activation stroke. A connection is easily made to this to provide the required 12 volt pulse. The quantity of petrol per stroke varies with the rate of pumping as shown in Fig. 3. At low pumping rates pump efficiency is poor due to leakage past the inlet valve. At higher rates of pumping the efficiency is increased due to the inertia of the liquid and the pump armature. The characteristic over the range of interest, between 0.4 sec./stroke and 4 sec./stroke, is sufficiently linear for a simple correction to be applied electronically. It is shown in the appendix that the characteristic of Fig. 4 is equivalent to a discharge of 3.23% per sec.

A four pole four way relay is controlled by the contact in the odometer so that it is energized and de-energized every 32.5 yds, with a ratio of approximately 50:50. The spacing of the contacts A-H is indicated diagrammatically in Fig. 4. The moving contacts B & C are connected together and adjusted to give a make before break action between A & D. A & D are therefore shorted momentarily each time the relay operates. F & G are connected together and adjusted to give a break before make changeover between E & H. The contacts were further adjusted so that the break of FG occurred before the make of BC in both directions. The effect is to short D momentarily to earth while FG is travelling between E & H.

CIRCUIT DESCRIPTION

The circuit diagram is shown in Fig. 2. The 12 V pulses from the petrol pump enter via diode D1, this eliminates the negative spike occurring when the pump coil is open-circuited. R_1 discharges C_1 to -12 V after each pulse. C_1 , C_2 , Tr1, D2 form the diode-transistor pump, a silicon diode D3 providing some compensation for the emitter-base voltage drops of Tr2 and Tr3 or Tr4. The current generator for compensating for petrol pump leakage is provided by R_2 . The switch J is the contact in the odometer; imagine that this contact is open (relay not energized) the contacts FG are switched on to E, and BC to A. C_3 assumes the voltage applied

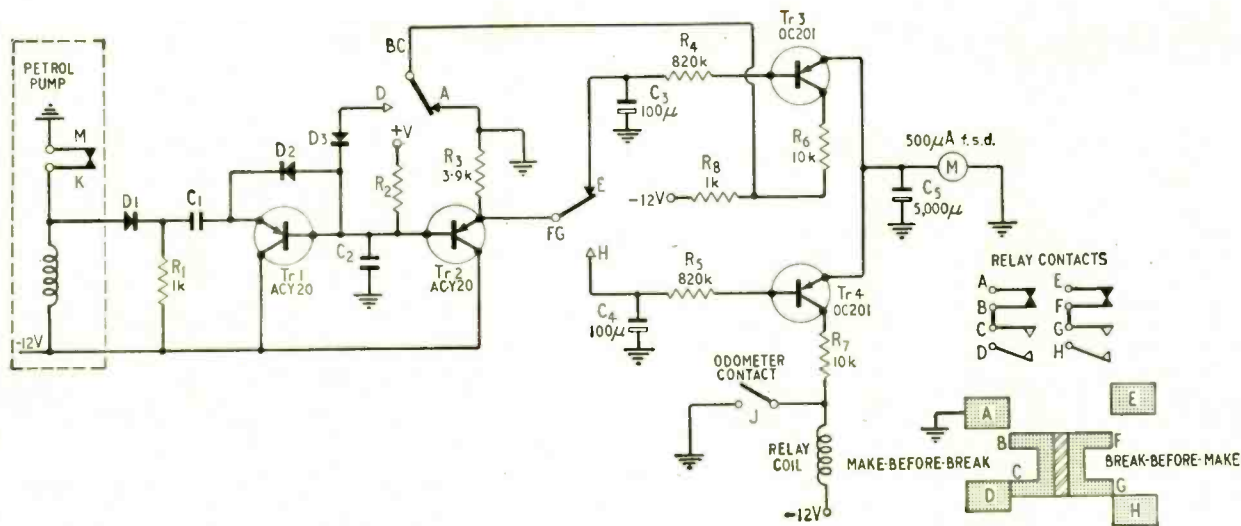


Fig. 2. Circuit diagram and the method of adjusting the relay contacts.

to C_2 via the emitter follower Tr2. The function of switch X (Fig. 1) is performed by grounding the collector of Tr3 via R_4 ; since BC is shorted to A which is at ground. Silicon transistors are used for Tr3 and Tr4 and since their emitters are limited to the order of 100 mV by the meter, the grounding of the collectors prohibits transistor action even in the inverted mode. The potential on C_4 feeds current to the base of Tr4 which amplifies it to drive the meter.

The closing switch J energizes the relay and BC switches to D and FG to H. D is grounded during this transition and discharges C_2 via D3 to ground. BC approaches -12 volts enabling Tr3 to amplify the current from C_3 and D3 is reverse biased. C_4 now assumes the charge across C_2 and Tr4 is immobilized by grounding its collector via R_7 to switch J. It is necessary that resistors R_4 and R_5 be sufficiently large to prevent appreciable discharge of C_3 and C_4 when feeding the meter. Tr3 and Tr4 must be matched, any slight variations in gain being compensated for by adjusting the value of R_4 and R_5 . The resistors R_6 and R_7 protect the meter in the event of one of the transistors going short circuit and also safeguard Tr4 from the inductive voltage spike generated by the collapsing field across the relay coil when J opens.

CALIBRATION

It is shown in the Appendix that the ratio of close/open periods of the relay has a secondary effect provided the periods are nearly equal. The ratio may be checked in a number of ways. A lamp or counter, switched by a relay contact, forming a suitable indicator, the number of counts being recorded over a known distance. Fig. 4 shows an alternative method for measuring the open/close distance ratio; it can also be used for measuring the relay shorting period. The capacitor C is alternatively charged and discharged between earth and -12 volts. Provided the time constant associated with R_2 and the meter resistance is sufficiently large, compared with the relay period, then the voltage across capacitor C remains essentially constant at V. Then:

$$\frac{T_{12}}{T_0} = \frac{V}{12 - V} \quad \left(\begin{array}{l} T_{12} \text{ is time A is at } 12 \text{ V} \\ T_0 \text{ is time A is at } 0 \text{ V} \end{array} \right)$$

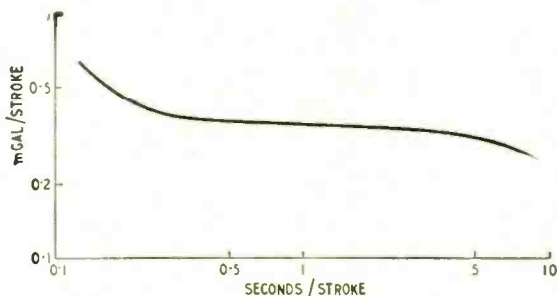


Fig. 3. The characteristic of the petrol pump in the writer's car.

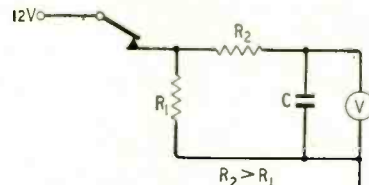


Fig. 4. The circuit employed for period ratio measurement.

The close/open distances in the author's case were 11.5 millimetres and 7.3 mm giving a ratio of 1.55:1.

The meter is calibrated by simulating normal operating conditions. The pulses from the pump are simulated by grounding the input diode D1 with a switch or bell-push (S1). The car is moved until contact J is open and a second switch (S2) wired in parallel. The quantity of petrol corresponding to a pulse at D1 is known and the average distance travelled, for J to be switched, is also known. Hence by switching S1 n times for every throw of S2 (at a rate which is within the normal operating range) until the meter reading is steady, the deflection for a known rate of consumption is obtained. The deflection for an integral number of m.p.g. is readily interpolated if a scale is retained on the meter for this purpose.

As explained in the appendix a correction is necessary if the relay does not operate on a 50:50 duty ratio. For the ratio quoted (1.55:1) the meter drive will be 5% higher when caused by the manual means described than when created by normal operating conditions.

The variation of battery voltage between charging and discharging is sufficient to give an unacceptable error. Accordingly the power supply to the circuit must either be stabilised with a zener diode or the calibration performed with the battery on charge.

The choice of the ratio of capacitors C_1 and C_2 is a compromise between generating a voltage step large enough to make semiconductor junction variations negligible and the probability of the voltage on C_2 approaching the supply voltage thereby saturating transistors Tr1 and Tr2. A ratio of 1:5 was chosen to give steps of approximately 2 V. Six pump strokes in a distance of 11.5 mm/s at 10 m.p.h. corresponds to 5.4 m.p.g. The heaviest consumption occurs at lowest speeds during acceleration where the decay of the capacitor voltage permits seven steps without saturation. The maximum time between resets will depend on the lowest speed at which a measurement is desired. At 10 m.p.h. the time to cover 11.5 mm/s is approximately 4 seconds. The potential on C_2 will vary by 5% of 2 V in this time if the leakage current is 2.5 μ A. Since this leakage may be compensated for in the value of R_2 (the system can be calibrated empirically) leakage can vary by this amount. The time constants $C_3 R_4$ and $C_4 R_5$ must also maintain the stored potential within acceptable limits. The decay will be less than 5% in 4 seconds if the time constant exceeds 80 seconds. The value of C_5 will depend on the conditions of use and the response time required.

R_3 must discharge C_3 or C_4 during the shortest summing time. 7 mm/s at 70 m.p.h. corresponds to 0.36 seconds. It is unlikely that consecutive sums will differ substantially, however, for a time constant of 0.39 sec., C_3 or C_4 will discharge to 40% of the initial value in 0.36 sec. The base current of Tr2 if significant, will cause a variable discharge of C_2 , however it may be used to supplement $I R_{22}$, particularly if R_3 is taken to + V.

APPENDIX

Suppose the petrol pump to have a linear characteristic extending from a stroke of period 0 seconds to the range of interest. (In practice, only that portion of the characteristic which coincides with the actual pump characteristic between 0.4 seconds and 4 seconds will be used.)

Let $Q\gamma$ be the quantity of petrol pumped per stroke of period γ , then for a linear characteristic:

$$Q\gamma = Q_0(1 - k\gamma) \quad \dots \quad (1)$$

From Fig. 4. when $\gamma = 0.4$, $Q_{0.4} = 0.356$ mgals/stroke
when $\gamma = 4.0$, $Q_4 = 0.315$ mgals/stroke

$$\text{Then: } \begin{matrix} 3.56 & 1 - 0.4k & \dots & \dots & \dots & \dots \\ 3.15 & 1 - 4.0k & \dots & \dots & \dots & \dots \end{matrix} \quad (2)$$

$$k = 0.032$$

For each stroke of the petrol pump a pulse is applied to the diode transistor pump, which raises its potential by V volts. The voltage V_n after n strokes is therefore $V_n = nv$.

The leakage of the petrol pump may be simulated, over the working range, by a current generator which discharges the storage capacitor C_3 at a constant rate. Let this rate be K_v volts per second. If C_3 is partially discharged over the period $n\gamma$, then V_n reduces to V'_n where $V'_n = nV(1 - K\gamma)$.

In order for the quantity of petrol pumped at a rate I/γ to be equivalent to the voltage of the diode pump: $V'_n = nQ\gamma$, i.e. $nQ_0(1 - k\gamma) = nv(1 - K\gamma)$ where $v \equiv Q_0$ and $K \equiv k$.

Let the minimum number of strokes that can occur in time T be n , then the number of strokes in a period T will vary between n and $(n + 1)$ depending on the random timing of the pump strokes and the reset mechanism. Let us suppose that the reset occurs just before the $(n + 1)$ th pulse, then $t = T - n\gamma$. Hence n pulses will be counted if $T - n\gamma < t < \gamma$ i.e. over a variation of t_1 of $[(n + 1)\gamma - T] = \Delta t_1$. $(n + 1)$ pulses will be counted if $0 < t < T - n\gamma$.

i.e. over a variation of t of $[T + n\gamma] = \Delta t_2$.

The probabilities will be proportional to these times since the events are random with respect to each other.

$$\text{i.e. } \frac{P(n)\Delta t_1}{P(n+1)\Delta t_2}$$

where $P(n) + P(n + 1) = 1$

$$\therefore \frac{1 - P(n)}{P(n)} = \frac{\Delta t_2}{\Delta t_1} = \frac{T - n\gamma}{(n + 1)\gamma - T}$$

$$\text{whence } P(n) = \frac{(n + 1)\gamma - T}{\gamma}$$

$$P(n + 1) = \frac{T - n\gamma}{\gamma}$$

The mean potential $\bar{V} = V_n P(n) + V_{(n+1)} P(n + 1)$

$$\therefore \bar{V} = \frac{nv[(n + 1)\gamma - T]}{\gamma} + \frac{(n + 1)v(T - n\gamma)}{\gamma} = \frac{Tv}{\gamma}$$

The mean potential, after discharge over the period T ,

$$\text{will be } V' = \frac{Tv}{\gamma} - TKv = \frac{v'T}{\gamma} \text{ where } v' = v(1 - K\gamma).$$

Suppose that alternate summing periods are of lengths T_1 and T_2 , where $T_1 \approx T_2$.

Then $Q_1 = (v'T_1)/\gamma$ and $Q_2 = (v'T_2)/\gamma$

The quantity Q over period $T_1 + T_2$ is

$$Q = Q_1 + Q_2 = \frac{v'}{\gamma}(T_1 + T_2)$$

The nature of the relay reset and storage system makes it difficult to ensure that it alternates with a 1 : 1 duty cycle. Suppose that the cycle time is T , where $T_1 + T_2 = T$ and $T_1 = \alpha T$,

so that $T_2 = (1 - \alpha)T$,

$$\text{then } V_1 = \frac{\alpha T v'}{\gamma} \text{ and } V_2 = \frac{(1 - \alpha) T v'}{\gamma}$$

The voltage V_1 accumulated over period T_1 is applied to the meter circuit for period T_2 , and the converse applies for V_2 . The charge received by the meter over the period T is therefore proportional to

$$\frac{\alpha T v'}{\gamma}(1 - \alpha) + \frac{(1 - \alpha) T v' \alpha}{\gamma}$$

$$\text{i.e. meter charge over period } T = q_T = 2\alpha(1 - \alpha)v' \frac{T}{\gamma}$$

The effect of a non 1 : 1 duty cycle for the relay is more apparent if we substitute $\epsilon = 0.5 - \alpha$ then $q_T = 2v'T(\frac{1}{4} - \epsilon^2) = v'T(0.5 - 2\epsilon^2)$.

In the system described $\alpha = 0.41$, $\therefore \epsilon^2 = 0.012$. The error which is readily compensated for reduces the meter reading by 4.8% from that obtained with a 1 : 1 duty ratio. It is apparent that α need not be measured very accurately provided it is near to 0.5.

Point-to-Point Review, 1967

By DAVID WILKINSON,* B.Sc., M.I.E.E.

DURING the year h.f. conditions continued to improve due largely to the increase in values of sunspot number and ionosphere index (IF2). The predicted value of the latter for December was 129, compared with 66 for the same month in 1966. The increase in solar activity, however, continued at a much slower rate than at the same phase of the previous sunspot cycle and there was little change in the monthly provisional number from and including September. Should the present trend continue, it would seem that the forecast of Professor Waldemeir, of Zurich, that the approaching maximum would be in the region of 100 may be fairly accurate.

The Greenwich provisional monthly mean sunspot number for the first eleven months of 1967 was 103.2 compared with 50.4 for the previous year. Forty-one sunspot groups of area equal to or greater than 500 millionths of the visible solar hemisphere were reported. Eight of these were of area of 1,000 millionths or greater, the largest (reaching 2,200 millionths — approximately 2,570 million square miles in area) did not produce any significant ionospheric disturbances during its passage across the sun's disc from July 21st to August 4th.

Considering that the predicted sunspot maximum is only a few months distant, 1967 was notable for the remarkable inactivity of the sunspot groups reported on the disc. Only 45 sudden ionosphere disturbances were reported up to mid-December (46 during 1966). Many were of a minor nature and had little effect on h.f. operation. Most of the activity occurred during February, March and May with 10, 9 and 12 fades respectively. From the end of May only 9 were reported.

So far, during the present cycle, reports of complete "blackouts" associated with intense solar flares have been conspicuous by their absence.

There was a slight increase in the level of magnetic activity during the year, the monthly mean Hartland "C" value† for 1967 being 0.62 com-

pared with 0.57 for 1966. Apart from a severe magnetic storm from May 25th-31st, during which a "C" value of 2.4 was attained on the 26th, there were few disturbances of note. On a number of occasions increased magnetic activity occurred during periods when there were no groups of notifiable size (500 millionths or greater) on the sun and there was some evidence that the disturbances were of the M region (27-day recurrence) type.


By the choice of suitably lower operating frequencies at critical times the effect of the disturbances was generally masked and h.f. communication was seldom seriously affected.

The increase in sunspot activity and values of IF2 (shown by the smoothed values in the graphs) resulted in higher maximum usable

frequencies (MUFs) and the influence of sporadic E on circuit operation was less marked. On many long-distance point-to-point circuits opportunity was taken to move up in frequency to the 23-25 MHz band for daylight operation. It was noted that, on many occasions, v.h.f. reception was possible over long distances.

Most h.f. circuits showed an increase in efficiency compared with 1966 and the monthly average percentage efficiency on four representative circuits using ARQ (automatic error detection and correction) and received in this country was 94% as against 92.9% for the previous year. These are equivalent to efficiencies of 99.3% and 99.1%, respectively, without the use of ARQ.

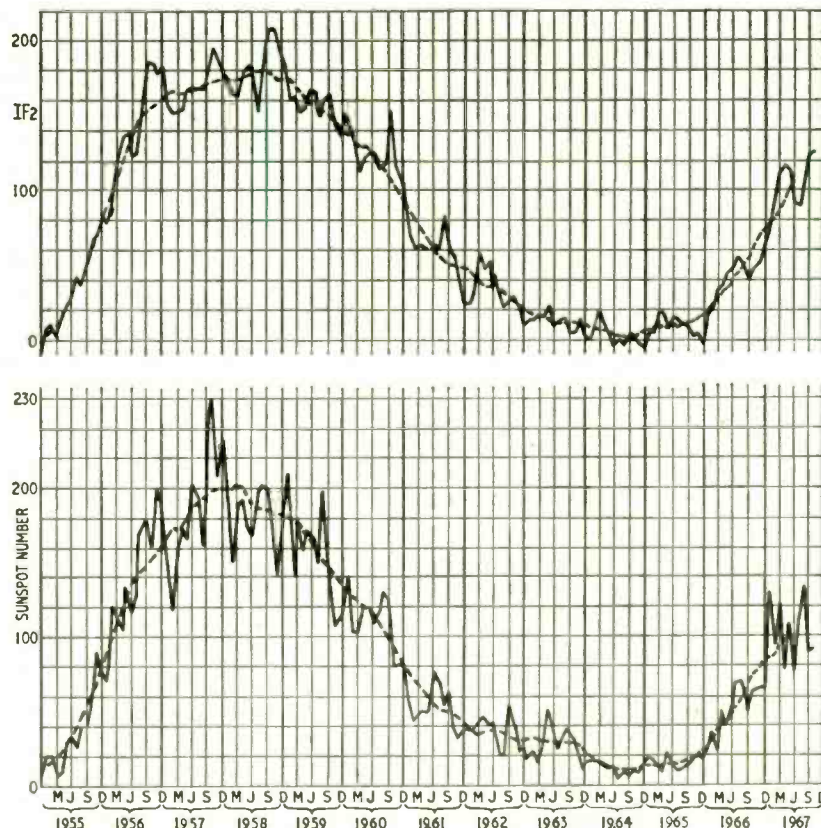There was considerable activity in the higher frequency bands, especi-



Monthly figures and smoothed values of the IF2 and of the sunspot numbers for the past thirteen years.

* Cable & Wireless Ltd.
† The mean of the "K" values recorded every three hours at Hartland, Devon.

ally in the field of satellite communications. As reported last year,† the first (F1) of the Intelsat II satellites suffered a failure of the apogee motor when launched in November 1966, and did not reach synchronous orbit. However, F2 and F3 were successfully launched in January and March 1967, and are now positioned respectively over the Pacific and Atlantic Oceans. In addition, because of the rapid growth of traffic, F4 in the Intelsat II series was also launched, in September, and is now in use in the Pacific Area. Intelsat I (Early Bird) continued to operate, having been in continuous use for 32 months by the end of the year.

The communication system in sup-

† *Wireless World*, March 1966, p. 135.

port of the NASA Apollo project was set up. This involves, in addition to the two stations on the U.S. mainland at Andover (Maine) and Brewster Flats (Washington), stations at Ascension Island, Canary Isles, Carnarvon (Western Australia) and two shipborne. Additional temporary stations were set up to provide public service channels between Thailand and the Philippines, and the U.S. mainland. Stations were completed at Fucino (Italy) and Buitrago (Spain), and the station at Moree (Australia) was almost finished. Stations in Argentina, Bahrain, Brazil, Chile, Hong Kong, Mexico, Peru, Philippines, Thailand, and at a number of other locations were under active discussion or being constructed. All these will

employ 85-foot, or larger, paraboloids in order to meet the full requirements of the I.C.S.C. (Interim Communications Satellite Committee) for standard earth stations.

Work on the Intelstat III satellites continued. It is expected that the first of this new generation will be launched in the Summer or Autumn of 1968. These 1200-circuit satellites will considerably increase the capacity available in the Atlantic and Pacific Oceans and will also, for the first time, give Indian Ocean coverage, permitting U.K.-Australia and U.K.-Japan circuits to be set up. Also, a full-time television service should be possible without the need to cut off part of the telephone service, as is necessary at present.

Literature Received

Racal RA 217 series solid-state h.f. communications receivers are described in a four-page brochure received from Group Publicity, Racal Electronics Ltd., "The Elms," 26 Broad Street, Wokingham, Berks.

WW 332 for further details

The performance characteristics and the applications of dry reed switches are discussed in a 41-page booklet issued by the Publicity Department, The M-O Valve Company Ltd., Brook Green Works, Hammersmith, London, W.6.

WW 333 for further details

The results of a two-year reliability study on Motorola i.p.c. encapsulated transistors are contained in report No. RD 104 published by Motorola Semiconductor Products Inc., York House, Empire Way, Wembley, Middlesex.

WW 334 for further details

We have received a set of pamphlets from Aero Electronics Ltd., Gatwick House, Horley, Surrey, that include details of a range of television signal generators, portable aerial masts for one- and two-man erection, quartz crystals, radiotelephones and educational equipment. Also included is a CV type valve equipment guide.

WW 335 for further details

Lasky's Radio Ltd., who recently celebrated their 35th birthday, have sent us a copy of their 12-page colour pictorial catalogue. Their headquarters are at 3-15 Cavell Street, Tower Hamlets, London, E.1, and they have five branches in London.

WW 336 for further details

Semiconductor Polarizing Filter for Infra-Red is the title of a leaflet on Siemens semiconductor i.r. filters and polarizers available from Cole Electronics Ltd., 7-15 Lansdowne Road, Croydon, CR9 2HB.

WW 337 for further details

Facilities for all aspects of printed circuit design and production offered by S.C.E.E. Ltd., Reddicap Trading Estate, Sutton Coldfield, Warwick, are described in the five-page leaflet PCB 10-1.

WW 338 for further details

A multi-channel carrier frequency system, that can be used with wire or foil strain gauges (half or full bridge connected), rotary transformers and transducers for the measurement of torque, load, displacement, vibration, acceleration, and pressure, is described in a leaflet from the Vibro-meter Corp., Haletop Civic Centre, Wythenshawe, Manchester 22.

WW 339 for further details

Received from the British Industrial Measuring and Control Apparatus Manufacturers' Association the 1967/69 edition of its handbook which describes the association, what it does, its members and their products. This 112-page publication will be sent free to branches and subsidiaries of industrial organizations at home and abroad, to Government departments, public authorities, public technical reference libraries and technical college libraries. The address is 23/24 Margaret Street, London, W.1.

WW 340 for further details

Aim Electronics Ltd., have just published their first short-form catalogue, **Advanced Instrumentation Modules**. Within its 20 pages, modular units available in each of three spheres of waveform technology are described. The same units may also be obtained either ready-assembled into complete systems or for assembly by the user. The three divisions in which systems are available are signal recovery and analysis, pulse generation and waveform sampling. The booklet ends with basic explanations of phaselock techniques, waveform sampling techniques

and lock-in amplifiers. Copies are available from Aim Electronics Ltd., 71 Fitzroy Street, Cambridge.

WW 341 for further details

A new comprehensive guide to five product ranges of particular interest to industrial electronics engineers and designers has been published by Newmarket Transistors Ltd. The 20-page guide described as a "Products Portfolio" gives in tabular form details of semiconductors, including industrial germanium and silicon devices, packaged circuits and film attachment devices. A special section is devoted to the company's customer-oriented microcircuit building service. Free copies for buyers, engineers and designers can be obtained from the Sales Office Manager, Newmarket Transistors Ltd., Exning Road, Newmarket, Suffolk.

WW 342 for further details

Electro-magnetic pick-ups that convert mechanical motion into an a.c. voltage without physical contact or external power are described in the 6-page Bulletin F-8 available from Ampex Electronics, Seminole Division, P.O. Box 8488, Fort Lauderdale, Florida 33310.

WW 343 for further details

The latest position regarding the preparation of metric standards is given in the B.S.I. publication PD 6286, "Metric standards published and in progress." Section 1 lists more than 800 standards already written in metric units. Some 250 standards independent of any system of units such as glossaries and colour codes are listed in Section 2. Sections 3 & 4 give details, under industry headings, of the 500 or so standards now being revised or awaiting revision in metric terms. The information in this 82-page booklet is complete to 31st August, 1967. B.S.I. Sales Office, Newton House, 110 Pentonville Road, London, N.1. Price is 10s.

NEWS FROM INDUSTRY

ADVICE ON MATERIALS TECHNOLOGY

THE United Kingdom Atomic Energy Authority (U.K.A.E.A.) has set up a Materials Technology Bureau at the Atomic Energy Research Establishment at Harwell. The purpose of this bureau is to stimulate enquiries on materials from industry and research organizations and to share knowledge accumulated by scientific and technological staff in the Authority. It is also intended to provide an advice consultancy service and to encourage visits between Authority staff and industrial firms. This may lead to the use of Authority facilities on specific problems either by visiting technologists or U.K.A.E.A. staff. Information services of a general nature will be provided free although a charge will be made for consultancy work and for the use of experimental facilities. Most of the knowledge acquired by the

U.K.A.E.A. during the course of their work, relates to materials—particularly conventional materials for unconventional use. The experience includes the use of modern techniques for the fabrication and preparation of metals and ceramics, including high-frequency and electron beam melting and casting, hydrostatic extrusion, planetary swaging, hot pressing, isostatic pressing (hot and cold) and vibro-compaction of powders. Other examples are the ultrasonic machining of glass and ceramics, together with the various jointing processes including electron beam and friction welding, roll-bonding and the brazing of metals to ceramics. Interested readers should contact the head of the Bureau, Mr. H. Lloyd, M.B.E., Ceramics Division, Building 35, A.E.R.E., Harwell.

COMPUTERS—A NEW CONTENDER

INITIALLY producing a range of three medium sized computers for the European market Philips Computer Industries are to be officially opened on June 14th at Apeldoorn in the Netherlands. The first production models of these general purpose machines will be absorbed by Philips for their own use, however, deliveries to outside customers are expected to start in the beginning of 1969. At present the staff at Apeldoorn numbers a thousand although throughout the Philips concern about 6,000 people are either directly or indirectly employed on computers. Philips started research into computers in 1950, which led to the construction of a number of machines, some for use within the company. Among these were PETER, PASCAL and STEVIN.

Later this research led to the production of machines for military applications, air traffic control, fire control and defence purposes.

In the Netherlands some 2,200 are employed on research whilst in other countries another 1,500 reinforce these activities. Work is proceeding on memories in the United Kingdom, peripheral equipment in Germany and multilayer circuit boards and software in Belgium.

The new range of machines will be called the P1000 series. They will use integrated circuits and will feature a fast memory. It will be a fairly simple matter to translate programmes written for other computers for use on these machines.

CAR DRIVING SIMULATOR

A NEW car driving simulator, the Drivotrainer, has been developed by the Raytheon Company, Massachusetts, U.S.A., which is capable of training up to 32 students simultaneously. In essence, it consists of 32 "cars," a large cinema screen, a control computer and an instructor's monitoring console. The student "drives" in response to the changing road conditions indicated by a colour film projected on the screen (which includes the rear mirror view), the film having previously been taken through the windscreen of a camera-equipped car. The film carries a sound track and binary coded information indexing all the proper driving responses

that match the actions seen on the screen. The computer scans each car and in the event of a student acting incorrectly, lights a message indicator informing the student of what he should do to correct his action. The cars can even run out of petrol and will stall if the student allows the petrol gauge to indicate zero. Another task of the computer is to keep a score for each student and to print out a detailed account of the student's actions compared to what they should have been. Advanced films prepare the student for handling emergency situations and enable them to drive in rain, snow, fog and ice in complete safety



Drivers on the London Transport Victoria line and its Brixton extension will be able to communicate directly with other trains using a v.h.f. radio link. So far Nelson Tansley Ltd., 144 Holland Park Avenue, W.11, have received orders for about 170 communication systems as shown in the photograph. These, in addition to inter-train communications, offer passenger address and cab-to-cab intercom facilities.

ELECTRONIC CONTROL OF LOCOMOTIVES

THE combined use of a radio link and digital control equipment has allowed freight trains to be operated more economically in America by enabling more trucks to be incorporated in a train. For instance, using the system, a typical train would consist of three 3,600 horse-power diesel units followed by as many as 300 trucks and three slave diesel units of similar horse power. The system, designated Locotrol, translates commands of an engineer in the lead locomotive and transmits them to the slave locomotives. Each message comprises 50 bits, transmitted over a 200 ms period, and includes address code, control information and an error check code. Each command contains an algebraic problem which must be solved for zero by the addressed locomotive before the order is accepted. If the result is something other than zero the slave requests that the message be repeated thereby ensuring the fidelity of the radio link. The equipment is manufactured by Radiation Inc.

An advanced educational television studio has been opened at Herriot-Watt University, Edinburgh, which it is hoped will substantially increase the effectiveness of teaching and strengthen

the university's ties with industry. Although equipped with black-and-white cameras (Marconi V322Bs) and ancillary equipment at the present time, the design of the studio renders it suitable for colour television use. Equipment includes a telecine system that will accept 16 or 35 mm film or slides and seven cameras with seven-inch electronic monitor/viewfinders. The studio is linked with lecture theatres, laboratories and staff rooms throughout the university. The studio control room design is in agreement with the latest in broadcasting philosophy, consisting of an array of four 14-in monitors, a nine-inch preview monitor and a comprehensive vision and sound control console.

Land reclaimed from the river Itchen, Southampton will be the site of a new colour television centre to be built for Southern Independent Television at a cost of £500,000. The prime contractor is the Marconi Company who will provide a substantial proportion of the equipment and will assist Southern Television with the planning and installation. The equipment will include a comprehensive control switching system to allow television to be fed in and out of the I.T.A. broadcasting network. Some of the fifteen colour television cameras to be supplied are destined for outside broadcast units currently under construction. The cameras will be supplied complete with colour balance equipment correcting for variations in colour temperature. A large number of distribution amplifiers will be installed for routing signals to monitors throughout the centre. A Marconi designed switching system will carry signals from Video tape recorders and Rank Cintel telecine equipment to the studio control rooms for integration into the programme.

A new Product Division has been formed at Basildon, Essex, within the Marconi Company which is known as the **Electro-Optical Systems Division**. This new division will exploit the growing use of electro-optics to extend human capability. This can be achieved either directly by extending human operator faculties or indirectly by using the system to train him more effectively. The division has been formed by combining the activities of two groups, the Closed-Circuit Television Division and Project Martel—a team producing the television guidance system for the Anglo-French missile Martel. The two activities represent a turnover in excess of £3M.

Johnson Matthey Metals Ltd. have introduced a new line, gold inlaid beryllium-copper, that should be of interest to manufacturers of plug and socket components, particularly those for use with printed circuit boards. The minimum dimensions of the 5% nickel-gold inlay are 0.25 in wide by 0.0002 in thick; in all cases the thickness of the inlay must exceed 3% of the total thickness of the strip.

A new telecine system announced by Marconi is capable of making fast (50 ns) cuts between any of four programme sources. Two versions are available, one for black-and-white reproduction only, using a Mk. VI camera, and one for colour or black-and-white built around the Mk. VII camera. Inputs can be from 35 mm or 16 mm cine projectors and/or a dual slide projector. A variable density filter in between the lamp-house and the film compensates for variations in film density whilst electronic circuits compensate for film dye imperfections. The system has been designed by Marconi with the exception of the film projection mechanisms which are of well-established professional manufacture. A sync. interlock drive motor is employed which allows precise registration of separate magnetic sound followers. The equipment is intended for use with a Westrex sound follower unit, but other units may be employed providing minor modifications are made.



The system has been designed by Marconi with the exception of the film projection mechanisms which are of well-established professional manufacture. A sync. interlock drive motor is employed which allows precise registration of separate magnetic sound followers. The equipment is intended for use with a Westrex sound follower unit, but other units may be employed providing minor modifications are made.

An exhibition of small American computers is to be held in various places throughout Britain early in the new year. The exhibition will open at the U.S. Trade Center and then go on tour in seven specially fitted British Rail display coaches. Places at which the exhibition will be held are:

London, U.S. Trade Centre, Jan. 16 to 19.
 Birmingham, Moor St. Station, Jan. 25 to 27.
 Manchester, Victoria Station, Jan. 29 to 31.
 Newcastle, Central Station, Feb. 1 to 3.
 Glasgow, Stobcross Freight Dept. Feb. 5 to 7.

In all, 16 exhibitors will show machines ranging from simple electronic calculators to complex process control computers.

A Norwegian firm, **Nera Bergen A/S**, has been awarded a contract by the Norwegian Director-General of Telecommunications worth 21.6M Norwegian Crowns (just over £1M) for microwave equipment to be used internally. The contract is for 1800 channel broadband equipment for the routes between Tromsø and Hammerfest; Stjøfjell and Rassegalvarre, Oslo and Bergen, in addition to equipment for 27 300-channel local branch links from the main network. The equipment has been developed by Nera Bergen and production has already begun. The expansion is the foundation for further work that will lead to a fully automated telephone network and it is hoped to link the more northerly districts of the country to the national telephone network in 1969.

The Central Treaty Organization have ordered seven meteorological radar systems from Plessey Radar which will be installed in Iran, Turkey and Pakistan early in 1968. The equipment, which is worth £131,000, consists of four wind-finding radars type WF2 and three type 42 weather radars.

After winning a colour television contract, the Marconi Company succeeded in delivering, installing and commissioning the equipment in Bangkok within six weeks. The contract, worth £160,000, was to supply and install, in an outside broadcast van supplied by the Bangkok Broadcasting and Television Corporation, two Mk. VII colour cameras, monitors, sound and vision mixing equipment and a video tape recorder. Thailand commenced live colour television broadcasts last November.

B. H. Morris & Co. (Radio) Ltd., of 84/88 Nelson Street, London, E.1, have been appointed sole U.K. distributors for the **Trio Corporation**, of Japan. The Trio product range consists of audio equipment and communications receivers. Featured in the range is a double conversion superhet crystal controlled communications receiver (Model JR500SE) that has a recommended retail price of about £60. It incorporates a crystal controlled b.f.o. and an S meter and covers 3.5 to 29.7 MHz.

An American manufacturer of precision components for the focusing, deflection and control of electron beams in cathode-ray tubes has appointed **Walmore Electronics**, 11-15 Betterton Street, Drury Lane, London, W.C.2 as their U.K. Agents. The firm, **Constantine Engineering Laboratories**, of New Jersey, produce a short form catalogue illustrating specialized applications that is available from Walmore.

The contract to provide the solar cells for the **ESRO** satellites TD1 and TD2 (see page 683) has been won by **Ferranti Ltd.** The satellites will carry a sun-oriented array of 11,520 silicon solar cells worth over £300,000. Ferranti solar cells are also being used on **ESRO 2** and **Ariel 3**.

DEMONSTRATING RECTIFIER ACTION IN SLOW MOTION

By T. PALMER,* B.A., Assoc.I.E.R.E.

VERY often it is useful to be able to clarify points of theory with a slow motion demonstration. The writer has previously described methods for demonstrating series circuits in phase-shift oscillators¹ and a.c. theory² in slow motion. This third article applies similar techniques to rectifier action, in particular illustrating one aspect that is difficult to show on an oscilloscope.

The demonstration comprises three separate stages. In stage one the output of a v.l.f. signal generator operating at about seven cycles per minute is applied to three meters: A_1 and A_2 swing in step with V_1 . Adjust the output voltage of the signal generator to give a peak reading of, say, one volt on V_1 . Then set R_1 to give a peak reading of $100\mu\text{A}$ on A_2 .

For stage two a diode is inserted (OA81) as shown. Now when meter V_1 gives a reading on the right of zero A_1 and A_2 follow, and when V_1 swings to the left A_1 and A_2 read zero. The peak forward current is now less than $100\mu\text{A}$ because of the forward resistance of the diode; restore this current to $100\mu\text{A}$ by re-adjusting R_1 —note the amount by which R_1 is reduced. This reduction corresponds to the forward resistance of the diode (although it would be truer to say that it represents the forward resistance when a forward current of $100\mu\text{A}$ is flowing).




Proceeding to stage three, capacity C_1 is added. This was originally made up of 20 separate $100\mu\text{F}$ tantalum capacitors but ordinary low voltage electrolytics should do. Eventually the circuit will reach a state of equilibrium where in each cycle the charge flowing into D_1 is equal to that flowing out of C_1 through R_1 . When this happens it can be clearly seen that the diode passes current for only a small fraction of the positive half cycle as indicated by the brief pulse of current shown on A_1 when V_1 has almost reached its maximum positive value. This is about the same as the peak current on A_2 and is around half a milliamp.

After the pulse C_1 discharges through R_1 and the readings on A_2 and A_3 are equal (as C_1 is discharging A_3 reads to the left of zero). Until the equilibrium condition is reached more charge flows into C_1 through D_1 than leaks out through R_1 in the intervals between pulses. The first pulses of current may have a peak value of 0.8mA . As C_1 becomes more and more charged in successive cycles this diode current diminishes until it reaches a value 0.5mA and the duration of the pulse decreases correspondingly.

The peak value of the diode current should be the sum of the

peak current on A_3 and the current through the resistor. If the meters A_2 and A_3 are heavily damped this may not be suggested by the meter readings; but the meters used originally did support the equation.

It is easy to extend this technique to other rectifier circuits—a bridge, for instance. It is recommended in this case to have a meter in series with each of the four diodes and one for the a.c. current and one for the d.c. current; six meters in all. It is a good idea for provision to be made for shorting out individual meters as the sight of six pointers swinging simultaneously at early stages in the demonstration can be confusing, to say the least.

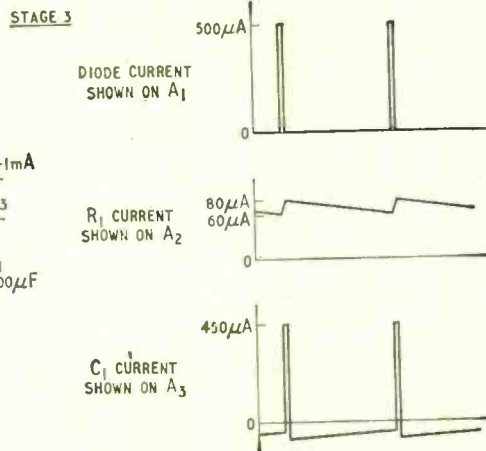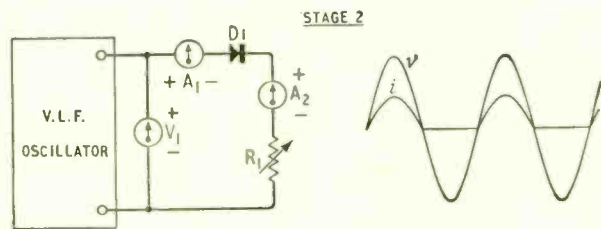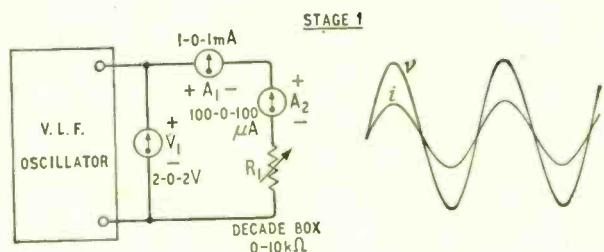


* Acton Technical College.

1. "Demonstrating a.c. theory," by T. Palmer. *Wireless World*, October 1963.
2. "Demonstrations at v.l.f.," by T. Palmer. *Wireless World*, June 1966.

NEW PRODUCTS

Colour TV Pattern Generator

THE adjustment and servicing of colour television receivers is simplified by the Philips pattern generator, type PM5506. It will be available in Britain from the M.E.L. Equipment Company Ltd., and will cost £245. The instrument takes full advantage of the "self checking" properties of the PAL system which enable a receiver to be adjusted using the picture tube as the only indicator. This is said to almost eliminate the need for an oscilloscope, but if one is used it can be synchronised by line and field sync pulses from the generator. The generator delivers ten pattern signals which are selected by ten push-buttons arranged in logical sequence across the front panel as follows: (1) black and white checkerboard of 6 × 8 squares for checking tuning, scanning, amplitude and linearity, (2) blank raster with constant white content for purity check, (3) blank raster with constant red content for purity check, (4) eight-step staircase for grey-scale tracking, (5) dots, 11 × 15, for adjustment of static and dynamic convergence, on 625 lines only, (6) crosshatch, 11 × 15 lines, for adjustment of static and dynamic convergence, on 625 lines only, (7) four colour bars for delay line phase and amplitude adjustment, using tube as indicator, (8) four colour bars for demodulator phasing, using tube as indicator, (9) four colour bars for matrix check, using an oscilloscope, and (10) eight colour bars similar

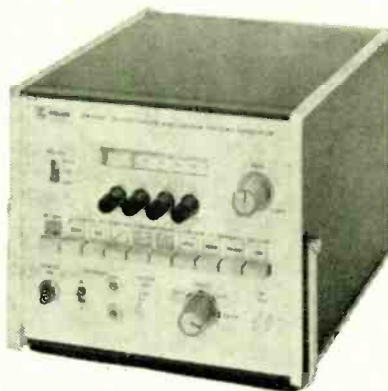


to the B.B.C. signal for general check. The standard is PAL 625 lines, and the range covered is 470 to 850 MHz, frequency being selected by push-buttons and continuous tuning. Outputs are 10 mV at u.h.f. (continuously variable) and 1 V at video, both into 75 ohms. Burst amplitude is variable for checking colour killer and a.g.c. The sound carrier can be modulated internally, unmodulated or switched off. Complete solid state construction has been used, and the generator measures 10½ × 8½ × 7½ in. The weight is 10 lb. M.E.L. Equipment Co. Ltd., Manor Royal, Crawley, Sussex.

WW 301 for further details

Solid Tantalum Capacitors

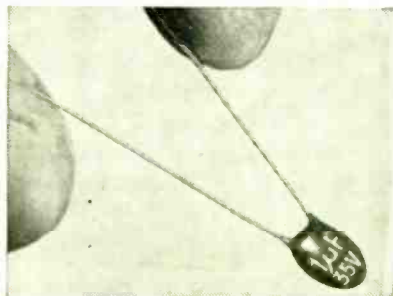LOW COST, epoxy encapsulated, solid tantalum capacitors, designated Kemet "E" Series capacitors, are now available from Union Carbide U.K. Ltd.,



Electronics Division. "E" Series capacitors have been designed for commercial and high quality electronics applications, e.g., in communication equipment, where high capacitance values are required in small space, for coupling, decoupling and timing circuits. The devices have a high volumetric efficiency, low leakage current, and reverse voltage capability. The capacitance tolerance is ±20% and the capacitors are designed for continuous operation between -55°C and +85°C. Kemet "E" Series capacitors are available from 3 V to 35 V, at 0.1 to 100 μF. Electronics Division, Union Carbide U.K. Ltd., 8 Grafton St., London, W.1.

WW 302 for further details

Tape Recorders

TWO tape recorders have been added to the Truvox range of sound recording and reproducing equipment. The new models, the R52 (two-track) and R54 (four-track), have an entirely new three-speed (7½, 3¼ and 1½ in/sec) Truvox deck. Known as the Series 50 models, they incorporate many other significant departures from previous designs. The combination of twin acoustically matched 7 × 4-inch speakers mounted in a wood cabinet is said to result in exceptionally good sound quality. The case, controls and mechanism have been designed for both flat and vertical operation of the unit. The Series 50 recorders have linear frequency characteristics from 30 Hz to 17 kHz at 7½ in/sec, with wow and flutter of less than 0.14%. Oscillator frequency is 90 kHz. With calibrated VU meter, tone control, full monitoring facilities, mixing and (on R54 only) dual play provision, the new units come within the definition of hi-fi equipment. Total output is 6 W. The three-figure digital counter has a push-button reset. Unbreakable control keys and key switches themselves are also of a new type, ensuring light yet positive action. Controls are interlocked and there is pause control, automatic tape-end stop, push-on spool retainers and an accessory storage compartment. Truvox decks have a large robust motor mounted below a solid aluminium deck plate with anodised lettering to identify controls. Micro-gap recording heads are used, and the solid-state electronics include selected matched silicon transistors. Low-noise, moulded-track potentiometers are also employed. Both models take 7-inch spools, giving 8½ hours and 17 hours of play respectively on double-play tape. Both are supplied complete with a moving-coil microphone, one 7-inch reel and 1,200 ft of tape. They weigh 25 lb (11.5 kg) and measure 13½ × 15 × 7 in (34 × 38 × 18 cm). The price is 56 gns for both models. Truvox Ltd., Hythe, Southampton.


WW 303 for further details



WIRELESS WORLD, FEBRUARY 1968

Modular Sound Systems

THE ASTRONIC A1700 Series of modular amplifying equipment has been designed to enable particular requirements to be met by building up a system using standard units, thereby keeping the cost of otherwise non-standard equipment down and reducing delivery delays. The 75 W power amplifier is intended for large p.a. installations, its output circuit incorporating current sensing diode networks which render it short-circuit proof. The amplifier can be racked up in multiples for parallel operation to give higher power outputs up to 750 W. Silicon transistors are used throughout all units and transformers are vacuum impregnated and dipped. Using either a 10 W, 25 W or 75 W power amplifier, up to seven input and control modules may be fitted to the main frame, any unwanted position being filled by a blank panel. Thus, a five-way microphone mixer with a music input and master gain control, or a two-way microphone with tape, gram and radio input modules together with master gain, can be constructed. A variety of standard modules are available. All input and control modules are constructed on etched aluminium front panels with suitably marked controls and components are marked on printed circuit boards. The pre-stages amplifier of both the 25 W and 75 W power amplifier are also on printed circuits boards, the main chassis being equipped with edge connectors into which these boards are plugged, alignment being ensured by guides. The modules are retained in the main frame by captive screws. Input, output and mains connection are situated at the rear of the case. The amplifier is constructed on a rigid sheet plated steel chassis and provided with adequately ventilated removable steel covers when used as a free standing amplifier. For rack mounting these covers become optional and the case end plates are changed to provide standard 19 in G.P.O. rack fixing. The inputs are: microphone, low impedance 15-50 Ω balanced with a sensitivity of 50 μ V; tape, high impedance 270 Ω unbalanced, sensitivity 150 mV; gram, high impedance 2 M Ω unbalanced, sensitivity 120 mV; radio, high impedance 270 k Ω unbalanced, sensitivity 150 mV. The controls consist of microphone module: bass filter, gain control, tape, gram, radio modules: treble control ± 15 dB at 10 kHz, bass control

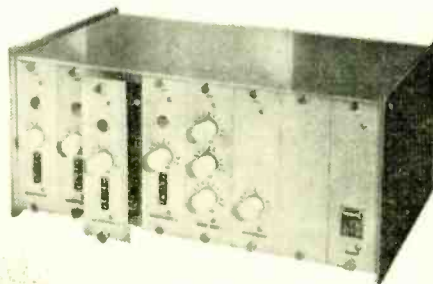


± 12 dB at 100 Hz, gain control. Distortion is less than 1% for full output on 10 W, 25 W and 75 W models. Response for microphone is ± 2 dB 50 Hz—10 kHz and music ± 2 dB 40 Hz—12 kHz. Noise on microphone is better than 50 dB and on music it is better than 60 dB. The dimensions are: standard free-standing unit 16 $\frac{1}{2}$ \times 7 \times 10 in deep; rack mounting model 19 \times 7 \times 10 in deep. Associated Electronic Engineers Ltd., Dalston Gardens, Stanmore, Middlesex.

WW 304 for further details

LEGEND INDICATOR

USING a bright-glow neon lamp, the miniature Bulgin mains legend indicator is operated directly from 200-250 V. The power consumption is approximately 1 W, with negligible temperature rise. Connections are by 110 Series push-on tags equally suitable for direct soldering. The two styles of legend available are black characters on lit amber background, or lit amber characters on a black background. This component will fit into a panel cut out to 1.32 in \times 0.512 in. A. F. Bulgin & Co. Ltd., Bye-Pass Road, Barking, Essex.

WW 305 for further details

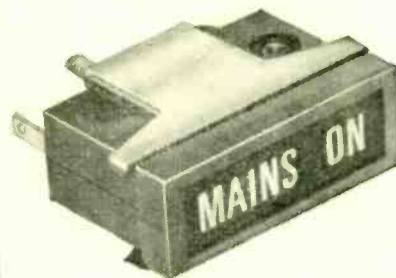

Flat-Lens Photodevices

TWO MINIATURE silicon planar photodevices from SGS-Fairchild Ltd., the BPY66 and BPY67, are said to entirely eliminate cross-talk and cross-light problems in photoelectric reading systems for punched card and punched tape equipment. Contained in hermetically sealed cylindrical Kovar cases only 2 mm diameter by 4.5 mm long, they feature a coaxial flat-lens construction that enables them to be mounted absolutely flush in the reading head so that each device receives light only from its associated source. Mounting can be achieved without the need for critical alignment, thus simplifying manufacture and maintenance of the equipment. Both devices are manufactured from specially diffused silicon chips which, despite the unusually small device dimensions, have a very large base surface to trap the maximum number of photons. Their planar construction guarantees an inherently low dark current and a high light-to-dark current ratio, enabling them to be used at very low light levels. The BPY66 is a sensitive photo-transistor capable of providing a photocurrent of 0.3 mA minimum in a light level of only 10 mW/cm². As it operates efficiently with tungsten lighting, it can be employed in optically coupled circuits, coding equipment, character recognition

and process control. The BPY67 is a photo-diode which, in the reverse-bias mode, features good photocurrent linearity. In the photo-voltaic mode, its open-circuit voltage varies in a logarithmic manner suitable for servo-type applications such as horizon detectors and proportional followers. A prime attribute of the BPY67 is speed; it is at least 10 times faster than a photo-transistor permitting detection of laser beam modulation up to several MHz.

WW 306 for further details

Feed-through Terminal

A MINIATURE feed-through terminal engineered for insertion into panels 0.320 in thick is available from Sealectro. Designated press-fit part no. FT-160-TUR, the new feed-through has a 0.148 in minor diameter measuring 0.500 in long. When installed in a 0.125 in or thicker panel, the insertion hole is 0.144 in \pm 0.002 diameter with a 60° countersink to a diameter of 0.174 in \pm 0.010—0.002. It features a gold over copper-plated brass lug, rated for 5.5 A continuously. Sealectro Ltd., Walton Road, Farlington, Portsmouth.


WW 307 for further details

Micro-miniature Coaxial Connector

SUITABLE for matched impedance coupling of 50 Ω lines, an r.f. micro-miniature coaxial connector by Thorn Special Products Ltd. has overall dimensions of 0.625 in length and 0.103 in diameter. Its low-loss characteristics result in a voltage standing-wave ratio of less than 1.16 at a frequency of 3.5 GHz. With simple push-pull coupling, the connector allows rapid assembly or servicing of miniaturised u.h.f. equipment. Contact resistance is less than 4 m Ω and the operating temperature range is -55°C to $+200^{\circ}\text{C}$. Made of gold-plated copper alloy, with crimped connections, the connector is internally insulated with p.t.f.e. The disengaging force of a mated connector is in excess of 4.4 N (16 ozf), while cable retention in each

half of the connector is greater than 44 N (10 lbf). The micro-miniature connector is supplied as a completed cable assembly, the pin and socket each being assembled with a 12-in length of 50 Ω Teflon jacketed coaxial cable (RG.178BU). Alternative lengths are available to order. Thorn Electrical Industries Ltd., Thorn House, Upper Saint Martin's Lane, London, W.C.2.

WW 108 for further details

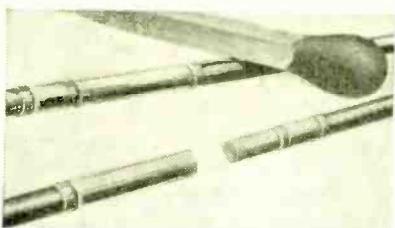

I.C. Audio Amplifier

AUDIO amplifier type PA 222 is an encapsulated eight-lead dual-in-line integrated circuit by General Electric (U.S.A.). It is intended for consumer and light industrial applications with a 1-watt output rating. The supply voltage required is 25V, the power gain is said to be 72dB with a 22 Ω load; with one watt output the noise figure is -55 dB. This unit has a frequency response of ± 3 dB over the range 55 Hz to 15 kHz. Price is £1 16s 0d and data sheets are available. Jermyn Industries, Vestry Estate, Sevenoaks, Kent.


WW 309 for further details

H.F. Communications Receiver

A NEW communications receiver (RC410/R) with a built-in frequency synthesizer has been introduced by G.E.C. (Electronics), replacing their BRT 400 range which ran to eight marks over the course of 20 years. The receiver covers 2-30 MHz and has facilities for s.s.b. reception (upper or lower sideband) as well as c.w., m.c.w. and d.s.b. The signal frequency is displayed digitally on a bank of in-line cold cathode tubes, the display being locked to the frequency synthesizer. Unusually the receiver is single-knob-tuned in 1 kHz or 100 Hz steps and has the "feel" of a conventional free-tuning receiver; frequency stability is quoted as being 5 Hz at 30 MHz. A f.e.t. is employed in the front end to provide a

good cross- and inter-modulation performance. Crystal filters are incorporated for A1, A2 and A3 modulation and a sideband filter for A3a and A3j is included. Sensitivity for 12 dB (signal-noise)/noise at the output in the A2, A3 mode is 2.5 μV and in the A1, A3a, and A3j better than 0.5 μV . The audio stage provides 1 W into 3 Ω or 10 mW into a 600 Ω balanced load. Image response is greater than 60 dB below signal response and other spurious responses are at least 70 dB down on the signal. Second- and third-order intermodulation selectivity is better than 60 dB below signal response. A notch filter with a 6 dB bandwidth of 800 Hz tunable 4 kHz about a centre frequency of 100 kHz providing a rejection of at least 30 dB is incorporated. A three-position switch selects a.g.c. attack times of 10, 20 or 30 ms and a.g.c. performance is such that the audio output level will not vary more than 6 dB for an input level variation of 90 dB referred to 1 μV . G.E.C. (Electronics) Ltd., Communications Division, Spon Street, Coventry CV1 3AZ.

WW 310 for further details

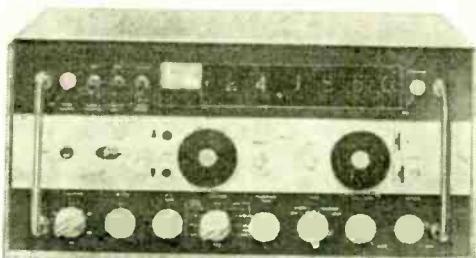


712

R.F. Bridge

AN IMPEDANCE bridge for accurate measurements in the 400 kHz to 60 MHz range is now available from General Radio Co. (U.K.) Ltd. The 1606-B radio frequency bridge is adaptable to coaxial connectors, and in particular the GR900 precision coaxial connector, for convenience in making highly repeatable measurements on devices fitted with such connectors. The GR900 coaxial connection also simplifies calibration of the bridge with precision resistance and capacitance standards. The screw-type terminals on the basic instrument can be adapted to GR900 coaxial connectors with the 1606-P2 adaptor kit, and to other coaxial systems with appropriate adaptors. The resistance range of the bridge is 0 to 1 k Ω , and the reactance range is ± 5 k Ω at 1 MHz (at other frequencies the reactance reading must be divided by the frequency in megahertz). General Radio Company (U.K.) Ltd., Bourne End, Buckinghamshire.

WW 311 for further details

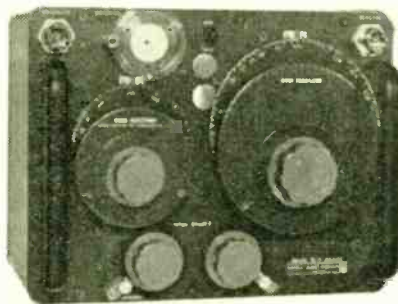

High Current Vacuum Variable Capacitor

A NEW high-current small-size ceramic vacuum variable capacitor, the CAQA-200, by ITT Jennings is available from S.T.C. This new variable capacitor utilizes high efficiency ceramic and copper materials with vacuum dielectric. The overall length is only 3.75 in with a diameter of 1.31 in. The CAQA-200 is capable of handling 50 A r.m.s. at 16 MHz. The temperature rating is 120°C by actual current testing. Capacitance range is 10 to 200 pF. Peak voltage is 3 kV at 60 Hz. Design of compact transmitter tank circuits is possible with the CAQA-200. Typical uses are as tank capacitors on medium power fixed frequency and pre-selected frequency transmitters. STC Components Marketing Division, Edinburgh Way, Harlow, Essex.

WW 312 for further details



INSTRUMENT RECORDER

A 7-CHANNEL instrumentation tape recorder-reproducer, weight 30 lb, and small enough to be stowed under an aeroplane seat, is now being marketed in the U.K. by Consolidated Electrodynamics. The Model 417 recorder can, in laboratory applications, be operated from 110/220 V a.c. In the field it runs off its own built-in, rechargeable batteries. It is equipped with a low mass differential capstan drive which is said to ensure good performance under difficult operating conditions. Other features include dynamic braking, low power consumption (maximum 12 W), and a switchable reproduce channel for field monitoring of all record channels. Frequency response of the model 417 is 200 Hz to 100 kHz direct and d.c. to 10 kHz f.m. The $\frac{1}{2}$ -in head arrangement is IRIG (Inter Range Instrumentation Group, U.S.A.) compatible. A choice of four new speed combinations is offered within the range $\frac{1}{8}$ in/s to 30 in/s. Optional facilities include remote control, voice track, continuous-loop adapter, end of tape sensor, and footage counter. Size of the Model 417 is only 14 in wide \times 15 $\frac{3}{8}$ in deep \times 6 $\frac{1}{2}$ in high. Consolidated Electrodynamics, 14 Commercial Road, Woking, Surrey.

WW 313 for further details

Resistance Boxes

RESISTANCE box Series 1200 by D.S. Controls gives a selection of 72 values of resistance from 1 Ω to 8.2 M Ω in a 10% tolerance preferred value range with two selector knobs. The ranges are $\times 10$; $\times 100$; $\times 1k$; $\times 10k$ $\times 100k$; $\times 1M$, and resistance types are high stability carbon film. Ratings available are 1200, 0.5 W; and 1201, 0.25 W to 4.7 M Ω and 0.5 W from 5.6 M Ω up. The size is 8 \times 5 \times 5 in and the weight is 3 $\frac{1}{2}$ lb. Prices are 1200, £15 10s 0d, and 1201, £19 10s 0d. D. S. Controls, 24 Broughton Road, Orpington, Kent.

WW 314 for further details

DC Servomotors

DIRECT current servomotors capable of reaching 1200 r.p.m. from zero in one millisecond are available from Honeywell. First model in the series, the HSM 30 servomotor, has very low armature inertia (0.00035 N cm s²), extremely rapid acceleration characteristics, (278,000 rad/s² initially at 24 V), a mechanical time constant (inertial) of 2.4 ms and a rated torque of 21 N cm (30 ozf in). Design of the servomotor represents a complete break from conventional motor design geometry in that all the rotating iron has been removed, leaving a moving coil, shell-type rotor configuration. Coils are encapsulated in a hollow, cylindrical shell of special high-temperature material, and a four-pole permanent magnet circuit is employed, using extremely high flux densities. In use the HSM 30 will start or stop in less than half the time of other motors of comparable frame size (4.0 in dia \times 3.6 in long). It can be directly coupled to the load for inertia match, so that gearing and belts can be eliminated, and can replace motor-brake or motor-clutch combinations, with the added advantage, in many cases, of solid state control. The new servomotor is suitable for use with tape capstan drives, intermittent motions, machine tool drives, drafting machines, digital and analogue positioning, computer

printers, readers, memory disc packs, etc. Honeywell Controls, Ltd., Brentford, Middx.

WW 315 for further details

RESONANT GATE TRANSISTOR

A NEW solid-state device called a resonant gate transistor (r.g.t.) is now available in evaluation quantities from Westinghouse Electric Corporation. The r.g.t. is a frequency selective device capable of providing Qs from 20 to 200, and its availability offers a solution to the problem of building tuned circuits without inductors. The operation of the r.g.t. results from a mechanical resonating beam or "tuning fork" of minute proportions actuated by electrostatic forces. A signal voltage, when superimposed upon a larger constant polarization voltage, sets the resonating beam in motion. Vibration of the beam is sensed by a conventional m.o.s. field effect transistor for which the beam serves as the gate electrode. The frequency range of the r.g.t. is at present limited to about 3 kHz - 30 kHz but higher frequencies can be obtained by using an overtone mode of vibration. Westinghouse Electric International, 1-3 Lr. Regent St., London, S.W.1.


WW 316 for further details

Biaxial Field Electromagnet

THE SCIENTIFICA 2 inch electromagnet has features that make it suitable for both research and advanced teaching. Either standard plane pole caps or ones with an axial bore hole through them can be used. The magnet is therefore supplied with two sets of pole caps, one being plane with optically polished faces, while the other pair are similar, but have in addition an axial hole of 1 in diameter. This enables additional experimental investigations to be carried out. In order to ensure maximum


field homogeneity for all field settings, the pole ferrous caps are precision machined and the pole faces are ground and polished to a flatness of 0.001 inch. A typical value for field homogeneity with an air gap of $\frac{1}{8}$ in and field strength of 2.4×10^5 A/m (3,000 gauss) is 1 part in 10^6 over a volume of 0.1 ml. The magnet is therefore suitable for use in a low resolution nuclear magnetic resonance spectrometer or an X-band electron spin resonance spectrometer. An all solid-state power supply has been designed for the 2 inch magnet, the control circuitry of which takes the form of an error activated loop system. Feedback in this circuit compensates for variations in both load resistance and supply voltage such that a 100% change in load will result in only a small percentage change in magnet current. Scientifica & Cook Electronics Ltd., 148, St. Dunstan's Avenue, Acton, London, W.3.

WW 317 for further details

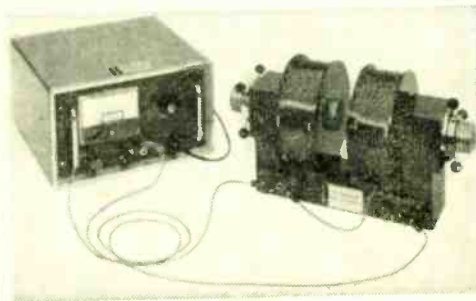

Low Frequency Measuring System

THE PHILIPS low frequency measurement system consists of a compatible family of solid state generators, amplifiers, attenuators and other equipment designed to meet new needs of measurement. The first six instruments in the range are now in quantity production and a further six are already planned and in the design stage. Others are envisaged for the future. Each instrument is self-contained and can be used singly or in combination with others in the system. Complete test sets can be assembled in minutes for special purposes and dismantled when no longer required and the individual units put to other work. A valuable feature of the system is the extension of the frequency range at both ends of the spectrum well beyond the ordinary concept of low frequency, the new frequency range extending from 0.0005 Hz to 1 MHz. This considerably increases possible applications and widens the appeal of the equipment. Typical applications include frequency amplitude response, gain measurement, gain response, gain response of attenuators and filters, two-tone tests, transmission tests, servo and process control measurement, medical electronics and education. Instruments now available include Type PM 5160 wide-band oscillator covering the range 1 Hz to 1 MHz. Features include capacitance tuning giving high resolution and a buffer amplifier to isolate the oscillator from the load. Type PM 5168 function generator is a function generator with some

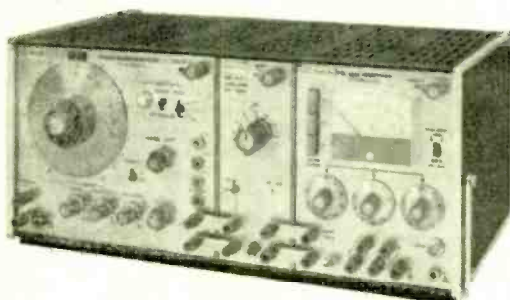


unique features. Simultaneous outputs give sine, triangular and square wave-form signals at a fixed amplitude. One of these waveforms is also available simultaneously from a fourth output but with adjustable amplitude and d.c. shift. A "hold" facility enables all waveforms to be held static at will. A mark/space ratio switch effectively provides ramp facilities. Single shot and external trigger facilities add to the versatility of the instrument. Frequency coverage is from 0.0005 Hz to 5 Hz. Like the PM 5168 function generator, this instrument also has sine, triangular and square wave outputs but the PM 5162 has an internal oscillator which can be switched on to three different sweeping ratios. Both the sweep frequency and sweep width are adjustable up to a maximum of 1:10,000. Additional features are single cycle sweep, external frequency modulation, and a frequency analogue output. The latter facility provides an output voltage proportional to the logarithm of the frequency. M.E.L. Equipment Co. Ltd., Manor Royal, Crawley, Sussex.

WW 318 for further details

Paper Tape Reader

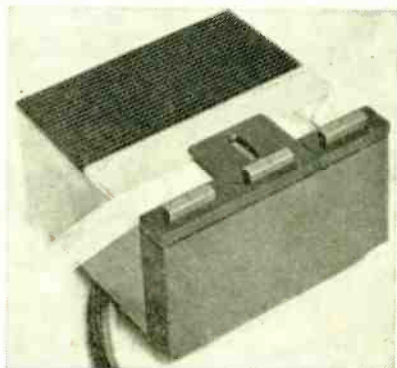PAPER tape reader GNT 24, made in Denmark, is a motor-driven reader that



can accept 5, 6, 7 or 8 channel tape or edge punched cards. Tape/card transportation is accomplished with a feed rake rather than the conventional sprocket wheel, and the equipment will read at up to 50 characters/sec step-by-step or 70 characters/sec continuous running. Sensing is mechanical and the motion of sensing pins is transferred to set reed switches in a contact unit. The switches remain set until the next reading action takes place. The dimensions of the reader are 6½ in × 6½ in × 3½ in and it is normally supplied as a free standing unit. A panel mounting version and spooling facilities will be available soon. Great Northern Telegraph Works, 5 St. Helen's Place, London, E.C.3.

WW 319 for further details

THYRISTOR-DIODE KIT

A THYRISTOR-diode kit has been introduced by International Rectifier, Hurst Green, Oxted, Surrey. The new kit is complementary to the IR zener "40 Plus" Semiconductor Kit which was designed for the circuit designer, development engineer and laboratory technician. The new kit provides all the semiconductor components required to set up single-phase and three-phase circuits for use in such applications as motor speed control, solid state switching, voltage control, temperature control, controlled battery chargers, light dimmers and flashers. The kit costs £12 and includes a design handbook, a thyristor slide-rule calculator, a selection of useful circuits, 15 thyristors and diodes with p.i.v. ratings from 50 V to 800 V and current ratings of 600 mA to 8 A, and a 2N2160 unijunction transistor. International Rectifier, Hurst Green, Oxted, Surrey.

WW 320 for further details

Optical Increment Encoder

OPTICAL increment encoders by Moore Reed Ltd., are housed in a 3.062 in diameter frame. The electrical output consists of 1,000 on-off square waves for one shaft revolution. A second output, of the same resolution but displaced relative to the first by a quarter cycle, provides means of direction sensing. Complement signals of both outputs are also provided to facilitate doubling the number of cycles by means of an exclusive OR gate. Thus 4,000 "edges" per shaft revolution can be realised. A fast rise time of under 2 μs can be obtained and thus the square wave can be maintained from effectively zero (shaft speed) up to 6,000 r.p.m. (100 kHz) with little change in mark/space ratio. A marker pulse occurring once per shaft revolution is also provided. Two additional outputs give "lamp healthy" or "lamp failed" signals. Long lamp life is achieved by a factory soak test to eliminate early mortalities, and under-running the lamp by 20% to 30% of its capacity. An additional feature is an easily interchangeable lamp and lens assembly. The amplification, squaring and buffer circuits are self-contained. Accurate control of shaft and spigot dimensions, shaft run-out and squareness, enables the encoder to be used where high precision is needed in the relationship between pulse output and shaft rotation. Moore Reed & Co. Ltd., Walworth, Andover, Hants.

WW 321 for further details


DOUBLE BALANCED MIXERS

BROADBAND double-balanced mixers from Hewlett-Packard are housed in a compact package (1.63×0.70×0.43 in) for mounting directly on printed circuit boards or in strip-line circuits. The 10514B, retains the characteristics of the 10514A but is in a more compact package, and is offered at a lower price. The frequency range of the 10514B is 0.2 to 5000 MHz at the local oscillator and signal ports; the third port is d.c. coupled. The frequency range of the 10534A, with BNC connectors, and the companion printed-circuit mounting Model 10534B, is 50 kHz to 150 MHz. As suppressed carrier modulators deriving sum and difference products of two input frequencies, the double-balanced mixers serve either as up-converters or down-converters with appropriate band filtering at the output. D.C. coupling at the X port enables them to serve also as phase detectors. Conversely, the X-port can be used as the input for a signal that modulates a signal applied to either of the other ports. These broadband, untuned mixers are thus useful as pulse modulators, capable of high carrier suppression between pulses, as current-controlled attenuators, as a.m. modulators, and also as spectrum or comb generators. Of particular importance, the i.f. noise specified for all the HP mixers is claimed to be very low (less than 0.1 μ V per root cycle at an output frequency of 10 Hz). Mixer conversion loss (single sideband) of the 0.2–500 MHz Model 10514B is less than 9 dB over the full input frequency range, and less than 7 dB, typically 6 dB, in a frequency range of 0.5 to 50 MHz. Mixer conversion loss of the 0.05–150 MHz Models 10534A and 10534B is less than 6.5 dB, between 0.2 and 35 MHz, and less than 8 dB throughout the rest of the range. Other performance data and comprehensive specifications for these mixers are given over a wide environmental range. By the use of hot-carrier diodes in the diode-bridge modulator circuit, these double-balanced mixers have high carrier suppression. Intermodulation products are also exceptionally low. All of the double-balanced mixers are designed for and specified in 50 Ω systems. Prices of the double-balanced mixer family for single unit purchases are Model 10514B 0.2 to 500 MHz PC mixer £57; Model 10514A 0.2 to 500 MHz BNC mixer £69; Model 10534B 50 kHz to 150 MHz PC mixer £23; and Model 10534A 50 kHz to 150 MHz BNC mixer £29; Hewlett Packard Ltd., 224 Bath Road, Slough, Bucks.

WW 322 for further details

Bi-directional Counter

A BI-DIRECTIONAL solid-state pulse counter (by A & R Design Ltd.) has a six-digit wide-angle view neon indicator display and direction sign, and is available either enclosed (as illustrated in photograph) or in open form for standard 19in rack mounting. Designed primarily for use with optical gratings using the moiré fringe effect for either linear or radial position indication, these counters can be driven by other transducers or signals. Driven by an optical grating transducer of sufficient accuracy, the counter can read position to within 1 μ m (0.00004in) linear or within 30sec of arc radially. Alternatively, the counter can be driven by any sine or square wave or pulse input at speeds up to 100 kHz, and because of its bi-directional nature if 2 inputs are employed that are 90° out of phase the direction of the count can be reversed by changing the phasing of the inputs, giving true bi-directional counting. The standard counter is fitted with a sign change at zero and the direction of the count is also reversed at zero, giving a true zero with upward count in either direction with sign change clearly indicating direction of count. The counter can be supplied with transducers and can also be supplied with predetermining counters, for sequence operations; with print-out units recording individual and total counts, for measuring, inspection or statistical analysis; and with automatic zeroing and remote control and print-

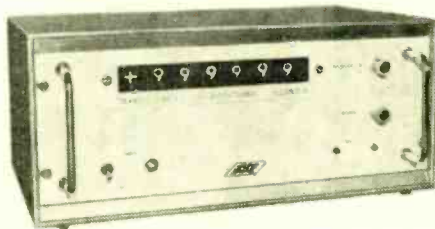

out facilities. Power supply 200/250 V 50Hz, 110V, 60Hz, or 24V d.c. to special order. A & R Designs Ltd., 1 Vineyards, Bath, Somerset.

WW 323 for further details

Driver Transistor

A SILICON planar transistor, type BSW70, by Mullard, is primarily intended for driving cold-cathode numerical indicator tubes. It has a V_{CE0} of 60 V and therefore adequately meets the "off" requirements of the number tube's cathodes—an essential condition for good visual performance. The BSW70 will become part of the company's "Practical Planar" range. Brief data is as follows:— V_{CE0max} . 100 V, V_{CEX} (at I_B 10 μ A, 25°C) 75 V, V_{CEsat} (at I_C 2mA) 0.5 V, h_{FE} (at I_C 2mA, V_{CE} 5 V) 50 min. P_{tot} continuous is 250 mW. Encapsulation TO-18. Mullard Ltd., Mullard House, Torrington Place, London, W.C.1.

WW 324 for further details

White Noise Test Set

THE Marconi Instruments white noise test set is an equipment used in the measurement of noise interference in wideband telecommunications systems. The test set comprises a noise generator, with bandwidth extending from below 12 kHz to above 12.388 MHz, and the noise receiver. The latter, connected to the receiving end of the link system, is switch-tuned to the centre frequency of a quiet test channel, and the noise breakthrough into the quiet channel is measured in terms of relative or absolute power. It is fitted with

an internal standardising noise source, so that its sensitivity can be set up independently from the noise generator. This feature is necessary when the receiver is to be used for out-of-band testing, utilizing the traffic as the noise source. A pW scale has been added to the attenuator calibration to facilitate measurement in terms of absolute power per unit bandwidth. Provision is made for adjusting the sensitivity on each reception channel independently, so that the sensitivity of the receiver can be equalised over its working range.


The price of the TF 2092A noise receiver is £415. The price of the OA 2090A white noise test set comprising the noise generator and receiver is £787. Marconi Instruments Ltd., St. Albans, Hertfordshire, England.

WW 325 for further details



Adjustable Loudspeaker

TO enable adjustments to be made for specific acoustic conditions desirable in recording, broadcasting and television studios, the Tannoy Monitor Gold speaker has a panel accommodating the treble roll-off and treble energy controls. The roll-off control permits extreme treble response to be attenuated while the energy control reduces the treble response from the cross-over point upwards. Of interest to general users is that the impedance of 8Ω now available in this type of speaker (dual concentric) is held to within close limits making this unit particularly suitable for use with solid-state amplifiers. The mass of the l.f. diaphragm assembly has been increased in order that the bass response will be better maintained in smaller enclosures. The 15 in unit h.f. diaphragm has been modified to use a lighter voice coil yielding an improvement in high frequency response. The crossover has been modified on the three units in this range, the "15,"

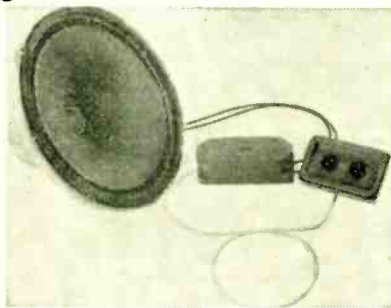

"12" and "IILZ," resulting in reduced intermodulation and smoother response. The frequency response, power handling capacity and cross-over frequencies for the "15," "12" and "IILZ" are respectively, 23 Hz to 20 kHz; 25 Hz to 20 kHz; 27 Hz to 20 kHz; 50 W, 30 W, 15 W; 1 kHz; 1 kHz; 1.2 kHz. Tannoy Products Ltd., West Norwood, London, S.E.27.


WW 326 for further details

Variable Power Supply

VARIABLE power supply Type 300 incorporates regulation and control circuits. The unit has been evolved to cater for educational, laboratory, test, circuit development, production and component evaluation applications. Voltage and current output monitoring is effected by a 2% dual scale (volt/ammeter) with a clearly calibrated continuously variable voltage control spanning from true zero to 25 V with a setting resolution of 0.2%. To ensure an interference-free supply of regulated power under the worst conditions of supply line or load change, spurious transients are held to less than 250 mV while transient recovery time does not exceed 10 μ s. The unit is protected against possible semiconductor and capacitor breakdown should a reverse polarity voltage be applied. Further safety provisions include automatic current limiting and a "short-circuit proof" facility, with automatic "reset." As load and line regulation is typically

held to within 0.1% and ripple and noise do not exceed 1 mV peak to peak, the unit meets the requirements of most sophisticated applications. Because of its ambient temperature operating range (0-50°C), initial "turn on" drift is kept to a minimum and can be ignored for most practical purposes. This unit can be used singly or stacked in parallel or in series to meet higher voltage or multirail requirements. The output is 0 to 24 V d.c. 0.5 A from the following inputs: 105-125 V or 200-250 V a.c. 50/60 Hz. Weir Electronics Ltd., Durban Road, Bognor Regis, Sussex.

WW 327 for further details

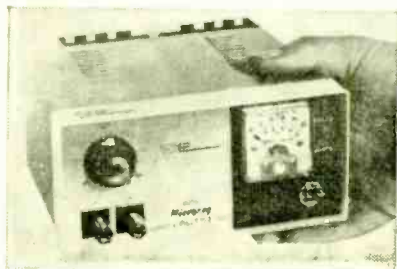

716

D.C. Transducer

SOMETIMES known as a "d.c. transformer," a direct current transducer is especially applicable to the measurement of d.c. in high voltage circuits. The device operates entirely from the magnetic field resulting from the d.c. The insulated current carrying conductor that passes through an Airpax d.c. transformer serves as a half-turn d.c. signal input winding to a toroidal magnetic core. This core is excited from an a.c. supply. Interaction of the two magnetic fields produces an output signal which, after rectification and filtering in a solid-state network, is linearly proportional to the measured current. The d.c. transformer produces no loading on the current carrying circuit because of loose coupling. An internal resistance limits the excitation current. Response time of the magnetic circuit is of the order of ten milliseconds. The Airpax high sensitivity d.c. transducers produce full-scale outputs from as little as 1 mA d.c. signal levels. The transducer fully isolates the output (meter) circuit from the input (metered) circuit in a manner similar to the isolation provided by instrument transformers used in metering a.c. circuits. With the d.c. transducer, d.c. in high voltage circuits can be measured to an accuracy of $\pm 1.0\%$ of full-scale. The internal circuit is designed for continuous operation and long life. The instrument is claimed to retain its accuracy from 0°C to +50°C and with a $\pm 5\%$ variation in the 115 V a.c. supply. The excitation is 60 Hz (50 Hz available on special order). Overloads in the input current line do not damage the unit, nor do short circuits in its output circuit. Airpax Electronics, Seminole Division, P.O. Box 8488, Fort Lauderdale, Florida 33310, U.S.A.

WW 328 for further details

DIGITAL CLOCK

TIME indication by the Racal integrated circuit digital clock Type 812, is in hours, minutes and seconds. Display is through six in-line numerical indicator tubes. Timebase facilities offered include an internal standard derived from a 1 MHz crystal oscillator or 50 Hz mains power frequency. The crystal oscillator has a short-term stability of ± 1 part in 10^6 because of cyclic oven control; long term stability is typically within three minutes of nominal setting over a period of a year. The 50 Hz stability is dependent on the mains supply. Also available are external standard frequencies of 1 MHz,


100 kHz, or 1 Hz, at a level of 1 V r.m.s. Other features of this clock include a timebase failure alarm and the following controls: (1) initial time setting, (2) clock start and synchronization, (3) time adjustments during operation, and (4) zero reset; and time interval measurements (stop watch application). The electrical output of information is 4 line b.c.d. weighted 1248 code per display unit, "0" state logic. Options available are higher stability timebases (two) and an alternative power supply. Racal Instruments Ltd., Dukes Ride, Crowthorne, Berkshire.

WW 329 for further details

R Trimmer

A MINIATURE rectangular trimmer by Reliance Controls Ltd., although a discrete component, is intended for use with integrated circuits or where space is at a premium. The trimmer, Type CW50, is 0.75 in long, 0.165 in wide, 0.28 in high, and has been designed for printed circuit applications with pins on the standard 0.1 in matrix. Operating torque is 2.1 N cm (3 ozf in). The resistance range is 100 Ω to 20 k Ω . Temperature range is -65° to $+125^{\circ}$, and the power rating is 1 W at $+40^{\circ}$ C.

WW 330 for further details

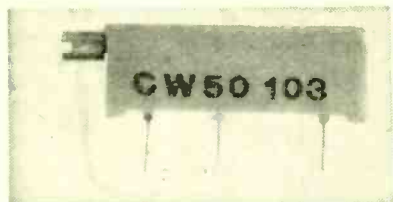

4-channel f.e.t.s

EIGHT new 4-channel f.e.t. switches, the G125F to 132F, are available in the Siliconix line of multi-channel f.e.t. switches and drivers, now available in this country from U.E.C.L. These n-channel junction devices, packaged four to a TO-84 can, are designed primarily for switching applications; however, they are also useful in amplifiers and voltage-controlled-resistor and constant current applications. The series offers a choice between separate or common-drain configurations, four r_{ds} , and two V_p ranges in each configuration. Maximum pinch-off voltages are 5 and 10; maximum "on" resistances are 500, 250, 90 and 45 Ω . The f.e.t.s have low I_{GSS} , 0.1 and 0.2 nA max. depending on device type, and 0.05 and 0.1 nA max $I_{D(ON)}$ and $I_{S(ON)}$. N-channel junction f.e.t.s provide several advantages; very low "on" resistance per unit capacitance, trade-off between V_p and $r_{ds(on)}$ to lessen the drive swing requirement and low leakage. On special order, Siliconix will package any of its junction f.e.t.s in a flat package. Ultra Electronics (Components) Ltd., Microelectronics Division, 35-37 Park Royal Road, London, N.W.10.

WW 331 for further details



WIRELESS WORLD, FEBRUARY 1968




THE HOUSE OF BULGIN
AT YOUR SERVICE

A SMALL SELECTION FROM OUR RANGE OF OVER 300 MOULDED INSULATION SWITCHES


An ever-increasing range of superior quality Miniature Switches, produced from the finest materials available, by fully automatic processes with constant testing to ensure the highest degree of reliability and finish. Fine Silver Contacts.

Single Pole models are available either Change-Over rated 250V. 2A \sim or Make-Break rated 250V. 3A \sim . Double Pole models are basically Change-Over, rated 250V. 2A \sim and easily wired to give Make-Break contacting.


SINGLE POLE RANGE

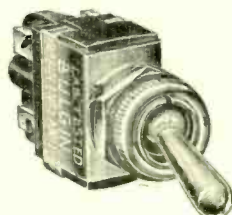


List No. S.M.265/PD
Toggle Operated

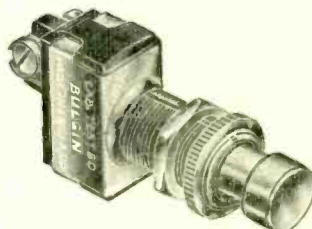

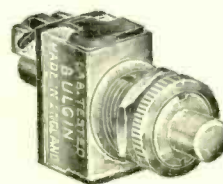
List No. S.R.M.259/TERM
Successional Push Action




List No. S.M.357
Biased Push Action

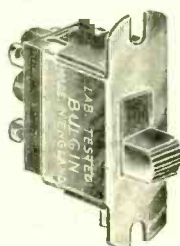

List No. S.M.593
Slide Operated

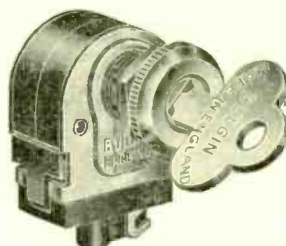


List No. S.M.319
Key Operated

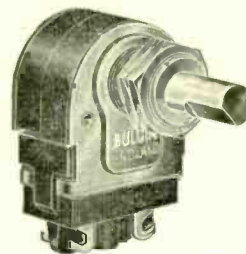


List No. S.M.254
Semi-Rotary Shaft


DOUBLE POLE RANGE

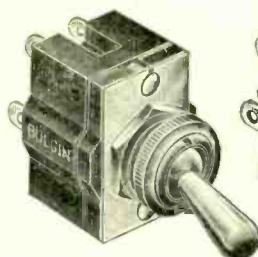

List No. S.M.270/PD
Toggle Operated

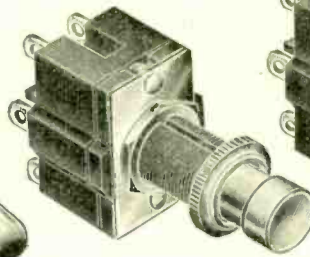

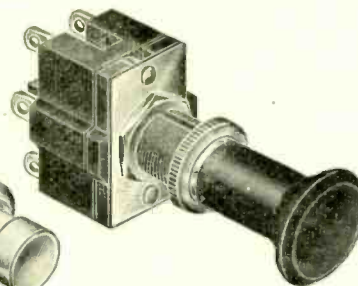List No. S.R.M.270
Successional Push Action



List No. S.M.446
Push Pull Operated

For full details send for leaflet IS09/C free on request.

A. F. BULGIN & CO. LTD.,
Bye Pass Rd., Barking, Essex.
Tel: RIPPleway 5588 (12 lines)

MANUFACTURERS AND SUPPLIERS OF RADIO
AND ELECTRONIC COMPONENTS TO

ADMIRALTY	MINISTRY OF WORKS	B.S.C.
WAR OFFICE	MINISTRY OF AVIATION	G.P.O.
AIR MINISTRY	MINISTRY OF SUPPLY	I.T.A.
HOME OFFICE	RESEARCH ESTABLISHMENTS	N.P.L.
CROWN AGENTS	U.K.A.A.	D.S.I.R.

FEBRUARY MEETINGS

Tickets are required for some meetings: readers are advised, therefore, to communicate with the society concerned

LONDON

1st. I.E.R.E.—“Satellite communication systems and the diverse engineering techniques which they require” by C. F. Davidson at 6.0 at 8-9 Bedford Sq., W.C.1.

2nd. I.E.E.—Colloquium on “MOSTS for analogue switching” at 2.30 at Savoy Pl., W.C.2.

5th. I.E.E.—“Future trends in the design of subscribers' telephone instruments” by F. E. Williams, F. A. Wilson and K. A. T. Knox at 5.30 at Savoy Pl., W.C.2.

6th. I.E.E. & R.Ae.S.—“Automatic landing of aircraft—control techniques in all-weather aircraft operations” by K. Smith at 5.30 at Savoy Pl., W.C.2.

7th. I.E.E.—“A new electrostatically focused and deflected vidicon” by Dr. H. G. Lubszynski, N. Barford, Dr. B. Mayo and J. Wardley and “Beam separation and low-noise read-out in isocons” by P. C. Ruggles, Dr. N. A. Slark, D. P. Mouser and P. H. Batev at 5.30 at Savoy Pl., W.C.2.

7th. I.E.R.E. & I.E.E.—Colloquium on “Fluid logic in peripheral equipment for computers” at 6.0 at the London School of Hygiene and Tropical Medicine, Keppel St., W.C.1.

8th. I.E.E.—“A system for transmission and display of weather information” by R. H. D. Hardy at 5.30 at Savoy Pl., W.C.2.

8th. Inst. Electronics.—“Measurement and control in the wire and cable industry” by P. Baxter at 6.45 at the School of Hygiene & Tropical Medicine, Keppel St., W.C.1.

9th. I.E.E.—“Evanescence mode filters” by G. F. Craven at 5.30 at Savoy Pl., W.C.2.

9th. R.T.S.—“A comparison of wired and wireless broadcasting for the future” by R. P. Gabriel at 7.0 at I.T.A., 70 Brompton Rd., S.W.3.

13th. I.E.R.E.—“The MOST integrated circuit” by P. Cooke at 6.0 at 8-9 Bedford Sq., W.C.1.

14th. I.E.E.—“Stimulus or constraint? The interplay of computer design and use” by F. J. M. Laver at 5.30 at Savoy Pl., W.C.2.

15th. I.E.E.—Colloquium on “Direct digital control of systems and processes” at 2.0 at Savoy Pl., W.C.2.

16th. I.E.E.—“A position fixing aid to marine surveying” by J. K. V. Lee at 5.30 at Savoy Pl., W.C.2.

21st. I.E.R.E.—Symposium on “Integrated harbour radar systems” at 6.0 at 8-9 Bedford Sq., W.C.1.

23rd. R.T.S.—“Data presentation by visual displays” by R. A. Ward and M. H. Cufflin at 7.0 at I.T.A., 70 Brompton Rd., S.W.3.

27th. I.E.E.—Colloquium on “Developments towards a computer-based information service in physics, electrotechnology and control” at 2.30 at Savoy Pl., W.C.2.

28th. I.E.E.—“Measurement as an aid to archaeological research” by Dr. E. T. Hall at 5.30 at Savoy Pl., W.C.2.

28th. I.E.R.E.—“Ultrasonic delay lines and their uses in television” by R. Gibson and S. M. Edwardson at 6.0 at 8-9 Bedford Sq., W.C.1.

BASINGSTOKE

8th. I.E.R.E.—“High voltage pulse techniques in fusion research” by Dr. N. R. McCormick at 7.30 at the Technical College.

BIRMINGHAM

20th. R.T.S. & I.E.R.E.—“Colour is our future” by Bill Ward at 7.0 at A.T.V. Ltd.

BRIGHTON

13th. I.E.R.E.—“Radio astronomy” by J. M. H. Hill at 6.30 at College of Technology.

BRISTOL

5th. I.E.R.E. & I.E.E.—“Computer control systems for materials handling plants” by J. P. Coley and W. J. Castens at 6.0 at the University, Queens Building.

13th. R.T.S.—“Colour TV receivers—general design problems” by B. J. Rogers at 7.30 at B.B.C., Whiteladies Rd.

CAMBRIDGE

1st. I.E.R.E. & I.E.E.—“Recent developments in wideband aerials” by M. F. Radford at 8.0 at the University Engineering Laboratories, Trumpington St.

29th. I.E.R.E. & I.E.E.—“The theory of oscillators” by P. J. Baxandall at 8.0 at the University Engineering Laboratories, Trumpington St.

CARDIFF

9th. S.E.R.T.—“Field effect transistors” by E. F. Munroe at 7.30 at Llandaff Technical College, Western Ave.

14th. I.E.R.E.—“Electronic techniques in electro-physiology” by D. P. Nelligan at 6.30 at University of Wales Institute of Science and Technology.

14th. R.T.S.—“Techniques for ‘pop’ music recording” by D. Heelis at 7.30 at Broadcasting House, Llandaff.

CHESTER

14th. I.E.E.T.E.—“The laser” by Dr. P. T. Andrews at 7.0 at College of Further Education, Eaton Rd.

CHESTERFIELD

5th. S.E.R.T.—“U.H.F. reception” by B. M. Goodwin at 6.30 at College of Technology, Infirmary Rd.

COVENTRY

5th. I.E.R.E.—“Post Office towers and trunks” by J. C. Billen at 7.15 at Lanchester College of Technology, Priory St.

DUNDEE

7th. I.Prod.E.—“An introduction to integrated circuits and methods of manufacture” by J. T. Brown and C. Turner at 7.30 at Queen's Hotel, Nethergate.

EDINBURGH

13th. I.E.R.E. & I.E.E.—“The use of satellites for long-distance telecommunications” by H. Stanesby at 6.0 at Carlton Hotel, North Bridge.

23rd. S.E.R.T.—“Colour television” by J. C. Allen at 7.30 at Napier Technical College, Colinton Rd.

EVESHAM

27th. I.E.R.E.—“Slow motion video disc recording” by C. R. Webster at 7.0 at B.B.C. Club.

FARNBOROUGH

22nd. I.E.R.E.—“Electrical interference in electronic systems” by D. Harrison at 7.0 at Technical College.

GLASGOW

12th. I.E.R.E. & I.E.E.—“The use of satellites for long-distance telecommunica-

tions” by H. Stanesby at 6.0 at University of Strathclyde.

21st. I.E.E.T.E.—“Cybernetics in management” by W. A. Gay at 7.0 at University of Strathclyde, Montrose St.

GRANGEMOUTH

22nd. S.Inst.Tech.—“Gas lasers and their applications” by H. Foster at 7.0 at Leapark Hotel, Bo'ness Head.

GREENOCK

2nd. S.E.R.T.—“Colour television” by J. McMaster at 7.30 at Watt Memorial College.

HALIFAX

8th. I.E.R.E.—“Machine tool control transducers” by D. Mather at 7.0 at Percival Whitley College of Further Education, Department of Engineering, Francis St.

HORNCHURCH

20th. S.E.R.T.—“Automatic landing systems” by F. J. Sullings at 7.0 at Haverling Technical College, 42 Ardsleigh Green Road.

LINCOLN

6th. S.E.R.T. “U.H.F. reception” by B. M. Goodwin at 7.30 at Technical College, Cathedral St.

LIVERPOOL

21st. I.E.R.E.—“Electronic standards conversion” by D. Stebbings at 7.0 at Regional College of Technology, Byrom St.

LOUGHBOROUGH

20th. I.E.R.E. & I.E.E. “The 57 effects of electric current” by Dr. G. S. Brosan at 6.30 at University of Technology.

MANCHESTER

22nd. C.E.I.—“Our present knowledge of the universe” by Sir Bernard Lovell at 6.30 at Renold Building, Manchester College of Science and Technology, Altrincham St.

NEWCASTLE-UPON-TYNE

7th. S.E.R.T.—“Interference” by T. Boast at 7.15 at Charles Trevelyan Technical College, Maple Terrace.

14th. I.E.R.E.—“Automatic landing—some design aspects of high integrity autopilots” by R. Bishop at 6.0 at Institute of Mining and Mechanical Engineers, Neville Hall, Westgate Rd.

22nd. S.Inst.Tech. — “Integrated circuits” by W. L. Clough at 7.0 at the Rutherford College of Technology.

OLDHAM

8th. S.E.R.T.—“Stereo broadcasting” at 8.0 at The Technical College.

PLYMOUTH

20th. I.E.E., I.E.R.E. & R.T.S.—“Concorde electronics” by H. Hill at 7.0 at College of Technology.

READING

13th. I.E.R.E.—“On-line control” by Dr. R. C. Butchart at 7.30 at J. J. Thomson Physical Laboratory, The University.


STOKE-ON-TRENT

16th. S.E.R.T.—“Sony video tape recorders” at 7.30 at North Staffs College of Technology, College Road.

WAKEFIELD

29th. I.E.E.T.E.—“The application of thyristors in industry” by E. J. Pepper at 7.0 at Adult Education Centre, Queen Street.

When is an Avo meter not an Avometer?

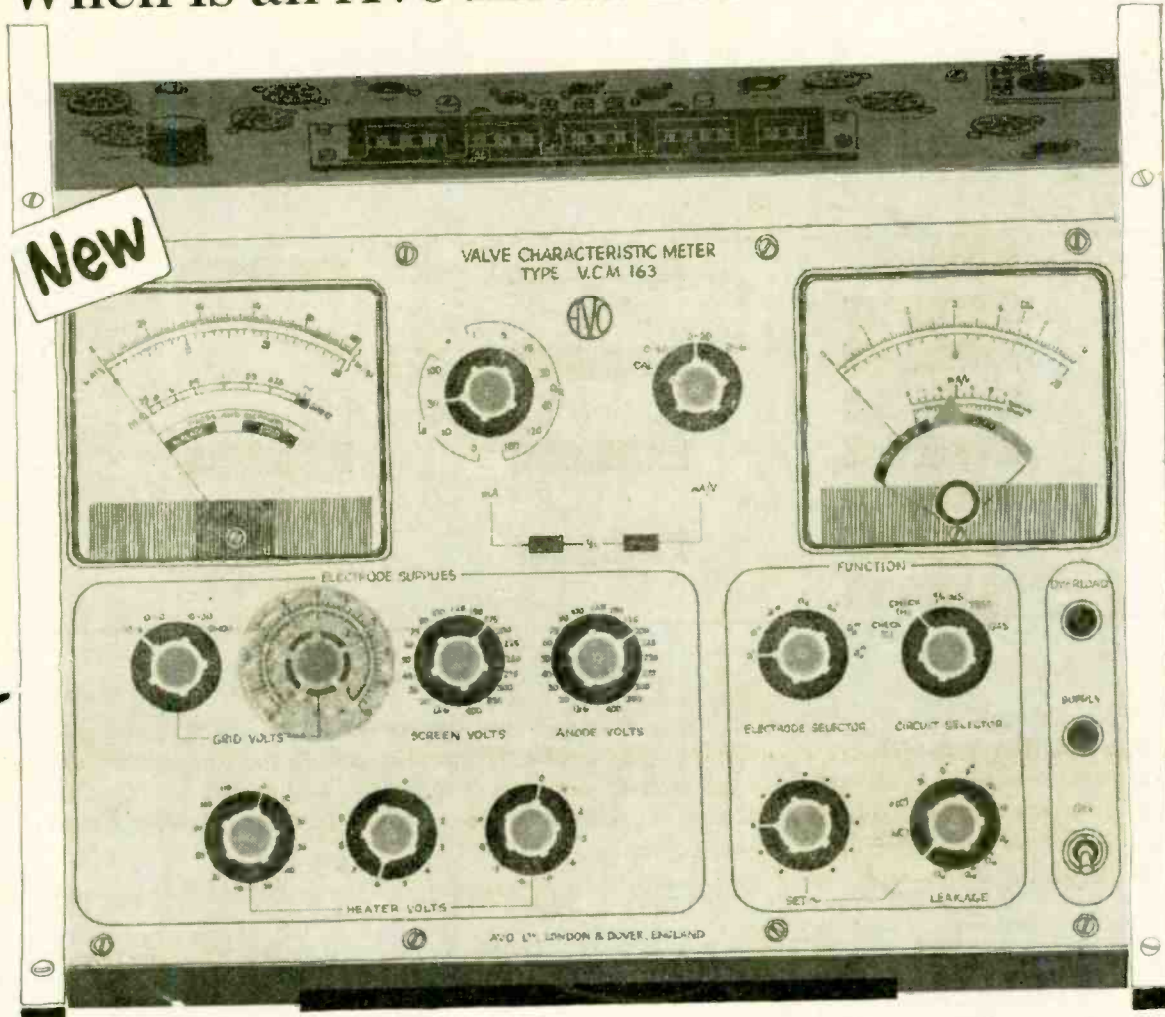

When it tests nuvistors, compactrons & 13-pin valves

The new Avo VCM163 Valve Characteristic Meter is one of the most versatile valve testers ever developed. With facilities for testing valves with as many as 13 pin connections (and 2 top caps), plus recently introduced types such as nuvistors and compactrons, the VCM163 provides both rapid fault diagnosis and comprehensive static/dynamic characteristics data. Nevertheless, it is even simpler to use than previous models - no backing-off is required. A separate meter displays mutual conductance values continuously during testing, and there is pushbutton monitoring of screen parameters. The full range of h.t. voltage - 12.6V to 400V - can be applied to anode and screen, heater voltage is adjustable in 0.1V steps from 0 to 119.9 and grid voltage may be varied continuously from 0 to 100V (calibrated). Get complete information about the VCM163 from your local dealer or Avo Ltd, Avocet House, Dover, Kent. Telephone Dover 2626. Telex 96283.



M GROUP


AVΩ MEANS BASIC MEASUREMENTS ALL OVER THE WORLD

WW-003 FOR FURTHER DETAILS

A

8 TRACKS

ON 1/4" TAPE

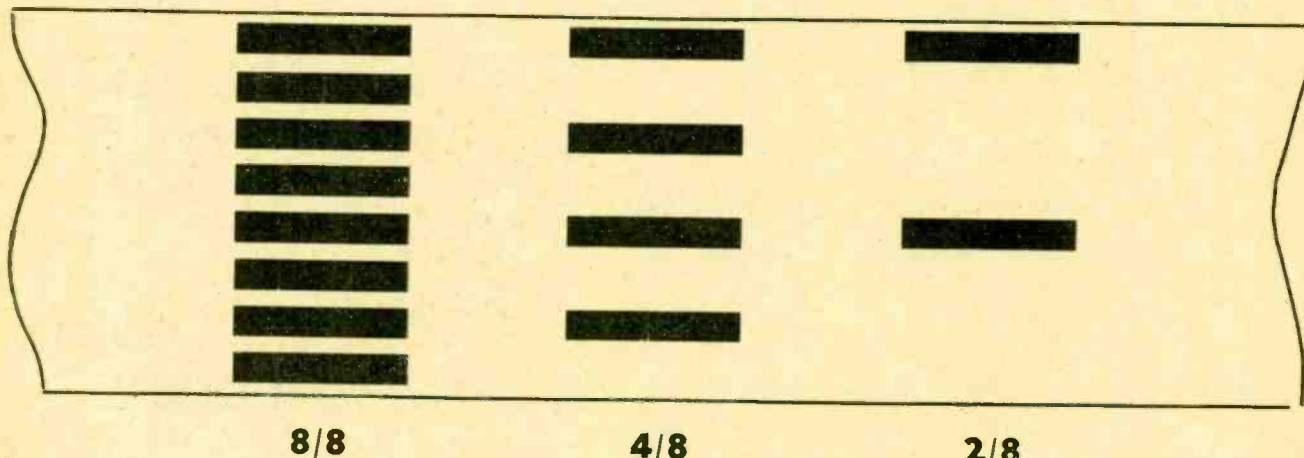

The ever-increasing application of digital techniques to data acquisition has prompted Marriott Magnetics to investigate track density in $\frac{1}{4}$ inch wide magnetic tape. The possibility of using readily available and comparatively cheap tape and tape transport mechanisms opens up new and attractive avenues of approach to many applications which hitherto have been dismissed on cost grounds. This 8/8 head is a valuable newcomer to our standard range which now includes 4/8 and 2/8 in addition to the 4/4—2/4 and 1/4 configuration.

Combination Record/Playback/Erase heads to the above configuration are available for some of the above types.

Marriott Magnetics were the very first company in the world to mass-produce miniature heads, and in 1959 Marriotts scooped the world by mass-producing a four-track head. Well over 5 million heads have been sold since then, and it is the company's firm intention to continue leading the world in the design and manufacture of Magnetic Recording Heads.

RESEARCH AND DEVELOPMENT

Marriott Magnetics' research and development activities are directed towards continuously improving the mechanical and electrical characteristics of their heads through the use of many new ideas, engineering approaches and manufacturing techniques. Much research and development effort is applied to the development of heads with unique configurations for many special and unusual instrumentation applications. A highly efficient pre-production group works closely with research and development to provide a fast service of prototypes, small quantity production and special heads.

MANUFACTURING

Marriott Magnetics maintain a complete facility; fully equipped with the machines, tools, optical equipment and electronic test instruments for mass production of precision heads. Machinery, assembly, test and inspection operations are performed by operators experienced in close tolerance and precision assembly work.

Material handling methods are used to permit cost reduction and quick delivery of Standard Heads. Assembly, test and inspection procedures are carried out under most controlled conditions.

ENGINEERING

Marriott Magnetics' engineering staff has extensive experience in application of design, manufacturing and test techniques to head production problems, and taking a new design through the prototype stage to quantity manufacture. The ability to analyse and to provide answers quickly to engineering problems peculiar to precision heads results in a quality product with superior operational characteristics and very uniform production runs.

QUALITY CONTROL

Continuous piece part inspection and evaluation of each Sub-Assembly are the two basic points of Marriott Magnetics' quality control system. Incoming materials and parts are closely inspected to ensure that mechanical and electrical specifications are met. All completed heads are vigorously inspected and performance tested to ensure complete customer satisfaction.

MARRIOTT MAGNETICS LTD.

WATERSIDE WORKS


PONSHARDEN

PENRYN

CORNWALL

Telephone: Penryn 3591-3363

WW—004 FOR FURTHER DETAILS

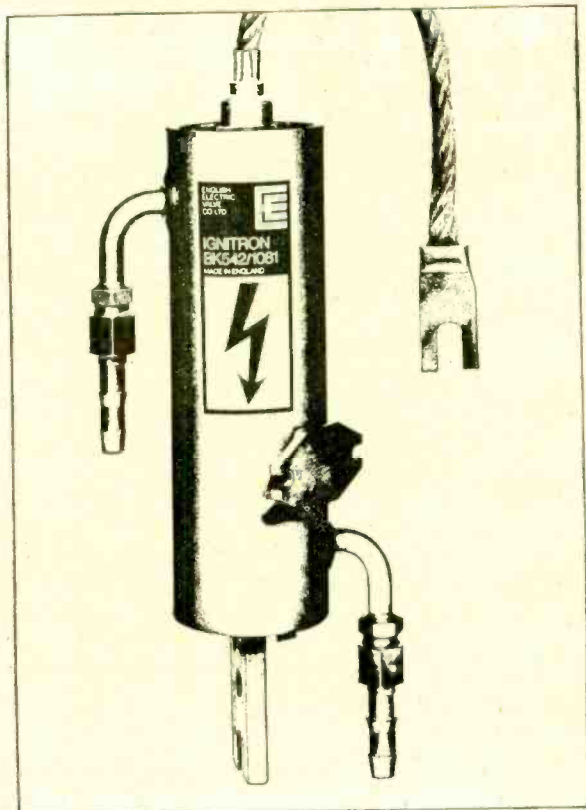

This looks like a 'B' size Ignitron

but it controls 65% MORE POWER and saves money

The new EEV Mini 'C' Ignitron

It's well-known that 'B' and 'C' Ignitrons are often used for applications which call for something in between. You can either overwork a 'B' or underwork a 'C'. Whatever you do wastes money. To cut out this waste EEV has developed a new Mini 'C' Ignitron which has a standard international 'B' size envelope, but can handle 65% more KVA than the 'B' size. The new tube has a number of advantages. Take-over voltage is low to minimise misfiring at low current conditions, which in turn increases ignitor life. When used in place of a standard 'B' size ignitron, you will find that the Mini 'C' lasts nearly twice as long. The cooling water is in direct contact with the vacuum envelope, and the inlet

has been streamlined for better water flow. This adds up to better cooling, especially at hot spots, and reduced clogging by sediment. Both water connections are of the quick release type. Plastic coating is optional. The Mini 'C' fits standard 'B' size sockets, so that you can use it to uprate existing equipment to provide new intermediate types. Makers of welding equipment will see in the Mini 'C' a means of extending their range, as there is no need for a new socket size calling for radical design changes. Use the Mini 'C' in place of an overworked 'B' size for longer life, or to replace an underworked 'C' size for lower running costs. In both cases it will save you money.

EEV's new Mini 'C' Ignitron is available from stockists throughout the country.

Coventry Factors Ltd, Coronet House, Upper Well Street

Downes & Davles Ltd, G.P.O. Box 555, 72 Chapeltown Street

Edmundson Electronics Ltd, 60-74 Market Parade, Rye Lane, Peckham

Gothic Electrical Supplies Ltd, Gothic House, Henrietta Street

Harper Robertson Electronics Ltd, 97 St George's Road

Smith & Cookson Ltd, 49-57 Bridgewater Street

The Needham Engineering Co. Ltd, P.O. Box 23, Townhead Street

Wireless Electric Ltd, Wirelect House, St Thomas Street

Coventry Tel: Coventry 21051

Manchester 1 Tel: Ardwick 5292

London SE15 Tel: New Cross 9731


Birmingham 19 Tel: Central 5060

Glasgow C3 Tel: Douglas 2711

Liverpool 1 Tel: Royal 3154-7

Sheffield 1 Tel: Sheffield 27161

Bristol 1 Tel: Bristol 294313

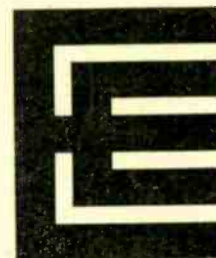

ENGLISH ELECTRIC VALVE COMPANY LIMITED CARHOLME ROAD, LINCOLN. TELEPHONE: 26352
 WW-005 FOR FURTHER DETAILS AP329

Let cathodeon provide you with a megacycle escort


(... anything from 1-140 motorcycles)

We at Cathodeon are very happy to sit back in our swivel chairs and let your orders for crystals drop into the mailbox day after day. It's a great life and doubtless has everything to do with our reputation for a first-class product and reliable delivery. But we know that, on occasion, you would also welcome some assistance in determining the optimum crystal specification for a new or unfamiliar application. That's where you can call on us again! If you're heading into strange territory, chances are Cathodeon have already mapped out the route and we'll gladly provide a megacycle escort to keep you on the right road.

Got the drift? Better 'phone Cathodeon now!—or write to the megacycle factory, Cathodeon Crystals Ltd., Linton, Cambridgeshire. Telephone: Linton 501. Telex: 81212. Cables: 'Quartz' Cambridge.


cathodeon

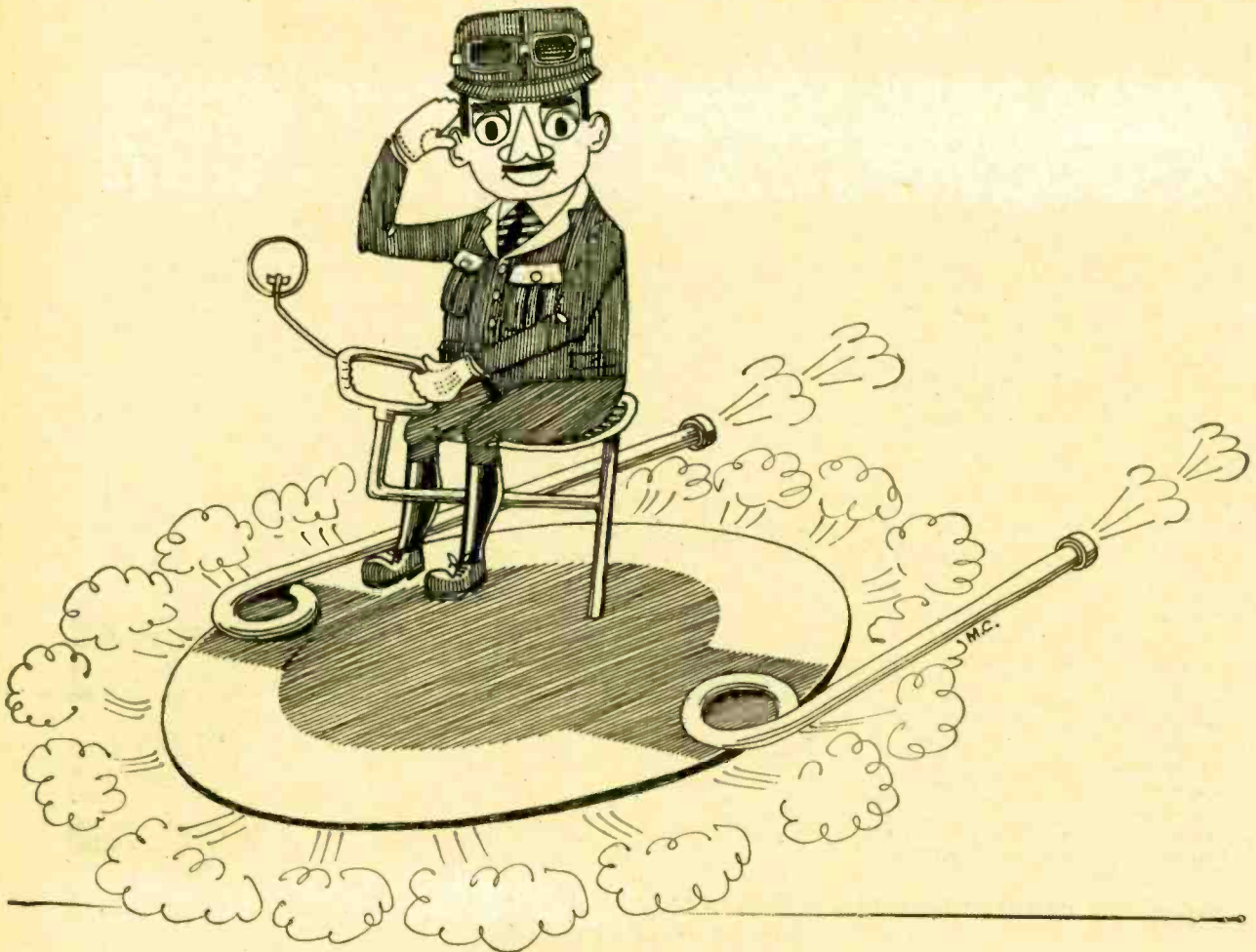QUARTZ CRYSTALS · CRYSTAL FILTERS · CRYSTAL OVENS



WW-006 FOR FURTHER DETAILS

Mercury Vapour Rectifiers

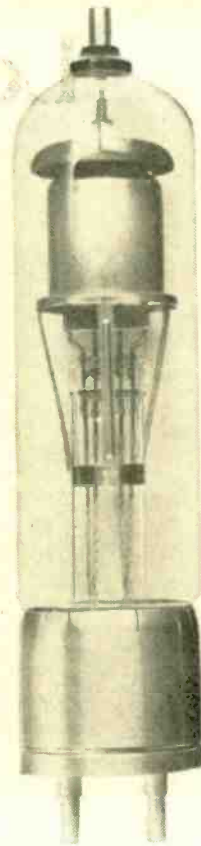

DATA

Type	Service type	Peak inverse voltage max. (kV)	Peak anode current max. (A)	Mean anode current max. (A)	Max. d.c. output 3-phase full wave	
					Voltage (kV)	Current (A)
869B	—	20.0	10.0	2.5	19.0	7.5
AH200	—	20.0	10.0	2.5	19.0	7.5
AH205/ 857B	CV2673	22.0	40.0	10.0	21.0	30.0
AH211A	CV532	16.0	8.0	2.0	15.2	6.0
AH221	CV5 CV1435	20.0	5.0	1.25	19.0	3.75
AH238	CV1629	13.0	5.0	1.25	12.4	3.75
BD10	—	1.0	25.0	8.0	0.95	24.0
BD12*	—	1.0	2 x 50	2 x 16.5	0.95	49.5


*Full wave rectifier.

This range of Mercury Vapour Rectifiers is available from your local EEV stockist. English Electric Valves production methods ensure the reliability and performance you are looking for and prices are competitive.

Coventry Factors Ltd, Coronet House, Upper Well Street	Coventry Tel: Coventry 21051
Downes & Davies Ltd, G.P.O. Box 555, 72 Chapelton Street	Manchester 1 Tel: Ardwick 5292
Edmundson Electronics Ltd, 60-74 Market Parade, Rye Lane, Peckham	London SE15 Tel: New Cross 9731
Gothic Electrical Supplies Ltd, Gothic House, Henrietta Street	Birmingham 19 Tel: Central 5060
Harper Robertson Electronics Ltd, 97 St George's Road	Glasgow C3 Tel: Douglas 2711
Smith & Cookson Ltd, 49/57 Bridgewater Street	Liverpool 1 Tel: Royal 3154-7
The Needham Engineering Co. Ltd, P.O. Box 23, Townhead Street	Sheffield 1 Tel: Sheffield 27161
Wireless Electric Ltd, Wirelect House, St Thomas Street	Bristol 1 Tel: Bristol 294313



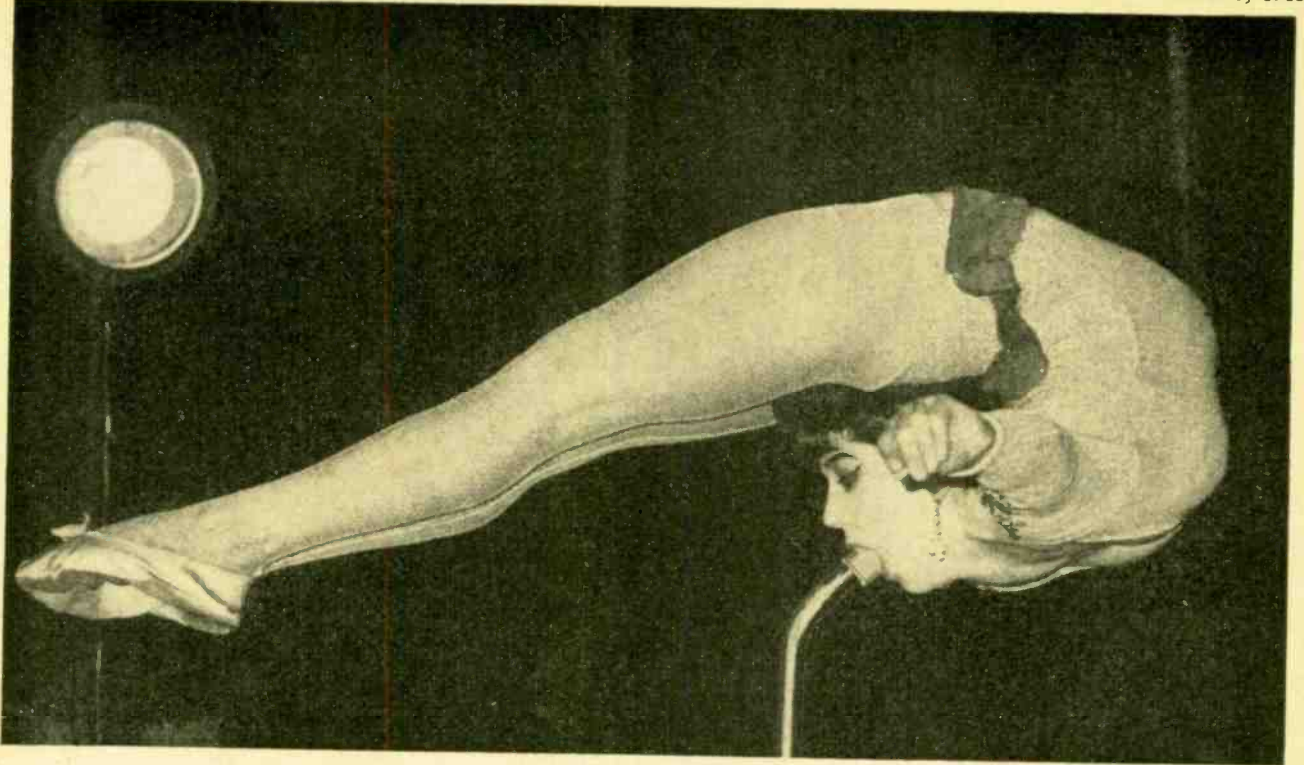ENGLISH ELECTRIC VALVE COMPANY LIMITED CARHOLME ROAD, LINCOLN, TELEPHONE: 26352
 WW-007 FOR FURTHER DETAILS



we are also a very flexible lot at Silentbloc

and when we get
the bit between our teeth
there's no letting go
until we have the solution to your
transmission, shock, vibration
or what-have-you problem.
There is usually more than one way
to approach the answer
and that is where
Silentbloc mental flexibility comes in—
our design team
will bend over backwards
to make sure it's the best possible,
not only functionally but cost-wise too.
The spotlight is on Silentbloc
mountings, couplings, bearings,
ball joints, link assemblies and
every kind of vibration-damping device.

SILENTBLOC


SILENTBLOC LIMITED • MANOR ROYAL • CRAWLEY • SUSSEX
Telephone: Crawley 27733 Telegrams: Silentbloc Crawley Telex: 87177

Andre Rubber Co. Ltd. is another Silentbloc Company. Silentbloc products are also manufactured by Silentbloc (Australia) Pty. Ltd. Melbourne.

WW—008 FOR FURTHER DETAILS

Broadway S/701

Voltage Stabilisers

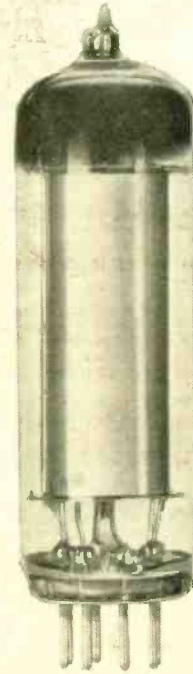

DATA

Type	Service type	Operating voltage approx. (V)	Striking voltage (V)		Tube current range (mA)	Regulation max. (V)	Base
			○	●			
OA2	CV1832	150	185	225	5-30	6.0	B7G
OA2WA‡	CV4020	150	165	225	5-30	5.0	B7G
OB2	CV1833	108	133	210	5-30	3.5	B7G
OB2WA‡	CV4028	108	133	210	5-30	3.0	B7G
OC2	CV8766	75	115	145	5-30	4.5	B7G
QS75/20	CV284†	75	110	160	2-20	6.0	B7G
QS75/60	CV434	75	117	—	5-60	5.0	B8G
QS92/10	CV188††	92	140	—	1-10	5.0	Br.4-pin
QS95/10	CV286	95	110	—	2-10	5.0	B7G
QS108/45	CV422	108	120	—	5-45	5.0	B8G
QS150/15	CV287	150	170	—	2-15	5.0	B7G
QS150/45	CV395	150	170	—	5-45	5.0	B8G
QS1202‡	CV4052	108	133	210	2-15	3.0	B7G/F
QS1203‡	CV4053	150	180	225	2-15	4.5	B7G/F
QS1215	CV5173	90	115	115	1-40	8.0	B7G

‡ A rugged and reliable type ○ In normal lighting ● In total darkness †† Also CV1070 (operating voltage 100V) † Also CV5083 (operating voltage 70V)

This range of cold cathode Voltage Stabilisers is available from your local EEV stockist. English Electric Valves production methods ensure the reliability and performance you are looking for and prices are competitive.

Coventry Factors Ltd, Coronet House, Upper Well Street	Coventry Tel: Coventry 21051
Downes & Davies Ltd, G.P.O. Box 555, 72 Chapelton Street	Manchester 1 Tel: Ardwick 5292
Edmundson Electronics Ltd, 60-74 Market Parade, Rye Lane, Peckham	London SE15 Tel: New Cross 9731
Gothic Electrical Supplies Ltd, Gothic House, Henrietta Street	Birmingham 19 Tel: Central 5060
Harper Robertson Electronics Ltd, 97 St George's Road	Glasgow C3 Tel: Douglas 2711
Smith & Cookson Ltd, 49/57 Bridgewater Street	Liverpool 1 Tel: Royal 3154-7
The Needham Engineering Co. Ltd, P.O. Box 23, Townhead Street	Sheffield 1 Tel: Sheffield 27161
Wireless Electric Ltd, Wiretop House, St Thomas Street	Bristol 1 Tel: Bristol 294313



ENGLISH ELECTRIC VALVE COMPANY LIMITED CARHOLME ROAD, LINCOLN, TELEPHONE: 26352
 WW-009 FOR FURTHER DETAILS

See all these models, and many more ... in the latest HEATHKIT Catalogue

NEW! 12+2W TRANSISTOR STEREO AMPLIFIER Model TSA-12

Luxury performance at lowest possible cost


Attractive low-silhouette styling in compact sizes
3 3/4" x h15 3/4" w x 10" deep.



- 17 transistors, 6 diode circuit • ± 1 dB, 16 to 50,000 c/s at 12 watts per channel into 8 ohms • Output suitable for 8 or 15 ohm loudspeakers • 3 stereo inputs for Grams, Radio and Aux. • Modern low silhouette styling • Attractive aluminium, golden anodised front panel • Handsome assembled and finished walnut veneered cabinet available • Matches Heathkit models TFM-1 and AFM-2 transistor tuners.

Kit £30.10.0 (less cabinet) Ready-to-use £42.10.0
Beautiful Walnut cabinet £25.0. extra

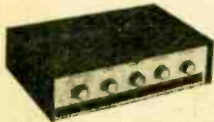LOW-COST TRANSISTOR STEREO AMPLIFIER, TS-23



Incorporates all the essential features for good quality sound reproduction from record, radio and other sources • 16 transistor, 4 diode circuit • Good frequency response • 3 watts r.m.s. (15 ohms) each channel • 6 position selector switch easily handles your record, radio or tape inputs—stereo or mono • Separate controls provide bass boost, treble cut, amplifier balance and volume • Printed circuit board construction • Compact, slimline styling • Measures 3 1/2 in. high x 13 in. wide x 8 in. deep • Beautiful walnut veneered cabinet (optional extra) • Attractive Perspex front panel.

Kit £17.15.0 (less cabinet) KIT £18.19.0 (with cabinet)
Walnut veneered cabinet £2/5/- extra.

TRANSISTOR AM-FM STEREO TUNER, AFM-2



- 18 Transistor, 7 diode circuit • AM-LW/MW, FM Stereo and FM Mono tuning • Automatic stereo indicator light • Stereo phase control for maximum separation, minimum distortion • Automatic frequency control for positive "lock-in" tuning • Automatic gain control for even, steady volume • Pre-assembled and aligned "front end" FM unit • Separate AM and FM printed circuit boards • Self-powered • Low-silhouette styling—matches AA-22U amplifier • Handsome fully finished walnut veneered cabinet, available as optional extra. Comprising: AFM-2T RF Tuning Heart kit £7/17/6 incl. P.T., AFM-2A IF Amplifier and power supply kit £24/9/6.

TOTAL PRICE KIT £32.7.0 incl. P.T.
Optional extra: Walnut veneered cabinet £2/5/- extra

TRANSISTOR FM STEREO TUNER, TFM-1S

(Mono version TFM-1M available)

- 14 transistor, 5 diode circuit for cool instant operation • Mono TFM-1M and Stereo TFM-1S models available • Automatic frequency control • Stereo phase control to maximise stereo separation, minimise distortion • 4-stage IF section ensures high sensitivity and selectivity • Filtered outputs for direct "beat-free" stereo recording • Automatic stereo indicator light • Prealigned, preassembled "front-end" tuner and one circuit board for fast, simple assembly. Cabinet £2/5/- extra. Comprising: TFM-TI RF Tuning Heart Kit, £5/16/- incl. P.T., TFMA-1M (Mono) IF Amplifier, Power supply £15/3/-. Kit or TFMA-1S (Stereo) IF Amplifier, Power supply £19/2/- Kit.



TOTAL PRICE KIT (Stereo) £20.19.0 incl. P.T.
TOTAL PRICE KIT (Mono) £24.18.0 incl. P.T.
Optional extra: Walnut veneered cabinet £2/5/- extra.

All models must perform to published specification when assembled in accordance with the instruction manual. ALL MODELS COVERED BY MONEY BACK GUARANTEE.

BERKELEY SLIM-LINE SPEAKER SYSTEM



- Specially designed to obtain optimum performance from the slim elegant cabinet • Beautiful walnut veneered, fully finished cabinet • Makes attractive addition to any room • Stood on end uses only 17 in. x 7 1/2 in. of floor space • Two specially designed loudspeakers give adequate power handling for most applications • 12 in. low resonance unit and 4 in. Mid/High frequency unit, covers 30-17,000 c/s. • Build it in an evening • Professional attractive styling • Use one for mono and a pair for stereo • Outstanding performance at a low price • Shelf or floor standing • Use vertical or horizontal • Designed to harmonize with modern or traditional decor.

KIT £19.10.0 Ready-to-Use £24.0.0

LOW-COST SHORTWAVE RECEIVER, GR-64E



- 4 bands—3 short wave bands cover 1 Mc/s to 30 Mc/s, plus 550 kc/s to 1,620 kc/s AM broadcast band • Built-in 5 in. permanent magnet speaker for a big, bold sound • Illuminated 7 in. slide-rule dial with extra logging scale • Easy to read lighted bandspread tuning dial for precise station selection • Relative signal strength indicator aids pin-point station tuning • 4-valve superhet circuit plus two silicon diode rectifiers • Variable BFO control for code and SSB transmissions • Built-in external antenna connections • Built-in AM rod antenna • Fast, simple circuit board construction assures stability • Handsome "low-boy" styling—charcoal grey cabinet, black front panel, and green and white band markings • Headphone jack for private listening. Power requirements: 115, 230 v. 50-60 c/s A.C. 30 watts. Dimensions: 13 1/2 in. wide x 6 in. high x 9 in. deep.

KIT £22.8.0 Ready-to-Use £27.8.0

LOW-COST SPEAKER SYSTEM SSU-1 (not illustrated)

- Build it yourself in an evening • All wooden parts accurately pre-cut, drilled and sanded • Wide frequency response • Two specially designed loudspeakers • Hi-Fi on a budget • Glue, sandpaper, etc. are included in kit • Use one for mono, two for stereo • Finish it to match your own furnishing • 16 page instruction manual • 7 in. or 15 in. legs optional extra, 1/4 • Use vertical or horizontal.

KIT £11.17.6 (less legs)

GENERAL COVERAGE RECEIVER, GG-1U (not illustrated)

- Powerful 10 transistor, 5 diode circuit • Tunes 580 to 1,550 kc/s and 1.69 to 30 Mc/s in five bands • Bandspread on all bands • Fixed-aligned ceramic IF transformers for best selectivity • Pre-assembled and aligned "front-end" for fast, easy assembly • Built-in 6 in. x 4 in. speaker • Tuning meter for pin-point tuning • Completely self-contained for portability.

KIT £37.17.6 Ready-to-Use £45.17.6



Send for the Latest FREE CATALOGUE

Now with more Kits more colour. Fully describes these models along with over 150 models for Stereo/Hi-Fi, test and laboratory instruments, amateur radio gear, intercom, radio educational kits. Includes helpful information on Hi-Fi in your home and planning your Hi-Fi system. Mail coupon or write Daystrom Ltd., Dept. WW1 Gloucester.

VISIT THE HEATHKIT CENTRES

233 TOTTENHAM COURT ROAD, LONDON, W.1
Open Mon.-Fri. 9 a.m.-5.30 p.m. Sat. 9 a.m.-1 p.m.

AND

17-18 ST. MARTINS HOUSE, BULL RING, BIRMINGHAM
Open Tues.-Sat. 9 a.m.-6 p.m. inclusive.

HEATHKIT

Please Address enquiries to: DAYSTROM LTD., Dept. WW.2, Gloucester.
Tel.: 29451

Enclosed is £..... post paid U.K. only

Please send model(s).....

Please send me FREE Heathkit Catalogue

NAME

ADDRESS

CITY

Prices and specifications subject to change without notice.

***WW-010 FOR FURTHER DETAILS

Heathkit World-Leader in INSTRUMENTS · HI-FI · RADIO · Electronic kits

The construction manual provided with the kit ensures successful assembly



5in. WIDE BAND GENERAL-PURPOSE OSCILLOSCOPE, 10-12U

- "Y" sensitivity 10 mV. r.m.s. per cm. at 1 kc/s. • Bandwidth 3 c/s-4.5 Mc/s. • Frequency compensated input attenuator X1, X10, X100. T/B, 10 c/s-500 kc/s. In 5 steps.
- Two extra switch selected pre-set sweep frequencies in T/B range. • T/B output approx. 10 v. peak to peak. • Built-in IV callibrator • Facility for "Z" axis modulation • Electronically stabilised power supply • Power req. 200-250 v. A.C., 40-60 c/s., 80 watts • Fused • Front panel, silver and charcoal grey • Cabinet, charcoal grey, size 8½ x 14 x 17in. deep. Net weight 23lb. 56-page construction and operation manual.

Kit £35.17.6. Ready-to-use £45.15.0

Attenuator and demodulator probes available as optional extras.

3in. PORTABLE GENERAL-PURPOSE SERVICE OSCILLOSCOPE, OS-2

- Modern styling, lightweight and compact size, make this the ideal scope for service man, laboratory technician, amateur radio enthusiast or hobbyist • "Y" bandwidth 2 c/s-3 Mc/s ± 3 dB. • Sensitivity 100 mV/cm • Push-pull vertical and horizontal amplifiers • Wide range time-base generator 20 c/s-200 kc/s in four ranges. • Automatic lock-in synchronisation • Mu-metal c.r.t. shield • Printed circuit board construction • Power req. 200-250 v. 50-60 c/s A.C. 40 watts • Fused • Front panel silver and charcoal grey. Size 5in. w. x 7½in. h. x 12in. deep. Weight: 9½lb.

Kit £23.18.0. Ready-to-use £31.18.0



6in. VALVE VOLTMETER, IM-13U

- Modern styling • Extra features • The ideal VVM for the Electronic Engineer • 6in. Ernest Turner 200µA. meter with multi-coloured scales
- Unique gimbal bracket allows bench, shelf or wall mounting • Measures A.C. (r.m.s.), D.C. volts 0-1.5, 5, 15, 50, 150, 500, 1,500 • Resistance range 0.1 to 1,000MΩ with int. battery • Vernier action zero and ohms adjustment • Roller-tinned printed circuit • High input resistance (11MΩ) • Comprehensive assembly and operation manual • Size 5 x 12½ x 4½in. Complete with test prod and leads.

Kit £18.18.0. Ready-to-use £26.18.0

4½in. Valve Voltmeter-V-7A (not illustrated). Kit £13.18.6.

Ready-to-use £19.18.6

GENERAL-PURPOSE SERVICE RF SIGNAL GENERATOR, RF-1U

- Ideal for the alignment and trouble shooting of RF, IF and audio circuits • Large easy-to-read dial • Pre-aligned coil and bandswitch assembly
- RF output of at least millivolts • 100 kc/s-100 Mc/s. fundamentals up to 200 Mc/s harmonics • 400 cycle audio signal with 4 v. output • Dimensions 9½in. wide x 6½in. high x 5in. deep.

Kit £13.18.0. Ready-to-use £20.8.0

AUDIO SIGNAL GENERATOR, AG-9U (not illustrated)

Kit £23.15.0. Ready-to-use £31.15.0



See these and other Heathkit models in the FREE catalogue

NEW! PORTABLE STEREO TAPE RECORDER, STR-1

- ½ track stereo or mono record and playback at 7½, 3½ and 1½ i.p.s. • 18 transistor circuit • Record level indicator • Digital counter with zero reset • Stereo mic and aux. inputs. • Speaker/headphone outputs.
- Built-in audio amplifier gives 4 watts rms output per channel. • Two high efficiency 8in. x 5in. speakers.

Versatile Recording facilities. So-easy-to-build. Outstanding performance for price.

Kit £45.18.0. Ready-to-use £59.15.0



NEW! PORTABLE STEREO RECORD PLAYER, SRP-1

- Compact, economical stereo and mono record playing for the whole family
- Mains operated • All "solid state" circuitry. Modern compact styling
- Detachable second loudspeaker gives optimum stereo effect • Automatic playing of 16, 33, 45 and 78 rpm records
- Suitcase portability • Two 8in. x 5in. speakers • Controls: Volume, Balance and Tone. Dimensions: overall 27in. wide x 14½in. high x 7½in. deep.

Kit £27.15.0. Ready-to-use price on request.



THE CAR RADIO TO COMPLETE YOUR MOTORING PLEASURE CR-1



Complete your motoring pleasure with this small, compact, high output unit. Superb long and medium wave entertainment whenever you drive. For 12v. positive or 12v. negative car earth systems.

- 8 latest semi-conductors (6 transistors, 2 diode circuit) • Powerful output (4 watts) will drive two speakers. • Styled to harmonise with most car colour schemes • Supplied in two units, pre-assembled and aligned RF unit kit. £1.13.6 inc. P.T. IF/AF amplifier kit £11.3.6.

Total price kit (excl. LS) . . . £12.17.0 inc. P.T.

L/speakers and accessories available as extras.

"OXFORD" LUXURY TRANSISTOR PORTABLE, UXR-2

This superb transistor radio is the ideal domestic or personal portable Medium and Long Wave receiver • Solid leather case and handle • Easy-to-read tuning scale • Extra large loudspeaker. Push button L, MW and tone • 10 semi-conductors (7 transistors plus 3 diodes) • Sockets for personal earphones, tape recorder, car aerial • Internal 9-volt battery (not supplied) lasts for months • Latest printed circuit techniques • Comprehensive, easy-to-follow, fully illustrated Instruction Manual.

Kit £14.18.0 inc. P.T. Ready-to-use price on request



• Prices quoted are Mail Order, and include free delivery in U.K. • Retail prices slightly higher.

DAYSTROM LTD.

DEPT. WW.2, GLOUCESTER, ENGLAND

Member of the Schlumberger Group including the Heath Company

MANUFACTURERS OF THE WORLD-FAMOUS EASY-TO-BUILD ELECTRONIC KITS

WW-011 FOR FURTHER DETAILS

LEVELL VOLTMETERS measure μV 's from 1Hz to 450MHz

TRANSISTOR A.C. MICROVOLTMETERS

Response from 1Hz to 3MHz with amplifier output available. Two versions differ only in meter size and bandwidth switch on type TM3B.

TYPE TM3A
£49

Complete with battery and input lead.

OPTIONAL EXTRAS
Leather case £4/10/-,
A.C. Power Unit £7/10/-.



TYPE TM3B
£63

Complete with battery and input lead.

OPTIONAL EXTRAS
Leather Case £5,
A.C. Power Unit £7/10/-.

VOLTMETER RANGES

15 μV , 50 μV , 150 μV . . . 500V f.s.d.
Accuracy $\pm 1\% \pm 1\%$ f.s.d. $\pm 1\mu V$ at 1kHz.

dB RANGES

-100dB to +50dB in 10dB steps. Scale
-20dB to +6dB. 0dB = 1mW into 600 Ω .

FREQUENCY RESPONSE

Above 500 μV : +3dB from 1Hz to 3MHz.
0-3dB from 4Hz to 1MHz.

On 500 μV : +3dB from 2Hz to 2MHz.

On 150 μV : +3dB from 4Hz to 1MHz.

On 50 μV : +3dB from 7Hz to 500kHz.

On 15 μV : +3dB from 20Hz to 200kHz.

AMPLIFIER OUTPUT

150mV at f.s.d. on all ranges. Will drive a load of 200k Ω and 50pF without loss.

POWER SUPPLY

One type PP9 battery, life 1000 hours; or, A.C. mains when Power Unit fitted.




BROADBAND VOLTMETERS

As A.C. Microvoltmeters plus H.F. probe to extend response to 450MHz. Two versions differ only in meter size and L.F. bandwidth switch on type TM6B.

TYPE TM6A
£85

Complete with battery and input lead.

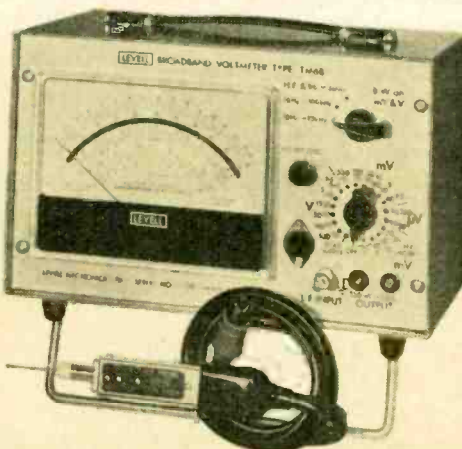OPTIONAL EXTRAS
Leather Case £4/10/-,
A.C. Power Unit £7/10/-.



TYPE TM6B
£99

Complete with battery and input lead.

OPTIONAL EXTRAS
Leather Case £5,
A.C. Power Unit £7/10/-.

H.F. VOLTAGE RANGES

1mV, 3mV, 10mV . . . 3V f.s.d. Square law scales. Accuracy $\pm 4\%$ of reading $\pm 1\%$ of f.s.d. at 30MHz.

H.F. dB RANGES

-50dB, -40dB, -30dB . . . +20dB.
Scale -10dB to +3dB. 0dB = 1mW into 50 Ω .

H.F. RESPONSE

± 0.7 dB from 1MHz to 50MHz.

± 3 dB from 300kHz to 400MHz.

± 6 dB from 400MHz to 450MHz.

L.F. RANGES

As TM3A and TM3B except for the omission or 15 μV and 150 μV .

POWER SUPPLY

One type PP9 battery, life 1000 hours on L.F. ranges and 400 hours on H.F. ranges; or, A.C. mains when Levell Power Unit is fitted.

LEVELL

PORTABLE INSTRUMENTS


Fully detailed leaflets are available on our complete range of portable instruments.

WW-012 FOR FURTHER DETAILS

LEVELL ELECTRONICS LTD., Park Road, High Barnet, Herts. Tel.: 01-449 5028

Instead of illustrating
a lot of meters you may
not need
let's just say Anders carry
the largest stocks in the U.K.

And you can say that again! We have just compiled a catalogue* and even we are surprised at the variety of standard and non-standard meters we offer for off-the-shelf delivery. Among them there is almost certain to be that meter you need in a hurry. It would be interesting (for both of us) to find out. It won't take a moment when you've got through to Euston 1639. (By the way, for 'meter' read 'meters'... whenever the occasion demands).

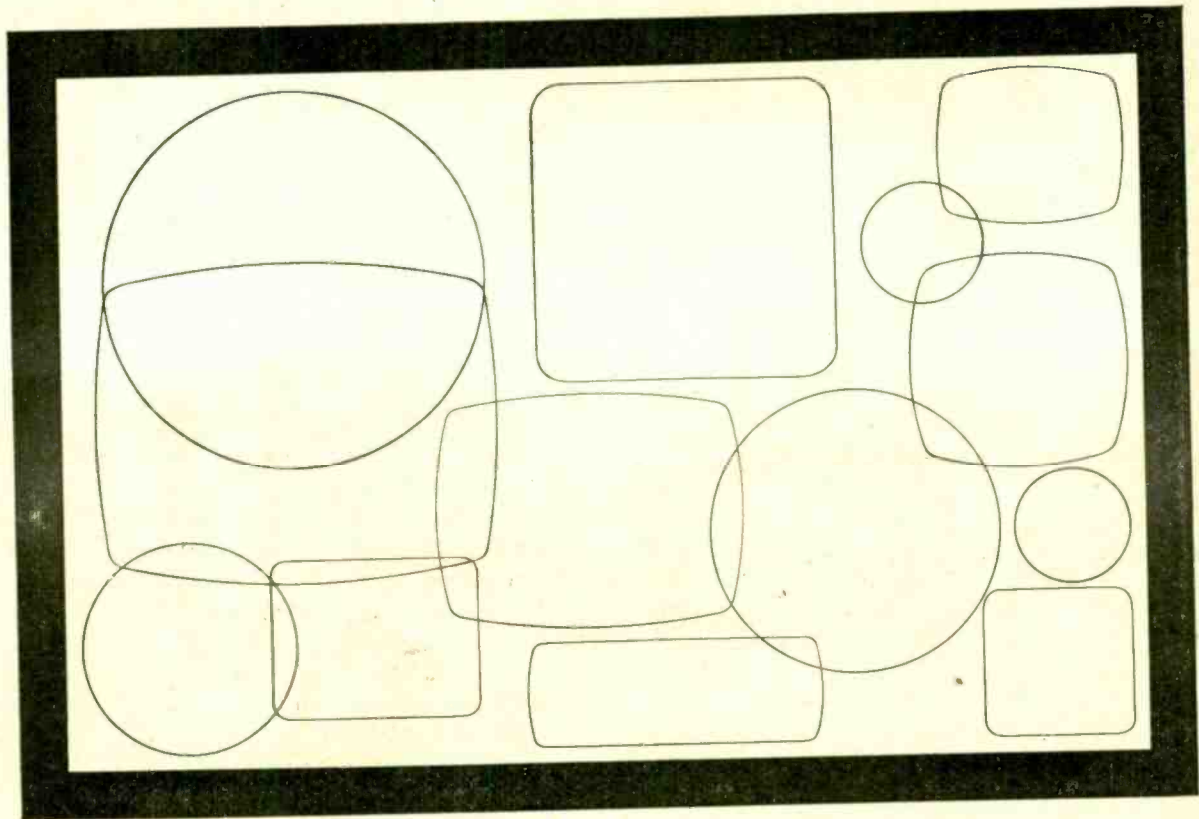

New TELEFRONT Series
with clear plastic bezels

**We'll gladly send one to any manufacturer or bona-fide engineer.*


Manufacture and distribution of electrical measuring instruments and electronic equipment. The largest stocks in the U.K. for off-the-shelf delivery. Prompt supply of non-standard instruments and ancillaries. Sole U.K. distribution of FRAHM vibrating reed frequency meters and tachometers.

ANDERS METER SERVICE

Anders Electronics Ltd · 48/56 Bayham Place · Bayham Street · London NW1 · Telephone 01-387 9092
Ministry of Aviation Approved

WW-013 FOR FURTHER DETAILS

ONE...

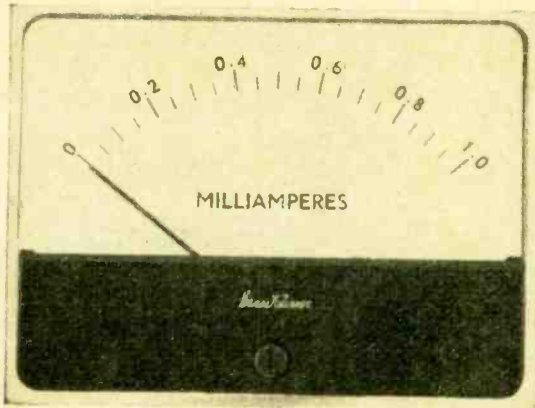

...OR ONE THOUSAND -
*To Your Specification
and Delivery*

Whether your need is for a single instrument or a thousand (or even more) the Ernest Turner organisation is geared to give the same renowned service. From a very wide choice of movements and case styles we can provide precisely the Instrument for your application, including the manufacture of special dials and provision of built-in or external units to permit indication of any electrical quantity.

We invite your specific enquiry for any number of instruments from one upward, and we should be pleased to send you a copy of our general catalogue 86/25 on request.

ERNEST TURNER ELECTRICAL INSTRUMENTS LTD.
CHILTERN WORKS, HIGH WYCOMBE
BUCKS

Tel: 30931-4

VALUABLE NEW HANDBOOK **FREE** TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

ELECTRONIC ENG.

Advanced Electronic Eng. — Gen. Electronic Eng. — Applied Electronics — Practical Electronics — Radar Tech. — Frequency Modulation — Transistors.

RADIO ENG.

Advanced Radio — Gen. Radio — Radio & TV Servicing — TV Eng. — Telecommunications — Sound Recording — Automation — Practical Radio — Radio Amateurs' Exam.

ELECTRICAL ENG.

Advanced Electrical Eng. — Gen. Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Electrical Science — Electrical Supply — Mining Electrical Eng.

MECHANICAL ENG.

Advanced Mechanical Eng. — Gen. Mechanical Eng. — Maintenance Eng. — Diesel Eng. — Press Tool Design — Sheet Metal Work — Welding — Eng. Pattern Making — Inspection — Draughtsmanship — Metallurgy — Production Eng.

CIVIL ENG.

Advanced Civil Eng. — Gen. Civil Eng. — Municipal Eng. — Structural Eng. — Sanitary Eng. — Road Eng. — Hydraulics — Mining — Water Supply — Petrol Tech.

AUTOMOBILE ENG.

Advanced Automobile Eng. — Gen. Automobile Eng. — Automobile Maintenance — Repair — Automobile Diesel Maintenance — Automobile Electrical Equipment — Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power? A.M.I.E.R.E., A.M.I.Mech.E., A.M.S.E., A.M.I.C.E., B.Sc., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., A.M.I.Chem.E., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

446A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT CAREER-GUIDANCE

PRACTICAL EQUIPMENT	INCLUDING TOOLS
Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam, R.T.E.B. Certificate, P.M.G. Certificate, Practical Radio, Radio & Television Servicing, Practical Electronics, Electronics Engineering, Automation.	The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.



You are bound to benefit from reading "ENGINEERING OPPORTUNITIES," Send for your copy now—FREE and without obligation.

POST NOW!

TO B.I.E.T. 446A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE. 3d. stamp if posted in an unsealed envelope.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS

.....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

WW-015 FOR FURTHER DETAILS

do you need a stable and accurate A.C. voltage source...?



Since its introduction the Bradley 125B A.C. Calibrator has established itself as a versatile A.C. voltage source, not only for the calibration of instruments and the testing of meters, but also as a stable source for driving high resolution digital measuring systems and calibration potentiometers. Further it is a well-tried instrument, which does not have a rival anywhere in the world, at the price . . . £395.

A.C. Output

The A.C. voltage (R.M.S. or average) is controlled by four stud switches giving a clear in-line digital read-out. The range is from 0 to 511 volts in 100 mV steps. The accuracy is 0.2% of setting, whilst the regulation is better than 0.15% and the distortion is less than 0.15%. The output is continuously referred to a Weston Standard Cell.

Output Frequency

Plug in oscillator units cover the range 40-2400 Hz. The instrument is

normally supplied with 1 plug-in unit giving output frequencies of 50, 60, 400 and 1000 Hz. An alternative unit giving 50, 400, 1000 and 2400 Hz can be supplied if required.

Percentage Deviation Indicator

A feature of the instrument is that the selected output voltage can be continuously varied over the ranges $\pm 5\%$ and $\pm 0.5\%$, with meter indication.

Ratio Transformer

A x 10 and x 100 Ratio Transformer is available as an extra. This will extend the output down to 1 mV in 10 mV and 1 mV steps.

The full specification is given in our booklet 'Calibration Equipment'. This also describes our D.C. voltage and current sources. May we send you a copy?

Or better still, try the instrument yourself.

We will be pleased for our Area Sales Engineer to call. Write, or phone 01-450 7811

BRADLEY INSTRUMENTS

G. & E. BRADLEY LTD

ELECTRAL HOUSE, NEASDEN LANE, LONDON, N.W.10

WW-016 FOR FURTHER DETAILS




Eddystone

Professional communications receivers

940 single conversion superheterodyne receiver

for c.w, a.m and s.s.b modes in the range 480 kHz to 30 MHz. The sensitive thirteen-valve circuit uses a low-noise, high-gain cascode r.f amplifier followed by a second r.f stage, two i.f amplifiers, phased crystal filter, separate detectors for a.m, c.w/s.s.b, silicon diode noise limiter and push-pull audio output. Sensitivity substantially constant at 3 μ V for a 15 dB signal-to-noise ratio, 30% modulation and 50 mW output. The efficient a.g.c circuit ensures a change of less than 9 dB in audio output with a carrier level increase of 100 dB above 5 μ V. Audio response level within 3 dB over the range 100 Hz to 8000 Hz. Connections for 2.5-ohm speaker and 600-ohm line, balanced or unbalanced. Power supply 110/125V and 200/240V a.c 40—60 Hz.

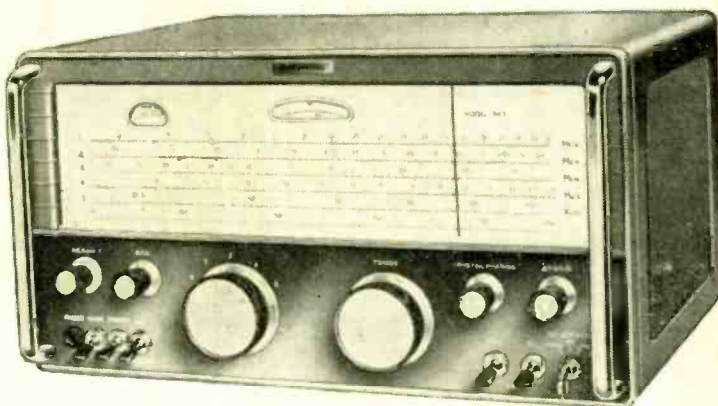

770R Mark II

for reception of c.w, a.m narrow and broadband f.m signals in the range 19 MHz to 165 MHz in six bands. Selectivity automatically adjusted to suit signal mode. Twenty valves and two germanium diodes are used in a highly sensitive circuit with push-pull audio output and provision for a 2.5-ohm speaker, 600-ohm balanced line or high resistance telephones. Power requirement 100/125V and 200/250V a.c 40—60 Hz.



770U Mark II receiver

for coverage of a.m and f.m signals in the range 150 MHz to 500 MHz in six bands. High sensitivity with circuitry using nineteen valves, four diodes and one transistor. The r.f section incorporates a specially designed tuner, a fully tuned grounded-grid amplifier followed by a diode mixer. Low-impedance outputs available at the first i.f of 50 MHz and also at the second i.f at 5.2 MHz. Power requirement 100/125V and 200/250V a.c 40—60 Hz.



830/7 wide-range receiver

fully tunable from 300 kHz to 30 MHz in nine ranges and accepting c.w, a.m and s.s.b signals. Overall bandwidth continuously variable within the limits of 1.3 kHz and 6 kHz and narrowed to 50 Hz with 100 kHz crystal filter. Instant changeover to crystal control with rapid selection of up to eight spot frequencies. Sensitivity better than 3 μ V for a 15 dB signal-to-noise ratio. Power requirement 100/125V and 200/250V a.c 40—60 Hz.


Write for list of UK and overseas agents to Eddystone Radio Limited, Alvechurch Road, Birmingham 31
Telephone: Priory 2231 Telex: 33708

A MARCONI COMPANY

LTD ED/37

WV—017 FOR FURTHER DETAILS

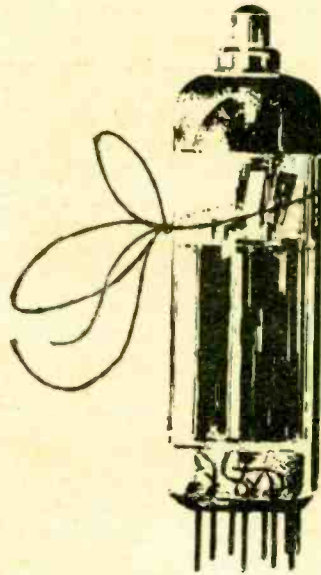IF THIS
IS NOT THE
ONE YOU
WANT WE STILL
HAVE A FEW
MILLION OTHERS



FOR EXPORT

VALVES FOR:

Radio and Television Manufacturers.
Radio and Television Service Departments.
Radio Relay Companies
Audio Equipment.
Electronic Equipment.
Instrumentation.
Computers.
Marine Radar.
Communication Equipment.
Research and Development.
Government Departments.
Aircraft Military and Civil.

*Ministry of Aviation Approved Inspection. Air Registration Board
Approved Inspection.*

**For quality, reliability and world-wide availability, rely on
Hall Electric's speed, intelligence and reputation.**

HALTRON

RADIO VALVES & TUBES

Hall Electric Ltd., Haltron House, Anglers Lane, London, N.W.5.

Telephone: 01-485 8531 (10 lines). Telex: 2-2573. Cables: Hallelectric, London, N.W.5.

WW-018 FOR FURTHER DETAILS

TIMERS MICRO SWITCHES

IMMEDIATE DESPATCH

PROCESS TIMERS

611-T Delay Relay



approx. 40/- each, dependent on quantity.

- ★ 2, 5, 15 & 25 secs. Delay.
- ★ 15 amp. c/o micro-switch fitted
- ★ LARGE RANGE OF A.C. & D.C. COILS.

AT-10 PNEUMATIC TIMER - delay relay



- ★ Fully adjustable up to 200 seconds. Fitted with 15 amp. S.P.D.T. switch.
- ★ One model provides delay after energise or delay after de-energise.

approx. £6.0.0 dependent on quantity.


STP Sub-Mini Process Timer SYNCHRONOUS MOTOR & CLUTCH



- Matchbox size frontal area.
- Automatic re-set.
- ★ PLUG-IN OCTAL BASE
- ★ INSTANTANEOUS AND TIMED OUT 2 AMP CONTACTS
- ★ RANGES: 10 SECS. TO 36 MINS.

approx. £5.0.0 each.

SYS MINI-TIMER

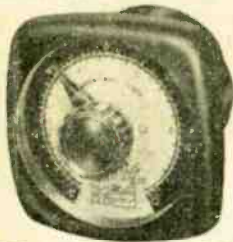

SYNCHRONOUS MOTOR & CLUTCH

- ★ 10 MILLION OPERATIONS
- ★ Instantaneous & Timed out 3 AMP contacts.
- ★ Repeat Accuracy $\pm 1\%$. 10 secs. to 28 Hrs. May also be used as impulse start and automatic reset.

dependent on quantity. approx. £9.15.0

MAINS OPERATED



YL 2 GPA PROXIMITY SWITCH

- ★ FOR BATCHING, CONVEYORS, MACHINE TOOL CONTROL, PACKAGING, SORTING, etc.
- ★ SENSES FERROUS OBJECTS
- ★ NEEDS NO MECHANICAL FORCE OR PRESSURE TO OPERATE
- ★ SOLID STATE SENSING HEAD INCLUDES CONSTANT VOLTAGE CIRCUIT

approx. £11.0.0 dependent on quantity.

OTHER INDUCTIVE AND CAPACITY TYPES AVAILABLE

U.L. APPROVED (Appr. No. 32667)

U.S. MIL. SPEC.

ALWAYS AVAILABLE FROM STOCK

S5G



- ★ 1 MILLION OPS. 5 amp. c/o Sub-miniature Micro-switch.

2/5 each per 1,000

VAQ




- ★ 10 amp. c/o PUSH BUTTON Panel mounting. Buttons in six colours.

4/2 each per 250.

HEAVY DUTY PUSH-BUTTON SWITCHES

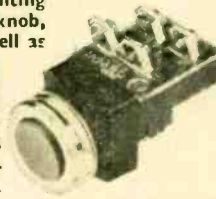7 different panel mounting actuators including; knob, key, and lever, as well as push on/push off. Up to 4 switch blocks can be fitted. Dust and splash proof, D/P slow make and break, 5 amp rating. Full literature on request.



VV-15-1A



- ★ 15/10 AMPS. c/o
- ★ 100,000 ops.

1/8 each per 1,000

Single Throw 1/4 each

LIMIT SWITCH

WL 10 FNJ

- ★ 10 AMP 2 CIRCUIT
- ★ 5 INCH FLEXIBLE ACTUATOR AS ILLUSTRATED

AS LOW AS 47/7 EACH.

FIVE OTHER STANDARD TYPES AVAILABLE



V-10-1B



- ★ 1 MILLION OPERATIONS.
- ★ 10 amp. c/o.

- ★ COMPARE OUR SPEC. & OUR PRICES WITH OTHER SIMILAR TYPES.

Screw Terms. 2/2 each per 1,000
V-10-1A Solder Tags 1/11 each per 1,000

CCR-5



New!

Approx. 4/- each per 1000. Light force wire operated Micro-switch. Designed for even more economical coin operation mechanism.

NEW RANGE OF SLOW BREAK-&MAKE HEAVY DUTY PUSH-BUTTON SWITCH ACTUATORS. PANEL MOUNTING, TO BE USED WITH 1 to 4 D/P S/T SWITCH BLOCKS. COLOURED KNOBS. ALSO PUSH-ON/PUSH-OFF TYPES. SUITABLE FOR MACHINE TOOLS, MOULDING & PACKAGING MACHINES & CONTROL PANELS. FULL LITERATURE & DETAILS ON REQUEST.

(Dept. W.W.9) **OMRON PRECISION CONTROLS**
 OMRON LTD: 313 Edgware Road, London, W.2 Tel.: 01-723 2370

WW-021 FOR FURTHER DETAILS

ERTAS SERVICE ?



ERTAS, or to give its full title – the **Ever Ready Technical Advisory Service**, is a specialised branch of the Ever Ready Organisation. Its aim is to help the portable appliance manufacturer to get the best possible performance from battery-operated products.

ERTAS is supported by highly specialised Research Scientists at Ever Ready's Central

Research Laboratories. Ever Ready welcomes you to take advantage of this department's far reaching technical services which ensure that the correct battery is selected for your particular requirement.

Up-to-date technical information on our latest products is available on request.



Write to Mr. S.H. Dear, Technical Sales Manager

THE EVER READY CO. (GB) LIMITED
 Ever Ready House · 1255 High Road
 Whetstone · London N20
 Tel: 01-445 8877

WW-022 FOR FURTHER DETAILS

QUAD for the closest approach to the original sound




QUAD 303 POWER AMPLIFIER

A two channel power amplifier of unique design capable of a standard of quality* limited solely by the capabilities of the accessories with which it is used.

**Distortion: harmonic, intermodulation, amplitude, steady state or modulated and however weighted, several times lower than any other amplifier known to us*

QUAD 33 CONTROL UNIT

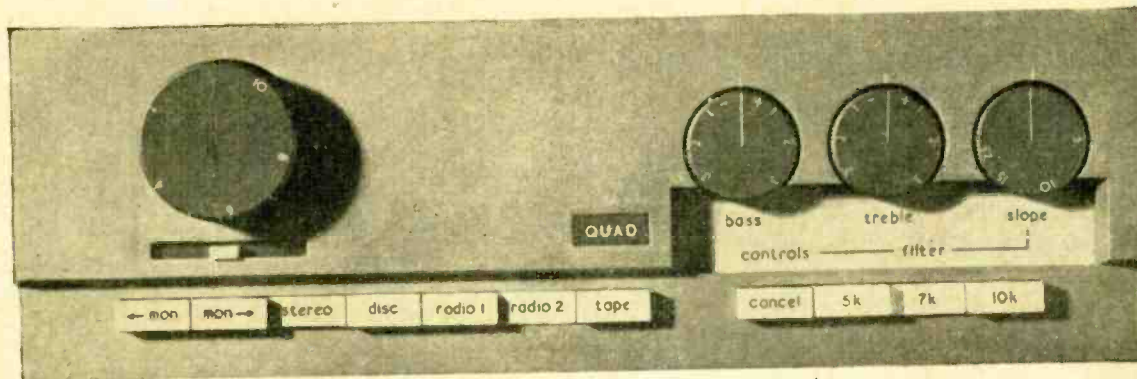
A self powered control unit to select, match, correct and amplify for the closest approach to the original sound inherent in the programme.



For further details, ask any dealer advertising in this magazine, or send a postcard to:—
ACOUSTICAL MANUFACTURING COMPANY LTD., HUNTINGDON.

WW—023 FOR FURTHER DETAILS

TRANSIT PACK PROTECTION WITH FOAMAIR

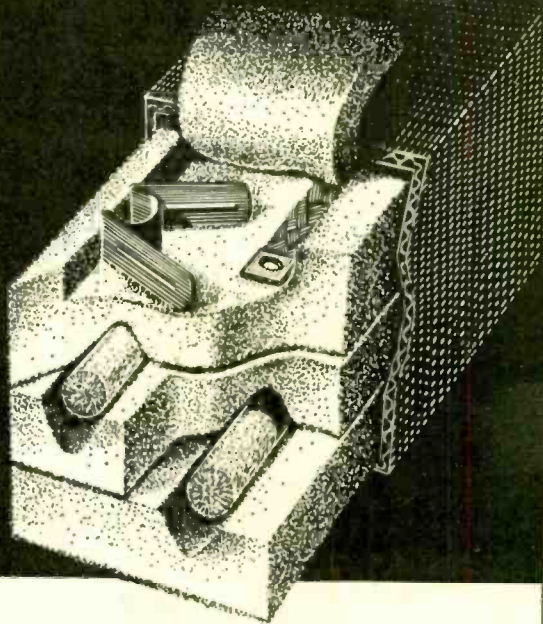

Prevention is better than claim. Even your most fragile apparatus will arrive intact when packed in Foamair. A flexible urethane, Foamair gives complete protection against vibration and shock.

The illustration shows a highly successful transit pack designed for exporting brittle furnace elements to Russia. Commissioned by Morganite Electroheat Limited, the bespoke pack was repeatedly tested at the prototype stage: complete consignments survived four-foot drop tests on to concrete.

As it can be cut or profiled to any shape, let us tailor Foamair to your product. If you cannot risk sending it, we'll arrange to have it collected. Then we'll safely consign it back to you packed in Foamair.



FOAMAIR LIMITED

21 West Ferry Road, Millwall, London, E.14.

Telephone: EAST 5665 (4 lines)

Member of the Kayfoam group of companies

WW-024 FOR FURTHER DETAILS

Litesold

20 WATT SOLDERING INSTRUMENT



- CONTROLLED TEMPERATURE

Design holds max. temp. of 380°C. within close limits.

- EASY BIT REPLACEMENT

Simple, fast replacement of low-cost copper bits. Non-wearing PERMATIP bits cut servicing costs.

- BEAUTIFULLY COMPACT

Length 7 $\frac{3}{8}$ in. Weight 1 $\frac{1}{4}$ oz. Max. handle dia. 0.715in.

- UNEQUALLED PERFORMANCE

Ideal for fast production soldering on the majority of modern electronic equipment.

- ALL VOLTAGES

- NEON INDICATOR

10, 18, 20 & 25 watt models supplied to special order with Neon Indicator.

The LITESOLD range includes six other models (10, 18, 25, 30, 35 and 55 watts), and many accessories. Please ask for colour catalogue L5.

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL

Tel. 01-688 8589 & 4559



WW-025 FOR FURTHER DETAILS




-the first name in mobile radio



PYE 'CAMBRIDGE' mobile radio

for dependable, reliability-tested, peak-performance, **always**

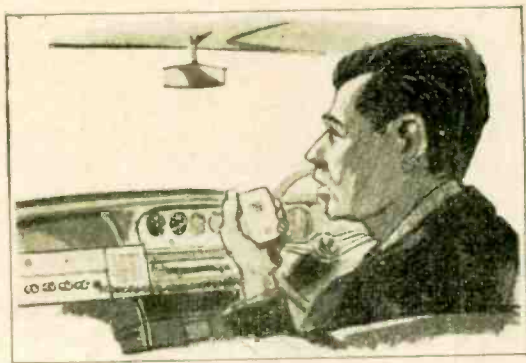
- All-transistor receiver—100 mA battery drain
- G.P.O. approved; meets U.S., Canadian and European specifications
- Sealed I.F. block fitters
- A.M. or F.M. versions
- Dust and splash proof
- Option of 12½ kc/s, 20/25/30 kc/s or 40/50/60 kc/s channel spacing
- 1 to 8 channels available




Pye Telecommunications Limited, Cambridge, England.
 Telephone Cambridge 61222. Telex 81166

M.R.13

WW—026 FOR FURTHER DETAILS




Porcelain
Steatite

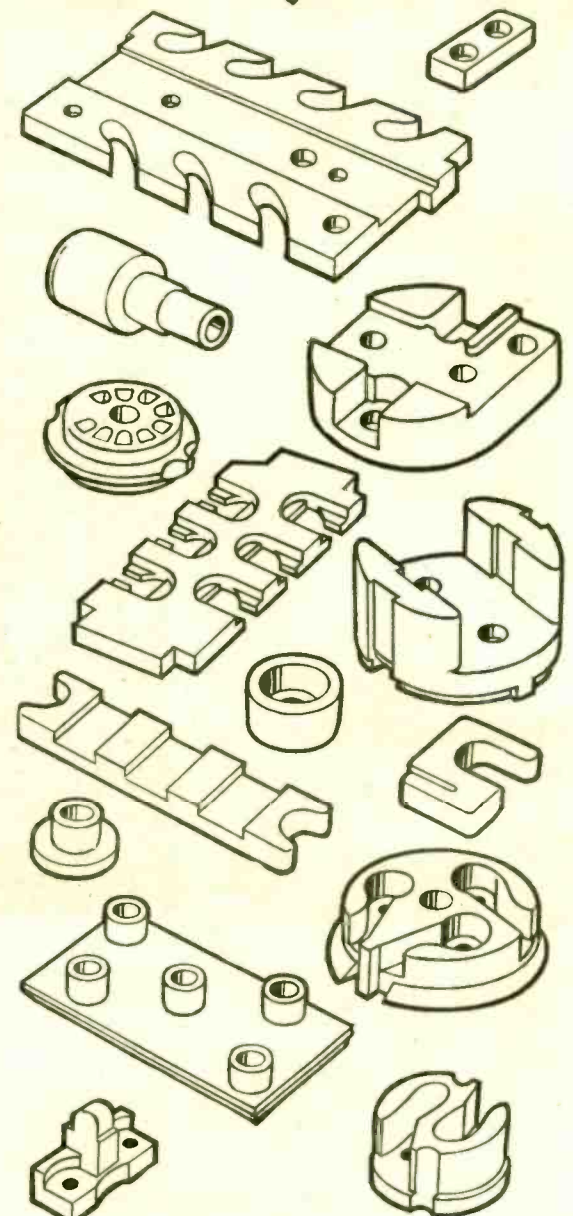


PARK ROYAL PORCELAIN CO., LTD.
 Incorporating V. G. Porcelain Co., Ltd.

GORST ROAD
 PARK ROYAL
 LONDON, N.W.10

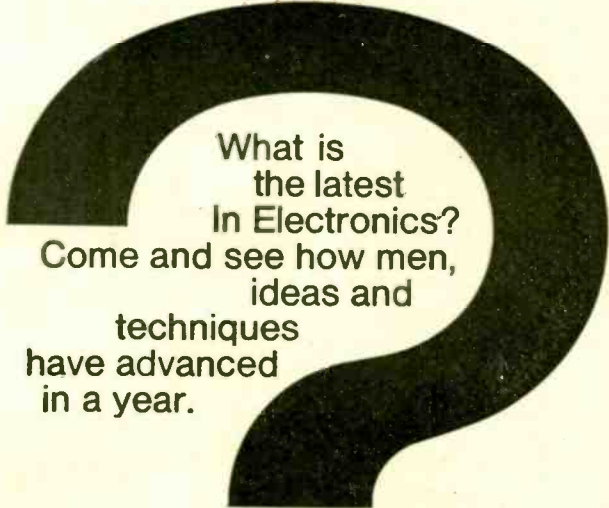Telephones:
 ELGAR 1411/7
 Telex:
 London 25589



What is
the latest
In Electronics?
Come and see how men,
ideas and
techniques
have advanced
in a year.



Be present at the

INTERNATIONAL EXHIBITIONS OF ELECTRONIC COMPONENTS AND OF AUDIO-EQUIPMENT

FROM APRIL 1st TO 6th 1968 - PARIS
 PORTE DE VERSAILLES



INTERNATIONAL CONFERENCE ON COLOUR TELEVISION

scientific and technical considerations
 FROM MARCH 25th TO 29th 1968 - PARIS


Programme and registration conditions on request

S.D.S.A. - RELATIONS EXTERIEURES
 16, RUE DE PRESLES - 75 PARIS 15^e - FRANCE

WW-027 FOR FURTHER DETAILS

WW-028 FOR FURTHER DETAILS

If i'd only tried **Pinnacle** first...

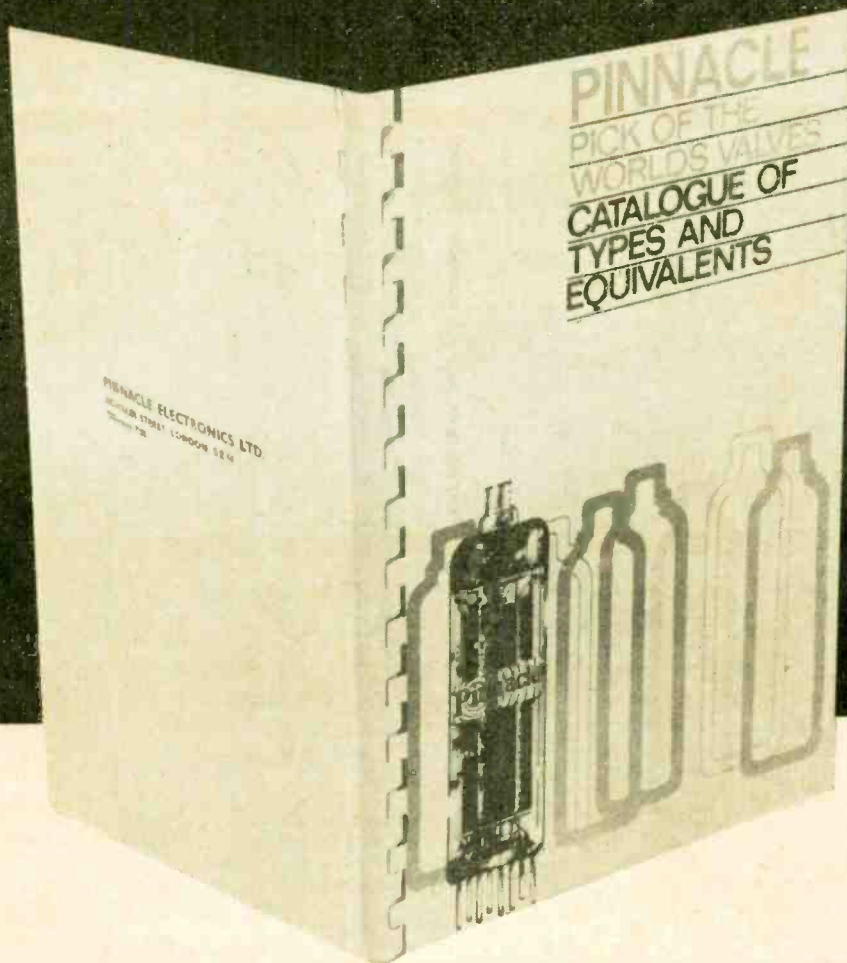


Pinnacle

The widest ranging and most comprehensive valve catalogue available from any independent supplier.

PINNACLE ELECTRONICS LTD ACHILLES STREET · NEW CROSS · LONDON S.E.14
Telephone: All Departments—01-692 7285 Direct orders—01-692 7714

WW-029 FOR FURTHER DETAILS

The Lilliput Series

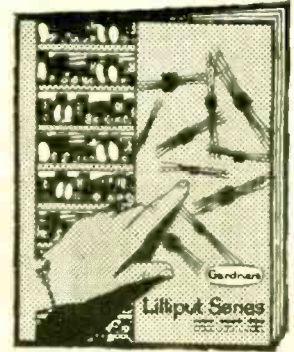


ULTRA MINIATURE, INVERTER, WIDE BAND, CARRIER MATCHING, DRIVER AND PULSE TRANSFORMERS, A.F. AND SMOOTHING INDUCTORS

Gardners Lilliput series of Ultra Miniature transformers has been specifically developed for compatibility with other wired-in modules used on printed circuit boards. Exceptional performance has been achieved by a unique form of construction incorporating extremely thin (down to 3:2 microns) high permeability core materials and a very short length of coil turn. Transformers in this new series are particularly suitable for pulse and switching circuits with rise times of 10 nanoseconds or less


GT 12A. Describes the Lilliput series of Ultra Miniature transformers and gives useful information and data on their application in transistor converter/inverter, wide band communication and high speed pulse circuits.

The Alpha Series

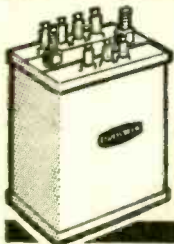FILTERS, DELAY LINES, TRANSFORMERS, MODULATORS, HIGH STABILITY INDUCTORS, TUNED CIRCUITS, OSCILLATORS




A range of custom built components from simple or hybrid transformers and modulators to highly complex multi-section filters or complete active networks of exceptional stability hermetically sealed to DEF. 5214 Humidity Class H1.

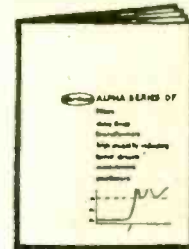

GT 16. Gives a general description of the Alpha series assemblies and describes their suitability for wound components where a high degree of stability is required.

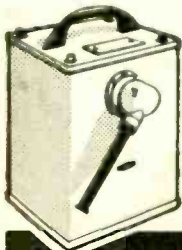Low Voltage Isolating and Auto Transformers



A comprehensive range of conventional double wound and auto transformers for applications in industry and in the home. Nearly 200 types are available in six different styles and with outputs from 6 volts to 240 volts and from 5VA rating to 2 kilowatts. All types are normally held in stock in reasonable quantities for immediate delivery.



GT 17. Everyone in the electronics industry uses low voltage, isolating and auto transformers at some time or other and this booklet describes the complete Gardner range of this type of transformer in a convenient and presentable form.

Complete coupon and post indicating publication(s) required



Gardners Transformers Ltd., Christchurch, Hampshire
Telephone: Christchurch 1734 Telex 41276

Lilliput Series	<input type="checkbox"/>	Alpha Series	<input type="checkbox"/>
Low Voltage Isolating, Auto Transformers	<input type="checkbox"/>		
Name		
Designation		
Company		
Address		

WW-030 FOR FURTHER DETAILS

EDDYSTONE COMMUNICATION RECEIVERS

For the Professional or Amateur user who likes the Best.



840C
£66

HIRE PURCHASE TERMS

Model	Cash Price	Deposit	12 mthly. of	Total H.P. Price	24 mthly. of	Total H.P. Price
EC10	£53	£15	£3 8 2	£55 18 0	£1 19 2	£62 0 0
840C	£66	£16 10 0	£4 8 9	£69 15 0	£2 7 6	£73 10 0
EB35	£60	£3	£15 6 3	£4 0 7	£63 13 3	£66 18 3
940	£133	£34	£8 17 3	£140 7 0	£4 14 9	£147 14 0
EA12	£185	£47	£12 7 3	£195 7 0	£6 12 3	£205 14 0

Payments over 30 months if desired.

Quotation on request.

Delivered Carriage paid by Passenger Train.

CARRIAGE PAID



Telephone: AINTREE 1445

SEND STAMP FOR LITERATURE TO

The Eddystone
Specialists

SERVICES LTD.
51 COUNTY ROAD
LIVERPOOL, 4

ESTAB. 1935

WW-031 FOR FURTHER DETAILS

Speed up Repair Work

Vital
time-saving
repair
data for
nearly
600
MODELS

AND STEP UP YOUR EARNINGS

Nearly 1,000 pages of Circuits, Data and Repair instructions—including the latest facts on colour TV... that's what you get in this big 2-volume RADIO & TV SERVICING. All the information you need for the 1965/67 Popular Television, Radio, Radiograms, Car Radios, Record Reproducers, Tape Recorders is here—to guarantee quicker turn-round of repair jobs... to increase your earnings. Thousands of sets of previous editions have been sold—solid proof of its value to you as essential workshop "equipment."

FOR THE FIRST TIME—ADVANCE DATA ON
COLOUR TV (Pal System)

A big 32-page section well worth seeing

STUDY IT — USE IT

FREE for 7 days



To: Euckingham Press Ltd., 4 Fitzroy Square, London, W.1.

Please send RADIO & TELEVISION SERVICING without obligation to buy if you accept my application. I will return it in 8 days or post

Tick (✓) Full cash price

here 10/- dep. & 16 monthly payments of 10/-

If you are under 21 your father must fill up coupon.

Full Name (BLOCK LETTERS)

Address

County

Occupation

Signature

Cash price £8. (Credit price £8.10s.) For-Eire & N.I. send £8 with coupon.

Please tick (✓) here

The address on left is

my own property

Rented

unfurnished

Furnished

Temporary

address

If none of the above

please answer here


Mr. Mrs. Miss

RV2/3431

WW-032 FOR FURTHER DETAILS

PRECISION CERAMICS

LOW-LOSS OR HIGH ALUMINA

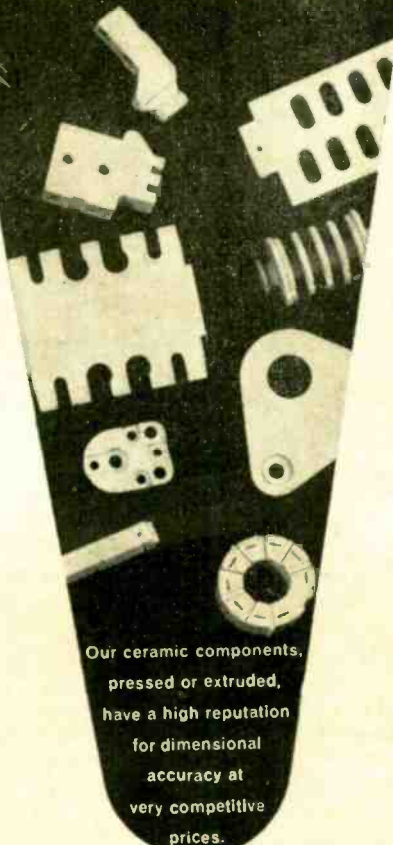

Our ceramic components, pressed or extruded, have a high reputation for dimensional accuracy at very competitive prices.

Full details available from:


W. GREENWOOD (LONDON) LTD.

21 GERMAIN STREET,
CHESHAM, BUCKS

Chesham
4808/9

WW-033 FOR FURTHER DETAILS

O.K!
**-so you're not a
 surgeon...**

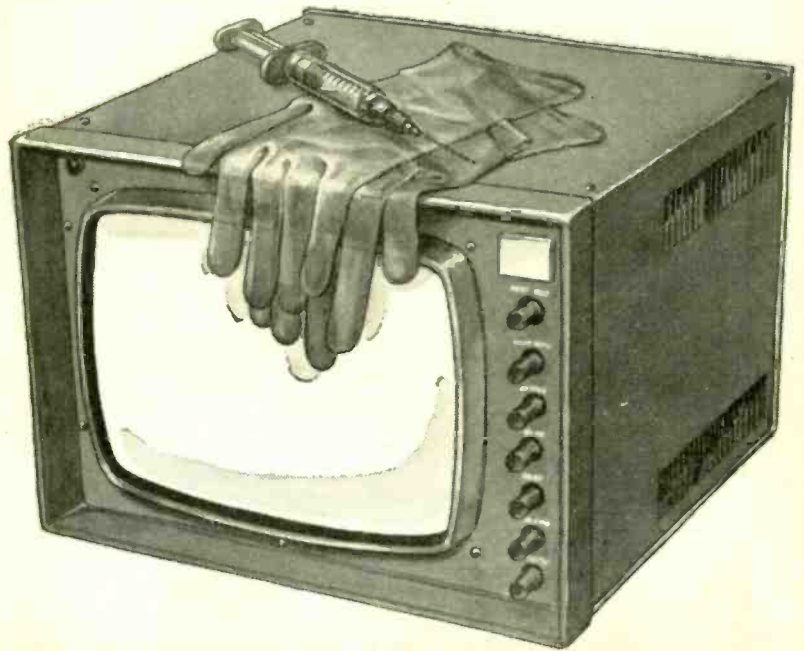

... but if you are concerned with hospital teaching or administration you can help bring the most advanced surgery techniques and the atmosphere of the operating theatre to as many young doctors as you can comfortably house, through the medium of G.E.C. Closed-Circuit Television.

Similarly, if you are concerned with educational training, in commerce or industry, the same G.E.C. equipment is readily available to you. Ask G.E.C. about it today. Send for full information on the high-quality equipment now available at a price which sets new standards for general purpose systems.

*Radio Telephones, Mobile
 Air-to-Ground, Long Distance &
 Hospital Communications.
 Closed Circuit Television.
 Remote Control & Supervisory Systems.*

**Communications
 Division**

G.E.C. Communications—increasing efficiency, helping the community.

G.E.C.

Electronics

Information Centre, G.E.C. (Electronics) Limited, Communications Division, Spon Street, Coventry
 Telephone: Coventry 24155. *A subsidiary of the General Electric Company Limited, of England*

WW—034 FOR FURTHER DETAILS

HOWELLS RADIO LTD.

MINISTRY OF AVIATION INSPECTION APPROVED

TRANSFORMERS
STANDARD RANGE OR DESIGNED TO YOUR SPECIFICATION
0-50KVA, "C" CORE, PULSE, 3 PHASE, 6 PHASE, TOROIDS, ETC.
Transformers for 20W Transistor Amplifier (W.W., Nov. 1966).

Driver	22/6	Carr.	2/-
Mains	29/6	Carr.	4/6

L.P. Filter, Chassis Mounting 11/6. Carr. 1/-.
L.P. Filter, Printed Circuit Mounting 14/6. Carr. 1/-.

***MAINS TRANSFORMERS**
350-0-350 v. 60 mA., 6.3 v. 2 A. £1/15/-. Carr. 4/6.
500 v. 300 mA. 6.3 v. 4 A., 6.3 v. 1 A. £3/12/6. Carr. 5/6
500-0-500 v. 0.25 A., 6.3 v. 4 Act., 6.3 v. 3 Act., 5 v. 3 A. £4/10/6. Carr. 6/6.
525-0-525 v. 0.5 A., 6.3 v., 6 Act., 6.3 v., 6 Act., 5 v. 6 A. £5/5/-. Carr. 6/6.

***LOW VOLTAGE**

30-0-30 v. 4 A.	£2/5/6.	Carr.	5/6.
15 v. 2 A.	£1/12/6.	Carr.	3/-.
15 v. 6 A.	£2/1/-.	Carr.	4/6.
15 v. 10 A.	£2/15/-.	Carr.	5/6.


STEP DOWN TRANSFORMER
Primary 0-415-440 v. Sec. 250 v. 1.5 A. £5/5/-. Carr. 6/6.
***PRIMARIES** 10-0-200-220-240 v.

CHASSIS, CABINETS & PRECISION METALWORK
ELECTRONICS—DEVELOPMENT & ASSEMBLY
CASH WITH ORDERS PLEASE
Carlton Street, Manchester 14, Lancashire
TEL. (STD 061) 226-3411

WW—035 FOR FURTHER DETAILS

PARKER'S SHEET METAL FOLDING MACHINES

NEW BENCH MODEL



Capacity 36in. wide x 18-gauge mild steel. Forms channels and angles down to 45 deg., which can be flattened to give safe edge. Depth of fold according to height of bench. Will form flanges. Weight approx. 2 cwt.

Price £25, carr. free. Also the well-known vice models of:


36in. x 18-gauge capacity	£12 10 0	} Carriage free
24in. x 18-gauge capacity	£7 5 0	
18in. x 16-gauge capacity	£7 5 0	

One year's guarantee: money refunded without question if not satisfied. Send for details:

A. B. PARKER FOLDING MACHINE WORKS
UPPER GEORGE STREET, HECKMONDWIKE, YORKSHIRE Tel: 3957

WW—036 FOR FURTHER DETAILS

A.C. SOLENOID type SAM/T

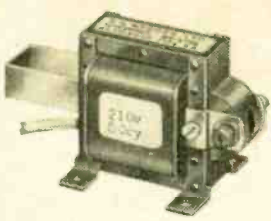


Now fitted with stainless steel guides—six times the life.
Continuous 14 oz. at 3in. Instantaneous to 5½lb.
Larger and smaller sizes available.
Also Transformers to 8kVA 3 phase.

R. A. WEBBER LTD.
KNAPPS LANE, CLAY HILL, BRISTOL 5. Phone: 65-7228/9

WW—037 FOR FURTHER DETAILS

W.G.

NEW SOLDER REMOVER




Instantly removes unwanted solder from printed circuits and other joints. Saves time, increases production, eliminates risk of damage to components.

79/6

Available now from
W.GREENWOOD INSTRUMENTS LTD
21 GERMAIN STREET, CHESHAM, BUCKS
Chesham 4808/9

WW—038 FOR FURTHER DETAILS

audiosuite BY GOODMAN'S

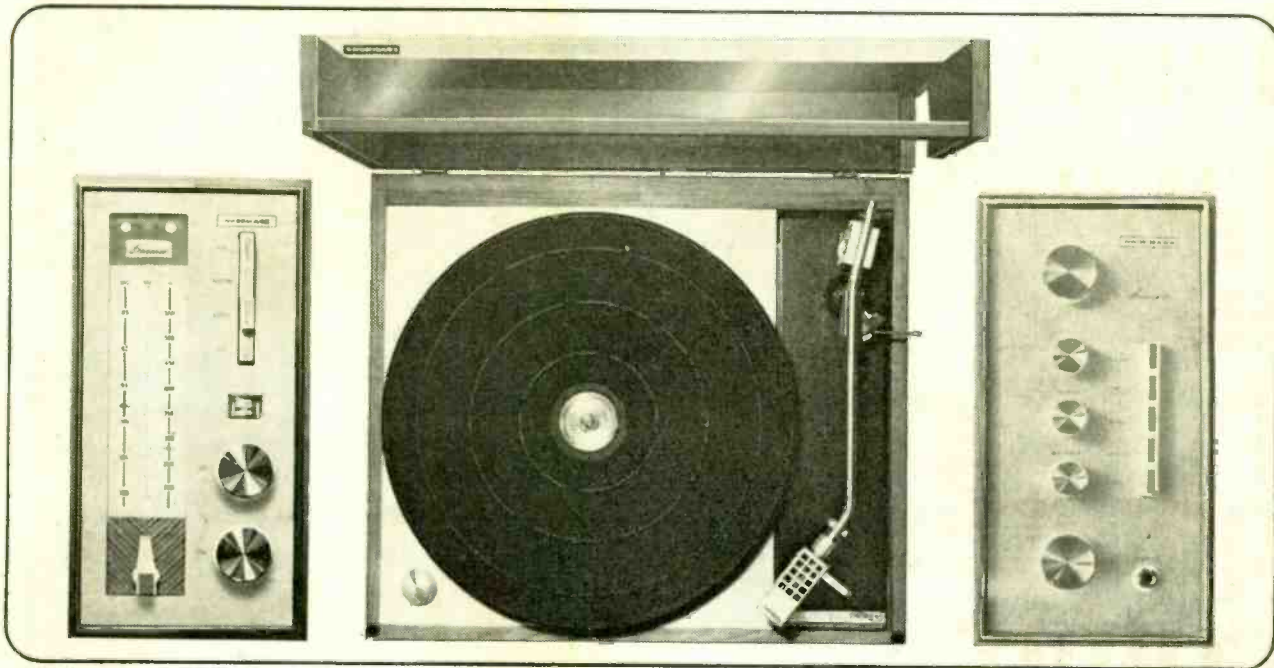

Take a 'top-flight' Amplifier, choose your loudspeaker from a quality-proven High Fidelity range, add a Tuner designed and built by experts and a transcription Record Player guaranteed by Goodman's and there you have it - the most compact, adaptable, handsome, and the most technically advanced audio system in the world - true High Fidelity. This is the AUDIO SUITE - by GOODMAN'S.

Ignore if you will, the handsome appearance, the compactness, the versatility of the Audio Suite. Judge it on the specification and performance alone.

Send for full technical details included in Goodman's High Fidelity Manual or, if you have one already, then send for

the Audio Suite booklet in full colour. When you've read all about it - call at your nearest Hi-Fi dealer - see it in the flesh and listen to a demonstration. Judge for yourself the simple sophistication of the controls and facilities, see how easy they are to use.

m-RANGE

The Audio Suite is completed - to individual choice - with loudspeaker systems from Goodman's 'M' Range.

MAXIM Unrivalled true High Fidelity in ultra compact size - only 10½" x 5½" x 7½" deep.

MEZZO II The most advanced High Fidelity Bookshelf reproducer. Flush-fitted attenuator. 12" x 19½" x 9" deep.

MAGNUM-K Studio quality, 3-speaker system, two attenuator controls. 24" x 15" x 11½" deep.

MAXIM



MAGNUM-K



MEZZO II



AUDIO SUITE

(Top right) **MAXAMP 30** High Fidelity Stereo Amplifier. (Top left) **STEREOMAX** High Fidelity AM/FM Stereo FM Tuner. (Top centre) **MT1000** High Fidelity Record Player complete with arm and cartridge.

All Audio Suite and M-Range units are available in Walnut or Teak finish to order.

FREE Please send free copy of Goodman's High Fidelity Manual (tick which required) Audio Suite Booklet and the name of my nearest Goodman's Dealer.

Name _____

Address _____ WW 2/68

GOODMANS LOUDSPEAKERS LTD · AXIOM WORKS · WEMBLEY · MIDDX. Tel: 01-902 1200

WW-039 FOR FURTHER DETAILS

**custom-built
quality
mass
produced
quantity
computer-speed
delivery...**



Quality, quantity and speed . . . they all add up to Harwin precision turned-parts service!

Quality first. Pins, lugs, inserts - in fact any turned part for electronics must be precision-made. Harwin do it to order - any size, any shape.

Now quantity. Thousands? Millions? Harwin can do it at speed . . . with quick delivery and low costs.

**It all adds up to Harwin service.
Let us have your turned parts problem
....we know three ways we can
solve it better!**

Harwin do you a good turn! Turned parts - indicator units lugs - stand-offs - brackets - insulators - resistors terminal boards . . . and more.

HARWIN


HARWIN ENGINEERS LTD
FITZHERBERT ROAD
FARLINGTON, HANTS.
Tel: Cosham 70451/2/3

WW-040 FOR FURTHER DETAILS

CONTELEC


**WIREWOUND
ADJUSTMENT
POTENTIOMETERS**
** Now Ex-Stock*

T125 SERIES

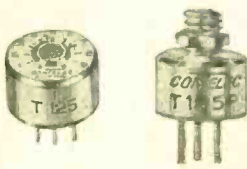

A really high quality single turn, humidity proof potentiometer. Resistance Range 10Ω to 50KΩ. Temperature Range 55°C to 150°C.

TYPE T84



A sub-miniature single turn humidity proof potentiometer. Resistance range 20Ω to 20KΩ. Temperature Range 55°C to 150°C.

*Full details of these
and other types from*

**W.GREENWOOD
(LONDON) LTD.**
21 GERMAIN STREET,
CHESHAM, BUCKS
Chesham
4808/9


WW-041 FOR FURTHER DETAILS

* Technically Proven For Exacting Performance



Model JR-500SE CRYSTAL CONTROL TYPE DOUBLE CONVERSION COMMUNICATION RECEIVER

- * Superior stability performance is obtained by the use of a crystal controlled first local oscillator and also, a VFO type 2nd oscillator.
- * Frequency Range: 3.5 MHz—29.7 MHz (7 Bands)
- * Hi-Sensitivity: $1.5\mu\text{V}$ for 10 dB S/N Ratio (at 14 MHz)
- * Hi-Selectivity: $\pm 2\text{ KHz}$ at -6 dB $\pm 6\text{ KHz}$ at -60 dB
- * Dimensions: Width 13", Height 7", Depth 10".

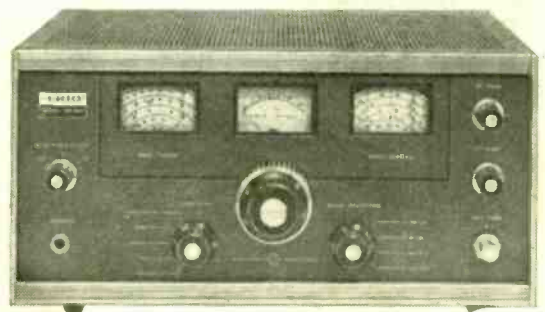

Model 9R-59DE BUILT IN MECHANICAL FILTER 8 TUBES COMMUNICATION RECEIVER

- * Continuous coverage from 550 KHz to 30 MHz and direct reading dial on amateur bands.
- * A mechanical filter enabling superb selectivity with ordinary IF transformers.
- * Frequency Range: 550 KHz to 30 MHz (4 Bands)
- * Sensitivity: $2\mu\text{V}$ for 10 dB S/N Ratio (at 10 MHz)
- * Selectivity: $\pm 5\text{ KHz}$ at -60 dB ($\pm 1.3\text{ KHz}$ at -6 dB) When use the Mechanical Filter
- * Dimensions: Width 15", Height 7", Depth 10".

TRIO

manufactured by TRIO Corporation, Tokyo, Japan.

Sole Agent for the U.K.

B.H. MORRIS & CO., (RADIO) LTD.


84/88, Nelson Street, London E.1, Phone : 01-790 4824

TO : B.H. Morris & Co., (Radio) Ltd.
84/88, Nelson Street, London E.1. ww
Send me information on TRIO COMMUNICATION
RECEIVERS & name of nearest TRIO retailer.

NAME :

ADDRESS :

WW-042 FOR FURTHER DETAILS

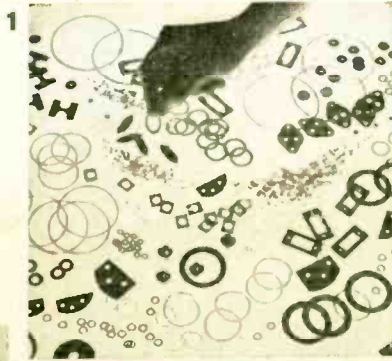


1




4

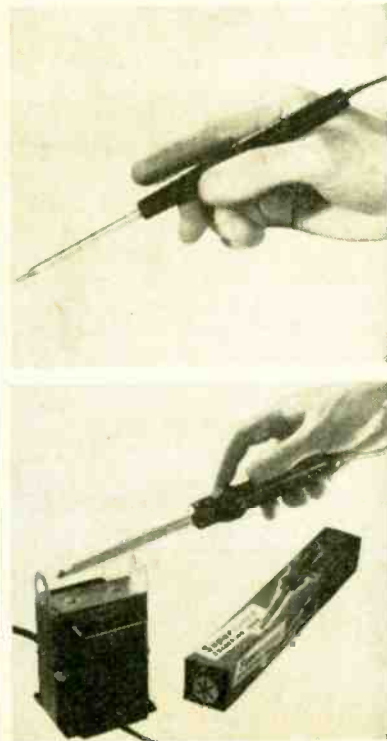Everything
you need for
precision
soldering
from
Enthoven




2

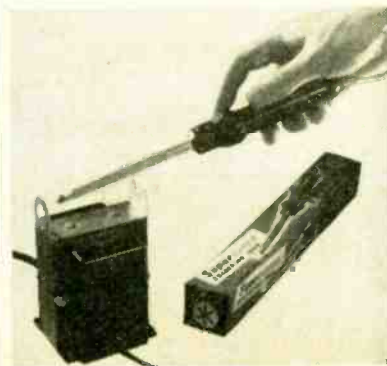

3




5

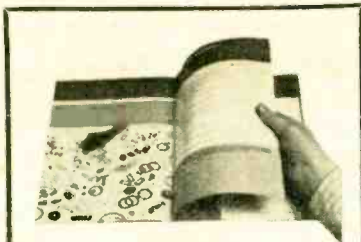

New free booklet describes the complete range of Enthoven Solder products. Ask now for your copy of 'Soldering with Enthoven.'

Tools, materials and knowledge. Two of the neatest irons ever made. The finest, most reliable materials—backed by over 150 years' experience of smelting and refining non-ferrous metals. And intimate knowledge of modern soldering techniques, the product of special experience built up over the years, confirmed when necessary in one of Europe's most advanced metallurgical laboratories. This is what Enthoven offer you. 1 Washers and preforms, cored and solid, standard and special. 2 Miniscope soldering iron for fine work. 3 Superspeed six-second heat soldering iron. 4 Preservative, metal, Tricene-de-oxidant, lacquer, flux, and thinners for printed circuits. 5 Superspeed solder . . . stellate cored, wide range of alloys, gauges and packings.

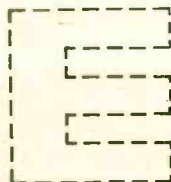


ENTHOVEN SOLDERS LIMITED

Head Office and Sales Office
Dominion Buildings South Place London EC2
Telephone: 01-628 8030

WW-043 FOR FURTHER DETAILS

SME

The best pick-up arm in the world

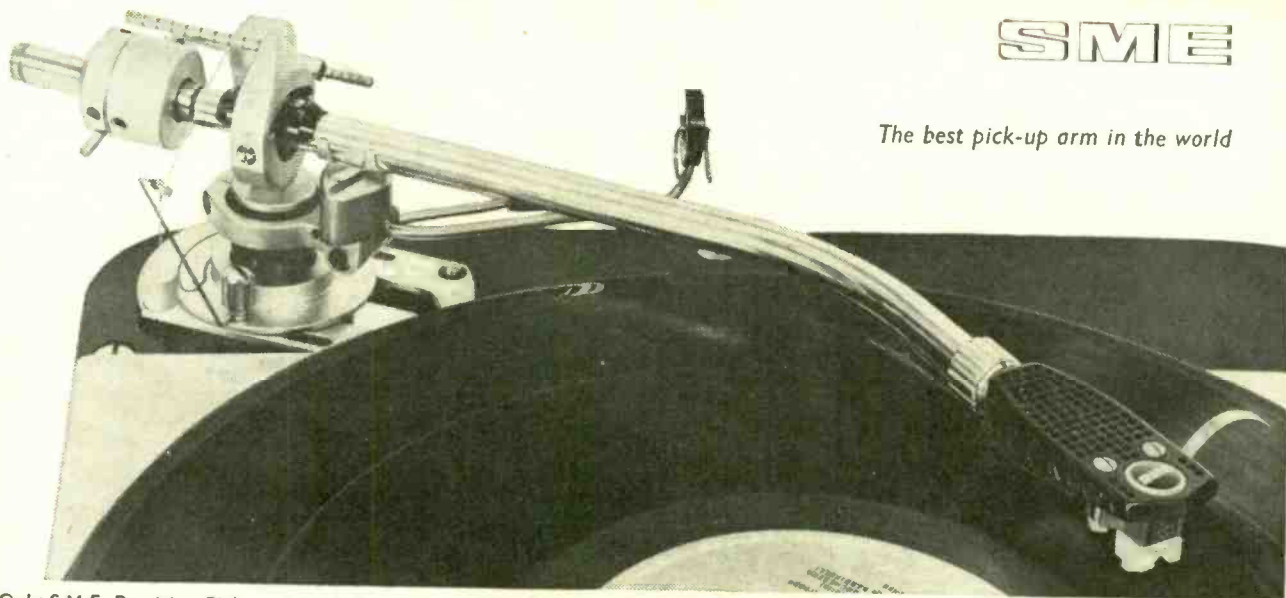


Only S.M.E. Precision Pick-up Arms offer all these features • Choice of arm length Model 3009 (9in.) or Model 3012 (12in.) for still lower tracking error—of special importance with elliptical styli • low inertia • High precision ball races and knife-edge bearings for minimum pivot friction • Linear offset chosen for lowest distortion • Automatic slow-descent with hydraulic control • Bias adjuster calibrated for tracking force • Exact overhang adjustment with alignment protractor • Precise tracking force from 1/4-5 grams applied without a gauge • Shielded output socket • Low capacity 4ft. connecting cable with quality plugs • Light-weight shell • Camera finish in satin chrome, gun-black and anodised alloy • Comprehensive instructions • Rational development—all improvements can be incorporated in any existing Series II arm.

For sales and service ring Steyning 2228

S M E LIMITED • STEYNING • SUSSEX • ENGLAND

WW-044 FOR FURTHER DETAILS


D.C. RELAY TYPE. R.3. TWIN

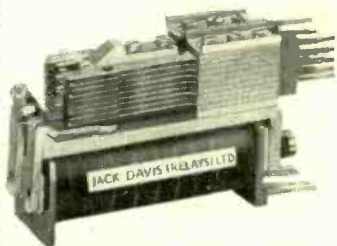

Twin coils and armatures.
Two completely independent relays in one.
A space and money saver!


MECHANICAL RELAY LATCH

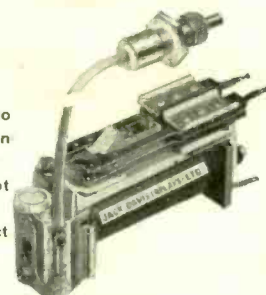Enables the P.O. 3000 type relay to be held in the closed position when the coil is de-energised and until manually released. Does not impair the versatility of the contact arrangements, nor affect the normal mounting position.



RELAYS

THE REMANENCE RELAY

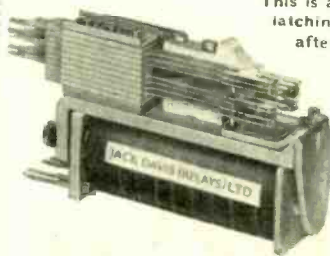

This is a 3000 type relay capable of latching in the energised position after the supply is removed until a suitable releasing current is applied in the opposite direction. This releasing current is controlled with a single coil, by reducing the operating current in reverse or with a double coil, via a pair of contacts employed on the relay to energise the second coil.

ELECTRO-MAGNETIC COUNTERS




MAJOR TYPE 6" × 1 1/2" × 1 1/2". Counts when coil is energised. 3V DC—220V DC. Speed approx. 8 per second.



MINOR TYPE 4 3/8" × 1" × 1". Counts when coil is de-energised. 3V DC 110V_{1/2} DC Speed approx. 10 per second.

JACK DAVIS (RELAYS) LTD. 9/10, Mallow Street, London, E.C.1
Telephone: CLerkenwell 3661-2

WW-045 FOR FURTHER DETAILS

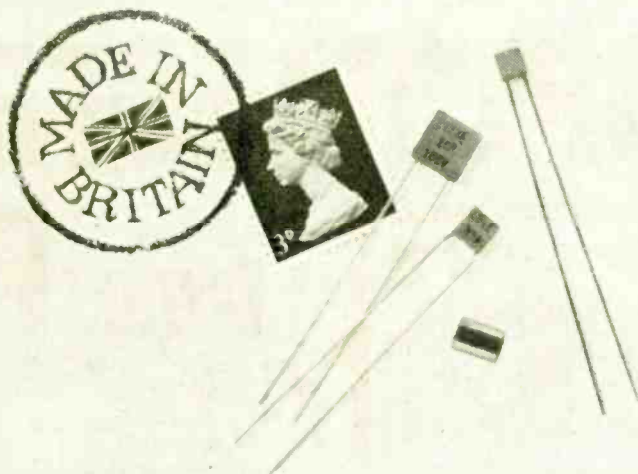

We make our monolithic capacitors in Britain

Monobloc ; an advanced product for sophisticated applications. A tiny component that has become the most exciting prodigy this side of the Atlantic. Its capacitance is vast, its size minute – up to 1 uf in $0.3 \times 0.3 \times 0.1$ in. (nine times smaller than a postage stamp). This capacitance-to-volume ratio is achieved by the unique monolithic construction. Wafer-thin ceramic dielectrics and platinum electrodes are fused into a solid, layered structure, to give a volumetric efficiency 10 to

100 times that of conventional capacitors. It's a rugged little device. The layered construction gives excellent stability and resistance to every form of shock and environmental stress.

We manufacture a preferred range, concentrated on the individual requirements of the British designer. There are other configurations available for more complicated designs : glass-encased, precision moulded, phenolic coated, and unencapsulated chips for hybrid integrated circuits.

The monolithic capacitor is already a pretty important contribution to the progress of modern electronics – our Monobloc Ceramicon design caters for projects of the future.

Contact us for the full details. Technical Sales,
Erie Resistor Limited,
South Denes,
Great Yarmouth, Norfolk.
Phone : 0493 4911
Telex : 97421

Monoblocs are featured in the 1968 edition 6 catalogue of S.T.C. Electronic Services.

Monobloc and Ceramicon are registered trade marks.



WW--046 FOR FURTHER DETAILS

A new science project combining the fascination of optics with electronics . . . the new field of

SUB LASER!

OPTOELECTRONICS

from PROOPS

Demonstrations of these devices operating as

SPEECH LINK
and
ON/OFF LINK

are being given daily at our only address.

52 TOTTENHAM COURT ROAD,
LONDON, W.1.

These new devices offer features which can be exploited in an extremely wide field of applications. Their outstanding modulation and switching capabilities, coupled with completely solid state circuit design and small physical size make them ideally suited to such purposes as short distance speech and data links, remote relay controls, safety devices, burglar alarms, batch counters, level detectors, etc.

MGA100



Post Free **28'6**
EACH

TYPE MGA 100 General Purpose Gallium Arsenide Light Source
A filamentless, Gallium Arsenide infra-red emitter, only 5.54 mm. dia. and 8.1 mm. long. Features a robust cylindrical package coaxial with the beam, facilitating optical alignment and heat-sinking.

MAX RATINGS

Forward current I_F max.* D.C. 400mA. Forward peak current I_F max.* (pk) 6A
Power dissipation* 600mW. Derating factor for T_{amb} greater than 25°C° 7.5mW/°C
Reverse voltage V_R max. 1-0V.

*When mounted on an aluminium heat sink 1in. X 1/2in. X 1/4in.

Supplied complete with suitable lenses, full Technical Data and Application Sheets, including Line of Sight Speech Link.


TYPE MSP3 Solid State Photo Receiving Device

An ultra-sensitive infra-red and visible light detector, this device is a complete silicon photo-electric receiver with a peak spectral response at 9500A. Size only 6.4 mm. dia. and 25.4 mm. long, yet absolutely complete, the device will generate sufficient power to drive an external relay. Chiefly intended for use in optical links based on Gallium Arsenide Light Sources, they are equally suitable for systems based on visible light. Features a robust cylindrical package coaxial with the incident light facilitating optical alignment and heat-sinking.

MAX RATINGS

Total dissipation (In free air, T_{amb} 25°C) 100mW. Derating Factor 2mW/°C
Output Current Intensity 100mA. Voltage 25V. Operating Temperature from 30° to +125 C.

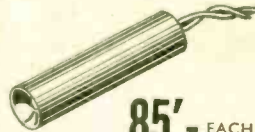Supplied complete with suitable lenses, full Technical Data and Application Sheets, including Line of Sight Speech Link.



85' - EACH
Post Free

MSP3

31F2



Post Free

Type 31F2 Micro-miniature Infra-Red Detector

Extremely small photo diodes of silicon NPN passivated planar construction and suitable for Punched Card Readers, Counters, Film Sound Track, etc.

Supplied complete with suitable lenses, full Technical Data and Application Sheets including Line of Sight Speech Link.

PROOPS BROTHERS LIMITED

52 Tottenham Court Road, London, W.1.
Telephone: LANgham 0141 (01-580 0141)

And these new solid state devices

RCA TRIACS Type 40432

Intended primarily for phase control of A.C. loads in light dimming, universal and induction motor control, heater control, etc., these gate controlled full-wave A.C. silicon switches, with integral trigger, switch from a blocking state to a conducting state for either polarity of applied voltage with positive or negative gate triggering.

Supplied complete with full Data and Application Sheets.



45' - EACH
Post Free


INTEGRATED CIRCUIT RCA-CA 3020 AF POWER AMPLIFIER & PRE-AMPLIFIER (or servo-amplifier)

The RCA-CA 3020 is an integrated-circuit, Multistage, Multi-Purpose AF Power Amplifier on a single monolithic silicon chip, providing a stabilized direct-coupled amplifier, performing pre-amp., phase inverter, driver and power output functions without transformers, and with one power supply suitable for sound, communications and control systems.

Supplied complete with full Data and Application Sheets.



42' - EACH
Post Free

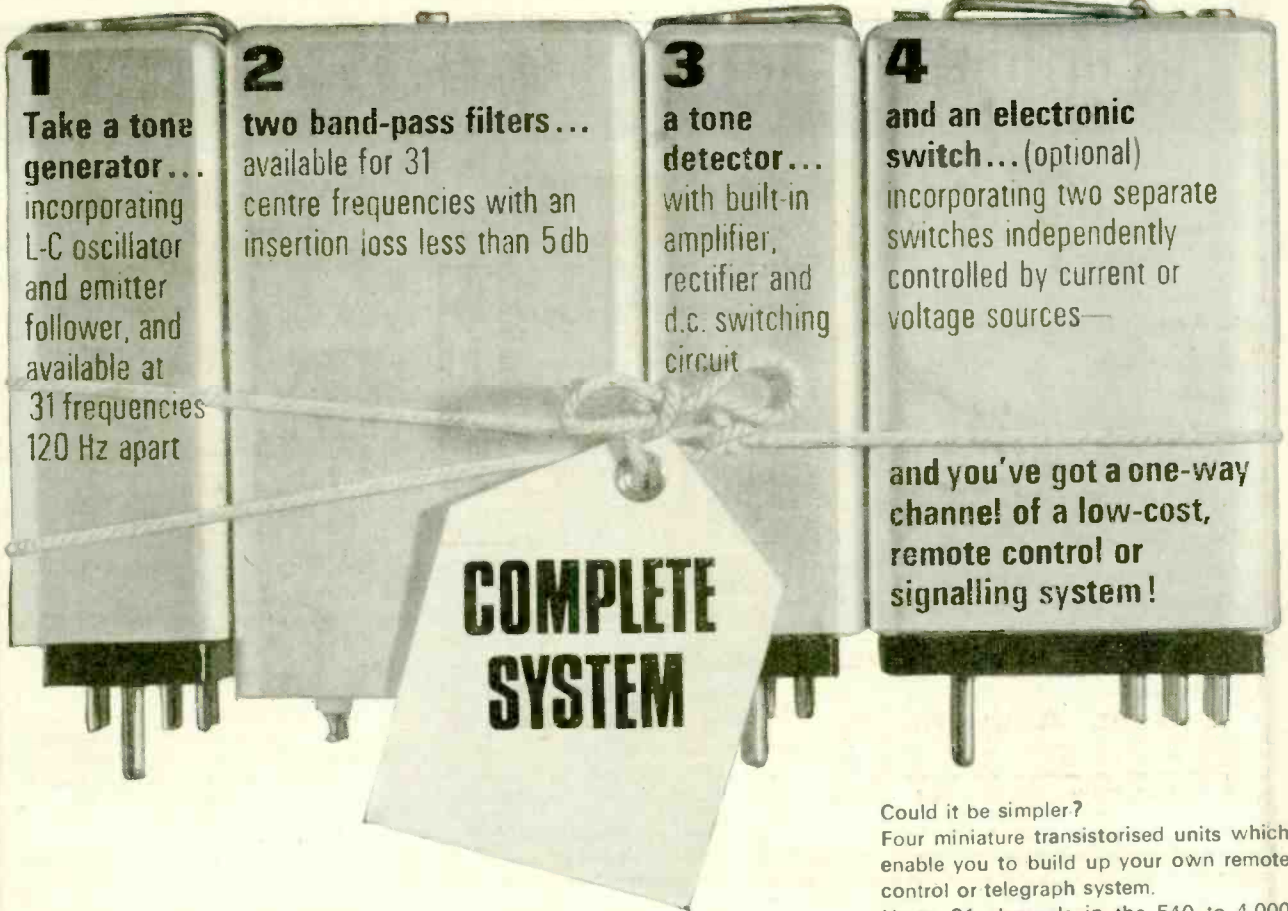

1 Take a tone generator... incorporating L-C oscillator and emitter follower, and available at 31 frequencies 120 Hz apart

2 two band-pass filters... available for 31 centre frequencies with an insertion loss less than 5db


3 a tone detector... with built-in amplifier, rectifier and d.c. switching circuit

4 and an electronic switch... (optional) incorporating two separate switches independently controlled by current or voltage sources—

and you've got a one-way channel! of a low-cost, remote control or signalling system!

COMPLETE SYSTEM

Could it be simpler?
 Four miniature transistorised units which enable you to build up your own remote control or telegraph system.
 Up to 31 channels in the 540 to 4,000 Hz range.
 Suitable for wire or radio link.
 Plug into standard type-3,000 relay bases or our universal chassis.
 Low pass filter (2.7 or 2.3 kHz) just added to the range.
 Hybrid and line transformers available.
 Off-the-shelf delivery for common types.
 Want to know more? Just write to:
 The Plessey Company Limited
 A T & E (Bridgnorth) Division
 Bridgnorth, Shropshire, England
 Telephone: Bridgnorth 4621 Telex: 33373

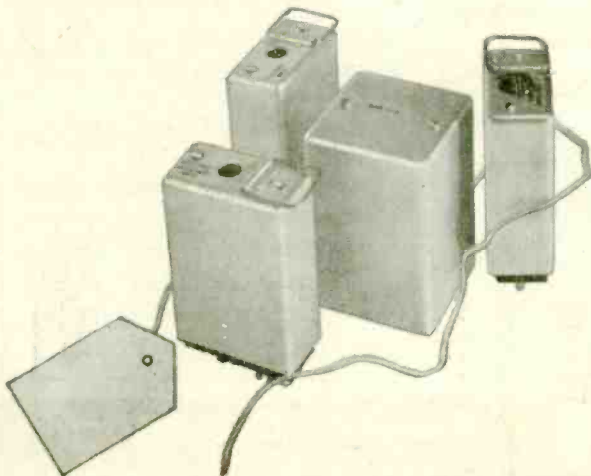


**PLESSEY
 Electronics**



WW-048 FOR FURTHER DETAILS

PE(RT)6A

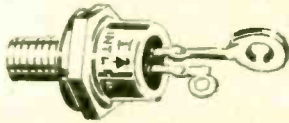
HARMSWORTH-TOWNLEY & CO. Components Dept. ask for
TODMORDEN LANCS Todmorden 2601 extension 1



INTERNATIONAL RECTIFIER

Quality Semi-Conductors.
 Complete Rectifier Assemblies up to thousands of Amps, Diodes, Thyristors, Zeners, Encapsulated Bridges, Photocells, Klipsel Surge Protectors.
 For experiment and teaching:—
ZENER KITS, THYRISTOR KITS.

Bulletins and prices on request.

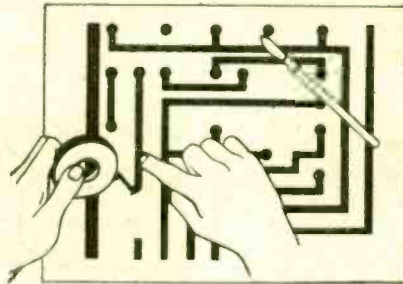

PRINTED CIRCUIT DRAFTING AIDS

Save drafting time and costs. Self-adhesive shapes and tapes. Terminal circles—fillets—tees—elbows—universal corners and mounting holes.

Bulletins and prices on request.

WW-049 FOR FURTHER DETAILS


ENGLISH ELECTRIC



GS FUSES


or the protection of rectifiers and thyristors.

Bulletins and prices on request.

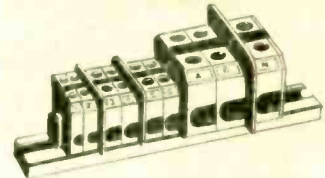


Rail Mounted Terminals and Terminal Blocks 0.5-250 Amps.

Bulletins and prices on request.

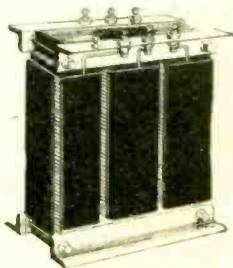


TRANSFORMERS

0.25 kVA to 300 kVA
 1 phase and 3 phase

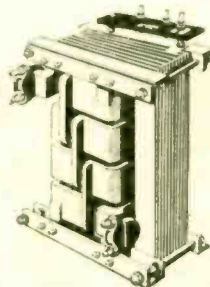

LOW VOLTAGE HIGH CURRENT TRANSFORMERS

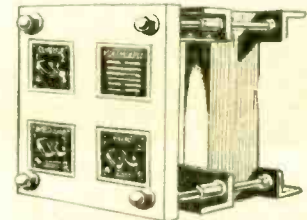with output currents of hundreds, thousands and tens of thousands of amps.
 1 phase and 3 phase.



VOLTMOBILES

64 steps on load switching Auto-Transformers. 1 phase and 3 phase. 20-400 Amps.
 Zero to 100% Volts or 125% of Input Volts.
 Voltmobiles are low-cost controllers, for furnaces, rectifier sets and other loads.

LET US HAVE YOUR SPECIFIC REQUIREMENTS



DC POWER SUPPLIES

For Magnets, Accelerators, Plating, Anodising, Spectroscopy, Plasma Arc, Toronto Arc, Electron Beams, Electrolysis, Welding, Quartz Lamps, Mercury Vapour Lamps. From 100 W to 200 KW.

HARMSWORTH-TOWNLEY & CO. Equipment Dept. ask for
TODMORDEN LANCS Todmorden 2601 extension 3


WW-050 FOR FURTHER DETAILS

SANSUI isn't just a pretty face (although every unit is superbly styled) and the vital statistics prove it!



MODEL 1000A
AM/FM Multiplex Stereo Tuner Amplifier

This is a high-quality, tubed unit that uses the latest Nuovistor devices and power tubes. Other features include High-cut and Low-cut Filters for virtually interference-free enjoyment, a Muting switch that further reduces noise, and an Automatic Frequency Control switch to eliminate 'drift'.
 RMS power: 40/40 W.
 Music power: 100 W (IHFM).
 Harmonic distortion: 1.0% at 1000 Hz RMS rated power output.
 Overall frequency response: 20-20,000 Hz \pm 1 dB.
 FM sensitivity: 1.8 μ V (IHFM).

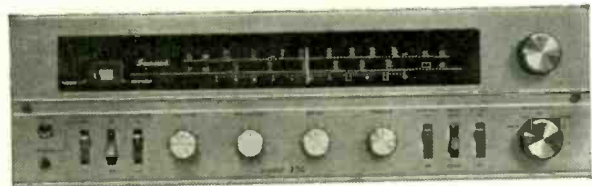

MODEL 250
AM/FM Multiplex Stereo Tuner Amplifier

A high-performance, tubed unit with many studio-equipment features. And at a modest price.
 RMS power: 10/10 W.
 Music power: 22 W (IHFM).
 Harmonic distortion: 1.5% RMS rated power output.
 Frequency response: 30-20,000 Hz \pm 2 dB at normal listening level.
 FM sensitivity: 4.0 μ V (IHFM).
 AM sensitivity: 30 μ V (IHFM).
MODEL 220 — AM/FM Stereo Tuner Amplifier
 A similar model to the 250, but without multiplex.



MODEL 500A
AM/FM Multiplex Stereo Tuner Amplifier

A tubed unit with a similar performance to the 1000A, but giving a lower power output.
 RMS power: 23/23 W.
 Music power: 50 W (IHFM).
 Harmonic distortion: 1.0% at 1000 Hz RMS rated power output.
 Frequency response: 20-20,000 Hz \pm 1.5 dB at normal listening level.
 FM sensitivity: 2.0 μ V \pm 3dB (IHFM).

Other equipment in the superbly styled Sansui range

- MODEL 3000A — Solid-state AM/FM Multiplex Stereo Tuner Amplifier. RMS power: 48/48 W. \pm 1 dB.
- MODEL 2000 — Solid-state AM/FM Multiplex Stereo Tuner Amplifier. RMS power: 32/32 W.
- MODEL AU-777 — Solid-state Stereo Control Amplifier. RMS power: 30/30 W.
- MODEL AU-70 — Stereo Control Amplifier. RMS power: 12/12 W.
- MODEL TU-70 — AM/FM Multiplex Tuner. FM: 88 to 108 MHz. AM: 535 to 1605 kHz.

Stereo Headphone SS-2 — Hi-Fi Speaker Systems —

- SP-50 — 2-way, 2-speaker system, 25 W.
- SP-100 — 3-way, 3-speaker system, 25 W.
- SP-200 — 3-way, 5-speaker system, 40 W.
- SP-300 — 3-way, 4-speaker system, 50 W.

Sansui

Sole U.K. Distributors:
Technical Ceramics Limited
 Cheney Manor, Swindon, Wiltshire. Telephone: Swindon 6251.

Accredited Midland & Northern Distributors to the retail trade
Audio Distributors Limited
 4 Lion Street, Kidderminster, Worcestershire
 Telephone: Kidderminster 3293

For complete details and fully illustrated colour leaflets, please send the coupon below, indicating the equipment in which you are interested, to:


Technical Ceramics Limited, Cheney Manor, Swindon, Wilts.
 Please send me fully illustrated leaflets, and advise me of the nearest Sansui Hi-Fi dealer.

Name _____
 Address _____

 _____ Model _____

WW-051 FOR FURTHER DETAILS

voltage problems?

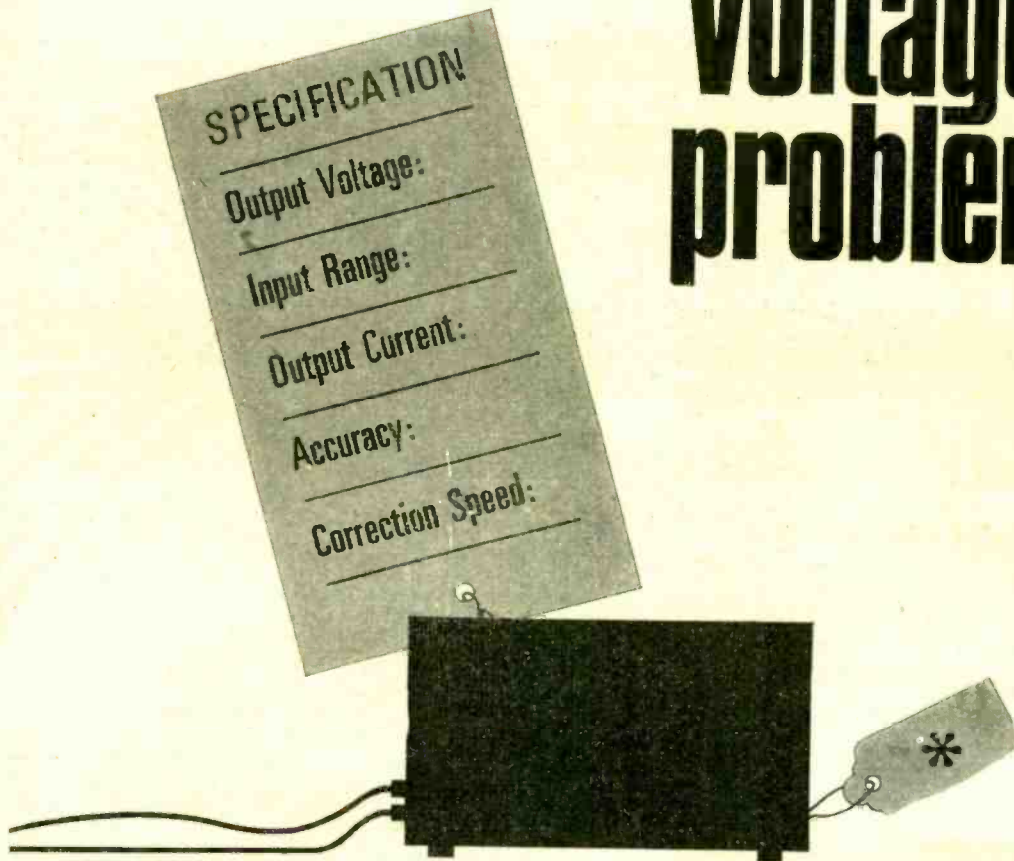

there is a standard
Claude Lyons voltage stabiliser
 already built to
***your* specification**
 * *and that includes price*

Claude Lyons make the most comprehensive range of voltage stabilisers available today. You will almost certainly find the stabiliser to suit your application in the Claude Lyons standard catalogue range. Distortionless servomechanical types from 1 to 120 kVA (and 360 kVA 3-phase). Solid-state types from 400 VA to 10 kVA. Simple tap-changing types from 600 VA to 2.4 kVA. All very high quality. All very reasonably priced. Full facts and figures from Publicity Department, Hoddesdon.

Claude Lyons Ltd ■ Valley Works, Hoddesdon, Herts. Hoddesdon 67161. Telex 22724. ■ 76 Old Hall Street, Liverpool 3. MARitime 1761. Telex 62181

CLAUDE LYONS


LEADER IN VOLTAGE CONTROL




WW-052 FOR FURTHER DETAILS

NOW MADE BY RESLOSOUND

Chapman Stereo Tuners

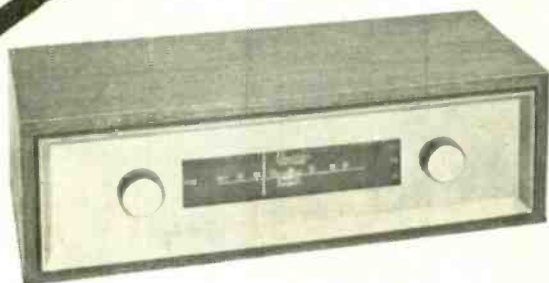

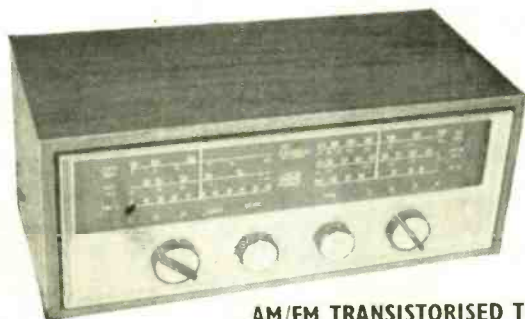VHF/FM TRANSISTORISED TUNER
type FM.1000A/B FM. 80-108
Mc/s. only. £28. + P.T. £5.12.7.



AM/FM TRANSISTORISED TUNER
type FM.1005A/B. Long, Med-
ium and two Short wavebands.
FM. 80-108 Mc/s. £48. + P.T.
£9.13.0.



AM/FM VALVE TUNER type S6BS/FM MK.II.
The finest Tuner in the Chapman range.
Medium and two Short wavebands, also six
bandspread ranges on 11, 13 16, 19, 25, 31
metres. FM. 80-108 Mc/s. FM. Stereo Decoder
optional extra. Much in demand overseas for
its exceptionally good short wave reception.
£64. + P.T. £12.17.5.

The Chapman range of High Fidelity Tuner units can be optionally fitted with multiplex decoders for stereo broadcast reception. Models FM.1000A/B and FM.1005A/B are also available in chassis form for fitting in owner's cabinet.

For Sales or Service write or 'phone

RESLOSOUND LTD Chapman Division



RESLO WORKS · SPRING GARDENS
ROMFORD · LONDON
Tel: ROMFORD 61926 (3 Lines)



RESLO also manufacture a complete range of public address
equipment, including amplifiers; reflex horns, cabinet and line
source loudspeakers; ribbon and dynamic microphones.

WW—053 FOR FURTHER DETAILS


Audix SOUND SYSTEMS
& ELECTRONICS

SILICON TRANSISTOR AMPLIFIERS

MODEL

A 80 — 70 WATTS.

A 25 — 30 WATTS.

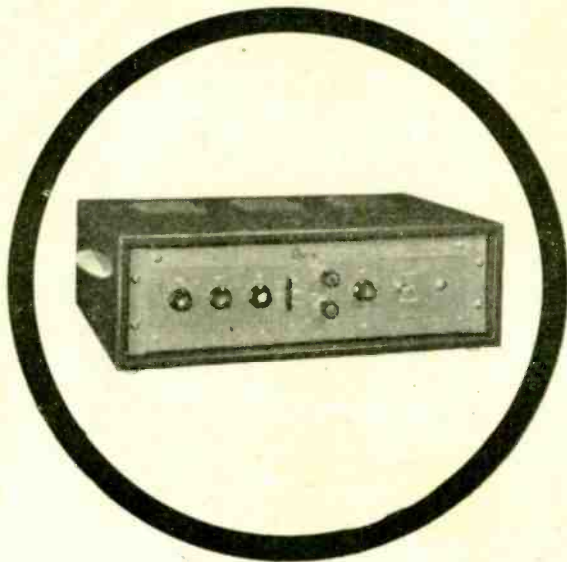

Five channel inputs—two mic, aux., gram., tape, and tape record master gain control, low distortion, standard rack or cabinet mounting, modular construction.

MODEL A.80. A.C. Mains. Dimensions 22in. wide x 7½in. high x 11½in. deep. Weight 40 lbs.

MODEL A.25. A.C. Mains. Dimensions 22in. wide x 5in. high x 8½in. deep. Weight 27 lbs.

WRITE FOR CATALOGUE AND PRICE LIST

Audix SOUND SYSTEMS

STANSTED, ESSEX.

TELEPHONE:— STANSTED 3132/3437

WW—054 FOR FURTHER DETAILS

CALL UP SCAM

THE MOST ADAPTABLE TELESCOPIC MAST IN SERVICE

SCAM Telescopic Masts are the most versatile in the World. They come as complete kits ready for immediate erection in the field. They are freestanding with easily fitted guys for the worst winds. Alternatively they are easily fitted by simple brackets to any vehicle. There are 3 models, 30, 40 or 50 feet extended. Each has the same design features and the same well-ried system of extension—just air from the handpump in the kit.

If you are in military communications you should know more about SCAM. Write to us now.

SCAM 40 Mast in action. NATO Stock Ref. 5820-99-105-3397.



CLARK

A. N. CLARK (ENGINEERS) LIMITED


BINSTEAD — ISLE OF WIGHT

Telephone: RYDE 3691 Telegrams: TELEMAT RYDE

AN ASSOCIATE COMPANY OF COUBRO & SCRUTTON
WW—055 FOR FURTHER DETAILS

CHOSEN FOR VITAL CIVIL AND MILITARY ROLES BY OVER FORTY GOVERNMENTS THROUGHOUT THE WORLD —

TEONEX VALVES

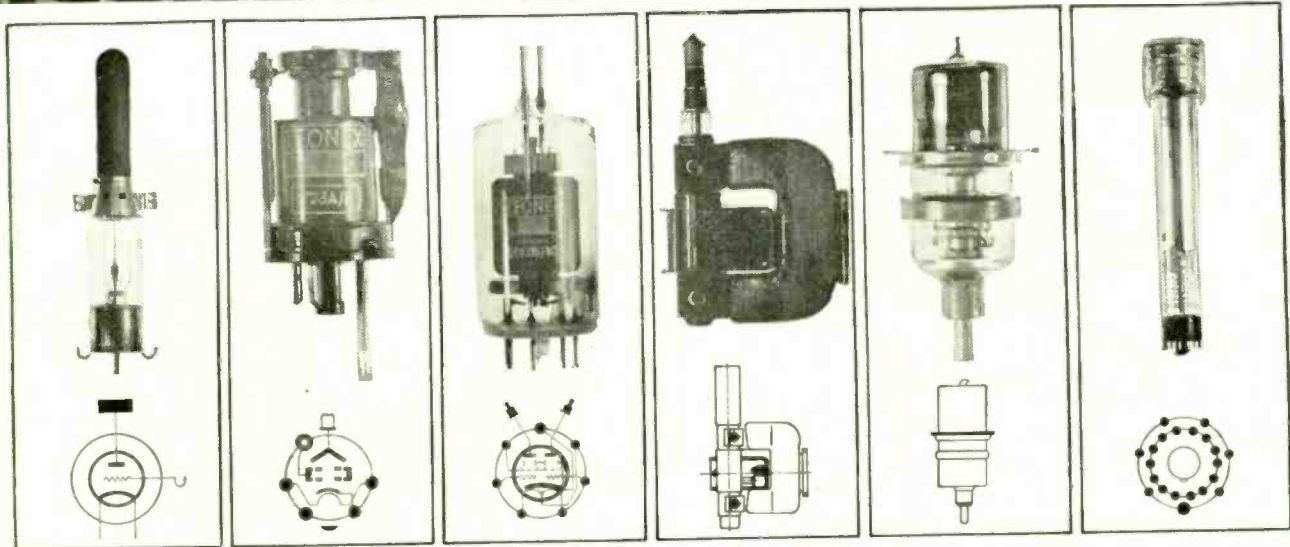

The same safeguards in manufacture and control that have won government contracts for TEONEX in over forty different countries apply equally to ensure top quality for private users too. When you require valves to comply with E.V.S. or M.I.L. standards — choose TEONEX. The TEONEX range (for use outside the U.K. only) incorporates the entire series of British-produced valves or their Continental equivalents, including a wide range of colour T.V. valves. Price list and technical specifications may be obtained from: -


Export Enquiries Only Please!

TEONEX LIMITED


2a, Westbourne Grove Mews,
London, W.11
England.



WW-056 FOR FURTHER DETAILS

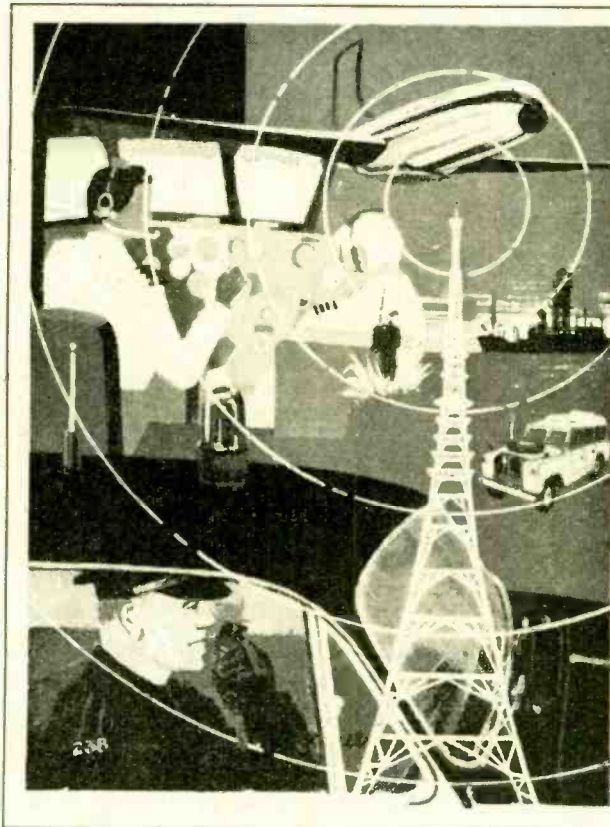

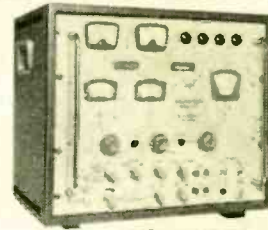331.C FREQUENCY METER AND STANDARD SIGNAL GENERATOR



NATO STOCK NO. 6625-99-104-4293 (CT 551)

Combines the ease of operation and readout of a counter with the versatility and sensitivity of a heterodyne wavemeter.

- Wide range (DC-3000 Mc/s) ● Very high sensitivity ● Magic eye zero beat detection ● Extremely stable reference standard (5 parts in 10¹⁰)
- Reading accuracy of ± 1 cycle ● 37000 Standard Frequencies available phase-locked to Crystal ● Automatic Harmonic Identification ● Many other built-in facilities ● Environmentally tested to DEF 133

Write for further details to:

J.A.C. ELECTRONICS LIMITED

BLACKWATER CAMBERLEY SURREY CAMBERLEY 5399

A MEMBER OF SOUTHERN INSTRUMENTS GROUP

WW-057 FOR FURTHER DETAILS

M. R. SUPPLIES, LTD., (Established 1935)

Universally recognised as suppliers of UP-TO-DATE MATERIAL, which does the job properly. Instant delivery. Satisfaction assured. Prices nett.

FANFLOW EXTRACTOR FANS. Undoubtedly to-day's greatest bargain for domestic or industrial use. For 200/250 volts A.C. 7,500 cu. ft. per hour. Easily installed, fitted weatherproof louvers which open when motor is switched on and closed when off. Only 6 1/2 in. dia. Our nett price only **£6/15/-** (despatch 4/6).

ELECTRIC FANS (Paper), for extracting or blowing. The most exceptional offer we have yet made. 200/250 v. A.C. Induction motor—silent running. 2,800 r.p.m. duty 100 C.P.M. Only 4 1/2 in. square and 2 in. deep. Ideal for domestic or industrial use. Easy mounting. **£3/5/-** (des. 3/6).

SMALL GEARED MOTORS. In addition to our well-known range (List GM.564) we offer small open type R.P. Units, 200/250 v. A.C., 1, 4, 12, 24, 60 r.p.m., approx. 5 in. long, with 1 in. shaft projection each side and enclosed gearbox. Suitable for display work and many industrial uses. Only **60/6** (des. 3/-).

SYNCHRONOUS TIME SWITCHES. (Our very popular speciality), 200/250 v. 50 c. for accurate pre-set switching operations. Bangamo B.254 providing up to 3 on-off operations per 24 hours at any chosen time, with day-omitting device (see optional). Capacity 20 amps. Compactly housed 4 in. dia., 3 1/2 in. deep. **£5/18/6** (des. 4/6). Also same excellent make new Domestic Model no wiring and easy setting and installation. Portable with lead and 13-amp. plug, same duty as above (less Day-omitting). **£4/9/6** (des. 4/6). Full instructions sent with each.

MINIATURE COOLING FANS. 200/250 v. A.C. With open type induction motor (no interference). Overall 4 in. x 3 1/2 in. x 2 1/2 in. Fitted 6-bladed metal impeller. Ideal for projection lamp cooling, light duty extractors, etc., still only **25/8** (des. 4/6).

MINIATURE RUNNING TIME METERS (Bangamo). We have great demands for this remarkable unit and can now supply immediately from stock. 200/250 v. 50 c. synchronous. Counting up to 9,999 hours, with 1/10th indicator. Only 1 1/2 in. square, with cyclometer dial, depth 2 in. Many industrial and domestic applications to indicate the running time of any electrical apparatus, easy to install. **60/-** (post paid).

AIR BLOWERS. Highly efficient units fitted induction totally enclosed motor 250/260 v. 50 c. 1 ph. Model 8D.26, 60 CFM (free air) to 11.5 CFM at 15 WG (size approx. 1 6/8 x 6 x 7 in. Outlet 2 1/2 in. square, **£8/10/-** (des. 5/-). Model 8D27, 120 CFM (free air) to 40 CFM at 1.2 WG, 8 x 7 x 9 in., outlet 2 1/2 in. sq., **£11/15/6** (des. 5/-). Model 8D28, 250 CFM (free air) to 127 CFM at 1.5 WG, 11 x 8 x 9 in., outlet 3 in. sq., **£13/17/6** (des. U.K. 7/6).

SYNCHRONOUS ELECTRIC CLOCK MOVEMENTS (as mentioned and recommended in many national journals), 200/250 v. 50 c. Self-starting. Fitted spindles for hours, minutes and central sweep second hands. Central one-hole fixing. Dia. 2 1/2 in. Depth behind dial only 1 1/2 in. With back dust cover. **35/-** (des. 1/6). Set of three brass hands in good plain style. For 5 7/16 in. dia. 2/6. For 8 1/16 in. dia. 3/6 set.

SYNCHRONOUS TIMER MOTORS (Bangamo). 200/250 v. 50 c/s. Self-starting 2 in. dia. x 1 1/2 in. deep. Choice of following speeds: 1 r.p.m., 12 r.p.m., 1 r.p.h., 1 rev. 12 hours, 1 rev. per day. Any one **39/6** (des. 1/6). Also high-torque model (G.E.C.), 2 1/2 in. x 2 in. x 1 1/2 in. 9 r.p.m., **57/6** (des. 1/6).

IMMEDIATE DELIVERY of Stuart Centrifugal Pumps, including stainless steel (mini models). Philips Variable Transformers (all models).

M. R. SUPPLIES, Ltd., 68 New Oxford Street, London, W.C.1
(Telephone: 01-636 2958)

Valradio TRANSVERTORS (TRANSISTORISED D.C. CONVERTERS/INVERTERS)



TYPE B12/200S.
PRICE £67-12-0

INTRODUCING THE VALRADIO "B" SERIES
SINEWAVE output 200W (120W also available).
FREQUENCY: 50 c/s ± 1 c/s (60 c/s to order).
OUTPUT V.: 115-230 v. $\pm 10\%$.
INPUT V.: 12 v. $-10\% + 25\%$ (24-50 v. also available).

- ★ FREQUENCY REGULATION OF $\pm 0.05\%$ WITH ADDITIONAL "RESONATOR".
- ★ INFINITE LIFE.
- ★ WILL OPERATE ALMOST ANY ELECTRONIC OR ELECTRICAL EQUIPMENT.
- ★ SUITABLE FOR SUPER-SENSITIVE RADIO & AUDIO EQUIPMENT.


OTHER MODELS from £10 to £179/12/- 12 v. to 110 v. D.C. up to 1kW
VALRADIO LTD., Dept. C10

BROWELLS LANE · FELTHAM · MIDDLESEX · ENGLAND
Telephone: FELTHAM 4837-4242 01-890 4837/4242

VALRADIO and STEREOSONOSCOPIES are the registered trade marks of VALRADIO LTD.

WW-058 FOR FURTHER DETAILS

Rely on **ADVANCE** to do it better

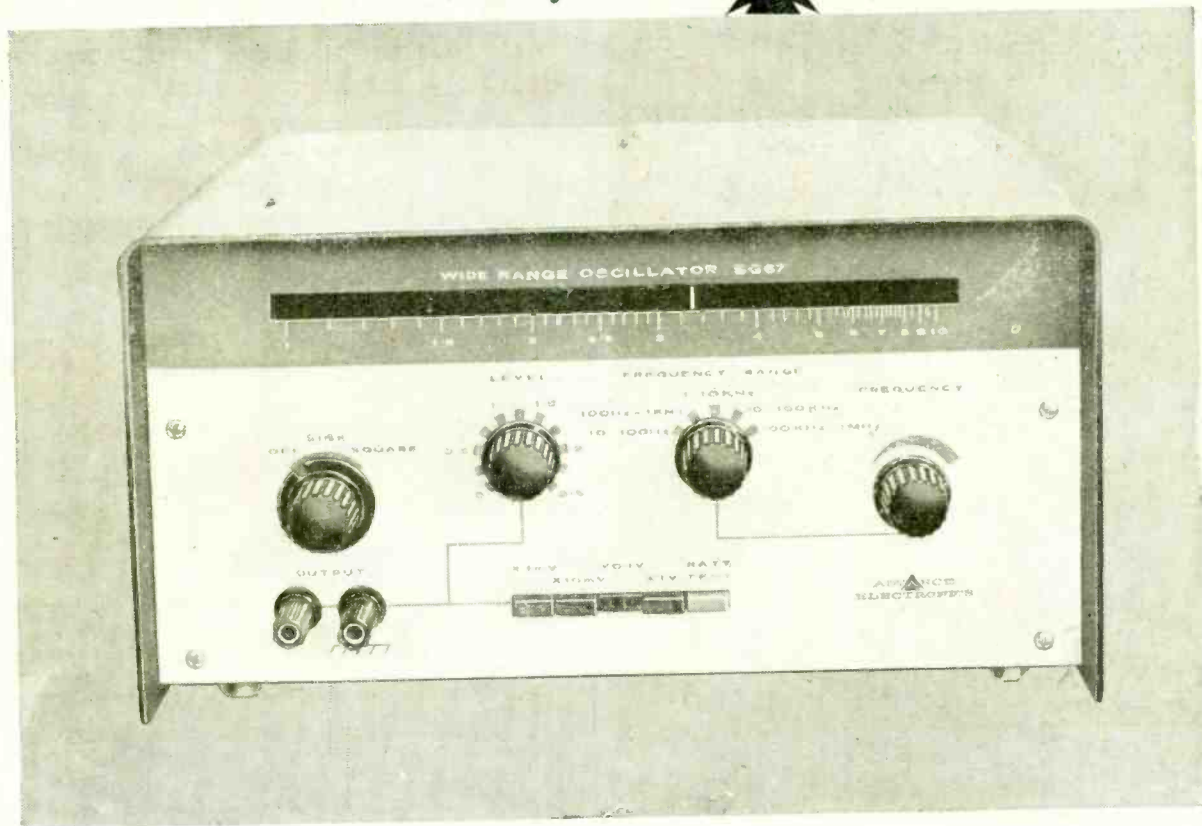

NEW

Wide Range Oscillator SG67

10Hz-1MHz Frequency Range

Sine wave or square wave

Frequency is continuously variable in five switched ranges covering 10Hz to 1MHz. Sine wave or square wave output selected by a switch.

Amplitude is controlled by a variable level control in conjunction with a four-position push-button attenuator giving an output up to 2.5Vr.m.s.

The SG67 is compact and portable, can be run from internal batteries or mains. Send for full specification now.


**ADVANCE
INSTRUMENTS**

Hainault Essex England. Telephone 01-500 1000. Telegrams Attenuate Ilford. Telex 263785

Division of **ADVANCE ELECTRONICS LIMITED**
WW-059 FOR FURTHER DETAILS

Pat. 110
mono-bloc
connectors
with
closed entry
contacts

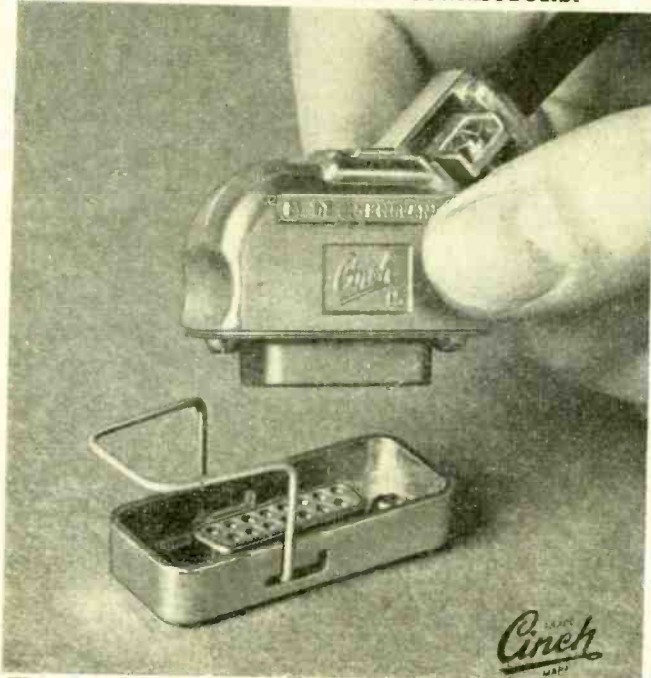FULLY APPROVED TO DEF 5925-5 STANDARD FOR
9, 15, 25, 37 AND 50 WAY CONNECTORS.




These connectors consist of one-piece Diallyl Phthalate moulding with hard gold plated plug pins, socket contacts, and beryllium copper contact clips. Closed entry contact design eliminates the risk of damage to the sockets by test probes. The shells are of passivated cadmium plated steel and the covers and cable clamps are of die-cast aluminium Grade LM6.

ELECTRICAL RATINGS Working voltage: 750 volts DC
Current capacity: 5 amps max per contact

CARR FASTENER CO LTD
the firm with the best connections

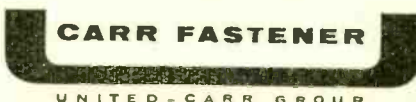Stapleford, Nottingham.
Telephone: Sandiacre 2661.
Sales offices: Wembley,
Birmingham, Sale, Glasgow.



WW-060 FOR FURTHER DETAILS

RADIONIC

RADIO & ELECTRONIC CONSTRUCTION SYSTEM


For professional or private use:

* INSTRUCTION

* EXPERIMENT

* DEVELOPMENT

An absorbing and exciting medium

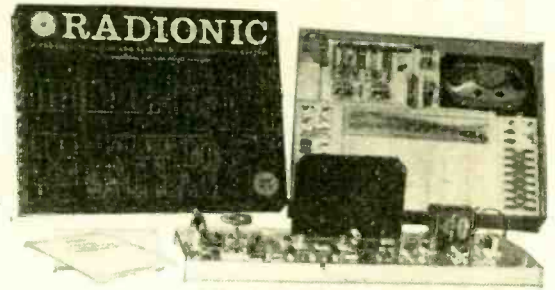

A No. 4 SET and 6-TRANSISTOR SUPERHET


Clear, simple versatile, this rugged system can build almost any electronic circuit. It is used by hundreds of educational establishments throughout the U.K.—Universities, Technical Colleges, Schools, the Armed Forces and Industry.

Selected by the Council of Industrial Design for all British Design Centres. Featured in Sound and Television broadcasts.


The system is beautifully engineered from top quality British components. No soldering. No mains. No prior knowledge needed. Simply arrange components on perforated transparent panel, position brass connecting strip underneath, fix with 6BA

nuts and circuit works with full efficiency. You can then dismantle and build another circuit. Your results are guaranteed by our Technical Department and News Letter Service. All parts available separately for conversion or expansion of sets.

- | | | |
|-----------|-----------|---|
| No. 1 Set | £6 0 2d. | 14 Circuits (Earphone) |
| No. 2 Set | £7 1 5d. | 20 Circuits (Earphone) |
| No. 3 Set | £11 2 7d. | 22 Circuits (7 x 4in. Loudspeaker output) |
| No. 4 Set | £15 3 8d. | 26 Circuits (include 6 Transistor and reflex superhets) |
- Prices (Post Free)

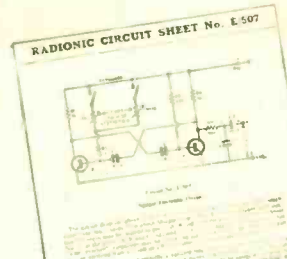

Theoretical Circuit.

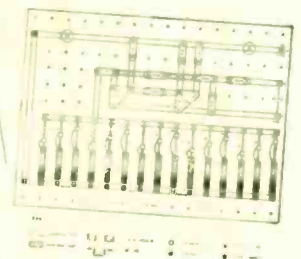

Practical Layout

Our 'E' Series of basic electronic circuits is available separately. (See Electronic Organ above)

SEND FOR DETAILS OF E/508—OUR DIGITAL COMPUTER

UNIQUE! Our "No soldering" printed circuit board for superhet portable. Simply insert components and tighten nuts.

Full details from:

RADIONIC PRODUCTS LIMITED
STEPHENSON WAY, THREE BRIDGES
CRAWLEY, SUSSEX

Tel. CRAWLEY 27028


Trade Enquiries invited

WW-061 FOR FURTHER DETAILS



RCA COLOUR TUBES

two totally unique advantages

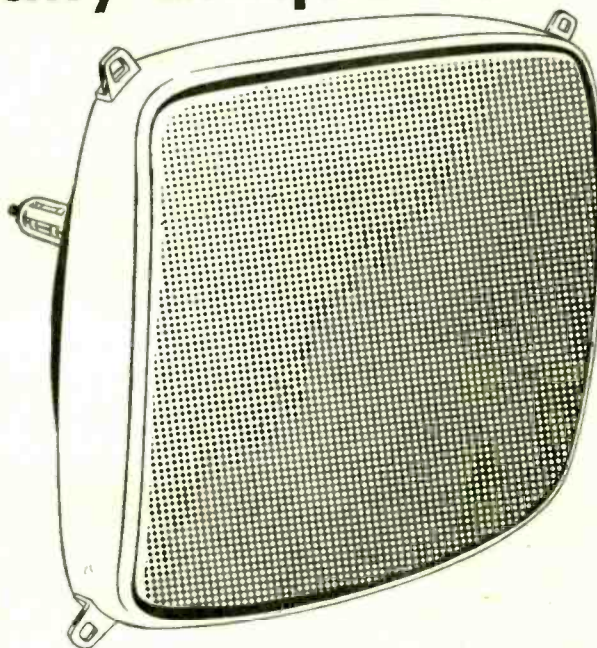

New Rare Earth Red Phosphor

These new red phosphors—exclusive to RCA—combined with efficient sulphide blue and green phosphors produce pictures at their brightest and most dependable. They completely overcome the imbalance of the three guns which cause red blooming, colour fringing and failure of the red gun due to overwork. RCA's New Rare Earth Red Phosphor achieves UNITY CURRENT RATIOS—equal beam current from each electron gun; higher brightness, picture contrast and highlight; much longer tube life.

Perma-Chrome

This is a four-point, temperature-compensated shadow mask assembly which accurately adjusts and sets the shadow mask position relative to the screen. Shadow mask expansion limits the performance of a rectangular colour-tube—Perma-Chrome renders this problem negligible. Perma-Chrome produces full-colour fidelity and temperature equilibrium throughout normal operation. It maintains excellent field purity and uniformity.

RCA 'HI-LITE' COLOUR PICTURE TUBES...

THE BRIGHTEST IN THE INDUSTRY

For full technical specification and application information, write to:

RCA COLOUR TUBES LTD · PINFOLD PLACE · PIMBO · SKELMERSDALE · LANCS · TEL: TAWD VALE 4951


WW-065 FOR FURTHER DETAILS

Belclere TRANSFORMERS


**SUB-MINIATURE AND MINIATURE TRANSFORMERS
WINDINGS AND ASSEMBLIES TO YOUR
SPECIFICATION — ALSO REED COILS**




PULSE WDG

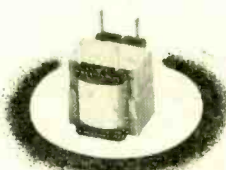


I. P. TFR.

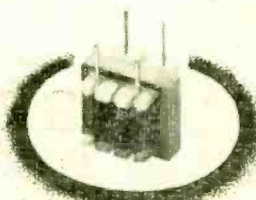

COUPLING TFR.

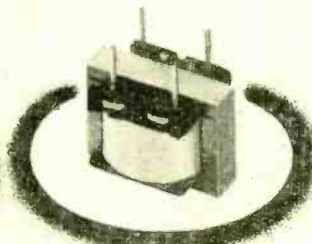

O. P. TFR.

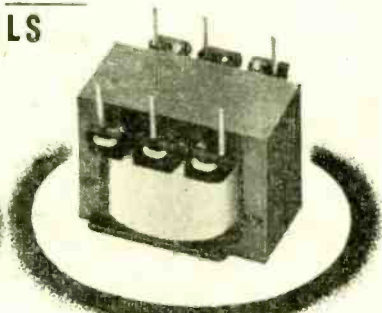

MAINS TFR.

(ILLUSTRATIONS—ACTUAL SIZE)

THE BELCLERE COMPANY LIMITED
COWLEY ROAD, OXFORD, ENGLAND.

Tel. Oxford 77266

WW-066 FOR FURTHER DETAILS

RE-CREATES THE FINER SHADES OF ORIGINAL SOUND


To re-create faithfully the finer shades of original sound, stored as complex mechanical patterns in the micro-grooves of modern records, calls for a cartridge in the precision instrument class. Goldring engineers have spent two years developing such a cartridge... the Goldring "800" Free Field Cartridge. At a comparatively modest cost this cartridge rivals the finest in the world, whilst at the same time guaranteeing the complete reliability for which the name "Goldring" has stood for sixty years in record reproduction.

**GOLDRING "800" FREE FIELD
STEREO CARTRIDGE £12.7.6**
tax paid

SPECIFICATION

Type	Magnetic—(Free Field)
Frequency Response	20 Hz—20 kHz
Sensitivity	1 mv. per cm/sec.
Separation	25dB at 1kHz and nowhere less than 15dB
Load	100k—47k/ohms
Compliance	20 x 10 ⁻⁶ cm/dyne
Stylus	0.0005" diamond replaceable
Effective Tip Mass	1 mg.
Tracking Weight	1—3 grms.
Head Weight	8 grms.
Vertical Tracking Angle	15°
Mu Metal Shield for hum protection.	

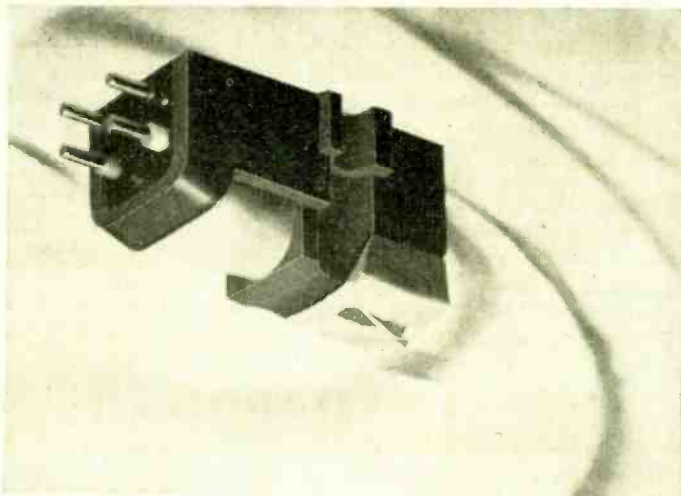GOLDRING '800' FREE FIELD STEREO CARTRIDGE




GOLDRING MANUFACTURING CO. (GREAT BRITAIN) LIMITED 486-488 High Road, Leytonstone, London, E.11

WW-067 FOR FURTHER DETAILS



STUMPI

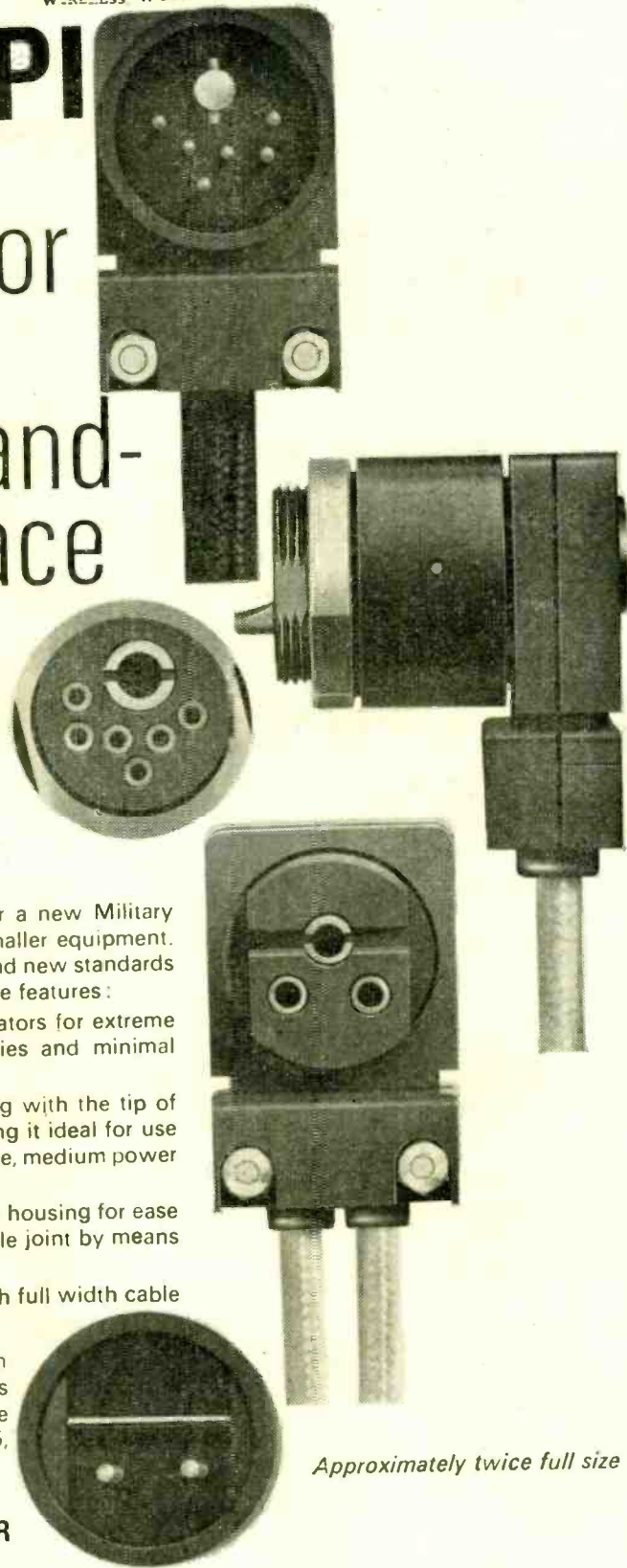a new
connector
for the
weight-and-
space race



— a new connector specifically designed for a new Military project and for the race toward ever lighter, smaller equipment. It uses the very latest materials to achieve brand new standards in compact, efficient design. Just look at these features:

1. Glass filled Nylon housings and insulators for extreme light weight, high insulation properties and minimal fire risk.
2. Compact design and positive coupling with the tip of one finger — low height feature making it ideal for use on portable equipment or as low voltage, medium power connectors.
3. "Split shell" construction of cable unit housing for ease of wiring. Elimination of strain on cable joint by means of right-angle contacts.
4. Crimp type contacts in cable unit, with full width cable clamp and sealing grommet.

The Stumpi range is a new conception in design, fully sealed, meeting the requirements of DEF.5325, and is initially available in three shell sizes with nominal contact ratings of 5, 20, 40 and 60 amps.

Approximately twice full size


**THERE IS A THORN CONNECTOR
FOR EVERY PURPOSE!**



THORN SPECIAL PRODUCTS LTD, Great Cambridge Road, Enfield, Middlesex. Tel: 01-363 5353 Telex: 263201-2-3. A subsidiary company of THORN BENDIX LIMITED

068 FOR FURTHER DETAILS

AP8

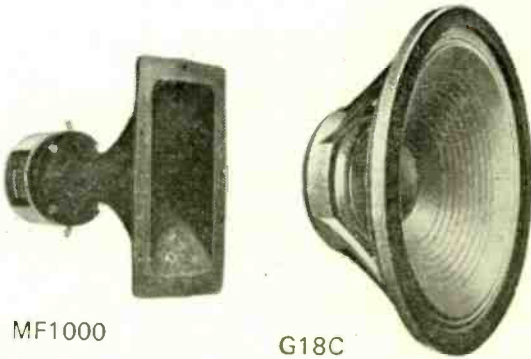

MF1000

G18C

GD972

Celestion POWER

loudspeakers for the perfectionist

—for guitars and organs


Write for Catalogue No: RCS162

Rola Celestion Ltd.

Ferry Works, Thames Ditton, Surrey, England.
Telephone: 01-398 3402 Telex: 266135

WW—069 FOR FURTHER DETAILS

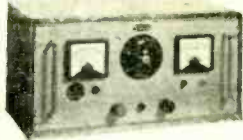**VARIABLE—HIGH CURRENT
SMOOTHED POWER SUPPLIES
WITH ACCUMULATOR PERFORMANCE
FROM A.C. MAINS**



PRICE: £131.5.0

- TYPES**
250VRU/30/20
250VRU/60/10
250VRU/120/5
250VRU/240/2.5

FEATURES. Type 250VRU 30/20. 0-30 v. Continuously Variable up to 20A.
RIPPLE CONTENT. Negligible. **IMPEDANCE and REGULATION** equivalent to accumulator performance **SILICON RECTIFIERS.** Inadvertent "SHORT" protection.
OVERLOAD CAPACITY. 200% for short periods. Supplied to M.O. Tech for servicing 28 v. aircraft instrumentation within B.C.A.R.'s. Ref. 10K CA3035. Suitable for "19" RACKMOUNTING.
FIXED OUTPUTS ALSO AVAILABLE Smoothed 12 or 24 v. up to 24A.
APPLICATIONS OPERATING AND SERVICING. Transistorised equipment e.g. 12-24 v. Mobile Radio Telephone. D.C. motors, etc., direct from AC—WITHOUT THE USE OF ACCUMULATORS.
AVOID THE EXTRA EXPENSE OF SUPER REGULATION YOU MAY NEVER NEED.

PRICES: £14.16.0 to £88.4.0.

Please write to
Department C3b
for current literature.



**BROWELLS LANE,
FELTHAM,
MIDDLESEX,
ENGLAND.**

Tel.: FELTHAM 4837-4242. 01-890-4837 4242

VALRADIO and STEREOSONOSCOPE are the registered trade marks of VALRADIO LIMITED.


WW—070 FOR FURTHER DETAILS

**TELEPRINTERS · PERFORATORS
REPERFORATORS · TAPEREADERS
EDITING & REPRODUCING SETS**

Codes: Int. No. 2 Mercury/Pegasus. Elliot 803.
Binary and special purpose Codes.



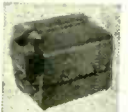**2-5-6-7-8 TRACK AND
MULTIWIRE EQUIPMENT**



TELEGRAPH AUTOMATION AND COMPUTER PERIPHERAL ACCESSORIES

Picture Telegraph, Desk-Fax, Morse Equipment; Pen Recorders; Switchboards; Converters and Stabilised Rectifiers; Tape Holders, Pullers and Fast winders; Governed, Synchronous and Phonic Motors; Teleprinter Tables and Cabinets; Silence Covers; Distortion and Relay Testers; Send/Receive Low and High Pass filters; Teleprinter. Morse, Teledeltos Paper, Tape and Ribbons; Polarised and specialised relays and Bases; Terminals V.F. and F.M. Equipment; Telephone, Carriers and Repeaters; Multiplex Transmitters; Diversity Frequency Shift, Keying Equipment; Line, Mains Transporters and Suppressors; Racks and Consoles; Plugs, Sockets; Key, Push, Miniature and other Switches; Cords, Wires, Cables and Switchboard Accessories; Teleprinter Tools; Stroboscopes and Electronic Forks; Cold Cathode Matrices; Test Equipment; Oscilloscopes; Miscellaneous Accessories and Spares.



W. BATEY & COMPANY

Gaiety Works, Akeman Street, Tring, Herts.
Tel.: Tring 3476 (3 lines) Cables: RAHNO TRING
STD: 044-282 TELEX 82362

WW—071 FOR FURTHER DETAILS

HF1300 Mk. 2



CX2012

GD974

Celestion Studio Series

loudspeakers for the perfectionist


—for high fidelity

Write for Catalogue No: RCS 2002

Rola Celestion Ltd.

Ferry Works, Thames Ditton, Surrey, England.
Telephone: 01-398 3402 Telex: 266135

WW—072 FOR FURTHER DETAILS

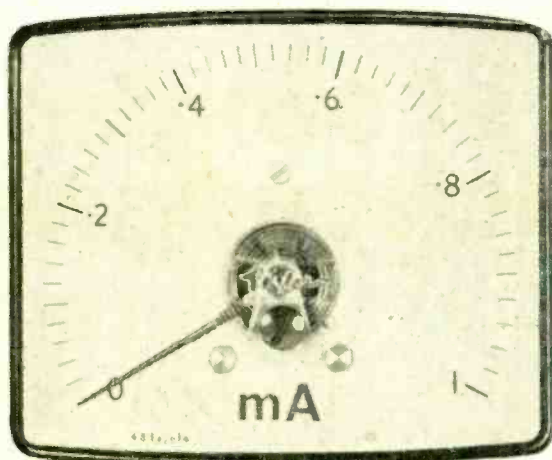

240° and fyne

The outlook is always favourable when you specify panel meters from the 'Wide Angle' range of Taylor Fynelines. These new Fynelines feature clear visibility of a precisely-marked full 240° scale. You get shadowless readings and the proven Taylor moving-coil movement with a standard accuracy of $\pm 2\%$ f.s.d. ($\pm 1\%$ f.s.d. available). So set your course fair with 'Wide Angle' Fynelines.

Lance or 'knife edge' pointers are fitted and mounting arrangements are identical with existing Fyneline and Vista panel meters.


Complete technical and price details from Taylor Electrical Instruments Ltd, Montrose Avenue, Slough, Bucks. Telephone: Slough 21381. Telex 84429.



WW-073 FOR FURTHER DETAILS

T5

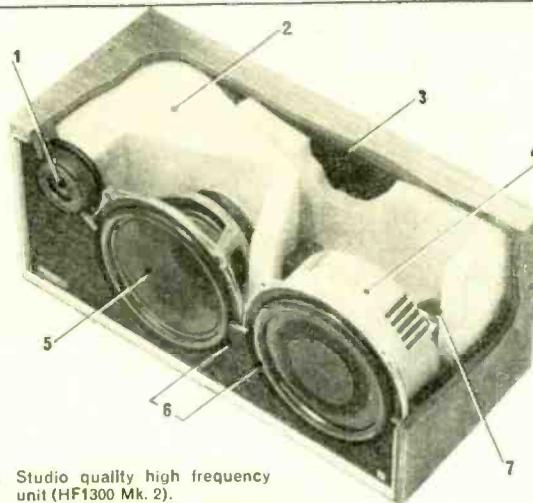Just what is this ABR, that makes such a vital difference to the 'DITTON 15'?



1. Studio quality high frequency unit (HF1300 Mk. 2).
2. Anechoic cellular foam wedge and lining eliminates standing waves.
3. High hysteresis panel loading material to eliminate structural resonances.
4. Auxiliary Bass Radiator (ABR) — plastic foam diaphragm giving high rigidity and low mass; double roll suspension allowing excursions up to 1" with minimal distortion.
5. High compliance bass unit with massive Ferroba II magnet structure for optimum magnet damping and cone treated with viscous damping layer to suppress resonances.
6. Units mounted flush to eliminate diffraction effects and tunnel resonances; covered by acoustically transparent grille cloth for maximum presence.
7. Full L-C half-section Crossover network.

It's an interesting story — and worth enquiring about.

Fill in the coupon

Celestion

Studio Series

loudspeakers for the perfectionist

ROLA CELESTION LTD.
 Ferry Works, Thames Ditton, Surrey Tel: 01-398 3402
 Please send me the full story on the 'Ditton 15'

NAME _____

ADDRESS _____

GD 997

WW-074 FOR FURTHER DETAILS



Pinnacle the largest single valve independent

THIS IS WHAT WE DO

Make available the widest range of valves for commercial and industrial use. Give a personalised service based on

intelligence and speed. Ensure that we only supply valves made by the world's foremost manufacturers. Provide valves selected for your special needs. Help out rapidly with that "awkward" valve that nobody

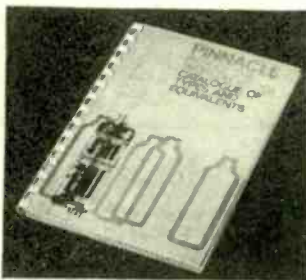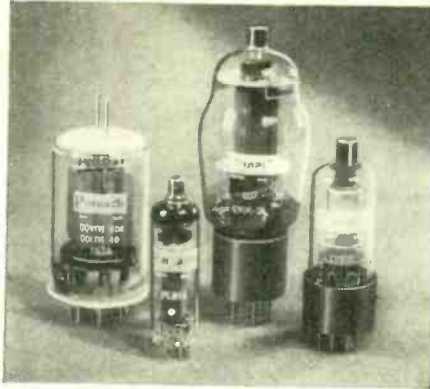else seems to have heard of. Specialise in European or American types which are not normally easily obtainable. Rush you a small order, or quote for a bulk requirement —1's or 1,000's are all the same to us.



IF I'D ONLY TRIED PINNACLE FIRST...


Every valve in either widespread or specialised use in the fields of Entertainment, Industry, Education and Research will be found in our catalogue, together with its main equivalents, classification, and the Pinnacle "P" number under which it may be ordered.

Pinnacle

PINNACLE ELECTRONICS LIMITED ACHILLES STREET • NEW CROSS • LONDON S.E.14
Telephone: All Departments—01-692 7285 Direct orders—01-692 7714

WW—075 FOR FURTHER DETAILS

Electronic components from the U.S.A.

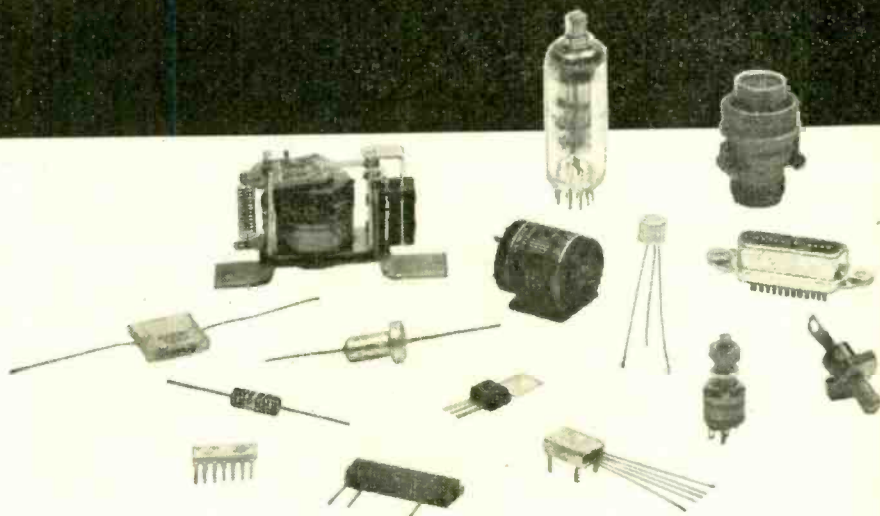

are only
hours away
via Milo.

International jetliners have helped to close the supply line gap between the U.S.A. and users of American-made electronic components in most parts of the world. But it takes more than a fast airplane to achieve a high degree of speed and efficiency in international procurement and distribution of electronic components.

Milo International, with years of successful experience plus a full staff of highly trained specialists, is thoroughly skilled in the complex technology of world-wide distribution. From your first inquiry to accurate delivery and detailed follow-through, Milo is completely capable of handling the entire process. Import Certificates, Export Licenses, Customs Declarations, Certificates of Conformance, Export Packaging, Delivery Verifications—these and all other technical requirements of international commerce are coordinated to guarantee reliable performance in simplifying and expediting each of your orders.

For whatever you may need in electronic components from the U.S.A., Milo can satisfy your requirements with prompt delivery, at direct factory prices, from a huge stock of thousands of components made by the leading American manufacturers including this partial listing:

- | | | |
|----------------------|----------------------|--------------------|
| Amperex | Eimac | R.C.A. |
| Amphenol | Electrons, Inc. | Raytheon |
| Arrow-Hart & Hegeman | Erie | Simpson |
| Bourns | General Electric | Sola |
| Burgess | Hardwick Hindle | Soliton |
| Cannon | Hickok | Sprague |
| Centralab | I.T.T. | Stancor |
| Cinch-Jones | J.F.D. | Superior |
| Clarostat | Kings | Sylvania |
| Cornell-Dubilier | Littelfuse | Texas Instruments |
| Corning | Mallory | Transitron |
| Dale Electronics | Oak | United Transformer |
| Delco Radio | Ohmite-Allen Bradley | Vector |
| | Potter & Brumfield | Xcelite |

For immediate price and delivery quotations, contact Milo by mail, phone, cable or International Telex.

 **MILO International**
World-Wide Electronic Component Suppliers
530 Canal Street, New York, N.Y. 10013 / Tel 212-233-2980 / Cable MILOLECTRO, N.Y. / Int'l. Telex 62528

WW-076 FOR FURTHER DETAILS

germanium devices
 silicon devices
 packaged circuits
 film-attachment active devices
 custom-built microcircuits

INDUSTRIAL SEMICONDUCTOR DEVICE MANUFACTURERS AND SOLID STATE ENGINEERS


**EXNING ROAD
 NEWMARKET
 SUFFOLK
 'PHONE ONE 8 3381**

Newmarket

TRANSISTORS LIMITED

WW-077 FOR FURTHER DETAILS

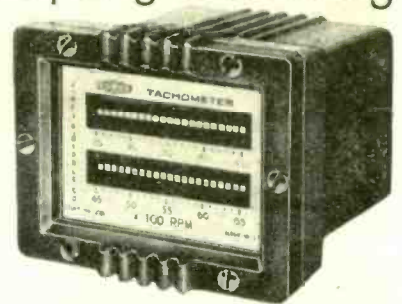Accurate and direct measurement of speed without coupling to moving parts



FRAHM

Resonant Reed TACHOMETERS

for hand use or permanent mounting.

Ranges and combinations of ranges from 900 to 100,000 r.p.m.

Descriptive literature on FRAHM Tachometers and Frequency Meters is freely available from the Sole U.K. distributors:

ANDERS METER SERVICE

ANDERS ELECTRONICS LTD. 48/56 BAYHAM PLACE, BAYHAM STREET LONDON NW1 TEL: 01-387 9092. *MINISTRY OF AVIATION APPROVED*
 WW-078 FOR FURTHER DETAILS

TECHNICAL TRAINING by ICS IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field. ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

- INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS.
- C. & G. TELECOMMUNICATION TECHNICIANS CERTS.
- C. & G. ELECTRONIC SERVICING
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS EXAMINATION.
- P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students Coached until Successful.

NEW SELF-BUILD RADIO COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-test meter—all under expert tuition.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES.

INTERNATIONAL CORRESPONDENCE SCHOOLS

International Correspondence Schools
 Dept. 222), Intertext House, Parkgate Road
 London, S.W.11.


NAME

ADDRESS
 Block Capitals Please

A WHOLE WORLD OF KNOWLEDGE AWAITS YOU!




..... 2.68

WW-079 FOR FURTHER DETAILS

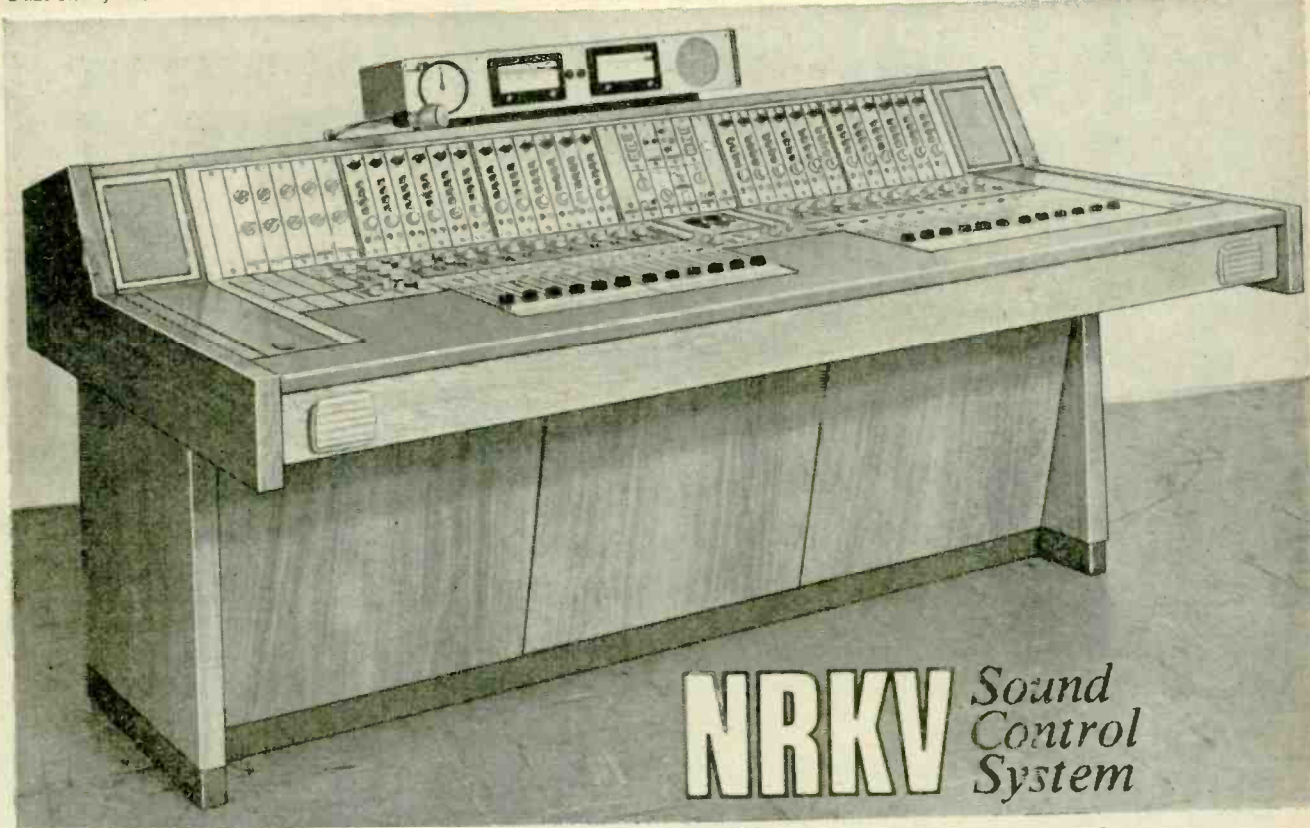

NRKV *Sound Control System*

a unique sound mixing system...

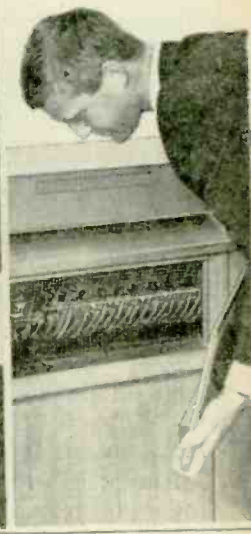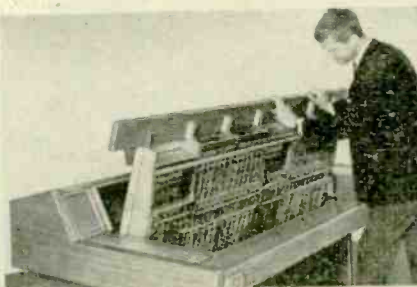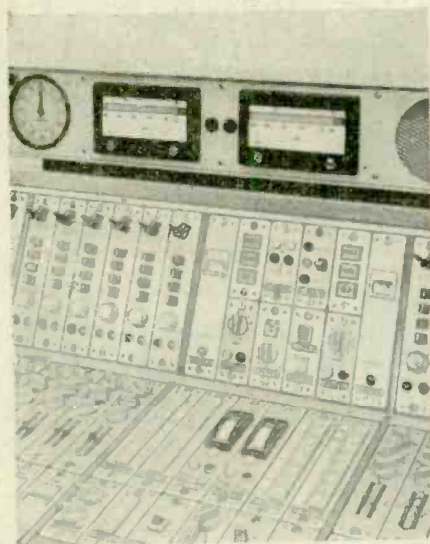

**KONGSBERG
VAPENFABRIKK
KONGSBERG
NORWAY**

Head office and plant: Kongsberg, Norway
Tel.: Kongsberg 37, telex: 1491, cable: Våpenfabrikken, Kongsberg

Oslo office: Drammensveien 40, VII
Tel.: Oslo 56 67 70, telex: 1114, cable: Konsern, Oslo

Central European office: Kongsberg Våpenfabrikk, Bonn
Walter Flex Strasse 1, West Germany
Tel.: Bonn 27 422, telex: 88 65 05, cable: Korakontor, Bonn

WW-080 FOR FURTHER DETAILS

Take a leaf from our book...



and send for your copy of the new **REGAVOLT** catalogue

36 pages packed with detailed information on the widest range of variable transformers made by a single manufacturer in Europe. All listed standard models are in stock for immediate delivery from our trade counter or by mail order, and are backed by a year's guarantee and a first class repair and replacement service.

Ask for list MT/625 (3rd Edition) NOW!



THE BRITISH ELECTRIC RESISTANCE COMPANY LTD.,
Queensway, Enfield, Middlesex. Tel: 01-804 2411 Telex: 263194

WW-081 FOR FURTHER DETAILS

608

LOUDSPEAKERS for every purpose



1255/15



TC 12

High Flux
high quality,
wide frequency,
highly sensitive
Cone units.

Cabinet speakers
contemporary styling
—painted and
oak veneer types





9/SFP



5/SFP

FD9

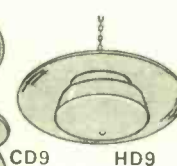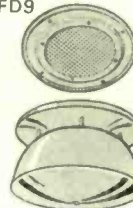


CD9

HD9

Circular Diffuser patterns
surface, flush and
suspension types


Projector loudspeakers
Re-entrant and
Exponential types
for fixed and
mobile use

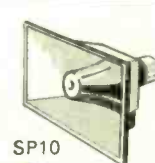

SP10



SP/10/W

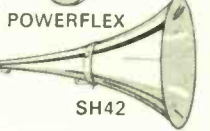

POWERFLEX

SH42



6 x 9



6 x 5



6 x 4

Column loudspeakers
wood-cased and
fibre glass types
for indoor and
outdoor use.

Grampian SOUND EQUIPMENT
—integrity that you hear

Send for leaflet giving full details—

GRAMPIAN REPRODUCERS LTD.,
Hanworth Trading Estate, Feltham, Middlesex. 01-894 9141

WW-082 FOR FURTHER DETAILS

ELECTRONICS ENGINEER
Expansion of research activities at the central... following positions in the Applied Physics and... Divisions and applications are invited.

ELECTRONICS PHYSICIST
To work on the detail design and development of Instr... tion for non-destructive testing and automation of... Control in the steel tube industry. This post will... require a graduate or equivalent who has had... experience in solid-state switching and digital... and some knowledge of display systems or... testing would be useful.

ELECTRONICS PHYSICIST
To work on the experimental... destructive testing and in pa... Processing of ultrasonic... recent graduate or some... an interest in theory... installed in the lab... theoretical work.

TRIPLEX SALES
Electronics Division. Post will include... transfer for the use of...

Senior Electronic Design Engineer:
To work on a wide range of automatic control equipment... A suitable degree or equivalent qualification is essential... and industrially based experience desirable. The post... will be involved in expanding the work of a new Depart... ment and applicants should have a genuine interest in... applying control techniques to industrial use.

Electronics Technician or Electronics Engineer:
Wide range of interesting automa... degree or an approved high... and an industrial background.

COMPUTER PLANNER
Southern Electricity
Salary £2,085 to £2,720
LOCATION: HAVANT

SENIOR STAFF
for ANALYSIS
INSTITUTE FOR INDUSTRIAL RESEARCH AND STANDARDS
Mechanical Engineering
ELECTRONICS
IRELAND

be in demand WITH CREI

DESIGN ENGINEER
Design engineer experienced in both linear and digital fields to work on... Character Recognition project involving mathematical simulations and t... electronic and semiconductor technologies. At least four years rele... appropriate degree (rel B 11).
Positions are situated at the C... amenities of the W...

PHYSICIST
Production Opportunities in Research

PHYSICIST
University graduates in Dairyng, Food Technology, science with a minimum of four years' industrial... experience are required for senior positions under the... Control Manager.

CREI CAN BE YOUR EDUCATIONAL LADDER.

to an exacting, exciting and rewarding career. Why? Because CREI offer the most up-to-date home study programmes closely related to the problems of industry and including the latest technological developments and advanced ideas.

No standard text books are used—these are often 2 years out-of-date when printed.

CREI Lesson material contains certain information not published elsewhere—is kept up-to-date continuously. (Over £50,000 is spent annually in revising text material.)

Step-by-step progress is assured by the concise, simply written and easily understood lessons.

Each programme of study is based on the practical applications to and specific needs of the Electronics Industry.

CREI PROGRAMMES ARE AVAILABLE IN:

- Electronic Engineering Technology
- Industrial Electronics for Automation
- Computer Systems Technology
- Nuclear Engineering
- Mathematics for Electronic Engineers
- Television Engineering
- Radar & Servo Engineering
- City & Guilds of London Institute: Subject 49 and Advanced Studies Subject No. 300.
- Over 40 years of experience—20,000 students now taking CREI courses throughout the World.

CREI THE EDUCATIONAL LADDER TO SUCCESS

C.R.E.I. (London) Walpole House, 173-176 Sloane Street, London, S.W.1.

POST THIS COUPON TODAY

PLEASE SEND ME (FOR MY INFORMATION AND ENTIRELY WITHOUT OBLIGATION) FULL DETAILS OF THE EDUCATIONAL PROGRAMMES OFFERED BY YOUR INSTITUTE

NAME

ADDRESS

ELECTRONICS EXPERIENCE

C.R.E.I. (LONDON) (DEPT. WW101)
WALPOLE HOUSE, 173/176 SLOANE STREET, S.W.1.

WW-083 FOR FURTHER DETAILS



AUDIO LABORATORY INSTRUMENTS

LOW DISTORTION OSCILLATOR (Series 2)

An instrument of high stability providing very pure sine waves, and square waves, in the range of 5 Hz to 500 kHz. Hybrid design using valves and semiconductors.

Specification

Frequency coverage: 5 Hz-500 kHz (5 ranges)
 Output Impedance: 600 Ohms.
 Output Voltage: 10 Volts r.m.s. max.
 Output Attenuation: 0-110 dB continuously variable.
 Sine Wave Distortion: 0.005% from 200 Hz to 20 kHz increasing to 0.015% at 10 Hz and 100 kHz.

Square Wave Rise Time: Less than 0.1 microseconds.
 Monitor Output Meter: Scaled 0-3, 0-10, and dBm.
 Mains Input: 100 V.-250 V. 50/60 Hz.
 Size: 17½ x 11 x 8 in.
 Weight: 25 lb.
 Price: £125.
 Rack mounting version available.

DISTORTION MEASURING SET (Series 2)

A sensitive instrument for the measurement of total harmonic distortion, designed for speedy and accurate use. Capable of measuring distortion products as low as 0.002%. Direct reading from calibrated meter scale.

Specification

Frequency Range: 20 Hz-20 kHz (6 ranges)
 Distortion Range: 0.01%-100% f.s.d. (9 ranges)
 Sensitivity: 100 mV.-100 V. (3 ranges)
 Meter: Square law r.m.s. reading.
 Input Resistance: 100 kOhms.
 High Pass Filter: 3 dB down to 350 Hz. 3 dB down to 35 Hz.
 Frequency Response: ±1 dB from second harmonic of rejection frequency to 250 kHz
 Power Requirements: Included battery.
 Size: 17½ x 11 x 8 in.
 Weight: 15 lb.
 Price: £90.
 Rack mounting version available.

VOLTMETER (new item)

A transistor operated voltmeter satisfying the requirements for audio frequency measurement.

Specification

Sensitivity: 1 mV.-300 V. f.s.d. (12 ranges)
 Calibration Accuracy: 2% f.s.d.
 Frequency Response: ±1 dB. 10 Hz-500 kHz.
 Input Impedance: 1 MOhm. 1 mV.-300 mV. 10 MOhm. 1 V.-300 V.
 Meter Scaled: 0-3, 0-10, and dBm.
 Power Requirements: Included battery.
 Size: 11½ x 6½ x 6 in.
 Weight: 7 lb.
 Price: £35.

RADFORD LABORATORY INSTRUMENTS LTD

Ashton Vale Road
 Bristol 3


WW-084 FOR FURTHER DETAILS

Those transistors cost money! Protect them!!

36A SPACESAVER DRAWER UNIT

42" high, 24½" wide, 12" deep. 36 drawers each 3" high, 5¼" wide, 10⅝" deep, with identification cards.

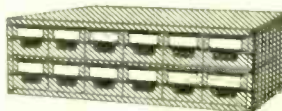
(CARRIAGE FREE ON MAINLAND) **£12.0.0** BRAND NEW



12A POPULAR DRAWER UNIT

9" high, 35" wide, 12" deep. 12 drawers each 3" high, 5¼" wide, 10⅝" deep, with identification cards. Ideal for shelf or table-top.

£4.15.0 BRAND NEW

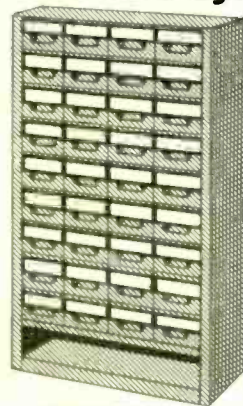

ORDER NOW

Send for FREE catalogue of our complete range of storage equipment.

N.C. BROWN LTD

INDUSTRIAL SALES DIVISION pacesetters in storage equipment

Eagle Steelworks, Heywood, Lancs. Tel: 69018
 London: 25/27 Newton St. WC2. Tel: 01-405-7931

Please send 36A Spacesaver Drawer Unit
 12A Popular Drawer Unit

Tick where applicable and send cash with orders under £5


NAME

ADDRESS

E29

WW-085 FOR FURTHER DETAILS

METER PROBLEMS?

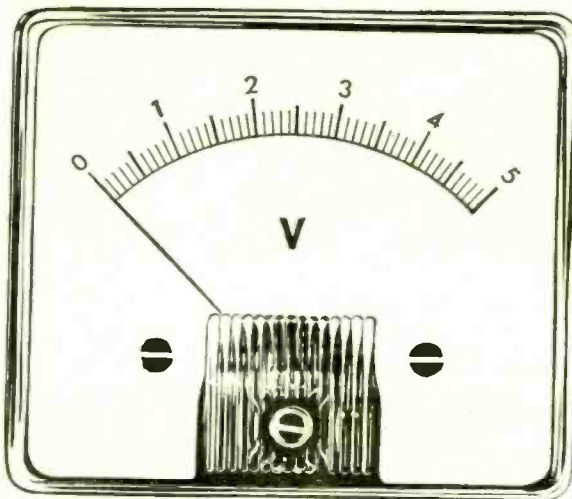

A very wide range of modern design instruments is available for 10/14 days delivery.

Full information from:

HARRIS ELECTRONICS (London) LTD.
 138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW-086 FOR FURTHER DETAILS

The new JT makes you wonder how small a connector can get



No connector could be more appropriate to modern space-saving requirements than the new JT. It's lighter, shorter and considerably more compact than anything of its type at present available. Simply designed (with fewer components) and precision made, the JT sets an entirely new standard in reliability for connectors. It is at home in conditions ranging from cryogenic to high temperature, offering much greater freedom to designers in many different fields.

AVAILABLE NOW – with up to 128 contacts in less than $1\frac{1}{2}$ " diameter.

Already in use on over 80 international projects.

JTA – general duty types.	JTC – Pressurised styles.
JTG – for RFI protection.	JTH – Hermetically sealed.
JTP – for potting.	JTRE – Crimped contacts.
JTS – for high temperatures.	JTL – 100% scoop proof.

There is a Thorn connector for every purpose!



THORN SPECIAL PRODUCTS LIMITED Great Cambridge Road, Enfield, Middlesex. Phone: 01-363 5353; Telex: 263201-2-3
A SUBSIDIARY COMPANY OF THORN BENDIX LIMITED

AP11

WW-087 FOR FURTHER DETAILS

This is the iron

THE ANTEX CN 240 15 WATT FOR ABSOLUTE PRECISION

Designed as the ideal instrument for continuous production work on printed circuits, transistors, micro-miniature assemblies etc., the CN 240 is the most widely used iron in the Antex range. It's well-balanced yellow handle is to be seen in electronics factories and on production lines all over the world. Fitted with a 3/32" Ferraclad bit as standard, there is a range of 17 other interchangeable bits of differing shapes and sizes available to make the CN truly the most versatile iron of its type.



PRICE 32/6



*The full Antex range of Precision Soldering equipment is detailed in the 16-page Antex catalogue - SEND TODAY FOR YOUR FREE COPY.

The CN is one of a range of Fine Precision Soldering tools and equipment by Antex



Model G 18W 32/6d.



Model E 20W 35/-d.





Model ES 25W 35/-d.



Model F 40W 42/6d.

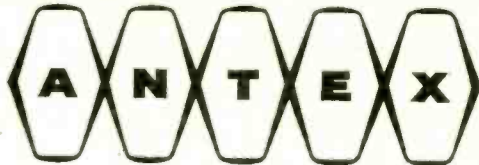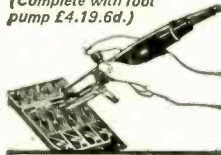Model ESS De-Soldering Tool £4.4.0d. (Complete with foot pump £4.19.6d.)



ANTEX LTD., GROSVENOR HOUSE, CROYDON CR9 1QE
TELEPHONE: 01-686 2774
WW-088 FOR FURTHER DETAILS



Armstrong
high fidelity sound

series 27 TUNER-AMPLIFIERS for the BUDGET SYSTEM



- 127 STEREO TUNER-AMPLIFIER (illustrated) £40.1.6
- 127M MONO TUNER-AMPLIFIER £29.18.9
- 227M MONO TUNER-AMPLIFIER £40.1.6
- OPTIONAL CASE, teak and vinyl hide £3.15.9

Three tuner-amplifiers, identical in size and similar in styling, each with the same high performance AM-FM Tuner incorporated. The 227M provides 10 watts power output whilst the 127M, with 5 watts output, is designed for those whose power requirements are more modest. The 127 is the stereo version of 127M, having two amplifiers, each of 5 watts output. All three have similar facilities; pick-up and tape inputs, tape recording output, bass and treble tone controls.

For full details and technical specifications of all models, including the new series 400, plus list of stockists, post coupon or write mentioning 2WW68.

ARMSTRONG AUDIO LTD., WARLTERS ROAD, N.7
Telephone 01-607 3213

Name

Address

2WW68

WW-089 FOR FURTHER DETAILS


This is an illustration of sixty-two different power units



Concealed behind this $4\frac{3}{8}$ " x $5\frac{1}{8}$ " front panel is a standard range of parts manufactured in large quantities, resulting in low production costs. The saving is passed on to you without affecting the superior performance and high reliability. For example, you can have a pre-set unit in the range 11 to 28 volts at 4 amps for as little as £34.

The 62 units in the new Series 30 range cover voltages from 0 to 500 with output currents up to 10 amps, depending on the voltage. A choice of protection circuits is available including 'crowbar' for your integrated circuits.

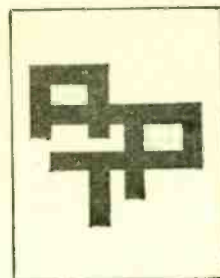
For complete details of this new approach to power supply design send for Series 30 full-colour folder and price list.



A.P.T Electronic Industries Ltd. Chertsey Rd., Byfleet, Surrey. Tel: Byfleet 41131.

WW-095 FOR FURTHER DETAILS

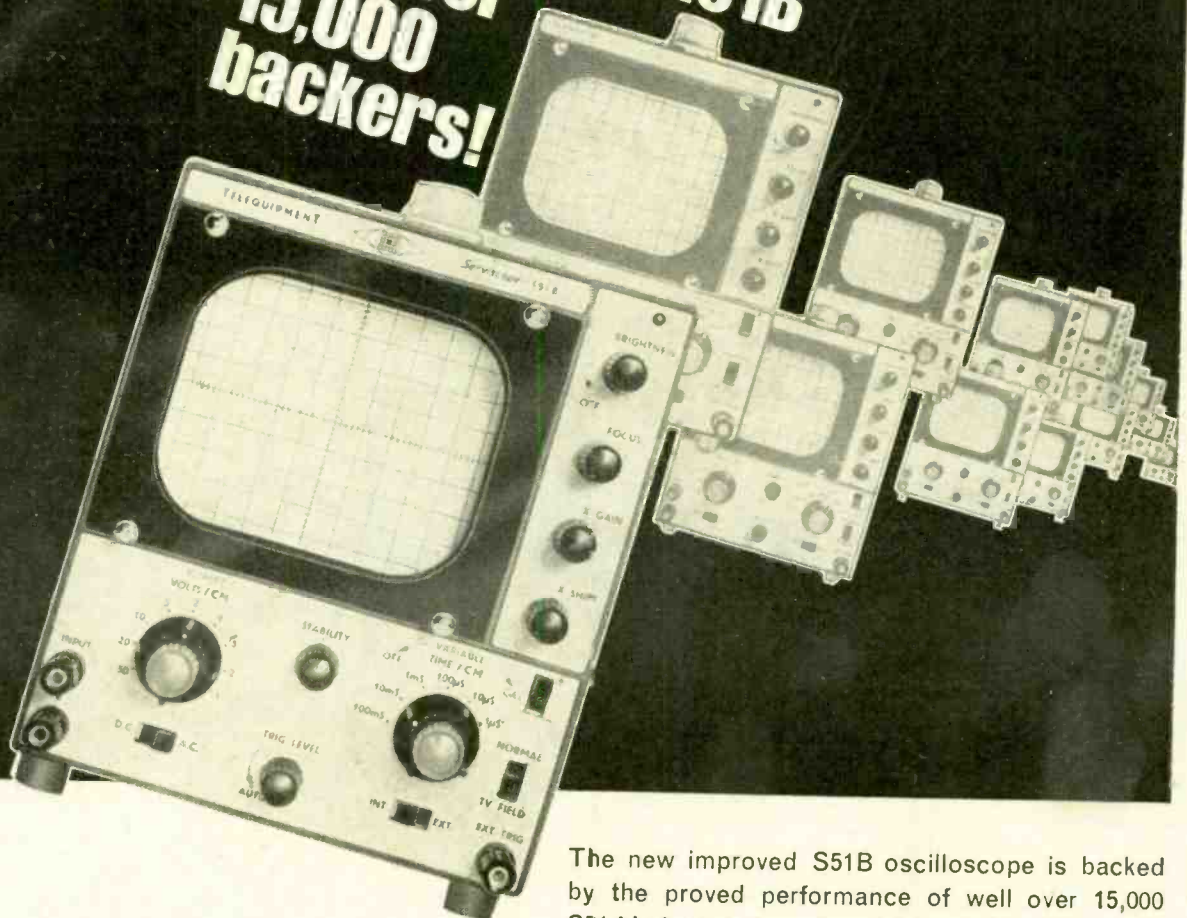the **NEW**
SERVISCOPE* S.51B
 has over
15,000
 backers!



The new improved S51B oscilloscope is backed by the proved performance of well over 15,000 S51A's in use throughout the world.

■ More scope—D.C. X-Amplifier standard ■ Only £55 in the U.K. ■ Large 5" screen—
 Bright trace ■ Small size—low weight ■ DC-3Mc/s—100mV cm sensitivity ■ Auto sync
 and trigger level control ■ Easy to use oscilloscope ■ Ideal for inspection, production
 control, transistor testing, training, monitoring etc. ■ Specification leaflet ready for you
 RIGHT NOW! *Serviscope is a registered trade mark of Telequipment Ltd.

TELEQUIPMENT



TELEQUIPMENT LIMITED • 313 CHASE ROAD • SOUTHGATE • LONDON N.14 • TELEPHONE: 01-882 1166
 WW-096 FOR FURTHER DETAILS

Wireless World

ELECTRONICS TELEVISION, RADIO, AUDIO

FEBRUARY 1968

Editor-in-chief:

W. T. COCKING, F.I.E.E

Editor:

H. W. BARNARD

Technical Editor:

T. E. IVALI

Editorial Assistant

B. S. CRANK

Drawing Office:

H. J. COOKE

Production:

D. R. BRAY

Advertisements:

G. BENTON ROWELL
(Manager)

J. R. EYTON-JONES

Iliffe Technical Publications Ltd.,
Managing Director: Kenneth Tett
Editorial Director: George H.
Mansell
Dorset House, Stamford Street,
London, S.E.1

Subscribers are requested to notify a change of address four weeks in advance and to return wrapper bearing previous address.

© Iliffe Technical Publications Ltd., 1968. Permission in writing from the Editor must first be obtained before letterpress or illustrations are reproduced from this journal. Brief extracts or comments are allowed provided acknowledgement to the journal is given.

VOLUME 73 No. 14

PRICE: 3s.

FIFTY-SEVENTH YEAR
OF PUBLICATION

- 665 Technical Manpower
666 Portable 1-MHz Frequency Standard *by L. Nelson-Jones*
672 Distortions Inherent in P.W.M. *by K. C. Johnson*
677 Log-Periodic Television Aerial
678 Transistor Rationalization *by T. D. Towers*
682 European Space Research
684 GaAs Miniature Radar
685 Acousto-electric V.H.F. Transmitter
693 Emitter-coupled Emitter-timed Multivibrators—2 *by G. B. Clayton*
696 The Simple Transistor Equivalent Circuit and the Impedance Transforming Node *by R. V. Leedham*
699 Pin-board Construction *by G. W. Short*
701 Ferrite Aerial Receivers *by R. S. Roberts*
702 Miles-per-Gallon Meter *by D. J. Grover*
705 Point-to-Point Review 1967 *by D. Wilkinson*
709 Demonstrating Rectifier Action in Slow Motion *by T. Palmer*

SHORT ITEMS

- 671 Further Notes on "V.H.F. Signal Generator"
692 Computer-aided Circuit Construction
692 Monolithic F.M. Discriminator
692 Picosecond Pulses Observed in Q-switched Lasers
707 Advice on Materials Technology

REGULAR FEATURES

- | | |
|---------------------------|----------------------------|
| 665 Editorial Comment | 698 World of Amateur Radio |
| 683 Books Received | 700 H.F. Predictions |
| 686 World of Wireless | 706 Literature Received |
| 688 Personalities | 707 News from Industry |
| 690 Letters to the Editor | 710 New Products |
| 692 Technical Notebook | 718 February Meetings |

PUBLISHED MONTHLY (3rd Monday of preceding month). Telephone: 01-928 3333 (70 lines), Telegrams/Telex: Wiworld Iliffepres 25137 London. Cables: "Ethaworld, London, S.E.1." Annual Subscriptions: Home: £2 6s Od. Overseas: £2 15s Od. Canada and U.S.A.: \$8.00. Second-Class mail privileges authorised at New York N.Y. BRANCH OFFICES: BIRMINGHAM: 401, Lynton House, Walsall Road, 22b. Telephone: Birchfields 4838. BRISTOL: 11 Marsh Street, 1, Telephone: Bristol 21491/2. COVENTRY: 8-10, Corporation Street. Telephone: Coventry 25210. GLASGOW: 123, Hope Street, C.2. Telephone: Central 1265-6. MANCHESTER: 260, Deansgate, 3. Telephone: Blackfriars 4412. NEW YORK OFFICE U.S.A.: 300 East 42nd Street, New York 10017. Telephone: 867-3900



**NO ONE OFFERS A
WIDER RANGE OF
MONITOR TUBES
THAN BRIMAR**

BRIMAR offers the most comprehensive range of monitor tubes in the country, together with the widest selection of phosphors.

The tubes range in size from 5" to 23". They can be used for television camera viewfinders, studio quality monitors, data displays and closed circuit television - twenty tubes in all! They have been designed to give maximum resolution under high ambient lighting conditions.

A variety of mounting and implosion protection methods, including self protection bonded glass faces are available from BRIMAR who are Britain's leaders in implosion protection.

Common features include magnetic deflection, electrostatic focus and aluminised screens.

The phosphors. In addition to the standard type for television, a wide selection of others is available offering varying degrees of persistence and colour.

**....OR A MORE
PERSONALISED
SERVICE!**

Every BRIMAR tube is backed by a first-class technical service and assistance on any type of problem involving its use in monitors - from special characteristics to circuit design. BRIMAR engineers are always available - contact is on a personal basis. Please telephone or write for full details.



Thorn-A.E.I. Radio Valves & Tubes Ltd.
7 Soho Square, London W1. Telephone: 01-437 5233

WW-097 FOR FURTHER DETAILS

1A 029

Marconi complete naval communications


A complete range of communications equipment using s.s.b, i.s.b and all other modes of h.f and m.f transmissions, designed specifically for naval communications systems.

- Simple, precise and highly accurate continuous decade selection of frequencies in 100 Hz steps.
- Rigid stability controlled by a single high accuracy frequency standard.
- Extreme simplicity of operation combined

with versatility of service and high quality performance.

- Synthesizers and wideband amplifiers employed in these systems, which make maximum use of semiconductors.
- NATO codified.
- Complete system planning and installation.

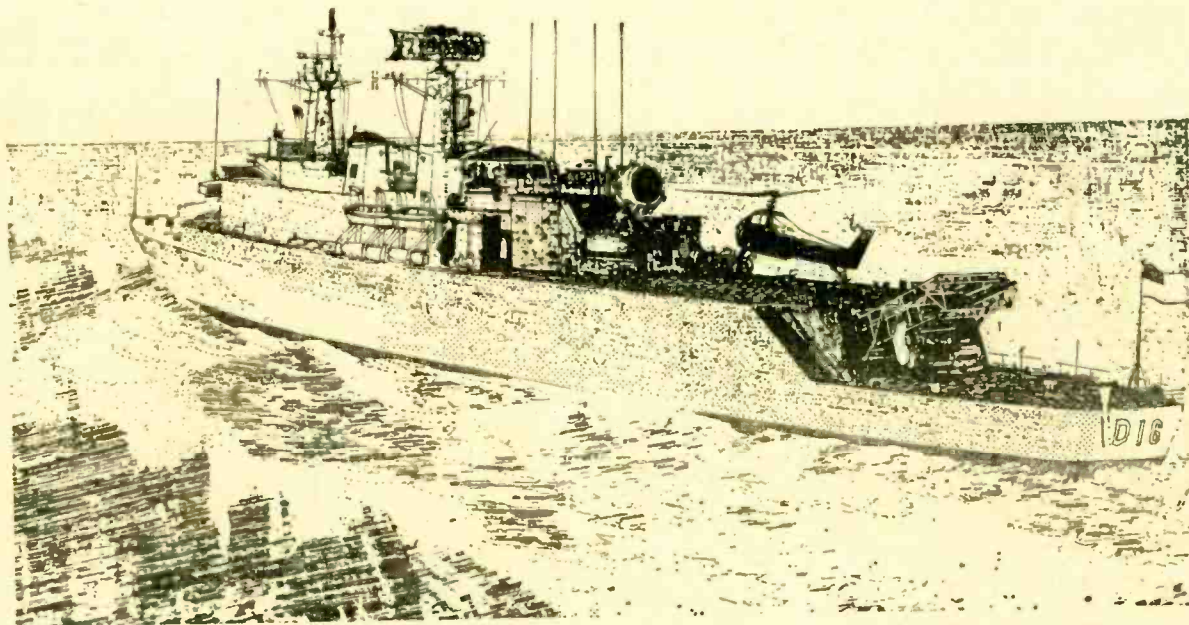This new range of Marconi equipment has already been used in the modernization of the communications of 10 Navies.



Marconi naval radio and radar systems

AN 'ENGLISH ELECTRIC' COMPANY

The Marconi Company Limited, Radio Communications Division, Chelmsford, Essex


WW-098 FOR FURTHER DETAILS

LTD/H661

More speed for 'Concorde'

Speed is as vital in the production of the Anglo-French 'Concorde' as in its performance. That's why magnetic tape systems are in use for the 'numerical control' of machine tools. 'Numerical control' makes it possible to machine complex parts without models or templates, thereby reducing production time and cutting down demands on skilled workers. All the movements of the machine slides, accurate to one five-thousandth of an inch, are produced by command

signals recorded on 'Scotch' Instrumentation Tape. Large quantities of tape are used for this purpose by Ferranti Ltd. while a considerable amount is also used by Bristol-Siddeley Engines Ltd. on their part of the 'Concorde' project, the development of the Olympus 593 engine. If 'Scotch' Instrumentation Tape can be of assistance to you, please complete and post the coupon below for TECHNICAL TALK publications and for 'Scotch' magnetic tape data sheets.

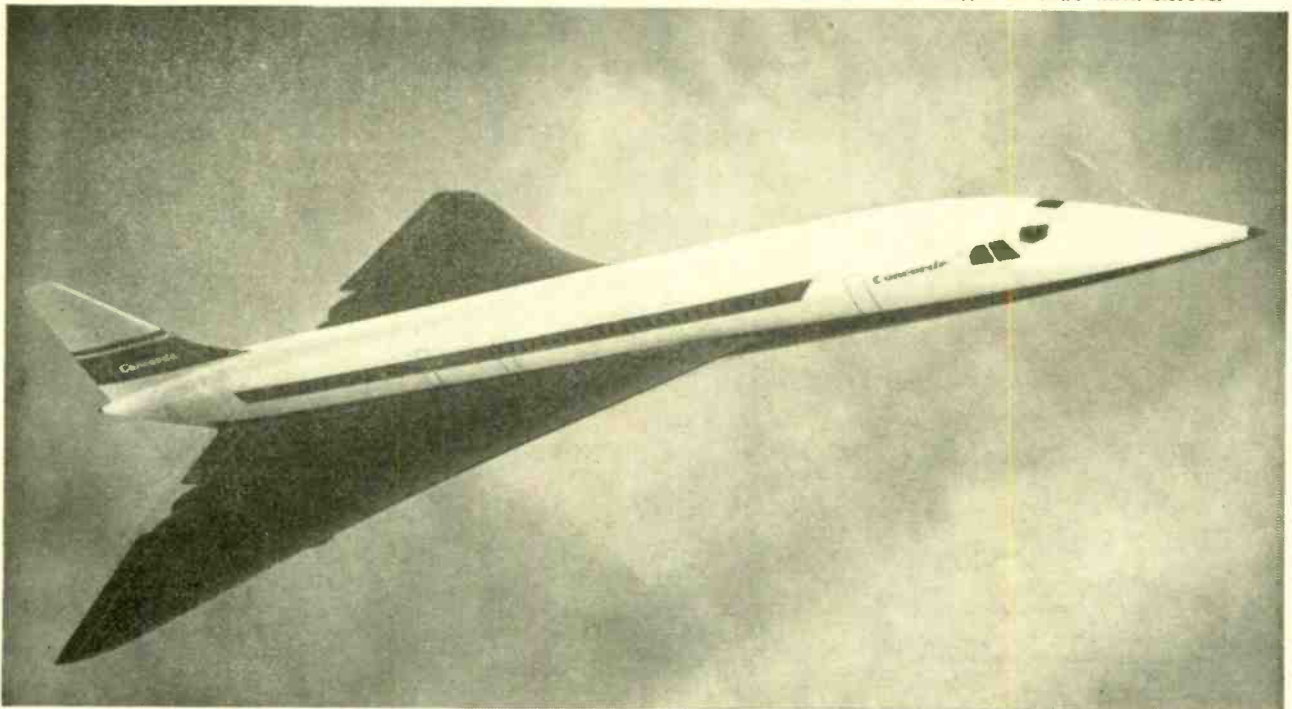

3M MINNESOTA MINING AND MANUFACTURING CO. LTD.

Manufacturers of 'Scotch' Instrumentation Tape, Professional Quality Magnetic Tape, Quadrature and Helical Scan Video Tapes.

3M and 'SCOTCH' are trademarks of Minnesota Mining and Manufacturing Company

To: Mr. G. C. WRIDE, 3M HOUSE, WIGMORE ST, LONDON W1

Please send me technical details and specifications on 'Scotch' Instrumentation Tape.

NAME


ADDRESS

.....W1.

WW-099 FOR FURTHER DETAILS

Vortexion quality equipment

TYPE C.B.L. TAPE RECORDER

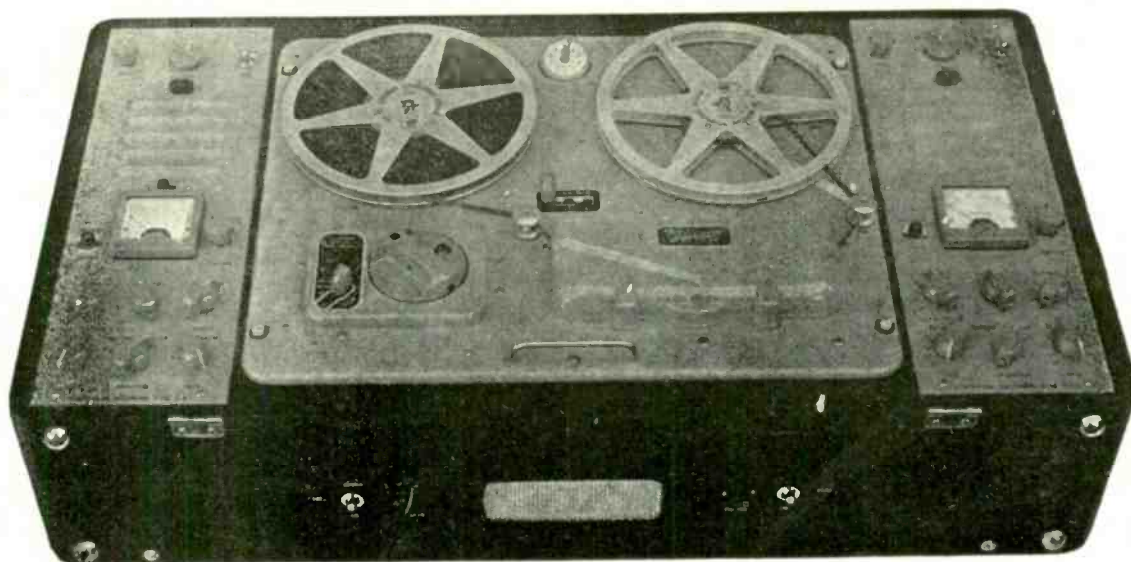

Here is a versatile stereophonic recorder which has no equal in its price group.

IT CAN record monaurally or stereophonically with its own mixed inputs from Gram, Radio or other sources and from high grade low impedance balanced line microphones. With good microphones, etc., the result is a suitable master for disc manufacturers. "Before and After" monitoring is provided together with adjustable metered bias for perfection.

IT CAN also make a recording on one track and then transfer it to the other track while measuring and listening to it and adding one or two more signals also metered. A special PPM type meter is now used.

IT CAN repeat the process and transfer this combined signal to the first track with one or two more signals. Composers use it for this purpose. One track may have music or commentary and the other cueing signals or commentary and either may be altered without the other.

IT CAN play back stereophonically or monaurally with its own amplifiers of $3\frac{1}{2}$ watts each.

Speeds $1\frac{7}{8}/3\frac{3}{4}/7\frac{1}{2}$ i.p.s. Price **£172 0s. 0d.**

Speeds $3\frac{3}{4}/7\frac{1}{2}/15$ i.p.s. Price **£180 0s. 0d.**

The Vortexion W.V.B. is a high quality monaural machine with "Before and After" monitoring. The recording inputs are a high sensitivity socket for moving coil or ribbon microphone and a high impedance socket for radio, etc., either of which can be selected by a switch. Superimposing and echo work can be done and the playback has reserve gain for abnormal requirements. This model cannot be converted for stereo playback, but it is a thoroughly reliable machine for the engineer specialising on monaural work.

Speeds $1\frac{7}{8}/3\frac{3}{4}/7\frac{1}{2}$ i.p.s. Price **£115 10s. 0d.**

Speeds $3\frac{3}{4}/7\frac{1}{2}/15$ i.p.s. Price **£128 0s. 0d.**

The Vortexion W.V.A. is a monaural machine which has a performance equal in sound quality to the other models. It possesses all the features of the W.V.B. except for "Before and After" monitoring, Dubbing and Echoes. The recording being made can be heard on the internal loudspeaker as in the W.V.B. and C.B.L. The controls are uncomplicated.

Speeds $1\frac{7}{8}/3\frac{3}{4}/7\frac{1}{2}$ i.p.s. Price **£96 7s. 0d.**

Speeds $3\frac{3}{4}/7\frac{1}{2}/15$ i.p.s. Price **£107 3s. 0d.**


All tape recorders have adjustable bias controls, low impedance mic. inputs for unlimited lengths of cable, highly accurate position indicators and meters to measure recording level and bias.

VORTEXION LIMITED, 257-263 The Broadway, Wimbledon, S.W.19

Telephone: 01-542-2814 and 01-542-6242/3/4

Telegrams: "Vortexion London S.W.19"

WW-100 FOR FURTHER DETAILS

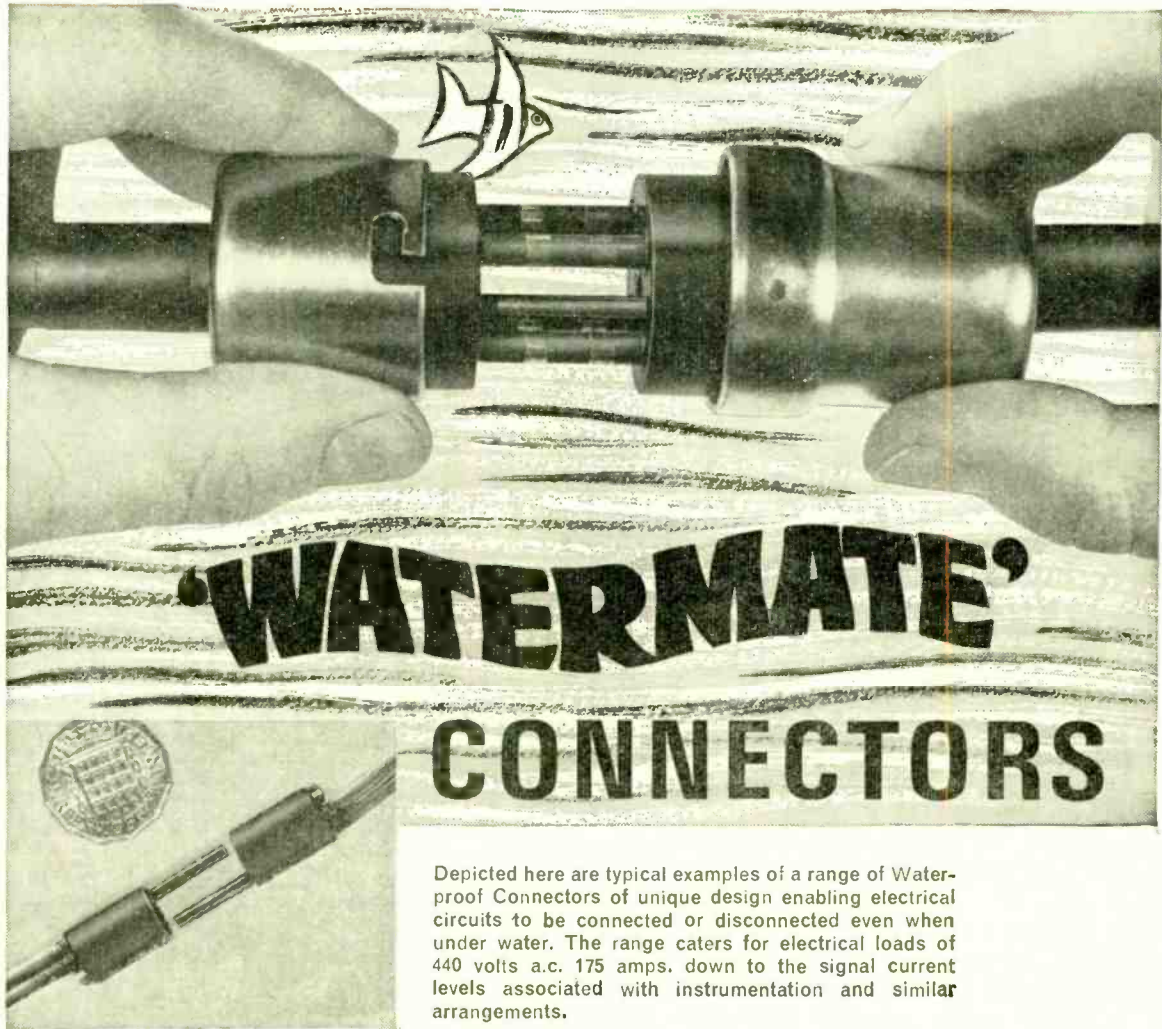

WATERMATE
CONNECTORS

Depicted here are typical examples of a range of Water-proof Connectors of unique design enabling electrical circuits to be connected or disconnected even when under water. The range caters for electrical loads of 440 volts a.c. 175 amps. down to the signal current levels associated with instrumentation and similar arrangements.

The basic design incorporates a patented principle referred to as "Watermate". Both plug and socket are moulded of a specially compounded neoprene rubber with unusually high insulation resistance and non-wetting surface. As mating occurs water, salt deposits, sand and other foreign matter are wiped from the sockets and ejected from a duct in the socket to form a leak-proof seal. The wiping action assures a dry connection at the moment of contact resulting in a leakage resistance of not less than 100 megohms **WHEN MATED UNDER WATER.**

They are pressure balanced and will not block up under high pressures. There are no glands or threads to seize up in water and the method of moulding to the associated neoprene jacketed cable provides an extremely robust and simple connector for both Military and Civil applications.


For full details of these Connectors and a new Underwater Reed Switch Assembly, please write or telephone to the Technical Sales Department.

MCMURDO

McMURDO INSTRUMENT CO. LTD., RODNEY RD, FRATTON, PORTSMOUTH, Tel: Portsmouth 35361 Telex: 86112 LUGTON & CO. LTD., 209/210 Tottenham Court Road, London, W.1. Tel.: Museum 3261. SASCO, P.O. Box No. 20, Gatwick Road, Crawley, Sussex. Telephone: Crawley 28703 (also: Chipping Sodbury 2641. Cumbernauld 25601. Hitchin 2242).

ARGENTINA: Corte & Mon S.R.L., Salta 1325, BUENOS AIRES. **AUSTRALIA:** McMurdo (Australia) Pty. Ltd., 15 Edinburgh St., Huntingdale, VICTORIA. **AUSTRIA:** Lipschitz & Co. Biberstrasse 22, VIENNA I.

WW—101 FOR FURTHER DETAILS

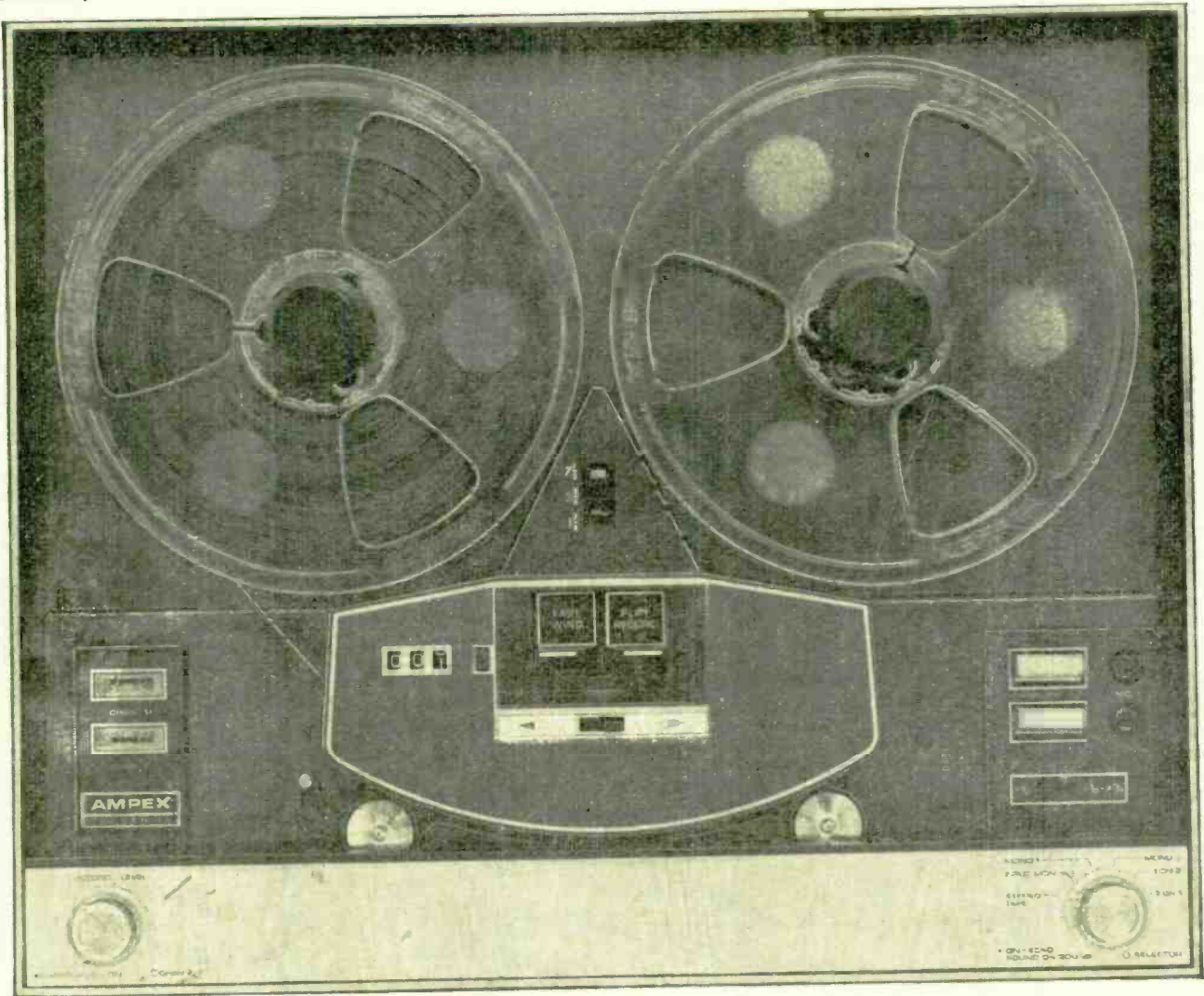

It's Ampex. It's 91 gns

The new Ampex 753 Tape Deck (complete with pre-amplifiers) gives you these important new features:

- off-tape monitoring sound-on-sound
- sound-with-sound echo control

The 753 is specially engineered for sound-on-sound recording and monitoring. You can mix narration with music tracks—add sound and music to your home-produced programmes. You get the famous Ampex stereo fidelity too. Precision engineering. And better performance than any price-range competitor. Plus rigid block construction—tapes align with heads to one thousandth of an inch, and the 753 finds every sound on the tape. deep-gap heads give three years' peak performance—few other makes give more than one year. stereo 4-track dual-capstan drive 3 speeds digital counter fast wind solid state throughout vertical or horizontal operation available in teak case.

For further information and list of dealers in the U.K. send coupon below, or write to: Ampex Great Britain Ltd., (Dept WW2) Acre Road, Reading, Berkshire.

Please send me 753 details and dealer list.

Name _____

Address _____

AMPEX

CA-9 WW2

WW-102 FOR FURTHER DETAILS


MST SUCCESS

**SALES NOW
EXCEED
£10,000,000**

More and more
countries are buying
Marconi Self-Tuning
h.f systems . . .

and one good reason is:
INCREASED RELIABILITY

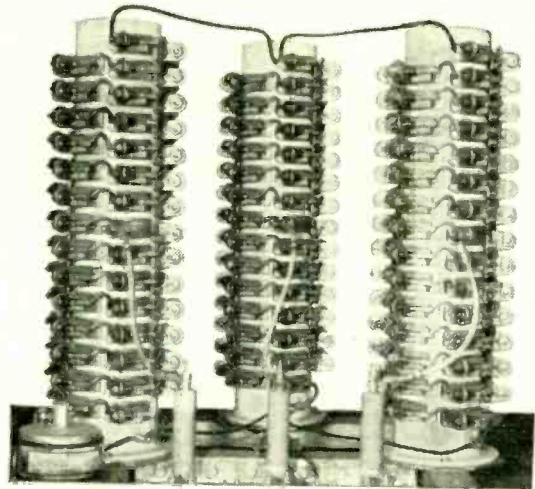- Wideband and distributed amplifiers simplify and reduce the number of moving parts, which are to the highest engineering standard, thus minimising mechanical failure.
- Silicon diode rectifiers, vacuum variable capacitors and extensive use of solid-state techniques give optimum reliability.
- MST receivers are all solid-state, eliminating mechanical variable capacitors and telegraph relays.



and other good reasons are:

Reduced capital outlay

MST designs reduce demands for space and need for standby equipment. Installation costs are decreased.

Economy of manpower

High equipment reliability together with full remote control facilities permit unmanned station working. Complete h.f systems can be controlled by one man.

Traffic interruption reduced

Frequency changes and retuning accomplished in less than one minute without loss of traffic.

World-wide acceptance

30 countries throughout the world have ordered more than £10,000,000 worth of MST equipment to improve their communications services.

Marconi telecommunications systems


The Marconi Company Limited, Radio Communications Division, Chelmsford, Essex, England

LTD/H78

AN 'ENGLISH ELECTRIC' COMPANY

WW-103 FOR FURTHER DETAILS

CONTIL AND PIDAM SYSTEMS

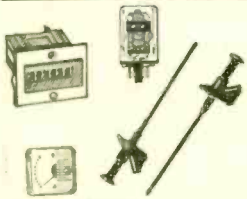


ACCESSORIES

A full range of accessories are available for PIDAM. Shown are the meter, scaled 0-9, at 35/6. Test prods insulated and flexible with fine steel clips at the tip, red or black at 13/-. High speed resetting counter including bezel and socket, with speed of over 40 operations per sec. 165/-. Plug-in Octal relay 24v. with two changeover at 17/6. Not shown: 8 range test meter, 42/-. Oscilloscope made for us by Advance, £25.


PIDAM (Plug-in Digital and Analogue Modules) perform all the usual logic functions, but, unlike other units, can be plugged in, using their B9A bases and can be quickly connected to the required configuration. To help learning, the module covers are easily removable for circuit examination and sets of components are available. The 16 modules have an enormous range of use, from a single MONO for a tachometer, to over 300 units in a computer Interface; nevertheless, their greatest asset is extreme simplicity. Design time is cut and elaborate breadboards superseded and any reader of "Wireless World" could, with PIDAM, build up a low cost system for his own needs.

PIDAM PLUG-IN MODULES, PRICES

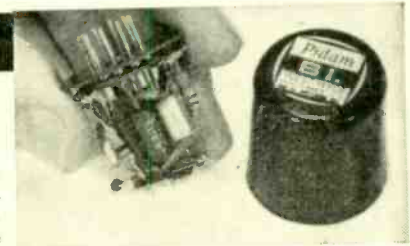per module range from 9/6 to 28/- and all necessary accessories are supplied. A complete starting kit is only £19/19/-. (normally £22/16/-).




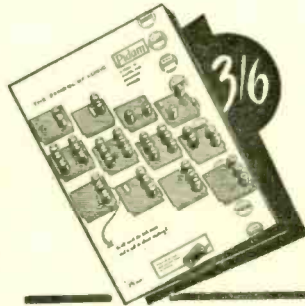B1 (Bistable) module shows B9A base for ease of connection. Pins 7, 8, 9 are always power connections.




PIDAM BROCHURE

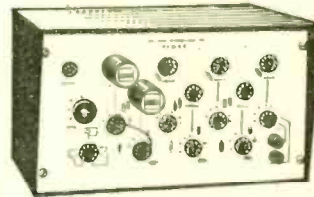Send for this complete explanatory booklet showing detailed examples of use and circuit diagrams of all modules. Examples and circuits given include voice-operated switch alarm, flashers, inchometer, timers, batch counters, etc. 3/6 post free.



PIDECE

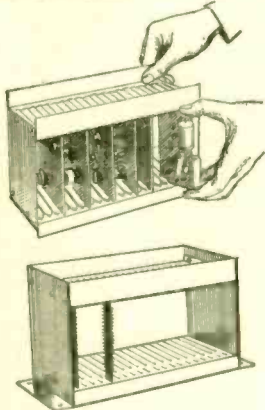(Plug-in Digital Educational Circuit.) This Pidece unit allows seven modules to be interconnected for demonstration or mock-up without soldering. Including internal power supplies, 370/-.



PRINTED CIRCUIT CHASSIS


Printed circuit chassis type "P" which fits into 1277 or 16127 case, or type "Q" which can be mounted on an aluminium chassis. Both types take up to 20 boards and connectors on 1/2 centres. Prices from 45/6 down to 37/- for quantities.

CONTIL CASES


Contil cases are mass-produced to give the lowest prices yet. In 21-gauge steel. Finished hammer blue, with 18-gauge front panel supplied with easy-to-strip protective covering for easy marking out. For ease of ordering Contil cases are described by their dimensions, i.e. 755 is 7" x 5" x 5". Individually packed, inc. feet and screws.

	ONE	FIVE
755	45/6	44/-
867 or 975	47/6	46/-
1277	53/-	51/-
16127	98/6	96/6
191010	133/-	130/-

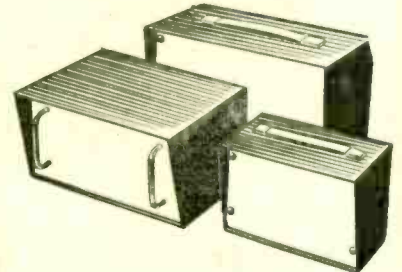Range of chromium-plated and Delrin handles available with matching chassis, spare panels, etc. Kit £11/19/- (normally £14/12/-).



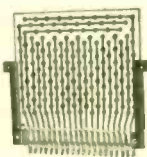"A" board shown plugged into "M" 20-way connector with "S" board supports. Note: Power supply rails at right angles to signal rails "A" boards, 8/6 each. 20-way "M" connector 9/-, "S" supports 3/- pair. Less for quantities.




DIVIDE BOARD

The Contil divide board can be used for decoding from 9 bistables giving a count up to 512. Includes resetting and decoding diodes and switches. Type "R" at 78/- each.



TRANSFORMERS

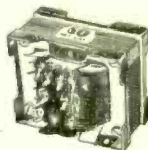Two West Hyde transformers are available for transistorised equipment one at 2 amps, giving 6, 10, 15, 18 and 30v. i.e., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 with 12-0-12 and 15-0-15. The second at 1 amp. 6, 10, 18v. taps. Price 34/- and 25/-.



"BRIGHTLIFE" NEONS

25,000 hr. average life with high intensity and resistor in housing; either 1/2" or 1" dia. Standard units 160-250v. with 6" lead variants. 10 at 2/6 each with 10 different caps. In quantity down to 1/7 each. Neon only, down to 6 1/2 each.

SUB-MINIATURE NEON


The smallest yet. Type "Q" overall dia. 1/8", body length 1/2". With resistor for mains, 3/9 each. Minimum quantity 10. Down to 2/6 each.



REED SWITCH

The West Hyde Reed Switch works at up to 2,000 times a second for more than fifty thousand million operations. Ideal for: over and under speed monitors, counting, timing, switching, rev. counting, etc. Hermetically sealed and moulded. Prices from 14/- each to 7/6 each per thousand.

DIGITAL COMPUTER MODULES

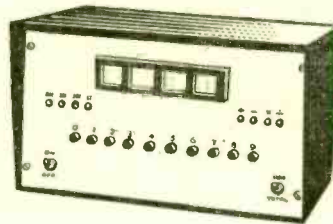

Digital computer modules are available including bistables, flip flops, comparators (coincidence gate), neon driver, 5NOR, 2NOR x 2, 5NAND, and RESET. Also available are neons for driver by transistors, display boards, divide boards, together with escutcheons that only require round holes

CONTIL LOW COST PRINTED CIRCUIT BOARDS

	ONE	TEN	FIFTY
Standard transistor board	8/6	7/6	7/-
Half board B9A	7/-	5/6	4/6
B7G or B9A boards inc. their four respective bases	9/6	8/6	8/-
Connectors, 20 way	9/-	8/6	8/-
10-way	5/-	4/6	4/-
"P" chassis to fit 1277 Contil	39/6	37/6	37/-

Printed circuit kit: including case, normally £14/8/6 for only £11/19/6.

PLEASE NOTE


All products ex-stock for normal quantities. Return of post service. No S.A.E. Minimum order £1. Fully detailed leaflets available. All prices include postage and packing.



WEST HYDE DEVELOPMENTS LTD.

30 HIGH STREET, NORTHWOOD, MIDDLESEX
Tel: Northwood 24941

WW-105 FOR FURTHER DETAILS

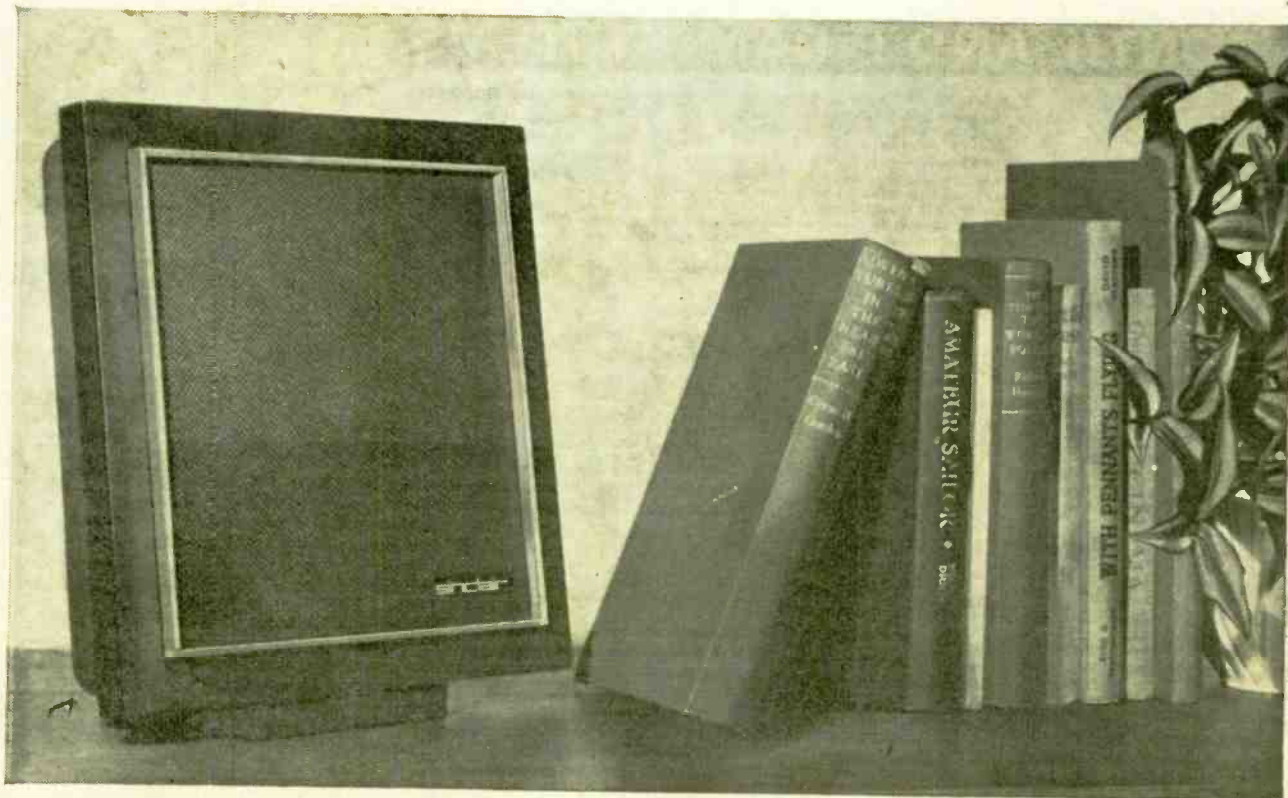

SINCLAIR Q.14 a truly superb loudspeaker

- ACOUSTICALLY CONTOURED SOUND CHAMBER
- MAXIMUM LOADING IN EXCESS OF 14 WATTS
- BRILLIANT TRANSIENT RESPONSE
- 15 OHMS IMPEDANCE
- OF COMPACT AND ORIGINAL DESIGN
- AN ALL-BRITISH PRODUCT

Price need no longer stop you enjoying first-class high-fidelity loudspeaker reproduction nor is size any longer a problem. (These considerations are of utmost importance to every enthusiast for stereo.) In the Sinclair Q.14 you will find a loudspeaker of such remarkable quality and so compactly and attractively styled that you will want to change over to Sinclair as soon as you hear it. This is no ordinary loudspeaker. Indeed, at a recent trade demonstration experts were greatly impressed on hearing the Q.14 against speakers costing many times as much. It proves beyond question that good reproduction need not be expensive.

When tested in an independent laboratory a Q.14 from stock showed exceptionally smooth response between 60 and 16,000 c/s with well sustained output both below and above these readings. Its remarkable transient response ensures clean-cut separation between instruments, voices, etc. Much

of its success results from the use of materials different from those found in conventional speaker manufacture. The unusual shape of the sealed, seamless pressure chamber allows the Q.14 to be conveniently positioned on shelves, in wall corners, or flush mounted in assemblies of one or more units.

"More than delighted"

"I have tested them (two Q.14's) side by side with two first class speakers in large reflex cabinets coupled to a very good Hi-Fi stereo set up and can honestly say the Q.14 is superior to the speakers I have been using. Every note came through perfectly. I am more than delighted. I would like to congratulate you on producing such a fine unit."—J.R.H., Blackpool.

Try the Q.14 in your own home by sending the order form off today. If you are not satisfied your money plus the cost of returning the Q.14 to us will be refunded in full.

SENT POST FREE TO ANY PART OF U.K.


£6 . 19 . 6

sinclair

SINCLAIR RADIONICS LTD. 22 NEWMARKET ROAD,
CAMBRIDGE.

Phone: OCA3-52996

WW-106 FOR FURTHER DETAILS

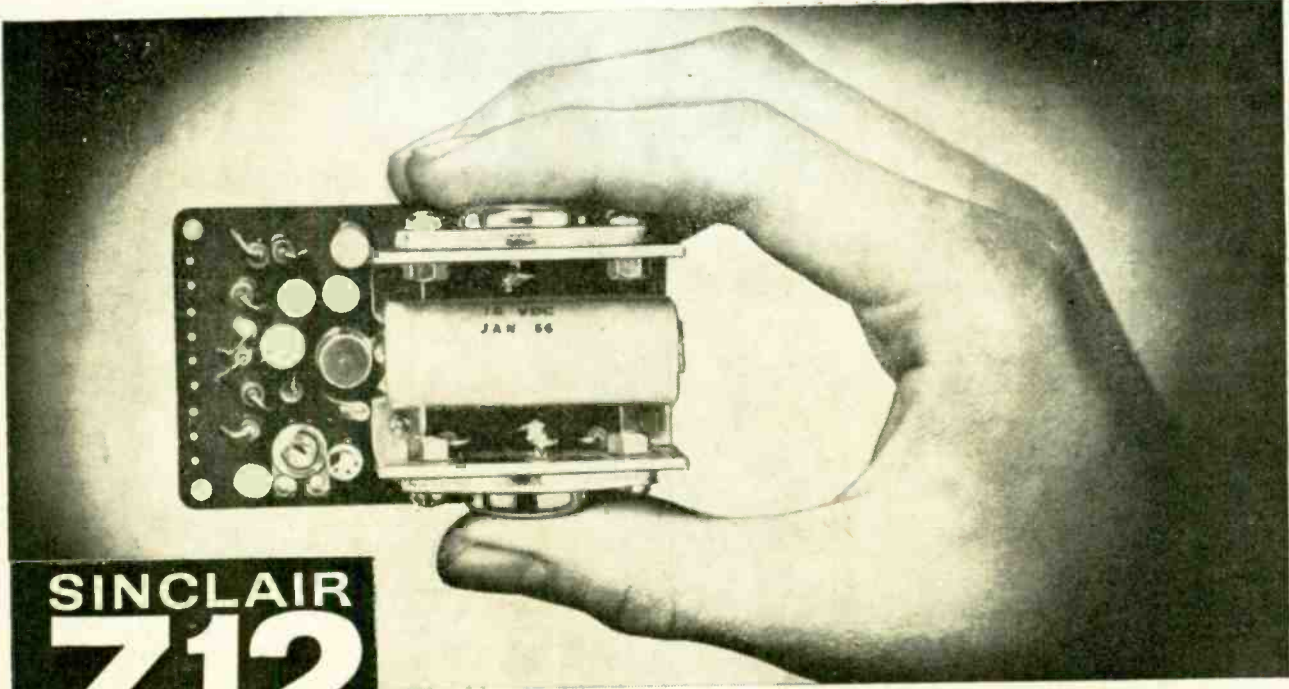

SINCLAIR Z.12

COMBINED 12 WATT HI-FI AMP AND PRE-AMP

Fantastic power & versatility

- 12 Watts R.M.S. continuous sine wave. (24 w. peak.)
- 15 watts music power (30 w. peak.)
- Ultralinear class B output
- Input —2mV into 2 K/ohm
- Output suitable for 15, 7.5 and 3 ohm speakers. Two 3 ohm speakers may be used in parallel
- 15-50,000 c/s ± 1 dB
- Ideal for battery operation
- 3" x 1 1/2" x 1 1/2"

BUILT, TESTED AND GUARANTEED

89/6

A NEW SINCLAIR POWER UNIT



The Z.12 proves beyond all question that high-fidelity can be combined with very low price. No other integrated amplifier system so successfully meets such a wide range of requirements. The Z.12 will operate from any power supply between 6 and 20 v. D.C. The output is suitable for any impedance between 1.5 and 15 ohms, and consequently for any loud-speaker including, of course, the Sinclair Q.14. This remarkable amplifier has facilities for matching to any types of conventional inputs, details of which are given in the Z.12 manual supplied. Included amongst popular applications for the Z.12 are mono and stereo high fidelity systems (two are needed for stereo), guitars, electric organs, car radios and P.A. and intercom systems, etc. It is also of great value in experimental work where dependable standards are required.

"All you claim for it"
 "The Sinclair Z.12 is all and more that you claim for it. Its performance is outstanding. Thank you for your prompt service."—S/Sgt. R., B.A.O.R.
"Performance excels that of many systems"
 "I have built a stereogram employing 2 Z.12 amplifiers and a PZ.3. I am delighted with the reproduction which is better than some I have heard costing over double the price. It has also silenced some of the old brigade who stubbornly believe that nothing can beat valves."—R.H., Argyll.

SINCLAIR STEREO 25 PRE-AMP/CONTROL UNIT
 For use with two Z.12s or any hi-fi stereo system. Frequency response 25 c/s to 30 kc/s ± 1 dB. Switched inputs for P.U., Radio, Microphone, etc. Equalisation correct to within ± 1 dB on RIAA curve from 50 to 20,000 c/s. 6 1/2 in. x 2 1/2 in. x 2 1/2 in. plus knobs. **£9.19.6**
 BUILT, TESTED AND GUARANTEED

PZ.4. Heavy duty, stabilized power pack to meet requirements of Z.12 assemblies in stereo, etc. Output 18 V.D.C. at 1.5A **99/6**

GUARANTEE
 Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full and at once without question.
 If you prefer not to cut page please quote WW268 when ordering.



SINCLAIR MICROMATIC

The world's smallest radio now includes magnetic ear-piece, yet costs less.

Prices of the Micromatic have been substantially reduced. Performance has been improved by the inclusion of a new magnetic type ear-piece. These two facts mean that still more enthusiasts can enjoy even better performance from this fabulous little set—and it's all British, too. Keep a Micromatic to hand always—it plays anywhere. Size 1 3/4 in. x 1 1/4 in. x 1 1/4 in. Formerly 59/6 in kit form and 79/6 built and tested. **KIT NOW 49/6** Built and tested **59/6**
 Two mercury cells for Micromatic—each 1/11.

MICRO FM

Less than 3 in. x 1 1/2 in. x 1 1/2 in. 7 transistor F.M. Superhet using pulse counting discriminator. Low I.F. makes alignment unnecessary. Tunes 88-108 Mc/s. The telescopic aerial suffices for good reception in all but poorest areas. Signal to noise ratio—30dB at 30 microvolts. One outlet for amplifier or recorder, one for use as a pocket portable. Complete Kit inc. earpiece. **£5.19.6**

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send POST FREE

NAME

ADDRESS


.....

.....

For which I enclose cash/cheque/money order. WW263

WW—107 FOR FURTHER DETAILS

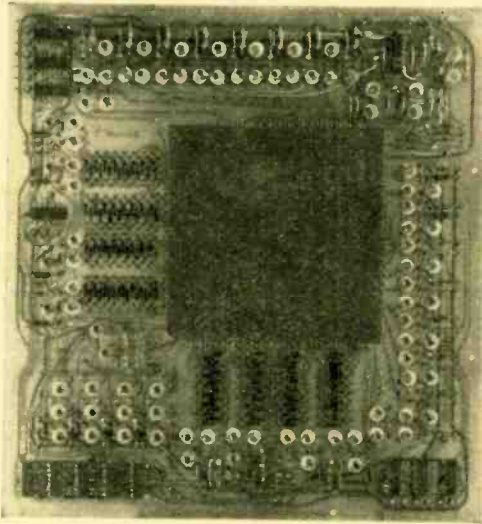AT LAST a small capacity CORE STORE 1024, 4 bit words at 1/4^{d.} a BIT



MEASURING 11" x 10 1/4" x 1 1/8"

This model is one of a range of Core Stores offering a variety of word/bit combinations.

Type CS550.	1024 Single bit words	at £135
Type CS442.	256 Four bit words	at £135
Type CS552.	1024 Four bit words	at £270
Type CS444.	256 Sixteen bit words	at £335
Type CS453.	512 Eight bit words	at £310

These stores comprise a core matrix, address selection, control circuitry and output staticisers mounted on a single unit.

We also undertake the complete design and manufacture of special purpose digital systems.

If you require a reliable low cost core store, contact



TREND ELECTRONICS LTD.
St. John's Works, Tylers Green
Nr. High Wycomb, Bucks.
Telephone: TYLERS GREEN 322


WW-108 FOR FURTHER DETAILS

putting
quarts



into
pints!
—electronically
speaking!

Vero are electronic packaging specialists. A wide range of standard Vero-boards, Card Frames, Module Racks and Cases are available from stock. In addition we are always prepared to discuss special designs and requirements, but prefer to be consulted early so that our designers can work closely with yours. Our design experience and know-how is invaluable in electronic problems where maximum space utilisation is important.

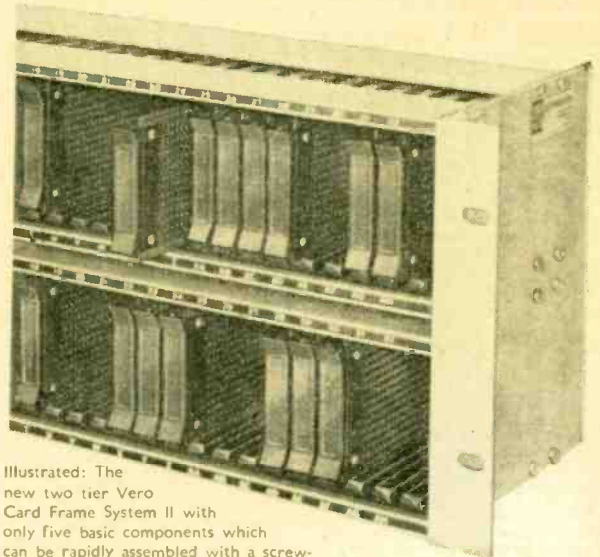


Illustrated: The new two tier Vero Card Frame System II with only five basic components which can be rapidly assembled with a screw-driver. Lightweight: excellent cooling: simple identification. multiple connector mounting.

Send now for full details to:-
VERO ELECTRONICS LTD
INDUSTRIAL ESTATE, CHANDLERS FORD, EASTLEIGH,
HANTS, S05 3ZR Tele: Chandlers Ford 2921/4. Telex 47551
BRANCHES AND AGENTS THROUGHOUT THE
WORLD

WW-109 FOR FURTHER DETAILS

FULLY APPROVED RELAYS QUICK DELIVERY


A.D.S. P.O. 3000 SERIES

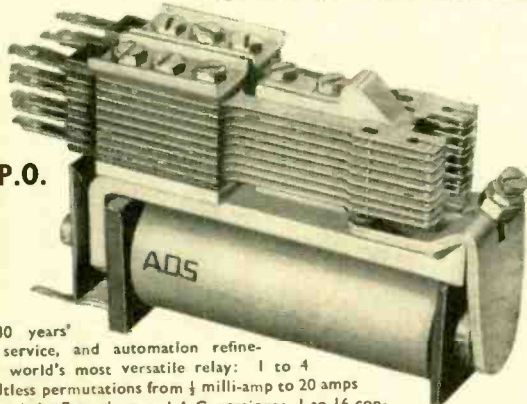

Through 30 years' telephone service, and automation refinements, the world's most versatile relay: 1 to 4 coils in limitless permutations from 1/2 milli-amp to 20 amps (0.1 to 400 volts); Fast, slow, and A.C. versions; 1 to 16 contact units (36 springs max.); Standard contacts 0.3 to 1 amp; Alternatives for switching Dry-state, Inductive, and 10 amp circuits. Insulation from 100 to 4,000 volts; Life up to 100 million operations; Plain or tropical finishes; Approx. dimensions 1 3/8" x 3 1/2" x 2 1/2" max. An A.D.S. 3000 Type to meet all specifications-G.P.O., E.I.D. C.E.G.B., ADMIRALTY, U.K.A.E.A., ALL COMMERCIAL, ETC.

A.D.S. P.I. PLUG-IN 3000 TYPE

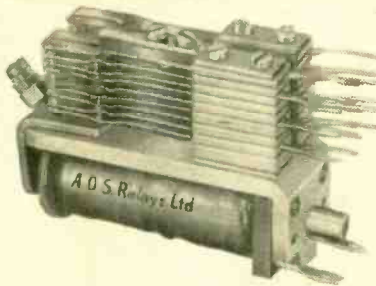Plug-in version, enabling relays to be changed in seconds. Fully approved.



A.D.S. MINI G.P.


Special ADS miniaturised 600 Type: Single or double windings; 1 to 8 contact units (24 springs max.); Ideally suited to printed circuit and general purpose uses; A sensitive miniature Relay built to suit each specific requirement: Minimum operation below 50 milliwatts (3 mA in 5,000Ω coil). A.C. coils available. Approximate dimensions: 3/4 in. x 1 1/2 in. x 2 1/4 in. (plus tags).

A.D.S. P.O. 600 SERIES

Miniaturised 3000 with similar, but restricted, specification; only 3/4 in. chassis space (twelve = nine 3000 Type); 1 or 2 coils: 1 to 6 contact units (14 springs max.). Approx. 1 1/2 in. x 3 3/4 in. x 1 1/2 in.

A.D.S. LITTE KING (at right)

Screw-Fix type 2, 3 and 4 pole. Quick-Change (Plug-in Type) 2 and 3 pole 12 and 24 v. D.C., 100 and 240 v. A.C. Ex-stock. Little space required: Screw-Fix 1.7 sq. in., Quick-Change 2.0 sq. in. King size switching: Screw-Fix 2 kVA, Quick change 1.5-kVA, 10 million operations (proof tested to 27 million). Power transfer=1,500. Max. current gain=1,400 (coil to all contacts). LK2C (2 pole screw-fix type)—10 amps/400 volts (1,000 VA max.) per pole.

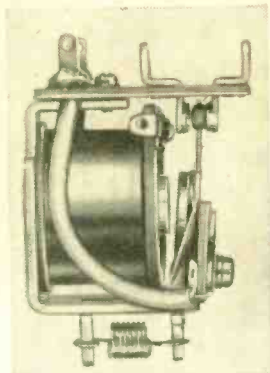


A.D.S. RELAYS LTD.

97 ST. JOHN STREET,
LONDON, E.C.1.
Telephone: 01-253 3393

WW-110 FOR FURTHER DETAILS

NEW SWITCHED ATTENUATOR

Type 687E

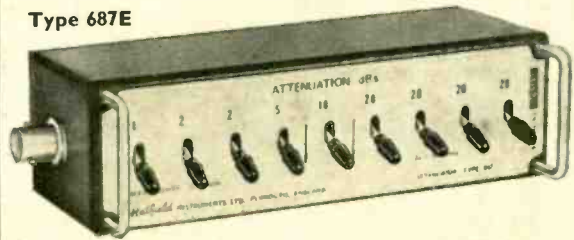

*** 600 ohms impedance**


The new Hatfield type 687E Switched Attenuator extends the present range of 50 and 75Ω impedance models (Types 687A and B), features 600Ω input and output impedance and frequency range D.C. to over 1 MHz. All three models provide precise switched attenuation from 1-100 dB in 1 dB steps and are housed in die-cast aluminium boxes only 5 1/2 x 1 5/8 x 2 1/2 in., fitted with two B.N.C. coaxial sockets.

Type Q



Impedance levels 50 or 75 ohms. Available for the ranges 0-1.1dB up to 50 MHz, 0-11dB in 1dB steps or 0-110dB in 10dB steps, frequency range D.C. to 500 MHz.

Type 708

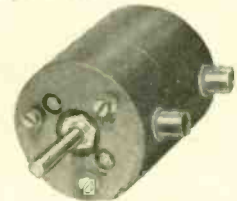

Offers reliable operation up to 100 MHz yet is low in cost, and can be used equally well in equipment or inserted in lines without mismatch.

Write for fully illustrated literature on the complete range of Hatfield Attenuators and for a copy of the new edition the SHORT FORM CATALOGUE.


HATFIELD INSTRUMENTS LTD. Dept. WW., Burrington Way, Plymouth, Devon.

Telephone: Plymouth (0752) 72773/5. Telegrams: Sigien, Plymouth.

HATFIELD BALUN

WW-111 FOR FURTHER DETAILS

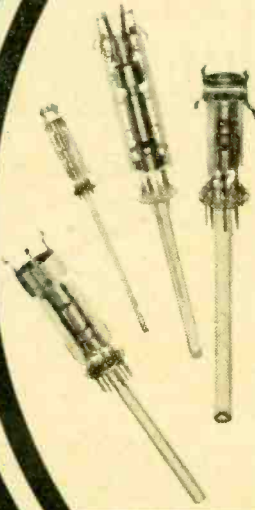SUPERIOR...WORLD LEADER in the manufacture of ELECTRON GUNS exclusively!



Now, from new, modern, expanded facilities . . . men, minds and machines coupled with professional experience, organization and resources produce SUPERIOR ELECTRON GUNS . . . unequalled throughout the world!

Precision guaranteed, quality built, with optimum functional reliability, SUPERIOR ELECTRON GUNS give you the widest range of electrostatic and magnetic focus types available . . . for color and black and white application in commercial, industrial, special purpose, military and European tube types.

Write today for further information and catalog of facilities and types.

SUPERIOR ELECTRONICS Company

(Division of AIKEN INDUSTRIES, Inc.)

CLIFTON, N. J., U. S. A. / CABLE ADDRESS: "SECO" CLIFTON, N. J., U. S. A.

LONDON STOCKISTS: ELECTRODE WELDING CO., LTD.

Jubilee Works Cobbold Road, Willesden, London N.W. 10, England

Telephones: Willesden 5050 / Willesden 6655-6

Telegrams: Elecwhyb Norphone London Cables: Elecwhyb. London, N.W. 10




© 1967 Superior Electronics Co.

WW-112 FOR FURTHER DETAILS

SOLDERING ?

—you need the Antex
SOLDERING TOOL KIT

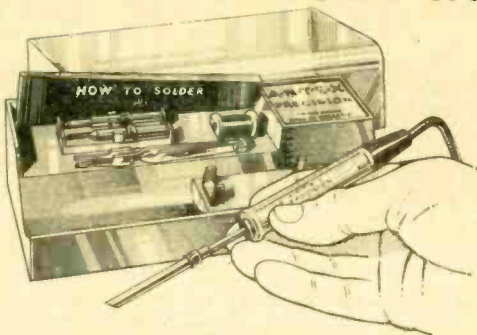

- Model CN240 15W Precision Iron with $\frac{1}{16}$ " bit,
- Two spare Interchangeable Bits ($\frac{3}{32}$ " and $\frac{1}{32}$ ")
- Reel of Solder ● Heat Sink ● Cleaning Pad
- PLUS 36-page booklet on "How-to-Solder"

British made. From The Army & Navy Stores, Harrods, and Radio Shops, or if unobtainable locally, direct from:

49'6" ANTEX LTD

GROSVENOR HSE · CROYDON · CR310E

Telephone: 01-686 2774

WW-113 FOR FURTHER DETAILS



STOCKISTS




MULTIMINOR MK. 1V

REPAIR SERVICE
7-14 DAYS

We specialise in repair, calibration and conversion of all types of instruments, industrial and precision grade to BSS.89.

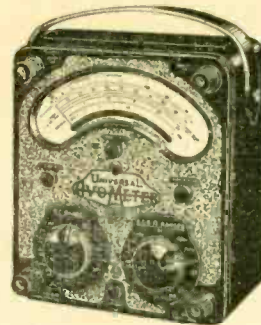Release notes and certificates of accuracy on request.



MODEL 8 MK. 1V

Suppliers of Elliott, Cambridge and Pye instruments

LEDON INSTRUMENTS LTD


76-78 DEPTFORD HIGH STREET, LONDON, S.E.8

Tel.: TIDeway 2689

E.I.D. & G.P.O. APPROVED

CONTRACTOR TO H.M. GOVT

WW-114 FOR FURTHER DETAILS

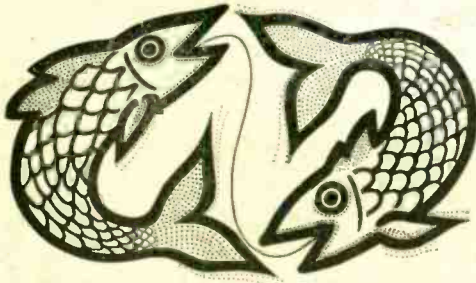

**If you were born under
PISCES**

remember there's an RTS in the month!

A period in which you can beat all targets. Aim high, but avoid placing undue reliance on jaded sources of supply. Temporary setbacks brilliantly overcome by resorting to RTS 'by-return' service on electronic components.


Lucky numbers: Cambridge (OCA3) 51471 -for orders
Cambridge (OCA3) 59101 -other business

Send for comprehensive catalogue today to see what RTS holds in store for you.

RTS for all your components, by return, even overseas!



RADIO AND TELEVISION SERVICES LIMITED
P.O. Box 11 Gloucester Street, Cambridge

A MEMBER OF THE  GROUP OF COMPANIES

WW-115 FOR FURTHER DETAILS

**Looking for
one like this?**



6mm tubular midget
flange S6/8 cap
over-all length
14.5 mm.


It is one of the many Vitality Instrument and Indicator Lamps that are made in an unusually large number of types, ratings and sizes. It may be just what you need for an existing or new project. If not, another from the hundreds of Vitality types and ratings may well be. Catalogue 66, free and post-free, details them all.

**Many a product owes its success to the intelligent addition of an indicator light.*


VITALITY BULBS

VITALITY BULBS LTD MINIATURE AND SUB-MINIATURE LAMP SPECIALISTS
BEETONS WAY, BURY ST. EDMUNDS, SUFFOLK. TEL. BURY 2071. S.T.D. 0284 2071
WW-116 FOR FURTHER DETAILS

**NEW
MODULATORS...
FROM STOCK**

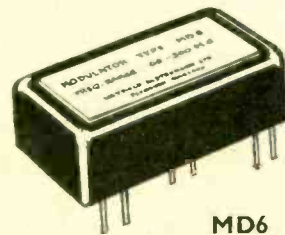

MD6

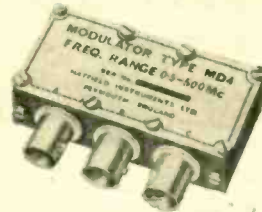

MD4

Recent additions to the Hatfield range of Attenuators, Hybrids, and Modulators include: TYPE MD4, a compact V.H.F. Double Balanced Modulator using "Hot Carrier" Diodes, capable of very good performance as an amplitude modulator, mixer, phase detector or current controlled V.H.F. Attenuator. Input and output frequency range is 0.5-300 MHz.

TYPE MD5, the newest development, with similar features to Type MD4, but fully encapsulated and suitable for direct mounting on printed circuit boards. Large scale production of this type makes possible an extremely competitive price.

Deliveries of both these types can be made from stock. Write now for fully detailed literature of the complete range, and for your copy of the new edition of the HATFIELD SHORT FORM CATALOGUE.


HATFIELD INSTRUMENTS LTD.
Dept. WW., Burrington Way, Plymouth, Devon.
Telephone: Plymouth (0752) 72773/5
Telegrams: SIGJEN, Plymouth.

HATFIELD BALUN

WW-117 FOR FURTHER DETAILS

WHITELEY for acoustic hoods

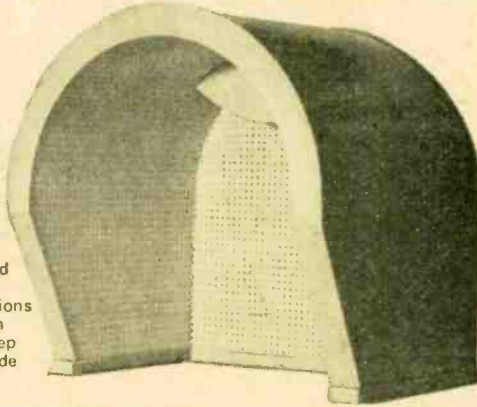
All noisy environments such as factories, workshops, department stores and hotels require the facility of an acoustic hood which permits telephone conversations to be held without the interference of annoying background noises. Whiteley acoustic hoods are strongly made from resin bonded ply and finished in a cellulose enamel which makes these suitable for indoor or outdoor use.



Standard Hood Dimensions
25" high
20 1/4" deep
24 1/2" wide



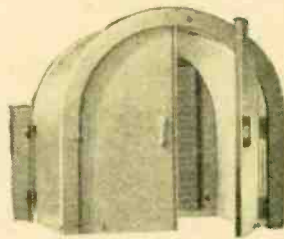Fitted with loudspeakers
Also available with internal light and/or a storage shell below hood



Fitted with doors for outdoor use

& directory holders



These attractive, and extremely functional directory holders will hold five directories neatly and securely, in individual swivel holders permitting easy identification and reference. The lower shelf provides additional storage space. The units are of cast alloy and are finished in an attractive grey epoxy resin enamel and constructed to strict G.P.O. design specifications.

Directory Holder Dimensions
17 1/4" high x 13 1/2" wide x 13 3/8" deep

For further details please write or telephone

WHITELEY ELECTRICAL RADIO CO. LTD

MANSFIELD · NOTTS · ENGLAND Tel: Mansfield 24762
London Office: 109 KINGSWAY, W.C.2 Tel: HOLborn 3074

WW-118 FOR FURTHER DETAILS

Solder with the NEW & IMPROVED PRIMAX OR PRIMAXA SPOTLIGHT SOLDERING GUN

INSTANT HEAT 6 Seconds!

Twin Spotlight

SEE WHERE YOU SOLDER!

PRIMAX
60 WW SPOTLIGHTS
99/8d EACH 5/- P & P.


PRIMAXA
100 WW SPOTLIGHTS
129/8d EACH
5/- P & P.

Distributors:

S. KEMPNER LIMITED
384A Finchley Road · LONDON · N.W.2.
Tel : 01-794 2371—01-435 6365

WW-119 FOR FURTHER DETAILS

WELWYN TOOLS

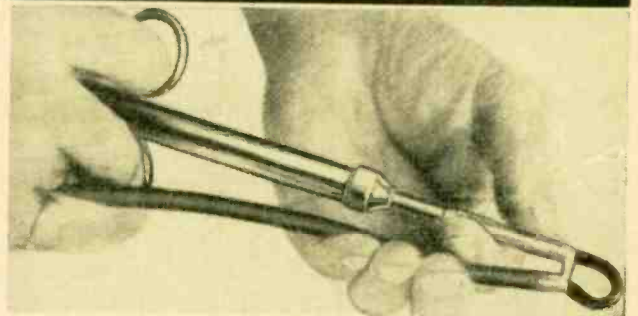

L67 - KIT - CN

For Inner Core Ejection and Heated Wirestripping Miniature Soldering and Electronic Instrument Work

USE W.T.C. Wire Ejectors, LUCO Electrically Heated Wire Strippers (see illustration), Finest Soldering Needles, Box Joint Miniature Cutters and Pliers including Tip Cutting Pliers, Printed Circuit Crimping and Cutting Pliers, Torque Wrenches and Piercing Punches. If you require quality tools ask for Catalogue WW/68.



Welwyn Tool Co. Ltd.

STONEHILLS HOUSE · WELWYN GARDEN CITY · WELWYN GARDEN 25403

WW-120 FOR FURTHER DETAILS



DIGITAL DISPLAY UNITS

£4.5.0

0-9 with decimals, lit by 6.3v bulb.

- * Assemble units into groups to give countless permutations of numbers.
- * Maximum legibility from a wide angle through uniform intense characters.
- * Applications in every industry, for instantaneous readout of anything numerical.
- * Price of £4/5/- includes post and packing.

Automatic Machine Service
(CARDIFF) LTD.

ACE HOUSE, FERRY, ROAD, CARDIFF. TEL. 41456

WW-121 FOR FURTHER DETAILS

THERE'S A **TRANSIPACK**®

STATIC INVERTER or NO-BREAK POWER SUPPLY

to suit you —



BEST

- DESIGN
- PERFORMANCE
- DELIVERY

SINE AND SQUARE WAVE
—UP TO 80 K.V.A.—

INDUSTRIAL INSTRUMENTS LIMITED
STANLEY RD., BROMLEY, KENT
Tel. 01-460 9212. Telegrams: Transipack, Bromley

WW-122 FOR FURTHER DETAILS

The new V51 helical range of MEC miniature wirewound potentiometers offers high resolution in very small size. 3, 5 & 10-turn units are available. Resistance values range from 220Ω 3-turn, resolution 0.262%, to 220K 10-turn, resolution 0.017%. 3-turn units have continuous power rating 0.25W, 5-turn 0.5W and 10-turn 1W at 70°C.

Sealed construction, proof against humidity, vibration, shock, altitude and acceleration to meet Def 5011 severities. Prices from 28/- depending on quantity.

Miniature Electronic Components Ltd.,
St. Johns Woking Surrey
Telephone Woking 63621


3 1/8" dia.



The smallest helical potentiometer available in UK.

m-e-c
Trimmer Potentiometers
Wire-wound Resistors
Miniature Switches
Elapsed Time Meters

WW-123 FOR FURTHER DETAILS

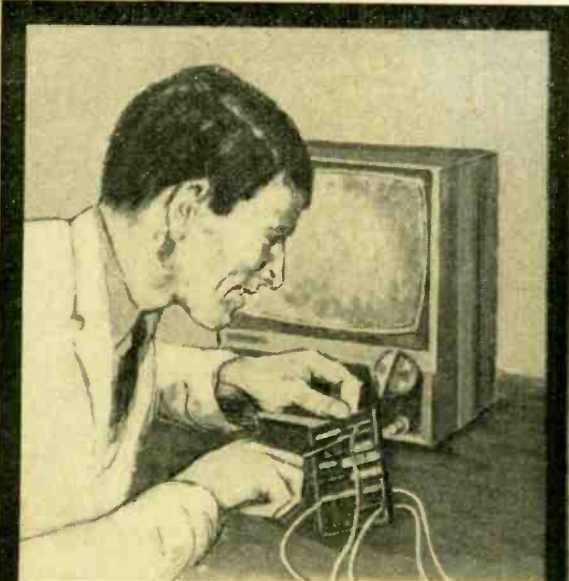

Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full time 16 month College Diploma Course which gives a thorough fundamental training for radio and television engineers, starts on 24th April 1968.

The Course includes theoretical and practical instruction on Colour Television receivers and is recognised by the Radio Trades Examination Board for the Radio and Television Servicing Certificate examinations. College Diplomas are awarded to successful students.


The way to get ahead in this fast growing industry—an industry that gives you many far-reaching opportunities—is to enrol now with the world famous Pembridge College. Minimum entrance requirements: 'D' Level. Senior Cambridge or equivalent in Mathematics and English.

To: The Pembridge College of Electronics
(Dept. WW), 34a Hereford Road, London, W.2
Please send, without obligation, details of the
Full-time Course in Radio and Television.

NAME


ADDRESS

WW—124 FOR FURTHER DETAILS

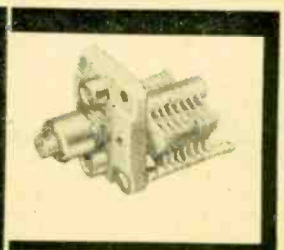

for
**VARIABLE
CAPACITORS**

**TERMINAL
STRIPS**

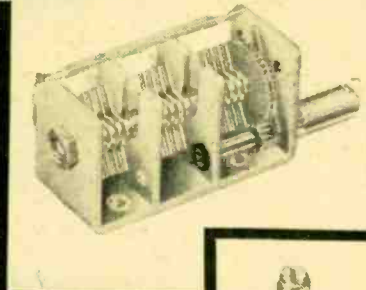

LEADTHROUGH INSULATORS



WINGROVE & ROGERS LTD
DOMVILLE ROAD · LIVERPOOL 13

Telephone: Stoneycroft: 2265

LONDON OFFICE: 75 Uxbridge Road · Ealing W.5. Tel: 01-567 7046

WW—125 FOR FURTHER DETAILS

AERIAL HANDBOOK

By **G.A. BRIGGS**
with **R.S. ROBERTS**
C.Eng. M.I.E.R.E. Sen M.I.E.E.E. as Technical Editor

Second Edition PUBLICATION DATE 26th JAN. 1968

176 Pages, Fine Art Paper. 144 Illustrations (including 50 new to this Edition and 14 Cartoons).

Price 15/- (16/- post free), Semi-Stiff cover.

22/6 (24/- post free), Cloth bound Library Edition.

The first edition of *Aerial Handbook* was published in Oct. 1964 and the 5,000 copies were sold out in just over a year.

This second edition has been delayed until the plans for Colour Television & Multiplex Stereo had matured and could be dealt with from the angles of Transmission and Reception.

The activities of the B.B.C. and I.T.A. are well covered. Relay Systems, Eurovision, World Satellites and Colour Conversion, Post Office Tower, etc., also receive attention in non-technical terms.

CONTENTS

Chapter	No. of Pages	Chapter	No. of Pages
1. General Principles	16	7. Indoor Aerials	9
2. Medium and Long Waves	7	8. Diplexers, Multiplexers and Splitters	6
3. Short Waves	3	9. Boosters and Attenuators	10
4. VHF and Band II (FM & Stereophonic Sound)	15	10. Transmitters (including Colour TV & Stereo)	44
5. Television, Bands I and III (UHF)	14	11. Relay and Communal Systems	20
6. Television, Bands IV and V (UHF)	14	12. Questions and Answers	7

Sold by Radio Dealers and Book Shops or in case of difficulty direct from the Publishers:



RANK WHARFEDALE LIMITED,
IDLE, BRADFORD, YORKSHIRE.
Tel.: Bradford 612552.

WW—126 FOR FURTHER DETAILS

WEYRAD

COILS AND I.F. TRANSFORMERS IN LARGE-SCALE PRODUCTION FOR RECEIVER MANUFACTURERS

- P.9 SERIES** 10 mm.×10 mm.×14 mm. Ferrite cores 6 mm. 472 kc/s operation, Single-tuned I.F.s and Oscillator Coils.
- P.55 SERIES** 12 mm.×12 mm.×20 mm. Ferrite cores 4 mm. 472 kc/s operation. Single-tuned I.F.s and Oscillator Coils.
- T.41 SERIES** 25 mm.×12 mm.×20 mm. Ferrite cores 4 mm. 472 kc/s operation. Double-tuned 1st and 2nd I.F.s and Single-tuned 3rd I.F. complete with diode and by-pass capacitor.

These ranges are available to manufacturers in versions suitable for most of the popular types of Transistors. The Oscillator coils can be modified to enable specific tuning capacitors to be used provided that bulk quantities are required.

**OUR WINDING CAPACITY NOW EXCEEDS
50,000 ITEMS PER WEEK**

On the most up-to-date and efficient machines backed by a skilled assembly labour force for all types of coils and assemblies.

WEYRAD (ELECTRONICS) LIMITED, SCHOOL ST., WEYMOUTH, DORSET

WW-127 FOR FURTHER DETAILS



It's easier...

to find small components in
a transparent **raaco** drawer cabinet



It keeps all your transistors, bulbs, screws, bolts, nuts, etc. VISUAL, ASSORTED AND ALWAYS AVAILABLE

THE MOST COMPACT SYSTEM FOR STORAGE OF SMALL ITEMS

- see at a glance avoids searching
 - heavy gauge reinforced steel frames
 - transparent, dividable plastic drawers
 - self-supporting, standardized units
 - stackable or suspendable for speedy erection or alteration into larger sections
 - more than 20 different models
- FOR MODERN AND EFFICIENT STORAGE OF ALL SMALL COMPONENTS INSIST ON

raaco

MODEL 36 A
£ 4.10.0


For detailed information and illustrated brochure write to

RAACO (London) Ltd.,
52/54 High Holborn,
London W. C. 1.


WW-128 FOR FURTHER DETAILS

Bullers CERAMICS

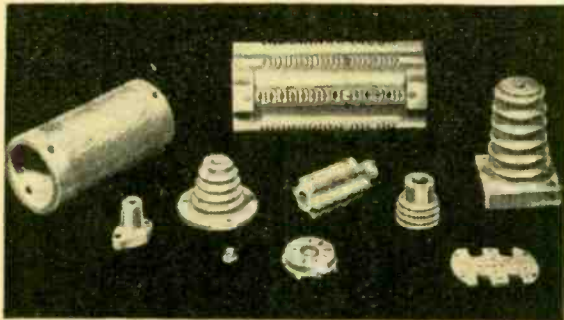
for the **ELECTRONIC INDUSTRY**
(and Electrical Appliance Manufacture)



Frequelex—for high-frequency insulation.

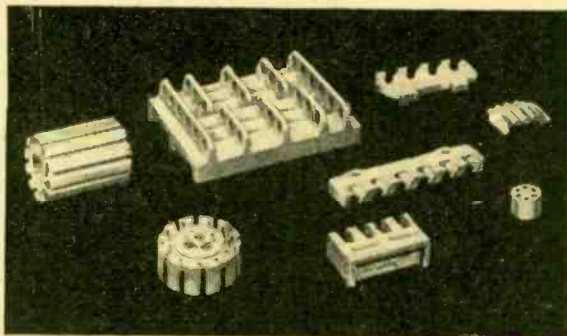

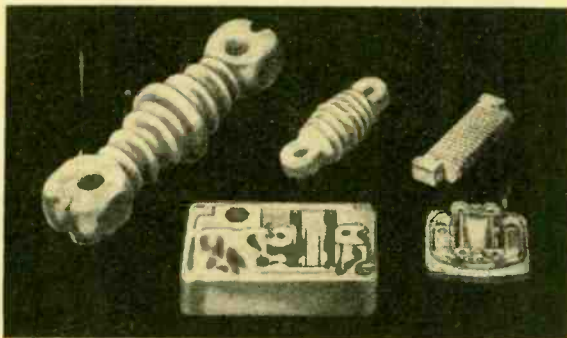Refractories for high-temperature insulation



Bullers porcelain for general insulation purposes.

Meticulous care in manufacture, high quality material, with particular attention applied to *dimensional precision and accuracy*, explain the efficiency and ease of assembly when using Bullers die pressed products. Write today for detailed particulars.

BULLERS LIMITED

Milton, Stoke-on-Trent, Staffs.

Phone: Stoke-on-Trent 54321 (5 lines)
Telegrams & Cables: Bullers, Stoke-on-Trent
London Office: 6 Laurence Pountney Hill, E.C.4
Phone: MANsion House 9971

WW-129 FOR FURTHER DETAILS

TELETON COMES TO THE U.K.

Already highly successful in Belgium, Germany, Switzerland, Holland, France, and Italy, we now proudly present the finest integrated Solid-State Hi-Fidelity Equipment for your approval. Ultra-modern designs have been created according to European technical standards and popular requirements. These outstanding products are supplied exclusively to us by MITSUBISHI Shoji Kaisha of Japan.

Superbly styled in oiled walnut, TELETON Tuner/Amplifiers include AM/FM Multiplex facilities, comprehensive filters, four inputs and up to fifty watts RMS output, at prices to suit even the most modest pocket.

As an example of unsurpassed value, the TELETON SRQ 302X Solid-State AM/FM Multiplex Stereo Tuner with integrated Amplifier (20 watts RMS) is available in a matt oiled-walnut case—price only 64 gns. retail!


There are over fifty TELETON products from which to choose, and these include Stereo Tape Recorders, Radios, Cassette Recorders, Transceivers, Memopacks and Stereo Loudspeaker Systems. Centralised bulk purchasing power enables us to compete most favourably with any Company in the U.K. and our home-based Service Department implements a full 12 months Warranty.

TELETON home-entertainment units are obtainable from most high-class specialist dealers, or from selected wholesalers. Representative brochures and price lists are available to bona-fide trade enquirers, and a comprehensive display of the products may be seen in our Showroom by arrangement.

Telephone or write for further details to—
TELETON ELEKTRO (U.K.) CO., LTD.,
66-68 Margaret Street,
London, W.1.

Telephone: 01-636 6491

WW-130 FOR FURTHER DETAILS

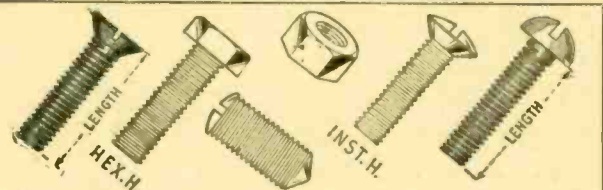

We supply B.A. Screws, etc. in brass, steel, stainless, phosphor bronze and nylon to laboratories throughout the Commonwealth.

We can also offer early delivery for many sizes of screws, etc. with Metric Threads.

Please send for List W9/65 (WW)

WALKER-SPENCER COMPONENTS LTD.
5, High Street, Kings Heath, Birmingham, 14.


Telephone: (021 for STD) HIGHBURY 3155 (Sales)

WW-131 FOR FURTHER DETAILS

Your choice of Live Sockets - Instantly!

A Lexor DIS-BOARD gives you up to 6 sockets from one power outlet. Portable or permanent fixing, compact units, with safety neon. Over 1,000 socket combinations available from stock. All types of fittings and finishes.

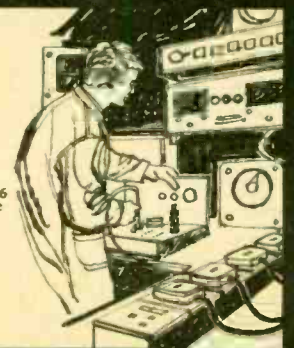brochure from
LEXOR DIS-BOARDS LIMITED,
Allesley Old Road, Coventry.
Telephone 72614 or 72207



WW-132 FOR FURTHER DETAILS

RECEPTION SETS R220/R220

These comprise two crystal controlled AM receivers and can be operated independent of each other on one spot frequency in the band 60-100 Mc/s., with built-in monitor speaker. They are housed in one metal cabinet, size 21½ x 12½ x 18½ in. and ready for immediate mains operation (200-250 v. 50 c/s.). Supplied BRAND NEW in original crate, complete with spares and manual. £20. Carr. 50/-.

POWER UNIT TYPE 24 FOR R.216 RECEIVER. A.C. operated 100-125 or 200-250 volts 50 c/s. BRAND NEW AND BOXED. £9/19/6. Carr. 10/6.

FILTER VARIABLE BAND PASS No. 1. Dual channel unit, each channel has variable slot frequency of 500-900 c/s., 1,200-1,600 c/s., and band pass facility. 600 ohms input and output, monitor input and high impedance output jacks. Standard rack mounting 3½ in. deep panel. Mains operation 200/250 v. 50 c/s. BRAND NEW. £5/19/6. Carr. 10/-.

HRO TUNING METER. 0-1 ma. New and boxed 25/- Post 2/-.

BC221 FREQUENCY METER
125 Kc/s. to 20 Mc/s.

This crystal controlled heterodyne frequency meter is too well-known to need further description. Those we offer are complete with correct individual calibration book and are carefully tested and guaranteed. New condition. **£30**

Laboratory Standard

Also some less calibration book, in working order. £9/19/6. Carr. 10/-.

V.H.F. SIGNAL GENERATOR

MARCONI TF-801A/1. Covers 10 to 310 Mc/s. (4 bands). DIRECTLY calibrated. Int. Mod. at 400, 1,000 and 5,000 c/s. Attenuated or force output. Guaranteed overhauled, accurate and in perfect working order. **£35.** Carr. 1/-.

BEST FREQUENCY OSCILLATORS

MARCONI TF-195M. Covers 10 cps. to 40 kc/s. in two sweeps. 0 to 20 kc/s. and 20 to 40 kc/s. Output 2 watts into 600 or 2,500 ohms. Panel meter indicates output voltage. A.C. mains operation 100 to 250 volts. First class condition. Fully tested. **£20.** Carr. 30/-.

AMERICAN HEADSET TYPE HS-30-U 600 impedance. BRAND NEW and boxed, 15/-, postage 2/6.

DISTORTION FACTOR METER

MARCONI TF-142E. This instrument measures the percentage of total harmonic distortion in the fundamental frequency range 100 to 8,000 c/s. The lowest scale engraving is 0.05%. Will handle 2 watts (continuous) and will give satisfactory readings with only 1 mV input. Mains operated. Output impedance 600 ohms. Very good condition. **£20.** Carr. 20/-.

MICROAMMETERS

R.C.A. 0-500 microamps. 2½ in. circular flush panel mounting. Dials are engraved 0-15, 0-600 volts. As used in the American version of the No. 19 set. BRAND NEW and boxed 15/-, P. & P. 1/6.

AR-88 SPARES

Knobs, Medium size, Set of 8 10/-
Knobs, Large size 5/6
Condenser (3x4 mfd.). Post 4/6 12/6
Mains Trans. (L.F.) (postage 9/-) 42/6

MINIATURE RELAYS

240 v. A.C. coils. Contact assembly 2 "makes" and 1 C.O. 5 amps. Size 2x1½ x 1 in. Unused and removed from brand new equipment 8/6 post paid.

MOVING COIL PHONES. Finest quality Canadian with chamolux ear-muffs and leather-covered headband. With lead and jack plug. Noise excluding and supremely comfortable. 22/6. As above but complete with moving coil microphones 25/-.

DLR-5 Low impedance headphones with attached throat microphone. 12/6. All these items BRAND NEW. Postage extra 2/6.

CINTEL NUCLEONIC SCALERS

Nos. 36402 and 36411. Unused with handbook. List Price £300/£320. Our Price **£65.**

CRT Type 89D as used in the Cossor 1035 Oscilloscope. Brand New 59/6. P. & P. 4/6.

ADVANCE TEST EQUIPMENT

H1B Audio Signal Generator	£30 0
J1B Audio Signal Generator	£30 0
J2B Audio Signal Generator	£35 0
TT1S Transistor Tester	£37 10
VM76 AC/DC Valve Voltmeter	£72 0
VM78 AC Millivoltmeter (transistorised)	£55 0
VM79 UHF Millivoltmeter (transistorised)	£125 0

These are current production, manufactured in U.K. by Advance Electronics Ltd. (not discontinued models). Showing a saving of approximately 33½% on nett trade price. BRAND NEW, all in original sealed carton. Carr. 10/- extra per item. Special offer of 10% discount for schools and technical colleges, etc.

OSCILLOSCOPE TYPE 13A

Double beam. Time base 2 c/s. to 750 kc/s. Band width up to 5 Mc/s. Calibration markers at 100 kc/s. and 1 Mc/s. Operates from A.C. mains 100 to 250 volts. A completely reliable quality instrument. Supplied fully checked with circuit £22/10/-, Carr. 30/-.

HRO MODEL 5T £30

The octal valve version. In mint condition. Complete with all nine general coverage coil sets covering 50 kc/s. to 30 Mc/s. Instruction Booklet and circuit, but less external power supply. Carriage 30/-. Complete manual available at 30/- extra.

PRICES NOW REDUCED CINTEL EQUIPMENT. ELECTROLYTIC CAPACITANCE AND INCREMENTAL INDUCTANCE BRIDGE No. 36601

A modern instrument, all solid state, which accurately measures the capacity of electrolytic condensers from 0.1µF to 1,000µF under operating conditions. Leakage current and polarizing voltage are separately metered. Inductances from 100 mH to 100 H can also be measured with current up to 100 mA. A.C. mains operation. Unused with handbook. List Price £220. Our Price **£70.**

WIDE RANGE CAPACITANCE BRIDGE. No. 1864. A matching instrument to the above. All solid state. Mains operation. Measures from 0.002pF to 100µF. Unused with handbook. List Price £250. Our Price **£75.**

MARCONI TEST EQUIPMENT

PORTABLE FREQUENCY METER TYPE TF.1026 SERIES

TF.1026/4 2,000/4,000 Mc/s., TF.1026/5 1,800/2,200 Mc/s., TF.1026/6 3,800/4,200 Mc/s., TF.1026/7 1,700/2,100 Mc/s., TF.1026/9 2,425/2,525 Mc/s. **£40 each.**

WIDE BAND MILLIVOLT METER TYPE TF.1371 100µv to 300 mv in five ranges. 30 c/s. to 30 mc/s. **£45.**

VACUUM TUBE VOLTMETER TYPE TF.1300 A.C. measurement 0.05 to 100 v., 20 c/s. to 300 Mc/s. D.C. measurement 0.1 to 300 v. Each over 5 ranges. Will also measure ohms, 50Ω to 5mΩ in 2 ranges. **£45.**

SENSITIVE VALVE VOLTMETER TYPE TF.1100 100µv to 300 v. A.C. in 12 ranges. 10 c/s. to 10 Mc/s. Can also be used as a wide-band amplifier. **£50.**

DELAY GENERATOR TYPE TF.1415.

Provides sweep-delaying facilities when used in conjunction with the TF. 1330 (series) or similar oscilloscope. Alternatively, it may be used independently as a general purpose delay generator. **£35.**


TF.867.A Standard Signal Generator	£200
TF.890.A/1 R.F. Test Set	£150
TF.1020.A/2 R.F. Power Meter	£50
T.F.1066.B/2 U.H.F. F.M. Signal Generator	£200
TF.1067 Heterodyne Frequency Meter	£65
TF.1102 Amplitude Modulator	£40
TF.1221 Heterodyne Unit	£125
TF.1274 V.H.F. Bridge Oscillator	£40
TF.1275 V.H.F. Bridge Detector	£40
TF.1350/1 Power Unit for TF.1346/1	£40
TF.1400 Double Pulse Generator	£100

Detailed technical specifications supplied upon request. Offered BRAND NEW at fraction of original cost.

CHARLES BRITAIN (Radio) LTD.

11 UPPER SAINT MARTIN'S LANE LONDON, W.C.2. 01-836 0545

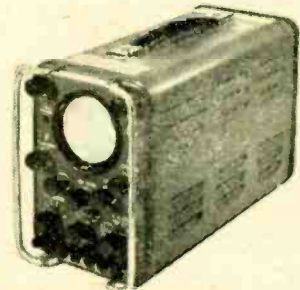Near Leicester Sq. Station. (Opposite Thorn House). Shop hours 9-6 p.m. (9-1 Thursdays). Open all day Saturday.



PORTABLE OSCILLOSCOPE CT.52.

A compact general purpose instrument with many unusual features. Size 9 in. high, 8 in. wide, 6½ in. deep. Time base 10 c/s. to 40 kc/s. Y plate sensitivity 40 v. per cm. Tube 2½ in. Frequency compensated amplifier up to 38 dB gain. Bandwidth up to 1 Mc/s. Single sweep facilities. Operates from A.C. mains 100-250 volts, 50 c/s. Complete with all test leads, metal transit case, instruction book and circuit diagram. BRAND NEW. Tested and guaranteed. £22/10/- Carr. 10/-.

SIGNAL GENERATOR CT-218 (FM/AM). MARCONI TF 937.

Covers 85 Kc/s. to 30 Mc/s. in 8 switched ranges. Effective length of film scale is 50ft. Output level variable in 1 dB steps from 1µV to 100mV (75Ω). Also IV Outputs down to 0.1µV from an outlet at 7.5Ω. Int. mod. at 400 c/s., 1 Kc/s., 1.6 Kc/s. and 3 Kc/s. FM at frequencies above 394 Kc/s. Variable mod. depth and deviation. Crystal calibrator 200 Kc/s. and 2 Mc/s. Monitor speaker for beat detection. Fully metered, blower cooled, Panclimatic. A.C. mains 100 to 150 and 200 to 250 volts, 45 to 100 c/s. 17 x 20½ x 17½ in. Weight 117 lbs. Fully tested and guaranteed. Fraction of original cost. **£65.** Carr. 50/-.

T.C.C. METALPACK CONDENSERS.

0.1 mfd. 500 v. D.C. wkg. at 70°C. Brand new, polythene wrapped, 7/6 doz., or £2 per 100. **T.C.C. METALMITE 350 v. D.C. wkg.** 0.1 mfd. (CP37N); 0.05 mfd. (CP35N); 0.91 mfd. (CP.32N) all at 5/6 doz. or 32/6 per 100. **SPRAGUE METAL CASED CONDENSERS** 0.01 mfd. 1,000 v. D.C. wkg., 5/6 doz., or 32/6 per 100.

T.C.C. VISCONAL CONDENSERS.

8 mfd. 800 v. D.C. wkg. at 71°C. CP 152 v. Size 3x1½x5 in. high. BRAND NEW (boxed), 8/6 each. **DUBLIER** 4 mfd. 600 v. wkg. CP 130T or similar. 1½ x 1½ x 4½ in. high. BRAND NEW (boxed), 4/6 each. All post paid.

STANDARD TRANSFORMERS

Vacuum Impregnated, interleaved, E.S. screen, universal mounting. Size 4x3½x2½ in. ALL BRAND NEW. 24/- each. Post 4/6. **Type 1.** 250-0-250 v. 80 mA. 6.3 v. 3.5 a., 6.3 v. 1 a., tapped at 2 a. **Type 2.** As above but 350-0-350 v. 80 mA. **Type 3.** 30 v. 2 a., tapped at 12, 15, 20 and 24 v. to give 3-4-5-6-8-9-10 v., etc. **Type 5.** 0-6-9-15 v. 4 a. Ideal for chargers.



LOW CAPACITANCE BRIDGE

MARCONI TF.1342. Range 0.002 pF. to 1,111 pF. Accuracy 0.2%. Three terminal transformer ratio arm bridge allows "in situ" measurements. Internal oscillator frequency 1,000 c/s. 12 x 17 x 8½ in. Weight 15½ lbs. A.C. mains 200 to 250 and 100 to 150 v. 40-100 c/s. With leads and handbook. **ABSOLUTELY BRAND NEW.** List Price £120. Our Price **£45.**

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1
THE VALVE SPECIALISTS Telephone PRIMROSE 9090
47 NORFOLK ROAD, LITTLEHAMPTON, SUSSEX. Littlehampton 2043

Please forward all mail orders to Littlehampton
ALL GOODS LISTED BELOW IN STOCK

0A2	5/-	12BA6	5/-	F0034	29/6	N78	38/4	UP42	9/-	GET102	4/0
0A2T	6/-	12BE6	5/3	F0040	9/6	N339	25/-	UP90	6/9	GET103	4/-
1A70T	7/8	12BH7	6/-	F0041	4/-	PAD308	7/8	UP95	7/3	GET113	4/-
1C5	4/8	12C1	17/8	F0055	4/6	PC390	9/8	UP96	9/-	GET116	7/8
1L13GT	7/-	12CT0T	6/8	F0063	4/6	PC388	6/6	UP99	5/6	GET118	4/8
1L4	2/6	12K5	8/-	F0084	6/-	PC393	6/9	UL41	9/-	GET119	2/6
1N5GT	7/9	12KT0T	3/6	F0095	5/-	PC97	5/9	UL46	9/6	GET173	8/6
1R4	4/9	12K90T	7/9	F0098	7/-	PC900	8/-	UL84	6/-	GET587	8/6
1T4	2/8	12Q70T	3/8	F0099	9/-	PC984	6/-	UM60	5/-	GET783	4/-
1U4	5/6	12R070T	9/-	F0207	19/9	PC985	6/9	UC1C	6/6	GET867	4/8
1U5	5/3	18A05	6/-	F0290	16/8	PC989	8/9	UD8	18/8	GET889	4/6
2D21	5/6	20D1	13/-	F0292	6/9	PC990	11/-	UY1N	10/3	GET890	4/8
2A4	3/6	20D1	20/5	F0296	8/6	PC189	6/3	UY21	9/-	GET896	4/6
2A5	8/-	20P2	11/6	F0298	12/6	PC780	7/-	UY41	6.6	GET897	4/6
2Q4	5/3	20L1	15/6	F0299	12/6	PC782	6/-	UY95	5/8	GET908	4/6
2Q45T	6/8	20P1	8/6	F0321	9/6	PC784	8/7	UY94	14/8	MAT100	7/9
2R4	4/8	20P3	17/-	F0345	6/-	PC896	8/7	VR105	5/8	MAT101	8/8
3R41Y	8/9	20P4	17/8	F0342	2/9	PC891	8/6	VR150	5/-	MAT120	7/9
3U40	4/9	20P5	17/-	F0381	5/-	PC892	9/8	W76	3/6	MAT121	8/6
3V40	8/-	20Z01	8/6	F0383	7/-	PC905	9/6	W81M	8/-	OA5	1/9
3V3GT	5/-	30C15	15/-	F0384	6/6	PC909	11/6	W107	10/8	OA10	8/6
3Z3	3/6	30C17	13/-	F0386	6/6	PC924	9/-	W129	10/7	OA47	2/-
3Z4C	7/6	30C18	9/8	F0382	6/6	PC932	6/9	X61	8/-	QA70	3/-
6A07	5/9	30P5	11/6	F0383	9/-	PC935	10/3	X61met12	10/-	QA73	3/-
6AK5	4/9	30P11	15/-	F0384	12/-	PC944	8/3	X63	5.6	QA79	1/9
6A34	16/8	30P12	15/-	F0385	11/-	PC945	8/3	X66	7/8	QA81	1/9
6A43	4/9	30P13	6/-	F0386	7/9	PC947	8/3	X73M	7/9	QA82	4/9
6A79	3/9	30P14	12/6	F0387	12/6	PC948	7/9	X83	5/-	QA84	4/6
6A9	5/8	30L15	14/-	F0389	23/9	PC949	10/6	X84	5/-	QA90	2/6
6AV6	5/-	30L17	13/-	F0392	6/6	PC983	19/6	X91	1/9	QA91	1/9
6R46	4/8	30P4	11/8	F0394	3/-	PC984	9/6	X92	1/9	QA95	1/9
6R49	8/8	30P4M1	6/-	F0396	7/-	PC985	13/6	X93	1/9	QA96	1/9
6R16	6/6	30P4M2	13/-	F0397	5/-	PC986	10/6	X94	1/9	QA99	1/9
6R16	6/6	30P12	11/-	F040	8/9	PC987	9/9	AA129	3/-	QA202	2/-
6R16	6/6	30P19	11/-	F041	9/-	PC988	19/9	2N404	6/-	QA210	9/6
6R17	9/-	30P15	15/-	F042	3/6	PC989	17/8	AA129	3/-	QA211	13/6
6R18	8/-	30P13	15/-	F043	2/6	PC990	2/6	AA129	3/6	QA220012	1/9
6R17	8/6	30P14	15/-	F044	6/-	PC991	6/-	AA131	5/-	QA220110	6/8
6R18	7/-	30P15	15/-	F045	4/9	PC992	6/-	AA132	2/-	QA2202	9/-
6R18	7/-	30P16	15/-	F046	4/9	PC993	6/-	AA133	2/-	QA2203	9/6
6R18	7/-	30P17	15/-	F047	4/9	PC994	6/-	AA134	2/-	QA2204	9/6
6R18	7/-	30P18	15/-	F048	4/9	PC995	6/-	AA135	2/-	QA2205	9/6
6R18	7/-	30P19	15/-	F049	4/9	PC996	6/-	AA136	2/-	QA2206	9/6
6R18	7/-	30P20	15/-	F050	4/9	PC997	6/-	AA137	2/-	QA2207	9/6
6R18	7/-	30P21	15/-	F051	4/9	PC998	6/-	AA138	2/-	QA2208	9/6
6R18	7/-	30P22	15/-	F052	4/9	PC999	6/-	AA139	2/-	QA2209	9/6
6R18	7/-	30P23	15/-	F053	4/9	PC1000	6/-	AA140	2/-	QA2210	9/6
6R18	7/-	30P24	15/-	F054	4/9	PC1001	6/-	AA141	2/-	QA2211	9/6
6R18	7/-	30P25	15/-	F055	4/9	PC1002	6/-	AA142	2/-	QA2212	9/6
6R18	7/-	30P26	15/-	F056	4/9	PC1003	6/-	AA143	2/-	QA2213	9/6
6R18	7/-	30P27	15/-	F057	4/9	PC1004	6/-	AA144	2/-	QA2214	9/6
6R18	7/-	30P28	15/-	F058	4/9	PC1005	6/-	AA145	2/-	QA2215	9/6
6R18	7/-	30P29	15/-	F059	4/9	PC1006	6/-	AA146	2/-	QA2216	9/6
6R18	7/-	30P30	15/-	F060	4/9	PC1007	6/-	AA147	2/-	QA2217	9/6
6R18	7/-	30P31	15/-	F061	4/9	PC1008	6/-	AA148	2/-	QA2218	9/6
6R18	7/-	30P32	15/-	F062	4/9	PC1009	6/-	AA149	2/-	QA2219	9/6
6R18	7/-	30P33	15/-	F063	4/9	PC1010	6/-	AA150	2/-	QA2220	9/6
6R18	7/-	30P34	15/-	F064	4/9	PC1011	6/-	AA151	2/-	QA2221	9/6
6R18	7/-	30P35	15/-	F065	4/9	PC1012	6/-	AA152	2/-	QA2222	9/6
6R18	7/-	30P36	15/-	F066	4/9	PC1013	6/-	AA153	2/-	QA2223	9/6
6R18	7/-	30P37	15/-	F067	4/9	PC1014	6/-	AA154	2/-	QA2224	9/6
6R18	7/-	30P38	15/-	F068	4/9	PC1015	6/-	AA155	2/-	QA2225	9/6
6R18	7/-	30P39	15/-	F069	4/9	PC1016	6/-	AA156	2/-	QA2226	9/6
6R18	7/-	30P40	15/-	F070	4/9	PC1017	6/-	AA157	2/-	QA2227	9/6
6R18	7/-	30P41	15/-	F071	4/9	PC1018	6/-	AA158	2/-	QA2228	9/6
6R18	7/-	30P42	15/-	F072	4/9	PC1019	6/-	AA159	2/-	QA2229	9/6
6R18	7/-	30P43	15/-	F073	4/9	PC1020	6/-	AA160	2/-	QA2230	9/6
6R18	7/-	30P44	15/-	F074	4/9	PC1021	6/-	AA161	2/-	QA2231	9/6
6R18	7/-	30P45	15/-	F075	4/9	PC1022	6/-	AA162	2/-	QA2232	9/6
6R18	7/-	30P46	15/-	F076	4/9	PC1023	6/-	AA163	2/-	QA2233	9/6
6R18	7/-	30P47	15/-	F077	4/9	PC1024	6/-	AA164	2/-	QA2234	9/6
6R18	7/-	30P48	15/-	F078	4/9	PC1025	6/-	AA165	2/-	QA2235	9/6
6R18	7/-	30P49	15/-	F079	4/9	PC1026	6/-	AA166	2/-	QA2236	9/6
6R18	7/-	30P50	15/-	F080	4/9	PC1027	6/-	AA167	2/-	QA2237	9/6
6R18	7/-	30P51	15/-	F081	4/9	PC1028	6/-	AA168	2/-	QA2238	9/6
6R18	7/-	30P52	15/-	F082	4/9	PC1029	6/-	AA169	2/-	QA2239	9/6
6R18	7/-	30P53	15/-	F083	4/9	PC1030	6/-	AA170	2/-	QA2240	9/6
6R18	7/-	30P54	15/-	F084	4/9	PC1031	6/-	AA171	2/-	QA2241	9/6
6R18	7/-	30P55	15/-	F085	4/9	PC1032	6/-	AA172	2/-	QA2242	9/6
6R18	7/-	30P56	15/-	F086	4/9	PC1033	6/-	AA173	2/-	QA2243	9/6
6R18	7/-	30P57	15/-	F087	4/9	PC1034	6/-	AA174	2/-	QA2244	9/6
6R18	7/-	30P58	15/-	F088	4/9	PC1035	6/-	AA175	2/-	QA2245	9/6
6R18	7/-	30P59	15/-	F089	4/9	PC1036	6/-	AA176	2/-	QA2246	9/6
6R18	7/-	30P60	15/-	F090	4/9	PC1037	6/-	AA177	2/-	QA2247	9/6
6R18	7/-	30P61	15/-	F091	4/9	PC1038	6/-	AA178	2/-	QA2248	9/6
6R18	7/-	30P62	15/-	F092	4/9	PC1039	6/-	AA179	2/-	QA2249	9/6
6R18	7/-	30P63	15/-	F093	4/9	PC1040	6/-	AA180	2/-	QA2250	9/6
6R18	7/-	30P64	15/-	F094	4/9	PC1041	6/-	AA181	2/-	QA2251	9/6
6R18	7/-	30P65	15/-	F095	4/9	PC1042	6/-	AA182	2/-	QA2252	9/6
6R18	7/-	30P66	15/-	F096	4/9	PC1043	6/-	AA183	2/-	QA2253	9/6
6R18	7/-	30P67	15/-	F097	4/9	PC1044	6/-	AA184	2/-	QA2254	9/6
6R18	7/-	30P68	15/-	F098	4/9	PC1045	6/-	AA185	2/-	QA2255	9/6
6R18	7/-	30P69	15/-	F099	4/9	PC1046	6/-	AA186	2/-	QA2256	9/6
6R18	7/-	30P70	15/-	F100	4/9	PC1047	6/-	AA187	2/-	QA2257	9/6
6R18	7/-	30P71	15/-	F101	4/9	PC1048	6/-	AA188	2/-	QA2258	9/6
6R18	7/-	30P72	15/-	F102	4/9	PC1049	6/-	AA189	2/-	QA2259	9/6
6R18	7/-	30P73	15/-	F103	4/9	PC1050	6/-	AA190	2/-	QA2260	9/6
6R18	7/-	30P74	15/-	F104	4/9	PC1051	6/-	AA191	2/-	QA2261	9/6
6R18	7/-	30P75	15/-	F105	4/9	PC1052	6/-	AA192	2/-	QA2262	9/6
6R18	7/-	30P76	15/-	F106	4/9	PC1053	6/-	AA193	2/-	QA2263	9/6
6R18	7/-	30P77	15/-	F107	4/9	PC1054	6/-	AA194	2/-	QA2264	9/6
6R18	7/-	30P78	15/-	F108	4/9	PC1055	6/-	AA195	2/-	QA2265	9/6
6R18	7/-	30P79	15/-	F109	4/9	PC1056	6/-	AA196	2/-	QA2266	9/6
6R18	7/-	30P80	15/-	F110	4/9	PC1057	6/-	AA197	2/-	QA2267	9/6
6R18	7/-	30P81	15/-	F111	4/9	PC1058	6/-	AA198	2/-	QA2268	9/6
6R18	7/-	30P82	15/-	F112	4/9	PC1059	6/-	AA199	2/-	QA2269	9/6
6R18	7/-	30P83	15/-	F113	4/9	PC1060	6/-	AA200	2/-	QA2270	9/6
6R18	7/-	30P84	15/-	F114	4/9	PC1061	6/-	AA201	2/-	QA2271	9/6
6R18	7/-	30P85	15/-	F115	4/9	PC1062	6/-	AA202	2/-	QA2272	9/6
6R18	7/-	30P86	15/-	F116	4/9	PC1063	6/-	AA203	2/-	QA2273	9/6
6R18	7/-	30P87	15/-	F117	4/9	PC1064	6/-	AA204	2/-	QA2274	9/6
6R18	7/-	30P88	15/-	F118	4/9	PC1065	6/-	AA205	2/-	QA2275	9/6
6R18	7/-	30P89	15/-	F119	4/9	PC1066	6/-	AA206	2/-	QA2276	9/6
6R18	7/-	30P90	15/-	F120	4/9	PC1067	6/-	AA207	2/-	QA2277	

LIND-AIR LTD (ELECTRONICS)

LONDON'S LEADING COMPONENT SHOPS


25 & 53 TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-580 4534/7679

Open 9-6 p.m. Monday to Saturday inclusive. Open Thursday until 7 p.m.

ALL POST ORDERS TO DEPT. WW 268, 25 TOTTENHAM CT. ROAD, LONDON, W.1

TRANSISTOR A.M. TUNER

ONLY **69/6**
P&P 2/6

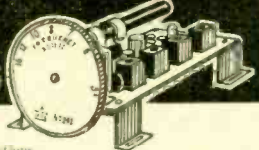

3 Transistor AM Tuner covering full medium wave. Size 4 1/2 in. x 2 1/2 in. Ready built. 9 v. battery operation. Complete with instructions.

SPECIAL OFFER OF GARRARD DECKS



Modernise your old radiogram with one of these latest brand new Garrard units.

Model 3000 with Sonotone 9TAHC Stereo Cartridge £8 19 6
 AT60 Mk. II less cartridge £10 19 6
 AT60 Mk. II less cartridge £12 19 6
 SP25 Mk. II less cartridge £10 19 6
 LAB80 Mk. II less cartridge £24 19 6
 Mono Cartridge 12/6 extra.
 Stereo Cartridge 19/6 extra.

TEAK FINISH PLINTHS with perspex cover 6 gns. (For LAB80 - 8 gns.). P. & P. 5/- Agents for Thorens, Dual, Colibring. Prices on request.

LINEAR AMPLIFIERS Latest A.C. Mains Models offering highest quality at modest cost.


LT86. All Transistor 12 watts Stereo. Inputs for Tuner, Gram., Mike. Separate Bass, Treble, Balance and Volume Controls. £15/15/-. Carr. 7/6. Teak case £3/10/- extra.

PTA15. All Transistor. 15 watts Mono. Inputs for Tuner, Gram., Mike, Guitar Bass, Treble and two volume controls. £15/15/-. Carr. 7/6. Teak case. £3/10/- extra.



LT45. 2 VALVE 6 watts Mono. Inputs for Tuner, Gram., Bass, Treble and Volume controls. £8/19/6. P. & P. 5/6. Metal cover 15/- extra. Full details sent on request.

MOTOR BARGAINS

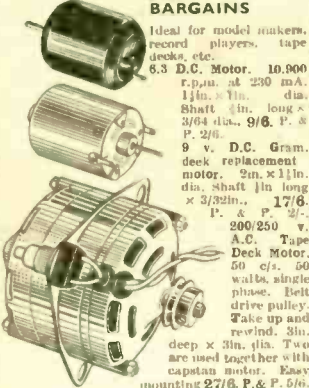

Ideal for model makers, record players, tape decks, etc.

6.3 D.C. Motor. 10.000 r.p.m. at 230 mA. 1 1/2 in. dia. Shaft 3/64 in. long x 3/64 dia. 9/6. P. & P. 2/6.

9 v. D.C. Gram. deck replacement motor. 2 in. x 1 1/2 in. dia. shaft 1/2 in. long x 3/32 in. 17/6. P. & P. 2/6.

200/250 v. A.C. Tape Deck Motor. 50 c/s. 50 watts, single phase. Belt drive pulley. Take up and rewind. 3 in. deep x 3 1/2 in. dia. Two are used together with capstan motor. Easy mounting 27/6. P. & P. 5/6.

EAGLE SUBSTITUTION BOXES

O.M.B. Capacitance ranges 0.001, .0010, .0022, .0047, .01, .022, .047, .1, .22, .50. With leads and clips. 21/-. P. & P. 2/6.

O.M.G. Two Resistance ranges. Low: 15 ohm 10 Kohm (1 watt resistors). High: 15 K ohm to 10 meg. ohm. (1/2 watt resistors). Selects 24 separate resistances. With leads and clips. 29/6. P. & P. 2/6.



AERIALS. TV/UHF/VHF/STEREO CRESTA Room Aerial Band 1/11/111. Cream finish. £49/-.

VEEMASTER Table Top VHF/UHF. Tunable Aerial. Chrome or grey. 70/-.

YAGAL. All Channel Table Top Aerial. BNC/12TV/VHF. 65/-.

HL355 LOFT AERIAL. HILO V + 5 for vertical. Band 1/111. With mounting arm and bracket. 49/-.

NEW MAJOR. 10-element BNC2 Aerial for loft or outdoor living. With roller bracket for up to 2 in. dia. mast. 42/6.

MULTIMETERS



TTC1001 (see illus.) 20,000 o.v. £319/8

C1000. 1,000 o.v. £22/2-

Caby N11 200-20,000 o.v. £8/10/-

Caby 340 4,000 o.v. £6/10/-


TMK900 30,000 o.v. £8/19/8

TTC Model 1030 50,000 o.v. £9/19/8

TTC Model 1031 100,000 o.v. £12/19/8

Also stockists of Avo. Nombres, Eagle etc. Test equipment. P.P. 3/6.


SELECTOR DRIVE

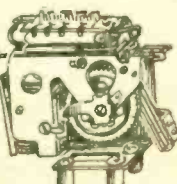

12/6

Numerous applications. Electro magnet and brass tooth wheel. A switch wiper and contacts are coupled to this and arranged to be on for 10 pulses and off for 15. An auxiliary contact is normally on but off 1 in every 25. Complete with suppressor, resistors, plus series contact for continuous operation. Ideal window displays, switching lamps, models, etc. 12 v. or 24 v. D.C. Brand new and boxed. 12/6. P. & P. 2/6. Many more similar items available.

TRANSISTOR F.M. TUNER

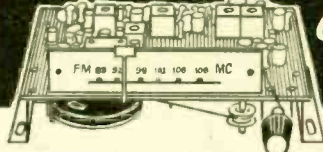

ONLY **£6-7-6**
P&P 4/6

6 Transistor, FM tuner Frequency range 88-108 Mc/s. Size 6 x 4 x 2 1/2 in. Ready built for use with most amplifiers. 9 v. battery operation. Complete with instructions. ONLY FROM LIND-AIR!

For the Stereo enthusiast Multiplex Adaptor for Stereo Radio reception. £5/19/6 extra.

SINCLAIR PRODUCTS




MICROMATIC RADIO. KIT ONLY 49/6. P. & P. 2/6. MICROMATIC RADIO BUILT. ONLY 59/6. P. & P. 2/6.

MICRO FM. KIT—£5/19/6 complete. P. & P. 2/6. Z.19 HI-FI AMP and PRE-AMP £4/9/6. P. & P. 2/6. STEREO 25 Control Unit. £9/19/6. P. & P. 2/6. PZ3. Mains Power Supply Unit £3/19/6. P. & P. 2/6.

MAGNAVOX-COLLARO 363 TAPE DECKS

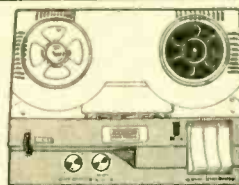The very latest 3-speed model—1 1/2, 3 1/2, 7 1/2 i.p.s. available with either 2 track or 4 track head. Features include: Pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor; interlocking keys. Size of top plate 13 1/2 x 11 x 3 1/2 in. deep below unit plate. For 200/250 v. A.C. mains 50 c.p.s. operation. New unused and fully guaranteed.



2 track model. £10/10/0
4 track model. £13/9/6

Carriage and Packing 7/6.

MARTIN TAPE PREAMPLIFIERS

FOR USE WITH ABOVE TAPE DECKS. 2 track model. £14/19/6; 4 track model. £15/19/6. Carriage and packing 7/6

2-3 WATT AMPLIFIER

An ideal basis for building your own portable record player. Just add speaker and turntable and you will have an above-average model for a mere fraction of the cost—2-3 watt printed circuit, with control panel on flying lead. On, OFF, TONE CONTROL AND VOLUME. Colourful schematic. Brimar valves: E280. ECL82 and composite installation booklet. Price £3/17/6 P. & P. 3/6.



PROFESSIONAL ELECTRIC INSTANT HEAT SOLDER GUN

Ideal for model makers, home repairs, electronics, radio, TV, etc. Unique features include interchangeable tips, extension barrel, comfortable grip with trigger control. "U" shaped 3 1/2 in. bit to minimise wear. Light beam is automatically directed on end of bit when ON/OFF trigger is in use. 85 watt element with special ventilation. Complete with 2-pin, 5 amp, plug 230-250 volts. Spares available. 49/6 plus 2/6 P.P.



AUTO TRANSFORMERS

Input 0-200, 220, 600 w.	£6 9 6
24 v. Output 110 v. 1,000 w.	£9 9 0
50 w.	£1 7 6
75 w.	£1 17 0
100 w.	£2 5 0
150 w.	£2 15 0
200 w.	£3 5 0
300 w.	£4 5 0
400 w.	£4 19 6
500 w.	£5 9 6

plus 2/6 P.P.


MAINS TRANSFORMERS

Input 200-250 v. 50 c/s.	
24 v. 3 amp.	£2 12 6
24 v. 5 amp.	£3 15 0
24 v. 7 amp.	£5 5 0
24 v. 12 amp.	£8 15 0

Post extra. Mains and Output Transformer Lists available on request.

We have a complete range of new and old types of Valves, Transistors and Diodes. Lists available on application.

ADMIRALTY B.40 RECEIVERS

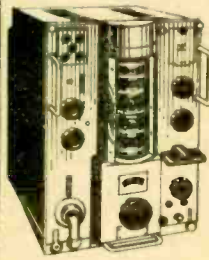

Just released by Ministry. High quality 16 valve receiver manufactured by Murphy. Coverage in 5 bands 650 Kcfs-30 Mc/s. 1/F. 500 Kcfs. Incorporates 2 R.F. and 3 I.F. stages. Impedance filter, noise limiter, crystal controlled B.F.O. calibrator, I.F. output, etc. Built-in speaker, output for phones. Operation 150/240 volt A.C. Size 19 1/2 in. x 13 1/2 in. x 10 1/2 in. Weight 11 1/2 lbs. Offered in good working condition. £28/10/-, carr. 30/- With circuit diagram. Also available B41 L.F. version of above. 15 Kcfs-700 Kcfs. £17/10/-, carr. 30/-.

COLLINS TCS TRANSMITTERS



Frequency range 1.5-12 Mc/s. in 3 bands. Employ 7 valves. V.F.O. or provision for Ntag, incorporates plate and aerial-current metres. Require ext. P.S.U. Offered in excellent condition. £8/10/6. carr. 10/-.

TWO-WAY RADIOS

SUPERB QUALITY, BRAND NEW & GUARANTEED

- 3 TRANSISTORS £6/15/- PAIR.
- 4 TRANSISTORS £6/10/6 PAIR.
- 3 TRANSISTORS £7/10/- PAIR.
- 6 TRANSISTOR £8/12/6
- 6 TRANSISTOR DELUXE PAIR.
- LAFAYETTE £12/10/- PAIR. POST EXTRA.
- 10 TRANSISTOR £22/10/- PAIR.
- 13 TRANSISTOR 500 MW 2-channel 30 Gns. PAIR.
- 30 TRANSISTOR 1 WATT 2-channel £35 PAIR.



MARCONI TEST EQUIPMENT

EX-MILITARY RECONDITIONED
 TF 1446 STANDARD SIGNAL GENERATORS, 85 Kcfs-25 Mc/s. £25. carr. 30/-.
 TF 3200. "Q" METER. BRAND NEW. COMPLETE WITH ALL ACCESSORIES. £75. carr. 30/-.
 T.F. 185A. BEAT FREQUENCY OSCILLATOR. 0-40 kcfs. 200/250v. A.C. £20. Carr. 30/-.
 All above offered in excellent condition fully tested and checked.



POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brass wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. 1in. dia. shafts. Bulk quantities available.
 25 WATT. 10/25/50/100/250/500/1000/1500/2000 or 5000 ohms. 14/6. P. & P. 1/6.
 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. 21/6. P. & P. 1/6.
 100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. 27/6. P. & P. 1/6.




SOLATRON CD71S.2 DOUBLE BEAM OSCILSCOPE

An extremely high quality oscilloscope originally costing £400. Switched beam. Identical Y1, Y2 amplifiers D.C. to 9 Mc/s. Sensitivity 3mV/cm to 100 V/cm. Time base 10 μsec. to X amplifier D.C. to 2.5 Mc/s. Z Modulation. 110/200/250v. A.C. Supplied in good working order. £65. carriage £2, or available as received from Ministry un-serviced £50. Carriage £2. (Handbook £2 extra.)

10 m/sec. Calibrator. X amplifier D.C. to 2.5 Mc/s. Z Modulation. 110/200/250v. A.C. Supplied in good working order. £65. carriage £2, or available as received from Ministry un-serviced £50. Carriage £2. (Handbook £2 extra.)

SOLATRON MONITOR OSCILSCOPE TYPE 101.

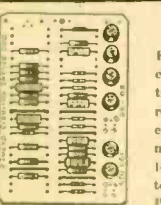An extremely high quality oscilloscope with time base of 10 μsec. to 20 msec. Internal Y amplifier. Separate mains power supply 200/250/270. Supplied in excellent condition with cables, probe, etc., as received from Ministry £8/19/6. Carriage 30/-.



PRINTED CIRCUITS

Five assorted printed circuit boards with transistors, diodes, resistors, condensers, etc. Guaranteed minimum 20 transistors. Ideal for experimenters. 5 Boards for 10/- P. & P. 2/-.

MODEL ZQM TRANSISTOR CHECKER

It has the fullest capacity for checking on A B and Cco. Equally adjustable for checking diodes, etc. Spec.: A: 0.7-0.99.67. B: 5-200. Cco: 0-50 microamps. 0.5mA. Resistance for diode 200 Ω — 1 MΩ. Supplied complete with instructions, battery and leads. £5/19/6. P. & P. 2/6.



TE-65 VALVE VOLTMETER

High quality instrument with 25 ranges. D.C. volts 1.5-1500 v. A.C. volts 1.5-1500 v. Resistance up to 1,000 megohms. 220/240 v. A.C. operation. Complete with probe and instructions £15. P. & P. 6/-. Additional Probes available: R.P. 35/-; H.V. 42/6.



T.E.40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: .01/.033/.1/3/13/30/100/300 v. R.M.S. 4eps. 1.3 Mc/s. Decibels—40 to +50 dB. Supplied brand new complete with leads and instructions. Operation 230v. A.C. £17/10/-. Carr. 5/-.



UNR-30 4 BAND COMMUNICATION RECEIVER

Covering 550 Kcfs-30 Mc/s. Incorporates variable BFO for CW/SSB reception. Built in speaker and phone jack. Metal cabinet. Operation 220/240v. A.C. Supplied brand new, guaranteed with instructions. £12/10/-, Carr. 7/6.




LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER



19 transistors, 8 diodes. IHF music power 30 watts at 8 ohms. Response 30-20,000 x 2 dB at 1 w. Distortion 1% or less. Inputs 3 mV and 250 mV. Output 3-16 ohms. Separate L. and R. volume controls. Treble and bass controls. Stereo phone jack. Brushed aluminium, gold anodized extruded front panel with complementary metal case. Size 10 1/2 in. x 8 1/2 in. x 7 1/2 in. Operation 110/230 volt A.C. £25. Carr. 7/6.

GARRARD DECKS

- 8 R P 12 player, mono or stereo £4 4 0
 - 1000 changer, mono or stereo £5 15 6
 - 2000 changer, mono or stereo £6 19 6
 - 450 Mono or stereo £7 17 6
 - 3000 changer, mono or stereo £8 19 6
 - 3000 Sonotone stereo £8 19 6
 - A78 Mk. II mono or stereo £8 19 6
 - A70 Mk. II less cartridge £12 12 0
 - A79 Mk. II Sonotone stereo £24 0 0
 - LAB80 II, changer, less cart. £27 0 0
 - 401 Transcription Deck £27 0 0
- All plus 5/- P. & P.

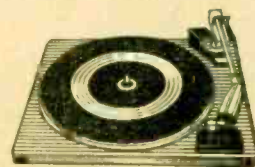

AVOMETER

In excellent condition, fully tested and checked. Complete with prods, leads and instructions. Model 47A £9/19/6 Model 7 £13/10/0 Model 8 £18/0/0 Model 9 £20/0/0 P. & P. 7/6 each.



SINCLAIR EQUIPMENT

- Z12. 12 watt amplifier 80/6
- P24. Power Supply 90/6
- Unit STEREO 25. 90/6
- amplifier £20/10/6
- Q.14 Speakers £8/19/6
- Micromatic Radio 48/6
- R11 48/6
- Micro P21 Radio 58/6
- R11 25/19/6

ALL POST PAID.

SPECIAL OFFER
 2 Z12 amps. P24 Power Supply, Stereo 25. Pre-amplifier £22



Variable Voltage TRANSFORMERS

Brand new, guaranteed and carriage paid. High quality construction. Input 230 v. 50-60 cycles. Output full variable from 0-250 volts. Bulk quantities available.
 1 amp. — £4/10/- 2.5 amp. — £5/17/6 5 amp. — £8 8 amp. — £13/10/-
 10 amp. — £17 12 amp. — £19/10/- 20 amp. — £32/10/-



SILICON RECTIFIERS

- 200 v. P.I.V. 200mA 2/6
 - 200 v. P.I.V. 6 amp. 5/6
 - 400 v. P.I.V. 3 amp. 7/6
 - 1,000 v. P.I.V. 5 amp. 7/6
 - 400 v. P.I.V. 6 amp. 5/6
 - 400 v. P.I.V. 8 amp. 7/6
 - 1,000 v. P.I.V. 600 mA. 6/6
 - 800 v. P.I.V. 600mA. 5/6
 - 70 v. P.I.V. 5 amp. 3/6
 - 400 v. P.I.V. 500mA. 5/6
 - 70 v. P.I.V. 1 amp. 3/6
 - 150 v. P.I.V. 150mA. 1/-
 - 150 v. P.I.V. 25 amps. 10/-
 - 700 v. P.I.V. 100 amp. 35/-
- Discount for quantities. Post extra.

THYRISTORS SILICON CONTROL RECTIFIERS

- 400 P.I.V. 3 amp. 7/8
- 100 P.I.V. 5 amp. 13/8
- 200 P.I.V. 5 amp. 15/6
- 400 P.I.V. 5 amp. 17/6

S.T.C. 1 WATT ZENER DIODES

BRAND NEW, LIST 17/6 each. Available 2.4/2.7/3.3/3.9/4.3/13/16/20/30/33 v. 5/- each type. P. & P. extra.

AMERICAN RECORDING TAPES

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.
 3in. 225ft. L.P. Acetate 4/-
 3in. 600ft. T.P. Mylar 10/-
 3in. 600ft. Std. plastic 8/6
 6in. 900ft. L.P. acetate 10/-
 6in. 1,200ft. D.P. Mylar 15/-
 6in. 1,800ft. T.P. Mylar 35/-
 6in. 1,200ft. L.P. acetate 12/6
 6in. 1,800ft. D.P. Mylar 22/6
 6in. 2,400ft. T.P. Mylar 45/-
 7in. 1,200ft. Std. acetate 12/6
 7in. 1,800ft. L.P. acetate 15/-
 7in. 1,800ft. L.P. Mylar 20/-
 7in. 2,400ft. D.P. Mylar 25/-
 7in. 3,600ft. T.P. Mylar 58/6

Postage 2/- Over £3 post paid.



RECORDING HEADS

Reuter 1-track. As fitted to Collaro Mk. IV and Studio Decks. High imp. record play back low imp. erase. Brand new. 19/6 pair. MINIFLUX 1-track set of 3. 29/6. Post extra.

MAGNAVOX 363 TAPE DECKS

3 speed. 1 1/2-7 1/2 ips. Carr. paid. 2-track £10/10/- 4-track £13/10/- 2-track Stereo £13/10/-.

R.C.A. AR88 SPEAKERS

Min. 3 ohm speakers in metal case. Black crackle finish to match our 88 Receivers. Available Brand New and Boxed with leads. 50/6. carr. 7/6.

★ TRANSISTORISED FM TUNER ★

1 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in. x 4in. x 2 1/2 in. 3 I.F. stages. 3 Double tuned discriminator, ample output to feed most amplifiers. Operates on 9 volt battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £8/10/- P. & P. 2/6.

STEREO MULTIPLEX ADAPTORS 5 Gns.

F.M. WIRELESS MICROPHONE

84-104 Mc/s. Transistorised Operates on 9 v. battery. Complete with additional secret tie-clip microphone. List £12/10/-. ONLY £8/15/-. P. & P. 2/6.



TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000s of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £5/19/6 pair. P. & P. 3/6.




G. W. SMITH & Co. (Radio) Ltd.

3-34, Lisle St., W.C.2. ALSO SEE OPPOSITE PAGE

SEW PANEL METERS

Send S.A.E. for full lists. Other ranges available. Please include postage. Special quotations for quantities.

CLEAR PLASTIC METERS

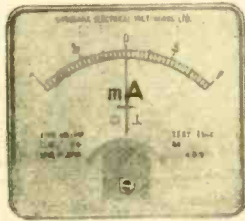

Type MR.52P. 2 1/4 in. square fronts.

50µA	57/6	10V. D.C.	32/6
50-0-50µA	57/6	20V. D.C.	32/6
100µA	47/6	50V. D.C.	32/6
100-0-100µA	47/6	300V. D.C.	32/6
500µA	37/6	15V. A.C.	32/6
1 mA	32/6	300V. A.C.	32/6
5 mA	32/6	8 Meter 1mA	32/6
10 mA	32/6	VU Meter	45/6
50 mA	32/6	1 amp. A.C.*	32/6
100 mA	32/6	5 amp. A.C.*	32/6
500 mA	32/6	10 amp. A.C.*	32/6
1 amp.	32/6	20 amp. A.C.*	32/6
5 amp.	32/6	30 amp. A.C.*	32/6

Type MR.38P. 1 21/32 in. square fronts.

50µA	32/6	6 amp.	22/6
50-0-50µA	29/6	3V. D.C.	22/6
100µA	29/6	10V. D.C.	22/6
100-0-100µA	27/6	20V. D.C.	22/6
200µA	27/6	50V. D.C.	22/6
500µA	25/6	150V. D.C.	22/6
500-0-500µA	22/6	300V. D.C.	22/6
1 mA	22/6	150V. A.C.	22/6
1.01 mA	22/6	40V. A.C.	22/6
5 mA	22/6	150V. A.C.	22/6
10 mA	22/6	300V. A.C.	22/6
50 mA	22/6	600V. A.C.	22/6
100 mA	22/6	8 meter 1 mA	22/6
500 mA	22/6	VU meter	35/6
1 amp.	22/6		

Type MR.85P. 4 1/4 in. x 4 1/4 in. fronts.

50µA	69/6	15 amp.	45/6
50-0-50µA	69/6	30 amp.	45/6
100µA	59/6	10V. D.C.	45/6
100-0-100µA	59/6	20V. D.C.	45/6
200µA	55/6	50V. D.C.	45/6
500µA	49/6	150V. D.C.	45/6
500-0-500µA	49/6	300V. D.C.	45/6
1 mA	45/6	15V. A.C.	45/6
1.01 mA	45/6	300V. A.C.	45/6
5 mA	45/6	20 amp. A.C.*	45/6
10 mA	45/6	30 amp. A.C.*	45/6
50 mA	45/6		
100 mA	45/6		
500 mA	45/6		
1 amp.	45/6		
5 amp.	45/6		


Type MR.45P. 2 in. square fronts.

50µA	39/6	20V. D.C.	25/6
50-0-50µA	35/6	50V. D.C.	25/6
100µA	35/6	300V. D.C.	25/6
100-0-100µA	32/6	15V. A.C.	25/6
200µA	27/6	300V. A.C.	25/6
500µA	25/6	8 meter 1mA	35/6
1 mA	25/6	VU meter	39/6
5 mA	25/6	1 amp. A.C.*	25/6
10 mA	25/6	5 amp. A.C.*	25/6
50 mA	25/6	10 amp. A.C.*	25/6
100 mA	25/6	20 amp. A.C.*	25/6
1 amp.	25/6	30 amp. A.C.*	25/6
5 amp.	25/6	10V. D.C.	35/6
10V. D.C.	25/6		

Type MR.65P. 3 1/4 in. x 3 1/4 in. fronts.

50µA	59/6	20V. D.C.	35/6
50-0-50µA	59/6	50V. D.C.	35/6
100µA	49/6	150V. D.C.	35/6
100-0-100µA	49/6	300V. D.C.	35/6
500µA	39/6	15V. A.C.	35/6
1 mA	35/6	300V. A.C.	35/6
1.01 mA	35/6	500V. A.C.	35/6
5 mA	35/6	VU meter	59/6
10 mA	35/6	1 amp. A.C.*	35/6
50 mA	35/6	5 amp. A.C.*	35/6
100 mA	35/6	10 amp. A.C.*	35/6
500 mA	35/6	20 amp. A.C.*	35/6
1 amp.	35/6	30 amp. A.C.*	35/6
5 amp.	35/6		
10 amp.	35/6		
20 amp. A.C.*	35/6		
30 amp. A.C.*	35/6		

BAKELITE PANEL METERS

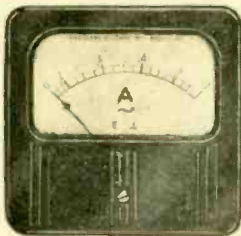

*Moving Iron, all other moving coil.

Type MR.65. 3 1/4 in. square fronts.

25µA	65/6	50 amp.	29/6
50µA	42/6	5V. D.C.	29/6
50-0-50µA	42/6	10V. D.C.	29/6
100µA	39/6	20V. D.C.	29/6
100-0-100µA	39/6	50V. D.C.	29/6
500µA	35/6	150V. D.C.	29/6
500-0-500µA	35/6	300V. D.C.	29/6
1 mA	29/6	30V. A.C.*	29/6
1.01 mA	29/6	50V. A.C.*	29/6
5 mA	29/6	150V. A.C.*	29/6
10 mA	29/6	300V. A.C.*	29/6
50 mA	29/6	1 amp. A.C.*	29/6
100 mA	29/6	5 amp. A.C.*	29/6
500 mA	29/6	10 amp. A.C.*	29/6
1 amp.	29/6	20 amp. A.C.*	29/6
5 amp.	29/6	30 amp. A.C.*	29/6
15 amp.	29/6	10V. D.C.	49/6
30 amp.	29/6	VU meter	49/6

NEW RANGE OF "SEW" EDGWISE METERS



MODEL PE 70. Dimensions 3 1/2 in. x 1 1/2 in. x 2 1/4 in. deep overall. Available as follows:

50 microamp	52/6	500 microamp	42/6
50-0-50 microamp	49/6	1 milliamp	39/6
100 microamp	49/6	300 V.A.C.	39/6
100-0-100 microamp	45/6	VU meter	55/6
200 microamp	45/6	Post extra.	

LA FAYETTE HI-FI STEREO HEAD TE-20RF SIGNAL GENERATOR PHONES



- * Air Cushioned headband
- * Soft rubber ear pads
- * Frequency response. 25 to 15,000 cycles. * High sensitivity. Impedance 8 ohms per phone. Supplied complete with all cables, wires, overhead junction box and 3-connection plug. 79/6. P. & P. 2/6.



Accurate wide range signal generator covering 120 kc/s-200 Mc/s. on 6 bands. Directly calibrated. Variable R.F. attenuator Operation 200/240 v. A.C. Brand new with instructions £12/10/- P. & P. 7/6. S.A.E. for details.




CATALOGUE

- * ELECTRONIC COMPONENTS
- * TEST EQUIPMENT
- * COMMUNICATION EQUIPMENT
- * HI-FI EQUIPMENT

We are proud to introduce our first comprehensive catalogue of Electronic Components and Equipment. Over 150 pages, fully illustrated, listing thousands of items, many at bargain prices. Free discount coupons with every catalogue. Everyone in electronics should have a copy.

Send today
5/- P&P

AVO CT.38 ELECTRONIC MULTIMETERS

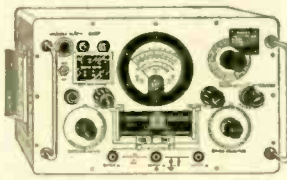

High quality 97 range instrument which measures A.C. and D.C. Voltage Current, Resistance and Power output. Ranges D.C. volts 250mV-10,000 v. (10 meg-110 megΩ input). D.C. current 10µA-25 amps. Ohms: 0-1,000 megΩ. A.C. volts 100 mV-.250 v. (with R.F. measuring head up to 300 Mc/s.). A.C. current 10µA-25 amps. Power output 50 microwatts-5 watts. Operation 0/110/200/250 v. C. Supplied in perfect condition complete with circuit, lead and R.F. probe £25. Carr. 15/-. AVO CALIBRATION TEST UNIT TYPE CT.155. For use with CT.38 Multimeter. Gives 7 standard voltages 250 mV/1 v/ 2.5 v./10/25/100 v. A.C. and 250 millivolts D.C. from internal standard cell. Operation 0/110/200/250 v. A.C. Brand new £7/10/-. P. & P. 10/6.

MULTIMETERS for EVERY purpose!



NEW MODEL 500, 30,000 O.P.V. with overload protection, mirror scale. 0 / .5 / 2.5 / 10 / 25 / 100 / 250/500/1,000 v. D.C. 0/2.5/10 / 25 / 100 / 250 / 500 / 1,000 v. A.C. 0/50µA/15/50/100 mA. 12 amp. D.C. 0/80/80K. Meg./80. MEG. £8/17/6. Post paid.



MODEL TE.80, 20,000 O.P.V. 0/10/50/100/500/1,000 v. A.C. 0/5/25/50/250/500/1,000 v. D.C. 0-50µA 5/50/500mA. 0/6/80K/600 K/6 meg. £4/17/6. P.F. 3/-

TE-900 20,000Ω/VOLT GIANT MULTIMETER 6 1/2 in. full view meter. 2 colour scale. 0/2.5/10/ 250/1,000/5,000 v. A.C. 0 / 2.5 / 12.5 / 10 / 50 / 250/1,000/5,000 v. D.C. 0/50µA / 1 / 10 / 100 / 500 mA / 10 amp. D.C. 0/2K/200K/20. MEG. OHM. £12/19/6. P. & P. 5/-



MODEL TE-70, 30,000 O.P.V. 0/2/15/50/300/ 600/1,200 v. D.C. 0/6/30/ 125/500/1,200 v. A.C. 0/30µA/3/30/300 mA. 0/16K/160K/1.6M/16 Meg. Ω. £5/10/-. P. & P. 3/-



MANY OTHER MODELS AVAILABLE FROM AS LOW AS 39/6.

NEW LAFAYETTE HA700 AM/CW/SSB AMATEUR COMMUNICATION RECEIVER

8 valves, 5 bands incorporating 2 MECHANICAL FILTERS for exceptional selectivity and sensitivity. Frequency coverage on 5 bands 150-400 Kc/s., 550-1,800 Kc/s., 1.6-4.0 Mc/s., 4.8-14.5 Mc/s., 10.5-30 Mc/s. Circuit incorporates R.F. stage, aerial trimmer, noise limiter, B.F.O. product detector, electrical bandspread, 8 meter, slide rule dial. Output for phones, low to 2K Ω or speaker 4 or 8 ohms. Operation 220/240 volt A.C. Size 7 1/2 in. x 15 in. x 10 in. Supplied brand new and guaranteed with handbook. 36 GNS. Carr. 10/-. S.A.E. for leaflet.



LAFAYETTE MODEL HA-500 SSB AM/CW 80 THROUGH 6 METRE RECEIVER



New outstanding Ham Bands only receiver covering the 80/40/20/15/10/6 metre bands. Incorporates 10 valves, product detector, two mechanical filters, 8 Meter, dual conversion on all bands, crystal calibrator, B.F.O. noise limiter, aerial trimmer, 1 P.S., 2,500 Mc/s. and 55 Kc/s. Output 8 ohms and 500 ohms. Operations 220/240 volt A.C. Supplied brand new and guaranteed with handbook 42 Gns. Carr. 10/-. 100 Kc/s. crystal. 35/-

G.W. SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

OPEN 9 a.m. to 6 p.m. every day Monday to Saturday. Trade supplied.

TRANSISTOR STEREO 8 + 8



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work, Cr-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief Specification: Freq. response ± 3 dB, 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -10dB. Negative feedback 18dB. over main amp. Power requirements at 20V. at 8 amp.

PRICES:
 Amplifier Kit £9 10 0. P. & P. 4/6.
 Power Pack Kit £2 10 0. P. & P. 4/-.
 Cabinet (as illus.) £2 10 0. P. & P. 5/6.
 (Special Offer—£14/10/0, post free if all above ordered at same time.)
 Circuit diagram, construction details and parts list (free with kit) 1/6 (S.A.E.).


HSL "FOUR" AMPLIFIER KIT
 3-VALVE + WATT USING ECC83, 6L4, EZ90 VALVES for A.C. mains 200/240 v. ★ Heavy duty double-wound mains transformer with electrostatic screen. ★ Separate bass, treble and volume controls, giving fully variable boost and cut, with minimum insertion loss. ★ Heavy negative feedback loop over 2 stages ensure high output at excellent quality with very low distortion factor. ★ Suitable for use with guitar, microphone or record player. ★ Provision for remote mounting of controls or direct on chassis. ★ All this builds on to a chassis size only 7 1/4 in. wide x 4 in. deep. Overall height 4 1/2 in. ★ All components and valves are brand new. ★ Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ★ Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder, etc. (No extras to buy). **PRICE 79/6.** P. & P. 6/-. Comprehensive circuit diagram, practical layout and parts list 2/6 (free with kit).

VIBRATORS. Large selection of 2, 4, 6, 12, and 32 volt. Non sync. 8/6. Sync. 10/-. P. & P. 1/6 per vibrator. S.A.E. with all enquiries.

S.T.C. SILICON AVALANCHE HALF-WAVE RECTIFIERS. Type RAB, 508 AF, 6 amps., 900 P.V.V. 1 1/2 in. long x 1/2 in. dia. approx. List 60/-. OUR PRICE 8/6. Post free.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished mono-audio amplifier with an output of 14 watts from 3 EL84s in push-pull Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shielded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up: 2 EL84s, ECC83, EF80, and EZ90 rectifier. Simple instruction booklet 1/0 (Free with parts). All parts sold separately. **ONLY £7/9/6.** P. & P. 8/6. Also available ready built and tested complete with standard input sockets. **£9/5/-.** P. & P. 8/6.

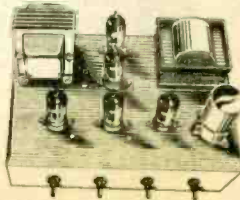

3-VALVE AUDIO AMPLIFIER MODEL HA34

Designed for Hi-Fi reproduction of records. A.C. mains operation. Ready built on plated heavy metal chassis, size 7 1/4 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83, 6L4, EZ90 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate bass, treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, etc., wired and tested for only **£4/5/-.** P. & P. 6/-.
BRAND NEW 3 OHM LOUSPEAKERS
 5in. 12/6; 8in. 15/-; 8in. 22/6; 10in. 27/6; 7 x 4 in. 16/-; 10 x 4 in. 27/6; P.M.L. 8 x 3 1/2 in. with high flux magnet 21/-; E.31. 1 1/2 x 3 1/2 in. with high flux ceramic magnet 42/- (10 ohm 45/-). P. & P. 5in. 2/-; 6in. 2/6; 8in. 2/6; 10 and 12in. 3/6 per spkr.
BRAND NEW. 1 1/2 in. 15W. H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Offered below list price at 89/6. P. & P. 5/-. Guitar models: 25W. **£5/5/-;** 25W. **£8/8/-.**
E.M.I. 3 1/2 in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3, 8 or 15 ohms. 15/-. P. & P. 2/6.

4-SPEED TUNER HEAD
 Beautifully designed and precision-engineered by Dornier and Wadsworth Ltd. Supplied ready fitted with twin .0005 tuning condenser for AM connection. Prealigned FM section covers 88-102 Mc/s. I.F. output 10.7 Mc/s. Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. Order quickly! Limited number also available with precision geared 3:1 reduction drive. 30/- P. & P. 3/-.
MATCHED PAIR AM/FM I.F.s. Comprising 1st I.F. and 2nd I.F. discriminator. (465 Kc/s/10.7 Mc/s). Size 1 in. x 1 1/2 in. x 2 1/2 in. H. Will match above tuner head. 11/- pair. P. & P. 2/6.

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1

● Peak output in excess of 11 watts. ● All standard British components. ● Built on printed circuit panel, size 6 x 3 in. ● Generous size driver and output transformers. ● Output transformer tapped for 3 ohm and 15 ohm speakers. ● Transistors (G.T. 14 or 81 Mullard OC81D and matched pair of OC81, 9/6). ● 9 volt operation. ● Everything supplied, wire, battery clips, solder, etc. ● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. **SPECIAL PRICE 45/-.** P. & P. 3/-. Also ready built and tested **52/6.** P. & P. 3/6.


4-SPEED PLAYER UNIT BARGAINS
 Mains Models. All brand new in maker's original packing.
SINGLE PLAYERS. Carr. 6/0 on each.
 B.S.R. TU12 **£3/9/6.** Garrard EP25 de luxe... **£10 19 6**
 B.S.R. GU7 with unit mounted pick-up arm... **£4 18 8**
AUTO CHANGERS. Carr. 6/0 on each.
 B.S.R. UA25 Super 8ilm **£6/2/6.** GARRARD 2000 **£7 10 0**
 GARRARD 3000 **£8/15/-.** GARRARD 1000 with Hi-Fi cartridge **£9/19/6.** Latest GARRARD AT90 Mk. II **£12 0 0**
 All the above units are complete with mono head with sapphire stylus or can be supplied with stereo head at 12/6 extra.

QUALITY RECORD PLAYER AMPLIFIER MK. II
 A top-quality record player amplifier employing heavy duty double wound mains transformer. ECC83, 6L4, EZ90 valves. Separate bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7 in. w. x 3 in. d. x 6 in. h. Ready built and tested. **PRICE 69/6.** P. & P. 6/-.
 ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet on right. **PRICE 89/6.** P. & P. 7/6.
DE LUXE QUALITY PORTABLE R/P CABINET
 Uncut motor board size 14 1/2 x 12 1/2 in. clearance 2 in. below, 3 1/2 in. above. Will take amplifier above and any B.S.R. or GARRARD Autochanger or single Player Unit (except AT60 or SP25). Size 18 x 15 x 8 in. **PRICE £23/9/6.** Carr. 9/6.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.
 170 HIGH ST., MERTON, LONDON, S.W.19 Tel: 01-540 3985
 S.A.E. all enquiries. Open all day Saturday (Wednesday 1 p.m.)

Wilkinsons FOR RELAYS

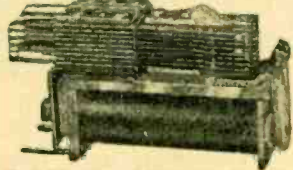

P.O. TYPE 3000 AND 600
BUILT TO YOUR REQUIREMENTS—QUICK DELIVERY
COMPETITIVE PRICES—VARIOUS CONTACTS
DUST COVERS—QUOTATION BY RETURN


LARGE STOCKS OF MINIATURE SEALED RELAYS, DETAILED LIST ON REQUEST

PORTABLE VOLTMETERS 0/100 Moving Iron AC/DC, 8in. mirror scale, in polished wood case, 99/6. Post 8/-. Resistor to double the range. 2/6.
PORTABLE AMMETERS, 0/3 AC/DC 3in., 35/-, p. 3/-.
AVOMETERS. Model 7. £13 10/-, post 7/-.
FREQUENCY METERS. 45/55 cycles per second. 230 volts; 6in. Flush Round. Brand new, £10/10/-.
RESISTORS wire wound or carbon, potentiometers, condensers, quantities ex-stock at low prices.
GEARED MOTORS, 3 R.P.M. or 1 R.P.M. 4 watts very powerful reversible, 24 v. A.C. 35/-, post 2/6, operated from 230 v. with our Transformer. 20/-.
BLUE LINE Heavy Duty Switches by Kraus & Naimer, Code AAL213 with extras, also C16S switches available from stock at less than maker's price.

KEY SWITCHES (3 position)
 4 C Non Lock 4 C Non Lock, 16 6.
 4 C Non Lock 6 C Lock, 20/-.
 2 C Lock 2 C Lock, 12/6.
 4 C Lock 4 C Lock, 17/6.
 Stop 4 C Lock, 12/6.
 Many other types.
Low Capacitance 8 C Muirhead, 17/6.
 Stop 2 C Lock, 7/6. All
 Stop 4 C Non Lock, 10 6. Post
 2 C Lock 6 C Lock, 17 6. 1/6

MAINS TRANSFORMERS. Output 300-0-330 volts, 250 mA, 6.3 volts, 9 amp., 25/-, Post 6/-.
AUTO TRANSFORMERS by S.T.C. Totally enclosed C-core type. 110/250 volts, 8 tappings, 50 cycles, 1,000 watts. Size 6 1/2 x 5 1/2 x 5 1/2 in., £4. P. 10/6.

RATIO ARM UNITS. Sullivan 600Ω + 600Ω. 50/-.
DOUBLE HEADPHONES. High resistance, 4,000Ω, 14 6. Sound powered type DHR, 17/6. Post 3/-.
SMALL MAGNETIC COUNTERS
 3 1/2 x 1 in., 10 counts per second with 4 figures. The following D.C. voltages are available, 6 v., 12 v., 24 v., 50 v. or 100 v.
MAGNETIC COUNTERS, with zero reset 230 v. A.C. or 110 v. Veeder Root 6 fig. 65/- ea. Counting Insts. flush type 48 v. D.C. 90/- ea. post 3/-.
P.O. STANDARD RACKS 6ft. U channel sides drilled for 19in. panels, heavy angle base 150/- ege. 20/-.
LIGHT TYPE 5ft. high £5.
JACK PLUGS. 2 Points, with base and screw-on cover, 2/6, post 9d.
 PO.201 with cord, 3/-, post 1/6.
 P.O. 316, 3 Point, 4/6, post 9d.

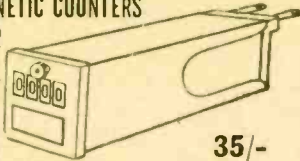

P.L.O. IN RELAYS, Londex 4 change-over HD contacts 28 v. D.C. or 240 v. A.C. with base and cover, 35/- ea.
RELAYS. 24 volt D.C., 4 Make, 4 Break, 10 amp. 5C/304 with Dust Cover, 12/6 each.
TRANSISTORS ASZ 20 7/6 ea. GET 875 special low gain selection 6/- ea. 28002 15/- ea. V30-30P 15/- ea. Diode 8X645 15/- ea.

HAIR HYGROMETER. 4in. round by Negretti & Zambra, scaled 0/100, reading relative percentage humidity, 65/- Post 3/-.
METERS GUARANTEED. Complete list available
 Microamps 0/100 2 1/2 in. MC 40/-
 Microamps 0/500 2 1/2 in. MC 25/-
 Microamps 0/500 2 1/2 in. MC 37/6
 Milliamps 0/50 2 1/2 in. MC 35/-
 Milliamps 0/500 3 1/2 in. MC 54/-
 Amps 0 5 2 in. MC 37/6
 Volts 5/0 5 2 1/2 in. MC 27/6
 Volts 0/20 2 1/2 in. MC 37/6
 Volts 0 5 A.C. 3 1/2 in. M.I. 55/-
 Volts 0/10 A.C. 3 1/2 in. MCR 70/-
 Microamps 0/50 scaled in Milli Rontgens 2 1/2 in. MC 45/-
 MilliVolts 350/0/350 (3.5/0/3.5) Millia 2 1/2 in. MC 35/-
PORTABLE VOLTMETERS. 0/250 Moving Iron AC/DC 6in. scale, in polished wood case, £7/10/-.
MINIATURE BUZZERS (as illus.), 12 volt with tone adjuster, 7/6.
HIGH NOTE BUZZERS 24 v. A.C./D.C. with tone adjuster, 2 1/2 in. dia. Bakelite case 10/6. Post 2/-.
SUBMINIATURE MICRO SWITCHES
 HONEYWELL 115M1-TN13. S.P.D.T. Size: .78in. x .250in. x .356in. 6/6 each.
MICRO SWITCH. Burgess MK4BR, robust die cast casing 8/6 each. Post 9d.



L. WILKINSON (CROYDON) LTD.
 LONGLEY HOUSE LONGLEY RD. CROYDON SURREY
 Phone: TMO 0236 Grams: WILCO CROYDON

VAN DAM ELECTRONICS — ROTTERDAM, HOLLAND

Snellemansstraat 11

SILICON TRANSISTORS

Type number	PNP/NPN	V _{ce} Volt	V _{eb} Volt	V _{eb} Volt	I _c mA	I _b mA	P _c mW	Hf _c H213	F _t Mhz	I _b O nA	Noise dB	Price
2N1613	N	50	75	7	500	15	3 W	40-120	75	10μA	J2	5 8
2N1711	N	50	75	7	500	15	3 W	100-300	100	10μA	—	5 8
2N1893	N	100	120	7	500	15	3 W	40-120	75	10μA	—	£1 1 0
2N2102	N	65	120	7	1 A	100	5 W	40-120	120	2μA	8	13 9
2N2926-or	N	18	18	5	100	5	200	90-180	200	500	2, 8	4 6
2N2926-gr	N	18	18	5	100	5	200	235-470	200	500	2, 8	5 4
2N3053	N	40	60	5	700	100	5 W	50-250	100	250	—	11 2
2N3054	N	55	90	7	4 A	2 A	29 W	25-100	1	—	—	£1 0 0
2N3055	N	60	100	7	15 A	7 A	115 W	20-70	—	—	—	£1 9 8
2N3702	P	25	40	5	200	5	300	60-300	100	100	—	6 0
2N3704	N	30	50	5	800	5	360	100-300	100	100	—	4 8
2N3707	N	30	30	6	30	5	310	100-400	20	100	5	8 6
2N3866	N	55(28)	55	3.5	400	20	5 W	—	800	5mA	—	£3 13 6
2N3903	N	40	60	5	200	5	310	50-150	250	—	6	8 6
2N3904	N	40	60	5	200	5	310	100-300	300	—	5	8 6
2N3905	P	40	40	5	200	5	310	50-150	200	—	5	9 5
2N3906	P	40	40	5	200	5	310	100-300	250	—	4	9 2
2N4124	N	25	30	5	200	5	310	120-360	300	50	5	8 6
2N4126	P	25	25	4	200	5	310	120-360	250	50	4	8 6
2N4284	P	25	25	5	100	5	250	35-150	10	100	—	5 6
2N4286	P	25	30	6	100	5	250	150-600	20	50	—	5 6
2N4288	N	25	30	6	100	5	250	150-600	20	50	—	5 6
2N4292	N	12	30	7	50	5	200	12dB	800	500	6	5 6
2N4347	N	120	140	7	5 A	3 A	100 W	20-70	2	2mA	—	£2 0 0
2N5034	N	40	55	5	6 A	6 A	83 W	20-70	2,8	—	—	18 2
2N5036	N	50	70	5	8 A	6 A	83 W	20-70	2,8	—	—	19 8
2SC100	N	15	40	5	200	—	150	30-—	400	—	—	18 2
2SC183	N	5	5	5	50	—	100	75-150	150	—	—	8 9
BC107b	N	45	45	5	100	5	300	125-500	300	1	2	4 3
BC108b	N	20	20	5	100	5	300	125-500	300	1	2	4 3
BC109c	N	20	20	5	100	5	300	240-900	300	1	4	4 9
BC147b	N	45	45	5	100	5	200	125-500	150	1	4	3 8
BC148b	N	20	20	5	100	5	200	125-500	150	1	4	3 5
BC149c	N	20	20	5	100	5	200	240-900	150	0.2	2	3 9
BC171b	N	45	45	5	100	5	200	240-500	300	0.2	2	2 6
BC172c	N	20	20	5	100	5	200	450-900	300	15	1	2 6
BC184c	N	30	45	5	100	5	300	450-900	150	15	1	6 9
BF117	N	140	140	5	100	—	1270	25-120	80	10	—	11 8
BSY79	N	120	120	5	30	—	300	30-150	100	50	—	8 6

Type number	PNP/NPN	V _{ce} Volt	V _{eb} Volt	V _{eb} Volt	I _c mA	I _b mA	P _c mW	Hf _c H213	F _t Mhz	I _b O nA	Noise dB	Price
MD7011 dual	N/P	30	50	5	300	15	2 x 1 W	40-70	200	100	—	£1 12 8
MJE340	N	300	300	3	500	100	20 W	30-240	10	100μA	—	17 2
MJE370	P	30	30	4	3 A	2 A	25 W	25-40	4	100μA	—	£1 6 0
MJE371	P	40	40	4	3 A	2 A	25 W	25-40	4	100μA	—	£1 16 2
MJE520	N	30	30	4	3 A	2 A	25 W	40-60	4	100μA	—	£1 19 3
MJE521	N	40	40	4	3 A	2 A	25 W	40-60	4	100μA	—	—
MP53394	N	25	25	5	100	5	310	35-170	300	100	—	5 2
MP56517	P	40	40	4	100	5	310	90-180	200	50	3	8 7
MP56531	N	60	60	5	600	5	310	90-270	390	50	3	9 5
MP56534	P	40	40	5	600	5	310	90-270	260	50	3	10 3
TIP14	N	60	80	7	4 A	2 A	10 W	30-150	40	50μA	—	17 2
TIP24	N	70	70	9	2 A	500	10 W	19-136	5	250μA	—	17 2
TIS18	N	13	25	3	30	4	200	20dB/1000Mhz	1200	500	—	19 9
TS2219	N	30	30	5	800	100	3 W	40-75	100	500	—	6 6
TS2905	P	30	30	5	600	100	3 W	40-75	100	500	—	7 5
40233	N	18	18	5	100	25	1 W	90-300	60	250	2	8 2
40310	N	35	35	2, 5	700	200	29 W	20-120	1	10μA	—	13 9
40314	N	40	40	2, 5	700	200	5 W	70-350	100	250	—	10 10
40316	N	40	40	1, 4	700	200	29 W	20-120	1	10μA	—	13 9
40317	N	40	40	2, 5	700	200	5 W	40-200	100	250	—	10 10
40319	P	40	40	2, 5	700	200	5 W	35-200	100	250	—	18 6
40360	N	70	70	4	700	200	5 W	40-200	100	500	—	12 0
40361	N	70	70	4	700	200	5 W	70-350	100	500	—	13 4
40362	P	70	70	4	700	200	5 W	35-200	100	500	—	18 10
40363	N	70	70	4	15 A	7 A	115 W	20-70	1	—	—	£1 11 11
40364	N	60	60	4	7 A	5 A	35 W	35-175	15	—	—	£3 0 7
40406	P	50	50	4	700	200	1 W	20-200	100	—	—	19 2
40407	N	50	50	4	700	200	1 W	70-350	100	250	—	11 6
40408	N	90	90	4	700	200	1 W	40-200	100	250	—	15 2
40409	N	90	90	4	700	200	3 W	50-250	100	250	—	16 0
40410	P	90	90	4	700	200	3 W	50-250	100	250	—	£1 2 8
40411	N	90	90	4	30 A	15 A	150 W	35-100	1	—	—	£3 4 6

Uni-Junction Transistors	V _{rb2} Volt	I _c -cont. mA	I _c -peak Amp.	I _b μA	I _b mA	P _c mW	R _{bb} K-ohm	I _b O nA	vO _{b1} Volt	Price
2N2160	30	70	2	25	8	450	4.0-12	12μA	3	£1 1 3
2N2646	30	50	2	25	6	300	4.7-9.1	50	6.5	15 6
2N4870	30	50	2	5	5	300	4.0-9.1	10	6	13 9
TIS43	30	50	1	5	2	300	4.0-9.1	10	3	13 3

SILICON SEMICONDUCTORS

Field Effect Transistors

Type Number	n/p Channel	V _{dg} Volt	V _{ds} Volt	V _{gs} Volt	I _g mA	I _{dss} mA	I _{gss} nA	P _c mW	Y _f umhos	F _t Mhz	Cap. in/out	Price
2N3819	N	25	25	7.5	10	2-20	2	200	2,000-6,500	100	8/4	10 8
2N3820	P	20	20	7-9	10	0.3-15	20	200	800-5,000	10	32/16	£1 5 5
2N4360	P	20	20	9.0	10	3-30	10	500	2,000-8,000	10	20/5	13 0
MPF102	N	25	25	8.0	10	4-20	2	200	2,000-7,500	100	7/3	9 5
MPF103	N	25	25	2.5	10	1-5	1	200	1,000-5,000	20	7/3	10 8
MPF104	N	25	25	3.5	10	2-9	1	200	1,500-5,500	20	7/3	10 8
MPF105	N	25	25	4.5	10	4-16	1	200	2,000-6,000	20	7/3	10 8
TIS34	N	30	30	7.5	10	4-20	5	200	3,300-6,500	200	6/2	13 3

Lasky's Radio

CONSTRUCTORS BARGAINS

THE SKYROVER DE LUXE



7 transistor plus 2 diode superhet, 6 waveband portable receiver covering the full Medium Waveband and Short Waveband 31-93M and also 4 separate switched band-spread ranges, 13M, 16M, 19M, and 20M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is factory assembled, wired and tested. Superhet, 470 Kc/s. Muftard Transistors. Uses 4 U2 batteries, 6in. Ceramic Magnet P.M. Speaker, 500 MW Output. Telescopic Aerial and Ferrite Rod Aerial. Tone Circuit. In wood cabinet, size 11½ x 6½ x 3in., covered with washable material, plastic trim and handle. Car aerial socket fitted.


Can now be built to **£8.19.6** Post 6/- extra.

H.P. Terms: 60/- deposit and 11 monthly payments of 12/9 Total H.P.P. £10/0.3.

Data 2/6. Refunded if you purchase parcel. All components avail. sep. A simple additional circuit provides coverage of the 1100/1950M. Long Waveband. All necessary components with construction data. Only 10/- extra. Post Free. This conversion is suitable for receivers already constructed.

TRANSISTOR FM TUNER CHASSIS

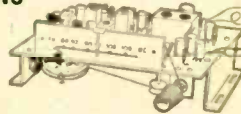Fully tunable—range 88 to 108 Mc/s. Completely wired on printed circuit. 10.3 Mc/s. I.F. 6 transistors and 3 diodes. Slow motion tuning drive. Size 6½ x 4 x 2½in. Operates from any 9 v. D.C. source. Full data and circuit.



LASKY'S PRICE **£6.10.0** Post 5/- extra.

MULTIPLEX ADAPTOR

Now you can enjoy stereo sound with the FM Tuner above. Brief spec.: MPX input sensitivity 100mV. Output 150 mV. Self powered by a 9 v. battery. 4 transistor and 6 diode circuit. Size 5½in. x 2½in. x 1½in. Also suitable for use with other FM tuners with MPX input.

LASKY'S PRICE **99/6** Post 5/-.

PACKAGE PRICE IF BOUGHT TOGETHER **£11.11.0**. Post 5/-.

LASKY'S PANEL METERS

Precision made in clear plastic HIOKI of Japan. Each meter boxed and fully guaranteed with all fixing nuts and washers. Sizes are of front panel. Spec. quotes for quantities. Add 1/3 post on each.



TYPE KR-5. 3 x 2½in. (4h.s.)	100µA	47/6
1 mA D.C.	32/6	37/6
5 mA D.C.	32/6	39/6
300 V. D.C.	32/6	

TYPE MK-38A 1½in. square		
1 mA DC	22/6	
5 mA DC	22/6	
100 V. DC	22/6	
500µA	29/6	
100µA	27/6	
3 mA 8 Meter	29/6	

TYPE MK-45A 2in. square		
1 mA DC	25/-	
5 mA DC	25/-	
300 V DC	25/-	
500µA	25/-	
1 mA 8 Meter	35/-	


TYPE KR-65 3½ x 3in.		
1 mA DC	36/-	
5 mA DC	35/-	
300 V DC	35/-	
100µA	49/6	
500µA	42/6	
1 mA 8 Meter	39/6	

TYPE MK-65A, 3in. square		
1 mA DC	36/-	
5 mA DC	35/-	
300 V DC	35/-	
300µA	39/6	
1 mA 8 Meter	37/6	

STUDIO DECKS

MAGNAVOX 363 TAPE DECKS

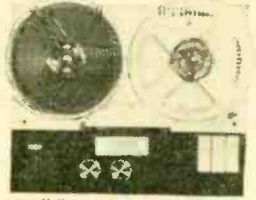The very latest 3 speed model—1½, 3½, 7½ i.p.s. available with either ¼ track or ½ track head. Features include: pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor; interlocking keys. Size of top plate 12½ x 11 x 5½in. deep below unit plate. For 200V 50 v. A.C. mains. 50 c.p.s. operation. New unused and fully guaranteed.



LASKY'S PRICE **£10.10.0** Carriage and model ½ track packing 7/6 extra
LASKY'S PRICE **£13.9.6** Carriage and model ¼ track packing 4/6 extra

SPECIAL FOR OVERSEAS CUSTOMERS—the new Magnavox-Collaro 363 Deck for 110/125 v. 50 or 60 c.p.s. mains now available, prices as above. Post to any part of the world. 35/-.

NEW MARTIN TAPE RECORD REPLAY AMPS.

Now available from stock—for use with the Magnavox 363 Tape Deck.
¼ track model.....LASKY'S PRICE **£14/19/6** Carriage & packing 4/6 extra
½ track model.....LASKY'S PRICE **£15/19/6** Carriage & packing 4/6 extra
Optional Extra: Control escutcheon to tape deck and amplifier controls.
LASKY'S PRICE **12/6**. Post & Packing 2/6.

Branches

- 207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271
Open all day Saturday, early closing 1 p.m. Thursday
- 33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605
Open all day, 9 a.m.—6 p.m. Monday to Saturday
- 152/3 FLEET STREET, LONDON, E.C.4 Tel.: FLEet St. 2833
Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

WW-140 FOR FURTHER DETAILS

SPECIAL INTEREST ITEMS!

TWO BAND TRANSISTOR CAR RADIO BARGAIN!

MODEL CR-62

A new high-quality imported all-transistor superhet car radio that really breaks the quality/price barrier. Unique features of this set are the four M/V band station pre-selection buttons which you yourself set to your own four favourite stations—this is in addition to full M/V band cover over 150-300 kc/s. (IF frequency 465 kc/s) maximum output. Six transistor (including one drift type) and one diode circuit provides powerful 2 W. output. The set is adjustable for use on either pos. or neg. ground 12 v. systems (external line fuse fitted). Standard mounting size 6½ x 6½ x 2½in.—front panel 4in. larger all round—finished in anodised aluminium with black push buttons. Complete with mounting brackets, full installation instructions and 2 baffle boards (for round or elliptical speaker). Fully guaranteed.



LASKY'S PRICE **£9.19.6** Post 5/-, 6 x 4in. elliptical 8Ω dynamic speaker. 17/6 extra—Post FREE.

SPECIAL OFFER—LOCKING CAR AERIAL

Model B3003 five section 40in. extension heavy chrome telescopic wing mounting type with unique locking device to protect the antenna when closed. Complete with mounting bracket, lead and plug and two "keys".

LASKY'S SPECIAL PRICE **39/6** Post free with the Royal CR-62. Sep. Post 2/6.

NEW FOR THE RECORDING ENTHUSIAST VOICE ACTUATED MICROPHONE

MODEL B 5001

This new voice actuated microphone is designed for use with tape recorders with facilities for remote control. The microphone is fitted with a three position switch allowing normal hand remote control, voice sensitivity action and off. The degree of voice or sound level required to operate the recorder can be adjusted. The microphone is self powered by one 9V (PP3 type) battery giving 6 to 10 hrs. operating time. Super sensitive 6 transistor circuit. Strong black plastic case. Length 7½in. Designed for hand-held use or lying flat. Fitted with 2.5 and 3.5 mm. plugs for fitting polarised sockets.



LASKY'S PRICE **£6.19.6** Post 3/6.

EXPORT TTC B4002 FM WIRELESS MIC.

Highly sensitive—suitable for either static or mobile use. Signal can be picked up by any FM radio or tuner which receives frequencies between 90-104 Mc/s. over several hundred yards. Size only 3 x 2½ x 1½in. (in leather case). Operates on one PP3 type battery. Complete with neck cord, clip-on dynamic extension mike (1 x 7 x ¾in.) and battery.



LASKY'S EXPORT PRICE **£6.19.6** Post Free. Anywhere in the World.

TTC 13/500. More powerful version of above—size 7½ x 1½ x 1½in. Operates on the PP3 type battery. LASKY'S PRICE **12 Gns.** Post Free. Anywhere in the World.

MICROPHONE BARGAIN

STC MODEL 414

A high quality omni-directional moving coil microphone—suitable for use with sound reinforcement and P.A. systems; tape recorders, transistor amplifiers, etc. Attractive grey moulded case for free standing or hand-held use—size 2½ x 2½ x 2½in. Complete with 6ft. screened cable. New and unused in maker's cartons—fully guaranteed.



Type A. Low Imp. 200Ω. LASKY'S PRICE **£1/19/6** Post 2/-
Type B. High Imp. 50KΩ. LASKY'S PRICE **£2/5/-** Post 2/-

MUSICASSETTES

There are now over 200 Musicassette titles available—Jazz—Pop—Shows—Classics—on Philips, Mercury, Fontana, C.B.S., Pye, Reprise, Chess, W.B., Kama Sutra, Parlophone. Send S.A.E. for full list of titles.

NEW INTERNATIONAL TAPE

FAMOUS AMERICAN MADE BRAND TAPE AT RECORD LOW PRICES

3in. Message tape, 150ft.	2/6	5½in. Long play, 1,200ft. Acetate	12/6
3in. Message tape, 225ft.	3/0	5½in. Standard play, 850ft. P.V.C.	11/6
3½in. Triple play, 400ft. Mylar	7/6	6in. Triple play, 2,400ft. Mylar	45/-
3in. Triple play, 900ft. Mylar	10/-	5½in. Long play, 1,200ft. Mylar	15/-
4in. Triple play, 900ft. Mylar	17/6	7in. Standard play, 1,800ft. Acetate	12/6
5in. Double play, 1,200ft. Mylar	15/-	7in. Standard play, 1,200ft. Mylar	19/6
5in. Long play 900ft. Acetate	10/-	7in. Long play, 1,900ft. Mylar	19/6
5in. Standard Play, 800ft. P.V.C.	8/6	7in. Double play, 2,400ft. Mylar	25/-
5in. Triple play, 1,800ft. Mylar	35/-	7in. Long play, 1,800ft. Acetate	15/-
5in. Double play, 1,800ft. Mylar	22/6	7in. Triple play, 2,600ft. Mylar	50/-

1/- Post extra per reel; 4 reels and over Post Free.

High Fidelity Audio Centres

- 42 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573
Open all day Thursday, early closing 1 p.m. Saturday
- 118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789
Open all day Saturday, early closing 1 p.m. Thursday

Lasky's Radio

DON'T MISS THIS!

HAVE YOU GOT YOUR COPY OF OUR GREAT "35th Birthday" CATALOGUE — FREE WITH OUR COMPLIMENTS

Printed in large 16 x 11in. modern magazine format the "Birthday Pictorial" contains thousands of different items from our vast stocks of Radio, Hi-Fi, TV, Test Gear, Components, Communications and other equipment.

PLUS many bargain offers and prices exclusive to Lasky's **AND** in addition every copy of the "Birthday Pictorial" is numbered and automatically enters you in our great "Birthday Draw" with over £100 in Gift Vouchers to be won.


All goods shown in the "Birthday Pictorial" are available over the counter from any of our branches — or by post to any address in the U.K. or overseas — bringing the benefits of shopping at Lasky's to you in your home.

SECOND REPRINT ISSUE NOW AVAILABLE

— JUST send your name, address and 6d stamp for postage only. **A MUST FOR EVERY ELECTRONICS & HI-FI ENTHUSIAST!**



RECORD PLAYERS

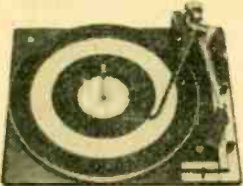

B.S.R. AUTOCHANGERS NEW LOW PRICES

Fully guaranteed complete with cartridge and stylus
 UA16 ov. battery model £5 19 6
 UA20 4-speed mains model £5 19 6

NEW—B.S.R. UA70 (Illustrated)
 4 speed mains autochanger superb modern styling at amazingly low price.
LASKY'S PRICE £9/19 6 (ex cartridge)

GARRARD AUTOCHANGERS

AT100 Mk. I £9 19 6
 AT100 Mk. II £12 19 6
 3000LM with stereo cartridge £8 19 6
 AT70 £17 17 0
 Lab. A Mono/Stereo £14 19 6
 Lab. A on plinth £15 19 6
 A50 £7 7 0

A1000 £6 6 0
 A2000 £6 16 6
GARRARD BASES
 WB1 £3 16 3 WB2 £5 5 0
CLEARVIEW PERSEPEX COVERS
 WB1 £3 17 0 WB2 £5 7 11

TRANSCRIPTION MOTORS
 GARRARD 401 £27 19 0
 GARRARD Lab. 80, Mk. II £25 0 0
CONNOISSEUR
 Craftsman II £17 2 11
 Craftsman III £22 19 6
 Model II £25 4 0
LENCO GL54 £17 1 9
LENCO GL48 £19 10 7
LENCO Q88 £15 15 0
LENCO GL70 £29 18 8
LENCO Q99 £21 19 5
THORENS TD105 I £26 5 0
THORENS TD105 II £40 8 8
THORENS TD124 II £40 5 8
THORENS TD160 £20 13 2

SINGLE PLAYERS
 Auto, start and stop. Complete with pick-up and crystal cartridge.
 EMI with Stereo cartridge £3 19 6
 COLLARO Junior 4-speed £3 9 6
 GARRARD RRP12 £4 7 8
 GARRARD SRP10 mains model £4 19 6
 GARRARD SRP10 batt. model £4 19 6
 GARRARD SP25 Light U/table £9 19 6
 GARRARD SP25 Heavy U/table £10 19 6
 (Garrard SP25's are ex-cartridge)
 PHILIPS AQ1016 £12 12 0
 BIRLUN PCAL Stereo £8 19 6

All other current models available. Postage on all above 5/- extra.

DEMONSTRATION STUDIOS

Lasky's High Fidelity Sound Centres

42 Tottenham Court Road, W.1 and 118 Edgware Road, W.2 are London's most comprehensive High Fidelity Sound Centres, designed to provide a real "Home-from-Home" for the discerning Hi-Fi Enthusiast. There you can see, hear and compare any combination of the finest quality equipment; our experienced staff are on hand to help you plan a complete system and to select the equipment most suitable to your requirements. In addition we are often able to offer considerable cash savings when you choose a complete system.

If you cannot visit any of our branches please send details of your requirements to our head office and we shall be pleased to quote without obligation. We operate the "Purchase Tax Free" scheme for overseas visitors. Full H.P. terms available.

PACKAGE DEALS

A Lasky's "Package Deal" allows you to purchase the complete Audio System of your choice at a worthwhile cash saving. We shall be pleased to quote our "Package Deal" price for any selection of equipment of your own choice. Send us detail of your requirements. H.P. and Easy Credit Terms can be arranged on "Package Deals."


LASKY'S RADIO FOR FINEST VALUE AND COURTEOUS SERVICE

WW-141 FOR FURTHER DETAILS

COMMUNICATION RECEIVERS

NOW AVAILABLE FOR THE FIRST TIME IN GREAT BRITAIN. TWO NEW TRIO RECEIVERS MODEL JR-500SE

This high performance receiver is made especially to cover the amateur bands and utilises a crystal controlled double heterodyne circuit for extra selectivity and stability. Brief spec.: Covers all the amateur bands in 7 separate ranges between 3.5 and 29.7 Mc/s. Circuit uses 7 valves, 2 transistors and 5 diodes plus 9 crystals; output 8 and 500 ohm and 500 ohm phone jacks. Special features: Crystal controlled oscillator • Variable BFO • VFO • AVC • ANL • 8 meters • 88B-4W • Stand-by switch • special double gear dial drive with direct reading down to 1.8 Mc/s • Remote control socket for connection to a transmitter. Audio output 1 watt. For use on 110/250 V A.C. Mains. Superb modern styling and control layout—finished in dark grey. Cabinet size 7 x 13 x 10in. Weight 18 lbs. Fully guaranteed, comp. with instruction manual and service data.

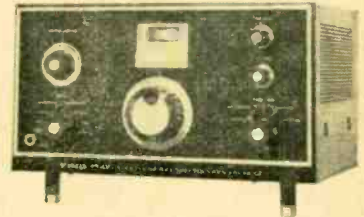

Carriage and Packing 12/6.

LASKY'S PRICE £61.19.0

MODEL 9R-59DE

Brief spec.: 4 band receiver covering 550 Kc/s to 30 Mc/s continuous and electrical band spread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. Special features: 88B-CW • ANL • Variable BFO • 8 meter • Sep. band spread dial • IF frequency 455 Kc/s • audio output 1.5 W • Variable RF and AF gain controls. For use on 110/250 V A.C. Mains. Beautifully designed control layout finished in light grey with dark grey case. Size: 7 x 10 x 10in. Weight 19 lbs. Fully guaranteed, comp. with instruction manual and service data.



Carriage and Packing 12/6.

LASKY'S PRICE £36.15.0

TAPE RECORDERS

JUST ARRIVED—FANTAVOX TAPE CASSETTE PLAYER

This machine is the first of its type and is designed specifically to replay pre-recorded tape cassettes made for the PHILIPS and other cassette systems. The cassette is simply slipped into the machine and is immediately ready to play—each cassette gives 15 minutes play (two tracks) no loss of time in rewinding—simply turn cassette over. Constant tape speed 1 1/2 i.p.s. Only two controls off/play and vol. Fully transistorised, powerful vol., built-in speaker, socket for personal earpiece. Operates on 5 powerful 40 ohm type 41 P.M. with wrist strap. Complete with cassette and batteries. There are now over 200 music cassette titles available. JAZZ, POP, SHOWS and CLASSICS—this machine allows you to play the music of your choice anywhere—anytime.



LASKY'S PRICE £9.19.6 Post 5/-.

OUTSTANDING VALUE—THE 'TELETON' 701

7-TRANSISTOR TWO-SPEED CAPSTAN DRIVE MAINS/BATTERY RECORDER

An outstandingly high quality machine that is unparalleled for value. Performance is equal on both mains and battery, excellent music and speech characteristics make this the ideal home or office recorder.



Look at these outstanding features:

- 7 transistor and 3 diode circuit—800mW output.
- Two speed, 1 1/2 and 3 1/2 i.p.s. capstan drive system (wow and flutter better than 0.3% at 3 1/2 i.p.s.).
- Built-in 110/240 v. A.C. inverter for mains operation or uses 4 x 1.5 v. batteries.
- Takes 5in. spools giving 3 hrs. track recording at 1 1/2 i.p.s. and 1 1/2 hrs. at 3 1/2 i.p.s.
- Fast forward and rewind.
- Twin track A.C. bias recording system—frequency response 100 to 7,000 c/s.
- Record level meter (acts as battery check on replay).
- Piano key function controls, plus vol. and tone controls.
- Continental type 5 pin inputs for microphone, telephone adaptor pick-up and direct recording from radio or other recorder; switched input for earphone.
- 2 1/2 x 4 1/2 P.M. Dynamic speaker.
- Plastic cabinet in two-tone grey with chrome metal trim and carrying handle.
- Accessories: Dynamic direct microphone with flip-on stand, telephone pick-up, 5in. spool of tape and empty spool, earphone, direct recording lead (works best with plug), batteries and instruction book with circuit comp. with all accessories. Fully guaranteed.

LASKY'S PRICE £22 Post FREE.

BI-PAK SEMICONDUCTORS

8 Radnor House
93-97 Regent Street
London, W.1
(DEPT. W.W.)

W.W. DIGITAL COMPUTER TRANSISTORS and DIODES

Trans. 2G-371/D1476	8d. each
Trans. Sil. 25301C	2/- each
Diodes Sil. 15130	4d. each

Prices for all qty's. All devices will meet W.W. specifications reqd. BRAND NEW.

ORP12 8/6
BC107
BC108 5/-
BC109

NEW UNTESTED SUPER-PAKS

Uncoded Devices

40	SIL. PLANAR TRANS NPN. Sil. 2N7008, 8BY26/27, 28103/4	10/-
30	DIAPY Metal Alloy Diffused Trans. Sil. MA101/2, DA353, MA820, PNP.	10/-
50	Sil. Planar Diodes 250mA. Sil. 1B121/130, 0A200/202	10/-
30	AF Germ. Alloy Trans. PNP. Sil. 2N2900 Series, OC717/5, AC126/8	10/-
12	Epoxy Case 500mA Sil. Rect. 100-500 p.p.s. Sil. BY101, BY130.	10/-
30	Fast Switching Sil. Diodes. Sil. 1N4149/18, 1N412/16, Micro-Min	10/-
10	1 Amp. Glass Sil. Rect. 200-800 p.p.s. Sil. BYX22/200-900	10/-

* VALUE PACKS for 68 NEW UNTESTED *

120	Glass Sub-Min.	GERM. DIODES	10/-
50	Mixed Germ.	TRANSISTORS	10/-
20	Mixed Volts.	ZENERS	10/-
30	NPN, PNP, MIXED	SIL. TRANS.	10/-
60	200mA Sub-Min.	SIL. DIODES	10/-
20	Germ. 1 Amp.	RECTIFIERS	10/-
40	Like OC81, AC128	TRANSISTORS	10/-
10	2 Amp. Scud	SIL. RECT.	10/-
25	Sil. NPN, 200 Mc/s.	TRANSISTORS	10/-
16	Top-Hat 750mA	SIL. RECT.	10/-
75	GERM. DIODES	GOLD BONDED	10/-
20	Like BAY 50 charge storage	DIODES	10/-
10	50-400 PIV 1 Amp.	SCR's	20/-

★ QUALITY-TESTED VALUE PAKS ★ BARGAINS ★

2	Drift Trans. 2N1225 Germ. PNP 100 Mc/s	10/-
6	Matched Trans. OC44/43/81/81D	10/-
16	Red 8400 AF Trans. PNP	10/-
16	White Spot R/P Trans. PNP	10/-
5	Silicon Rects. 5 A 100-400 PIV	10/-
5	10 A Silicon Rects. 100 PIV	10/-
2	OC1 140 Trans. NPN Switching	10/-
1	12 A 820 100 PIV	10/-
3	84L Trans. 2N2802 PNP	10/-
4	Zener Diodes 250 mW 3-12 V	10/-
3	200 Mc/s Sil. Trans. NPN 8BY26/27	10/-
3	Zener Diodes 400 mW 33 V 5% Tol.	10/-
4	High Current Trans. OC42 Epvt.	10/-
2	Power Transistors 1 OC235 1 OC335	10/-
5	Silicon Rects. 400 PIV 250 mA	10/-
4	OC73 Transistors Mullard Type	10/-
1	Power Trans. OC20 100 V	10/-
4	OC202 Sil. Diodes Sub-min.	10/-
2	Low Noise Trans. NPN 2N4339/30	10/-
1	84L Trans. NPN VCB 100 ZTR8	10/-
8	OA81 Diodes (CV448)	10/-
4	OC72 Transistors Mullard Type	10/-
1	OC77 Transistors Mullard Type	10/-
5	Metal Alloy Transistors Mal. Type	10/-
4	84L Rects. 400 PIV 500 mA	10/-
5	OC7894 Trans. Epvt. OC34	10/-
5	OC7883 Trans. Epvt. OC45	10/-
3	VHF Sil. Epoxy Trans. NPN 100 Mc/s	10/-
2	2N768 Sil. Trans. 300 Mc/s NPN	10/-
3	OC741 AF Germ. Trans. PNP Epvt. OC71	10/-
3	OC731 LF Low Noise Germ. Trans. PNP	10/-
6	1N914 Sil. Diodes 75 PIV 75 mA	10/-
8	0A90 Germ. Diodes Sub-min. 1N69	10/-
3	NPN Germ. Trans. NK7773 Epvt. AC130	10/-
2	OC22 Power Trans. Germ.	10/-
2	OC25 Power Trans. Germ.	10/-
2	OC73 Mullard Type	10/-
4	AC128 Trans. PNP High Gain	10/-
2	AC127/128 Comp. pair PNP/PNP	10/-
10	Assorted Gold Bonded Diodes	10/-
2	2N1307 PNP Switching Trans.	10/-
20	Germ. Diodes General Purpose	10/-
7	OC8211 Germ. Diodes Epvt. OA71	10/-
3	AF116 Mullard Type Trans.	10/-
12	Assorted Germ. Diodes Marked	10/-
8	AC124 Germ. PNP Trans.	10/-

FREE One 10/- Pack of your own choice free with orders valued £4 or over

5	1 Amp. Germ. Rect. 200 PIV	10/-
1	ORP61 Photo-conductive cell	10/-
4	Silicon Rects. 100 PIV 750 mA	10/-
3	AF117 Trans. Mullard Type	10/-
7	OC81 Type Trans.	10/-
3	OC71 Trans. Mullard Type	10/-
3	2N2926 Sil. Epoxy Trans.	10/-
7	OC71 Type Trans.	10/-
3	12 Volt Zeners 400 mW	10/-
25	Trans. Beatronics 1B1018, 8012, etc.	10/-
1	TK400A Power Germ. Trans. - ADV32	10/-
2	28701 Sil. Trans. Texas	10/-
2	Zeners 2Z150F. 15 M F watt	10/-
3	12 Volt Zeners 400 mW	10/-
2	10 A 600 PIV Sil. Rects. 18425R	15/-
3	BC108 Sil. NPN High Gain Trans.	15/-
2	Zener Diodes 25 V 18 and 22 V	15/-
4	2N910 NPN Sil. Trans. VCB100 80Mc/s	15/-
2	1000 EPV Sil. Rect. 1.5 A RB310 AF	15/-
1	High Vol. AF Trans. PNP ACV17	15/-
3	18V95A Sil. Trans. NPN 200 Mc/s	15/-
3	OC200 Sil. Trans. Mullard	15/-
2	84L Power Rects. 1N213	15/-
1	84L Power Trans. NPN 100 Mc/s TK201A	15/-
6	Zener Diodes 215 V Sub-min.	15/-
1	2N1392 PNP Epvt. Planar Sil. Trans. 15/-	15/-
3	2N697 Epvt. Planar Trans. Sil.	15/-
4	Germ. Power Trans. Epvt. OC16 Mullard	15/-
1	Unijunction Trans. 2N2646 Epvt. DOE29	15/-
2	Sil. Trans. 200 Mc/s 60V BZ83/94	15/-
1	84L Planar Trans. NPN 100 Mc/s BSY25	15/-
1	84L Trans. 18104 100 Mc/s 1P 200 NPN	15/-
2	SCRs on PIV 1 A 10-3 can	15/-
1	Tunnel Diode 1N3720 (TD15) G.E.	15/-
1	Unijunction Trans. 2N216 TO-5 can G.E.	15/-
2	84L Rects. 5 A 400 PIV Stud Type	15/-
2	Germ. Power Trans. OC329	15/-
1	10 A 84L Stud Rect. 800 PIV	15/-
1	Tunnel Diode AEX111 1050 Mc/s STC.	15/-
2	2N3712 Sil. Epoxy Planar BF E225 max.	20/-
6	BY 100 Type Sil. Rects.	20/-
25	Sil. and Germ. Trans. Mixed, all marked	20/-
10	New Power Trans. CBC replaces OC16/26/28	30/-
1	28024 Sil. Power Trans. NPN 100 V 100 W	30/-
1	Sil. Potenti Bridge Rect. 800 PIV 2 A	30/-

UNIJUNCTION

UT46, Epvt. 2N2046, Epvt. T1843 7/6

SIL. RECTS TESTED

PIV	750mA	8A	10A	30A
50	2/	3/	4/	8/
100	2/3	3/8	6/	15/
200	2/6	4/8	6/6	20/
300	3/	4/8	8/	25/
400	3/6	6/	9/	25/
500	4/	6/6	9/6	30/
600	4/3	7/	10/	37/
800	4/9	8/	15/	40/
1000	6/	10/	17/6	50/

SCR'S LOWEST PRICE LARGEST RANGE

PIV	1AMP	7A	16A	30A
25	5	7/6	8	30/-
50	7/6	8/6	10/8	35/-
100	8/6	10/	15/	45/-
200	15/6	15/	20/	55/-
300	15/	20/	25/	60/-
400	17/6	25/	35/	80/-
500	30/	40/	45/	85/-
600	40/	50/	55/-	


Our vast stocks change daily with hundreds of Semi-conductor bargains becoming available. Just send 2/6 to cover 3 months mailing of our latest stock lists. eqvt. charts, circuits, etc.

Minimum Order 10/- CASH WITH ORDER PLEASE. Add 1/- postage and packing Per Order. GUARANTEED by return postal service. Cerebras add extra for Air Mail.

NO EXCUSES! NO DELAYS! FROM STOCK!

VARIABLE VOLTAGE TRANSFORMERS


PORTABLE

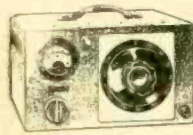

Input 230 v. A.C. Output variable 0-260 v. A.C. at 1.5 amp. Fitted in beautifully finished steel case. Complete with voltmeter, pilot lamp, fuse switch, carrying handle. **£8.10/-**. P. & C. 10/-.

OPEN TYPES

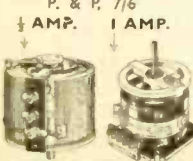Designed for Panel Mounting Input 230 v. A.C. 50/60 Output variable. 0-260 v. 1 amp. ... **£3 3 0**
1 amp. ... **£4 10 0**
2 amp. ... **£5 12 6**
P. & P. 7/6



50 AMPS



1 AMP.

INPUT 230 v. A.C. 50/60

BRAND NEW. Lowest prices in the country. All Types (and Spares) from 1 to 50 amp. available from stock.

0-260 v. at 1 amp.	£4 10 0
0-260 v. at 2.5 amps.	£5 17 6
0-260 v. at 4 amps.	£8 7 6
0-260 v. at 5 amps.	£9 0 0
0-260 v. at 8 amps.	£13 10 0
0-260 v. at 10 amps.	£17 10 0
0-260 v. at 12 amps.	£19 10 0
0-260 v. at 15 amps.	£22 0 0
0-260 v. at 20 amps.	£32 10 0
0-260 v. at 37.5 amps.	£65 0 0
0-260 v. at 50 amps.	£85 0 0

20 DIFFERENT TYPES AVAILABLE FOR IMMEDIATE DELIVERY. P. & C. EXTRA

CONSTANT VOLTAGE TRANSFORMERS



Input 185-250 v. A.C. Output constant at 230 v. A.C. Capacity 250watt. Attractive metal case. Fitted red signal lamp. Rubber feet. Weight 17lbs. Price £11.10/- P. & P. 10/-.

Double Wound Variable Transformers

Fully isolated, low tension secondary winding. Input 230 v. A.C. OUTPUT CONTINUOUSLY VARIABLE 0-36 v. A.C.
0-36 v. at 5 amp. **£8.10.0**—p. & p. 8/6
0-36 v. at 20 amp. **£19.10.0**—15/- p. & p.
These fully shrouded Transformers, designed to our specifications, are ideally suited for Educational, Industrial and Laboratory use.

36 volt 30 amp. A.C. or D.C. Variable L.T. Supply Unit

INPUT 220/240 v. A.C. OUTPUT CONTINUOUSLY VARIABLE 0-36 v.

Fully isolated. Fitted in robust metal case with Voltmeter Ammeter. Panel Indicator and chromo handles. Input and Output fully fused. Ideally suited for Lab. or Industrial use. **£55** plus 40/- p. & c. Similar in appearance to above illustration.

SERVICE TRADING CO

LIGHT SENSITIVE SWITCHES

Kit and parts including ORP.12 Cadmium Sulphide Photocell. Relay Transistor and Circuit. Now supplied with new Siemens High Speed Relay for 6 or 12 volt operations. Price 25/-, plus 2/6 P. & P. ORP.12 and Circuit 10/- post paid.



A.C. MAINS MODEL

incorporates mains transformer rectifier and special relay with 3x5 amp. mains c/o contacts. Price inc. circuit 47/6, plus 2/6 P. & P.


LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing to take MBC bulb. Separate photo cell mounting assembly for ORP.12 or similar cell with optic window. Both units are single hole fixing. Price per pair £2/15/0, plus 3/6 P. & P.



UNIVERSAL DEMONSTRATION TRANSFORMERS

Stenzyl Type

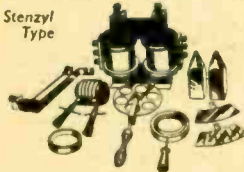

A complete composite apparatus, comprising a robustly built Transformer and electro-magnet with removable coils and pole pieces, coil tapped for 230 v., 220 v., 110 v., 115 v. 6, 12, 36, 110 v.

A.C. These coils are also used for D.C. experiments. Complete with all accessories as shown. £19 plus 15/- carr. Leaflet on request.

PHOTO MULTIPLIER

Type CV337, this supersedes type 931A, complete with special P.T.F.E. base and divider network 57/6 incl. P. & P.

RESETTABLE HIGH SPEED COUNTERS

3 figure, 24 v. D.C. operation (illustrated). Similar to above, but may be pre-set to any number up to 999 reducing to zero. Either type 32/6, P. & P. 2/6d. 4 figure, 1,000 ohm coil, 36-48 v. D.C. operation. £3/10/-. P. & P. 1/6.



PHOTO ELECTRONIC COUNTER

Can be set for counts of up to 500 per minute. 210-250 v. A.C. powered. Kit of Components, including photo cell, high speed non-resettable counter, transformer, relay, etc., together with clear circuit diagram, £3/2/6, plus 3/6 P. & P. With resettable counter, £4/2/6, P. & P. 3/6.

LATEST HIGH SPEED MAGNETIC COUNTERS (NON-RESETTABLE)

4 figure, 10 impulses per second. Type 100A, 500 ohm coil. Type 100B, 2,300 ohm coil. Either 15/- each, plus 1/6 P. & P.

230 VOLT A.C., GEARED MOTORS

Type D15G 5 r.p.m. 1.7lb. inch, £2/9/6, P. & P. 3/- Type B16G 80 r.p.m. 2.6lb. inch, £2/2/-, P. & P. 3/- Type D16G 13 r.p.m. 1.45lb. inch, £2/17/6, P. & P. 3/-

PRECISION FLATPOT

Manufactured by M.E.C. 50 k., 45 turn. Fly leads all metal sealed construction. 10/6d. Plus 1/6 P. & P.



INSULATED TERMINALS
Available in black, red, white, yellow, blue and green. New 15/- per doz. P. & P. 2/-.

TRANSISTORISED MORSE OSCILLATOR

Fitted 2 1/2 in. Moving Coil Speaker. Uses type PP3 or equiv. 9 v. battery. Complete with latest design Morse Key. 22/6, plus 1/6 P. & P.

NICKEL CADMIUM BATTERY

Sintered Cadmium Type 1.2 v. 7AH. Size: height 3 1/2 in., width 2 1/2 in. x 1 1/2 in. Weight: approx. 13 ozs. Ex-R.A.F., Tested, 12/6. P. & P. 2/6.

GENUINE NEW MULLARD 6 AMP. SILICON DIODES NOT Rejects or Seconds

BYZ13 200 PIV 7/- BYZ12 400 PIV 8/-
BYZ11 600 PIV 9/- BYZ10 800 PIV 10/-

100 WATT POWER RHEOSTATS (NEW)

Ceramic construction, winding embedded in Vitreous Enamel, heavy duty brush assembly designed for continuous duty. AVAILABLE FROM STOCK IN THE FOLLOWING II VALUES: 1 ohm 10a., 5 ohm 4.7a., 10 ohm 3a.; 25 ohm 2a.; 50 ohm 1.4a.; 100 ohm 1a.; 250 ohm .7 a.; 500 ohm .45 a.; 1,000 ohm .280 mA.; 1,500 ohm .230 mA.; 2,500 ohm .2 a. Diameter 3 1/2 in. Shaft length 3/4 in. dia. 3/8 in., 27/6. P. & P. 1/6.



50 WATT POWER RHEOSTATS

1 ohm 7a.; 5 ohm 3a.; 10 ohm 2.25a.; 25 ohm 1.4a.; 50 ohm 1a.; 100 ohm .7a.; 250 ohm .45a.; 500 ohm .3a.; 1,000 ohm .22a.; 2,500 ohm .14a. All at 21/- each. P. & P. 1/6.

25 WATT POWER RHEOSTATS

10 ohm 1.5a.; 25 ohm 1a.; 50 ohm .75a.; 100 ohm .5a.; 250 ohm .3a.; 500 ohm .2a.; 1,000 ohm .15a.; 1,500 ohm .12a.; 2,500 ohm .1a.; all at 14/6, each. P. & P. 1/6.

SWING ARM RHEOSTAT

Especially designed for educational use. 0-10 ohm in precision 1 ohm steps. Max. current 5 amp. Size: Height 1 9/16 in. Width 1 1/2 in. Depth 6 1/2 in. Price £4/19/6. P. & P. 7/6.

DRY REED SWITCHES

New special offer of Dry Reed Switches, 1/2 amp. contact, 1 1/2 x 3/4 in., 4 for 10/-, post paid.

VENNER ELECTRIC TIME SWITCH

200-250 v. A.C. 20 amp. contacts twice on, twice off, at any manually pre-set time. Spring reserve (in case of power cut) fully tested £3/9/6, P. & P. 4/6d. Or complete in weather-proof metal case (Illustrated) £3/19/6, plus 4/6 P. & P. Can be supplied with solar dial, on at dusk—off at dawn. Prices as above.



RADIO ALTIMETER

This precision instrument, built to highest Ministry specification, is based on a 24V. D.C. LOW INERTIA (Integrating) Motor. The Motor, fitted with gold brushes and drawing only 800 microamp at 24V, D.C., drives two precision pots with platinum wipers through close tolerance gear-trains, including miniature slipping clutch, combined with two sub-miniature pots for calibrating the electrical bridge circuit. The 3 in. calibrated dial, with a number aperture indicating one rev. per revolution of pointer with maximum of 5 revs., gives an effective scale length of approx. 30 in. Offered at fraction of Manufacturer's price: 32/6 plus 6/- P. & P.



SANWA Multi Range Meters

Acknowledged throughout the world as the ultimate in test meters. NEW MODEL U-50D MULTI-TESTER, 20,000 O.P.V. MIRROR SCALED WITH OVERLOAD PROTECTION. Ranges: D.C. volts: 100mV, 0.5 v., 5 v., 250 v., 1,000 v. A.C. volts. 2.5 v., 10 v., 50 v., 250 v., 1,000 v. D.C. current: 5µA, 0.5 mA., 5 mA., 50mA., 250 mA. Size- 5 1/2 x 3 1/2 x 1 1/2 in. Complete with batteries £5.15.0 Post paid. Three other models available from-stock. Descriptive leaflet on request.



SLIDER RESISTANCE

200 ohm 1.25 amp. 37/6. P. & P. 3/6.
5 ohm 10 amp. 37/6. P. & P. 3/6.

230 v. A.C. RELAY. 2 c/o 2 amp. contacts. 9/6 ex new equip. P. & P. 1/6.

THYRISTOR 400 piv. 5 amp. 14/6 post paid.
THYRISTOR 400 piv. 8 amp. 28/6 post paid.

Condenser 5,000 m/d 50 v. 1 1/2 x 4 1/2 in. 12/6. New.

LATEST TYPE SELENIUM BRIDGE RECTIFIERS

30 volt 3 amp., 11/- plus 2/6 P. & P.
30 volt 5 amp., 14/-, plus 2/6 P. & P.

MOVING COIL HEADPHONE AND MIKE
Soft rubber ear-pieces with M/C Mike fitted 5-way plug as on No. 19 set. New, in maker's packing, 16/6 plus 3/6 C. & P.

A.C. AMMETERS 0-1, 0-10, 0-15, 0-20 amp. F.R. 2 1/2 in. dia. All at 21/- each.

A.C. VOLTMETERS 0-25 v., 0-50 v., 0-150 v. M.I. 2 1/2 in. Flush round all at 21/- each. P. & P. extra.
0-300 v. A.C. Rect. M-Coil 2 1/2 in. 29/-
0-300 v. A.C. Rect. M-Coil 3 1/2 in. Type W23 25/-



Latest type VARLEY MINIATURE RELAY in Transparent Case. 4 c/o 700 ohm 14/6. Base 4/-, 2 c/o 700 ohm coil, Size 1 1/2 x 1 1/2 x 1 1/2 in. 15/- inc. base. VARLEY TYPE VP4 (similar to illus.), 5,800 ohm. 4 c/o. New 12/6, less base. Similar to above. Mfd. by GRUNER 4 c/o, 2,400 ohm coil. New, 10/-, less base.

UNISELECTOR SWITCHES NEW 4-BANK 25-WAY UNISELECTOR

25 ohm coil, 24 v. D.C. operation. £4/17/6 plus 2/6. P. & P.



8-BANK 25-WAY FULL WIPER

24 v. D.C. operation, £6/10/-, plus 4/- P. & P.

STANDARD SIZE UNISELECTOR SWITCHES USED

75 ohm coil, 24 v. D.C., 6 bank 25 position, 5 non-bridging, 1 bridging wiper. 6 bank arranged to give 3 bank, 50 positions ex-equipment. 35/- each. P. & P. 2/6.

MINIATURE UNISELECTOR SWITCH

3 banks of 11 positions plus homing bank. 40 ohm coil. 24-36 v. D.C. operation. Carefully removed from equipment and tested. 22/6, plus 2/6 P. & P.



AIR BLOWER

Highly efficient blower unit fitted with totally enclosed 200/250 v. A.C. 50 cycles. 3/8 h.p. motor, producing 2,800 r.p.m. outlet 2 1/2 x 1 1/2, used, but in first class condition and tested. Price £3/15/-. P. & P. 7/6d.



AUTO TRANSFORMERS. Step up, step down. 110-200-220-240 v. Fully shrouded. New. 300 watt type £3 each. P. & P. 4/6. 500 watt type £4/2/6 each. P. & P. 6/6. 1,000 watt type £5/5/- each. P. & P. 7/6.

L.T. TRANSFORMERS

Type No.	Sec. Taps	Price	Carr.
1	30, 32, 34, 36 v. at 5 amps	£4/5/-	6/-
2	30, 40, 50 v. at 5 amps	£6/5/-	6/6
3	10, 17, 18 v. at 10 amps	£4/10/-	4/6
4	6, 12, v. at 20 amps	£5/17/6	6/6
5	17, 18, 20 v. at 20 amps	£6/12/6	6/6
6	6, 12, 20 v. at 20 amps	£6/5/-	7/6
7	24 v. at 10 amps	£4/15/-	5/6

ALL MAIL ORDERS. ALSO CALLERS AT:

57 BRIDGMAN ROAD, LONDON, W.4. Phone: 995 1560 Closed Saturdays.

SERVICE TRADING CO.

SHOWROOMS NOW OPEN

Many Bargains for the caller.

AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, W.C.2.

Tel.: GER 0576

Jason KITS

★ TAPE ★

We offer you fully tensilised polyester/nylon and P.V.C. tapes of identical quality high wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. **TRY ONE AND PROVE IT YOURSELF.**

Standard		Long	
3in. 150ft. 2/3	3in. 225ft. 2/9	4in. 300ft. 4/6	4in. 450ft. 5/6
4in. 300ft. 4/6	5in. 900ft. 10/6	5in. 600ft. 7/6	5 1/2in. 1,200ft. 13/-
5 1/2in. 900ft. 10/6	7in. 1,800ft. 18/6	7in. 1,200ft. 12/6	

Double		Triple	
3in. 300ft. 4/-	4in. 900ft. 13/-	4in. 900ft. 13/-	5in. 1,800ft. 25/-
4in. 600ft. 8/-	5in. 2,400ft. 34/-	5 1/2in. 2,400ft. 34/-	7in. 3,600ft. 44/-
5in. 1,200ft. 15/-			
7in. 2,400ft. 27/-			

Postage 1/- reel.
Post Free less 5% on three reels.
Quality and Trade enquiries invited.
NOTE. Large tape stocks at all branches.

UNREPEATABLE ★ SNIPS ★

GARRARD AT6 Mk. II 9 Gns.
GARRARD SRP12 (110/230v.) 59/-
COLLAHO 9 VOLT 49/-
4 SPD. HEAVY T/T LIGHT ALEM (hat 27) (p&p 5/-)
ABOVE LESS CARTRIDGES
Mono. Cart. add 12/6
Stereo Ceramic Cart. add 19/-

AUTOCHANGE PORTABLE CABINETS. As used on 18 gns. record player. Due to fortunate purchase we offer complete with motor board and all fittings at only **49/-**

PLEASE NOTE. A wide range of cabinets to suit all branches.

100 HI-STABS 9/6
1% to 5%, 100Ω to 5 mΩ.

CO-AX low loss, 8d. yd. 25 yds. 12/6, 50 yds. 25/-; HBC2 H/D fringe 1/6 yd. 25 yds. 30/-.

100 RESISTORS 6/6
1/2W 1-3 watt.

MICROPHONE CABLE. Highest quality, black, grey, white, 1/- YD.

100 CONDENSERS 9/6
Miniature Ceramic, Silver, Mica, etc. 500 to 5µF. LIST VALUE OVER 24.

LATEST GARRARD (POSTAGE 5/-)

IRP12	£4.70
SRP25 (De Luxe Die Cast)	£5.10.0
SRP25	£5.10.0
Model 50	£5.10.0
Model 1,000	£6.5.0
Model 2,000	£6.10.0
Model 3,000	£6.10.0
Lab 80 Mk. II	£11.11.0
A70	£13.10.0
LAB 80 Mk. II	£24.10.0
401	£27.10.0
ER60 Stereo Ceramic Cartridge	24/-

PLINTHS
Teak de luxe finish cut out for SP25. Model 50, 1,000, 2,000, 3,000
A70
Ditto, super Perspex clear cover, complete £5.15.0
Lab 80, 401, A70, Superb new hinged lid, teak and Perspex plinth (List £12.10.0) £9.19.0

Transistorised FM Tuner

Demonstration without obligation at all branches



Postage 2/-

This beautiful compact 6 transistor machine (size 6 x 4 x 2 1/4 in.) will give quieter, more interference free reception. Months of use from a standard 9 volt battery or its small power requirements can be drawn from any amplifier. Low noise frequency changer with smooth 2 kHz tuning leading no less than three I.F. stage, coupled to a double-tuned discriminator terminating in an L.P. stage giving ample output for all quality amplifiers.

TRADE QUANTITY QUOTATIONS

**Order now!
£6-10**

HUGE DEMAND ENABLES PRICE REDUCTION

CALLERS A very wide range of electronic components stocks at all branches. Your enquiries welcomed.

TECHNICAL TRADING

All Mail Orders to Brighton please

SILICON H.T. RECTIFIERS

Guaranteed performance. Top makes. Tested 250 v. working
120 mA 2/9
(3 for 5/6)
500 mA 7/6
(3 for 19/6)

HEAVY DUTY 14/20 watt AMPLIFIER KITS
Famous make consisting integrated controls, high/low gain preamp stages leading EL34 Push Pull Output, C core transformers, complete with instructions down to the last bolt. Current model at fraction of list price. **8 1/2 Gns.**


★ LONDON—10 Tottenham Court Rd. Tel: MUS 2639
★ PORTSMOUTH—350-352 Fratton Rd. Tel: 22034
★ SOUTHAMPTON—72 East St. Tel: 25851
★ WORTHING—132 Montague St. Tel: 25851
★ BRIGHTON—Devonian Court, Park Crescent Place
All Mail Order (24-hour Robophone) Brighton 680722

(Please note Postage extra on all items)

FREE FLOG LIST NO 2

SEND S.A.E. OR CALL AT ANY BRANCH FOR YOURS

Scores Special Bargains



NEW FROM ILIFFE

“Unitech Outlines”

the highly successful American series
of paperback technical titles are now available from ILIFFE

First 8 titles

OUTLINE OF ELECTROMAGNETIC THEORY	M. Zaret, Ph.D.
OUTLINE OF ELECTRONIC CIRCUIT ANALYSIS	A. R. Cohen, Ph.D.
OUTLINE OF LINEAR CIRCUITS AND SYSTEMS—Part I	A. R. Cohen, Ph.D.
OUTLINE OF PULSE CIRCUITS	C. H. Houppis, M.S.
	and J. Lubelfeld, Dipl. Engr. (Telecomm.)
OUTLINE OF SERVOMECHANISMS	S. A. Davis, M.E.E.
OUTLINE OF TRANSISTOR CIRCUIT ANALYSIS	A. Gronner, M.E.E.
OUTLINE OF ATOMIC PHYSICS	S. E. Liverhant, Ph.D.
OUTLINE OF FOURIER ANALYSIS	Hwei T. Hsu

Each volume 35s. net
from leading booksellers Postage 1s. 4d.

ILIFFE BOOKS LTD.
DORSET HOUSE
STAMFORD STREET
LONDON, S.E.1

WW—142 FOR FURTHER DETAILS

CONVECTOR HEATER



Just screw it together. Uses 1,260 watt copper clad element which gives you black heat. Will last a lifetime. Ideal for bedroom. It's so safe. Complete in crackle finished case. 29/6. easily worth double. Carriage & ins. 3/6.

MINIATURE WAFER SWITCHES



4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control, 10/- post free.



G.E.C. 13 amp SWITCHED SOCKET

An excellent opportunity to re-equip your workshop, or if you are a contractor to restock for future ring main jobs. We offer 12 GEC switch sockets, Brown Bakelite surface mounting. Latest ring main type listed at 6/6 each. You can have a box of 12 for 30/- only—thus showing you a saving of 22/8/-. Postage and insurance 4/6 extra.

FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. 19/6. Kit B—30-40 w. 17/6. Kit C—80 w. 17/6. Kit D—125 w. 22/-. Kit E—65 w. 19/6. Kit MF1 is for 6in., 9in. and 12in. miniature tubes 19/6. Postage on Kits A and B 4/6 for one or two. Kit D and E 4/6 on first kit then 3/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each kit ordered.

GANGED POTS

Standard type and size with good length of spindle—made by Mor-ganite. List price is 10/- each but if you act quickly you can have them at 12/- doz. (or 1/6 each if less than doz.). Following valves in stock all "lin"—100K+100K—500K+500K all new and unused. Post 2/9 on 1st doz. then 1/- per doz. 6 doz. or more post free.



HURSEAL AUTOMATIC TIME SWITCH

12 hour, 15A to control heating, lighting, radio, immersion heaters, etc. Regular price 24/4/- Limited quantity 39/6. P. & F. 3/-.

HI-FI SPEAKER BARGAIN

12in. High fidelity loud-speaker. High flux permanent magnet type with either 3 or 15 ohm speech coil. Will handle up to 10 watts. Brand new by famous maker. Price 29/6. With built-in Tweeters 35/6, plus 3/6 post and insurance.



MAINS RELAYS

Type A. 210/250V. A.C. coil, 2 types, one for single hole chassis mounting, has 3 pairs heavy duty changeover contacts, 8/6 each.
Type B. In clear plastic case on tin base, plugs into octal valve holder. 2 pairs changeover contacts, 12/6 each.

COPPER CLAD ELEMENT

1,260 watts—4ft. long but bent to U shape, ideal for overhead heater—just mount reflector above. 12/6 each plus 4/6 post. 26 doz. post paid.

MAINS TRANSFORMER. Upright mounting with primary tapped 200, 220, 240 v. H.T. secondary w 250-0-250 v. at 80 mA. and it has two L.T. secondaries of 6.3 v. 1j amp.—unused (removed from equipment), 15/- plus 3/6 post and insurance.



PP3 Eliminator. Play your pocket radio from the mains! Save 6s. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions. Only 6/6 plus 1/- post.

Where postage is not definitely stated as extra then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

INFRA-RED HEATERS



Make up one of these latest type heaters. Ideal for bathroom etc. They are simple to make from our easy-to-follow instructions—uses silica enclosed elements designed for the correct infra-red wave length (2 microns). Price for 750 watts element, all parts metal casing as illustrated. 19/6, plus 3/6 post and ins. Full switch 3/- extra.

DRILL CONTROLLER



CONTROL DRILL SPEEDS

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-clip control. Kit includes all parts, case, everything and full instructions 19/6, plus 2/6 post and insurance. Or available made up 32/6.

THIS MONTH'S SNIP INTERCOM BARGAIN



Will save time and improve efficiency. Ideal in home—office—shop—surgery, etc. Complete outfit comprises Master unit and three substations each of which can call the master and have full two-way working. No wiring problems as subs fitted with 60ft. twin flex and they plug into sockets. Also included is packet of staples—and battery. Nothing else to buy. 24/19/6 plus 4/6 post and insurance.

GARRARD AUTO RECORD PLAYER Model 2000



This is one of the latest products of the World's most experienced maker of fine record reproducers. Its superior features include—automatic playing of up to 8 mixed size records—stopping and starting without reejecting—manual playing—pick-up pivots to give—manual turntable for max. stability adjustment

low stylus pressure—large diameter turntable for dropping position and stylus pressure. Size is 13 1/2 x 11 1/2 in. clearance 4 1/2 in. above 2 1/2 in. below—fitted with latest hi-compliance cartridge for stereo—and mono. L.P. and 78. Supplied complete with mounting template and service sheet. Offered this month at the Special Snip price of 26/19/6 plus 7/6 carriage and insurance.


THE VECTRONOME CAPSTAN DRIVEN TAPE RECORDER



This is a truly portable, self-contained instrument with built-in microphone and loudspeaker using a 5-transistor amplifier with P.P. output and suitable for operation from mains or by chargeable batteries. Tape capacity is 25 minutes on easily changed spools. A tape position indicator gives quick reference to any part of dictation. Recording level is automatically preset during dictation and can be adjusted to suit operator. Interlock prevents unintentional erasures. Tape speed controlled by fly wheel driven capstan. Very portable in neat case with carrying handle, overall size of which is approximately 8 1/2 x 7 1/2 x 2 1/2 in. with tape, nickel cadmium re-chargeable batteries and mains battery charger 29/19/6 (rather less than one-third original price). Postage and insurance 7/6. Unused and in perfect working order.

RADIO STETHOSCOPE

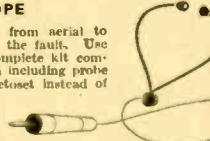Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece 29/6—twin setcase instead of earpiece 7/6 extra—post and ins. 2/9.



THE "TECHNICAL" RECORD PLAYER

4 speed, gram. motor with light weight pick-up, motor electronically balanced and free from wow and flutter. Speed change by push button—16, 33, 45, 78 r.p.m. Price 39/6, 2 Valve amplifier 32/6. Elliptical Speaker 9/6. Cartridge extra mono 10/6, stereo 15/6—plus 4/6 post and insurance. DON'T MISS THIS TERRIFIC BARGAIN.



TUBULAR HEATERS

New and unused made by G.E.C.—rated at 60 watts per ft.—these are ideal in airing cupboards, bedrooms, offices, stores, greenhouses, etc., curtains or papers can touch them without fear of scorching or fire. Supplied complete with fixing brackets and available in the following sizes. Prices which are about 1/2 of list price include carriage by B.R.S. 8ft. 30/- 10ft. 36/- 12ft. 42/- Also in twin assemblies (one pipe above the other), 4ft. 40/- 5ft. 46/- 6ft. 52/-.

FLOOD LAMP CONTROL

Our dim and full switch is ideal for controlling photo flood lamps; it gives two lamps in series, two lamps full brilliance and lamps off. Similar control of other appliances can be arranged where used in pair or where circuit can be split exactly in half. Technically the switch is known as a double-pole change over with out. Our price 4/6.



MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA. (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP5, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, 5,000 and 500 nfd. condensers, Zener diode and instructions. Ideal snip at only 16/6, plus 3/6 postage.

DOOR INTERCOM

Know who is calling and speak to them without leaving bed, or chair. Outfit comprises microphone with call push button, connectors and master inter-com. Simply plug together. Originally snip at £10. Special snip price 79/6, plus 3/6 postage.




GEARED MOTOR

HALF REV. PER MINUTE
Made by famous Smith Electric, mains operated and quite powerful. Size 3 1/2 x 2 1/2 x 1 1/2 in. deep. Secondary use as process timer. Internal switch can be made to break circuit within a period up to 2 mins. 17/6. P. & F. 2/6 unless ordered with other goods.



MAINS MOTOR

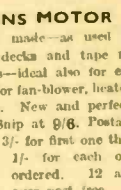Precision made—as used in record decks and tape recorders—ideal also for extractor fan-blower, heater, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.



RELAY SWITCHES. These enable micro switches, delicate thermostats or other low current devices to control up to 30 amps.—ideal to switch thermal storage heaters—motors, etc., made by the famous A.E.I. group these are listed at 22s each—you can buy if you hurry at a very keen price of 39/6 each and we will include diagram and data. Mounted on panel size approximately 6 x 7 x 2 in. deep.

THERMOSTATS

Type "A" 10 amp. for controlling room heaters, greenhouse, airing cupboard. Has spindle for pointer knob. Quickly adjustable from 50-50°F. 9/6 plus 1/- post. Suitable box for wall mounting 5/- . P. & F. 1/-.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-55°F. Internal screw alters the setting so this could be adjustable over 30° to 100°F. Suitable for controlling furnace, oven kiln, immersion heater or to make flame-start or fire alarm. 8/6 plus 2/6 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point, 2/3 amps. Has many uses, one of which would be to keep the loft pipes from freezing. If a length of our blanket wire (16 yds, 10/-) is wound round the pipes. 7/6. P. & F. 1/-.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperatures, 7/6, plus 1/- post.

Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developed and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/-, plus 2/- post and insurance.

ELECTRONICS (CROYDON) LIMITED
(Dept. W.W.), 102/3 TAMWORTH RD., CROYDON, SURREY (Opp. W. Croydon Stn.)
S.A.E. WITH ENQUIRIES PLEASE
also at 266 LONDON ROAD, CROYDON, SURREY.

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS

Heavy cast construction. Latest high efficiency ceramic magnets. Treated cone surrounds giving low fundamental resonance. "D" indicates Tweeter. Cone providing extended frequency range. Impedance 3 or 15 ohms. Response 40-18000 c.p.s. Highly recommended models capable of outstanding results. Exceptional value.

HF510 8in. 8 watt £2 9 9 HF120 12in. 15 watt £3 9 9
 HF600 8in. 8 watt £2 19 9 HF120D 12in. 15 watt £3 19 9
 HF810 8in. 10 watt £4 19 9 HF138 12in. 15 watt £4 9 9
 HF101D 10in. 15 watt £5 19 9 HF180 12in. 15 watt £5 9 9

SENSATIONAL VALUE IN HIGH FIDELITY STEREO SYSTEMS

Extremely attractive cabinets finished in Teak, Satin Teak or Walnut Veneer. Finished Perspex "hinged" lid Special Inclusive Price

69 Gns. Carr. 35/- Fully wired consisting of (1) The very latest Garrard SP25 Mk. II PLAYER UNIT 4-speed with heavy turntable, HYDRAULIC LOWERING device, etc., etc. Fitted CS 90 P.U. Cartridge. Ready wired on Plinth (baseboard) Fitted plugs for instant use.



Inc. Garrard SP25 Mk. II 4-speed Player Unit (with heavy cast turntable mounted on plinth with leads and plugs and fitted Goldring CS90 high compliance ceramic cartridge with diamond stylus. Assembled TA12 Stereo Amplifier in cabinet and pair of Dorset Speaker Units. Total if purchased individually £67. Special inclusive price for above 46 Gns. Carriage 25/- only. Or Dep. £6/9/3 and 9 mthly. payments £5/5/2 (Total £58/14/9)

RECORD PLAYING UNITS

All types available on Credit Terms. Ready for plugging in to Amplifier or Tape Recorder.

RP2 Consisting of Garrard SP25 Mk. II with heavy cast turntable and fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Plinth 22 Gns. and cover. Normally approx. £26. Carr. 10/- ONLY

RP3 As above but with Goldring Lenco (L68 Transcription unit and CS90 Cartridge. 27 1/2 Gns. Normally approx. 32 gns. Carr. 15/- ONLY

RP3M with Pickering Magnetic Cartridge. 35 1/2 Gns. Normally approx. 39 gns.

AUDIOTRINE PLINTHS
 For Record Playing units. Teak finish. cut for Garrard. 1,000, 2,000, 3,000 RPM Mk. II AT90. SP25 or Goldring O168. Available with clear Perspex cover as illustrated. 66/£5/19/11 complete. Carr. 8/6 or slightly deeper type cut for TA12 but suitable for Super 15 and 30. £6/15/11 inc. cover. Perspex cover sold separately at 3 Gns. Lintex number, slightly damaged but repaired by manufacturer. 39/9 to clear.

LINEAR TAPE PRE-AMPLIFIER Type LP/1
 Switched Equalisation. Positions for Recording at 1 1/2, 3 1/2, 7 1/2, per sec. and Playback. EM54 Recording Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and Hi-Fi amplifier suitable most 10 1/2 Gns. Tape Decks. Terms available.

HIGH FIDELITY LOUDSPEAKER UNITS
 Cabinets of latest styling Satin Teak or Walnut, acoustically lined (and ported where appropriate). Credit Terms available

DORSET Size 16 x 11 x 9in. Response 45-18,000 c.p.s. Rating 8-10 watts. Fitted Audiotrine HF910D speaker. £8.19.9 or 3 or 15 ohms.

DORCHESTER Size 24 x 15 x 10in. Fitted Audiotrine HF101D Speaker. Rating 15 watts. Impedance 3 or 15 ohms. Frequency response 30-20,000 c.p.s. 12 1/2 Gns.

GLOUCESTER Size 25 x 16 x 10in. 12in. High flux, 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Smooth response 40-20,000 c.p.s. Impedance 15 ohms. Outstanding value. 12 1/2 Gns.

STANTON Mk. III Size 18 x 11 x 10in. Rating 10 watts. Incorporating Audiotrine HF810D Speaker with rolled rubber surround, 15,000 lines. Handsome Scandinavian design cabinet. Response 30-20,000 c.p.s. Impedance, 3 or 15 ohms. Fitted Tweeter. The deep excursions of the cone produce powerful bass notes. Excellent response ensures smooth realistic output. 15 Gns.

TA6 6 WATT HIGH FIDELITY SOLID STATE AMPLIFIER

Employing latest type Transistors. 200-250 v. A.C. mains operated. Frequency Response 30-20,000 c.p.s. -2dB Harmonic Distortion 0.3%. At 1,000 c.p.s. Separate Bass and Treble "lift" and "cut" controls. 3 input sockets for Mike, Gram, Radio or Tape Input Selector Switch. Output 3-15 ohm speakers. Max. Sensitivity 5mV. Fully enclosed enamelled case. 9 1/2 x 2 1/2 x 5 1/2in. Attractive brushed silver finish face plate 10 1/2 x 3 1/2in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. Complete factory built with 12 mths. guarantee. Post paid 8 gns. Carr. 7/6. 6 Gns.

HI-FI LOUDSPEAKER ENCLOSURES

All types of pleasing modern design, acoustically lined and ported and beautifully finished in light Teak or Walnut veneer.

JES. Size 20 x 11 x 8in. Gives pleasing results with any 8in. Hi-Fi speaker. 4 Gns.

SE8. For optimum performance with any Hi-Fi 8in. speaker. Size 22 x 15 x 9in. 5 Gns.

SE10. For 10in. Hi-Fi Speaker. Size 24 x 15 x 10in. 6 Gns.

SE12. For outstanding performance with any 12in. Hi-Fi speaker. Cut for tweeter. Size 25 x 16 x 10 1/2in. 7 Gns.

ALL LEADING MAKES HI-FI EQUIPMENT AND FURNITURE IN STOCK

VERDIK High Fidelity Amplifiers
 Mullard 510 circuit. Separate Pre-amp and Power amp. List 18 Gns. Limited number at only 12 Gns.

MAGNAVOX 3-SPEED TAPEDECKS WITH MATCHING 5 WATT HIGH QUALITY A.C. MAINS RECORD/PLAYBACK AMPLIFIER

For 3 ohm speaker. Switched equalisation for each speed. Magic Eye Recording level indicator. 2 TRACK 24 Gns. 4 TRACK 27 Gns.


R.S.C. TFM1 TRANSISTORISED VHF/FM RADIO TUNER

Total cost of parts with detailed wiring diagrams and instructions. Carr. 10/- 12 1/2 Gns.

Or factory built 151 Gns. Or in Teak finished cabinet as illustrated 19 Gns. Terms: Deposit £5 matching our Super 15 and 30 amplifiers and 9 monthly payments 39/- Total £22/11/-.

R-S-C TA12 13 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED. SOLID STATE CONSTRUCTION. HIGH FIDELITY. OUTPUT OF 6.5 WATTS PER CHANNEL. Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio, Tuner, Tape Recorder, Mike, etc. 3 separate switched input sockets on each channel. Separable Bass and Treble controls. Slide Switch for mono use. Speaker Output 3-15 ohms. For 200-250 v. A.C. mains. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise -70dB. Sensitivity (1) 300mV (2) 100mV (3) 100mV (4) 2mV. Handsome brushed silver finish face and knobs. Complete kit of parts with full wiring diagrams and instructions. 11 Gns. Carr. 7/9. Factory built with 12 months guarantee. £14/19/9. £16/14/- Total finished cabinet as illustrated £3/13/6 extra. Or larger size as used in Stereo System 86/6.

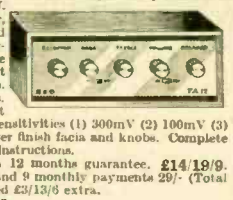

R.S.C. HIGH FIDELITY SPEAKER SYSTEMS

Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker, cross-over unit and Tweeter. Smooth response and extended frequency range ensure surprising realistic reproduction. Standard 10 watt rating. Or Senior 15 watt 5 Gns. Inc. Audiotrine HF 126 speaker. 6 Gns. Carr. 6/6.

FR3 3 SPEAKER SYSTEM Carr. 5/9
 Inc. Audiotrine HF126, 12in. Bass unit, with 16,000 line magnet. 5in. 10 watt 11,000 line mid-range speaker HF 510M. High Flux 4in. Tweeter. Cross-over units for mid- and high-frequencies and circuit. Housed in suitable cabinet will provide quality comparable with very expensive units. Rating 15 watts. Impedance 15 ohms. 9 Gns.

AUDIOTRINE HIGH FIDELITY MODULES Model MT 34
 Consisting of HF 510M Mid-range speaker, Tweeter and Cross-over used in FR3 3 Speaker system above mounted on baffle board 10 1/2 x 5 1/2in. wired and ready for connecting across a 12in. 15 ohm speaker. £5.15.0 Carr. 6/6

MODEL FR 12/54 This is the FR 3 3 speaker system fully wired and mounted on baffle board 12 1/2 x 17 1/2in. 10 Gns. Carr. 10/6.

LINEAR SOLID STATE HI-FI AMPLIFIERS IN STOCK

★ High Sensitivity. ★ 200-250 v. A.C. Mains operation. ★ Sharp A.M. Rejection. ★ Drift free reception. ★ Output ample for any amplifier (approx. 500 mv.). ★ Simple alignment instructions. ★ Output available for feeding tuning meter. ★ Output for feeding Stereo Multiplexer. ★ Tuner head using Silicon Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Visually and of the same high standard of performance reliability. The pre-wired tuning head facilitates speed and simplicity of construction. Printed circuitry. Only first grade components used. A quality product at half the cost of comparable units. Stereo version available. All parts 19 1/2 Gns. Assembled 25 1/2 Gns. In cabinet 29 Gns. Carr. 10/-.

R.S.C. SUPER 15 HI-FI AMPLIFIER R.S.C. SUPER 30 STEREO AMPLIFIER

FULLY TRANSISTORISED 200/250 v. A.C. Mains. OUTPUT 10 WATTS R.M.S. cont. into 15 ohms. 15 WATTS R.M.S. cont. into 3-4 ohms. LATEST TRANSISTOR TRANSFORMERS. AD149. AD149. OC127Z. OC281Z. OC34. OC44. OC48Z. OC54. AC107. 5 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES SENSITIVITY: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5mV. Radio/Aux. or Ceramic P.U. 110mV. FREQUENCY RESPONSE: ±2 dB 20-20,000 c.p.s. TREBLE CONTROL: +15dB to -14dB at 10 Kcs. NEG. FEEDBACK: 62dB. BASS CONTROL: +12dB to -15dB at 60 cps. HUM LEVEL: 70dB. HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.25%. Carr. 19/6. Complete kit of parts with full constructional details and point to point wiring diagrams. Supplied factory built 15 1/2 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18/3/9). Or fitted in beautiful walnut or Teak veneered cabinet as illustrated 4 Gns. extra. ALL COMPONENTS, ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING BRITISH MANUFACTURERS.

SOLID STATE CIRCUITRY

THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Dynamic or Ribbon) CURRENTLY AVAILABLE - SPECIFICATIONS COMPARABLE WITH UNITS AT ALMOST TWICE THE COST

A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuits. Close tolerance Ganged Pots. Matched Components. CROSS TALK: -62dB at 1,000 c.p.s. CONTROLS: 5 position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch. INPUT SOCKETS (Matched Pairs). (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone. Operation of the Input Selector Switch assures appropriate equalisation. High 18 s.w.g. Chassis. Size approx. 12in x 3 1/2in x 8in. Neon Panel Indicator. Attractive Face Plate and Brun Silver Matching Knob. Above facilities, except for Ganging and Balanced Control, apply also to Super 15. SUPER SOUND OUTPUT CAN BE OBTAINED BY USING THESE UNITS WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts, point to point wiring diagrams and detailed instructions. Carr. 15/- 19 Gns. Unit factory built with 12 months full guarantee 281 Gns. or deposit £8/2/- and 9 monthly payments 50/- (Total £30/17/-). Fitted cabinet as Super 15 30 Gns. Carr. 15/- or deposit £8/2/6 and 9 monthly payments 64/- (Total £34/18/6).

- BRADFORD** 10 North Parade (Half-day Wed.) Tel. 25349
- BIRMINGHAM** 30 1/2 Lower Castle St. (Half-day Wed.) Tel. 22904
- BIRMINGHAM** 30 1/2 Lower Castle St. Western Arcade opp. Snow Hill Station 021-236 1279. No half-day
- DERBY** 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON** 13 Post House Wynd (Half-day Wed.) Tel. 680-43
- EDINBURGH** 133 Leith Street (Half-day Wed.) Tel. Waverley 5766
- GLASGOW** 326 Argyle St. (No half-day) Tel. City 4158 403 Sauchiehall St. (Opp. Locarno) Tel. 332 1572
- HULL** 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: 102 Henconner Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2, 5/9 extra under £5. Trade supplied. S.A.E. with enquiries please. H.P. CATALOGUE 4/8. Open all day Sat. except High Holborn branch.

- LEICESTER** 32 High Street (Half-day Thurs.) Tel. 56420
- LEEDS** 5-7 County (Mecca) Arcade Brigate (No half-day) Tel. 28252
- LIVERPOOL** 73 Dale St. (No half-day) Tel. CENTRAL 3573
- LONDON** 238 Edgware Rd., W2 (Half-day Thurs.) Tel. PAD 1629
- LONDON** 96 High Holborn, WC1 Tel. HOL 9874 (Half-day Sat.)
- MANCHESTER** 60A-60B Oldham St. (No half-day) Tel. CENTRAL 2778
- MIDDLESBROUGH** 106 Newport Rd (Half-day Wed) Tel. 47096
- NEWCASTLE UPON TYNE** 41 Blackett St. Opp. Fenwicks Store (Half-day Wed.) Tel. 21469
- SHEFFIELD** 13 Exchange Street, Castle Market Bldgs. (Half-day Thursday) Tel. 20716



R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

5 watts high quality output on each channel. Sensitivity 50 millivolts. Suitable all crystal or ceramic stereo heads. Ganged Bass and Treble Controls. Valve line-up ECC83, ECC83, EL84, E281. For 2-ohm speakers. **£8.15.0**

Complete kit, with full wiring diagrams and instructions. Carr. 10/-
Or supplied factory assembled with 12 months' guarantee for 11 gns. Terms: Dep. 3 gns. and 9 monthly payments 22/9 (Total £18/7/6). Carr. 11/6.

LOUDSPEAKER CORNER CONSOLE CABINETS. Attractive design with polished walnut finish. Model 8 for 12" speaker and M for 10" speaker. Size 28x19x12in. **59/11** Model 8 for 12" speaker and M for 10" speaker. Size 28x19x12in. **59/11** Model 8 for 12" speaker and M for 10" speaker. Size 28x19x12in. **5 Gns.**

BASS REFLEX CABINETS FITTED HI-FI 8in. LOUDSPEAKER
Limited number. Finish imitation walnut. Provides excellent reproduction. Peak rating 10 watts. Response 45-15,000 c.p.s. Optional **7 Gns.** Carr. 8/6. 3 ohm or 15 ohm impedance. Size approx. 17 x 12 x 9ins.

R.S.C. STEREO/20 HIGH FIDELITY AMPLIFIER

PROVIDING 10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL SUITABLE FOR "MIKE", GRAM., RADIO OR TAPE 7 Valves ECC83 (2), ECL86 (4), E281. Frequency Response: ±2dB 30-20,000 c.p.s. Hum Level: 45dB down. Sensitivity: 20 millivolts max. Harmonic Distortion: (each channel): 0.2%. ★ Frequency tone compensation and Input Selector Switch. ★ Stereo/Mono switch. ★ Neon panel indicator. ★ Handsome Perspex Frontplate. ★ Separate push-button controls. ★ Point-to-point wiring diagrams. Carr. 12/6. Outputs for 3 and 15 ohm speakers. Or factory assembled, with our usual 12 months' guarantee **19 gns.** Carr. 12/6. Or send Dep. **£4/10/0** and 9 monthly payments of **£2** (Total **£22/10/0**). Send S.A.E. for leaflet.



R.S.C. A10 HIGH FIDELITY 30 WATT AMPLIFIER

Highly sensitive. Push-Pull high output, with Harmonic/Tone Control Stages. Performance figures equal to most expensive amplifiers available. Hum level -70dB. Frequency response ±3dB 30-20,000 c.p.s. Specially designed sectionally wound ultra linear output transformer with 10 output valves. All first grade components. Valves ECC83, ECC83, 6X4, 6X4, 6X4. Separate Bass and Treble Controls. Sensitivity 12 millivolts so that any kind of Microphone or Pick-up is suitable. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc., Gram., Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram. and "Mike" can be mixed. **290-250 v. 12 Gns.** Carr. 12/6. Output for 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. **12/6** Supplied factory built with ECL84 output valves. 12 months' guarantee for 15 gns. Terms: Deposit **£4/13/0** and 9 monthly payments of **£2/9** (Total **£17/11/0**). Twin-handled perforated cover can be supplied for 25/-. Send S.A.E. for leaflet.

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with associated controls allow mixing of "Mike" and gram. etc. High sensitivity. Valves ECC83, ECC83, EL84, EL84, E281. High quality sectionally wound output transformer and manufacturer's INDIVIDUAL CONTROLS FOR Musical Instruments such as String Bass, Electronic Organ, etc. Reserve Power 300 v. 30 mA. and 6.3 v. 1.5 a. for Radio Tuner or Tape Pre-Amp. Size approx. 12 x 9 in. For A.C. mains 200-250 v 50 c.p.s. Output for 3 and 15 ohm speakers. Complete kit. Full instructions and comprehensive wiring diagrams. **£8.15.0** (Carr. 11/6). S.A.E. for leaflet. TERMS: Deposit **72/6** and 9 monthly payments of **£2/-** (Total **£13/10/6**). Twin handled metal cover available at 25/- extra.

R.S.C. A11 TRANSISTORISED VERSION of above Complete Kit **9 Gns.** Carr. 9/6

TWO-WAY TELEPHONE AMPLIFIERS only **£3.19.9**

Dry hat. operated. Listen and talk back with both hands free. A handsome, highly efficient Japanese product.

R.S.C. 4 watt GRAM AMPLIFIER KIT

Complete set of parts to build a good quality compact unit suitable for use with any record playing unit. Mains isolated chassis. Separate Bass and Treble controls. Output for 2-ohm speaker. For 200-250 v. A.C. **59/11**

SELENIUM RECTIFIERS F.W. (Bridged)

All 6/12 v. D.C. output. Max. A.C. input 18 v. Ia. 3/11. 2a 8/11. 3a 9/8. 4a 12/8. 6a. 15/8. 10a. 25/9. 24v. 15a. 35/8.

POWER PACK KIT Consisting of mains transformer. Metal Rectifier, electrolytics, smoothing choke, chassis and circuit, 200/250 v. A.C. mains. Output 250 v. 60 mA. 6.3 v. 2a. Supplied with case in lieu of chassis **26/11**. Or **22/11** assembled **39/11**.

R.S.C. BATTERY MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 approx. Completely replaces batteries supplying 1.5 v. and 90 v. where A.C. mains 200-250 v. 50 c.p.s. is available. Complete kit with diagram **47/9** or ready for use **59/11**.

R.S.C. 6/12v CAR BATTERY CHARGER KITS

For 200-250 v. A.C. mains with variable charge rate selector. Complete kit with Ammeter and circuit. **4 amp 49/9. 6 amp Heavy Duty 69/9** All types factory built 10/- extra.

GLASGOW - LONDON

New branches open. See opposite page

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair Ideal for vocalists and Public Address. 15 ohm matching. Type C48. 25-30 WATTS. Fitted four 7 1/2 inch high 7 watt speakers Overall size approx. 42 x 10 x 5in or Desktop 44/- and 15 Gns. monthly payments 34/9. Carr. 10/-. (Total £18/1/6). Type C412. 40 WATTS. Fitted four 12in. 12,000 line 10 watt speakers Overall size approx. 56 x 14 x 9in. Carr. 13/-. Or Deposit £3/13/- and 9 monthly payments of 50/- (Total £26/8/-).

12in. HIGH QUALITY L'SPEAKERS in teak veneered cabinets.

10 Watt Model. Gauss 12,000 lines. 3 or 15 ohms. **5 Gns.**
20 Watt Model. 15 ohm. Size 18x18x10in. Gauss 12,000 lines. **8 Gns.**
Terms available
Rexine covered 10/- extra.
30 Watt Model. Rexine covered **10 gns.**

LOUDSPEAKERS Limited number on fraction

pedance. Brand new, guaranteed. Terms available.
12in. 20 WATT DUAL COLE £5.11.9 Carr. 6/9.

12in. 30 WATT DUAL COLE £6.19.9 Normally £13 approx. Carr. 10/-
15in. 40 WATT Carr. 13/- 12 Gns. Massive units. Usually 16 gns.

FANE 18in. 100 WATT SPEAKER

Specially constructed for tremendous power handling. Peak 200 watts. Guaranteed 2 years. **19 Post free**

TRANSISTOR SALE until Oct. 7, Oct. 22, Oct. 29, 7/9. A.P.17 6/9. Post 6d. for 3.

FM DIAL & DRIVE ASSEMBLIES 13/9

STAR 9v. GRAM TURNABLES 3 Gns. 2-speed, 33 and 45 r.p.m. with pick-up.

R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primaries 200-250v. 50c/s. Screened. MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in. 250v. 60mA. 6.3v. 2a. 14/1
250-0-250v. 60mA. 6.3v. 2a. 15/1
FULLY SHROUDED UPRIGHT MOUNTING
250-0-250v. 100mA. 6.3v. 2a. 0-5-0.3v. 2a. 18/1
250-0-250v. 100mA. 6.3v. 2a. 0-5-0.3v. 2a. 23/1
300-0-300v. 100mA. 6.3v. 2a. 0-5-0.3v. 2a. 33/1
300-0-300v. 130mA. 6.3v. 2a. c.t. 6.3v. 1a. 41/1
For Mullard 510 Amplifier
350-0-350v. 100mA. 6.3v. 2a. 0-5-0.3v. 2a. 33/1
350-0-350v. 100mA. 6.3v. 2a. 0-5-0.3v. 2a. 37/1
420-0-420v. 200mA. 6.3v. 2a. c.t. 5v. 3a. 67/1
420-0-420v. 200mA. 6.3v. 2a. d.3v. 4a. 6v. 3a. 69/1
450-0-450v. 250mA. 6.3v. 2a. c.t. 6v. 3a. 79/1
TOP SHROUDED DROP-THROUGH TYPE
250-0-250v. 100mA. 6.3v. 2a. 0-5-0.3v. 2a. 19/1
250-0-250v. 100mA. 6.3v. 3.5a. 21/1
250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a. 22/1
350-0-350v. 80mA. 6.3v. 2a. 0-5-0.3v. 2a. 22/1
250-0-250v. 100mA. 6.3v. 2a. 0-5-0.3v. 2a. 32/1
300-0-300v. 100mA. 6.3v. 2a. 0-5-0.3v. 2a. 32/1
300-0-300v. 150mA. 6.3v. 2a. 0-5-0.3v. 1a. 32/1
Suitable for Mullard 510 Amplifier... 39/6
350-0-350v. 100mA. 6.3v. 2a. 0-5-0.3v. 2a. 32/1
350-0-350v. 150mA. 6.3v. 2a. 0-5-0.3v. 2a. 36/11
FILAMENT or TRANSISTOR POWER PACK Type 6.3v. 1.5a. 6/9. 6.3v. 2a. 7/9. 6.3v. 3a. 9/8. 6.3v. 5a. 10/9. 12v. 1a. 8/9. 12v. 2a. 10/9. 12v. 3a. 12/9. 12v. 397a. 800/9. 12v. 398a. 802/9. 12

USED SCIENTIFIC EQUIPMENT

High Vacuum Pumps from $\frac{1}{4}$ to 120 c.f.m., diffusion pumps from 1in.-9in., gauges and accessories, etc.	P.O.A.
Air Liquefier. Phillips PW 2000/25. 4 litres/hour. As new	£1,000
Induction Heater from 1 kW at £180 to 6 kW. and higher, from Dielectric Heater. Pye 12 kW, 27 Mc/s., £450. Redifon 4 kW. 10 Mc/s.	£300
Inspection Enlarger. Hilger X50	£120
PH Meter. EIL continuous reading, as new, 0-14 PH	£120
Recording Polarograph. Cambridge	£250
Sedimentation Balance. Gallenkamp PC650	£100
Centrifugal Sediometer. Gallenkamp PC700	£125
End Runner. Pascal 10in., little used	£80
Tube Furnace. 2in. x 12in., controlled atmosphere 1,000°C.	£250
Chart Recorders, Pyrometers and Controllers. All types and sizes, from	£25-£200
High Precision Potentiometer. Cambridge Standard Instrument, measures up to 48 v. X 0.0001 volts	£450
High Voltage Pulse Generator. 10 kV. 600 m.a. DC supply with delay lines, chokes, etc., 2 Micro sec., 6 microsec., 10 microsec.	£400
Thermocouple Amplifier. Barr & Stroud with PSU	£120
Radio Isotope Container. Pantatron CR2	£240
Geiger Muller Tubes. BF3 tubes, etc.	P.O.A.
Spot Welder. Bench Mounted, £75, and others for mounting.	
Variable Transformer. Motor driven, 3 phase 10 kW., Berco...	£45
Various chassis, cabinets, laboratory equipment, etc., etc.	

ASK FOR CATALOGUE.

V. N. Barrett & Co. Ltd.,
286a, Lower Addiscombe Road, Croydon
CR0 7AB 01-654-6470

WW-145 FOR FURTHER DETAILS

SUPER QUALITY NEW RESISTORS

High Stability **Carbon Film** **Low Noise**
 $\frac{1}{4}$ W 5% E24 series, 5.1 Ω to 330k Ω , 1/10 doz. mixed; 14/6 100 mixed; 13/100 in 100's of one ohmic value.
 1 Ω to 4.7 Ω available, 1d. extra per resistor.
 $\frac{1}{2}$ W 10% E12 series, 4.7 Ω to 10M Ω , 1/9 doz. mixed; 13/6 100 mixed; 12/- 100 in 100's of one ohmic value.
 $\frac{1}{2}$ W 5% E24 series, 4.7 Ω to 10M Ω , 2/2 doz. mixed; 17/- 100 mixed; 15/6 100 in 100's of one ohmic value.
 1W 10% E12 series, 10 Ω to 10M Ω , 4d. each, 3/3 doz. mixed.
 All mixtures to your specification. Large quantities stocked.
 Quality carbon skeleton pre-sets: 100, 250, 500, 1k, 2k, 2.5k, 5k, 10k, 20k, 25k, 50k, 100k, 250k, 500k, 1M, 2M, 2.5M, 5M, 10M Ω .
 All available in horizontal or vertical mounting, 1/- each.
 Volume controls: 100, 250, 500 Ω series to 10M Ω linear, 2/3 each.
 5k, 10k, 25k Ω and series to 5M Ω log, 2/3 each.
 Electrolytics, low cost: 5, 10, 25, 50 μ F 10V, 5, 10 μ F 25V 9d. each. 100, 200 μ F 10V, 25, 50 μ F 25V 1/-d. each.
 Mullard electrolytics, sub-min C426, whole series stocked.
 Ceramic discs: 0.01 μ F 50V 5d., 0.02, 0.05 μ F 50V 6d.

SEMICONDUCTORS

SILICON

Low noise, high gain: BC169 2/9; BC109 4/-; 2N3707 5/-; 2N4058 5/6.
 High gain: BC168 2/6; BC108 3/11; 2N2926/yellow 3/6; 2N4062 5/6.
 High power: 2N3055 16/6; 40465 16/3; MJE521 21/3; MJE371 PNP 24/6.
 Field effect: MPP105 10/-; 2N3819 14/9; 2N3820 24/6.
 Many others: BC167 3/-; BC107 4/-; 2N3702 4/-; 2N3703 4/-; 2N3704 4/-; 2N3705 4/-; CS2925 5/-; CS2926/red 3/9; C407 6/-, etc.

GERMANIUM

Many types including: ACY22 3/6; 2G308 6/9; 2G309 7/9; 2N1304 4/-; 2N1305 4/-; NKT274 3/8; NKT403 16/3; 2N2147 16/9; 2N2148 13/6; AD161 9/-; AD162 9/-; 2G371 2/9; MAT101 8/6; MAT120 7/9.
MINIATURE SILICON DIODES: 30V 75mA 1/3 each; OA202 2/-.
 Other diodes: OA47, OA70, OA81 1/9 each; OA90 OA91, OA95 1/3 each.

PEAK SOUND PRODUCTS

CIR-KIT No. 3 Pack 12/6; adhesive copper strip 5ft. $\times \frac{1}{4}$ or $\frac{1}{2}$ in. 2/-.
 Perforated board 0.1in. matrix, 5in. \times 3 $\frac{1}{2}$ in. 4/-; 2 $\frac{1}{2}$ in. \times 3 $\frac{1}{2}$ in. 2/6.
 Transistorised Stereo Amplifier kit type SAB-8 £10/10/-.
 Cabinet £3; Power supply kit £3. Post free and 15% discount!
ALL GOODS BRAND NEW. NO SURPLUS. FAST DELIVERY.
DISCOUNTS: 10% over £3; 15% over £10. P. & P. 1/-, free over £1

ELECTROVALUE

6 MANSFIELD PLACE, ASCOT, BERKSHIRE

ADVANCE TEST EQUIPMENT

VM76	Valve Voltmeter R.F. Measurements in excess of 100 MHz and d.c. measurements up to 1,000V with accuracy of $\pm 2\%$. D.c. range—300 mV-1 kV f.s.d. A.c. range—300 mV-300 V r.m.s. Resistance in 8 ranges, 0.02-500 Megohms. Manufacturer's price £90: Our price £72	VM79:	UHF Millivoltmeter Transistorised. A.c. range 10 mV-3 V f.s.d., 10 ranges. D.c. current range 0.01 μ A-0.3 mA f.s.d., 10 ranges. Resistance 1 Ohm-10 Megohms in 7 decade ranges. Complete with probe. Manufacturer's price £180: Our price £125
VM77C:	A.C. Millivoltmeter 1 mV-300 V full scale in 12 ranges. Freq. range 15 c/s-4.5 Mc/s. Input impedance 10 Megohms 20 pF. Calibrated in r.m.s. volts for sine wave input and dB. 100-250 V a.c. input. Manufacturer's price £55: Our price £40	J1B:	Audio Signal Generator 15 c/s-50 kc/s in 3 ranges. Output 600 Ohms, 0.1 mW-1 W (0.25-24 V), variable. Attenuation 20 dB-600 Ohms (Attenuator is incorporated), output 10 mW (2.5 V). 100-250 V a.c. Manufacturer's price £46: Our price £30
VM78:	A.C. Millivoltmeter Transistorised. 1 mV-300 V in 12 ranges. Freq. 1 c/s-1 Mc/s. Input impedance 2 Megohms 60 pF. Calibrated in r.m.s. for sine wave and input dB. Manufacturer's price £70: Our price £55	J2B:	Audio Signal Generator Same specification as for the J1B except that this model has an additional 2 in. meter calibrated 0-40 V a.c. Manufacturer's price £50: Our price £35
TT1S:	Transistor Tester (CT472) Suitable for measuring medium and low powered transistors. Current gain (B) can be measured in range 10 to 500 for p.n.p. and n.p.n. types, either in circuit using the clip on probes provided. Small compact instrument. Manufacturer's price £57: Our price £37/10/-	H1B:	Audio Signal Generator 15 c/s-50 kc/s in 3 ranges. Sine wave 200 μ V-20 V r.m.s. Square wave 1.4 mV-140 V peak to peak (approx.). 100-250 V a.c. Manufacturer's price £42: Our price £30

Special offer of 10% discount for schools and Technical Colleges, etc. These were manufactured in U.K. by Advance Electronics Ltd. BRAND NEW, all in original sealed carton. Carr. 10/- extra per item.

S.A.E. for all enquiries. If wishing to call at Stores, please telephone for appointment.

W. MILLS

3-B TRULOCK ROAD, TOTTENHAM, N.17
Phone: Tottenham 9213

CONDENSERS. 10 mfd. 1,000 v., 12/6, post 2/6. 8 mfd., 1,200 volts, 12/6, post 3/-. 8 mfd. 600 volts, 8/6, post 2/6. 0.25 mfd., 2 kv., 4/-, post 1/6.

AUTOMATIC PILOT UNIT Mk. 2. This complex unit of diodes and valves, relays, magnetic clutches, motors and plug-in amplifiers, with many other items, price £7/10/-. £1 carriage.

APNI ALTIMETER TRANS. REC., suitable for conversion 420 mc/s. complete with all valves 28 v. D.C. Dynamotor and 3 relays, 11 valves, price £3 each, carr. 10/-.

ROTARY TRANSFORMERS. 24 v. input, 175 v. at 40mA output, 25/-, plus 2/- post. 12 v. input, 225 v. at 100 mA. output, 25/-, plus 3/- post. (All the above are D.C. only.)

AVO MULTIRANGE No. 1 ELECTRONIC TEST SET: £25 each, carr. £1.

HRO RECEIVER. Model 5T. This is a famous American High Frequency superhet, suitable for CW, and MCW., reception crystal filter, with phasing control. AVC and signal strength meter. Freq. range 50 kc/s. to 30 mc/s., with set of nine coils. Receiver only in working order, £18/10/-. carr. 15/- each. Set of nine coils, £12/10/-. available only with set. Power unit for HRO 100/240 v. A.C., £2/15/-. carr. 10/-.



SPECIAL OFFER: Complete HRO SET (Receiver, Coils & Power Unit) for £30, plus 30/- carr.

HRO-M-SETS available with UX type valves; secondhand cond., with 5 coil and power unit, £20 each, carr. 30/-.

CONVERTERS. Type 8a, 24 v. D.C., 115 v. A.C. at 1.8 amps 400 cycles, 3-phase, £6/10/- each, post 8/-.

MARCONI DEVIATION TEST SET, TF934: freq. 2.5-100 Mc/s. Can be extended to 500 Mc/s. Deviation range 0-5, 0-25 and 0-75 Kc/s. £35 each, carr. £1.

MARCONI IMPEDANCE BRIDGE, TF-373: inductance 5µh-100H in 5 ranges, capacity 5pF-100µF in 5 ranges, resistance .05 meg.-1 meg., power supply 250 v. A.C. £37/10/- each, carr. 15/-.

CT-49 ABSORPTION AUDIO FREQUENCY METER: freq. range 450 c/s-22 Kc/s., directly calibrated. Power supply 1.5 v.-22 v. D.C. £12/10/- each, carr. 15/-.

TACAN. Trans./Receiver, same as ARN21, British made, STC, TR9171 complete with five 2C39As with associated valve-holders. As new price £25. Used condition, £15, carriage £1.

RELAY UNITS. 2 high speed relays H96E, 1700+1700 ohms, 1 change-over relay 14,000 ohms, 1 CV 455, 100 ohms and 1 meg. pot., etc. Mounted in box, 4in. x 6in. x 30in., 30/- each, 4/- post.

RECEIVERS. Type AR88D: freq. 540 Kc/s-32 Mc/s. £45 each, carr. £2. **AR88 SPEAKERS.** New in cartons, metal case with black crackle finish 59/6 ea., post 7/6.

AR88 SPARES. Antenna Coils L5 and 6 and L7 and 8. Oscillator coil L.55. Price 10/- each, post 2/6. By-pass Capacitor K.98034-1, 3 x 0.05 mfd. and M.98034-4, 3 x 0.01 mfd., 3 for 10/-, post 2/6. Trimmers, 95534-502, 2-20 p.f. Box of 3, 10/-, post 2/6. Block Condenser, 3 x 4 mfd., 600 v., £2 each, 4/- post. Filter Choke, L45 and 50, K901433-501, 25/- each, 4/- post.

AIRCRAFT RECEIVER ARR2. 235-258 Mc/s. tunable, 24 v. D.C. input, £3 ea. 7/6 carr.

HEWLETT PACKARD TYPE 400C: 115 v./230 v., input 50/60 c/s. Freq. range 20 c/s-2 Mc/s. Voltage range: 1 mV-300 v. in 12 ranges. Input impedance 10 megohms. Designed for rack mounting, £30 each, carr. 15/-.

COMMAND RECEIVERS: Model 3-6 Mc/s. and 6-9 Mc/s., as new, price £5/10/- each, post 5/-.

SIGNAL GENERATORS:

MARCONI TF-144G: freq. 85 Kc/s-25 Mc/s, internal and external modulation, power supplies 200/250 v. A.C. (secondhand cond.), price £25 ea.; or available in transit case, complete with spares, in first class condition £30 ea., carr. on both 30/- ea.

TS155c/UP (as new): price £75 each, carr. £1.

CT53. Freq. range 8.9-300 Mc/s. with Calibration chart. Output 1µV-100 mV. internal square wave and sine wave modulation at 100 c/s., external modulation 50 c/s-10 Kc/s, 230 v. A.C. Complete with chart, etc., price £27/10/- ea., carr. £1.

MARCONI TF801A/1 Freq. 10-300 Mc/s, 4 bands, output 200mV, Attenuator 0-110dB. Input 75 ohms. £65 each, carr. £1.

MARCONI TF516-F/1: Covering 10-18 Mc/s, 33-58 Mc/s., 150-300 Mc/s. £12/10/- each, carr. £1.

MARCONI CT218: price £65 each, carr. 30/-.

CT.480 and 478: 1.3-4.2 Mc/s, F.M. or A.M., price £75 each, carr. 30/-.

TELEPHONE EQUIPMENT:

GPO 'CANDLESTICK' TYPE TELEPHONE. Upright model with receiver, ideal novelty for converting to lampshade. Available any colour, £5/10/- ea., post 7/6.

TELEPHONE WIRE: 220 yds., £1 a roll, post 6/-.

GPO TERMINAL BLOCKS, 7/6 each, **FUSE AND PROTECTOR,** 7/6 each. Post on both 2/6.

TELEPHONES (PORTABLE) TYPE "F." Suitable for all outdoor activities up to a range of 5 miles. Price £7/10/- each, as new, complete with carrying case. Price, £5/10/- each, secondhand. Carr. 10/-.

TELEPHONE EXTENSION CORD. Brown, 3-way; come in lengths of 6ft. and 14ft., 7/6 and 15/- respectively. Post 2/6.

BC-433-G COMPASS RECEIVER: Freq. 200-1,750 kc/s. in 3 bands, suitable for aircraft, boats, etc. Complete with 15 valves, power supply input 24 v. D.C. at 2 amps. Receiver only £5 each. Carr. 15/-.

TCS MODULATION TRANSFORMERS, 20 watts, pr. 6,000 C.T., sec. 6,000 ohms. Price 25/-, post 5/-.

NIFE BATTERIES: 6 v. 75 amps., new, in cases, £15 each, £1 carr.; 6 v. 160 amps., new in cases, £25 each, £1/10/- carr.; 4 v. 160 amps., new, in cases, £20 each, £1/10/- carr.

L.R.7 Cells, only 1.5 v. 75 amps., new, £3 each, 12/- carr. The above batteries are low resistance designed to give heavy surge for starting and can be stored for long periods without any effect to their performance.

WAVE GUIDES FLEXIBLE CG-152 APM40. Length 18 inches. Price £2 each, post 4/-.

MACHMETERS: Range 0:1 and 0:1.2. 6A/3384 & 5325 respectively, price 30/- each, postage 5/-.

FUEL INDICATOR Type 113R: 24 v. complete with 2 magnetic counters 0-9999, with locking and reset controls mounted in a 3in. diameter case. Price 30/- each, postage 5/-.

DRY BATTERIES, NO. 1. HT 90 v. and 7½ v., size 2½in. x 3½in. x 5in., 5/- each, or 5 for £1, post 4/- and 7/6 respectively.

BATTERY NO. 4 (suitable for bells, etc.) 4½v., size 4½in. x 6in. x 2½in. 5/- each. Post 3/-.

UNISELECTORS (ex equipment): 10 Bank, 50 Way, alternate wipe, £2/5/- ea. 6 Bank, 25 Way, alternate wipe, £2/2/6 ea. 8 Bank, 25 Way, £2/5/- ea. 6 Bank, 25 Way, £2 ea. 4 Bank, 25 Way, 35/- ea. All the above are 75 ohm coil. Postage 4/- per uniselector.

FREQUENCY METERS: IM-13 or BC-221; 125-20,000 Kc/s., £25 each, carr. 15/- TS174 U; 20-250 Mc/s. modulated, £45 each, carr. 15/- TS323/UR; 20-450 Mc/s., £75 each, carr. 15/- FR-67/U: This instrument is direct reading and the results are presented directly in digital form. Counting rate: 20-100,000 events per sec. Time Base Crystal Freq.: 100 Kc/s. per sec. Power Supply: 115 v., 50/60 c/s., £100 each, carr. £1.

AMERICAN EQUIPMENT: Power supply, PP893/GRC 32A; Filter D.C. Power Supply F-170/GRC 32A; Cabinet Electrical CY 1288/GRC 32A; Antenna Box Base & Cables CY 728/GRC; Mast Erection Kits, 1186/GRC; Receiver type 27 8B; Directional Antenna CRD 6; Comparator Unit, CM,23; Directional Control CRD 6, 567/CRD and 568/CRD; Azimuth Control Units, 260/CRD.

GEARED MOTORS: 24 v. D.C., current 150 Ma, Output 1 r.p.m. 30/- each, 4/- post. Assembly unit with Letcherbar Tuning Mechanism and potentiometer, 3 r.p.m., £2 each, 5/- post.

MOTORISED ACTUATOR: 115 v. A.C. 400 c/s. single phase, reversible, thrust approx. 3 inches complete with limit switches, etc. Price £2/10/- each, postage 5/- (ex equipment).

D.C. MOTOR: 27 v. D.C. with gear box, 4 r.p.m. Price 25/-, postage 3/- (ex equipment).

Actuator Type SR-43: 28 v. D.C. 2,000 r.p.m., output 26 watts, 5 inch screw thrust, reversible, torque approx. 25 lbs., rating intermittent, price £3 each, post. 5/-.

FRACTIONAL MOTORS & FANS: Low Inertia Motor 5UD/5361-Type 903, 24 v. input D.C., £2/10/- each, 5/- post.

Model PM84: 28 v. D.C. @ 2 amps., 4,500 r.p.m., output 40 watts continuous duty complete with magnetic brake. Price £2 each, postage 4/-.

Model SR-2: 28 v. D.C. 7,000 r.p.m., duty intermittent, output 75 watts, price 25/- each, postage 4/-.

A.C. Motor 115 v. 50 c/s. 1/300 H.P., 3,000 r.p.m. Capacitor 1mfd, 25/- post 3/-. Dalmotor SC5, 28 v. D.C. at 45 amps; 12,000 r.p.m. output 750 W. (approx. 1 h.p.), brand new, £2/10/- each, post 7/6.

CATHODE RAY TUBE UNIT: With 3in. tube, colour green, medium persistence complete with nu-metal screen, £3/10/- each, post 7/6.

TRANSMITTER/RECEIVER TCS-12: Freq. 1.5 Mc/s-12 Mc/s, output 25 W., complete stations available with antenna equipment, mast, and petrol generator. Trans-receiver, complete with 12 v. D.C. Power Unit and A.T.U. £25 each, carr. £2/10/-.

Petrol Generator Unit for the above £20 each, carr. £3. Complete aerial system £10 each, carr. £2.

S.A.E. for all enquiries. List available 6d. If wishing to call at Stores, please telephone for appointment.

W. MILLS

3-B TRULOCK ROAD, TOTTENHAM, N.17

Phone: Tottenham 9213

TRANSISTOR BARGAIN SALE! NEW STOCK AT UNBEATABLE PRICES!
 OC4, OC45, OC81D now only **1/8** each! **250/-** per 100.
 OC71, OC73 equivalent **1/-** each! **£30/-** per 100.
 A8Y23 Switching Transistors **2/6** each! **£10/0-** per 100.
 2N733 N.P.N. Silicon Planar, 300mW, 250 Mc/s. High speed switching ... **2/6** each!
 B8Y28 N.P.N. Silicon Planar, Epitaxial, 300mW, 300 Mc/s ... **2/6** each!
 B8Y50 N.P.N. Silicon Planar, Epitaxial, 300mW, 100 Mc/s ... **2/6** each!
 AE212 P.N.P. Germanium Alloy DMR, low noise V.H.F. amplifier ... **2/6** each!
 Complete sets of transistors for radio:—
 2G344A/2G345A/2G347A/2G378A/2G378A + diode ... **15/-** only!
 OC44/OC45/OC46/OC81D/OC81/OC81 + diode ... **10/-** only!
 Light sensitive transistors similar to OC171 ... **2/-** each!
 UNMARKED, UNTESTED TRANSISTORS TO CLEAR ... **7/6** for 50!
 Silicon diodes. Make excellent detectors. Also suitable for keying electronic organs. **1/-** dozen for 10/-.
 BY 100 type rectifiers. **SPECIAL REDUCED PRICE! ONLY 2/6 each. 24/- doz.**

ELECTROLYTIC CONDENSERS! FANTASTIC SELECTION!

50µF 450 volts .. 1/3	30 + 4	275 volts .. 10/-
64µF 275 volts .. 1/3	32 + 8	275 volts .. 1/9
500µF 30 volts .. 1/2	8 + 8	450 volts .. 1/9
800µF 15 volts .. 1/2	8 + 16	450 volts .. 2/-
500µF 25 volts .. 10/-	50 + 50	275 volts .. 2/1
10/10/16, 360 v .. 2/2	40 + 40 + 20	275 volts .. 10/-
50/50/50, 350v .. 2/7	100/100, 50v .. 3/2	250µF, 50v .. 10/-
1,000µF, 70v .. 3/2	1,000µF, 12v .. 4/6	12,500µF, 30v .. 18/-
3,000µF, 35v .. 3/8	1,250µF, 50v .. 4/-	30,000µF, 30v .. 25/-
1,500µF, 50v .. 4/-	150/350, 300v .. 4/-	1,000µF, 15v .. 1/6
	250/250, 325v .. 4/-	1,000µF, 18v .. 1/6
	2000/2000, 25v .. 4/8	500µF, 15v .. 10/-

All at 9/- per dozen, 20 per 10/- (four selection).

0.25µF .. 3 volt	0.4µF .. 60 volt	30µF .. 10 volt
1µF .. 6 volt	0.4µF .. 70 volt	32µF .. 1.5 volt
1µF .. 10 volt	0.4µF .. 3 volt	40µF .. 3 volt
1µF .. 15 volt	0.4µF .. 12 volt	40µF .. 6.4 volt
1µF .. 40 volt	0.4µF .. 15 volt	50µF .. 6 volt
1µF .. 60 volt	0.4µF .. 150 volt	50µF .. 9 volt
1.25µF .. 16 volt	0.4µF .. 3 volt	50µF .. 12 volt
2µF .. 3 volt	0.4µF .. 6 volt	64µF .. 2.5 volt
2µF .. 9 volt	0.4µF .. 25 volt	64µF .. 9 volt
2µF .. 15 volt	0.4µF .. 300 volt	100µF .. 3 volt
2µF .. 50 volt	0.4µF .. 50 volt	100µF .. 9 volt
2µF .. 70 volt	0.4µF .. 275 volt	100µF .. 12 volt
2µF .. 100 volt	10µF .. 6 volt	100µF .. 15 volt
2µF .. 350 volt	10µF .. 10 volt	150µF .. 25 volt
1µF .. 350 volt	10µF .. 12 volt	200µF .. 3 volt
2.5µF .. 16 volt	10µF .. 25 volt	200µF .. 4 volt
2.5µF .. 25 volt	12µF .. 8 volt	250µF .. 18 volt
3µF .. 3 volt	12µF .. 20 volt	200µF .. 16 volt
3µF .. 12 volt	12.5µF .. 40 volt	250µF .. 2.5 volt
3µF .. 25 volt	14µF .. 30 volt	250µF .. 12 volt
3µF .. 450 volt	16µF .. 150 volt	250µF .. 8 volt
3.2µF .. 6 volt	16µF .. 3 volt	250µF .. 25 volt
3.2µF .. 6.4 volt	20µF .. 6 volt	320µF .. 9 volt
3.2µF .. 64 volt	20µF .. 9 volt	350µF .. 10 volt
4µF .. 4 volt	20µF .. 15 volt	400µF .. 2.5 volt
4µF .. 12 volt	25µF .. 6 volt	400µF .. 15 volt
4µF .. 25 volt	25µF .. 12 volt	500µF .. 4 volt
4µF .. 64 volt	25µF .. 15 volt	500µF .. 6 volt
4µF .. 100 volt	25µF .. 25 volt	640µF .. 2.5 volt
5µF .. 6 volt	30µF .. 6 volt	780µF .. 12 volt
5µF .. 25 volt	30µF .. 6 volt	

All at 15/- per 100, 3/- per dozen.

MULLARD POLYESTER CAPACITORS. ALL HALF PRICE

0.0022µF 400 volts .. 4d.	0.15µF 400 volts .. 7d.
0.0018µF 400 volts .. 4d.	0.22µF 160 volts .. 7d.
0.0015µF 400 volts .. 4d.	0.27µF 140 volts .. 8d.
0.0012µF 400 volts .. 4d.	0.05µF 125 volts .. 7d.
0.01µF 400 volts .. 4d.	1µF 125 volts .. 1/8

VERY SPECIAL VALUE! Silver Mica, Ceramic, Polystyrene Condensers. Well assorted. Mixed types and values. **10/- per 100.**

RESISTORS. Give-away offer! Mixed types and values. 4 to 1 watt. 6/6 per 100 or 55/- per 1,000.
 Also 1 to 3 watt close tolerance. Mixed values, 7/6 per 100, 55/- per 1,000.

WIRE-WOUND RESISTORS. 1 watt, 3 watt, 6 watt, 8d. each. 7 watt and 10 watt 9d. each.

CONNECTING WIRE THIN, P.V.C. INSULATED
 10yds 1/-; 100yds 7/8; 500yds 25/- (post 4/6); 1,000yds 40/- (post 6/-).

VALVES. BRAND-NEW AND BOXED. ROCK-BOTTOM PRICES!

DY87 .. 5/10	EY96 .. 5/10	PCL98 .. 7/4
EA1020 .. 6/1	EY87 .. 5/10	PFL200 .. 10/2
EA1023 .. 6/5	PA 8C90 .. 6/2	PL36 .. 8/8
EA1023 .. 6/5	PC97 .. 5/10	PL81 .. 7/4
EA1090 .. 6/2	PC94 .. 6/5	PL83 .. 7/4
EA1096 .. 7/4	PCF80 .. 7/4	PL94 .. 5/-
EP90 .. 6/2	PCF80 .. 7/4	PL500 .. 10/7
EP85 .. 6/2	PCL82 .. 8/3	PY32 .. 7/10
EP183 .. 8/2	PCL83 .. 8/6	PY81 .. 5/10
EP184 .. 8/2	PCL84 .. 7/4	PY82 .. 4/1
EY51 .. 5/10	PCL86 .. 7/4	PY800 .. 5/10

A further 10% discount will be given on lots of 50 of any one type.

Signal Injector Kit, 10/-. Signal Tracer Kit, 10/-.

NEEDLES FOR RECORD PLAYERS. HALF PRICE!
 All types below at 3/8 each!
 GC2LP, GC2LP. GC8LP, BF40LP, GP67LP, GP37, GP53, TC8 Stereo LP, Studio O LP.

CARRIDGES
 SONOTONE MONO 10/-, ACOS 15/-, ACOS STEREO SAPPHIRE 20/-, DIAMOND 25/-.
 All complete with needles!

VEROBOARD
 1in. x 2 1/2in., 1/1; 2 1/2in. x 5in., 3/11; 2 1/2in. x 3 1/2in., 3/3; 3 1/2in. x 5in., 5/6; 3 1/2in. x 3 1/2in., 3/11.
 Terminal Pins, 36 for 3/-; Spot Face Cutter, 7/3.
 Special Offer—Cutter and 5 boards, 2 1/2in. x 1in., 9/9.
 Pin Insert Tool 9/6.

ORDERS BY POST—TO G. F. MILLWARD, 17 PEEL CLOSE, DRAYTON BASSETT, STAFFS.

PLEASE INCLUDE APPROPRIATE POSTAGE COSTS
 No Enquiries without stamped addressed envelope please

For customers in the Birmingham area, goods may be obtained from: Rock Exchanges, 231 Alum Rock Road, Birmingham 8 (Post Orders to Drayton).

All overseas enquiries & orders please address to:
COLOMOR (ELECTRONICS) LTD.
 170 Goldhawk Rd., London, W.12. Tel. (01) 743 0899



MARCONI SIGNAL GENERATOR TYPE TF801B/3/5
 Frequency range 12-485 Mc/s in five ranges. Directly calibrated frequency dial. Output waveform: C.W. sine wave A.M., pulse A.M. (from ext. source only). Internal modulation frequency 1,000 c/s. Output: a, normal—continuously variable d.c. directly calibrated from 0.1µV to 0.5 v. b, high; up to 1 v. modulated for 2 v. unmodulated, output impedance 50 ohms. Fine frequency tuning control, carrier on/off switch.

built-in crystal calibration for 2 Mc/s and 10 Mc/s. Stabilised voltage supply. In excellent "as new" condition. Laboratory checked and guaranteed. £115. Carr. 30/-. Including necessary connectors, plugs and instruction manual.

MARCONI SIGNAL GENERATOR TF 801A/1. 10-300 Mc/s. in 4 bands. Internal at 400 c/s, 1 kc/s. External 50 c/s to 10 kc/s. Output 0-100 db below 20 mV from 75 ohms source. Completely new with accessories and instruction book. £85. P. & P. 20/-.

CR 150 RECEIVER, 2 Mc/s-60 Mc/s, with specially built PSU for mains. £49/10/-.
METERS. 4 1/2in. x 4 1/2in., 4in. long, mirror scale panel mounted, calibrated 0-1 mA. 55/-, P. & P. 3/-.
LABORATORY TYPE VOLT. METERS. 160 v. A.C./D.C. 8in. mirror scale in wooden boxes, 9 1/2in. x 8 1/2in. x 3 1/2in. with carrying handle, brand new, 32/-, P. & P. 3/-.
SPARES FOR A.R.88D. RECEIVERS. Ask for your needs from our huge selection.
VARIOMETER for No. 19 sets, 17/6, P. & P. 3/-.
TELEPHONE HANDSETS. Standard G.P.O. type; new 12/-, P. & P. 2/-.

INSET MICROPHONE for telephone handset, 2/6. P. & P. 2/-.
LIGHTWEIGHT, LOW RESISTANCE HEADPHONES. Type H.S. 33. Largely used by pilots. Brand new, 27/6, P. & P. 3/-.
MINIATURE METERS. General Electric 1 1/2in. round flush, clip mounted; 1 mA D.C. 22/6, 25 mA D.C. 20/-, P. & P. 65 mA D.C. 18/-, 3/-, 150 mA D.C. 15/-.

"S" METER FOR H.R.O. RECEIVERS. Brand new, £2/10/-, Carriage paid U.K.
CRYSTALS for H.R.O. in original National Union Housing, 25/-, P. & P. 2/-.
PRECISION VHF FREQUENCY METER TYPE 183. 20-300 Mc/s with accuracy 0.03% and 300-1,000 Mc/s with accuracy 0.3%. Additional band on harmonics 5.0-6.25 Mc/s with accuracy + - 2 x 10^-4. Incorporating calibrating quartz 100 kc/s + - 5 x 10^-8 120/220 v. A.C. mains. £85. Carriage £2.


FIELD TELEPHONES TYPE "F"
 Housed in portable wooden cases. Excellent for communication in- and out-doors for up to 10 miles. For pair including batteries and 1/6th mile field cable on drum. £5/10/-, Carriage 10/-.

FOR EXPORT ONLY
53 TRANSMITTER made up to "as new" standard. All spares available.
COLLINS TCS. Complete installations and spare parts.
FIELD TELEPHONE SETS TYPE "J" YA 7815. Portable. Ideal for tropical climates.
R.C.A. TRANSMITTER TYPE ET 4336. 2-20 Mc/s., complete with M.O., Cryst. mult. and speech ampl. Fully tested and guaranteed. All spares available.

BC 610 E TRANSMITTER. Complete with speech amplifier BC 614E. Aerial tuning unit BC 939A, exciter units, tank coils, etc. Fully tested and guaranteed. All spares available.
No. 19 SETS. HP output increased to 25 watts. Complete installations supplied.
RONTGENS/HOUR MICRO-AMMETERS. FSD 100µamp. 3in. x 3in. x 1in. width with switching dials. 32/6. P. & P. 3/-.

END OF RANGE ITEMS
 Offered at special low prices as only a few left, all are in fully tested guaranteed condition.
VALVE VOLTMETER TS 428B/1. £10/10/-.

P. C. RADIO LTD.
 170 GOLDHAWK ROAD, W.12 SHEpherd's Bush 4946



SEMICONDUCTORS

DISTRIBUTED EXCLUSIVELY BY

BI-PRE-PAK LTD. DEPT. B.
222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
PHONE: SOUTHEND (0502) 46344

BRAND NEW UNTESTED TRANSISTORS **SAVE £'s TEST THEM YOURSELF** **WE TELL YOU WHAT TYPES THEY ARE** **DON'T TAKE CHANCES ON UNKNOWN LOTS**

LOOK — TRANSISTORS 1/- EACH

SILICON ★ PLANAR ★ N.P.N. ★ P.N.P.
All these types available

2N929	2N131	2N696	2N2906
2N501	2N512	2N697	2N2904
2N2411	2N102	2N1507	2N731
2N726	2N103	2N1613	2N732
2N706	2N104	2N1711	2N733
2N706A	2N2220	2N1893	
2N3011			

ALL TESTED AND GUARANTEED TRANSISTORS—UNMARKED. Manufacturers over-runs for the new PRE-PAK range.

PRE-PACKS

No.	DESCRIPTION	PRICE
AL.	6—Silicon rectifiers BY100 type	20/-
A3.	20—Mixed marked and tested trans.	20/-
A15.	2—Power Comp. Pair. AD161/2	20/-
A19.	5—Zener diodes Inc. Book of Instructions	20/-
B1.	50—Unmarked untested, trans., new	10/-
B2.	4—Solar cells, Inc. Book of Instructions	10/-
B3.	4—OA5 gold bonded, diodes Mullard	10/-
B5.	7—Matched set, OC44, 45/81D/81+diode	10/-
B6.	15—Red spot AF, trans. or white spot RF	10/-
B8.	2—Power trans. OC26/35 type	10/-
B9.	1—Light sensitive cell, ORP12 type	10/-
B10.	10—60V trans. germ. PNP latest type	10/-
B44.	1—Tunnel diode, AEX11, 1050 Mc/s.	10/-
H21.	2—Sil. recs. 10 amp., 50-100 PIV	10/-
B42.	5—Switching trans. TK22C BTC	10/-
C2.	1—Und junction. 2N2160 or 2N2640	15/-
C4.	2—RF power trans. OC22 and BUY11	15/-
C31.	4—Sil. recs. 800 PIV 1 amp. top hat	15/-
C32.	2—Power trans. TK 400A/NKT404 VCB4 IC 8 amp.	15/-
D18.	1—ORP60 type light sensitive cell	5/-

25	B8Y 96 A NPN SILICON	TRANSISTORS 10/-
10	1000 PIV. 1 AMP. MIN. SILICON.	DIODES 10/-
25	B8Y 26-27 NPN SILICON	TRANSISTORS 10/-
10	10 WATT SILICON ALL VOLTAGES	ZENERS 10/-
25	BFY50-51-52 NPN SILICON	TRANSISTORS 10/-

10	4 AMP. 8TUD SILICON	RECTIFIERS 10/-
25	BC107-8-9 NPN SILICON	TRANSISTORS 10/-
40	IN914-6 SUB. MIN. SILICON	DIODES 10/-
50	MIN. GERMANIUM HIGH QUALITY	DIODES 10/-
25	2N706-A NPN SILICON	TRANSISTORS 10/-

TRANSISTORS	PRICE	B8Y25	10/-	OCI71	4/-	POWER TRANSISTORS	
AC107	6/-	B8Y26	5/-	OC200	5/-	OC20	10/-
AC123	2/6	B8Y27	5/-	OC201	8/-	OC23	10/-
AC127	2/6	B8Y28	5/-	OC44	1/11	OC25	8/-
AC128	3/-	B8Y29	5/-	OC45	1/9	OC26	5/-
AC17	5/-	B8Y29A	5/-	2N711	10/-	OC28	7/6
AF114	4/-	OC41	2/6	2N1302	4/-	OC35	5/-
AF115	3/-	OC71	2/6	2N1303	4/-	OC38	7/6
AF116	3/-	OC72	2/6	2N1304	5/-	DIODES	
AF117	4/-	OC73	2/6	2N1305	5/-	AAV42	2/-
AF118	3/6	OC81	2/6	2N1306	6/-	OA10	2/-
AF119	3/6	OC81D	2/6	2N1307	6/-	OA70	1/9
AF178	10/-	OC83	4/-	2N1307	8/-	OA79	1/9
ASV66	2/-	OC139	2/6	2N1309	7/6	OA81	1/8
BCZ11	7/6	OC140	2/6	2N1309	7/6	OA182	2/-
BFY50	15/-	OC170	2/6	28303	2/6	IN914	1/6

'FREE' ★ ★

Packs of your own choice to the value of 10/- with all orders over £4.

LARGE RANGE — LOW PRICE

SILICON CONTROLLED RECTIFIERS. SEND FOR FULL RANGE AND CIRCUIT DIAGRAMS. FREE OF CHARGE.

GREAT NEWS ★ ★

We now give a written guarantee with all our semi-conductors.

FIRST EVER LOGIC KITS. Learn for yourself how computers work, even make one for yourself. Full instructions for thoughts and crosses machine. Binary counters, timers, etc. L1 5 gms., L2 10 gms. No need to purchase both kits, you can start with L2 which incorporates L1. DETAIL FREE


MAKE A REV. COUNTER FOR YOUR CAR. THE 'TACHO-BLOCK.' This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev counter for any car. State 4 or 6-cylinder. **20/- each**

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

MULLARD

AAV11	2/-	BFY50	6/-	OC82	4/6
AC107	14/6	BFY51	5/-	OC82D	4/3
AC137	6/-	BFY52	6/-	OC83	3/6
AC138	4/-	BF184	8/-	OC84	4/-
AC176	6/-	B8X79	3/-	OC123	7/-
AD149	11/-	BTY79-400R	27/6	OC139	12/-
AD161	7/6	BTY87-150R	23/-	OC140	12/-
AD162	7/6	BTY91-150R	35/-	OC169	6/-
AOY17	5/-	B8X36-100	3/-	OC170	4/-
ACY20	3/6	BTY87-500R	47/-	OC171	6/-
ACY21	4/-	BYZ10	11/-	OC200	6/-
ACY22	2/6	BYZ12	7/6	OC201	10/-
AFZ11	10/-	BYZ13	5/-	OC202	13/-
AFZ12	11/9	BZY93 C24	12/-	OC203	8/-
AF114	4/9	BY100	5/-	OC204	11/-
AF115	4/9	BYX20-200	8/-	OC205	10/6
AF116	4/9	GET102	5/4	OC271	19/6
AF117	4/9	GET103	4/4	ORP12	9/-
AF118	9/-	GET111	10/-	ORP60	8/-
AF186	12/-	GET573	10/-	ORP63	9/-
AF239	12/-	OC19	5/-	ORP93	18/-
ASV26	5/-	OC20	33/-	ORP90	10/6
ASV28	5/-	OC22	13/-	OA5	3/-
ASZ21	4/-	OC23	25/-	OA10	4/-
ASV29	6/6	OC24	19/-	OA47	1/6
ATZ10	38/6	OC25	7/-	OA70K	1/6
BA115	2/6	OC26	12/-	OA79K	1/6
BC107	5/-	OC28	12/-	OA81K	1/6
BC108	5/-	OC29	15/-	OA85K	1/6
BC109	5/-	OC35	9/6	OA90K	1/6
BCY10	20/-	OC36	13/-	OA91K	1/6
BCY12	22/-	OC41	3/6	OA95K	1/6
BCY30	7/-	OC42	4/-	OA90K	2/-
BCY31	13/-	OC44	3/-	OA92K	2/-
BCY32	8/-	OC45	3/-	OA210	7/6
BCY33	8/-	OC71	3/-	8X631	7/-
BCY34	8/-	OC72	4/6	8X636	10/-
BCY38	19/-	OC73	3/-	8X638	13/-
BCY39	10/-	OC75	5/-	SZ20C	12/-
BCY40	16/-	OC76	3/-	818V	95/-
BCY71	15/-	OC81	3/-	818C	95/-
BCZ11	17/-	OC81D	3/-	8VC1	19/9

GUARANTEE: All the above-listed semi-conductor devices are Brand New, First Grade, and guaranteed. We will replace at no charge any device found to be faulty. Further: all devices carry the Manufacturer's name or Trade Mark, type number and batch number. We do not offer for sale devices often described as "new and tested" or bearing re-marked type numbers, these often have a short and unreliable life. L.S.T. COMPONENTS.



SINCLAIR

ADT140	12/6
ST141	5/-
ST140	3/-

FAIRCHILD

INTEGRATED CIRCUITS

Epoxy TO5 10 lead
μL 900 Buffer @ 9/-
μL 914 Dual Gate @ 9/6
μL923 J-K Flip Flop @ 12/6
4-page reprint on IC usage circuits (data, etc.) 2/6

J.E.D.E.C.

2N385A	
2N388A	15/-
2N896	9/-
2N706	4/-
2N706A	6/6
2N711	7/6
2N132	10/-
2N192	5/-
2N1303	5/-
2N1304	6/-
2N1305	6/-
2N1306	8/-
2N1307	8/-
2N1308	10/6
2N1309	10/9
2N2147	17/-
2N2160	14/9
2N2646	10/-
2N3436	6/9

PLANAR BARGAIN


2N2928Y	3/-
or 4 for	10/-

Over 2,000 transistor and diode types ex stock.


Resistors: 1 Watt 5% Miniature type, low noise—high stability. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 & decades to 820K. 1-25 pieces 4d. 25-99 3d. 100 pieces or over, 2a. each.
10% tolerance, 1 Watt, 1 Meg-8.2 Meg., same price.
Preset potentiometers. Standard or Sub-miniature types, 20% tolerance. Lin. vertical or horizontal.
100, 250, 500 ohm, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1 Meg, 2.5 Meg, 5 Meg. All at 1/6d. each. Discounts for quantities over 12 of 1 value.

WIRELESS WORLD DIGITAL COMPUTER

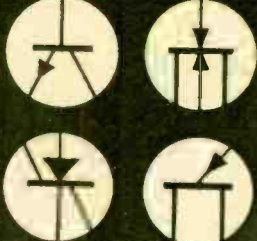Send for our complete part list. Competitive prices for all components. Transistors, Diodes, Resistors, Capacitors, Neons, Veroboard, etc.



BARGAINS IN SEMICONDUCTORS ALL TYPES



LST COMPONENTS

7 COPTFOLD ROAD BRENTWOOD ESSEX BRENTWOOD 7904 24 HOUR POSTAL SERVICE

FAIRCHILD AF 11 20W SOLID STATE AMPLIFIER KIT £8.8.0d Complete

Includes Printed circuits board, Semiconductors, Resistors, Capacitors, Heat sink and short circuit protection components. S.A.E. for details

1968 CATALOGUE over 40 pages AVAILABLE SHORTLY

POST & PACKING 9d. per order EXPORT ENQUIRIES WELCOME

TRANSISTOR MANUALS
R.C.A. 27/6d.
G.E. 29/9d.

RETAIL AND WHOLESALE SUPPLIED.

www.americanradiohistory.com

IMMEDIATE DESPATCH FULL SPARES AND SERVICE AVAILABLE



20 Amp. LT. SUPPLY UNIT

As supplied to Min. of Defence and Crown Agents for overseas Govt.
LATEST DESIGN HEAVY DUTY 12/24 VOLT D.C.
 Output: Adjustable up to **20 AMPS. CONTINUOUS** at 12/24 volts. **FULLY FUSED**, Neon indicator, 0-20 amp. meter. Size 16 x 12 x 20in high, in heavy gauge steel cabinet. Grey Hammer finish—Weight 50 lbs. Input: 220/230/240 v. A.C. 50 cycles.
ONLY £32.10.0 Plus 40/- C. & P. G.B. (Inland)

30 Amp. LT. SUPPLY UNIT

UP TO 18 v. D.C. WITH SMOOTH STEPLESS VARIATION
 Designed for CONTINUOUS use at max. loading

★ Fitted voltmeter and ammeter. ★ Instantaneous overload cut-out.
 Input: Mains A.C. Robust construction, 2 tone finish, steel case.

£55.0.0

C. & P. 40/- G.B. (Inland).

Entirely suitable for plating plants, Laboratory supplies, etc.

5 AMP. A.C. & D.C. VARIABLE SUPPLY UNIT

Specification: Output: 0-260 v. A.C. 0-240 v. D.C.

- ★ Smooth stepless voltage variation from 0-Max.
- ★ Current consistent throughout the controlled range.
- ★ Ammeter and voltmeter fitted, and neon indicator.
- ★ Fully fused input and output.

Strong steel case, with carrying handle and rubber feet. 11 x 7 x 14in. high. Made in England.

£30.0.0

C. & P. 40/- Gc. Britain (Inland).

CURRENT PRODUCTION — BUY DIRECT FROM MANUFACTURER



VARIABLE VOLTAGE TRANSFORMERS

Modern styling for modern equipment

'SLIDE-TRANS' & 'SLIDUP' MODELS

Fully rated current consistent at all points along the winding

AVAILABLE ONLY FROM I.M.O.



- ★ SMOOTH CONTINUOUS ADJUSTMENT
- ★ ALL MODELS SHROUDED FOR SAFETY (IDEAL FOR EDUCATIONAL AUTHORITIES)
- ★ BENCH OR PANEL MOUNTING
- ★ UP TO 260v. AVAILABLE FROM ALL MODELS

All models 230v. A.C. 50/60 c.p.s. input

1 Amp.	£4 . 10 . 0
2.5 Amp.	£5 . 17 . 6
5 Amp.	£9 . 0 . 0
8 Amp.	£13 . 10 . 0
10 Amp.	£18 . 5 . 0
12 Amp.	£19 . 10 . 0
20 Amp.	£32 . 10 . 0



C. & P. EXTRA

TRANSISTORISED MEGOHMMETER

- ★ PUSH BUTTON TO READ

500 v. - 1,000 Megohms. Superb, portable instrument. Supplied c/w batteries, probes and carrying case.

ONLY £25.0.0 C. & P. 7/6.



36 FT. AERIAL MAST

NEW LATEST PATTERN TUBULAR MAST

Check these vital points:

- ★ Made from 6 x 1 1/2in. Sheradized steel sections, for durability and strength.
- ★ Extra strong locating base.
- ★ Top cap fitted with pulley and halyard.
- ★ 2 sets (8) Rotproof Guys.
- ★ Rustproofed Steel Picketing Stakes.

ONLY £15.0.0

ex works

Carr. 20/- Returnable wood case 40/-

PORTABLE VARIABLE A.C. POWER SUPPLY UNIT

Designed for engineers whose requirements call for a visual indication of volts applied.

OUTPUT: 0-260 v. 1 1/2 amps.

INPUT:

230 v. A.C. 50/60 c.p.s.

Fitted with fuse, voltmeter, safety indicator on-off switch and lead.

Size 8 x 5 x 5in. high.

PRICE

£8.17.6

C. & P. 12/6



CONSTANT VOLTAGE TRANSFORMERS

BEAT WINTER!

AUTOMATIC MAINS STABILISER



ONCE AGAIN WE CAN EXPECT THE USUAL VOLTAGE DROPS DUE TO THE COLD WEATHER

- ★ No attention
- ★ No Maintenance
- ★ No Moving Parts
- ★ Corrected Wave

Input: 190-250 v. A.C. Output: 240 v. A.C.

Accuracy: ±1%. Capacity: 250 watts.

Maintain "spot-on" test-gear readings at all times

Weight: 21 lb. Fitted signal lamp and switch.

Size: 11 x 6 1/2 x 6in. high.

£12.10.0

C. & P. 20/-

LATEST SOLID STATE VARIABLE VOLTAGE CONTROLS

- ★ COMPLETELY SEALED
- ★ COMPACT AND COMPLETE
- ★ PANEL MOUNTING

230 A.C. Input 25-230 volts output

5 amp. model £8

10 amp model £13/5/-



PORTABLE TRANSISTOR TESTER

SUITABLE FOR PRODUCTION & LABORATORY USE

SPECIFICATION:


Alpha 0.7 to 0.997

Beta 5-300

ICO 0-50µA, 5mA.

Capable of measuring GERMANIUM AND SILICON DIODES.

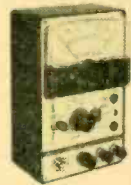DESIGNED WITH RESISTANCE SCALE 200 ohms to 1 Megohm as an ADDED FEATURE. Housed in heavy duty plastic case, c/w internal battery.



Only **£6.19.6**
 Plus 7/6 C. & P.


I.M.O. (ELECTRONICS) LTD.

(Dept. W.W.7), 313 Edgware Road, London, W.2.

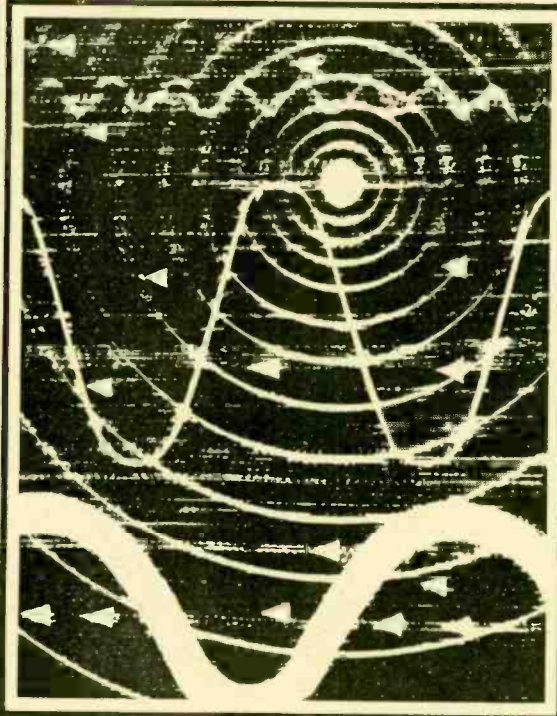01-723 2233/4

1968
April 27 — May 5

**Electrical Engineering
at the
Hanover Fair**



Hanover Fair — the words stand for a concentrated display of everything used in your particular field, opportunity for full quality and price comparison, priceless business information. Make your buying decisions in Hanover, where you can check many competitive offers simply by walking a few paces.

If you're interested in studying economic developments within the larger framework, Hanover is the ideal location. In just two decades Hanover has become one of the world's major market places, an assembly of more than 5,500 firms from thirty countries.
Make sure you see all this in 1968.

HANOVER FAIR

Today's Market
for Tomorrow's Needs



Schenkers Limited, Royal
London House, 13, Finsbury
Square, London, E.C.2
Telex: 22625

WW-136 FOR FURTHER DETAILS

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R6, 1R6, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 16/9. DAF96, DF96, DK96, DL96, 4 for 25/-.

1A7GT 7/8	7Y4 6/6	DF91 2/9	EF91 3/6	PCL84 7/-	UCC85 6/6
1H5GT 7/3	10F1 9/9	DF96 6/-	EF97 7/6	PCL86 8/3	UCF80 5/8
1N5GT 7/9	10F13 10/6	DH77 4/-	EF183 6/9	PCL86 8/3	UCF82 9/9
1R5 5/6	12AT7 3/9	DI81 12/6	EF184 5/9	PEN44 9/9	UCR81 6/9
1R4 4/9	12AU6 4/9	DK32 7/9	EI90 8/6	PEN36C15/-	UCL82 7/-
1R6 3/9	12AU7 4/9	DK91 5/9	EL33 8/9	PFL200 13/-	UCL83 8/9
1T4 2/9	12AX7 4/9	DK92 9/3	EL34 9/6	PL36 9/-	UF41 10/6
3A5 8/6	12K8GT 7/6	DK96 7/-	EL41 9/6	PL81 6/9	UF80 7/-
384 4/9	20F2 10/6	DL33 6/9	EL84 4/9	PL82 6/6	UF89 5/9
3V4 5/9	20L1 14/6	DL35 5/-	EL90 5/-	PL83 7/-	UL41 8/9
5U4G 4/6	20P1 9/-	DL92 4/9	EL95 8/-	PL84 6/3	UL44 20/-
5V4G 8/-	20P3 14/9	DL94 5/9	EM34 13/9	PL500 13/-	UL84 8/6
5Y3GT 5/-	20P4 17/-	DL96 6/-	EM80 5/9	PX25 10/6	UY41 5/6
3Z40 7/6	25U4GT11/6	DY96 5/9	EM81 6/9	PY32 8/6	UY85 5/9
6/30L2 11/9	30C1 6/6	DY87 5/9	EM84 6/3	PY33 8/6	VP48 10/8
6AL5 2/3	30C15 11/6	EABC80 6/6	EM87 7/6	PY80 5/3	VP1821 21/-
6AM6 3/6	30C17 12/6	EAF42 8/6	EY61 7/-	PY81 5/3	Z77 3/6
6AQ5 4/9	30C18 11/9	EB91 2/3	EY86 6/8	PY82 5/-	Transistors
6AT6 4/-	30F5 12/-	EBC33 7/-	EZ40 5/9	PY83 5/9	AC107 10/-
6AU6 5/6	30F11 12/6	EBC41 8/-	EZ41 6/9	PY88 7/3	AC127 6/-
6BA6 4/6	30FL4 12/6	EBF80 6/-	EZ50 4/6	PY800 5/-	AD140 15/6
6BE6 4/3	30L1 5/6	EBF89 5/9	EZ81 4/9	PY801 6/8	AF102 13/-
6B06G 15/-	30L15 14/-	ECC81 3/9	KT61 8/9	R19 6/6	AF115 6/6
6BJ6 6/9	30L17 13/-	ECC82 4/9	KT81 15/-	R20 12/9	AF116 6/6
6BR7 7/8	30P4 12/-	ECC83 7/-	N78 14/9	TH21C 9/6	AF117 5/-
6C86 6/6	30P12 11/6	ECB84 6/3	PC86 9/6	U26 11/6	AF118 8/6
6F1 7/9	30P19 12/-	ECC85 4/9	PC88 9/6	U26 11/6	AF124 7/8
6F13 3/6	30PL1 12/6	ECP80 7/-	PC97 5/6	U47 13/6	AF125 7/6
6F14 9/-	30PL13 14/6	ECP82 6/9	PC900 7/9	U49 13/6	AF126 7/-
6P23 12/6	30PL14 14/6	ECP86 9/-	PC94 5/6	U52 4/6	AF127 7/-
6K7G 11/8	35LGT 5/-	ECH85 6/-	PC989 11/-	U78 3/6	OC22 9/9
6K80 3/3	35W4 4/6	ECH82 10/-	PC189 8/9	U191 11/-	OC26 9/6
6K8GT 7/6	35Z4GT 4/6	ECH81 5/3	PCF80 6/6	U301 12/8	OC28 5/-
6L18 8/-	6053 12/6	ECH84 6/6	PCF82 6/-	U801 18/-	OC44 3/9
6V6G 3/8	AZ31 9/-	ECL80 6/-	PCF86 9/9	UABC80 6/3	OC45 3/3
6V8GT 8/8	B36 4/8	ECL82 6/3	PCF800 11/8	UAF42 7/9	OC71 3/6
6X4 5/6	B79 12/6	ECL85 7/9	PCF801 7/9	UB41 6/6	OC72 4/8
6X6GT 5/9	CCH35 9/-	EF39 3/9	PCF802 9/6	UBC41 6/9	OC75 5/9
7B6 10/9	DAC32 7/3	EF41 9/6	PCF805 11/9	UBF80 6/-	OC81 3/6
7B7 7/-	DAF91 8/9	EF80 4/9	PCF806 11/6	UBF89 6/9	OC81D 3/6
7C5 15/-	DAF96 8/-	EF85 5/-	PCF809 12/8	UBL21 9/-	OC82 5/9
7C8 6/9	DCX90 8/6	EF86 6/3	PCL82 8/6	UC92 5/-	OC82D 5/-
7H7 5/6	DF33 7/9	EF89 5/-	PCL83 8/6	UCC84 7/9	OC170 5/-

READERS RADIO

85 Torquay Gardens, Redbridge, Ilford, Essex. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra.
Any Parcel Insured against Damage in Transit 6d. extra.

transistor television receivers

T. D. Towers, M.B.E., M.A., B.Sc., M.I.E.E.
A.M.I.E.R.E.

This book covers virtually every aspect of transistors in television receivers, with examples drawn from the United Kingdom, U.S.A., France, Germany, Russia and Japan. Although transistor sets may never entirely displace valve operated, mains-driven, large screen sets, for personal-portable sets the transistor has no rival.

194 pp. 188 illustrations. 55s net 56s 3d by post.

* For the designer, and the interested serviceman, this is a book packed with information.

RADIO AND ELECTRICAL RETAILING

* He (the author) has done the job so thoroughly that his book—the first in the field—is likely to remain first in the field for quite a while.

MUSIC TRADES REVIEW

* ... gives the reader a clear perspective of the subject and provides an important chapter on servicing methods.

ELECTRICAL AND RADIO TRADING

available from leading booksellers

ILIFFE BOOKS LTD

Dorset House, Stamford St., London, S.E.1.

VIKING AMPLIFIER

50 WATT AMPLIFIER

An extremely reliable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money.

TECHNICAL SPECIFICATIONS

4 electronically mixed channels, with 2 inputs per channel, enables the use of 8 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets.

SENSITIVITIES AND INPUT IMPEDENCES
 CHANNEL 1 4MV. AT 470K. } These 2 Channels (4 inputs) are suitable for
 CHANNEL 2 4MV. AT 470K. } microphone or guitars.
 CHANNEL 3 200MV. AT 1M. } Suitable for most high output instruments
 CHANNEL 4 200MV. AT 1M. } (gram, tuner, organ etc).
 INPUT SENSITIVITY RELATIVE TO 10W OUTPUT.

TONE CONTROLS ARE COMMON TO ALL INPUTS.
BASS BOOST +12 db AT 60 Hz/s. **BASS CUT** -12 db AT 15 KHz/s.
TREBLE BOOST +11 db AT 15 KHz/s. **TREBLE CUT** -12 db AT 15 KHz/s.
 WITH BASS AND TREBLE CONTROLS CENTRAL -3 db POINTS ARE 30 Hz/s. AND 20 KHz/s.

POWER OUTPUT
 FOR SPEECH AND MUSIC 50 WATTS RMS. 100 WATTS PEAK.
 FOR SUSTAINED MUSIC 45 WATTS RMS. 90 WATTS PEAK.
 FOR SINE WAVE 38.5 WATTS RMS. NEARLY 80 WATTS PEAK.
 TOTAL DISTORTION AT RATED OUTPUT 3.2% AT 1 KHz/s.
 TOTAL DISTORTION AT 20 WATTS 0.15% AT 1 KHz/s.
 OUTPUT TO MATCH INTO 8 OR 15 OHMS SPEAKER SYSTEM.

NEGATIVE FEED BACK 20 db AT 1 KHz/s.
SIGNAL TO NOISE RATIO 60 db.
MAINS VOLTAGES. Adjustable from 200-250 V. A.C. 50-60 Hz/s. A protective fuse is located at the rear of unit.
VALVE LINE UP: Double purpose ECC83 x 3, EL34 x 2 and GZ 34.




PRICE
27 gns.

P. & P. 20/-

STAR SR 150 COMMUNICATION RECEIVER

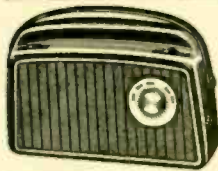Frequency range: 535 kc/s-30 Mc/s. 4 wavebands. 5 valve superhet. Incorporates BFO, bandsread tuning, "S" meter, external telescopic aerial and ferrite aerial. Built-in 4in. speaker. Easy-to-read dial. For 240 v. A.C. operation. Complete, brand new, with full instruction manual. 15 gns. P. & P. 10/-.



NEW! The DORSET TRANSISTOR PORTABLE RADIO with BABY ALARM Facilities

600 milli-watt solid state 7 transistor plus diode and thermistor. Completely modulated high quality portable radio featuring complementary N.P.N. and P.N.P. output stage. The comprehensive easy-to-follow drawings supplied make this the easiest-ever transistor radio set of parts, with the following features:

- ★ Simple connections to only 6 tags on the R.F./I.F. module, 31.F. stages, osc. coil and 3 transistors which, with their associated components are completely wired.
- ★ Only 4 connections on the A.F. module to complete the 4 transistor 600 milli-watt solid state amplifier.
- ★ Pre-aligned R.F./I.F. module built and tested.
- ★ A.F. module built and tested.
- ★ Fully tunable over M.W. and L.W. bands. M.W. 540-1,640 Kc/s. (557-1,833 metres). L.W. 150-275 Kc/s. (2,000-1,100 metres).
- ★ Intermediate Frequency 470 Kc/s.
- ★ Sensitivity: M.W. at 1 Mc/s 10 microvolts plus or minus 3 dB. L.W. at 200 Kc/s. 40 microvolt plus or minus 4 dB.

- ★ High Q internal ferrite rod aerial on both wavebands.
- ★ Class "B" modulated output stage with thermistor controlled heat stabilization. Class "B" output stage ensures long battery life. Current drain is proportional to the output level. Total current drain of the receiver under no signal conditions is 10-12 mA. At reasonable listening level 20-30 mA.
- ★ Extension sockets for car aerial input, tape recorder output (Independent of volume control) and Ext. Speaker.
- ★ All components (except speaker) mount on the printed circuit board. Easy to follow instructions. Size of cabinet 12in. long, 8in. high and 3in. deep.
- ★ Fingertip controls.

BRESGES Geared Motor
 240 V. A.C. Mains 50 Hz. 0.19 amp (65 watt). Ungeared speed 2,750 R.P.M. Geared speed 80 R.P.M. Constant Gear ratio 35:1. Reversible. Spindle dia. 12 mm. (0.473in.). Spindle length 1 1/2in. 7 1/2in. long x 4 1/2in. wide x 4 1/2in. deep. Cost £20, our price £7/19/6. 7/6 P. & P.

RADIO AND T.V. COMPONENTS (ACTON) LTD

21A HIGH STREET, ACTON, LONDON W.3.


SHOP HOURS 9 a.m. to 6 p.m. EARLY CLOSING WEDNESDAY.

Terms C.V.O. Goods not despatched outside U.K. All enquiries stamped add, envelope.

323 EDGWARE ROAD, LONDON, W.2. Early closing Thursday.
 PERSONAL SHOPPERS ONLY. All orders by post must be sent to our Acton address.

'ELEGANT SEVEN' MK IIIa SPECIAL OFFER

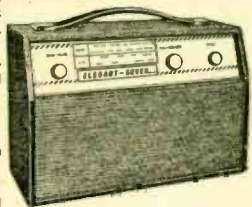Power supply kit to purchasers of "Elegant Seven" parts, incorporating mains transformer, rectifier and smoothing condenser. A.C. mains 200/250 volts. Output 9 v. 100 mA. 9/6 extra.



- ★ De luxe wooden cabinet size 12 1/2 x 8 1/2 x 3 1/2 in.
- ★ Horizontal easy to read tuning scale printed grey with black letters, size 1 1/2 x 2 1/2 in.
- ★ High "Q" ferrite rod aerial.
- ★ I.F. neutralization on each separate stage.
- ★ D.C. coupled push pull output stage with separate A.C. negative feedback
- ★ Room filling output 350 mW.
- ★ Ready etched and drilled printed circuit board back printed for foolproof construction.
- ★ Fully comprehensive instructions and point-to-point wiring diagram.
- ★ Car aerial socket.
- ★ Fully tunable over medium and long wave. 168-535 metres and 1,250-2000 metres.
- ★ All components, ferrite rod and tuning assembly mount on printed board.
- ★ Sin. P.M. Speaker.
- ★ Parts list and circuit diagrams 2/6 free with parts.

ONLY **£4.40** Plus 7/6 P. & P.

Buy yourself an easy to build 7 transistor radio and save at least £10. Now you can build this superb 7 transistor superhet radio for under £4/10/-. No one else can offer such a fantastic radio with so many de luxe star features.

MARCONI INDUSTRIAL TELEVISION CAMERA CHANNEL TYPE BD 871

Comprises a small Vidicon Camera type 4339C and its camera control unit type 4340G together with a suitable monitor or receiver these two units form a closed circuit camera channel. Suitable monitors type BD 879 are also available. Technical manuals with instructions and circuits are available. ONE ONLY. Complete with 3 monitors. £250.



FIRST QUALITY PVC TAPE

Size	Std.	850ft.	9/-	5in. L.P.	850ft.	10/6	ON EACH
7in.	Std.	1,200ft.	11/6	3in. T.P.	600ft.	10/6	1/6
3in.	L.P.	240ft.	4/-	5in. T.P.	1,800ft.	25/6	
5 1/2in.	L.P.	1,200ft.	11/6	5 1/2in. T.P.	2,400ft.	32/6	4 OR MORE
5 1/2in.	D.P.	1,800ft.	18/6	7in. T.P.	3,600ft.	42/6	POST FREE.
7in.	L.P.	1,800ft.	18/6	4in. T.P.	900ft.	15/-	

FOUR PLUS FOUR Stereo Amplifier

A superb High Quality, yet inexpensive stereo amplifier. Due to great demand we are now able to offer this precision made instrument at a fantastically low price. Its quality, reliability and styling has in no way been marred by its low price.

SPECIFICATIONS
 Elegant styled cabinet (sizes 16in. wide 5in. high, 8 1/2in. deep) in black rexine and woodgrained sides. Brushed aluminium front panel with contrasting black/silver knobs.

CONTROLS
 Stereo/Mono switch. Gram/Aux. switch. Volume left. Volume right. Treble (cut and lift). Bass (cut and lift). Separate on/off switch. Neon pilot indicator.

INPUTS AND OUTPUTS (per channel)
 Gram, Aux., Tape out and Speaker out. A switched mains socket is also provided at the rear of unit.

Employs Mullard valves throughout. ECC83 and 2X ECL 86. With a metal bridge rectification.

TECHNICAL SPECIFICATIONS
 Gram sensitivity 40 mv. at 1 KHz. Aux. sensitivity 50 mv. at 1 KHz. (sensitivities are given for rated output). 4 watts R.M.S. per channel (8 watts R.M.S. in monoaural position). Output matches into standard 3 ohms speaker system. Suitable 10in. x 6in. speakers are available at 29/6 each + 5/- P. & P. Bass control at 100 Hz lift +9db, cut -10 db.

Treble control at 10 KHz. Lift +8db, cut -13db. Total harmonic distortion 0.35% at 3 watts and 2% for rated output at 1 KHz. Negative feedback 13db at 1 KHz. Mains supply 220-250 v. A.C. 50-60 Hz. PRICE 13 gns. P. & P. 15/-.

600 mW SOLID STATE

4-TRANSISTOR AMPLIFIER

Frequency response -3dB points 90 c/s. and 12 kc/s. Price 15/- plus 1/- P. & P. 7 x 4 speaker to suit, 13/6, plus 2/- P. & P.

BSR TAPE DECKS 200/250 v. A.C. mains

- Type TD2. Tape speed 3 1/2 twin track, £6/19/6.
- Type TD10, 2-track, 3 speed, plus rev. counter, £7/19/6.
- Type TD10, 4-track, 3 speed, plus rev. counter, £9/5/- P. & P. on each 7/6.

3 TO 4 WATT AMPLIFIER

3-4 Watt Amplifier, built and tested. Chassis size 7 x 3 1/2 x 1in. Separate bass, treble and volume control. Double wound mains transformer, metal rectifier and output transformer for 3 ohms speaker. Valves ECC81 and 6V6, £2/5/- plus 5/6 P. & P.



M. I. P. PYROMETER

Temperature Range

50°F - 230°F and 10°C - 110°C


Built in a robust case, (5 1/2 in. x 4 in. x 1 1/2 in.)

Complete with probe and batteries.

Only £5.0.0. Plus 5/- P. & P.

A very useful instrument, directly calibrated in centigrade and Fahrenheit on an easy to read moving coil meter.

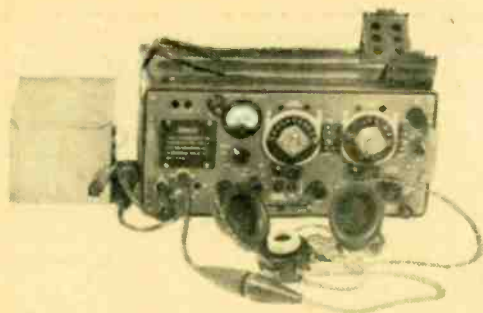Particularly suitable where heat-resistance plays an important part in the functions of:— Instruments, Cars, Cooling or Heating Systems, etc.




TRANS/RECEIVER TWO-TWO

This is one of the Latest Releases by the Govt. of an extremely recent R/T set covering 2-8 Mc/s. in two switched Bands, containing 13 Valves (3 EL32s in TX Output) which can be used for Morse CW or R/T. Also has Netting Trimmer, BFO, RF & EF Controls, Switched Meter for checking all parts of set, Size 17in. X 8in. X 12in. Power required LT 12 volts DC, HT 325 Volts D.C. Supplied Brand New and Boxed with Headphones & Mike, also Two Spare Valves and Circuit of set. Few only at £5/10/-, Carr. 50/- . New Plug in Power Supply made by us for either 12 volts D.C. Input £5/10/- or 200/250 Volts A.C. £3/17/6.

LARGE QUANTITY OF SARAH V.H.F. TRANS/RECEIVERS AVAILABLE FOR IMMEDIATE EXPORT.


General Information. This set is normally carried in the life jacket of Airmen, it is a complete miniature lightweight radio Trans/Receiver, which is used to give a Beacon plus two way speech communication in the event of finding themselves in the sea. It comprises a Transmitter-Receiver, a speech unit, a coding unit and a power supply either Battery OR Transistor. These three items are permanently interconnected and all units are completely sealed and watertight using a combined speaker/Mike, Press to talk or listen buttons, Fold up Aerial, a total of three Valves are used, power required 6.3 Volts LT 90 Volts and 435 Volts DC RT. Frequency 243Mc/s. Transmitter output pulse power—Beacon 15 Watts, Talk 3 Watts. Supplied in maker's boxes in Grade 1 condition singly at 45/-, post 5/- with circuit. New batteries if available 7/6 each.

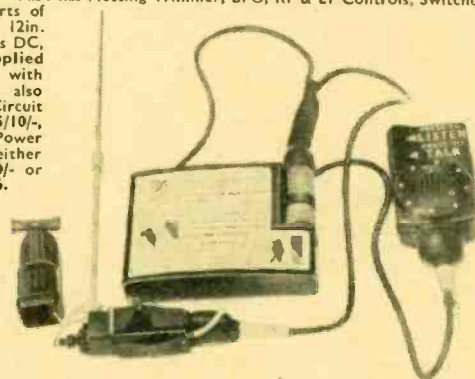

FEW ONLY LEFT!

WALKIE-TALKIE MK111 AND CRYSTAL CALIBRATOR NO.9

We have a few of these V.H.F. 12 Valve Transreceivers operating on 3 switched channels between 60 Mc/s-95 Mc/s, complete with all 6 Crystals, Headphones, Mike, Mobile Aerial and Dipole Aerial, all Connectors plus Alloy Tripod for mounting the set on. Power Input 12 volts D.C., TX output 3 Watts, Internal Speaker (All Valves BG7). All Air Tested O.K., Supplied in good Grade 2 Condition at £10/- each, Carr. 30/- . Also available in Matched Pairs £25 per pair, Carr. 30/- Tested.

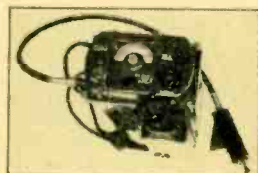

JOHN'S RADIO

OLD CO-OP, WHITEHALL ROAD,
DRIGHLINGTON, BRADFORD.
TEL.: DRIGHLINGTON 732

TITANIUM CONE LOUDSPEAKERS

TITANIUM CONE—provides the highest standard of definition ever achieved.

BERYLLIUM COPPER SUSPENSION—provides powerful low-distortion bass.


MASSIVE CERAMIC MAGNET—for large and easy power handling.

HIGH "PERFORMANCE TO SIZE" RATIO—securing deep fundamental from small systems.

MODULAR APPROACH—allows flexibility of system design.

VERSATILE—the ideal driver for the home constructor.

HIGH DEFINITION PRODUCT

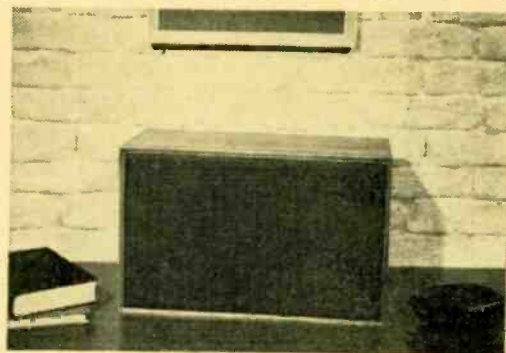

The "Titan-Mini" is a no compromise bookshelf system employing a Titanium Cone Loudspeaker module. The remarkable characteristic of the hyperbolic titanium cone lies in its ability to reproduce detail in complex sound with hitherto unheard of accuracy. Due to the beryllium copper suspension stabilising the free air resonance the cabinet is designed as a low friction phase inverter and provides the perfect load to the driver.

For further details on this unique product please request from:



AUDIO & DESIGN LIMITED
40, QUEEN STREET MAIDENHEAD BERKS. TEL. 25204

BARGAIN OPPORTUNITIES FROM




Amplifiers

IN KIT FORM AND COMPLETE

MULLARD

10-10

STEREO

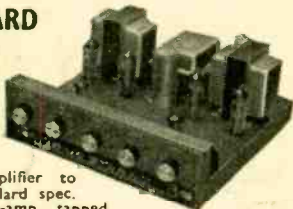

Valve amplifier to exact Mullard spec. With pre-amp, tapped o/p transformer 3 and 15Ω all controls, H.T. and L.T. outlet, mono, stereo and speaker phase switching. Complete with escutcheon, knobs, plugs, etc. Ready built (p. & p. 12/6) **£20.0.0**

In kit form with chassis, knobs, plugs, etc. (p. & p. 12/6) **£17.10.0**

MULLARD 5-10 MONO

5 valve 10 watt basic amplifier, complete with valves and instructions. (p. & p. 7/6) **£9.19.6**

With passive network and control panel (p. & p. 7/6) **£11.19.6**

2 valve pre-amp and control assembly, complete kit with valves and instructions. (p. & p. 6/-) **£6.12.6**

SPECIAL MULLARD 2+2 PRE-AMP

Stereo pre-amp and control unit. Complete kit with valves and instructions. S.A.E. brings details. BUILT—13 gns. Kit, complete 10 gns. (P. & P. either 7/6).

PEAK SOUND SA 8-8

14 Transistor Kit builds into superb hi-fi amp. 8W per channel (16W mono) with integrated pre-amp to take high quality ceramic p.u. Unusually easy to build by following the instructions (1/6 purchased separately and refunded when kit is bought). This makes one of the best and most economical stereo transistor amps., we have ever offered. All purchases backed by TRS service facilities. When built and fitted in its special cabinet the SA 8-8 equals the best in modern styling.

AMPLIFIER KIT (p. & p. 4/-) **£9.10.0**

POWER PACK KIT (p. & p. 4/-) **£2.10.0**

MODERN SLIMLINE WOOD CABINET (p. & p. 5/-) **£2.10.0**

COMPLETE ASSEMBLY post free if ordered at same time. **£14.10.0**

7 VALVE AM/FM RC CHASSIS

A superbly powerful high performance instrument for the keenest enthusiasts. Provides tuning on long, medium and F.M. wavebands. Excellent sensitivity. Permeability tuning on F.M. Large clear dial, A.V.C. good neg. feedback. Magic eye 3W output. A.C. 220/250V. Circuit diagrams available. Aligned, tested and ready for use (Carr. and ins. 7/6). S.A.E. brings full details. **£13.19.6**

SINCLAIR Z.12 AMPLIFIER

This famous amplifier operates from 6 to 20V D.C. and is adaptable to a wide range of applications because of its very small size. Supplied ready built with comprehensive instructions 89/6 manual. Post free.

SINCLAIR STEREO 25

De luxe pre-amp control unit for use with two Z.12s. Smart front panel and knobs. Ready built. Post free. **£9.19.6**

SINCLAIR PZ.3 Power supply unit for two Z12s and stereo 25. Post free **79/6**

JUST INSTALLED—A new arrangement enabling you to hear in our shop any combination of our advertised amplifiers, speakers, tuners, etc. Personal shoppers are particularly invited to come along and hear this for themselves.

SHOPPING BY POST

Please send cash with Order or pay C.O.D. Please mention "Wireless World".

POSTAGE. Unless stated add 1/- on 1lb. orders, 1/9 on 1lb., 3/6 on 2lb., 5/- on 6lb., 6/6 on 10lb., 8/- on 14lb. Over, 10/6.

GARRARD UNITS AND PLINTHS

FOR IMMEDIATE DELIVERY

LM3000 Record Player with 9T.A. Stereo Cartridge. Brand new as from factory. **£8.15.0**

AT.60 Mk. II De-luxe Auto-changer, diecast turntable. Less cartridge **£11.19.6**

SP.25 De luxe single record player, diecast turntable Less cartridge. **9 1/2 gns.**

Packing and carriage on any one of above 7/6 extra.

Garrard Plinth. Ideal mounting for the Garrard Units offered here. Will readily suit any hi-fi set-up. In fine Teak Complete with useful soft plastic dust cover. Carriage and pack 5/- **75/-**

Garrard clear-view rigid perspex cover (carriage 3/6) **57/6**

CARTRIDGE OFFER
The following are offered to all purchasers of GARRARD UNITS AND PLINTHS:
MONO
5NB Turnover crystal
17/6
TCSM crystal 25/-
Acos GP 91-1 19/6
STEREO
Ronette 1058, 32/6
Sonotone 9TA/MC, 37/6
Ditto with diamond 47/-
DECCA DERAM—diamond stylus. List 94/6. our price 79/6.

6 VALVE AM/FM TUNER



Med. and V.H.F.—6 valves metal rectifier. Self-contained power unit. Magic-eye, 3 push-button controls. Diode and high output sockets. Illuminated 2-colour dial. chassis 11 1/2in. x 4in. x 5 1/2in. A.C. 200/250 v. Unbeatable value. Complete kit, inc. Power Pack as illustrated, 11 gns. Carr. 7/6. Ditto less Power Pack, 10 gns. Carr. 7/6. Circuit and Const. details 4/6. Free with kit.

SINCLAIR MICROMATIC AT NEW REDUCED PRICES

The world's smallest radio now includes hi-fi magnetic earpiece, yet costs even less. Complete kit formerly 49/6 59/6, now **49/6**


Ready built and tested 59/6 formerly 79/6, now **59/6**

SINCLAIR MICRO FM Complete kit for building 7-transistor cigarette packet size tuner/receiver unit. For use with amplifier, etc. or pocket receiver. With earpiece and **£5.19.6** telescopic aerial.

TRS FM DECODER

Based on Mullard design and produced by T.R.S. Built-in indicator. 6-transistor model, readily adaptable for use with valve tuners as well. For 9-15 v. operation. Complete kit with Mullard specified inductors already aligned. **£5.5.0** (p. & p. 2/6).

EXCLUSIVE TRS TAPE WALLET OFFER

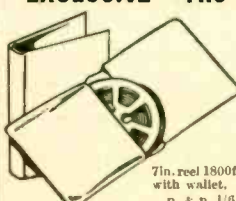

With each reel of this fine tape by an internationally famous manufacturer we give you a beautifully made wallet strongly made in simulated leather with space for a reel of tape each side. This is professional quality full frequency tape with metallised leader/stop foils. These library wallets solve once and for all the problems of storing tapes efficiently and tidily.

5 1/2in. reel, 1200ft. 17/6 5in. reel, 900ft. 12/6 with wallet.
7in. reel 1800ft., 22/6 TAPE REELS—7in. 2/3; 5 1/2in.—2/-; 5in.—2/-; 3in.—1/3 (p. & p. 6d.).
p. & p. 1/6 per reel

You can start to enjoy not only the bargains to be found in TRS latest 8-page printed list, but the personal service TRS give with every transaction however large or small. SEND 6d. FOR LATEST TRS LIST TODAY.

FOR ONLY 6d.

LARGE STOCKS OF TRANSISTORS. TRANSISTOR COMPONENTS. COILS. SWITCHES. VALVES. SPEAKERS. ETC. ALWAYS AVAILABLE AT KEENE'S BEST PRICES.
VEROBOARD—All standard sizes, including 2 1/2in. x 5in., 3/8; 2 1/2in. x 3 1/2in., 3/-; 3 1/2in. x 5in., 5/2; 3 1/2in. x 3 1/2in., 3/9; 2 1/2in. x 1 7/8in., 12/6. All accessories and tools in stock.
STEREO BALANCE CONTROLS. Logi Anti-Log 5K, 1 or 2 Meg. 9/- ea.
RESISTORS—Modern ratings, full range 10 ohms to 10 megohms. 10% 1/- W., 4d. each; 20% 1W, 6d each; 2W 6d each; 5% Hi-stab 1W, 5d. each; 1W, 6d each; 1.2-10 meg. 10% 1W, 4d each; 1W, 5d 5d each. 1% Hi-stab, 1W, 1/6 each (below 100Ω, 2/- each).
WIREWOUND RESISTORS—25Ω to 10kΩ 5W, 1/6 each; 10W, 1/9 each. 15W, 2/3 each.
CONDENSERS—Silver Mica. All values 2pF to 1,000pF, 6d each. Ditto ceramic. 9d. Tub. 450V T.C.O., etc. 0.001-0.01 mF. 10d each; 0.1-350V, 10d each; 0.02-0.1mF, 500V, 1/- each. TCC 350V 0.25, 1/9 each; 0.5, 2/- each.

CLOSE TOLS/MICAS—10% 5-600pF, 9d; 100-5,000pF, 1/-; 2-100pF, 11d 100-350pF, 1/2; 270-800pF, 1/-; 800-5,000pF, 2/-.
ALUMIN. CHASSIS—18g. Plain undrilled, folded four sides, 2in. deep. 6in. x 4in., 4/6; 8in. x 6in., 5/9; 10in. x 7in., 6/9; 12in. x 6in., 7/6; 12in. x 8in., 8/- etc.
TYGAN FRET or Vynaf speaker fabric, 12in. x 12in., 2/-; 12in. x 18in., 3/-; 12in. x 24in., 4/-, max. width 48in.
BONDACOUST Speaker Cabinet Acoustic Wadding, approx. 1in. thick 18in. wide, any length cut, 2/3 ft., 6/- yd.
SILICON RECTIFIERS—Miniature—Wire ended, 1in. x 1in. MULLARD Type BY100 800 v. 500mA, 8/6, BY236 250 v. 500mA, 5/-, BY114 450 v. 500mA 8/-, BY237 500 v. 500mA, 6/6.
NEON MAINS INDICATOR LAMP. Wire ends, 3/6.
ENAMELLED COPPER WIRE, 2 oz. reels—14c-20c, 3/-; 22c-28c, 3/6; 30-34g 4/3; 36-38g, 4/9; 38-40g, 5/-.
TINNED COPPER WIRE, 10g-22g, 2 oz. 4/-.

SAVE ON SPEAKERS

TRS TEAK ENCLOSURES, size 2 1/2in. x 1 1/2in. wide x 7 1/2in. Cut to take tweeter and 8in. or 10in. unit to order. Acoustically loaded for finest quality FANTASTIC **£4.15.6** VALUE at (Add 7/6 for post cost of packing and forwarding)

15 OHM UNITS
8in., 15,000 lines, ceramic magnet 10 watts. Foam suspended cone **£5.19.6**
10in. Goodman Axiom **£7.5.0**
Type 10 **£5.15.0**
8in. FR8 **£5.15.0**
£4.10.0
W B 8in. HF12 **£6.0.0**

Goodman's 8in. Axiette **£6.0.0**
The above units are particularly recommended for use with the TRS Teak Acoustic Enclosure and wherever high-fidelity standards are required at modest outlay.
EMI. 3-ohm Elliptical speaker 1 1/2 x 8in. heavy duty **55/-** unit
SINCLAIR Q.14
A remarkable new reproducer from a famous house, 9 1/2in. sq. 15 ohms. Truly superb quality obtainable in stereo, **£6.19.6** each

NEW IMPROVED "CIR-KIT"
Now incorporates 0.1in. matrix board in convenient sizes, together with improved "CIR-KIT" material. Easier than ever to use. No drilling necessary. See HI-FI NEWS, Nov. issue. 5ft. spool of "CIR-KIT" 2/-, "CIR-KIT" Matrix Board, 6in. x 3 1/2in., 4/-; 3 1/2 x 2 1/2in., 2/6; 3 1/2in. x 2in., 1/8.

B.B.C. 2—U.H.F. Low Loss Cable, 1per yard 1/8.
80 OHM CO-AX CABLE—Famous make—1st Grade Quality. Semi-air-spaced, low-loss, high quality 80 ohm Aeraxial Cable. Stranded Conductor, standard 1in. dia. approx. 6d per yard. Special Discount for Quantity Lengths: 20 yds., 1/-; carr. 2/-; 40 yds., 17/6; carr. 3/-; 60 yds., 25/-, carr. 3/6. Super Aeraxial (Pine quality), 1/044, 1/3 per yard.
COAX CABLE ACCESSORIES
Coax Plug (Aerial) etc., each, 1/3
Car Radio Type, EKO, etc., 1/6
Coax Sockets, Chassis Mounting
Helling Lee, etc., each, 1/-
Coax Sockets (cable end type) each 1/9
Cable Couplers—back-to-back sockets 1/6
Outlet Boxes—1 in 1-out, each, 4/-
Ditto 1 in—2 out compensated, 10/- each.
Attenuators Plug in type Aerialle
Adjustable 4dB-20dB, each 7/6
Band 1-Band 2-Band 3 Cross over Unit (Splitter Box) 13/6
Band 1, Band 3 10/6

TRS SPECIAL SERVICE IN TRANSFORMERS


All types, and chokes available in singles or small production runs to specification at competitive prices. Enquiries invited. Private enquiries, please send S.A.E.

TRS RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK RD., THORNTON HEATH, SURREY.

Established 1946
Telephone: THO 2188 Hours 9 a.m.—6 p.m. (1 p.m. Wednesday) Few doors from Thornton Heath Stn. (Southern, Victoria Section)

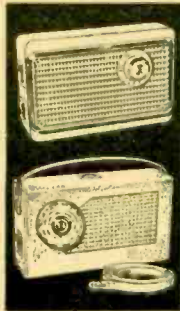BUILD YOURSELF A QUALITY TRANSISTOR RADIO!



TRANSONA FIVE MED. LONG & TRAWLER BAND. 5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, 2 1/2 in. speaker, 6 1/2 x 4 1/2 x 1 1/2 in. Total Building Costs 42/6. P. & P. 3/6. Plans and Parts list 1/6 (free with parts).

MELODY SIX. MED & LONG WAVES. 6 transistors and 2 diodes. Push-pull output, tuning condenser, ferrite rod aerial. 3 in. speaker, etc. 6 1/2 x 3 1/2 x 1 1/2 in. Total Building Costs 59/6. P. & P. 3/6. Plans and parts list 2/- (free with parts).



POCKET FIVE. MED. & LONG WAVES & EXTENDED MED. WAVE BAND. 5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, 2 1/2 in. speaker, etc. 5 1/2 x 1 1/2 x 3 1/2 in. Total Building Costs 39/6. P. & P. 3/6. Plans and parts list 1/6 (free with parts). Also available **POCKET FIVE MEDIUM AND LONG WAVE VERSION** with miniature speaker 29/6. P. & P. 3/6.

SUPER SEVEN. MED. LONG & TRAWLER BAND 7 transistors and 2 diodes. 3 in. speaker, 2 R.F. stages, push-pull output, etc. 7 1/2 x 5 1/2 x 1 1/2 in. Total Building Costs 69/6. P. & P. 3/6. Plans and parts list 2/- (free with parts).



ROAMER SEVEN Mk. 4. 7 wavebands—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. 7 transistors and 2 diodes. Ferrite rod aerial and telescopic aerial. Socket for car aerial. 7 x 4 in. speaker. Airt spaced ganged tuning condensers, etc. Size 9 x 7 x 4 in. Total Building Costs 85/10/6. P. & P. 6/6. Plans & parts list 3/- (free with parts).



ROAMER SIX. 6 wavebands—MW1, MW2, SW1, SW2, LW and Trawler Band. 6 transistors and 2 diodes. Ferrite rod and telescopic aerials. 3 in. speaker. Top grade components. Size 7 1/2 x 5 1/2 x 1 1/2 in. Total Building Costs 79/6. P. & P. 3/6. Plans and parts list 2/- (free with parts).

RADIO EXCHANGE. 61 High Street, Bedford.

Phone: 52367

Callers side entrance Barratts Shoe Shop. Open 9-5 p.m. (Sat. 9-12.30 p.m.)

MARCONI AUDIO TESTER, TYPE TF89
This directly calibrated AF oscillator from 50c/s to 12kc/s has a maximum output of 300mV into 600 ohm and is fitted with an output level meter and 600 ohm ladder attenuator of 0-50dB. An alternative 5,000 ohm outlet is provided and the level in each case is continuously variable. AF measurements; the voltmeter may be used for AF inputs (external) over the ranges of 0 to 80V in 4 ranges, providing a very useful facility. Supplied in excellent condition and working order for only £18.10.0. Power supply 240V a.c. (internal).

COSSOR DOUBLE BEAM OSCILLOSCOPES TYPE 1035

An attractive end of contract run enables us to offer these fine professional scopes in perfect working order at only £25 each plus 25/- P. & P. Brief technical spec.: 4 in. flat face C.R.T.; bandwidth 20c/s to 10Mc/s; timebase repetitive, triggered or single stroke 15µsec to 150msec; size 16 in. x 11 in. x 19 in. Also Cossor 1049 DC Coupled DB Scope same size and appearance as 1035. Price £30 plus 25/- P. & P.

DIGITAL VOLTMETER

For the first time ever, we proudly present a three digit a.c./d.c. voltmeter for less than £100! Manufactured by the world-famous Hawker Siddeley Group at its Gloucester Works, the Digimeter Type B.I.E. 2123 is a fully transistorised multi-range instrument possessing the following distinctive features:

Electrical Characteristics: D.C. ranges: 10mV to 400V in four ranges (1,000V for positive voltages). Accuracy: the greater of ±0.1% of ±1 digit. A.C. ranges: 100mV to 250V r.m.s. in three ranges. Accuracy: the greater of ±0.5% or ±1 digit over the frequency range 30c/s to 10kc/s. Range change is manual. Input impedance: D.C.-15MΩ on two lower ranges. 1MΩ on two higher ranges. A.c.-a.c. coupled, approximately equivalent to a shunt impedance of 8KΩ in series with the parallel impedances 180KΩ and 550pF. Input characteristics: Single ended, floating. The potential between terminal connected to 0V and earth should not exceed 400V d.c. or 250V a.c. Input filter: 55dB attenuation at 50c/s. Conversion time: 300msec.

Sampling rate: 1 reading per 2sec. or manually controlled. Power Supply: 100/120V; 200/250V 50 c/s. **Mechanical Characteristics:** Dimensions: 10 1/2 in. high x 7 in. wide x 13 in. deep. Weight: 15lbs. Display details: Three digit with decimal point indication. Character height 1 in. At the price we can offer these instruments no laboratory can afford to be without one! They are ideally suited to production and inspection application. Brand new in manufacturer's packing. With Handbook. **£92.10.0** Carriage extra at cost

IMMEDIATE DELIVERY!

SOLARTRON LABORATORY OSCILLOSCOPE TYPE 711/S2

This magnificent scope will take pride of place in any service dept., college or university, offered at one-fifth of manufacturer's price, in perfect working order and excellent condition, £80 plus carriage. Brief specification: bandwidth DC-7Mc/s; sensitivity 3mV/cm to 100V/cm; sweep velocity 0.33cm/sec to 3.3cm/µsec; X expansion variable up to X 10; size 16 in. x 13 in. x 27 in. deep.

MARCONI AF ABSORPTION WATTMETER TYPE TF938/CT44

Designed to measure the power output of all audio equipment in the range of 10 micro watts to 6 watts in 3 ranges. Impedance 2.5 to 20Ω switched in 11 ranges. Indication to large 5 in. meter, a small portable modern instrument. Price £25 plus P. & P. 12/6.

SOLARTRON CALIBRATING UNIT AT203

Providing an output range 10µV to 10V, in the frequency range of DC to 300kc/s. An extremely useful instrument of high accuracy for calibrating meters, and research work where the voltage output must be easily selected and of high standard. Offered in first class condition, fully tested, for 240V a.c. supply at £50.

P. F. RALFE

Radio & Electrical Supplies
423 GREEN LANES, HARRINGAY,
LONDON, N.4. MOUNTVIEW 6939

SPECIAL OFFER OF COLVERN 10 TURN HELIPOTS TYPES CLR26/1001/9

Values: 1,000Ω and 100kΩ. Brand new stock. Price 30/-, P. & P. 1/6.

POWER RHEOSTATS

3 ohms 8.5A, 35/-, P. & P. 3/6.
7.5 ohms 5.5A, 35/-, P. & P. 3/6.
50 ohms 1.5A, 12/6, P. & P. 1/6.
3kΩ 75W, 12/6, P. & P. 1/6.
All heavy duty types Toroidal wound on ceramic formers.

COMMUNICATIONS RECEIVERS

Marconi CR150/3. 2-60Mc/s Double-conversion, crystal calibrator, etc. C/w case, in as new condition. Only £35. Mains P. S. U. £5.
AR88D, like new, 540kc/s-32Mc/s, £55.
Murphy B40 640kc/s-30.5Mc/s. Recond. to maker's specification, £37.
Redifon R50M 94Kc/s-32Mc/s in 8 bands, perfect condition, £75.

INDUSTRIAL POWER AMPLIFIERS

Output 175 watts can be supplied with variable frequency oscillator 10c/s to 14kc/s. C/w with all usual facilities for, 19 in. rack mounting supply volts 250V a.c. Price £75 + carriage.

CAPACITANCE BRIDGE ELECTROLYTIC

B.P.L. Cat. No. ZD00506. Measures capacitance under full working loads (variable voltage selection), easy to operate. C/w voltmeter, leakage current meter, balance indicator, discharge switch, etc. Range 2 mfd. to 2,200 mfd. A modern instrument in new condition, and guaranteed accurate. Price £35, P. & P. 20/-.

STC MOVING COIL STUDIO MICROPHONES TYPE 4035A

A limited quantity of these superb low impedance microphones for sale at approx. one-third of maker's price. C/w type 4069A jack plug in as new little used condition. Price £7/10/-, P. & P. 3/6.

WESTON RF AMP METERS 0-3A

Two inch flush round panel mounting, black scale, white pointer. These first grade meters are offered now at 25/-, P. & P. 2/6.



POWER SUPPLY 22 £14.0.0 TRANSISTORISED

6d. STAMP FOR ALL LEAFLETS

NOMBREX

NEW STYLE IMPROVED INSTRUMENTS
OTHER MODELS AVAILABLE—

- R.F. GENERATOR 31 £12.10.0
- C.R. BRIDGE 32 £10.10.0
- INDUCT. BRIDGE 33 £20.0.0

SEE PREVIOUS ISSUES FOR DETAILS
ALL IN FULL PRODUCTION

POST & PKG. 6/6 EACH EXTRA


NOMBREX LIMITED - EXMOUTH - DEVON



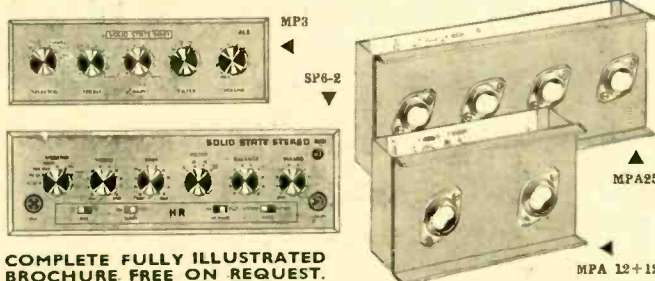A. F. GENERATOR 30 £19.10.0 TRANSISTORISED

TRADE AND EXPORT ENQUIRIES INVITED

**NEW SOLID STATE HIGH FIDELITY EQUIPMENT
POWER AMPLIFIERS—PRE-AMPLIFIERS
POWER SUPPLIES—BRITISH MADE**



COMPLETE FULLY ILLUSTRATED BROCHURE FREE ON REQUEST.

We PROUDLY PRESENT THIS RANGE OF AUDIO EQUIPMENT developed from DINSDALE Mk. II—each unit or system will compare favourably with other professional equipment selling at much higher prices.

Brief details are below:—

SYSTEM	COMPRISING	SYSTEM PRICE
★ A	5 watt mono for 3 to 5 ohm speakers	£10.30
★ 1	12 watt mono for 3 to 5 ohm speakers.	£13.17.6
★ 2	12 watt mono for 12 to 16 ohm speakers.	£14.12.6
★ 4	24 watt mono two channel for 12 to 16 ohm speakers.	£20.15.0
★ 8	20 watt mono/stereo for 12 to 16 ohm speakers.	£24.0.0
★ 9	24 watt mono/stereo for 3 to 5 ohm speakers.	£26.15.0
★ 14	40 watt mono/stereo for 7½ to 16 ohm speakers.	£29.10.0

VHF FM TUNER 87/105 Mc/s Transistor Superhet. Geared tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3½ x 2½ in. Complete with dial plate. 5 Mullard Transistors, Plus 4 Diodes. (Cabinet Assembly 20/- extra).



TOTAL COST TO BUILD £6.19.6 P.P. 2/6

FM STEREO DECODER

7 Mullard Transistors. Printed Circuit Design with Stereo Indicator. For use with any valve or transistor FM. Uses pot cores to Mullard design and ger. and silicon transistors. As used by B.B.C. and G.P.O. Complete Kit Price **£5.19.6 P.P. 2/6**



BUILD A QUALITY TAPE RECORDER

using **MARTIN RECORDAKITS**
★ **TWO-TRACK.** Deck £10/10/0. Martin Amplifier, £14/19/6. Cabinet and speaker 7 gns. Complete kits with FREE 7in. 1,200ft. tape, spare spool. Today's Value £45. **27 gns. P.P. 15/-**
★ **FOUR-TRACK.** Deck £13/10/0. Martin Amplifier £15/19/6. Cabinet and speaker 7 gns. Complete kits with FREE 7in. 1,200ft. tape, spare spool. Today's Value £50. **30 gns. P.P. 15/-**



MW/LW QUALITY TRANSISTOR RADIO TUNER

Fully tunable superhet with excellent sensitivity and selectivity. Complete with front panel, 9 volt operated. For use with any amplifier or tape recorder. **TO BUILD £3.19.6**



MANUFACTURERS We wish to Purchase large quantities of **NEW TRANSISTORS & DEVICES**—Please write or phone (01) 723-1008/9, EXTN. 4.

QUARTZ CRYSTALS
1 Mc/s. HC6U sub-min. 20/-
6/12 volt 80C oven Cathodeon ... 22/6
1 Mc/s. plus 100 kc/s. 3 pin ... 22/6
Send for list of 500 types. 1/- post paid

NUMICATORS
Mullard Z520M with base ... 22/6
Hivac YN3 wire leads. 15/-
931A photo mult. with base... 60/-
Z801u Tube 15/-

MAYFAIR PORTABLE ORGAN

BELGRAVIA CONCERT ORGAN
details on request



TOTAL COST 99 gns
Deferred terms available

- ★ Fully TRANSISTORISED POLYPHONIC British design.
- ★ Build this superb Instrument STAGE BY STAGE in your own home.
- ★ A Truly portable instrument for all enthusiasts.
- ★ Call in for a DEMONSTRATION

ORGAN COMPONENTS

We carry a comprehensive stock of organ components for TRANSISTOR AND VALVE FREE PHASE designs: complete details on request.

AUTO-BAN TRANSISTOR CAR RADIO British Made


BUY NOW!



6-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wavechange. Supplied built, boxed, ready to use with Speaker and Baffle. Car fixing kit and manufacturers' current guarantee. special Bargain Offer. Positive or Negative Earth. **LIST PRICE 12 GNS.** De-luxe Push-button version **£11/19/6. P.P. 4/8. £9.9.0** Send for details on our range of Car Radios.

PORTABLE GEIGER COUNTERS FOR MEASUREMENT OF RADIO-ACTIVITY

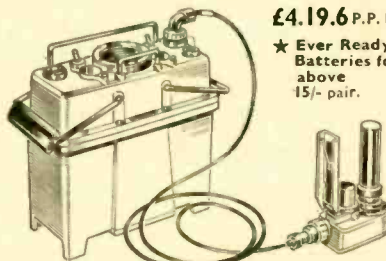Supplied complete with instructions, haversack, cables and probe. List price £70. **BRAND NEW**



£4.19.6 P.P. 10/-
★ Ever Ready Batteries for above 15/- pair.

GARRARD RECORD DECKS



COMPLETE RANGE FROM £5.19.6
SEND FOR ILLUSTRATED BROCHURE

Full details on advertised products free on request.

SALFORD 193A XTAL CHECKER

110/250v A.C. In new condition. **£12.10.0 plus carriage 10/-**

TRANSISTORS SEMICONDUCTORS

SEND FOR NEW 1968 FREE LIST No. 36 OF 1000 TRANSISTOR DEVICES.

- We have the
- ★ **LARGEST RANGE—OVER 1000 TYPES**
- ★ **COMPETITIVE PRICES**
- ★ **1st GRADE STOCKS**
- ★ **FULLY GUARANTEED**

24-PAGE ILLUSTRATED BROCHURE LISTING 2,000 DEVICES. Data and circuits including Valve and Quartz Crystal lists. 1/- post paid.

BUILD THESE PW/PE DESIGNS

- I.C. F.M. TUNER (with CA3014) ... 99/8
- ANTI-DAZZLE MIRROR ... 79/8
- EXPLORER ... £4/5/- with drilled chassis and cabinet
- STABILISED POWER SUPPLY. ... 49/8
- PHOTO FLASH SLAVE UNIT ... 42/6
- SOLID STATE IGNITION ... £6/19/6
- SWITCHED F.M. TUNER. 77/8
- THYRISTOR POWER CONTROLLER*

Parts LIST and PRICES ON REQUEST*

CATALOGUE LATEST EDITION 225 PAGES. 6,000 ITEMS. 1,000 ILLUSTRATIONS.

- ★ 20 pages of transistors and semi-conductors devices, Valves and Crystals.
- ★ 150 pages of components and equipment.
- ★ 50 pages of microphones, decks and Hi-Fi equipment.



The most COMPREHENSIVE—CONCISE—CLEAR COMPONENTS CATALOGUE in G.T. BRITAIN. Complete with 10/- worth DISCOUNT VOUCHERS.

Send today 8/6 POST PAID

FREE WITH EVERY COPY.


HENRY'S RADIO LTD.



303 EDGWARE ROAD LONDON, W.2

WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND LIST FOR QUOTATION.
PHONE 01-723 1008/9
OPEN MON-SAT. 9 a.m.-6 p.m., THURS. 9 a.m.-1 p.m.

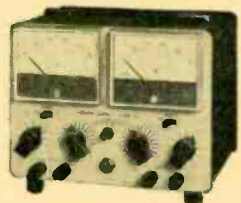VOLTMETERS SIGNAL GENERATORS POWER SUPPLIES



S.I. Twin Power Supply.



G.2. L.F. Signal Generator.



M.I. Voltmeter.

Linstead Instruments are designed for accurate yet continuous hard work. Here are shown just three in the range which are receiving such glowing comments as "... does everything that instruments costing several times its price can do" (letter available for inspection). These are products which can be relied upon time and time again. Below we give a brief specification of three.

S.I. Twin stabilised Power Supply
Controlled by silicon transistors. Two supplies each. 0 to 20V, 0 to 0.5A. Full overload and short circuit protection. £45 nett U.K.

G.2. L.F. Signal Generator
10 Hz to 100 kHz $\pm 2\%$ ± 1 c/s. Sine wave. 0.6V low distortion. Square wave. 0-9V. No droop H.F. rise time μ s. 1 Watt into 3 ohms. £24 nett U.K.

M.I. Electronic Voltmeter
15 A.C. ranges. 1 mV to 500V. 10 Hz to 100 kHz. 3 D.C. ranges. 0-400V. Input Impedance. 10 Mohms on A.C. and D.C. £26 nett U.K.

LINSTEAD ELECTRONICS
35 NEWINGTON GREEN, LONDON, N.16 Tel: CL1 4825

R.S.T. VALVE MAIL ORDER CO.

146 WELLFIELD ROAD, STREATHAM, S.W.16

AZ31 9/-	EY31 7/-	Q8150/30	8A05 5/6	88A2 7/3	OC24 15/-
C1C 12/-	EY81 7/-	8A86 6/-	90A3 45/-	OC35 11/-	
CBL31 15/-	EY83 8/6	Q8150/36	90AV 45/-	OC26 7/6	
OCH35 21/-	EY84 7/6	20/-	90C1 12/-	OC28 16/-	
DAF91 4/-	EY86 6/6	Q8150/45	90C4 16/-	OC29 15/-	
DAF96 6/3	EZ41 8/-	20/-	91A6 4/6	90CV 25/-	OC35 11/6
DCS90 7/-	EZ80 8/-	Q8150/90	91B5 4/6	15012 9/6	OC34 4/6
DF91 3/-	FZ81 5/-	20/8	91B7 7/6	15013 8/6	OC45 4/-
DF96 6/3	GT1C 17/6	61J6 7/-	91B8 7/6	801 6/-	OC71 4/6
DH3/91 80/-	QZ30 10/-	QV03-12	91B9 7/6	803 35/-	OC72 6/-
DK91 5/-	GZ32 9/6	10/-	91N6 7/6	807 7/-	OC74 6/-
DK92 8/-	GZ34 10/-	QV04-7 12/6	91Q7A 7/-	811 30/-	OC75 6/-
DK96 7/-	GZ37 12/6	QV05-25 7/-	91R7 8/6	813 75/-	OC76 6/-
DL66 15/-	H63 8/-	QV06-20	91W7 9/6	864A 13/6	OC78 6/-
DL92 4/8	HL4LDD	25/-	91W7 9/6	872A 57/6	OC78 6/-
DL94 5/8	KT61 13/6	R10 15/-	91W7 9/6	8651 7/6	OC81 4/-
DL96 7/-	KT61 12/6	R17 8/-	91W7 9/6	8654 8/-	OC81D 5/6
DL810 12/8	KT86 16/-	R18 7/6	91W7 9/6	8657 7/-	OC81M 5/6
DL816 30/-	KT67 45/-	R19 7/-	91W7 9/6	8687 10/-	OC81PM
DL819 30/-	KT81 (7C5)	R25/500	91W7 9/6	9691 25/-	6/-
DM70 5/-	15/-	80/-	91W7 9/6	9749 10/-	OC92 6/-
DY86 6/-	KT81(GEX)	R130 25/-	91W7 9/6	9763 10/-	OC92D 6/-
DY87 6/-	R130P 35/-	R130P 25/-	91W7 9/6	9842 65/-	OC93 6/-
E880C 12/-	KT88 27/6	R18 24/-	91W7 9/6	9869 13/-	OC169 5/-
E180F 17/6	KTW61 10/-	R181 3/6	91W7 9/6	9872 7/-	OC170 7/-
E182CC22/6	KTW62 10/-	STV290/40	91W7 9/6	9887 10/-	OC171 8/-
EA8C80 6/8	ML4 17/6	25/-	91W7 9/6	9891 18/-	OC200 7/8
EB91 3/-	N75 15/-	8TV290/80	91W7 9/6	9890 8/-	OC202 3/6
EB833 7/-	PC86 9/6	8U2150 12/6	91W7 9/6	9891 15/-	XA101 2/6
EBP80 6/8	PC88 8/6	8U2150A	91W7 9/6	9892 14/-	XA111 3/6
EBP89 6/8	PC97 7/6	8U2150A	91W7 9/6	9893 7/-	XA112 4/6
EBL31 27/8	PC900 9/6	12/6	91W7 9/6	9894 7/-	XA125 5/6
ECL800	PC884 5/6	U19 35/-	91W7 9/6	9895 9/-	XA141 7/-
ECC33 15/-	PC890 16/-	U24 24/-	91W7 9/6	9897 10/-	XA142 8/-
ECC40 9/6	PCF80 6/3	U25 13/6	91W7 9/6	9898 25/-	XA143 8/-
ECC81 3/9	PCF86 8/-	U26 13/6	91W7 9/6	9899 4/6	9003 9/-
ECC82 4/9	PCF88 7/-	U101 18/6	91W7 9/6	9903 9/6	
ECC83 5/9	PCF88 8/6	U364 11/9	91W7 9/6	9904 3/6	
ECC85 7/-	PCF85 8/6	U361 23/6	91W7 9/6	9905 4/8	
ECC88 5/8	PCF86 8/6	UAB20 5/6	91W7 9/6	9906 7/-	
ECC90 6/8	PEN84 20/-	UAF42 8/9	91W7 9/6	9907 6/-	
ECC92 7/-	PEN40DD	UCH42 8/6	91W7 9/6	9908 6/-	
ECH15 11/-	12/-	UCH81 6/3	91W7 9/6	9909 6/-	
ECH42 9/-	PFL200	UCL32 7/-	91W7 9/6	9910 17/9	
ECH81 5/3	14/-	UCL43 8/9	91W7 9/6	9911 7/8	
ECH83 7/-	PL36 9/-	UL41 8/9	91W7 9/6	9912 42/-	
ECL80 6/6	PL81 7/6	UL94 6/-	91W7 9/6	12AC6 10/-	
ECL82 6/3	PL84 9/6	UY41 3/3	91W7 9/6	12AD9 11/-	
ECL83 9/6	PL500 13/6	UY85 5/-	91W7 9/6	12A E9 9/6	
ECL86 8/9	PX4 14/-	VP48 25/-	91W7 9/6	12A H9 30/-	
EF9 20/-	PX25 12/6	VR105/30	91W7 9/6	12AT8 4/6	
EF37A 7/-	PY32 8/6	5/-	91W7 9/6	12AT7 3/9	
EF39 6/-	PY33 8/6	5/-	91W7 9/6	12AU7 4/8	
EF80 5/-	PY81 6/-	W81 6/-	91W7 9/6	12AX7 5/9	
EF86 6/3	PY82 5/6	Z66 15/-	91W7 9/6	12BE6 5/3	
EF89 5/-	PY83 6/-	Z319 25/-	91W7 9/6	12E1 17/6	
EF91 3/6	PY800 7/-	Z750 23/-	91W7 9/6	12K7UT 6/-	
EF92 2/6	PY801 7/-	Z803U 15/-	91W7 9/6	12K8UT 8/-	
EF98 9/-	PZ30 10/-	O42 5/9	91W7 9/6	12Q7T 4/6	
EF183 6/-	QV02/4	O82 6/-	91W7 9/6	20Y2 19/-	
EF184 6/-	45/-	OZ4 4/6	91W7 9/6	25Z4 6/3	
EF904 21/-	QQV03/10	183GT 8/-	91W7 9/6	25Z5GT 7/-	
EF90 10/-	30/-	2D21 5/-	91W7 9/6	25Z6GT 8/6	
EL90 7/8	QQV03/20	2E90 20/-	91W7 9/6	30C15 13/6	
EL33 12/6	105/-	3A5 7/-	91W7 9/6	30C17 15/6	
EL34 9/6	QQV04/15	3B28 40/-	91W7 9/6	30F5 15/6	
EL41 8/6	105/-	3C45 47/-	91W7 9/6	30PL1 16/-	
EL42 8/6	QQV06/40	4X L60A	91W7 9/6	30L15 16/3	
EL41 7/9	80/-	5R4GY 9/9	91W7 9/6	30L17 14/3	
EL84 4/3	QQV05/10	5V40 8/-	91W7 9/6	30PL13 17/-	
EL85 7/8	70/-	5V40 8/-	91W7 9/6	30PL14 16/3	
EL86 7/6	Q870/20 5/6	5V40 8/-	91W7 9/6	30PL14 16/3	
EL360 22/-	Q875/30 5/6	5V30T 5/-	91W7 9/6	35L6GT 5/9	
EL820 6/-	Q875/60	5Z40 6/9	91W7 9/6	NKT404	
EL821 6/-	90/-	630L13	91W7 9/6	35W4 4/8	12/8
EL822 16/-	Q883/3 7/3	6AK5 4/6	91W7 9/6	35Z4GT 5/6	NKT675 6/-
EL820 20/-	Q892/10 4/-	6AK6 6/6	91W7 9/6	50C5 5/9	NKT677 5/-
EM31 15/-	Q895/10 5/6	6AL5 3/-	91W7 9/6	50CD60	NKT713 7/8
EM90 7/-	Q8108/45	6A38 3/6	91W7 9/6	80 31/-	OC16 20/-
EN84 7/-	6A78 19/-	80 5/-	91W7 9/6	85A1 25/-	OC19 17/6
EN32 25/-	Q8150/158	6A44 4/-	91W7 9/6		OC20 15/-

All valves brand new and boxed
Special 24 Hour Express Mail Order Service
Postage 6d. per Valve
Mon.-Sat. 9 a.m.-5.45 p.m.
Closed Sat. 1.30-2.30 p.m.
Open Daily to Callers
Tel. 01-769 0199/1649
SENDS A.E. FOR LIST OF 2,000 TYPES

Another member is needed for the editorial team of

WIRELESS WORLD

Readers (25/35) with a flair for writing and an interest in the presentation of technical information are invited to send details of education and experience to the:

Editor-in-Chief,
Wireless World, Dorset House,
Stamford Street, London, S.E.1.

DUE TO THE RISING COST OF COPPER WE ARE COMPELLED TO INCREASE OUR PRICES OF THE ABOVE LISTED TRANSFORMERS BY 10%. PLEASE ADD THIS AMOUNT WHEN ORDERING.

MULTI-TAPPED TRANSFORMERS MOST TYPES, FULLY SHROUDED AND TERMINAL BLOCK CONNECTIONS. ALL PRIMARIES 220-240 VOLTS

TYPE	SEC. TAPS	AMPS.	PRICE	CARR.
1A	25-33-40-50	15	£7 19 6	9/-
1B	25-33-40-50	10	£5 19 6	7/6
1C	25-33-40-50	6	£4 19 6	7/6
1D	25-33-40-50	3	£2 19 6	6/-
2A	4-16-24-32	12	£5 7 6	7/6
2B	4-16-24-32	8	£4 2 6	7/6
2C	4-16-24-32	4	£2 12 6	6/-
2D	4-16-24-32	2	£1 15 0	5/-
3A*	25-30-35	40	£12 15 0	15/-
3B*	25-30-35	20	£7 19 6	9/6
3C	25-30-35	10	£5 10 0	7/6
3D	25-30-35	5	£3 5 0	6/-
3E	25-30-35	2	£2 7 6	4/6
4A*	12-20-24	30	£9 15 0	10/-
4B	12-20-24	20	£5 19 6	8/6
4C	12-20-24	10	£3 19 6	7/6
4D	12-20-24	5	£2 15 0	6/-
5A	3-12-18	30	£7 5 0	7/6
5B	3-12-18	20	£5 9 6	7/6
5C	3-12-18	10	£3 5 0	6/-
5D	3-12-18	5	£2 5 0	5/-
6A	48-56-60	2	£2 17 6	4/6
6B	48-56-60	1	£1 19 6	4/6
7A	6-12	50	£7 15 0	9/6
7B	6-12	20	£4 10 0	7/6
7C	6-12	10	£2 19 6	6/6
7D	6-12	5	£2 2 6	5/-
8A	12-24	1	19 6	4/-
9A	15-30	1 1/2	19 6	4/6
10A	9-15	2	19 6	4/6
11A	6-3	15	£1 17 6	5/6

Note: By using the Intermediate Taps many other voltages can be obtained. Example: Range One: 7-8-10-15-17-25-33-40-50 v. Range Two: 4-8-12-16-20-24-32 v. Range Five: 3-6-9-12-15-18 v.

Samson's Electronics Ltd. 9 & 10 CHAPEL STREET, LONDON, N. W.1 01-723 7851 01-262 5125

BRAND NEW SURPLUS L.T. TRANSFORMERS. ALL BY FAMOUS MAKERS LATEST ARRIVALS

- PRI 240 v. Sec. 6.5 v. 46 amps. conservatively rated. Table top connections. Open type construction. 75/-, Carr. 7/6.
- PRI 240 v. Sec. 24 v. 12.5 amps. As above 75/-, Carr. 7/6.
- PRI 200-250 v. Sec. tapped 13-13 1/2 14 CT. 13-13 1/2-14 v. 2 amps. and 8 v. 1/2 amp. 27/6, open type table top connections. 27/6, P.P. 5/-.
- PRI 200-240 v. Sec. 6.2 v. 12.5 amps. Open type terminal block connections. 25/-, P.P. 6/6.
- PRI 200-240 v. Sec. (1) tapped 38-40 v. 10 amps. Sec. (2) 6.2, 6.8, 7.3, 7.9, 8.5, 9, 9.5, 10, 10.6 v. 18 amps., open type T.B. connections. £7/10/-, Carr. 10/-.
- PRI 240 v. Sec. tapped 53.6 55.2 v. 10 amps. "C" core T.B. connections. 75/-, Carr. 7/6.
- PRI 220-240 v. Sec. tapped 75, 80 v., 2.4 amps. and 6 v. 1A. "C" core table top connections. 75/-, Carr. 7/6.
- PRI 230-240 v. Sec. (1) 4.5 v. 30A. Sec. 8 v. 1A. Sec. (3) 4.5 v. 1A table top connections. Fully shrouded. 75/-, Carr. 7/6.
- PRI 240 v. Sec. (1) 45 v. 25 mA. Sec. (2) 1 v. 1/2 A. "C" core. 15/-, P.P. 3/6.
- PRI 240 v. Sec. (1) 22.3 v. 0.9A. Sec. (2) 21 v. 60mA "C" core. 15/-, P.P. 3/6.

BLOCK CAPACITORS New and Guaranteed. Send for List, over 2,000 in stock at a fraction of maker's price.

Maker	Mfd.	D.C.V.	Temp.	Price	Carr.
T.C.C.	10	750	60°C	10/8	2/6
T.C.C.	10	350	60°C	6/8	2/-
T.C.C.	8	1,500	60°C	17/6	3/6
T.C.C.	8	1,000	60°C	10/8	2/6
T.C.C.	8	750	60°C	8/6	2/-
T.C.C.	8	600	60°C	7/6	2/-
T.C.C.	8	400	71°C	6/6	2/-
T.C.C.	2	2,000	60°C	12/6	2/-
Dubilier	4	600	60°C	7/6	2/-
Dubilier	4	800	71°C	5/6	2/-
Dubilier	1	3,000	100°C	17/6	2/-
Dubilier	0.5	5,000	60°C	17/6	2/-
Dubilier	0.1+0.1	6,000	71°C	8/6	2/-

SPECIAL OFFER OF BRAND NEW H.T. TRANSFORMERS

- Fraction of maker's price. All tapped primaries 200-250 v. Table top connections. Enclosed type. GARDINER'S
- Sec. 500-0-500 v. 200 mA. 6.3 v. 4A. 6.3 v. 3A. 6.3 v. 2A. 5 v. 2A. 85/-, P.P. 7/6.
 - Sec. 450-0-450 v. 180 mA. 6.3 v. 3A. 6.3 v. 3A. 6.3 v. 3A. 5 v. 3A. 75/-, P.P. 7/6.
 - Sec. 350-0-350 v. 180 mA. 6.3 v. 3A. 6.3 v. 2.5A. 6.3 v. 2.5A. 6.3 v. 2A. 6.3 v. 0.5A. 5 v. 2.8A. 75/-, P.P. 7/6.
 - Sec. 450-0-450 v. 95 mA. 6.3 v. 3A. 6.3 v. 3A. 6.3 v. 2A. 5 v. 3A. 65/-, P.P. 7/6.
 - Sec. 400-0-400 v. 85 mA. 250 v. 50 mA. 6.3 v. 5A. 6.3 v. 4.75A. 6.3 v. 0.5A. 6.3 v. 0.2A. 75/-, P.P. 7/6.
 - Sec. 250-0-250 v. 50 mA. 6.3 v. 2A. 6.3 v. 2A. 5 v. 2.5A. 37/6, P.P. 5/-.
 - Sec. 300 v. 37.5 mA. 300 v. 37.5 mA. 47/6, P.P. 5/-, 4kV D.C. wkg. 4 v. 1A. 4 kV. D.C. wkg. 4 v. 0.3A.
 - Sec. 225 v. 100 mA. 6.3 v. 2.5A. 6.3 v. 1A. 37/6, P.P. 5/-.
 - Sec. 45 v. 87 mA. 6.3 v. 4.5A. 6.3 v. 1.5A. 6.3 v. 1A. 6.3 v. 0.2A. 29/6, P.P. 4/-.
 - Sec. tapped 450-470 v. 275 mA. 42/6, P.P. 5/-.

SPECIAL OFFER OF WODEN TRANSFORMERS BRAND NEW

- PRI tapped 200-250 v. F.5. Sec. Tapped 8-15-25-28-30-33-35 v. 15 amps. Tropically finished table top connects. £5/17/6, Carr. 10/-.
- PRI 240 v. E.5. Sec. No. 1. 50 v. 4 A. Sec. No. 2. 18-0-18 v. 1 A. 55/-, P.P. 7/6.
- PRI tapped 200-250 v. E.5. Sec. 1. 315-0-315 v. 110 mA. Sec. 2. 175-0-175 25 mA. Sec. 3. 5 v. 1.9 A. Sec. 4. 6.3 v. 3.1 A. Sec. 5. 6.3 v. CT4A. Sec. 6.3 v. CT12A. Sec. 6.3 v. 1A. "C" core table top connections. 50/-, P.P. 7/6.

ADVANCE COMPONENTS, LTD.

Stabilised low voltage power supply units, Type DC3. Input 200-215-230-245 v. Output 12 v. 1.25 A. at 55°C. stabilised within ±1% at full load with supply voltage variation up to ±15%. Ripple less than 1.5% R.M.S. of total output. Supplied brand new.

Microwave Valves

C. H. Dix, B.Sc., F.I.E.E. and W. H. Aldous, B.Sc., A.R.C.S., D.I.C., F.I.E.E.

This book is for the technically educated reader (graduate or H.N.C. level) who wants to understand the physical processes and operation of microwave valves. These processes are described from a fundamental viewpoint with some appropriate mathematical treatment. The treatment is based on the motion of electrons in electric and magnetic fields and the properties of the various types of r.f. circuits and transmission lines that are used in the devices. Microwave triodes are discussed, but the emphasis is on beam devices, both linear and crossed field, and in describing these the space charge wave approach is used consistently. Further chapters cover the formation and focusing of electron beams, the noise properties of devices, construction and applications. 275 pp. 185 illustrations incl. 8 plates. 55s net, 56s 1d by post.

Short-Wave Listening

J. Vastenhoude

This easily understood book is intended as a guide for the benefit of the increasingly large numbers of regular listeners to short-wave transmitting stations and also for radio amateurs who are interested in short-wave listening, and fully covers the many problems and possibilities of the subject, ranging from interference to DX clubs. 112 pp. 33 illustrations and 4 plates. 12s 6d net, 13s 5d by post.

Foundations of Wireless

M. G. Scroggie, B.Sc., F.I.E.E.

Seventh Edition

This standard work covers the whole basic theory and, starting from the most elementary principles and assuming no previous knowledge on the reader's part, deals with receivers, transmitters, amplification, valves, transistors, aerials, power supplies and transmission lines. The treatment of frequency changers has been brought into line with modern practice, while common-grid and cascade v.h.f. amplifiers, e.h.t. generators and transistor d.c. voltage raisers are also covered. 388 pp. 278 diagrams. 21s net, 22s 5d by post.

obtainable from all booksellers

ILIFFE BOOKS LTD

DORSET HOUSE

STAMFORD STREET

S.E.1

Z AND AERO SERVICES LTD

PEN RECORDERS



Elliot portable recording milliammeters.
As D.C. recorder: 1 mA. FSD. Movement resistance 1200Ω.
As A.C. current or voltage recorder: Movement resistance at 50 c/s. 1800Ω. Sensitivity 1 mA. A.C. FSD.
As decibel meter: source impedance 600Ω. Range +5 to -10 dB. Frequency response 50 c/s. to 15 kc/s.
Chart drive: 230 v. A.C. at 1in. and 6in. per hour. Movement is fitted with "high" and "low" alarm contacts which can be set for any value of the current.
Strip chart 3 1/2in. wide. Curvilinear tracking. PRICE £40
Packing and carriage 15/-.

RECORD PORTABLE RECORDING MILLIAMMETERS

These are similar to the above but are somewhat smaller and lighter, and D.C. resistance of the movement is 400Ω. Other details as above. PRICE £42 10 0
Packing and carriage 15/-.
These are also available as decibel meters. Type 19 A/C.T.A. Range +3/0/-3 dB 6 + with current of 500μA at 0 dB. Movement resistance 1900Ω £45 0 0

THYRISTORS

Type 3/40, 400 p.l.v., 3 amps, stud mounted; Gate voltage 3.0 v. at 20 mA 7/6
Blue 8spot, 200 p.l.v., 5 amps, stud mounted; Gate voltage 3.25 v. at 120 mA 12/6
Green spot, 400 p.l.v., otherwise as above 17/6

TEXAS SILICON FULL-WAVE BRIDGE RECTIFIERS

1B20K10 100 p.l.v. 2 amps, dimensions 1.4 x 1.4 x .6in. 25/-
1B40K10 100 p.l.v. 4 amps, dimensions 1.4 x 1.4 x .6in. 30/-
1B100M10 100 p.l.v. 10 amps, dimensions 2 1/2 x 2 1/2 x 1in. 85/-
Postage 1/6 per rectifier.


24-WATTS 210-240V. SOLDERING IRONS

Recently imported extremely attractive and sturdily built soldering irons with angle bits. Chromium plated steel body and polished wooden handle. No Bactelite or breakable plastics used in construction.
Price 16/-
Square bits 1/3
Square heating element 3/-
Handling and postage 2/-.

HEADPHONES No. 10 ASSY. (OR CANADIAN No. 1 ASSY)


Moving Coil Headphones with moving coil Hand Microphone fitted with press-to-talk switch. Rubber earpads. Cord terminated with army type 5-point moulded connector. Low impedance. Brand new, 20/- ea. P. & P. 3/6 per set.

SLIDEWIRE WHEATSTONE BRIDGE

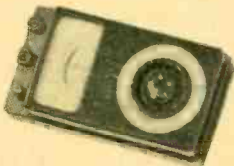

Battery Powered Portable Resistance Bridge. Range 0.5 to 50 ohms with multiplier settings of 0.1-1-100-1000, providing a measuring range of 0.05 to 50,000 ohms. Accuracy in the middle 3 ranges—0.5% approx.
PRICE £15 15 0

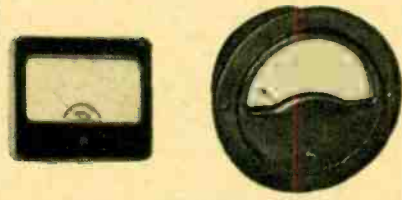CURRENT PRODUCTION FIRST QUALITY MOVING COIL METERS



1.5% Accuracy

Type 70DA and 70DV, 80 mm. square flange. Flush mounted. 38 mm. dia. body. 40 mm. depth from the panel.
Type 85DA and 85DV, 85 mm. dia. flange. Flush mounted. 37 mm. dia. body. 45 mm. depth from the panel.
Type 120DA and 120DV, 120 mm. square flange. Flush mounted. 88 mm. dia. body. 40 mm. depth from the panel.

RANGE	70DA	85DA	120DA
40μA	—	58/-	82/-
60μA	68/-	53/-	78/-
100μA	62/-	49/-	74/-
150μA	—	44/-	—
250μA	54/-	42/-	65/-
400μA	52/-	—	—
600μA	49/-	36/-	60/-
1mA	46/-	—	—
2.5mA	—	—	58/-
25mA	—	—	58/-
40mA	46/-	34/-	—
60mA	—	—	58/-
100mA	—	—	—
150mA	46/-	34/-	—
250mA	46/-	—	—
400mA	46/-	—	—
600mA	46/-	34/-	—
1A	46/-	—	58/-
1.5A	—	—	58/-
2.5A	46/-	—	58/-
4A	—	—	—
10A	—	35/-	60/-
40A	—	39/-	64/-

RANGE	70DV	85DV	120DV
6V	82/-	—	—
10V	—	40/-	—
15V	—	40/-	62/-
25V	—	—	—
40V	82/-	—	—
60V	82/-	—	62/-
100V	—	40/-	62/-
150V	82/-	40/-	—
250V	53/-	46/-	65/-
400V	—	47/8	69/-
600V	58/-	50/-	77/-

ZENER DIODES

5% 260 mW
OAZ200 4.7v 10/-
OAZ201 5.1v 9/6
OAZ202 6.5v 7/-
OAZ203 6.3v 7/-
OAZ204 6.8v 7/-
OAZ205 7.5v 7/-
OAZ206 8.2v 7/-
OAZ207 9.1v 9/6

15% 260mW
OAZ208 4.3v 6/6
OAZ209 4.7v 6/6
OAZ210 6.2v 6/-
OAZ211 7.5v 6/-
OAZ212 11.0v 6/6
OAZ213 12.0v 6/6

5% 1 Watt
Z2A24CF 2.4v
Z2A27CF 2.7v
Z2A30CF 3.0v
Z2A38CF 3.6v
Z2A160CF 16.0v
Z2A300CF 30.0v
All at 5/6.

5% 10-WATT STUD MOUNTED

Z4.7v.; Z5.1v.; Z5.6v.; Z6.2v.; Z6.8v.; Z7.5v.; Z8.2v.; Z9.1v.; Z11.0v.; Z12v.; Z14v.; Z15v.; Z16v.; Z18v.; Z20v.; Z24v.; Z27v.; Z30v.; Z35v.; Z36v.; Z43v.; Z47v.—all at 7/6.

DRY REED INSERTS

Glass dry reed inserts approx. 1 1/2in. dia. x 1in. long with axial leads. One "make" contact of 100mA capacity at 50V. Can be operated by permanent magnet or 30-50 Amp-turns relay rods. PRICE 18/- per doz. post free.

BEEHIVE TRIMMERS

30pF and 50pF, 15/- per dozen, in any combination. 2/- P.P.

MICROWAVE DIODES

Cartridge Type
3000 mc/s.: 1N21, 4/-; 1N21B, 6/-; 1N28, 20/-; 6,000 mc/s.: C82A, 5/-; CV101, 5/-; CV102, 5/-; CV201, 12/-.
8,375 mc/s.: 1N23, 4/-; 1N23A, 4/-; 1N23B, 8/-; 1N23C, 8/-; 1N23CR, 20/-; 1N23WE, 100/-; C810B, 70/-.
10,000 mc/s.: C83A (CV253), 20/-.
12,000 mc/s.: C83B, 17/6; C84B, 37/6; C89B, 30/-; C810BR, 70/-; CV111, 8/-; CV112, 8/-; CV2226, 70/-; CV2258, 85/-; CV2356, 200/-; 81M2 (CV2154), 37/6; 81M3 (CV2155), 37/6.
34,860 mc/s.: VX3130 (CV2301), 65/-.

AVALANCHE SILICON RECTIFIERS

Type RAN508AF, 960 p.l.v. at 6 amps. max., stud mounted 10/6

CATHODE RAY TUBES

2AP1—2in. screen, Green Trace Medium Persistence Oscilloscope Tube. EHT required 500 to 1000v. Sensitivity approx. 100v. DC/in to 200v. DC/in. 6.3v. heaters. USM11 Base. Overall length 7 1/2in.
3AFP1—DH7-01—2 1/2in. screen Flat Face Green Trace Medium Persistence Oscilloscope Tube. EHT required 700-1000v. Suitable for symmetrical and asymmetrical operation. Sensitivity Y = 30v. DC/in; X = 60v. DC/in. 6.3v. heaters. B9G Base. Overall length 10in.
3BP1—3in. screen Green Trace Medium Persistence Oscilloscope Tube. EHT required 1500 to 2000v. Sensitivity approx. 100-100v. DC/in at 1800v. and 150-200v. D.C./in at 2000v. 6.3v. heaters. B14A base. Overall length 10 1/2in.
4BP1—4in. screen Flat Face Green Trace Medium Persistence TWIN GUN Oscilloscope Tube. EHT required 1000 to 1800v. Sensitivity Y = 26v. DC/in; X = 40v. DC/in. 6.3v. heaters. B12F Base. Overall length 12in.
PRICE £00/-

Please consult our Catalogue for full range of Cathode Ray Tubes.



VALVES FOR EXPORT

Here are a few examples from our stock of over 2,500 items.

OA2	3/-	2D21	3/11	6B4G	12/6	6SN7GT	3/2
OA3	5/8	2E26	18/4	6CY6	13/11	6V6GT	3/2
OB2	3/6	3C45	46/-	6CW4	9/8	310A	20/8
OC2	14/4	3V4	3/2	6DB4	8/2	311A	25/8
OD3	4/7	5Y4GB	3/11	6J4	6/1	329A	23/-
1B3GT	3/6	5Y3GT	3/6	6J5GT	3/6	329A	23/-
1U4	2/8	6Z4GT	4/4	6J7	5/2	807	6/4
1V2	3/9	6AK5	3/6	6L6GC	4/11	811A	34/6
1Z2	20/2	6AL5	1/9	6N7GT	4/4	813A	70/-
		6AQ5	2/8	6SL7GT	3/8	829B	52/-

THE ABOVE PRICES ARE FOR DIRECT EXPORT, I.E. FOR DELIVERY TO OVERSEAS ADDRESS, OR TO THE SUPPLIERS, FOR VALVES TYPE MARKED AND BULK PACKED, IN LOTS OF 100 PER TYPE.

FULL EXPORT PRICE LIST AVAILABLE ON REQUEST

OUR NEW 1967/68 VALVE CATALOGUE AND PRICE LIST IS NOW READY. IT CONTAINS FULL REFERENCE DATA ON SEMI-CONDUCTORS, CATHODE RAY TUBES, ETC. Please send s.a.c. (quarto).

Head Office:

44a WESTBOURNE GROVE, LONDON, W.2.

Tel: PARK 5641/2/3
Cables: ZAERO LONDON

Retail branch (personal callers only)
85 TOTTENHAM COURT RD.,
LONDON W.2. Tel: LANgham 603

A.R.B. Approved for inspection and
release of electronic valves, tubes,
klystrons, etc.

Please send all enquiries, correspondence and Mail orders to Head Office



FULLY
GUARANTEED



VALVES
FIRST QUALITY

Table of electronic valves with columns for part numbers, descriptions, and prices. Includes sections for 'SOME HARD-TO GET-ITEMS IN STOCK' and 'BECAUSE OF DEVALUATION AND CONSEQUENT INCREASE IN PURCHASE PRICE...'

WHEN ORDERING BY POST PLEASE ADD 2/6 IN £ FOR HANDLING AND POSTAGE. NO C.O.D. ORDERS ACCEPTED. IN ORDER TO AVOID DELAYS PLEASE SEND ALL MAIL ORDERS AND CORRESPONDENCE TO OUR HEAD OFFICE AT 44a WESTBOURNE GROVE, W.2, AND NOT TO THE RETAIL SHOP

WE REQUIRE URGENTLY: KLYSTRONS 2K25 AND 723A/B; VALVES 4C35, 3C22, 845, 810, 30/- EACH PAID SUBJECT TO TEST.

WW-148 FOR FURTHER DETAILS

ELECTRONIC BROKERS LIMITED

PRECISION HELICAL POTENTIOMETERS



BECKMAN MODEL J. Continuous Instrument Potentiometer, 2in. dia., 10 k., 35/-. Brand new. Res. tol. +5%. Lin. tol. +0.15%. Also Colvern type, 100 k., 1 k.+1 k. dual.

BECKMAN MODEL A. 10 turn Precision Wirewound Potentiometers, available in the following values: 100 ohms, 10 k., 100 k. Offered at 50/-. Well below list price. Also Colvern, types 50 k., 30 k., 3 k., and 1.5 k. at 5 turn.

BECKMAN MODEL 7216. 10 turn Precision Potentiometer, 2 1/2 dia., 2 k., 60/-. Brand new. Miniature Beckman Multi-turn Continuous Dial, adjustable up to 15 turn, with separate brakelocking lever, 3/8 dial. Will fit most pots., 45/-. Half list price.

SINE/COSINE POTENTIOMETER. By Kelvin & Hughes, SCP4 33 k. Offered at a sixth of manufacturer's price, £12/10/-.

PLUG-IN PRECISION DUAL SPEED DRIVE D.S.D.7.

0.1 accuracy (dial calibration). Readings one from 0° to 360° on two concentric dials, coarse increments of 10° and fine increments of 0.1°. Miniature coupling provided to transmit rotation to a synchro. This precision drive permits rapid positioning and extremely accurate repositioning of rotational components such as synchros and resolvers, which can be mounted directly to the frame of the drive, £19/10/-.

SPERRY PRECISION D.C. TACHOGENERATOR Type L526. Brand new, in manufacturer's original packing. 5V/1,000 R.P.M. Size 11, Model 2, £12/10/-.

"MINICUBE" BLOWER. Sub-miniature, only 1 in. square. Operates on 26 V-400 c.p.s. input power, 1 or 2 ph. Output 2.2 c.f.m. at free air wt. 1 1/2 oz. Brand new. Made by Saunders Associates. Offered at third of manufacturer's price, £19/10/-.

GEAR BOXES. By Vactric. Size 11, 149.1: 2 and 300.2: 1, £4/10/-.

INSTRUMENTS FOR DYNAMIC ANALYSIS

LOW FREQUENCY RESOLVED COMPONENT INDICATOR BY SOLARTRON—Type VP 253.2A for the analysis of Dynamic Response of systems and components to the highest accuracy with rejection of harmonics and noise over the frequency range. Used for the measurement of transformer magnetising and core loss. Performance of synchros and fractional motors and other electro mechanical units. Also design and testing of Feedback Amplifier, Filters, etc.

This instrument will indicate by means of two centre zero 6 in. scale meters the resolved components of a signal voltage with respect to the applied reference energisation. Frequency Range: 0.5 c/s-1 KC/s.

Signal Voltage Ranges: 50 MV, 150 MV, 500 MV, 1.5 V, 5 V, 15 V, 50 V and 150 V with either balanced or unbalanced input.

Signal Input Resistance: 10 MΩ unbalanced.
20 MΩ balanced.

Reference Input:

Four-phase reference energisation is required, each phase having a level of 10 V r.m.s. with respect to virtual earth. Reference Input Resistance: 6.2 MΩ per phase.

Harmonic and Unrelated Frequency Discrimination better than 40 dB. Mains voltage 90/130 or 230/240 V. Standard Rack Panel, 19 in. x 12 1/2 in. high, £175 new condition, complete with manual.

T.F.A. A.C. CARRIER CONVERTOR JY 641A BY SOLARTRON—For direct use with resolved component indicator VP 253.2 for the testing of A.C. servo systems, demodulation of the output from Synchros and other forms of pick-off.

Modulation of Carrier to provide signals for Magnetic Amplifier, Synchros, etc.

Carrier Input Frequency: 50 c/s, 60 c/s, 200 c/s, 400 c/s.

Carrier Input Level: 20, 26, 90, 115, 200 or 230 r.m.s.

Size 22 in. x 12 1/2 in. x 12 in. Wt. 60 lb., £95.

T.F.A. REFERENCE RESOLVER JY 641A BY SOLARTRON—For use with resolved component indicator VP 253.2 for D.C. amplifier design, calibration and test of Accelerometer Transducer and in conjunction with T.F.A. A.C. carrier convertor JY 641A for A.C. carrier amplifier design, calibration and test of Synchros, etc., £125.

MINIATURE PRECISION SAMPLING SWITCHES, 100-CHANNEL. Consisting of 4 tracks of 25 contacts, each running at 80.2 r.p.m. Driven by a Vactric P.238 6.3 V. D.C. @ 5,000 r.p.m. through a Vactric gearbox 11 H7-J. Gear ratio 80.2:1. Max. torque 2 lb. inch, £18/10.

48-CHANNEL. Consisting of 2 tracks of 24 contacts driven by E.M.I. precision motor and gearbox, 6.3 V D.C. through a E.M.I. S.31 gearbox, £12/10/-.

HIGH TEMPERATURE PRESSURE TRANSDUCER—Type NT4-317, by Solartron. Highly accurate and stable performance. Suitable for uses in explosives and mining, research, moulding, pressing and extrusion research. High temperature environmental instrumentation, etc. Available in the following pressures only: 0.75 p.s.i., 100, 150, 160, 250, 500 absolute, 1,000, 1,500, 5,000 p.s.i. Gauge 0±150 p.s.i. differential, £19/10/-. Size 1/2 in. dia. 1 in. length. It should be noted that although these transducers are offered new condition, in manufacturer's packing, they do require individual calibration.

SOLARTRON PRESSURE SCANNING VALVE NT.999.3—This unit enables a single pressure transducer to be used to measure up to 24 separate pressures: in one second. For inlet pressure range of 0.1 p.s.i. to 40 p.s.i. depending on which transducer is used.

The transducer is housed inside the valve and is exposed to the unknown pressures in order. This unit is offered with Vactric synchronous motor, 400 cycle 30/60 V, 8,000 r.p.m., with gearbox ratio of 149.06:1. New condition, in manufacturer's original packing. Offered at a fraction of the original cost, £49/10/-.

A variety of Size 11 motors and gear heads can be fitted instead but we regret this will have to be undertaken by the intended purchaser.

500 WATT CONSTANT VOLTAGE TRANSFORMER. By advance MT.262+A-190-260 V, 50 cycle, 500 watts, 230 V., £12/10/-.

A.R.L. HIGH-SPEED GALVANOMETER FILM RECORDER. 10 mirror Galvos. at 1 Kc. Just like a camera.

EVERSHED 'S' VIGNOLE. 2 pen Recorder with Amplifier. 2, 1 1/2, 3 and 6 in. per sec., £25

SOLARTRON PLATINUM RESISTANCE THERMOMETER PROBES. NT4-1039/1 Probes in a stainless steel case $\frac{1}{4}$ in. dia. Resistance at 0 C. is 130.0±0.3

ohms. Time response: \leq 3 seconds. Temperature range: -42°C. to 500°C. Length of Probe, 2 in. New condition. List price £25. Our price £4/10/-.

G.E.C. HERMETICALLY-SEALED RELAYS. A complete range of these hard-to-get relays for replacement are available. Send for list.

S.T.C. STANTALUM CAPACITORS. From 0-15-100 mfd. Polarized and non-polarized. Also Plessey Cascanet, 50 m.f.d., 70 V, 250 m.f.d. 15 V, 140 m.f.d. 30 volt. Send for list.

SCOOP INDUSTRIAL BUYERS OC25, £17/10/. per 100. Mullard OC81D £7/10 per 100.

SUDECO PRECISION FOUR DIGIT IMPULSE COUNTER, with pre-selection for counting back to zero as soon as the pre-set number of impulses have been received, 24 V. D.C., 185 mA, £3/19/6. Black finish.

RELAYS
G-V controls. Hermetically-sealed thermal timing relays available in the following: 7.5 seconds at 28 V., 20 sec. at 6.3 V., 30 sec. at 28 V., 120 sec. at 28 V., 180 sec. at 28 V. All £1 each.

LEACH. Balanced Armature Relays, 3 pole. D.T.—10 amp, 24/28 V. D.C., 25/-.

CHOPPERS. S.P.D.T. 6 volt, 400 cycles, octal base, 7/6.
DELAY RELAY. Hermetically Sealed Thermo-static Delay. Impervious to atmospheric conditions and altitudes S.P.S.T. Normally opens with a 30 second delay, 7/6.

WE PURCHASE

PLUGS AND SOCKETS, MOTORS, TRANSISTORS, VALVES AND KLYSTRONS, RESISTORS, CAPACITORS, POTENTIOMETERS, TEST EQUIPMENT, RELAYS TRANSFORMERS, METERS, CABLES, ETC.

PROMPT PAYMENT AND COLLECTION
TURN YOUR CAPITAL INTO CASH

ELECTRONIC BROKERS LIMITED 8, BROADFIELDS AVENUE, EDGWARE, MIDDX.

TEL. 01-958 9842

WW-149 FOR FURTHER DETAILS

ILIFFE BOOKS

Mathematical Techniques in Electronics and Engineering Analysis

Students' Edition.

J. W. Head, M.A. (Cantab.), F.Inst.P., M.I.E.E., F.I.M.A.

Divided into two parts, the first part consists of general mathematical techniques—the solution of equations; series and partial fractions; differentiation and integration; versors, vectors and trigonometry; and various labour saving devices. The second part deals with more specialised applications of mathematics to problems in electrical and electronic engineering. 224pp. 67 illustrations. 18s net limp, 1s 1d postage.

Unified Circuit Theory in Electronics and Engineering Analysis

Students' Edition.

A new approach to solving non-steady state problems. J. W. Head, M.A. (Cantab.), F.Inst.P., M.I.E.E., F.I.M.A., and C. G. Mayo, M.A., B.Sc., F.I.E.E.

Steady-state conditions present no mathematical difficulties, but more advanced techniques are required when dealing with the non-steady state. The authors of the present book prefer, and advocate, the use of operational calculus, which they maintain has the outstanding advantage of directness and simplicity of working that makes it easy for practising engineers and students alike to appreciate the significance of each necessary process. The early part of the book is concerned with electrical circuits; the latter part is more theoretical. 174pp. 20 diagrams. Limp 18s. Postage 10d.

obtainable from all booksellers

ILIFFE BOOKS LTD
DORSET HOUSE STAMFORD STREET S.E.1

CLASSIFIED ADVERTISEMENTS

DISPLAYED SITUATIONS VACANT AND WANTED: £6 per single col. inch.
LINE advertisements (run-on): 7/- per line (approx. 7 words), minimum two lines.

Where an advertisement includes a box number (count as 2 words) there is an additional charge of 1/-.
SERIES DISCOUNT: 15% is allowed on orders for twelve monthly insertions provided a contract is placed in advance.

BOX NUMBERS: Replies should be addressed to the Box number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London, S.E.1.

No responsibility accepted for errors.

Advertisements accepted up to **FEBRUARY 6** for the **MARCH** issue, subject to space being available.

SITUATIONS VACANT

AN OVERSEAS CAREER with International Aeradio Limited. TO meet the requirements of constant growth and expansion, we invite applications from technicians and engineers for an overseas career in North, West and East Africa, the Mediterranean area and the Arabian Gulf. If you have recently completed service in a trade such as Ground Wireless Fitter in the R.A.F., R.E.M.E. Army, or have other experience in the maintenance of H.F. and V.H.F. communications, R.T.T. and navigation aids, we should be interested to hear from you. Successful candidates would normally spend six weeks at our Radio Engineering School, Southall, Middlesex, before proceeding overseas, but in some cases start with suitable qualifications and experience may be offered immediate postings. Overseas staff receive a tax-free salary with married and child allowances if appropriate and accommodation, bachelor or married is provided free; other benefits include generous U.K. leave and membership of an excellent pension and life assurance schemes. **WRITTEN** applications please, to Personnel Manager, International Aeradio Limited, Aeradio House, Hayes Rd., Southall, Middlesex. [19]

TRAINED engineers required for interesting work on radio/radar equipments at a flying unit in North Wales.—Apply: Short Bros. & Harland, Ltd., R.A.E. Llanbedr, Merioneth, N. Wales.

RADIO Engineer/Mechanic, first-class communications work, required by large company engineers, 12 ms. service overseas, excellent opportunity.—Write age, experience, Box W.W. 1909, "Wireless World."

EXPERIENCED enthusiasts required, London. W.I. for tape editing, disc cutting, mobile work, evenings, weekends, state experience and salary expected.—Box W.W. 1951, "Wireless World."

SENIOR EXECUTIVE ENGINEERS, POST OFFICE. Four posts in London for men and women normally aged 35 or over (well-qualified younger candidates considered). The successful candidates will be concerned with: (a) Leadership of a team engaged on the design and development of large vehicular and non-vehicular equipment for the mechanisation of the installation of external engineering plant required for the provision of telecommunications services; (b) Leadership of a team engaged on the design and development of specialised mail handling machinery and equipment for the full scale mechanisation of the postal services; (c) Leadership of a small group of engineers making theoretical studies of transmission techniques to be used for the provision of radio and other services by communications satellites; (d) The mechanical and electrical development, and standardisation of, relays and telephone exchange switching mechanisms. Qualifications: Posts (a) and (b); degree in mechanical engineering, or corporate membership of the Institution of Mechanical Engineers or an equivalent or higher qualification. For post (a) knowledge of the design and operation of mechanical aids together with experience of hydraulic and/or pneumatic equipment and a knowledge of modern manufacturing techniques desirable. For post (b) experience in the design of manipulative machinery or mechanised handling plant essential; a flair for invention in this field and the ability to design experimental rigs desirable. Posts (c) and (d); degree in engineering, or an equivalent or higher qualification. For post (c) basic knowledge of the technical methods used in modern commercial communications essential; general knowledge of satellite technology and related principles desirable. For post (d) experience in the development and large scale production of light electromechanical apparatus, preferably in the telecommunications field essential; appreciation of cost and value engineering desirable; general knowledge of telephone exchange switching and signalling an advantage. Salary (Inner London) £2,050 to £2,609. Starting salary may be above the minimum. Non-contributory pension. Promotion prospects.—Write to Civil Service Commission, Savile Row, London. W.1. for application form, quoting S/6847/68. Closing date 15th February, 1968. [1949]

**FOR
 SALE AND WANTED
 ADVERTISEMENT FORM
 TURN TO
 PAGE No. 139**

ELECTRONIC DESIGN & DEVELOPMENT ENGINEERS (ALL GRADES) SALARIES UP TO £2,800 P.A.
ELECTRONIC TEST & SERVICE ENGINEERS (ALL GRADES) SALARIES UP TO £1,600 p.a.
TECHNICAL SALES ENGINEERS (EXPERIENCED) SALARIES UP TO £2,500 p.a.
TECHNICAL AUTHORS (ALL GRADES) SALARIES UP TO £1,800 p.a.
 ALSO
DRAUGHTSMEN, PRODUCTION ENGINEERS
 We have over 500 registered vacancies for above types of engineers in the Home Counties and South England areas. If you have had at least 2 years' experience in British Industry and require a job which offers first class prospects, top salaries and interesting work.
 Phone (any time day or night) or write to:—
ELECTRONICS APPOINTMENTS LTD.,
 Norman House,
 105-109, Strand, W.C.2
 TEMple Bar 5557-8.



if **ELECTRONIC TEST TECHNICIANS**

this big 'if' is worth up to £1,500 a year to you

We need really experienced Electronic Test Technicians who can tackle fault-finding, test and calibration problems in complex electronic equipment with confidence and flair.

If you think you can meet our spec. there are vacancies waiting at our new plant in the Herts/Beds area offering the following benefits—and more:

- Up to £1,500 basic salary.
- Up to £200 re-location expenses (plus help with house purchase).
- Full staff conditions, plus superannuation, plus free life assurance.
- Stable, permanent employment, plus the chance to advance in a vigorous, expanding company.
- 5-day week, plus generous, progressive holiday scheme.

Please quote reference No. WW 164

tr **TAYLOR RECRUITMENT**
 85 GLOUCESTER PLACE, LONDON W.1
 Strict confidence will be observed. Just state separately the companies to whom you do not wish your application forwarded



The Civil Service

Professional and Technical appointments

RADIO AND ELECTRONIC ENGINEERS BOARD OF TRADE (CIVIL AVIATION)

Qualified engineers required as Assistant Signals Officers in the field of Civil Aviation for the provision and installation of advanced electronic equipment—including the latest type of radar, telecommunications, navigational aids, etc.

QUALIFICATIONS: Degree or Dip.Tech. with 1st or 2nd class honours in Electrical Engineering or Physics, or have passed all examinations for M.I.E.E., A.M.I.E.R.E. or A.F.R.Ac.S.

AGE: 23 and normally under 35 on 31st December, 1968 (extension for Forces and Overseas Civil Service).

SALARY (Inner London): On the scale £1,160-£2,092 depending on age and qualifications. Good prospects of promotion.

Pensionable appointments.

(Reference: S/85/ASO).

EXECUTIVE ENGINEERS AND ASSISTANT EXECUTIVE ENGINEERS POST OFFICE

EXECUTIVE ENGINEERS are required for research, development and design work for electronic telephone exchanges, satellite communications, submarine telephony, novel line and radio transmission systems, electro-acoustics, mechanical aids and postal mechanisation. Most of these posts are in London.

There are also posts in engineering management to direct and control the provision and maintenance of communications installations and plant. These posts are available in London and in a number of provincial centres.

ASSISTANT EXECUTIVE ENGINEERS are required in London and provinces for work on the development and design of communications systems and postal service equipment.

QUALIFICATIONS: Executive Engineers: Degree or Dip. Tech. in Mechanical or Electrical Engineering, or Physics or Applied Physics, or have achieved Corporate Membership of the I.E.E., I.Mech.E., or I.E.R.E. Final year students may apply. **Assistant Executive Engineers:** G.C.E. (or equivalent) pass in English language, and one of the following: H.N.D., in Electrical or Mechanical Engineering or Applied Physics; a pass in (or exemption from) Parts 1, 2 and 3 of the examinations of I.E.E., or I.Mech.E.; a pass in (or exemption from) Sections A and B of the I.E.R.E. examinations; a pass in (or exemption from) Parts 1 and 2 of the examination of the Council of Engineering Institutions, in subjects acceptable to one of the Institutions named above.

SALARIES (national): Executive Engineer: £906 (at 21)-£1,677 (at 34 or over)-£1,884.

Assistant Executive Engineers: £734 (at 18 or under)-£1,097 (at 25 or over)-£1,631.

Salaries increased for officers serving in London, £125 Inner London, £75 Outer London. non-contributory pension, Promotion prospects to higher grades with maxima of £2,484 and £3,105.

AGE: Executive Engineer: At least 21 and under 35 on 31st December, 1968. (Some extensions for service in H.M. Forces or Overseas Civil Service.)

Assistant Executive Engineer: At least 17½ and under 27 on 31st December, 1968.

Applications for both posts from well qualified older candidates will be considered. (Reference: S/353)

APPLICATION FORMS are obtainable from the Secretary, Civil Service Commission, Savile Row, London, W.1. Please quote appropriate reference.

Engineers & Technicians

required for test and repair work on a variety of equipment including:—

**Television transmission equipment
Audio amplifiers and control equipment
Electronics instruments**

Preference is given to applicants with City & Guilds or equivalent qualifications. Juniors taking day-release courses will be enabled to continue their training. There are good opportunities for promotion to laboratory and other specialised work. Apply giving full details to

**Personnel Manager, British
Relay (Electronics) Ltd.,**

1-7 Croft Street, Deptford, London, S.E.8.

World wide News and News Picture Agency requires competent versatile

TELECOMMUNICATIONS ENGINEERS

for extremely interesting work in London, Europe, Middle East and Africa.

Applicants must have a sound knowledge of Radio/Electronics and general principles of Line/Radio Telegraphy/Telephony.

Apply in writing giving all details of past experience, present salary, languages spoken, etc., to:

Mr. D. Till,

Director of Communications,
UNITED PRESS INTERNATIONAL,
8 Bouverie Street, E.C.4.

RADIO AND TELEVISION ENGINEER

A Radio/Television Engineer is required for the Industrial unit of the Decca Radio and Television Company at Battersea.

He should have experience in Bench installation work, Radio Amplifiers, S.R.E., Television off air and closed circuit Television.

Salary will be commensurate with experience and conditions are good.

Apply to the Personnel Officer (Ref. RT/74), Decca Radio and Television, Ingate Place, Queenstown Rd., Battersea, S.W.11. Telephone: MACaulay 6677, Ext. 31.



ELECTRONICS ENGINEER

An Electronics Engineer, preferably with H.N.C. is required to assist with the development of experimental computer control systems in our laboratories at Battersea.

A salary will be commensurate with age and previous experience. Conditions of employment are attractive and include pension scheme.

Applications stating age and experience should be sent to:

Personnel Officer,

BISRA - The Inter-Group Laboratories of the British Steel Corporation,
24 Buckingham Gate, London, S.W.1.

Please quote reference number PE/28 in your reply.

A CAREER IN THE SUNSHINE



**RADIO
TECHNICIAN
TRAINING**



IN THE

RAAF

Vacancies exist in the Royal Australian Air Force for men who are interested in being trained in the Technical Radio fields. Applicants should be United Kingdom citizens residing in the U.K. and aged between 18 and 33 years. Qualified personnel up to the age of 43 years are also invited to apply.

Free passage to Australia is provided for families and pay commences from date of enlistment in London.

Further information can be provided by writing or phoning:—

**RAAF CAREERS OFFICER (Dept. WW1) AUSTRALIA HOUSE
STRAND, LONDON W.C.2. Telephone No: 01-836 2435**

P9176



**THE EUROPEAN SPACE
RESEARCH ORGANISATION**

ESRO

wish to recruit for its

**LAUNCHING RANGE
IN KIRUNA (Sweden)**

HEAD OF RADAR SECTION

to be responsible for:

1. Maintenance and operation during campaigns of:
 - tracking radar (C Band—SELENIA type RIS 4C)
 - the radar data transmission system digital computer-punched paper tape—target acquisition system).
2. Possible development and extension of the system, with the assistance of six senior technicians.

University degree or equivalent in electronic engineering and minimum of three years' experience in tracking radar equipment and data transmission equipment is required. Experience as group leader desirable.

Preference will be given to candidates below 35 years of age, although applications from older candidates will be considered.

Applications for this post should be sent to the Assistant Director for Personnel, ESRO, 114 Avenue de Neuilly, 92-Neuilly, France, quoting reference TR-7-add. 63.

How to switch

**from a good
career in
engineering
to a better one
servicing
computers**

To become a successful IBM Data Processing Customer Engineer, you need more than engineering qualifications. You need to be able to talk confidently and well to any level of customer management, and to have a pleasing personality in your work. As a DPCE, you work in direct contact with your customers, on some of the world's most advanced data processing equipment.

You must have a sound electronic and electro-mechanical background, such as ONC/HNC Electronic or Electrical, or Radar/Radio/Instrument Fitters course in the armed services.

You will get thorough training on data processing equipment throughout your career. Starting salaries depend on experience and aptitude, but will not be less than £1,100 a year. Salary increases are on merit—within 3 years you could be earning £1,750. Drive and initiative are always well rewarded at IBM; promotions are made on merit and from within the company.

If you are between 21 and 31, and would like this chance to become part of a rapidly expanding and exciting computer industry, write to IBM.

Send details of training, experience and age to Mr. D. Dennis, IBM United Kingdom Limited, 389 Chiswick High Road, London, W4, quoting reference DP/WW/229.

IBM

IMPERIAL CHEMICAL INDUSTRIES LIMITED
HEAVY ORGANIC CHEMICALS DIVISION

TELECOMMUNICATIONS MANAGER

For this senior vacancy candidates, who technically must be abreast of the latest developments in the communications field, should be capable of planning the future development of the various installations servicing the Tees-side sites of I.C.I., including the data transmission needs of computers.

Managerially he will be responsible for the installations and for the staff who operate them and will liaise with telecommunication and computer specialists in other Divisions and areas of the Company. Requests for application forms should be addressed to:



Mr. R. B. Poots,
Personnel Officer,
Imperial Chemical Industries Limited,
Heavy Organic Chemicals Division,
Organic House,
BILLINGHAM,
Co. Durham.

RADIO TELEFIS EIREANN

The Irish national broadcasting organisation invites applications for posts as:—

TECHNICIAN

Applications are invited from Technicians for employment in operations, maintenance and installation areas of Radio and Television Broadcasting.

Applicants should be of a high technical standard. Minimum qualifications would include City & Guilds Intermediate Telecommunication Technicians Certificate, Ordinary National Certificate in Radio, or equivalent. Post training experience in Radio or Telecommunications would be an advantage.

The age limit is 35 years.

Application Forms may be obtained by writing, enclosing an addressed envelope to:—

Manager, Personnel Administration,
Radio Telefis Eireann,
Donnybrook,
Dublin, 4,
Ireland

Closing date for receipt of completed Application Forms 26th January, 1968.
Envelopes should be marked "Technician" W.W.

FED UP WITH YOUR PRESENT JOB?

We require a number of junior engineers with drive and initiative for:—

Circuit design—development and prototype construction, etc.; Electro-mechanical drafting—printed circuit/chassis layouts, etc.; Production line test and inspection engineers; Production line fault finders.

Excellent prospects and full training given, day release considered. Salary up to £1,000 depending on experience and qualifications.

Send full details in writing of experience to date and present salary to:—

Solid State Controls Limited
30/40 Dalling Road, London, W.6

ARE YOU AN ENGINEER— OR HOPING TO BE ONE?

A missile systems expert is just one of the things you could become, in today's Royal Navy.

Are you a professional engineer with a degree or Dip Tech? You can enter the Navy as an acting Sub-Lieutenant. If you don't have a degree but have been accepted for a university place, you may qualify for an allowance of about £770 p.a. while you study—and get naval training too. If you have 'A' levels in pure and applied maths and physics, but no university place, we'll give you full engineering training with a degree at the end.

The ships and aircraft of today—and tomorrow—call for top engineers. We make sure they get the best training. As an Engineer Officer you will be encouraged to keep abreast of the latest developments, and will be given opportunity for post-graduate studies. You could also have direct responsibility for equipment design.

Your naval training—like that of all our officers—will begin at The Naval Training College, Dartmouth. You learn to take responsibility, both for your men and for complex equipment.

You'll see the world. Your ship might go anywhere: on important naval trials, or on special operations, when the Navy is asked to bring aid, rescue or relief to civilians. You'll have a highly professional status and the salary to match. For the right man, the way to the top lies clear ahead—ability and intelligence are the qualifications for promotion.

For details write to: Capt. J. H. F. Eberle, RN, Officer Entry Section (WW/F), Old Admiralty Buildings, London, S.W.1.

COMMUNICATIONS ENGINEERS

Engineers with U.K or overseas field experience of the maintenance of radar broadcasting or communications equipment are required by the Marconi Company at Chelmsford. They will be engaged in the preparation of the technical handbooks produced by the Company on all the latest equipment. While previous writing experience is desirable it is not essential. There are no age limits.

An attractive salary will be paid and there are excellent conditions of employment.

Marconi



Applications quoting reference WW/TEC/15 should be sent to Mr N. Finegan, Central Personnel Services, The Marconi Company Limited, English Electric House, Strand, London WC2.

AN 'ENGLISH ELECTRIC' COMPANY

Government of ZAMBIA REQUIRES TELECOMMUNICATIONS TECHNICIANS

for the General Post Office, on contract for one tour of 36 months in the first instance. Commencing salary according to age and experience in scales (including overseas addition) indicated below. A supplement of not less than £200 a year is also payable direct to an officer's home bank account. Gratuity 25% of total salary drawn. Both gratuity and supplement are normally TAX FREE. Liberal leave on full salary or terminal payment in lieu. Free passages. Quarters at low rental. Children's education allowances. Contributory pension scheme available in certain circumstances. Special terms of service apply to serving civil servants including employees of the General Post Office. Applications must be submitted through their own Establishment Division/Head of Department.

Candidates for appointment as Equipment Technicians (salary scale rising from £1,460 to £1,855 a year) must possess at least the Intermediate City and Guilds Group Course Certificate and have had ten years or more training and practical experience in one or more of the following branches: (i) Carrier Systems: (ii) H.F. and V.H.F. Radio: (iii) Telegraph Machines: (iv) Automatic Exchanges: (v) Mixed duties covering categories (i)-(iv). (Reference M3D/62916/WF).

Candidates for appointment as Line Technicians (Salary scale rising to £1,580 a year) must possess at least two appropriate City and Guilds Certificates and have had ten years or more training and practical experience in one or both of the following branches: (i) Underground and Overhead Cable Distribution: (ii) Subscribers Installations. (Reference M3D/62959/WF).

Apply to CROWN AGENTS, M. Dept., 4 Millbank, London, S.W.1, for application form and further particulars, stating name, age, and brief details of qualifications and experience, and quoting the relevant reference.



**EUROPEAN SPACE
RESEARCH ORGANISATION
ESRO**

offer interesting positions in their Establishments

**THE CONTROL CENTRE
Darmstadt (West Germany)**

**THE TRACKING STATION
Redu (Belgium)**

**THE LAUNCHING RANGE
Kiruna (Sweden)**

Candidates are required for the following positions

- TF1: ELECTRONICS SENIOR ENGINEER**
- TF2: ELECTRONIC ENGINEER**
- TF3: ELECTRONIC TECHNICIANS**
for Technical Facilities Section
- SCA: SPACECRAFT CONTROLLERS**
(Senior and Junior)
- ET1: ELECTRONIC ENGINEER**
and
- ET2: ELECTRONIC TECHNICIANS**
for Telemetry Data processing
- EN1: ELECTRONIC ENGINEERS**
for Network and Communications of
Operation Group
- ETC: ELECTRONIC TECHNICIANS**
in Communications
- HRS: ELECTRONIC ENGINEER**
for Head of Radar Section of ESTRANGE,
Kiruna, Sweden
- SCP: SENIOR COMPUTER PROGRAMMER**

For further details please write to the

**PERSONNEL OFFICE,
ESTEC**

Domeinweg, Noordwijk, Holland

Stating for which post you wish to apply and quoting
reference CC/SG-12-67

transistor television receivers

T. D. Towers, M.B.E., M.A., B.Sc., M.I.E.E.,
A.M.I.E.R.E.

This book covers virtually every aspect of transistors in television receivers, with examples drawn from the United Kingdom, U.S.A., France, Germany, Russia and Japan.

Although transistor sets may never entirely displace valve operated, mains-driven, large screen sets, for personal-portable sets the transistor has no rival.

194 pp. 188 illustrations.

55s net 56s 3d by post.

* For the designer, and the interested serviceman, this is a book packed with information.

RADIO AND ELECTRICAL RETAILING

* He (the author) has done the job so thoroughly that his book—the first in the field—is likely to remain first in the field for quite a while.

MUSIC TRADES REVIEW

... gives the reader a clear perspective of the subject and provides an important chapter on servicing methods.

ELECTRICAL AND RADIO TRADING

available from leading booksellers

ILLIFE BOOKS LTD

Dorset House, Stamford St., London, S.E.1.

**City and County of Bristol
BRISTOL TECHNICAL COLLEGE
DEPARTMENT OF NAVIGATION,
MARINE RADIO AND RADAR**

Applications invited for post of
**ASSISTANT LECTURER GRADE B
IN RADIO AND RADAR** Ref. No. T67/74/1

Duties to commence 1st May, 1968.
Applicants should hold a First Class P.M.G. Certificate in Radio Telegraphy. Additional qualification such as B.O.T. Radar Maintenance Certificate, H.N.C. in Electronics or Electrical Engineering, Aircraft Radio Maintenance Engineer's Licence (Categories A & B) or similar an advantage.

Salary Scale: £955-£1,625 with additions for approved qualifications. Starting salary dependent upon approved experience and qualifications.

Further particulars and application forms (returnable by 29th January), from Registrar, Bristol Technical College, Ashley Down, Bristol, 7. Quoting ref.

UNIVERSITY OF NOTTINGHAM

**DEPARTMENT OF ELECTRICAL
AND ELECTRONIC ENGINEERING**

EXPERIMENTAL OFFICER

Applications are invited for the above appointment to commence as soon as possible. Candidates should have a good knowledge and practical experience of basic electronic circuit techniques using both vacuum-tube and solid-state devices; they will normally be expected to have H.N.C. or equivalent qualification. Salary will be within the range of £915 to £1,525 per annum. Forms of application and further particulars, returnable not later than 29th January, 1968, from the Registrar.



We are expanding our activities in the field of television-by-wire, and need an experienced development engineer who can undertake important work on both immediate and long-term projects, involving both transmitting and receiving systems and equipment.

Good Laboratory experience and proven ability are the main requirements for the appointment, which offers very good security and opportunities for promotion to an engineer of the right calibre. All enquiries will be treated in strict confidence, and should be addressed to

**The General Manager, British Relay (Electronics) Ltd.,
1-7 Croft Street, Deptford, London, S.E.8.**

ELECTRONIC MAINTENANCE ENGINEERS

There are excellent opportunities in the Installation and Maintenance Division of E.M.I. Electronics Ltd., for engineers to carry out maintenance work on a wide variety of electronic equipment, including laboratory test gear, tape recorders, broadcast and studio T.V. equipment, and electronic automation equipment.

Candidates should be between 21 and 45, have had at least three years' experience of this type of work, and be willing to travel.

Good commencing salaries will be paid, and staff conditions include a contributory pension scheme and free life assurance. Grants towards re-location expenses will be made in suitable cases.

EMICAREERS



Applications, giving concise personal/career details to:
P. JONES · GROUP PERSONNEL DEPARTMENT · E.M.I. LTD
BLYTH RD · HAYES · MIDDLESEX · TEL: 01-573-3888 · EXT: 411

**TECHNICAL/COMMERCIAL
ASSISTANTS**

RADIOS AND TAPE RECORDERS

A vacancy exists in the technical-commercial department of both the Radio and Tape Recorder Divisions of Philips Electrical Limited, for an assistant to the Manager.

Applicants for both these positions should be between 25 and 35 years of age and be qualified to H.N.C. or City and Guilds final standard. Membership of an appropriate professional institution would be an added advantage.

The job is basically one of liaison and communication between the commercial, financial, production and design functions. A knowledge of the Radio and Tape Recorder market, with regard to appearance, price and performance is desirable. Experience in methods of measuring expressing performance and field test reporting is essential. If you would like to know more about these positions, please write to:

**E. G. Johnson,
PHILIPS ELECTRICAL LTD.,
Century House, Shaftesbury Avenue,
London, W.C.2**

ELECTRONIC ORGANBUILDERS REQUIRE

TEST & INSPECTION ENGINEERS; men with sound Electro-mechanical background, valve and transistor amplifier experience, some musical knowledge an advantage.
DRAUGHTSMEN with at least 5 years' Electro-mechanical and Electronic experience, minimum qualification ONC or equivalent.

These positions carry good salaries and prospects.

Applications, giving age & career details to: Mr. J. Meredith,
COMPTON ORGANS LIMITED, CHASE ROAD, London, N.W.10.

RADIO TECHNICIANS

A number of suitably qualified candidates are required for unestablished posts, leading to permanent and pensionable employment in Cheltenham and other parts of the U.K. (including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to candidates who can offer "O" level and GCE passes in English language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technical Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19—£812 at 25—£1048 (highest age pay on entry) rising on 1.1.68 to at 19—£898, at 25—£1,076.
Prospects of promotion to grades in salary range £1,159-£1,941. There are a few posts carrying higher salaries.

Annual leave allowance of 3 weeks 3 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:—

Recruitment Officer (RT),
Government Communications Headquarters,
Oakley, Priors Road,
Cheltenham, Glos.

TECHNICAL ASSISTANT

Applications are invited from young electrical or electronic engineers with a live mind to work in the Group patents department of Pye of Cambridge Ltd.

The successful applicant will have a flair for describing technical equipment and be required to liaise between patent agents, inventors and legal advisers.

An attractive salary taking into account age and experience will be offered.

Please apply, giving full details of age, qualifications and experience to: The Personnel Manager, Pye of Cambridge Ltd., St. Andrew's Road, Cambridge.

ENTHUSIASTS Have you considered a career in Technical Authorship? If you have sound experience in electronics or communications and ability to write clear concise English we would train applicants as Technical Authors. The commencing salaries range from £1,300 to £1,700 depending on experience with the prospects of high future rewards and earnings.

Box No. 5039, c/o Wireless World

THE UNIVERSITY OF LEEDS

Applications are invited for the position of Electronics Technician in the department of Biochemistry. Duties will include the maintenance of electrical and electronic equipment used in all types of chemical analysis.

Qualifications: O.N.C. or H.N.C. with Electronics endorsements, City and Guilds Finals, Radar Fitter with appropriate industrial experience.

Salary within the Senior Technician range (£912 - 1,150) plus a qualification allowance where applicable. Apply to: Dr. T. A. Scott, Department of Biochemistry, 9 Hyde Terrace, Leeds, 2.

TELECOMMUNICATIONS TECHNICAL OFFICERS**DIPLOMATIC WIRELESS SERVICE****Hanslope Park, Bucks. and Crowborough, Sussex**

Several posts for men, normally aged 23 or over but well qualified younger candidates considered, for installation, modification, maintenance and operation of (a) radio transmitters and receivers, remotely tuned aerial systems, teleprinters and voice frequency telegraph equipment over a worldwide network, OR (b) very high power transmitters, receiving equipment, tape recorders, generating plant, etc., at several high power broadcasting stations.

QUALIFICATIONS: O.N.C. in Electrical Engineering, or City and Guilds Intermediate Certificate in Telecommunications (old syllabus, i.e., subject No. 50) plus Radio II, or Intermediate Telecommunications Certificate (new syllabus, i.e., subject No. 49) plus Certificate in Mathematics B, Telecommunications Principles B, and Radio and Line Transmission B, or equivalent standard of technical education, and at least 5 years' appropriate training and experience.

SALARY (national): £983 (at 21) to £1,066 (at 23) to £1,283 (at 28 or over). Scale maximum £1,449. Prospects of promotion. Non-contributory pension.

WRITE to Civil Service Commission, Savile Row, London, W.1, for application form, quoting S/6670/67. Closing date 7th February 1968. Candidates who have already applied should not do so again.

University of Salford**SENIOR TECHNICIAN**

THERE is a vacancy in the rapidly expanding Department of Electrical Engineering for a **SENIOR TECHNICIAN**.

The successful applicant may work in a research group and be concerned with building, maintaining and operating research equipment; or in an electronic workshop, where equipment for teaching and research is manufactured and maintained.

The post will particularly appeal to those who have practical experience of a variety of electro-mechanical and electronic equipment and who prefer to work on their own initiative in a wide variety of fields.

The salary scale is £1,040 to £1,385 per annum for which the desirable minimum educational qualification is H.N.C. The starting point on the scale will depend on age, experience and qualifications. The post is superannuable.

Applications, giving details of age, education and experience, should be sent to the Registrar, University of Salford, Salford 5, Lancs., by 29th January, 1968, quoting reference E/99/IE.

FIELD SERVICE ENGINEER FOR PUBLIC ADDRESS EQUIPMENT AND AUDIO AMPLIFICATION EQUIPMENT

Covering London and Southern Counties. Experience Essential. Good Salary. Expense Allowance. Company Vehicle or Vehicle Allowance provided.

Write:

SERVICE MANAGER, MAGNETA (B.V.C.) LTD.,
Parsons Green Lane, London, S.W.6.

WORKS Manager required for progressive company engaged in transformer winding and light electronic assembly in the South Midlands. The position should appeal to a man with some technical knowledge and the ability to obtain increased production.—Write Box W.W. 1950. "Wireless World."

RECORD COMPANY requires a qualified Sound Engineer to operate and maintain studio and disc cutting equipment. Previous experience in the use of modern professional sound equipment and a genuine interest in music essential. Attractive salary offered commensurate with the responsibilities of this important position.—Replies to Box W.W. 1962, "Wireless World."

RADIO ENGINEERS required by the National Guard of Saudi Arabia. Initial contracts for one year, including six weeks' paid leave in United Kingdom. Unmarried men preferred. Salary and allowances approximately £3,500 per annum net. Candidates should have good knowledge of modern HF SSB communications equipment and VHF techniques. Previous experience of petrol engines and teleprinters an advantage. Duties involve repair and maintenance of static, mobile and portable radio equipment throughout Saudi Arabia, and training of local personnel as radio mechanics and operators. Frequent air and road travel is involved. Initial applications, giving brief details of qualifications, experience and past employment, should be made to Brigadier H. E. R. Watson, c/o H.Q., National Guard, P.O. Box 182, Riyadh, Saudi Arabia, by civil air mail at full postage rates. [1961]

**University of Wales
INSTITUTE OF SCIENCE AND
TECHNOLOGY
CARDIFF****DEPARTMENT OF APPLIED PHYSICS
M.Sc./DIPLOMA COURSE in ELECTRONICS**

Applications are invited for places in the full-time one-year M.Sc./Diploma course in Electronics, commencing 30th September, 1968.

Further details can be obtained from the Registrar and Secretary, University of Wales Institute of Science and Technology, King Edward VII Avenue, Cathays Park, Cardiff, CF1 3NU. Application forms should be completed and returned to the Institute as soon as possible.

Computer Engineers

Due to continued expansion NCR require additional **ELECTRONIC** and **ELECTRO-MECHANICAL ENGINEERS** for Computer Maintenance. Posts are available for men wishing to become Site Engineers. Training Courses are arranged for suitably qualified men. H.N.C. Electronics, City & Guilds Final or equivalent standard required. Men from Forces with radar experience welcome. Knowledge of electronic or electro-mechanical equipment necessary. Good Pension and Bonus Plan in operation. Please write for Application Form to The Personnel Officer. NCR, 1000 North Circular Road, London, NW2, quoting Publication and month of issue.

Plan your future with



INSTALLATION ENGINEERS

The Installation and Maintenance Division of E.M.I. Electronics Ltd., requires Installation Engineers. New contracts for 1968 include the complete installation of equipment for T.V. studios, and of Robotug transport systems. Successful applicants will be responsible for the planning and on-site supervision of Installation, for a wide range of commercial electronic equipment including closed-circuit T.V. systems and automated systems, in addition to those already mentioned. Applicants should have a good knowledge of electronic equipment, and preferably some experience of installation work. A sound knowledge of basic electrical and electronic theory is necessary. Commencing salaries and staff benefits are good, and relocation grants may be made in suitable cases.

EMICAREERS

Applications, giving concise career and personal details to:-
P. JONES - GROUP PERSONNEL DEPARTMENT
E.M.I. LIMITED - BLYTH ROAD - HAYES - MIDDX



A FULL-TIME technical experienced salesman required for retail sales; write giving details of age, previous experience, salary required to—The Manager, Henry's Radio, Ltd., 303, Edgware Rd., London, W.2. [67]
WEST London Aero Club invite "A" and "B" licensed engineers with capital and/or necessary equipment to commence Radio Workshop. Alternative propositions may be considered. Write full details to—White, Waltham Airfield, near Maidenhead, Berks. [68]

A ASSISTANT Editor required to work on technical books, mainly concerning radio, electronics and electrical engineering; experience of handling book or periodical, also technical MSS. and illustrations desirable, a knowledge of electrical/electronics technology. Progressive post in a rapidly expanding organisation in modern offices in Feltham, Middx.—Please write to: The Managing Editor, Practical and Home Division, The Hamlyn Group, Hamlyn House, 42, The Centre, Feltham, Middlesex. [1956]

ROLLS-ROYCE Aero Engine Division Laboratory Assistant

We have a vacancy in the experimental services section of our Advanced Research Laboratory for an assistant to help in the construction, wiring and testing of prototype electronic and electrical apparatus and in the checking and calibration of laboratory electronics. The section provides instrumentation support to the scientific staff of the laboratory.

Applicants should have experience in electronic laboratory practice and in the wiring and testing of transistor circuits and preference will be given to candidates who have an O.N.C. in electrical engineering or equivalent qualification.

Please write for application form giving brief details of career to date, to:

Laboratory Manager,
ROLLS-ROYCE LIMITED,
Old Hall, Burton Road,
Littleover, Derby, DE3 6FJ.



ST. LAURENCE'S HOSPITAL, DUBLIN 7
(Richmond, Whitworth & Hardwicke Hospitals)

ELECTRONICS MAINTENANCE TECHNICIAN

Salary: £800 x £50—£1,200 per annum.

Applications are invited for the above position from persons holding the following qualifications:

- (a) City & Guilds Telecommunications Technicians Certificate B Level Examination, and
- (b) City & Guilds Electronic Servicing Certificate Final, or equivalent qualifications.

Particulars and application forms available from the Secretary to whom completed applications must be returned so as to reach him not later than 12 noon on 23rd February, 1968.

ROYAL HOLLOWAY COLLEGE (University of London)

Englefield Green, Surrey

SENIOR ELECTRONICS TECHNICIAN required to assist with design and construction of equipment used in advanced teaching and research. This appointment offers the opportunity for a wide range of interesting and non-repetitive work. Salary on the scale £912—£1150 plus qualification allowance and London Weighting. 37½ hour week. 4 weeks holiday. Applications should be made to the Secretary.

BOOKS, INSTRUCTIONS, ETC.

MANUALS. circuits of all British ex-W.D. 1939-45 wireless equipment and instruments from original R.E.M.E. instructions; s.a.e. for list, over 70 types.—W. H. Bailey, 167a, Moffat Road, Thornton Heath, Surrey. CR4-8PZ. [66]

TAPE RECORDING ETC.

SAVE on cost of Hi-Fi. See Audio Supply notice (ad ert No. 1954, Services Offered column). [1955]

TAPE to disc transfer, using latest feedback disc cutters; EPs from 21/-; s.a.e. leaflet.—Deroy, High Bank, Hawk St., Carnforth, Lancs. [70]

TAPE/Disc/Tape transfer editing, duplicating, if quality and durability matter (especially with LPs from your previous tapes) consult Britain's oldest transfer service. Fund raising records published for schools musical societies (tax free).—Sound News Productions, 10, Clifford St., London, W.1. Reg. 2745. [1952]

SERVICE & REPAIRS

REPAIRS.—Our modern service department equipped with the latest test equipment including a wow and flutter meter and multiplex stereo signal generator is able to repair Hi-Fi and tape recording equipment to manufacturers' standard.—Teleonic Ltd., 92, Tottenham Court Rd., London, W.1. 01-636 8177. [21]

FIELD AIRCRAFT SERVICES

Radio/Radar Centre, London Airport

require three additional

RADIO MECHANICS

for bench and light aircraft work. Aircraft experience not essential and suitable applicants will be considered for relevant training.

Apply by letter or telephone to:

Mr. D. W. Griffiths,
Heathrow Airport-London,
Hounslow, Middlesex.
Tel.: SKY 2141.

Eastern GAS

COMMUNICATIONS DEPARTMENT

COMMUNICATIONS TECHNICIAN

Eastern Gas is in the process of modifying an extensive mobile radio network covering a large geographical area. Due to this, it is necessary to strengthen the Communications Department by the appointment of a suitably qualified person to assist in all planning and operational aspects of V.H.F. and U.H.F. mobile radio networks.

The successful applicant will be based at the Board's Headquarters at Watford, Herts.

The salary for this position will be within the range £1,170-£1,400 per annum, with initial placing according to qualifications and experience.

Apply in writing, giving full personal particulars, and quoting reference number 4069 to Area Personnel Manager, Eastern Gas, 49 Clarendon Road, Watford, Herts., within 10 days from the appearance of this advertisement.

TELEPRINTER MECHANIC

Responsibility will initially be for the development and maintenance of logic controlled systems at locations within a 20 mile radius of Southall.

This position will appeal to a man with a sound knowledge of Telegraphic or logic switching who seeks the opportunity to commence a career with a fast expanding Company. Driving licence desirable.

Our business is telecommunications. A good salary will be offered commensurate with experience. The Company has an excellent pension and life assurance scheme. Substantially reduced holiday air fares are available to most parts of the world.

Please apply in writing stating details of age and experience to:

General Manager, Personnel,
INTERNATIONAL AERADIO LIMITED
Aeradio House, Hayes Road,
Southall, Middlesex.

V.H.F. WIDE-BAND AMPLIFIERS

Specification:
Bandwidth, 40-230MHz; Gain, 20DB±1.5DB Max. Output (1 carrier) 3 volts; Input/Output Impedance 75 ohms; 19in. Rack Mounting. Two-stage Distributed Circuit.
Power Requirement, 100-250 volts 50 watts
Built to Professional Standards. Brand New and Fully Guaranteed.

For Sale at the Reduced Price of £30.0.0.
Further details Box No. 5040, c/o "Wireless World."

ELECTRONIC SUBCONTRACTORS

A subsidiary of a large American Company manufacturing high quality Electronic products has capacity available for assembly wiring or manufacture of electronic equipment. We should be pleased to quote promptly for your requirements however large or small.

Write or telephone Mr. Brandon or Mr. Mills.

Baldwin Burns Ltd.,

Chesham Close,

Romford,

Essex.

Romford 46465

Research in Opto-Electronics

We are still building our team for work in Modern Optics, and need an experienced

Electronics Engineer

with enthusiasm for new fields of engineering. His chief duty will be to study applications of the basic research now in hand on pattern recognition and other optical information processing.

Please write to:—

The Personnel Manager (Ref. 46),
Hawker Siddeley Dynamics Ltd.,
HATFIELD,
Herts.




TELEVISION ENGINEERS

with Management in mind

Rapidly expanding Company in CCTV requires seven senior engineers to control its Sales/Servicing operations in the London, Midlands—Birmingham, North West—Manchester, East Anglia—Cambridge, Southern—Southampton, West—Bristol, and Yorkshire—Leeds areas. Ability to maintain one inch helical scan video VR 7003 recording machines, T/V monitors and vidicon cameras essential.

In addition to servicing CCTV installations, they will be required to promote new business in their areas. Estate car will be provided and there is a pension scheme. Salary to be negotiated and promotion for the right men guaranteed. Write giving full details to:—

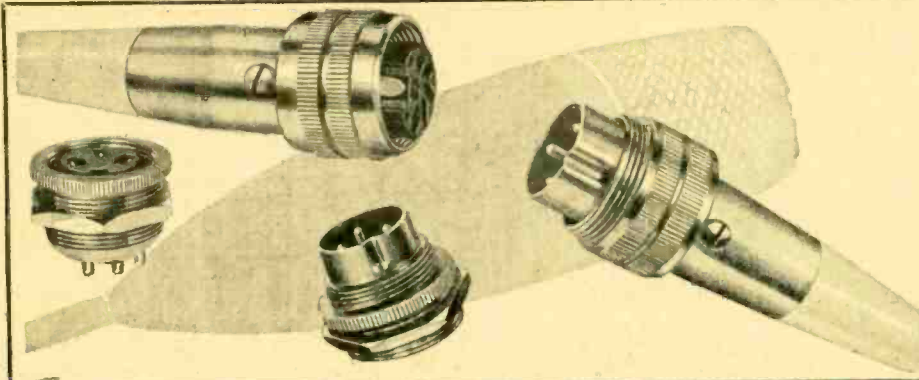Technical Director, Television Applications Ltd., 9/11 Windmill St., London, W1



WW-150 FOR FURTHER DETAILS

Sole Distributors
Super-Electronics Ltd.

5 Violet Hill
London, N.W.8
Tel. Maida Vale 8281

Airborne Electronics

SERVICE TECHNICIANS

RCA Great Britain Limited, is an International Electronics Company with diverse interests in the field of electronic engineering. Our Service Division operating at A & AEE, Boscombe Down, Wiltshire is engaged on servicing and maintaining airborne electronic equipment, particularly AIRBORNE RADARS, ELECTRONIC NAVIGATIONAL AIDS, and HF, VHF AND UHF COMMUNICATIONS.

A number of interesting vacancies have arisen which offer excellent opportunities for developing the initiative and furthering the career of young men between 22 and 35. They must have relevant experience preferably on the specific equipment mentioned above.

These positions carry monthly paid staff status with excellent fringe benefits, including three weeks paid holiday each year. A competitive salary will be paid and there are excellent promotion prospects.

Please write or 'phone for an application form to:—



Mr. A. Freemantle.
Great Britain Limited,
Lincoln Way, Windmill Road,
Sunbury on Thames, Middlesex.

Telephone Sunbury on Thames 85511, Ext. 105
A SUBSIDIARY OF RADIO CORPORATION OF AMERICA.



new VARI-STAT

thermostatic soldering iron

High Production Model D
Miniature Iron 50 watt
Voltage 12-250 volt
Weight 1 3/4 oz.
"Screw on" Bit sizes 3/32in., 1/8in., 3/16in., 1/4in.

PRICE
55/-

Our range also includes:
Standard Instrument Model 50W
Standard Instrument Model 70W
High Production Instrument Model 125W
Industrial Model 500W
All these irons give excellent bit and element life since the thermostat completely eliminates overheating and controls reserve heating capacity which makes possible continuous soldering without chilling of the bit. The consistent temperature makes these irons ideal for printed circuit work.

CARDROSS ENGINEERING CO. LTD.,
Woodyard Road, Dumbarton.
Phone: Dumbarton 2655

WW-151 FOR FURTHER DETAILS

4-STATION INTERCOM



Our Price Only
~~Usually 18/6~~ **£7/5/0**

Solve your communication problems with this new 4-Station Transistor Intercom system (1 master and 3 subs), in de luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9 v. battery. On/off switch. Volume control. Ideally suitable to modernise Office, Factory, Workshop, Warehouse, Hospital, Shop, etc., for instant inter-departmental contacts. Complete with 3 connecting wires, each 66ft. and other accessories. Nothing else to buy. P. & P. 7/6 in U.K.

INTERCOM/BABY ALARM



Originally 6/9ns
OUR PRICE ONLY
65/-

Same as 4-Station Intercom for two-way instant conversation. Ideal as Baby Alarm and Door Phone. Complete with 66 ft. connecting wire. Battery 2/6. P. & P. 3/6.

7-STATION INTERCOM

(1 MASTER & 6 SUB-STATIONS) in strong metal cabinets. Fully transistorised. 3 1/2 in. Speakers. Call on Master identified by tone and Pilot lamp. Ideally suitable for Office, Hotel, Hospital and Factory. Complete with 50 yards cable and batteries. Price 21 gns. P. & P. 12/6 in U.K.

Transistor TELEPHONE AMPLIFIER




Usually 6/9ns
OUR PRICE ONLY
59/6

Why not increase efficiency of Office, Shop and Warehouse with this incredible De-Luxe Portable Transistor TELEPHONE AMPLIFIER which enables you to take down long telephone messages or converse without holding the handset. A useful office aid. A must for every telephone user. Useful for hard of hearing persons. On/off switch. Volume Control. Operates on one 9 v. battery which lasts for months. Ready to operate. P. & P. 2/6 in U.K. Add 2/6 for Battery. Full price refunded if returned in 7 days.

WEST LONDON DIRECT SUPPLIES (W.W.),
169 Kensington High Street, London, W.8

**THIS IS ONE OF THE
WORLD'S MOST
ADVANCED
OSCILLOSCOPES.**

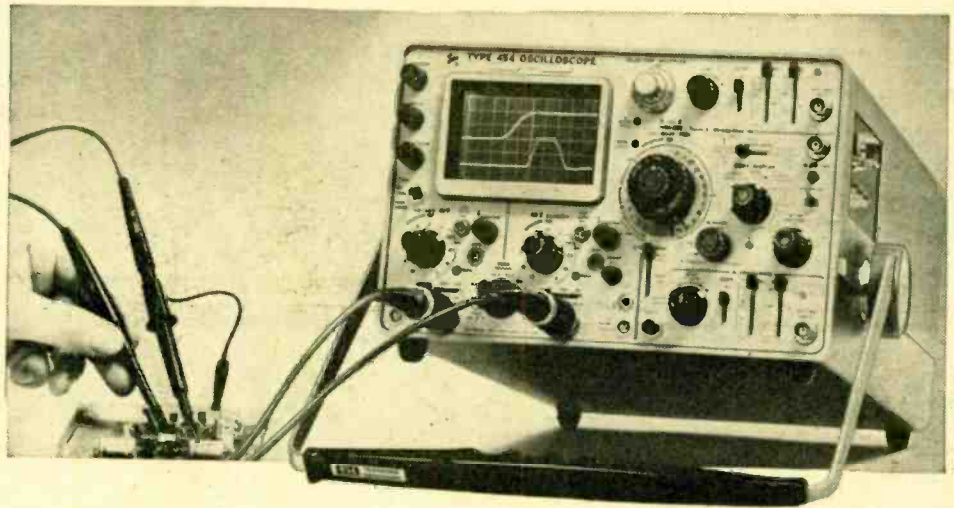**WHY NOT HELP US
MARKET OR
MAINTAIN IT?**



We are looking for Marketing and Maintenance Engineers who would take pride in being part of a team providing Tektronix Products and services in a diverse and expanding field.

If you have a sound basic knowledge of Oscilloscope applications or circuitry with a pleasant telephone manner and the ability to write good letters, or a flair for repair and calibration, we would like to hear from you.

We offer pleasant working conditions, progressive salary opportunities, profit sharing and non-contributory life assurance and pension scheme.

To be considered for one of these outstanding opportunities, write to



**Mr. R. M. Garrett, Field Engineering Manager,
Tektronix U.K. Ltd., Beaverton House,
Station Approach, Harpenden, Herts.**

MINIATURE KEY SWITCHES. (P.O. Lever Type 1000), centre off. 2 c/o each way. 7/6 ea.
RE-SETTABLE HIGH SPEED COUNTER (3 x 1 x 3/4 in.) 3 digit. 12/24/48 v. (state which), 32/6 ea. P.P. 2/6.
HIGH SPEED MAGNETIC COUNTERS (4 x 1 x 1/2 in.) 4 digit. 6/12v. 24/48v. (state which), 6/6 ea. P.P. 1/-.
SOLARTRON OSCILLOSCOPES. CD7115, £50 carr. 70/-; CD643 £50, carr. 70/-; QD910 £75, carr. £5. All units in first class condition. Complete with manuals.
R.F. AMMETERS 3in. Rnd. 0/6 amp. 10/- ea. P.P. 2/6.
COPPER LAMINATE PRINTED CIRCUIT BOARD (8 1/2 x 5 1/2 in.), 2/6 sheet, 5 for 10/-.

BULK COMPONENT OFFERS

100 Capacitors (latest types) 50pF to .5µF.
 250 Resistors 1/2 and 1 watt.
 250 Resistors 1/2 and 1 watt.
 150 Hi-Stab Resistors, 1/2, 1/2 and 1 watt.
 25 Vitreous W/V Resistors, 5%.
 12 Precision Resistors 1% (several standards included).
 12 Precision Capacitors 1 and 2% (several standards included).
 12 Electrolytics (miniature and standard sizes).
ANY ITEM 10/-, ANY 5 ITEMS £2

VENNER LIGHTWEIGHT ACCUMULATORS (1 oz. 1 1/2 x 1 1/2 x 3/4 in.) 2 v. 1.5 a.h., 12/6 ea. (with electrolyte and charging inst.).
CARPENTER POLARISED RELAY 18,000 turns at 4000Ω 15/- (with base). ALL Types of G.E.C./SIEMENS/S.F.C. Sealed relays stocked.
MAINS RELAY (240 v. A.C.) 12 H.D. make contacts, 20/- ea., P.P. 2/6.
REED RELAYS (2 Herkoms) S.T.C. 2426-582-15, 2 make. 10-15 volt coil, 15/- ea.
"3000" TYPE RELAYS (Ex. New Equip.) 10 for 25/- (our choice), p.p. 5/-.
RESOLVED COMPONENT INDICATOR (Solartron VP253-2A Condition new, £35 (with manual), carr. 50/-.
TELEPHONE HANDSET (Type 706) 17/6 ea., P.P. 2/6.
ZENER DIODES 3 to 50 volt. 5%. 1.5 watt, 3/6; 10 watt, 5/6 ea.

BLOWER/EXTRACTOR FANS (By PAPST Motors) 4 1/2 x 4 1/2 x 2in. cast moulding. 450 C.F.M. Engineered to very fine limits. 50/- ea., P.P. 2/6.
THYRISTOR LAMP DIMMER/SPEED CONTROL KITS. 200 watt kit, 27/6, P.P. 2/6; 500 watt kit, 37/6, P.P. 2/6.

SILICON CONTROLLED RECTIFIERS (Thyristors) BTY87 (100r) 100 p.i.v. 12 amp., 15/- ea.; TBY91 (150r) 150 p.i.v. 16 amp., 20/-; CRS25/10 100 p.i.v. 25 amp., 30/-; CRS25/40 400 p.i.v. 25 amp., 60/-; CRS1/20 200 p.i.v. 1 amp., 5/6; CRS1/40 400 p.i.v. 1 amp., 7/6; CRS3/40 400 p.i.v. 3 amp., 10/- ea.
SILICON DIODES RS220af 2/-ea., £1 doz.; RS240 3/-ea., 30/- doz.; RS280 4/- ea., 40/- doz.; IS103/BY100 4/- ea., 40/- doz.; RAS310af (avalanche) 6/- ea., 60/- doz.; IS413 5/- ea., 50/- doz.; RS610, 10/- ea. RS640 20/- ea., RS812 40/- ea.; RS845 60/- ea.

PRODUCTION BATCH COUNTER (BURNDENPT) BE403, Condition: New £15 ea., P.P. 20/-.
OSCILLOSCOPES Cossor 1035, £17/10/-; 1049, £20; Solartron D300, £20, P.P. any unit £2/10/-.
E.M.I. MINIATURE RELAYS (24v. 1 c/o) 1/2 x 1/2 x 3/4 in. Wt. 1/2 oz. 7/6 ea.
TELEPHONE DESK SETS (type 706), Brand new, 95/-, P.P. 5/-.

SILICON BRIDGE UNITS. GEXS41 80 p.i.v. 10a., 37/6; ELIBD-RC 100 p.i.v. 10a., 37/6; GA31-A (Germ.) 200 p.i.v. 2a., 20/-.
SORENSEN VOLTAGE REGULATORS. Type LT-1000-25. £25 ea.
P.C. CONNECTORS (13 way in-line), 4/6 pair.
LARGE CAPACITY ELECTROLYTICS. 2,000 µF. 150v.; 4,000 µF. 90v. 7/6 ea. 6,300 µF. 63v.; 10,000 µF 30v.; 16,000 µF 15v.; 25,000 µF 15v. 10/- ea. All 4 1/2 x 2in. screw terminals. P.P. 1/- ea.

SPEAKER BARGAINS. E.M.I. 13 x 8in. with double tweeters 15 ohm, 65/-, P.P. 5/-. As above less tweeters 3 or 15 ohm, 45/- ea., P.P. 5/-.
FANE 12in. 20 watt (Dual Cone), 95/-, P.P. 5/-.
PHASE SENSITIVE VOLTMETERS (Solartron UP250/253) £65.

TRANSFORMERS L.T. 50v. at 5 amp. 19.0-19v. 1/2 amp. 25/-, P.P. 5/-.
TRANSFORMERS H.T. 625-0-625v. at 110 ma., 6.3v. at 2a., 6.3v. at 3a. c.t. Parmeko Neptune series, 35/-, P.P. 5/-.
ELECTRIC SLOT METERS (1/-) 25 amp. L.R. 240v. A.C., 85/- ea., P.P. 5/-.
QUARTERLY ELECTRIC CHECK METERS, 40 amp. 240v. A.C., 20/- ea., P.P. 5/-.
TRANSISTOR POWER SUPPLY. 2 x 12v. at 250 ma. 240v. 50 c/s. input, 25/- ea., P.P. 5/- (made by E.M.I.).
STEP-DOWN TRANSFORMERS. PRI. 200/250v. Sec. 1. 115v. at 1.25 amps.; Sec. 2. 25v. at 5 amp., 25/- ea., P.P. 5/-.

PATRICK & KINNIE
 81 PARK LANE, HORNCHURCH, ESSEX
 Tel.: ROMFORD 44473.

**DIOTESTER
 IN-CIRCUIT TRANSISTOR TESTER**



THE DIOTESTER detects faulty diodes and transistors when still in circuit without need for unsoldering.

BRITEC LIMITED

17, Charing Cross Road, London, W.C.2
 Tel: 01-930-3070

WW-152 FOR FURTHER DETAILS

MISCELLANEOUS

METALWORK, all types cabinets, chassis, racks, etc. to your own specification, capacity available for small milling and capstan work up to 1in bar.
PHILPOTT'S METALWORKS, Ltd., Chapman St., Loughborough.

ARTICLES FOR SALE

GOOD second-hand Ferrographs often available—Reg. 2745 (London). [1953]
SOLARTRON CD568 Oscilloscope, Bandwidth 5Mc/s, variable t/b delay. £25.—Hicks, Dartford 26687. evenings. [200]

VACUUM pumps, gauges, etc. recorders, general scientific and laboratory equipment, catalogue.—V. N. Barrett & Co. Ltd., 01-654 6470. [69]
SOLARTRON C.T. 436 miniature military scope, double beam, D.C.-6mc/s bandwidth, sensitivity 10MV/CM, brand new with manual; £30 o.n.o.—Box W.W. 203, Wireless World.

2 new, unused, Belling-Lee Filtron R.F.I. filters.
B.P.S.R. 201; suit research lab., electronics training school, etc. Best offer.—Box W.W. 1960, "Wireless World."
TEST sets 219, mains operated, 30/-, carriage £1; amplifying units 505 for spares, containing 10 valves, EP70, EP73, etc., transformers, pots, etc.; 5/-; carriage 7/6; Vibrators, 12-volt 4-pin, new and boxed, 2/-, post 1/-.—The Harlequin, Wigton, Cumberland. [201]


B.C.2 TV, RADIO, TAPE REC. SERVICE SPARES.
UHF 625, modify your set to B.C.2. Manufacturers conversion kits & tuners, list available. Philips 625 conversion kit, new, including 7 valves & circuit. £4/18 6 (less valves 39/6), p/p 8/-, GEC/Sobeil Dual 405/625 IF amp and output chassis, new, incl. circuit 38/6, p/p 4/6, Ferguson 625 IF amp chassis, new, incl. 6 valves 55/- (less valves 17/6), p/p 4/6. New UHF tuners, incl. valves 32/6 (less valves 12 6) or transistorised 70/-, p/p 4/6. New VHF tuners, GEC transistorised 70/-, A.B. Philips, Dual standard, Brayhead 3003 30/-, Gylidon C 20/-, K.B. 16M/s or 38Mc/s 10/-, p/p 4/6. Many others available. Fireball tuners, push button tuners, used, 17/6, p/p 4/6. TV Signal Boosters, transistorised, Pye Labgear Bl/53 and UHF battery 75/-, UHF mains 97 6. UHF mast-head 105/-, post free. L.O.P.T.s., scan coils, frame output trans., mains droppers, etc. for all popular makes. CRTs 14, 17, 19 inch from £4 5 (callers only). Tape recorder belts, heads, motors, etc. Salvaged components, large selection transformers scan coils, turrets, etc. Enquiries invited. C.O.D. despatch available.—MANOR SUPPLIES, 64, Golders Manor Drive, London, N.W.11; callers, 589b, High Road, North Finchley, N.12 (near Granville Road). HIL. 9118 (day). SPE. 4032 (evg.). Early closing Thursday 1 p.m. [60]

EXCLUSIVE OFFER

PERMANENT OR TRANSPORTABLE STEEL 60-FOOT AERIAL TOWERS

As supplied to British and other Governments

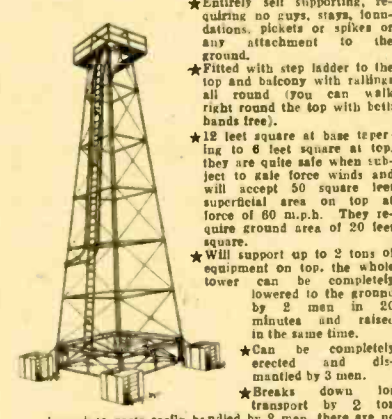★ Unique design
 ★ Scientific Construction
 having the following remarkable features.



★ Entirely self supporting, requiring no guys, stays, foundations, pickets or spikes or any attachment to the ground.
 ★ Fitted with step ladder to the top and balcony with railings all round (you can walk right round the top with both hands free).
 ★ 12 feet square at base tapering to 6 feet square at top, they are quite safe when subject to gale force winds and will accept 50 square feet superficial area on top at force of 60 m.p.h. They require ground area of 20 feet square.
 ★ Will support up to 2 tons of equipment on top, the whole tower can be completely lowered to the ground by 2 men in 30 minutes and raised in the same time.
 ★ Can be completely erected and dismantled by 3 men.
 ★ Breaks down for transport by 2 ton lorries into parts easily handled by 2 men, there are no small loose parts, no nuts or bolts to get lost or damaged; all screws and adjustments are fully protected from rust and so designed to be free from damage when re-assembled or left loose on the ground.
 ★ Footproof—the tower cannot be erected if not assembled correctly. No skilled labour is required and no special tools are necessary.
 ★ Can be raised and lowered, erected and dismantled and removed as many times as desired.
 ★ Everything necessary for the complete tower to put into use and raised and lowered is provided: full drawings and instructions.

These fine Towers were made in England by B.I.C. and cost the Government £2,200 each. They are B.I.C. & E.W. and in maker's original packing. You can see one erected at our Premises.

**Cost £2,200
 Price Brand New
 £345**

10-page list of over 1,000 different items in stock available—keep one by you.

★ Uniselectors 10 Bank 25 Way	£1 15
★ 7 Track Tape Readers	£12 10
★ 7 Track Tape Punched	£12 10
★ 6ft. Enclosed Rack Cabinets	£25 0
★ T-200 Panadaptors 450/470 Keys	£30 0
★ A-1 Multi-core Cable Testers 2 Kv.	£40 0
★ Nardia 500 w. Ultrasonic Cleaner	£85 0
★ Silidms Shelves rack mounting	£3 0
★ Magnetic Recording Wire, 1-in. reel	£2 0
★ 3M Video Recording Tape, 1in.	£5 10
★ Marconi S.S.B. Receivers RB-22 2/32 mc/s.	£80 0
★ R.C.A. 420 Mc/s Yagi 3 el. Beams	£5 10
★ Model 15 Teletype Page Printers	£25 10
★ Model 14 Teletype Tape Readers	£25 10
★ Model 14 Teletype Repetitors	£25 0
★ R.C.A. 25 watt Projector Loudspeakers, range 1 mile	£14 10
★ Metro-Vickers Vacuum Pumps 230 v. A.C.	£22 10
★ Precision Mains Filter Units	£12 10
★ E.M.I. Recording Bridges	£7 10
★ Avo Geiger Counters	£7 10
★ Philco W.S. No. 43 Transmitters 350W	£75 0
★ E.M.I. 8794 Waveform Monitors on trolleys	£45 0
★ Motorola 6 v. Mobile Transmitters 50/40 Mc/s	£12 10
★ Pen-type Personal Dosimeters	£5 15
★ Monitor Type 56 and Power Units	£7 10
★ Marconi TF 1053 Noise Meters	£45 0
★ AN/UPM-17 Spectrum Analysers 10/16000 Mc/s	P.U.R.
★ AN/URM-33, 34, 35 Signal Generators 1000/8000 Mc/s.	P.U.R.

Carriage extra at cost on all above.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements—we can probably help—all enquiries answered.

**P. HARRIS
 ORGANFORD — DORSET**
 WESTBOURNE 85051

OSMABET LTD.

WE MAKE TRANSFORMERS ALONG WITH OTHER THINGS.
AUTO TRANSFORMERS 0-110-200-220-240 v. A.C. up or down, fully shrouded, fitted terminal blocks. 50 w. 22/6; 75 w. 27/6; 100 w. 32/6; 150 w. 37/6; 200 w. 55/-; 300 w. 70/-; 400 w. 85/-; 500 w. 120/-; 600 w. 135/-; 1,000 w. 160/-; 1,500 w. 212; 2,000 w. 217; 3,000 w. 221; 4,000 w. 225.
MAINS ISOLATION TRANSFORMERS. Input 200-240 v. A.C. 1:1 ratio, 100 w. 70/-; 200 w. 110/-; 500 w. 240/-.

MAINS TRANSFORMERS. Input 200-240 v. A.C. TX1 425-0-425 v. 250 mA., 0.3 v. 4 a. ct., 6.3 v. 4 a. ct. 0-5-6, 3 v. 3 a. 110/-; TX2 250-0-250 v. 150 mA., 6.3 v. 4 a. ct. 0-5-6, 3 v. 3 a. 60/-; TX4 300-0-300 v. 60 mA., 6.3 v. 2 a., ct. 6.3 v. 1 a. 45/-; TX5 300-0-300 v. 120 mA., 6.3 v. 1 a., 6.3 v. 2 a. ct., 6.3 v. 2 a. 60/-; TX7 45-0-45 v. 1 a. 50/-; TX8 250-0-250 v. 65 mA., 6.3 v. 1.5 a. 22/6. TX1M. 250 v. 60 Ma., 6.3 v. 0.75 a., 6.3 v. 1.5 a. 15/-.

INSTRUMENT TRANSFORMERS. Prim. 200-240 v. A.C. OMT3, Tapped sec., 5-20-30-40-50 v.; giving 5-10-15-20-25-30-35-40-50-50, 10-0-10, 20-0-20, 30-0-30 v. A.C. 1 a. 27/6; 2 a. 37/6. OMT5, Tapped sec. 40-50-60-80-90-100-110 v., giving 10-20-30-40-50-60-70-90-100-110, 10-0-10, 20-0-20, 30-0-30, 40-0-40, 50-0-50 v. A.C. 1 a. 40/-.

HEATER TRANSFORMERS. Prim. 200-250 v. A.C.; 6.3 v. 1.5 a. 9/6; 6.3 v. 3 a. 15/-; 6.3 v. 6 a. 25/-; 12 v. 1.6 a. 15/-; 12 v. 3 a. 22/6; 12 v. 0.5 a. 7/6; 24 v. 3 a. 50/-; 24 v. 0 a. 70/-; 24 v. 8 a. 110/-; 24 v. 12 a. 140/-.

Comprehensive range of transformers and chokes stocked. Carriage extra all transformers from 3/6 to 7/6 each.

TRANSFORMERS WOUND TO YOUR SPECIFICATION

POWER PACK, input 200/240 v. A.C., nominal output 12 v D.C., capacitor smoothed, bridge rect., 500 mA., 37/6. P.P. 2/6.

BATTERY ELIMINATORS, input 200/240 v. A.C., output 9 v. D.C. 150 mA., PF9 45/-; PF9 15 mA. 17/6. leaded a.a.e.

RULK TAPE ERASER, and head demagnetiser, 200/250 v. A.C., suitable any size spool, any type head, 35/-, leaded a.a.e.

LOUDSPEAKERS, new stock, famous make, full range available, all less 30% list, heavy duty 15 or 25 watt, 3 or 15 ohms list 105/-; 35 watt 15 ohms 168/-. Carriage 1/6. Lead a.a.e.

AUTOCHANGERS, Garrard, 1/4 cartridge, 1,000 100/-; 2,000 110/-; 3,000 130/-; BSR Super Slim UA25 w/cartridge. 100/-. All brand new, carriage 7/6 each.

CONDENSERS, electrolytic, 2,500/50 v. 5/6; 6,000/15 3/6; 10,000/25 2/6; 100/450 v. 3/6; 100 x 400/275 v. 3/6; 100 x 200/350 v. 4/6; min. postage 1/6.

FLUORESCENT LOW VOLTAGE LIGHTING, input 6, 12, 24 v. D.C. Extensive range of fluorescent fittings and starters. List s.a.e.

S.A.E. all enquiries please. Mail Order Only.

46, KENILWORTH ROAD, EDGWARE, MIDDX.


Tel.: 870negrave 9314.

ADJUSTABLE HOLE & WASHER CUTTERS

The right tool for trepanning holes 1" - 1 1/2" in diameter

Adjustable hole and washer cutters 18% Tungsten High Speed Tool bits

In our range of 17 Models

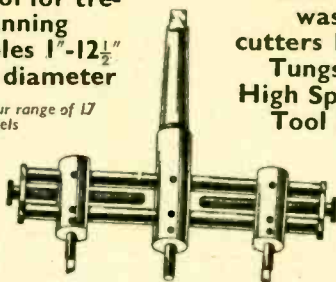

Write for illustrated brochure of our full range with straight or Morse taper 1-4 or Bitstock shank

All models available from stock

AKURATE ENGINEERING CO. LTD.


Cross Lane, Hornsey, London, N.8

TEL FITZROY 2670

WW-153 FOR FURTHER DETAILS

TO INSERT AN
ADVERTISEMENT
 IN THE
CLASSIFIED SECTION
 TELEPHONE
WIRELESS WORLD
 WATERLOO 3333
 EXT. 210

Quartz Crystal Units

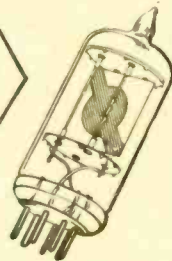

For

ACCURACY

RELIABILITY

PRICE ECONOMY

you can
DEPEND
 on

Write for
 illustrated
 Brochure &
 Price List

THE QUARTZ CRYSTAL CO. LTD.

Q.C.C. Works, Wellington Crescent,
 New Malden, Surrey (MALden 0334 & 2988)

WW-154 FOR FURTHER DETAILS

AMERICAN

TEST & COMMUNICATIONS EQUIPMENT

AN/APN-9 Loran Receiver Indicators, suitable for navigation or Scope conversion, price from £5. S.A.E. for details.

AN/ARC-33 Transceivers 225/399.9 Mc/s.
 AN/VRG-19 F.M. Transceivers. 152/174 Mc/s. £10.

AN/URC-4 & AN/URC-11 "Handy-Talkies"
 AN/ARN-6 & AN/ARN-44 Compass Receivers
 AN/TRC-8 U.H.F. Radio Relay Sets.

AN/FPN-13 X band Radar Beacons.
 CU-168/FRR 2/32 Mc/s Antenna Couplers.

AN/PSM-2A "Megger" Insulation Testers 500V 6-1,000 Meg.

AN/URM-30 Tesi Set for AN/URC-4s.

AN/PSM-6 Multimeters 1K-20 kΩ/PV.

AN-URM-61 Signal Generator 1.8/4 Gc/s.

TS-47 Test Oscillator 40/500 Mc/s. £25

T-216/GR Xtl Synthesizer Signal Generator 225/399.9 Mc/s.

AN/UPM-11A X Band Range Calibrators.

AN/USM-24A Measuring Oscilloscopes.

TS-413C/U Signal Generators 75 Kc/40 Mc/s.

TS-497B/UUR Signal Generator 2/400 Mc/s.

TS-147A/UP Radar Test Sets.

TS-917A/CG (Stelma TDA-2) Telegraph Distortion Analysers.

ME-22/PCM Decibel Meters-45/+25 DBM

Tektronix 541, 543 & 545 spare Tubes Type 5BHP2A. Price £14.

NEW GENERAL CATALOGUE

AN/103 1/-

SUTTON ELECTRONICS

Salthouse, Nr. Holt, Norfolk. CLEY 289.

PHOTO ELECTRIC CONTROL SYSTEM

Comprises a light source unit with optional Infra Red filter and lens system to force the light. Also a photo-electric Relay control unit. Both housed in metal cases for bench or wall mounting, sensitivity control, mains on-off switch. Works from 230/240 v. A.C. Mains. Can be used as a simple on-off switch by breaking the beam of light (invisible if Infra Red filter is used) and as such it will operate as a burglar alarm, or will open doors, etc. Also in conjunction with a counter or other equipment it will perform many functions in the factory or warehouse. Price **£9.19.6**

F.M. WIRELESS MICROPHONE 94-104 Mc/s. Transistorised. Operates from 9 v. battery. Complete with additional secret tie clip microphone. List £12/10/- **£6.15.0**

ONLY These cannot be operated in U.K.

TRANSISTORISED FM TUNER 6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in. x 4in. x 2 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9 volt battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for **£6.17.6** money

LOUDSPEAKERS. 2" 9/6
 40 ohm, 2 1/2" 80 ohm, 12" TWIN CONE 10 35/-
 watt, 15 or 3 ohm
 TWEETER 16 ohm 29/6
 10 watt, 15K-CPS
 CROSSOVER NETWORK 16 ohm 17/-

ADAPTOR. Printed circuit board, 4 trans. 8 diodes 9 v. with full instructions **£5.19.6**

BSR TAPE HEADS BRAD. 2 TRACK **39/6** pair

BSR TAPE HEADS MALL 4 TRACK **39/6** pair

REFLEX CONE TYPE WATERPROOF SPKR. 5 watt, 3 ohm, 300-16,000 c/s PA & Music **£4.5.0** Relay

MULTIMETERS **32/-** from

S.A.E. for full selection and bargain offers in Multimeters, Radios, Baby Alarms, Intercoms, Walkie-Talkies, and Rectifiers. All Post Free. C.O.D. 3/6.

DURHAM SUPPLIES

175E Durham Road, Bradford 8, Yorkshire

You are interested
 in Radio and
 T.V.?—Why not
**PUT SOME LETTERS
 AFTER YOUR NAME**

You can rapidly qualify in your spare time by means of an absorbingly interesting Chambers Postal Course. We offer expert and highly personal training backed by a "SATISFACTION-OR-MONEY-BACK" Agreement. Over 75 years' experience... thousands of successes.

FREE 100-PAGE GUIDE

Choose from hundreds of Courses—Practical Radio (apparatus supplied), Radio & T.V. Servicing, Applied Electronics, P.M.G. Cert., City & Guilds, R.T.E.B., A.M.I.E.R.E., Radio Amateurs Exam., etc. Send today for the informative 100-Page *Chambers Guide To Success*—FREE. (Please state Career, exam, or subject of interest).

Chambers College

(Dept. 855F) 148 Holborn, London, E.C.1.

SLYDLOK FUSES 15 amp. 230 v. D.C. 440 v. A.C. 1/6 ea., 15/- per doz.

HEADPHONES. Balanced armature. DLR5. Brand New. 9/6 pr. Moving coil type, with ear muffs for noise excluding. 12/6 pr. Same fitted with moving coil mike, 17/6 pr. Carbon hand mike. 7/6 each. P. & P. 2/- each item. No. 10 Assembly Headsets and Mic., moving coil. 17/6 ea. P. & P. 2/6.

TANNOY LOUDSPEAKERS. Re-entrant type, ideal for public address, enclosed in waterproof wooden case, complete with steel baffle designed to produce directional reproduction at 5 watts. 7.5Ω. 27/6 each. Carr. 5/-.

SMALL GEARED MOTORS. 12-24 v. D.C., reversible, with gears attached 15/- ea.; with blower attachment, 12/6 ea.; with fan assembly, 12/6 ea.

TRANSMITTER. BC 625, part of T/R. SCR522. For spares only. Chassis only. Complete with valves except 832s and Relay. 21/- ea. Carr. U.K. 4/-.

SIEMENS HIGH SPEED RELAYS. H96B type, 50 +50 ohms, 6/- ea.; Type H69D, 500+500 ohms, 6/- ea.; Type H96E, 1,700+1,700 ohms, 7/5 each. Carr. 1/-.

"TELE L" TYPE FIELD TELEPHONES. These telephones are fitted in strong steel case complete with Hand Gen. for calling each station. Supplied in new condition and tested. 70/- per pr. Carr. 7/6.

POST OFFICE TYPE RELAYS. 3,000 sers. 2 c/o. 2 m., slugged coil 140 ohms; 2 c/o, slugged coil 500 ohms. All at 6/- each. Carr. 1/-.

TELEPHONES. Type, by Ericsson. Telephones, 2 1,000Ω 1 br. 2 mc. c/o plus 3 c/o. 12/6 ea., 2,000Ω 4 c/o. 10/- ea.; 500Ω 4 c/o. 10/- ea. P. & P. 1/- ea.

MORSE KEYS. No. 8 assembly complete with leads, terminals and cover. 6/6 each. Carr. 2/-.

VIBRATORS. 6 v. 4 pin; 12 v. 4 pin; 12 v. 7 pin. Syn. All 6/- each. Carr. 1/-.

ELECTRO MAGNETIC COUNTERS. Register up to 9999, coil res. 300Ω 5/- each. Carr. 1/-. Ex-equipment.

ELECTRIC PRIMING PUMPS. AMERICAN SURPLUS. 24 v. D.C. Overall size 7 x 2 1/2 x 2 1/2 in. P.O.P.H. Brand New. 37/6 each. Carr. 2/-.

G.P. TYPE DESK TELEPHONES. Type 162CB, no bell or ringing dial, black only. Brand new, boxed, 27/6. Carr. 2/6 each.

P.O. TYPE TELEPHONE HAND GENERATORS. 38 v. A.C. New 7/6. P. & P. 1/-.

MODULATION TRANSFORMERS. 150 watts, suitable for pair 813s, driving 313s. Size 6in. x 5in. x 3 1/2in. Brand new, boxed. Price 27/6. Carr. 4/6.

MEGGER INSULATION TESTER 500 v. Iwth Contest range from 0.1 ohm to infinity. Bakelite case with hand gen. £9 ea. Carr. 5/6. 2 ranges, ex-Hoover stock.

CUT OUT. 12 v. or 24 v. operation. Heavy duty silver contacts (Sc 849), 7/6 ea. Carr. 1/6.

LIGHTWEIGHT HEADSET (part of "88" W. Set Equip.) complete with Boom mic., carbon made to highest Ministry Spec. Moving coil earpieces. Our price 35/- set. Carr. 3/-.

Also Super Lightweight hand set, 17/6 ea. Carr. 2/-.

200 AMP. 24 v. D.C. GENERATORS. Type P3, ex-Air Ministry, £9/10/- ea. Carr. 10/6.

YURA MINIATURE RUSSIAN TRANSISTOR RADIOS. Med. wave, complete with rechargeable merc. batteries and 2 spare batteries and charger, leather case, only 65/-.

P. & P. 2/-.

P.C.R. 12 V. VIBRATOR POWER PACKS. Brand new, 22/6 ea. P. & P. 5/-.

CONDENSERS. Paper, Sprague .1 mfd. 500 v., 5/- doz. .1 mfd. 1,500 v. 7/- doz. (incl. P. & P.).

HEAVY DUTY TERMINALS. Ex-equip. Black only will take spade terminals and wander plug. 1/6 pr. 15/- doz. pairs. P. & P. 1/6 ea. doz.

11FT. WHIP AERIALS. 6 Section. Copperised steel and painted. Dia. 3/8-in. Complete with moulded base 2 1/2 x 3 1/2 in. 12/6 complete. P. & P. 2/6.

FATIGUE METERS. 24 v. D.C. Consisting of 6 x 496D Relays. 500+500Ω. 6 x 300Ω Electro Mag. counters, etc. £3/10/- ea. Carr. 4/6.

AUTO TRANSFORMERS (AMERICAN). 3kVA. 220/110 v. Hand regulator provides 7 taps. Size 12 x 12 in. Wt. approx. 1/2 cwt. £12 and 10/- carriage.

S.A.E. all enquiries.

P. S. Radio and Electrical Stores
108 CHESTER ST., BIRKENHEAD, CHESHIRE

Tel. BIRKENHEAD 6067

Terms Cash with Order.

ALL GOODS GUARANTEED
CONVERTOR/BATTERY CHARGER. Input 12 v. D.C., output 240 v. 50 c/s. 170 watts max. Input 240 v. 50 c/s., output 12 v. 5 amp. D.C. Fully fused with indicator lamps. Size 9 1/2 x 10 x 4 1/2 in. Weight 19 lb. An extremely compact unit that will give many years reliable service, supplied with plug and leads. Only £4/10/- P. & P. 15/-.

DEKATRON SCALER/TIMERS. Various models from £6 to £12. Also available Ratemeters from £14. Write for details.

TRANSISTORS—Not remakes.
ACY 19 Mul. 4/- ea. 2S301 Tex. 4/- ea.
BCZ 11 Mul. 4/6 ea. 2S701 Tex. 4/- ea.
GET885 Mul. 4/- ea. 2S702 Tex. 4/6 ea.
2N1305 Rca. 4/6 ea. V30/201P New. 4/6 ea.
MA393 3/6 ea. V60/10P. New. 4/- ea.
2S018 Tex. 7/- ea.

VALVES
6AK5 3/- ea. D192/94 3/- ea.
6SN7 2/6 ea. 12SN7/B36 2/- ea.
12AT7 2/- ea. 6CH6 3/6 ea.
E180F 8/6 ea. 6BR7 6/- ea.
2D21 3/6 ea.

COUNTER TUBES GCI OB. 12/6 ea. Trigger tubes CV2224/G1/371K 15/- ea. GTE175M 8/- ea.

BROOKS CRYSTALS. 500kc/s: 2, 5, 10 mc/s., 10/- ea.

RELAYS
American miniature gold contacts, 4 pole co 48 v. Brand new boxed 6/6 ea.

Carpenters type 51A1/50. Brand new boxed 8/- ea. 3000 Series 5 k/ohms, 2 pole make, HD contacts 3/6 ea.

Siemens sealed HS, 48 v., spco type H96E, 3/- ea. American miniature 4-pole co 12/24 v. 200 ohms, sealed 5/6 ea.

FRACTIONAL H.P. MOTORS. 240 v. 50 c/s. Brand new. Ideal models, fans, etc. 8/6 ea.

TRANSFORMERS. All 200/250 inputs, tapped 0-6-12-18, 3 amp. 15/- ea. 7 amp. 30/- ea.

H.T. TRANSFORMERS, e.g., 450-0-450, 250 mA. 3 x 6.3-3 amp. 1 x 5 v. 2 amp. Potted Parmeko/Gardiners, as new 50/- ea. Write stating requirements.

NEW DIODES. Mullard genuine OAB1, 1/6 ea. CV448/425, 1/- ea.

METROSILS. Ideal pulse suppression 2/- ea.

EHT CONDENSERS. 7.5 kv. working, with clips. 0.1 mfd. 5/6 ea., 0.25 mfd. 8/6 ea.

Cash with order. Post paid over 10/-.

CHILTMead LTD.,
22 Sun Street, Reading, Berks.

FOR SALE
E.M.I. RE.404 Studio Stereo/Mono Mixing Console transistorised throughout. 10 Channels (5 left and right). Complete with presence filters. Tone Controls and provision for M.S. & A.B. working with spreader facility. Fully isolated Monitor System incorporated. Manufactured in 1962. Price £1,250.

Enquiries to:
CALAN ELECTRONICS LTD.
6 Croft Street, DALKEITH, Scotland.
Phone: DALKEITH 2344

GODLEYS
SHUDEHILL, MANCHESTER 4
Telephone: BLACKfriars 9432


Sole Manchester Distributors for world famous BRYAN AMPLIFIERS

Agents for Ampex, Akai, Ferrograph, Tandberg, Brenell, B & O, Vortexion, Truvox, Sony, Leak, Quad, Armstrong, Clarke & Smith, Lowther, Fisher, Goodmans, Wharfedale, Garrard, Goldring, Dual, Decca, Record Housing, Fitrope, G.K.D., etc.

Any combination of leading amplifiers and speakers demonstrated without the slightest obligation.

TELFORD OSCILLOSCOPE CAMERAS

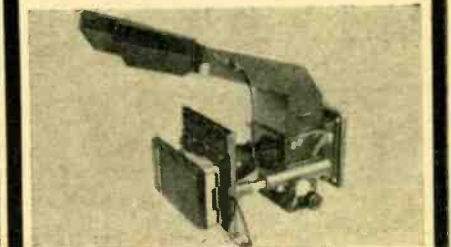MODULAR CONSTRUCTION — ADD TO BASIC CAMERA AS REQUIREMENT ARISES



TYPE A OSCILLOSCOPE CAMERA

- ★ VIEWING SYSTEMS INCLUDE PARALLAX-FREE VIEWING DURING EXPOSURE
- ★ ADAPTORS FOR ALL POPULAR SCOPES
- ★ LENSES f1.5, f1.9, f2.8, f3.5. CHOICE OF OBJECT/IMAGE RATIOS
- ★ ACCESSORIES INCLUDE SOLENOID OPERATION AND DATA RECORDING
- ★ FILM BACKS: POLAROID® 10 SECOND PRINTS: ROLL, PACK, OR CUT FILM ALL CONVENTIONAL PHOTO MATERIALS INCLUDING 35 mm.

® Registered trade mark of Polaroid Corp. U.S.A.

TYPE A. Illustrated; other types available
Full details will be gladly supplied on request

TELFORD PRODUCTS LTD
4 WADSWORTH ROAD,
GREENFORD, MIDDx.
Tel: 01-998 1011
MEMBER OF BENTIMA GROUP.
WW—155 FOR FURTHER DETAILS



WORLD RADIO & T.V. HANDBOOK

1968 ED. 42/- P. & P. 1/-

RADIO HANDBOOK by Editors and Engineers, new 17th ed. 84/-, P. & P. 4/6.
ELECTRONIC COUNTING, CIRCUITS, TECHNIQUES, DEVICES by Mullard, 27/6, P. & P. 1/-.
TAPE RECORDER SERVICING MECHANICS by Schröder, 21/-, P. & P. 1/-.
COLOUR T.V. TRAINING MANUAL by Oliphant, 40/-, P. & P. 4/6.
COMPUTER DICTIONARY AND HANDBOOK by Sippel, 90/-, P. & P. 4/6.
SYNCHROS AND SERVOS by Brite Training and Retraining Inc. 35/-, P. & P. 1/-.
ELECTRONICS HOBBIES MANUAL by Standard Telephones, 10/6, P. & P. 1/3.
TRANSISTOR SUBSTITUTION HANDBOOK, new 7th ed., 15/-, P. & P. 1/-.

Where possible 24-hour service guaranteed.

UNIVERSAL BOOK CO.

12 LITTLE NEWPORT ST., LONDON, W.C.2
 (Leicester Square Tube Station)

RADIO/ELECTRONIC Retailers advised to send for periodic lists of new/surplus spares and components: good profits.—Details from Box W.W. 202, "Wireless World".

QUANTITIES of Barretter valves, CL33, CY31 and CIC, wanted, new and boxed; have for exchange new 6AQ5, EL84, 6BR7 and EC88 valves, or will buy for cash.—Harrington Photographic, 435, Green Lanes, London, N.4. 01-340 5241. [1910]

SOUND recording equipment (professional), including mixers and spares. Ampex 350 portable recorders, power packs, etc., surplus to requirements major London Studio; s.a.e. for lists.—Box WW 1965, "Wireless World."

A Better deal for cash customers. We do not provide interest free credit but offer a generous discount of 15% for cash. Equipment despatched brand new in sealed cartons on receipt of remittance with order. Agents for all leading makes. Demonstrations, service guidance.—Write or phone. Callers welcome. Open all day Saturday, Thursday half day.—Audio Services, Ltd., 82, East Barnet Rd., New Barnet, Herts. Tel. Barnet 6605. [20]

ARTICLES WANTED

GLASS working machinery, re-unning plant, vacuum pumps, gauges, spares, plant, etc.—Tel. Mr. Barrett. 01-654 6470. [1963]

VALVE voltmeter—2 millivolts to 30 volts. Marconi. Dawe or Advance model preferred. Also Roband R050A Oscilloscope for Video Servicing.—01-472 2110 [1964]

WANTED, all types of communications receivers and test equipment.—Details to R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London E.11. Lev. 4986. [63]

NEW GRAM AND SOUND EQUIPMENT

GLASGOW—Recorders bought, sold, exchanged; cameras, etc., exchanged for recorders or vice-versa.—Victor Morris, 343, Argyle St., Glasgow, C.2. [11]

BUILDING A "SCOPE"

Indicator unit type 10Q53. One of the finest units to appear on the surplus market, modern manufacturer, 10.B.7.G. and 3.10, valves, built in E.H.T. unit producing 3kV. to a modern version of the 5in. V.C.R.517 tube, brilliance, focus, X and Y shift. Controls on front panel, circuit diagram supplied. Ideal for conversion to an oscilloscope. Size of unit 7in. x 7 1/2in. x 19in. long. Used but good condition 60/-, carriage 19/-. Circuit diagram sold separately, 3/9, Post Free.

New Catalogue No. 17. Government and manufacturers surplus. Also new components, 3/- post free.

RADIO CONTROL
 BRIGHTON
 ARTHUR SALLIS
 93 NORTH ROAD BRIGHTON SUSSEX
 EX-GOV'T ELECTRICAL SURPLUS

SURPLUS BARGAINS (EX GOVT.)

PAMOUS No. 19 SET TRANS-RECEIVER. Covers 2-8 Mc/s. in 2 bands. 11 valve superhet transceiver including 807 P.A. Power reqs. LT. 12 v. H.T. rec. 275 v. H.T. transmit 500 v. D.C. Slightly used. 55/- Selected condition. 85/- All 19 set ancillary parts available.
No. 31. TRANSCIEVER VHF, 40/48 Mc/s. Tunable. 90/60/44 volts battery operation, 70/-
No. 88. TWO-WAY RADIO, 40/42 Mc/s. Crystal controlled. 4 channel. 50/- each.
No. 38. TWO-WAY RADIO, 7-9 Mc/s. Tunable. 40/- each. B44. VHF RADIO TELEPHONE. 60-95 Mc/s. Crystal controlled. 12 v. D.C. operation. 27/10/-
No. 82. TRANSMITTER RECEIVER, 1.0-10 Mc/s. Tunable or crystal controlled. 12 v. D.C. operation. £16/10/-
R.C.A. C29 TRANSMITTER RECEIVER, 2-8 Mc/s. Complete station. Brand new. 12 or 24 v. D.C. operation. £19/10/-
No. 52 RECEIVERS. Few left. Used (serviceable). 27/10/-
TUBULAR STEEL TELESCOPE AERIAL MASTS. 30ft. 4 section, 70/- 32ft. as above with 12ft. whip, 80/- 34ft. 6 section, 90/-
MAKE YOUR OWN AERIAL MAST! 5ft. 8in. 2in. dia. interlocking steel sections (7 sections make 25ft. mast) 20/- per section.
NYLON GUY ROPES, with semi-automatic tensioner. 33ft.. 6/6. 50ft. 7/6. 60ft. 9/-
CLASS "D" WAVEMETER. 92/6.
ROTARY TRANSFORMERS by HOOPER. 12 v. D.C. input. Output 250 v. D.C. at 125 mA. 25/- 12 v. D.C. input. Output 490 v. D.C. at 65 mA. 25/-
REJECTOR UNIT. For rejecting unwanted signals. Switched 4 ranges. 1.2-10 Mc/s. 30/-
E.F. ANTENNA TUNER (A.T.U.). 160/80/40 metres. 25/-
MOVING COIL HEADPHONES. Soft rubber earpads. 19/6.
D.L.R. BALANCED ARMATURE HEADPHONES. 12/6.
HEADSET WITH BOOM MICROPHONE. As used with 88 Set. 22/6.
MOVING COIL HEADPHONES AND MICROPHONES. 21/6.
MOVING COIL FIST TYPE MICROPHONE. 17/6.
TELETYPE SETS. High Power No. 1. Mk. II, with amplifier. New and unused. 70/- each; or less amplifier. 55/- each
ALL ITEMS CARRIAGE PAID MAINLAND ONLY
 Lists giving fuller details of these and many other surplus bargains, 2/- S.A.E. all enquiries (Please print clearly).
A. J. THOMPSON (Dept. WW)
 "Eiling Lodge" Codicote, Hitchin, Herts. Tel.: Codicote 242

FOR SALE 2,000,000 TRANSISTORS

BRITISH MANUFACTURERS SURPLUS
 Owing to the reorganisation and expansion by the manufacturers of these transistors, it has been necessary to clear them as surplus to requirements. These devices would normally be tested several times into different groups, approx. 50% would be used as good industrial transistors and a further 35% would make diodes. The remaining 15% would be disposed of as scrap rejects.

Offering these devices in varied quantities make them ideal for **AMATEUR ELECTRONICS, RADIO HAMS** and for **EXPERIMENTAL USE IN SCHOOLS, COLLEGES** and **INDUSTRY**.

All transistors are in mixed lots, mainly PNP but some NPN, all are Germanium type. Prices and quantities as follows:—

100 pieces (approx. count by weight)	10/-
300 " " " " " "	25/-
500 " " " " " "	40/-
1,000 " " " " " "	60/-
10,000 " " " " " "	£25

Larger quantities by negotiation.

TERMS:—CASH WITH ORDER, all goods sent by return. Please add 2/- towards Post & Packing orders up to £3, over £3, 5/-. Monthly accounts for Education Authorities, etc. on receipt of an Official Order. Minimum order £3.

EXPORT ENQUIRIES WELCOME

All correspondence, cheques, Postal Orders, etc. to:
DIOTRAN SALES, P.O. Box 5, 63, High St., WARE, HERTS. Tel. WARE 3442

CURSONS TRANSISTORS ALL GUARANTEED

1/- each. BAY31, BAY50, DK10, OA70, OA81.
 2/- each. XA101, XA102, OC71, OC72, OC81, OC81D, OC44, OC45, GET16, FST3/1, ACY22.
 3/- each. OC139, OC140, 2N708, 2N2894, BY100, RA5310AF, 2N914, BSY26, BSY27, BSY95A, AFZ12, BFY18, BFY19, BFY26.
 7/6 each. RASS08AF, CRS3/40, BLY10, BLY11, BUY10, BUY11, ADY22, ADY23, ADY24, OC26.

ZENER DIODES

3.9 v. to 26 v., 1/4 w. 3/0 each; 1.5 w. 4/-; 7 w. 5/- ea.

CURSONS, 78 BROAD STREET, CANTERBURY KENT. S.A.E. LATEST NEW LIST

WE BUY

any type of radio, television, and electronic equipment, components, meters, plugs and sockets, valves, and transistors, cables electrical appliances, copper wire, screws, nuts, etc. The larger the quantity the better. We pay Prompt Cash.

Broadfields & Mayo Disposals, 21 Lodge Lane, London, N.12

RING 445 2713
 445 0749
 958 7624
 958 9842

SURPLUS HANDBOOKS

19 set Circuit & Notes	4/8 p/p 6d
1155 set Circuit & Notes	4/8 p/p 6d
H.R.O. Technical Instructions	3/6 p/p 6d
38 set Technical Instructions	3/6 p/p 6d
48 set Working Instructions	3/6 p/p 6d
88 set Technical Instructions	5/- p/p 6d
8C.221 Circuit & Notes	3/6 p/p 6d
Wavemeter Class D Techn. Ins.	3/6 p/p 6d
18 set Circuit & Notes	3/6 p/p 6d
8C.1000 (31 set) Circuit & Notes	3/6 p/p 6d
CR.100/B28 Circuit & Notes	8/6 p/p 6d
E.107 Circuit & Notes	5/- p/p 6d
A.B.88D Instruction Manual	15/- v/p 1/6d
62 set Circuit & Notes	4/6 p/p 6d
52 set Sender and Receiver Circuits	6/- post free
Circuit Diagrams 3/- each, post free.	
R.116(A), R.122(A), R.1355, R.F.24, 25 & 26, A.1134, T.1154	
CR.300, BC.942, BC.943, E.M.P. "R" BC924, 22 SET.	
Resistor Colour Code Indicator, 1/6, p/p 6d.	

Postage rates apply to U.K. only.
 Mail order only to:
INSTRUCTIONAL HANDBOOK SUPPLIES, Dept. W.W., TALBOT HOUSE, 28 TALBOT GARDENS, LEEDS. 8.

DAMAGED METER?

Have it repaired by Glaser

Reduce overheads by having your damaged Electrical Measuring Instruments repaired by L. Glaser & Co. Ltd. We specialise in the repair of all types and makes of Voltmeters, Ammeters, Microammeters, Multirange Test Meters, Electrical Thermometers, Recording Instruments, Leak Detectors, Temp. Controllers, all types Bridges & Insulation Testers, etc.

INSTRUMENT REPAIRS

As contractors to various Government Departments we are the leading Electrical Instrument Repairers in the Industry. For prompt estimate and speedy delivery send defective instruments by registered post, or write to Dept. W.W.:-

L. GLASER & CO. LTD.
 1-3 Berry Street, London, E.C.1.
 Tel.: Clerkenwell 5481-2

RS **symbol of quality** **trade only**
for electronic components - by return

VALVES

VALVE cartons by return at keen prices; send 1/- for all samples and list.—J. & A. Boxmakers, 75a, Godwin St., Bradford, 1. [10]

VALVES WANTED

WE buy new valves, transistors and clean new components, large or small quantities, all details, quotation by return.—Walton's Wireless Stores, 55, Worcester St., Wolverhampton. [62]

CAPACITY AVAILABLE

AIRTRONICS, Ltd., for coil winding, assembly and wiring of electronic equipment, transistors sub-unit sheet metal work.—3a, Waterland Rd., London, S.E.15. Tel. 01-852 1706. [61]

TRAIN TODAY FOR TOMORROW

Start training TODAY for one of the many first-class posts open to technically qualified men in the Radio and Electronics industry. ICS provide specialized training courses in all branches of Radio, Television and Electronics—one of these courses will help YOU to get a higher paid job. Why not fill in the coupon below and find out how?

Courses include:

- RADIO/TV ENG. & SERVICING
- AUDIO FREQUENCY
- CLOSED CIRCUIT TV
- ELECTRONICS—many new courses
- ELECTRONIC MAINTENANCE
- INSTRUMENTATION AND SERVOMECHANISMS
- COMPUTERS
- PRACTICAL RADIO (with kits)
- NEW PROGRAMMED COURSE ON ELECTRONIC FUNDAMENTALS

Guaranteed Coaching for:

- Inst. Electronic & Radio Eng's.
- C. & G. Telecom. Techns' Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Cert.
- Radio Amateur's Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education

Start today - the ICS way

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 230 Parkgate Rd., London, S.W.11.
 Please send FREE book over

Name

Address

2.68

RESISTANCE WIRES
EUREKA-CONSTANTAN

Most Gauges Available

NICKEL-CHROME MANGANIN
NICKEL-SILVER

COPPER WIRE

ENAMELLED, TINNED, LITZ, COTTON AND SILK COVERED

SMALL ORDERS PROMPTLY DESPATCHED—B.A. SCREWS, NUTS, WASHERS, SOLDERING TAGS, EYELETS and RIVETS
 EBONITE and BAKELITE PANELS, TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS

SEND STAMP FOR LIST. TRADE SUPPLIED

POST RADIO SUPPLIES

33 Bourne Gardens, London, E.4
 Telephone 01-254-4688

B.P.A. ELECTRONICS can undertake immediately, short or long-term contracts for:— Electronic and Electro-Mechanical assembly and wiring, Coil windings (including toroidal), cable forming, vacuum impregnation and encapsulation, printed circuit board manufacture including layout and preparation of artwork, inspection to A.I.D. or A.R.B. if required.—Boulton Paul Aircraft Ltd., Wolverhampton. Tel. Fordhouses 3191. [1956]

SERVICES OFFERED

JOIN Audio Supply Association 7/6 p.a. 65-page photo-graphically illustrated, non-advertising HI-FI catalogue 5/-; equipment housing booklet 1/6; your best guides for safe buying.—10, Clifford St., London, W.1. [1954]

TUITION

TV and Radio, City & Guilds, R.T.E.B. Certs., etc., on "satisfaction or refund of fee" terms, thousands of passes. For full details of exams and home training courses (including practical equipment) in all branches of radio, TV, electronics, etc., write for 132-page handbook—free, please state subject.—British Institute of Engineering Technology (Dept. 150K), Aldermaston Court, Aldermaston, Berks. [115]

DISCOUNT TRANSISTORS

Quantity prices (in brackets) for 5 OR MORE SAME TYPE. First grade, guaranteed.

AD161/2 .. 15/- pair	T1S61M .. 4/- (3/6)
AF239 .. 12/- (8/-)	2N706 .. 3/6 (3/-)
BC107 .. 4/- (3/9)	2N2926 .. 3/- (2/6)
BC109 .. 4/- (3/9)	2N3702 .. 4/- (3/6)
BC168 .. 2/6 (2/-)	2N3703 .. 4/- (3/6)
B-5000 .. 10/- (9/-)	2N3704 .. 4/- (3/8)
IS44 .. 2/6 (2/-)	2N3705 .. 4/- (3/6)
T1302B .. 18/- (16/-)	2N3707 .. 5/- (4/6)
T1407 .. 6/- (5/6)	2N3983 .. 6/- (5/6)
T1S60M .. 4/- (3/8)	2N4058 .. 5/6 (5/-)

RECTIFIERS: IS557 800piv, 0.5A, 3/6 (3/-); INTEGRATED CIRCUIT, CA3020, 550mW class B a.f. amp. with RCA data sheet, 33/- (30/-); THERMISTOR RS4 for "WW" RC oscillator 21/- Mail order only. Orders over 10/- U.K. post paid.

AMATRONIX LTD. (Dept. WW2)
 396 SELSDON ROAD, CROYDON, SURREY, CR2 0DE

KINGSTON-UPON-HULL Education Committee, P.R.I.C. College of Technology, Principal E. Jones, M.Sc.

FULL-TIME courses for P.M.G. certificates and the radar maintenance certificate, also in electrical and electronic engineering.—Information from College of Technology, Queen's Gardens, Kingston-upon-Hull. [118]

STUDY radio, television and electronics with the world's largest home study organisation, I.E.R.E., City & Guilds, R.T.E.B., etc. Also practical courses with equipment. No books to buy. Write for free prospectus to ICS (Dept. 442), Intertext House, London, SW11. [24]

RADIO officers see the world. Sea-going and shore appointments. Trainee vacancies during 1968. Grants available. Day and boarding students. Stamp for prospectus.—Wireless College, Colwyn Bay. [12]

GENUINE BRAND NEW PRODUCTS AT LESS THAN HALF PRICE

BRAND NEW BRITISH RECORDING TAPES—P.V.C. POLYESTER AND MYLAR, with fitted leaders in polythene and boxed, manufactured by reputable British firm, all 100% tested, not to be confused with sub-standard, imported or usual tapes.

S.P.	3"	160'	2/-	5"	600'	6/-
	5 1/2"	900'	8/-	7"	1,200'	9/-
L.P.	3"	225'	2/6	5"	900'	8/6
	6 1/2"	1,200'	10/-	7"	1,800'	12/-
D.P.	3"	350'	4/6	5"	1,200'	12/-
	5 1/2"	1,800'	16/-	7"	2,400'	20/-

Brand new pre-recorded beginners and brush-up courses on tape, in FRENCH, GERMAN, ITALIAN, SPANISH. Full set course of 26 lessons recorded at 3 1/2 L.p.s. on Scotch & E.M.I. Course lasts 1 hr. and is complete with manual. Our price just 19/6, retail 59/6.

100% TESTED TRANSISTORS

OC23	8/-	AF118	4/-	AD149	8/-
OC25	8/-	AF117	4/-	AFZ12	8/-
OC28	8/-	AF118	4/-	BCY33	6/6
OC28	8/-	AF119	4/-	BCY34	6/6
OC35	10/-	AF127	4/-	BCY38	6/6
OC38	12/6	AC107	8/-	BCY39	6/6
OC44	3/-	AC126	4/-	BFY50	5/6
OC45	3/-	AC127	4/-	BFY61	5/6
OC46	3/-	AC128	4/-	BFY52	5/6
OC70	3/-	AD149	8/-	GET103	4/-
OC72	3/-	OC181	4/-	GET113	4/-
OC73	3/-	OC189	4/-	GET116	10/-
OC73	3/-	OC170	4/-	GET118	5/-
OC78D	3/-	OC171	4/-	GET119	5/-
OC81	3/-	OC173	4/-	GET121	5/-
OC81D	3/-	OC200	8/-	GET567	5/-
OC78	3/-	OC22	8/-	GET873	4/-
OC78	3/-	OC30	8/-	GET887	4/6
OC82	3/-	OC38	12/6	GET889	4/6
OC82D	3/-	OC77	4/-	GET990	4/6
OC84	4/6	OC81	4/-	GET897	4/6
AF114	4/-	OC123	4/6	GET897	4/6
AF115	4/-	2N404	6/6	GET898	4/-

TRANSISTORS, MATCHED SETS

- 1 OC44+2 OC45, per set, 10/-
- 1 GET874P sleeved Yellow OC44, per set, 10/-
- 1 GET873P sleeved White OC45 1st I.F., per set, 10/-
- 1 GET873P sleeved Blue OC45 2nd I.F., per set, 10/-
- 1 OC81D+2 OC81, per set, 9/6
- 1 OC82D+2 OC82, per set, 9/6
- OC83 GET118/119, set of 3, 9/6

SILICON DIODES

- BYZ 12 (400 v. P.I.V., 6 amp.) 5/-
- BYZ 13 (200 v. P.I.V., 6 amp.) 5/6

ELAC SPEAKERS, 7 x 4in. Price 12/6.

4 TRANSISTOR PUSH/PULL ULTRA. Lin amplifier, 1 watt output, battery operated, designed for electronic instruments, microphones and public address. Many other uses. Price 15/6.

CABINET TO MATCH ABOVE. 10/-

VOLUME CONTROLS, with switch, price 3/6.

TRANSISTORISED CAR RADIOS, normally £12/10/- Our price £6/19/6.

TELESCOPIC CAR AERIALS, 3 extensions, price 17/6

ALL GOODS SUPPLIED CARRY OUR MONEY BACK SATISFACTION GUARANTEE

Postage on all orders 1/-.
 STARMAN, 28, Linkerscroft Avenue, Ashford, Middlesex, Ashford S3020.

DUXFORD ELECTRONICS (W.W.) DUXFORD, CAMBS.

C.W.O. P. & P. 1/-. Minimum order value 5/-. (Trade inquiries invited).

POTENTIOMETERS (Carbon): Long life, low noise. $\frac{1}{2}$ W at 70°C $\pm 20\%$ $\leq \frac{1}{2}$ M, $\pm 30\%$ $> \frac{1}{2}$ M. Body dia. $\frac{1}{8}$ in. Spindle 1in. x $\frac{1}{16}$ in. 2/- each. Linear: 1k, 2.5k, 5k, etc., per decade to 10M. Logarithmic: 5k, 10k, 25k, etc., per decade to 5M.

SKELETON PRE-SET POTENTIOMETERS (Carbon): Linear: 1k, 2.5k, 5k, etc., per decade to 5M. Miniature: 0.3W at 70°C. $\pm 20\%$ $\leq \frac{1}{2}$ M, $\pm 30\%$ $> \frac{1}{2}$ M. Horizontal (0.7in. x 0.4in. P.C.M.) or Vertical (0.4in. x 0.2in. P.C.M.) mounting 1/- each.

Submin. 0.1W at 70°C $\pm 20\%$ $\leq \frac{1}{2}$ M, $\pm 30\%$ $> \frac{1}{2}$ M. Horizontal (0.4in. x 0.2in. P.C.M.) or Vertical (0.2in. x 0.1in. P.C.M.) mounting, 10d. each.

RESISTORS (Carbon film): High stability, very low noise, $\frac{1}{2}$ W at 70°C. Body $\frac{1}{16}$ in. x $\frac{1}{16}$ in. Values in each decade: 10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91 from 4.7 Ω to 1M. $\pm 5\%$, 2d. each. 1.2M, 1.5M, 1.8M, 2.2M, 2.7M, 3.3M, 3.9M, 4.7M, 5.6M, 6.8M, 8.2M, 10M, $\pm 10\%$, 2d. each.

SILICON RECTIFIERS: 0.5A at 70°C. 400 P.I.V., 3/-; 800 P.I.V., 3/3; 1,250 P.I.V., 3/9; 1,500 P.I.V., 4/-.

SEMI-CONDUCTORS (All New): OAR, OAB1, 1/6. OC44, OC45, 1/9. OC71, OC72, OC73, OC81, OC8D, OC82D, OC170, OC171, 2/3. OC140, AF115, AF116, AF117, 3/-. SEND S.A.E. FOR FULL CATALOGUE.

FREE to ambitious engineers! 132-page Guide to City & Guilds, A.I.O.B., A.R.I.C.S., G.C.E., etc., on "Satisfaction or Refund" terms, thousands of Passes—over 600 Home Study Courses in all branches of Engineering, Building, Radio, Electronics, etc.—Write: B.I.E.T. (Dept. 151K), Aldermaston Court, Aldermaston, Berks. [14]

MARSHALL'S SEMICONDUCTOR CENTRE

Fully guaranteed devices at low prices

2/6 ea.	4/- ea. or 3 for 10/-	4/8 ea. or 5 for 20/-	6/6 ea.
OC45	ACV17	BY100	3N404
OC71	ACV18	GET887	2N1091
OC72	ACV19	GET889	2N2297
	ACV22	GET890	BCY33
	ACV28	GET896	BCY34
	AF114	GET897	BCY38
	AF115	GET898	BCY39
	AF116		OC26
	AF117	8/- ea.	OC28
	AF118		OC28
	AF125	AD140	OC25
	AF127	AD149	OC30
	GET102	GET118	OC200
	GET103	GET573	OC202
	GET113	GET587	OU205
	GET118		
	GET119	OC22	
	OC77	OC24	
		OC20	

NEW ADDITIONS TO OUR RANGE

4/6	NKT214	292	294	274
	NKT271	272	274	275
5/-	NKT146	224	225	
5/6	NKT135	212	244	245
	NKT281	713	734	773
6/-	NKT125	126	210	211
	NKT213	129	225	229
	NKT238	239	240	242
	NKT674	677	781	
6/6	NKT241	603	613	736

NEWMARKET SILICON SILIND RANGE 7/6 ea.

2N696	5/-	NKT10419	NKT10519	BFX85	10/-
2N697	5/-	NKT10339	NKT10439	BFX86	9/-
2N698	4/6	NKT13329	NKT13429	BFX87	10/-
2N706	4/6	2N1306	6/6	28501	5/6
2N709	4/6	2N1307	6/6	28502	5/6
2N708	5/-	2N1308	8/-	28503	5/8
2N743	4/6	2N1309	8/-	28731	4/6
2N744	4/6	2N2220	5/-	28732	4/6
2N763	4/6	2N2221	5/-	28733	4/6
2N914	6/6	2N2222	5/-	BCY10	6/6
2N1151	12/6	2N2905	8/-	BCY13	6/6
2N1132	12/6	2N2906	8/-	BCY70	8/6
2N1302	4/6	2N2907	8/-	BCY71	10/6
2N1303	4/6	28102	7/6	BCY72	5/6
2N1304	5/6	28103	7/6	BF115	4/6
2N1305	4/6	28104	7/6	BFX84	8/-

Post & Packing 1/- per order. Quantity discounts available
A. MARSHALL & SON (LONDON) LTD.,
28 Cricklewood Broadway, N.W.2.
Telephone: 01-452-0161 Dept: W.W.15

LAWSON BRAND NEW TELEVISION TUBES

Complete fitting instructions are supplied with every tube.

Terms: C.W.O. Carriage and insurance 10/-.

LAWSON TUBES

18 CHURCHDOWN ROAD
MALVERN, WORCS.

Tel. MAL 2100

The continually increasing demand for tubes of the very highest performance and reliability is now being met by the new Lawson "Century 99" range of C.R.T.s.

"Century 99" are absolutely brand new tubes throughout manufactured by Britain's largest C.R.T. manufacturers. They are guaranteed to give absolutely superb performance with needle sharp definition screens of the very latest type giving maximum Contrast and Light output; together with high reliability and very long life.

"Century 99" are a complete range of tubes in all sizes for all British sets manufactured 1947-1967.

2 YEARS FULL REPLACEMENT GUARANTEE.
WW-156 FOR FURTHER DETAILS



12"—£4 : 10 : 0
14"—£5 : 10 : 0
17"—£5 : 19 : 0
19"—£6 : 19 : 0
21"—£7 : 15 : 0

£17 2/6in. D.C. OSCILLOSCOPE NEW

A brand new, specially designed, oscilloscope for the amateur featuring the following:

2 1/2in. dia. green medium persistence trace. Push pull D.C. Y amplifier. Frequency up to 0.1 MHz or 1.0 MHz. Calibrated Y attenuator for precision voltage measurement. Wide range Time Base. X Amplifier. Flyback suppression. 12in. wide, 9in. high, 10in. deep. Fully guaranteed 12 months. S.A.E. for full details.

£16 15/6 (post and packing included)

C.W.O. or C.O.D. (charges extra)

MITRE ELECTRONIC PRODUCTS

204 Buckingham Road, Hampton, Middlesex

I.E.R.E. City & Guilds and R.T.E.B. exams. Specialised ICS home-study course will ensure success. For details of wide range of exam. and diploma courses in radio, TV and electronics, also new practical courses with kits, write to: ICS (Dept. 522), Intertext House, London, SW11. [23]

TEST EQUIPMENT — SURPLUS AND SECONDHAND

SIGNAL generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc. In stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [64]



FABULOUS VALUE

TRANSISTORISED HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4 1/2" deep. 14 transistors plus 4 diodes, separate Bass and Treble—10 watts total power. Frequency response 50-15,000 c/s.


EASY TO INSTALL
NO TECHNICAL KNOWLEDGE
REQUIRED
ONLY 26 + P&P 17/6

H.P. terms available. Deposit £6:16:6d and 12 monthly payments of 38/5d (Total H.P. £29:17:6d). Send £7:14:0d today.

FANTASTIC BARGAIN OFFER!

"TRANSCONTINENTAL" FULLY TRANSISTORISED STEREO PHONIC RADIOGRAM CHASSIS

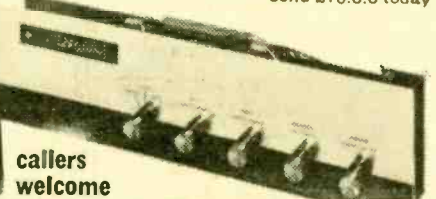Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price **ONLY 34 1/2 GN.** P&P 17/6
10 Watts Total output
17 Transistors & 10 diodes
EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY
H.P. available £9:2:6d deposit plus 18 monthly payments of £1:15:9d (Total H.P. £41:6:0).
Send £10.0.0 today



callers
welcome

POST
THIS
COUPON
NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name _____
Address _____
W _____

LEWIS radio 100 CHASE SIDE, SOUTHGATE,
LONDON, N.14. TELEPHONE PAL 3733/9666

WW-157 FOR FURTHER DETAILS

LONDON CENTRAL RADIO STORES

10-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box handset. Thoroughly overhauled. Guaranteed. £3/10/- per unit.

20-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box. Thoroughly overhauled. Guaranteed. £7/15/- per Unit.

MODERN HAND SETS with coiled lead, grey, white and black. £2/6. P.P. 3/-.

TELEPHONE COILED HAND SET LEADS, 3 core 5/8, P.P. 1/-.

MODERN DESK PHONES, 2 tone grey or black, with internal bell and handset with 0-1 dial. £4/10/-. P.P. 7/6.

WIRELESS SET No. 38 A.F.V. Freq. range 7.3 to 9.0 Mc/s. Working range 1 to 2 miles. Size 10 1/2 x 4 x 6 1/2 in. Weight 6 1/2 lb. Includes power supply 8B- and spare valves and vibrator also tank aerial with base. £6 per pair or £3 single. P.P. 25/-.

ELECTRICITY SLOT METERS (1/- in slot) for A.C. mains. Fixed tariff to your requirements. Suitable for hotels, etc. 200/250 v. 10 A. 80/-; 15 A. 90/-; 20 A. 100/-; P.P. 7/6. Other amperages available. Reconditioned as new. 2 years guarantee.

QUARTERLY ELECTRIC CHECK METERS. Reconditioned as new. 200/250 v. 10 A. 42/6; 15 A. 52/6; 20 A. 57/6. Other amperages available. 2 years guarantee.

TWIN GONG TELEPHONE, extension bells, 21/-.

8-BANK UNISELECTOR SWITCHES. 25 contacts, alternate wiping £2/15/-; 8-bank half wipe £2/15/-; 6-bank half wipe, 25 contacts 47/6. P.P. 3/6.

DESK PHONES. Black Bakelite cases, complete with hand set and internal bell with 0-1 dial. 42/6. P.P. 6/-.

HIGH-SPEED ELECTRO-MAGNETIC COUNTERS. Ex-Govt 4 digit. 25/50 v. D.C. Size 4 x 1 1/2 in. Single coil, 2,300Ω. Single coil 600Ω, 8/6. P.P. 3/6.

EX. GOVT. BALANCED ARMATURE THROAT MIKES complete with plug, new. 7/6. P.P. 3/6.

DESK PHONES from 35/- . Various types in stock. Final End Selectors, Relays, various callers, also 19 Receivers in stock. All for callers only.

23 LISLE ST. (GER 2969) LONDON W.C.2
 Closed Thursday 1 p.m. Open all day Saturday

RECEIVERS AND AMPLIFIERS—SURPLUS AND SECONDHAND

HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. 165

TECHNICAL TRAINING

CITY & GUILDS (Electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V., automation, etc., send for 132-page handbook—free.—B.I.E.T. (Dept. 152K), Aldermaston Court, Aldermaston, Berks. 115

BECOME "Technically Qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV, servicing and maintenance. R.T.E.B., City & Guilds, etc., highly informative 120-page Guide—free.—Chambers College (Dept. 837K), 148, Holborn, London, E.C.1. 116

P.M.G. Certificates, City & Guilds and I.E.R.E. Examinations. Also many non-examination courses in Radio, TV and Electronics. Study at home with world famous I.C.S. Write for free Prospectus stating subject to—International Correspondence Schools (Dept. 443), Intertex House, Parkgate Rd., London, S.W.11. 125

BOOKS

"ULTRASONIC delay Lines" G. F. Brockelsby, B.Sc., A.R.C.S., A.M.I.E.E., J. R. Palfreeman, R. W. Gibson, B.Sc. (Eng.), Grad. I. Mech. E. The authors are members of a team which has been working on ultrasonic delay lines, since the early days, at the Mullard Research Laboratories. This is the first book to be written specifically on the subject, which has important applications in radar, radio and television, electronic computers, pulse-forming networks, correlation techniques and multi-channel communication systems. The early chapters discuss basic principles and the various type of delay lines are then covered. The chapter on electronics for delay lines deals fully with the design of broad-band amplifiers, oscillators, etc., either with transistors or valves. The last two chapters are devoted to the delay line measurements and the many applications of delay lines. Among the five appendices there is one containing nearly 60 curves which give the characteristics of many delay line materials. The final appendix discusses one of the latest developments, ceramic transducers, 65/- net, 66/3 by post.

COLOUR TELEVISION

With particular reference to the

PAL SYSTEM

There are 157 diagrams and photographs and 83 illustrations, in colour.

by G. N. Patchett

40/- Postage 1/-

MODERN TAPE RECORDING & HI FI, by K. Peters. 30/- . Postage 1/-.

SYSTEMATIC ANALOGUE COMPUTER PROGRAMMING, by A. S. Charlesworth & J. R. Fletcher. 25/- . Postage 1/-.

ELEMENTS OF FEEDBACK & CONTROL, by A. M. Hardie. 55/- . Postage 1/-.

ELECTRONIC ENGINEER'S REFERENCE BOOK, by L. E. C. Hughes & F. W. Holland. 126/- . Postage free.

COMPUTER DICTIONARY & HANDBOOK, by C. J. Sippl. 90/- . Postage 2/-.

RADIO VALVE DATA, 8th ed., compiled by "WW." 9/6. Postage 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON, W.2

'Phone: PADddington 4185
 Closed Sat. 1 p.m.



Two New Titles From Iliffe Books

ILIFFE BOOKS have acquired the exclusive UK, European and Commonwealth sales rights of these important books

Integrated Circuit Engineering

Basic Technology

By the Staff of Integrated Circuit Engineering Corporation,

Phoenix, Arizona

391 pp fully illustrated 220s net. 4s 6d. postage.

Microelectronic Technology

Selected Articles from Semi-conductor Products and Solid State Technology

Edited by Samuel L. Marshall

232 pp fully illustrated 130s net. 1s 6d. postage.

available from leading booksellers

ILIFFE BOOKS LTD DORSET HOUSE, STAMFORD ST., LONDON, S.E.1



THE ONLY COMPREHENSIVE RANGE OF RECORD MAINTENANCE EQUIPMENT IN THE WORLD!

Send stamps value 9d. for 16 page booklet and supplementary data sheets Nos. 1 and 4 giving the fullest and latest information.

CECIL E. WATTS LIMITED
Darby House
Sunbury-on-Thames, Middx.

★ **HAMMERITE HAMMER ENAMEL** ★
AIR DRYING • JUST BRUSH ON
1/2 pint 8/-, p/d. 1/9. 1 pint 16/-, p/d. 3/-.
Blue, silver, black, bronze (and others).
NO PRIMERS NEEDED. Just try it.
Brushed sample, interesting list FREE.
INDUSTRIALISTS !!! SAVE TIME
AND \$\$\$'s (2 pints will do a Mini!)
FINNIGAN SPECIALITY PAINTS (W) Mickley Square,
Stocksfield, Northumberland. Tel: Stocksfield 2280

TRIAL TIN
covers 5 sq. ft.
3/9
9d. post.

WW-158 FOR FURTHER DETAILS

BERRY'S RADIO
Require
COUNTER SALES STAFF AND STENOGRAPHERS
(fully experienced applicants only)
5 day week, L.Vs., PERMANENCY
25 HIGH HOLBORN, LONDON, W.C.1

WW-160 FOR FURTHER DETAILS

INSTANT ** ELECTRICITY ANYWHERE!



AMAZING NEW AMERICAN DYNAMOTOR UNIT which runs from any 12-v. CAR BATTERY and produces a BIG ELECTRICAL OUTPUT of 250/240 v. at 220 watts. Marvellous for TELEVISION, ELECTRICAL DRILLS, MAINS LIGHTING and all Universal A/C/DC mains equipment. Wonderful for A.C. FLUORESCENT LIGHTING. ONLY £12/10 - plus 30/- cart. envelope for illustrated details. Open 7 days a week.

Send stamped addressed envelope for illustrated details. Open 7 days a week.

SCIENTIFIC PRODUCTS (Dept. H)
Onward Building (rear of Fleetwood Arms Hotel), Mount Street, Fleetwood, Lancs.

REDUNDANT OR SURPLUS RADIO — ELECTRONIC STOCKS WANTED
OSMABET LTD.
46 KENILWORTH ROAD, EDWARE, MIDDX.
TEL: STONEGROVE 9314

SERVO AND ELECTRONIC SALES LTD.
NOW OFFER A
RECONDITIONING SERVICE FOR INDUSTRIAL INSTRUMENTS
Moving Coil Multi-range Meters, Electrical and Electronic Test Equipment of all kinds. Estimates given for all repairs.
67 London Road, Goddard, Surrey. Tel.: 01-888 1612
(Instrument Repairs and Counter Sales)
WE ARE SPECIALISTS SUPPLIERS IN ELECTRONICS,
AND ELECTROMECHANICS
Also at: 43 High St., Orpington, Kent Tel.: 31066 33978
Mill Road, Lydd, Kent Tel.: Lydd 252

DINSDALE MK II AMPLIFIERS
Printed circuits and parts for mono and stereo versions. Special new power amp. printed board eliminates earth loop problems.
BAILEY 20 WATT AMPLIFIER. All parts available for this unit including Radmetal-cored Driver Transformer and recommended bi-filar wound Mains Transformer.
MULLARD 10W. A.B. TRANSISTOR AMPLIFIER. SPECIAL CLEARANCE.
Printed Circuit Boards to Mullard specification, fully drilled and fluxed. Price 4/- each or 7/- for two post free.
Layout Diagrams 9d. each. All other parts available. Please send S.A.E. for all Lists.

HART ELECTRONICS
321 Great Western Street, MANCHESTER 14

FOR SALE—
4 Westminster Multiwinders, 10-way Automatic Interleave.
PRICE: £100 each and carriage. Can be viewed by arrangement.
Large range of
TRANSFORMER LAMINATIONS
in Radiometal, Mumetal & H.C.R. "C" and "E" cores—Case and Frame Assy's. Please send for list.
J. BLACK
44 Green Lane, Hendon, N.W.4
Tel.: 01-203 1855 & 3033

DEIMOS LTD
TAPE RECORDER FOR RESEARCH, INDUSTRY AND PROFESSIONAL AUDIO
single and multichannel
8 CORWALL LANE, HILLINGDON, MDX.
HAYES 3561
WW-159 FOR FURTHER DETAILS

TRANSFORMERS
MAINS TRANSFORMERS
IVA TO 2.5 KVA
AUTO TRANSFORMERS
20 watts to 5,000 watts
Trade and Professional Enquiries Only
OLYMPIC TRANSFORMERS LTD
224 HORNSEY ROAD
LONDON, N.7
NOR 2914

RESISTORS
1/2 watt carbon film 5%
All preferred values in stock from 10 ohms to 10 megohms, 2d. each.
Send S.A.E. for free sample.

CAPACITORS
Mullard Miniature Metallised Polyester P.C. Mounting, all 250V. D.C. working. 0.01mf., 0.022mf., 0.047mf., 0.1mf., 0.22mf., all at 6d. each. Hunts tubular 0.1mf. 200V. working at 3d. each. Send 6d. stamp for extensive list of low-priced Electronic Components, Instruments & Equipment. Please include 1/- postage & packing on all orders under £1.
Dept. WW8.
BRENSAL ELECTRONICS LIMITED,
CHARLES STREET, BRISTOL, 1.

WANTED
High Band, Fixed Station (25 Watt minimum) in working order or repairable. Full details, Manufacturer, Model, Age, Condition, Price, etc.
Box No. 5041 /o "Wireless World"

ENTHUSIASTS
for tape recording subscribe to the Magazine with the ZEBRA stripes!
25/- (U.S.A.) \$3.75) yrly. incl. postage.
FREE SPECIMEN COPY ON REQUEST
PRESTIGE HOUSE, 14-18 HOLBORN, LONDON, E.C.1. 01-242 4851

WANTED—
Redundant or Surplus stocks of Transformer materials (Laminations, C. cores, Copper wire, etc.), Electronic Components (Transistors, Diodes, etc.), P.V.C. Wires and Cables, Bakelite sheet, etc., etc.
Good prices paid
J. BLACK
44 Green Lane, Hendon, N.W.4
Tel. 01-203 1855 and 3033

VIDIO RECORDING TAPE
LARGE QUANTITIES OF HALF-INCH AND ONE-INCH VIDIO RECORDING TAPE AVAILABLE, TESTED AND GUARANTEED.
ALSO QUANTITIES OF HALF-INCH AND ONE-INCH PRECISION TAPE SPOOLS AND CASES.
PRICES ON APPLICATION
RADIO TRADERS LTD.
8 STEPHAN STREET,
TOTTENHAM COURT ROAD,
LONDON, W.1
Tel. 01-636 4666

YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL WAY —

Get these **air drying GREY HAMMER** OR **BLACK WRINKLE (CRACKLE) Finishes** NOW!

Yukan Aerosol spraykit contains 16 oz. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 14/11 at our counter or 15/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 oz. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 3 cans plus optional transferable snap-on trigger handle (value 5/3 for 18/11 carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount to:
YUKAN, W/W, 307a, EDGWARE ROAD, LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.
 Open all day Saturday. Closed Thursday afternoons.

WW—161 FOR FURTHER DETAILS

"ABACS of Nomograms." By A. Glet. Translated from the French by H. D. Philpen and J. W. Head. Most engineers have made use of nomograms at some time in their careers, and are fully alive to the fact that they are a very convenient tool when the same formula has to be solved repeatedly for several sets of variables. It is fair to say, however, that only a small proportion of even those who habitually employ nomograms know how to construct them for their own use. Most of the comparatively small literature on the subject is written for mathematicians and is extremely difficult for the practical engineer to comprehend. This book is essentially practical and not only demonstrates the many and varied applications of the abac of nomogram, but shows how even those without highly specialized mathematical knowledge may construct their own charts. 35/- net from all booksellers. By post 36/- from Iliffe Books Ltd., Dorset House, Stamford St., London, S.E.1.

"SONOCOLOR" CINE RECORDING TAPE
 Superior quality 5" reel, 900ft. L.P. with strobe markings, also cine light deflector-mirror. Suitable all tape recorders and OUR PRICE 14/- EACH cine projectors. List 28/- Post 2/6



SMITHS PRECISION SIX MINUTE DELAY ACTION SWITCH
 Clockwork actuated

10/6 EACH (3 or more Post 2/6 post free).

Separate switching up to 6 mins. 15 amps. 250 volts. MADE FOR ROLLS WASHERS. Ideal photographic timer, sequence switching operations, etc., etc. Brand new units at a fraction of their value.

SPECIAL PURCHASE STELLA RECORD PLAYER
 Amplifier and Loudspeaker—all transistor—top performance of discs at 33 $\frac{1}{3}$, 45 and 78 r.p.m. LP xtal cartridge. Smart red or blue plastic cabinet. WORTH DOUBLE



OUR PRICE £8.5.0 Post 5/-



THE INSTANT BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER

200/250 A.C. Leaflet S.A.E. 35/- Post 2/6

TRANSISTOR BOOSTER—
 DOUBLE YOUR VOLUME!

Black plastic cabinet speaker with 20ft. lead for transistor radio, intercom, mains radio, tape recorder. Size: 7 $\frac{1}{2}$ in. x 5 $\frac{1}{2}$ in. x 3in. 30/- Post 2/6



SPECIAL OFFER! BRAND NEW B.A.S.F. TAPES
 60 min. Cassette C60 (For Philips etc.) 17/6
 7 in. L.P. 1,800 ft. (Cat. LGS35) 45/- Post 2/6—3 or
 7 in. D.P. 2,400 ft. (Cat. LGS26) 70/- more post free.

RADIO COMPONENT SPECIALISTS
 337 WHITEHORSE RD., CROYDON. Tel: 01-684-1665

HORSTMANN 20AMP ELECTRIC TIME SWITCH
 36 HR SPRING RESERVE



200/250 volts, 20 amp. contacts, ON/OFF twice every 24 hours at any manually pre-set times. By-pass override, 36 hour spring reserve, overcomes stopping in case of power cut. Can be supplied with Solar dial if required, on at dusk, on at dawn. Used but perfect. LIMITED QUANTITY. 69/6 P. & P. 4/6.

Waterproof metal case approx. 6in. x 3 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. 10/- extra. **HORSTMANN 15 DAY CLOCKWORK TIME SWITCH** Jewelled movement. Once ON/OFF every 24 hours at any manually pre-set times. Key and mounting bracket. Used but perfect. 5 amp model. Fully guaranteed. 35/- P. & P. 4/6. **VENNER 200/250v. FLASHER UNITS, ON/OFF every second.** 200W contacts. Suppressed. Reconditioned. 42/6 inc. post.

Box 365, KINGSWOOD SUPPLIES (w.w.10) 4, SALE PLACE, LONDON, W.2. Tel: 01-723 8189.

WW—162 FOR FURTHER DETAILS

"TELEVISION Engineering Principles and Practice. vol. III. Waveform Generation." by S. W. Ames. B.Sc. (Hons.), A.M.I.E.E., and D. C. Birkinshaw, M.B.E., M.A., M.I.E.E. The third volume of a comprehensive work on the fundamentals of television theory and practice, written primarily for the instruction of BBC engineering staff. This volume gives the application in television and sinusoidal, rectangular, sawtooth and parabolic waves and shows the mathematical relationship between them. The main body of the text is devoted to the fundamental principles of the circuits commonly used to generate such signals, the treatment being largely descriptive in nature and therefore less mathematical than that of the previous volume. The work is intended to provide a comprehensive survey of modern television principles and practice. 30/- net from all booksellers. By post 31/- from Iliffe Books Ltd., Dorset House, Stamford St., London, S.E.1.

CLASSIFIED ADVERTISEMENTS

Use this Form for your Sales and Wants

To "Wireless World" Classified Advertisement Dept., Dorset House, Stamford Street, London, S.E.1

PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW

- Rate; 6/- PER LINE. Average seven words per line.
- Name and address to be included in charge if used in advertisement.
- Box No. Allow two words plus 1/-.
- Charges etc., payable to "Wireless World" and crossed "& Co."
- Press Day 6 February for March 1968 issue.

NAME.....

ADDRESS

.....

REMITTANCE VALUE..... ENCLOSED

Please write in block letters with ball pen or pencil.

NUMBER OF INSERTIONS.....

'Hike-Mike' really started something... ...the finest range of radio microphone systems in the world

From the very successful general purpose unit Hike-Mike has developed a whole range of special purpose microphone transmitters each one precision made for precision performance. Suitable for both hand-held and Lavalier operation. Write now for descriptive literature of these and the full range of Audac Audio Equipment. Demonstrations with pleasure.

AUDAC RADIO MICROPHONE AND SOUND REINFORCEMENT SYSTEMS

AUDAC MARKETING COMPANY LIMITED / CAREY ROAD / WAREHAM / DORSET / TELEPHONE WAREHAM 2245.



WW-163 FOR FURTHER DETAILS

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 119-129

Acoustical Mfg. Co., Ltd.	PAGE 21	Electro-Winds, Ltd.	PAGE 88	Linstead Electronics, Ltd.	PAGE 114	Salford Elec. Inst. Co., Ltd.	PAGE 48
Adcola Products, Ltd.	Cover 41	English Electric Valve Co., Ltd.	3, 5, 7	London Central Radio Stores	137	Sallis, Arthur, Radio Control Ltd.	134
A.D.S. Relays, Ltd.	79	Enthoven Solders, Ltd.	35	London Microphone Co., Ltd.	64	Samsons (Electronics), Ltd.	115
Advance Electronics, Ltd.	45	Erie Resistors, Ltd.	35	L.S.T. Components	106	Scientific Products	138
Akurate Eng. Co., Ltd.	132	Ever Ready Co. (G.B.), Ltd.	20	Lyons Claude, Ltd.	40	S.D.S.A.	24
Amatronic, Ltd.	135	Ferranti, Ltd.	63	Marconi Co., Ltd.	69, 74	Service Trading Co.	96, 97
Ampex (Great Britain), Ltd.	75	Finligan Speciality Paints	138	Marriott Magnetics, Ltd.	2	Servo & Electronic Sales	138
Anders Electronics, Ltd.	11, 56	Foamair, Ltd.	22	Marshall, A.	136	Sinclair Radionics, Ltd.	76, 77
A.N.T.E.X., Ltd.	62, 80	Gardners Transformers, Ltd.	26	Mayco Products, Ltd.	134	S.M.E., Ltd.	34
A.P.T. Electronic Industries, Ltd.	65	General Electric Co., Ltd.	28	McMurdo Instrument Co., Ltd.	134	Smith, G. W. (Radio), Ltd.	90, 91
Armstrong Audio	62	Glaser, L., Co., Ltd.	134	Mills, W.	102, 103	Starman Tapes	135
Audac, Ltd.	140	Godleys	133	Milo International	104	Super Electronics	129
Audio & Design	110	Goldring Mfg. Co., Ltd.	30	Miniature Electronic Components, Ltd.	85	Superior Electronics Inc.	80
Audix, B. B.	42	Goodmans Industries, Ltd.	30	Minnesota Mining & Mfg. Co., Ltd.	70	Sutton Electronics	132
Automatic Machine Services	85	Goodman Reproducers, Ltd.	58	Milward, G. P.	104	Swanco	101
Avco, Ltd.	1	Greenwood, W. (London), Ltd.	27, 29, 31	Modern Book Co.	44	Tape Recording Magazine	138
Avon Communications & Electronics, Ltd.	64	Hall Electric, Ltd.	16	M.R. Supplies, Ltd.	44	Taylor Elec. Inst., Ltd.	53
Barrett, V. N.	102	Hanover Fair	108	Multicore Solders, Ltd.	Cover 1v	Technical Ceramics, Ltd.	39
Batey, Wm. & Co.	52	Harmsworth, Townley & Co.	38	Newmarket Transistors, Ltd.	56	Technical Trading Co.	98
Beldere Co., Ltd.	50	Harris Electronics (London), Ltd.	60	Nombrex, Ltd.	112	Telesonics, Ltd.	66
Belling & Lee, Ltd.	18	Harris, P.	131	Olympic Transformers	138	Teleton	86
Bentley Acoustic Corp., Ltd.	88	Hart Electronics	138	Omron, Ltd.	19	Telford Electronics	133
Berry's Radio	138	Harverson Surplus Co., Ltd.	92	Osmabet, Ltd.	132, 138	Teonex, Ltd.	43
Bl-Pak Semiconductors	96	Harwin Engineers, Ltd.	31	Parker, A. B.	29	Thompson, A. J.	134
Bl-Pre-Pak, Ltd.	106	Hatfield Instruments, Ltd.	79-81	Park Royal Porcelain Co., Ltd.	24	Thorn-AEI Radio Valves & Tubes, Ltd.	68
Black, J.	139	Henry's Radio, Ltd.	113	Partridge Transformers Ltd.	64	Thorn Special Products, Ltd.	51, 61
Bradley, G. & E., Ltd.	14	H.P. Radio Services, Ltd.	27	Patrick & Kinnie	131	Trend Electronics, Ltd.	78
Bresnal	138	Hunt, A. H. (Capacitors), Ltd.	47	P.C. Radio Ltd.	104, 105	Trio Corporation	32
Britain, Chas. (Radio), Ltd.	87	Iliffe Books Ltd.	98	Pinnacel Electronics, Ltd.	25, 54	T.R.S. Radio	111
Britec, Ltd.	131	I.M.O. (Electronics), Ltd.	107, 108, 114, 115, 118, 130, 137	Plessy Co., Ltd.	37	Turner, Ernest, Elec. Insts., Ltd.	12
British Elec. Resistance Co., Ltd.	58	Industrial Instruments, Ltd.	83	Post Radio Supplies	135	Unifab	88
British Institute of Engineering Technology	13	Instructional Handbooks Supplies International Correspondence Schools	134, 56, 135	Proops Bros., Ltd.	36	Universal Book Co.	134
Brown, N. C., Ltd.	60	J.A.C. Electronics, Ltd.	44	Pye Telecommunications, Ltd.	23	Valradio, Ltd.	44, 52
B.S. Radio and Electrical Stores	133	Jackson Bros. (London), Ltd.	17	Quartz Crystal Co., Ltd.	132	Van Dam	95
Buckingham Press, Ltd.	27	John's Radio	110	Rasco	85	Vero Electronics, Ltd.	73
Bulgin, A. F., & Co., Ltd.	77	Kempner, S., Ltd.	82	Radford Electronics, Ltd.	60	Vitality Bulbs, Ltd.	81
Bullers, Ltd.	86	Keyswitch Relays, Ltd.	Cover II	Radio & T.V. Components (Acton), Ltd.	109	Vortexion, Ltd.	71
Cardross Eng., Ltd.	129	Kingswood Supplies	139	Radio & T.V. Services, Ltd.	81	Walker-Spencer Components	86
Carr Fastener Co., Ltd.	46	Kongsberg	57	Radio Components Specialists	139	Watts, Cecil E., Ltd.	138
Cathodeon Crystals, Ltd.	4	Lasky's Radio, Ltd.	94, 95	Radio Exchange	112	Webber, R. A., Ltd.	29
Chambers Coloure	132	Lawson Tubes	136	Radonic Products, Ltd.	46	Welwyn Tool Co., Ltd.	82
Chilthead, Ltd.	133	Ledon Instruments, Ltd.	80	Radiospares, Ltd.	135	West Hyde Developments, Ltd.	129
Clark, A. N. (Engineers), Ltd.	42	Levell Electronics, Ltd.	136	Radio Traders	138	West London Direct Supplies	75
C.R.E.I. (London)	59	Levor Electronics, Ltd.	86	Rafie, P. F.	112	Weyrad (Electronics), Ltd.	85
Cursons, B. W.	134	Light-Soldering Developments Ltd.	22	Rank-Wharfedale, Ltd.	48, 84	Whiteley Electrical Radio Co., Ltd.	82
Davis, Jack (Relays), Ltd.	34	Lind-Air (Electronics), Ltd.	89	Rastra Electronics, Ltd.	68	Wilkinson, L. (Croydon), Ltd.	92
Daystrom, Ltd.	8, 9	Eddystone Radio, Ltd.	15	R.C.A.	49	Wingrove & Rogers, Ltd.	84
Deimos, Ltd.	138	Elcom, Ltd.	64	Readers Radio	108	Yukan Products	139
Durham Supplies	132	Electronic Brokers, Ltd.	118	Resound, Ltd.	41	Z. & I. Aero Services, Ltd.	116, 117
Duxford Electronics	136	Electronics (Croydon), Ltd.	99	Rola Celestion, Ltd.	52, 53		
Dynatron, Ltd.	134	Electrovalue	102	R.S.T. Valve Mail Order Co.	114		

Printed in Great Britain for the Publishers, ILLIFF TECHNICAL PUBLICATIONS LTD., Dorset House, Stamford St., London, S.E.1. by COREWALL PRESS, Paris Garden, London, S.E.1. Wireless World can be obtained abroad from the following: AUSTRALIA: and New Zealand: Gordon & Gotch, Ltd. 192/1, A. H. Wheeler & Co. CANADA: The Wm. Lawsoe Subscription Service, Ltd.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd.; William Dawood & Sons (S.A.) Ltd. UNITED STATES: Eastern News Co., 306 West 11th Street, New York 14. CONDITIONS OF SALE AND SUPPLY: This periodical is sold subject to the following conditions, namely that it shall not, without the written consent of the publishers first given, be lent, re-sold, hired out or otherwise disposed of by way of Trade at a price in excess of the recommended maximum price shown on the cover; and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorized cover by way of Trade; or added to or as part of any publication or advertising, literary or pictorial matter whatsoever.

ADCOLA
PRODUCTS LIMITED
 (Regd Trade Mark)
SOLDERING EQUIPMENT

MANUFACTURERS OF THE WORLD'S FINEST SOLDERING INSTRUMENTS

CATALOGUE SURVEY No. 4 THE L.107.

THIS INSTRUMENT IS THE BIG BROTHER OF THE L64 AND IS PARTICULARLY SUITED TO THE LARGEST TAGGING WORK FOUND IN SOME INDUSTRIES. ALTHOUGH IT IS OF ROBUST CONSTRUCTION IT WEIGHS ONLY $6\frac{1}{2}$ OZS. AND OPERATOR FATIGUE IS OBIATED. THE STANDARD SIZE IS $\frac{1}{4}$ " BUT ALTERNATIVE SIZES RANGE FROM $\frac{1}{8}$ " TO $\frac{5}{16}$ " TO COVER ALL TYPES OF APPLICATION. IN ACCORDANCE WITH NORMAL ADCOLA POLICY, SPECIAL TEMPERATURE AND VOLTAGES ARE AVAILABLE AT NO EXTRA CHARGE.



Send for details to
HEAD OFFICE SALES & SERVICE

ADCOLA PRODUCTS LTD
 ADCOLA HOUSE, GAUDEN ROAD,
 LONDON, S.W.4.

Telephones: 01-622-0291/3

Telegrams: SOLJOINT, LONDON, S.W.4

AUSTRALIAN ASSOCIATES: ADCOLA PRODUCTS PTY. 673 WHITEHORSE ROAD. MONT ALBERT, MELBOURNE
 AGENTS IN ALL LEADING COUNTRIES



The world's finest cored solder

ERSIN

Multicore

5 CORE

SOLDER

FOR THE FACTORY

STANDARD GAUGES IN WHICH MOST ALLOYS ARE MADE AND LENGTHS PER LB. IN FEET.

S.W.G.	INS.	M.M.	FT. PER LB.	
			60/40	SAVBI
10	.128	3.251	25.6	24
12	.104	2.642	38.8	36
14	.080	2.032	65.7	60.8
16	.064	1.626	102	96.2
18	.048	1.219	182	170
19	.040	1.016	262	244
20	.036	.914	324	307
22	.028	.711	536	508
24	.022	.558	865	856
26	.018	.46	1292	1279
28	.014	.375	1911	1892
30	.012	.314	2730	2695
32	.010	.274	3585	3552
34	.009	.233	4950	4895

STANDARD ALLOYS INCLUDE LIQUIDUS

TIN/LEAD	B.S. GRADE	MELTING TEMP.	
		°C.	°F.
60/40	K	188	370
Savbit No 1	—	215	419
50/50	F	212	414
45/55	R	215	419
40/60	G	234	452
30/70	J	255	491
20/80	V	275	527

HIGH AND LOW MELTING POINT ALLOYS

ALLOY	DESCRIPTION	MELTING TEMP.	
		°C.	°F.
T.L.C.	Tin/Lead/Cadmium with very low melting point	145	293
L.M.P.	Contains 2% Silver for soldering silver coated surfaces	179	354
P.T.	Made from Pure Tin for use when a lead free solder is essential	232	450
H.M.P.	High melting point solder to B.S. Grade 5S	296-301	565-674

- Contains 5 cores of non-corrosive high speed Ersin flux. Removes surface oxides and prevents their formation during soldering. Complies with B.S. 219, 441, DTD 599A, B.S.3252, U.S. Spec. QQ-S-571d.
- Savbit alloy contains a small percentage of copper and thus prolongs the life of copper soldering iron bits 10 times. Liquidus melting temperature is 215°C—415°F. Ministry approved under ref. DTD/900/4535
- Solder Tape, Rings, Preforms and Washers, Cored or Solid, are available in a wide range of specifications.
- Liquid fluxes and printed circuit soldering materials comply with Government specifications. Ask for special details.



Arax 4-core acid cored solder

Used in 38 industries it has replaced tinman's and blowpipe solders, fluid and paste fluxes and killed spirits for rapid and precision soldering in metal fabrication processes.

Arax Flux—exclusive to Multicore—has the fastest speed

of flux in any cored solders. Flux residue is easily removable with water or, where flame heating is employed, is entirely volatilised. Residue will not contaminate plating baths. No pre-cleaning is necessary and the speed ensures that the solder will flow between the laps by capillary action, thus using the minimum amount of solder. Not recommended for wire to tag joints in radio or electrical equipment.

Bib accessories can be supplied in bulk packings at very competitive prices

wire stripper and cutter

Strips insulation without nicking wires, cuts wires and cables cleanly. Model 3 is semi-permanently adjusted. Model 8 incorporates a unique 8-gauge selector.



A

recording tape splicer



Precision made, chrome plated complete with razor cutter. Provides quick and accurate tape editing. Standard model for 1/2" tape. NEW 3/4" type is available for computer and video tape.

B

instrument cleaner

Anti-static. Specially formulated for cleaning delicate instrument panels, plastic, chrome, glass and printed surfaces. Antiseptic, non-toxic, non-flammable, does not smear. Used and recommended by leading electronic manufacturers. In 1-gallon and 5-gallon containers and 4 fl. oz. bottles.



C

tape head maintenance kit size E

Cleans tape heads and all parts of the tape path of magnetic tape decks. Applicator and Polisher Tools and Sticks are available separately.



D

For further information please apply on your Company's note paper mentioning the product references Dept. WW, Multicore Solders Limited, Hemel Hempstead, Herts. Telephone: Hemel Hempstead 3636