
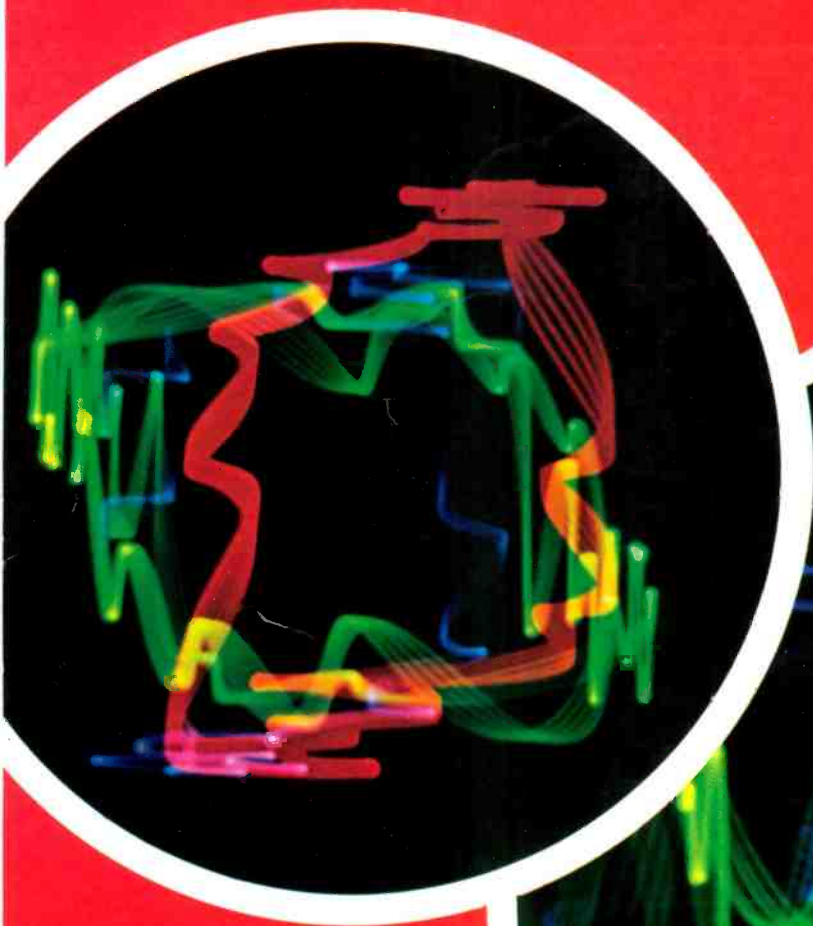


wireless world

JULY 1977 40p

Intruder alarm
Ladder crystal filters

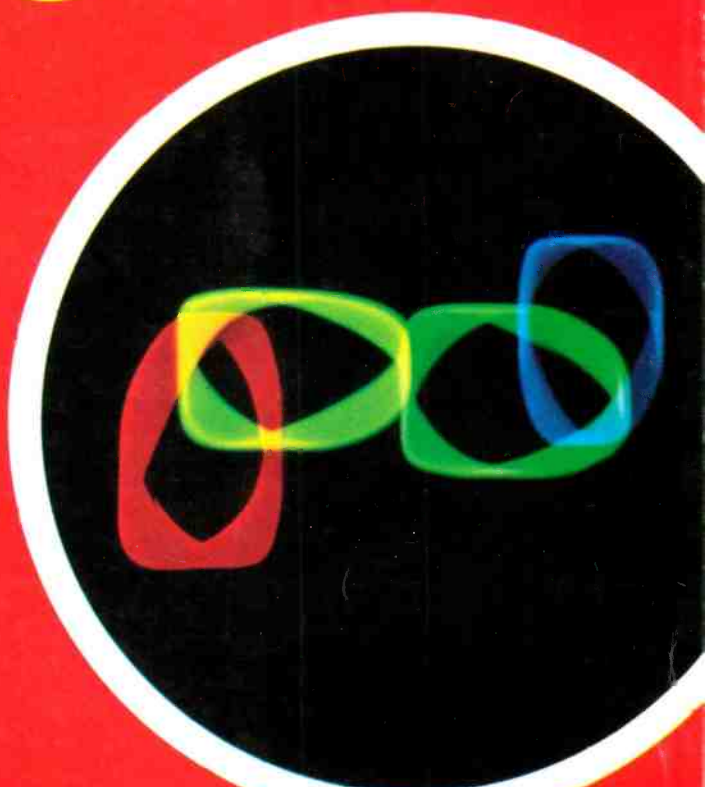

Kinetic images from sound

mi COUNTER-REVOLUTION

There's been a revolution in **mi**'s design and production departments at St. Albans to bring you a new range of low cost high-quality frequency meters up to 560MHz.

The revolution in design is a new LSI chip built for **mi** by an associated GEC Company, which incorporates all the LF circuitry to reduce the total i/c component count below any competitor. Result: quick and easy to make, very reliable and easy to service.

The revolution in production is our new high volume production line which uses "Autotest" at both module and final test stages to enable **mi** to produce high quality counters at low cost.



See the benefits of the **mi** counter-revolution and reap them for yourselves:

- 10Hz to 80MHz Model TF2430
- 10Hz to 200MHz Model TF2431
- 10Hz to 560MHz Model TF2432
- All direct counting—no prescaling to slow down readings
- Easy to use—few controls
- AGC on all channels—no sensitivity controls
- Wide dynamic range
- Resolution switchable to 0.1Hz
- LSI chip contains all LF circuitry—high reliability
- Bright 7 or 8 digit LED display with leading zero suppression
- Meets IEC 348 and BS4743 safety requirements
- Choice of frequency standards
- Will accept mains voltage on all high impedance inputs

Two-year guarantee

Counterplot with us! Circle our number on the reader service card (or ring or write) our counterintelligence is at your service.



MARCONI INSTRUMENTS LIMITED
 Longacres, St. Albans, Hertfordshire, England, AL4 0JN
 Telephone: St. Albans 59292 Telex: 23350
 A GEC-Marconi Electronics Company


wireless world

Electronics, Television, Radio, Audio

JULY 1977 Vol 83 No 1499

Contents

- 35 The Ernie and Arnie show?
- 36 Microwave intruder alarm *by M. W. Hosking*
- 40 Kinetic images from sound *by Thomas E. Mintner*
- 43 Multi-system ambisonic decoder *by M. A. Gerzon*
- 48 News of the month
 - Viewdata cracks the PO armour
 - MRUA call for mobile "Annan"
 - Plessey chief wants social responsibility
- 51 Digital television via satellite *by M. E. B. Moffat*
- 54 H.F. predictions
- 55 Eliminating adjacent-channel interference *by P. L. Taylor*
- 58 Letters to the editor
 - Annan and cable
 - Improving Matrix H surround sound?
 - Transient intermodulation distortion
- 62 Crystal ladder filters *by J. Pochet, F6BQP*
- 64 Logic design — 6 *by B. Holdsworth and L. Zissos*
- 66 World of amateur radio
- 67 Time code clock alarm *by N. C. Helsby*
- 71 Decoupling *by S. W. Amos*
- 75 Paris components show
- 79 Modification of weather satellite facsimile machine for radio weather charts *by G. R. Kennedy*
- 84 New Products
- 86 Sidebands *by "Mixer"*
- 123 APPOINTMENTS VACANT
- 136 INDEX TO ADVERTISERS

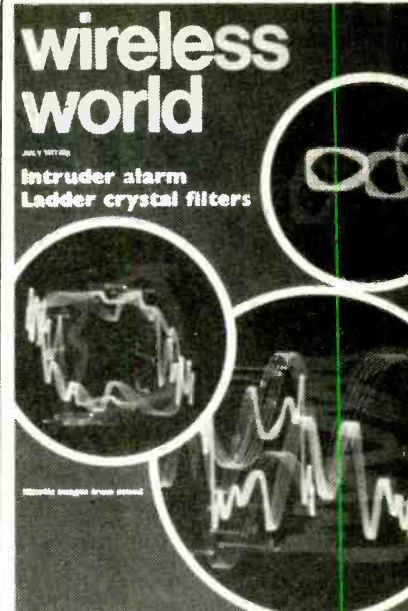

Front cover shows multi-colour projected laser traces produced from sound signals. System is outlined in "Kinetic images from sound" p.40

IN OUR NEXT ISSUE

Shortwave broadcasting efficiency. System developed by Radio Canada International to measure how successful a s.w. broadcasting service is in reaching its intended listeners.

Distortion in audio amplifiers analyses the mechanism of distortion resulting from transistor non-linearities in low-noise circuits. A design example follows later.

Amateur radio equipment. A survey outlining design and performance trends in commercial transmitters, receivers and transceivers at present available for amateur operators.

ISSN 0043 6062

ibpa
International Business
Press Association

ABC
ASSOCIATION OF
BUSINESS OF CALCUTTA

Current issue price 40p, back issues (if available) 50p, at Retail and Trade Counter, Paris Garden, London SE1. By post, current issue 55p, back issues (if available) 50p, order and payment to Room 11, Dorset House, London SE1 9LU.

Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.

Telephones: Editorial 01-261 8620. Advertising 01-261 8339.

Telegrams/Telex: Wiworld Bisnespres 25137 BISPRS G. Cables: Ethaworld, London SE1.

Subscription rates: 1 year: £7.00 UK and overseas (\$18.20 USA and Canada). Student rate: 1 year, £3.50 UK and overseas (\$9.10 USA and Canada).


Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.

Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Subscribers are requested to notify a change of address.

USA mailing agents: Expeditors of the Printed Word Ltd., 527 Maidson Avenue, Suite 1217, New York, NY 10022. 2nd-class postage paid at New York. © I.P.C. Business Press Ltd, 1977

We measure up to your standards


B900
Automatic Digital Bridge 1kHz 0.1%

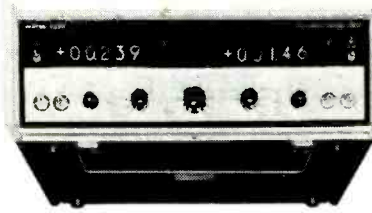

B224
Wide-range Audio Bridge 1592Hz
(200Hz–20kHz external)



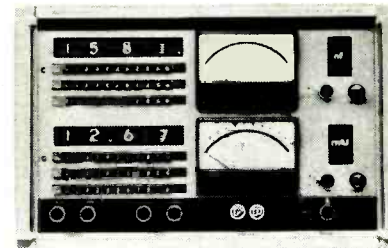B331
Self-balancing 0.01% Precision Bridge



B642
Autobalance Universal Bridge 0.1%



B421
Direct-reading Component Meter 0.25%



Whether you check components at Goods Inwards, during production or on Final Test, Wayne Kerr has the bridge you need. For fast measurements of resistance, capacitance and inductance, or for continuous monitoring of changing values, you can select the ideal instrument from our comprehensive range.

All models—AF, RF and VHF—have a wide measurement range and are easy to use. Many have automatic readout and automatic lead compensation; most will measure components *in situ*.

Only part of our range is illustrated. Send in the coupon for further information.



Wilmot Breeden Electronics
Ferrograph Rendar Wayne Kerr

Wilmot Breeden Electronics Limited,
442 Bath Road, Slough,
SL1 6BB, England.
Telephone: Burnham (06286) 62511
Telex: 847297

Please send me the Wayne Kerr short form catalogue.

Name

Position

Company

Address

Telephone

(WW 7/77)



Wilmot Breeden
Electronics Limited,
442 Bath Road,
Slough, SL1 6BB,
England.

WAYNE KERR BRIDGES

WW—058 FOR FURTHER DETAILS


LOW COST TESTERS



LEVELL

PORTABLE INSTRUMENTS

INSULATION TESTER

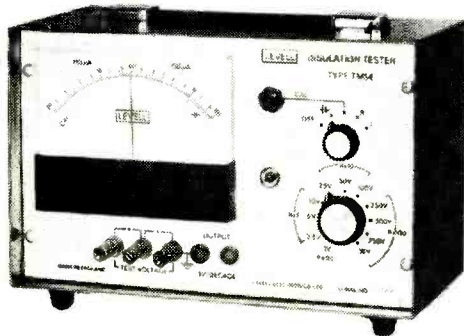

A logarithmic scale covering 6 decades is used to display either insulation resistance or leakage current at a fixed stabilised test voltage. The current available is limited to a maximum value of 3mA for safety and capacitors are automatically discharged when the instrument is switched off or to the CAL condition. The instrument operates from a 9V internal battery.

RESISTANCE RANGES

10M Ω to 10T Ω (10^{13} Ω) at 250V, 500V, 750V and 1kV.

1M Ω to 1T Ω at 25V, 50V and 100V.

100k Ω to 100G Ω at 2.5V, 5V and 10V.

10k Ω to 10G Ω at 1V.

Accuracy $\pm 15\%$ +800 Ω on 6 decade logarithmic scale.

Accuracy of test voltages $\pm 3\%$ ± 50 mV at scale centre.

Fall of test voltages $< 2\%$ at 10 μ A and $< 20\%$ at 100 μ A.

Short circuit current between 500 μ A and 3mA.

CURRENT RANGE

100pA to 100 μ A on 6 decade logarithmic scale.

Accuracy of current measurement $\pm 15\%$ of indicated value.

Input voltage drop is approximately 20mV at 100pA, 200mV at 100nA and 400mV at 100 μ A.

Maximum safe continuous overload is 50mA.

MEASUREMENT TIME

< 3 s for resistance on all ranges relative to CAL position.

< 10 s for resistance of 10G Ω across 1 μ F on 50V to 500V.

Discharge time to 1% is 0.1s per μ F on CAL position.

RECORDER OUTPUT


1V per decade $\pm 2\%$ with zero output at scale centre.

Maximum output ± 3 V. Output resistance 1k Ω .

type
TM14

£110

TRANSISTOR TESTER

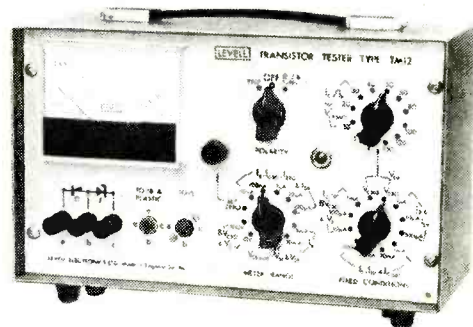

Tests bipolar transistors, diodes and zener diodes. Measures leakage down to 0.5 nA at 2V to 150V. Current gains are checked from 1 μ A to 100mA. Breakdown voltages up to 100V are measured at 10 μ A, 100 μ A and 1mA. Collector to emitter saturation voltage is measured at 1mA, 10mA, 30mA and 100mA for I_C/I_B ratios of 10, 20, 30. The instrument is powered by a 9V battery.

TRANSISTOR RANGES (PNP OR NPN)

I_{CBO} & I_{EBO} : 10nA, 100nA, 1 μ A, 10 μ A and 100 μ A f.s.d. acc. $\pm 2\%$ f.s.d. $\pm 1\%$ at voltages of 2V, 5V, 10V, 20V, 30V, 40V, 50V, 60V, 80V, 100V, 120V, and 150V acc. $\pm 3\%$ ± 100 mV up to 10 μ A with fall at 100 μ A $< 5\%$ +250mV.

BV_{CBO} : 10V or 100V f.s.d. acc. $\pm 2\%$ f.s.d. $\pm 1\%$ at currents of 10 μ A, 100 μ A and 1mA $\pm 20\%$.

I_B : 10nA, 100nA, 1 μ A ... 10mA f.s.d. acc. $\pm 2\%$ f.s.d. $\pm 1\%$ at fixed I_E of 1 μ A, 10 μ A, 100 μ A, 1mA, 10mA, 30mA, and 100mA acc. $\pm 1\%$.

h_{FE} : 3 inverse scales of 2000 to 100, 400 to 30 and 100 to 10 convert I_B into h_{FE} readings.

V_{BE} : 1V f.s.d. acc. ± 20 mV measured at conditions on h_{FE} test.

$V_{CE(sat)}$: 1V f.s.d. acc. ± 20 mV at collector currents of 1mA, 10mA, 30mA and 100mA with I_C/I_B selected at 10, 20 or 30 acc. $\pm 20\%$.

DIODE & ZENER DIODE RANGES

I_{DR} : As I_{EBO} transistor ranges.

V_Z : Breakdown ranges as BV_{CBO} for transistors.

V_{DF} : 1V f.s.d. acc. ± 20 mV at I_{DF} of 1 μ A, 10 μ A, 100 μ A, 1mA, 10mA, 30mA and 100mA.

See us at Leeds
Electronics Exhibition
28/30 June, 1977

type
TM12

£105

LEVELL ELECTRONICS LTD.

Moxon Street, High Barnet, Herts. EN5 5SD
Tel: 01-449 5028/440 8686

Prices are ex-works with batteries. Carriage and Packing extra. VAT extra in U.K. Optional extras are leather cases and mains power units. Send for data covering our range of portable instruments.



British Central
Electrical Ltd
Briticent House
172 Honeypot
Lane

Stanmore

Telephone:
01-204 9111
Branches at -
Slough 28616
Mitcham
01-640 9121
Cosham (07018)
83621
Yeovil 5596
Twickenham
01-894 7561
Chingford
01-529 3715



D.T.V. Group Ltd
126 Hamilton Road
West Norwood
London SE27
Telephone:
01-670 6166



Farnell
Electronics Ltd
Canal Road
Leeds LS12 2TU
Telephone: Leeds
(0532) 636311




Lock Distribution
Neville Street
Middleton Road
Oldham
Telephone:
061-652 6166



Spenco
Electronics
(Phoenix) Ltd
79 Carron Place
Kelvin Industrial
Estate
**East Kilbride,
Scotland**
Telephone:
East Kilbride
(03552) 36311

Your nearest phone will solve your encapsulant problems. Immediately.

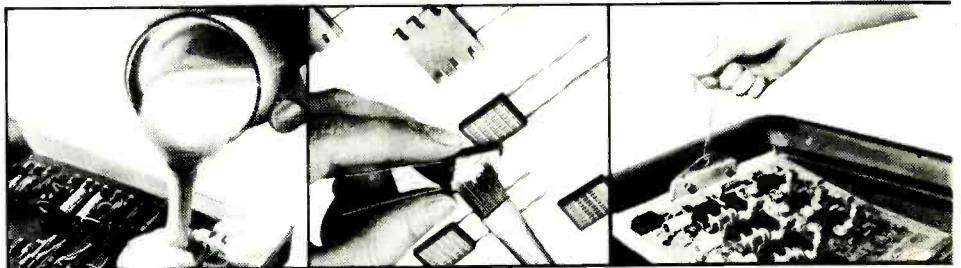Whatever your encapsulant, potting or sealant requirements, your local specialist Dow Corning distributor is able to supply you immediately. Wherever you are, there is a local Dow Corning silicone trained electrical/electronics product expert to help you.



DOW CORNING

DOW CORNING

Not a win on the pools, a trip to a Pacific paradise, or a reduction in income tax, but distortionless "current dumping".

Z's 1 to 4 are the four passive components which interconnect the current dumpers, (the output transistors which supply the power), to the small high quality amplifier which provides the error signal, so that when the above condition is met the current in the load, the loud-speaker, is independent of the current in the dumpers and hence distortion is solely dependent on the quality of the error amplifier, which because it is small can be very good.

Wonderful indeed.

For further details on current dumping and other Quad products write to Dept. WW
The Acoustical Manufacturing Co. Ltd., Huntingdon, Cambs., PE18 7DB Telephone (0480) 52561

"Something wonderful happens when $Z_1Z_3=Z_2Z_4$ "*



* Elektor Electronics Magazine No. 8, Dec. 1975

QUAD
for the closest approach to the original sound
for twenty-five years

QUAD is a Registered Trade Mark

WW-074 FOR FURTHER DETAILS



Overload the Avometer 73 and it'll cost you this much to repair it.

If you accidentally connect the mains to this multi-meter on any range for up to 10 seconds, it'll only cost you the price of a new fuse to repair it. Better than buying a new instrument. Better than the safety hazard of conventional fuse protection without the AVO fail-safe circuit. This improved overload protection is just one of the features which makes the Avometer Model 73 a must for electrical and electronics maintenance work of all descriptions.



Other features include: ■ Sensitivity of 20,000Ω/VDC
■ AC current included in a useful set of ranges
■ Tough, resilient case ■ Remarkably low cost.

Get in touch with us today for further details and order from your wholesaler or AVO Distributor.



Avometer Limited,
Archcliffe Road, Dover, Kent, CT17 9EN.
Telephone: (0304) 202620.

Thorn Measurement and Components Division

WW-078 FOR FURTHER DETAILS

Gardners

The Best of British

Where performance is paramount, professionals prefer Gardners...

We, at Gardners, have been in the communications business for many more years than we care to remember — so have our Audio Transformers. Used throughout the world by leading broadcasting and recording companies or wherever only the highest technical standards and levels of reliability are good enough our products are still preferred by professionals who know...

From microphone to tape (or film), speakers or headphones, studio consoles, manpacks, amplifiers, modems, we at Gardners have tried to anticipate your needs. Miniaturisation (yes!) plus good performance (yes!) through to exceptional performance (of course!). Impedance changing, coupling, isolation, bridging, low and high power, with or without D.C. Choose from our standard range of 95 models! Every one an example of sheer professionalism.

All have low loss, low distortion, low phase-shift, low pick-up, BUT wide frequency range.

Cat. No.	Impedance Input	Impedance Output (OHMS)	Turns Ratio Sec/Pri	Operating Level dBm at 50Hz	Frequency Response
MU 7501	0.3/15	100k	83/188.1	8	± 1 dB 50Hz-10kHz
MU 7503	0.200/600	100k	13/23.1		
MU 7514	600	600/2.4k	1.1/1.1		
MU 7518	10k CT	10k	1.1/1.1		
MU 7521	3.75/15	600 CT	6.32/12.64	16.5	± 0.5 dB 30Hz-20kHz (* ± 1dB at 20kHz)
MU 7522	3.75/15	100k*	82/164		
MU 7524	150/600	600 CT	1/2.1		
MU 7525	600 CT	300/1.2k	1.1/1.41		
MU 7530	10k CT	10k	1.1/1.1	12	± 0.5 dB 10Hz-100kHz
MU 7534	50/200	100k*	22.4/44.8		
MU 7566	600 CT	10k/2.5k	4.08/2.04		
MU 7567	600/150	50k	9.13/18.26		
MU 7582	200/50	600 CT	1.73/3.46	20	± 0.5 dB 10Hz-100kHz
VM 7461	15/3.75	600	6.35/12.7		
VM 7464	600/150	600	1/2.1		
VM 7466	600	10k/2.5k	4.14/2.07		
VM 7468	50/12.5	50k	32/64	4.75	± 1 dB 30Hz-22kHz

We would emphasise that the above is a representative selection only. Send for Brochure GT5 for complete listings. All units described are normally AVAILABLE FROM STOCK.

SPECIAL DESIGN SERVICE
If your requirements cannot be met by our standard range, then we will gladly design for your production needs.



Gardners


Gardners Transformers Ltd.
Christchurch Dorset BH23 3PN
Telephone 02015-2284
Telex 41276 Gardners XCH

Approved manufacturers of
electronic transformers, modular power supplies, inverters and
converters to Defence Standard 05-21

WW7/77

WW-011 FOR FURTHER DETAILS

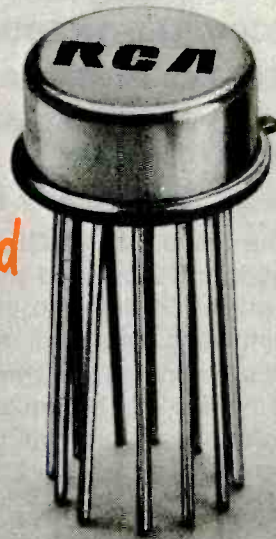“How can a range of op amps be more rugged, more reliable and cost less?”



“Pull up a chair and look at our table.”

RCA has combined the best of Bipolar and MOS to give BiMOS. Two technologies on one chip that means a greatly improved product performance – at no extra cost.

The table gives an indication of just what you can expect from a simplified range that covers virtually every application.

The BiMOS philosophy is in step with the trend towards standardising on fewer components that can do more jobs. It can help reduce costs all along the line – from design, manufacture and purchasing, to inventory control and incoming inspection.

Good news for those concerned about profitability today.

Whether you're a systems designer, an engineer or in management, BiMOS gives you something to think about. And act upon.

Op amp category	What BiMOS contributes	RCA device
General purpose	Wide applicability. Low cost	CA3160 CA3140 CA3130
FET Input	Lower device cost Reduced circuit cost	CA3160 CA3140 CA3130
Wideband 4.5 to 70 MHz	High slew rate with low ringing	CA3160 CA3140 CA3130 CA3100
Micropower down to 1.5 mW	Strobability.	CA3160 CA3130
High output current up to 22 mA	Eliminates driver stage. Low device cost. Rail-to-rail output swing.	CA3160 CA3130


The BiMOS op amp range. Proof that two technologies are better than one.



380 Bath Road, Slough, Berks. SL1 6JE. Tel: Burnham (06286) 64051. Telex: 847573.
A Crellon Company



HIGH POWER DC-COUPLED AMPLIFIER

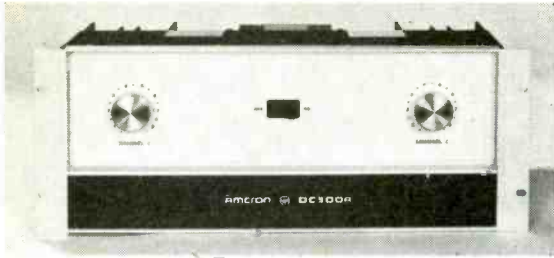

- ★ UP TO 500 WATTS RMS FROM ONE CHANNEL
- ★ DC-COUPLED THROUGHOUT
- ★ OPERATES INTO LOADS AS LOW AS 1 OHM
- ★ FULLY PROTECTED AGAINST SHORT CCT, MISMATCH, ETC.
- ★ 3 YEAR WARRANTY ON PARTS AND LABOUR

The DC300A Power Amplifier is the successor to the world famous DC300 which is so widely used in Industrial, and Research applications in this country. It is DC-coupled throughout so providing a power bandwidth from DC to over 20,000Hz. The ability of the DC300A to operate without fuss into totally reactive loads while delivering its full power, and maintaining its faithful reproduction of Pulse or complex waveforms has established the DC300A as the world's leading power amplifier. Each of the two channels will operate into loads as low as 1 ohm, and the amplifier can be rapidly connected as a single ended amplifier providing over 650 watts RMS into a 4 ohms load, and still providing a bandwidth down to DC. Below is a brief specification of the DC300A, but if you require a data sheet, or a demonstration of this fine equipment please let us know.

Power Bandwidth	DC-20kHz @ 150 watts + 1db - 0db.	Slewing Rate	8 volts per microsecond
Power at clip point (1 chan)	500 watts rms into 2.5 ohms	Load impedance	1 ohm to infinity
Phase Response	+0. -15 DC to 20kHz. 1 watt 8Ω	Input sensitivity	1.75 V for 150 watts into 8Ω
Harmonic Distortion	Below 0.05% DC to 20kHz	Input Impedance	10K ohms to 100K ohms
Intermod. Distortion	Below 0.05% 0.01 watt to 150 watts	Protection	Short, mismatch & open cct. protection
Damping Factor	Greater than 200 DC to 1kHz at 8Ω	Power supply	120-256V. 50-400Hz
Hum & Noise (20-20kHz)	At least 110db below 150 watts	Dimensions	19" Rackmount. 7" High. 9 3/4" Deep
Other models in the range: D60 — 60 watts per channel		D150A — 150 watts per channel	

Other models available from 100 watts to 3000 watts



MACINNES LABORATORIES LTD.

MacInnes House, Carlton Park Industrial Estate
Saxmundham, Suffolk IP17 2NL. Tel: (0728) 2262 2615

MACINNES FRANCE

18 Rue Botzaris
Paris 75019, France
Tel: 206-60-80 or 206-83-61

WW-032 FOR FURTHER DETAILS

The International Microphone



For over 40 years Beyer Dynamic microphones and headphones have served the needs of professional 'Sound Men' throughout the world.

The M500 (Illustrated) is only one of a range of microphones now serving thousands of users who still demand high quality performance and reliability. Brochure showing the full range of microphones, headphones and accessories available on request.

BEYER DYNAMIC

BEYER DYNAMIC (GB) LTD

1 Clair Road, Haywards Heath, Sussex. Tel: 51003


WW-043 FOR FURTHER DETAILS

MAPLIN



ELECTRONIC ORGAN

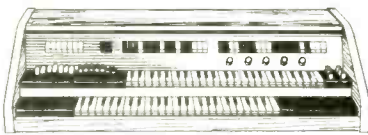The only organ you can build in stages and tailor to your requirements as you go along — and at each stage you'll have a fully working instrument! We haven't got the gimmicks yet — they're coming soon! — but we have got the most beautiful sounds — you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



GRAPHIC EQUALISER



This high quality Graphic Equaliser will enhance even the most sophisticated system at a fraction of the cost of a ready-made equaliser of equal quality. You can get all the parts from us except woodwork including drilled and printed metalwork. Construction details in our leaflet 15p.



TOOLS




We stock an excellent range of tools especially for the electronics enthusiast. From miniature wiring tools to multimeters including soldering irons and desoldering tools, screwdrivers, cutters, pliers, strippers, miniature electric drills for p.c.b.'s, transistor tester, etc. Full details on catalogue pages 167 to 176.

PEDAL UNIT






A completely self-contained pedal unit 13 note 2-octave range 4 organ stops. It can be added to any organ! A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist! Full construction details in our catalogue — post the coupon below now!

T.V. GAME

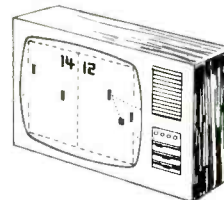

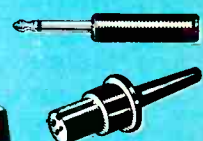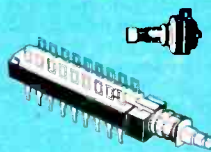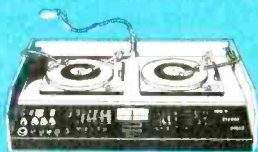Play fascinating games NOW on your own tv in your own living room. The kids will think it's magic when the scores pop up on the screen. Lay your bets — anyone could win — with Maplin's prices everyone can win. Complete kit to play four games only £24.50. Add 35p for copy of construction details. See our June newsletter for details of rifle kit.



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices — our latest special offers (they save you pounds) — details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 47379

IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations!

Over 30 pages of complete projects to build!

Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!

DON'T MISS OUT! SEND 60p NOW!

POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue by return of post. I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME _____

ADDRESS _____

WW7




Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 3/4" x 8 1/4" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design of Digital Systems.

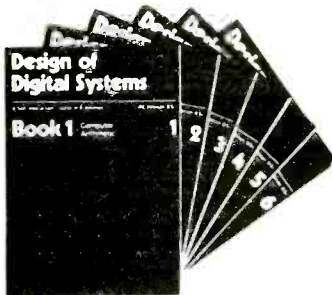

£6.20

plus 80p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request

VAT zero rated

Also available — a more elementary course assuming no prior knowledge except simple arithmetic.
Digital Computer Logic and Electronics.

In 4 volumes:

£4.20

plus 80p P. & P

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

Offer Order both courses for the bargain price £9.70, plus 80p P. & P.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To Cambridge Learning Enterprises, Dept. COM, FREEPOST Rivermill House, St. Ives, Huntingdon, Cambs, PE17 4RR
*Please send me . . . set(s) of Design of Digital Systems at £7.00 each p & p included

*or . . . set(s) of Digital Computer Logic and Electronics at £5.00 each, p & p included

or . . . combined set(s) at £10.50 each, p & p included

Name

Address

*delete as applicable

No need to use a stamp — just print FREEPOST on the envelope

WW7



UP
UP
AND
AWAY!

Look up to a Versatower installation and your radio communications will achieve new heights!

Acclaimed as the World's leading telescopic tilt-over tower in the international field of radio communication.

A complete range of models: from 20 to 120 feet, static and mobile.

Full details and specifications are in our brochure.

Send for it today!

Strumech Engineering Limited,
Portland House, Coppice Side,
Brownhills, Walsall,
West Midlands WS8 7EX.
Telephone: Brownhills 4321

Due to the enormously increased demand for Versatower systems we have now opened our new West Works. Phone us — we'll be glad to show you around.

STRUMECH
VERSATOWER
SYSTEM



WW-027 FOR FURTHER DETAILS

Litesold TC 50 Thermostatic Iron



- Built-in thermostat
- Adjustable with special key
- Close drift-free control
- Mains or 24 volts

Details from
LIGHT SOLDERING DEVELOPMENTS LIMITED
 97-99 Gloucester Road, Croydon, Surrey.
 Tel: 01-689 0574 Telex: 8811945

WW — 073 FOR FURTHER DETAILS

BIMBOARD

Stop Ruining Your I.C.'s And Wasting Time Soldering
 Plug Into The Revolutionary New

BIMBOARD


The Only Professional Quality Breadboard That
 Accepts All DIL Packages With 6 To 40 Pins

Incorporates Bus Strips For Vcc And Ground

Includes A Component Support Bracket

Has Over 500 Individual Sockets

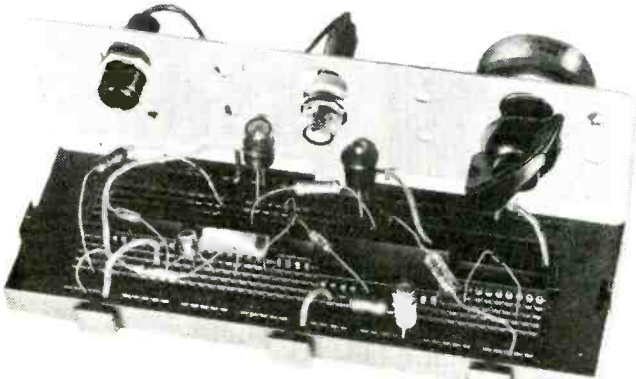And Allows You To Use And Re-Use
 IC's, Transistors, LED's, 7 Segment Displays,
 Diodes, Resistors, Capacitors



Only £9.72 (cheque with order) Including VAT and P.P.
 Special Quantity Discounts Available For
 Radio Clubs, Retail Outlets, Distributors

BOSS INDUSTRIAL MOULDINGS LTD

Higgs Industrial Estate, 2 Herne Hill Road, London, SE24 0AU, England
 Telephone 01-737 2383 Tele* 919693



Shure fries 'em

Shure Safety Communications Micro-
 phones are tested for level and response
 at a searing 69.4° ... often up to an incredi-
 ble 85° C. for day-long periods and even
 though the inside parts are too hot to touch

...They work

WW-059 FOR FURTHER DETAILS

The potentiometer with greater potential

The new DC Potentiometer Model T7100 is, without doubt, an exceptional piece of laboratory equipment. What makes it so, is its high accuracy over its six decades of measurement available at the same time. Dial 1 offers an accuracy of $\pm(0.001\% + 0.1 \mu\text{V})$; Dial 2 $\pm(0.001\% + 0.1 \mu\text{V})$ and Dials 3-6 $\pm 0.1 \mu\text{V}$.

This 'triple pot' offers not only exceptional long term accuracy and stability, but also a built-in self calibration check. Added to this, wound components have been replaced by resistors printed on a heat sink substrate—so there is virtually no source of drift, or thermal emfs.

The T7100 is as good as it looks. It's worth finding out more about. Get in touch with us today for the full facts.




Sullivan

H.W. Sullivan Limited,
Archcliffe Road, Dover, Kent, CT17 9EN
Tel: 0304 202620 Telex: 96283

THORN Measurement Control and Automation Division

WW — 070 FOR FURTHER DETAILS

ELECTRONIC INDUSTRIAL THERMOMETER

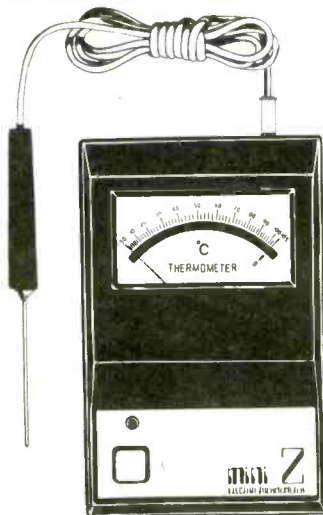

THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied with carrying case, Probe and internal 1½ volt standard size battery.


Model "Mini-Z 1" measures from -40°C to $+70^{\circ}\text{C}$. Price £25.00
Model "Mini-Z 2" measures from -5°C to $+105^{\circ}\text{C}$ Price £25.00
Model "Mini-Z Hi" measures from $+100^{\circ}\text{C}$ to $+500^{\circ}\text{C}$ £27.50
(VAT 8% EXTRA)

Write for further details to

HARRIS ELECTRONICS (LONDON)
138 GRAY'S INN ROAD, LONDON, WC1X 8AX
(Phone 01-837 7937)

WW—010 FOR FURTHER DETAILS

Keep your tools handy in case...

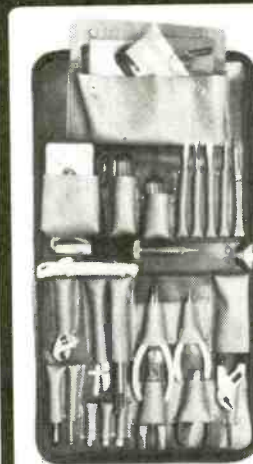

With JENSEN

special quality industrial tool kits and cases

Send now for details of the superb Jensen range of tools, meters and accessory equipment, all in the most handy and robust cases — also available separately. Jensen products are specifically designed for industrial use, perfect for all engineers, technicians, electricians, instrument repairmen etc. Choice of more than twenty kits and cases.

Write for free Jensen catalogue to:

SPECIAL PRODUCTS DISTRIBUTORS LTD,
81 Piccadilly, London W1V 0HL. Tel: 01-629 9556. Cables: Speciproduct London W1.

WW—053 FOR FURTHER DETAILS



*Illustration actual size

ORYX SUPER 30

The feature packed general purpose iron built to professional standards for only £2.95 + (8%vat)

When we introduced the Super 30 last year it was the best general purpose soldering iron at its price in Britain—it still is, at only £2.95p. (plus 8% VAT)


The ORYX Super 30 offers you all these features as standard: Neon safety light, Long life element, Iron coated screw-on tip, Stainless steel shaft, Styled handle, Two minute element change and a stainless steel clip-on hook.

Industrial Distributors include:
Electroplan Ltd., Orchard Road, Royston, Herts SG8 5HH
GDS (Sales) Ltd., 380 Bath Road, Slough, Berks SL1 6JE
ITT Electronic Services, Edinburgh Way, Harlow, Essex CM20 2DF

Greenwood Electronics

Greenwood Electronics, Portman Road, Reading, RG3 1NE
Telephone: 0734 595844, Telex 818659

WW—012 FOR FURTHER DETAILS

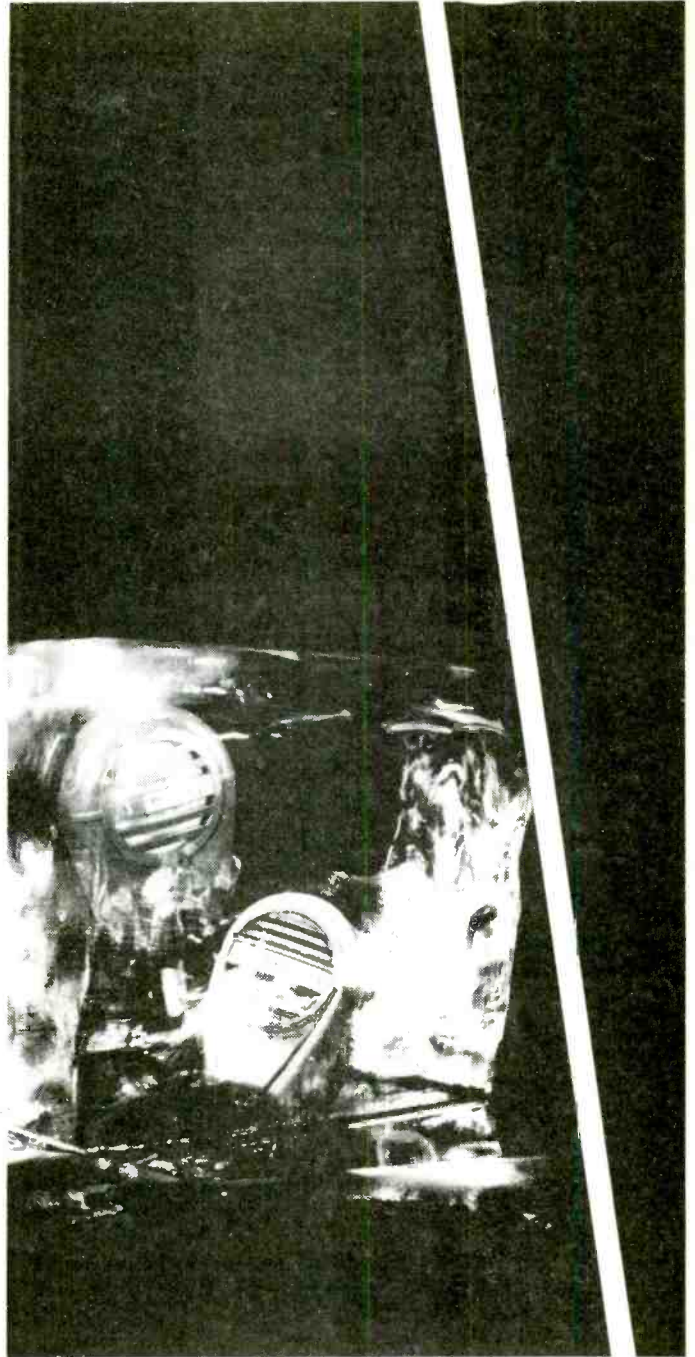


Shure freezes 'em

Shure Safety Communications Microphones are plunged to an appalling -45.6° C. for 1/2 hour periods during severe temperature tests, and even though they're covered with frost

...They work

WW-060 FOR FURTHER DETAILS

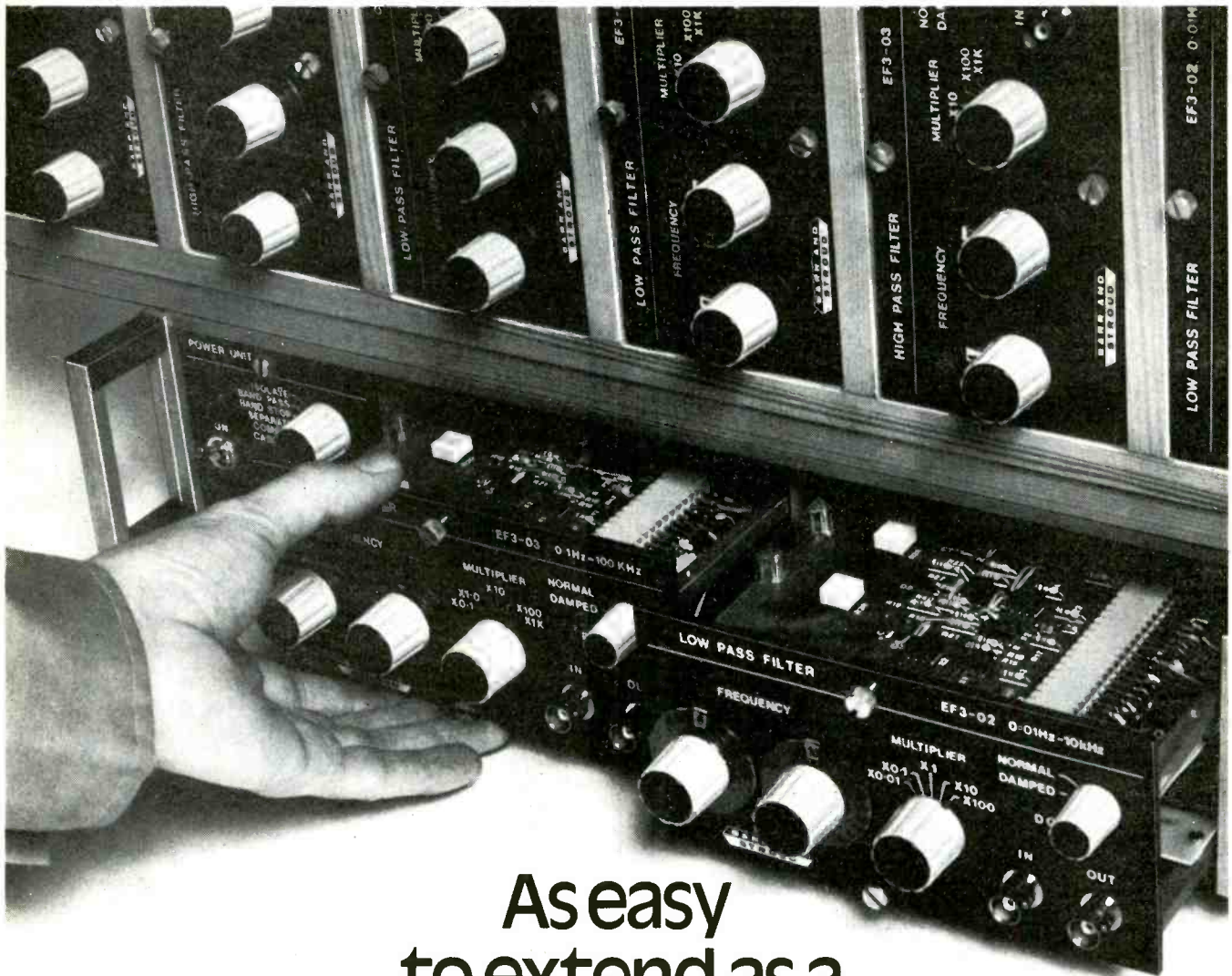

As easy to extend as a cassette library... EF3 Modular Filtering System from Barr & Stroud

When dealing with a variety of projects, electronic filtering requirements change rapidly and need to be met with minimum fuss and maximum flexibility. The Barr & Stroud EF3 Modular Filtering System is designed around the most compact of basic main frames containing the power unit and function switching with capacity for two slide-in filter units. The modular concept allows you to begin with the minimum of a mainframe and one filter unit. Thereafter you can extend your 'library' of filter capability as requirements dictate and budgets make possible.

The EF3 is a system that grows with every plug-in module and constantly expands as new modules are developed and introduced. Current modules give a pass band capability from d.c. to 10MHz and within this spectrum filter units can be operated individually or in a combination to give low-pass, high-pass, band-stop, band-separate or band-combine modes.

The EF3 system is a part of the comprehensive Barr & Stroud range of electronic filters that could well meet all your filtering requirements. If not,

Barr & Stroud welcome the opportunity to study your problem and come up with a custom-built solution. The full spectrum of Barr & Stroud capability in electronic filtering is covered in a range of literature available on request.


**BARR AND
STROUD**

Glasgow and London

BARR & STROUD LIMITED
London Office:
1 Pall Mall East, London SW1 5AU
Telephone: 01-930 1541
Telex: 261877

Cut costs by 50% with the same high performance.

Isn't that what new ideas are all about?

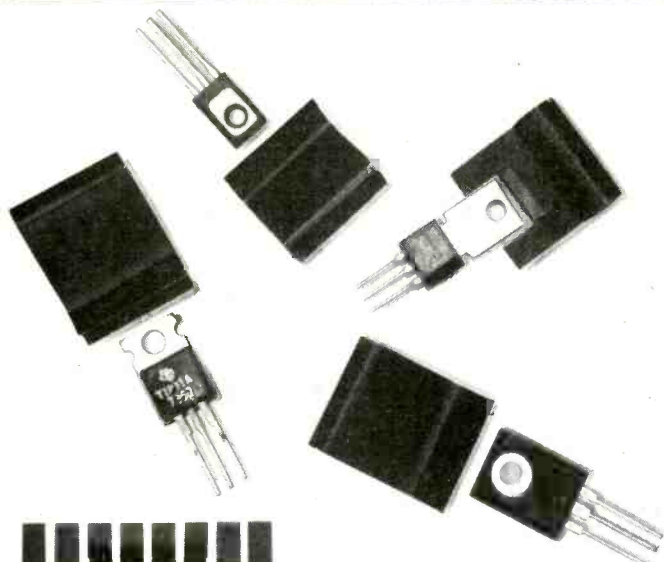

Light in weight and low in cost, new Thermalloy heat sinks are designed specifically for plastic or metal case power devices.

They are remarkably simple to use, no extra mounting hardware is required—and they can be attached to the device after board assembly.

The slip on types have positive retention and can be supplied with locking tabs.

For full details of the range, simply return the coupon—cutting costs without cutting performance is a good idea you ought to know about.



Thermalloy

MCP Electronics Ltd. Alperton, Wembley, Middlesex
Tel: 01-902 5941.



Please send me full details on Thermalloy heat sinks.

Name _____

Company _____

Address _____

Tel: _____

WW 7/77



...They work


SHURE[®] communications microphones

Look for the name Shure moulded into the back of the case of every microphone you buy. It identifies the microphones that have undergone the most rigid and demanding tests in the industry. And, it's your peace-of-mind assurance of reliability, know-how, quality, quality-control, and conscientious fast service!

Shure Electronics Limited
Eccleston Road, Maidstone ME15 6AU
Telephone: Maidstone (0622) 59881

WW-061 FOR FURTHER DETAILS

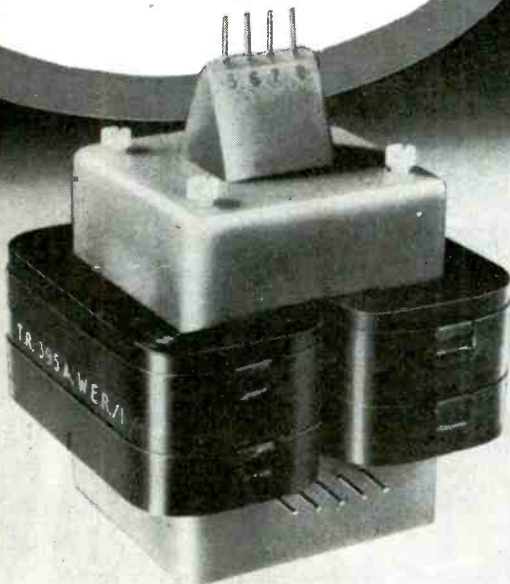*"They want **safety isolation** for their voice band circuits"*



One more request item. We met it with a neat little transformer. Now, in two versions, it joins the list of useful Whiteley products, and everyone involved in communications system design will be interested in the protection they provide. Inserted in voice band circuits, they effectively isolate equipment from the hazards of adjacent high voltage power circuits on the 'line' side. High isolation level between line and equipment windings gives protection against voltage surges, lightning strikes and fault conditions. One version is designed for 17Hz signalling circuits, the other with several voltage ratios also suits a 50Hz ringing circuit. All are Post Office and C.E.G.B. approved, and the second version is also approved with extra protection diodes added. Requests for data sheets welcome. Or if you want to request a product spec of your own - we're always interested!


Surprising how often you'll find

**Whiteley
make it.**

Whiteley Electrical Radio Co. Ltd
Mansfield, Notts NG18 5RW, England. Tel: 0623 24762.

WW-052 FOR FURTHER DETAILS

METER PROBLEMS?

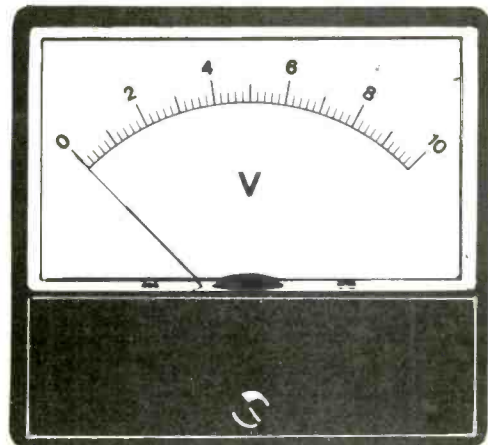

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW-009 FOR FURTHER DETAILS

Contractors to H.M. Govt. P.O.

REPAIRS OF ELECTRICAL MEASURING INSTRUMENTS 7-14 DAYS SERVICE

◀ MODEL 8 MK.V



STOCKISTS
ALSO SUPPLIERS OF GEC
RISSO AND OTHER
MULTI-RANGE TEST SETS

WE SPECIALISE IN ASSEMBLIES, AND IN THE
REPAIR, CALIBRATION AND CONVERSION
OF ALL TYPES OF INSTRUMENTS, INDUSTRIAL
AND PRECISION GRADE

LEDON INSTRUMENTS LTD.

**GLADSTONE WORKS, GLADSTONE RD,
FOLKESTONE, KENT.
TEL: (STD) 0303 57555**

WW-023 FOR FURTHER DETAILS

IMO relays. You shouldn't pay more.

Although at IMO we have a fine range of relays which suit many needs, we'd be the first to say there are some applications that would be better off with Omron relays.


True, *some* Omron relays are more expensive than the IMO equivalents, but understandably so. Because they're designed to be used in specifications where a *critically*

higher standard of reliability is vital.

So, now the finest timers and relays are under the same roof. Not to mention the same consistent, reliable and helpful IMO service.

IMO and Omron; a combined range that covers just about every need in every price bracket. Why settle for less?

Omron relays. You shouldn't pay less.

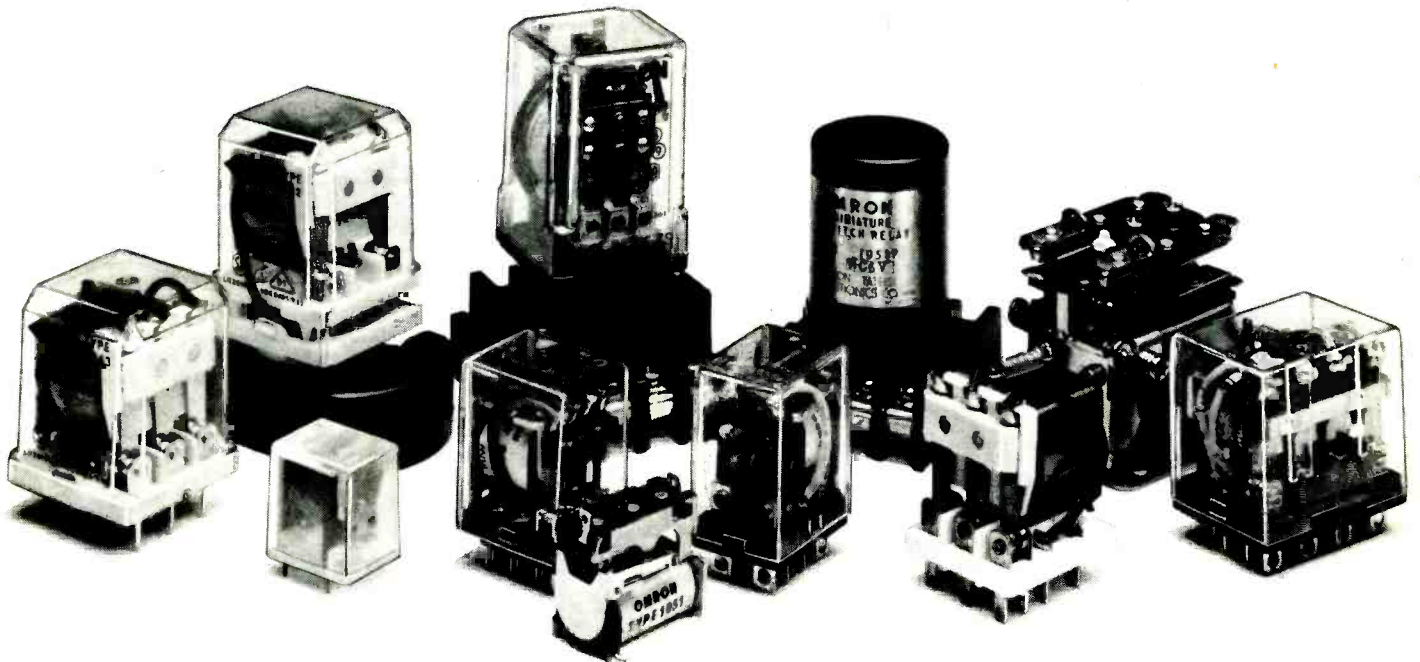

IMO. Now most people know

To: IMO Precision Controls Ltd.
349 Edgware Road, London W2 1BS. Tel: 01-723 2231.

WW 7/77

Please send me full details on IMO and Omron relays.

Name _____

Position _____

Company _____

Address _____

Tel. _____


PLASTIC FASTENERS FOR ELECTRONICS




SELF-ADHESIVE CABLE CLIPS are a quick and simple means of securing cables, cords and small looms to flat surfaces. No drilling or fixing screws necessary. The peel-off backing is removed immediately before placing the clip. The coating adheres to most clean, flat surfaces and withstands a wide range of humidity and temperature. Cable clips are moulded in natural nylon and have rounded edges to prevent damage to the cables.



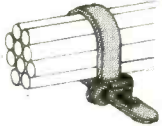
CABLE STRAPS are semi-permanent fasteners for strapping wires and cables into tight, compact looms. The ratchet fastener is adjustable and can be released by pinching-in the sides of the fastener head. Cable straps are made from black nylon.



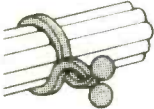WIRE TIES are a flexible means of fastening wires and small cables into orderly, compact looms. They are quick and easy to fit and can be re-used, greatly reducing re-loomng times. Wire ties are made from nylon and are available in various sizes each determined by a different colour.



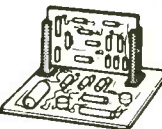
The **P.C. BOARD GUIDE** is a self-retaining edge support for printed circuit boards. It has good panel retention and grips p.c. boards firmly and securely. The guide is available in two types of material - yellow acetal or grey Noryl, for high temperature and voltage applications.




P.C. BOARD SPACERS are simple to fit, one-piece mouldings for use with p.c. boards. They have a self retaining shank for fastening into panels and a T-shaped anchor for securing p.c. boards of 0.062" thickness. They have good resistance to vibration and are suitable for board-to-board or board-to-chassis use.



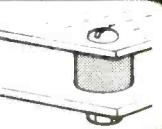
P.C. BOARD STAND-OFFS are quickly assembled, self-retaining panel supports for p.c. boards. Made from natural (off white) nylon and have good resistance to vibration. Suitable for panels up to 0.079" thickness. Stand-Offs accept a No. 4 self-tapping screw.



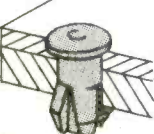PLASTIC RIVETS fasten panels, fittings and name plates to metal plastic and wood. Resilient enough to fix into brittle materials like fibreglass, hardboard and glass. Shank, head and pin are one piece. Fixing is by driving the pin through the head into the space between the legs, gripping the work.



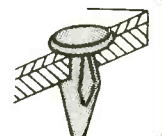DRIVE FASTENERS hold two or more panels together. Easily fixed, normally by thumb pressure. No special tools required. Boat-shaped **DRIVE** Fasteners are for panels of thin and medium thickness and are removable. Ribbed **DRIVE** Fasteners are used in blind holes where hole length exceeds length of shank.



PLASTIC HOLE PLUGS are quick, inexpensive means of plugging unwanted holes. Hole Plugs keep out dust, dirt and moisture. Attractively shaped heads give a neat finish. The snap action grip of the Hole Plug makes a vibration resistant seal. Hole Plugs are made from nylon and are non-corrosive.



LOKUT ANCHORS are used to strengthen holes by providing additional screw thread engagement in materials where self-tapping screws would be unsatisfactory. Made from high strength nylon and used in insulation, and electrical chassis work. Easily fitted by hand.



1000's OF OTHER TYPES OF PLASTIC AND METAL FASTENERS
LEAFLETS ON REQUEST

HARMSWORTH

HARMSWORTH, TOWNLEY & CO. LTD.
HAREHILL TODMORDEN LANCS OL14 5JY
Phone TODMORDEN 2601 (STD 070-681 2601)

WW-036 FOR FURTHER DETAILS

The Quickest, Simplest Way of Punching Holes in Sheet Metal

Q-Max punches make clean, accurate holes every time. In no time. With no filing, no jagged edges, virtually no burrs - with no hard work. And no holes are barred. Round or square, Q-Max punches are available in sizes down to 10mm up to 75mm for use on sheet metal up to 16 gauge. No wonder they're used by all government services (Atomic, Military, Naval, Air, GPO, Ministry of Works) and all over the world by radio, motor and industrial manufacturers, plumbing and sheet metal trades and garages.

57
metric
and linear
sizes



Q-MAX

SHEET METAL PUNCHES

Wholesale and Export enquiries welcomed. Further details from,

"Q-MAX" (ELECTRONICS) LTD
44 PENTON STREET - LONDON N1 9QA Tel: 01-278 2500

WW-007 FOR FURTHER DETAILS

FREQUENCY COUNTERS

1/10 Hz to 1.2GHz

High performance instruments measuring frequency, period, time, freq./ratio and calibrated output facility. Fast delivery. Specials by arrangement.



TYPE 801B

CRYSTAL OVEN
OPERATING MANUAL
TWO TONE BLUE CASE

£274 250 MHz

Sensitivity 10mV. Stability 5 parts 10.¹⁰

Resolution ± 1 Count

301M	32MHz 5 Digit £95	401A	32MHz 6 Digit £132
501	32MHz 8 Digit £188	701A	80MHz 8 Digit £205
801B/M	250MHz 8 Digit £274	901M	520MHz 8 Digit £375
		1001M	1.2GHz 8 Digit £670

Start/Stop versions plus £15

Memory versions available if not suffixed M £25 extra

Type 101 1MHz 100KHz 10 KHz Crystal Standard £95
Type 103 Off/Air Standard £95

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Depts., Crystal Manufacturers and Electronic Laboratories world-wide

RCS

R.C.S. ELECTRONICS

6 WOLSEY ROAD, ASHFORD
MIDDX. TW15 2RB

Telephone: Ashford (Code 69)
53661/2

WW-028 FOR FURTHER DETAILS

Eddystone VHF/UHF antennae

VHF Sleeve Dipoles

Available in versions from 100MHz to 500MHz for general mast or tower mounting (Cat. 1530) and as special marine version covering 156–165MHz (Cat. 992).

Strong, weatherproof, potted construction of Fibreglass sealed with epoxy resin. Cat. 1530 aeriels are slide fit inside standard scaffolding mast, but sherardised mild steel mounting brackets can be provided (standard for Cat. 992 marine dipole).

Bandwidth \approx 5% of centre frequency. Gain is unity over half-wave dipole, 3dB over isotropic. Impedance 50 Ω or 75 Ω .

Heavy Duty Folded Centre Fed Dipoles


Cat. 1531 available for frequencies 50MHz to 220MHz. Most standard radiotelephone bands can be covered with wide bandwidth and good VSWR characteristics. Gain is unity over dipole, 3dB over isotropic. Impedance 50 Ω . Very rugged construction of anodised aluminium alloy with low density polythene insulator. Boom and brackets supplied. Marine version available in stainless steel.

Eddiscone Omnidirectional Antennae

Ideal for applications requiring well-defined gain, VSWR and bandwidth characteristics.

Four main versions cover range 27MHz to 870MHz with 75 Ω or 50 Ω impedance, and special versions can be provided if required. Gain is unity \approx 1dB compared with a half-wave dipole.

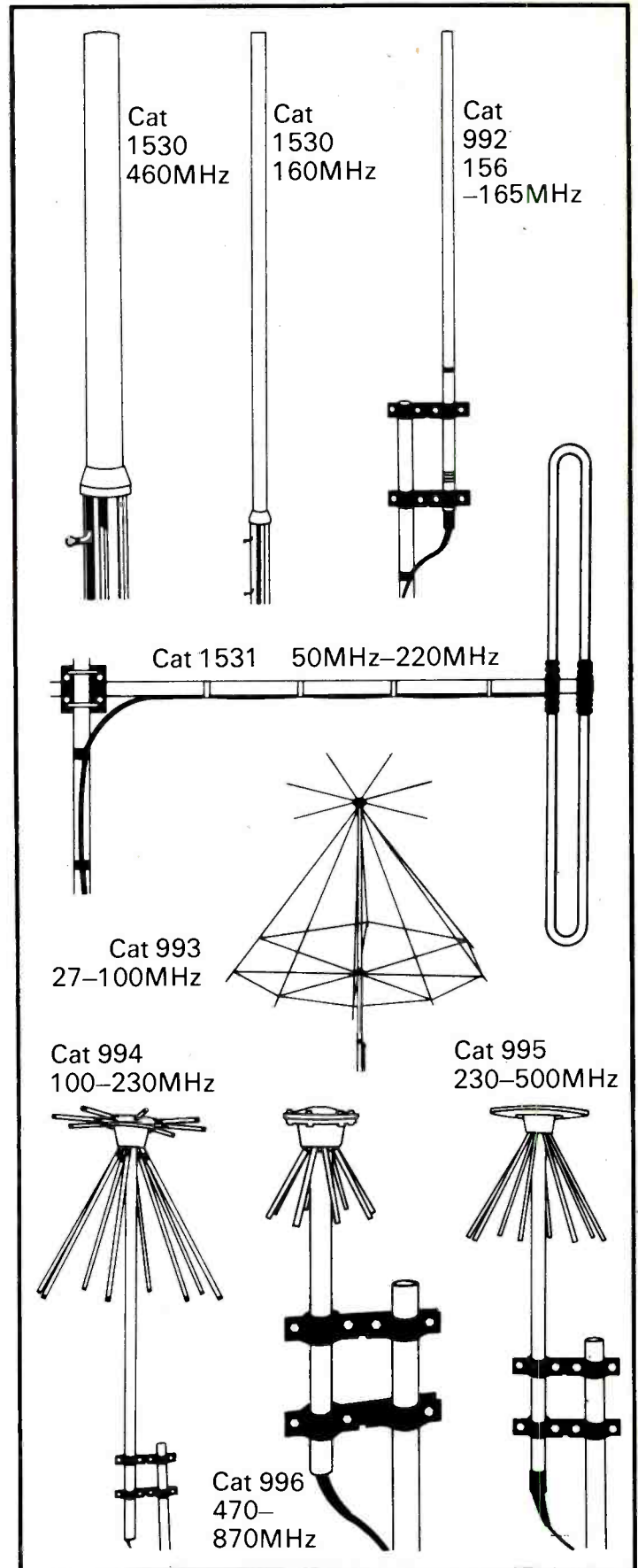Rugged construction of anodised aluminium with epoxy resin sealing. All versions supplied with brackets for mounting on masts of 1 $\frac{1}{2}$ " to 2 $\frac{1}{2}$ " diameter.



PLEASE WRITE FOR FULL DETAILS

Eddystone Radio Limited

Member of Marconi Communication Systems Limited


Alvechurch Road, Birmingham B31 3PP, England

Telephone: 021-475 2231 Telex: 337081

A GEC-Marconi Electronics Company



The detectors

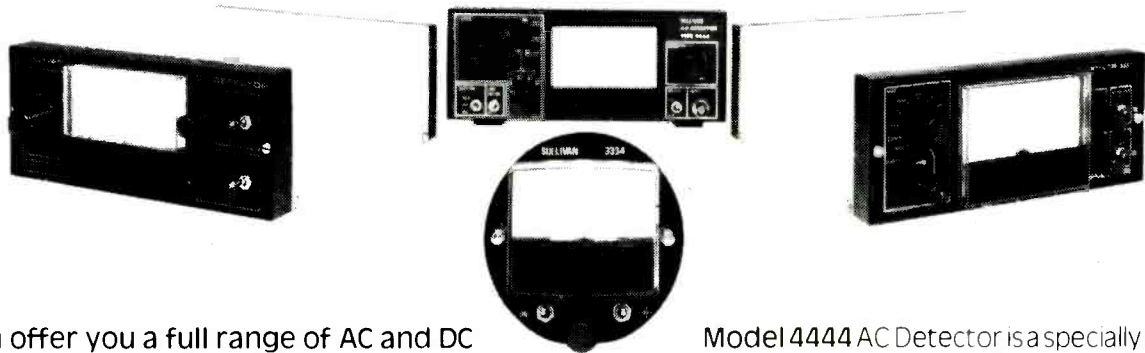

Sullivan offer you a full range of AC and DC Null Detectors. There is a wide span of ranges available, with battery operation, portability and high quality being common to all.

NEW Model 3336 DC Detector is a versatile production and laboratory instrument offering discrimination of $1\mu\text{V}$ in $10\text{k}\Omega$ and sensitivity of $10\mu\text{V}$. This instrument offers low zero drift, linear or logarithmic response and high stability.

NEW Model 3337 Microvolt Detector has 9 centre zero ranges from 10V to $1\mu\text{V}$. It has a resolution of $0.1\mu\text{V}$ into $10\text{k}\Omega$. Battery operation eliminates mains voltage interference. There are many other features, too, not least of which is a surprisingly competitive price

Model 4444 AC Detector is a specially designed, battery operated solid state AC detector for the detection of very low level imbalance signals from modern AC bridge and potentiometric measuring systems.

Model 3334 DC Null Detector is a compact unit specially designed for null point measurement. It is small in size, low cost and rugged and these are just three of the features that make it ideal when replacing pot galvanometers in potentiometers and bridges. For fuller facts about Sullivan Detectors, simply contact:

Sullivan

H. W. Sullivan Limited, Archcliffe Road,
Dover, Kent CT17 9EN
Tel: 0304 202620 Telex: 96283


Thorn Measurement and Components Division

WW — 071 FOR FURTHER DETAILS

FAST RESPONSE STRIP CHART RECORDERS

Made in USSR

Series H3020

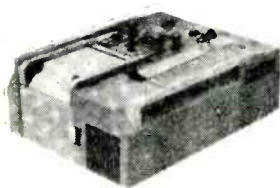


Basic error: 2.5%
Sensitivity: 8mA F.S.D.
Response: 0.2 sec.
Width of each channel:
Single and three-pen
recorders: 80mm
Five-pen recorders: 50mm

Chart speeds, selected by push buttons: 0.1-0.2-0.5-1-0.2-5-5.0-12.5-25 mm/sec.
Chart drive: 200-250V 50Hz
Recording: Syphon pen directly attached to moving coil frames
Curvilinear co-ordinates.
Equipment: Marker pen, timer pen, paper footage indicator, 10 rolls of paper, connectors, etc.

H3020-1 (Single pen): 285mm wide x 384mm deep x 165mm high
PRICE £108.00
H3020-3 (Three pen): 475mm wide x 384mm deep x 165mm high
PRICE £160.00
H3020-5 (Five pen): 475mm wide x 384mm deep x 185mm high
PRICE £295.00

Series H327

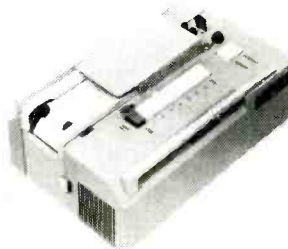

Polarized moving iron movements with syphon pens directly attached. Built-in solid state amplifier (one per channel) provides 8 calibrated sensitivity steps. Two marker pens are provided.
Basic error 4% Frequency response from DC to 100Hz 2dB.

Sensitivity: 0.02 - 0.05 - 0.1 - 0.2 - 0.5 - 1 - 2 - 5 volts/cm
Width of each recording channel: 40mm
Chart drive: 220-250V 50Hz
Chart speeds: 1-2-5-10-50-125-250mm/sec

Type H3271-1. Single pen: Dimensions 259 x 384 x 165mm
Weight 15 kilos **PRICE £265.00**
Type H327-3. Three pen: Dimensions 335 x 384 x 165mm
Weight 20 kilos **PRICE £520.00**
Type H327-5. Five pen. Dimensions 425 x 385 x 165mm
Weight 25 kilos **PRICE £770.00**

Note: Prices are exclusive of VAT

Available for immediate delivery

Z & I AERO SERVICES LTD.

44A WESTBOURNE GROVE, LONDON W2 5SF

Tel. 01-727 5641

Telex: 261306

WW — 083 FOR FURTHER DETAILS

F.M. TUNERS, MODULES & KITS by

Icon Design



	Tuner	Kit
T1 PUSH-BUTTON VERSION	£110.00	£98.47
T2 TOUCH TUNED	£115.00	£101.31
T3 DIGITAL (AS SHOWN)	£139.00	£132.14

This tuner must surely provide the best value for money available today. Combining the best of the modules shown below, it includes a full digital readout of frequency to a resolution of 0.1 MHz, so that exact station identification can be made. In addition, six pre-set stations may be selected by touch controls having internal solid state lamps, while manual tuning allows easy searching for distant stations under the guidance of the digital meter.

A switchable mute system allows reception of the weakest stations while muting inter-station noise and spurious responses. Perfect reception is assured by not permitting any station to be heard which is far enough out of tune to cause distortion. The tuning indicator lamp provides a means of very fine tuning, and is automatically extinguished between stations.


A powerful A.F.C. system is also incorporated which holds all stations in tune, while not preventing manual tuning.

Good stereo reception is assured by the use of a phase locked decoder with full 'birdie' and spurious output filtering.


Finally, but not least, the external appearance and styling bring a fresh new look to Hi-Fi. The sturdy wooden cabinet is finished in mat teak veneer, housing an attractive gold and brown, anodised aluminium front panel, which carries black controls and inscriptions. The indicator lamps and digital displays are in red, giving the finishing touches to a tuner you will be proud to own.

MAIN RECEIVER MODULE M1

We have claimed before that this F.M. system is the most advanced on the market, and after nearly three years we repeat our claim. Some have borrowed ideas, some have not, but no other tuner gives you all the features of this unit. How many tuners mute the spurious tuning effects found at either side of a correctly tuned station? How many tuners fade the sound out as you tune too far off station for good quality sound? How many tuners kill the tuning indicator so that it does not indicate when there is no station there? How many offer you drift free tuning? We could go on. If you want a tuner that has been well thought out and engineered, start with this module.

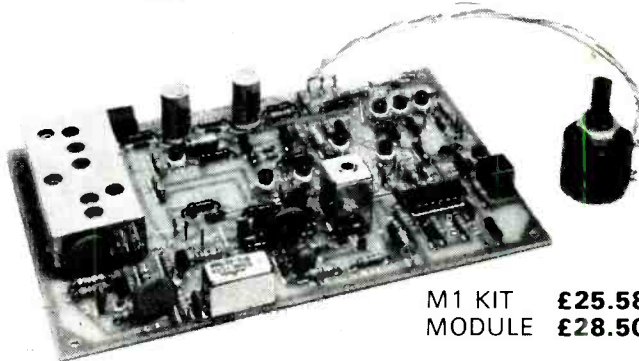

M1 KIT **£25.58**
MODULE **£28.50**

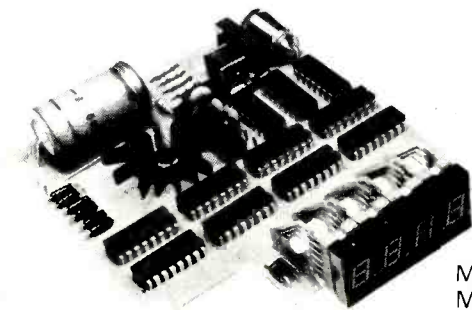


M6
MODULE ONLY
£44.40

DIGITAL FREQUENCY METER M6

We are very proud of this one. We don't have to say it's the best, as far as we know it's the only one! On a board less than 4" square is all the electronics of a stable counter with i.f. offset (added) and a stabilized power supply! With the aid of a small daughter board (not shown) which fits neatly into the above module (M1), the exact station frequency is displayed to the nearest 0.1 MHz. It's a tuning scale 20" long with accurate calibrations every 0.1"! You get the transformer, daughter board (ready wired in), polarized filter, and a list of station frequencies. What more do you want?

TOUCH TUNE MODULE M5

This module must put the finishing touches to an outstanding combination. Six pre-set stations at the touch of a button. No moving parts to go wrong, or contacts to get dirty. Internal illumination shows you which button has been touched, while the tuning adjustment is made using high reliability multi-turn cermet pots for repeatable selection of the most used stations, yet retaining the use of separate manual tuning. This module interfaces directly with the M1 above, being wired between the board and the normal manual tuning control. A touch of sheer genius!

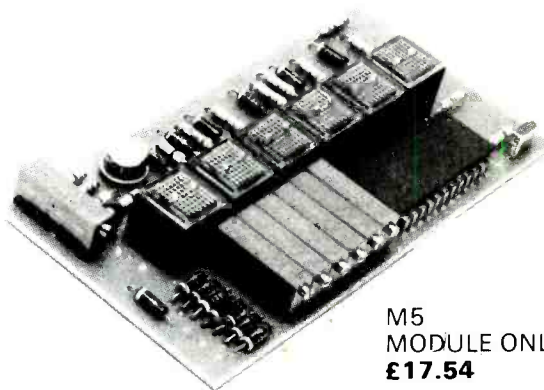


M5
MODULE ONLY
£17.54

OTHER MODULES etc.

M2 Stereo decoder	£7.60	kit	£6.22
M3 Push button 'M5'	£15.95	kit	£14.70
M4 Power supply	£6.30	kit	£5.90
SL1310 decoder IC	£1.95		
TBA750 f.m. i.f.	£1.55		
20v regulator IC	£1.50		
LP1186 front-end	£7.75		
Filter, SFJ10 7MA	£1.55		
7 segment L.E.D. (c/a)	£1.99		
Descriptive booklet	£0.50	(£1.00 export)	

ALL PRICES + 12.5% VAT

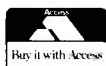

ORDERING INFORMATION

All U.K. orders post free plus 12.5% VAT. Export orders, allow extra for postage at cost, no VAT due, credit will be refunded.


Payment by sterling cheque on London bank, or credit card, International M.O. etc.

Other items and kits available, send for illustrated leaflets, price list and order form etc. from —

Icon Design

33 Restrop View
Purton, WILTS
SN5 9DG

JES AUDIO INSTRUMENTATION

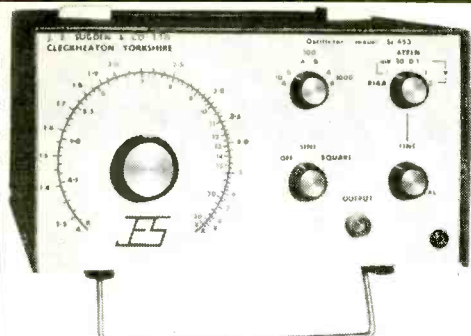

Illustrated the Si453 Audio Oscillator

SPECIAL FEATURES:

- ★ very low distortion content—less than 0.03%
- ★ an output conforming to RIAA recording characteristic
- ★ battery operation for no ripple or hum loop
- ★ square wave output of fast rise time

£60.00

also available

Si451 Millivoltmeter

- ★ 20 ranges also with variable control permitting easy reading of relative frequency response

£60.00

Si452 Distortion Measuring Unit

- ★ low cost distortion measurement down to 0.01% with comprehensive facilities including L.F. cut switch, etc.

£48.00


ALL PRICES PLUS VAT

J. E. SUGDEN & CO. LTD., CARR STREET, CLECKHEATON, W. YORKS. BD19 5LA.

Tel. 0274-872501

WW-020 FOR FURTHER DETAILS

When we make something new

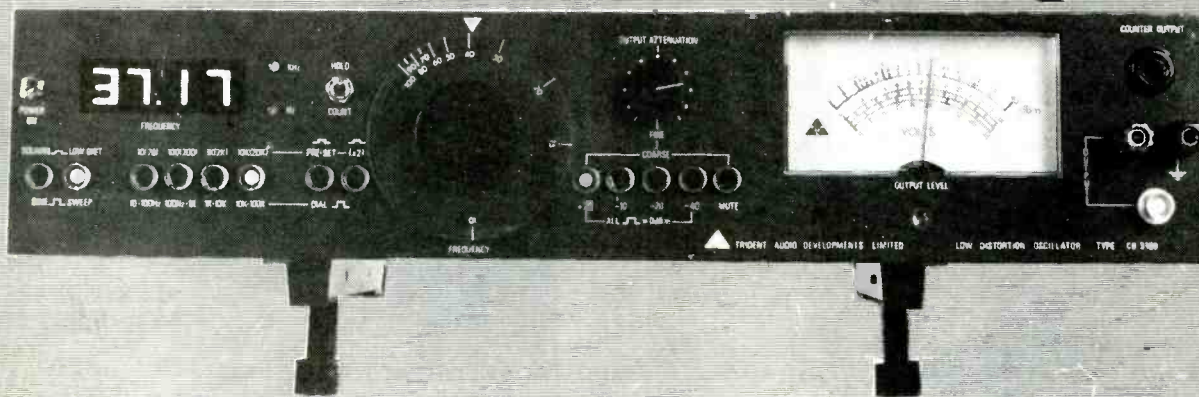

it's got to be better. . . .

OSCILLATOR/FREQUENCY COUNTER. This versatile instrument has been designed to meet the exacting requirements of the professional audio engineering field. The integral crystal/referenced digital counter ensures precise measurement of frequency and typical output distortion is 0.006% THD @ 1kHz. The unit covers the range of 10Hz to 100kHz in four pushbutton ranges, with eight preset frequencies from 10Hz to 20kHz to facilitate easy response checking of audio equipment. The output may be switched to give fast first-time square wave. The frequency-counter may be separately accessed via the COUNTER INPUT socket on the front panel.

LIKE OUR NEW LOW DISTORTION

For further details contact:
Trident Audio Developments Ltd.
Sales Office: 112/114 Wardour St., London, W1
Tel. 01-734 9901. Telex 27782 Tridisc



Factory address: Shepperton Studios
Squiresbridge Rd., Shepperton, Middx.
Tel. Chertsey (09328) 60241

WW-088 FOR FURTHER DETAILS



**INTRODUCING
THE NEW
CROFTON C1
CCTV CAMERA**

The C1 Camera is a completely new design offering a high specification CCTV Camera suitable for both professional and amateur use.

The design offers high sensitivity with good signal to noise ratio by incorporating an F.E.T front end. Wide range and stable automatic sensitivity control circuit allows camera to be operated in a wide range of lighting conditions. All controls are internal and once set remain stable over long time periods.

Small size and weight make this a most versatile camera for general usage. Special one off Retail price including Vidicon (Less Lens) £140.59 inclusive. Kits also available.

Send s.a.e. for information
CROFTON ELECTRONICS LTD.
Dept. E, 35 Grosvenor Road, Twickenham
Middx. Tel. 01-891 1923
Secondhand cameras and monitors
always available

WW-049 FOR FURTHER DETAILS



Audio Connectors

Broadcast pattern jackfields, jackcords, plugs and jacks.

Quick disconnect microphone connectors
Amphenol (Tuchel) miniature connectors with coupling nut.


Hirschmann Banana plugs and test probes
XLR compatible in-line attenuators, and reversers.

Low cost slider faders by Ruf.

Future Film Developments Ltd.
90 Wardour Street
London W1V 3LE
01-437 1892/3

WW-037 FOR FURTHER DETAILS

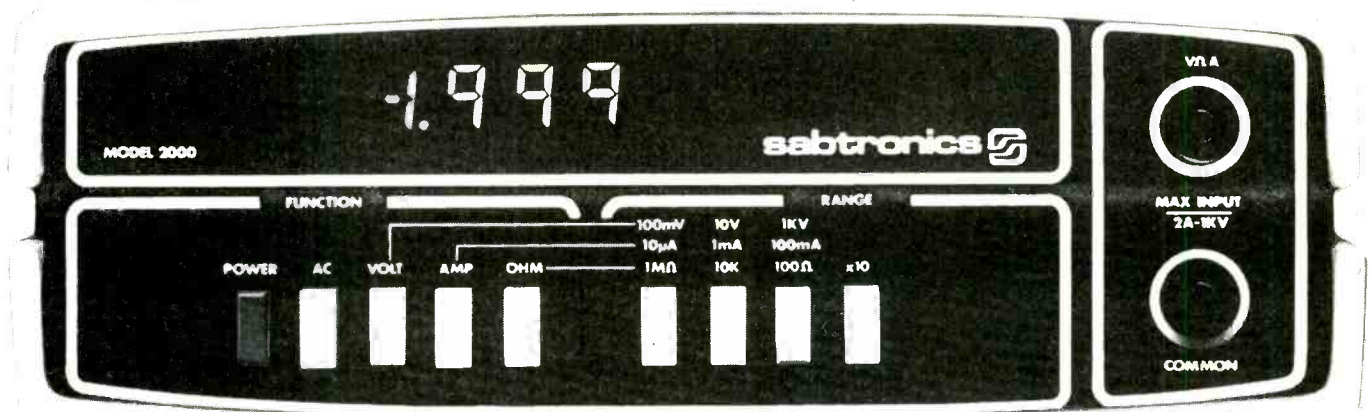We've just made the impossible . . . a professional 3 1/2 digit DMM Kit for less than £70



The Sabtronics Model 2000 is an impossible £69.95! And that price still includes phenomenal accuracy, range and professional features.


This all-new bench/portable multimeter, reading to ± 1999 , has a basic accuracy of $0.5\% \pm 1$ digit, and has five functions giving 28 ranges, 100% overrange and overload protection. So you know it's no toy!

Besides, what toys are as automatic as the 2000? With automatic overrange indication, automatic polarity, even automatic zeroing!

Yet the 2000 is easy to assemble. We send you all the parts you need, even the high-impact case. We also send you clear, step-by-step assembly instructions.

So you end up with a professional quality 3 1/2 digit DMM for the unheard of price of less than £70. From Sabtronics, specialists in digital technology. And manufacturers of the impossible.

Order yours today!

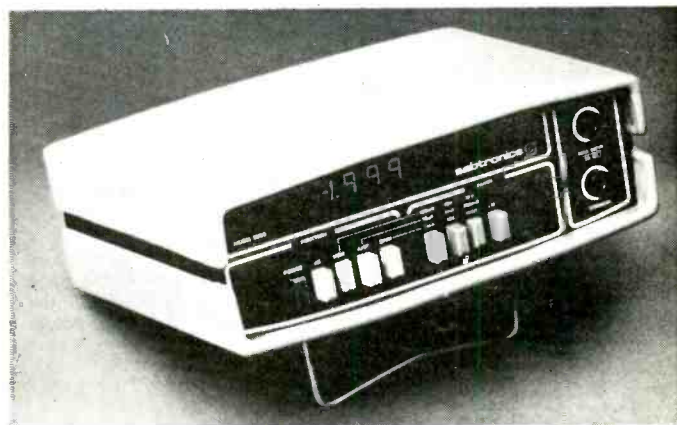

Made in U.S.A.

sabtronics 
USA

Sabtronics (U.K.) Ltd.
50 Galton Road
Westcliff-on-Sea
Essex

SPECIFICATIONS: (condensed)

- DC volts in 5 ranges: 100µV to 1000V.
- AC volts in 5 ranges: 100µV to 1000V.
- DC current in 6 ranges: 10nA to 2A.
- AC current in 6 ranges: 10nA to 2A.
- Resistance in 6 ranges: 1Ω to 20MΩ.
- Input Impedance: 10MΩ.
- Display: 9mm (.36") LED.
- Power requirements: 4.5 VDC to 6.5 VDC. (4 "C" cells - not included).
- Size: 8"W x 6.5"D x 3.0"H. (203W x 165D x 76H mm).

ORDERING INFORMATION FOR READERS OUTSIDE THE U.K.

The price listed is for readers in the U.K. only which includes import duties and V.A.T.

For readers in overseas countries the price is £49.95 plus £5.00 for Handling and postage, not included are any import duties or other taxes levied upon receipt of goods overseas. Payments from overseas customers should be made only by Bank drafts or International money orders and payable to Sabtronics International. Orders should be sent to:

Sabtronics International
Winkelriedstrasse 35
6003 Luzern
Switzerland

ww7
To: **Sabtronics (U.K.)**
50 Galton Road
Westcliff-on-Sea, Essex

Please send me Sabtronics Model 2000 DMM Kit(s) at £69.95 each incl. V.A.T. and Postage.

Total enclosed herewith: £

Name

Address

City County

Readers Overseas please see ordering Information.

The world's most famous company in communication, the Nippon Electric Company Ltd., Tokyo, has developed the famous NED CQ radio amateur gears, being with regard to design, quality, reliability and price real pace-setters for today's communicators.

First in history of amateur radio, such a big and famous company with more than 80 years of experience in construction of communication facilities, made its experience available to radio amateurs around the world.

The NEC, which has declared microwave space communication to its speciality, knows perfectly which attributes equipments must have for becoming bestsellers.

Today we present:

NEC CQ 110 E DIGITAL



allband, HF, 300watts transceiver, 160 / 80 / 40 / 20 / 15 / 11 / 10A / 10B / 10C / 10D / WWV, modes FSK, USB, LSB, CW, AM, with separate 8 pole X-tal lattice filters for each mode fitted. Further features: Side tone at CW, VOX (automatic transmit-receive by talking into microphone), 11 meter CB band, all channels easily selectable through digital counter, excellent receiver sensitivity at extreme crossmodulation security by application for the 7360 low noise beam, deflection mixer tube.

This feature alone makes of the NEC CQ 110 E a top rider. Fixed channel communication on 22 channels is possible. A 60 page manual and a high quality dynamic microphone are supplied with the transceiver. Speaker, AC 100-235 volts and DC 13.5 volts power supplies are built in of course.

NEC CQ 301



allband HF, 3KW, linear amplifier, 160/80/40/20/15/11/10 meter, for modern amateur communication. Two EIMAC 3-500 Z triodes, in zero bias grounded grid application guarantee long trouble free communication. The NEC CQ 301 can be driven by our CQ 110E or other exciters capable of about 50-100 watts of drive. AC power supply 100-235 volts is built in of course.

RETAILERS: Do not hesitate to accept our offer. Join us in selling these bestsellers!

Sole distributor in Europe:

CEC Corp., Via Valdani 1 — CH 6830 CHIASSO—SWITZERLAND
Phone: (091) 44 26 51. Telex: 79959 CH

WW—040 FOR FURTHER DETAILS

Test Equipment

Multimeters



The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.



Please send me details of all your test equipment.

NAME


ADDRESS

Eagle International, Precision Centre, Heather Park Drive,
Wembley HA0 1SU Tel: (01)-902 8832

Eagle

WW/4

BULK ERASURE PROBLEMS?

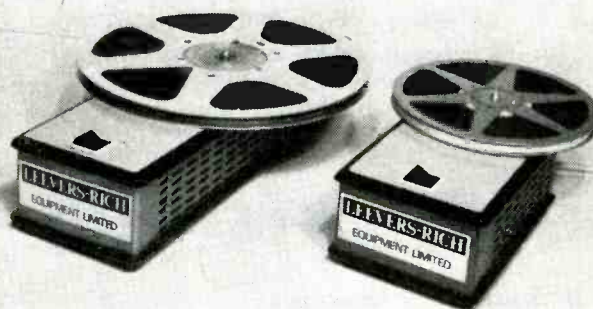

LR71
MAX REEL SIZE 11 1/2"

LR70
MAX REEL SIZE 8 1/4"


If it's personal we can only advise a diet or joining weightwatchers. If it's to do with tape, then why not consider the LR70/71 bulk tape erasers. They are simple to operate and will erase cassettes, cartridges and reels of tape up to a maximum reel size of 11 1/2" and tape width of 1", quickly and efficiently within the time it takes to read this advertisement.

The LR70/71 bulk erasers are currently used in Broadcast Companies, Recording Studios, Government Departments, Educational Establishments and the Computer Industry.

Moderately priced and available from:

LEEVERS-RICH EQUIPMENT LIMITED
INCORP. BIAS ELECTRONICS
319 Trinity Road, Wandsworth, London SW18 3SL
Telephone 01-874 9054
Cables: Leemag London SW18. Telex 923455 Wembley

WW—033 FOR FURTHER DETAILS

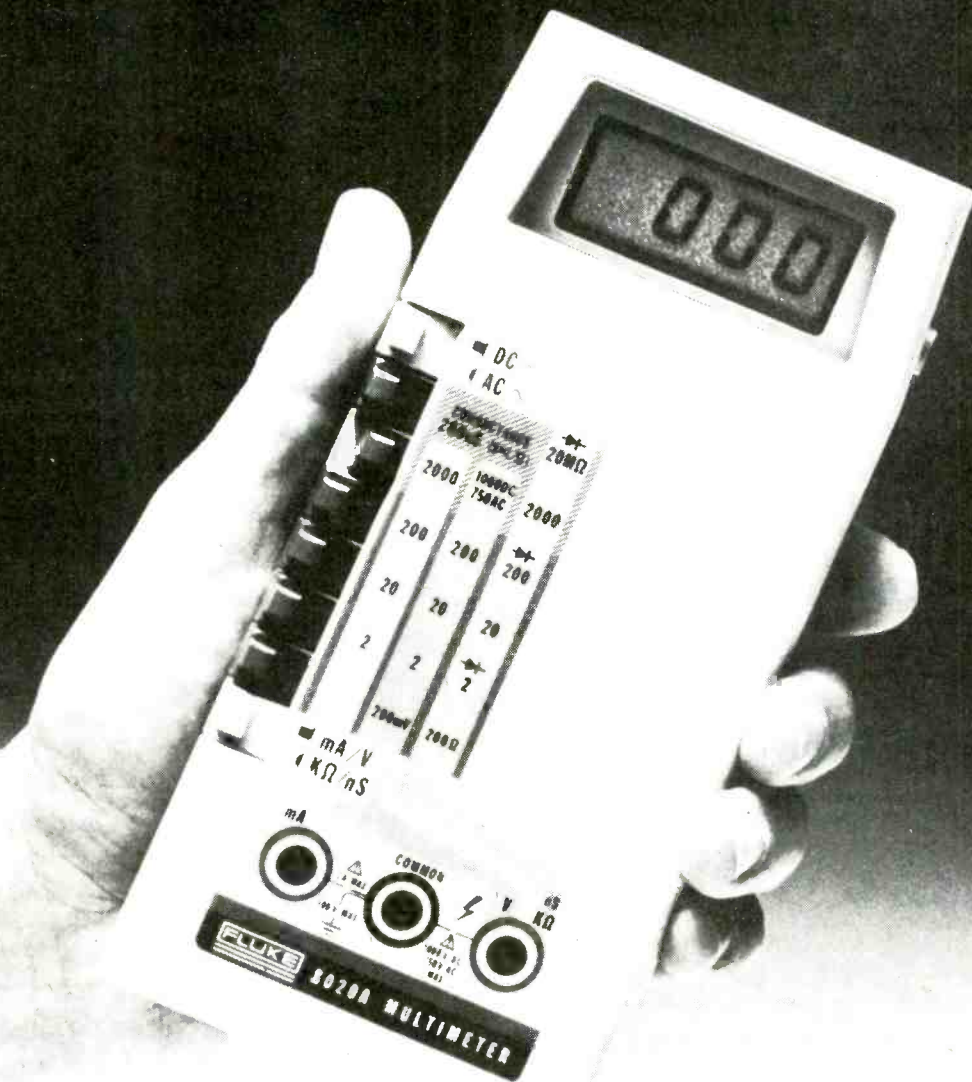

NOW, A PROFESSIONAL DMM FOR UNDER £100

You're a professional and therefore insist on a professional instrument. Now it's here - our 8020A - a pocket-size DMM weighing only 370 grammes. It has the accuracy and the functions of a lab instrument, yet fits your pocket and purse, costing only £99.

It goes wherever you go. Your 8020A DMM operates for two hundred hours on a standard 9 volt battery. And wherever it goes it is supported by Fluke's renowned worldwide service.

Look at the features. You won't find any other instrument in size or price which, besides full DMM capability,

FUNCTION	RANGES	ACCURACY
DC Volts	(5) 100 μ V-1000V	$\pm 0.25\%$
AC Volts	(5) 100 μ V-750V	$\pm 0.75\%$
DC Amps	(4) 1 μ A-2000mA	$\pm 0.75\%$
AC Amps	(4) 1 μ A-2000mA	$\pm 1.5\%$
Resistance	(6) 100m Ω -20M Ω	$\pm 0.2\%$
Conductance	(2) leakage from 200nS-2mS	
Diode Test	(3) 2k Ω , 200k Ω , 20M Ω	

offers conductance and diode test. And Fluke's wide accessory-range.

Fluke International Corporation
Garnett Close Watford WD2 4TT
Tel.: 0923-33066
Telex: 934583

ITT Instrument Services,
Edinburgh Way,
Harlow, Essex CM20 2DF,
Tel.: (0279) 295.22.

Contact us for your nearest dealer or distributor.



200 Hours operation from 9V battery.

FLUKE MAKES IT EASIER!

WW-092 FOR FURTHER DETAILS



When you're already unique in your field - why bother to be better?

BECAUSE it's the only way to keep pace with Europe's fast-expanding electronics industry. That's why there are some major changes in Electronics Weekly. Apart from more pages and a new look throughout, you'll find:

- MORE NEWS** in each department.
- MORE COVERAGE** especially of innovations.
- MORE COMMENT** on developments behind the news.
- MORE TECHNICAL SURVEYS.**




Order your own copy by using this form

To: Electronics Weekly, Room 218, Dorset House, Stamford Street, London SE1 9LU
 I wish to take out a one-year subscription to Electronics Weekly. Remittance enclosed for £6.00 (U.S.A./Canada \$15.60). Cheques made payable to IPC Business Press Ltd.

NAME _____
 (Please print)
 Address _____

Registered in England No. 677128
 Regd. Office, Dorset House, Stamford Street, London SE1 9LU

nombrex

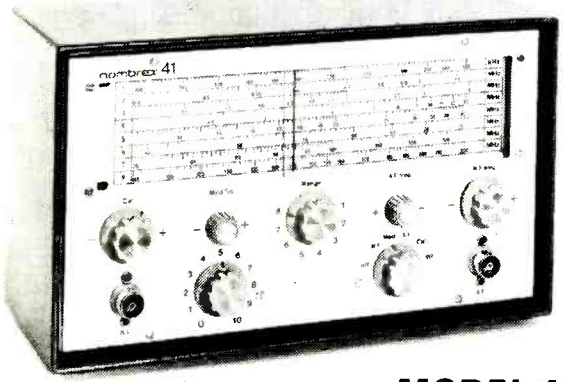

MODEL 41 R.F. SIGNAL GENERATOR Price £54.85 PLUS V.A.T.

- ★ 150 KHz — 220 MHz on fundamentals.
- ★ 8 clear scales — Total length 130mm.
- ★ Spin-Wheel Slow Motion Drive 11 - 1 ratio.
- ★ Overall Accuracy — 2½%.
- ★ Modulation, Variable depth and frequency.
- ★ Internal Crystal Oscillator providing calibration checks throughout all ranges.
- ★ Mechanical scale adjustment for accurate alignment against internal 1MHz crystal oscillator.
- ★ Powered by 9V Battery.

Trade and Export enquiries welcome
 Send for full technical leaflets
 Post and Packing £1.00 extra

**NOMBREX LTD., POUND PLACE, WOLBOROUGH STREET,
 NEWTON ABBOT, DEVON, TQ12 1NE
 Tel. Newton Abbot 68297**

WW-029 FOR FURTHER DETAILS

fault finding - no fiddle

With the AVO TT 169 in-circuit transistor tester. Go/No Go tests almost any transistor, diode or thyristor without de-soldering, without damage. Find out how it can save you time, save you money. You'll find the price is no fiddle either. Contact your local wholesaler, or us:



AVO Limited, Dover, Kent CT17 9EN.
 Telephone: Dover (0304) 202620

Thorn Measurement Control and Automation Division.

WW-046 FOR FURTHER DETAILS

ELECTRONORGTECHNICA carbon film RESISTORS

1/8 and 1/4w 70°C 5% tol. E.12
 EX-STOCK
£4.90 PER 1,000 PLUS & POSTAGE
 OF ONE VALUE V.A.T.

Minimum export order £100
 Contact John Gingell

Z & I AERO SERVICES LTD.
 44A Westbourne Grove
 London W2 5SF
 TEL: 01-727 5641 TELEX 261306

WW-075 FOR FURTHER DETAILS

TIME + FUEL + EFFORT = MONEY

You can effectively reduce costs by the installation of a STORNO mobile radio system.

To investigate further, write, telephone or telex to


Storno

RADIO COMMUNICATION SYSTEMS

Storno Limited, Frimley Road, Camberley, Surrey.
Telephone: Camberley (0276) 29131 Telex: 858154

WW-055 FOR FURTHER DETAILS

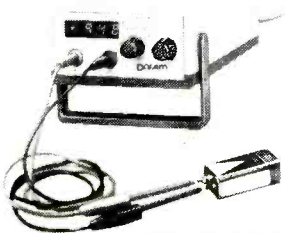Big saving, good looking, fast checking NEW Doram DIGITAL MULTIMETER— BUILD IT YOURSELF AND SAVE UP TO £40!



KEY DATA

Volts DC	200mV, 2V, 20V, 200V, 1000V Input impedance 4.2M Ω . Maximum sensitivity 100 μ V.
Volts AC	200mV, 2V, 20V, 200V, 500V Input impedance 4.2M Ω . Maximum sensitivity 100 μ V.
Current AC/DC	200 μ A, 2mA, 20mA, 200mA, 2A
Resistance	200 Ω , 2K Ω , 20K Ω , 200K Ω , 2M Ω

A clear, functional multimeter, featuring extremely accurate digital display, in superbly styled shatterproof carry-case. It could cost £100! But the complete Doram kit with case, printed circuit board, leads and all components is yours for just £54.50 plus £4.36 VAT.

Based on Ferranti technology with accuracy $\pm 0.6\%$, the new Doram Multimeter is an indispensable tool at a terrific saving. Measurement is indicated by a 3½ digit display updated twice per second — display flashes to indicate overload.

And it saves you money before it's even built!

DEPEND ON DORAM

Thousands of kit makers do for top value and modern technology.
Doram Electronics Ltd, PO Box TR8, Wellington Road Industrial Estate, Wellington Bridge, Leeds, West Yorkshire LS12 2JF.
Registered in London No. 1155856 Directors: R A Marler, D I Turner, F Chable.

Yes, I want to save up to £40

Please send me (subject to availability) complete kit(s) for Doram DIGITAL MULTIMETER at (£54.50 + £4.36 VAT incl. p & p) total **£58.86**. I understand I can return the unused kit(s) within 7 days and claim my money back if kit(s) returned undamaged in the form received and ready for re-sale.

Please send me complete DORAM KITS CATALOGUE(s) showing an additional 25 kits, at 25p each.

I enclose cheque/PO value

NAME (BLOCK CAPITALS)

ADDRESS


TOWN

COUNTY

POST TO: DORAM ELECTRONICS LTD., DEPT. WM2, PO BOX TR8, LEEDS, WEST YORKSHIRE LS12 2UF

643A FUNCTION GENERATOR

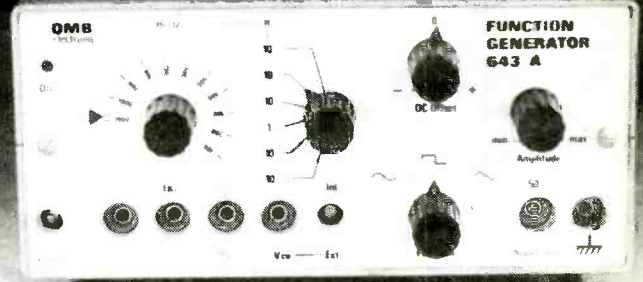SINE, SQUARE & TRIANGLE
0.01 Hz to 1.1 MHz
10V pp $\pm 5V$ DC OFFSET
1000 : 1 Vco RANGE



643A FUNCTION GENERATOR £85 + £2.50 p&p

Other products include

643 FUNCTION GENERATOR	£98	VW065
745 COUNTER TIMER	£94	VW066
744 COUNTER TIMER	£85	VW067
631 FILTER OSCILLATOR	£108	VW068

WW064

Delivery is normally ex-stock — telephone for confirmation
Prices exclude VAT and are correct at time of going to press. Subject to change without notice.

OMB electronics

Riverside, Eynsford, Kent. Tel. 0322 863567

POWER UNITS

Valradio

PRODUCTION TESTING ★ DEVELOPMENT
SERVICING



TYPE 250VRU/30/25

Input 200-250v 50Hz or 100-120v 60Hz to order. Output 1: 0-30v 25A DC. Output 2: 0-70v 10A AC. Output 3: 0-250v 4A AC.

PRICE: £233.60 excluding VAT

Regulated and unregulated outputs with output voltages of 12, 24, 50, 110 or 220v DC are also available at very competitive prices.

Send for further details of these versatile units to:-

Valradio

BROWELLS LANE, FELTHAM, MDDX.
TW13 7EN
PHONE: 01-890 4242 or 4837

WW-054 FOR FURTHER DETAILS

The Finest —

KEYBOARDS

The "S.K.A." Plastic Keyboard was developed by Kimber Allen Ltd in co-operation with a Swedish company and the manufacturers state that in their opinion it is the finest moulded plastic keyboard made and is not to be confused with cheaper keyboards available.

The keys are moulded in Acrylic plastic, a material chosen for its hard wearing properties and ideal feel to the touch. They are moulded in two parts, the key face, which has to be perfect in appearance and finish, and the action, which has to be strong and carry the mechanism. The strong section of aluminium extrusion upon which they are mounted is specially designed to take all the pressures of playing. Springs, felts, and contact actuators are supplied ready-fitted.

The contact assemblies are constructed of laminated bakelite, thus giving smooth slot walls and completely free movement of the gold-clad contact wires. Types available as follows (Contact pairs normally open):

GJ-SPCO: 24p each **GE-4 pairs :** 45p each
GB-2 pairs: 27p each **GH-5 pairs :** 57p each
GC-3 pairs: 36p each **4PS-SPCO & 3 prs:** 53p ea


Palladium Wire Bus Bars — 1 octave lengths : 50p each

We also stock kits and PCBs for the P. E. Synthesiser, P. E. Joanna (electronic piano), P. E. Minisonic, and other sound synthesising and modifying projects published in Practical Electronics. Send SAE for full list (Overseas send 40p).

PHONOSONICS

DEPT. WW77, 22 HIGH STREET
 SIDCUP, KENT DA14 6EH

& CONTACTS

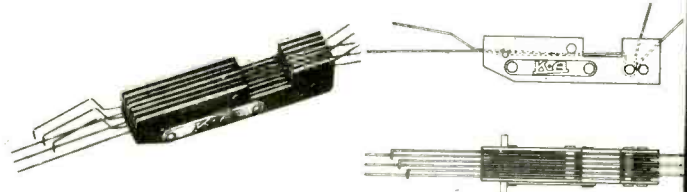

U.K. POST & HANDLING:
Keyboards: £1.50 each
Contacts:

Orders under £15.00: 25p
Orders over £15.00: 50p

37 Note C-C Keyboard :
£25.50

49 Note C-C Keyboard :
£32.25

61 Note C-C Keyboard :
£39.75

VAT: Add 12 1/2 % to final total on all U.K. orders
EXPORT ORDERS ARE WELCOME but please see our price list for Export Postage Rates. **N.B. EIRE, CHANNEL ISLES & B.F.P.O. classify as Export.**

MAIL ORDER AND C.W.O. ONLY — SORRY BUT NO CALLERS PLEASE
 Prices are correct at time of Press, E. & O.E. Delivery subject to availability

WW—038 FOR FURTHER DETAILS

Crimson Elektrik

AUDIBLY SUPERIOR POWER AMPLIFIER MODULES

A power amp. built with CE modules will be audibly comparable to the very best amps. commercially available, but at a much reduced cost. T.H.D. is typically .01% by the use of output triples & moderate feedback, while t.i.d. is no worry with a slew-rate limit of 16v/μs (only 9v/μs is required for the power bandwidth of CE 1008). Settling time < 15μs. ★ S/N > 110dB ★ 120x80x25mm. ★ Fully protected ★ 250mw/56kn ★ 12Hz-35kHz, -3dB ★ 14Trs. 4Di


Power Supplies: Featuring high quality Toroidal transformers with 120-

CPS 1 For 2xCE 608 or 1xCE 1004 £12.55 240v primary & screen;
 CPS 2 For 2xCE 1004 or 2 or 4xCE 608 £14.55 2 large capacitors;
 CPS 3 For 2xCE 1008 £15.85 rectifier; fixings.

Power amp. modules:
 CE 608 60Wrms/8n, ±35v, £14.55
 CE 1004 100Wrms/4n, ±35v, £17.55
 CE 1008 100Wrms/8n, ±45v, £21.55

H/sinks: 50mm 85p; H/duty 100mm. £1.50

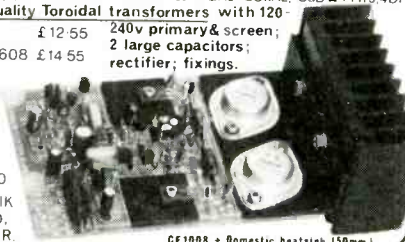
All prices inclusive
 CRIMSON ELEKTRIK
 74 STATION ROAD,
 RATBY, LEICESTER



CE 1008 + Domestic heatsink, (50mm.)


WW—048 FOR FURTHER DETAILS

QUARTZ CRYSTALS - FAST!

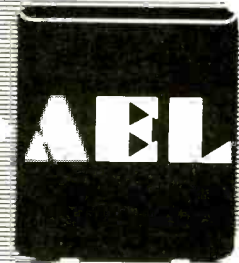

AEL CRYSTALS LIMITED
 Gatwick House, Horley, Surrey, England RH6 9SU
 Telephone: Horley (02934) 5353 Telex: 87116 (Aerolon Horley)
 Cables: Aerolon Telex Horley

WW—045 FOR FURTHER DETAILS

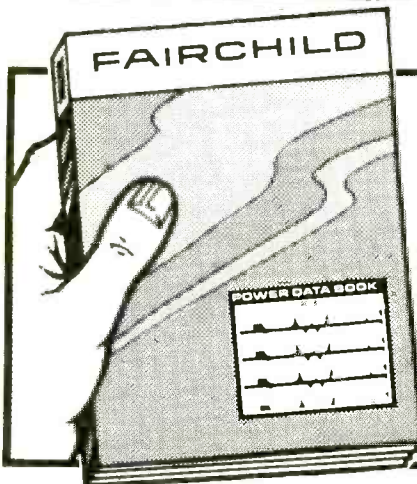

FAIRCHILD POWER AT YOUR FINGERTIPS

Included in this new Databook

- * Power Transistor Selection Guides
 - * Industry Cross Reference List
 - * Full Technical Specifications
 - * Chapters on Reliability, Packaging and Heatsinking, Safe Operating Area
- Price £2.00 each incl. P & P**


Available from any of our distributors

- | | |
|----------------|-----------------------------|
| Barlec | East Grinstead (0342) 24383 |
| Celdis | Reading (0734) 585171 |
| Comway | Bracknell (0344) 24765 |
| Eurocom | High Wycombe (0494) 36146 |
| ITT-ESD | Harlow (0279) 26777 |
| Macro | Burnham (06286) 63011 |
| Most | Manchester (061) 831 7672 |

OTHER DATABOOKS AVAILABLE INCLUDE:
 LINEAR, MOS/CCD, BIPOLAR MEMORY,
 MACROLOGIC, LOW POWER SCHOTTKY
 TTL, F8 MICROPROCESSOR, DISCRETE
 ASK YOUR DISTRIBUTOR FOR DETAILS

Four Good Reasons for using Zettler Relays:

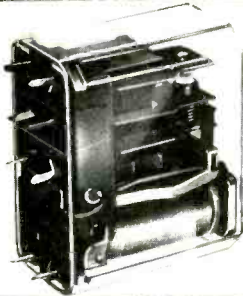Zettler Relays are first class quality. We have about 50 years experience in producing relays. Zettler Relays are readily available. Most are available ex stock Harrow. Zettler Relays are proved in practical applications. Millions are used in our own electronic systems and products. Zettler has the right relay for most applications, e. g.:



Miniature Extra Heavy Duty Relay AZ 230

Capable of switching high power in spite of small physical size.
Contact: 1 changeover.
Contact material: Silver cadmium oxide.
Rating: 3.5 kVA, 16 A, 250V AC max.
Dielectric strength: 2.5 kV rms.
Coils: 5 V DC - 110 V DC.
Size: 35.5x19x30.2 mm.
Printed circuit mounting.



Let us help you with your switching problems.

ZETTLER

est. 1877

Zettler UK Division
Brember Road · Harrow, Middx. HA2 8AS · Tel. (01) 422 0061


Zettler offers more than technology

Please look us up at
LEEDS ELECTRONICS EXHIBITION
UNIVERSITY OF LEEDS 28th, 29th, 30th JUNE

WW-008 FOR FURTHER DETAILS

FYLDE

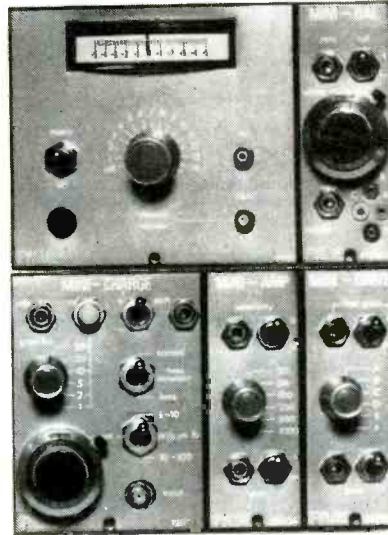TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS




reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE

Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston PR1 2XQ
Telephone 0772 57560

WW-024 FOR FURTHER DETAILS

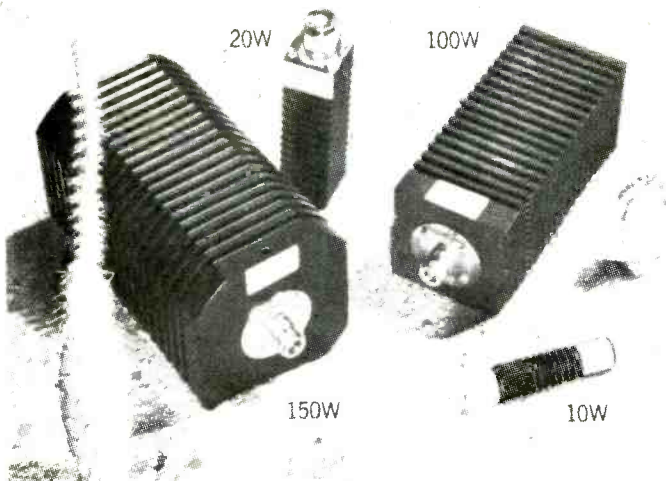

PAY LESS FOR LOADS?

With nearly 3 decades of experience built into every TERMALINE® Coaxial Load Resistor, buying BIRD will often cost no more or save you money. BIRD QC Quick-Change Connectors on many models offer a choice of any common RF connector, eliminating the need for performance-degrading adapters.

Twenty aircooled dry Loads (2W to 225W), thirteen aircooled liquid Loads (20W to 5kW) and nineteen watercooled TERMALINE® models (1kW to 50kW) are listed in our 1977 Catalog. Ask for it.

EXCLUSIVE U.K. REPRESENTATIVE FOR BIRD ELECTRONICS

aspen

electronics limited

2 KILDARE CLOSE, EASTCOTE, MIDDX. HA4 9UW.

Tel: 01-868 1188. Telex: 8812727

WW-044 FOR FURTHER DETAILS

HVS NON-CONTACT MEASUREMENT AND CCTV DISPLAYS



NON-CONTACT MEASUREMENT, using standard CCTV cameras. Fast, versatile measurements for Production and Test:

VP 101/2 TARGET LOCATORS for automatic positioning.
VP 103 TARGET HEIGHT INDICATOR for dimension checking.

VP 104 AUTOMATIC VISIBLE FLAW DETECTOR

VP 105 INTENSITY INDICATOR checks brightness at selected spot.

CCTV DISPLAYS compatible with standard CCTV equipment.

BAR GRAPH GENERATORS 8-32 way displays.

SUBTITLE/INDICATOR superimposes pre-stored and typed-in messages, also movable arrow and box, on CCTV picture.

HAMPTON VIDEO SYSTEMS LTD.
Heath Road, Twickenham. Tel. 01-891 1974

WW-062 FOR FURTHER DETAILS



Auto Ranging capacitance bridge

Wide Range C-Meter measures electrolytics in less than 1 second. No bridge balancing means you eliminate errors and save time.

Automatic Capacitance Bridge features fast, accurate measurement from 1pF to 2000µF. Full Autoranging means you get the facts without confusion.

Price £235

Available direct from

electroplan

PO Box 19
Orchard Road
Royston, Herts
SG8 5HH
(0763) 41171

★ Two terminal measurements
★ Less than 2 seconds to measure
★ Autoranging — 1pF to 2000µF
★ Accuracy — ± 0.5%
★ Large digital display

★ Low profile metal instrument case
★ Continuous measurement

ESP Electronic Services & Products Ltd.
Middle March, Daventry, Northants
(03272) 76720

WW—087 FOR FURTHER DETAILS

Speed up your precision work with MINIATURE POWER EQUIPMENT

- SUPER 30 KIT** — 30 tools incl. drill
without stand £19.39 pp 85p
- PIS DRILL STAND** £5.13 pp 35p
- PI-DRILL** £9.67 pp 35p
- FLEXIBLE DRIVE SHAFT**
£5.94 pp 25p
- TRANSFORMER**
continuous ac/12v dc £7.56 pp 70p
- VARIABLE SPEED TRANSFORMER**
£9.50 pp 70p

Replacement drills, stones, burrs, etc.
40p each. Circular saw blades, set of 4
with arbor, £2.50

P & P any quantity, 20p. 9" x 4" S.A.E.
please for leaflet and order form

All VAT inclusive



Drill can be
held in
the hand



PRECISION PETITE LTD

119a HIGH STREET TEDDINGTON MIDDLESEX TW11 8HG
Tel. 01-977 0878-24 Hour recorded service

WW—050 FOR FURTHER DETAILS


Heyco Nylon 1/2" cable clamps



£8.73
PER THOUSAND

Even less for quantities over 10,000. Above is just one example from a range of 26 sizes to accommodate cables from 1/8" to 1 1/2" in diameter. Lightweight. Tough. Position any number of wires safely and neatly. Excellent insulators.

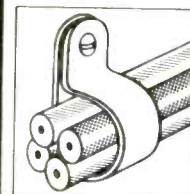FREE SAMPLES
and full technical details on request.



26
SIZES

Secured by single screw (not supplied)



HEYCO MANUFACTURING CO. LTD.
Uddens Trading Estate, Nr. Wimborne, Dorset
BH21 7NL Tel: Ferndown (STD: 0202) 871411/2/3
Telegrams: HEYCOMAN Wimborne. Telex: 41408

WW — 081 FOR FURTHER DETAILS

ACTIVE CROSSOVER SYSTEM

LATEST MAGNUM MODULE FOR LINEAR PHASE ACTIVE CROSSOVER NETWORKS

With the **CP-LX1** — the latest in the expanding range of **MAGNUM AUDIO MODULES** — you can build an active crossover network for any multiple speaker system, using one CP-LX1 per crossover frequency. In addition to the improved loudspeaker damping and transient response resulting from such systems, the **CP-LX1** scheme is readily adjustable so that a desired specification may be achieved with an ease and confidence not possible with passive systems. Moreover, any subsequent adjustments may be made for a few pence so that optimum performance is always achievable. As with all **MAGNUM AUDIO MODULES**, full application data is provided. Should you wish, we will also provide your **CP-LX1** preset to your choice of frequency (order as **CP-LX1-P** and frequency).

CPLX1 £8.65 VAT £1.08
CP-LX1-P £9.65 £1.21

SEND SAE for details of the CP-LX1 and other MAGNUM AUDIO MODULES.

CP-P1 Stereo Preamplifier £13.30 VAT £1.66
CP-FG1 Audio Function Module £11.75 VAT £1.47
CP-2-15/20 20 + 20W or 40W Amplifier £12.85 VAT £1.61
CP-PS-18/2D Power Supply Module £6.50 VAT £0.81

Also available pots, switches knobs, sockets etc. and Mother PCBs.
Prices include full application data, post and packing.
Barclaycard and Access facilities available.
Products guaranteed 2 years

Cliffpalm Ltd.

DEPT. JW, 13 HAZELBURY CRESCENT
LUTON, BEDS, LU1 1DF. Tel: 0582 415832

WW — 085 FOR FURTHER DETAILS



Better instruments. Better service.

We have established a nationwide network of approved service organisations to deal with the repair and maintenance of our instruments. Every repair is backed by a full 12 month guarantee. Here's where to find them.

ENGLAND London Instrument Repair Centre, Acton Lane, Chiswick, London W4 5HJ. Trade Reception: Cunnington Street. Tel: 01-995 9212
 London Instrument Repair Centre, Archcliffe Road, Dover, Kent. Tel: Dover (0304) 202620
 Farnell International Instruments Ltd., Sandbeck Way, Wetherby, West Yorkshire LS22 4DH. Tel: Wetherby (0937) 3541
 T.E.R. Instrumemnts Ltd., Peel Lane, Astley, Manchester M29 7JH. Tel: Atherton (05234) 2275 or 5611
 Midlands Instrument Repair Centre, Thorn Automation Ltd., Armitage Road, Rugeley, Staffs. Tel: Rugeley (08894) 5151


SCOTLAND Falcon Electronics, 92 High Street, Johnstone, Scotland. Tel: Johnstone (0505) 23377

WALES Electro Services, 25 Chepstow Road, Newport, Gwent NPT 8BX. Tel: Newport (0653) 211243



The manufacturers' joint service organisation.

WW-034 FOR FURTHER DETAILS

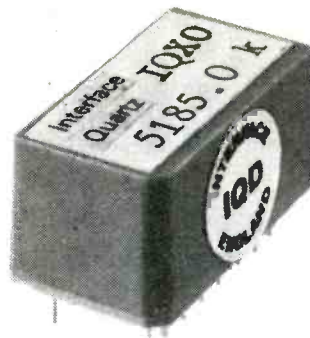

IQXO

MINIATURE QUARTZ CRYSTAL OSCILLATORS

INTERFACE QUARTZ DEVICES LTD.

World-wide exporters of crystals & filters
 Manufacturers of DIP crystal oscillators
 from 240Hz to 20MHz

sole agents for

FILTRONETICS LC & crystal filters from 10Hz to 100MHz

STATEK Ultra miniature low frequency crystals

ELECTRO DYNAMICS High volume timing crystals

29 Market Street, Crewkerne, Somerset England TA18 7JU
 Telephone (0460) 74433 Telex 46283 inface g

WW-015 FOR FURTHER DETAILS

DETECKNOWLEDGEY

DETECKNOWLEDGEY ?

Not a spelling mistake, but a new publication from AMBIT that sets out to explain some of the basic theory that surrounds metal location techniques. It is an explanation, that builds up from first principles, why iron sometimes reacts like a non-ferrous metal, what determines detector range, what the shortcomings are, how to avoid them. In fact, it explains about BFO, IB, VCO and Pulse Induction techniques, as a result of research carried out to produce our range of locators, and why we chose the methods we used. As a general purpose reference work for designers, constructors, users etc., we think you will find it unique. £1.00 inc. postage.

Bionic Ferret Metal Locators

As a result of our investigations, we offer you three metal locators now: The VCO 4000, the IB phase angle meter, and the 'Pulsedec' pulse induction metal locator. It is impossible to catalogue the relative virtues of each type here, so please send an SAE for details.

Components for Wireless: ICs, Coils, Ceramic & Mechanical Filters, trimmers etc

Linear ICs		Tuner modules/TOKO parts	
CA3089E/KB4402	1.94	ICL8038CC*	4.50
MC1310/KB4400	2.20	NE555V*	0.70
TBA120/SN76660	0.75	NE565/6/7*	2.50
uA753	1.80	NE560B*	3.50
HA1137W	2.20		
CA3090AQ	3.75	Discrete devices	
HA1196	4.20	40673/MEM616*	0.57
uA720/CA3123E	1.40	MEM680*	0.75
HA1197	1.40	MEM614*	0.38
TBA651	1.81	BF256L/S	0.34
LM380N	1.00	MVAM115 varicap	0.95
LM381N	1.81	MVAM125	0.90
LM3900*	0.75	MVAM2	1.35
TDA2020	2.99	BB104	0.45
TCA940	1.80	BB105	0.30
TBA810AS	1.09	BA102/BA121	0.30
MC1312	1.50	ZTX/BC107/8/9	0.14
7805UC*	1.55	ZTX/BC212/4	0.17
78M12* /TDA1412	1.20	BC413	0.18
78M20*	1.20	ZTX451/551	0.18
78M24*	1.20	BD609	0.70
uA723CN*	0.80	BD610	1.20
TAA550B*	0.50	more in price list.....	

PLEASE NOTE: Vat is extra, at 12.5% except where marked * (8%). PP 22p per order. An A5 size SAE for free current price lists, or 40p for the complete catalogue. Write to: 37a High Street, Brentwood, Essex. CM14 4RH. (tel. 0277-216029)

ambit international

WW-094 FOR FURTHER DETAILS

LEEDS ELECTRONICS EXHIBITION

28/29/30 June 1977
 Tuesday, Wednesday & Thursday
 10 am to 6 pm

Department of Electrical & Electronic
 Engineering
 University of Leeds

Bargain Time!

Unique alpha-numeric listings of ratings and characteristics of a very wide range of semi-conductors of international origin and with an extensive substitution guide.

USED WORLDWIDE - PROFESSIONALLY

TO INTRODUCE THE

new 7TH edition of



THE SEMICON

INTERNATIONAL TRANSISTOR INDEX
AND THE DIODE/SCR INDEX

WE HAVE

A SPECIAL OFFER


FOR NEW AND EXISTING SUBSCRIBERS

SEND FOR DETAILS • DON'T DELAY

● AVAILABLE FOR
A LIMITED PERIOD ONLY

SEMICON INDEXES LTD.

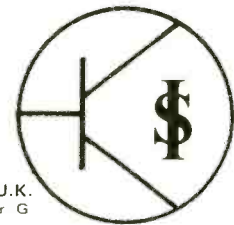7, KING'S PARADE, KING'S ROAD, FLEET, HAMPSHIRE. GU13 9AB. U.K.
TELEPHONE: FLEET (025 14) 28526 TELEX: 858855 Barmer G



WW — 056 FOR FURTHER DETAILS



Wilmslow Audio

THE Firm for Speakers!

SEND 10p STAMP FOR THE WORLD'S BEST
CATALOGUE
OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS,
ETC.
AND DISCOUNT PRICE LIST

ATC ● AUDAX ● BAKER ● BOWERS & WILKINS
● CASTLE ● CELESTION ● CHARTWELL ●
COLES ● DALESFORD ● DECCA ● EMI ●
EAGLE ● ELAC ● FANE ● GAUSS ●
GOODMANS ● HELME ● I. M. F. ●
ISOPHON ● JR ● JORDAN WATTS ● KEF ●
LEAK ● LOWTHER ● MCKENZIE ●
MONITOR AUDIO ● PEERLESS ● RADFORD
● RAM ● RICHARD ALLAN ● SEAS ●
TANNOY ● VIDEOTONE ● WHARFEDALE

WILMSLOW AUDIO (Dept. WW)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount Hi-Fi, etc., at 5 Swan Street and 10 Swan Street

Tel. Wilmslow 29599 for Speakers Wilmslow 26213 for Hi-Fi

WW—013 FOR FURTHER DETAILS

DATA AND COMMUNICATIONS TERMINALS

Teletype 28, 32, 33, 35, 40
TermiNet 30, 300 & 1200 (30 and 120 cps)
Teleterm 1132 and 1200 series (portable/fixed 30 cps)
with integral coupler and RS 232C)
Other page printers (by Siemens, ITT Creed, etc.)

- ★ Spares, repairs, overhauls and maintenance
- ★ Other types and models available
- ★ Refurbished units also available
- ★ Short and long period rentals
- ★ Minicomputer interfaces
- ★ Quantity discounts
- ★ Immediate delivery

TELEPRINTER EQUIPMENT LTD.
70-80 AKEMAN STREET
TRING, HERTS., U.K.

Telephone 0442-82-4011
Cables RAHND Tring
Telex 82362
A/B Batelcom Tring



WW—026 FOR FURTHER DETAILS

15 — 240 Watts!


HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — two simply combined for stereo.

APPLICATIONS: Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

SPECIFICATIONS:
 INPUTS: Magnetic Pick-up 3mV Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; input impedance 47k Ω at 1kHz
 OUTPUTS: Tape 100mV; Main output 500mV R.M.S.
 ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz
 DISTORTION: 0.1% at 1kHz; Signal/Noise Ratio 68dB
 OVERLOAD: 38dB on Magnetic Pick-up; SUPPLY VOLTAGE: \pm 16-50V
Price £5.22 + 65p VAT P&P free
 HY5 mounting board B1 48p + 6p VAT P&P free

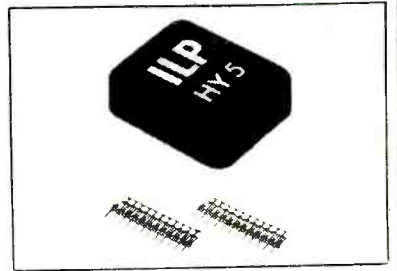


HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C. heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build

APPLICATIONS: Updating audio equipment — Guitar practice amplifier — Test amplifier — Audio oscillator

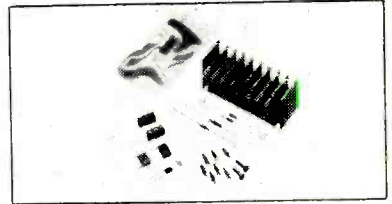SPECIFICATIONS:
 OUTPUT POWER 15W R.M.S. into 8 Ω ; DISTORTION: 0.1% at 15W
 INPUT SENSITIVITY 500mV; FREQUENCY RESPONSE 10Hz-16kHz — 3dB
 SUPPLY VOLTAGE: \pm 18V
Price £5.22 + 65p VAT P&P free.



HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

APPLICATIONS: Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

SPECIFICATIONS: INPUT SENSITIVITY 500mV
 OUTPUT POWER 25W RMS in 8 Ω LOAD IMPEDANCE 4-16 Ω ; DISTORTION 0.04% at 25W at 1kHz
 SIGNAL/NOISE RATIO 75dB; FREQUENCY RESPONSE 10Hz-45kHz — 3dB
 SUPPLY VOLTAGE \pm 25V; SIZE 105 50 25mm
Price £6.82 + 85p VAT P&P free




HY120 60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range designed to meet the most exacting requirements including load line and thermal protection, this amplifier sets a new standard in modular design.

FEATURES: Very low distortion — Integral Heatsink — Load line protection — Thermal protection — Five connections — No external components

APPLICATIONS: Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

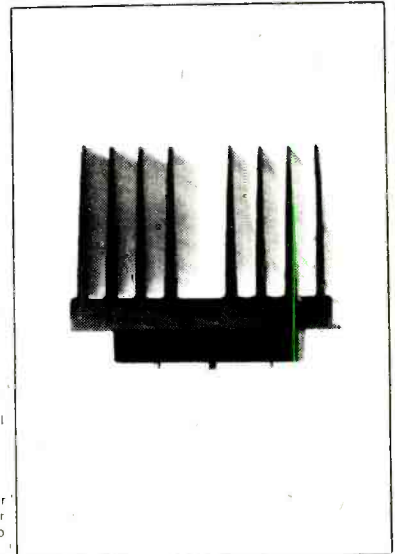SPECIFICATIONS:
 INPUT SENSITIVITY 500mV
 OUTPUT POWER 60W RMS into 8 Ω ; LOAD IMPEDANCE 4-16 Ω ; DISTORTION 0.04% at 60W at 1kHz
 SIGNAL/NOISE RATIO 90dB; FREQUENCY RESPONSE 10Hz-45kHz — 3dB; SUPPLY VOLTAGE \pm 35V
 Size: 114 x 50 x 85mm.
Price £15.84 + £1.27 VAT P&P free.



HY200 120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions, such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — Integral Heatsink — No external components

APPLICATIONS: Hi-Fi — Disco — Monitor — Power Slave — Industrial — Public address

SPECIFICATIONS:
 INPUT SENSITIVITY 500mV
 OUTPUT POWER 120W RMS into 8 Ω ; LOAD IMPEDANCE 4-16 Ω ; DISTORTION 0.05% at 100W at 1kHz
 SIGNAL/NOISE RATIO 96dB; FREQUENCY RESPONSE 10Hz-45kHz — 3dB; SUPPLY VOLTAGE \pm 45V
 SIZE 114 x 100 x 85mm.
Price £23.32 + £1.87 VAT P&P free.


HY400 240 Watts into 4 Ω

The HY400 is I.L.P.'s 'Big Daddy' of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — No external components

APPLICATIONS: Public address — Disco — Power slave — Industrial

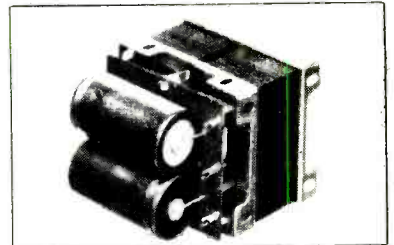SPECIFICATIONS:
 OUTPUT POWER 240W RMS into 4 Ω ; LOAD IMPEDANCE 4-16 Ω ; DISTORTION 0.1% at 240W at 1kHz
 SIGNAL/NOISE RATIO 94dB; FREQUENCY RESPONSE 10Hz-45kHz — 3dB; SUPPLY VOLTAGE \pm 45V
 INPUT SENSITIVITY 500mV; SIZE 114 x 100 x 85mm.
Price £32.17 + £2.57 VAT P&P free.




POWER SUPPLIES

PSU36 suitable for two HY30's £5.22 plus 65p VAT P/P free
 PSU50 suitable for two HY50's £6.82 plus 85p VAT P/P free
 PSU70 suitable for 2 HY120's £13.35 plus £1.10 VAT P/P free
 PSU90 suitable for one HY200 £12.65 plus £1.01 VAT P/P free
 PSU180 suitable for two HY200's or one HY400 £23.10 plus £1.85 VAT P/P free
 B1 48p (plus 6p VAT)

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd
 Crossland House
 Nackington, Canterbury
 Kent CT4 7AD
 Tel (0227) 63218

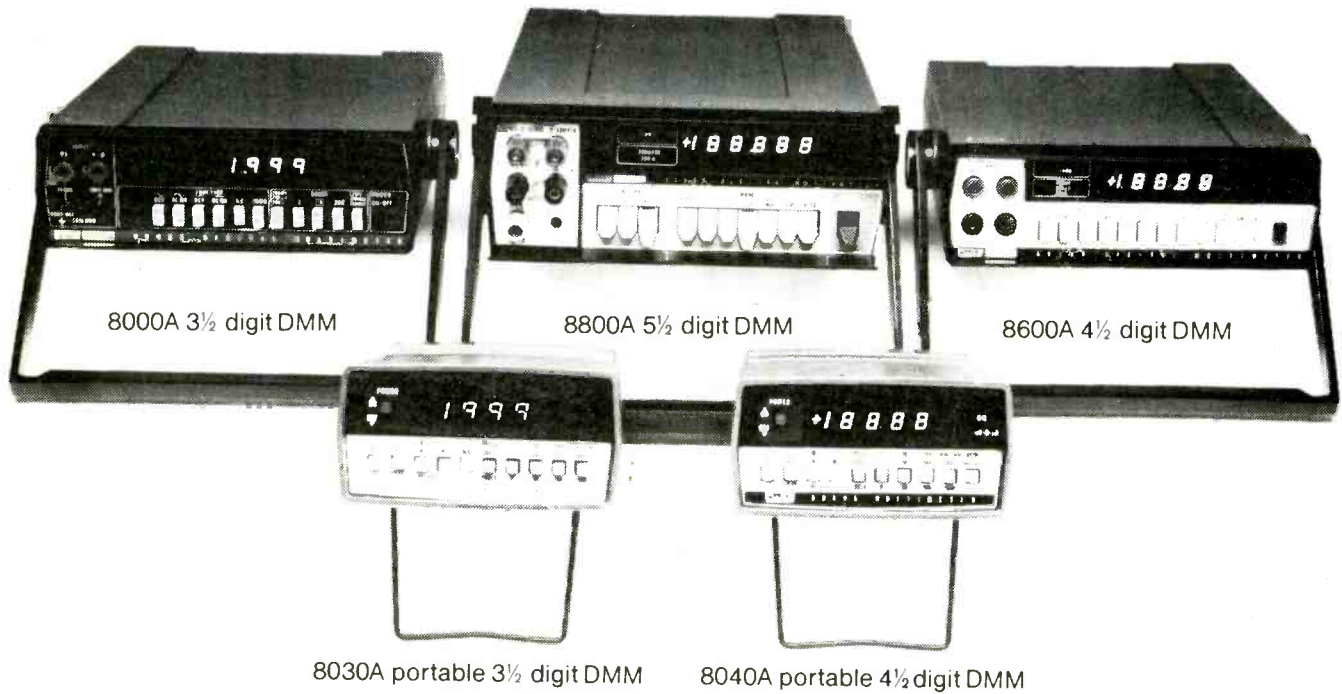Please Supply _____
 Total Purchase Price _____
 I Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclaycard account
 Account number _____
 Name & Address _____
 Signature _____



Lots of people think ITT are the only people selling Fluke DMM's

It's true in one sense – ITT are the sole UK stocking distributors for the range of Fluke DMM's. But of course, as the world's leading DMM's, Fluke really sell themselves. What we do is back them up with a streamlined, thoroughly dependable and quick-off-the-mark service that's as much a No. 1 in its field as Fluke are in their's.

Write or phone for more details.
Edinburgh Way, Harlow, Essex. Telex: 81525

ITT instrument services

**The only way to buy.
Harlow (0279) 29522.**

wireless world

Editor:
TOM IVALL, M.I.E.R.E.

Deputy Editor:
PHILIP DARRINGTON
Phone 01-261 8435

Technical Editor:
GEOFFREY SHORTER, B.Sc.
Phone 01-261 8443

Assistant Editors:
MIKE SAGIN
Phone 01-261 8429
RAY ASHMORE, B.Sc., G8KYY
Phone 01-261 8043
JOHN DWYER
Phone 01-261 8620

Production:
D. R. BRAY

Advertisement Controller:
G. BENTON ROWELL

Advertisements:
PHILIP NOSSEL (Manager)
Phone 01-261 8622

LEO KEMBERY
Phone 01-261 8515

CHRIS PRIER
Phone 01-261 8037

Classified Manager
BRIAN DURRANT
Phone 01-261 8508 or 01-261 8423

EDDIE FARRELL (Classified Advertisements)
Phone 01-261 8508

JOHN GIBBON (Make-up and copy)
Phone 01-261 8353

Publishing Director:
GORDON HENDERSON

The Ernie and Arnie show?

Mr Ernest Harrison, chairman and managing director of Racal Electronics, has been calling for further rationalization of the British electronics industry. It is "bound to come" he declared at a press lunch. And "it won't be too long in coming, I believe". Asked if he had had any discussions with the National Enterprise Board, he replied "Yes, we've all been involved, not just Racal but all the other companies as well". Mr Harrison's main concern is to improve Britain's chances of obtaining big overseas orders. He feels that the present system, of several UK companies bidding competitively, without Government support, fares badly against that of other countries which have their governments assisting one or two large groups. Mr Harrison made it clear what he had in mind, at least for Racal. "We want another group matching GEC" he said. "A bit of competition might be good for Arnold Weinstock, good for his company and good for the country".

In principle rationalization is a good thing. Its purpose is to eliminate wasteful duplication of resources, the splitting in too many ways of capital investment, materials, labour and other factors of production inevitable in normal business competition. It should mean that whatever resources are available in an industry they will all be used continuously and efficiently. And the government, which has to be seen to be even-handed, is much more likely to give diplomatic and financial support to a single large group tendering for an overseas contract than it is to favour invidiously one of several companies in a freely competitive situation.

In practice, however, rationalization means take-overs. These can be achieved by agreement, when the willing "victim" is in a weak financial state, or covertly, by secret buying of shares on the stock market (as Racal started to do with Ultra some months ago). Now one immediate effect of rationalization for merger purposes is

loss of jobs, as happened in GEC, for the improved efficiency required can seldom be achieved without this shedding of labour. With unemployment as serious as it now is in Britain, those considering rationalization of the electronics industry will have to weigh very carefully the certain social consequences against the expected economic benefits.

Another problem inherent in rationalization is that it can create a business monopoly. One could argue that if we had two big groups in electronics, say GEC and Racal, there would be competition between them. Well, there is competition between ICI and Unilever, but no sign that these two giants are fighting each other to the death. Between them they dominate the market for a wide range of household products in Britain. Experience shows that when a small group of companies holds a captive market there is a tendency towards price fixing – remember the telephone equipment "ring" of the 1950s – and the people who work for them feel they are in a safe job, so there is no need to labour hard but just keep one's nose clean. Both of these facts of life are against the interests of the public.

Finally, if an industry is concentrated into one or two big groups that industry is ripe for nationalization. We have just seen the British Aircraft Corporation and Hawker Siddeley Aviation being merged and nationalized into British Aerospace. What this will achieve remains to be seen. But a recent French parliamentary report on their aircraft industry considers that the possible nationalization of Dassault and merging with the already nationalized Aerospatiale to form a single national group would do more harm than good. It would eliminate competition which, the report says, is essential and "exerts a decisive influence on export sales". Maybe there are some experiences here for our electronics industry chiefs to ponder on.

Microwave intruder alarm

Construction of Doppler radar to detect movement

by M. W. Hosking, M.Sc., M.I.E.E., *British Aircraft Corporation*

Based on the Doppler frequency shift principle, this domestic intruder alarm system uses straightforward and simple techniques, together with materials that are readily available to everyone and brings what has hitherto been a costly and professional system within the reach of a domestic budget. Most of the components can also be used to make a simple voice communications link, with the main addition of an audio modulator. Construction of a voice link, including the microwave transmitter and receiver will be described in a later article.

The microwave transmitter and detector circuits are constructed in waveguide. But, for those who do not wish to go to the lengths of building these components, a complete intruder alarm kit is available with these items already built and set to the correct frequency. This complete system has been given type approval by the British Home Office as satisfying their transmission regulations.

General principles

The microwave intruder alarm operates on the principles of a small radar system. It transmits a signal at the appropriate frequency which travels outward as a radio wave until it meets an object, whereupon a portion of the signal is reflected back again toward the receiver. If this returned signal can be detected and suitably processed, then

information can be extracted about the reflecting object.

With the advent of solid-state sources of microwave signals ("Realm of microwaves" *Wireless World* Feb. 1973) the way has opened for very small, cheap, low-power transmitters operating from low-voltage, d.c. power supplies. In this instance, the transmitter is a Gunn diode operating from a 7V rail. The device is encapsulated in a package about the size of a match head, but to control the frequency spectrum and to extract power efficiently, it is mounted in a waveguide resonant cavity. The detector, a Schottky barrier diode, is also waveguide-mounted. Further details, including a method of fabrication for those who wish to build their own will be given in a later article.

If the reflecting object shown in the schematic arrangement of Fig. 1 is moving toward or away from the receiver then, in similar fashion to the train-whistle example usually cited at school, the receiver frequency will differ from that transmitted. The difference between the two is the Doppler frequency. In addition to the directly transmitted signal, a small portion is arranged to couple directly into the receiver and acts as a local oscillator drive. The returning frequency-shifted

signal at frequency $f_o \pm f_d$ is thus mixed with this local oscillator at frequency f_o and the output circuit bandwidth adjusted to extract the beat frequency difference, f_d .


The creation of a Doppler shift in frequency can be visualized by considering the two waveforms in a little more detail. As the transmitted signal moves out, with its amplitude varying sinusoidally, its phase angle relative to the starting point will change by 2π radians (360 degrees) every time the distance increases by a wavelength. In this case, the wavelength is about 28mm. Exactly the same thing is happening to both the returning signal and to that forming the local oscillator. These two are mixed together in the diode to form the beat or difference frequency.

The amplitude at this i.f. is a phase function of the two input signals. If the path, $2R$, traced by the reflected signal was half a wavelength different than that taken by the direct local oscillator wave, then the two would subtract at the receiver. The output would not actually go to zero, as the two signals are not normally comparable in amplitude, but would be a minimum. Conversely, when both inputs had traversed an integral number of whole wavelengths, they would combine in phase to produce an i.f. output of maximum amplitude. If the reflecting object happens to be moving, then the relative phase of the two inputs is also changing. The local oscillator path remains constant, but the path taken by the radar signal is varying at twice the reflector speed, $2V$ m/s.

Back at the mixer, the effect is as if the two wavetrains were sliding past each other at $2V/\lambda$ wavelengths per second to produce an alternating output voltage at this rate as they reinforced or subtracted from each other. This is the Doppler frequency $f_d = 2V/\lambda$.

To comply with the regulations, the transmitter must operate at 10.687GHz i.e. $\lambda = 28.07$ mm. Thus, the Doppler frequency is 71.25Hz for each m/s of reflector speed, or 31.85Hz per mile/h. Fig. 2 shows this relationship in graphical form.

Fig. 1. Principle of the c.w. Doppler radar wherein the transmitter is also the local oscillator.

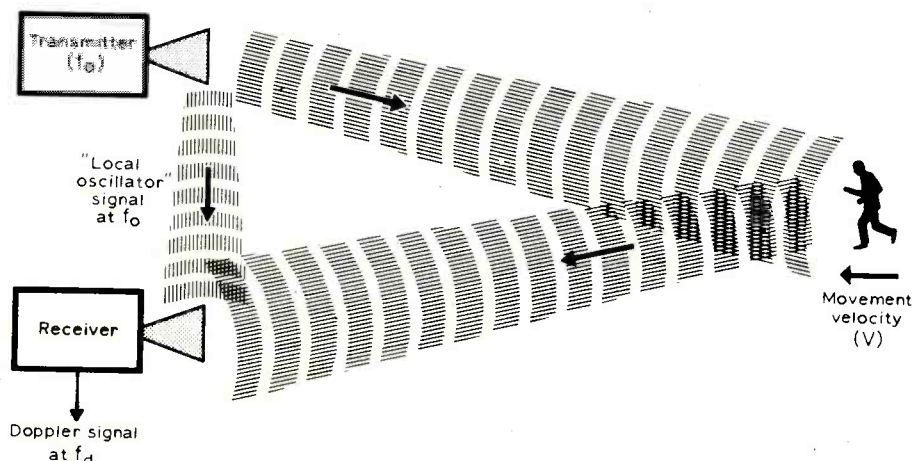

Extraction of this Doppler signal can be used as an efficient means of detecting a moving object against a stationary background. For use as in intruder alarm, the reflections from walls and furniture will all be stationary in phase difference and so will produce no alternating beat frequency, whereas a moving object will generate an i.f. typically in the low audio range. This signal can then be amplified and used to trigger an alarm. This type of system thus gives the type of selectivity that is required and, operating as it does in this relatively uncluttered area of the frequency spectrum, is not so vulnerable to interference. There are no beams to break, as in some systems, as the signal fills the whole room and movement anywhere can trigger the alarm. Nor is it sensitive to spurious acoustic noises as are another class of alarm systems. A gain control on the alarm allows the triggering threshold to be adjusted to suit the size of room and the reflecting target, i.e. to choose the larger reflection from a human as opposed to that from the domestic pet.

Transmitter and receiver

The general design of the transmitter and receiver cavities for the ready-made Mullard CL8960 unit are shown in Fig. 3(a) and Fig. 3(b) the schematic electrical connections. The operating frequency is controlled by the length of the transmitter waveguide between the Gunn device and the back wall. However, insertion of the tuning screw perturbs the field within the cavity in such a way as to appear initially as an inductance and to lower the resonant frequency $f \propto \sqrt{L/C}$. The side-by-side arrangement is to allow coupling of the local oscillator signal which occurs by direct leakage into the receiver waveguide. However, the level of signal is very low at about $10\mu\text{W}$ and a small amount (30-35 μA) of forward bias is necessary on the mixer diode.

Some precautions are necessary when making the electrical connections to avoid damage to the microwave semiconductor devices. The mixer diode

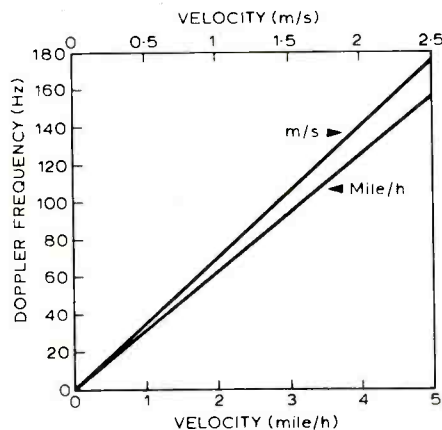


Fig. 2. Graph shows how the Doppler frequency varies with target speed for the case of a transmitter at 10,687MHz.

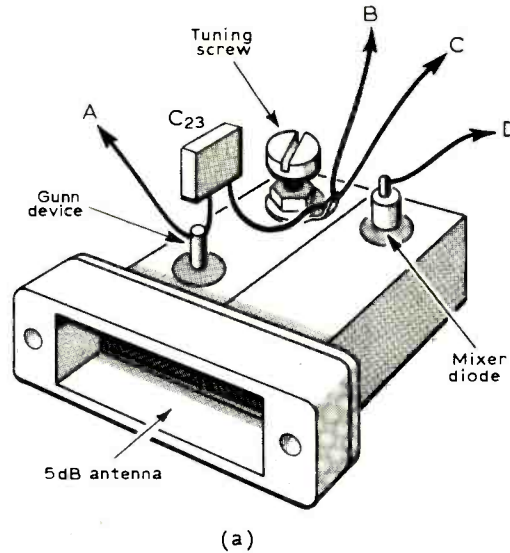


Fig. 3. General view of the Doppler module (a) and schematic electrical connections (b)


is easily damaged by voltage transients on the mains supplies, so it is recommended that soldering appliances be disconnected from the mains just prior to making the mixer connection and during any subsequent contact with this component. Forward bias should not be allowed to exceed 1 mA. The Gunn device will not tolerate a reversed supply voltage, so check before connecting. As supplied, the mixer is fitted with a shorting wire to the case and this should be left in place until assembly is finally completed and then removed. The Gunn device appears as a dynamic negative resistance and it is possible for oscillations to be induced in the supply circuit. To avoid this, connect a small 10nF capacitor directly across the terminals as shown in Fig. 3(b).

- General conditions of operation for the assembly are:
- Frequency 10,687 ± 12 MHz (preset)
- Gunn device supply voltage + 7.0 ± 0.1V (+7.5V max.)
- Gunn device supply current 130 to 165mA (140mA typ.)
- Mixer diode forward bias 30 to 34 μA .
- Power output 8mW typ. (10mW max.)

The microwave module is supplied with a small, 5-dB gain antenna, constructional details of a 20dB gain horn will be given later. The magnitude of the Doppler output at the mixer terminals is a function of the size of the reflecting object and its range. Typically, however, a man would have a radar cross section of 1m² and, using the 5dB antenna, the received signal would be 100 dB down on that transmitted at a range of 15m. This will produce about 40 μV of Doppler signal for signal-plus-noise to noise ratio of 18dB.

Fitted with the 5dB gain antenna, the Doppler module is reasonably matched to free space and has a polar pattern of the form shown in Fig. 4. The wide-beam coverage together with the filling-in effect from multiple reflections

Fig. 4. Beamwidth of the Doppler module in two planes using the 5dB antenna which illustrates the wide angular coverage obtainable.

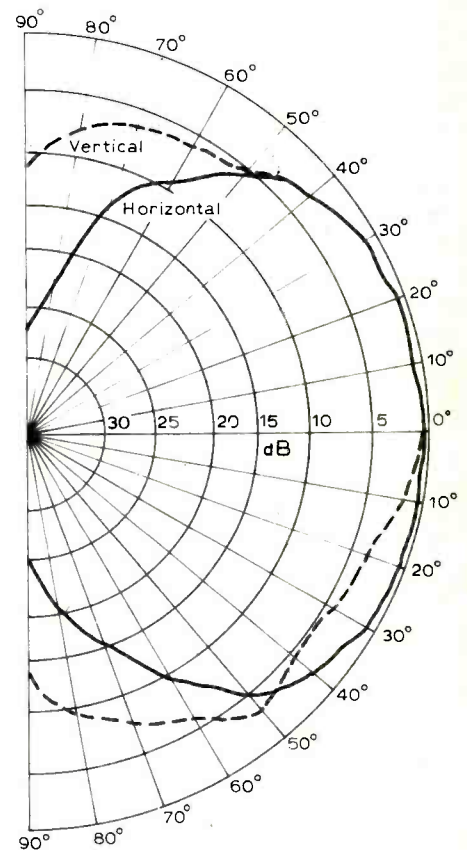


means that comprehensive coverage of a room is effectively achieved.


An interesting game has evolved at home: in a room about 30ft long, children endeavour to creep and crawl up on the intruder alarm without being detected. No matter how subtle the approach, this has not so far been achieved without triggering the alarm.

Receiver and alarm

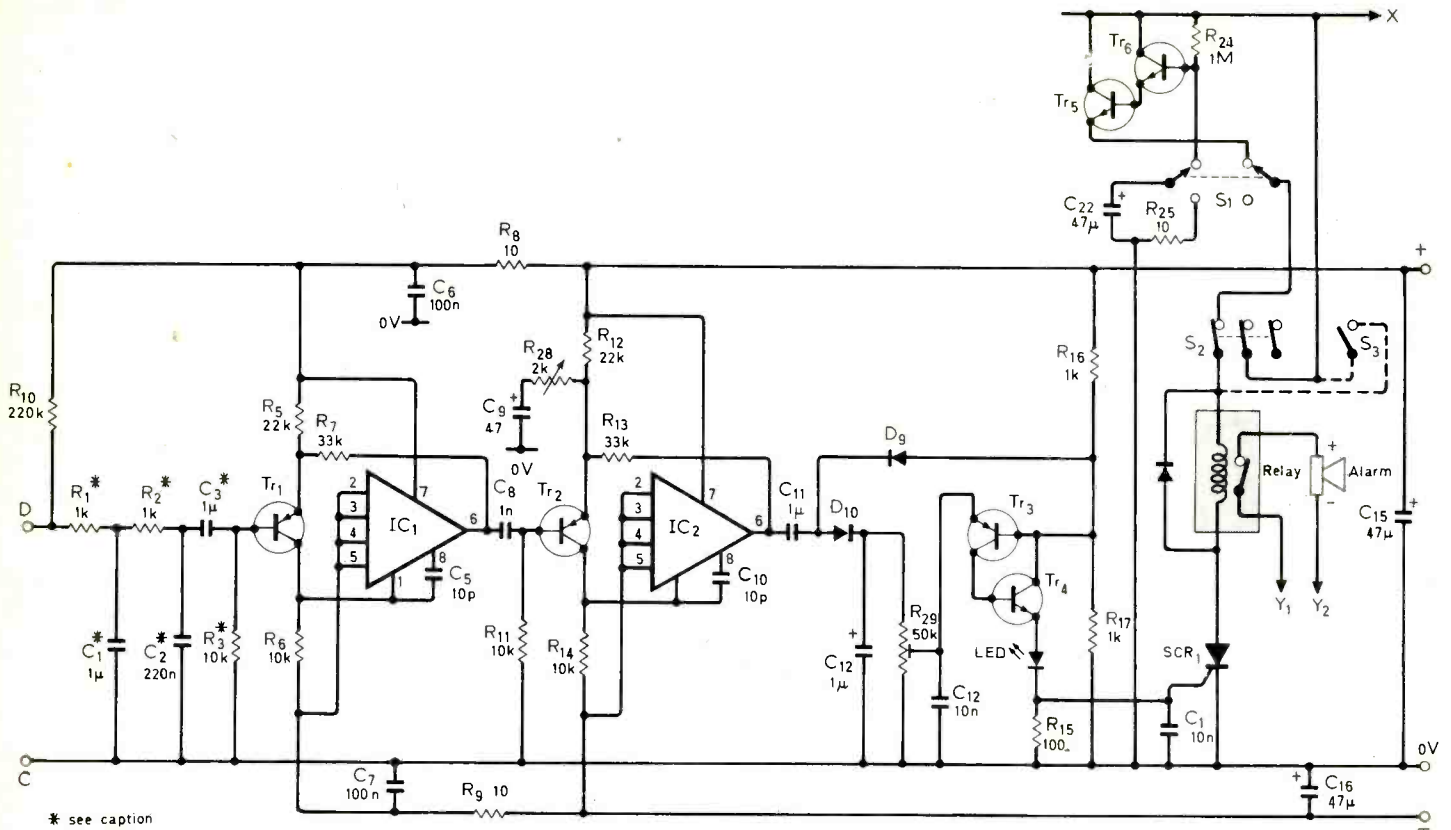It is necessary to selectively amplify the Doppler signal to a level sufficiently high to trigger an alarm, whilst at the same time rejecting false alarms from spurious noise levels (Fig. 5).



* see caption

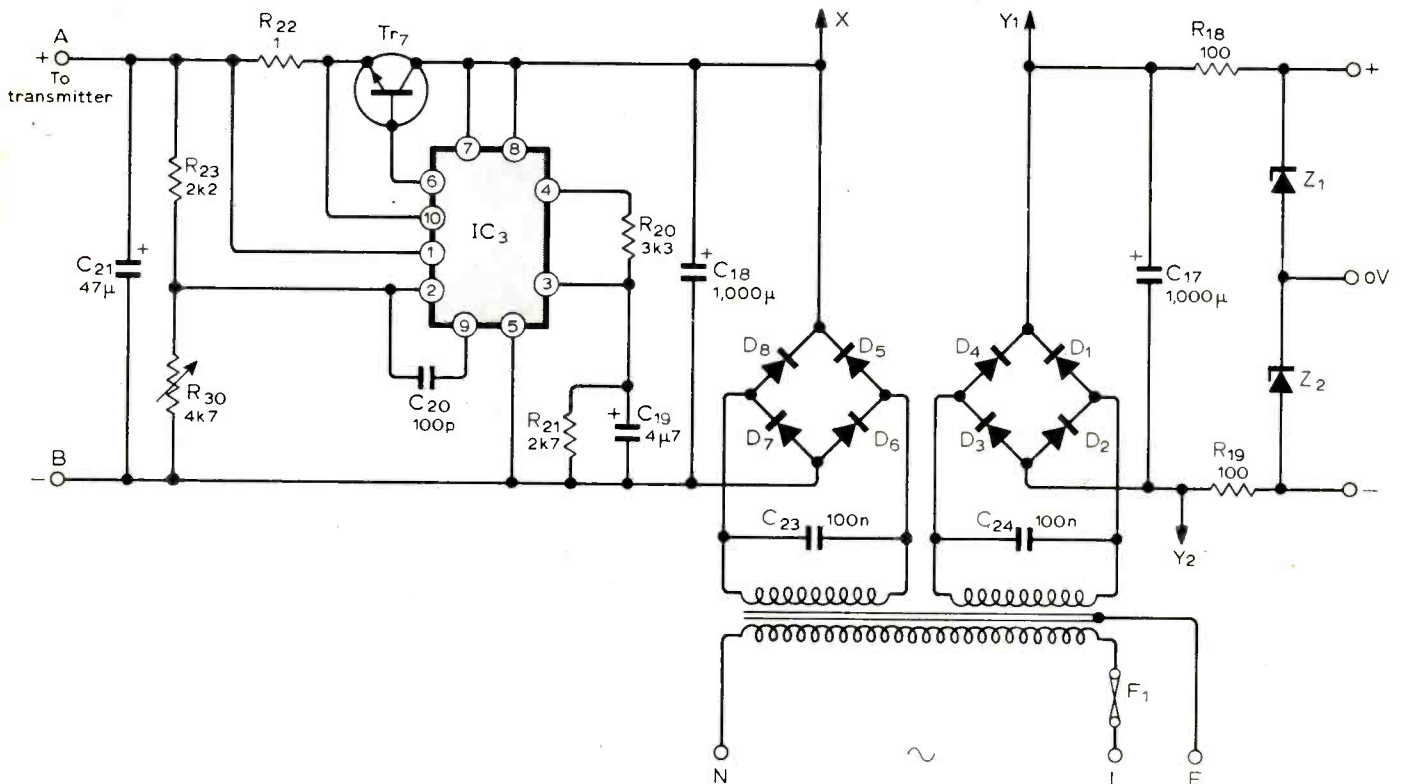

More conventional circuits could be used for the amplifier, but the intruder system has been developed side-by-side with a voice link and as much commonality as possible has been built into the two systems.

Sensitivity of the Doppler receiver is a function of the i.f. amplifier input noise figure and bandwidth. The narrower the bandwidth, the less the contribution of

Fig. 5 (top). Amplifier and alarm trigger circuit with power supply (bottom) to p.c.b. and transmitter.

Components marked with an asterisk may have different values in the kit design.

thermal noise power. Thus, the first section of the circuit is an RC filter having the measured bandpass charac-

teristic of Fig. 6. The combination of Tr₁ and IC₁ provide a first stage voltage gain of about 1000, together with a reasonable input noise figure. The slightly unusual connections to the operational amplifier are mainly for the benefit of the voice link receiver, as they provide a means of achieving a high slew rate from a normal 748 op-amp by by-passing the input stages.

Resistors: ¼-watt rating except where indicated.

R ₁	1kΩ	R ₁₆	1kΩ
R ₂	1kΩ	R ₁₇	1kΩ
R ₃	10kΩ	R ₁₈	100Ω
R ₄	33Ω	R ₁₉	100Ω
R ₅	22kΩ	R ₂₀	3.3kΩ
R ₆	10kΩ	R ₂₁	2.7kΩ
R ₇	33kΩ	R ₂₂	1Ω
R ₈	10Ω	R ₂₃	2.2kΩ
R ₉	10Ω	R ₂₄	1MΩ
R ₁₀	220kΩ	R ₂₅	10Ω, ½ watt
R ₁₁	10kΩ	R ₂₆	56Ω, 5 watt
R ₁₂	22kΩ	R ₂₇	1kΩ
R ₁₃	33kΩ	R ₂₈	2kΩ
R ₁₄	10kΩ	R ₂₉	50kΩ
R ₁₅	100Ω	R ₃₀	4.7kΩ

General

Transformer 6VA miniature. Two independent 12V, 0.25A secondary windings with interwinding screen.

Relay 18V, 1kΩ coil with internal diode. Contacts rated 250mA, 50V.

Alarm 18V audible warning device, 60mA mean current, 1A peak.

F₁ 500mA mains fuse

S₁ miniature d.p.d.t.

S₂ 3-pole screened jack plug and socket

S₃ s.p.s.t. on/off

Doppler module Mullard CL8960 or approved alternative.

Self-oscillating mixer Mullard CL8630S or approved alternative.

Capacitors

C ₁	1μF	C ₁₄	10nF
C ₂	0.22μF	C ₁₅	47μF, 10V
C ₃	1μF	C ₁₆	47μF, 10V
C ₄	47μF, 10V	C ₁₇	1000μF, 25V
C ₅	10pF	C ₁₈	1000μF, 25V
C ₆	0.1μF	C ₁₉	4.7μF, 10V
C ₇	0.1μF	C ₂₀	100pF
C ₈	1μF	C ₂₁	47μF, 20V
C ₉	47μF, 10V	C ₂₂	47μF, 20V
C ₁₀	10pF	C ₂₃	0.1μF
C ₁₁	1μF	C ₂₄	0.1μF
C ₁₂	1μF, 16V	C ₂₅	47μF, 10V
C ₁₃	10nF	C ₂₆	10nF

Semiconductor devices

Tr _{1,2,3}	ZTX 500 or equivalent
Tr _{4,5,6}	ZTX 302 or equivalent
Tr ₇	Plastic style 3055
IC _{1,2}	SN72748 or equivalent
IC ₃	μA 723 or equivalent
D ₁ to D ₈	1N4001 or equivalent
D _{9,10}	1N914
SCR ₁	TIC44 or equivalent
LED ₁	small red
Z _{1,2}	BZY88-C8V2

Suppliers

The system built around the CL8960 module can be obtained as a kit of parts or in ready-built form — see advertisement by Integrex.

Both kit and ready-built system have been given type approval by the Home Office for internal use on premises, under the type name Intruder 1 and have undergone thorough performance and reliability testing.

A set of two p.c.bs is available for £4 inclusive from M. R. Sagin, 23 Keyes Road, London NW2. One board accommodates the intruder alarm circuit together with the power supply components, and the second board accommodates the voice link circuit.

as providing a daily check on the system.

An alternative uses the jack plug and socket arrangement. Inserting the plug by-passes the delay circuit and allows the alarm to be set by a remote switch taken out of the room and located at some convenient point. The circuit has been tested with over 100ft of flex between alarm and switch. Whichever method is used, once fired, the s.c.r. and hence the alarm will remain on until reset by the appropriate switch.

To be concluded

An end to listen-only answering machines

The proliferation of telephone answering machines is likely to advance even more rapidly if a device made by LMG Electronics gains wide acceptance. Normally the user of one of these hideously unsociable devices has to travel back to his office in order to hear the rude things people have shouted into it, but the LMG system enables an accredited caller to dial into the machine from a distant telephone and hear the messages over the phone.

According to an article by the company's founder, Mr Graham Bent, in *NRDC Bulletin* number 45 the idea is not new "but operation hitherto has been cumbersome, and only a single rewind could be initiated." The LGM device controls stop, start, rewind, playback and erase on the answering machine by means of coded pulses of tone generated by the user on a distant phone. The audible tone pulses are produced by a pocket unit the interrogator holds against the mouthpiece of the telephone he is using. One control button provides an operating code of five trains of pulses. Only this pulse can open the machine to remote operation. "There are over 40,000 possible combinations," the article says. Once the recognition code has been established the machine receives short common pulse trains enabling control of the machine from four buttons. The unit is powered from a 9V battery which should last 12 months.

When LGM approached the National Research and Development Council they asked for £3,000 repayable over 12 months but the NRDC thought they were being optimistic and lent them £4,000 repayable over three years. The loan was unsecured at 20% instead of the more usual royalty on sales. In addition the firm had £5,000 of Bent's money and a similar amount from the bank. That was in 1972. The NRDC loan was repaid "A few months ago," according to Graham Bent.

The second amplifier provides a good voltage gain which can be varied with the potentiometer R₂₈. The diode pump and clamping circuit of C₁₁, C₁₂, D₉ and D₁₀ defines the voltage threshold and time constant necessary to switch on the Tr₃, Tr₄ Darlington drive to fire the s.c.r. Potentiometer R₂₉ provides additional control of the drive level and the l.e.d. gives a visual indication of each time that a trigger signal is generated. It is also used for initially setting the maximum gain that can be obtained from IC₂ before any instability occurs.

In the prototype, the alarm itself is an 18V audible warning device which emits a penetrating, modulated wail at about 3kHz. However, as the alarm trigger takes place through a relay, it would be a straightforward matter to connect up to other warning devices such as a door bell, or to add an extra feature such as camera and flash unit.

Assuming that the intruder alarm will be fitted in a room or hallway of domestic premises, it is obviously necessary that the circuit should be activated when everybody is out of the way, otherwise one's own movement would trigger the alarm. Two options are provided in Fig. 5 for achieving this. Firstly, the positive supply rail for the s.c.r. and relay is routed via the Tr₅, Tr₆ combination, so that sufficient current to operate the relay can only flow when Tr₅ and Tr₆ are switched on. This can

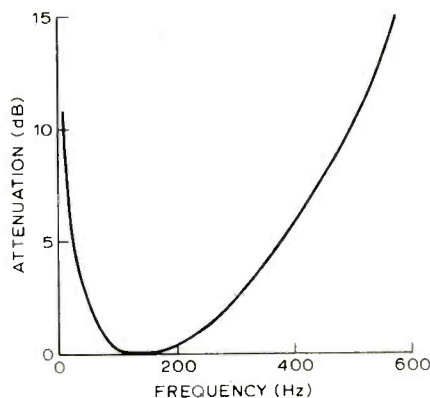


Fig. 6. Typical input filter response for the amplifier showing emphasis placed on the Doppler frequency from slow-moving objects.

only occur when C₂₂ has charged through the high resistance path of R₂₄. Thus, when the overall system is switched on, the Doppler module, amplifiers and supply rails are all activated, but the relay will not operate to trigger the alarm until after a short delay. This delay is set by the timeconstant of R₂₄ and C₂₂ which, in this case has been chosen as 45-60 seconds: ample time to leave the room and close the door. Using this method, the alarm will be triggered on re-entering the room, say the next morning. If this was acceptable, then it could be looked upon

Kinetic images from sound

American developments in a modern art form

by Thomas E. Mintner, *University of Iowa*

With the advent of certain technologies such as video, lasers and integrated electronic circuitry the contemporary artist or composer has resources available which allow forms of expression unheard of as little as fifteen years ago. One obvious example is the field of electronic music, where the proliferation of synthesizers and similar devices has resulted in a deluge of electronic music studios, compositions, live performances and commercial applications. A related area is concerned with devices and compositions designed to take advantage of simultaneous presentation of music with light and images.


Historically, this area ranges from essays on "colour music"¹ dating from the early part of this century to devices utilizing the latest technology. Now, as in the past, efforts in this area come not from any one discipline, but from composers, artists and sculptors, engineers, dancers and architects. Technologically, there is a wide span from simple colour light boxes to video or laser devices incorporating advanced combinations of electronic and electro-optical techniques. This article is not intended to be a comprehensive listing

of all such aural/visual devices or works, but rather an overall view with detailed information on some projects with which the author has been associated.

If there can be one conclusion drawn from most of the artistic attempts at correlation of audible and visual information, it is that effective and natural co-ordination is difficult to achieve.

Although some early attempts were severely hampered by a lack of suitable technology, there is a still more basic problem. The fundamental differences in the two sensory systems involved are many. Since our senses of sight and hearing tend to complement each other in day-to-day activities, we may tend to overlook the many perceptual differences which must be confronted when we attempt to create a set of stimuli (a composition) that will utilize both senses together. Investigation of these

Fig. 1. One method of deflecting a laser beam by a sound source: a small mirror is attached to the loudspeaker cone. The laser beam is further modified by passing it through a clear diffuser.

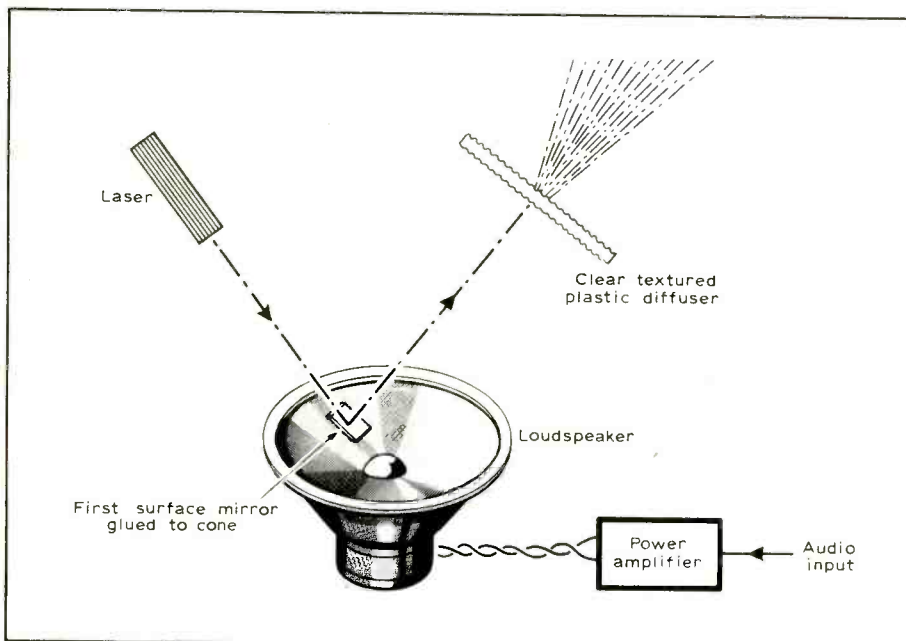

two sensory systems is still at the level of basic research and modelling for even relatively simple stimuli. Complex signals such as music or visual arts can also be analysed in terms of their content, both from the point of view of their respective disciplines (e.g. music theory) and from the more general basis of information theory.

Given these facts, it is not hard to understand the limited success of early "colour organ" type efforts at music-light correlation. Generally, it was assumed that there would be some sort of fixed relation between the colour spectrum and the musical scale (12 note), with perhaps differences in colour intensity used to represent octave displacement of pitches. There were also numerous other schemes, all with similar problems. However, it should be noted that at least one major composer wrote an orchestral work, still performed and recorded, with a notated part in the score for "tastiera per luce" or keyboard of light. This is A. N. Scriabin's *Prometheus, The Poem of Fire* (1909-10). Scriabin's correlation theories are somewhat more interesting than those above, and in fact a modern realization of his composition has been performed.

Colour organs, along with the pioneering work of artists such as Thomas Wilfred, who was the originator of the Lumia (or light box) in art, are part of a broad range of efforts relating more to colour than image. With the development of the cathode-ray tube it became relatively simple to generate visual image analogues to sound and music through the use of X-Y display techniques. This involves routing two sets of signal information or two similar components of the same information (e.g. left and right stereo channels of recorded music) to the vertical and horizontal inputs respectively of a cathode-ray tube. As early as 1953 an American artist exhibited his Oscillons - images created by photographing specially generated signals fed to a c.r.t.²

In the mid and late 1960s there was increased development of new techniques. Lowell Cross described his experiments and compositions with

X-Y display art as a kinetic form with music in articles for *Source* magazine.^{3,4} The use of this type of display as an adjunct to electronic music allowed for another level of interest in a live or taped performance. Although the analogues produced with these methods are not necessarily the only way to interface the elements of sound and visual information, they are generally effective, and have been used in many works in recent years. Cross progressed from oscilloscopes to specially modified television sets and eventually to laser deflection systems, as we shall see later.

During the same period, various artists and composers began experimenting with video imagery. One technique which was "discovered" for artistic purposes was video feedback. In its simplest form, a camera is pointed at the video monitor that it is feeding. As in the familiar situation in audio, oscillations are set up because of the relatively uncontrolled feedback path. By controlling this path, it is possible to use feedback as a versatile method of image generation. Various limiting and processing devices may be inserted into the feedback loop to modify and control the images. The author's introduction to this method was in 1969 in work with Glenn R. Sogge and Timothy Skelly, both composers and artists. At that time, considerable effort was sometimes necessary to convince studio supervisors that video feedback experimentation under controlled situations would not necessarily leave the video chain in flames! However, once this was done, it became possible to present a series of concerts/events with specially generated video imagery and electronic music.

Up to this point there was no actual electronic interface between the two domains. The initial attempt in this direction, which was moderately successful, was as follows. Oscillators being used in the generation of musical sounds were connected and mixed so that their outputs were fed to a balanced modulator as well as to their normal destinations. These oscillations were then modulated with a frequency high enough that the upper sidebands were in a video frequency range. The output of the modulator was then sent through an encoder to produce a composite video signal. In the intervening years various video processors and "synthesizers" have been developed using i.c. technology and methods borrowed from electronic music. Composers, film-makers, and video artists are continuing to experiment in this area.

One example of such experimentation from the Center for New Performing Arts of the University of Iowa is the Video Colour Quantizer System. The basic system is a modification of a standard unit manufactured by Colorado Video, Inc., an American firm. Franklin Miller, a film-maker at the university, started the experimentation

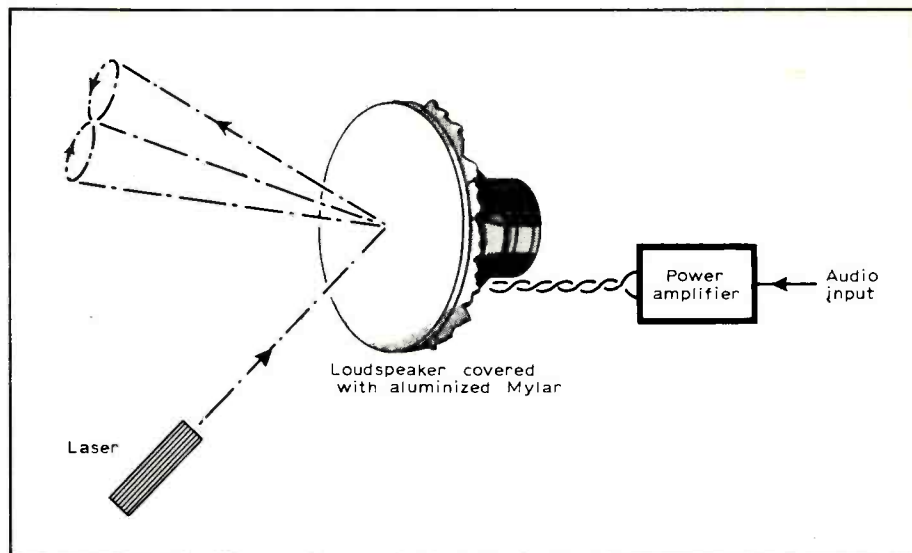


Fig. 2. Method of laser beam deflection used in the Sonovision system.

with this unit. Basically the quantizer is a device which accepts a monochrome video signal and has sixteen adjustable signal comparator thresholds relating to the amplitude of the video signal. At these various levels from black to white along the grey scale, sixteen points can be set to trigger production of sixteen different pre-assigned, synthetically generated colours. With the colour mixing unit incorporated in this version any combination of colours may be set to allow modifications such as synthetic colour generation, grey scale reversal and other effects.


A recent grant has allowed the design and construction by the author of a voltage control interface for the quantizer system. With this interface the sixteen threshold points, or "slice levels," can be determined by the application of a d.c. or a.c. control voltage. This means that a colour assigned to a given grey level range may be made to change with the applied voltage, or that a threshold can be shifted electrically to alter (by colour addition) several other colour areas in the image. In addition, the master outputs of red, green, and blue can each be gated with a control trigger. Signals routed to this total of nineteen control inputs may be used directly, as in the case of electronic music, or may be generated from other music through the use of an amplitude detector or a pitch-to-voltage converter. Another performance possibility is to use control signals derived from other than musical sources, or to split the allocation of control inputs, with some control voltages coming from musical material, and some from other sources, such as devices sampling video signals or sensors attached to dancers. As a part of the grant programme, two colour films are to be produced, one by the author, and one by Peter Tod Lewis, composer and director of electronic music at the

University of Iowa. These films will have specially composed sound tracks to control the video colour quantizer interface.

Another interface project is a work realized by West Coast US artists and engineers Bob Watts, Bob Diamond and David Behrman. The work, called the *Cloud Music*, uses a video camera trained on the sky during daytime periods. As clouds pass into the field, the changing video signal, sampled at various cursor points on the screen, controls a system by composer David Behrman which produces electronic music "on the spot." The piece functions as a kind of performing sound sculpture (depending, of course, on the weather).

Shortly after small lasers became commercially available, artists began experimenting with them in a variety of ways. The laser light itself is the object of some of these investigations. The highly collimated beams lend themselves to a variety of illumination tasks, including large outdoor geometric constructs using the stationary beams of high power lasers. On the question of light and sound correlation, however, we find that most uses of lasers involve methods of scanning the beam. Various approaches have been tried, and the most sophisticated systems in use today use galvanometer mirror scanners to produce X-Y scanning. Thus we find that principles of music-light correlation applicable to oscilloscope type displays find a new and much larger scale medium in X-Y laser scanning.

In addition to this simple X-Y scanning there are other techniques which are sometimes combined with X-Y systems. By passing a laser beam through an uneven glass or plastic surface, for example, one can generate patterns of a "cellular" nature which results from the interference of the laser light with itself as it passes through the material. If the beam is deflected slightly as it passes through the material, kinetic images related to the deflection signal (e.g. music) may be generated. One of the deflection methods which

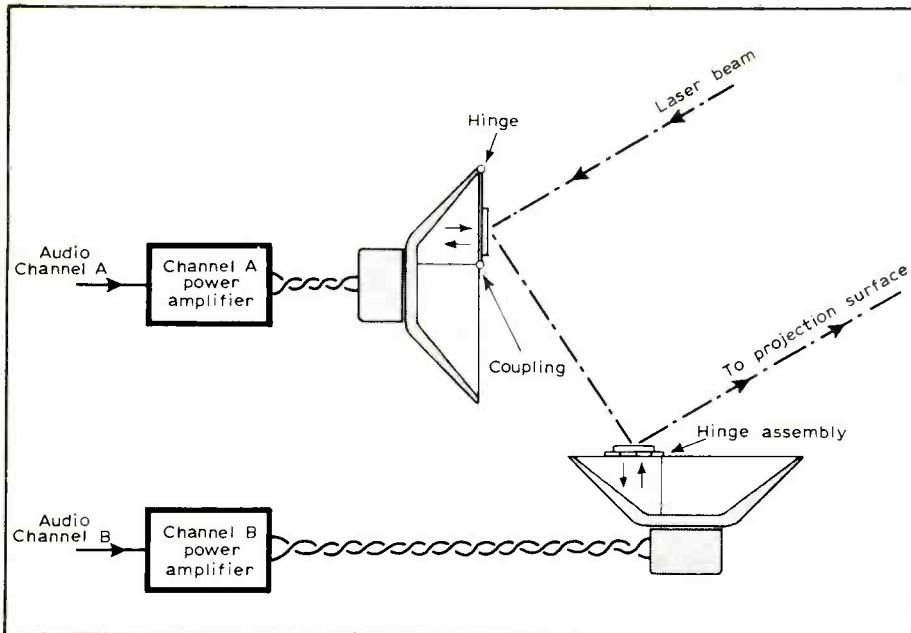

could be used in this application involves attaching a small first surface mirror to a loudspeaker (Fig 1). A signal fed into the speaker will cause the mirror to move and deflect the beam. An early experimenter in this area was Lloyd Cross (not to be confused with Lowell Cross), who developed a system called Sonovision⁵ using a loudspeaker covered with a reflective membrane (Fig. 2). In addition, the system, which was intended to be commercially available, had a rotating prism assembly for generating more complex multiple images. A slightly more useful version of this idea uses two loudspeakers (Fig. 3), each of which has a hinged mirror assembly connected to the cone. The hinges restrict the movement of each mirror to one axis. Thus a simple X-Y scanning system is formed. The deflection is limited to relatively low frequencies and the system response is not at all linear because of the many mechanical resonances.

More sophisticated X-Y scanning systems use commercially available galvanometer mirror scanners. The first such system assembled for the artistic purpose of exploring kinetic inter-relationships between light and sound was Video/Laser I, an experimental laser deflection system initiated by Lowell Cross, Carson Jeffries and David Tudor at Mills College, USA. This was in May 1969. Soon after, another such system was commissioned for use in the Pepsi-Cola Art and Technology Pavilion at the 1970 World Exhibition in Osaka, Japan. Both of these early systems have been dismantled. However, Video/Laser III, the latest system constructed by Cross and Jeffries for the Center for New Performing Arts at the University of Iowa had its premiere in a concert with orchestra on November 29, 1972.⁵ Improvements and additional electronic control devices are being added on a continual basis by Lowell Cross and the author.

The system used is as follows. The

Fig. 3. Beam deflection system using two loudspeakers, each with a hinged mirror moved by a connecting member attached to the cone.

output beam of a 2-watt krypton-argon laser is split into its component beams. This is achieved by passing the initial greenish-white output beam through a direct vision prism. Any four of the approximately sixteen available colours may then be selected and routed to the four beam deflection systems. Each system contains a beam chopper/interrupter and two mirror scanners for deflection (X and Y). Each deflection component of each channel has its own direct coupled amplifier, and any audio signal may be fed to the systems. The devices used have certain frequency response limitations because of necessary compromises between maximum scanning angle and frequency response.

The maker of the scanners, General Scanning, Inc., through a subsidiary, is now involved in X-Y scanning systems for artistic purposes also. One such system, called Skywriter, is designed with X-Y inputs and an accompanying vector generator system to produce a variety of line images, including a kind of animation.

Multi-colour laser systems using large lasers are capable of creating extremely large images on any suitable projection surface, indoors or out, though generally the area must be in relative darkness for best results. The Video/Laser III system mentioned above is used in a variety of performance situations, often with electronic music as a sound source. It is conceived of as an experimental performance and research instrument.

One fairly recent performance with the Video/Laser III system may demonstrate how the original art of "colour music" has progressed to its current position. A performance of A. N. Scriabin's *Prometheus* was given on

September 24, 1975, with the laser system functioning to realize fully, perhaps for the first time, Scriabin's wishes for the keyboard of light. A specially constructed keyboard interface was used, with a performer playing the written part as indicated in the orchestral score. The keyboard controlled the gating of the various colours, while the images were generated both directly from the orchestral sound and also by electronic means with auxiliary equipment. In addition to the lighting effects, fog and various scents were present in the hall at appropriate points in the performance.

This unusual meeting between the latest technology for realization of one type of kinetic music/light performance and the ideas of one of the earliest and most interesting proponents of this art form may serve as an appropriate point to conclude this brief survey. However, work involving video, lasers, and other systems for the realization of this very old dream of "music light" will undoubtedly be continuing for years to come.

References

1. A. Wallace Rimington, *Colour Music: The Art of Mobile Colour*, Hutchinson & Co. 1912.
2. Ben Laposky, "Oscillons: Electronic Abstractions" *Kinetic Art: Theory and Practice*, Dover Publications 1974.
3. Lowell Cross, Carson Jeffries, David Tudor, "Audio/Video/Laser," *Music of the Avant Garde*, issue No. 8.
4. Lowell Cross, "Musica Instrumentalis-Video II(b), Video II(c), VideoII(1) *Music of the Avant Garde*, issue No. 9.
5. S. R. Wagler, "Sonovision: A Visual Display of Sound," *Kinetic Art: Theory and Practice*, Dover Publications 1974.

The front cover of this issue shows examples of projected multi-coloured images produced by the Video/Laser III equipment described by the author.

Teletext a permanent service?

Officials of the British Radio Equipment Manufacturers' Association estimate that there should be about 12,000 teletext receivers in operation by the end of this year. This figure will include purpose-built sets by British manufacturers, existing colour TV sets fitted with external teletext adaptors, and sets with external decoders similar to the *Wireless World* design. BREMA members are hoping to get the price of sets down to about £750 to £800.

The set makers are anxious for a statement from the government that teletext, at present an experimental service, will soon be established as a permanent public service. Unless this happens they seem unlikely to achieve any substantial sales to the public. Sources close to the Home Office hint that such an announcement could come in the autumn of this year.

Surround sound decoders — 6

Multi-system ambisonic decoder

1 — Basic design philosophy

by Michael A. Gerzon, M.A., *Mathematical Institute, Oxford*

This series of articles describes a decoder capable of decoding all major existing and proposed two-channel surround-sound systems, including the Ambisonic System 45J, SQ, Regular Matrix, BMX and BBC Matrix H. For systems other than SQ, the decoder gives full psychoacoustically optimized results using NRDC Ambisonic decoding technology. In addition, Ambisonic playback of mono, stereo and of three-channel studio-format signals is provided. The decoder is suitable for three-amplifier/four-speaker, four amplifier/four-speaker, and four-amplifier/six speaker reproduction.

The NRDC Ambisonic project has developed a comprehensive technology for creating, encoding and decoding sound¹⁻⁴. While this ambisonic technology can give of its best only with optimized programme material and encoding (i.e. the System 45J described in reference 1), the methods can be applied to getting improved results from nearly all existing surround-sound systems. Later articles in this series will give the detailed circuit and some constructional details for a decoder for all the above-listed two-channel systems. As this decoder does a great deal more than any previously-published decoder designs, it is necessary to describe its many facilities in some detail, as well as giving some idea of what the circuitry is intended to do.

The aim of any surround-sound decoder is to provide the listener with an illusion of sounds coming from all (horizontal) directions around him. Moreover, if the decoder is well designed, the directions should be those intended by the recording engineer, and should be heard by a listener through the usable listening area. Conventional "quadraphonic" decoder designs give very poor images for sounds in inter-loudspeaker directions, especially at the sides, resulting in a rather gimmicky 'ping-pung-pang-pong' effect at the four corners.

The full theory used to design ambisonic decoders is mathematical, and computing facilities are required to

carry out the extremely complex design calculations involved. It is clearly not possible to give full details here of why the various parts of the decoders have the exact values that they do, but some idea of what is going on can be given.

Two previous articles in *Wireless World*^{1,5} have described some, but not all, of the psychoacoustics lying behind ambisonic decoder design. Essentially, the ears use different methods of localizing sounds, not just one or two. The more of these hearing mechanisms that are satisfied the better the sound and accuracy of the result. In particular, if a decoder satisfies several different methods of hearing, the brain has to do far less work to unscramble the complex sound reaching the ears, and the result is particularly "relaxed" listening, with little listener fatigue. While the mathematics of the design is aimed at getting accurate sound localization for all directions, it is undoubtedly true that the biggest musical benefit comes from this consequent low listening fatigue, rather than from any ability to "shoot the pianist".

Some aspects of sound that ambisonic decoders are designed to optimize are now described. At low frequencies, below 500 or 700Hz, there are three important aspects of sound localization: the "Makita" direction of a sound (the direction one turns to to face the apparent sound direction), the "velocity magnitude" (the degree to which the sound stays in its correct localization as one turns to other directions), and the "phasiness" (the degree to which unwanted components of sound not in phase with the desired sound are heard). It turns out that for all systems other than SQ, it is possible to design a decoder matrix below 700Hz to get the Makita localization correct for all encoded sound directions. In addition, a careful adjustment of the gain of the various signal components in the decoder permits the velocity magnitude to be made correct also. Thus, at low frequencies, a listener will hear all directions correctly reproduced in direction, no matter which way one faces.

Phasiness is more of a problem with two-channel systems, as it is not

possible to design decoders that get rid of it altogether. The effect of phasiness is not only to blur the sound image, but also to create an unpleasant sensation often described as "pressure on the ears" that actually makes some people feel sick, although others don't seem to notice it much. Studies by the BBC^{6,7} and NHK⁸ have given a good indication of how much phasiness can be tolerated. In addition, it is found in practice that phasiness is more acceptable for sounds behind the listener than for sounds in front. Two-channel ambisonic decoders are therefore designed for very low phasiness in the front sector of sounds, while giving rather higher phasiness in the rear.

There is another reason why phase shifts cause poor directional reproduction that comes into action below 300Hz. In a real-world listening room, the loudspeakers are at a finite distance from the listener (often about 2.5 metres for British listening rooms), which means that the sound wave from each loudspeaker arrives as a curved wave-front at the listener, rather than as a plane wave. This curvature can be shown to cause the "phasiness" components of the reproduced directional sound to be converted into rotations of sound images around the listener at low frequencies. However, it is possible to remove these low-frequency errors by means of two high-pass filters in the "velocity signal" paths in the decoder. These speaker-distance compensation filters are RC types with -3dB points at about 20Hz for 2.7m speaker-to-listener distance. This may seem too low to worry about, but listening tests here confirmed the design theory and show that image displacements of as much as 15 to 30° can occur for instruments such as double basses when situated behind the listener unless distance compensation is used. Distance compensation does not turn a bad decoder into a good one, but it does give a "tighter" and more well-defined sound to an already good decoder design.

The ears use different methods of locating sounds at higher frequencies say from 700Hz to 5kHz. However, a rather magical result emerges from the

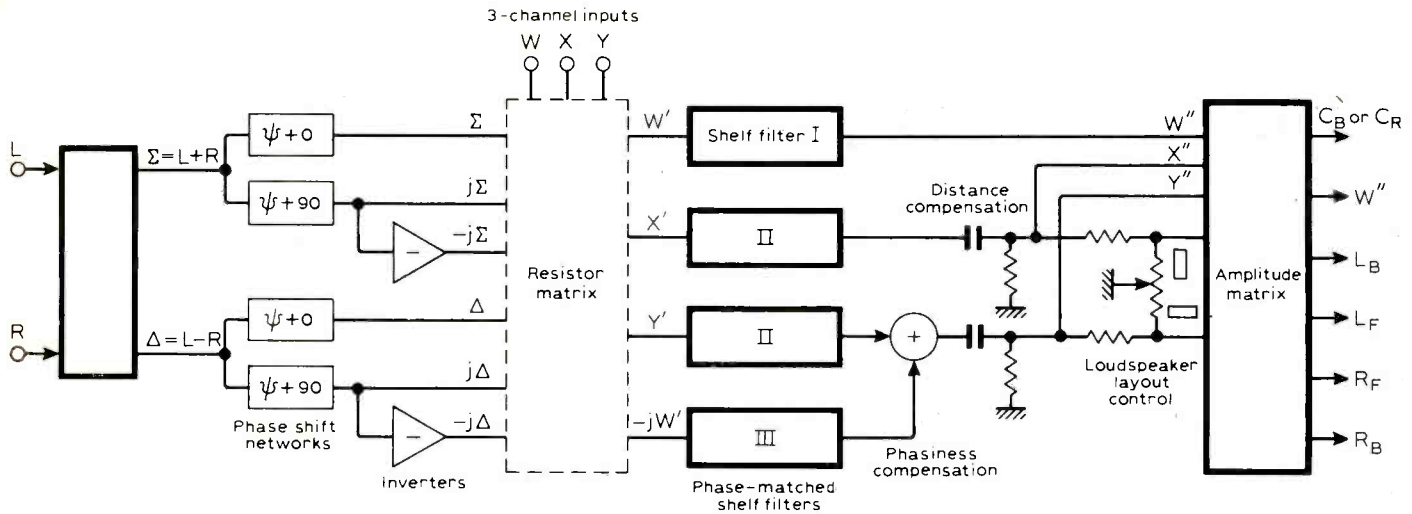


Fig. 1. Block diagram of multi-system ambisonic decoder, switching arrangements omitted. Shelf filters, inoperative for SQ decoding, depend on system being decoded, as does the resistor matrix. Also not shown is switching for C_B or C_R output.

design theory that states that, in effect, the basic sound localization of a decoder will automatically be the same at low and higher frequencies provided that the loudspeaker outputs of the decoder are derived via a particular type of amplitude matrix, the matrix involved depending only on the loudspeaker layout being used by the listener.

Besides getting the basic high frequency localization correct, it is necessary to minimize phasiness in this frequency range also, and to ensure that the sound image does not move around as the listener faces other directions. To get this last requirement right, it turns out that the best decoder design at higher frequencies involves different relative signal gains from those apt at low frequencies, so that the decoder has to be made frequency-dependent. The

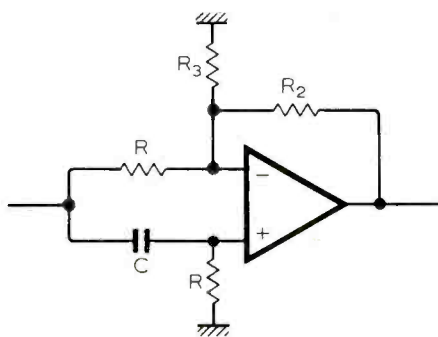


Fig. 2. Phase-compensated shelf-filter circuits allow frequency-dependent decoding. Conventional RC shelf filters would cause unwanted phase differences between signal paths.

effect of minimizing the image movement as the listener rotates his head is to avoid an unpleasant "in-the-head" sensation often, but incorrectly, described as "closeness" of sound by other authors⁹.

There are numerous other detailed aspects of decoder design, particularly those involving the way reverberation is reproduced (where a careful choice of encoding system such as 45J¹ can help), the effect heard by listeners seated away from the centre of the listening area, and the tone quality of the sound. It may seem strange that absolutely flat frequency response reproduction can sound coloured when reproduced through several speakers, the coloration depending on the precise speaker feeds used in the decoder. Many simple "matrix quadrasonic" decoders suffer from a tubby bass or harsh treble due to these effects. However, it is possible to account for most of these effects by the psychoacoustic design theory, and to minimize them in the decoder design. In practice, sounds encoded at the back are allowed to sound a little more colored than frontal sounds in ambisonic designs, because the ears appear to be more tolerant of marginal faults at the back, although one should assume that they are infinitely tolerant!

All decoder designs for two-channel encoding systems are a compromise between conflicting factors, and no design can achieve perfect performance in all ways. In this respect, the design of decoders is akin to loudspeaker design in being in the final analysis an art based on experience and listening. However, the science (i.e. the comprehensive psychoacoustic theory) is a very necessary part of reducing the almost infinitely complex design problem to a point where the designer can be sure of achieving his particular compromise as well as possible. The compromises inherent in these designs are based on the requirements:

- for front-stage material, the surround-sound should be subjectively superior to stereo for musical listening

(few existing designs meet this minimal requirement!),

- good results for listeners facing non-frontal directions and in non-central listening positions, especially behind-centre, and
- "musicality" of effect on both "ambient" and "surround" programme material, leading to low listening fatigue.

To some extent these requirements conflict with those based solely on the localization of direct sounds, such as in the experimental results quoted in ref. 10, where image sharpness for a forward-facing central listener has been achieved in a simple matrix decoder at the expense of "in-the-head" sound and severe image mislocation for non-forward-facing and non-central listeners. Good single-sound localization for most directions and listening positions can be achieved using a signal-actuated variable matrix decoder, but such decoders give a high level of listening fatigue on music due to the constant variation of signal parameters. Such decoders may be useful for surround-drama, where accuracy of localization becomes more important than "musicality" or low listening fatigue, and a fully-fledged ambisonic 'variable matrix' design is under development for such specialist applications. However, there is no doubt that a non-variable decoder is going to remain the preferred method of serious listening to music despite its superficially less "impressive" performance.

The basic diagram of the ambisonic decoder to be described in detail in later parts is shown in Fig. 1. Left and right signal inputs are fed to a sum-and-difference matrix to derive the sum $\Sigma = L + R$ and difference $\Delta = L - R$, because this leads to simplification of the later parts of the decoder, as well as to a slightly greater tolerance to small component errors. These two signals are each fed to 0° and 90° phase shift networks, and the 90° -shifted signal is also phase inverted to yield a -90° phase shifted signal in each case. The


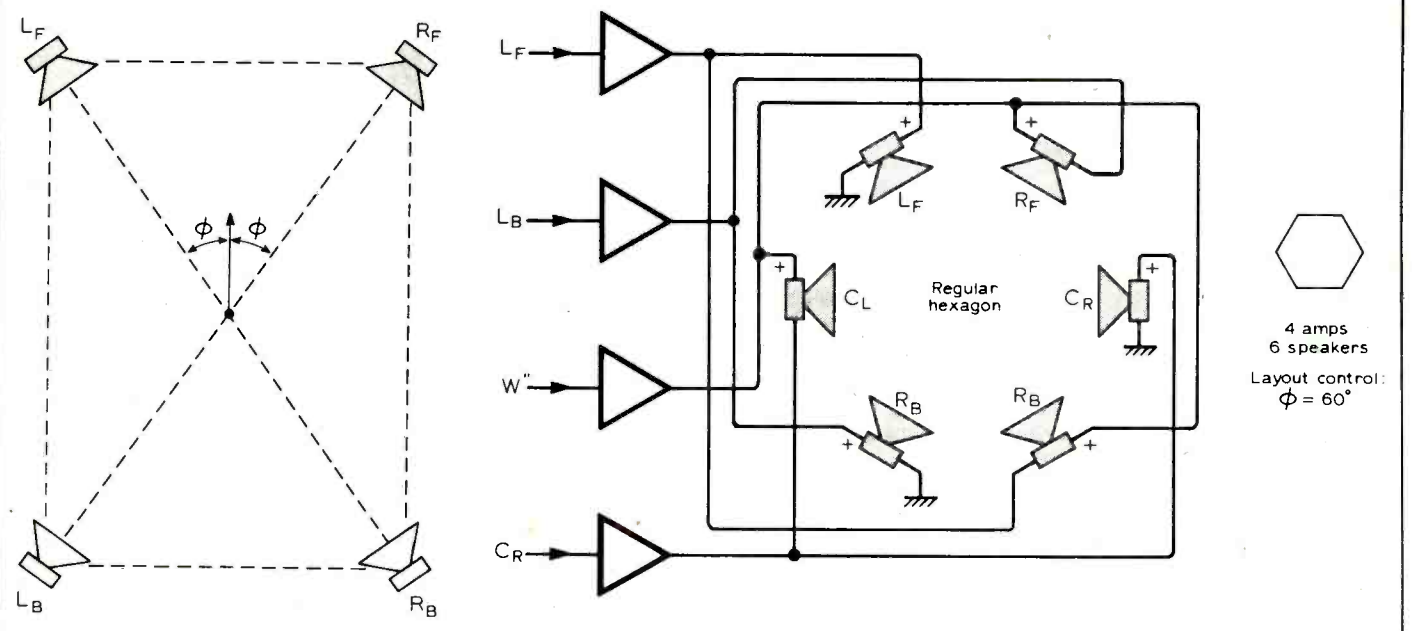
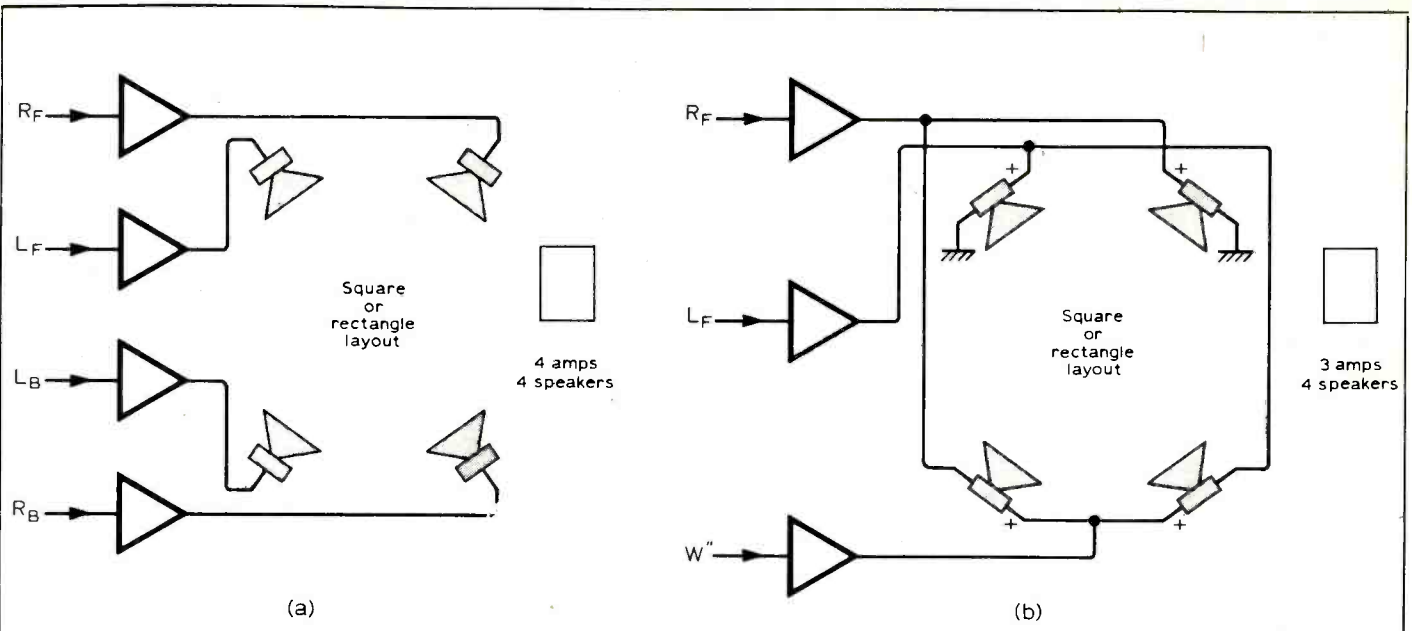


Fig. 3. Methods of feeding four loudspeakers using four amplifiers (a), and three amplifiers (b). Speaker terminals marked + are the positive-phase terminals in each case.

Fig. 4. Compensation is provided for non-square layouts. Angle ϕ is set on a layout control.

Fig. 5. Better results can be obtained from four-amplifier, six-speaker regular hexagon decoding. Connections are shown for two hexagon layouts with the angle ϕ used in the equations of the output matrix.

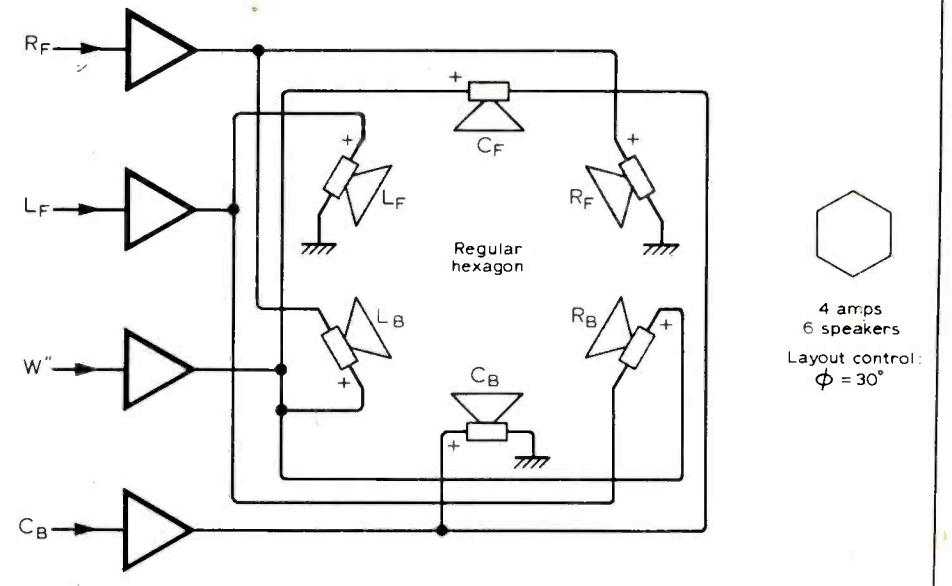

phase-shifters used are high precision types, as the ears are capable of hearing very small errors in localization (as little as 2° in real life). Previous "quadrophonic" decoders have not required such high precision mainly because they gave in any case a poor decoded effect due to sub-optimal design.

The six signals are then fed to a resistor matrix, which derives the required combination of these signals to produce the correct pressure and velocity signals W' , X' , Y' , for the particular encoding system in use. (For a discussion of this aspect see ref. 1, in particular in connection with its Fig. 2). The resistor matrix used is different for different encoding systems, so that switching is provided for different resistor resistance values. The resistor matrix, which involves no active circuitry, also includes a switched three-channel input option suitable for use with three-channel ambisonic mastertapes. In a later article we hope to describe live ambisonic recording for the keen tape enthusiast. These three channel inputs only cost a few resistors and input sockets in the present decoder, and so come virtually for free; in addition, they provide useful test signal inputs for setting-up purposes. We shall give the resistor matrix formulas for the various encoding systems for the signals W' , X' , Y' in part 2 of this series. An output $-jW'$ is provided for phasiness-control in some systems, as described in references 1 and 3.

The frequency-dependent aspects of the decoder are provided by the shelf filters which give one decoding matrix at low frequencies and a second at high frequencies, with the transition centred at 400Hz. Were conventional RC shelf filters to be used, there would be phase shifts between the various signal paths, which would cause quite bad localization errors. For this reason, the shelf filters are designed to give phase shifts identical to one another by making them "all-pass" types. The basic circuit of the phase-compensated shelf filters is shown in Fig. 2. The particular arrangement shown has an input impedance of R at all frequencies, which means that it is seen by the resistor matrix as a resistive load, suitable for terminating a matrix circuit. The value of R_2/R controls the ratio of high-to-low-frequency gain of the shelf, and R_3 provides extra h.f. gain to make up the losses of the preceding resistor matrix.

Thus the shelf filters are made to do five different jobs: terminate the matrix circuit, provide gain, give a different matrix circuit at low and high frequencies, give matched phases over the transition frequency band, and give an overall flat frequency response to the decoder at all frequencies.

An additional complication arises because different methods of encoding require different shelf filters in the decoder. In practice, the shelf filters required for BMX, RM, 45J and BBC H

differ only slightly, so that a compromise choice has been made to do all these systems. Decoding mono, stereo and three-channel studio format requires, for best results, a different set of shelf filters, and SQ requires that no shelf filters be used. (SQ decoders cannot be designed to give full ambisonic results; there is a mathematical theorem to this effect. The decoder for SQ provided is, however, less phasey in quality than the SQ designs on the market, and was designed specifically for incorporation into this design. It is not in accordance with CBS Laboratories' SQ specification, but in the author's opinion, it is better than decoders that are.)

The switching of the shelf filters involves equipping the op-amps of Fig. 2 with several filter circuits, which are switched in and out as required.

The outputs of shelf filters acting on Y' and $-jW'$ (see Fig. 1) are added to reduce front-stage phasiness, and the velocity signals are then subjected to the RC high-pass distance compensation. This gives us three signals W'' , X'' and Y'' representing respectively the signal pressure, forward component of acoustic velocity, and leftward component of acoustic velocity heard by the listener. These are fed to an output amplitude matrix, which includes a layout control adjustment to adjust the outputs of the decoder to match different shapes of rectangular loudspeaker layout in the room.

The decoder provides six different outputs L_B (left back), L_F (left front), R_F (right front), R_B (right back), W'' (pressure) and either C_B (due back) or C_R (due right), switched. The way these six outputs can be used is itself an interesting story, for they can be used to provide decoding via four loudspeakers in a wide range of rectangle shapes using either four amplifiers, Fig. 3(a), or, remarkably, using just three power amplifiers as shown in Fig. 3(b). The three-amplifier set-up in no way means that there is any compromise in the psychoacoustics of the decoded signal, as precisely the same speaker signals are produced as in Fig. 3(a)!

To see this, we first remark that the outputs of the decoder are given by the formulae

$$\begin{aligned} L_B &= \frac{1}{2}(W'' - \sqrt{2} \sin \phi X'' + \sqrt{2} \cos \phi Y'') \\ L_F &= \frac{1}{2}(W'' + \sqrt{2} \sin \phi X'' + \sqrt{2} \cos \phi Y'') \\ R_F &= \frac{1}{2}(W'' + \sqrt{2} \sin \phi X'' - \sqrt{2} \cos \phi Y'') \\ R_B &= \frac{1}{2}(W'' - \sqrt{2} \sin \phi X'' - \sqrt{2} \cos \phi Y'') \end{aligned}$$

where ϕ depends on the setting of the layout control, being 45° for a square layout, and being equal to the angle ϕ shown in Fig. 4 for a rectangle layout. From these formulae

$$L_B + R_F = L_F + R_B = W'',$$

so that

$$\begin{aligned} L_B &= W'' - R_F \\ R_B &= W'' - L_F, \end{aligned}$$

and it will be seen that the rear speakers of Fig. 3(b) indeed are connected so that the potentials of their "positive phase" terminals relative to their negative phase terminals are $W'' - R_F$ and $W'' - L_F$

respectively.

Even more remarkable however, are the four-amplifier six-loudspeaker arrangements possible with this decoder. It has been known for several years that decoders using six loudspeakers are capable of better results than is possible using four, no matter how well-designed the decoder may be. If properly used, the extra speakers give more solid image location over a larger area, with less tendency for the image to hug the loudspeakers than when using four, particularly on difficult waveforms such as audience applause. It has not been possible to market six-speaker equipment; few homes could properly accommodate it, and the market for such special equipment was thus too small to justify manufacture. However, the ambisonic decoding method permits the same decoder and the same four amplifiers to be used for six speakers for the few who can manage it, making this improved form of decoding domestically available for the first time. We emphasise that in no way does the use of four amplifiers imply substandard results: exactly the same speaker signals are given as one would design a psychoacoustically optimized six-amplifier decoder to give.

The six-speaker connections for two shapes of regular hexagon layout are shown in Fig. 5. The three speakers that are fed in a "simple" manner in each case form an equilateral triangle of speakers; this helps minimize the subjective effects of slight mismatches of amplifier gain. The signals C_B and C_R are

$$\begin{aligned} C_B &= \frac{1}{2}(W'' - \sqrt{2} X'') \\ C_R &= \frac{1}{2}(W'' - \sqrt{2} Y''). \end{aligned}$$

Although detailed instructions for calibrating and using the decoder will be given at the end of this series of articles, it is worth emphasizing now that all amplifiers and loudspeakers

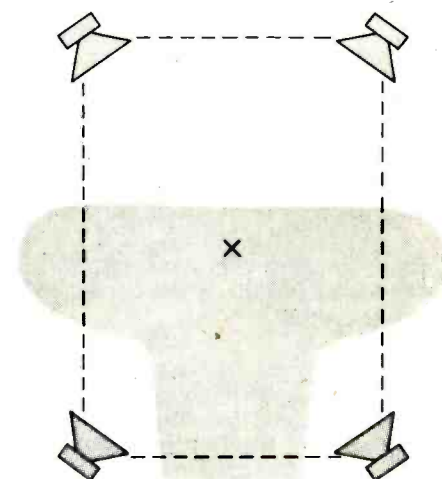


Fig. 6. Approximate listening area for ambisonic decoding (shaded) with a rectangle speaker layout obtained for BMX, 45J, Matrix H and RM systems as well as stereo. Optimal listening is at the centre (X).

must be accurately matched for correct ambisonic results. Unlike "quadraphonic" decoders, both front and rear loudspeakers co-operate to produce sounds in any direction. Thus, for example, the rear speakers provide outputs that help to reinforce the localization of sounds that are reproduced in front of the listener. Thus one cannot try turning the rear speakers up or down in the mistaken idea that the front and rear are independent of one another. When the outputs are not matched, the sound field tends to "fall apart"; in fact turning down the rear speakers often makes them much more audible (as distracting noises at the back) than in a correct balance.

While it is not absolutely necessary to have all power amplifiers of the same make, they should be adjusted for identical gains and phases, and one should check (e.g. by using an X-Y oscilloscope display) that they have substantially identical phase responses over the audio band. If in doubt, identical amplifiers should be used. While identical speakers should be used, a small number of speaker manufacturers (e.g. IMF Electronics) have taken trouble to match the different models in their range carefully, and in such cases different models can be used at front and rear. Again, if in doubt, use identical speakers for best results.

The decoder not only reproduces surround sound from a variety of existing systems, but also handles mono and stereo, using ambisonic techniques to get the most natural possible reproduction (using four or six speakers) from existing records and broadcasts. Except for exceptional stereo material, the decoder does not create "pseudo surround sound", but reproduces stereo over a conventional frontal stage with a subtle enhancement over two-speaker stereo, and without any gimmickry. The mono decode mode reproduces a mono source from straight in front, but the

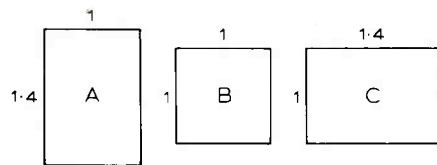


Fig. 7. Most stable front images are provided by arrangement (a), most stable side images by (c), while (b) is a compromise between these extremes.

rear speakers help to lock the image solidly in space behind the front loudspeakers. Neither mono or stereo decode modes enhance badly recorded material, but neither do they degrade it any further. In practice, many ambient SQ classical recordings, such as those released by EMI, will be found to reproduce better in the stereo decode mode than via SQ decode mode, owing to the inherent limitations of the SQ system.

Fig. 6 shows the approximate usable listening area for most decoding modes (excluding SQ) in a typical domestic room using a rectangle layout. The listening area will in practice depend on the loudspeakers used, the room acoustics, the layout shape used, the programme material, and also on the system being decoded. The type of listening area shown has been obtained both with ambisonic recordings made in concert halls, and with commercial "easy listening" (*sic*) music in the BMX, 45J, Matrix H and RM systems, as well as with stereo material played in stereo decode mode.

It is found that a longer-than-wide layout of four speakers as in Fig. 7(a) gives the most stable front images for non-central listener and the least stable side images. A wider-than-long layout as in Fig. 7(c) gives excellent stable side images for most listeners, although the front stage tends to be drawn over to the nearest speaker. A square layout,

Fig. 7(b), is a compromise in terms of image stability between these extremes. Extremely thin rectangles (whether long or wide) cannot be expected to give good results, although the layout control adjustment will help to minimize the inevitable defects.

Part 2 will give details of the decoding matrices used. Patent rights in circuits described in this and subsequent parts of this article are owned by the National Research Development Corporation. A kit of parts for the decoder will be available from Integrex Ltd - see advertisement.

References

1. Gerzon, M.A. NRDC surround-sound system. *Wireless World*, vol. 83, April 1977, pp.36-9.
2. Gerzon, M.A. Ambisonics Part II: Studio techniques, *Studio Sound*, vol. 17, Aug. 1975, pp.24-6, 28, 30, Correction: *ibid* vol. 17, Oct. 1975, p.60.
3. Gerzon, M.A. Optimum Choice of Surround-Sound Encoding Specification, preprint A5, 56th AES Convention, Paris, 1st March, 1977.
4. Gerzon, M.A., Design of precisely coincident microphone arrays for stereo and surround sound, in collected papers, 50th AES Convention, London, March 1975.
5. Gerzon, M.A. Surround sound psychoacoustics, *Wireless World*, vol. 80, 1974, pp.483-6.
6. Bower, J. S. Subjective effects of inter-channel phase-shifts on the stereophonic image localization of wideband audio signals, BBC Research Department Report, BBC RD1975/27, Sept. 1975.
7. Bower, J. S. Subjective effects of inter-channel phase-shifts on the stereophonic image localization of narrowband audio signals, BBC Research Department Report, BBC RD1975/28, Sept. 1975.
8. Nakabayashi, K. Method of analyzing the quadraphonic sound field, *J. Audio Eng. Soc.*, vol. 23, 1975, pp.187-93.
9. Meares, D. J. and Ratliff, P.A. Development of a compatible 4-2-4 quadraphonic matrix system. BBC Matrix H, *EBU Review* (Technical) no. 159, Oct. 1976.
10. Ratliff, P. A. and Meares, D. J., BBC Matrix H. *Wireless World*, vol. 83, May 1977, pp.41-5.

Broadcasting satellite receivers

Mullard's research laboratories have released details of the microwave receivers which they, in co-operation with Philips at Eindhoven, have built for picking up broadcast television signals from "Hermes", the Canadian-American Communications Technology Satellite (News, April, p.40). The receivers convert the 12GHz f.m. broadcast signals picked up by small dish aerials to a form suitable for feeding into the aerial socket of standard NTSC colour television sets. Five receivers and associated 1.6m (or in some cases 1.2m) diameter metal-coated glass-fibre-reinforced polyester parabolic aerials were supplied by Philips, and one receiver of somewhat different design but using the same aerial was

supplied by Mullard. To accommodate satellite drift provision was made for remote control motor tracking of the aerials on a single axis.

An outdoor part of the receiver with an integral waveguide horn is placed at the focus of the aerial and provides fixed-tuned conversion from 12GHz to 410MHz, with a noise figure of about 7dB. It consists of a microstrip Schottky-barrier-diode mixer, followed by a 40dB amplifier. The local oscillator is a Gunn device delivering about 10mW at approximately 11.7GHz and, in the Mullard version, this is located in an aluminium cavity integral with the converter. Dielectric temperature compensation maintains frequency drift within 5MHz (over the range -40°C to $+40^{\circ}\text{C}$) which is well within the range of the automatic frequency control applied to the second mixer. This is located in an indoor unit fed with the 410MHz signal by a coaxial cable.

The indoor part of the receiver provides further conversion to 120MHz prior to limiting and frequency discrimination to yield the NTSC composite video colour signal and 5.14MHz f.m. sound signal. The last-mentioned is converted to the normal 4.5MHz inter-carrier frequency and with the video is used to amplitude-modulate a 500MHz carrier to provide a 10mV signal suitable for the aerial input of a standard NTSC colour television set. Extensive use is made of integrated circuit techniques.

The Mullard receiver is installed at the Canadian government communications research centre in Ottawa. The aerials were aligned first by a simple level of compass then final adjustment was made by means of the satellite signal itself and a signal strength meter. Mullard say excellent picture and sound quality was achieved and the received signal strength was close to the expected level of -105dBW .

News of the Month

Plessey chief wants social responsibility

Sir John Clark, chairman and chief executive of Plessey, has expressed concern about unemployment caused by technical change. Plessey workers making electromechanical telephone exchange equipment are threatened with redundancies as a result of the Post Office's unexpectedly sudden decision to change to electronic exchanges. Speaking at the opening of the London Electronic Component Show, Sir John asked "Should technology be pursued for technology's sake? And what impact will the changes caused have on people? We are constantly being told we live in the technical age. But there is, I think, an optimum beyond which it is not cost-effective to go. The impact of change on people should be given the most urgent consideration. Not only how it will affect the jobs they do and how they do them, but also on the crucial social question of whether some jobs will remain to be done at all.

"In contemplating the equation of change", continued Sir John, "the social consequences must be taken into account and weighed carefully against any other advantages which might accrue. This is why one of your major

customer-industries – namely telecommunications, which as you know Plessey has a considerable interest in – has appealed to the Government against the cumulative effects of Post Office cuts, recently announced, in the traditional electromechanical telephone systems. Of course we believe the British telecommunications industry should move forward quickly into the new technical area with equipments brought to modern technical standards. But some regard must be paid to social responsibility by the decision-makers. By their decisions, they have the power to wipe out the livelihood of thousands of people without adequate time being given for an orderly and manageable transition from the old to the new. In my view, it should not be done without due regard to the consequences."

Plessey is one of the companies mentioned by Mr Ernest Harrison, chairman of Racal, as possibly being involved in a rationalization of the British electronics industry (see leader).

A to D conversion at 30MHz

A design group at Cambridge Consultants working on high speed analogue-to-digital conversion have developed a convertor which they describe as the fastest eight-bit a.d.c. in Europe. It will perform, they say, "a full accuracy eight-bit conversion every 33ns." Two have now been delivered, one each to Plessey Ltd. whose Allen Clark Research Centre developed a high speed comparator using the circuit

A new independent viewing centre for use with the EMI X ray scanner. It provides a display and data reprocessing at a point remote from the main scanner. The area of interest can be enlarged and there are other image manipulation facilities.



element, and the Admiralty Surface Weapons Establishment.

Two years ago CC were working on a military contract for which they developed a six-bit, 30MHz convertor. Cambridge believed the technology available would allow the development of an eight-bit version. With the completion of the previous contract, however, they needed funding and a client to build both the circuit element to Cambridge's specifications and a circuit in which to use it. The money came from the Ministry of Defence directorate for Components, Valves & Devices (CVD), and Plessey's comparator circuit provided an opportunity to use Cambridge's expertise.

The Cambridge equipment is designed for use in radar signal processing and transient recorder applications where low aperture uncertainty, a parameter affecting the accuracy of sampling at a signal's zero crossing point, and full accuracy at high sampling rates are required.

A commercial version, the ADC30.8 is available from Cambridge Consultants. It includes a matched, high speed, low jitter sample hold, operates from a 50 ohm analogue input and samples with an aperture time uncertainty of 10ps r.m.s. The sample command input and the offset binary coded digital output, overrange and internal 30MHz clock signals are all of 50 ohm impedance and e.c.l. compatible. The unit, priced at £3,510, comes with power supplies in a 19in case. The designers were Dr Chris Davies and Julian Coles, and the project manager was Dr Robin Smith-Saville.

Post Office buys solid state stored speech

The Post Office have installed two prototype, automatic, changed-number intercept equipments for service trials in Birmingham and Chelmsford telephone exchanges. If, at the moment, a number is changed the caller, on dialling the old number normally has his call intercepted by the operator, who then tells him the new number. The new system puts the caller through to an automatic spoken message which is stored digitally in memory. This stored message is passed on to the caller.

The equipment supplied by Pye TMC, builds up the message from a limited vocabulary of words and phrases. Each word or phrase is decoded from its digital form and kept going round an audio highway. If one were to listen to one of these highways one would hear a single word or phrase repeated continuously. Line circuits which recognise that a call has reached a disused line are programmed to select the highways in the correct sequence to build up a message for that line. A test message is available by dialling Chelmsford 62101.

MRUA call for mobile radio "Annan"

Following the Home Secretary's call for comments before the 1979 World Administrative Radio Conference the Mobile Radio Users' Association have published their submission to the Home Office. The Association, who say they represent 80% of all private mobiles in the UK, submit that

- Mobile radio use should be encouraged on economic grounds.
- Demand will increase, also because of the need for economies.
- The Home Office's predictions of spectrum requirements "are based on reports which appear negative in spirit."
- 100MHz extra spectrum is needed for mobile radio, the extra frequencies being found by moving fixed services to higher bands, standardising on 12.5kHz channel spacing, and releasing frequencies from bands 1 and 3, and other places in the spectrum allocated but under-used.
- Mobile radio is important enough to justify setting up a body like the Annan Committee whose conclusions should be published.

The MRUA say the submission is based on feedback from their members, study of the Home Office Warden Report and Pye's Pannell report, a survey which MRUA did of all p.m.r. users in the UK, and other submissions which they have seen. The MRUA believe that mobile radio is the one use of spectrum which gives tangible and measurable economic benefits and, since most western countries' problems at the moment appear to be economic, mobile radio ought to have first priority. The UK commercial and industrial world was not yet conscious of the benefits offered by p.m.r. and so the government should actively encourage them to use it, instead of restricting p.m.r.'s use. Demand may be artificially low, say MRUA, because of delays in issuing licences. The submission continues: "Our main objection to the policy apparently to be followed by the UK delegation is that their attitude from all indications to date appears to be negative. It seems to be a matter of how few people should use radio and how small the necessary allocation can be, whereas we feel the attitude should be the opposite."

MRUA also say they believe that if the government has allocated to it large areas of the spectrum which they do not use they should release them for p.m.r.

To standardise on 12.5kHz would "in some measure degrade system performance, but this must be tolerated in the interests of spectrum economy. However we are of the opinion that any further channel splitting is not a true economy with existing modulation systems owing to degradation of signal to noise ratio." This view had been expressed before when channels had

been progressively split as technology developed: "Our objection to a further split in channels is not based on any shortcomings of the equipment, which may well be capable of performing at narrower spacings; it is based on the degraded signal-to-noise performance resulting from the reduced bandwidth. The MRUA would oppose any move away from the general policy of two frequency working as a result of pressure from any other administration. They also believed that fixed point to point links should be moved eventually to beyond 512MHz. Propagation difficulties and high costs would prevent the use, for the time being, of frequencies in the 850-960MHz band for p.m.r.

"We believe that in the interests of progress it is too easy to underestimate the information capacity of simple speech. Speech has the advantage of infinite flexibility and to a small extent an additional range of meanings resulting from tone of voice. It is unlikely that data systems will ever match this, and they are costly both in capital and maintenance terms. We believe that there are a few p.m.r. applications which could usefully consider data, whereas we believe that many government services, such as police and fire brigades, could make great use of data for routine messages, and thus effect spectrum economy in those regions of the bands."

No two uses of p.m.r. are alike, they add, and they would oppose any blanket for measuring channel occupancy.

The British Gas Corporation have published a paper presented to a private meeting of the Joint Radio Committee

of the nationalised industries held at Lincoln College Oxford in late March. The main points of the speech made by East Midlands Gas Marketing Board director Peter Quinn are that: the use of self-identification in the calling procedure takes up to 20% of the message length, and can exceed the message time; that the greater demands on operators made by selecting among a number of base stations "is not ideal, and that his time could be more beneficially spent controlling work allocations, etc"; that operators need to be well trained to control incoming calls, and to ensure that all calling mobiles are correctly acknowledged, passed on immediately or put on standby; the amount of information that has to be passed on by a fitter takes some time and "represents poor use of the channel"; and the passing on of a message to a third party often involves bringing whoever is to receive the message into the radio room to take over the equipment for the duration of the call, with considerable disturbance.

On selective call systems Mr Quinn noted that their use in the gas industry had reduced call sign transmission time, shown a caller immediately that his call had been received, alerted fitters returning to vehicles that a call had been made while they had been away, all of which produced "better channel management and hence the possibility of supporting more mobiles per channel."

The normal view of selective calling systems among other users appears to be that until interference becomes very much worse the selective calling equipment would provide unrequired facilities at greater cost. Hence Mr Quinn's remark that they had been "slow to find supporters." He added that they would be an essential part of future fully automated systems.

Viewdata cracks the PO armour

Details are emerging of the Post Office's delayed Viewdata market trial, to begin in the middle of next year. One thousand sets are to be distributed among interested viewers selected to represent an exact cross-section of the British population, according to income and social class, chosen from 6,000 applicants. The Post Office have even stipulated that the suppliers of the sets, ITT, Philips, Thorn, GEC and so on, supply a proportion of the 1,000 according to their market share. Although the news that the Post Office and the manufacturers were co-operating closely was published in the annual report of the British Radio Equipment Manufacturers' Association, issued on May 19, the Post Office is reluctant to discuss the experiment as yet. In a statement issued to *Wireless World*

they said: "We have agreed with BREMA on an integrated approach to the development of Viewdata decoders. This employs a unit in the tv sets which will also include the line interface with the telephone network and as such will demodulate the incoming signals from the telephone line and also generate appropriate loop-disconnect pulses for calling the designated Viewdata computer." They said they would be making an announcement shortly.

The Post Office originally requested that the sets used for the test should be as near as possible to the final production models but the manufacturers told them this would be out of the question in the time available. For that reason rather more equipment will be hanging outside the set than the viewer who buys Viewdata equipment would

expect to see if the trial is successful. In addition the Post Office will be providing isolating equipment and "line terminating units" which perform the same function as the standard PO modem but have a lighter specification. When the full Viewdata service is operating the Post Office will make available higher quality lines to make possible this slight easing of tolerances. The manufacturers will be building into the sets or connecting to them a teletext decoder and a Viewdata decoder module.

Clearly this is the first time the Post Office has moved from its determination to prevent anyone connecting any equipment to a telephone line other than that it has supplied itself. Equally clear is that unless it agreed to this the Viewdata service would founder. While the Post Office is taking no chance of risk to its personnel or equipment — there is some talk of using two stages of isolation from the telephone line — there is no doubt that some in the electronics industry will see this as setting a precedent.

Meanwhile in Germany the competition to run the Viewdata service is hotting up, and for once British manufacturers are making the running in supplying to whoever wins. At the end of May representatives of the German press met in Hamburg to decide their tactics for running the proposed teletext service, and at the largest German electronics show, the Funkausstellung, (August 26 — September 4) both they and the broadcasters will be competing to show that they and not the other are the ones who deserve the prize. The German press are arguing that teletext is a newspaper of the air, while the broadcasters argue that it is

part of their medium. And with Viewdata coming the German PTT in Bonn, who have already bought the Viewdata software programme, want to keep a grip on the system whoever wins. The German post office have already taken the BBC's Ceefax service and shown it to some of their staff, and the BBC have German sub-editors working with them. At the Funkausstellung there will be demonstrations, including those by British tv manufacturers, notably GEC. Philips and ITT will also be involved.

GEC have also announced that they have delivered to the German Post Office a 4080 computer system for the proposed German equivalent to Viewdata, the Bildschirmtext. The hardware also includes a 128kbyte core store, 4.8/4.8 Mbyte fixed/exchangeable cartridge disc, magnetic tape storage and paper tape equipment. GEC say the equipment was installed at Darmstadt five weeks after official receipt of the order.

In February we reported (p.40) on a system which used teletext to provide information for the deaf. Now teletext is being used for the blind. Clarke and Smith last year developed with the National Research & Development Council a Braille computer terminal that would fit into a suitcase. It consists of a typewriter keyboard for writing and a 48 character, 14 inch long touch strip operated by t.t.l. controlled solenoids. The information is put in one line at a time and the operator signals "next line" for the tactile display to be changed. The operator can also skip back to previously-read lines.

The snag at the moment is the high price, £2,800, but a read-only version is available at around £500.

Naval weapon life study

The Royal Navy has initiated a three year study aimed at reducing the life cycle costs of naval weapons equipment. Announcing the contract to carry out the study, Mr Brian Mair, manager of Plessey's Product Assessment Laboratories, said the analytical study was intended "to produce rules by which designers of future weapons equipment can predict the life cycle cost of that equipment." The reasons for the study "will become apparent when you consider the way modern technology has changed the Navy's equipment."

Naval equipment has become much more complicated, and difficult to repair. It is no longer possible to keep a full set of spare parts on board ship and expect sea-going personnel, no matter how well trained, to be able to repair it on the spot. It is more likely that plug-in modules would be used which can be repaired when the ship is returned to port. All that is needed is to identify a faulty module and replace it. The difficulty, which the Navy hopes the Plessey study will sort out, is that ships may be at sea for long periods. It is not certain which equipment is more likely to fail, or how much spare equipment it is economical to store in a ship, even with the high reliability the Navy needs. The design of the equipment can make these variables more predictable. As Mr Mair said, "There is an increasing cost of materials support to the Navy for modern weapons equipment. The designer can make trade-offs between reliability of equipment and subsequent maintenance costs. The study is to understand these trade-offs and to study how they can be more effective in the use of money in future.

The cost of the study is undisclosed, but most of the expenditure will be in the salaries of the 14 scientists who will be engaged on it for the next three years. According to a Plessey statement, "The Plessey team will be devising a series of computer operated models in a form which can easily be used by project design teams. The data, vital to validate the models, is being obtained with the co-operation of other major defence contractors."

Brian Mair is now taking charge of an expanded business. Product Assessment Laboratories is now augmented by Plessey Reliability Service and Plessey Calibration Service. The group is called Plessey Assessment Services, of which Mair is business manager. His previous post as manager of PAL will be taken over by Geoff Matthews. The expansion means that PAS will be recruiting over 50 engineers and technicians over the next two years to work at their Titchfield, Hants, base.

Alternative to cellular radiotelephone proposed

Three radio common carrier firms have asked the FCC for permission to build and test a new radio telephone and paging system in competition with the ART cellular system in the Washington-Baltimore area (WW June p40). The alternative would cost just over \$1 million with equipment and technical help to be provided by Harris Corporation. The group have told the FCC they could test and install the service by the 1979 deadline. It would, according to Harris, be less costly to build and maintain, and would use digital transmission to provide the "ultimate in communications security." The pocket pagers and radiotelephones provided to customers would be lighter and less expensive than those currently in use.

The Harris system would use a single powerful transmitter to cover the same area instead of the many base station transmitters within small geographic

cells proposed in the cellular system. It would also operate in the 900MHz band. The single, high power, broadband transmitter, similar to that used in broadcasting, would cover 30 to 50 miles in radius. Ninety-six or more channels could be accommodated by time division multiplexing to mobile units. Broadband remote receivers could pick up conventional narrow band f.m. signals from the mobile units. The receivers would "transmit the spectrum occupied by mobile units back to the central base station via microwave links, where signal processing will occur. The system does not require wireline links between satellite receivers and the base station. The only telephone lines that will be required are those interfacing the [radio common carrier's] main terminal with the telephone company's central office equipment".

Digital television via satellite

Multiplexed 60Mbit/s PAL television and sound signals sent through Intelsat IV from Goonhilly

by M. E. B. Moffat, M.A., D.Phil., M.I.E.E., M.Inst.P. *BBC Research Department*

For many years now the transmission of colour television and sound signals via geostationary satellites has made possible the world-wide exchange of programmes for broadcasting, either "live" or with a few hours delay to suit programming. Such transmissions usually involve analogue baseband signals and f.m. techniques, but in recent years interest has grown in digital coding in conjunction with multi-phase-shift keying modulation.

Provided that efficient bit-rate reduction and modulation methods are used, theory shows that digital coding can form the basis of a better tv transmission system than f.m. for the economic use of r.f. bandwidth and power. The DITEC system of Comsat Laboratories in the USA, described in 1972¹, was the first practical attempt to realise a digital system of this kind. It has been used in North America for the experimental transmission of NTSC 525 line, 60 field/s, 4.2MHz bandwidth colour television signals in the form of a 33.6Mbit/s digital signal through geostationary satellites. Four-phase-shift keying modulation was used, occupying an r.f. bandwidth of about 20MHz, which is about half of that available in an Intelsat IV transponder.

To transmit a high-quality picture using 33.6Mbit/s for PAL 625 line, 50 field/s, 5.5MHz bandwidth colour television signals, i.e. for System I signals as broadcast in the UK, is a more difficult problem than DITEC had to cope with. This is because of the higher horizontal and vertical resolution, offset somewhat by the reduced field-rate.


In 1974 the UK Post Office agreed to support a BBC Research Department proposal that experimental digital transmissions of System I signals should be attempted via an Intelsat IV satellite. The bit-rate envisaged for the video signals was between 44Mbit/s and 54Mbit/s. Added to this would be bit-rates corresponding to error-correction and audio signals, bringing the total bit-rate of the "package" up to 60Mbit/s, the capacity of the experimental channel through the satellite.

The experiments took place in April and May 1976 (see *Wireless World*, August 1976, page 71); they were envisaged as a further contribution to a

programme of field-research into digital tv and audio transmission. They were not the first PO-BBC co-operative exercise on digital video transmission. 120Mbit/s video waveguide-transmission experiments were demonstrated jointly by the Post Office, the BBC and GEC in September 1970 at the inauguration of the first 1km length of circular waveguide at the Post Office Research Department. In 1971, Standard Telecommunications Laboratories and the BBC demonstrated 120Mbit/s video transmission through an optical fibre at the IEE's centenary celebrations. In 1975, the BBC co-operated with the PO, STC, GEC and Plessey in 120Mbit/s cable-transmission tests, involving two 60Mbit/s video-audio packages provided by the BBC Research Department (see *News of the Month*, *Wireless World*, February 1976, and Reference 2).

Further transmission tests with satellite, cable, optical fibre, s.h.f. link, and waveguide systems are envisaged, and some of these tests may use a video bit-rate as low as 30 to 34Mbit/s, if the continuing work on bit-rate reduction leads to satisfactory picture quality at these rates. A precise choice of bit-rate in the 30 to 34Mbit/s region would take into account the bit-rates of 34368kbit/s

Fig. 1. Diagram outlining the transmission system used in the 60Mbit/s experiments at Goonhilly Downs.

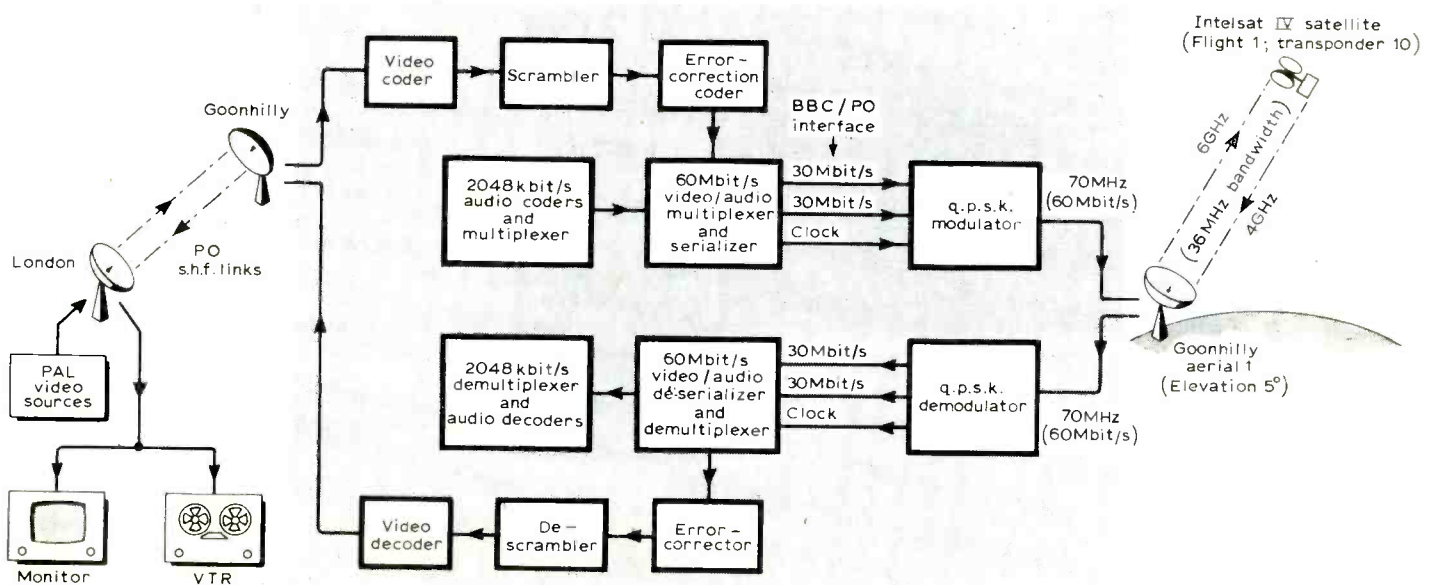

and 32064kbit/s from the transmission bit-rate hierarchies proposed for Europe and Japan respectively.

Experimental transmission system

The transmission system used in the 1976 satellite experiments is shown in Fig. 1. The primary video sources were provided in London by the BBC Designs Department; they comprised a flying-spot colour slide-scanner, BBC Television network channels, conventional test-waveform generators, and a transverse-scan video-tape recorder.

Much use was made of the slide-scanner, with a wide selection of colour transparencies drawn from a new set prepared by the European Broadcasting Union – one of which is shown in Fig. 2(a) – together with other slides often used by television authorities in subjective assessments of picture quality.

The analogue video signal was trans-

mitted by the Post Office via permanent cables and s.h.f. f.m. links to and from their Earth station at Goonhilly Downs in Cornwall. For the digital tests, the analogue video signal was fed to BBC Research Department equipment temporarily located at Goonhilly; this equipment was by-passed on one occasion to afford a brief test using an f.m. channel through a satellite.

The digital video signal was incorporated in a video-audio 60Mbit/s multiplex, which was fed as two 30Mbit/s signals and a clock signal to a quadrature phase-shift keying (q.p.s.k.) modulator, built by the Post Office Telecommunications Development Department.* The 36MHz bandwidth, 70MHz i.f. output from the modulator

*The corresponding demodulator was developed by Marconi Research Laboratories.

was up-converted to s.h.f., amplified, and transmitted through Aerial 1 to and from the Intelsat IV Flight 1 satellite stationed over the Indian Ocean, occupying virtually the full bandwidth available in one transponder. Video and audio monitoring was provided at Goonhilly and at the BBC Designs Department in London. Audio transmission, both ways, between the Designs Department and Goonhilly was provided by BBC sound-in-synchs equipment.

Video coding

In the digital video coder the analogue PAL signal was sampled at precisely twice the PAL colour subcarrier frequency, i.e. at $2f_{sc}$, about 8.87MHz. According to Nyquist's theory this is too low a sampling frequency to conserve the video information. However, G. J. Phillips and M. Weston of the BBC Research Department had shown that, because of the nature of the line spectrum of the video signal, sub-Nyquist sampling at $2f_{sc}$ conserves virtually all of the wanted video information; unwanted "alias" components fall halfway between the lines of the video spectrum and are removed by comb-filtering, with the teeth of the comb spaced at line-frequency.³

Eight bits per sample were used in the initial video signal quantisation, including its line and field synchronising signals.

The eight-bit sample-words were re-quantised non-linearly as six-bit words, or, optionally, five-bit words, using differential pulse-code modulation (d.p.c.m.) or a hybrid of differential and "straight" p.c.m. termed h.d.p.c.m. When five-bit video words were used, a dummy sixth bit was added for instrumental convenience. Six-bit straight p.c.m. was also provided. The essence of h.d.p.c.m. is that straight p.c.m. is used for a sample when the numerical difference between its actual value and its value predicted in the d.p.c.m. coder is large. In this $2f_{sc}$ equipment the second-previous sample is used as the prediction. Large differences result from sharp luminance transitions, for which the eye accepts relatively coarse quantising, perhaps because they are relatively rare. When the difference is small, and can therefore be accurately represented by five-bit or six-bit words, differential p.c.m. is used, i.e. the five-bit or six-bit word gives the value of the difference rather than the absolute value of the sample; in plain coloured areas the difference is zero.

Of the various options available, six-bit h.d.p.c.m. was the one mostly used.

Video scrambling

During preliminary tests with the q.p.s.k. modem it was found that the channel performance was not independent of the transmitted bit-sequence. The salient problem arose with carrier recovery in the demodulator, where

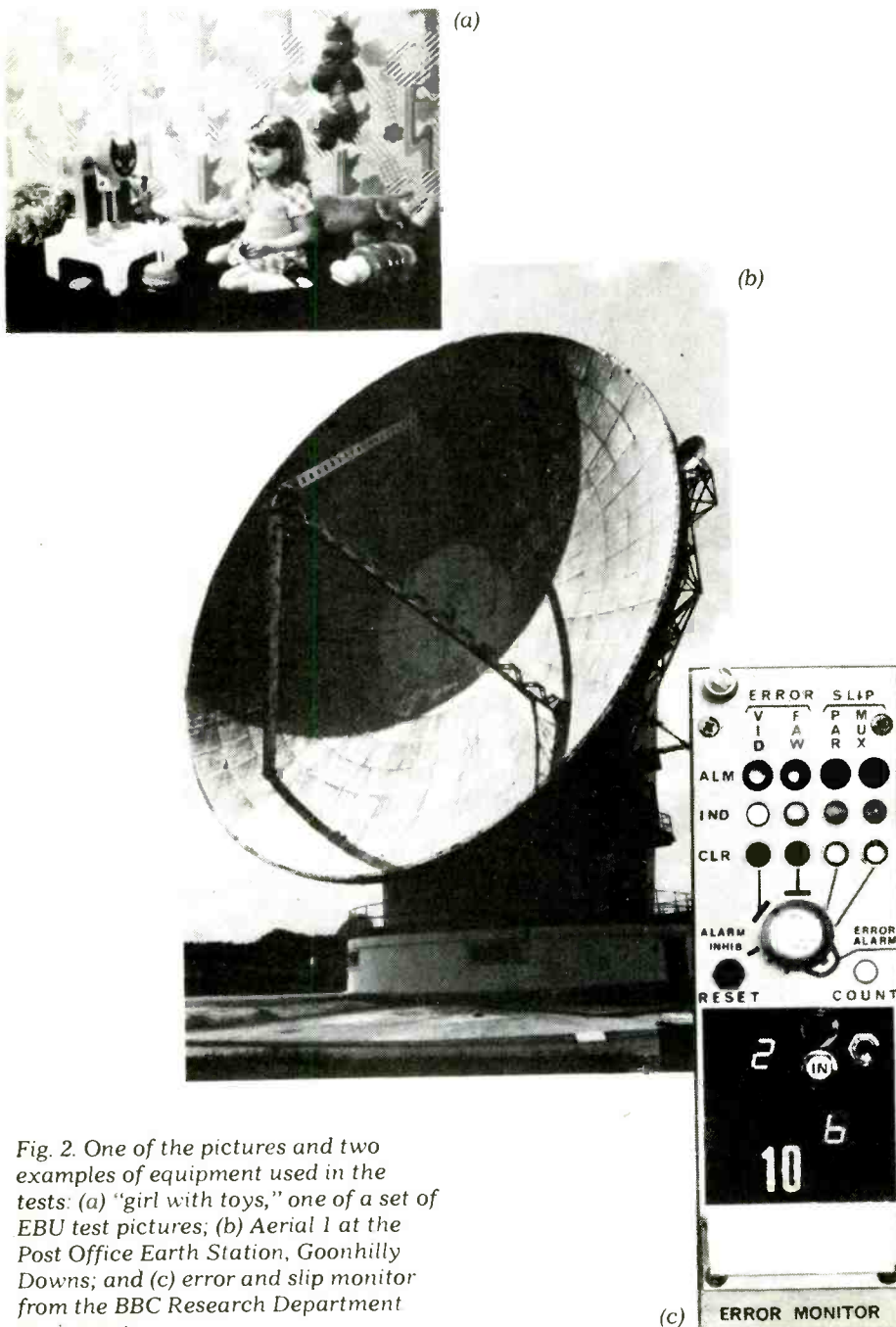


Fig. 2. One of the pictures and two examples of equipment used in the tests: (a) "girl with toys," one of a set of EBU test pictures; (b) Aerial 1 at the Post Office Earth Station, Goonhilly Downs; and (c) error and slip monitor from the BBC Research Department equipment.

recovery was quite all right with pseudo-random bit-sequences but was somewhat picture-dependent with digital video signals; certain pictures gave rise to troublesome and lengthy bit-sequences. The problem arose because the troublesome bit-sequences contained insufficient carrier-recovery information for the particular type of recovery circuit used, which was designed for digital telephony applications and not for the experiments described here. The problem was overcome by scrambling the digital video signal to make it appear pseudo-random for transmission, and de-scrambling it before decoding. The way in which this was done is outlined in Fig. 3, where the modulo-2 addition is equivalent to the exclusive OR logic function. The square boxes represent one-bit shift registers clocked at the serial bit-rate. The modulo-2 sum on the figure shows how the output of the de-scrambler always equals the input to the scrambler.

Video error-correction

P.c.m. video-transmission errors cause small points of enhanced or reduced brightness to appear in the picture. But d.p.c.m. transmission errors are more serious since the effect of a single error is to cause a streak across the picture from the point at which the error occurred to the right-hand side where the sample difference is reset to zero. H.d.p.c.m. transmission error-streaks do not often extend so far because they stop where the coding mode changes from d.p.c.m. to p.c.m.; indeed this effect is the main advantage of h.d.p.c.m. However, even h.d.p.c.m. is not rugged enough to withstand a random transmission-error rate of more than about 1 in 10^8 , without more than a very-slight picture impairment, and the error-rate on the satellite channel was expected to be somewhat higher than 1 in 10^8 . Therefore a form of video error-protection was provided in the BBC equipment.

The method used is known as Wyner-Ash convolutional error-correction with a (16,15) code.⁴ The numbers mean that the ratio of the number of error-correcting bits to the number of video-data bits is 1:15. Six error-correctors of this kind were provided to operate independently on each bit of the six-bit video words. Six-bit words at a rate of $2f_{sc}$ give a serial bit-rate of 53.2Mbit/s. Adding the error-correcting bits brought this rate up to 56.8Mbit/s.

The use of six independent error-correctors meant that a burst of up to six consecutive bit-errors could be corrected. This feature was important because the use of q.p.s.k. could extend a single phase-shift error beyond a single video-bit period. Placing the error correction coders downstream from the scrambler avoided upsetting the burst-correcting feature by scrambling.

The performance of this error-correction method was such that an actual

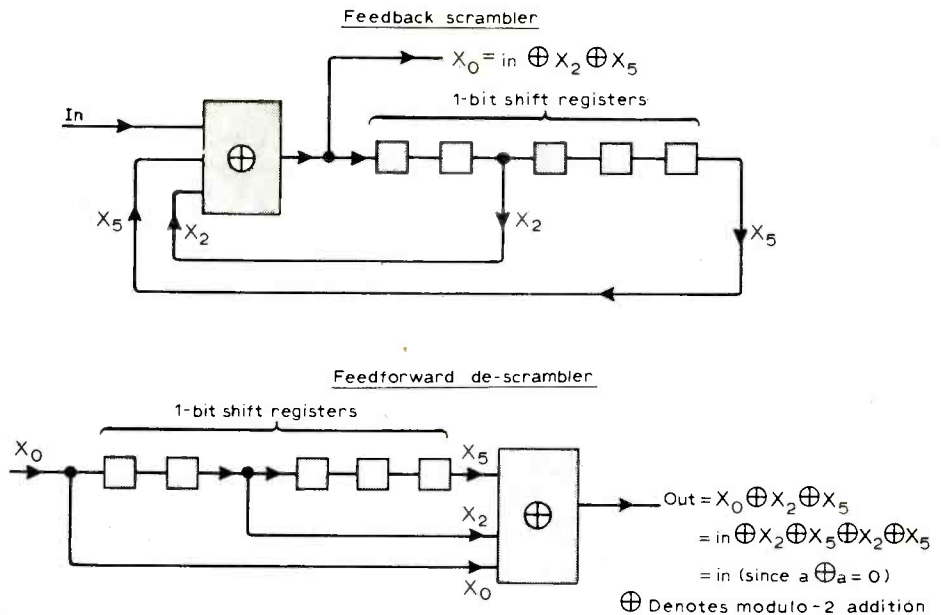


Fig. 3. Five-stage scrambler and de-scrambler.

random transmission-error rate of 1 in 10^9 was reduced in effect to a rate of about 1 in 10^8 .

Audio coding

The 3.2Mbit/s between the bit-rate of the error-corrected video signal and the 60Mbit/s satellite channel capacity was used for audio signals, and for multiplexing and synchronisation. The audio coding equipment was designed to multiplex six high-quality 15kHz sound signals into 2048kbit/s (including audio synchronisation and error-protection signals) using "near-instantaneous" digital companding.⁵ This is a companding technique in which, in this case, a block of 32 ten-bit sound-sample words is coded to a quantising accuracy which corresponds to 13, 12, 11 or 10 bits per sample depending upon the peak value of the audio signal occurring in the block of 32 samples. In the equipment used in the satellite experiments two of the possible six audio channels were equipped with coders and decoders.

Multiplexing

The audio multiplexer and demultiplexer were designed to give and receive a serial 2048kbit/s signal, coded and timed for interfacing with national and international digital transmission paths meeting CCITT standards. The 60Mbit/s video-audio multiplexer combined the serial 2048kbit/s signal with the parallel 56.8Mbit/s error-protected video signal, the latter being provided on six wires each bearing approximately 9.5Mbit/s. Because the protected video signal thus comprised six-bit words, it was convenient to form up the multiplex "frame" from six-bit words, some of them audio, most of them video, a few for synchronisation,

and a few bits spare in some of them for auxiliary signalling. The frame length was 1800 bits ($30\mu\text{s}$).

To maintain the proper relationship between the output (60Mbit/s) and input bit-rates, without locking any of them together, the content of some of the synchronisation words was controlled to comprise either dummy data or real video or audio bits; this "elastic" timing method is known as "positive justification."

The 60Mbit/s output was then divided into the two serial 30Mbit/s signals and a clock signal to drive the Post Office q.p.s.k. modulator; similar signals were returned from the q.p.s.k. demodulator to the 60Mbit/s demultiplexer, as shown in Fig. 1.

Error and slip monitor

Perhaps the most important parameter to monitor on a digital transmission channel is the bit-error rate. It is a sensitive indicator of the state of most parts of the channel equipment and transmission path. The error-monitor module used in the experiments is shown in Fig. 2(c). Fed with data from the error-correction and multiplexing equipment, it gave a clear presentation of the overall error rate or error count, together with a display of lights and audible alarms to indicate bit-errors in the video (VID) and synchronising (FAW), signals, and slips in overall synchronisation (MUX) and synchronisation of video error-correction (PAR).

The test transmissions

For most of the test transmissions the slide-scanner in London was used as the video source, but some more critical tests were done using a BBC digital video waveform generator⁶ located at Goonhilly. The audio source was usually a stereophonic tape-recorder at Goonhilly, replaying orchestral or piano music, but synthesised audio signals and live speech were also used, the

latter chiefly as a commentary to accompany the transmitted video signals for tape-recording in London.

The elevation of the Goonhilly aerial beam above the horizon was necessarily small, namely about five degrees, which is about the smallest elevation for satisfactory analogue or digital transmission. Consequently, careful adjustment of parameters such as group-delay equalisation of filters was needed. When this was done, a bit-error rate of about 1 in 10^6 was attained, which was random in nature and adequate, using error protection, for high-quality picture and sound transmission. Indeed, with this channel condition, the video and audio qualities were negligibly affected by transmission to and from the satellite. This was shown by bridging across the transmission path at the 70MHz i.f. stage or at the 60Mbit/s BBC/PO interface.

A brief comparison was made between the picture quality attained with the 60Mbit/s package using six bits per video sample (h.d.p.c.m.) and that with an analogue f.m. arrangement provided by the Post Office, virtually the full bandwidth of one transponder on the satellite being occupied in both cases. The consensus was that, although both picture qualities were very good, the digital picture was slightly better than the f.m. picture. The absolute impairment of the digital picture was known from previous research to be "just perceptible," the salient feature of the impairment being a small loss of diagonal resolution, a characteristic of sub-Nyquist sampling. The salient impairment of the f.m. picture was slightly increased chrominance noise.

Conclusions

The informal subjective assessments of picture and sound quality obtained during the experiments suggested the long-term possibility of attaining slightly higher quality using digital techniques rather than analogue f.m. techniques, without requiring additional r.f. bandwidth or incurring unacceptable interference between satellite channels. This possibility will be studied further in the broader context of efficient use of satellite channels having usable r.f. bandwidths both narrower and wider than the 36MHz used in these experiments. However, the current use of equipment employing f.m. transmission techniques, which provides a service even under degraded propagation conditions or in reduced bandwidth situations such as two television channels per 36MHz transponder, makes it unlikely that analogue f.m. will be superseded by digital techniques in the near future.

Acknowledgements. The author acknowledges the valuable contributions to the experimental work made by a large number of colleagues in the BBC

Research, Designs, and Communications Departments, and in the Telecommunications Development and Service Departments and External Telecommunications Executive of the UK Post Office. The permission of the BBC Director of Engineering to publish this paper is also acknowledged. The co-operation of the authorities responsible for Intelsat operations in providing free use of the satellite channel for the experiments was greatly appreciated.

References

1. Golding, L. S. 1972. DITEC — A digital television communications system for satellite links. Proceedings of the Second International Conference on Digital Satellite Communication. Paris, Editions Chiron, 1972, pp.384-397.
2. Osborne, D. W. 1976. Experimental digital transmission of multiplexed audio and video signals at 120Mbit/s. International Broadcasting Convention 1976. IEE Conference Publication No. 145, pp. 84-88.
3. Devereux, V. G. and Phillips, G. J. 1974. Bit-rate reduction of digital video signals using differential p.c.m. techniques. International Broadcasting Convention 1974. IEE Conference Publication No. 119, pp. 83-89.
4. Stott, J. H., Oliphant, A. and Osborne, D. W. 1974. Digital video: error-correcting codes and a practical study of a Wyner-Ash error-corrector. BBC Research Department Report No. 1974/40.
5. Croll, M. G., Osborne, D. W. and Spicer, C. R. 1974. Digital sound signals: the present BBC distribution system and a proposal for bit-rate reduction by digital companding. International Broadcasting Convention 1974. IEE Conference Publication No. 119, pp. 90-95.
6. Chambers, J. P. 1974. The use of digital techniques in television waveform generation. International Broadcasting Convention 1974. IEE Conference Publication No. 119, pp. 40-46.

High-fidelity Designs


The second edition of our popular collection of reprinted articles, High-Fidelity Designs, is now on sale. It is bigger, with twenty-five of the most popular articles on audio equipment and techniques that we have published in the last few years. Some of the material in the first edition has been kept, but most of the content is new, including David Read's tuners, the Dolby noise reducer, the Linsley Hood cassette deck and Doug Self's advanced preamplifier. Jack Dinsdale's and John Greenbank's horn loudspeakers are also printed again here. The book is obtainable from booksellers at £2.50 or direct from General Sales Department, Room 11, Dorset House, Stamford Street, London SE1 9LU, at £2.75 inclusive of postage and packing. Cheques and postal orders should be made out to IPC Business Press.

HF predictions

As an example of the use of the charts take reception of 14MHz. From South Africa the earliest that signals can be expected is 0500. Reception should always be possible between 0630 and 1830 but signal-to-noise ratio will be poor between 0730 and 1500. Fadeout will occur between 1830 and 2100.

From South America a skywave path should always be possible between 1100 and 2200 but a workable signal-to-noise ratio is likely only after 1900.

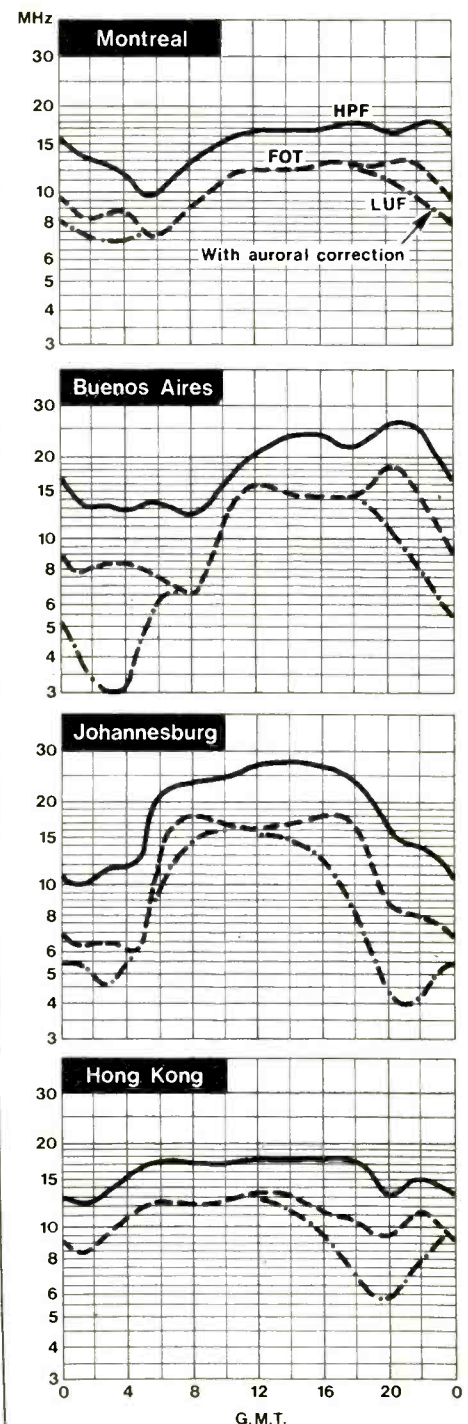Availability of North America and the Far East will be erratic with generally poor signal-to-noise ratios.



Eliminating adjacent-channel interference

by P. L. Taylor, M.A., F.I.E.E., F.I.M.A., *University of Salford*

Adjacent-channel interference between amplitude-modulated signals can be overcome, even when the carrier frequencies are so close together that the sideband of one signal overlaps the carrier of the other.

The problem of adjacent-channel interference has been with us almost since radio communication began. Fig. 1 illustrates the situation in which it arises: the carrier frequency of an unwanted amplitude-modulated signal U is too close to the carrier frequency of a wanted signal W . The result is that some of one sideband of U intrudes into the part of the spectrum occupied by W . A receiver tuned to W must have a pass-band sufficiently wide to accept the sidebands of W , and so cannot reject the unwanted sideband of U . The audible result, after detection, is unintelligible and annoying "sideband splash" or "monkey chatter" caused by the beating of the unwanted frequencies with the carrier of W .

If U is not too close to W , as in Fig. 1(a), then it is possible to design the receiver to accept only the "clean" sideband of W (which contains all the modulation information in itself) and to treat the result as a single-sideband signal; but this requires very sharp and precise filtering, which of course is expensive. If the two carrier frequencies are as close together as is shown in Fig. 1(b) it has been generally

Fig. 1. If the carrier of an unwanted signal U is too close to that of a wanted signal W there is interference. In case (a) it is possible to filter out the "clean" sideband of W . Up to now it has been thought that nothing could be done in a situation such as (b).

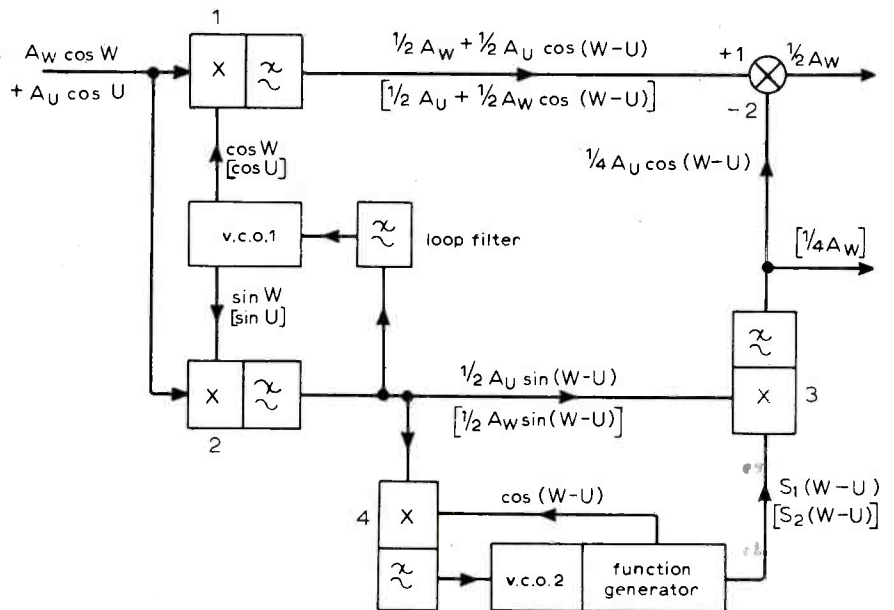
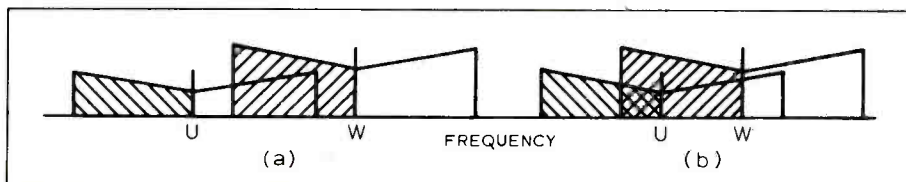


Fig. 2. Block diagram for both methods of overcoming interference.

thought that there is nothing one can do about the situation. In addition to the monkey chatter one must put up with an inter-carrier whistle at the difference frequency between the two carriers.

Here are two methods^{1,2} which provide solutions to the problem. Both begin with synchronous demodulation of the wanted signal, as in the homodyne and synchrodyne receivers.† For brevity, the wanted signal will be represented by $A_W \cos W$, where $W = 2\pi f_w t$, f_w being the frequency of the wanted carrier. Similarly, the unwanted signal will be represented by $A_U \cos U$. We want to recover A_W , uncontaminated by A_U .

In synchronous demodulation, the

wanted carrier is multiplied by an oscillation having exactly the same frequency and phase. The result is

$$A_W \cos W \times \cos W = \frac{1}{2} A_W + \frac{1}{2} A_W \cos 2W$$

(Table I may be a helpful reminder).

Thus the wanted signal A_W is recovered, together with an oscillation at twice the carrier frequency, which is easily removed by filtering.

Table I

$$\begin{aligned} \cos A \cos B &= \frac{1}{2} \cos(A-B) + \frac{1}{2} \cos(A+B) \\ \sin A \sin B &= \frac{1}{2} \cos(A-B) - \frac{1}{2} \cos(A+B) \\ \sin A \cos B &= -\frac{1}{2} \sin(A-B) + \frac{1}{2} \sin(A+B) \end{aligned}$$

$$\cos(-C) = \cos C; \sin(-C) = -\sin C$$

First method

Figure 2 is the block diagram, in which the expressions in square brackets should be ignored, since they relate to

† This is history repeating itself. When Professor Tucker did his work on the synchrodyne he was led to consider the present problem, and suggested an approximate solution. Some while ago the author was casting round for projects for his final-year undergraduate students and thought it might be interesting to see what could be made of the synchrodyne using modern technology. He, too, was led to consider the problem; this time the suggested solution is exact.

the second method. The combined signals are applied to demodulator 1, where they are multiplied by $\cos W$. The output of this demodulator (after filtering) is now $\frac{1}{2}A_W + \frac{1}{2}A_U \cos(W-U)$. The second term in this expression is the audible interference. The multiplier $\cos W$ is obtained from a voltage-controlled oscillator VCO₁ which is phase-locked to the wanted carrier via demodulator 2. VCO₁ produces quadrature outputs. The phase-lock loop will settle itself so that the v.c.o. output which is presented to demodulator 2 is in quadrature with the wanted signal, so this output must be represented by $\sin W$ and the quadrature output will be $\cos W$. It is arranged that when capture has occurred the loop bandwidth is reduced to about 1Hz by extra filtering so that the oscillator is not disturbed by the other frequencies present in the signals. Also, the loop includes an integrator so that the phasing is exact.

Now the output of demodulator 2 contains the component $\frac{1}{2}A_U \sin(W-U)$, but no component involving A_W . The clue is too obvious to be missed: if the phase of this oscillation could be changed from $\sin(W-U)$ to $\cos(W-U)$ it could be used to cancel the unwanted component in the output of demodulator 1. This could be done by multiplying, in a third demodulator, by $\sin 2(W-U)$:

$$\frac{1}{2}A_U \sin(W-U) \times \sin 2(W-U) = \frac{1}{4}A_U \cos(W-U) - \frac{1}{4}A_U \cos 3(W-U)$$

Thus the desired phase-shifting has been accomplished but at the cost of introducing a 3rd-harmonic oscillation, and, if $(W-U)$ is small, it may not be possible to filter it out. But if $\frac{1}{2}A_U \sin(W-U)$ is multiplied by the series

$$S_1(W-U) = \sin 2(W-U) + \sin 4(W-U) + \dots + \sin 2n(W-U),$$

the result is:

$$\frac{1}{4}A_U \sin(W-U) S_1(W-U) = \frac{1}{4}A_U \cos(W-U) - \frac{1}{4}A_U \cos(2n+1)(W-U).$$

The intermediate products give rise to sum- and difference-frequency terms which cancel, leaving the interfering oscillation at a frequency which may be made as high as desired by a suitable choice of n ; this oscillation may now be filtered out easily. Thus, the desired cancellation signal is obtained, and processing is completed as shown in Fig. 2.

A waveform, whose Fourier series components form $S_1(W-U)$, is obtained from a function generator which is described later. The generator is phase-locked via VCO₂ and demodulator 4 to the beat frequency $(W-U)$. Note that the series S_1 is one in which all the first $(n-1)$ harmonics are equal in amplitude to the fundamental, which has a frequency twice that of the beat frequency.

Second method

If the unwanted signal is stronger than the wanted signal it will probably be easier to lock VCO₁ on to the unwanted carrier, so that (taking the expressions in brackets in Fig. 2) the output of demodulator 2 becomes $\frac{1}{2}A_W \sin(W-U)$. Thus, the unwanted signal is rejected directly at this stage, but the problem now is that the wanted signal is modulated on a carrier frequency that lies within the audio range.

The wanted signal could be demodulated by multiplying by $\sin(W-U)$:

$$\frac{1}{2}A_W \sin(W-U) \times \sin(W-U) = \frac{1}{4}A_W - \frac{1}{4}A_W \cos 2(W-U)$$

but this introduces an interfering oscillation, at twice the beat frequency, which may still be too low to filter out. But if $\frac{1}{2}A_W \sin(W-U)$ is multiplied by the series

$$S_2(W-U) = \sin(W-U) + \sin 2(W-U) + \dots + \sin(2n+1)(W-U)$$

the result is

$$\frac{1}{2}A_W \sin(W-U) S_2(W-U) = \frac{1}{4}A_W - \frac{1}{4}A_W \cos(2n+2)(W-U).$$

The intermediate products give rise to sum- and difference-frequency terms which cancel, leaving the interfering oscillation at a frequency which may be made as high as desired by suitable choice of n ; it is thus easily filtered out. In this method the wanted signal is taken from the output of demodulator 3.

Function generation

It would be possible to generate the series S_1 or S_2 by taking a number of oscillators, of appropriate harmonic frequencies, and phase-locking them together and to the beat frequency $(W-U)$. But this would be clumsy, and would also require that the demodulator 3 should be a true multiplier. The simplicity of a switching demodulator may be retained as follows.

In normal use a switching demodulator acts to change the sign of the signal to be demodulated in step with alternate half-cycles of the multiplier oscillation. That is, it effectively multiplies the signal by a square wave switching function f , drawn as the solid line in Fig. 3, which alternates between the values $+1$ and -1 with the same period T as the

multiplier oscillation. As drawn in Fig. 3, the function f is odd (in the mathematical sense), that is, $f(-t) = -f(t)$, and the graph has rotational symmetry about the point $t=0$. Hence its Fourier series consists of odd functions (sine terms) only:

$$f(t) = \frac{4}{\pi} \left[\frac{2\pi}{T} + \frac{1}{3} \sin 3 \frac{2\pi}{T} + \frac{1}{5} \sin 5 \frac{2\pi}{T} + \dots \right]$$

Thus, the demodulator does multiply the signal by the required frequency (the first term in the series). It also multiplies by the higher frequencies in the series, but the results are usually filtered out.

Now, suppose that two extra edges are introduced, at t_1 and t_2 , to give the dotted wave. Since S_1 consists only of sine terms the rotational symmetry must be preserved, by introducing corresponding edges at $-t_1$ and $-t_2$. Now t_1 and t_2 can be chosen at will; the question is, can we choose them so that the first two harmonics of the new waveform have amplitudes equal to the fundamental? The answer is yes, and the result is quite general: if n extra edges are introduced, then the first n harmonics can be made to have amplitudes equal to the fundamental.


The correct instants t_1, t_2, \dots, t_n are found as follows. The expression for the Fourier series of the new waveform is found in the usual way, and from it the conditions that the coefficients of the first n harmonics shall be equal are found. This results in a set of simultaneous equations in the unknown t . However, the equations are non-linear, so the solution of them is best entrusted to a computer.

Thus a square waveform can be designed such that the first terms in its Fourier series form S_1 . A similar argument leads to a waveform the terms of which form S_2 . There is a small complication in this case because only the odd harmonics are required. Both series continue with higher-order terms, but these do not matter because the unwanted products to which they give rise will be filtered out anyway.

The waveforms may be generated quite easily by digital techniques. VCO₂ is made a high-frequency oscillator, the cycles of which are presented to a digital counter. The counter output is presented in turn to a number of digital comparators (one for each edge) which are hard-wired with numbers defining the instants at which the edges occur. Whenever a coincidence is detected, an edge is generated by triggering a bi-stable.

In an alternative method, numbers representing the differences between successive edges are placed in a read-only memory (r.o.m.). A presettable counter is loaded with the first number, and is counted down to zero by VCO₂. When zero is reached an edge is generated, the number in the next address in the r.o.m. is loaded into the counter and so on until the cycle is

Fig. 3. Illustrating the derivation of the special switching functions.

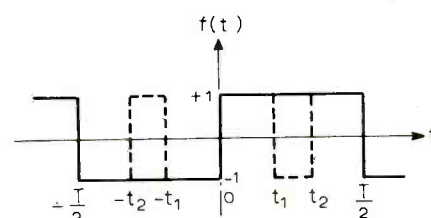

completed and control is returned to the first address in the r.o.m. This method is more economical of hardware, and more flexible because the numbers for several series can be stored in one r.o.m. Any waveform can be selected simply by choosing the appropriate starting address.

Sidebands

Though the mathematical analysis given above indicates that the methods should work, and experiment shows that they do work, it is not so far clear exactly how it is that the overlapping sidebands are disentangled.

Take as an example the first method. Suppose that initially VCO_1 has not locked on to the wanted signal, but is running at some frequency F higher than W . The output of both demodulators 1 and 2 is a group of signals at the sum- and difference-frequencies, as in Fig. 4(a). Only the lower frequency group is retained; the other is eliminated by the low-pass filter.

Now suppose that F is reduced towards W . The lower frequency group moves towards zero frequency and a stage is reached when some of the sideband frequencies of the wanted signal should become negative, as shown at (i) in Fig. 4(b). The practical effect differs in the two demodulators. In the case of demodulator 1 the product is $\cos W \times \cos F$, and therefore is also a cosine. The cosine of a negative quantity is the same as the cosine of the same positive quantity (see Table I) so the negative frequency components are reflected about zero frequency, without change of sign, to become positive frequency components as shown at (ii). In demodulator 2, which is multiplying $\cos W \times \sin F$, the output is a sine; and the sine of a negative quantity is minus the sine of the same positive quantity, so in this case the reflected components must be shown as negative, as at (iii).

Finally, let F be reduced to equal W so that VCO_1 locks. In the output of demodulator 1 the lower sideband of the wanted signal folds back to reinforce the upper sideband, and both now start from zero frequency, i.e. the wanted signal is demodulated. This is shown in Fig. 4(c). The unwanted signal is modulated on to the beat frequency $(W-U)$ and its lower sideband is folded back. In the output of demodulator 2, Fig. 4(d), the sidebands of the wanted signal exactly cancel each other, being of opposite sign, so the wanted signal does not appear in the output of this demodulator.

Now consider the effect of multiplying (d) by the series S_1 . The resulting spectrum of the output of demodulator 3 is shown at (e). First, there are sum- and difference-components centred on the frequency of the first term in the series, $2(W-U)$. We are now dealing with a sine \times sine product, which is a cosine, so the part of the lowest sideband which is partially reflected about zero is reflected without change

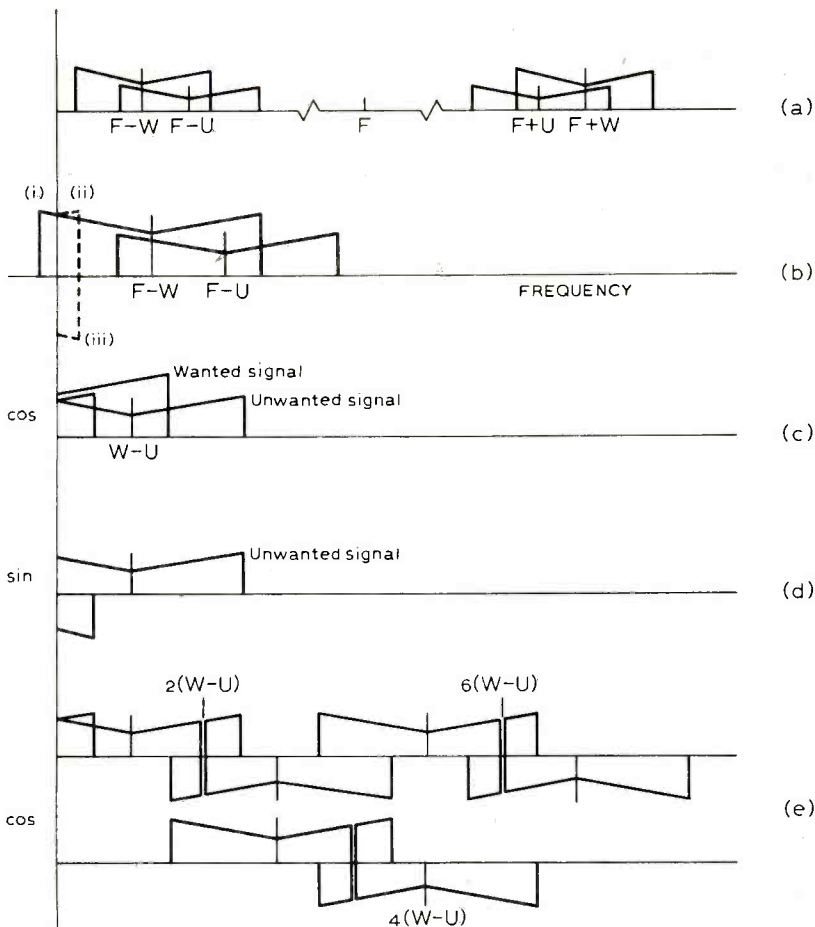


Fig. 4. (a) Result of multiplying the incoming signals by a frequency F greater than W . (b) If F is only slightly greater than W some reflection of the lower sideband occurs. (c), (d) Outputs of demodulators 1 and 2 respectively when $F = W$. (e) The result of multiplying (d) by the series S_1 .

of sign; and the sum-frequency components have a negative sign.

For clarity, the sum- and difference-frequency components centred on the frequency of the next term, $4(W-U)$, are shown on a lower line. The diagram is drawn for the case where it is necessary to go only as far as the third term in the series, of frequency $6(W-U)$. When all the various bands are added together there is a lot of mutual cancellation; there are left only the lowest group of frequencies, which are now of the right form for subtraction from (c), and the highest group; in between there is a big gap, so that filtering out the highest group is easy.

The foregoing description makes it clear that the methods are really exploiting the fact that an a.m. signal has two symmetrical sidebands to effect mutual cancellation of unwanted signals. It is also clear that the cancellation will be less than exact if the sidebands suffer differential gain and/or phase shift in their passage through the r.f. and i.f. stages of a receiver. It is unlikely,

therefore, that these methods will form a satisfactory basis for an "add-on" unit for an existing receiver, in which these aspects of performance will probably not have received much attention. It is also clear that, unfortunately, they will not work for s.s.b.!

I am very grateful to Mr L. J. Unsworth for constructing the experimental apparatus in which these ideas were tested.

References

1. Patent applied for.
2. Taylor, P. L. 'Methods of separating overlapping amplitude-modulated signals', *Electronics Letters*, 19th August 1976, **12**, 17, pp. 424-425.
3. Tucker, D. G. 'The history of the homodyne and synchrodyne', *J. Brit. I.R.E.*, April 1954, **14**, pp. 143-154.

Space shuttle comms

The Battelle Institute say the communications industry could save millions of dollars in the 1980s if their satellites used the space transportation system of which the shuttle is a part. A NASA funded study is being carried out at Battelle's Columbus Laboratories with five satellite manufacturers to make their systems compatible with s.t.s.

Letters to the Editor

ANNAN AND CABLE

The Annan Committee was asked to report, among other things, on the future technology of broadcasting and any changes in organisation which would be required as a result. It was perhaps a silly question to put to a group of academics, politicians, trade unionists and assorted odd bodies and it has drawn a silly answer. At the time of its appointment some senior engineers in broadcasting recommended that it should have a technical sub-committee which could keep it straight on the facts and prevent it from having the wool pulled over its eyes by important people with their own interests to serve. That this, unfortunately — but inevitably — has happened is shown most clearly by the Committee's report on cable. They accept, quite correctly, that the future of broadcasting lies primarily in cable and that the next 15 years will be the swan-song of conventional broadcasting (paragraph 25.2); but they provide no guidance as to how the inevitable transfer from wireless to wire might be made and prefer to leave it all to the woolly generalisation of the Post Office about the possibilities of integrated national networks in the late 1990s.

How little they have understood the technology of cable is clear from their reference (paragraph 25.41) to broad band Post Office systems on the one hand and private narrow band networks on the other. The Post Office system in Milton Keynes, to which so much importance is attached, is a conventional f.d.m. type using a v.h.f. trunk network with final distribution at v.h.f. for 405 lines and sound programmes and at u.h.f. for 625 lines. It is no "broader" than anybody else's network of that type and nothing like as "broad" as the switched h.f. system which has been developed in the private sector.

In short, the Committee was overcome by the air of unchallengeable authority in which the Post Office managed to present themselves and refused to allow that the people of this country should be permitted — while waiting for the Post Office's new millennium — to pay the existing cable operators for a wider choice of programmes if they wanted to. In spite of all their expressed desire for diversity and the claim that "we act in accordance with the concept of pluralism which has been the leitmotiv of all of us in this Report", they have rejected for no discernible reason the one immediate possibility of achieving those ends. A possibility, moreover, which involves no cost to anybody except those who wish to pay for more diversity and those who are prepared to risk their own money in providing it.

This is the answer to those, including both Annan and yourself in last month's issue, who quote the cost of a national broad band network from the Technical Sub-Committee of the Television Advisory Committee and rule it all out because we cannot afford a billion. Nobody is suggesting we should but, even so, it does not sound so much when related to the 6 billion which we are cheerfully spending to equip ourselves for colour. What is suggested is that the investment already made in networks with a capacity of six channels or more should be put to use so that the public can decide what extra services, if any, it will support. When we know that, the basis of any further investment in cable will be secure.

Having recognised both the importance of cable for the future and the need to conserve the frequency spectrum, one might have expected the Committee to look with some care at the proposal that the remains of Phase I of the u.h.f. transmitter programme covering groups of population exceeding 1,000 and Phase II for populations between 500 and 1,000, might employ wire instead of wireless wherever it was simpler and cheaper to do so. This proposal was first made by the TAC/TSC in 1972 and was supported by the Crawford Committee in November 1974. Nothing has happened, mainly because there is a genuine difficulty about how such cable networks might be financed. Everyone concerned had hoped that the Annan Committee might make some sensible recommendation for finance and administration but all they do is to propose that Phase II should be completed at once by transmitters at a cost of £114 per person or over £300 per home covered. That is around five times as much as it would cost to do the job by cable which would also avoid altogether the need for still more space for broadcasting in the frequency spectrum. Here again, they have simply bowed to the authority of the BBC with its insatiable appetite for the frequency spectrum and its determined view of cable as a rival instead of an ally and a source of extra revenue for them which it so easily could be.

As you say, the proposal for a telecommunications advisory committee to determine national policy for all telecommunications, not only broadcasting, is overdue and very welcome. Considering its importance and the intensity of the opposition such a proposal will meet from the heavily entrenched broadcasting and telecommunications establishments, it is a pity that the Committee did not devote more than the odd paragraph or two to the reasons for it and the form it should take.

R. P. Gabriel,
Rediffusion Ltd,
London, SW1.

IMPROVING MATRIX H SURROUND-SOUND?

Reading the surround-sound articles in *Wireless World*, 45J by Michael Gerzon in April 1977, and Matrix H by Dr P. A. Ratliff and D. J. Meares in May 1977, it is apparent that the main difference between the two systems is the effect of the coding of the back sector sounds.

In Matrix H the better mono and stereo compatibility of a bent locus is considered more important, whilst in 45J the listener with a surround-sound decoder is favoured

with the improved side image localization and ambience reproduction of a circle locus (whose side view on the energy sphere is a straight line).

Those who have to choose between the two systems will resort, inevitably, to decision by committee.

However, Michael Gerzon mentions other properties of 45J coding which are not referred to in the BBC article and which, if incorporated, might offer in improvement to Matrix H coding. If my understanding is correct they are:

1. Reduce the centre-front interchannel phase angle from 48° to 45° to improve the stereo phasiness of front-sector sounds and to improve mono compatibility.

2. Reduce the curvature of the pan locus until it just touches the "speaker position" curve and, therefore, no longer goes through the left-only and right-only points. If the circle locus of 45J is better than a bent locus for ambience reproduction, it is intuitively obvious that reducing the curvature of the Matrix H locus will improve its ambience reproduction.

3. Optimize the distribution of the different encoded directions within the elliptical cross-section of the pan locus, to improve the reproduced ambience in surround-sound and to widen the stereo presentation for front stage sounds and, therefore, improve the stereo compatibility.

Perhaps the BBC men would be kind enough to comment, favourably or otherwise.

Andrew Sturt,
London Weekend Television,
London, SE1.

RADIO SETS OF THE FUTURE

Further to the interesting article by Duncan MacEwan in the May issue ("Radio in the '80s"), the following observations come to mind.

The average listener to the portable radio of today probably doesn't find station finding very difficult, and just listens to background music on Radio 1 or 2 all the time.

Is there really a need for a "better" portable set with improved f.m. reception (for the serious listener)? This probably couldn't be all that cheap: for a few pounds more he or she could obtain a budget priced hi-fi tuner-amplifier and get far better results if "serious" music listening is the object.

What I suggest we do not need is legislation, the effect of which is costly, and multi-channel push-button complicated receivers that are not wanted or necessary, that could spring into life when the great gods news and sport come on the air every few minutes!

There is room for improved, easily readable printed information on programmes: the poor design, layout, typography and general presentation of the *Radio Times* is perhaps the obvious example.

E. Gilbert,
London N18.

Mr MacEwan replies:

I think Mr Gilbert may be overestimating people's ability to find their way around the crowded dial; certainly our own extensive Audience Research supports this. Radio has

to be interested in not only the average listener, but in the others including potential listeners. Radio 3 has a weekly patronage figure of 5 million people, Radio 4 a daily following of 6 million and Local Radio about 2 million; the BBC has no wish to neglect what our correspondent might regard as minorities – quite the reverse.

I believe there is a growing market for the higher quality portable – listening in the kitchen, study or bedroom should surely not be confined to narrow band a.m. transmissions or limited to daylight hours – and what of the music lover, those following educational courses, etc. Radio today is very much about choice – choice of programme and choice of quality.

On the *Radio Times* issue he makes a fair point, but the truth of the matter is that the extra page (or even two pages which would be necessary to meet his wishes and mine) would change the journal's balance sheet from a fairly healthy if faint black colour to a very bright red and that the BBC cannot afford.

Duncan MacEwan.

DIGITAL FILTERS USING MICROPROCESSORS

It was with great interest that I read recently V. J. Rees' article "Digital filter design" in your October 1976 issue. I am impressed with much of what he said. With a variety of digital filtration algorithms available, it is indeed useful to check out the response to a simple sawtooth or square-wave input, whether aided by calculator or computer. Not only does this, as Gérald Garon (Letters, May issue) indicates, increase understanding, it may also point out some of the pitfalls. In V. J. Rees' example the input was a $\pm 10V$ 50Hz sawtooth, the single-pole low-pass filter had a turnover frequency of $180/\pi$ Hz and the sampling period was 1ms. In Fig. 1 I have drawn the actual filter response as the smooth solid curve. The algorithm used by V. J. Rees was:

$$V_0 = AV_1 + BV_0' \quad (1)$$

with $A = \tau/CR = k$, and $B = e^{-\tau/CR} = e^{-k}$, where V_1 and V_0 are the input and output voltages for the present sample, V_0' is the output in the previous sample, τ is the

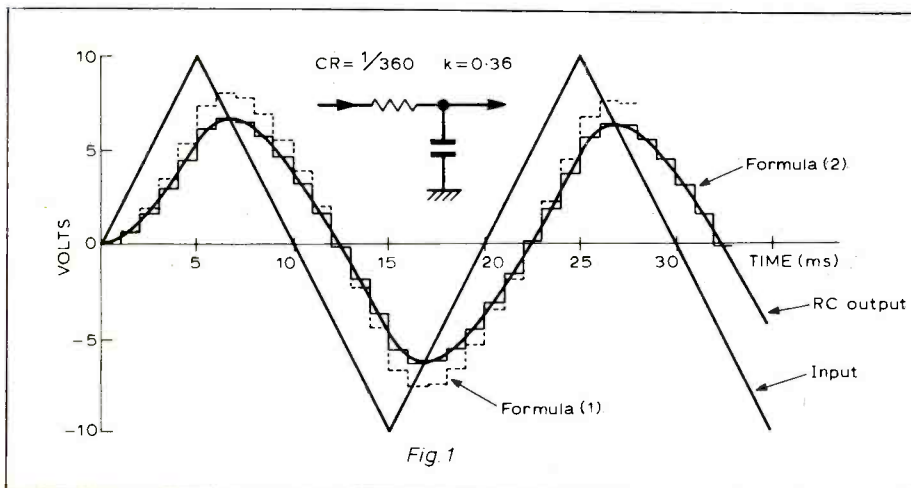


Fig 1

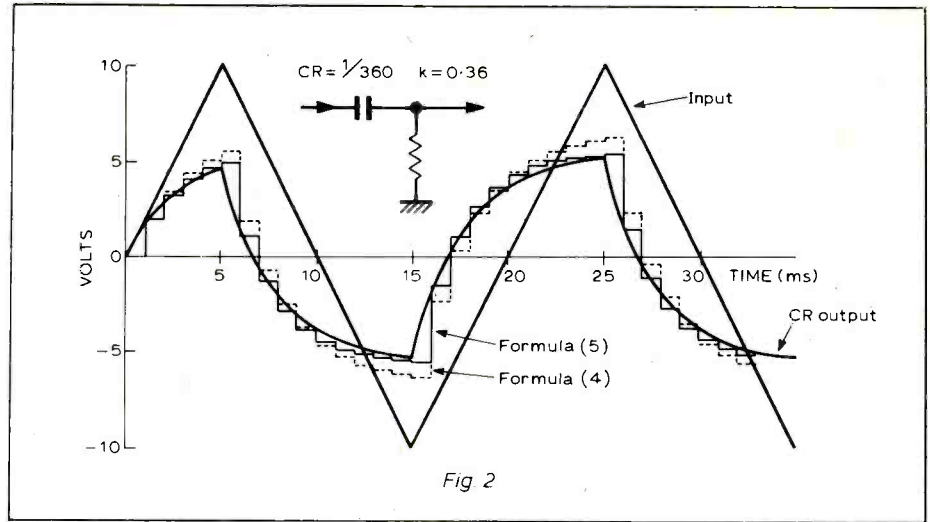


Fig 2

sampling period and CR the time constant of the filter. Taking V. J. Rees' figures, I have plotted out the result of formula (1) as a staircase – as the output of one's d.-to-a. converter would be. The error at the peaks is over 20%. The performance of formula (1) would indeed correspond to the theoretical curve if k were small – like 0.01. In practice one can rarely afford the luxury of such a high sampling rate. Normally, either one's computer is too slow or a great deal of other real-time signal processing is required as well as the filtration.

An alternative low pass algorithm is as follows:

$$V_0 = AV_1 + BV_0' \quad (2)$$

with $A = 1 - e^{-k}$, $B = e^{-k}$ and $k = \tau/CR$.

The performance of this formula is shown as the solid staircase in Fig. 1. Not only is formula (2) much more accurate at sizeable values of k but, as shown by Gérald Garon, it is also faster when rearranged to use only one multiplication:

$$V_0 = 1 - C(V - V_0') \quad (3)$$

with $C = e^{-k}$ Gérald Garon also obtained in his elegant M6800 programme a "high pass" output as well as the low pass output of formula (3). This high pass algorithm may be written:

$$V_0 = V_1 - V_1' + BV_0 \quad (4)$$

with $B = e^{-k}$ where V_1' is input in previous sample (4)

In Fig. 2 I have again used the sawtooth input and kept τ and CR at the same 1ms and $1/360$ respectively. Again the response of the capacitor and resistor high pass filter is shown as the solid curve (also courtesy a PD P12). The effect of formula (4) is indicated by the dotted

staircase. Once more there are errors of nearly 20% at the peaks. A rather more accurate high pass formula that still only requires one multiplication is:

$$V_0 = V_1 - V_1' + BV_0' \quad \text{with } B = 1 - k \quad (5)$$

Formula (5) is plotted as the solid staircase in Fig. 2 – the errors at the peaks seem to be around 4%.

Finally, I'd just like to add the filtration of e.g. to the list of applications where a "slow" microprocessor like the M6800 has proved adequate. In a 2ms sampling period there is still plenty of time left over for other useful processing.

T. A. Perkins,
MRC Neurological Prostheses Unit,
London, SE5.

REVIVING NICKEL-CADMIUM CELLS

I ran across Mr Johnson's article on reviving NiCd cells in the February issue and used the method successfully to rejuvenate a set of four cells which had been in the discard bin for some months.

These four AA cells had perished when a young visitor left my pocket calculator on, a fact which went unnoticed for a week or so. When I found they would then not hold a charge, they were replaced and left on the back of the bench for about six months. After reading the article, I checked them and, sure enough, each cell was shorted and read zero volts.

I first processed one cell as described, with a battery charger as the current source and an ammeter as the load – the only deviation being that the low-current was removed during the high-current phases. The cell came "unstuck" after the first jolt, eventually responded to the overcharge state, and provided 500 mAh on slow discharge. I then processed the other three cells as a series unit and achieved the same results, in much less time than it would have taken to do each one individually. Perhaps I was fortunate in having cells in approximately the same condition.

After a 24-hour normal 50mA charge, all four cells in series were drained across a dummy load at 50mA, and lasted close to eleven hours, with the No. 1 cell going dead

first. Two more charge-discharge cycles were then tried, this time with a portable radio drawing 10-15 mA as a load; with intermittent use of 4-5 hours per day, the cells provided approximately 500mAh each time, with the No 2 cell going dead first in these cases. Fully charged voltage was 1.30V (1.35 in overcharged state); at the time of one cell going down the remaining three read 1.25-1.27V.

The cells are completely anonymous, no type of manufacturer's marking, so I do not know what quality they represent. The fact is, though, that thanks to Mr Johnson's article, they represent a handsome salvage.

B. G. Doutre,
Montreal,
Quebec, Canada.

LONG WAVES FOR AMATEURS?

Mr May's announcement (Letters, May issue) that he is "normally in favour of amateur radio" must have caused all amateurs to read the rest of his letter with justifiable suspicion.

His present approval, or disapproval, of us appears to be based on a lamentable lack of research. It is a shame to see in the pages of *Wireless World* the suggestion that amateur radio is "just for low power local broadcasting." We will happily accept the accusation that we use low power, indeed we do so with a certain pride in our aerial systems and operating techniques. On the other hand we must point out that contacts with the antipodes are routine and that amateur signals have been bounced off the Moon, which is hardly local! The use of the term "broadcasting" instead of "transmitting" displays an almost unbelievable ignorance and must have upset many people, including, no doubt, some at the Home Office.

In reply to Mr May's warning about interference, we can only point out that amateurs have learnt to live with interference from domestic machines and broadcast stations as well as from each other. We often operate on channels the professionals would describe as unusable.

It may be recalled that in the early days of radio the amateurs were given frequencies thought to be too high for "serious" use. It is tempting, but inaccurate, to draw a parallel here; we merely suggest that anyone truly concerned that the very low frequencies are being underrated could do worse than give them to radio amateurs.

N. R. W. Long (G4BIN), J. G. Morgan (G3ZHL)
and R. A. L. Williams (G4EAL),
Cambridge University Wireless Society.

INTERFERENCE FROM AMATEUR STATIONS

Sporadic listening to professional usage of the "ether" leaves me with the impression that interference by amateurs is but a drop in the ocean of the problem as a whole. I look forward anyway to the second part of the article by I. Jackson in the issue of March 1977 [see June issue — Ed.]. In the meantime, you can see from the enclosed cutting from the *Electrician* of February 9, 1912, that, like the poor, interference by amateurs has always been with us.

"Wireless Telegraph Notes. — The *Electrical World*" states that an investigation of the extent of interference by amateur wireless-telegraph operators in the transmission of legitimate messages between ship and shore stations has been undertaken by the United States Navy Department. The immediate cause of the investigation was a delay of more than one hour in the transmission of messages of distress from the torpedo-boat destroyer "Terry". During this delay the wireless-telegraph apparatus on the vessel was disabled, and the exact position of the ship in distress could not be ascertained. It is estimated that at least 500 stations are in use and owned by amateur operators in the neighbourhood of New York."

Or is it that amateurs have always been a vulnerable minority, and therefore a convenient scapegoat? Having no personal involvement, I could wish only that all users of the radio spectrum would turn over a new leaf, starting with the commercial stations that sit on top of the standard frequency transmissions. Blatant use of 2182kHz for personal chit-chat during the silent listening periods is not at all uncommon, almost certainly maritime mobile users fouling their own nest. And yet there are parts of the radio spectrum which get very little use at all!

Desmond Thackeray,
Department of Chemical Physics,
University of Surrey,
Guildford.

AURAL SENSITIVITY TO PHASE

Though I believe that the effects of phase shift on the waveform and the sound quality of the signal in a monaural channel are of no importance provided that the concomitant time delays stay within the CCIR limits, Mr Lipshitz's letter in the May issue draws attention to one of the many situations where phase shifts are of importance in their effect on sound quality. There are many others.

It has long been the practice of amplifier designers to arrange for the compensation of distortion between the stages in an amplifier by adjusting the operating conditions of successive stages to allow the distortion introduced by one stage to be reduced by the introduction of distortion in the opposite phase by the following stage, the explanation of Mr Lipshitz's results. Similarly, it has been the practice of recording engineers to minimise the peak signal amplitudes and hence the amplitude dependent distortions by appropriate phasing of the signal components. These phase dependent distortion compensating effects make it difficult to measure and specify the amplitude distortion in any good f.m. receiver. The distortion introduced by the best signal generators is of the same order as that introduced by the best current receivers and in consequence the measured overall distortion may vary between almost zero and twice that introduced by the receiver, depending upon the relative phase of the distortion introduced by generator and tuner.

The sound quality of a loudspeaker is subtly dependent upon the relative polarity (phase) of the studio microphone and the listener's loudspeaker but, unless equipment of professional quality is used throughout, the effect is extremely difficult to detect, in

part because it is critically dependent upon volume setting.

These are some of the many situations where phase shifts may introduce audible effects but little use can be made of this by the ordinary user, for the distortion cancellation is dependent upon the relative phase and relative amplitude of the recorder-reproducer distortions.

Mr Lipshitz's letter draws attention to a situation where nature anticipated engineers in this practice of distortion cancellation. It has long been known that the negative and positive peaks in ordinary conversation speech are of unequal amplitude, but nature apparently arranged this to compensate for the non-linear stiffness relation of the ear drum. Which effect came first is difficult to identify.

James Moir,
Chipperfield,
Herts.

I suggest that if one regards the ear as a non-linear transducer followed by a set of high-Q tuned circuits each driving a mean amplitude meter, the outputs of which are separately sent to the brain, all arguments are resolved and all observations and tests accounted for, are they not?

As far as the brain is concerned it only receives one parameter for each frequency, namely amplitude of the signal arriving at the resonator; it receives no information concerning phase. However, when a sine wave arrives at the ear, because of non-linearity it produces its own harmonics. If now for example a given amplitude of second harmonic is added to the signal this will be reinforced or reduced in amplitude by the time it reaches the inner ear by the harmonic of the original signal produced by the distortion of the first stage of the ear. In this sense the ear is phase sensitive, as altering the phase of the 2nd harmonic fed to the outer ear alters the amplitude of the second harmonic received by the inner ear.

If, however, we have a generator in which we can control the amplitude of all the harmonics, after altering the phase of one or more we can usually by altering the amplitude only of these and the other harmonics apparently reproduce the original sound. This is because changes in amplitude of applied signal correct for the changed cancellation reinforcement pattern of the "ear produced" harmonics. In this sense the ear is not phase sensitive.

There are cases when this is not true. If for example the amount of second harmonic applied is of the right amplitude and phase to cancel the ear-produced 2nd harmonic, the amount of this arriving at the inner ear will be nil. If we now alter the phase of the 2nd harmonic from our speaker, cancellation will no longer take place and second harmonic will reach the inner ear. No amount of change of amplitude will cause the amount of second harmonic reaching the inner ear to be reduced to zero.

One cannot answer the question "is the ear sensitive to phase?" by a yes/no answer, only by "the inner ear is insensitive to phase but the outer ear distorts".

J. H. Asbery,
Wembley,
Middlesex.

Perhaps I may be allowed to reply to Mr Coleman's letter in the February 1977 issue, even in isolation from the long correspondence on aural phase sensitivity. There is, I

think, very little in that letter which relates to his earlier convictions (as expressed in September 1976 letters), whilst those few points he chooses to expand from my reply in December 1976 show further misconceptions or even mistakes.

The phasor representation of amplitude and angle defines the variation of output amplitude and phase of a linear realisable system to an input sinusoid, to which it is responding in the steady-state. In this condition, any characteristic phase advance or delay may be assigned. The concept may be extended to isolated waveforms, wherein the Fourier Integral allows the response of the system in the transient state to be described in terms of its steady-state characteristics. There are cases, for example in simultaneous amplitude and angle modulation, where the concept of instantaneous phase may be defined, though this cannot be done simply by specifying an elementary reference time. If Mr Coleman wishes to attach any meaning to system phase other than the widely accepted one, he should specify the conditions and give his own reasons for doing so.

I am content to be identified with James Moir, in a commonsense approach to resolving any problem; in teaching or in research, to picture a problem in another domain may help its understanding, which is advantageous. Commonsense is not born of ignorance, as Mr Coleman would seem to baffle your readers into accepting; it is a quality by which the truly knowledgeable scientist may be distinguished from the untrained academic mind.

My grasp of basic principles is not so uncertain that I could believe Coleman's claim that "tone bursts which differ in the framing of phase of the sine wave with respect to the burst envelope have spectra of different shapes." A little commonsense would reveal that by shifting the carrier with respect to the pulse train in this waveform a simple linear phase shift of all spectral lines is produced, as was the purpose of my experiment. Hence it is Mr Coleman's conclusions which are invalid, not mine.

Roger C. Driscoll,
The Polytechnic of North London,
London, N7.

TRANSIENT INTERMODULATION DISTORTION

I would like to comment on the very informative article on transient intermodulation distortion by Bert Sundqvist published in your February 1977 issue.

He has shown by analysis that in order to prevent transient intermodulation distortion in an amplifier, the method proposed by Professor M. Otala¹ (that of extended open-loop bandwidth in the power amplifier with subsequent passive band limiting in the preamplifier) need not be adhered to rigidly and the simpler method of band limiting the first stage of the amplifier achieves the same result. He suggested three methods for producing this band limiting: (1) input lag compensation, (2) use of a high-impedance current source as collector load, (3) operation of the first stage with a very low collector current. Of these, however, only the third seems to be new, as far as preventing transient intermodulation distortion is concerned.

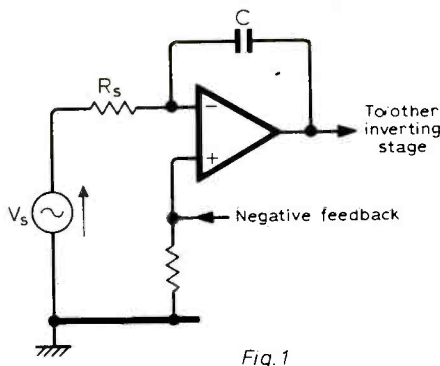


Fig. 1

To see why this is so, consider the frequency limiting mechanisms at work in the basic common emitter stage. There are mainly two. Firstly, the transfer mechanism, which is a physical motion of charge carriers, introduces dispersion and delay of the carriers and this results in the fall off of current gain (produces f_t). Secondly, existing between the various terminals of the transistor are frequency dependent impedances that are predominantly capacitive and these contribute to frequency limiting.

Considering Fig. 1, C represents the collector to base capacitance of the common emitter stage. Using Miller's theorem, this capacitance can be replaced by C_1 and C_2 as shown in Fig. 2, where A_v is the voltage gain between the inverting input and output

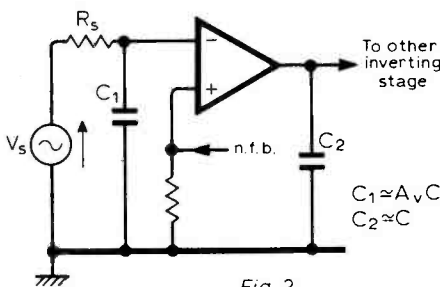


Fig. 2

(corresponding to the base and collector of the transistor). The time constant introduced by R_s and C_1 produces a dominant pole, and in general this is the mechanism that produces frequency roll-off in the common emitter stage. Input stage lag compensation increases C and a very high-impedance collector load increases A_v . Both result in a reduction of the bandwidth of the resulting input RC network. However, this RC network lies outside the loop of the feedback amplifier of which this stage is a part and indeed corresponds to the passive RC filter that Professor Otala recommends be placed before the input of power amplifiers in order to prevent the transmission of frequencies outside their open-loop bandwidths.

Thus, the only new technique which the results of Mr Sundqvist's analysis has uncovered is the reduction of the cut-off frequency of the input transistor which can be done by lowering the collector current, as he suggests. In fact, this method is more directly as a result of his analysis since the first pole within the loop encountered by an input signal is that due to fall-off of current gain of the input transistor.

Stephan Gift,
University of the West Indies,
St Augustine, Trinidad.

Reference

1. M. Otala, J. Lohstroh, An Audio Power Amplifier for Ultimate Quality Requirements, *IEEE Transactions on Audio*, vol. AU-21, no. 6, December 1973.

Mr Sundqvist replies:

I would like to thank Mr Gift for his clear explanation of the input stage frequency roll-off mechanisms. When I wrote my article I had not yet considered the details of how the frequency roll-off should be effected in practice. However, I would suggest that any band limiting procedure that gives a high input capacitance should be avoided, as this could give trouble when using a pre-amplifier with high output impedance, especially in combination with long connecting cables.

I have two other comments on my article which could be of interest to the readers. Using the original Otala design method, one ends up with a power amplifier with very wide bandwidth. However, the total audio system bandwidth is still limited by the pre-amplifier roll-off at 20-30 kHz. Although I do not think that an excessively large bandwidth is always desirable, this has always seemed to me to be a waste of good design work. Using the method outlined in my article the system bandwidth can be made as large or small as desired, as no frequency limits are involved in the design.

I would also like to point out that there are other methods to avoid t.i.m. without using Professor Otala's design method. My article was written in January, 1976, and since then Malmqvist¹ has published an interesting analysis of why t.i.m. is not produced by the Xelex range of amplifiers in spite of their relatively heavy feedback.

Bert Sundqvist,
Umeo,
Sweden.

Reference

1. M. Malmqvist, "Transient distortion", *Musiktidningen*, vol. 4, no. 4, p.53, Aug. 1976 (in Swedish); presented at the 56th AES Convention, Paris, March 1977.

INDUSTRIAL CONSULTANCIES IN UNIVERSITIES

I noticed with interest your article in the February 1977 issue on the "Crisis in scientific and engineering education," and am writing to comment on certain statements made in the article.

Most of the universities in the UK have established industrial consultancy or liaison offices of one kind or another. The current count is some 33 universities with such offices. In general, consultancy work carried out for industry using university facilities is conducted or monitored by these units and the universities require a proper return to them for such use. While it would be highly undesirable to restrict the contact of individual academics with their industrial counterparts, most universities now require that academic staff be given permission for any consultancy work that they undertake and there is normally some limit as to the level of additional remuneration they can receive from such work.

In conclusion I would comment that most of the universities have established liaison bureaux and industrial consultancies which are free to exploit results of research, and there is a growing degree of co-operation between university staff and their opposite numbers in industry.

R. J. L. McLaren,
Centre for Industrial Research and Consultancy,
University of Dundee.

Crystal ladder filters

How to build low-cost s.s.b. filters using surplus crystals

by J. Pochet, F6BQP

This article gives design calculations for making crystal filters for s.s.b. applications and includes results of tests made on samples constructed by the author. The arrangement used in each case is that of a ladder filter where the crystals are connected in series. This very simple arrangement, see Fig.1, enables constructors to make low-cost filters, in comparison with commercial units, by using crystals having identical resonant frequencies.

The filters to be described in this article were made using 8314kHz crystals, as these were readily available to the author. The measurements were made in a laboratory with automatic instruments of high precision. Table 1 gives the results of measurements on one of the filters compared with the well-known XF9A filter. Definitions of the terms are shown in Fig. 2.

The results obtained from these tests are very satisfactory; the ultimate out-of-band rejection, better than 95dB.

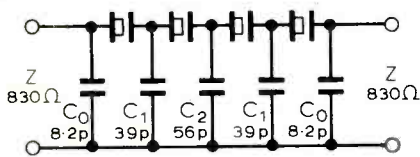


Fig. 1. Typical crystal ladder filter for 830 ohms impedance. In the ladder arrangement all the crystals, in this case devices having resonant frequencies of 8314kHz, are connected in series.

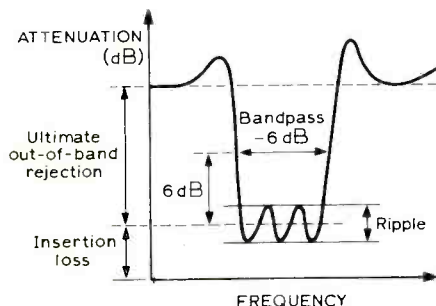


Fig. 2. Attenuation/frequency characteristic for a crystal ladder filter indicating the definitions used in the text.

Table 1 — Comparative results between a four-crystal ladder filter and the XF9A filter

	Ladder filter	XF9A filter
Insertion loss	1.4dB	2.5dB
Ripple	0.8dB	0.8dB
Bandpass:		
-3dB	1800Hz	2350Hz
-6dB	2050Hz	2540Hz
-20dB	2950Hz	3200Hz
-40dB	5200Hz	4250Hz
-50dB	6950Hz	4650Hz
Ultimate out-of-band rejection	> 95dB	> 48dB
Impedance	830 ohms	500 ohms

is excellent, the slopes of the sides of the filter are a little less steep than those of the XF9A, and the pass-band at -6dB is a little narrower. It should be mentioned that the measured characteristics of the XF9A filter are better than those claimed by the manufacturers.

How to design the filter

A filter of this kind can be made using two, three or four crystals in series. Fig.


3 gives the values of the capacitors as a function of the impedance and frequency values adopted. The choice of impedance is important because, in effect, the more this is reduced the more the pass-band is reduced and the higher will be the insertion loss. This is because the series resistance of the crystal becomes more significant in relation to the impedance.

On the other hand, if one chooses an impedance which is too high, the calculations will result in low capacitance values, and construction then becomes limited by the stray circuit capacitances.

In practice, for a frequency of about 8 to 10MHz, the impedance should be about 800 to 1000 ohms to obtain a pass band of 2100Hz, suitable for s.s.b.

It is necessary to underline the importance of the impedance of a filter, no matter what type is used. It is also of paramount importance that the filter should be correctly terminated because any significant mismatch could lead to a pass-band ripple of some 10dB.

Fig. 3. Typical crystal ladder filters. All crystals are of the same resonant frequency — preferably between 8 and 10MHz for s.s.b. units. The coefficients indicated against each capacitor should be multiplied by $1/2\pi fR$, where R is the design impedance and f is the resonant frequency of the crystal in hertz, to give the correct capacitor value. Three and four-crystal filters are capable of giving very good results. Two-crystal filters, although reasonably good, have relatively poor shape factors. See text.

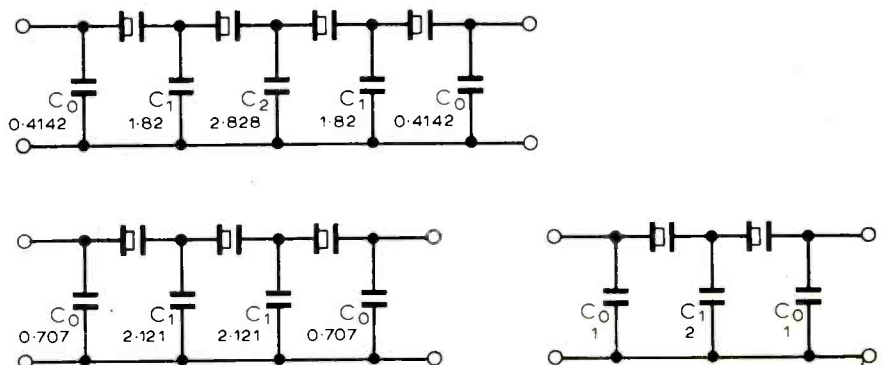

It is possible to adjust the values of the capacitors; reducing them increases the passband but also increases the ripple in the pass-band (If a ripple of 2dB can be accepted, the passband can be increased by up to 20%). Note that it is advisable not to take advantage of this opportunity unless the necessary test instruments are available to check the results of any such adjustments (a wobulator and oscilloscope are the ideal instruments for this type of adjustment).

The following is an example of how to calculate capacitor values for crystal ladder filters.

When R is the design impedance and f is the resonant frequency of the crystal in Hz, if f is 8314kHz, and R is 830 ohms, then $1/2\pi fR$ is equal to 23pF. From this one may obtain capacitor values for a four-crystal filter, as follows.

$$C_0 = 0.4142 \times 23 = 9.5\text{pF (8.2pF)}$$

$$C_1 = 1.82 \times 23 = 41.8\text{pF (39pF)}$$

$$C_2 = 2.828 \times 23 = 65\text{pF (56pF)}$$

and for a three-crystal filter:

$$C_0 = 0.707 \times 23 = 16.3\text{pF (15pF)}$$

$$C_1 = 2.121 \times 23 = 48.8\text{pF (47pF)}$$

and for a two-crystal filter:

$$C_0 = 1 \times 23 = 23\text{pF (22pF)}$$

$$C_1 = 2 \times 23 = 46\text{pF (47pF)}$$

The values in brackets refer to 10% preferred values.

These three filters have been built and the results obtained are shown in Table 2. In all three cases the passband ripple is less than a decibel. The results showed that with three or more crystals one may obtain a very good filter. Although the two-crystal filter gives a reasonably good out-of-band rejection (50dB), the sides are not very steep and the shape factor is modest. With a single crystal the out-of-band rejection is only about 20dB.

Remarks

In the cases described above the passband extends from approximately 8314 to 8316kHz. The series-resonant frequency of the crystals therefore determines the lower limit of the passband; this is of interest since it is necessary only to use an additional crystal, of the same frequency as the others, for the carrier, to permit the selection of the upper sideband.

The choice of filter frequency depends on the availability of the crystals. It is possible to use frequencies from 5 to 20MHz, but if one has the choice it is preferable to use 8 to 10MHz. As an example, for a frequency of 5MHz it would be necessary to use an impedance of at least 1500 ohms in order to obtain the necessary bandwidth for s.s.b.

By using a lower frequency and lower

Table 2 — Measurements on two, three and four crystal ladder filters (for 8314kHz and 830 ohms impedance)

	Two crystals	Three crystals	Four crystals
Insertion loss	0.9dB	1.1dB	1.4dB
Bandpass:			
-6dB	2150Hz	2050Hz	2050Hz
-10dB	2700Hz	2350Hz	2250Hz
-20dB	4850Hz	3400Hz	2950Hz
-30dB	8900Hz	5050Hz	3900Hz
-40dB	16,100Hz	7500Hz	5200Hz
Ultimate out-of-band rejection	>50dB	>75dB	>95dB

impedance, it is possible to make an excellent c.w. filter.

The filters described above could be constructed on a p.c.b. and fitted into a small metal box, which should be connected to ground to avoid stray leakages.

An example circuit arrangement

Let us finish with an example of a circuit arrangement allowing the filter to be inserted at points of impedance equal to its own. This circuit is shown in Fig. 4. The output impedance of the first stage is practically equal to the collector resistance of Tr_1 (common emitter configuration) and the input impedance of the second stage (Tr_2 in common collector configuration). In this way the correct termination of the filter is obtained with the advantage of a very low output impedance (that of Tr_2), suitable for connection to the mixer on transmit and the i.f. stage on receive.

This circuit could also be very useful for measuring the filter's response curve with a sufficiently stable h.f. generator, a digital frequency meter and a voltmeter incorporating an h.f. probe, or better still a wobulator.


In conclusion the author recognizes that it would be interesting to study this technique further; trying for example readily-available surplus FT243 crystals, or low-cost 27MHz crystals having 9MHz fundamentals.

Pat Hawker comments: This is a free translation of an article, "Essais, mesures et realisation de filtres a quartz" by J. Pochet, F6BQP, published in *Radio-REF*, journal of the Reseau des Emetteurs Francais, in May 1976. For many years the vast majority of crystal bandpass filters used in h.f. communications have been based on the half-lattice or lattice configuration, plus some limited use of the bridged-T approach. The recent use of higher frequency filters, particularly around 5, 9 and 10.7MHz has opened the way to greater use of the attractive ladder filter. At these frequencies it is possible with three or four identical frequency crystals and with practical values of impedance and capacitors to achieve passbands of between 2 to 3kHz, reasonably good shape factors and high ultimate out-of-band rejection.

While it would seem possible to obtain better shape-factors and ultimate rejection by using more crystals, this will usually require careful adjustment of capacitor values and is less easy to arrange in a symmetrical form having equal input and output impedances.

Fig. 4. One method of connecting a crystal filter into a transceiver circuit to ensure correct impedance matching. See text.

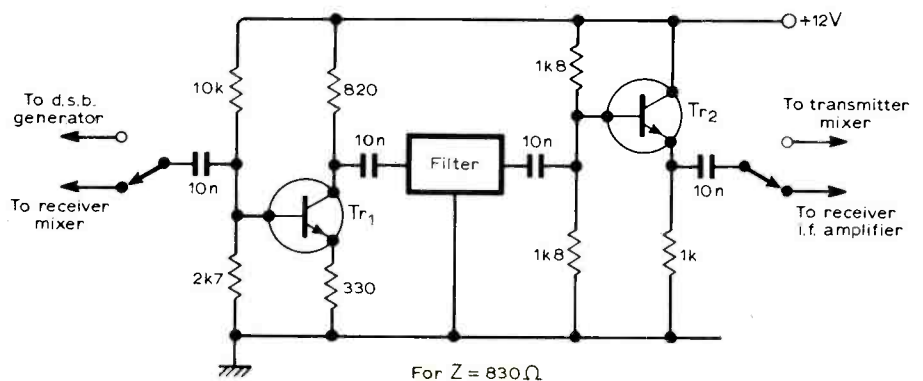Acknowledgement. *Wireless World* thanks Pat Hawker, G3VA, for translating this article from the original French.



Logic design — 6

Examples of clock-driven circuits

by B. Holdsworth* and D. Zissos†

*Chelsea College, University of London

†Dept. of Computing Science, University of Calgary, Canada

Some examples of the design of clock-driven circuits using the techniques set out in the last article can now be considered.

Example 1. Paper Tape Reader

Design a circuit that will stop the paper tape reader, shown in Fig. 9(a), by turning signal *m* off when the character sequence 4-5-6 is detected, and at the same time generates a buzzer signal *b*.

A synchronizing pulse is generated by the reader each time a new character is output.

(1) **I/O characteristics.** See Fig. 9(a)

(2) **Internal characteristics.** A suitable state diagram is shown in Fig. 9(b)

(3) **State reduction.** The state table corresponding to Fig. 9(b) is shown in Fig. 9(c). Examination of this table shows that merging of rows is not possible.

(4) **Primitive circuits.** Suitable binary codes are allocated on the state diagram. By direct reference to this

diagram the input equations to the JK flip-flops are obtained.

$$S_A = S_15 + (S_26)$$

where the term in brackets is an optional product.

$$S_A = \bar{A}B5 + (AB6)$$

The optional product cannot be used for reduction purposes.

Hence, $S_A = \bar{A}B5$ and $J_A = B5$

$$R_A = S_2A + S_2\bar{A}6 + (S_0)$$

$$= S_2\bar{6} + (S_0)$$

$$= AB\bar{6} + (\bar{A}\bar{B})$$

The optional product cannot be used for reduction purposes.

Hence, $R_A = AB\bar{6}$ and $K_A = B\bar{6}$

$$S_B = S_04 + (S_14) + (S_15) + (S_24)$$

$$= \bar{A}\bar{B}4 + (\bar{A}B4) + (\bar{A}B5) + (AB4)$$

The optional product ($\bar{A}B4$) need not be used for simplification purposes since \bar{B} will be eliminated when converting from S_B to J_B .

Hence, $S_B = \bar{A}\bar{B}4$ and $J_B = \bar{A}4$

$$R_B = S_1\bar{4}5 + S_2\bar{4}6 + S_26 + S_0\bar{4}$$

$$= S_1\bar{4}5 + S_2\bar{4} + (S_0\bar{4})$$

$$= \bar{A}B\bar{4}5 + AB\bar{4} + (\bar{A}\bar{B}\bar{4})$$

$$= B\bar{4}5 + AB\bar{4} + (\bar{A}\bar{B}\bar{4})$$

The optional product cannot be used for simplification purposes, hence



$$R_B = B\bar{4}5 + AB\bar{4} \text{ and } K_B = \bar{4}5 + A\bar{4}$$

The circuit is shown in Fig. 9(d).


Example 2. One-shot circuit

High-frequency clock pulses are fed to terminal X in Fig. 10(a). Design a circuit

Fig. 9. Circuit of Example 1 is shown at (a). Its state diagram is at (b) and its state table at (c). The resulting circuit is shown at (d).

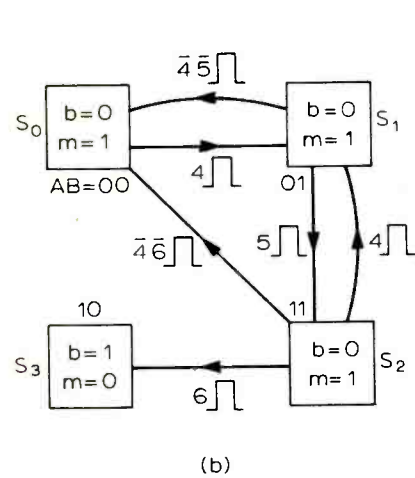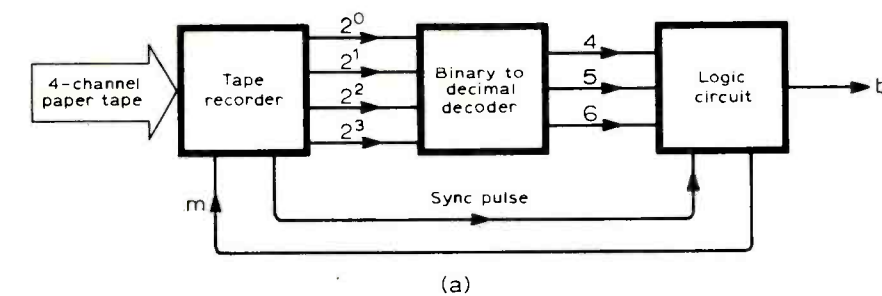

Input	4	5	6	$\bar{4}\bar{5}\bar{6}$
S_0	S_1 m=1 b=0	S_0 m=1 b=0	S_0 m=1 b=0	S_0 m=1 b=0
S_1	S_1 m=1 b=0	S_2 m=1 b=0	S_0 m=1 b=0	S_0 m=1 b=0
S_2	S_1 m=1 b=0	S_0 m=1 b=0	S_3 m=0 b=1	S_0 m=1 b=0
S_3				

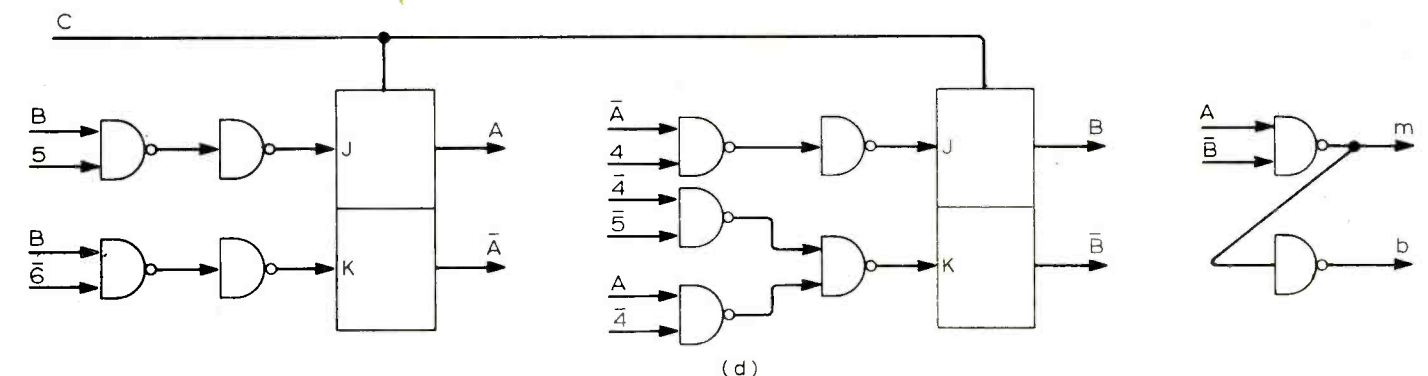

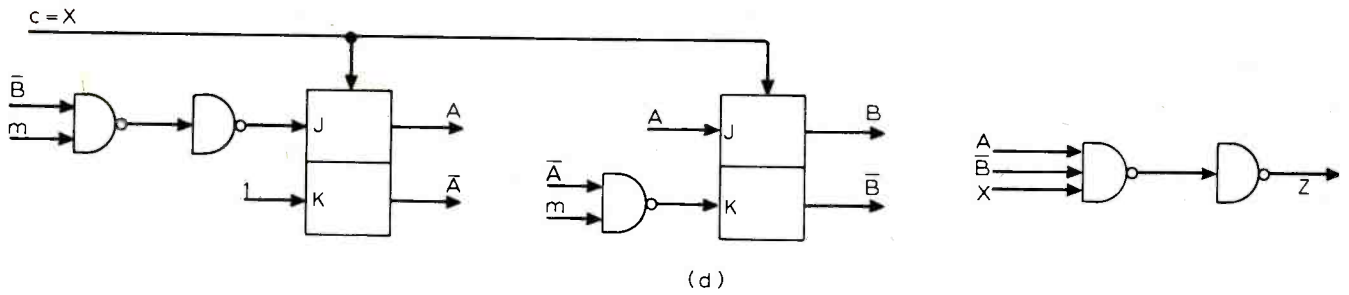
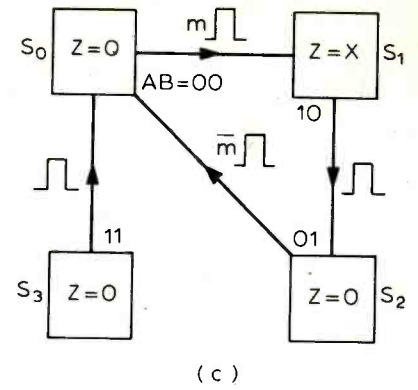
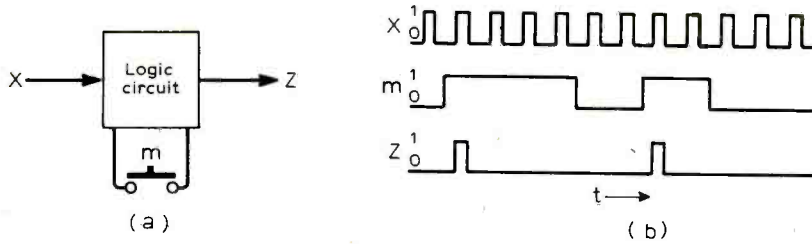


Fig. 10. Problem of Example 2, (a) and the required timing at (b). The state diagram is seen at (c) and the circuit realization is shown at (d).

so that each activation of a manual switch m allows one complete clock pulse output on line Z . The duration of signal m can be assumed to be greater than the pulse width.

(1) **I/O characteristics.** These are shown in the time diagrams of Fig. 10(b).

(2) **Internal characteristics.** A suitable state diagram is shown in Fig. 10(c).

(3) **State reduction.** It is left as an exercise for the reader to construct the state table and examine the possibility of state reduction.

(4) **Primitive circuit.** By direct reference to the state diagram the following turn-on and turn-off equations are obtained.

$$S_A = S_0 m = \bar{A}\bar{B}m. \text{ Therefore } J_A = \bar{B}m.$$

$$\begin{aligned} R_A &= S_1 + S_3 + (S_2) + (S_0\bar{m}) \\ &= \bar{A}\bar{B} + AB + (\bar{A}\bar{B}) + (\bar{A}\bar{B}m) \\ &= A. \text{ Therefore, } K_A = 1. \end{aligned}$$

$$S_B = S_1 + (S_2 m) = A\bar{B} + (\bar{A}\bar{B}m) = A\bar{B}. \text{ Therefore } J_B = A.$$

$$\begin{aligned} R_B &= S_2\bar{m} + S_3 + (S_0) \\ &= \bar{A}\bar{B}\bar{m} + AB + (\bar{A}\bar{B}) \\ &= B\bar{m} + AB. \text{ Therefore } K_B = \bar{m} + A. \end{aligned}$$



$$Z = S_1 X = A\bar{B}X$$

The circuit implementation of these equation is shown in Fig. 10(d).

Example 3. Pulse distributor

Signal X in Fig. 11(a) is a pulse train. The input pulses are to appear at the output terminals as shown in Fig. 11(b).

continued on p.74

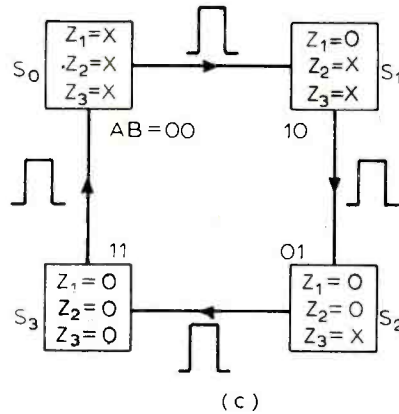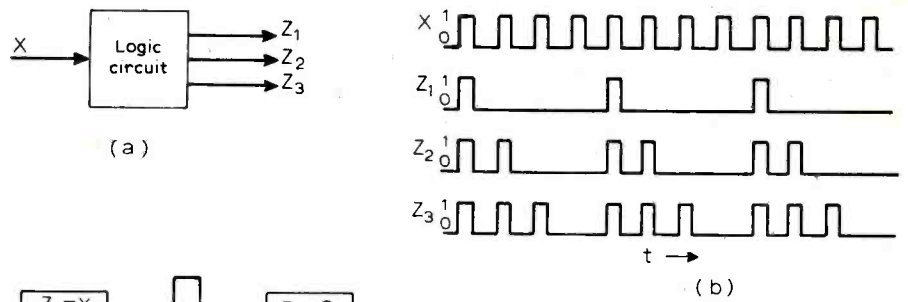

S ₀	S ₁
S ₁	S ₂
S ₂	S ₃
S ₃	S ₀

State values:
 S₀: Z₁=Z₂=Z₃=X
 S₁: Z₂=Z₃=X
 S₂: Z₃=X
 S₃: Z₁=Z₂=Z₃=X

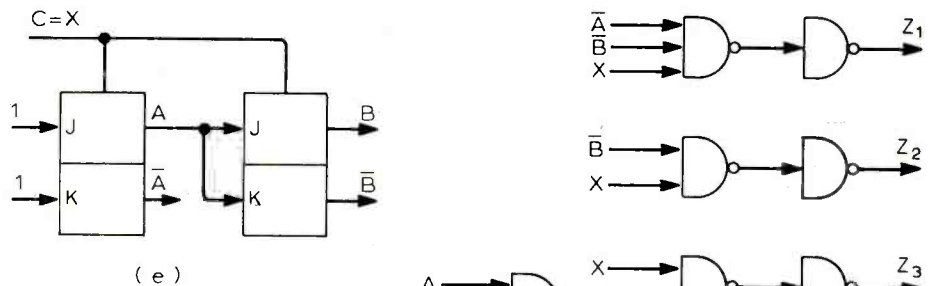


Fig. 11 (a) is the problem for Example 3, with the specified output at (b). State diagram (c) and state table (d) result in the circuit shown at (e).

World of Amateur Radio

Cost of new licences

Somewhere, sometime, somebody in authority will have to make his mind up whether amateur radio should be treated purely as a tolerated hobby or as a socially useful form of technical self-training. For it is becoming more and more expensive for a youngster to obtain a British amateur licence. The latest increase in the fee for taking the Post Office amateur-licence Morse test — it goes up from £4 to £6 on July 1 — means that this charge (which was only 50p until October 1970) will have gone up by a factor of 12 in less than 7 years! It is similarly difficult to keep abreast of the steadily rising cost of taking the Radio Amateurs Examination, since this involves not only the City & Guilds fee but also the local centre fee. Applicants for these examinations may also have to meet substantial travelling costs, and, of course, if successful pay the first annual licence fee. All of this is certainly not a way of encouraging a new generation of amateurs.

Yet such costs could surely be greatly reduced by adopting some elements of the system used in some overseas countries of bringing the local clubs and groups into the licence-issuing process. Is it for instance really necessary for the Morse Test to be given by one of the now relatively small number of trained Post Office operators? There are plenty of local amateurs who could do this, with any necessary precautions against abuse.

If Lord Wallace, the RSGB president, can argue that the communications industry has reason to be grateful for the enthusiasm and expertise implanted in young industry apprentices by their participation in amateur radio, is it not time that the whole procedure was looked at with a view to making this more possible? One can understand the Post Office view that it cannot be expected to subsidise the cost of Morse tests — the real question is should they be involved at all?

European v.h.f./u.h.f. records

The following is a listing of current European distance records for the amateur bands above 144MHz as pub-

lished recently in the Dutch journal *Electron*:

144MHz F5JC/SM5AGM (tropo, 1930km); SM6FBQ/UA3TCF (aurora, 1830km); SM5LE/UA9GL (meteor scatter, 2200km); SM7BYU/9H1CD (sporadic E, 2250km).

70-cm F8MM/SM5LE (tropo, 1560km); SM5CUI/UA3ACY (aurora, 1260km); SM5LE/VK2AMW (moon-bounce, 15,680km).

23-cm G3LQR/SM5CCY (tropo, 1100km); PAOSSB/VK3AKC (moon-bounce, 20,000km).

13-cm OK1KIR/OK1WFE (tropo, 400km)

9-cm PAODBQ/G3LQR (tropo, 230km)

6-cm G3BNL/G3EEZ both portable (tropo, 160km)

3-cm OK1VAM/OK1WFE (tropo, 200km).

This list brings out several interesting contacts although the two records attributed to Czech stations appear to have been overtaken by the G3LQR/OZ9OR tropo contact on 13cm (760km) and the G4BRS/GM3OXX contact on 9cm (521km) recorded during the past year.

Band scan

Microwave beacons are now operational on The Wrekin (GB3WRN) on 1296.91MHz and near Sheffield (GB3UOS) on 3456MHz.

The weekly GB2ATG rtty news bulletins transmitted on Sunday mornings (1200 local time on 3590kHz, 1230 and 1245 on 144.6MHz) are now also being sent on 3590kHz at 1900 local time on Sunday evenings.

The well-known New Zealand short-wave listener, Arthur Cushen, was heard recently being interviewed on the Club Forum programmes transmitted by Radio Australia on Saturday mornings. This is one of a number of amateur and s.w.l. programmes broadcast regularly on the h.f. broadcast bands; the Dutch programmes on Radio Netherlands were recently judged the most popular in a ballot organised by I.S.W.L.

The "Phase 1" programme of amateur u.h.f. repeaters has been completed with the coming into operation of GB3IH at Ipswich, GB3LV at Cheshunt and GB3LW in Central London.

859 certificates of Morse proficiency have been issued by the Royal Naval Amateur Radio Society since the regular transmissions on G3BZU were begun in 1962. These transmissions are made on the first Tuesday of every month on or about 3520kHz at 2000 hours local time. Speeds from 15 to 40 words per minute in increments of 5 w.p.m. are sent for 3 minutes each, and must be copied without any errors to obtain a certificate or endorsement. A charge of 30p is made for a 15 or 20 w.p.m. certificate and endorsement "stickers" for other speeds require only

a stamped addressed envelope. Present manager of the service is Mick Puttick, G3LIK, and transmissions are made from the RNARS headquarters station in Hampshire using a KW Viceroy transmitter and dipole aerial (RNARS, G3BZU, HMS Mercury, Leydene, Petersfield, Hampshire).

The American National Association of Broadcasters has recently petitioned the FCC, seeking the right to rebroadcast transmissions made on Citizens' Band and amateur radio bands. It has been suggested to broadcast stations that they could broadcast emergency traffic or weather reports and information vital to public safety and convenience.

In the picture

Mike Cox, G8HUA, of Brigg, South Humberside has taken over from Joe Rose, G8CTG, as general secretary of the British Amateur TV Club. CQ-TV also shows, in a letter from Peter Cossins, VK3BFG, that there are now some 20 fast-scan amateur tv stations in the Melbourne area. A weekly WIA news bulletin is transmitted on amateur tv every Sunday morning and pictures are from time to time exchanged with VK7EM in Tasmania some 400km distant.

Several British amateurs are now using standard u.h.f. transverters driven from h.f. or v.h.f. standard equipment with simple homebuilt video modulators: for example, Lawrence Woolf, GJ8AAZ (formerly GC6RAX/T) uses an FT620 drive source, Modular Electronics 50 to 432MHz transver. To receive 70-cm atv signals the output from the transverter is fed into a Band 1 tv receiver; for transmission a 50MHz video modulator uses just one transistor plus an SL610c integrated circuit.

In brief

The number of amateur licences in the USA has for the first time passed the 300,000 mark, an increase of over 10 per cent in a year. . . . Of 2351 Austrian licences, 1317 are for h.f./v.h.f. operation, 980 for v.h.f. only and 54 are club stations. . . . The RSGB's VHF National Field Day runs from 1600 GMT July 2 to 1600 GMT July 3 with groups operating up to four separate stations, one each for the 70, 144, 432 and 1296MHz bands. . . . The Royal Naval Amateur Radio Society is holding its annual mobile rally at "HMS Mercury" (a shore establishment between Clanfield and East Meon, near Petersfield, Hants) on Sunday, June 19 with trade stands, arena events and a static display of pre-1963 racing cars. Talk-in stations GB3SN on 144MHz, 70MHz and 3660kHz. . . . *Sprat*, the journal of the G QRP (low power) Club, points out that it is illegal for a station to sign /QRP but calling CQ QRP is within the terms of the licence.

PAT HAWKER, G3VA

Time code clock alarm

by N. C. Helsby, M.A. *University of Essex*

The provision of an alarm circuit is relatively simple and requires the digital comparison between a stored alarm time in b.c.d. form and the current received time also in b.c.d. The alarm time is determined by the positions of thumbwheel switches, which are easy to set and give a continuous read-out. The received time is present on the inputs to the display of the clock, except during the instant that the new code is being received serially. The alarm is blanked during this time by the application of waveform G to the digital comparator circuit. When the GMT to BST changeover is carried out automatically, and the alarm is connected to the output of the converter, a further blanking signal is applied in the form of waveform H. During the time that H is high the alarm is inhibited while the output of the converter continuously changes until all of the information has been received by the date decoder.

Exclusive-OR gating is used to make the comparison between the actual time and the alarm time. This system is cheaper than digital comparators, and full information about the comparison such as greater-than and less-than is not required. The output of each exclusive-OR gate is only low when both inputs are either high or low. Any exclusive-OR output being high will keep Tr_1 turned on, including the outputs G and H previously mentioned. However, when all outputs are low the collector of Tr_1 goes high and clocks $IC_{5(a)}$. Although rarely occurring in normal use, it should be noted that a break in transmission or noisy conditions could cause a particular display to be "skipped" and prevent detection of the required alarm time. The virtue of high accuracy may justify the extension of the alarm time to include seconds, which requires two more sections to the thumbwheel switch unit and one extra 7486 i.c. plus diodes. It is equally possible to reduce the precision and hence reduce the chance of skipping the alarm time, by not including the minutes' comparison, and setting the alarm to the nearest ten minutes or even to the nearest hour.

The time at which the alarm is

cancelled is determined by counting minutes, although seconds may be substituted if preferred, and resetting the D type flip-flop after a pre-selected number of minutes. The c.m.o.s. decade counters IC_6 and IC_7 have ten decoded outputs allowing pre-selection of a count from 0 to 99. When the pre-selected count is reached, both inputs to $IC_{8(b)}$ are high which resets the D type until the next alarm is detected. A reset may be effected at any time before this by the use of Sw_1 . During the alarm period a relay is energized allowing a wide variety of functions to be switched electrically and independently. If a number of circuits need to be automatically switched on and off at different times and for different periods, several alarm circuits can be used in parallel.

Printed circuit boards

A set comprising two double-sided boards and one single-sided board for the date decoder/BST switch, display, and alarm circuit is available for £8.00 inclusive from M. R. Sagin, at 23 Keyes Road, London N.W.2. The decoder board allows leading zero blanking, and the alarm board offers automatic cancelling after a preselected number of minutes.

A set of five p.c.b.s and special components are still available for the original time code clock as detailed in the August 1976 issue of *Wireless World*.

Correction

IC_3 in Fig. 2 of the June issue should be a 4013 and not a 4015 as shown in the components list.

Component list for one alarm circuit (shown overleaf)

Integrated circuits

1, 2, 3, 4	7486
5	4013
6, 7	4017
8	4011

Resistors

1, 2, 4, 5	100k
3	8.2k
6	2.7k

Capacitors



1, 3	0.1 μ F disc
2	47 μ F 6V electrolytic

Misc.



$Tr_{1,2}$	BC182
D_{1-16}	1N916 or similar


thumbwheel switch sections	Doram 338-399 and 338-406
----------------------------	---------------------------

Sw_1	push to make push button (or use s.p.c.o. switch for possibility of alarm inhibit position)
--------	---

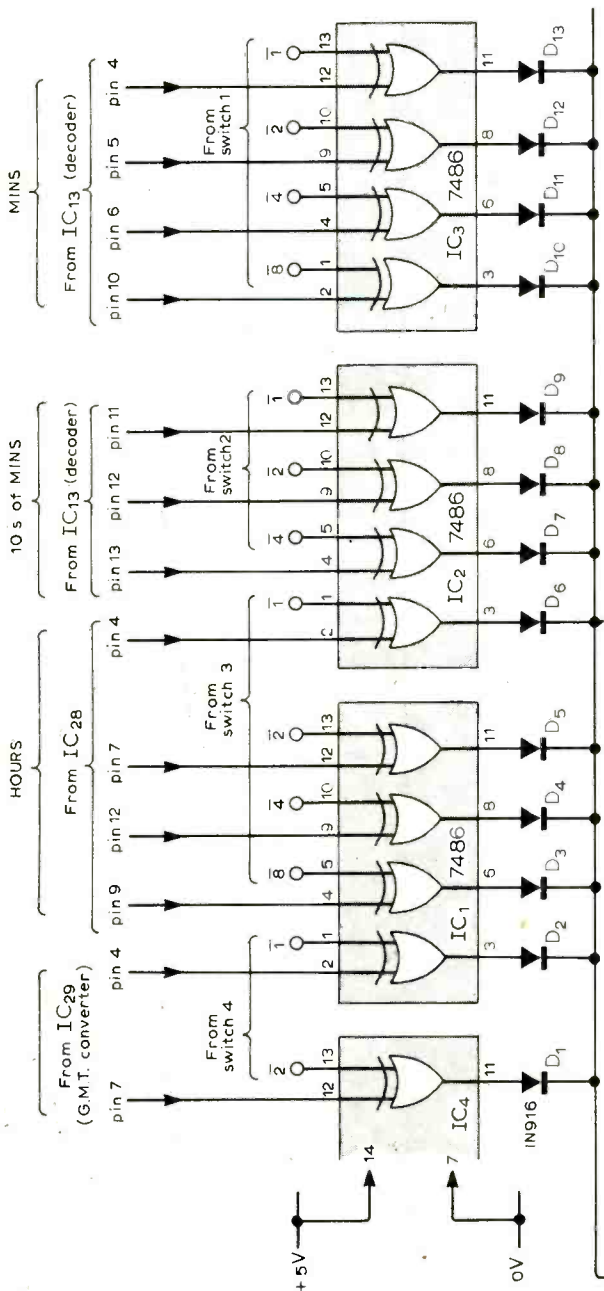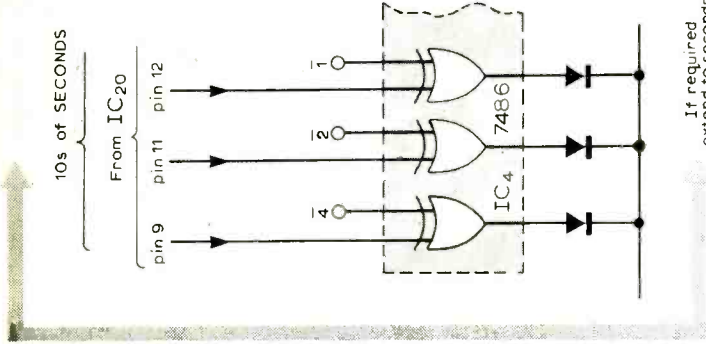

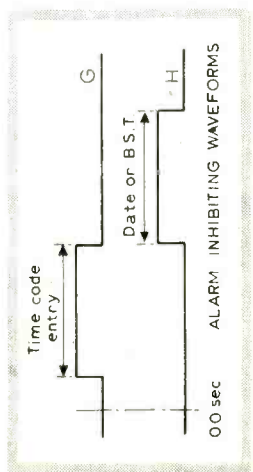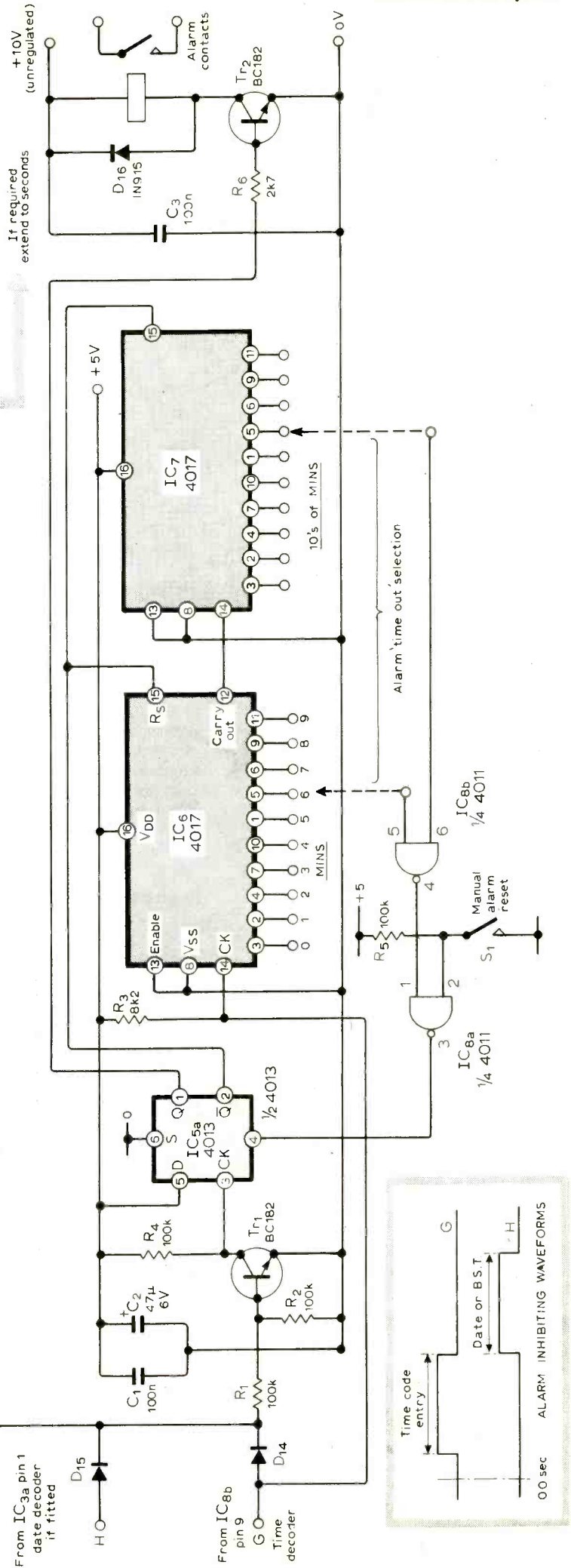Complete alarm circuit. To improve noise immunity the 13 exclusive-OR gate inputs from the thumbwheel switches can be fitted with 8.2 kΩ pull-up resistors to +5V. The complementary b.c.d. code contacts in the switches should be used and are marked with a bar.



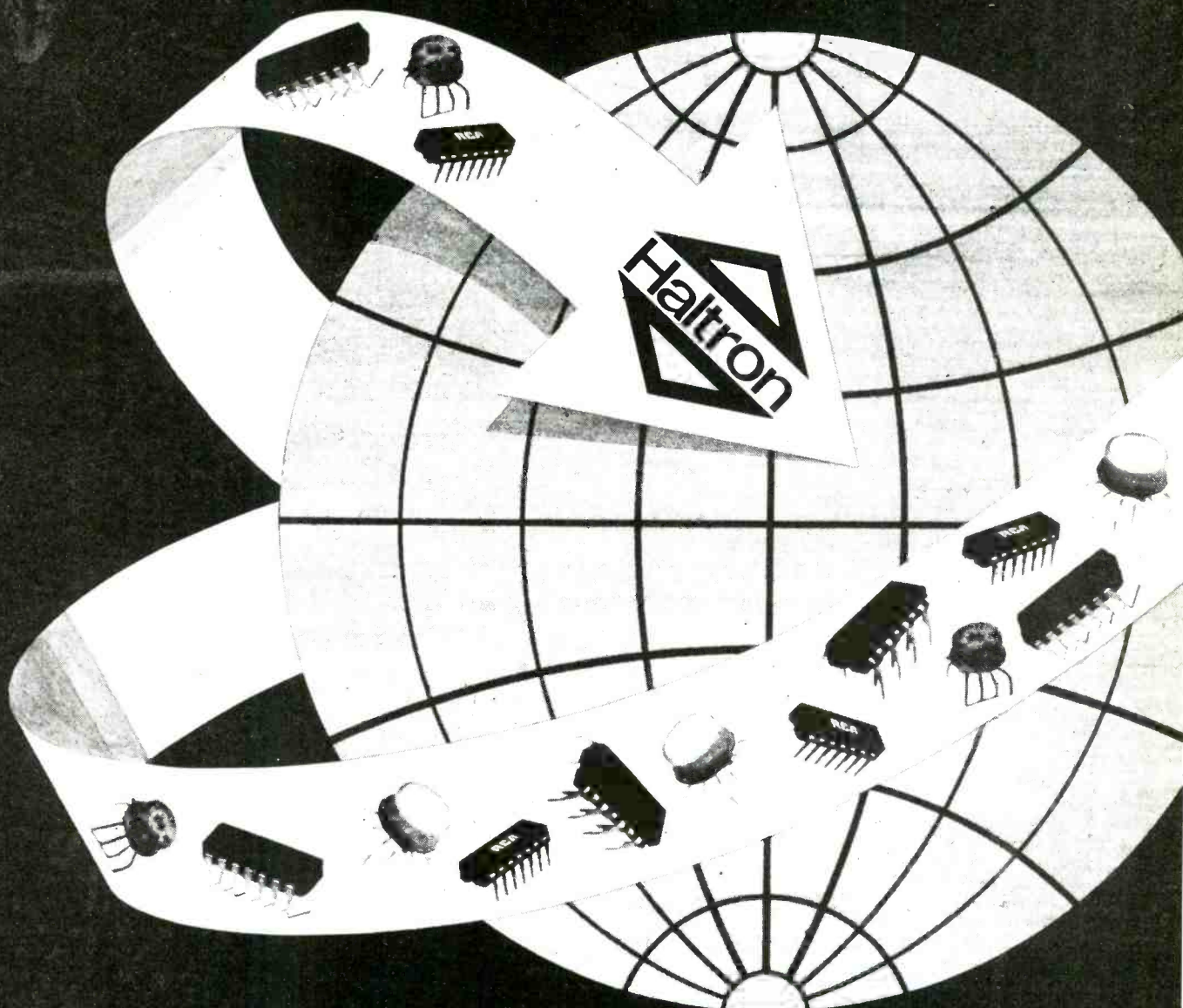


**The world over-
You get the
best service
from Haltron**

For high quality electronic valves, semiconductors and integrated circuits – and the speediest service – specify Haltron. It's the first choice of Governments and many other users throughout the world. Haltron product quality and reliability are clearly confirmed. The product range is very, very wide. And Haltron export expertise will surely meet your requirements. Wherever you are, get the best service. From Haltron.



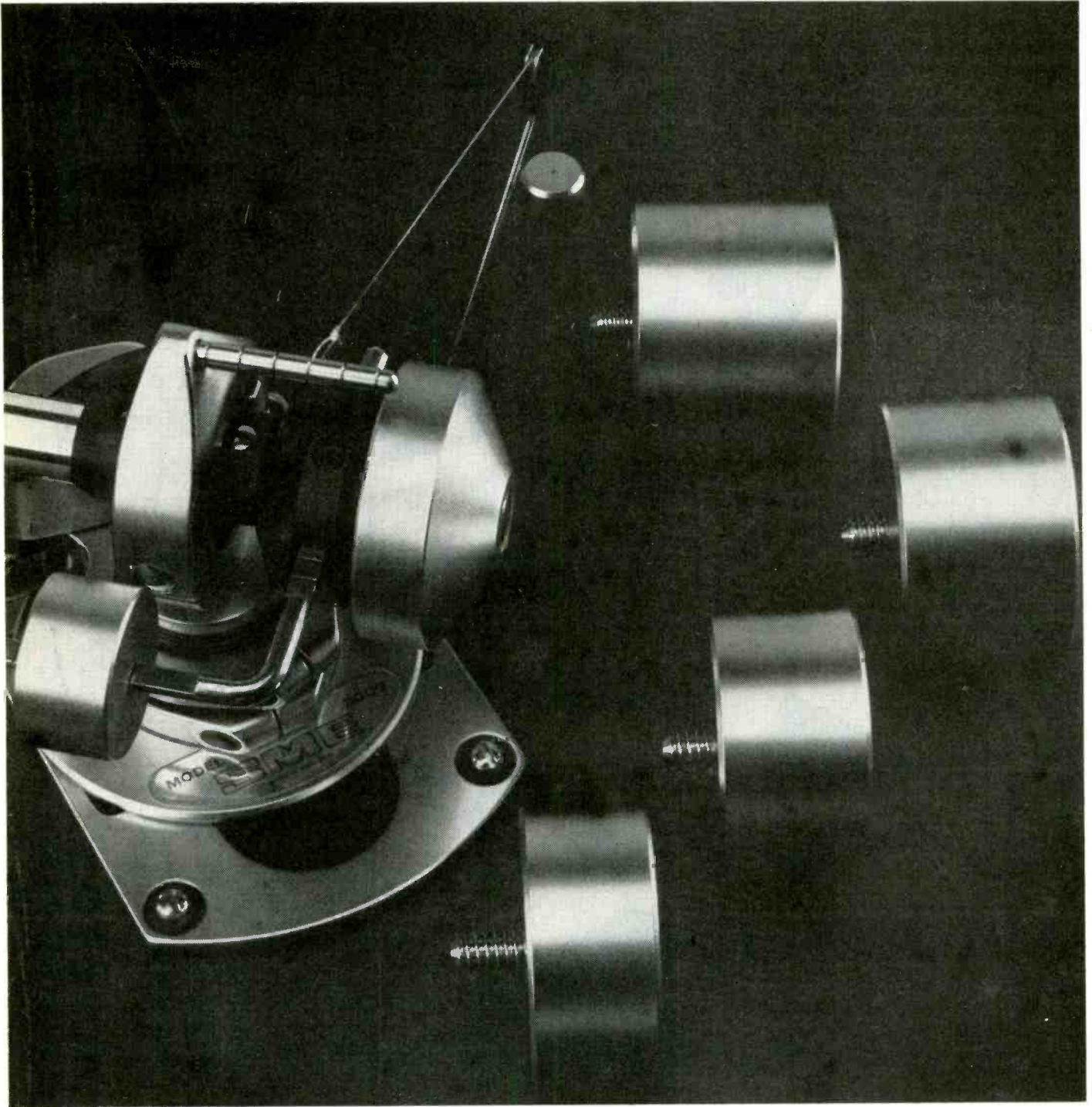Hall Electric Limited,
Electron House,
Cray Avenue, St. Mary Cray,
Orpington, Kent BR5 3QJ.
Telephone: Orpington 27099
Telex: 896141



3009+VERSATILITY

Series II Improved precision pick-up arms balance cartridges weighing between 4-9 grams. This can be extended to $1\frac{1}{2}$ - $21\frac{1}{2}$ grams, however, by the use of alternative balance weights, thereby covering the wider range of cartridges now available.

The best performance from your arm and cartridge is obtained with the correct balance weight, and information sheet No 21 enables you to select what is required. A copy will be sent on request.

Write to Dept 0644 · SME Limited
Steving · Sussex · BN4 3GY

SME

The best pick-up arm in the world

Decoupling

Some circuits and some thoughts on their purpose

by S. W. Amos, B.Sc., M.I.E.E.

Decoupling is usually defined in technical dictionaries as the reduction of unwanted coupling between stages in multi-stage equipment and, in the example usually quoted, the unwanted coupling is caused by an impedance in the common power supply. Such coupling can cause oscillation and the remedy is to include a decoupling network as illustrated in Fig. 1 which shows the essential components of a three-stage RC-coupled amplifier. R_s represents the resistance of the power supply and $R_d C_d$ is the decoupling network. By redrawing the circuit diagram as in Fig. 2 we can see that it has the form of an astable multivibrator circuit. R_s is the effective collector load of Tr_3 and, if large enough, causes the circuit to generate relaxation oscillations at a frequency determined primarily by the capacitors C_2 and C_3 and the associated base resistors. In audio amplifiers the oscillation frequency is usually very low — of the order of 1Hz — and gives rise to an audible effect known as motor boating. The decoupling network is situated between Tr_3 collector and Tr_2 base in one of the cross couplings which gives rise to oscillation and, if it introduces sufficient attenuation at low frequencies, can prevent oscillation.

Fig. 2 is useful in showing, for example, that there is little point in putting a decoupling network in the collector circuit of Tr_2 . Such a circuit would appear at the point marked X in Fig. 2: it would smooth the supply to Tr_2 but would do nothing to discourage multivibrator action.

R_d and C_d serve purposes other than the prevention of multivibrator oscillation. For example they act as smoothing components for the supply to Tr_1 and attenuate any 50Hz or 100Hz ripple. Such ripple is applied directly to the base of Tr_2 and is subjected to the gain of this and subsequent stages of the amplifier. For example if $R_d = 1$ kilohm and $C_d = 100\mu F$ any 100Hz components present at the output of the power supply are attenuated by a factor of approximately 60 (the reactance of $100\mu F$ being 16 ohms at 100Hz).

But possibly the most important effect of a decoupling network is on the transfer of signal-frequency energy from one stage to the next. To illustrate this consider Fig. 3, which shows a common-emitter tuned amplifier. $R_d C_d$ are collector decoupling components similar to $R_d C_d$ in Fig. 1. But by arranging $R_d C_d$ as shown in Fig. 3 we can see that C_2 plays an important role in the output circuit of the transistor. The output signal from the transistor is, of course, generated between collector and emitter and, to minimise signal loss, these two electrodes should be connected by low-impedance paths to the output load, i.e. the primary winding of the output transformer T_2 . There is a

direct connection between the collector and one end of the load: the decoupling capacitors C_2 and C_3 , provided they have suitable capacitances, provide a low-reactance path between emitter and the other end of the load.

Similar considerations apply at the input of the amplifier. The input signal should be applied between the base and the emitter of the transistor. The source of input signal is the tuned secondary winding of the transformer T_1 and one end of this is directly connected to the base. A low-impedance path from the other end of the tuned winding to the emitter is provided by the decoupling capacitor C_1 (which effectively short-circuits the lower arm R_2 of the

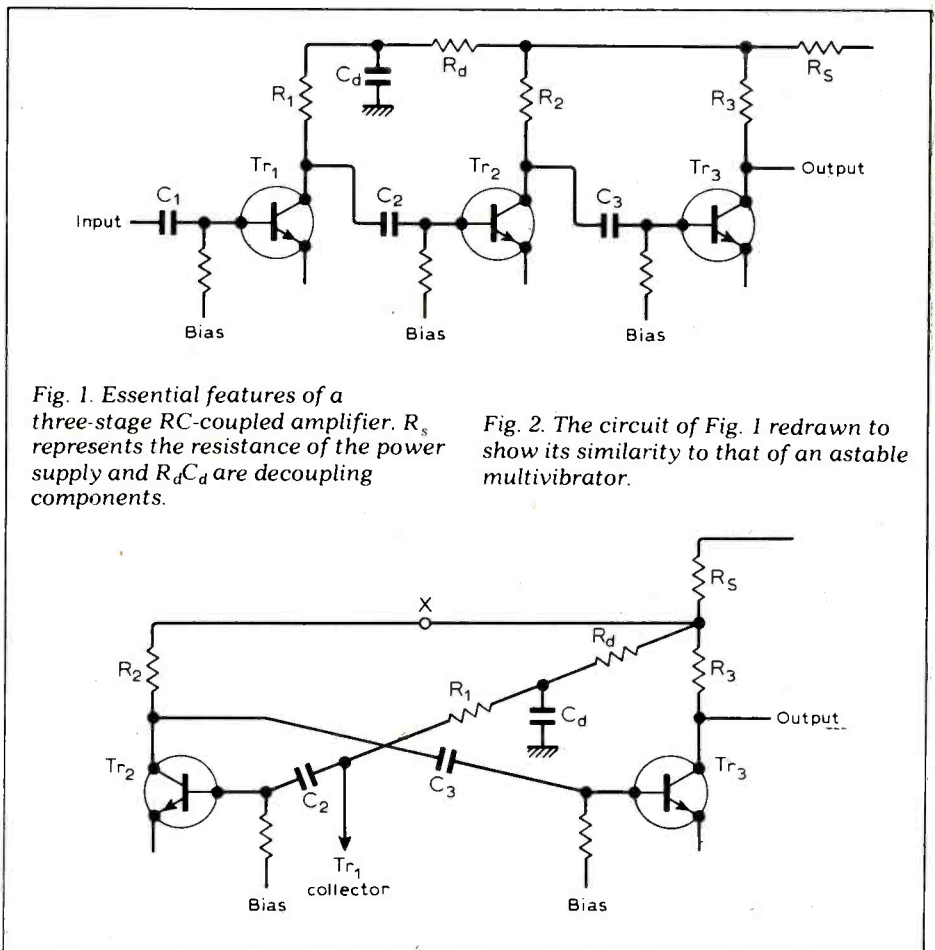


Fig. 1. Essential features of a three-stage RC-coupled amplifier. R_s represents the resistance of the power supply and $R_d C_d$ are decoupling components.

Fig. 2. The circuit of Fig. 1 redrawn to show its similarity to that of an astable multivibrator.

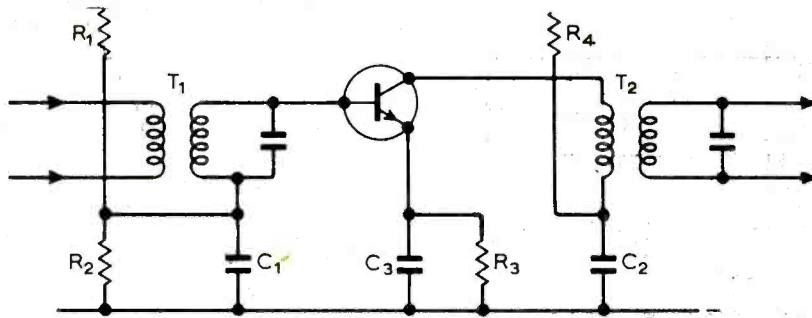


Fig. 3. C_1 , C_2 and C_3 are decoupling capacitors providing low-impedance paths for the input and output signals of the transistor.

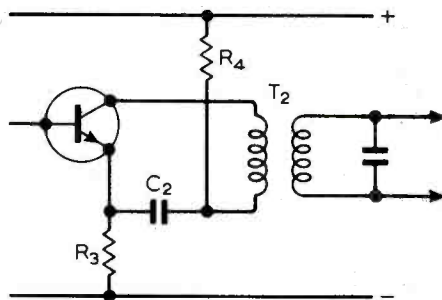


Fig. 4. A simplification of the output-circuit decoupling of Fig. 3.

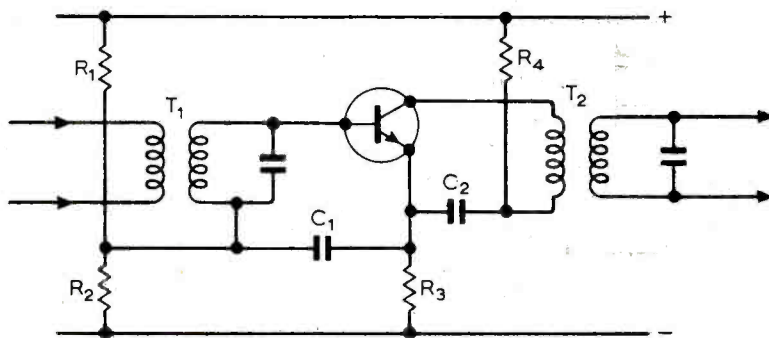


Fig. 5. A simplification of the input- and output-circuit decoupling of Fig. 3.

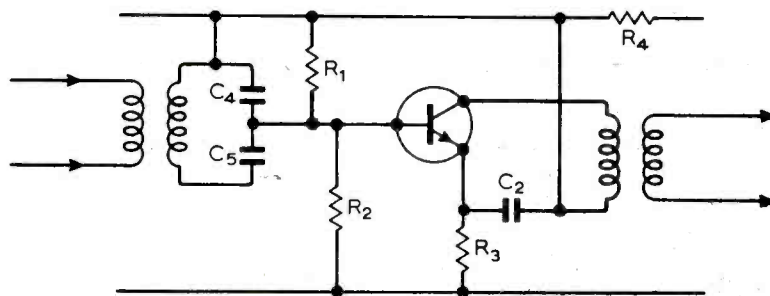


Fig. 6. A circuit in which a single capacitor (C_2) provides input and output decoupling.

potential divider) and C_3 (which similarly short-circuits the emitter resistor R_3).

C_1 , C_2 and C_3 in Fig. 3 thus provide examples of an important function of decoupling components: by providing low-impedance paths they confine signals to the areas where they are wanted and, by implication, prevent them from entering areas where they could cause difficulties.

Emitter decoupling

C_3 was introduced in the preceding paragraphs as a means of providing low-impedance paths for the input and output signals of the transistor. It has, however, another function and this is to eliminate the negative feedback introduced by the emitter resistor R_3 . This feedback is generally undesirable because it reduces the gain of the transistor and increases the input and output resistances. Increase in the input resistance would be a nuisance if this resistance is used to determine the passband of the tuned input transformer T_1 . To be effective in eliminating feedback C_3 must have a low reactance at the operating frequency. Because the reactance of a capacitor is inversely proportional to frequency, feedback elimination becomes less effective as frequency is reduced and the value of C_3 is therefore so chosen that effective elimination is achieved at the lowest frequency of interest: it is then automatically better at higher frequencies. This requirement also ensures that the capacitor is large enough to provide low-impedance paths for the input and output signals. It might be thought that the value of the emitter decoupling capacitor would be determined by R_3 and the operating frequency, the loss due to feedback being 3dB at the frequency for which the reactance of C_3 equals R_3 . This is not true, however, because the internal emitter resistance r_e of the transistor is effectively in parallel with R_3 and is normally much smaller than R_3 . Thus the true 3dB loss frequency is that for which the reactance of C_3 is equal to the parallel resistance of R_3 and r_e . From this relationship it is possible to deduce the value of the decoupling capacitor to use in a particular circuit. It is given by the following expressions.

For bipolar transistors

$$C = \frac{h_{fe}}{2\pi f_{min}(h_{fe} + R_e)}$$

where R_e is the value of the external emitter resistor.

For field-effect transistors and valves

$$C = \frac{1}{2\pi f_{min} \left(g_m + \frac{1}{R} \right)}$$

where R is the value of the external source or cathode resistor.

The formal deduction of these expressions was given by P. Engstrom in *Wireless World* for December, 1971.

We have so far discussed collector, base and emitter decoupling. In valve technology decoupling is also required for the screen grid of pentodes (still used in high-power equipment such as transmitters). For an a.f. pentode the effect of resistance in the external screen-grid circuit is precisely analogous to that of resistance in the external cathode circuit, i.e. it causes negative feedback and reduced gain. To eliminate this effect an external screen-grid decoupling capacitor is introduced and its value can be calculated from the expression given above by substituting g_s the screen conductance for g_m and R_s the external screen-grid resistance, for R .

R.f. pentodes also require screen-grid decoupling but here it is necessary for a different reason. As its name suggests the screen grid is required to act as an electrostatic screen between anode and grid circuits and to do this it must be effectively connected to cathode at signal frequencies though at a positive potential to give a reasonable anode current. A capacitor between screen grid and cathode enables this to be done and such a capacitor can legitimately be called a decoupling component because it confines anode and grid signals to their respective areas and prevents leaks between them which could cause r.f. instability.

Decoupling circuits

Examination of Fig. 3 shows that the circuit could be simplified and the impedance of the output signal path further reduced by omitting C_3 and returning C_2 to emitter as shown in Fig. 4. Indeed this arrangement must be adopted in certain circuits where signals are injected into the emitter, e.g. some types of oscillator or frequency-changer circuit. A disadvantage of this circuit is that the smoothing of the collector supply by R_4C_2 is offset by the ripple injected into the emitter circuit via R_3 . But possibly a more serious objection to the circuit of Fig. 4 is that R_3 is no longer decoupled and so provides negative feedback. However, this disadvantage can be overcome by applying to the input circuit the same technique used for the output circuit and which led to the circuit diagram of Fig. 4, i.e. by returning C_1 (Fig. 3) to emitter as shown in Fig. 5, which also includes output-circuit decoupling. Although the emitter resistor R_3 is not now shunted by a low-reactance capacitor there is no negative feedback: this is because the input signal is applied directly between base and emitter and the signal generated across R_3 by the collector current is not returned to the base circuit.

In some tuned amplifiers the step-down ratio required in the input transformer is achieved by use of a capacitance potential divider. It is then possible to dispense with capacitor C_1

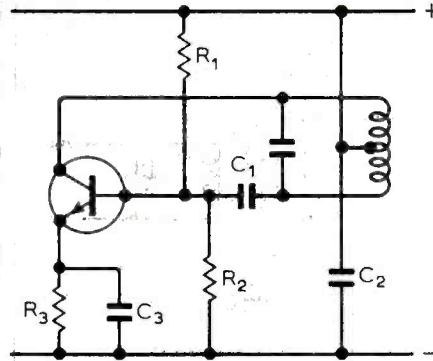


Fig. 7. A Hartley oscillator circuit.

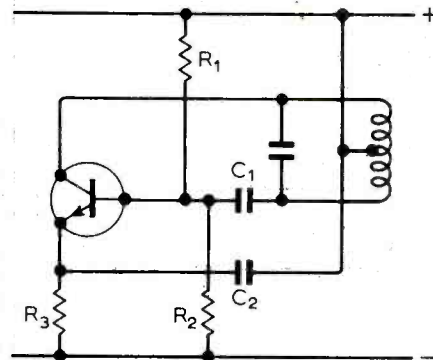


Fig. 8. The circuit of Fig. 7 with simplified decoupling arrangements.

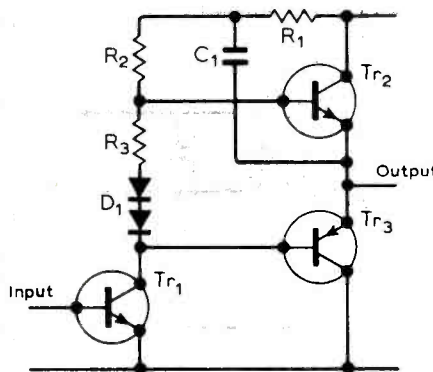


Fig. 9. Essential features of the Tobey-Dinsdale circuit.

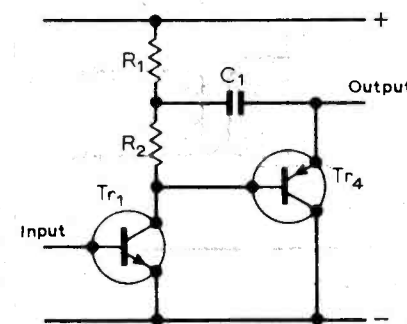


Fig. 10. Simplification of the previous diagram.

by returning the potential divider to the positive supply lines as shown in Fig. 6. Here the single decoupling capacitor C_2 provides a low-impedance path for input and output signals. C_4 and C_5 in series tune the secondary winding and C_4 is larger than C_5 to give the required impedance match to the low input resistance of the transistor.

Hartley oscillator

Similar decoupling techniques are possible in oscillator circuits. In the Hartley oscillator, for example, one end of the tuned circuit should be connected to collector, the other end to base and the inductor tapping to emitter. Fig. 7 shows a tapping diagram in which stabilisation of the mean collector current is achieved by the potential divider R_1R_2 and the emitter resistor R_3 . Such an arrangement is likely to be used if the transistor is required to operate in class A as in oscillators required to give a particularly pure waveform. The required low-impedance connection to the collector is achieved by direct coupling and to the base by the low-reactance capacitor C_1 . The connection between tapping and emitter is, however, achieved via the decoupling capacitors C_2 and C_3 . C_2 is sometimes a smoothing capacitor in the power supply but to minimise impedance in the tapping-emitter connection C_2 should preferably be a separate local component. As before, C_3 can be dispensed with provided C_2 is returned to emitter as in Fig. 8.

Tobey-Dinsdale circuit

A particularly interesting application of decoupling occurs in the Tobey-Dinsdale amplifier circuit, a development of the Lin circuit. The essential features of the decoupling circuit are shown in Fig. 9. The intention here is to drive the complementary pair Tr_2, Tr_3 as common-emitter amplifiers from the output of Tr_1 . The impedance of D_1R_3 is very small and thus Tr_2 and Tr_3 are effectively in parallel although, because they are complementary, their output currents are in push pull. We can thus simplify the circuit by replacing Tr_2 and Tr_3 by a single transistor Tr_4 as in Fig. 10 and the output current from Tr_1 must be directed into the base-emitter junction of Tr_4 . There is a direct connection from Tr_1 collector to Tr_4 base and thus a low-impedance connection is required between Tr_4 and Tr_1 emitters. Unfortunately such a connection would short-circuit the output of the amplifier which is taken from Tr_4 emitter. The inclusion of a resistor in Tr_1 emitter circuit would not make the circuit satisfactory because the internal emitter resistance of Tr_1 would still act as a shunt on the amplifier output: moreover the return of the output signal to Tr_1 emitter would give rise to considerable feedback. This problem is solved, as shown in Figs 9 and 10, by providing a low-impedance path between Tr_4 emit-

ter and R_1 , R_2 junction. The decoupling capacitor C_1 performs this function so that Tr_4 effectively short-circuits R_2 and thus ensures that most of the signal-frequency output of Tr_1 enters Tr_4 . For successful operation R_2 should, of course, be large compared with the input resistance of Tr_4 i.e. of the complementary pair. If C_1 were instead returned to the negative supply rail the base-collector junctions of Tr_2 and Tr_3 would be effectively connected across R_2 : the complementary pair would then operate as emitter followers and their high input resistance would make it difficult to drive adequate current into them.

A consequence of returning C_1 to the top end of R_2 is that the decoupling resistor R_1 is effectively in parallel with the output load of the complementary pair: thus R_1 must be large compared with this load resistance.

Inductors in decoupling circuits

Many of the decoupling circuits which have been discussed include a resistor in the supply lead. This reduces the collector supply voltage available to the transistor and the need to retain an adequate collector voltage limits the resistance that can be used for decoupling. This difficulty can be overcome by use of an inductor in place of a resistor, for its reactance then determines the effectiveness of the decoupling circuit while the resistance determines the loss of collector supply voltage. A.f. inductors are, however, bulky and expensive components and

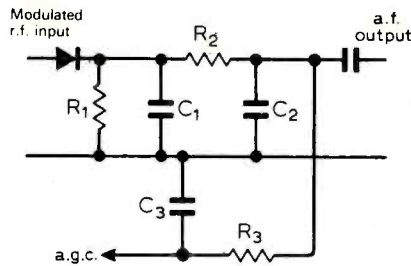


Fig. 11. The diode detector circuit provides two examples of decoupling.

this solution is generally reserved for r.f. amplifiers where small and inexpensive inductors can give adequate reactance. At u.h.f. and v.h.f. ferrite beads threaded on supply leads can give adequate reactance and these can be combined with bush capacitors to form particularly compact decoupling networks.

Diode a.m. detectors

In all the examples of decoupling networks so far considered we have concentrated on the provision of low-reactance paths to confine signals to the areas where they are required. We could, however, alternatively regard these networks as examples where the signals are prevented from reaching areas where they are not required. For example in Fig. 3 signals in the output circuit are prevented from entering R_4 by the provision of C_2 and from entering R_3 by the provision of C_3 . R_4C_2 and R_3C_3 are both, in fact, current dividers in which the current is mainly confined to

the capacitor by making its reactance small compared with the associated resistance. In some decoupling circuits the same end is achieved by the use of potential dividers and the diode a.m. detector circuit of Fig. 11 provides two examples. R_3C_3 is intended to convey direct current to the earlier stages of the receiver to control their gain but it must prevent audio signals from reaching these earlier stages. To be effective therefore the reactance of C_3 must be small compared with R_3 even at the lowest audio frequency of interest, say 50Hz. R_3 is normally given a value large compared with the diode load resistance so that there is no appreciable shunting effect. 50 kilohms might be a suitable value for R_3 and C_3 can then be $1\mu\text{F}$ which has a reactance of 3 kilohms at 50Hz.

Similarly R_2C_2 is intended to prevent r.f. signals from entering the a.f. amplifier but it should not, of course, attenuate audio signals significantly. Thus the reactance of C_2 should be large compared with R_2 even at the highest audio frequency: it will then be even larger at lower frequencies. It would be satisfactory therefore to make the reactance of C_2 equal to R_2 at, say, 10kHz. The loss will then be 3dB at 10kHz, 1dB at 5kHz and less at lower frequencies. If the reactance of C_2 is equal to R_2 at 10kHz it will be only 1/46th of R_2 at 460kHz, approximately the intermediate frequency of a.m. receivers. This gives a loss of 35dB. If R_2 is 820 ohms C_2 could be $0.02\mu\text{F}$ which has a reactance of 800 ohms at 10 kHz.

● continued from p.65

Design a clock-driven circuit using JK flip-flops and NAND gates that will satisfy the given specification.

(1) **I/O characteristics.** As shown in Fig. 11(a) and 11(b).

(2) **Internal characteristics.** The internal state diagram of the required circuit is shown in Fig. 11(c).

(3) **State reduction.** The state table is shown in Fig. 11(d) and examination of this table shows that no state reduction is possible in this case.

(4) **Primitive circuit.** Binary codes are allocated as shown on the state diagram. By direct reference to this diagram the following equations are obtained.

$$S_A = S_0 + S_2 = \bar{A}\bar{B} + \bar{A}B = \bar{A}$$

Therefore $J_A = 1$

$$R_A = S_1 + S_3 = A\bar{B} + AB = A$$

Therefore $K_A = 1$

$$S_B = S_1 + (S_2) = A\bar{B} + (\bar{A}B) = \bar{A}\bar{B}$$

Therefore $J_B = A$

$$R_B = S_3 + (S_0) = AB + (\bar{A}\bar{B}) = AB$$

Therefore $K_B = A$

$$Z_1 = S_0X = \bar{A}\bar{B}X$$

$$Z_2 = S_0X + S_1X = \bar{A}\bar{B}X + A\bar{B}X = \bar{B}X$$

$$Z_3 = S_0X + S_1X + S_2X$$

$$= \bar{S}_3X = \bar{A}\bar{B}X = (\bar{A} + \bar{B})X$$

The circuit implementation of these equations is shown in Fig. 11(e).

Professor D. Zissos will conduct a **five day course** on Logic, Interfaces and Microprocessors from July 4 to 8 at the Southgate Technical College, London N14. Further details from Interprojects Ltd, 29 Church Street, Edmonton, London N9 9DY.

Philips and MCA will present their first UK public demonstration of the optical video disc system at the **Video Disc '77** conference in London, November 8 and 9, say the organisers. The last Video Disc conference was held two years ago, before which similar demonstrations were to be held but the only equipment shown was the now defunct Teldec.

Announcements

The **World Radio Club** have announced revised times of transmission on the BBC World Service: the Sunday transmission at 0815 GMT will be cancelled. The times from Wednesday, September 7 will be: Wednesday, 0815 to 0830, 1330 to 1345 and 2315 to 2330 GMT, and Friday 2100 to 2115 GMT.

2,000 candidates responded to NASA's invitation to participate in the *Spacelab* experiment in 1980 (See WW May 1977, p66). NASA say they and the European Space Agency have now selected 222 representing the US and 14 other countries: NASA chose 81 from the US and the rest from India, Japan, Canada, France and Belgium. The other 136 investigators came from 10 ESA member states, Austria and Norway.

Salon International des Composants Electroniques

New products seen at the Paris show

For one week in April, Paris again became the centre of world electronics. It brought together 1260 exhibitors, of which 534 were French and 726 were from 30 other countries. Entrance passes alone indicated that there were 75,972 visitors, from 87 countries, almost 13% of these being from foreign countries. Although this is 5.1% more than last year, it must be remembered that last year's show did not include a section on test and measuring equipment.

Apart from increases in the number of foreign exhibitors this year – for example, there were about 30% more British and 10% more West German participants – and the introduction of newcomers from countries such as Korea and India, there were also changes in the mixture of activities of the companies exhibiting. Although exhibitors from the USA increased by almost 60%, the number of major American semiconductor companies was less than in 1976.

It is always difficult, at a show of this size, to assess a particular industry, but, if judged solely on the enthusiasm of the exhibitors and visitors at the show, a fair conclusion would be that the European electronics industry is alive and well.

Several families of power semiconductors were launched by RCA Solid State – Europe. Among these developments was a 'quick-connect' package intended for medium- and high-power silicon controlled rectifiers and triacs. The package, which may be fixed on a TO-3 heatsink, uses AMP type connectors. An example device in the new package is the T6260 40A triac. Also being launched by RCA was the Versawatt TO-220 range of silicon controlled rectifiers. These fast-switching devices are designed for reverse-blocking applications and have turn-off times as short as 6µs. The rectifiers are rated at 5A r.m.s. with maximum trigger currents of 50mA. RCA was also showing a new range of epibase power transistors in TO-3 packages, which they claim is the largest range of its kind on the market. This range includes the 2N3055 device, which is also available in hometaxial construction.

Other products launched by the company included a range of medium-power n-p-n transistors, several integrated circuits and a microprocessor aid. The transistors, designated as RCP111/3/5 and /7, are high-voltage, low collector-base capacitance types, especially designed for television applications such as video and audio output stages, regulators and linear amplifiers. The new microprocessor aid is a hand-held data terminal which offers a low-power, soft-copy alternative to conventional printing terminals. It uses a calculator-type keyboard and an eight-digital i.e.d. display. The Cosmac CDP18S021 Micro-terminal, as it is called, is designed to interface with Cosmac hardware support systems to provide control, communications and debugging functions.


On the AEG-Telefunken stand was the TDA1062, an f.m. tuner unit for car radios. The unit consists of a mixer, modulator and phase-sensitive detector

suitable for frequencies up to 200MHz. It also has a built-in a.g.c. amplifier for external p-i-n diodes, and is adaptable to capacitance diodes. Variometer or variable capacitor tuning may be used and tuning a voltage of only 2 to 7.5V is necessary. The makers claim that no alignment is needed. Another device was the TDA1068 noise suppressor, which is designed for the a.f. section of car radios. It will work from a supply voltage from 9.5 to 15V and is suitable for mono or stereo operation. Three PAL colour-TV devices, TDA2140/50 and /60, were also shown. Type 2140 is a sub-carrier reference oscillator, type 2150 forms a luminance and chrominance amplifier and type 2160 contains the synchronous modulator and RGB matrix.

Of particular interest on the Texas Instruments stand was the TBM0103, a non-volatile, 92,304-bit, magnetic-bubble memory on a single chip. The bubble chip is comprised of a gadolinium-gallium garnet substrate upon which a magnetic epitaxial film is grown. Patterns of permalloy metal are deposited on the film to define the path of bubble domains, which are made to move in a shift-register fashion when in the presence of a rotating magnetic field. The 14-pin d.i.l. module measures 1.0 × 1.1 × 0.4in and is specified for 100kHz operation, with an access time of 4ms for the first bit and a cycle time of 12.8ms for the 144-bit page. Continuous-rated power consumption is ½W.

Four differential line-transceiver i.c.s, types SN55118, SN55119, SN75118 and SN75119, were also announced by Texas Instruments. These devices are designed for interfacing between t.t.l.-type digital systems and differential data transmission lines. Each circuit combines a three-state driver and a receiver in one package.

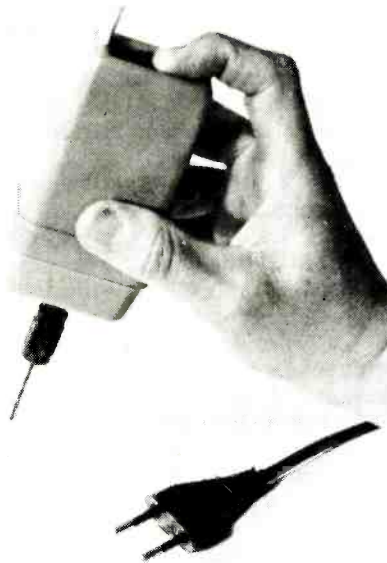A m.o.s.f.e.t. transistor has been developed by Texas Instruments to help manufacturers improve the performance of the r.f. section of Citizen's Band tuners. The TIS148 transistor provides 20dB conversion gain with only a 3.2dB conversion noise figure when used as a mixer for 27MHz. The device also eliminates the need for an r.f. amplifier.



The new miniature 220 to 250V Bimrill shown by Boss Industrial Mouldings Limited. The drill is supplied with three collets for accepting twist drills, burrs and mops with shanks up to 1/8 in diameter. Its 7500 rev/min motor is powerful enough to drill through brass and steel.

A new 16-bit microprocessor has also been introduced by Texas. It is believed to be the first monolithic central processing unit produced using bipolar integrated injection logic (i²l). The SBP9900 microprocessor uses this technique to provide selection by the user of speed and power and static operation, to enable a single non-critical d.c. power supply to be used and to ensure direct t.t.l.-compatible inputs and outputs.

A digital multimeter was launched at the show by Gould Advance Limited. The new instrument called the Alpha III, is a low cost version of the Beta multimeter launched in 1976. The instrument has a 3½-digit l.e.d. display and is claimed to operate for more than 50h from one set of batteries.


Nippon Electric were showing a microcomputer board teaching kit called the TK-80. The kit, which until the show had not been introduced to the European market, provides all the hardware elements, software tools and information for tutorial introduction to, and advanced details for, the μ PD8080A 8-bit microcomputer and its software. The TK-80 is built around NEC's μ COM-8 microcomputer family of l.s.i. devices, including the μ PD8080A c.p.u., a clock generator, a r.a.m., a r.o.m., a keyboard and an l.e.d. display.

The largest of all the stands at the show was that representing Thomson-CSF, who had a large array of new products ranging from transistors and capacitors to brushless d.c. motors and cathode-ray tubes. Included in the devices from the Electron Tubes division was the TH5108 electronically-tunable, X-band Gunn diode source. This model delivers more than 30mW over its ± 100 MHz tuning range and its centre operating frequency can be anywhere in the 9200 to 9300MHz band. The frequency drift for this varactor-tuned source is less than 200kHz/°C.


The THX914, also from Thomson-CSF, is a plasma display panel having a capacity of over 1300 characters (32 lines of 42 characters) with a useful screen area of 163mm square. The THX914, which is t.t.l.-compatible, has all the normal functions of an a.c.-driven plasma panel, with a fast access time of 200 μ s to write a five-by-seven point character.

Another device from the Electron Tubes Division was the THX1107 c.c.d. device which is a development of the THX1105, first introduced in 1976. This analogue delay line has 512 elements, a maximum bandwidth of 5MHz and a distortion figure of 1% for a 500mV output signal.

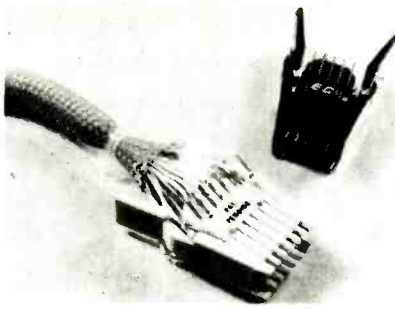SGS-Ates have managed to produce i.c. amplifiers capable of handling high currents ($I_{C(max)} = 3.5A$) and high voltages ($V_{CE(sus)} > 44V$). This has allowed a typical output power of 20W into a 4 Ω loudspeaker, with a distortion of less than 1%, using a single and inexpensive integrated audio amplifier, the TDA2020. Output powers of 180W



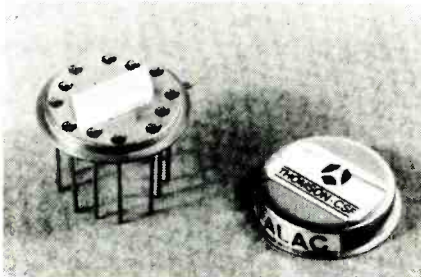A dual-in-line test clip, displayed by UMD Amphenol, is suitable for use on 14 and 16 contact devices. The clip, called the DIP/LOC, is designed to lock on to an i.c. to ensure positive contacts with all leads.



A new surface-acoustic-wave filter designed for PAL television receivers shown by Siemens Electron Tube Division. With this device it is possible to design an i.f. stage that features superior performance and stability characteristics compared to the conventional L-C type. These types of filter are particularly suitable for teletext decoder circuits.

can be achieved using two of these amplifiers. SGS-Ates is also developing a new family of power transistors giving up to 50A current handling capability, high switching speeds of less than 0.5 μ s, and operating frequencies of 50MHz. Devices in the range also have low leakage currents. The transistors will be manufactured in planar technology, so that they will withstand adverse operating conditions.

A large selection of new devices was being shown by Siemens. An audio amplifier i.c., in a TO220 case, was developed by the company specifically for use in car radios. With two 4 Ω loudspeakers connected in parallel, the TDA 2870 provides 10W from 14.4V, and when used with only one 4 Ω loudspeaker the output power is 5W. The device has built-in temperature-sensing overload and short-circuit-current protection. In addition it has a low thermal resistance of 5°C/W maximum.

Among the new power semiconductors from Siemens was a fast silicon diode for TV receivers, a mains thyristor and two fast power diodes. The silicon diode, type BY302, has a soft recovery performance and a reverse recovery time of 250ns. The thyristor, type D10, has a high blocking stability and a mean on-state current of 8A. The power diodes, types SSiN36 and SSiN46, are intended preferably for use in forced-

commutated s.c.r. circuits. Model N36 is a screw bolt design having a maximum allowable r.m.s. current rating of 550A and model N46 is of the disc type, rated at 900A. Maximum forward voltage ratings for the devices are 2.05V and 2.00V respectively.

Other power devices were the BStP49 and the BStQ63, both high-speed thyristors, and the BStR68L power thyristor, all in flat-pack ceramic insulated cases. These devices were developed mainly for line-commutated converters. Maximum r.m.s. on-state currents and turn-off times (at the maximum junction voltage) for the P49 and Q63 are 1100A & 10 μ s and 1000A & 50 μ s respectively.

Also seen at the show

Continental Device (India) Limited; a solar cell designed to supply transistor radios. The device provides about 6V at 300mW (in India), and is available in different sizes and with various specifications.

Intersil; types 7106 and 7107 c.m.o.s. monolithic a.-d. converters designed for direct drive of 3½-digit l.e.d. displays or equivalent l.-c. displays.

Raytheon; type 2901A, a four-bit microprocessor slice, said to be 30% faster than the 2901. Three quad op-amps; type HA4741, which has no crossover, the pin-compatible LM348 with built-in overload protection, and type RC4156, having an improved noise figure and a 3.5MHz bandwidth.


Silicon Transistor Corporation (STC); the model STA9160 switching transistor in a TO-3 can. This device has ratings of 500W and 100A, and a V_{ceo} of 120V.

Jaybeam Limited; a 2.5m skeleton parabolic dish antenna having yagi and shrouded feed assemblies. Models available include an 18dBd (w.r.t. a dipole) antenna for the 400MHz band, a 24dBd antenna for u.h.f. TV bands, and a 26dBd antenna for the 900MHz band. In addition there is a 28dBd dish for 1500MHz and a 31dBd dish for 2GHz.

ITT; a battery-operated laser torch designed specifically for use with night vision equipment. The lens system can be adjusted and will provide a spot diameter from 1.5 to 8m at 100m range.

Hewlett Packard; two dual optically-coupled isolators, models HCPL-2730 and 2731. These units have very high transfer ratios (10:1) and low input currents of 500 μ A and will operate up to 200k-bits/s. Isolation between inputs and outputs is 3000V.

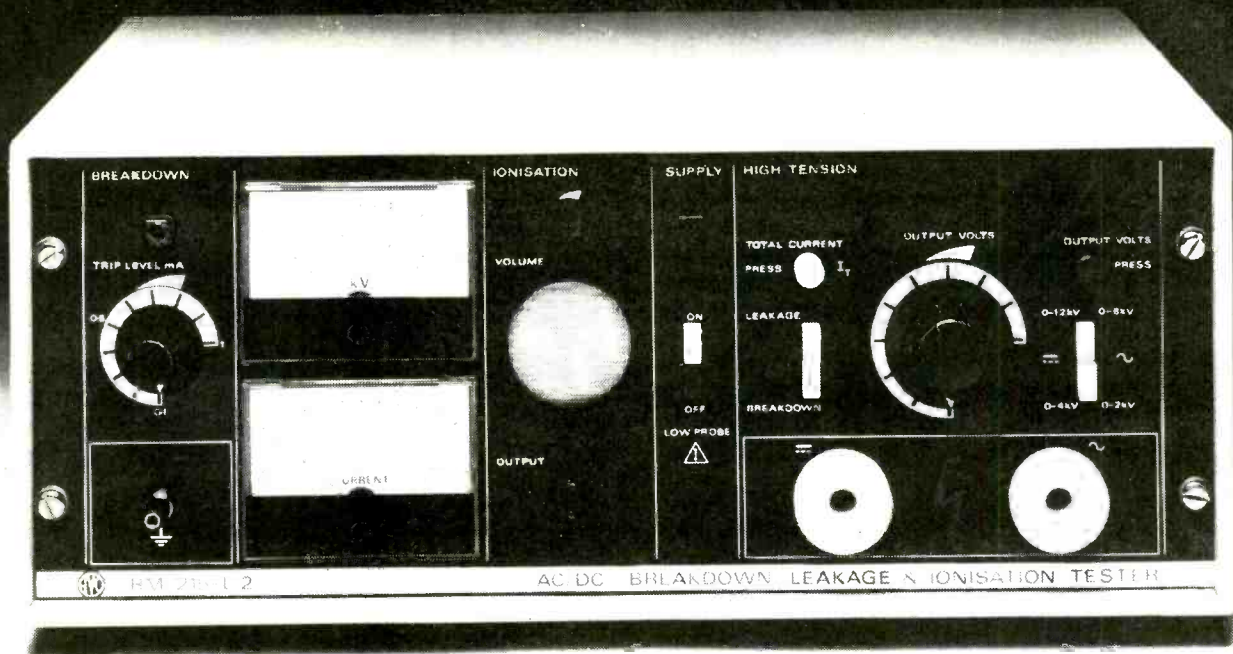Thomson-CSF; a bipolar power transistor, designed by the Microwave Microelectronics Division, which is claimed to be one of the best r.f. transistors on the market. The 250W p.e.p. device, model TH430, is intended for s.s.b. transmitters in the range 2 to 30MHz. It has a power gain of at least 14dB.



Ion out your quality control problems

The AVO Breakdown and Ionisation Tester RM215-L/2 is specifically designed to help solve all manner of quality control problems.

It measures resistive leakage current under both AC & DC voltage testing conditions as well as total AC leakage current. Test voltages up to 12 kV DC and 6 kV AC are continuously variable and breakdown current level is adjustable up to 1 mA. A built-in loudspeaker gives audible detection of ionisation and there are connections for earphone or an oscilloscope.

The circuit features low internal resistance yet at the same time limits the maximum output current, even at short circuit.

With the RM215-L/2 you can carry out general flash testing, measurement of breakdown voltage – even after breakdown – and the detection (and counting) of spurious flashovers.

Equally suited to both destructive and non-destructive testing, the RM215-L/2 is a piece of test equipment you cannot afford to be without. If you have some problems that need to be 'ioned' out, get in touch for full details.

APPLICATIONS

- Flash testing of electrical components.
- Measurement of breakdown voltage on electrical components and materials.
- Measurement of insulation resistance at high voltage.
- Measurement of d.c. leakage current.
- Measurement of a.c. leakage current and total current.
- Non-destructive insulation testing of materials and components.
- Detection of ionisation in electrical assemblies.

Designed to meet B.S., V.D.E. and I.E.C. Safety Requirements.



Avo Limited, Dover, Kent.
Tel: Dover (0304) 202620.

THORN Measurement Control
and Automation Division.


SOC20.



The most powerful Monolithic IC amplifier in the world.

20 watts output (continuous sine wave) . . .
 Less than 0.2% total harmonic distortion at *all* powers,
all frequencies . . .
 And totally electronically indestructible!

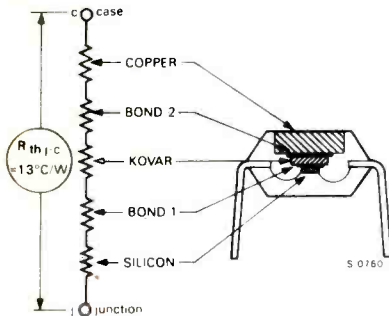
Until recently, all monolithic IC chips suffered from two basic design weaknesses. First, thermal runaway causing heat to build up as current increased; and second, short circuiting.



Standard plastic package with copper slug.

Until the SOC20 IC chip! This extraordinary new power amplifier chip is uniquely designed to improve thermal dissipation. It also has two separate built-in circuits, one of which measures on-chip temperature. If this should rise above 150°C the output transistors are switched off thus preventing thermal runaway.

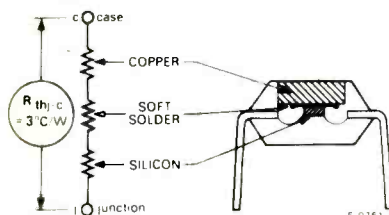And short circuits? The other circuit continuously monitors both current and voltage. If the product of current and voltage rises above a critical level, the



SOC20 plastic package with chip directly soft-soldered to copper slug.

drive is adjusted to bring the transistors within safe operating limits.

The amplifier can drive speakers of any impedance – maximum power will only fall outside the recommended 4 Ω – 8 Ω range.

And *any* pin on the chip may be shorted to *any* voltage in the system for *any* length of time . . . and *no* damage will occur!

Superb quality . . . extraordinary power

The SOC20 isn't only safe . . . it's also extraordinarily sophisticated. Total harmonic distortion is less than 0.2% at all powers and all frequencies – and in normal use is well below 0.1%.

If power is at a premium, use two SOC20 amplifiers in 'Full Bridge' to give over 40 watts continuous into 8 Ω speakers.

The SOC20 is naturally guaranteed unconditionally for one year. Although with the SOC20's unique patented design, we think you'll have little cause to make use of any guarantee!

Specification

Maximum supply voltage
 ± 22 V (44 V total)
 Output power
 20 watts continuous 4 Ω or 8 Ω
 Open loop gain
 100 dB
 Supply voltage rejection
 50 dB
 Input noise voltage
 4 nV
 Number of transistors
 18

Supplied with free printed circuit board, heat sink mounting bracket, comprehensive instructions, and suggested applications.

The SOC20 will work on any supply from 12-44 volts and therefore can be used for in-car as well as domestic applications. Apart from its obvious audio uses the fact that it is DC coupled throughout makes it ideally suited for servo systems – in radio-controlled models for example.

Incorporate the SOC20 in your equipment today!

SOC20's cost £4.95 each, or £7.95 a pair for, say, stereo applications. Only a few readily-available components are needed to build a full amplifier unit.

Of course, the SOC20 comes with a 10-day money-back guarantee.

Sinclair Instrument Ltd,
 6 Kings Parade,
 Cambridge, Cambs., CB2 1SN.
 Tel: Cambridge (0223) 311488.

To: Sinclair Instrument Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me.....(qty) SOC20 Monolithic IC Amplifiers (£4.95 each or £7.95 per pair, inclusive of VAT at 8%).

I enclose cheque/money order/

postal order for £_____

Name _____

Address _____

WW/7

(PLEASE PRINT). Offer valid in UK only.

Weather-satellite picture facsimile machine — 5

Modification of the facsimile machine for radio weather charts

by G. R. Kennedy

Parts one to four of this article described a prototype rotating-drum facsimile machine for producing APT, SR and WEFAX transmission pictures. This final part describes modifications to the basic design of the machine so that it may be used specifically for meteorological purposes. The modifications will enable both weather satellite and radio facsimile broadcasts to be printed.

Weather charts, prepared by hand or computer, are transmitted by short-wave and long-wave radio by most national meteorological organisations, (see Ref. 13). The internationally adopted standards for drum rotation speeds and index of co-operation (i.o.c.) are 60, 90 and 120 rev/min and 576 or 288 respectively. The 288 index is sometimes referred to as 'alternate line scanning'. 90 rev/min charts are invariably for aeronautical use. The transmissions are frequency shift keyed $\pm 400\text{Hz}$ on short-wave and $\pm 150\text{Hz}$ on long wave. Some charts are sent on one sideband of a double side-band trans-


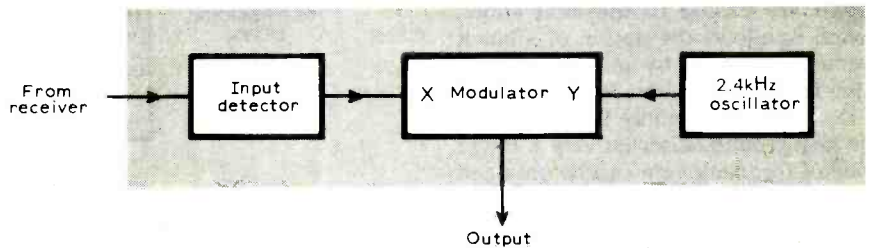


Fig. 16. Frequency-shift keying (f.s.k.) terminal block diagram,

mission, often with teleprinter traffic on the other. Reception requires a good communications receiver with a stable beat frequency oscillator (b.f.o.) and a frequency shift keying (f.s.k.) terminal connected to the receiver audio output (see Fig. 16). This provides a machine-compatible output to the facsimile machine described earlier. The audio

signal from the receiver is detected and applied to one input port of an analogue modulator or mixer, an accurate 2.4kHz signal being applied to the other. The output is the product of the two signals. Since most charts are black and white, the detector is arranged to latch between two levels corresponding to black and white; this enhances copy under poor signal conditions. For those cases where greys are required, such as for the Russian composite chart and Meteor satellite transmissions, the detector can be switched to respond to varying levels. The detector and a.m. modulator are powered from a stabi-

Fig. 17. Input detector of f.s.k. terminal circuit.

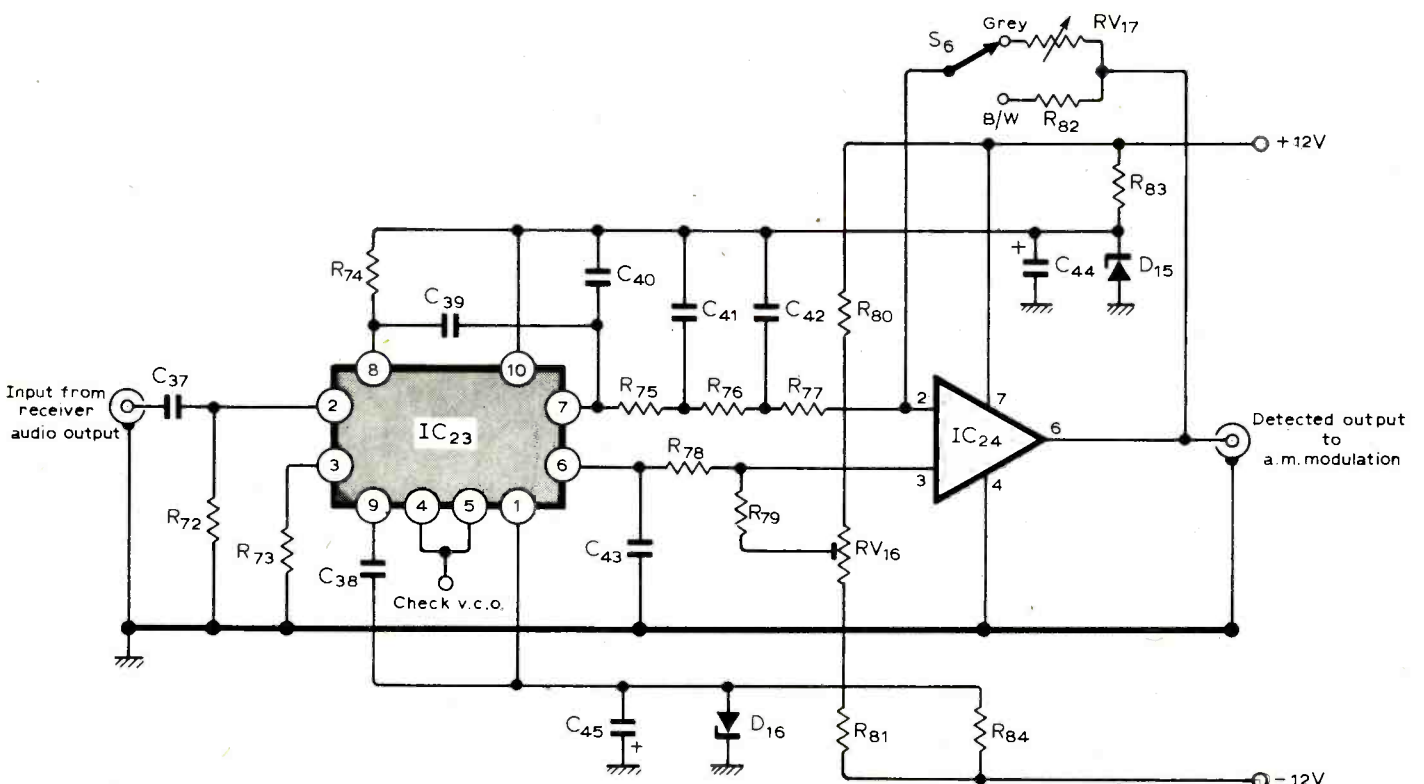

lized power supply with a very low output ripple.

The circuit details for the input detector are shown in Fig. 17. The receiver audio is applied to one input of the phase-lock loop IC₂₃ via C₃₇, while the other input is balanced to ground. The output comprising the f.m. demodulation of the input frequency-shift passes through the low-pass filter R₇₅, R₇₆, R₇₇, C₄₁ and C₄₂ to operational amplifier IC₂₄. The d.c. level from IC₂₃ is maintained by the input to the non-inverting input of the op-amp via R₇₈. C₄₃ decouples any residual v.c.o. signal, and together with the low-pass filter removes the loop p.s.d. sum frequency. IC₂₄ is run with its negative rail to ground to ensure that only positive signals are passed to the next stage. Switch S₆ allows the option of a black and white picture by placing a large value feedback resistor, R₈₂ across IC₂₄ so that it latches solidly between positive and ground. Alternatively a lower value of feedback gain can be obtained by selecting RV₁₇ which can be preset to give the required grey scale. The grey reference level for half carrier shift is finely set by preset RV₁₆.

The output of the detector is applied to the detector i/p terminal of balanced modulator IC₂₅ via RV₁₉, which sets the modulation depth. IC₂₅ is a double balanced mixer which is used here to amplitude modulate the detected signal onto a 2.4kHz carrier. This is fed in via RV₁₈, which sets the carrier level, to the carrier input. Input biasing is effected by R₈₆, R₈₇, R₈₈ and R₈₉. The residual level of the output carrier is set by RV₂₀ so that the carrier is modulated to 75%, the residual 25% being used in the facsimile machine for clocking. The gain is preset by R₉₀, the bias by R₉₂ and R₉₃ and R₉₄ are the chip output transistor collector loads. The output terminals are at approximately +10V, so the output signal is a.c. coupled by C₄₈. R₈₅ and R₉₁ set the carrier mean d.c. level. The -5V rail is derived from the -12V supply by R₉₅, D₁₇ and C₄₉. (Note: pin assignments are shown in Fig. 18 for the 'L' 14 pin d.i.l. version of the Motorola MC1496. With appropriate pin connections, the Motorola 'G' version or the Signetics NE5596 'A' or 'K' can be used).

With the circuit values given, the v.c.o. frequency of IC₂₃ is 5.5kHz. This was found to be a good compromise between the upper frequency limit of the receiver audio amplifier and the lower frequency limit for black to white transitions for fine detail. Tests showed that for a b.f.o. frequency of 3kHz fine lettering was not discernable, and few communication receivers have a good response above 8kHz.

A crystal-controlled 2.4kHz generator is shown in Fig. 19. There are many ways of producing the frequency accurately, but this shows a method using a fairly standard crystal bar. The 144kHz crystal is the feedback element in a simple t.t.l. gate oscillator, IC₂₆. The



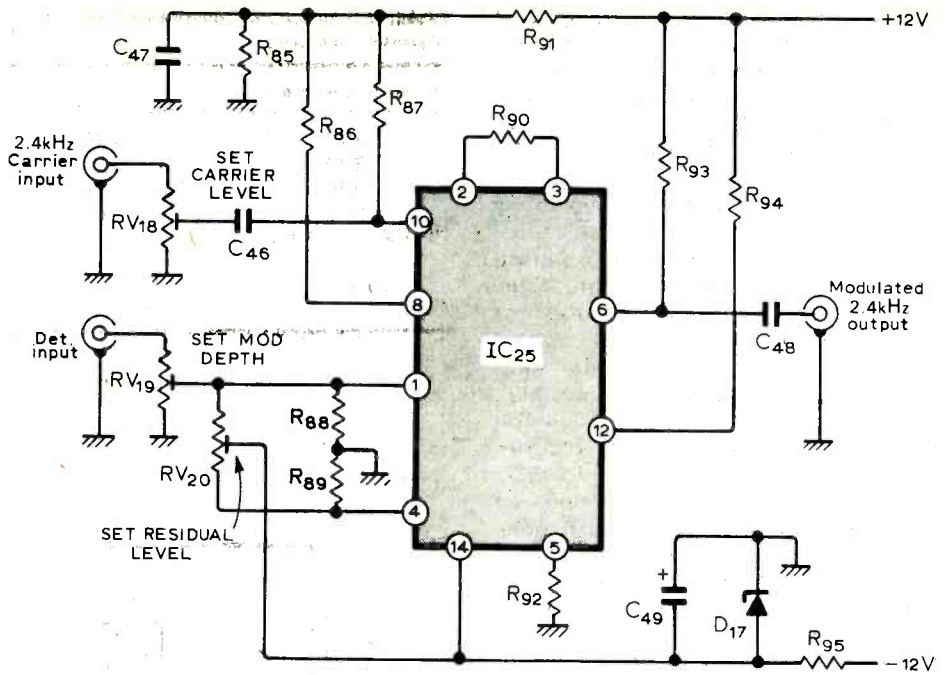


Fig. 18. Amplitude modulator of f.s.k. terminal circuit.

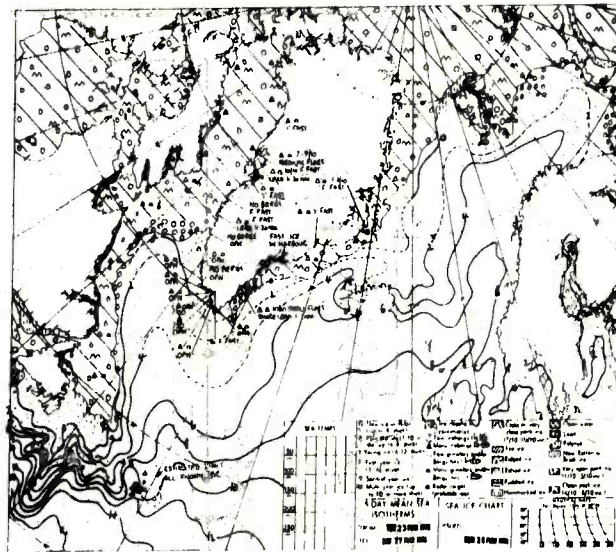

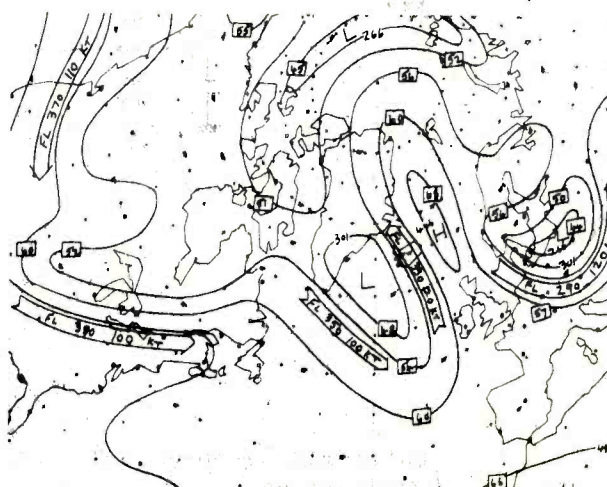120 rev/min radio weather facsimile chart. A typical chart for general meteorological use, showing sea ice and 5 day mean sea isotherms.



90 rev/min radio weather facsimile chart. Charts sent at 90 rev/min are invariably for aeronautical use. This chart shows upper air wind speed for pilots flying the North Atlantic.

output is divided by five in IC₂₇ and further divided by 12 in IC₂₈. The resultant 2.4kHz is taken directly to the f.s.k. modulator IC₂₅ and buffered and inverted in IC₂₉. This output is used in the facsimile machine to drive the motor circuitry and detector. The inversion in IC₂₉ partially corrects for phase shift in the f.s.k. input detector and precludes RV₈, the sample pulse delay pot in the facsimile machine having to be adjusted differently for satellite pictures and facsimile charts. The power supply circuit for the f.s.k. terminal, shown in Fig. 20, uses i.c. voltage regulators IC₃₀ and IC₃₁ with external transistors Tr₂₀ and Tr₂₁ to increase the regulating sensitivity. This gives no output protection, but gives a very high input rejection and hence extremely low ripple. If a less smoothed supply is used, hum bars are prone to appear on the final print as a regular speckling of the chart lines.

The actual modifications to the facsimile machine itself are straightforward and involve the addition of a phase-locked frequency generator, two binary dividers, and switching to change the motor drive frequencies. Fig. 21a shows the essentials of the basic system before modification. Note that the APT/SR switch S has been added to illustrate the routing of APT or SR line division frequencies — in the basic machine the 1/5 line position of the line division switch S₃ can be used for APT/WEFAX. The modifications to the basic design are shown in Fig. 21b. The line division switch remains, but the APT/SR switch is enlarged to give positions for 60, 90, 120 and 240 drum revolutions per minute, as well as the SR line division rates of 240 rev/min for 1/5 line, 192 rev/min for 1/4 line and 144 rev/min for 1/3 line. For 60, 120 and 240 rev/min the 2.4kHz is divided by 50 and is selected by S_{7b} to pass directly to the motor drive power amplifier, or divided by two, or divided by four, to give 240, 120 or 60 rev/min respectively. For 90 rev/min the path is the same as for 60 rev/min except that the 2.4kHz is increased 1½ times to 3.6kHz to give an output of 60 rev/min times 1½, i.e. 90 rev/min. The 3.6kHz generator is shown in Fig. 22. The 2.4kHz input is applied to phase-lock loop IC₃₂. The output of the 3.6kHz v.c.o. is amplified by Tr₂₂ and taken to the drum function switch S_{7a} and to duodecal divider IC₃₃ connected as a divide-by-three circuit. The 1200 Hz output from this circuit is returned to IC₃₂ in order to phase lock the v.c.o. to the 2.4kHz input. The SR signal path remains the same as in the basic scheme. Since the motor drive circuit is not as efficient at lower frequencies, RV₁₁ in the motor drive circuit (Fig. 12) is advanced when the chart modification is carried out. The drive at the higher frequencies is then automatically reduced by S_{7d} switching the RV₁₁ wiper to ground via R₁₁₁ for 240 rev/min and R₁₁₂ for the SR frequencies. The motor drive voltage therefore remains

Table 1. Settings for gain potentiometer RV₆ (on a scale of 0-10) as used on the prototype facsimile machine.

Charts (rev/min)	I.o.c.		Setting
120	228	(no expansion, linear)	8.20
120	576	(no expansion, linear)	7.20
90	576	(no expansion, linear)	7.00
60	576	(no expansion, linear)	6.80
NOAAs, Meteor-25		with appropriate log/lin and expander settings)	3.00
ATS-3		with appropriate log/lin and expander settings)	4.50

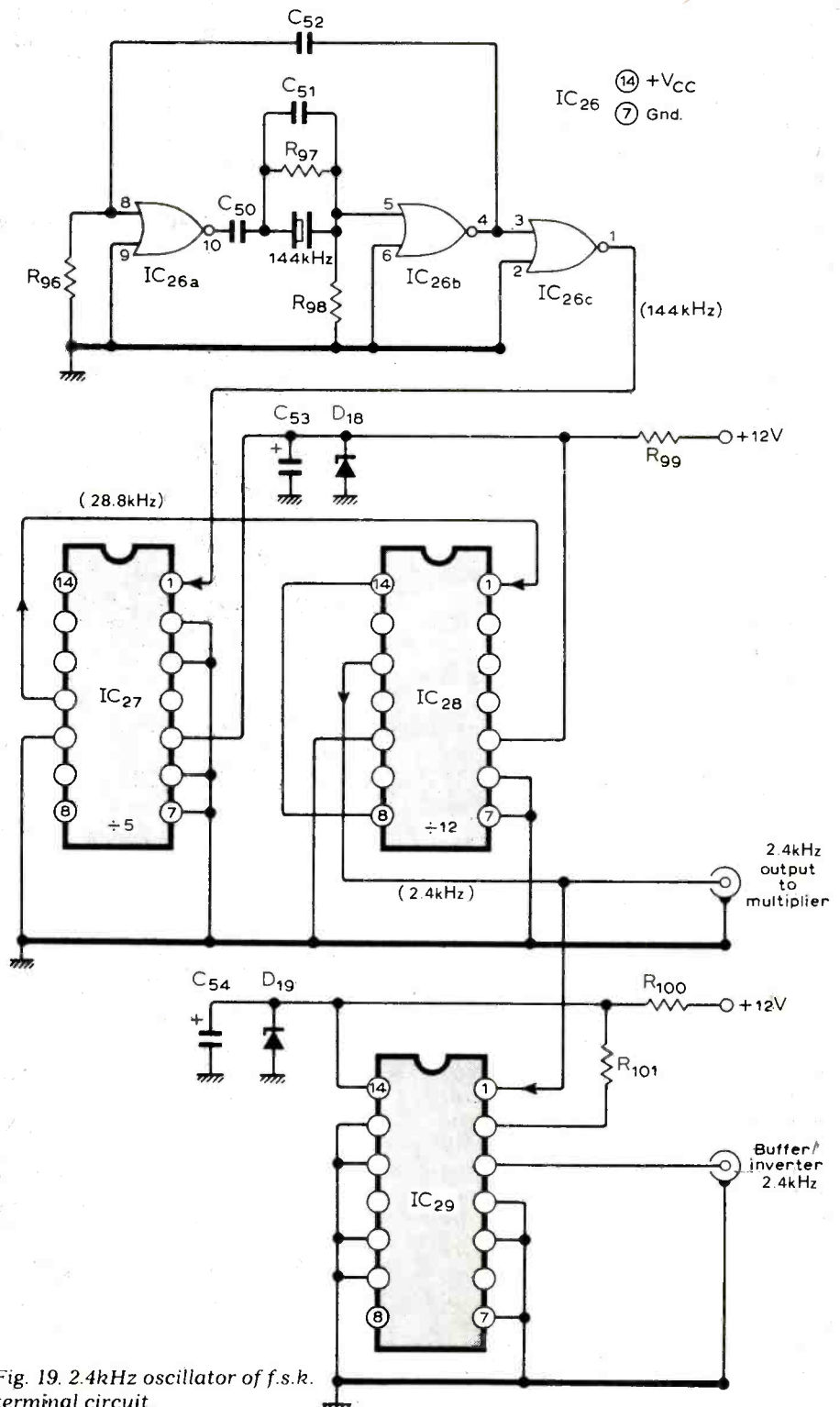


Fig. 19. 2.4kHz oscillator of f.s.k. terminal circuit.

Fig. 20. Low-ripple power supply for f.s.k. terminal circuit.

approximately constant at all drum rates. Depending on the type of transformer used in the motor power amplifier, the values of coupling capacitors C_{24} , C_{25} and of tuning capacitor C_{27} in Fig. 12 may have to be increased, although in the prototype this was not found to be necessary.

The traverse modification concerns the provision of two traverse speeds by switching and an alternative gear train. The same gears are used for SR pictures and 120 rev/min charts, but for 60 rev/min charts the standard synchronous motor used for the traverse would not run on a 12Hz supply in the prototype and simple switching was arranged to apply 50Hz mains to the motor with a replacement gear train to give the correct rate of drive. For 120 rev/min the switching between the synchronous low speed (normal) and the 50Hz rate (fast) gives approximately the correct drive speeds for 576 and 288 i.o.c. respectively. At 60 and 90 rev/min, charts are normally only sent at 576 i.o.c. The gearing has to be changed to a ratio of 7:1, using the motor and roller size described earlier. The situation for printing satellite pictures remains the same, i.e. direct drive (1:1) for ATS-3, 2:1 at "normal" for NOAAs, and 2:1 at "fast" for Meteor-2. (Note: as a guide, in the original machine the 7:1 nominal gearing was 60-107 for motor to shaft, 23-90 for shaft to roller, these representing teeth of diametrical pitch 100).

Operation for radio facsimile charts

The facsimile machine gain pot setting has to allow for the effective writing speed of the crater-tube light beam at different drum and traverse rates. The prototype used an analogue turns counting dial for setting RV_6 (see Fig. 7). The settings used are set out in Table 1.

The output of the f.s.k. terminal is taken to the expander input, with the expander set for a direct signal i.e. no expansion. Phasing is carried out as for satellite pictures. No strobing is used and the monitor oscilloscope is triggered from the sync output socket. The drum edge pulse thus appears every two or four sweeps of the oscilloscope time-base; this is quite adequate for positioning the drum and chart edges. Detector switch S_6 is set to black-and-white, the receiver is tuned to the required signal and the beat frequency oscillator set to give bright/dim keying of the crater tube. This can be done without great precision on short-wave

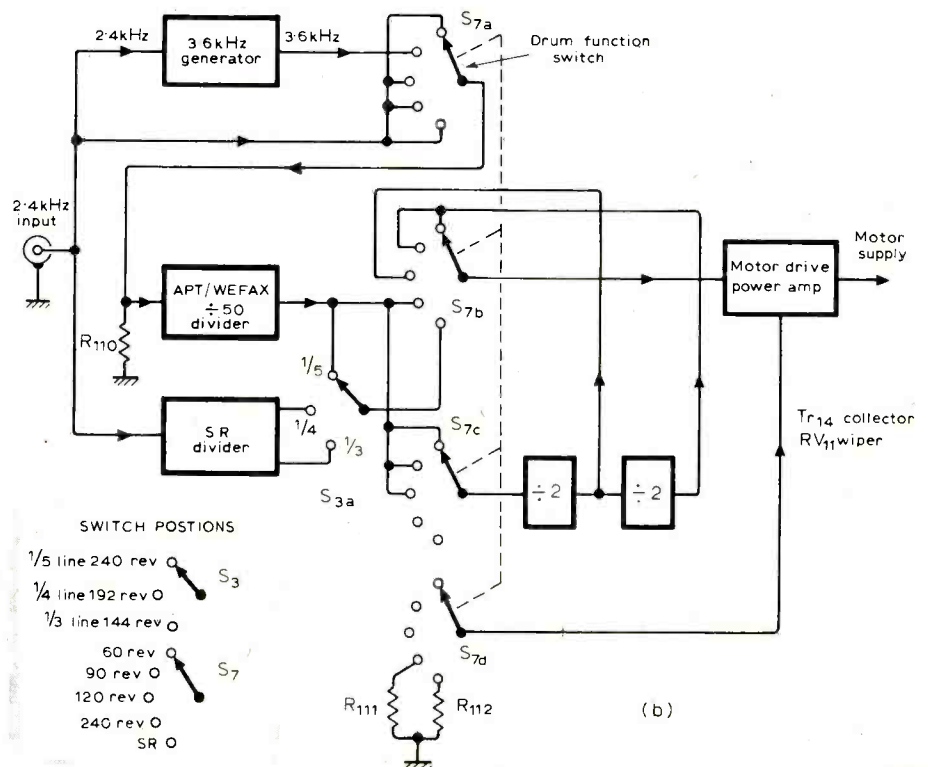
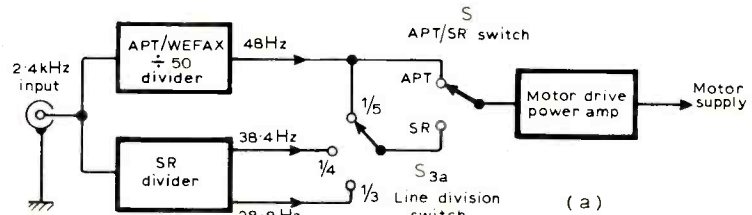
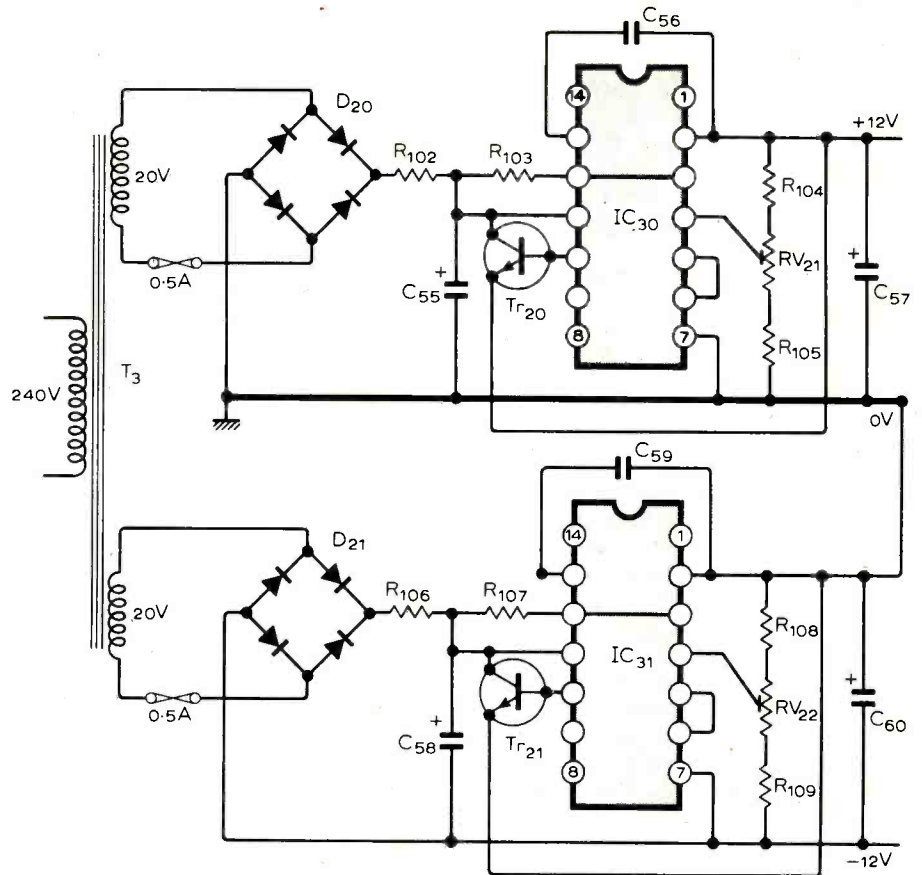


Fig. 21. Essential modifications to the facsimile machine, showing (a) - before modification and (b) - after modification.

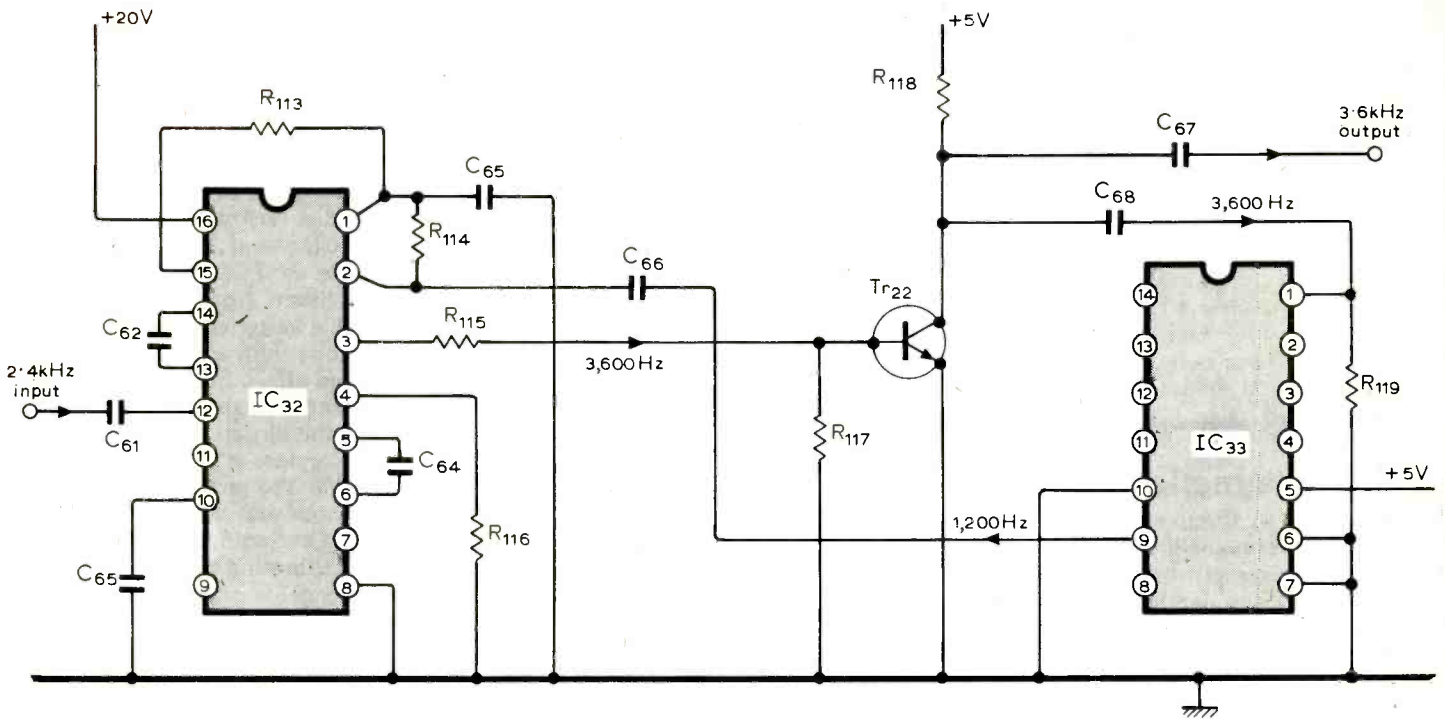


Fig. 22. Phase-locked 3.6kHz generator circuit for "90 rev/min" charts. Correction note! On IC₃₂ the connection shown from pin 10 to ground via C₆₅ should be a connection from pin 11 to ground via C₆₃.

but requires more finesse on v.l.f. signals due to the reduced frequency shift. Received chart quality can be improved in the presence of interference by reducing the receiver i.f. bandwidth to just encompass the carrier shift. As a matter of detail, most transmissions have a white inter-chart level and short duration black edge phasing pulses. Those stations of French, or previously French colonial origin, send a black resting level and half-line black/white phasing bars. According to which side of the carrier the b.f.o. is tuned — for double sideband transmissions — the chart may be printed as black lines on white or vice-versa. The option is useful not only for slide production but also to enable a readable copy to be obtained if there is severe interference to one side of the carrier.

The Russian weather charts, that contain strips of computer-processed Meteor satellite pictures, require the detector to be switched to grey on S₆ and RV₁₇ adjusted for optimum results, consistent with black lines being printed on the chart.

Photographic materials

The author has found that a most suitable material for all prints, both satellite pictures and radio facsimile charts, is Ilford's Ilfospeed 2.1.M and 3.J. M, a fast-processing resin coated, polyethylene laminated paper. For development an Ilfospeed developer is available, although Kodak D-19 used in its concentrated working solution strength has given excellent results.

It should be noted that this article refers to special radio transmissions and any enquiry concerning reception licencing should be addressed to the relevant licencing authority.

Components list

Resistors (¼W 20% unless otherwise stated)

72	560	96	1.8k
73	560	97	150k
74	4.7k	98	1.8k
75	3.3k	99	120, 1W
76	3.3k	100	270, ½W
77	3.3k	101	470
78	10k	102	10
79	10k	103	2.2k
80	4.7k	104	680
81	4.7k	105	680
82	1.2M	106	10
83	270, 1W	107	2.2k
84	270, 1W	108	680
85	1k	109	680
86	47	110	2.7k
87	47	111	100
88	47	112	330
89	47	113	1k
90	1k	114	1k
91	1k	115	1.5k
92	6.8k	116	1.8k
93	3.9k	117	100
94	3.9k	118	1k
95	330, ½W	119	1k

Transistors

20	BFY51 or similar
21	BFY51 or similar
22	2N3704 or similar

Transformer

3	0-20V @ 1A
	0-20V @ 1A
	RS Components

Switches

6	SPST toggle
7	4 pole 5 way rotary

Crystal

144kHz quartz bar (Senator Crystals)

Diodes

15-19	5.1V400mW zeners
20	RS REC70 or similar
21	RS REC70 or similar

Integrated circuits

23	NE565	29	SN7437N
24	SN72741N	30	LA723C
25	MC1496L	31	LA723C
26	SN7402N	32	NE562B
27	SN7490N	33	SN7492N
28	SN7492N		

Variable resistors (presets)

16	2.5k 10 turn		
17	0.5M	20	10k
18	10k	21	2k
19	20k	22	2k

Capacitors (—F unless otherwise stated)

37	0.022	53	100/25V
38	0.01+0.0015	54	100/25V
39	0.0012	55	200/35V
40	0.022	56	100p
41	0.047	57	100/35V
42	0.047	58	200/35V
43	0.082	59	100p
44	100/25V	60	100/35V
45	100/25V	61	0.1
46	0.22	62	1.0 Mylar
47	0.33	63	0.068
48	0.10	64	0.068
49	47/12V	65	0.082
50	0.0068	66	0.082
51	560p	67	0.47
52	0.01	68	1.0

New Products

Electromagnetic pump

The Appliance Components Eckerle ETU21 electromagnetic piston pump will handle both corrosive and non-corrosive thin, clean liquids. The latest version is fitted with Delrin inlet and outlet fittings but a more expensive model with stainless steel fittings is available. Measuring 2¼ in × 3¼ in, the pump is self-priming and will handle up to 11 gallons an hour. It may be driven via a silicon semiconductor diode for a 12 to 240V 50Hz a.c. supply, and operates at 25 times a second. Maximum discharge height is 65ft and the maximum vertical lift is 10ft. Apart from non-return valves, the only moving part is the metal piston. Internal metal components, which require no lubrication, are made from corrosion resistant materials. The materials used for the moulded seals and valves can be selected to suit the liquid being handled. Appliance Components Ltd, Cordwallis Street, Maidenhead, Berks SL6 7BQ. **WW 301**

I/O ports

Bidirectional, latched input/output ports (interface vector bytes) are announced by the Signetics group of Mullard. The 8-bit ports are intended as interface elements for microprocessors, being compatible with the 8X300 micro. Each i.v. byte contains eight data latches, which can receive data from

either a microprocessor port or a user port, the two modes being under separate control. Priority is given to the user port.

The bytes are programmed by the user or manufacturer to recognize an 8-bit address, which opens the port and allows data through when a 'select' signal is applied. Data transfer is stopped when the address no longer matches the programmed, internal address of the byte. Types 8T32 and 8T36 possess three-state outputs, while the 8T33 and 8T35 bytes are open-collector units. 8T32 and '33 are synchronous, '35 and '36 asynchronous. The voltage supply needed is 5V and the modules are in 24-pin packages. Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD. **WW 302**

Component meter

The Wayne Kerr component meter B424 measures resistance, capacitance and inductance on the bridge principle. The display reads up to 1999, and measurements are given up to 20MΩ, 20mF and 2kH. Resolution on the most sensitive ranges is 10mΩ, 0.1pF and 0.1μH. An analogue output is available to feed ancillary equipment. The instrument has an accuracy of 0.25% (± one digit) on all ranges, and is suitable for battery or mains operation. Selection of R, C or L is by push-button, and range-changing by 9-position rotary switch. Illuminated pointers indicate the most appropriate range, and the display also includes decimal points and units. Operating the range switch automatically selects the most suitable test frequency: 1kHz or 100/120Hz. Two test terminals are normally used, but a third is available if required for screened connections. Bias voltage is provided for polarising electrolytics under test. When inductors with high-permeability cores are being measured the test signal level is held below 100mV. Wilmot Breeden Electronics Ltd, 442 Bath Road, Slough, Berks SL1 6BB. **WW 303**




WW 303

Fluxmeter


The Austrian made Norma Fluxmeter detects voltage time integrals to measure magnetic flux, flux density and mutual induction. The range is from 0.1 to 50mWb in six ranges with a sensitivity of 1μWb and an accuracy of ± 1% of f.s.d. The instrument has an auto-zero facility and a recorder output, with a source resistance of 2kΩ, on which 1V corresponds to f.s.d. The instrument operates either from the mains or rechargeable batteries. Two probes are available, one with a turns × area of 10⁻²m², and the other 6 × 10⁻⁴m². A standard source is also available with a 3.5 × 15.5mm airgap having an induction, say Cropico, of 500 mT⁴, accurate to within 1%. The unit measures 160 × 240 × 310mm and weighs 3.8kg. The price is £964 excluding v.a.t. The search coils and calibrating magnet are extra. Cropico say delivery is around three to four weeks. Cropico Ltd, Hampton Road, Croydon CR9 2RU. **WW 304**

Microwave power meter

The Sanders Division of Marconi Instruments have introduced a programmable, thin film, thermo-electric (t.f.t.) power meter, type 6550B, for power measurement at microwave frequencies. Replacing the type 6550A, the meter has binary-coded decimal, programmable ranging, automatic range and scale selection and auto-zero

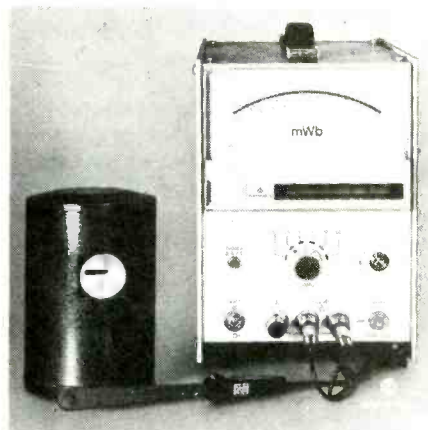

WW 304

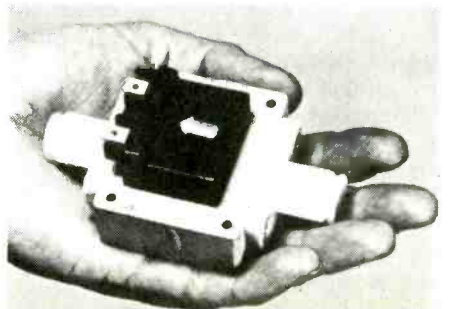

WW 301


facilities. It can be used with a range of t.f.t. power heads covering frequencies between 10MHz and 40GHz with a power range from $1\mu\text{W}$ to 3W. The instrument can be used in automatic test systems, but in its manual modes is also suitable for use as a conventional power meter. The t.f.t. power heads available are compatible with all the power meters in the company's range. Marconi Instruments Ltd — Sanders Division, Gunnels Wood Road, Stevenage, Herts, SG1 2AU.
WW 305

Dual-in-line reed relay

A range of d.i.l. packaged reed relays is now offered by Feme. Single-pole normally-open, double-pole normally-open, and single-pole changeover contact arrangements are available as standard with coil voltage ratings of 5, 6, 12, and 24 volts d.c. Rhodium contacts are used to obtain maximum life at power levels within the ratings of the contacts. Quiller Components Ltd, Cardigan House, Winton, Bournemouth, Dorset, BH9 1AU.
WW 307

Dot matrix printer

A dot matrix serial printer developed by Honeywell Information Systems Italia is controlled by a built-in microprocessor. Its printing head (see photo) has needles operated electromagnetically to a 7×7 or 7×9 dot matrix and operates

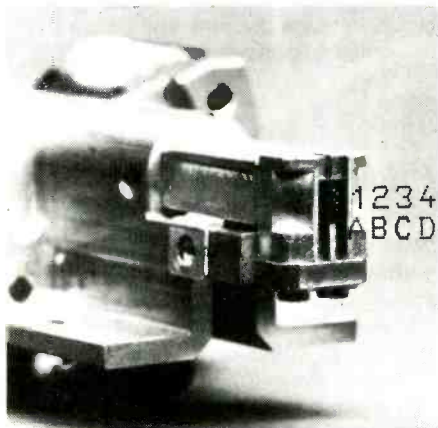

WW 309



WW 307

at speeds up to 120 characters per second. There are 132 print positions and the character set, which can be changed by replacing a character generating read-only memory, comprises 128 symbols. An original and up to four copies can be printed, and options such as front feed or dual paper movement are available. At every print interruption the print head automatically moves a space to the right to make the printed characters visible. The inked ribbon is contained in a removable cartridge. Honeywell Information Systems Italia, Caluso, Turin, Italy.
WW 309

25MHz oscilloscope

A range of measuring facilities usually found on wider-band instruments is provided by Philips on the dual-trace PM3214. The delayed timebase, which can be displayed effectively at the same time as the main sweep and strobe, is calibrated and can be made to start immediately after the delay or on receipt of a trigger after the delay. Sensitivity is 2mV per centimetre from 0 to 25MHz and triggering modes include full-range auto, a.c. or d.c. and television line or frame.

For those occasions when signal "low" cannot be earth, the instrument is double-insulated to enable it to be used without an earth connexion. Batteries may alternatively be used and a variety of mains supply voltages can be accommodated. Pye Unicam Ltd, York Street, Cambridge.
WW 311

Television off-air receiver

A crystal controlled mono-channel, mono-standard receiver for off-air professional television applications has been introduced by Barco. Designated VSD2/X, the receiver is supplied for any channel between 47 and 865MHz, including mid-band channels, and for television standards BG, DK, I, and L. The channel selectivity is sufficiently

high that the receiver can be used in situations where the field strength of the adjacent (disturbing) channel is several times higher than the strength of the chosen channel. Relative indication of the field strength is presented on a front panel meter. N.V. Cobar Barco Electronic, Video Systems Department, Th. Sevensiaan 106, 8500 Kortrijk, Belgium.

WW 306

1000-watt transceiver

The National Radio transceiver type NCX-1000 has a transmitter power output of 1000 watts p.e.p. on s.s.b.; 1000 watts c.w. (normal c.w. duty cycle); and 500 watts a.m. or f.s.k. Its frequency coverage is 3.5 to 30MHz. Output impedance is 25-100 ohms (minimum tuning range of pi network). Carrier and opposite sideband suppression is greater than 40dB, while receiver sensitivity is better than $0.5\mu\text{V}$ for 10dB (s + n)/n ratio. Selectivity is 2.7kHz (a crystal lattice filter is used) and the receiver dynamic range is 105dB. Image and i.f. rejection is better than 60dB. Export Division, EMEC Inc., P.O. Box 1285, Hallandale, Florida 33009, USA.
WW 310

Operational amplifier

The 1435/1435-83 is a differential input operational amplifier designed for amplification of wideband complex waveforms with frequency components from d.c. to 1GHz. Gain accuracy is 0.01%. This is reflected in the settling time specification of 70ns to 0.01% for a 10-volt output step. There is a level frequency response beyond 100kHz and smooth 6 dB/octave roll-off beyond 100MHz. When handling complex waveforms such as square pulses, overshoot is less than 1% of output pulse amplitude. Operating temperature is -55°C to $+125^\circ\text{C}$. Teledyne Philbrick, Heathrow House, Bath Road, Cranford, Middlesex TW5 9QQ.

WW 308



WW 305

Sidebands

by mixer

Bletherization

The on-going initiation of marketing-oriented buzzwords develops in their enunciator an in-built motivation for the generation of enhanced input/output ratios. When it comes to the crunch, marketing is an aggressively-formulated scenario of both software and hardware-oriented data organization, using sophisticated, number-crunching equipment for the on-line analysis of a cash-flow situation. At the end of the day, the viability of any throughput-motivated validation operation must hopefully depend on the dialogue between personnel engaged in hardware generation and those who basically adjust output-level values to maximize financial advantage, in a committed operation. When intelligence communication is contradicted, obscurantization can be generated by sophisticated employment of in-built jargonisation, soonest. Or something.

Update

Some of our readers who have been amateur constructors since capacitance was measured in jars have been baffled by the newer system of component values that are now common. We have explained them before, but we still receive the odd query: if you've been used to dealing with $0.01\mu\text{F}$ capacitors for fifty years, it comes as a shock to find that you should have been calling the wretched things 10n.

Briefly, it goes something like this. The idea developed from a British Standard designed to avoid decimal points and long strings of noughts on components themselves. On circuit diagrams, the nature of the component can also be omitted — a capacitor is obviously measured in fractions of a farad, so the F is redundant. The decimal point is replaced by the multiplier of the unit (k, M, μ , etc) and the full range of noughts needed is two. For example, $0.0033\mu\text{F}$ would be written 3n3, meaning 3.3 nanofarads (nano = 10^{-9}). A resistor of $3,300\Omega$ is 3k3 and an inductor of 0.0048 henries becomes 4m8 (4.8mH). A $0.1\mu\text{F}$ capacitor is 100n, and so on. It's much simpler than the old way and it does avoid decimal points, which can so easily be missed out.

Sounds philological

The sheer labour that engineers go through to bring forth a new device or system fades into insignificance beside the agonies of mind they suffer when they have to think up a name for it. The systems of sound reproduction that use three or more loudspeakers are no exception, in that they have been called everything from quadraphonic to surround-sound, from perisonic to four-channel: and they are just the printable ones. Surely, it's now time to settle down, put away the Latin, Greek and Oxford English dictionaries and come up with a sensible name.

"Quadraphony" is not a good choice. To start with, it's a Graeco-Roman mess, conceived on the wrong side of the blankets, and secondly, the meaning is wrong. It implies a square sound, which is surely not what is intended: a square-sounding punk rock group is not an idea I can easily contemplate. In any case, it should be quadro-, the adjectival form, not quadra-. Or perhaps quadri-, if the number four is intended.

"Surround-sound" has been used rather a lot and has the merit of describing the effect rather than the means of producing it, which could change — it avoids the use of any part of a word meaning "square" or "four". We already have systems, which can use three or six loudspeakers, to which the term quadraphonic is not applicable. My feeling is, though, that the word is too long and is ugly when used adjectivally.

"Ambisonic" is good, but is used almost as a trade-name. For this reason, it is unlikely to be adopted by organizations who have their own nominal axes to grind.

Any reference to the number four is not a good idea, even if it were always the right number. It has most relevance to a system using four completely separate channels, but this can't be used for all types of sound reproduction and can't, therefore, be used in an overall description. My own suggestion is to term the reproduced surrounding sound field the phonosphere and to coin the word "phonospheric" to describe such equipment. I shall now sit back and await retribution for my temerity.

2p or not 2p?

Not that tuppence will get you very far in this inflationary age, but it does seem extraordinary that a plain, ordinary (or even coloured ordinary) resistor can cost up to 5p. It seems possible, since the majority of our readers are employed in the electronics industry, that whenever they are seized with the desire to build an amplifier, a commensurate number of relevant components promptly disappears from their labs (a company I know of used to keep small components for engineers to use as they needed them, without having to sign a stores chit, on the basis that each engineer would probably only build one tele-

vision set and one amplifier and that number of components could be written off).

But that is irrelevant if the prospective builder is not able to liberate components or does not possess the legendary "junk box", beloved of writers of books entitled "The Practical Guide to . . ." So, they are faced with problems of supply and, having located a source, the cost. Time was when you could find a radio shop in any town which sold components, not teak-finished furniture with knobs on, where you could buy everything needed. I remember buying everything I needed for a 12in television set, quite casually, from the local shop. (I won't say how long ago, but Sutton Coldfield and Ally Pally had it all to themselves.)

The only way you can buy stuff now is to send off to a mail order establishment, and very good some of them are, if expensive. I would have thought, and I have no doubt that a great number of component suppliers will put me straight here, that the High Street shops of yore could still perform a very useful function and make a profit doing it. Admittedly, they couldn't stock all the exotic bits and pieces we are now used to, but the ordinary components and materials ought to be no problem. They would be able to buy in bulk from manufacturers who won't deal with the public and, in any case, couldn't handle an order for a few pence. Free of the burden of postage, packing and insurance, they could probably sell components at a lower price, and to boost their sales they could assemble kits of parts for the more popular small designs and sell them both directly and by mail order. Perhaps the new 'byte' shops will do something like that.

Cuckoos

"Nah, well, it's analogue, innit? Wot yer want's a digital readaht." Thus spake a young man of nearly six at the recent RSGB exhibition, as his friend (well turned seven) commented on some frequency-measuring instruments. They caught sight of me and, since it looked as though they might draw me into the discussion, I hurried away before they discovered my relative ignorance of such matters.

But really, haven't these infants more immediately fascinating pursuits to occupy them? Have grass-snakes and guinea-pigs totally disappeared from these islands? Surely not, and yet here were these two, looking as unlike infant prodigies as it is possible to imagine, discussing oscillator stability and instrument design while outside, the toads were toadying and field-mice fielding away like anything.

The sign of a mis-spent youth may no longer be a degree of proficiency at snooker, but deftness with a couple of c.m.o.s. chips and a bit of Veroboard.

Safe, tough, efficient and versatile – that's our new miniature CX iron.

Safe because it is virtually leak-free (leakage current less than 1 μ A). Earth it if you like – three core lead. It is made to conform with B.S. 3456 and has a breakdown voltage of more than 4000V.

Tough because the handle is almost unbreakable and the ceramic shaft is covered by a stainless steel shaft.

Efficient because the element is situated right inside the soldering bit and the heat generated by its 17 watts is not wasted.

Versatile because the iron can be used for a wide variety of soldering jobs; with six easily interchangeable, slide-on bits, ranging from $\frac{1}{4}$ " right down to $\frac{1}{64}$ " (1mm). It's suitable for small, miniature and micro miniature joints.

Available for 220-250 volts or 100-120 volts. Weight – 1 $\frac{1}{2}$ oz (40 gram). Length 7 $\frac{1}{2}$ " (19cm). Price – **£3.40** fitted with standard bit $\frac{3}{32}$ " (2.3mm). Spare bits £0.46; £0.72; £0.84 exclusive of VAT.

Stocked by most of the well-known wholesalers and many retailers. Or direct from us if you are desperate.

Model X.25 is a general purpose soldering iron, also with two shafts for toughness and perfect insulation. Available for 220-250 volts or 100-120 volts at 25 watts and priced at **£3.40** exclusive of VAT.




Stand model S.T.3 has a chromium plated steel spring, two sponges for cleaning the bits and is priced at **£1.40** exclusive of VAT.



Mayflower House, Plymouth
Telephone (0752) 67377/8 *telex* 45296
Giro 2581000

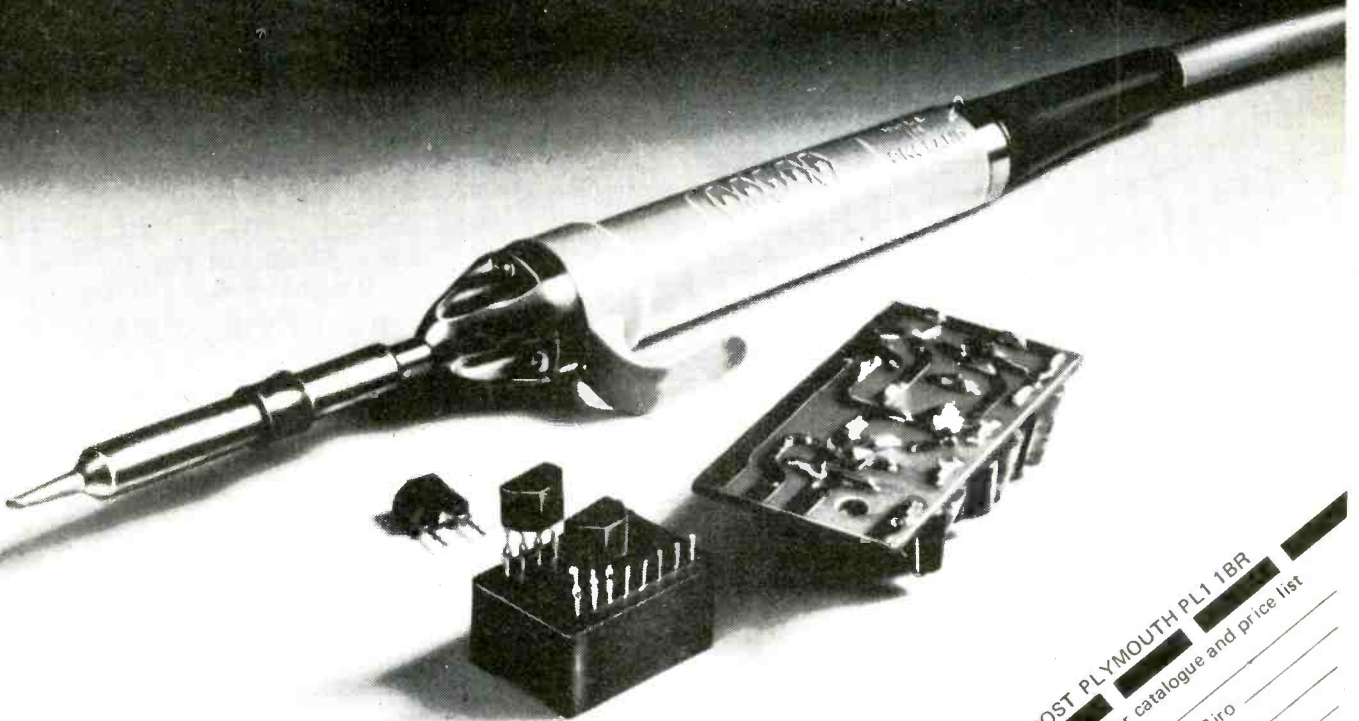Forget all you've ever read about miniaturised soldering irons. This is the NEW ANTEX CX.



to ANTEX LTD. FREEPOST PLYMOUTH PL1 1BR

Please send: Colour catalogue and price list

Plus: I enclose cheque/P.O./Giro

NAME _____

ADDRESS _____


The SC/MP LCDS that is truly a Low Cost Development System

PLUGGABLE
MEMORY CARDS
these are half Eurocard

TTY INTERFACE
for paper tape and
hard copy

DISPLAY
to monitor your progress

KEYBOARD
to enter your program

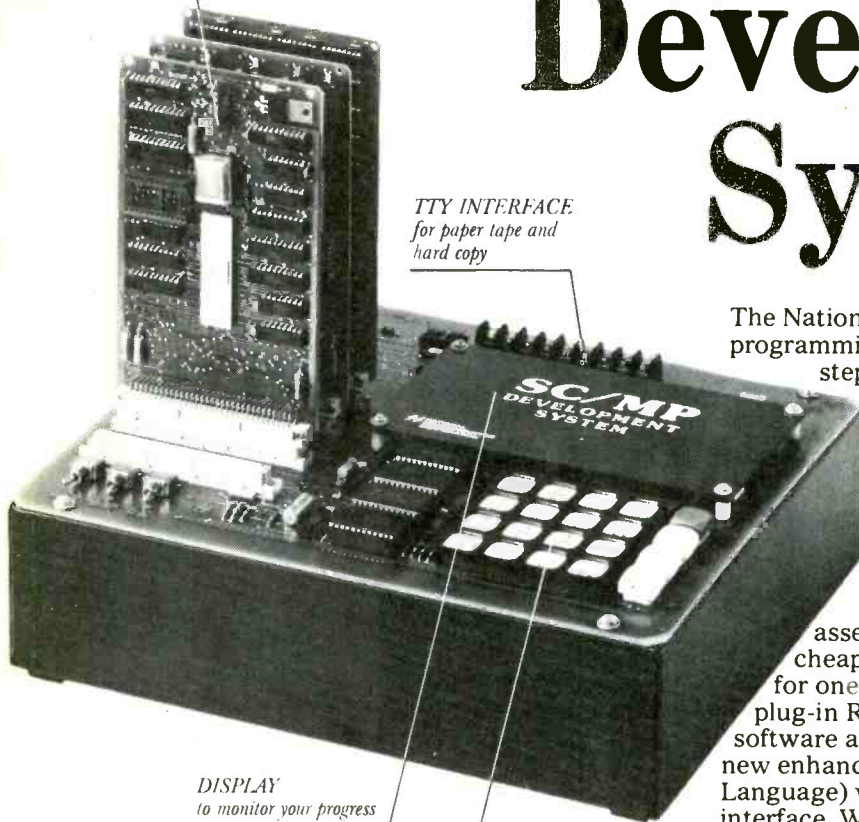

The National Semiconductor LCDS really does make programming simple. You can develop your own program step-by-step to see how it works and if it works.

And with it you can develop the potential of your SC/MP microprocessor.

The simple keyboard and display give you a chance to look at your program as you go—so you can learn programming in your own way. A built-in routine makes software debug so easy.

LCDS is not a kit—it comes fully assembled and tested at less than £350, which is cheaper than the software expert is likely to charge for one program. It is expandable too with additional plug-in RAM, ROM/PROM Eurocards. Available software aids include a Line-by-Line Assembler and a new enhanced language—NIBL (National Industrial BASIC Language) which allows plain English man/machine interface. We make technology work. Every time.

ALSO AVAILABLE THE FAMOUS INTROKIT + KEYBOARD KIT

SC/MP INTROKIT

£68.61 + VAT
p8p 75p

CONTAINS ALL YOU NEED TO GET STARTED ON LOW BUDGET MICROPROCESSOR KIT. EUROCARD + CON. SC/MP CHIP. 512 X 8 PROM. 256 X 8 RAM. VOLTAGE REG. XTAL. TTY INTERFACE. ETC. REQUIRES +5 -12 VOLT SUPPLY. IF YOU DON'T HAVE A TTY, THEN OUR KEYBOARD KIT IS WHAT YOU NEED.

KEYBOARD KIT

£65.84 + VAT
p8p 75p


16 X HEX COMMAND KEYS. ABORT AND GO KEYS. TERMINATE AND MEMORY KEYS. 6 DIGIT HEX DISPLAY. COMPLETE SYSTEM CONTAINS KIT BUG PROM.

AVAILABLE FROM

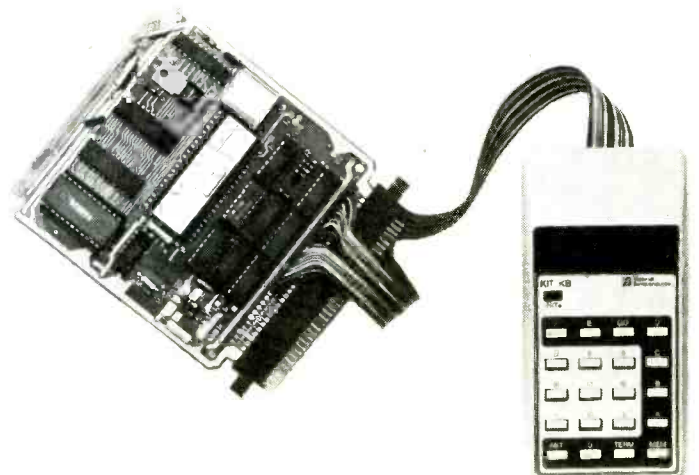A. MARSHALL (LONDON) LTD
42 CRICKLEWOOD BROADWAY
LONDON NW2 3ET
TEL: 01-452 0161 TELEX: 21492

and at 85 West Regent Street, Glasgow (041-332 4133)
1 Straits Parade, Fishponds, Bristol (0272-654201)

Distributors and stockists for all National Semiconductor commercial and consumer devices.



WW063 FOR FURTHER DETAILS

Two books from Wireless World

These books are of very special appeal to all concerned with designing, using and understanding electronic circuits. They comprise information previously included in Wireless World's highly successful

Circards – regularly published cards giving selected and tested circuits, descriptions of circuit operation, component values and ranges, circuit limitations, modifications, performance data and graphs. Each of these magazine-size hard cover books contains ten sets of Circards plus additional circuits and explanatory introduction.

1

circuit designs

Collected Circards

PWilliams/J Carruthers/JHEvans/JKinsler

A WIRELESS WORLD PUBLICATION

BOOK 1

- | | |
|----------------------|---------------------------|
| Basic active filters | Constant-current circuits |
| Switching circuits | Power amplifiers |
| Waveform generators | Astable circuits |
| AC measurements | Optoelectronics |
| Audio circuits | Micropower circuits |

2

circuit designs

Collected Circards

PWilliams J Carruthers JHEvans JKinsler

A WIRELESS WORLD PUBLICATION

BOOK 2

- | | |
|---------------------|------------------------------------|
| Basic logic gates | C d as – signal processing |
| Wideband amplifiers | C d as – signal generation |
| Alarm circuits | C d as – measurement and detection |
| Digital counters | Monostable circuits |
| Pulse modulators | Transistor pairs |

ORDER FORM

To : General Sales Department,
IPC Business Press Limited,
Room 11, Dorset House,
Stamford Street, London SE1 9LU.
Please send me _____ copy/copies of
Circuit Designs – Number 1 at £10.40
Circuit Designs – Number 2 at £12.50
each inclusive. I enclose remittance value £.....
(cheques payable to IPC Business Press Ltd.)

Name (please print)

Address

Company registered in England and a subsidiary of Reed International Limited Registered No. 677128 Regd. office Dorset House, Stamford Street, London SE1 9LU.

MARCONI TEST EQUIPMENT

TF329G circuit magnification meter. £125
TF455E Wave analyser. New. £135
TF801D RF signal generator. £195
TF1101 RC Oscillators. £65
TF995B/2 AM/FM generator. £425
TF1041B V.T. Voltmeter. £65
TF2200 Oscilloscope. £225
TF1100 Sensitivity v/voltmeter. £70
TF1152A/1 RF power meter. £75
TF890A/1 RF test set. £425
TF1417 200mHz frequency counter. £150
TF144H/S signal generator. £325
TF1370 Wide-range RC oscillator. £125
TF2163 UHF attenuator DC-1GHz. £95
TF2500 Af power meter. £135
TF2606 Differential DC voltmeter. £205
TF2604 Electronic voltmeter. £105
TF1066B/1 AM/FM Sig. gen. 10-470MHz
TF791D Deviation Meter

MARCONI TF995B/2. AM/FM GENERATORS.

200kHz-220MHz in 5 bands.
 0.1 μ V-200mV. Continuously variable
 FM in two ranges to 75kHz. Price and
 Full spec. upon request. £425

EVER-READY NICKEL-CADMIUM BATTERIES.

Size 'D' (HP2) 1.25V, 3.5 AH. Only small quantity
 available at £2 + 10p post.

APT POWER SUPPLIES.

Stabilised and regulated. 6V (variable) at 3A.
 Brand new. £25

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.) Counting up to
 15 turn 'Helipot'. Brand new with mounting
 instructions. Only £2.50 each

FRACMO Geared motors. 24V. AC 0.5RPM.
 68A. Torque 40lb. in. Price including starting
 capacitor. £10.50


CENTRIFUGAL TYPE Blowers.

12V DC.
 Outlet diam. 7 cms. Overall diam. 15 cms and
 17 cms deep. Very powerful fans. £9.50

P. F. RALFE ELECTRONICS

10 CHAPEL STREET, LONDON, NW1
 TEL: 01-723 8753

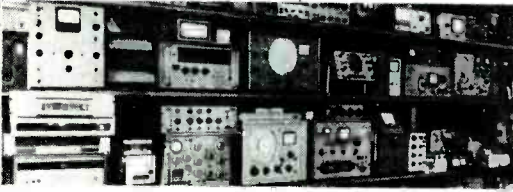NOTICE. All the pre-owned equipment shown has been
 carefully tested in our workshop and reconditioned where
 necessary. It is sold in first class operational condition and most
 items carry our three months' guarantee. Calibration and most
 certificates can be arranged at cost. Overseas enquiries
 welcome. Prices quoted are subject to an additional 8% VAT



HEWLETT PACKARD 432A. Power meter
BRANDENBURG 0-20KV EHT Gen. £105
AIRMEC 210A Modulation meter 3-300mHz
APT504 Power supply. 0-500V at 250mA £35
BPL Capacitance decade (5) CD133. 100pf. 1 uf £45
HEWLETT PACKARD 431C power meter £125
CABLE TEST SET CT491 (to 1/2 mile) £85
FLUKE 891A DC Differential voltmeter.
GERTSCH Frequency meter and deviation meter
 20-1000mHz £250
GR Standard sweep frequency generator. 400kHz-230mHz
 £485
ADVANCE SG63A AM/FM Sig. Gen. £75
BOONTON 230A power amplifier RF £325
MUIRHEAD PAMETRA Wave Analyser.
MUIRHEAD K134A Wave Analyser. Battery op
HEWLETT PACKARD 693D sweep oscillator £350
MEDISTOR type A-75A Potentiometric
 microvoltmeter £115
PYE EHT scalamp voltmeter 0-40KV £125
RACAL 1 2mHz counter timer, 6 Digits. SA535B £85
RADIOMETER Wave analyser type FRA2B
 0-16kHz £160
SCHNEIDER type cf52 100mHz frequency
 counter £235
SCHOMANDL Frequency meter type FD1 £125
SOLARTRON Pulse generator type G01101.2 £65
TEKTRONIX type 575 Transistor curve tracer
TEKTRONIX 585A oscilloscope with 82" P.I. DC-80mHz
TEKTRONIX type 526. Vectorscope £580
TEKTRONIX type 180A Time mark generator £110

ROHDE & SCHWARZ EQUIPMENT

Midget crystal clock type XSZ. BN 15221.
 Selective UHF v/meter, bands 4&5. USVF.
 Selectomat. RF Voltmeter. USWV.
 BN 15221. £450
 Standard attenuator 0-100db. 0-300mHz.
 DPR
 UHF Sig. Gen. type SDR 0.3-1 GHz.
 £750
 UHF Signal generator type SCH. £175
 UHF Test receiver type USVD. £325
 POLYSKOP SWOB I.
 POLYSKOP SWOB II.
 SBTF. T.V. Signal generator, vision-sound
 modulator and transmitter.

ICL type 2640 Paper tape readers 250cps.
 New £95
 Westrex 8-hole paper-tape punches £95
 Sound-proof case available £15

MUFFIN INSTRUMENT COOLING FANS

Made by Rotron Holland. These are very high quality, quiet
 running fans, specially designed for the cooling of all types
 of electronic equipment. Measures 4.5x4.5x1.5
 115V AC. 11 Watts. The list price of these is over £10 each.
 We have a quantity available brand new for only £4.50
 each

500V TRANSISTORISED INSULATION TESTER

Lightweight, small size (13x7x4cms). Reads insulation
 from 0.2-100M Ω at 500V pressure. Runs from
 standard 9V PP3. Brand new £16.50

ADVANCE Transistorised Inverter.

24V DC-240V AC. 50 Hz. 150W. £75
PACE ELECTRONICS VARI PLOTTER
 Type 1100E £175

MUIRHEAD DECADE OSCILLATORS

type 890A.
 1Hz-110kHz in four decade ranges.
 Scope monitored output for high
 accuracy of frequency. Excellent
 generator. £135.

TRAMPUS

A SEMICONDUCTOR POWERHOUSE (Trade & Export Welcome)
TRAMPUS ELECTRONICS LTD., 58-60 GROVE ROAD, WINDSOR, BERKS, SL4 1HS
 Tel: Windsor (07535) 54525 - Callers welcome Mon.-Sat. 9 a.m.-5 p.m.

Fast service. Same-day despatch on ex stock product. Quality devices,
 all full spec. Same Trampus low prices. Barclaycard and Access by post
 or telephone. £5 minimum. VAT: Add 8% to prices marked *. Add
 12 1/2% VAT to all other prices. Post and packing 20p UK. Send CWO
 except Government Dep'ts., etc. Free catalogue list with Sale Bargains
 and Micro Processors (Send SAE).

IC's	All price each	TRANSISTORS	TTL	CMOS
555 DIL 8 PIN TIMER	33p	AD161 162 ea.	7400	4001/2 23p
723 TO99 REGULATOR	49p	BC107	7401	18p 4009 10 55p
723 DIL 14 PIN REG	69p	BC107B	7402	18p 4011 20p
741 DIL 8 PIN OP AMP	28p	BC108	7404	20p 4D13/16 60p
741 DIL 14 OR TO99	39p	BC108 B OR C	7410	20p 4017/20
747 DUAL 741	89p	BC109	7413	39p 4024 88p
748 DIL 14 PIN	33p	BC109 B OR C	7420/30	29p 4028 100p
748 DIL 8 PIN	49p	BC147/8/9	7440	20p 4029 125p
7805 TO3 5V REGULATOR	£1.00	BC167/8/9	7441/141	79p 4030 60p
7805 PLASTIC 5V Reg.	£1.35*	BC177/8/9	7447	84p 4046/47
7812 OR 7815	£1.50	BC182/3/4 A OR L	7470/72	29p 4040 £1.10
78013 OR 78023 AF	£1.89	BC212/3/4 A OR L	7473/74	35p 4049 89 22p
8038 SIGNAL GENERATOR	£5.00	BCY70/71/72	7475	60p 4067 £3.80
LM300	£1.00	BD131 OR 132 ea.	7476	39p 4510 £1.40
LM301 DIL 14 PIN OPA	39p	BFY50 OR 51	7490	49p 4511 £1.72
LM301 DIL 8 PIN	59p	MJ2955 (PNP3055)	7491/92	75p 4528 £1.58
LM309K TO3 5V REG	£1.00	MJE2955	74121	33p 4553 £5.00
LM318 70V OS OPA	£2.25	MJE3055	74123	46p CMOS DATA
LM35CN 2W AF 12V	£1.00	ORP12	74196	£1.27
LM387 2 X PRE AMP	£2.00	TIP 41 OR 42A		BOOK £3.50
LM3900 QUAD OP AMP	75p	TIP2955		
NE536 FET OPA	£4.00	TIP3055		
NE555 TIMER	39p	TIS43		
NE556 2 X 555 TIMER	£1.00	ZX107/8/9		
5N766 11 & 60 IF	£1.25	2N2646		
TBA 810 7W AF	£1.00	2N2904/5		
		2N2926 RB		
		2N2928 YG		
		2N3053		
		2N3055		
		2N3702/3/56		
		2N3704		
		2N3819E FET		
		2N3820 FET		
		2N3904/5/6		
		2N4557 FET		
		2N5777 OPTO		
		SILICON GREASE		
		MINI SATCHET		
		INS. BUSH SETS		
		MATCHING		

LEDs 1/8" & 2" DIA.
 RED NO CLIP 12p
 TIL209 & CLIP 15p
 2" RED & CLIP 17p
 COLOURLED LEDs 29p

DISPLAYS (RED LED)
 0.3" DL704/0L707 £1.00
 0.6" DL747 JUMBO £1.69
 DALO PCB PEN 2 TIPS 74p
 DECON. DESOLDER BRAID
 REEL 74p
 SRBP 6" x 4" 60p. FEC TUBE £1.00

MPU & BARGAIN PAKS IN
 LISTS

NEW COMPONENTS

Resistors. 5% carbon E12 2.7 Ω to 10M
 1/4W 1p. 1W 2p. Preset pots. Subminiature
 0.1W e3 100 Ω to 4M7 vertical 9p.
 Horizontal 9p. Potentiometers 0.25W E3
 4K7 to 2M2 log or 1in. single 24p, dual
 75p. Polystyrene capacitors E12 63V
 22pf to 8200pf 3 1/2p. Ceramic capaci-
 tors vert 50V E6 22pf to 4700 3p. Mylar
 capacitors 100V vert 001, 002, 005
 4p, 01, 02, 025 4 1/2p. Polyester
 capacitors 250V E6 vert 01 to 1mf
 5 1/2p, 15, 22 7p, 47mf 11p. Electroly-
 tics 50V 47, 1, 2mf 5p, 25V 5, 10mf 5p,
 16V 22, 47mf 6p, 100mf 7p, 220 mf 9p,
 470mf 11p, 1000mf 18p. Zener diodes
 400mW E24 3V3 to 33V 8 1/2p.

MAINS TRANSFORMERS

6-0-6V 100mA 94p. 9-0-9V 75mA 94p.
 12-0-12V 50mA 94p.
 0/12/15/20/24/30V 1A £3.65.
 0/12/15/20/24/30V 2A £4.95.
 18V 1A £1.95. 6-0-6V 1 1/2A £2.55.
 9-0-9V 1A £2.19. 12-0-12V 1A £2.49.
 15-0-15V 1A £2.69. 30-0-30V 1A £3.39.

PRINTED CIRCUIT KITS, ETC.*

Contains etching dish, 100 sq. ins. of pc
 board, 1 lb. ferric chloride, etch resist pen,
 drill bit and laminate cutter. £3.65.
 1 lb. ferric chloride 95p. 100 sq. ins. pc
 board 75p. Etch resist pen 75p.

S-DECS AND T-DECS*

S-DeC £1.94
 T-DeC £3.61
 u-DeC £3.97
 u-DeC £6.97
 16 diff IC carriers £1.91

SINCLAIR PROJECT 80 MODULES

P25 £4.95. 240 £5.75.

BI-PAK AUDIO MODULES

S450 tuner £20.95. AL60 £4.60. PA100
 £14.95. MK60 audio kit £31.95. Stereo
 30 £15.50. SPM80 £3.65. BMT80
 £3.32.

FERRANTI ZN414

IC radio chip £1.44. Extra parts and pcb for
 radio £3.85. Case. £1. SAE for data

TV GAMES CHIP

AY-3-8500 £11.50. Printed circuit and kit
 of extra parts £7.95. Add-on colour kit
 P.O.A. Send see for data.

BATTERY ELIMINATOR BARGAINS

3-WAY MODELS

With 4-way multi-jack connector Type 1
 3/4 1/2/6V at 100mA £2.30. Type 2
 6/7 1/2/9V 300mA £2.90.

100MA RADIO MODELS

With press-stud connectors. 9V £3.45. 6V
 £3.45. 9+9V £5.45. 4 1/2+4 1/2V £5.45.
 6+6V £5.45.

150MA CASSETTE MODELS

7 1/2V with 5-pin din plug £3.65.
FULLY STABILIZED MODEL
 £5.45. Switched 3/6/7 1/2/9V 400mA.

BATTERY ELIMINATOR KITS

100mA radio types with press stud battery
 terminals. 4 1/2V £2.10. 6V £2.10. 9V
 £2.10. 4 1/2V+4 1/2V £2.50. 6V+6V
 £2.50. 9V+9V £2.50.
Stabilized 8-way types transistor stabili-
 zed to give 1 low hum
 3/4 1/2/6/7 1/2/9/12/15/18V 100mA
 model £3.20. 1 Amp model £6.50.
Heavy duty 13-way types
 4 1/2/6/7 1/2/8 1/2/11/13/14/17/21/25/28V
 1A £4.95. 2A £7.95.
Car Converter Kit. Input 12V DC. Output
 6/7 1/2/9V 1A regulated £1.95. 2 Amp
 £14.95.

SINCLAIR IC20

IC20 10W+10W stereo amp kit with
 printed circuit £4.95. P220 power supply
 for above £3.65. VP20 control and preamp
 kit £8.95. Send see for data.

JC12 AND JC40 AMPLIFIERS

JC12 6W IC au-
 dio amp with data
 and printed circuit
 £1.95. Also new
 JC40 20W model
 with pcb £3.95.
 Send s a e for free leaflet

SINCLAIR MICROWONDERS

Sinclair pocket TV £165. Cambridge
 scientific calculator £8.45. Oxford
 scientific £10.60.

SWANLEY ELECTRONICS

DEPT. WW, PO BOX 68, 32 GOLDSSEL ROAD, SWANLEY, KENT BR8 8TQ

Mail Order only. No callers. Send s a e for free data on kits. Post 30p on orders under
 £4.50, otherwise free. Prices include VAT. Official orders welcome. Overseas customers
 deduct 7% VAT on items marked * and 11% on others.

DIY SPEAKER KITS

15-WATT KIT IN CHASSIS FORM

When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the enclosures illustrated below. Size 13" x 8" (approx.) woofer (EMI), tweeter, and matching crossover components. Power handling capacity 15 watts rms. 30 watts peak.



£17.00 PER STEREO PAIR
+ P & P £3.40

EASY-TO-BUILD WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-

simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms. 30 watts peak, each unit. Cabinet size 20" x 11" x 9 1/2" (approx.).

£25.50

PER STEREO PAIR
+ p & p £5.50

COMPACT FOR TOP VALUE

How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £7.50 - just what you need for low power amplifiers. These infinite baffle enclosures come to you ready mired and professionally finished. Each cabinet measures 12" x 9" x 5" (approx.) deep, and is in wood simulate. Complete with two 8" (approx.) speakers for max. power handling of 7 watts.



per stereo pair
£7.50
+ p & p £1.70

SPEAKERS Two models - Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/2" (approx.).


★£34 PER PAIR
+ p & p £6.50

Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" (approx.)

★£52 PER PAIR
+ p & p £7.50

EASY TO BUILD RECORD PLAYER KIT

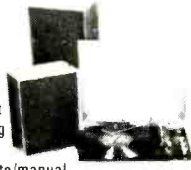Ideally suited for the constructor who requires a complete stereo unit at a budget price, comprising ready assembled stereo amp, module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phones socket and record/replay socket



£26.95

+ p & p £4.05

CAR RADIO KIT

Complete with speaker, baffle and fixing strip. The Tourist IV for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs are used for manual tuning and volume control. The modern style fascia has been designed to blend with most car interiors and the finished radio will slot into a standard car radio aperture.

MOTOR TOP 10 AWARD

Power Supply Nominal 12 volts


positive or negative earth (altered internally) Power Output 4 watts into 4 ohms.

£12.50
+ p & p £1.50

PERSONAL SHOPPERS ONLY

Viscount IV 20 x 20 Amplifier as illustrated, plus 1 pair of speakers finished in teak with melamine panels 8" drive unit and 3 1/2" approx tweeter. 22" x 13" x 10 1/2" size approx.

£45.00
SPECIAL OFFER

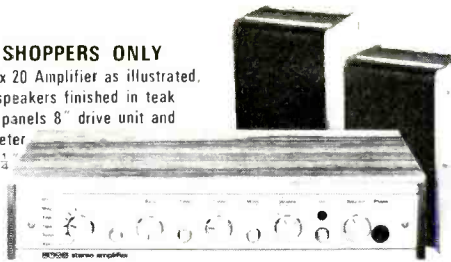

illustrated above 20 x 20 WATT STEREO AMPLIFIER

Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary. Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20 x 20 watts rms, 40 x 40 watts peak.

★ £29.90
+ p & p £2.10

SPECIAL OFFERS

For example Duo speaker system II or III, Viscount Amplifier, MP60 type turntable complete

DEDUCT 10% DEDUCT 15%

Mailorder only (not on postage) Personal Shoppers only
★ on complete stereo systems using starred Products

PERSONAL SHOPPERS ONLY

DECCA DC1000 Stereo cassette, ready built tape deck, replay/record P.C.B. with pair record/replay heads **£3.95**

AM. FM. TUNER P.C.B. with Mullard L.P. 1186, 1185, 1181 modules **£9.50**

CROWN 5 push button car radio, LW, MW, 12v Pos. neg. earth 5 watts output, tone control complete with speaker and fixing kit, in dash type **£15.95**

STEREO CASSETTE TAPE PLAYER Negative earth only, 3 watts per channel output **£16.50**


AM. FM. STEREO MULTIPLEX CAR RADIO/cassette player in dash fixing Negative earth 5 watts output **£39.00**

SONIX 'TROOPER' Boys Military style maifs, battery radio only **£6.95**

VISCOUNT COMBI

£65.00

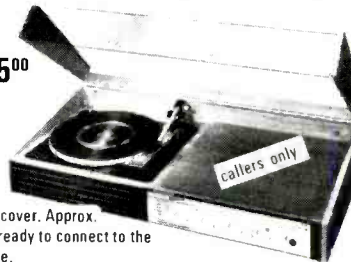For personal shoppers only, this unit comprises: The 20 x 20 Viscount amplifier BSR MP60 Type turntable housed in an attractive teak finished console with smoked acrylic cover. Approx. 30 1/2" x 14 1/2" x 7 1/2" complete ready to connect to the speaker system of your choice.



BSR TURNTABLES

BSR MP60 TYPE Single play record player (Chassis form) **£15.95** less cartridge. P & P £2.00

Cartridges to suit above ACOS MAGNETIC STEREO **£4.95** CERAMIC STEREO **£1.95**

BSR automatic record player deck (Chassis form) with cueing device and stereo ceramic head. **£9.95** P & P £2.00



TURNTABLE illus. Popular BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover. Ready wired **★ £29** + p & p £4.50

30 x 30 WATT AMPLIFIER KIT

Specially designed by RT-VC for the experienced constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched, drilled and formed. Cabinet is finished in teak veneer. Silver fascia and easy-to-handle aluminium knobs.



Output 30 x 30 watts rms. 60 x 60 peak. **£29.00** + p & p £2.10

DECCA 20 WATTS STEREO SPEAKER

This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3 1/2" diameter approx. domed tweeters comp with crossover networks **£20.00**

£4.00 p & p stereo pair

PYE STEREO GRAM CHASSIS

(Complete with circuit diagrams) Complete ready to install - Wave bands LM, VHF STEREO, VHF MONO. Controls for tuning volume, balance, bass and treble. Power output 7 watts R.M.S. per channel 14 watts peak 8 ohms. 22" x 8" approx chassis speakers and BSR auto record player deck. **£35.00** PERSONAL SHOPPERS ONLY

Order giving your credit card number ONLY

ALL PRICES INC. VAT. AT 12 1/2% FOODS NOT DISPATCHED OUTSIDE UK All items subject to availability. Prices valid at 1st June and subject to change without notice. We are unable to show all our products, so please send stamped addressed envelope for our fully descriptive catalogue and any further information.



323 EDGWARE ROAD, LONDON W2 Personal Shoppers EDGWARE ROAD 9am - 5.50pm. Half day Thurs. 21E HIGH STREET, ACTON, LONDON W3 6NG ACTON: Mail Order only No callers

PORTABLE MONO DISCO CONSOLE



with built-in pre-amplifiers Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simply connects into your existing slave or external amplifier. **£64.00**

35-WATT MONO DISCO AMP

£27.50
+ p & p £2.50

Size approx. 13 1/2" x 5 1/2" x 6 1/2"

Here's the mono unit you need to start off with. Gives you a good solid 35 watts rms, 70 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"

Sloping fascia, you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth acting, vertically-mounted slide controls - master volume, tape level, mic level, deck level, PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. p & p £4.00



PRACTICE GUITAR AMPLIFIER WITH BUILT-IN SPEAKER

This budget practice amplifier, has been specially designed for the amateur, who requires a quality self-contained unit with all facilities. 2 inputs - 1 for mic or guitar, the 2nd for record player or cassette deck, it also can be used for cine-sound amplification. 2 volume controls, 1 for each input, also base and treble controls. Power output with internal speaker, 12 watts RMS, with remote speaker (not supplied) 20 watts RMS. Size approx. 17" x 9" x 11". **£32.50** + p & p £3.00




HOME 8 TRACK CARTRIDGE PLAYER

Automatically switches programmes monitored by indicators, with manual override track selection. This unit will match with the Unisound modules and is compatible with the Viscount IV amplifier with Sim teak cabinet, approx. 9" x 8" x 3 1/2". **£14.60**



4 x 4 STEREO AMP KIT

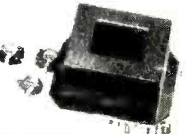For the experienced constructor who wants to design his own stereo. Kit includes all necessary components including constructors manual. Plus Pair of easy to build 4 watt speakers in kit form, with teak simulate finish cabinets 12" x 9" x 5" approx.



NEW sinclair

FANTASTIC SAVING. I.C. 20, 20 WATTS STEREO AMPLIFIER KIT WITH PZ 20 POWER UNIT

A build-it-yourself stereo power amplifier with latest integrated circuitry. 10W RMS per channel output, full short-circuit and overheat protection. Complete with PZ20 Power Supply **£5.95** + p & p £1.10 LIST £14.50



WH WEST HYDE

Instrument cases

WEST HYDE

WH



Offer instrument manufacturers low-cost cases ex-stock. Blue PVC coated steel strength and rigidity. PVC aluminium grey front and rear panels are removable. PCB and PSU mounting system available. Also available in black. 301 price of 302, Bk 302 303, Bk 304 305




A range of eyebrow cases in blue textured acrylic. Front panels normally white zintec or PVC/aluminium, also available unpainted up to 1277 size. Aluminium panels 20p extra 1st size, 22p extra next 4 sizes.

All dimensions are WidthxHeightxDepth

PRICES	1 off inc.	P & P but not VAT
MOD-3 (including chassis)		
301 7x3 x5 1/2"	6.33	
302 7x4 x5 1/2"	6.79	
303 7x6 x5 1/2"	6.66	
304 11x3 x5 1/2"	7.79	
305 11x4 x5 1/2"	9.19	
306 11x6 x5 1/2"	10.99	
CONTIL TEXTURED		
755 7x5x5"	8.32	
867 8x7x6"	9.88	
975 9x5x7"	9.88	
1277 12x7x7"	11.38	
1277 unpainted	8.46	
16127 16x7x12"	15.69	
191010 19x10x10"	21.57	
ELF CASES Grey (inc chassis)		
Elf 6x4x4"	3.20	
Bare Elf (less ft, ch, pnl)	2.15	
Giant Elf 8x5 1/2 x5"	4.50	
Long Elf 9x4x3"	3.60	
Jumbo Elf 10 1/4 x5 1/2 x5 1/4"	5.40	
MOD-2 CASES (including chassis)		
A 4.5x 3x 6.5"	8.62	
B 4.5x 7x 6.5"	9.24	
C 4.5x10x 6.5"	10.80	
D 9 x 3x 6.5"	9.26	
E 9 x 7x 6.5"	10.38	
F 9 x10x 6.5"	12.19	
G 13 x 3x 6.5"	10.25	
H 13 x 7x 6.5"	11.77	
I 13 x10x 6.5"	13.82	
J 18 x 3x 6.5"	13.16	
K 18 x 7x 6.5"	15.40	
L 18 x10x 6.5"	19.05	
M 4.5x 3x13"	10.16	
N 4.5x 7x13"	10.93	
O 4.5x10x13"	12.89	
P 9 x 3x13"	10.82	
Q 9 x 7x13"	12.36	
R 9 x10x13"	14.52	
S 13 x 3x13"	12.65	
T 13 x 7x13"	14.54	
U 13 x10x13"	17.07	
V 18 x 3x13"	15.97	
W 18 x 7x13"	18.70	
X 18 x10x13"	22.95	



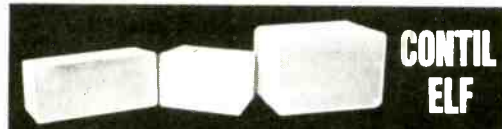Mod-2 cases over 24 sizes. Front and back panels grey PVC. Aluminium chassis included. Packed flat. Outer casing blue PVC steel or up to size L also available in Wood-grain and black. (Price as for next price higher i.e. A Black is B price)



These tough little cases add very little to the cost of a job. Front panel aluminium with protective coat. Elf cases are available in 4 sizes, all dough-moulded in grey glass polyester, all panels, feet and chassis included.

All West Hyde cases are available with substantial discounts for quantities. Most cases have discounts at 5 off and 25 off with discounts up to 25% at 100 off. Prices include P & P and are less 10% if collected, on first three price breaks on cases only.


BUY A CASE FROM A SMALL RANGE, YOU GET A CASE—BUY A CASE FROM A BIG RANGE, YOU GET A SOLUTION



A prestige anodised case, black PVC steel top and bottom which can be supplied foured at no extra cost. Free standing or rack mounting, available in rack or half-width assembled in special polystyrene pack for safe postage.

Instrument cases

BRIGHTCASE MARK II		
BC212 (3 1/2" Full Rack)	21.91	
BC222 (3 1/2" Half Rack)	15.84	
BC312 (5 1/2" Full Rack)	24.04	
BC322 (5 1/2" Half Rack)	17.72	
Rack Brackets available		
No extra for Louvers add L		
MINOS		
M2 65x100x50mm	.70	
M3 100x130x50mm	.89	
M2 Bare	.46	
M3 Bare	.53	
SAMOS		
S1 100x 50x50mm	1.36	
S2 100x100x50mm	1.56	
S3 100x150x50mm	1.74	
S4 125x 50x75mm	1.96	
S5 125x100x75mm	2.24	
S6 125x150x75mm	2.63	
S7 125x200x75mm	2.92	
HEAVY DUTY CASE		
8x 8x5"	14.89	
10x10x7"	16.54	
12x10x7"	20.95	

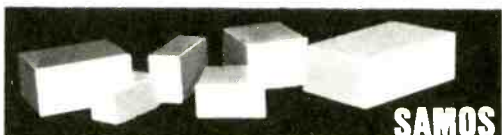

Miniature instrument cases in blue and white PVC steel. Assemble in the lower half, clip-in feet, 2 screws allow the cover to hinge off cases, 2 more to fix. PC feet are available to hold up to 4 PC boards horizontally in case.



Smart miniature ABS cases in tough rigid high gloss black. Front panels either ali or PVC steel. Built-in slots for PC cards, dividers etc. Chassis or PC boards can be supported on "P" clips from internal pillars.

OVER 400 DIFFERENT CASES IN STOCK—SIZE RANGE OVER 5000:1 IN VOLUME
Prices correct June, 1977



Available in 3 sizes. Heavily constructed in zintec steel, welded corners with heavy hinges. 2 screw fixings and foam around the door. In the base is a gland plate with gasket and a chassis with screws provided.

THE INSTRUMENT

Send for catalogue
WEST HYDE DEVELOPMENTS LIMITED
Ryefield Cres., Northwood Hills, Northwood, Middx., HA6 1NN
Telephone: Northwood 24941/26732/27051
Telex: 823231 West Hyde Nthwd.

CASE SPECIALISTS

SPECIAL OFFER
FREE CASIO FX-110 SCIENTIFIC CALCULATOR

with every CASIOTRON watch, listed below, purchased before 1st Sept., 1977. Other calculators by arrangement, or a further £10 discount in lieu.



CASIOTRON. Arguably the best watch in the world. 8 functions and backlight. Stopwatch (time out facility) to 13 hours. Dual time zones. Water resistant to 4 atmospheres (130 feet). All stainless steel case and bracelet. Mineral glass face. Battery hatch. 15 months' battery life. Rapid adjustment/setting facility. Illustrated (left) is the S15B. GS 15 B Heavy G.P. on bracelet. GS 15 L Heavy G.P. on strap.

Illustrated (right) is the R18B
PRICES: (without calculator deduct £10).
R18B (RRP £64.95) **£59.95**
S15B (RRP £89.95) **£79.95**
GS15B (RRP £129.95) **£109.95**
GS15L (RRP £109.95) **£94.95**
S17B (RRP £99.95) **£89.95**
S14B (X-1) (RRP £129.95) **£109.95**
Other Casiotron watches from **£39.95**




Brilliant new FX-110 from Casio (RRP £22.95) **£17.95**. 3B scientific functions including DECIBEL CONVERSIONS and standard deviations. Brilliant 10 digit display in a 6 x 3 3/8 x 1/2 inch package. Economical 3-way power source system (AC battery or rechargeable). A.C. adaptor/charger **£3**. Rechargeable batteries (pair) **£3**. FX-2000 LCD 1000 hour battery life. 36 scientific functions **£24.95**. Programmables: FX-201P **£49.95**, FX-202P **£69.95**. Pro. FX-1 Magnetic card programming **£124.95**. Texas SR52. **£194.50**. Sinclair Cambridge Programmable **£16.95**. Send 15p for our Illustrated Catalogue. Over 50 electronic watches from **£11.95**.

Prices include VAT, P&P. Access. Barclaycard welcome or send cheque, P.O. to—

TEMPUS Dept. W.W.
19/21 Fitzroy Street
Cambridge CB1 1EH
Telephone (0223) 312866

WW — 080 FOR FURTHER DETAILS

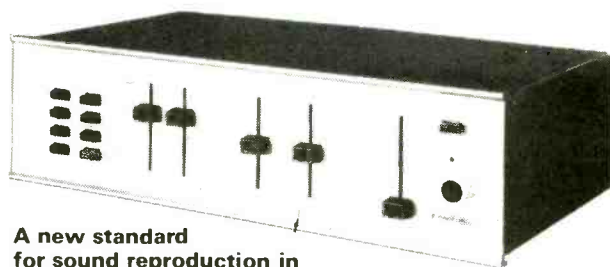RADFORD HD250
High Definition Stereo Amplifier



A new standard for sound reproduction in the home! We believe that no other amplifier in the world can match the overall specification of the HD250.

Rated power output: 50 watts av. continuous per channel into any impedance from 4 to 8 ohms, both channels driven.

Maximum power output: 90 watts av. per channel into 5 ohms.

Distortion, preamplifier: Virtually zero (cannot be identified or measured as it is below inherent circuit noise.)

Distortion, power amplifier: Typically 0.006% at 25 watts, less than 0.02% at rated output (Typically 0.01% at 1 KHz)

Hum and noise: Disc.—83dBV measured flat with noise band width 23 KHz (ref 5mV); —88dBV "A" weighted (ref. 5mV)

Line —85 dBV measured flat (ref 100v)
—88 dBV "A" weighted (ref 100v)

Hear the HD250 at

SWIFT OF WILMSLOW
Dept. WW, 5 Swan Street, Wilmslow, Cheshire
(Tel: 26213)

Mail Order and Personal Export enquiries: Wilmslow Audio, Swan Works, Bank Square, Wilmslow (Tel. 29599)

Now available ZD100 power amplifier and ZD22 pre-amplifier

WW — 089 FOR FURTHER DETAILS

BY POPULAR REQUEST

Demand for reprints of Wireless World constructional projects for audio equipment is so high that we have gathered 25 of the best of them together in High Fidelity Designs. These are the 'most requested' articles which **you** have asked for and all have been fully updated. Hurry for your copy — it's likely to sell out fast!

High fidelity designs

Tape / disc / radio / amplifiers / speakers / headphones

A BOOK FROM WIRELESS WORLD

£2.50 from newsagents and bookshops or £2.75 by post from the publishers

Contents: ● FM tuner design ● Novel stereo FM tuner ● Low-noise, low-cost cassette deck ● Wireless World Dolby noise reducer ● Wideband compander design ● High-quality compressor/limiter ● An automatic noise-limiter ● Modular integrated circuit audio mixer ● The "walltenna" ● Electronic piano design ● Advanced preamplifier design ● High quality tone control ● Multi-channel tone control ● Bailey-Burrows preamplifier ● 30-watt high fidelity amplifier ● 30-watt amplifier modification ● Baxandall tone control revisited ● Active crossover networks ● Electrostatic headphone amplifier ● Class A power amplifier ● An I.C. peak programme meter ● Horn loudspeaker design ● Horn loudspeaker ● Transmission-line loudspeaker enclosure ● Commercial quadrophonic systems

To: General Sales Department, Room 11, Dorset House
Stamford Street, London SE1 9LU

Please send me copy/copies of
High Fidelity Designs at £2.75 each inclusive.

I enclose remittance value £
(cheques payable to IPC Business Press Ltd.)

NAME
(please print)

ADDRESS

Company registered in England No. 677128
Regd. office Dorset House, Stamford Street, London SE1 9LU

PAKS - PARTS - AUDIO MODULES

PANEL METERS

4" RANGE
 Size 4 1/4" x 3 3/4" x 1 3/4"
 Value No Price
 0-50UA 1302 **£4.50**
 0-100UA 1303 **£4.50**
 0-500UA 1304 **£4.50**
 0-1MA 1305 **£6.00**
 0-50V 1306 **£6.00**

2" RANGE
 Size 2 3/8" x 1 3/4" x 1 1/2"
 Value No Price
 0-50UA 1307 **£3.50**
 0-100UA 1308 **£3.50**
 0-500UA 1309 **£3.50**
 0-1MA 1310 **£3.50**
 0-50V 1311 **£3.50**

MR2P TYPE
 Size 42x42x30mm
 Value No Price
 0-50UA 1313 **£4.80**
 0-1MA 1315 **£3.20**

EDGEWISE
 Size 3 1/2" x 1 3/4" x 2 1/4"
 Cut out 2 3/4" x 1 1/4"
 Value No Price
 0-1MA 1316 **£4.05**
 0-500UA 1317 **£4.05**

MINIATURE BALANCE/TUNING METER
 Size 23x22x26mm
 Sensitivity 100/0/100MA
 No 1318
 Price **£1.95**

BALANCE/TUNING
 Size 45x22x34mm
 Sensitivity 100/0/100UA
 No 1319
 Price **£2.00**

MIN. LEVEL METER
 Size 23x22x26mm
 Sensitivity 200UA
 No 1320
 Price **£1.95**

Vu METER
 Size 40x40x29mm
 Sensitivity 130UA
 No 1321
 Price **£2.00**

MINI-MULTI-METER
 Size 60x24x90mm
 Sensitivity 1000 ohms/V
 AC VOLTS 0-10, 50, 250, 1000
 DC VOLTS 0-10, 50, 250, 1000
 DC CURRENT 0.1-100mA
 Resistance 0-150K ohms
 No 1322
 Price **£5.95**

HIGH SENSITIVITY TEST METER
 Sensitivity 50 000 ohms/V
 Size 6 1/2" x 4 1/2" x 2 1/2"
 AC Volts 0-1.5 to 0/500 in 10 Ranges
 DC Volts 0-0.5 to 0/500 in 12 Ranges
 DC Current 0.25 up to 0/10A in 10 Ranges
 Resistance 0-100 ohms to 0/16 meg in 4 Ranges
 BA155 -20 to 62dB in 10 Ranges
 No 1324
 Price **£19.75**

P&P
 Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.

TRANSISTORS BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC126	£0.16	BC107	£0.08	BC550	£0.14	BFY52	£0.14	TIP2955	£0.95	2N3708	£0.07
AC128	£0.12	BC148	£0.09	BC556	£0.12	BIP19	£0.38	TIP3055	£0.75	2N3708A	£0.07
AC128K	£0.26	BC149	£0.09	BC557	£0.14	BP120	£0.38	TIS343	£0.22	2N3709	£0.07
AC132	£0.15	BC157	£0.12	BC559	£0.14	20 MP	£0.80	UT46	£0.18	2N3710	£0.07
AC134	£0.15	BC158	£0.12	BD115	£0.50	BRV39	£0.45	ZTX107	£0.10	2N3819	£0.20
AC137	£0.15	BC159	£0.12	BD116	£0.80	BU105	£1.90	ZTX108	£0.10	2N3820	£0.40
AC141	£0.15	BC167	£0.12	BD121	£0.65	BU105/02	£1.95	ZTX109	£0.10	2N3821	£0.60
AC141K	£0.30	BC168	£0.12	BD123	£0.65	BU204	£1.70	ZTX300	£0.12	2N3823	£0.40
AC142	£0.18	BC169	£0.12	BD124	£0.70	BU205	£1.70	ZTX500	£0.14	2N4058	£0.12
AC176	£0.12	BC169C	£0.12	BD131	£0.35	BU208	£2.40	2N11613	£0.20	2N4059	£0.18
AC176K	£0.26	BC170	£0.10	BD132	£0.38	BU208/02	£2.95	2N1711	£0.20	2N4060	£0.14
AC178	£0.25	BC171	£0.10	BD131/2	£1.22	£0.38	2N1889	£0.45	2N4061	£0.12	
AC179	£0.25	BC172	£0.10	132 MP	£0.80	MJE2955	£0.88	2N1890	£0.45	2N4062	£0.12
AC180	£0.30	BC173	£0.12	BD133	£0.80	MJE3055	£0.60	2N1893	£0.30	2N4284	£0.18
AC180K	£0.30	BC177	£0.16	BD135	£0.38	MJE3440	£0.45	2N1427	£0.75	2N4285	£0.18
AC181	£0.20	BC178	£0.16	BD136	£0.38	MP1813	£0.45	2N2160	£0.80	2N4286	£0.18
AC181K	£0.30	BC179	£0.16	BD137	£0.38	MP197	£0.38	2N2192	£0.38	2N4287	£0.18
AC187	£0.15	BC180	£0.25	BD138	£0.45	MPF104	£0.39	2N2193	£0.38	2N4288	£0.18
AC187K	£0.26	BC181	£0.25	BD139	£0.54	MPF105	£0.39	2N2194	£0.38	2N4289	£0.18
AC188	£0.15	BC182A	£0.10	BD140	£0.60	MPSA05	£0.20	2N2199	£0.22	2N4290	£0.18
AC188K	£0.26	BC183	£0.10	BD139/1	£1.20	MPSA06	£0.20	2N2217	£0.22	2N4291	£0.18
AD140	£0.85	BC183AL	£0.10	140 MP	£0.80	MPSA55	£0.20	2N2218A	£0.20	2N4292	£0.18
AD142	£0.85	BC184	£0.10	BD155	£0.80	MPSA56	£0.20	2N2129	£0.20	2N4293	£0.18
AD143	£0.85	BC184AL	£0.10	BD175	£0.60	OC22	£1.50	2N218A	£0.20	2N4921	£0.55
AD149	£0.80	BC207	£0.11	BD176	£0.60	OC23	£1.50	2N219A	£0.24	2N4923	£0.65
AD161	£0.36	BC208	£0.11	BD177	£0.68	OC24	£1.40	2N290A	£0.21	2N5136	£0.10
AD161K	£0.36	BC209	£0.12	BD178	£0.68	OC25	£0.60	2N2905A	£0.21	2N5138	£0.10
AD162	£0.36	BC209	£0.12	BD178	£0.68	OC26	£0.60	2N2906A	£0.21	2N5194	£0.56
AD161/1	£0.75	BC212	£0.11	BD201/5	£0.75	OC27	£0.90	2N2906A	£0.16	2N5245	£0.38
AF114	£0.20	BC213	£0.11	202 MP	£1.80	OC29	£1.00	2N2906A	£0.19	2N5294	£0.34
AF115	£0.20	BC213L	£0.11	BD203	£0.70	OC35	£0.90	2N2907A	£0.22	2N5296	£0.35
AF116	£0.20	BC214	£0.12	BD204	£0.68	OC36	£0.90	2N2907A	£0.22	2N5457	£0.32
AF117	£0.20	BC214L	£0.12	BD203/3	£0.70	OC71	£0.15	2N2928Y	£0.08	2N5458	£0.38
AF118	£0.40	BC237	£0.16	204 MP	£1.80	OC77	£0.15	2N2928Y	£0.08	2N5551	£0.40
AF124	£0.30	BC238	£0.16	BDY20	£0.80	IC44	£0.44	2N2928Y	£0.08	2N6027	£0.32
AF125	£0.30	BC251	£0.16	BF457	£0.37	TIP29A	£0.44	2N2928Y	£0.08	2N6121	£0.70
AF127	£0.32	BC301	£0.28	BF458	£0.37	TIP29B	£0.52	2N3053	£0.16	2N6122	£0.70
AF139	£0.58	BC302	£0.32	BF459	£0.50	TIP29C	£0.62	2N3055	£0.16	40313	£0.36
AF180	£0.58	BC303	£0.32	BF594	£0.15	TIP30A	£0.50	2N3055	£0.16	40317	£0.36
AF181	£0.58	BC304	£0.38	BF596	£0.17	TIP30B	£0.60	2N3414	£0.16	40318	£0.36
AF186	£0.58	BC327	£0.16	BF939	£0.25	TIP30C	£0.70	2N3415	£0.16	40319	£0.36
AF239	£0.98	BC328	£0.15	BF940	£0.25	TIP31A	£0.54	2N3415	£0.16	40320	£0.36
AL102	£0.98	BC337	£0.15	BF979	£0.28	TIP31B	£0.66	2N3416	£0.29	40326	£0.36
AL103	£0.95	BC388	£0.28	BF980	£0.28	TIP31C	£0.68	2N3417	£0.29	40327	£0.45
AU104	£1.00	BC440	£0.30	BFX29	£0.25	TIP32A	£0.64	2N3614	£0.85	40346	£0.42
AU110	£1.00	BC441	£0.30	BFX30	£0.30	TIP32B	£0.78	2N3616	£0.90	40347	£0.55
AU113	£1.00	BC460	£0.38	BFX84	£0.23	TIP32C	£0.78	2N3616	£0.90	40348	£0.58
BC107A	£0.08	BC461	£0.38	BFX85	£0.24	TIP41A	£0.66	2N3646	£0.09	40360	£0.38
BC107B	£0.08	BC477	£0.20	BFX86	£0.25	TIP41B	£0.70	2N3702	£0.08	40361	£0.38
BC107C	£0.08	BC478	£0.19	BFX87	£0.25	TIP41C	£0.80	2N3703	£0.07	40406	£0.40
BC108A	£0.08	BC479	£0.20	BFX88	£0.25	TIP42A	£0.72	2N3705	£0.07	40407	£0.28
BC108B	£0.08	BC547	£0.12	BFX90	£0.55	TIP42B	£0.78	2N3706	£0.08	40408	£0.48
BC108C	£0.08	BC548	£0.12	BFY50	£0.14	TIP42C	£0.95	2N3707	£0.08	40409	£0.52
BC109B	£0.08	BC549	£0.12	BFY51	£0.14	TIP42C	£0.95	2N3707	£0.08	40409	£0.52

74 SERIES TTL ICs

FULL SPECIFICATION GUARANTEED ALL FAMOUS MANUFACTURERS

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.14	7409	£0.15	7441	£0.64	7482	£0.85	7493	£0.40	74122	£0.50
7401	£0.14	7410	£0.14	7442	£0.64	7483	£0.95	7494	£0.88	74123	£0.70
7402	£0.15	7411	£0.23	7445	£0.90	7484	£0.98	7495	£0.75	74124	£0.70
7403	£0.15	7412	£0.23	7446	£1.29	7485	£0.96	7496	£0.89	7415A	£0.90
7404	£0.15	7413	£0.27	7447	£0.78	7486	£0.90	74100	£1.00	74180	£1.10
7405	£0.15	7414	£0.28	7448	£0.80	7489	£2.90	74110	£0.50	74181	£2.00
7406	£0.30	7416	£0.28	7475	£0.48	7490	£0.42	74118	£0.90	74190	£1.50
7407	£0.30	7417	£0.28	7480	£0.50	7491	£0.75	74119	£1.85	74198	£2.00
7408	£0.15	7440	£0.15	7481	£0.95	7492	£0.45	74212	£0.30	74199	£1.90

CMOS ICs

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price		
CD4000	£0.14	CD4012	£0.18	CD4022	£0.95	CD4031	£2.20	CD4046	£1.30	CD4071	£0.28
CD4001	£0.18	CD4013	£0.50	CD4023	£0.18	CD4035	£1.05	CD4047	£1.10	CD4072	£0.28
CD4002	£0.18	CD4015	£0.90	CD4024	£0.72	CD4037	£0.95	CD4049	£0.55	CD4081	£1.18
CD4006	£0.98	CD4016	£0.50	CD4025	£0.18	CD4040	£0.95	CD4050	£0.55	CD4082	£0.28
CD4009	£1.15	CD4017	£0.90	CD4026	£0.98	CD4041	£1.12	CD4055	£1.20	CD4511	£1.60
CD4008	£0.95	CD4018	£1.00	CD4027	£0.60	CD4042	£0.82	CD4054	£1.20	CD4512	£1.40
CD4009	£0.55	CD4019	£1.00	CD4028	£0.85	CD4043	£0.98	CD4056	£1.40	CD4516	£1.40
CD4010	£0.55	CD4020	£1.10	CD4029	£1.15	CD4044	£1.94	CD4069	£0.40	CD4518	£1.08
CD4011	£0.18	CD4021	£0.98	CD4030	£0.55	CD4045	£1.40	CD4070	£0.40	CD4520	£1.25

LINEAR ICs

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
CA3011	£0.80	LM304	£3.00	MC1351P	£0.85	UA703A	£0.25	SN76013N	£1.40
CA3014	£1.37	LM308H	£0.95	MC1352P	£0.85	UA709C	£0.23	SN76023N	£1.40
CA3018	£0.70	LM309K	£1.75	MC1456G	£0.85	72709	£0.46	SN76110	£1.50
CA3020	£1.40	LM320 5V	£2.00	MC1466L	£3.95	709P	£0.25	SN76115	£1.90
CA3028A	£1.10	LM320-12V	£2.00	MC1469R	£2.50	UA710C	£0.40	SN7666	£0.75
CA3031	£1.30	LM320-15V	£2.00	MC1496G	£0.90	72710	£0.30	SL403	£1.75
CA3038	£1.35	LM320-24V	£2.00	NES36	£2.00	UA711C	£0.32	SL14A	£1.75
CA3042	£1.15	LM3809	£1.00	NES15A	£2.10	72711	£0.32	TAA508B	£0.35
CA3043	£1.55	LM3811A	£1.15	NES40	£2.40	UA723C	£0.50	TAA621A	£2.00
CA3046	£0.50	LM3900N	£0.63	NES55	£0.40	72723	£0.50	UA6611A	£1.50
CA3052	£1.80	MC724P							

BI-PAK

High quality modules for stereo, mono and other audio equipment.



NEW

PUSH-BUTTON STEREO FM TUNER

OUR PRICE ONLY **£20.45**

Fitted with Phase Lock-loop Decoder

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls.

Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T538.

The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:
Sensitivity 3µ volts
Stereo separation 30db
Supply required 20-30v at 90 Ma max.

MPA 30



Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

£2.85

STEREO PRE-AMPLIFIER



PA 100

OUR PRICE **£13.75**

A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

MK. 60 AUDIO KIT: Comprising 2 x AL60s, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs, 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £29.55** plus 85p postage.

TEAK 60 AUDIO KIT: Comprising Teak veneered cabinet size 16 3/4" x 11 1/2" x 3 3/4", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £10.70** plus 85p postage.

Frequency Response + 1dB 20Hz 20KHz. Sensitivity of inputs
1 Tape Input 100mV into 100K ohms
2 Radio Tuner 100mV into 100K ohms
3 Magnetic P.U. 3mV into 50K ohms
P.U. Input equalises to R1AA curve with 1dB from 20Hz to 20KHz
Supply - 20-35V at 20mA

Dimensions -
299mm x 89mm x 35mm.

NEW AL30A

10w R.M.S. AUDIO AMPLIFIER MODULE


The AL30A is a high quality audio amplifier module replacing our AL20 & 30. The versatility of its design makes it ideal for record players, tape recorders, stereo amps, cassette and cartridge players. A power supply is available comprising a PS12 together with a transformer T538, also for stereo, the pre-amp PA12

SPECIFICATION:

- Output Power 10w. R.M.S.
- Load Impedance 8 to 6ohms.
- Sensitivity 90mv for full output.
- Frequency Response 60Hz to 25KHz ± 2db.
- Supply 22 to 32 volts.
- Input Impedance 50K.
- Total Harmonic Distortion Less than .5% (Typically .3%).
- Max. Heat Sink Temp 80°C.

● Dimensions 90 x 64 x 27mm

ONLY £3.60

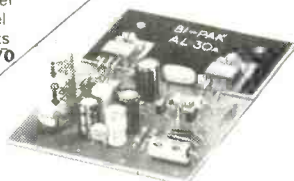

VAT ADD 12 1/2%

POSTAGE & PACKING

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

STEREO 30

COMPLETE AUDIO

7+7 WATTS R.M.S.



£16.25

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available. Ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins)

TRANSFORMER £2.45 plus 62p p & p
TEAK CASE £5.25 plus 62p p & p.

AL 60 25 Watts (RMS)

- ★ Max Heat Sink temp 90C.
- ★ Frequency response 20Hz to 100KHz
- ★ Distortion better than 0.1 at 1KHz
- ★ Supply voltage 15-50v
- ★ Thermal Feedback
- ★ Latest Design Improvements
- ★ Load - 3,4,8, or 16 ohms
- ★ Signal to noise ratio 80db
- ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast

NEW PA12

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL30A Amplifier Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range, 12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V. 5mA. Size 152mm x 84mm x 33mm.

£6.70

£4.35 PS12

Power supply for AL30A, PA12, SA450, etc.

Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size 63mm. 105mm. 30mm. Incorporating short circuit protection.

Transformer BMT80
£2.60 + 62p postage

£3.75

Input voltage 15-20v A.C. Output voltage 22-30v D.C. Output current 800 mA Max. Size 60mm x 43mm x 26mm. **OUR PRICE £1.30**
Transformer T538 £2.30

BI-PAK

P.O. BOX 6, WARE, HERTS.

SHOP AT 18 BALDOCK ST., WARE, HERTS
OPEN 9 to 5.30 Mon. / Sat

VALVE MAIL ORDER CO.

Climax House, Fallsbrook Rd., Streamham
London SW16 6ED
Tel: 01-677 2424 Telex: 946 708

SEMICONDUCTORS

AA119 0.20	ASZ16 1.25	BC172 0.13*	BD131 0.51	BF244 0.35*	CRS3/05 0.45	OA95 0.06	OC140 1.95	ZTX301 0.13*	2N1131 0.26	2N3702 0.15*
AA130 0.13	ASZ16 1.25	BC173 0.15*	BD135 0.35*	BF257 0.37	CRS/60 0.95	OA202 0.10	OC141 2.25	ZTX302 0.17*	2N1132 0.28	2N3703 0.15*
AA132 0.15	ASZ17 1.25	BC177 0.19	BD136 0.36*	BF259 0.45	GEX56 1.50	OA210 0.75	OC170 0.60	ZTX303 0.17*	2N1133 0.37	2N3704 0.15*
AA213 0.25	ASZ20 0.75	BC178 0.18	BD137 0.37*	BF259 0.45	GEX56 1.50	OA211 0.75	OC171 0.60	ZTX304 0.19*	2N1134 0.37	2N3705 0.15*
AA215 0.31	ASZ21 1.50	BC179 0.20	BD138 0.40*	BF337 0.53*	GJ3M 0.75	OA220 0.65	OC200 1.00	ZTX311 0.12*	2N1304 0.45	2N3706 0.14*
AA217 0.25	AU110 1.70*	BC182 0.11*	BD139 0.43*	BF338 0.53*	GJ5M 0.75	OA220 0.65	OC201 1.50	ZTX314 0.20*	2N1305 0.45	2N3707 0.18*
AC107 0.75	AU113 1.70*	BC183 0.11*	BD140 0.47*	BF384 0.38	MJE520 0.65	OC24 3.50	OC202 1.25	ZTX300 0.13*	2N1306 0.50	2N3708 0.14*
AC125 0.30	AU119 1.70*	BC184 0.12*	BD141 2.00	BF528 1.58	GM0378A 1.50	OC207 0.65	OC203 1.25	ZTX301 0.14*	2N1307 0.50	2N3709 0.15*
AC126 0.25	BA145 0.15*	BC182 0.14*	BD181 1.38	BF561 0.25*	KS100A 0.40*	OC16 1.25	OC205 1.75	ZTX502 0.16*	2N1308 0.60	2N3710 0.14*
AC127 0.25	BA148 0.15*	BC213 0.14*	BD182 1.48	BF598 0.25*	MJE340 0.58	OC20 2.00	OC206 1.75	ZTX503 0.17*	2N1309 0.60	2N3711 0.15*
AC128 0.25	BA154 0.10	BC214 0.17*	BD237 0.80	BFW10 0.90	MJE370 0.65	OC22 2.50	OC207 1.25	ZTX531 0.20*	2N1613 0.33	2N3712 1.60
AC141 0.20	BA155 0.12	BC237 0.17*	BD238 0.85	BFW11 0.90	MJE371 0.81	OC23 2.75	OC208 1.25	ZTX532 0.20*	2N1614 0.33	2N3713 1.70
AC141K 0.50	BA156 0.13	BC238 0.12*	BDX10 0.75	BFX84 0.38	MJE520 0.65	OC24 3.50	OC209 1.25	ZTX550 0.16*	2N1883 0.33	2N3714 2.65
AC142 0.20	BA162 0.85	BC301 0.45	BDX32 2.25	BFX85 0.41	MJE525 0.65	OC25 0.90	OC210 0.70	IN914 0.07	2N1889 0.33	2N3715 0.15*
AC142K 0.25	BAX13 0.07	BC303 0.60	BDY20 1.42	BFX87 0.35	MJE2955 1.25	OC26 0.90	R2009 2.25*	IN916 0.07	2N1890 0.33	2N3716 0.15*
AC176 0.25	BAX16 0.07	BC307 0.20*	BDY60 0.75	BFX88 0.32	MJE3055 0.75	OC28 2.00	R2010B 2.25*	IN916 0.07	2N1891 0.33	2N3717 0.15*
AC187 0.25	BC107 0.12	BC308 0.18*	BF115 0.39	BFY50 0.28	MPF102 0.30*	OC29 2.00	TIC44 0.36	IN4003 0.08	2N2218 0.33	2N3718 0.15*
AC188 0.25	BC108 0.12	BC320 0.22*	BF152 0.25	BFY51 0.26	MPF103 0.30*	OC35 1.50	TIC228D 1.30	IN4004 0.09	2N2219 0.42	2N3719 1.60
ACY17 0.65	BC109 0.13	BC328 0.18*	BF153 0.25	BFY32 0.26	MPF104 0.30*	OC36 1.50	TIP208 0.25	IN4005 0.10	2N2220 0.35	2N3720 0.22*
ACY18 0.65	BC113 0.15*	BC337 0.18*	BF154 0.25	BFY64 0.30*	MPF105 0.30*	OC41 0.50	TIP29A 0.50*	IN4006 0.15	2N2222 0.22*	2N3906 0.22*
ACY19 0.65	BC114 0.18*	BC338 0.18*	BF159 0.35	BFY90 1.32	MPSA06 0.20*	OC42 0.50	TIP30A 0.60*	IN4007 0.15	2N2223 2.75	2N4058 0.20*
ACY20 0.65	BC115 0.19*	BCY30 1.00	BF160 0.30	BSX19 0.34	MPSA50 0.20*	OC43 1.50	TIP31A 0.62	IN4009 0.15	2N2227 0.17	2N4059 0.15*
ACY21 0.65	BC116 0.19*	BCY31 1.00	BF167 0.39	BSX20 0.34	MPSU01 0.32*	OC44 0.50	TIP32A 0.75	IN4148 0.07	2N2369A 0.21	2N4060 0.20*
ACY39 1.00	BC117 0.22*	BCY32 1.00	BF173 0.39	BSX21 0.32	MPSU06 0.40*	OC45 0.50	TIP33A 1.00	IN5400 0.14	2N2484 0.21	2N4061 0.17*
AD149 0.70	BC118 0.16*	BCY33 0.90	BF177 0.38	BT106 1.25	MPSU56 0.45*	OC71 0.45	TIP34A 1.20	IN5401 0.16	2N2484 0.50	2N4062 0.18*
AD161 0.75	BC148 0.10*	BCY70 1.00	BF178 0.45	BTY79 400V	NK140 2.00	OC72 0.45	TIP41A 0.70	IN5402 0.16	2N2484 0.16	2N4063 0.17*
AD162 0.75	BC128 0.25*	BCY39 3.00	BF179 0.48	BTY79 400V	NK140 2.00	OC73 1.00	TIP42A 0.90	IN5403 0.16	2N2484 0.16	2N4064 0.17*
AF106 0.45	BC135 0.15*	BCY40 1.25	BF180 0.45	BU205 2.25*	NKT404 1.73	OC74 0.50	TIP295 1.00	IN5404 0.08	2N2484 0.25	2N4286 0.20*
AF114 0.25	BC136 0.19*	BCY42 0.30	BF181 0.45	BU206 2.25*	NE555 0.45	OC75 0.60	TIP3055 0.50	IN5405 0.08	2N2484 0.25	2N4287 0.20*
AF115 0.25	BC137 0.16*	BCY43 0.32	BF182 0.45	BU208 2.50*	OA5 0.75	OC76 0.50	TIS43 0.35*	IN5406 0.08	2N2484 0.25	2N4288 0.25*
AF116 0.25	BC147 0.10*	BCY58 0.23	BF183 0.45	BY100 0.45	OA7 0.55	OC77 1.20	ZS140 0.25*	IN5407 0.08	2N2484 0.25	2N4289 0.25*
AF117 0.25	BC148 0.10*	BCY70 1.00	BF184 0.39	BY126 0.14	OA8 0.55	OC78 0.75	ZS170 0.20*	IN5408 0.08	2N2484 0.25	2N4290 0.25*
AF139 0.40	BC149 0.13*	BCY71 0.22	BF185 0.37	BY127 0.15	OA7 0.55	OC81 0.75	ZS178 0.54*	IN5409 0.08	2N2484 0.25	2N4291 0.25*
AF186 1.50	BC157 0.12*	BCY72 0.17	BF194 0.12*	BZK61 0.20	OA70 0.30	OC82 0.75	ZS271 0.22*	IN5410 0.08	2N2484 0.25	2N4292 0.25*
AF239 0.45	BC158 0.11*	BCZ11 1.50	BF195 0.11*	Series	OA79 0.30	OC83 0.55	ZS278 0.54*	IN5411 0.08	2N2484 0.25	2N4293 0.25*
AFZ11 2.75	BC159 0.13*	BD115 0.60	BF196 0.13*	BZ785 0.13	OA81 0.30	OC84 0.60	ZTX107 0.11*	IN5412 0.08	2N2484 0.25	2N4294 0.25*
AFZ12 2.75	BC167 0.13*	BD121 1.50	BF197 0.14*	Series	OA85 0.30	OC122 1.50	ZTX108 0.11*	IN5413 0.08	2N2484 0.25	2N4295 0.25*
ASV26 0.45	BC170 0.16*	BD123 1.50	BF200 0.32	CRS1/05 0.45	OA90 0.80	OC123 1.55	ZTX109 0.12*	IN5414 0.08	2N2484 0.25	2N4296 0.25*
ASV27 0.50	BC171 0.14*	BD124 1.00	BF224 0.20*	CRS1/40 0.60	OA91 0.08	OC139 1.25	ZTX300 0.12*	IN5415 0.08	2N2484 0.25	2N4297 0.25*

VALVES

A1834 6.00	DK91 1.00*	E182CC 5.72	ECC91 1.35*	EP95 0.30*	EN92 1.94	GZ33 4.00*	M8212 8.82	PCC89 1.05*	PL599 2.16*	Q206-20 18.95
A2087 10.48	DK92 1.25*	E186F 7.68	ECC189 1.00*	EP98 1.20*	EY51 0.75*	GZ34 4.20*	M8223 2.30	PCC189 0.65*	PL599 2.16*	R10 5.00
A2134 4.81	DK96 1.00*	E188CC 4.92	ECC807 1.75	EF183 0.50*	EY81 1.65*	GZ37 3.50*	M8224 2.80	PCC805 0.95*	PL801 1.10*	R17 1.65*
A2293 4.10	DL92 0.75*	E283CC 12.22	ECC808 2.25*	EF184 0.50*	EY83 1.75*	KT61 4.00*	M8225 2.60	PCC806 0.95*	PL802 1.10*	R18 3.86*
A2426 9.20	DL96 1.10*	E288CC 11.00	ECC809 2.25*	EF185 0.50*	EY84 1.75*	KT66 4.50*	M8248 6.54	PCC82 1.05*	PV33 0.88*	R19 1.00*
A2501 8.53	DL510 8.25	EAB76 1.50	ECH35 2.00*	EK90 0.65*	EY500A 1.38*	KT66 4.50*	M8248 6.54	PCC82 1.05*	PV33 0.88*	R20 1.00*
A2824 4.85	DL515 8.25	EACB80 0.40*	ECH42 1.15	EK91 0.65*	EY500A 1.38*	KT66 4.50*	M8248 6.54	PCC82 1.05*	PV33 0.88*	R21 1.00*
A3343 18.43	DL516 8.25	EAF42 1.25*	ECH81 0.50*	EL33 3.50*	EZ35 0.55*	M8079 8.38	MX115 11.69	PCC200 1.05*	PV500A 1.36*	RG3-250 8.85
AZ31 1.10*	DL519 8.25	EAF801 1.75*	ECH83 0.50*	EL34 3.50*	EZ40 1.25*	M8080 3.80	MX152 61.65	PCC201 1.05*	PV500A 1.36*	RG3-250 8.85
AZ41 1.15*	DM70 1.25	EBA78 1.75*	ECL84 0.80*	EL36 0.75*	EZ41 1.25*	M8081 6.16	MX152 61.65	PCC202 1.05*	PV500A 1.36*	RG3-250 8.85
BK448 48.70	DM71 1.25	EBA79 1.75*	ECL85 0.80*	EL37 0.75*	EZ42 1.25*	M8082 6.16	MX152 61.65	PCC203 1.05*	PV500A 1.36*	RG3-250 8.85
BS90 27.25	DY86 0.75*	EBC41 1.25*	ECL86 0.80*	EL38 1.10*	EZ43 1.25*	M8083 6.50	MX163 11.89	PCC204 1.05*	PV500A 1.36*	RG3-250 8.85
BS810 27.75	DY802 0.65*	EBC81 1.10*	ECL87 0.80*	EL39 1.10*	EZ44 1.25*	M8084 6.50	MX164 12.56	PCC205 1.05*	PV500A 1.36*	RG3-250 8.85
BT5 31.15	E55L 21.89	EBC90 0.65*	ECL88 0.80*	EL40 1.10*	EZ45 1.25*	M8085 6.50	MX165 12.56	PCC206 1.05*	PV500A 1.36*	RG3-250 8.85
BT17 55.84	E80CC 4.86	EBC91 0.65*	ECL89 0.80*	EL41 1.10*	EZ46 1.25*	M8086 6.50	MX166 12.56	PCC207 1.05*	PV500A 1.36*	RG3-250 8.85
BK448 48.70	DM71 1.25	EBC92 0.65*	ECL90 0.80*	EL42 1.10*	EZ47 1.25*	M8087 6.50	MX167 12.56	PCC208 1.05*	PV500A 1.36*	RG3-250 8.85
BT29 169.70	E80F 5.57	EBC93 1.75*	ECL91 0.80*	EL43 1.10*	EZ48 1.25*	M8088 6.50	MX168 12.56	PCC209 1.05*	PV500A 1.36*	RG3-250 8.85
BT69 173.65	E80L 5.34	EBC94 1.25*	ECL92 0.80*	EL44 1.10*	EZ49 1.25*	M8089 6.50	MX169 12.56	PCC210 1.05*	PV500A 1.36*	RG3-250 8.85
BT75 72.80	E81CC 5.76	EBC95 1.25*	ECL93 0.80*	EL45 1.10*	EZ50 1.25*	M8090 6.50	MX170 12.56	PCC211 1.05*	PV500A 1.36*	RG3-250 8.85
BT95 66.85	E81L 5.61	EBC96 1.25*	ECL94 0.80*	EL46 1.10*	EZ51 1.25*	M8091 6.50	MX171 12.56	PCC212 1.05*	PV500A 1.36*	RG3-250 8.85
CB131 1.50	E82CC 6.85	EBC97 1.25*	ECL95 0.80*	EL47 1.10*	EZ52 1.25*	M8092 6.50	MX172 12.56	PCC213 1.05*	PV500A 1.36*	RG3-250 8.85
CB132 2.00*	E82CC 6.85	EBC98 1.25*	ECL96 0.80*	EL48 1.10*	EZ53 1.25*	M8093 6.50	MX173 12.56	PCC214 1.05*	PV500A 1.36*	RG3-250 8.85
CB31 1.00*	E84L 5.25	EBC157 190.00	EFL50 0.60*	EL49 1.10*	EZ54 1.25*	M8094 6.50	MX174 12.56	PCC215 1.05*	PV500A 1.36*	RG3-250 8.85
CIK 10.00	E86C 8.93	ECC33 3.50*	EFL51 0.60*	EL50 0.60*	EZ55 1.25*	M8095 6.50	MX175 12.56	PCC216 1.05*	PV500A 1.36*	RG3-250 8.85
C3A 10.00	E88C 5.24	ECC35 3.50*	EFL52 0.60*	EL51 0.60*	EZ56 1.25*	M8096 6.50	MX176 12.56	PCC217 1.05*	PV500A 1.36*	RG3-250 8.85
C3A 10.00	E88CC 1.00	ECC40 1.25*	EFL53 0.60*	EL52 0.60*	EZ57 1.25*	M8097 6.50	MX177 12.56	PCC218 1.05*	PV500A 1.36*	RG3-250 8.85
DA41 18.10	E90CC 5.02	ECC41 1.25*	EFL54 0.60*	EL53 0.60*	EZ58 1.25*	M8098 6.50	MX178 12.56	PCC219 1.05*	PV500A 1.36*	RG3-250 8.85
DA42 8.81	E90F 5.02	ECC42 0.45*	EFL55 0.60*	EL54 0.60*	EZ59 1.25*	M8099 6.50	MX179 12.56	PCC220 1.05*	PV500A 1.36*	RG3-250 8.85
DA100 31.86	E91H 4.66	ECC43 0.45*	EFL56 0.60*	EL55 0.60*	EZ60 1.25*	M8100 6.50	MX180 12.56	PCC221 1.05*	PV500A 1.36*	RG3-250 8.85
DAF91 0.40*	E92CC 4.86	ECC44 0.50*	EFL57 0.60*	EL56 0.60*	EZ61 1.25*	M8101 6.50	MX181 12.56	PCC222 1.05*	PV500A 1.36*	RG3-250 8.85
DAF96 1.00*	E93F 5.38	ECC45 0.55*	EFL58 0.60*	EL57 0.60*	EZ62 1.25*	M8102 6.50	MX182			

Zambia Gibraltar Chile Spain United Arab Emirates Singapore New Guinea Israel

POWERTRAN ELECTRONICS

INCORPORATING

AMBIENTACOUSTICS

HI-FI NEWS 75W/CHANNEL AMPLIFIER



By J. L. Linsley Hood

In Hi-Fi News there was published by Mr. Linsley-Hood a series of four articles (November, 1972-February, 1973) and a subsequent follow-up article (April, 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power levels. The power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Liniac which is employed in the two most critical points of the system, namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimline unit pictured has been made practical by highly compact PCBs and a specially designed Toroidal transformer.

- | Pack | Price |
|--|--------|
| 1. Fibreglass printed-circuit board for power amp | £1.15 |
| 2. Set of resistors, capacitors, pre-sets for power amp | £2.50 |
| 3. Set of semiconductors for power amp | £6.50 |
| 4. Pair of 2 drilled, finned heat sinks | £1.10 |
| 5. Fibreglass printed-circuit board for pre-amp | £1.90 |
| 6. Set of low noise resistors, capacitors, pre-sets for pre-amp | £4.10 |
| 7. Set of low noise, high gain semiconductors for pre-amp | £2.40 |
| 8. Set of potentiometers (including mains switch) | £3.50 |
| 9. Set of 4 push-button switches, rotary mode switch | £5.40 |
| 10. Toroidal transformer complete with magnetic screen/housing primary: 0 117-234 V; secondaries: 33-0-33 V, 25-0-25 V | £10.95 |

- | Pack | Price |
|--|--------|
| 11. Fibreglass printed-circuit board for power supply | £8.85 |
| 12. Set of resistors, capacitors, secondary fuses, semi-conductors for power supply | £5.40 |
| 13. Set of miscellaneous parts including DIN skts, mains input skt, fuse holder, inter-connecting cable, control knobs | £6.20 |
| 14. Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc | £8.20 |
| 15. Handbook (free with complete kit) | £0.30 |
| 16. Teak cabinet 18.3" x 12.7" x 3.1" | £10.70 |
- 2 each of packs 1-7 inclusive are required for complete stereo system. Total cost of individually purchased packs £90.80

Designed in response to demand for a tuner to complement the world-wide acclaimed Linsley Hood 75W Amplifier, this kit provides the perfect match. The Wireless World (Skingley and Thompson - April, May 1974) published original circuit has been developed further for inclusion into this outstanding slimline unit and features a pre-aligned front end module, excellent a.m. rejection and temperature compensated varicap tuning, which may be controlled either continuously or by push button pre-selection. Frequencies are indicated by a frequency meter and sliding LED indicators, attached to each channel selector pre-set. The PLL stereo decoder incorporates active filters for 'birdy' suppression and power is supplied via a toroidal transformer and integrated regulator. For long term stability metal oxide resistors are used throughout.

- | Pack | Price |
|--|--------|
| 1. Fibreglass printed board for front and RF strip, demodulator, AFC and mute circuits | £2.15 |
| 2. Set of metal oxide resistors, thermistor, capacitors, ceramic preset for mounting on pack 1 | £4.80 |
| 3. Set of transistors, diodes, LED, integrated circuits for mounting on pack 1 | £5.25 |
| 4. Pre-aligned front end module, coil assembly, three section ceramic filter | £8.50 |
| 5. Fibreglass printed circuit board for stereo decoder | £1.10 |
| 6. Set of metal oxide resistors, capacitors, ceramic preset for decoder | £2.60 |
| 7. Set of transistors LED, integrated circuit for decoder | £2.90 |
| 8. Set of components for channel selector switch module including fibreglass printed circuit board, push-button switches, knobs, LEDs, preset adjusters etc. | £9.40 |
| 9. Function switch, 10 turn tuning potentiometer, knobs | £5.80 |
| 10. Frequency meter, meter drive components, fibreglass printed circuit board | £10.35 |

- | Pack | Price |
|--|--------|
| 11. Toroidal transformer with electrostatic screen. Primary: 0-117V 234V | £4.90 |
| 12. Set of capacitors, rectifiers, voltage regulator for power supply | £2.10 |
| 13. Set of miscellaneous parts, including sockets, fuse holder, fuses, inter-connecting wire, etc. | £2.05 |
| 14. Set of metal work parts including silk screen printed fascia panel, acrylic silk screen printed tuning indicator panel insert, internal screen, fixing parts, etc. | £8.30 |
| 15. Construction notes (free with complete kit) | £0.25 |
| 16. Teak cabinet 10.3" x 12.7" x 3.1" | £10.70 |
- One each of packs 1-16 inclusive are required for complete stereo FM tuner. Total cost of individually purchased packs £81.15

Published in Wireless World (May, June, August 1976) by Mr. Linsley-Hood, this design, although straightforward and relatively low cost nevertheless provides a very high standard of performance. To permit circuit optimization separate record and replay amplifiers are used, the latter using a discrete component front-end designed such that the noise level is below that of the tape background. Push button switches are used to provide a choice of equalization time constants, a choice of bias levels and also an option of using an additional pre-amplifier for microphone use. The mechanism used is the Goldring-Lenco CRV, a unit distinguished in its robustness and ease of operation. Speed control and automatic cassette ejection are both implemented by electronic circuitry. This unit which is powered by a toroidal transformer and uses metal oxide resistors throughout offers an excellent match for the Wireless World Tuner and the Linsley-Hood 75 Watt Amplifier.

PRICE STABILITY

Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement for two months from issue date provided that this advertisement is quoted with your order. E&OE VAT rate changes excluded. All components are brand new first grade full specification devices. All resistors (except where stated) are low noise carbon film types. All printed circuit boards are fibre-glass, drilled, roller tinned and supplied with circuit diagrams and construction layouts.

Value Added Tax not included in prices.

EXPORT ORDERS. No VAT charged. Postage charged at actual cost plus 50p documentation and handling. Please make payment by Irrevocable Letter of Credit £500 minimum. Bank Draft, Postal Order, International Money Order in Sterling. **SECURICOR DELIVERY.** For this optional service (U.K. Mainland only) add £2.50 (VAT INC.) per kit. **U.K. ORDERS.** Subject to 12 1/2 % * surcharge for VAT. Carriage free. **MAIL ORDER ONLY** (*or at current rate if changed)


FREE TEAK CASE WITH FULL KITS
£79.80
KIT PRICE ONLY

WIRELESS WORLD FM TUNER



FREE TEAK CASE WITH FULL KITS
KIT PRICE only **£70.20**

LINSLEY-HOOD CASSETTE DECK

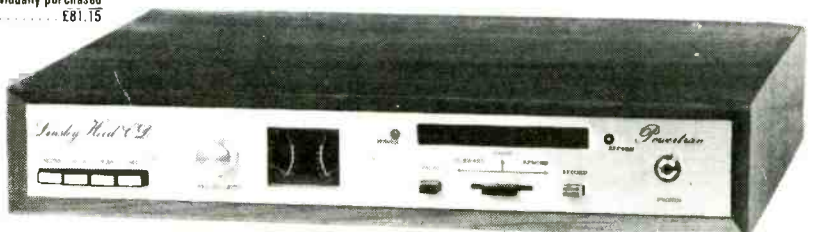

- | Pack | Price |
|--|--------|
| 1. Stereo PCB (accommodates 2 rep. amps, 2 rec. amps, 2 meter amps, bias/erase osc, relay) | £3.35 |
| 2. Stereo set of capacitors, M.O. resistors, potentiometers for above | £9.80 |
| 3. Stereo set of semiconductors for above | £8.50 |
| 4. Miniature relay with socket | £2.90 |
| 5. PCB, all components for solenoid, speed control circuits | £3.80 |
| 6. Goldring Lenco mechanism as specified | £21.95 |
| 7. Function switch, knobs | £1.90 |
| 8. Dual VU meter with illuminating lamp | £8.70 |
| 9. Toroidal transformer with E.S. screen prim. 0-117V 234V, Sec. 15V | £4.90 |

- | Pack | Price |
|---|--------|
| 10. Set of capacitors, rectifiers, I.C. voltage regulator for power supply (Powertran design) | £2.80 |
| 11. Set of miscellaneous parts, including sockets, fuse holder, fuses, interconnecting wire, etc. | £3.40 |
| 12. Set of metalwork including silk screened fascia panel, internal screen, fixing parts, etc. | £7.10 |
| 13. Construction notes | £0.25 |
| 14. Teak cabinet 18.3" x 12.7" x 3.1" | £10.70 |
- One each of packs 1-14 inclusive are required for complete stereo cassette deck. Total cost of individually purchased packs £90.05

SPECIAL PRICE FOR COMPLETE KITS £85.90

Further details of above given in our FREE CATALOGUE **EXPORT CUSTOMERS.** Please send five INTERNATIONAL REPLY COUPONS OR £0.50 for catalogue to DEPT WW7 be sent by airmail

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NN

Indonesia Brazil Switzerland Canada Saudi Arabia New Zealand Norway Iceland Sweden

Falkland Islands
 Portugal
 Guyana
 India
 Greece
 Jordan
 States of America
 United States of America
 Yugoslavia
 Ascension Island
 Malaysia

Guernsey Cyprus Belgium Uganda Brunei Trinidad South West Africa Italy Java Grenada

AUDIO KIT SUPPLIERS TO THE WORLD



T20+20 and our new T30+30 20W, 30W AMPLIFIERS

Designed by Texas engineers and described in Practical Wireless the Texan was an immediate success. Now developed further in our laboratories to include a Toroidal transformer and additional improvements, the slimline T20 + 20 delivers 20W per channel of true Hi-Fi at exceptionally low cost. The design is based on a single F/Glass PCB and features all the normal facilities found on quality Hi-Fi amplifiers, including scratch and rumble filters, adaptable input selector and head phones socket. In a follow up article in Practical Wireless further modifications were suggested and these have been incorporated into the T30 + 30. These include RF interference filters and a tape monitor facility. Power output of this new model is 30W per channel.

SPECIAL PRICES

FOR COMPLETE KITS!

T20+20
KIT PRICE only **£ 34.20**

T30+30
KIT PRICE only **£ 39.50**

Pack	T20	T30
1. Set of low noise resistors	1.60	1.70
2. Set of small capacitors	2.60	3.40
3. Set of power supply capacitors	2.20	2.50
4. Set of miscellaneous parts	3.50	3.50
5. Set of slide, mains, P.B. switches	1.50	1.50
6. Set of pots, selector switch	2.80	2.80
7. Set of semiconductors, ICs, skts.	7.25	7.25


Pack	T20	T30
8. Toroidal transformer — 240V prim. e.s. screen	5.60	7.20
9. Fibreglass PCB	3.50	3.90
10. Set of metalwork, fixing parts	5.20	6.20
11. Set of cables, mains lead	0.40	0.40
12. Handbook (free with complete kit)	0.25	0.25
13. Teak cabinet 15.4" x 6.7" x 2.8"	4.50	4.50

2 MATCHING TUNERS!

WW SFMT II

Following the success of our Wireless World FM Tuner kit we are now pleased to introduce our new cost reduced model, designed to complement the T20 and T30 amplifiers. The frequency meter of the more advanced model has been omitted and the mechanics simplified, however the circuitry is identical and this new kit offers most exceptional value for money. Facilities included are switchable afc, adjustable, switchable muting, channel selection by slider or readily adjustable pre-set push-button controls and LED tuning indication. Individual pack prices in our free list.


KIT PRICE
£47.70

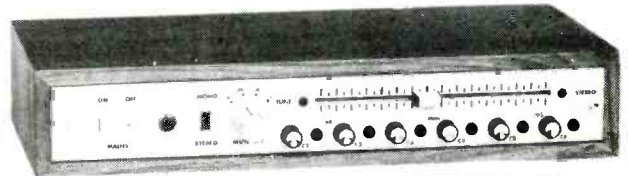

POWERTRAN SFMT

This easy to construct tuner using our own circuit design includes a pre-aligned front end module, PLL stereo decoder, adjustable, switchable muting, switchable afc and push-button channel selection. As with all our full kits, all components down to the last nut and bolt are supplied together with full constructional details.

KIT PRICE
£35.90

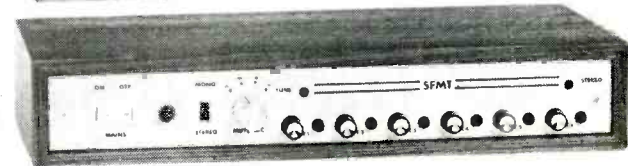

CONVERT NOW TO QUADRAPHONICS!



SQM1 — 30 KIT PRICE **£40.75**

With 100s of titles now available no longer is there any problem over suitable software. No problems with hardware either. Our new unit the SQM1-30 simply plugs into the tape monitor socket of your existing amplifier and drives two additional speakers at 30W per channel. A full complement of controls including volume, bass, treble and balance are provided as are comprehensive switching facilities enabling the unit to be used for either front or rear channels, by-passing the decoder for stereo-only use and exchanging left and right channels. The SQM1-30 matrix decoder is based upon a single integrated circuit and was designed by CBS whilst the power and tone control sections are identical to those used in our T30 + 30 amplifier which the SQM1-30 matches perfectly. Kit price includes CBS licence fee.



Special offer to T20 + 20 and Texan owners!
Owners of T20 + 20 and Texan amplifiers, which have no tape monitor outlet, purchasing an SQM1-30 will be supplied on request, a free conversion kit to fit a tape monitoring facility to the existing amplifier. This makes simple the connection to the highly adaptable SQM1-30 quadraphonic decoder/rear channel amplifier.

Wireless World Amplifier Designs. Full kits are not available for these projects but component packs and PCBs are stocked for the highly regarded Bailey and 20W class AB Linsley Hood designs, together with an efficient regulated power supply of our own design. Suitable for driving these amplifiers is the Bailey Burrows pre-amplifier and our circuit board, for the stereo version it features 6 inputs, scratch and rumble filters and wide range tone controls which may be either rotary or slider operating. For those intending to get the best out of their speakers, we also offer an active filter system, described by D. C. Read, which splits the output of each channel from the pre-amplifier into three channels, each of which is fed to the appropriate speaker by its own power amplifier. The Read/Texas 20W, or any of our other kits are suitable for these. For tape systems a set of three PCBs have been prepared for the integrated circuit based, high performance stereo Stuart design. Details of component packs are in our free catalogue.

30W Bailey Amplifier	
BAIL Pk 1 F/Glass PCB	£1.00
BAIL Pk 2 Resistors, Capacitors, Potentiometer set	£2.35
BAIL Pk 3 Semiconductor set	£4.70
20W Linsley Hood Class AB	
LHAB Pk 1 F/Glass PCB	£1.05
LHAB Pk 2 Resistor, Capacitor, Potentiometer set	£3.20
LHAB Pk 3 Semiconductor set	£3.35
Regulator Power Supply	
60VS Pk 1 F/Glass PCB	£0.85
60VS Pk 2 Resistor, Capacitor set	£2.20
60VS Pk 3 Semiconductor set	£3.10
60VS Pk 6A Toroidal transformer (for use with Bailey)	£8.80
60VS Pk 6B Toroidal transformer (for use with 20W LH)	£7.25
Bailey Burrows Stereo Pre-Amp	
BBPA Pk 1 F/Glass PCB stereo	£2.80
BBPA Pk 2 Resistor, capacitor semiconductor set, stereo	£6.70
BBPA Pk 3R Rotary Potentiometer set, Stereo	£2.85
BBPA Pk 3S Slider Potentiometer set with knobs, Stereo	£3.10
Active Filter	
FILT Pk 1 F/Glass PCB	£1.40
FILT Pk 2 Resistor, Capacitor set (metal oxide 2%, polystyrene 2 1/2%)	£4.20
FILT Pk 3 Semiconductor set	£2.25
2 off Pks 1, 2, 3 reqd for stereo active filter system	
Read/Texas 20W Amp	
READ Pk 1 F/Glass PCB	£1.00
READ Pk 2 Resistor, Capacitor set	£1.20
READ Pk 3 Semiconductor set	£2.30
6 off pks 1, 2, 3 required for stereo active filter system	
Stuart Tape Recorder	
TRRP Pk 1 Replay Amp F/Glass PCB stereo	£1.30
TRRC Pk 1 Record Amp F/Glass PCB Stereo	£1.70
TRSP Pk 1 Bias Erase Stabilizer F/Glass PCB stereo	£1.20

Further details of above and additional packs given in our FREE LIST

SQ QUADRAPHONIC DECODERS

Feed 2 channels (200-1000mV as obtainable from most pre-amplifiers or amplifier tape monitor outlets) into any one of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume, Front Back, LF-RF balance, LB-RB balance and Dimension controls can all be implemented by simple single gang potentiometers. These state-of-the-art circuits used under licence from CBS are offered in kits of superior quality with close tolerance capacitors, metal oxide resistors and fibre-glass PCBs designed for edge connector insertion. All kit prices include CBS licence fee.

M1. Basic matrix decoder with fixed 10:40 blend. All components, PCB	£5.90
L1. Full logic controlled decoder with 'wave matching' and 'front back logic' for enhanced channel separation. All components PCB	£17.20
L2A. More advanced full logic decoder with 'variable blend' for increased front back separation. All components, PCB	£22.60
L3A. Decoder similar to L2A but with discreet component front end with high precision 6-pole phase shift networks for increased frequency response. All components (carbon film resistors), PCB	£25.90
Also available with M.O. resistors, cermet pre-set — add	£4.20

SEMICONDUCTORS as used in our range of quality audio equipment.

2N699	£0.20	BC108	£0.10	BF257	£0.40	MPSA05	£0.25	TIP29C	£0.55
2N1613	£0.20	BC109	£0.10	BF259	£0.47	KPSA12	£0.35	TP30C	£0.60
2N3055	£0.45	BC109C	£0.12	BF839	£0.30	MPSA14	£0.30	TP41A	£0.70
2N3442	£1.20	BC125	£0.15	BF879	£0.30	MPSA55	£0.25	TP42A	£0.80
2N3711	£0.09	BC126	£0.15	BFY51	£0.20	MPSA65	£0.35	TP41B	£0.75
2N3904	£0.17	BC182	£0.10	BFY52	£0.20	MPSA66	£0.40	TP42B	£0.90
2N3906	£0.20	BC212	£0.12	CA3046	£0.70	MPSU05	£0.50	1N914	£0.07
2N5087	£0.25	BC182L	£0.10	LP1186	£6.50	SBA750A	£1.90	1N916	£0.07
2N5457	£0.45	BC184L	£0.11	MC1310	£2.20	SL301	£1.30	15920	£0.10
2N5459	£0.45	BC212L	£0.12	MC1351	£1.05	SL3045	£1.20		
2N5461	£0.50	BC214L	£0.14	MC1741CG	£0.65	SN72741P	£0.40	FILTERS	
2N5830	£0.35	BCY72	£0.13	MF4010	£0.95	SN72748P	£0.40	FM4	£1.00
40361	£0.40	BD529	£0.55	MJ481	£1.20	TIL209	£0.20	SFJ10 7MA	£1.50
40362	£0.45	BD530	£0.55	MJ491	£1.45	TIP29A	£0.40		
BC107	£0.10	BDY56	£1.60	MJE521	£0.60	TIP30A	£0.45		

EXPORT NO PROBLEM

Our Export Department will be pleased to advise on postal costs to any country in the world. Some of the countries to which we sent kits in 1976 are shown surrounding this advertisement.

Tunisia Germany Nauru Hong Kong Australia Eire Gambia Denmark France Muscat & Oman

Sierra Leone Jamaica Holland Kenya Malta Windward Isles Austria Czechoslovakia South Africa Finland Nigeria Luxembourg

Z & I AERO SERVICES LTD.

Head Office: 44A WESTBOURNE GROVE, LONDON W2 5SF
Tel.: 727 5641 Telex: 261306

Retail Branch:
85 Tottenham Court Road
London W1. Tel: 580 8403

MULTIMETER F4313 (Made in USSR)



SENSITIVITY:
1200V DC range: 10,000 Ω/V
Other DC ranges: 20,000 Ω/V
1200 AC range: 6,000 Ω/V
600V AC range: 15,000 Ω/V
300V AC range: 15,000 Ω/V
Other AC ranges: 20,000 Ω/V


AC/DC current ranges: 60-120-600μA-3-12-300mA-1-2-6A
AC/DC voltage ranges: 60-300mV-1.2-6-30-120-300-600-1200V
Resistance ranges: 300Ω-10-100-1000K
Accuracy: 1.5% DC, 2.5% AC (of full scale deflection)

Mirror scale and knife edge pointer. Taut suspension of movement. Transistor amplifier is used for all AC ranges thus achieving a common linear scale for both AC and DC ranges.

Meter is protected by a transistorised cut-out relay circuit. Range selection is achieved by clearly marked piano keys. Power source: 5 1.5V dry cells. Dimensions: 95 x 225 x 120mm.

Price £39.50 plus VAT
Packaging and postage £1.10

OSCILLOSCOPE CI-5 (Made in USSR)

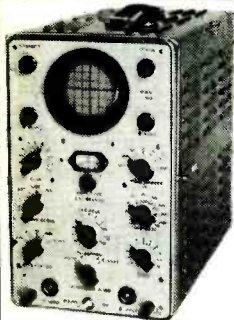

Extremely simple and easy to use single beam oscilloscope. Well proved design based on standard octal valves makes servicing and maintenance straightforward and inexpensive. Because of its bandwidth of 10 MHz the instrument is suitable for general electronic applications and educational purposes where a sophisticated instrument would be both too expensive and delicate. 3in. tube giving a 50 x 50mm clear display. Amplitude and time base calibrations. Sensitivity 30mm/v max. Triggered and free-running time base, suitable for displaying pulses from 0.1 μsec. to 3 m sec. A.C. mains operation.

Price £55.00 ex. works, plus VAT
Packing and carriage (U.K. only) £3.00

FULLY GUARANTEED

0A2	0.45	12A5	0.65	EY87	0.50	PL504	0.90
0A3	0.55	12A05	0.55	EY88	0.50	PL508	0.90
0B2	0.45	12A17	0.45	EZ40	0.60	PL509	1.30
0C3	0.45	12A07	0.38	EZ41	0.75	PY31	0.50
0D3	0.45	12A06	0.60	EZ80	0.30	PY33	0.63
183GT	0.55	12A07	0.90	EZ81	0.35	PY81	0.45
1R5	0.55	12A07	0.38	KT66	3.40	PY82	0.45
5R4GY	1.00	12B4A	0.80	KT88	4.80	PY83	0.50
5U4G	0.55	12B6A	0.60	PC66	0.65	PY88	0.50
5Z4G	0.55	12B6E	0.60	PC88	0.65	PY500A	1.10
5Y3GT	0.65	12B7H	0.60	PC84A	0.45	TT21	6.30
6A5	0.65	12X4	0.50	PC85	0.45	TT22	6.30
6A5K	0.45	19A05	0.75	PC88	0.65	UABC80	0.50
6A5L	0.30	30A5	0.70	PC89	0.55	UJ42	0.70
6A5S	0.65	35A3	0.70	PC189	0.65	UBC41	0.50
6A56	0.80	35A5	0.80	PCF80	0.40	UBC81	0.50
6A7E	0.60	35C5	0.70	PCF82	0.40	UBF80	0.50
6A76	0.50	35E5	0.70	PCF86	0.65	UBF89	0.50
6A78A	0.75	35A5	0.80	PCF200	0.80	UC84A	0.75
6A86	0.40	35W4	0.60	PCF201	0.85	UC85	0.50
6B6A	0.38	50C5	0.70	PCF802	0.55	UCF80	0.75
6B6E	0.45	58C80	0.40	PCF200	0.75	UAC2	0.80
6B6J	0.75	58C91	0.55	PCF801	0.75	UCL81	0.50
6B6M	0.80	58F42	0.70	PCF801	0.75	UCL82	0.40
6B6Z	0.55	58F801	0.65	PCF802	0.75	UCL83	0.70
6C4	0.40	58C81	0.50	EL82	0.60	UCL84	0.50
6C86	0.50	58F80	0.50	EL83	0.60	UCL85	0.50
6E48	0.75	58F83	0.50	EL84	0.60	UCL86	0.50
6GK5	0.70	58F89	0.40	EL95	0.70	UCL87	0.50
6J4	0.75	58C86	0.75	EL95	0.70	UCL88	0.50
6J5GT	0.55	58C88	0.75	EM80	0.55	UCL89	0.50
6J6	0.35	58C91	2.80	EM81	0.60	UCL90	0.50
6L6GT	0.60	58C81	0.45	EM84	0.45	UCL91	0.55
6SL7GT	0.55	58C82	0.38	EM84	0.45	UCL92	0.50
6SM7E	0.55	58C83	0.38	EM84	0.45	UCL93	0.50



All prices are exclusive of VAT

MINIMUM EXPORT ORDER £100

LARGE STOCKS OF SEMICONDUCTORS

1976/1977 CATALOGUE AVAILABLE 30p

WW - 084 FOR FURTHER DETAILS

AMATEUR COMPONENTS

ORCHARD WORKS, CHURCH LANE, WALLINGTON, SURREY SM6 7NF

MAIL ORDER DIVISION OF SEMICONDUCTOR SUPPLIES (CROYDON) LTD.

For Semiconductors Capacitors Resistors I/C Sockets L.E.D.'s and

Hi-Fi Accessories

AC125	20	BC108B	12	BC173	15	BC207A	16	BCY58	22	BF257	30	BU133	1.95	TIP31A	57	ZTX504	25	2N1671	1.50	ZN3638A	16	ZN4304	44.00
AC126	20	BC108C	13	BC173A	16	BC307B	16	BCY70	17	BF258	40	BU205	2.00	TIP31B	64	ZTX510	16	2N1671A	1.60	ZN3642	17	ZN4410	50.00
AC127	30	BC109	13	BC173B	16	BC307C	16	BCY71	18	BF259	42	BU206	2.00	TIP31C	79	ZTX520	23	2N1711	1.80	ZN3644	17	ZN4416	70.00
AC127K	30	BC109B	14	BC173C	16	BC308	12	BCY72	14	BF271	40	BU208	2.35	TIP32	60	ZTX531	23	2N1711B	1.80	ZN3643	17	ZN4416E	40.00
AC128	18	BC109C	14	BC174	16	BC212A	13	BCY73	30	BF273	30	BY126	16	TIP32A	67	ZTX532	20	2N1889	34	ZN3644	18	ZN4871	50.00
AC128K	26	BC113	12	BC177	17	BC212B	13	BCY74	34	BF274	34	BY127	16	TIP32B	76	ZTX538	18	2N1890	34	ZN3645	18	ZN5126	18.00
AC132	35	BC114	15	BC177A	17	BC213A	12	BCY75	30	BF336	32	BY133	20	TIP32C	94	ZTX541	20	2N1893	28	ZN3646	17	ZN5127	19.00
AC141	20	BC115	15	BC177B	18	BC213B	12	BCY76	30	BF337	33	BY164	40	TIP33	84	ZTX542	25	2N1990	50	ZN3647	18	ZN5128	16.00
AC141K	30	BC116	15	BC178	18	BC213C	14	BCY77	30	BF338	34	BY110	14	TIP33A	84	ZTX550	20	2N102	50	ZN3692	15	ZN5129	17.00
AC142	20	BC118A	15	BC178A	18	BC213D	12	BCY78	30	BF339	26	MJE2955	1.40	TIP33B	105	ZTX551	21	2N1260	90	ZN3693	17	ZN5131	17.00
AC142K	25	BC117	18	BC178B	18	BC213E	12	BCY79	30	BF340	26	MJE3055	90	TIP33C	31	IN914	06	2N1292	40	ZN3694	17	ZN5132	17.00
AC151	24	BC118	10	BC178C	18	BC213F	14	BCY80	30	BF341	32	OA5	71	TIP34	100	IN916	07	2N1924	44	ZN3702	11	ZN5133	17.00
AC151K	34	BC119	28	BC179	18	BC213G	15	BCY81	30	BF342	34	OA10	62	TIP34A	117	IN4001	07	2N2193	35	ZN3703	11	ZN5135	18.00
AC153	27	BC125	16	BC179B	19	BC214	15	BCY82	30	BF343	34	OA7	14	TIP34B	126	IN4002	07	2N2193A	40	ZN3704	14	ZN5136	18.00
AC153K	37	BC126	20	BC179C	19	BC214A	14	BCY83	30	BF344	26	OA73	30	TIP34C	159	IN4003	07	2N2194	35	ZN3705	14	ZN5137	18.00
AC176	22	BC128	25	BC182	11	BC214B	14	BCY84	30	BF345	26	OA73	30	TIP35	237	IN4004	08	2N2194A	40	ZN3706	14	ZN5137	18.00
AC176K	28	BC132	14	BC182A	12	BC214C	20	BCY85	30	BF346	32	OA7	14	TIP35A	261	IN4005	09	2N2218	30	ZN3707	14	ZN5142	16.00
AC187	22	BC134	14	BC182B	12	BC214D	18	BCY86	30	BF347	26	OA81	30	TIP35B	280	IN4006	10	2N2218A	33	ZN3708	11	ZN5143	16.00
AC187K	27	BC135	14	BC182L	11	BC214E	16	BCY87	30	BF348	26	OA81	30	TIP35C	320	IN4007	11	2N2219	30	ZN3709	15	ZN5163	34.00
AC188	20	BC136	16	BC182LA	11	BC214F	12	BCY88	30	BF349	25	OA85	30	TIP36	302	IN4009	06	2N2219A	33	ZN3710	11	ZN5172	16.00
AC188K	27	BC137	16	BC183	10	BC214G	12	BCY89	30	BF350	25	OA85	30	TIP36A	363	IN4148	06	2N2220	20	ZN3711	11	ZN5294	50.00
AD149	70	BC138	28	BC183A	10	BC214H	15	BCY90	30	BF351	25	OA85	30	TIP36B	363	IN4149	08	2N2221	20	ZN3712	20	ZN5296	50.00
AD161	92	BC139	35	BC183B	10	BC214I	15	BCY91	30	BF352	25	OA85	30	TIP36C	410	IN4149	08	2N2221A	21	ZN3712A	21	ZN5298	50.00
AD162	80	BC140	30	BC183C	10	BC214J	15	BCY92	30	BF353	25	OA85	30	TIP36D	410	IN4149	08	2N2222	20	ZN3713	310	ZN5401	52.00
AF114	24	BC141	32	BC183L	10	BC214K	15	BCY93	30	BF354	25	OA85	30	TIP36E	410	IN4149	08	2N2222A	20	ZN3714	310	ZN5402	40.00
AF115	24	BC142	22	BC183M	10	BC214L	15	BCY94	30	BF355	25	OA85	30	TIP36F	410	IN4149	08	2N2223	20	ZN3715	310	ZN5403	40.00
AF116	24	BC143	28	BC183N	10	BC214M	15	BCY95	30	BF356	25	OA85	30	TIP36G	410	IN4149	08	2N2224	20	ZN3716	310	ZN5404	40.00
AF117	24	BC144	12	BC183O	10	BC214N	15	BCY96	30	BF357	25	OA85	30	TIP36H	410	IN4149	08	2N2225	20	ZN3717	310	ZN5405	40.00
AF118	20	BC147A	10	BC183P	10	BC214O	15	BCY97	30	BF358	25	OA85	30	TIP36I	410	IN4149	08	2N2226	20	ZN3718	310	ZN5406	40.00
AF124	30	BC147B	11	BC184	11	BC214P	15	BCY98	30	BF359	25	OA85	30	TIP36J	410	IN4149	08	2N2227	20	ZN3719	310	ZN5407	40.00
AF125	30	BC148	08	BC184A	12	BC214Q	15	BCY99	30	BF360	25	OA85	30	TIP36K	410	IN4149	08	2N2228	20	ZN3720	310	ZN5408	40.00
AF126	28	BC148A	09	BC184B	12	BC214R	15	BCY00	30	BF361	25	OA85	30	TIP36L	410	IN4149	08	2N2229	20	ZN3721	310	ZN5409	40.00
AF127	28	BC148B	09	BC184C	12	BC214S	15	BCY01	30	BF362	25	OA85	30	TIP36M	410	IN4149	08	2N2230	20	ZN3722	310	ZN5410	40.00
AF139	34	BC148C	09	BC184D	12	BC214T	15	BCY02	30	BF363	25	OA85	30	TIP36N	410	IN4149	08	2N2231	20	ZN3723	310	ZN5411	40.00
AF178	120	BC149	10	BC184E	12	BC214U	15	BCY03	30	BF364	25	OA85	30	TIP36O	410	IN4149	08	2N2232	20	ZN3724	310	ZN5412	40.00
AF179	120	BC149B	12	BC186	25	BC214V	15	BCY04	30	BF365	25	OA85	30	TIP36P	410	IN4149	08	2N2233	20	ZN3725	310	ZN5413	40.00
AF180	120	BC149C	12	BC187	26	BC214W	15	BCY05	30	BF366	25	OA85	30	TIP36Q	410	IN4149	08	2N2234	20	ZN3726	310	ZN5414	40.00
AF181	120	BC153	18	BC204	15	BC214X	15	BCY06	30	BF367	25	OA85	30	TIP36R	410	IN4149	08	2N2235	20	ZN3727	310	ZN5415	

RETURN OF POST MAIL ORDER SERVICE

BSR HI-FI AUTOCHANGER STEREO AND MONO £11.95 Post 75p
Plays 12", 10" or 7" records, Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2" x 11 1/4". 3 speeds. Above motor board 3 3/4". Below motor board 2 1/2". With STEREO and MONO CARTRIDGE. B.S.R. SINGLE PLAYER similar to above with stereo cartridge and cueing device. Large turntable £13.50. B.S.R. P128 with magnetic cartridge. Balanced arm cueing device £24.50. Post £1



PORTABLE PLAYER CABINET
Modern design. Rexine covered. Vynair front grille. Chrome fittings. Size 17 x 15 x 8in. approx. £4.50 Post 75p
Motor board cut for BSR or Garrard deck

HEAVY METAL PLINTHS £6.50 Post £1.50
With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A" Size 12 1/2 x 14 3/4 x 7 1/2 in. Model "B" Size 16 x 13 3/4 x 7 in. £7.50.
Extra large plinth & cover, teak wood base. Size 20" x 17 1/2" x 9" £19.50. Call's only.

COMPLETE STEREO SYSTEM
Two full size loudspeakers 13 1/2 x 10 x 3 3/4 in. Player unit clips to loudspeakers making it extremely compact. overall size only 13 1/2 x 10 x 8 1/2 in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. Attractive Teak finish. 240V a.c. mains £22.50
£1 carriage



SMITH'S CLOCKWORK 15 AMP TIME SWITCH
0-6 HOURS £3.30 Post 35p
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new and fully guaranteed.



TEAKWOOD LOUDSPEAKER GRILLES will easily fit to baffle board. Size 10 1/2 x 7 1/2 in. £4.5p.

R.C.S. "MINOR" 10 watt AMPLIFIER KIT
This kit is suitable for record players, guitars, tape playback, electronic instruments or small P.A. systems. Two versions available. Mono £11.25; Stereo £18. Post 45p. Specification 10W per channel, input 100mV, size 9 1/2 x 3 x 2 in. approx. S.A.E. details. Full instructions supplied. AC mains powered.

VOLUME CONTROLS
5K-1 to 2M-1 LOG or LIN L/S 35p, D.P. 60p, STEREO L/S 85p, D.P. £1. Edge 5K S.P. Transistor 45p.

80 Ohm Coax 8p yd. STANDARD TYPE VHF. FRINGE LOW LOSS 15p yd. Ideal 625 and colour PLUGS 10p. SOCKETS 10p. LINE SOCKETS 18p. OUTLET BOXES 50p.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Will control up to 500 watts AC mains £3.25 Post 35p

STEREO PRE-AMP KIT. All parts to build this pre-amp 3 inputs for high, medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2.95 Post 35p

E.M.I. 1 1/2" x 8in. SPEAKER SALE!
With tweeter and crossover 10 watt State 3 or 8 ohm As illustrated. £5.95 Post 45p
Ditto 15 watts, 8 ohm £8.50 Post 65p

With tweeter and crossover 20 watt Bass res. 25 c.p.s. Flux=11 000 gauss Post 75p 4 or 8 or 15 ohm. 20 to 20 000 c.p.s. £9.50

Bookshelf Cabinet £7.50 Post £1.00
Teak finish. For EMI 1 1/2 x 8 speakers.

THE "INSTANT" BULK TAPE ERASER AND HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. Will also demagnetise small tools. £4.50 Post 50p



BLANK ALUMINIUM CHASSIS. 6 x 4-70p; 8 x 6-90p; 10 x 7-£1.15; 12 x 8-£1.35; 14 x 9-£1.50; 16 x 6-£1.45; 16 x 10-£1.70. ANGLE ALI. 6 x 3/4 x 3/4 in-15p.

ALUMINIUM PANELS. 6 x 4-17p; 8 x 6-24p; 14 x 3-25p; 10 x 7-35p; 12 x 8-43p; 12 x 5-30p; 16 x 6-43p; 14 x 9-52p; 12 x 12-68p; 16 x 10-75p.

MANY ALI BOXES IN STOCK. MANY SIZES

ELAC 9 x 5in HI-FI SPEAKER TYPE 59RM £3.45 Post 35p
This famous unit now available, 10 watts 8 ohm.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS
All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available, 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required. £2.95 Post 45p

R.C.S. POWER PACK KIT £3.35 Post 30p
12 VOLT, 750mA. Complete with printed circuit board and assembly instructions.

12 VOLT 300mA KIT, £3.15. 9 VOLT 1 AMP KIT, £3.35.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER - BRITISH MADE
Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with battery 9-12V or H.T. line 200-300V d.c. operation. Size 1 3/4 x 1 1/4 x 3/4 in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. Full instructions supplied. Details S.A.E. £1.45 Post 30p

ELECTRO MAGNETIC PENDULUM MECHANISM
1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc. £9.5p Post 30p

MAINS TRANSFORMERS ALL POST 50p

250.0-250V 70mA, 6.5V, 2A	£3.45
250.0-250 80mA, 6.3V 3.5A, 6.3V 1A or 5V 2A	£4.60
350.0-350 80mA, 6.3V 3.5A, 6.3V 1A or 5V 2A	£5.80
300.0-300V 120mA, 2 x 6.3V 2A C.T., 6.3V 2A	£7.00
220V 45mA, 6.3V 2A	£1.75
HEATED TRANS. 6.3V 1/2 amp £1; 3 amp £1.40	

GENERAL PURPOSE LOW VOLTAGE Tapped outputs at 2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £4.60. 1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4.60. 2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8.70. 5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11.25. 6.06V 500mA £1, 9V 1 amp £1, 12V 300mA £1, 12V 500mA £1, 12V 750mA £1, 10V, 30V 40V 2 amp £2.75, 20V, 3 amp £2.45, 40V, 2 amp £2.95, 30V 5A and 34V 2ACT £3.45, 0, 5, 8, 10, 16V, 1/2 amp. £1.95, 20V 1/2 amp. £1.75, 20V, 1 amp. £2.20, 20V 3 amp. £2.50, 20-0-20V 1 amp. £2.95, 30V 1/2 amp. £2.75; 20V, 40V, 60V or 20-0-20V 1 amp. £3.50. 30-0-30V 3 Amp £7.

AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £5; 250W £6; 400W £7; 500W £8.

FULL WAVE BRIDGE CHARGER RECTIFIERS 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

CHARGER TRANSFORMERS 1 1/2 amp £2.75; 4 amp £4.60. 12V. 1 1/2A HALF WAVE Selenium Rectifier, 25p.

R.C.S. BOOKSHELF SPEAKERS
13 x 10 x 6 in. 50 to 14,000 cps 8 watts rms 8 ohms £16 pair Post £1.30



KUBA-KOPENHAGEN STEREO



TUNER-AMPLIFIER CHASSIS AM-FM 5+5 WATT
This Continental 4-band radiogram chassis uses first class quality components throughout. Features: Large fascia panel with 7 push buttons for medium, long, short, VHF-FM, AFC, phono, mains on-off 4-rotary controls, tuning, volume, tone, balance. Facia size 17 x 4 1/2 inches. Chassis size 17 x 4 1/2 x 5 1/2 inches. DIN-connector sockets for tape record/playback, loudspeakers, phono pick-up, external FM-AM aerials. Automatic stereo beacon light. Built-in ferrite rod aerial for medium/longwave. A.C. 240V mains. Circuit supplied. Above speakers are suitable. £33.50 Post £1.50

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p; 420/500V £1.30
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 420/500V £1.30.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
3900mF 100V £1.60, 4700mF 63V £1.20.
5000mF 6V 25p; 12V 42p; 35V 85p.

MANY OTHER ELECTROLYTICS IN STOCK

SHORT WAVE 100pF air spaced gangable tuner, 95p.
TRIMMERS 10pF 30pF 50pF 5p, 100pF 150pF 15p.
CERAMIC, 1pF to 0.01mF, 5p. Silver Mica 2 to 5000pF 5p.
PAPER 350V-0 17p; 0.5 13p; 1mF 150V 20p; 2mF 150V 20p; 500V-0 001 to 0.05 5p; 0.1 10p; 0.25 13p; 0.47 25p.
MICRO SWITCH SINGLE POLE CHANGEOVER 20p.
SUB-MIN MICRO SWITCH, 25p. Single pole change over.
TWIN GANG, 385 + 385pF 50p; 500pF standard 75p; 365 + 365 + 25 + 25pF. Slow motion drive 65p.
120pF TWIN GANG, 50p; 365pF TWIN GANG, 50p.
NEON PANEL INDICATORS 250V. Amber or red 30p.
RESISTORS, 1/4W, 1/2W 1W 20% 2p; 2W, 10p; 10W, 10p to 10M HIGH STABILITY. 1/2W 2% 10 ohms to 6 meg., 12p.
DIRE 5% Preferred values 10 ohms to 10 meg., 5p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 12p each.
TAG STRIP 28-way 12p.
TAPE OSCILLATOR COIL, Valve type, 35p.
BRIDGE RECTIFIER 200V PIV 1/2 amp 50p.
TOGGLE SWITCHES S.P. 20p, D.P.S.T. 25p, D.P.D.T. 30p.
MANY OTHER TOGGLES IN STOCK
PICK-UP CARTRIDGES ACOS GP91 £1.50, GP93 £2.50.
SONOTONE stereo £2.00, SHURE M75 FCS £8.

BAKER MAJOR 12" £14.95 Post £1.00
30-14,500 c/s, 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance, 40 c/s. Rated 25W. NOTE: 4 or 8 or 16 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. Post £1.60p each. Please state 3 or 8 or 15 ohms. £18.95

BAKER "BIG-SOUND" SPEAKERS. Post £1.00 each

Group 25" 12in	Group 35" 12in	Group 50/15" 15in
30W £11.95	40W £13.95	75W £24.95
4 or 8 or 16 ohm	4 or 8 or 16 ohm	8 or 16 ohm

BAKER LOUDSPEAKER, 12 INCH. 60 WATT. GROUP 50/12, 8 OR 15 OHM HIGH POWER.
FULL RANGE PROFESSIONAL QUALITY RESPONSE 30-16,000 CPS £20.95 Post £1.60
MASSIVE CERAMIC MAGNET WITH ALUMINIUM PRESENCE CENTRE DOME.

TEAK VENEERED HI-FI SPEAKERS AND CABINETS
For 12in or 10in speaker 20x13x12in £14.50 Post £2.
For 13x8in. or 8in. speaker £8.50 Post £1.
For 6 1/2in. speaker and tweeter 12x8x6in £5.80 Post 75p
Many other cabinets in stock. Phone your requirements.

R.C.S. 100 watt VALVE AMPLIFIER CHASSIS
Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A. where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output socket. Produced by demand for a quality valve amplifier. 100V line output to order. Send for leaflet. Suitable carrying cab £14. Price £85 carr. £2.50



SPEAKER COVERING MATERIALS. Samples Large S.A.E.
LOUDSPEAKER CABINET WADDING 18in. wide 20p ft. Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £3.60
De Luxe Horn Tweeters 3-18kc/s, 30W, 8 ohm, £7.50.
CROSSOVERS. TWO-WAY 3000 c/s 3 or 8 or 15 ohm £1.90. 3-way 950 cps/3000 cps £2.20.
LOUDSPEAKERS P.M. 3 OHM 7x4in. £1.50; 6 1/2in., £1.80; 8x5in., £1.90; 8in., £1.95.

SPECIAL OFFER: 80 ohm, 2 1/4in., 2 1/4in., 35 ohm, 3in., 25 ohm, 2 1/2in., 3in., 5x3in., 2x4in., 8 ohm, 2 1/2in., 3in., 3 1/2in., 5in., 15 ohm, 3 1/2in., dia. 6x4in., 7x4in., 5x3in., 3 ohm, 2 1/2in., 2 1/2in., 3 1/2in., 5in. dia. £1.25 each.
PHILIPS LOUDSPEAKER, 8in., 4 ohms, 4 watts, £1.95
RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8in. diameter 4W £2.50, 10in. diameter 5W £2.95; 12in. diameter 6W £3.50. 3/8"/15 ohms, please state.
PIEZO ELECTRIC HORN TWEETER. Handles up to 100 watts. No crossover required £9.95.

Tweeter Volume Control 15 ohms 10W with one inch long threaded bush for wood panel mounting. 1/2in. spindle. 65p.

BAKER 150 WATT PROFESSIONAL MIXER AMPLIFIER
All purpose transistorised. Ideal for Groups, Disco and PA. 4 inputs speech and music. 4 way mixing. Output 4/8/16 ohms a.c. Mains. Separate treble and bass controls. Master volume control. Guaranteed. Details S.A.E. £68 £1.50 carr.
NEW MODEL MAJOR-50 watt, 4 input, 2 vol. Treble and bass. Ideal disco amplifier. £49 Carr £1



100 WATT DISCO AMPLIFIER
volume, treble, bass controls. 500 M.V. or 1 volt input. Four loudspeaker outputs 4 to 16 ohm. All transistor £59

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER
Add musical highlights and sound effects to recordings. Will mix Microphone records, tape and tuner with separate controls into single output. 9V. £6.95

TWO STEREO CHANNEL VERSION £8.95
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready Built, with volume, Treble and bass controls. 18 volt d.c. Mains Power Pack £3.45

ALUMINIUM HEAT SINKS. FINNED TYPE. Sizes 6 1/2" x 4 1/2" x 2 1/4" 95p. 6 1/2" x 2" x 2 1/4" 65p.
BALANCED TWIN RIBBON FEEDER 300 ohms. 5p yd.
JACK SOCKET STD. open-circuit 20p, closed circuit 25p; Chrome Lead-Socket 45p. Mono or Stereo.
Phono Plugs 8p. Phono Socket 8p.
JACK PLUGS Std. Chrome 30p; Plastic 25p; 3.5mm 15p.
STEREO JACK PLUG 30p. SOCKET 25p.
DIN SOCKETS Chassis 3-pin 10p. 5-pin 10p.
DIN SOCKETS FREE 3-pin 25p; 5-pin 25p. DIN PLUGS 3-pin 25p; 5-pin 25p. VALVE HOLDERS, 10p; CANS 10p.
TV CONVERGENCE POTS 15p Each
Valves = 5, 7, 10, 20, 50, 100, 200, 250, 470, 2000 ohms


R.C.S. SOUND TO LIGHT KIT
Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. £14. Post 35p. Easy to build. Full instructions supplied. Cabinet £3.

PERIOD LOUDSPEAKER CABINETS. Two styles available, Regency and Queen Anne. Size approximately 34 x 19 x 16in. These cabinets are slightly soiled and are priced from £10 each. Callers only.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON
Radio Books and Components Lists 20p. (Minimum posting charge 30p.) All prices include VAT. (We accept Access or Barclaycard. Phone your Order) Tel. 01-684 1665

TEAC

TEAC A3340(S)
4-CHANNEL
RECORDER

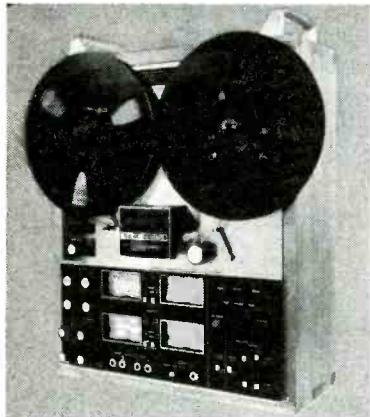


Industrial version upgraded to studio requirements, with increased signal to noise performance and improved reliability. Four totally independent channels each with sel sync, input mixing, switchable VU's and all the facilities for easy multitracking. This industrial model is in more studios than any other version.

Available only from ITA
(Semi-pro version also available)
IMMEDIATE DELIVERY

REVOX

REVOX A-700 SERIES

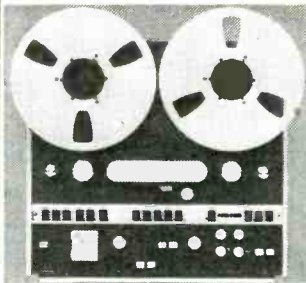

The new big Revox — ideal for all studio requirements. Highly sophisticated design features include servo tape tension, full deck logic, crystal controlled servo electronics, 3 speeds, tape footage counter.

BEST PRICES!

The famous A77 has been consistently improved over the past 8 years and is now available in the latest Mk. 4 version.

The wide choice of specifications includes versions for duplicating and logging applications. Backed by UK's latest fastest service.

A-77 SERIES Mk 4



Hire service. Check our prices

BEST PRICES!

ITA

ITA 10-4
MODULAR MIXER



Ten balanced inputs, four output groups, 4 limiters, bass mid and treble EQ, modular construction, headphone monitoring. Extremely high quality construction only matched by mixers costing around £1,000.

10-4 **£690**

20-4 **£1190**

EIGHT OUTPUT £1360

IMMEDIATE DELIVERY

Also available for hire

PRICES EXCLUSIVE OF V.A.T.

Industrial Tape Applications



1-7 Harewood Avenue, Marylebone Road, London NW1
Telephone: 01-724 2497 Telex: 21879

WW — 095 FOR FURTHER DETAILS


Tune into the world...



The 31st edition of World Radio TV Handbook... the only complete directory of international broadcasting and TV stations... endorsed by UNESCO, Eurovision, Intervision and the world's leading broadcasting organizations. Includes 'Listen to the World', a special editorial section; the latest world time charts and tables; with comprehensive coverage of short-wave, long-wave and medium-wave.

The essential guide to anyone associated with broadcasting or television... national or international, professional or amateur DX-er.

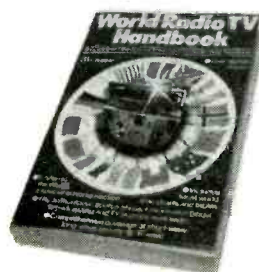Copies at £5 each can be obtained from Argus Books Limited, Station Road, Kings Langley, Herts.



Please send me _____ copies of World Radio TV Handbook at £5 each. I enclose a cheque for £ _____

NAME _____

ADDRESS _____

VALVES

Table of vacuum tube valves with columns for part numbers and prices. Includes types like A1065, ARB, ARP3, etc.

PLUMBICON TUBES TYPE XO 1071 Mullard. Table listing various tube types like PY80, PY81, PY82, etc., with prices.

COLOMOR THE VALVE WITH A GUARANTEE. Advertisement for Colomor valves with a list of types and prices.

VIDEON TUBE TYPE P 863 B English Electric

TRANSISTORS 12 1/2 % Please add VAT 12 1/2 % for valves, etc.

Table of transistors with columns for part numbers and prices. Includes types like AA212, AF125, BC172A, etc.

COLOMOR (ELECTRONICS LTD.) 170 Goldhawk Rd., London, W.12. Tel. 01-743 0899. Open Monday to Friday 9-12.30, 1.30-5.30 p.m.

UHF POWER GENERATORS

TYPE SLR0 from 275 to 2750 mc/s. Maximum output from 275 to 500 Mc greater than 6W. From 500 to 1700 Mc greater than 20W Modulation AM 1000c/s depth to 100%.

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc. retail 749 3934, trade and export 743 0899. VAT FOR TEST EQUIPMENT 8% PLEASE ADD 8%

OTHERS IN STOCK inc. integrated circuits, CRT & special valves. Min. Mail Order £1. UK POSTAGE £1. £2 20p. £2-£3 30p. £3-£5 40p. Over £5 free Casual callers welcome.

E.H. RESEARCH LABORATORIES INC. MODEL 133A PULSE GENERATOR. Features Ultra-linear ramp rise and fall independently variable 50v output into 50 ohms.

FOR EXPORT ONLY RCA ET4336, 2 Mc/s-20Mc/s, 350W also modified version of increased output 1000W Collins 231D 4.5 kW, 3 MHz-24 MHz 10 channel Auto. or manual tuning.

OVER 300,000 IN STOCK! MULTIWAY AND R.F. CONNECTORS BY PRACTICALLY ALL U.K. AND OVERSEAS MANUFACTURERS. ANALYTICAL EQUIPMENT GAS CHROMATOGRAPHY RESEARCH OVEN PV4051/4056 (other GC items in stock). IONISATION AMPLIFIER PV4075. STAINLESS STEEL VACUUM CONTAINERS FOR LIQUIDS. AIRCREW CHRONOGRAPHS. Tantalum Capacitors (KEMET, ITT, PLESSEY, ETC.). SYNCHROS AND SERVO MOTORS EX STOCK. SPECIALIST STOCKISTS OF SERVO MOTORS, SYNCHROS, TEST EQUIPMENT, METERS AND CONNECTORS. Servo and Electronic Sales Ltd. (Established 1953) 24 HIGH ST., LYOOD, KENT. Tel. Lydd 20252 (STO 0679) VAT No. 201-1296-23 TELEX 965265 ALL PRICES INCLUDE CARR. + VAT EXCEPT WHERE STATED. WWW - 089 FOR FURTHER DETAILS

SINTEL FOR THE ZILOG Z80 KITS AND FAST SERVICE

SINTEL INDUSTRIAL MODULE KITS

Using only the highest quality components — Fibreglass roller-tinned PCBs — ICs and Displays direct from 'Blue-chip' Manufacturers.

KITS FOR TTL LATCHED COUNTER MODULES

Each kit includes a set of displays (0.5" Red LED type TIL321/FND507) and two PCBs, one each per digit of 7447, 7475 and 7480, plus brackets, resistors, capacitors, a single in-line plug and socket, nuts, screws, washers, instructions, etc. Sockets are NOT included and we recommend that you order Soldercon Pins separately (112 for a 2 digit module, 224 for a 4 digit module and 336 for a 6 digit module). Each module consists of one vertical PCB holding the displays, fixed by two brackets to a horizontal PCB, which holds the remaining components.

- Full Kit for 2 digit TTL Counter with Latch Order as **526-412** £10.52
- Full Kit for 4 digit TTL Counter with Latch Order as **657-412** £17.98
- Full Kit for 6 digit TTL Counter with Latch Order as **721-412** £25.86



KITS FOR CMOS LATCHED COUNTER MODULES

Similar to the TTL kits above but using 0.5" common cathode LEDs, two 4511 and one 4518 CMOS ICs for each pair of digits.

- Full kit for 2 digit CMOS Counter with Latch Order as **588-470** £10.42
- Full kit for 4 digit CMOS Counter with Latch Order as **659-470** £18.11
- Full kit for 6 digit CMOS Counter with Latch Order as **191-470** £25.85

PCBs used in our TTL Latched Counter Modules are also available separately including brackets, layout, circuit and instructions.

- 2 digit TTL Counter PCB Set Order as **915-950** £2.97
- 4 digit TTL Counter PCB Set Order as **246-950** £4.53
- 6 digit TTL Counter PCB Set Order as **610-950** £6.16

For other items from this range available separately, please send for FREE Catalogue.

KIT FOR SINGLE PCB CMOS COUNTER MODULE WITH LATCH

Order as **142-269** £8.60

SETS OF JUMBO DISPLAYS WITH DISPLAY HOLDING PCB

Each kit consists of the appropriate number of 0.5" red LED displays (either common anode TIL321/FND507s or common cathode TIL322/FND500s) and a display holding PCB. OPTIONS: PCBs wired for multiplexing or non-multiplexing, clock format or counter format.

TYPE	COMMON ANODE Part No.	Price	COMMON CATHODE Part No.	Price
Non-Multiplexed	2 digit Counter	574-822 £3.37	446-822 £2.97	
	4 digit Counter	777-822 £6.63	128-822 £5.83	
	6 digit Counter	684-822 £9.89	271-822 £8.69	
Multiplexed	4 digit Clock	801-822 £8.66	262-822 £5.86	
	6 digit Clock	417-822 £10.15	452-822 £8.95	
	8 digit Counter	719-822 £13.09	515-822 £11.49	

LOW COST SOLDERCON IC SOCKETS

100 pins for 50p, 1,000 pins for £4, 3,000 pins for £10.50.

COMPONENTS Send for Catalogue

CLOCK CHIPS	MPUs	VEROPINS	CD4020	1.28	CD4047	1.04	CD4085	0.74
AY51202 3.10	6800 24.84	(c.200)	CD4021	1.04	CD4948	0.58	CD4086	0.74
AY51224 3.50	SC/MP CPU	Veropins-Pkt. 1.18	CD4022	0.94	CD4049	0.58	CD4089	1.60
MK50253 5.60	ISPBA/5000 14.50		CD4023	0.23	CD4050	0.58	CD4093	0.92
			CD4024	0.80	CD4051	0.94	CD4094	1.94
			CD4025	0.23	CD4052	0.94	CD4095	1.08
			CD4026	1.78	CD4053	0.94	CD4096	1.08
			CD4027	0.58	CD4054	1.20	CD4097	3.85
			CD4028	0.92	CD4055	1.36	CD4098	1.13
			CD4029	1.18	CD4056	1.36	CD4099	1.90
			CD4030	0.58	CD4059	4.93	CD4502	1.24
			CD4031	2.30	CD4060	1.15	CD4510	1.41
			CD4032	1.02	CD4063	1.13	CD4511	1.72
			CD4033	1.44	CD4066	0.63	CD4514	2.84
			CD4034	1.97	CD4067	3.85	CD4515	3.24
			CD4035	1.22	CD4068	0.23	CD4516	1.40
			CD4036	3.29	CD4069	0.23	CD4518	1.25
			CD4037	0.98	CD4070	0.51	CD4520	1.19
			CD4038	1.10	CD4071	0.23	CD4527	1.64
			CD4039	3.20	CD4072	0.23	CD4532	1.39
			CD4040	1.11	CD4073	0.23	CD4555	0.90
			CD4041	0.86	CD4075	0.23	CD4556	0.90
			CD4042	0.86	CD4076	1.34	MC14528	1.22
			CD4043	1.01	CD4077	0.45	MC14553	4.68
			CD4044	0.96	CD4078	0.23	IM6508	8.05
			CD4045	1.45	CD4081	0.23		
			CD4046	1.37	CD4082	0.23		

CMOS

Mainly RCA

Some of the Books available from Sintel
 RCA CMOS and Linear IC Databook 6.70
 National Semiconductor Databook 3.45
 MOT CMOS Databook Vol. 5 Series B 3.50

Offices at Link Property, 209 Cowley Road, Oxford, but please do not use this as a postal address.

ORDERS: C.W.O. add VAT @ 8% + 25p P&P. TELEPHONE and CREDIT (Invoice) Orders add VAT @ 8% + 50p P&P, and please see "FAST SERVICE". EXPORT Orders (min. £10) welcome, no VAT but add 10% (Europe), 15% (Overseas) for Air Mail P&P. For Export postage rates on heavy items — contact us first.



SEND YOUR ORDER TO: SINTEL PO BOX 75C, OXFORD Tel. 0865 49791

SINTEL CHOOSES THE ZILOG Z80

COMING IN A FEW MONTHS
A COMPUTER USING THE Z80
 In kit form and ready-built
 We think it's worth waiting for

Sintel offers you the world's most advanced 8-bit microprocessor, designed by the team who created the 8080. The Z80 is manufactured by Zilog (backed by Exxon, the world's largest corporation) and by Mostek — the world's leading memory manufacturer.

- Here are some features that will warm the expert's heart
- 158 instructions, including all 78 of the 8080A
 - Automatic dynamic RAM refresh
 - Superb set of addressing modes
 - 4-bit rotates for BCD multiplication
 - Loop counting and exit with single instruction
 - Great interrupt handling
 - 12 general purpose registers

- Single +5V power supply
- Static operation
- Single, simple clock
- 1.6 sec cycle time
- Block mode instruction
- Two index registers

Z80/ OR MOSTEK MK3880 FROM SINTEL ONLY £29.50

Send in your name and address to go on our Z80 Mailing List

- Zilog Z80 data already available from SINTEL
- Zilog Z80 — CPU Technical Manual c.80 pages £5.60
- Zilog Z80 — CTC Product Specification (Four channel programmable Counter Timer Circuit) c.7 pages £0.80
- Zilog Z80 — P10 Technical Manual (Programmable two port input output device) c.25 pages £3.30
- Zilog Z80 Datasheet £0.75

HIGH QUALITY KITS



ACK £27.80

ATTRACTIVE SIX DIGIT ALARM CLOCK KIT

Six red 0.5" digits • White case • Touch switch snooze • Battery backup • Crystal timebase plus other features • Size: h. 40mm, w. 205mm, d. 140mm • Complete less mains cable, plug and battery.
 Order as **ACK + XTK** £34.33
 Available without crystal control and battery backup, which can be added later.
 Order as **ACK** £27.80

FOUR DIGIT MANTLEPIECE OR OFFICE CLOCK

Four bright green 0.5" digits • White Case • Battery backup • Crystal control • Size: h. 40mm, w. 154mm, d. 85mm • Complete less mains cable, plug and battery.
 Order as **GCK + GBBK + XTK** £19.65
 Available without crystal control and battery backup.
 Order as **GCK** £14.40



SIX DIGIT CAR CLOCK WITH INDEPENDENT JOURNEY-TIMER

Crystal controlled • Shows time or elapsed time in hrs, mins, secs • Runs off car 12v supply • NINE PUSH BUTTONS FOR Start-Stop-Reset, selecting display to show time or elapsed time • All controls functional irrespective of display mode • Size: h. 40mm, w. 205mm, d. 140mm.
 Order as **CKK** £42.00



FOUR DIGIT CAR CLOCK

Four red 0.5" digits • White case • Battery backup • Crystal control • Suitable for all 12v negative earth cars • Size: h. 40mm, w. 154mm, d. 85mm • Complete less battery.
 Order as **AUT-CK** £17.85



50HZ CRYSTAL TIMEBASE KIT

Use to improve accuracy of your digital clock • As a 50Hz source in a clock with battery backup • Accurate to within a few seconds a month • Size: h. 14mm, w. 64mm, d. 49mm.
 Order as **XTK** £6.28



FAST SERVICE. We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Monday-Friday) will be despatched on the same day by 1st class post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value of £5. Official orders, no minimum.

CATRONICS FREQUENCY COUNTERS

Without doubt the best performance / price ratio available

CATRONICS DMF5
 10Hz to 250 MHz



TCXO VERSION ALSO available. For laboratory use and others requiring a precision reference oscillator, a special high stability version is available using a temperature controlled crystal oven oscillator.
 Frequency stability is better than ± 1 ppm over the temperature range to +60°C after a 5 minute warm up period.

PRICE ONLY £177.50 + VAT

- Full 7 digit U-35" amber display
- IC memory giving a "non-blinking" display
- Automatic suppressed zeros on 3 leading digits to reduce power consumption
- TTL and ECL i.c.s. used to give a high degree of reliability
- 10MHz master oscillator for high accuracy
- 12V (-ve earth) dc input and 210-260V mains pu fitted

PRICE ONLY £137.50 + VAT



CATRONICS LTD (Dept 727)

Communications House, 20 Wallington Square, Wallington, Surrey, Tel: 01-669 6700

WW-727 FOR FURTHER DETAILS

TELETEXT DECODERS

by CATRONICS Ltd.

Our kit contains all the printed circuit boards and components necessary to build the complete decoder



PRICES (INCLUDING VAT)	Standard version using 2513	New version with Texas X887	Post & Packing
Set of 5 PCBs	£20.70	£20.65	30p
Component Kit (incl. PCBs)	£122.35	£133.70	£1.50
Add-on Unit for lower case PCB	£2.70	—	—
Component Kit (incl. PCB)	£14.15	—	—
Cabinet	£14.85	£14.85	£1.00

PLATED-THROUGH hole PCBs for TEXAS version only at additional cost of £27.00
 A reprint of the series of articles is available at £1.50 + large 14p SAE (including free in complete kit)

COMPONENTS ALSO AVAILABLE SEPARATELY — SAE for price list
 READY BUILT & TESTED DECODERS £241.87 + £5 Carr.

STOP PRESS

MATRIX H DECODER

Kits available for Matrix H Decoder Design as featured in last month's "Wireless World" — send SAE for details

Are you receiving us? NEW Doram
**DIGITAL FREQUENCY
 METER YOURS FOR ONLY**
£54.50 + £4.36 VAT



The DFM you must have at a price that could save you up to £25. It's easy to see how accurate this new Doram meter is thanks to 4 digit display with extra shift left to check 5 digits for even greater accuracy!

You can see the well-designed shatterproof case with its built-in handle/display tilt-foot looks so much more expensive than many a kit product.

But Doram kits always give you the best for less. This complete kit with case, printed circuit boards, all components and instructions is yours for only £54.50 + £4.36 VAT.

KEY DATA

Frequency range	20Hz to 50MHz in 3 steps
Sensitivity	20mV r.m.s.
Input Impedance	1M Ω in parallel with 30pF
Input Coupling	AC
Maximum Input	10V r.m.s.
Frequency Standard	1MHz, .001% calibration tolerance
Display	4 Digit LED display with shift left for 5 digit readout
Accuracy	± 1 digit (.01%)
Supply Voltage	220-240V ac with 12V dc 100mA output for prescaler supply

The meter covers 20Hz to 50MHz with prescaler (additional purchase) provision allowing you to measure up to 500MHz. Input impedance and sensitivity are very high with read-out accurate to $\pm 0.01\%$!

So the message comes through loud and clear—don't miss this latest Doram digital bargain.

DEPEND ON DORAM

Thousands of kit makers do for top value and modern technology. Doram Electronics Ltd, PO Box TR8, Wellington Road Industrial Estate, Wellington Bridge, Leeds, West Yorkshire LS12 2UF.
 Registered in London No. 1155856. Directors: R. A. Maier, D. I. Turner, F. Chabale.

Yes, I want to save up to £25

Please send me (subject to availability) complete kit(s) for DORAM DIGITAL FREQUENCY METER at (£54.50 + £4.36 VAT inc p & p) total £58.86. I understand I can return unused kit(s) within 7 days and claim my money back if kit(s) returned in the form received and ready for re-sale.

Please send me complete DORAM KITS CATALOGUE(s) showing an additional 25 kits at 25p each. I enclose cheque/PO value.

NAME (BLOCK CAPITALS) _____

ADDRESS _____

TOWN _____

COUNTY _____

POST TO: DORAM ELECTRONICS LTD., DEPT. WF2, PO BOX TR8, LEEDS, WEST YORKSHIRE LS12 2UF

SURROUND SOUND KITS



Demodulator TDM29
 A new JVC design with improved muting.

Type A Variatrix
 Decoder Synthesizer
 (with or without SQ Option).

Decoder
 Type 3A
 Type 5A

PRICE LIST (VAT in brackets; overseas customers neglect)

CD4	Complete kit	£35.00+	(£4.38)
	PCB ICS; and coils only	£18.00+	(£2.25)
QS	Variatrix Decoder Kit	£32.00+	(£4.00)
	*As above but with SQ option	£36.00+	(£4.50)
SQ	Type L3A Kit	£26.50+	(£3.31)
	Type L5A Kit	£31.50+	(£3.94)
	PCBs (for both types)	£6.90+	(£0.86)
	Master Switch Kit	£9.50+	(£1.19)
	4 Gang Potentiometer	£2.00+	(£0.25)

(Overseas Airmail £4 per kit)

For details send SAE to

COMPOR ELECTRONICS LIMITED
 9 DELL WAY, LONDON W13 8JH. Telephone 01-998 8221

WW—041 FOR FURTHER DETAILS

INJECTION AND COMPRESSION MOULDING TO YOUR REQUIREMENTS ALSO INDELIBLE PRINTING OF G.R.P. ALUMINIUM AND COATED PANELS. GLASS FIBRE CASES. D.M.C. OR S.M.C. GREY, BUT OTHER COLOURS BY ARRANGEMENT.

SIZES	BOX	WITH
	ALONE	ADDITION*
8"x5 1/2"x5"	£1.94	£2.71
9"x4"x3"	£1.30	£2.07
6"x4"x4"	£1.10	£1.96
5"x3"x1 1/2"	£0.51	
4"x4"x1 1/2"	£0.54	

Plus VAT and carriage

WITH FRONT PANEL, INSIDE PANEL (BOTH ALUMINIUM) AND 4 RUBBER FEET

TRADE PRICES ON REQUEST

Polythene Bags to your requirement, Dept. DP

THOMAS MAUGHAN & ASSOCIATES
 (DEPT. AW)

CLARENCE MILL, BOLLINGTON, NR. MACCLESFIELD, CHESHIRE
 Tel: BOLLINGTON 74294

WW—022 FOR FURTHER DETAILS

TRANSFORMERS

ALL EX-STOCK — SAME-DAY DESPATCH

MAINS ISOLATING VAT 8% **12 and/or 24-VOLT**

PRI 120/240V SEC 120/240V
 Centre Tapped and Screened

Separate 12v windings
 Primary 220-240 Volts

Ref.	VA (Watts)	£	P&P	Amps		£	P&P	
				12v	24v			
07*	20	4.40	79	111	0.5	0.25	2.20	43
149	60	6.20	96	213	1.0	0.5	2.64	78
150	100	7.13	114	71	2	1	3.41	78
151	200	11.16	150	18	4	2	4.03	96
152	250	12.79	184	70	6	3	5.35	96
153	350	16.28	184	108	8	4	6.98	114
154	500	19.15	215	72	10	5	7.67	114
155	750	29.06	OA	116	12	6	8.99	132
156	1000	37.20	OA	17	16	8	10.38	132
157	1500	45.60	OA	115	20	10	13.18	208
158	2000	54.80	OA	187	30	15	17.05	208
159	3000	79.05	OA	226	60	30	26.82	OA

*115 or 240 sec only

50 VOLT RANGE

Primary 220-240V
 SEC. TAPS 0-19-25-33-40-50V

Ref.	Amps	£	P&P
102	0.5	3.41	78
103	1.0	4.57	96
104	2.0	6.98	114
105	3.0	8.45	132
106	4.0	10.70	150
107	6.0	14.62	164
118	8.0	17.05	208
119	10.0	21.70	OA

30 VOLT RANGE

Primary 220-240V
 SEC. TAPS 0-12-15-20-25-30V

Ref.	Amps	£	P&P
112	0.5	2.64	78
79	1.0	3.57	96
3	2.0	5.27	114
20	3.0	6.20	132
21	4.0	7.44	150
51	5.0	8.37	132
117	6.0	9.92	145
88	8.0	11.73	164
89	10.0	13.33	184

60 VOLT RANGE

Primary 220-240V
 SEC TAPS 0-24-30-40-48-60V

Ref.	Amps	£	P&P
124	0.5	3.88	96
126	1.0	5.58	96
127	2.0	7.60	114
125	3.0	10.54	132
123	4.0	12.23	184
40	5.0	13.95	164
120	6.0	15.66	184
121	8.0	20.15	OA
122	10.0	24.03	OA
189	12.0	27.13	OA

AUTO TRANSFORMERS

Ref.	VA	Watts	TAPS	£	P&P
113	20	0-115-210-240v	2.48	.71	
64	75	0-115-210-240v	3.95	.96	
4	150	0-115-210-220-240v	5.35	.96	
66	300	"	7.75	1.14	
67	500	"	10.99	1.64	
84	1000	"	18.76	2.08	
93	1500	"	23.28	OA	
95	2000	"	34.82	OA	
73	3000	"	48.00	OA	

HIGH VOLTAGE

MAINS ISOLATING

Pri 200/220 or 400/440

Sec 100/120 or 200/240

VA	Ref.	£	P&P
60	243	5.89	1.32
350	247	14.11	1.84
1000	250	35.65	OA
2000	252	54.25	OA

DECS SOLDERLESS BREADBOARDING

S Dec 70 contacts £1.98

T Dec 208 contacts £3.38

U Dec 'A' IC's etc. £3.99

U Dec 'B' IC's etc. £6.99.

VAT 8% P&P 40p

BRIDGE RECTIFIERS

200v	400v	200v	400v	400v	400v	500v
2A	2A	4A	4A	6A	10A*	
55p	55p	65p	80p	£1.00	£2.35	

P&P 29p. VAT 12 1/2%
 *VAT 8%

METERS

AV08	£68.95
AV071	£28.00
AV073	£37.80
AVOMM5	£21.94
WEE MEGGER	£55.05
AVO TT169	£26.00
UA4315	£14.95

Includes steel carry case in-circuits transistor tester
 Avo Cases and Accessories
 P&P £1.50. VAT 8%

TI MINI-MULTIMETER

DC-1000V AC-1000V

AC/DC-1000(V)/V

DC-100mA Res — 150K

Bargain at £5.30

VAT 8% P&P 62p

STEREO F.M. TUNER

4 Pre-selected stations

Switched AFC

Supply 20-35v 90Ma Max

£21.63. P&P 40p. VAT 12 1/2%

MAGNETIC TO CERAMIC CARTRIDGE CONVERTER

Operating Voltage 20/45v

ONLY £2.85 P&P 36p

VAT 12 1/2%

SCREENED MINIATURES Primary 240V

Ref.	mA	Volts	£	P&P
238	200	3-0-3	1.99	.55
212	1A, 1A	0-6-0-6	2.85	.78
13	100	9-0-9	2.14	.38
235	330, 330	0-9-0-9	1.99	.38
207	500, 500	0-8-9-0-8-9	2.59	.71
208	1A, 1A	0-8-9-0-8-9	3.53	.78
236	200, 200	0-15-0-15	1.99	.38
214	300, 300	0-20-0-20	2.56	.78
221	700(DC)	20-12-0-12-20	3.41	.78
206	1A, 1A	0-15-20-0-15-20	4.63	.96
203	500, 500	0-15-27-0-15-27	3.99	.96
204	1A, 1A	0-15-27-0-15-27	5.39	.96
S112	500	0-12-15-20-24-30	2.64	.78

CASED AUTO. TRANSFORMERS

240V cable input USA 2-pin outlets

	20VA	75VA	150VA	300VA	500VA	750VA	1000VA	2000VA
£	£4.96	£6.03	£8.48	£12.53	£15.73	£18.55	£22.68	£37.65
P&P	96	114	114	145	164	176	OA	OA
Ref.	113W	64W	44W	66W	67W	83W	84W	95W

HIGH QUALITY MODULES VAT 12 1/2%

10 watt RMS Amplifier	£3.66
25 watt RMS Amplifier	£4.57
Pre-Amp for 3-5-10w	£6.95
Pre-Amp for 25w	£13.88
Power Supplies for 3-5-10w	£1.35
Power Supplies for 25w	£3.76
Transformer for 5-10w	£2.41
Transformer for 25w (one module)	£4.79
P&P Amps/Pre-Amps/Power Supplies	40p
P&P Transformers	96p

STEREO 30

Complete chassis, inc 7+7w r.m.s. amps, pre-amp, power supply, front panel, knobs (needs mains trans.). £19.05. Mains trans. £2.45. Teak veneered cab. £5.25. P&P £1.02. VAT 12 1/2%

POWER UNITS

CC12-05. 3, 4, 5, 7, 5, 9, 12v 500Ma	£5.29
STABILISED 3, 6, 7.5, 9v at 400Ma	£5.95
3300. 6, 7.5, 9v at 300Ma plugs direct into 13A socket (fused)	£3.30

P&P 70p. VAT 12 1/2%

ANTEX SOLDERING IRONS

15W £3.46. 18W £3.46. 25W £3.20

Soldering iron kit £4.93

Stand for above £1.45. P&P 46p. VAT 8%

PLEASE ADD VAT AFTER P&P

PANEL METERS AND SEMICONDUCTOR

STOCKISTS AUDIO ACCESSORIES & BARGAIN

PAKS SAVE POSTAGE CALLERS WELCOME

(MON-FRI) OR SEND STAMP FOR LISTS

PRICES CORRECT AT 7/4/77


Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

WW-076 FOR FURTHER DETAILS

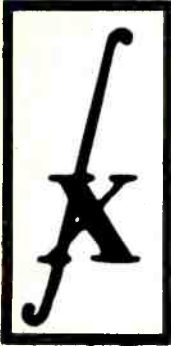

NEW PRODUCTS!

NRDC-AMBISONIC 45J

SURROUND SOUND DECODER

The **first ever** kit specially produced by Integrex for this British NRDC backed surround sound system which is the result of 7 years' research by the Ambisonic team. W.W. July, Aug, and Sept. '77

The unit is designed to decode not only 45J but virtually all other 'quadrophonic' systems (Not CD4), including the new BBC Matrix H 10 input selections.

The decoder is linear throughout and does not rely on listener fatiguing logic enhancement techniques. Both 2 or 3 input signals and 4 or 6 output signals are provided in this most versatile unit.

Complete kit, including licence fee £45.00 + VAT

INTRUDER 1 RADAR ALARM

With Home Office Type approval.

As in this issue of "Wireless World", designed by Mike Hosking, 240V ac mains operated and disguised as a hardbacked book. Detection range up to 30 feet. Complete kit. Exclusive designer approved kit £46.00 + VAT.

Wireless World DolbyTM noise reducer

Trademark of Dolby Laboratories Inc.



Featuring

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

Typical performance

Noise reduction better than 9dB weighted.
Clipping level 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output

Dynamic Range > 90dB

30mV sensitivity.

Complete Kit **PRICE: £39.90 + VAT**

Also available ready built and tested **Price £54.00 + VAT**

Calibration tapes are available for open-reel use and for cassette (specify which) **Price £2.20 + VAT ***

Single channel plug-in DolbyTM PROCESSOR BOARDS (92 x 87mm) with gold plated contacts are available with all components **Price £8.20 + VAT**

Single channel board with selected fet **Price £2.50 + VAT**

Gold Plated edge connector **Price £1.50 + VAT ***

Selected FETs **60p** each + VAT, **100p** + VAT for two, **£1.90** + VAT for four

Please add VAT @ 12½% unless marked thus*, when 8% applies (or current rates)

We guarantee full after-sales technical and servicing facilities on all our kits, have you checked that these services are available from other suppliers?



INTEGREX LTD.

Please send SAE for complete lists and specifications

Portwood Industrial Estate, Church Gresley,

Burton-on-Trent, Staffs DE11 9PT

Burton-on-Trent (0283) 215432 Telex 377106

INTEGREX

S-2020TA STEREO TUNER / AMPLIFIER KIT

SOLID MAHOGANY CABINET

A high-quality push-button FM Varicap Stereo Tuner combined with a 24W r.m.s. per channel Stereo Amplifier.




Brief Spec. Amplifier Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc.), THD less than 0.1% at 20W into 8 ohms. Power on/off FET transient protection. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section uses 3302 FET module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88—104MHz. 30dB mono S/N @ $1.2\mu\text{V}$. THD 0.3%. Pre-decoder 'birdy' filter.

PRICE: £58.95 + VAT

NELSON-JONES STEREO FM TUNER KIT

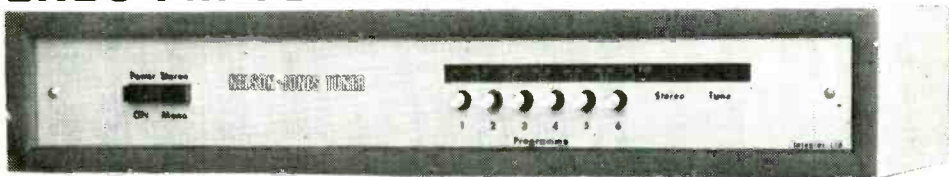A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter/dual IC IF amp.



Brief Spec. Tuning range 88—104MHz. 20dB mono quieting @ $0.75\mu\text{V}$. Image rejection — 70dB. IF rejection — 85dB. THD typically 0.4%.

IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

Compare this spec. with tuners costing twice the price.

Mono £32.40 + VAT

With ICPL Decoder £36.67 + VAT

With Portus-Haywood Decoder

£39.20 + VAT

STEREO MODULE TUNER KIT

A low-cost Stereo Tuner based on the 3302 FET RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC Variable INTERSTATION MUTE. PLL stereo decoder IC. Pre-decoder 'birdy' filter. Push-button tuning

PRICE: Stereo £31.95 + VAT



Sens. 30dB S/N mono @ $1.2\mu\text{V}$

THD typically 0.3%

Tuning range 88—104MHz

LED sig. strength and stereo indicator

S-2020A AMPLIFIER KIT

Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring

Power 'on/off' FET transient protection.



Typ Spec. 24 + 24W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Headphone output. Tape In/Out facility (for noise reduction unit, etc.). Toroidal mains transformer.

PRICE: £33.95 + VAT

ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS

BASIC NELSON-JONES TUNER KIT £14.28 + VAT **PHASE-LOCKED IC DECODER KIT £4.47 + VAT**

BASIC MODULE TUNER KIT (stereo) £16.75 + VAT **PUSH-BUTTON UNIT £5.00 + VAT**

PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER KIT £8.00 + VAT

LYNX ELECTRONICS (London) LTD.

'92 Broad Street, Chesham, Bucks. Tel (02405) 75154
VAT 8% except * which are 12 1/2 % Return Post Service
P&P 30p. Overseas 90p. Matching 20p per pair New Price List 20p
Prices correct at 30th April, 1977. ACCESS WELCOME

REGULATORS

723	0.45
7805	1.50
7812	1.50
7815	1.60
7818	1.50
LM309K	0.95
LM340-5	1.35
LM340-12	1.35
LM340-15	1.35
LM340-18	1.35

OPTO ELECTRONICS

CLASS II DISPLAYS	
L.E.D.	
2 Red	0.13
2 Green	0.20
2 Clear	0.10
TIL209	0.10
MODULE	
FCS8000	2.95

CLOCK CHIPS

MM5314	3.25
MM5316	3.85
AA-5-1224A	3.25
AA-5-4007D	9.95

IC SOCKETS

8 Pin	0.13
14 Pin	0.14
16 Pin	0.15
24 Pin	0.45
40 Pin	0.80

TRANSISTORS

AC126	0.15	BC182	0.11*	BDY60	1.70	BU133	1.60*	2N29250	0.09*
AC127	0.16	BC182L	0.12*	BDY61	1.65	BU204	1.60*	2N2926R	0.10*
AC128	0.16	BC183	0.10*	BDY62	1.15	BU205	1.90*	2N2926Y	0.09*
AC128K	0.25	BC183L	0.10*	BDY95	2.14	BU206	2.60*	2N2926G	0.10*
AC141	0.22	BC184	0.11*	BDY86	4.96	BU208	2.60*	2N3053	0.20*
AC141K	0.34	BC184L	0.12*	BDY97	2.45	MJ480	0.80	2N3055	0.50
AC142	0.18	BC186	0.20*	BF179	0.30	MJ481	1.05	2N3137	1.10
AC142K	0.32	BC187	0.24*	BF180	0.30	MJ490	0.90	2N3440	0.56
AC176	0.16	BC207B	0.12*	BF181	0.30	MJ491	1.15	2N3442	1.20
AC176K	0.32	BC212	0.11*	BF182	0.30	MJE340	0.40*	2N3570	3.60
AC187	0.18	BC212L	0.12*	BF183	0.30	MJE520	0.45	2N3702	0.10*
AC187K	0.18	BC213	0.12*	BF184	0.20	MJE521	0.55	2N3703	0.10*
AC188	0.18	BC213L	0.14*	BF185	0.20	OC29	0.95	2N3704	0.10*
AC188K	0.32	BC214	0.14*	BF194	0.10*	OC44	0.32	2N3705	0.10*
AD149	0.80	BC214L	0.15*	BF196	0.12*	OC45	0.32	2N3706	0.10*
AD161	0.35	BC237	0.16*	BF197	0.12*	OC46	0.20	2N3707	0.10*
AD162	0.35	BC238	0.16*	BF224J	0.18*	OC70	0.30	2N3708	0.09*
AF114	0.20	BC300	0.34	BF244	0.17*	OC71	0.35	2N3709	0.09*
AF115	0.20	BC301	0.32	BF257	0.30*	OC72	0.22	2N3710	0.10*
AF116	0.20	BC302	0.40	BF336	0.35*	OC84	0.40	2N3711	0.10*
AF117	0.20	BC303	0.46	BF337	0.32*	OC139	1.30	2N3715	1.70
AF118	0.50	BCY30	0.55	BF338	0.45*	OC140	1.30	2N3716	1.80
AF124	0.25	BCY31	0.55	BFW30	1.25	OC170	0.23	2N3771	1.60
AF125	0.25	BCY32	0.60	BFW59	0.30	TIP29A	0.44*	2N3772	1.90
AF126	0.25	BCY33	0.55	BFV60	0.36	TIP30A	0.52*	2N3773	2.10
AF139	0.35	BCY34	0.55	BFV60	0.36	TIP31A	0.54	2N3819	0.28*
AF239	0.37	BCY38	0.50	BFX30	0.30	TIP32A	0.64	2N4347	1.10
AL102	1.45	BCY39	1.15	BFX84	0.23	TIP41A	0.68	2N4348	1.20
AL103	1.30	BCY40	0.75	BFX85	0.25	TIP42A	0.72	2N4470	0.35*
AU107	3.30*	BCY42	0.30	BFX85	0.25	2N404	0.40	2N4870	0.35*
AU110	1.75*	BCY54	1.60	BFX86	0.25	2N696	0.20	2N4871	0.35*
AU113	1.80*	BCY70	1.80*	BFX87	0.20	2N697	0.20	2N4918	0.60*
BC107	0.12	BCY71	0.18	BFX89	0.20	2N706	0.15	2N4920	0.50*
BC107B	0.12	BCY72	0.12	BFY11	1.10	2N1131	0.15	2N4922	0.58*
BC108	0.12	BD115	0.15*	BFY18	0.50	2N1302	0.18	2N4923	0.48*
BC108B	0.12	BD131	0.36	BFY40	0.50	2N1303	0.40		
BC109	0.12	BD132	0.40	BFY41	0.80	2N1304	0.40		
BC109B	0.12	BD135	0.36*	BFY50	0.20	2N1304	0.45		
BC109C	0.15	BD136	0.39*	BFY51	0.18	2N1305	0.45		
BC117	0.19*	BD137	0.40*	BFY52	0.18	2N1306	0.50		
BC119	0.25	BD138	0.48*	BFY53	0.25	2N1307	0.55		
BC125	0.18*	BD139	0.58*	BFY64	0.35	2N1308	0.60		
BC126	0.20*	BD144	2.20	BFY90	0.90	2N1309	0.60		
BC140	0.32	BD157	0.80	BSX19	0.16	2N1711	0.24		
BC141	0.28	BD181	0.86	BSX20	0.18	2N1202	0.44		
BC142	0.23	BD182	0.92	BSX21	0.18	2N2217	0.30		
BC143	0.23	BD183	0.97	BSX21	0.18	2N2369	0.14		
BC147	0.09*	BD184	1.20	BSY52	0.28	2N2369A	0.14		
BC148	0.09*	BD232	0.60	BSY53	0.39	2N2483	0.20		
BC149	0.09*	BD233	0.48	BSY54	0.33	2N2484	0.16		
BC157	0.09*	BD237	0.55	BSY55	0.74	2N2646	0.50		
BC158	0.09*	BD238	0.60	BSY65	0.30	2N2711	0.20		
BC159	0.09*	BD410	0.60	BSY95A	1.80	2N2712	0.15		
BC160	0.32	BDX32	2.30	BU105	1.80*	2N2904A	0.20		
BC161	0.38*	BDY10	1.50	BU105/02	1.90*	2N2905	0.18		
BC168	0.09*	BDY11	2.00	BU108	3.00*	2N2905A	0.22		
BC169	0.12*	BDY20	0.80	BU109	2.50*	2N2906	0.18		
BC169C	0.14*	BDY38	0.60	BU126	1.80*	2N2925	0.14*		

CMOS-PLASTIC

4000BE	0.20
4001BE	0.20
4002BE	0.20
4003BE	0.20
4007BE	0.20
4008BE	0.83
4009BE	0.52
4010BE	0.62
4011BE	0.20
4012BE	0.20
4013BE	0.50
4014BE	1.00
4015BE	0.95
4016BE	0.54
4017BE	1.00
4018BE	1.10
4019BE	0.50
4020BE	1.12
4021BE	1.03
4022BE	0.95
4023BE	0.20
4024BE	0.88
4025BE	0.20
4026BE	1.55
4027BE	0.62
4028BE	0.91
4029BE	1.10
4030BE	0.55
4041BE	0.80
4042BE	0.83
4043BE	1.00
4044BE	0.84
4046BE	1.32
4049BE	0.54
4050BE	0.54
4059BE	0.60
4061BE	0.80
4070BE	0.26
4071BE	0.80
4072BE	0.26
4073BE	0.20
4082BE	0.78
4510BE	1.42
4511BE	1.80
4516BE	1.35
4518BE	1.25
4520BE	1.20

TTL 7400 SERIES

7400	0.16	748D	0.55
7401	0.16	748Z	0.75
7402	0.16	748E	0.32
7403	0.16	7489	2.02
7413	0.40	7496	0.49
7405	0.18	7490AN	0.65
7408	0.18	7492	0.57
7409	0.18	7493	0.45
7410	0.18	7494	0.85
7412	0.25	7495	0.67
7413	0.40	7496	0.82
7414	0.72	74100	1.07
7417	0.43	74107	0.35
7420	0.16	74121	0.34
7425	0.30	74122	0.47
7427	0.30	74123	0.65
7413	0.16	74141	0.78
7432	0.28	74145	0.88
7437	0.30	74154	1.30
7441AN	0.76	74164	0.93
7442	0.65	74165	0.93
7445	0.90	74174	1.40
7447AN	0.81	74175	0.94
7448	0.81	74180	1.06
7470	0.32	74181	2.70
7472	0.26	74191	1.33
7473	0.30	74192	1.20
7474	0.32	74193	1.35
7475	0.47	74194	1.20
7476	0.36	74196	1.64

THYRISTORS

PIV	1A	3A	A	4A	6A	10A	15A
(T05)	(S104)	(C106)	(T0220)	(T0220)	(T0220)	(T0220)	(T0404)
200	0.35	0.50	0.45	0.40	0.58	0.83	1.01
400	0.40	0.50	0.50	0.45	0.68	0.86	0.98
600	0.65	0.85	0.70	-	1.09	1.19	1.26
							1.80
BT106	BT107	BT108	BT109	BT116	2N3525		
£1.00	£1.60	£1.60	£1.00	£1.00	£1.00	£0.50	

TRIACS - Plastic TO-220 Package Isolated Tab

	4A	6.5A	8.5A	10A	15A
(a)	(b)	(a)	(b)	(a)	(b)
100V	0.60	0.60	0.70	0.70	0.78
200V	0.64	0.64	0.75	0.87	0.87
400V	0.77	0.78	0.80	0.83	0.97
600V	0.96	0.99	1.01	1.10	1.26
					1.50
					2.11
					2.17

SPECIAL OFFER SECTION

SG309K	£0.95	TIL209 Red Led	0.10	OCF 71	£1.15
NPN TO-3 POWER TRANSISTORS		TO-18 NPN TRANSISTORS		RECTIFIERS OO-4 PACKAGE	
Fully tested but unmarked Similar to 2N3055 except BVCE = 50+ HFE (gain) = 20+ at 3A VCE SAT < 1.3V at 3A		Medium Voltage High Gain Type BSY65 Similar to BC107/8/9		10A 50V 0.80. Stud Anode Polarity 10A 100V 0.80. Stud Cathode or 10A 400V 1.20.	
5 pcs £1.00 25 pcs £4.00 50 pcs £7.50 100 pcs £13.00		TO-3 HARDWARE Micra Washers, Solder tag, Nuts, Bolts		50 sets for 65p	

MEMORIES

2102A	6.80	3.60	BY206	0.15	BZX61 Series	IN914	0.04*
2112A	4.75	BYX36	BY207	0.20*	BZX83 Series	IN4001	0.04*
6508	7.95	300 0.12	600 0.15	800 0.18	BYY88 Series	IN4002	0.05*
2107	10.00	1200 0.21	1200 0.21	1200 0.21	OA5	IN4003	0.06*
2112	4.50	300 0.50	600 0.55	900 0.60	OA10	IN4004	0.07*
2513	8.50	900 0.65	900 0.65	900 0.65	OA10	IN4007	0.10*
2602	2.50	1200 0.65	1200 0.65	1200 0.65	OA200	IN4148	0.04*

It's the cat's whiskers!



A fascinating excursion into the past. The author has unearthed some 400 trade names from the crystal set days, along with nearly 200 manufacturers—giving the name of the set, technical description and original price. He also reviews the first days of broadcasting and looks at the difficulties experienced by crystal set users. Concise information and over 40 illustrations make this book a valuable work of reference as well as a rare piece of nostalgia for collectors.

VINTAGE CRYSTAL SETS 1922-1937

£2.50 from bookshops

£2.80 inclusive direct from Wireless World, Room 11, General Sales Dept., IPC Business Press Ltd., Dorset House, Stamford Street, London SE1 9LU.

Name _____
Address _____

carbon film resistors

£1.50 ^{+VAT} per 1000!

0.125W 5% TOL. RADIAL LEAD

SUPPLIED ONLY IN MULTIPLES OF 1000pcs per OHMIC VALUE

MIN. ORDER £25 WHILE STOCKS LAST

0.25W, 0.5W, 1W & 2W AXIAL LEAD RESISTORS AND POLYSTYRENE CAPACITORS ALSO AT LOW PRICES SEND FOR LISTS AND SAMPLES

PBRA LTD THREE ELM LANE

GOLDEN GREEN TONBRIDGE TN11 0LH


phone HOPFIELD (073274) 345

WW-090 FOR FURTHER DETAILS

**ANY MAKE-UP OR
COPY QUERIES
CONTACT
JOHN GIBBON
01-261 8353**

TELERADIO SPECIALISTS IN DESIGNS by John Linsley Hood

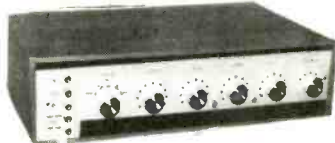Example: 25 to 75 watt. Very Low Distortion HIGH FIDELITY STEREO AMPLIFIER. D.C. Coupled. T.H.D. hardly measurable. £73 in kit form (+ 1 1/2% VAT)



PP extra

Supplied as a Kit of parts or in ready assembled module form.

Also available: Phase Locked Loop; F.M. Tuner; Millivoltmeter; Audio Signal Generator; T.H. Distortion Analyser; F.M. Signal Generator/Wobulator

Send SAE for comprehensive illustrated lists and up-to-date prices

TELERADIO ELECTRONICS

325 Fore Street, Edmonton, London N9 0PE

Telephone: 01-807 3719

Closed Thursdays

STEREO DISC AMPLIFIER 2

FOR BROADCASTING, DISC MONITORING AND TRANSFER WITH THE HIGHEST QUALITY Stereo Disc Amplifier 2 is a self-contained mains powered unit which accepts cartridge inputs and produces balanced line level outputs. Permanent rumble filtering and switched scratch filtering is included. 1KHz @ 6mV set for 0dBV 7 loaded 600 ohms

Distortion
Output + 10dBV 7 30Hz - 20KHz below noise
Output + 20dBV 7 1KHz 88dB, 0.004%; 30Hz-20KHz 82dB 0.008%

Intermodulation distortion 50Hz + 7KHz 4 1
Output + 10dBV 7 Static 90dB, 0.003% limit of measurement

Dynamic Intermodulation Distortion 3.18KHz square wave (single pole -3dB 100KHz) + 15KHz sine wave, 4 1
Preemphasised input 1V pk-pk -60dB 0.1%

Cartridge impedance interaction on frequency response.
High inductance cartridge, 1H Inductance less than 0.2dB

Clipping Point Complementary to RIAA Curve 1KHz clips at +24dBV 7 output 30Hz-20KHz Within 0.5dB
Clipping determined by onset of peaky distortion products or THD exceeding -80dB

Differential Phase Shift 50Hz-20KHz Within 0.5
Worst error at LF and HF filter turnovers. Within 5

Crosstalk 1KHz -76dB, 30Hz-20KHz -60dB

SURREY ELECTRONICS

The Forge, Lucks Green, Cranleigh, Surrey GU6 7BG (STD 04866) 5997

DEMA ELECTRONICS INTERNATIONAL

TTL 7400 SERIES

NEW LOW PRICES

7400 £0.09	7441 £0.58	7486 £0.25	74156 £0.69
7401 0.09	7442 0.48	7489 1.45	74157 0.69
7402 0.10	7443 0.48	7490 0.32	74158 0.69
7403 0.10	7444 0.60	7491 0.55	74160 0.89
7404 0.13	7445 0.70	7492 0.35	74162 0.89
7405 0.13	7446 0.80	7493 0.35	74163 0.89
7406 0.22	7447 0.65	7494 0.40	74164 1.05
7407 0.22	7448 0.60	7495 0.45	74165 1.05
7408 0.13	7450 0.12	7496 0.55	74166 1.05
7409 0.13	7451 0.12	74100 0.89	74170 1.65
7410 0.09	7453 0.12	74107 0.23	74175 0.85
7411 0.16	7454 0.12	74121 0.23	74180 0.80
7413 0.25	7460 0.11	74122 0.37	74181 2.00
7416 0.22	7470 0.24	74123 0.45	74182 0.80
7417 0.22	7472 0.21	74145 0.57	74192 0.95
7420 0.11	7473 0.25	74150 0.75	74193 0.95
7426 0.23	7474 0.25	74151 0.59	74194 0.85
7430 0.11	7475 0.35	74153 0.69	74195 0.78
7432 0.22	7476 0.24	74154 1.05	74198 1.20
7437 0.25	7483 0.69	74155 0.69	74199 1.70
7438 0.19	7485 0.85		

CMOS 4000

4000A £0.14	4010 £0.36	4021 £0.65	4035 £0.75
4001 0.14	4011 9.14	4022 0.14	4042 0.55
4002 0.14	4012 0.14	4023 0.65	4049 0.35
4006 0.75	4013 0.36	4024 0.50	4050 0.35
4007 0.14	4014 0.65	4025 0.14	4066 0.46
4008 0.65	4015 0.65	4027 0.36	4069 0.15
4009 0.36	4016 0.38	4028 0.59	4071 0.15
	4020 0.75	4030 0.36	

LINEARS

LM300	TO99	£0.45	562	B DIP	£2.45
301	V DIP	0.25	565	A DIP	1.40
302	TO99	0.40	566	V DIP	1.40
304	TO100	0.50	567	V DIP	1.55
305	TO99	0.45	709	A DIP	0.20
307	V DIP	0.38	710	A DIP	0.25
	TO99	0.45	711	A DIP	0.18
308	A DIP	0.59	723	A DIP	0.38
324	A DIP	1.07	739	A DIP	0.65
339	A DIP	1.15	741	V DIP	0.22
340T	TO92	1.25	747 (1456)	A DIP	0.44
380	A DIP	0.80	748	V DIP	0.24
381	A DIP	0.90	5556 (1456)	V DIP	0.95
550	A DIP	0.55	5558 (1458)	V DIP	0.45
555	V DIP	0.35	LM 3900	A dip	0.25
556	B DIP	0.75	ICL8038 Funct. Gen.		2.80
560	B DIP	2.45	8864 22 Pin pkg.		1.45

MEMORIES w/DATA

1101	256 Bit Ram Mos	£0.75		
1103	1024 Bit Ram Mos	0.75		
7489	(8225) 64 Bit Ram TTL	1.45	5002	Cal Chip £0.79
82S23	Programmable ROM	1.95	5005	Cal Chip 0.79
5260	1024 Bit Ram Low Pwr.	1.45	5725	Cal Chip 1.10
5261	1024 Bit Ram L Power	1.56	5312	Clock Chip 2.50
1702A	2048 Bit Ram	5.25	5316	Clock Chip 3.95
2102	1024 Bit Status Ram	1.50	CT7001	Clock Chip 3.85

CALCULATORS & CLOCK w/DATA

V=Mini Dip A=14L Dip B=16L DIP TO99 8-Pin Header
TO100 10-Pin Header
Data sheets supplied on request. Add 20 ea. excepted as noted.

DISCOUNTS:

10% on orders over £10
15% on order over £25

MIN. ORDER
£2.00

All Items Guaranteed by
DEMA ELECTRONICS

TERMS: PRICES LISTED ARE BRITISH POUNDS & PENCE. SEND CHEQUE WITH ORDER. ACCESS CARD, BANKAMERICARD, BARCLAY CARD ACCEPTED. (Card No. and expiration date requested). TERMS OFFERED TO SCHOOLS & INSTITUTIONS.

POSTAL AND HANDLING CHARGES

SHIPMENT VIA AIR MAIL
under 4.99 add 45 £10 and over
5 00-9 99 add 35 No Charge

DEMA ELECTRONICS INTERNATIONAL

P.O. Box 407
San Remo, CA 94583 USA

SPECIAL LOW PRICE ARRANGEMENTS FOR VISITING OVERSEAS TRADE FAIRS



IPC Electrical-Electronic Press Ltd., the world's largest publishers of computer, electrical and electronic journals, have made special arrangements for readers wishing to visit important overseas trade fairs. The cost, in most cases, is little more than the normal air fare but includes - travel by scheduled airline from Heathrow and Manchester * first-class hotel accommodation * arrival and departure transfers * admission to the trade fair * services of an experienced tour manager. The current programme comprises the following tours.

To obtain a brochure and booking form, tick the box against the tours in which you are interested, complete the coupon and post to the exclusively appointed travel agent, Commercial Trade Travel Ltd., Carlisle House, 8 Southampton Row, London WC1. Telephone 01-405-8666 or 01-405-5469.

International Exhibition of
Computers and Peripheral
equipment - SYSTEMS

Munich

October 17-21
1977

Internecon/Industrial
Elektronik

Vienna

November 9-12
1977

International Exhibition for
Electronic Production -
PRODUCTRONICA

Munich

November 22-26
1977

Please send details of the tours indicated above.


NAME..... COMPANY.....

ADDRESS..... Telephone.....

<h3>TTLs by TEXAS</h3> <table border="0"> <tr><td>7400</td><td>16p</td><td>74109</td><td>89p</td></tr> <tr><td>7400</td><td>28p</td><td>74110</td><td>55p</td></tr> <tr><td>7400</td><td>33p</td><td>74111</td><td>90p</td></tr> <tr><td>7400</td><td>33p</td><td>74112</td><td>96p</td></tr> <tr><td>7401</td><td>18p</td><td>74116</td><td>200p</td></tr> <tr><td>7402</td><td>18p</td><td>74118</td><td>84p</td></tr> <tr><td>7403</td><td>18p</td><td>74120</td><td>120p</td></tr> <tr><td>7404</td><td>23p</td><td>74121</td><td>32p</td></tr> <tr><td>7404</td><td>36p</td><td>74122</td><td>54p</td></tr> <tr><td>7405</td><td>25p</td><td>74123</td><td>76p</td></tr> <tr><td>7406</td><td>43p</td><td>74125</td><td>73p</td></tr> <tr><td>7407</td><td>43p</td><td>74126</td><td>70p</td></tr> <tr><td>7408</td><td>25p</td><td>74128</td><td>75p</td></tr> <tr><td>7409</td><td>27p</td><td>74132</td><td>70p</td></tr> <tr><td>7410</td><td>18p</td><td>74136</td><td>75p</td></tr> <tr><td>7410</td><td>28p</td><td>74141</td><td>72p</td></tr> <tr><td>7411</td><td>24p</td><td>74142</td><td>35p</td></tr> <tr><td>7412</td><td>25p</td><td>74145</td><td>90p</td></tr> <tr><td>7413</td><td>36p</td><td>74147</td><td>190p</td></tr> <tr><td>7414</td><td>35p</td><td>74148</td><td>160p</td></tr> <tr><td>7416</td><td>33p</td><td>74150</td><td>140p</td></tr> <tr><td>7417</td><td>36p</td><td>74151</td><td>72p</td></tr> <tr><td>7420</td><td>18p</td><td>74153</td><td>85p</td></tr> <tr><td>7421</td><td>40p</td><td>74154</td><td>150p</td></tr> <tr><td>7422</td><td>22p</td><td>74155</td><td>90p</td></tr> <tr><td>7423</td><td>37p</td><td>74156</td><td>90p</td></tr> <tr><td>7425</td><td>30p</td><td>74157</td><td>90p</td></tr> <tr><td>7427</td><td>37p</td><td>74158</td><td>140p</td></tr> <tr><td>7428</td><td>36p</td><td>74159</td><td>190p</td></tr> <tr><td>7430</td><td>18p</td><td>74160</td><td>120p</td></tr> <tr><td>7432</td><td>36p</td><td>74161</td><td>120p</td></tr> <tr><td>7437</td><td>36p</td><td>74162</td><td>120p</td></tr> <tr><td>7438</td><td>36p</td><td>74163</td><td>120p</td></tr> <tr><td>7440</td><td>19p</td><td>74164</td><td>120p</td></tr> <tr><td>7441</td><td>75p</td><td>74165</td><td>220p</td></tr> <tr><td>7442</td><td>70p</td><td>74166</td><td>160p</td></tr> <tr><td>7443</td><td>140p</td><td>74167</td><td>340p</td></tr> <tr><td>7444</td><td>140p</td><td>74170</td><td>250p</td></tr> <tr><td>7445</td><td>120p</td><td>74172</td><td>720p</td></tr> <tr><td>7446</td><td>150p</td><td>74173</td><td>160p</td></tr> <tr><td>7447</td><td>80p</td><td>74174</td><td>200p</td></tr> <tr><td>7448</td><td>80p</td><td>74175</td><td>85p</td></tr> <tr><td>7450</td><td>18p</td><td>74176</td><td>120p</td></tr> <tr><td>7451</td><td>20p</td><td>74177</td><td>100p</td></tr> <tr><td>7452</td><td>20p</td><td>74179</td><td>160p</td></tr> <tr><td>7453</td><td>20p</td><td>74180</td><td>110p</td></tr> <tr><td>7454</td><td>18p</td><td>74181</td><td>298p</td></tr> <tr><td>7460</td><td>18p</td><td>74182</td><td>82p</td></tr> <tr><td>7470</td><td>36p</td><td>74185</td><td>150p</td></tr> <tr><td>7472</td><td>30p</td><td>74186</td><td>920p</td></tr> <tr><td>7473</td><td>34p</td><td>74190</td><td>160p</td></tr> <tr><td>7474</td><td>34p</td><td>74191</td><td>160p</td></tr> <tr><td>7475</td><td>45p</td><td>74192</td><td>120p</td></tr> <tr><td>7476</td><td>36p</td><td>74193</td><td>160p</td></tr> <tr><td>7480</td><td>50p</td><td>74194</td><td>120p</td></tr> <tr><td>7481</td><td>95p</td><td>74195</td><td>95p</td></tr> <tr><td>7482</td><td>90p</td><td>74196</td><td>120p</td></tr> <tr><td>7483</td><td>90p</td><td>74197</td><td>120p</td></tr> <tr><td>7484</td><td>110p</td><td>74198</td><td>250p</td></tr> <tr><td>7485</td><td>120p</td><td>74199</td><td>250p</td></tr> <tr><td>7486</td><td>34p</td><td>74221</td><td>160p</td></tr> <tr><td>7489</td><td>320p</td><td>74251</td><td>160p</td></tr> <tr><td>7490</td><td>40p</td><td>74265</td><td>90p</td></tr> <tr><td>7491</td><td>85p</td><td>74278</td><td>290p</td></tr> <tr><td>7492</td><td>55p</td><td>74279</td><td>140p</td></tr> <tr><td>7493</td><td>40p</td><td>74283</td><td>190p</td></tr> <tr><td>7494</td><td>90p</td><td>74290</td><td>150p</td></tr> <tr><td>7495</td><td>70p</td><td>74293</td><td>150p</td></tr> <tr><td>7496</td><td>84p</td><td>74298</td><td>200p</td></tr> <tr><td>7497</td><td>340p</td><td>74365</td><td>150p</td></tr> <tr><td>74100</td><td>120p</td><td>74366</td><td>150p</td></tr> <tr><td>74104</td><td>65p</td><td>74390</td><td>200p</td></tr> <tr><td>74105</td><td>65p</td><td>74390</td><td>250p</td></tr> <tr><td>74107</td><td>36p</td><td>74393</td><td>225p</td></tr> </table>	7400	16p	74109	89p	7400	28p	74110	55p	7400	33p	74111	90p	7400	33p	74112	96p	7401	18p	74116	200p	7402	18p	74118	84p	7403	18p	74120	120p	7404	23p	74121	32p	7404	36p	74122	54p	7405	25p	74123	76p	7406	43p	74125	73p	7407	43p	74126	70p	7408	25p	74128	75p	7409	27p	74132	70p	7410	18p	74136	75p	7410	28p	74141	72p	7411	24p	74142	35p	7412	25p	74145	90p	7413	36p	74147	190p	7414	35p	74148	160p	7416	33p	74150	140p	7417	36p	74151	72p	7420	18p	74153	85p	7421	40p	74154	150p	7422	22p	74155	90p	7423	37p	74156	90p	7425	30p	74157	90p	7427	37p	74158	140p	7428	36p	74159	190p	7430	18p	74160	120p	7432	36p	74161	120p	7437	36p	74162	120p	7438	36p	74163	120p	7440	19p	74164	120p	7441	75p	74165	220p	7442	70p	74166	160p	7443	140p	74167	340p	7444	140p	74170	250p	7445	120p	74172	720p	7446	150p	74173	160p	7447	80p	74174	200p	7448	80p	74175	85p	7450	18p	74176	120p	7451	20p	74177	100p	7452	20p	74179	160p	7453	20p	74180	110p	7454	18p	74181	298p	7460	18p	74182	82p	7470	36p	74185	150p	7472	30p	74186	920p	7473	34p	74190	160p	7474	34p	74191	160p	7475	45p	74192	120p	7476	36p	74193	160p	7480	50p	74194	120p	7481	95p	74195	95p	7482	90p	74196	120p	7483	90p	74197	120p	7484	110p	74198	250p	7485	120p	74199	250p	7486	34p	74221	160p	7489	320p	74251	160p	7490	40p	74265	90p	7491	85p	74278	290p	7492	55p	74279	140p	7493	40p	74283	190p	7494	90p	74290	150p	7495	70p	74293	150p	7496	84p	74298	200p	7497	340p	74365	150p	74100	120p	74366	150p	74104	65p	74390	200p	74105	65p	74390	250p	74107	36p	74393	225p	<h3>C-MOS I.C.s</h3> <table border="0"> <tr><td>CD4000AE</td><td>20p</td></tr> <tr><td>CD4001AE</td><td>20p</td></tr> <tr><td>CD4002AE</td><td>20p</td></tr> <tr><td>CD4006AE</td><td>95p</td></tr> <tr><td>CD4007AE</td><td>20p</td></tr> <tr><td>CD4009AE</td><td>61p</td></tr> <tr><td>CD4011AE</td><td>20p</td></tr> <tr><td>CD4012AE</td><td>20p</td></tr> <tr><td>CD4013AE</td><td>55p</td></tr> <tr><td>CD4015AE</td><td>90p</td></tr> <tr><td>CD4016AE</td><td>50p</td></tr> <tr><td>CD4017AE</td><td>100p</td></tr> <tr><td>CD4018AE</td><td>110p</td></tr> <tr><td>CD4019AE</td><td>52p</td></tr> <tr><td>CD4020AE</td><td>120p</td></tr> <tr><td>CD4022AE</td><td>100p</td></tr> <tr><td>CD4023AE</td><td>22p</td></tr> <tr><td>CD4024AE</td><td>80p</td></tr> <tr><td>CD4025AE</td><td>22p</td></tr> <tr><td>CD4026AE</td><td>170p</td></tr> <tr><td>CD4027AE</td><td>65p</td></tr> <tr><td>CD4028AE</td><td>98p</td></tr> <tr><td>CD4029AE</td><td>120p</td></tr> <tr><td>CD4030AE</td><td>55p</td></tr> <tr><td>CD4040AE</td><td>120p</td></tr> <tr><td>CD4042AE</td><td>90p</td></tr> <tr><td>CD4043AE</td><td>100p</td></tr> <tr><td>CD4046AE</td><td>140p</td></tr> <tr><td>CD4047AE</td><td>100p</td></tr> <tr><td>CD4049AE</td><td>63p</td></tr> <tr><td>CD4050AE</td><td>57p</td></tr> <tr><td>CD4054AE</td><td>120p</td></tr> <tr><td>CD4055AE</td><td>140p</td></tr> <tr><td>CD4056AE</td><td>135p</td></tr> <tr><td>CD4060AE</td><td>130p</td></tr> <tr><td>CD4069AE</td><td>27p</td></tr> <tr><td>CD4071AE</td><td>27p</td></tr> <tr><td>CD4072AE</td><td>27p</td></tr> <tr><td>CD4073AE</td><td>30p</td></tr> <tr><td>CD4081AE</td><td>21p</td></tr> <tr><td>CD4082AE</td><td>27p</td></tr> <tr><td>CD4093AE</td><td>95p</td></tr> <tr><td>CD4510AE</td><td>130p</td></tr> <tr><td>CD4511AE</td><td>160p</td></tr> <tr><td>CD4516AE</td><td>112p</td></tr> <tr><td>CD4518AE</td><td>130p</td></tr> <tr><td>CD4528AE</td><td>120p</td></tr> <tr><td>MC14553</td><td>525p</td></tr> </table>	CD4000AE	20p	CD4001AE	20p	CD4002AE	20p	CD4006AE	95p	CD4007AE	20p	CD4009AE	61p	CD4011AE	20p	CD4012AE	20p	CD4013AE	55p	CD4015AE	90p	CD4016AE	50p	CD4017AE	100p	CD4018AE	110p	CD4019AE	52p	CD4020AE	120p	CD4022AE	100p	CD4023AE	22p	CD4024AE	80p	CD4025AE	22p	CD4026AE	170p	CD4027AE	65p	CD4028AE	98p	CD4029AE	120p	CD4030AE	55p	CD4040AE	120p	CD4042AE	90p	CD4043AE	100p	CD4046AE	140p	CD4047AE	100p	CD4049AE	63p	CD4050AE	57p	CD4054AE	120p	CD4055AE	140p	CD4056AE	135p	CD4060AE	130p	CD4069AE	27p	CD4071AE	27p	CD4072AE	27p	CD4073AE	30p	CD4081AE	21p	CD4082AE	27p	CD4093AE	95p	CD4510AE	130p	CD4511AE	160p	CD4516AE	112p	CD4518AE	130p	CD4528AE	120p	MC14553	525p	<h3>OP. AMPS</h3> <table border="0"> <tr><td>1458</td><td>Dual Op Amp Int. Comp</td><td>8 pin DIL</td><td>70p</td></tr> <tr><td>301A</td><td>Ext. Comp.</td><td>8 pin DIL</td><td>36p</td></tr> <tr><td>3130</td><td>COSMOS/Bi-Polar MosFet</td><td>8 pin DIL</td><td>100p</td></tr> <tr><td>CA3140</td><td>BIMOS</td><td>8 pin DIL</td><td>100p</td></tr> <tr><td>LM318N</td><td>High speed</td><td>8 pin DIL</td><td>200p</td></tr> <tr><td>LM324N</td><td>Quad Op. Amp</td><td>14 pin DIL</td><td>120p</td></tr> <tr><td>3900</td><td>Quad. Op. Amp.</td><td>14 pin DIL</td><td>70p</td></tr> <tr><td>709</td><td>Ext. Comp.</td><td>8/14 pin DIL</td><td>20p</td></tr> <tr><td>741</td><td>Int. Comp.</td><td>8/14 pin DIL</td><td>32p</td></tr> <tr><td>747</td><td>Dual 741</td><td>14 pin DIL</td><td>70p</td></tr> <tr><td>748</td><td>Ext. Comp.</td><td>8/14 pin DIL</td><td>36p</td></tr> <tr><td>776</td><td>Programmable Op. Amp.</td><td>TO-5</td><td>140p</td></tr> </table>	1458	Dual Op Amp Int. Comp	8 pin DIL	70p	301A	Ext. Comp.	8 pin DIL	36p	3130	COSMOS/Bi-Polar MosFet	8 pin DIL	100p	CA3140	BIMOS	8 pin DIL	100p	LM318N	High speed	8 pin DIL	200p	LM324N	Quad Op. Amp	14 pin DIL	120p	3900	Quad. Op. Amp.	14 pin DIL	70p	709	Ext. Comp.	8/14 pin DIL	20p	741	Int. Comp.	8/14 pin DIL	32p	747	Dual 741	14 pin DIL	70p	748	Ext. Comp.	8/14 pin DIL	36p	776	Programmable Op. Amp.	TO-5	140p	<h3>TRANSISTORS</h3> <table border="0"> <tr><td>AC125</td><td>25p</td><td>BFX86</td><td>30p</td><td>*N2926B</td><td>7p</td></tr> <tr><td>AC126</td><td>20p</td><td>BFX87</td><td>30p</td><td>*N2926B</td><td>10p</td></tr> <tr><td>AC127</td><td>20p</td><td>BFX88</td><td>30p</td><td>*N2926B</td><td>12p</td></tr> <tr><td>AC128</td><td>18p</td><td>BFY50</td><td>22p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AC141</td><td>20p</td><td>BFY51</td><td>22p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AC142</td><td>20p</td><td>BFY52</td><td>22p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AC176</td><td>20p</td><td>BFY90</td><td>120p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AC187X</td><td>25p</td><td>BRV39</td><td>45p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AC188</td><td>20p</td><td>BSX20</td><td>20p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AC188K</td><td>25p</td><td>*BU105</td><td>140p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AD149</td><td>49p</td><td>*BU108</td><td>250p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AD161</td><td>45p</td><td>*MJE340</td><td>85p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AF162</td><td>45p</td><td>*MJE341</td><td>85p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AF174</td><td>20p</td><td>*MJE342</td><td>85p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AF175</td><td>20p</td><td>*MJE2501</td><td>225p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AF176</td><td>20p</td><td>*MJE2955</td><td>120p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AF177</td><td>20p</td><td>*MJE2955</td><td>130p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AF178</td><td>25p</td><td>*MJE3001</td><td>225p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AF195</td><td>43p</td><td>*MJE3005</td><td>75p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>AF239</td><td>48p</td><td>*MPS006</td><td>90p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BC107 B</td><td>9p</td><td>*MPSA12</td><td>50p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BC108 B</td><td>9p</td><td>*MPSA56</td><td>32p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BC109 B</td><td>10p</td><td>*MPSU06</td><td>62p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BC109C</td><td>12p</td><td>*MPSU56</td><td>78p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC117</td><td>22p</td><td>OC28</td><td>120p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC147</td><td>9p</td><td>OC35</td><td>90p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC148</td><td>9p</td><td>OC36</td><td>90p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC149C</td><td>10p</td><td>*OC71</td><td>20p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC157</td><td>11p</td><td>*R2008B</td><td>200p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC158</td><td>10p</td><td>*R2010B</td><td>200p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC159</td><td>11p</td><td>*RIP29A</td><td>40p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC163C</td><td>12p</td><td>*RIP29C</td><td>55p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC172</td><td>11p</td><td>*RIP30A</td><td>48p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC177</td><td>18p</td><td>*RIP30C</td><td>60p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC178</td><td>17p</td><td>*RIP31A</td><td>52p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC179</td><td>18p</td><td>*RIP31C</td><td>52p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC182</td><td>12p</td><td>*RIP32A</td><td>58p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC183</td><td>13p</td><td>*RIP32C</td><td>58p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC187</td><td>30p</td><td>*RIP33A</td><td>90p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC212</td><td>11p</td><td>*RIP33C</td><td>115p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC213</td><td>10p</td><td>*RIP34A</td><td>115p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC214</td><td>14p</td><td>*RIP35A</td><td>160p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC461</td><td>30p</td><td>*RIP42A</td><td>290p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BC478</td><td>30p</td><td>*RIP36A</td><td>270p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BCY70</td><td>18p</td><td>*RIP36C</td><td>340p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BCY71</td><td>22p</td><td>*RIP37A</td><td>65p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BD124</td><td>130p</td><td>*RIP31B</td><td>65p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BD131</td><td>63p</td><td>*RIP31C</td><td>78p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BD132</td><td>65p</td><td>*RIP42A</td><td>70p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BD135</td><td>48p</td><td>*RIP42B</td><td>70p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BD136</td><td>50p</td><td>*RIP42C</td><td>72p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BD139</td><td>52p</td><td>*RIP2955</td><td>82p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BD140</td><td>58p</td><td>*IS93</td><td>30p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BD20</td><td>125p</td><td>*IX108</td><td>10p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BD32</td><td>200p</td><td>*IX300</td><td>13p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF115</td><td>22p</td><td>*IX502</td><td>15p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF167</td><td>23p</td><td>*IX502</td><td>18p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF170</td><td>23p</td><td>*N457A</td><td>190p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF173</td><td>25p</td><td>*N697</td><td>22p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF177</td><td>28p</td><td>*N698</td><td>45p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF178</td><td>28p</td><td>*N706</td><td>20p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF179</td><td>33p</td><td>*N708</td><td>20p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF180</td><td>33p</td><td>*N918</td><td>40p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF184</td><td>32p</td><td>*N930</td><td>18p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF194</td><td>10p</td><td>*N1131</td><td>18p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF196</td><td>9p</td><td>*N1132</td><td>18p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF197</td><td>15p</td><td>*N1304</td><td>65p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF200</td><td>32p</td><td>*N1306</td><td>75p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF257</td><td>32p</td><td>*N1307</td><td>75p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF258</td><td>36p</td><td>*N1308</td><td>50p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF259</td><td>38p</td><td>*N1309</td><td>50p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>BF337</td><td>30p</td><td>*N1613</td><td>25p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF339</td><td>30p</td><td>*N1711</td><td>25p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF340</td><td>30p</td><td>*N1893</td><td>30p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF341</td><td>30p</td><td>*N2102</td><td>55p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF342</td><td>30p</td><td>*N2219</td><td>20p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF343</td><td>30p</td><td>*N2222</td><td>20p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF344</td><td>30p</td><td>*N2369</td><td>14p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF345</td><td>30p</td><td>*N2484</td><td>25p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF346</td><td>30p</td><td>*N2904A</td><td>25p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF347</td><td>30p</td><td>*N2905A</td><td>25p</td><td>*N2926B</td><td>22p</td></tr> <tr><td>*BF348</td><td>30p</td><td>*N2906A</td><td>24p</td><td>*N2926B</td><td>22p</td></tr> </table>	AC125	25p	BFX86	30p	*N2926B	7p	AC126	20p	BFX87	30p	*N2926B	10p	AC127	20p	BFX88	30p	*N2926B	12p	AC128	18p	BFY50	22p	*N2926B	22p	AC141	20p	BFY51	22p	*N2926B	22p	AC142	20p	BFY52	22p	*N2926B	22p	AC176	20p	BFY90	120p	*N2926B	22p	AC187X	25p	BRV39	45p	*N2926B	22p	AC188	20p	BSX20	20p	*N2926B	22p	AC188K	25p	*BU105	140p	*N2926B	22p	AD149	49p	*BU108	250p	*N2926B	22p	AD161	45p	*MJE340	85p	*N2926B	22p	AF162	45p	*MJE341	85p	*N2926B	22p	AF174	20p	*MJE342	85p	*N2926B	22p	AF175	20p	*MJE2501	225p	*N2926B	22p	AF176	20p	*MJE2955	120p	*N2926B	22p	AF177	20p	*MJE2955	130p	*N2926B	22p	AF178	25p	*MJE3001	225p	*N2926B	22p	AF195	43p	*MJE3005	75p	*N2926B	22p	AF239	48p	*MPS006	90p	*N2926B	22p	BC107 B	9p	*MPSA12	50p	*N2926B	22p	BC108 B	9p	*MPSA56	32p	*N2926B	22p	BC109 B	10p	*MPSU06	62p	*N2926B	22p	BC109C	12p	*MPSU56	78p	*N2926B	22p	*BC117	22p	OC28	120p	*N2926B	22p	*BC147	9p	OC35	90p	*N2926B	22p	*BC148	9p	OC36	90p	*N2926B	22p	*BC149C	10p	*OC71	20p	*N2926B	22p	*BC157	11p	*R2008B	200p	*N2926B	22p	*BC158	10p	*R2010B	200p	*N2926B	22p	*BC159	11p	*RIP29A	40p	*N2926B	22p	*BC163C	12p	*RIP29C	55p	*N2926B	22p	*BC172	11p	*RIP30A	48p	*N2926B	22p	*BC177	18p	*RIP30C	60p	*N2926B	22p	*BC178	17p	*RIP31A	52p	*N2926B	22p	*BC179	18p	*RIP31C	52p	*N2926B	22p	*BC182	12p	*RIP32A	58p	*N2926B	22p	*BC183	13p	*RIP32C	58p	*N2926B	22p	*BC187	30p	*RIP33A	90p	*N2926B	22p	*BC212	11p	*RIP33C	115p	*N2926B	22p	*BC213	10p	*RIP34A	115p	*N2926B	22p	*BC214	14p	*RIP35A	160p	*N2926B	22p	*BC461	30p	*RIP42A	290p	*N2926B	22p	*BC478	30p	*RIP36A	270p	*N2926B	22p	*BCY70	18p	*RIP36C	340p	*N2926B	22p	*BCY71	22p	*RIP37A	65p	*N2926B	22p	BD124	130p	*RIP31B	65p	*N2926B	22p	BD131	63p	*RIP31C	78p	*N2926B	22p	BD132	65p	*RIP42A	70p	*N2926B	22p	BD135	48p	*RIP42B	70p	*N2926B	22p	*BD136	50p	*RIP42C	72p	*N2926B	22p	*BD139	52p	*RIP2955	82p	*N2926B	22p	*BD140	58p	*IS93	30p	*N2926B	22p	*BD20	125p	*IX108	10p	*N2926B	22p	*BD32	200p	*IX300	13p	*N2926B	22p	BF115	22p	*IX502	15p	*N2926B	22p	BF167	23p	*IX502	18p	*N2926B	22p	BF170	23p	*N457A	190p	*N2926B	22p	BF173	25p	*N697	22p	*N2926B	22p	BF177	28p	*N698	45p	*N2926B	22p	BF178	28p	*N706	20p	*N2926B	22p	BF179	33p	*N708	20p	*N2926B	22p	BF180	33p	*N918	40p	*N2926B	22p	BF184	32p	*N930	18p	*N2926B	22p	*BF194	10p	*N1131	18p	*N2926B	22p	*BF196	9p	*N1132	18p	*N2926B	22p	*BF197	15p	*N1304	65p	*N2926B	22p	BF200	32p	*N1306	75p	*N2926B	22p	BF257	32p	*N1307	75p	*N2926B	22p	BF258	36p	*N1308	50p	*N2926B	22p	BF259	38p	*N1309	50p	*N2926B	22p	BF337	30p	*N1613	25p	*N2926B	22p	*BF339	30p	*N1711	25p	*N2926B	22p	*BF340	30p	*N1893	30p	*N2926B	22p	*BF341	30p	*N2102	55p	*N2926B	22p	*BF342	30p	*N2219	20p	*N2926B	22p	*BF343	30p	*N2222	20p	*N2926B	22p	*BF344	30p	*N2369	14p	*N2926B	22p	*BF345	30p	*N2484	25p	*N2926B	22p	*BF346	30p	*N2904A	25p	*N2926B	22p	*BF347	30p	*N2905A	25p	*N2926B	22p	*BF348	30p	*N2906A	24p	*N2926B	22p	<h3>DIODES</h3> <table border="0"> <tr><td>*B810</td><td>25p</td></tr> <tr><td>*BY126</td><td>12p</td></tr> <tr><td>*BY127</td><td>10p</td></tr> <tr><td>IN4001</td><td>50p</td></tr> <tr><td>IN4002</td><td>5p</td></tr> <tr><td>IN4004</td><td>6p</td></tr> <tr><td>IN4005</td><td>6p</td></tr> <tr><td>IN4007</td><td>7p</td></tr> <tr><td>IN5401</td><td>13p</td></tr> <tr><td>IN5404</td><td>18p</td></tr> <tr><td>IN5407</td><td>23p</td></tr> </table> <h3>ZENER</h3> <table border="0"> <tr><td>2.7 V to 33V*</td><td>9p</td></tr> <tr><td>*1W</td><td>18p</td></tr> </table> <h3>NOISE</h3> <table border="0"> <tr><td>*Z5J</td><td>110p</td></tr> </table> <h3>BRIDGE RECTIFIERS</h3> <table border="0"> <tr><td>*1A 50V</td><td>22p</td></tr> <tr><td>*1A 100V</td><td>24p</td></tr> <tr><td>*1A 200V</td><td>28p</td></tr> <tr><td>*1A 400V</td><td>30p</td></tr> <tr><td>*1A 600V</td><td>36p</td></tr> <tr><td>*2A 50V</td><td>39p</td></tr> <tr><td>*2A 100V</td><td>35p</td></tr> <tr><td>*2A 200V</td><td>40p</td></tr> <tr><td>*2A 400V</td><td>47p</td></tr> <tr><td>*2A 600V</td><td>45p</td></tr> <tr><td>*3A 200V</td><td>60p</td></tr> <tr><td>*3A 600V</td><td>72p</td></tr> <tr><td>*1A 100V</td><td>84p</td></tr> <tr><td>*2A 100V</td><td>90p</td></tr> <tr><td>*6A 50V</td><td>96p</td></tr> <tr><td>*6A 100V</td><td>96p</td></tr> <tr><td>*6A 200V</td><td>108p</td></tr> <tr><td>*6A 400V</td><td>120p</td></tr> <tr><td>10A 400V</td><td>200p</td></tr> <tr><td>25A 400V</td><td>270p</td></tr> </table> <h3>TRIACS</h3> <table border="0"> <tr><td>Antip volts</td><td>85p</td></tr> <tr><td>3 400</td><td>99p</td></tr> <tr><td>6 400</td><td>99p</td></tr> <tr><td>6 500</td><td>107p</td></tr> <tr><td>10 400</td><td>120p</td></tr> <tr><td>15 500</td><td>180p</td></tr> <tr><td>15 400</td><td>130p</td></tr> <tr><td>15 500</td><td>180p</td></tr> <tr><td>15 400</td><td>130p</td></tr> <tr><td>15 400</td><td>130p</td></tr> <tr><td>15 400</td><td>130p</td></tr> <tr><td>15 400</td><td>130p</td></tr> <tr><td>15 400</td><td>130p</td></tr> <tr><td>15 400</td><td>130p</td></tr> </table>	*B810	25p	*BY126	12p	*BY127	10p	IN4001	50p	IN4002	5p	IN4004	6p	IN4005	6p	IN4007	7p	IN5401	13p	IN5404	18p	IN5407	23p	2.7 V to 33V*	9p	*1W	18p	*Z5J	110p	*1A 50V	22p	*1A 100V	24p	*1A 200V	28p	*1A 400V	30p	*1A 600V	36p	*2A 50V	39p	*2A 100V	35p	*2A 200V	40p	*2A 400V	47p	*2A 600V	45p	*3A 200V	60p	*3A 600V	72p	*1A 100V	84p	*2A 100V	90p	*6A 50V	96p	*6A 100V	96p	*6A 200V	108p	*6A 400V	120p	10A 400V	200p	25A 400V	270p	Antip volts	85p	3 400	99p	6 400	99p	6 500	107p	10 400	120p	15 500	180p	15 400	130p	15 500	180p	15 400	130p	15 400	130p	15 400	130p	15 400	130p	15 400	130p	15 400	130p
7400	16p	74109	89p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7400	28p	74110	55p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7400	33p	74111	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7400	33p	74112	96p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7401	18p	74116	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7402	18p	74118	84p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7403	18p	74120	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7404	23p	74121	32p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7404	36p	74122	54p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7405	25p	74123	76p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7406	43p	74125	73p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7407	43p	74126	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7408	25p	74128	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7409	27p	74132	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7410	18p	74136	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7410	28p	74141	72p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7411	24p	74142	35p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7412	25p	74145	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7413	36p	74147	190p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7414	35p	74148	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7416	33p	74150	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7417	36p	74151	72p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7420	18p	74153	85p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7421	40p	74154	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7422	22p	74155	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7423	37p	74156	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7425	30p	74157	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7427	37p	74158	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7428	36p	74159	190p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7430	18p	74160	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7432	36p	74161	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7437	36p	74162	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7438	36p	74163	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7440	19p	74164	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7441	75p	74165	220p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7442	70p	74166	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7443	140p	74167	340p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7444	140p	74170	250p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7445	120p	74172	720p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7446	150p	74173	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7447	80p	74174	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7448	80p	74175	85p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7450	18p	74176	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7451	20p	74177	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7452	20p	74179	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7453	20p	74180	110p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7454	18p	74181	298p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7460	18p	74182	82p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7470	36p	74185	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7472	30p	74186	920p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7473	34p	74190	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7474	34p	74191	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7475	45p	74192	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7476	36p	74193	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7480	50p	74194	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7481	95p	74195	95p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7482	90p	74196	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7483	90p	74197	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7484	110p	74198	250p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7485	120p	74199	250p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7486	34p	74221	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7489	320p	74251	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7490	40p	74265	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7491	85p	74278	290p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7492	55p	74279	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7493	40p	74283	190p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7494	90p	74290	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7495	70p	74293	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7496	84p	74298	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7497	340p	74365	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
74100	120p	74366	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
74104	65p	74390	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
74105	65p	74390	250p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
74107	36p	74393	225p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
CD4000AE	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4001AE	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4002AE	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4006AE	95p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4007AE	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4009AE	61p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4011AE	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4012AE	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4013AE	55p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4015AE	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4016AE	50p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4017AE	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4018AE	110p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4019AE	52p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4020AE	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4022AE	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4023AE	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4024AE	80p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4025AE	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4026AE	170p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4027AE	65p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4028AE	98p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4029AE	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4030AE	55p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4040AE	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4042AE	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4043AE	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4046AE	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4047AE	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4049AE	63p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4050AE	57p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4054AE	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4055AE	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4056AE	135p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4060AE	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4069AE	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4071AE	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4072AE	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4073AE	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4081AE	21p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4082AE	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4093AE	95p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4510AE	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4511AE	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4516AE	112p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4518AE	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
CD4528AE	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
MC14553	525p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
1458	Dual Op Amp Int. Comp	8 pin DIL	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
301A	Ext. Comp.	8 pin DIL	36p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
3130	COSMOS/Bi-Polar MosFet	8 pin DIL	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
CA3140	BIMOS	8 pin DIL	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
LM318N	High speed	8 pin DIL	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
LM324N	Quad Op. Amp	14 pin DIL	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
3900	Quad. Op. Amp.	14 pin DIL	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
709	Ext. Comp.	8/14 pin DIL	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
741	Int. Comp.	8/14 pin DIL	32p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
747	Dual 741	14 pin DIL	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
748	Ext. Comp.	8/14 pin DIL	36p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
776	Programmable Op. Amp.	TO-5	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
AC125	25p	BFX86	30p	*N2926B	7p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AC126	20p	BFX87	30p	*N2926B	10p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AC127	20p	BFX88	30p	*N2926B	12p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AC128	18p	BFY50	22p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AC141	20p	BFY51	22p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AC142	20p	BFY52	22p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AC176	20p	BFY90	120p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AC187X	25p	BRV39	45p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AC188	20p	BSX20	20p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AC188K	25p	*BU105	140p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AD149	49p	*BU108	250p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AD161	45p	*MJE340	85p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AF162	45p	*MJE341	85p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AF174	20p	*MJE342	85p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AF175	20p	*MJE2501	225p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AF176	20p	*MJE2955	120p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AF177	20p	*MJE2955	130p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AF178	25p	*MJE3001	225p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AF195	43p	*MJE3005	75p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
AF239	48p	*MPS006	90p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BC107 B	9p	*MPSA12	50p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BC108 B	9p	*MPSA56	32p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BC109 B	10p	*MPSU06	62p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BC109C	12p	*MPSU56	78p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC117	22p	OC28	120p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC147	9p	OC35	90p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC148	9p	OC36	90p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC149C	10p	*OC71	20p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC157	11p	*R2008B	200p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC158	10p	*R2010B	200p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC159	11p	*RIP29A	40p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC163C	12p	*RIP29C	55p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC172	11p	*RIP30A	48p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC177	18p	*RIP30C	60p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC178	17p	*RIP31A	52p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC179	18p	*RIP31C	52p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC182	12p	*RIP32A	58p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC183	13p	*RIP32C	58p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC187	30p	*RIP33A	90p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC212	11p	*RIP33C	115p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC213	10p	*RIP34A	115p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC214	14p	*RIP35A	160p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC461	30p	*RIP42A	290p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BC478	30p	*RIP36A	270p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BCY70	18p	*RIP36C	340p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BCY71	22p	*RIP37A	65p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BD124	130p	*RIP31B	65p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BD131	63p	*RIP31C	78p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BD132	65p	*RIP42A	70p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BD135	48p	*RIP42B	70p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BD136	50p	*RIP42C	72p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BD139	52p	*RIP2955	82p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BD140	58p	*IS93	30p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BD20	125p	*IX108	10p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BD32	200p	*IX300	13p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF115	22p	*IX502	15p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF167	23p	*IX502	18p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF170	23p	*N457A	190p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF173	25p	*N697	22p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF177	28p	*N698	45p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF178	28p	*N706	20p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF179	33p	*N708	20p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF180	33p	*N918	40p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF184	32p	*N930	18p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF194	10p	*N1131	18p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF196	9p	*N1132	18p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF197	15p	*N1304	65p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF200	32p	*N1306	75p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF257	32p	*N1307	75p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF258	36p	*N1308	50p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF259	38p	*N1309	50p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
BF337	30p	*N1613	25p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF339	30p	*N1711	25p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF340	30p	*N1893	30p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF341	30p	*N2102	55p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF342	30p	*N2219	20p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF343	30p	*N2222	20p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF344	30p	*N2369	14p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF345	30p	*N2484	25p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF346	30p	*N2904A	25p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF347	30p	*N2905A	25p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*BF348	30p	*N2906A	24p	*N2926B	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
*B810	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*BY126	12p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*BY127	10p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
IN4001	50p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
IN4002	5p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
IN4004	6p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
IN4005	6p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
IN4007	7p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
IN5401	13p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
IN5404	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
IN5407	23p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
2.7 V to 33V*	9p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*1W	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*Z5J	110p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*1A 50V	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*1A 100V	24p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*1A 200V	28p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*1A 400V	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*1A 600V	36p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*2A 50V	39p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*2A 100V	35p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*2A 200V	40p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*2A 400V	47p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*2A 600V	45p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*3A 200V	60p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*3A 600V	72p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*1A 100V	84p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*2A 100V	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*6A 50V	96p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*6A 100V	96p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*6A 200V	108p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*6A 400V	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
10A 400V	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
25A 400V	270p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
Antip volts	85p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
3 400	99p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
6 400	99p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
6 500	107p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
10 400	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15 500	180p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15 400	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15 500	180p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15 400	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15 400	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15 400	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15 400	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15 400	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15 400	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
<h3>VOLTAGE REGULATORS - FIXED - PLASTIC</h3> <table border="0"> <tr><td>1 Amp Positive</td><td>1 Amp Negative</td></tr> <tr><td>5V 7805</td><td>140p</td></tr> <tr><td>12V 7812</td><td>140p</td></tr> <tr><td>15V 7815</td><td>140p</td></tr> <tr><td>18V 7818</td><td>140p</td></tr> <tr><td>24V 7824</td><td>140p</td></tr> <tr><td>LM309K 1 Amp 5V</td><td>103 140p</td></tr> <tr><td>LM309H 100mA 5V</td><td>TO5 75p</td></tr> <tr><td>TBA625B 12V 0.5A</td><td>TO5 120p</td></tr> </table> <h3>VARIABLE VOLTAGE REGULATOR</h3> <p>723 2V to 37V 150mA 14 pin DIL 45p</p> <h3>DUAL VOLTAGE REGULATOR</h3> <p>1468 ±15V 100mA 16 pin DIL 300p. (Adjustable by resistors from ± 8V to ± 20V).</p> <h3>LOW PROFILE DIL SOCKETS BY TEXAS</h3> <p>8 pin 13p, 14 pin 14p, 16 pin 15p, 18 pin 36p, 22 pin 40p, 24 pin 50p, 28 pin 60p, 40 pin 75p.</p>	1 Amp Positive	1 Amp Negative	5V 7805	140p	12V 7812	140p	15V 7815	140p	18V 7818	140p	24V 7824	140p	LM309K 1 Amp 5V	103 140p	LM309H 100mA 5V	TO5 75p	TBA625B 12V 0.5A	TO5 120p	<h3>TEXAS 75 SERIES</h3> <table border="0"> <tr><td>75107</td><td>160p</td></tr> <tr><td>75450</td><td>120p</td></tr> <tr><td>75451</td><td>160p</td></tr> <tr><td>75452</td><td>72p</td></tr> <tr><td>75453</td><td>72p</td></tr> <tr><td>75454</td><td>72p</td></tr> </table>	75107	160p	75450	120p	75451	160p	75452	72p	75453	72p	75454	72p	<h3>LINEAR I.C.s</h3> <table border="0"> <tr><td>*AY 1-0212</td><td>Tone Generator</td><td>16 pin DIL</td><td>600p</td></tr> <tr><td>*CA3023A</td><td>Diff Cascade Array</td><td>105</td><td>95p</td></tr> <tr><td>ICA3046</td><td>5 Transistor Array</td><td>14 pin DIL</td><td>200p</td></tr> <tr><td>*CA3046B</td><td>Quad Low Noise Amp</td><td>16 pin DIL</td><td>200p</td></tr> <tr><td>*CA3053</td><td>Diff Cascade Amp</td><td>705</td><td>70p</td></tr> <tr><td>*CA3080E</td><td>Op Transcond Amp</td><td>8 pin DIL</td><td>90p</td></tr> <tr><td>*CA3089E</td><td>FM IF System</td><td>16 pin DIL</td><td>225p</td></tr> <tr><td>*CA3090</td><td>FM stereo Multi Dec</td><td>16 pin DIL</td><td>400p</td></tr> <tr><td>ICL8038CC</td><td>VCO Fun Gen</td><td>14 pin DIL</td><td>340p</td></tr> <tr><td>LM339N</td><td>Vol Quad Comp</td><td>14 pin DIL</td><td>200p</td></tr> <tr><td>LM377N</td><td>Quad 2W Aud Amp</td><td>14 pin DIL</td><td>175p</td></tr> <tr><td>CD4030A</td><td>2W Audio Amp</td><td>14 pin DIL</td><td>95p</td></tr></table>	*AY 1-0212	Tone Generator	16 pin DIL	600p	*CA3023A	Diff Cascade Array	105	95p	ICA3046	5 Transistor Array	14 pin DIL	200p	*CA3046B	Quad Low Noise Amp	16 pin DIL	200p	*CA3053	Diff Cascade Amp	705	70p	*CA3080E	Op Transcond Amp	8 pin DIL	90p	*CA3089E	FM IF System	16 pin DIL	225p	*CA3090	FM stereo Multi Dec	16 pin DIL	400p	ICL8038CC	VCO Fun Gen	14 pin DIL	340p	LM339N	Vol Quad Comp	14 pin DIL	200p	LM377N	Quad 2W Aud Amp	14 pin DIL	175p	CD4030A	2W Audio Amp	14 pin DIL	95p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																								
1 Amp Positive	1 Amp Negative																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
5V 7805	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
12V 7812	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
15V 7815	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
18V 7818	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
24V 7824	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
LM309K 1 Amp 5V	103 140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
LM309H 100mA 5V	TO5 75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
TBA625B 12V 0.5A	TO5 120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
75107	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
75450	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
75451	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
75452	72p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
75453	72p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
75454	72p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
*AY 1-0212	Tone Generator	16 pin DIL	600p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
*CA3023A	Diff Cascade Array	105	95p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
ICA3046	5 Transistor Array	14 pin DIL	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
*CA3046B	Quad Low Noise Amp	16 pin DIL	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
*CA3053	Diff Cascade Amp	705	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
*CA3080E	Op Transcond Amp	8 pin DIL	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
*CA3089E	FM IF System	16 pin DIL	225p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
*CA3090	FM stereo Multi Dec	16 pin DIL	400p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
ICL8038CC	VCO Fun Gen	14 pin DIL	340p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
LM339N	Vol Quad Comp	14 pin DIL	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
LM377N	Quad 2W Aud Amp	14 pin DIL	175p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
CD4030A	2W Audio Amp	14 pin DIL	95p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					

'Wenden' range modular amplifiers

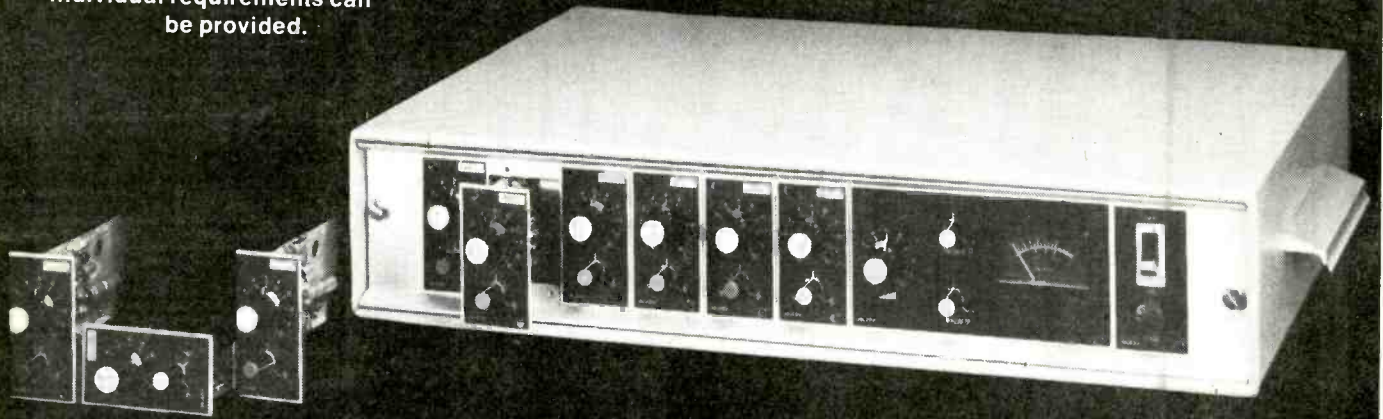A range of communications amplifiers having power ratings from 15 to 200 watts, plug-in input facilities ensure individual requirements can be provided.



Manufacturers of sound systems and electronics

Station Road, Wenden
Saffron Walden
Essex CB11 4LG
Saffron Walden
(0799) 40888


audix

3% Measuring Accuracy
Stabilised Power Supplies
10 MHz Dual Trace
10 mV Sensitivity

SCOPEX 4D10A

Now YOU can afford the Best at

£175
UK ex VAT

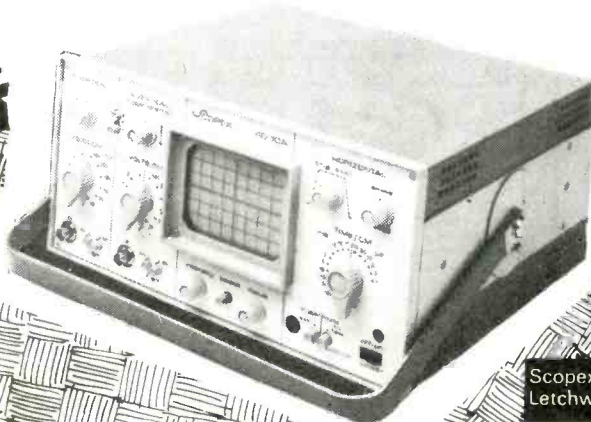

SCOPEX

Scopex Instruments Limited, Pixmore Industrial Estate, Pixmore Avenue, Letchworth, Herts. SG6 1JJ Letchworth 72771 (STD 046 26)

<p>MARCONI TF675F WIDE RANGE PULSE GENERATOR +/- variable outputs up to 50V. Optional delay. Small compact unit £18 ea.</p>	<p>ROYAL INVERTORS manufactured USA. 28V. DC Input. Output 115V AC 400HZ up to 2KVA. Brand new. Crated £12.50 ea.</p>	<p>MARCONI NOISE GENERATOR TF987/1 4 Ranges 0-5, 0-10, 0-15, 0-30. Due to large purchases now priced at £15 ea.</p>	<p>AVO TRANSISTOR ANALYSER CT446 Suitcase style NOW £27.50 each</p>
---	---	---	---

<p>FOR THE VDU BUILDER. New stock of Large Rectangular Screen 30 x 20cm tube. Type M38 at the ridiculous price of £4 each. And also still available the CME1220, 24 x 15cm at £9 ea. Base connections for both tubes supplied.</p>	<p>WE ARE BREAKING COMPUTERS UNIVAC/HONEYWELL/ICL 1900 etc. Boards. Power Supplies. Core Stores are available CALL AND SEE</p>	<p>EDWARDS HIGH VACUUM PUMPS Type 1SC30 @ £55 each. Type ES35 @ £45 each Carriage £2.50</p>
---	--	--

<p>UNIVAC MAGNETIC TAPE UNITS Complete with heads and 10 reels of tape £77.50 Carriage paid</p>	<p>1/2" MAG TAPE Approx. 2,000ft. NOW 25p each P&P £1</p>
---	---

<p>R&S DIAGRAPH & GENERATOR 3-300MHZ. Very nice condition £440. PHODE & SCHWARZ ADMITTANCE METER BN3511. As new £65. POLARAD RECEIVER Model FIM-B2. Complete 1-10GHZ £375. MARCONI OSCILLATOR TF1101 20HZ-20KHZ. Nice condition. Special price £50. MARCONI Wide Range Oscillator TF1370. Freq. range 10HZ to 10MHZ. Sine Wave 10HZ to 100KHZ. Square Wave. High outputs up to 31 6V. Fantastic value at £90 ea. MARCONI ADAPTOR TM6113 for TF2700. TF1313. TF8668B £20 ea. AIRMEC 4 trace scope Type 279. Large screen £95. MARCONI TF142F DISTORTION FACTOR METER giving percentage distortion on a directly calibrated dial and includes an spurious components up to 30KHZ £29.50 ea. MARCONI PORTABLE FREQUENCY METER TF1026/11. 100 to 160MHZ. Very fine condition £25. DECCA NAVIGATOR DISPLAY UNIT. Very impressive £12.50 ea. COURTENAY MAJOR Mk. 2. 250 joules. 5 outputs. Can be combined — 1250 joules. No heads. £30. MARCONI SIGNAL GENERATORS. TF801B from £140; TF801D £240. Usually available ex-stock</p>	<p>AIRMEC MODULATION METER 210 £95. HILGER & WATTS SPECTROMETER H1170 £240 RHODE & SCHWARZ Tunable Indicating Amplifier UBM £75 TEKTRONIX 180A Time Marker Generator £55 S.E. Labs Oscilloscope Type 102 £220 GENERAL RADIO PULSE SWEEP & TIME DELAY GENERATOR Type 1391B £120</p>
--	--

SPECTRUM ANALYSER by NELSON ROSS. Plug-in for TEKTRONIX Oscilloscopes 561/506 etc. Freq 0-500KHZ **£225.**

ITEMS OFTEN AVAILABLE

CORE STORES with Drivers from **£100.**
Some small RAM Boards from **£15.**
DISK PACK — new singles **£20 each.**
Good used **TWIN PACKS** **£10 each.**
Good used **MULTI PACK** **£25 each.**
CORE PLANES (no drivers) from **£5.**
HEADS for **PACKS** (individual) **£15 each.**
P.C. MOTORS (Disk Drives?) **£15 each.**

RHODES & SCHWARZ POWER METER. BNRD-BN2412/50 **£50.**
MARCONI RF POWER METER. TF1020A/1.50 ohm **£65.**
HEWLETT PACKARD 11 Channel Numerical Printer **£30.**
I.C. TESTER by SCHLUMBERGER. Model TCL232 — tests 741, 709, etc. Dual in lines; flat packs or TOs **£65 ea.**

SOLARTRON CD1212 SB 40 meg. **£85.** DB 24 meg. twice **£120.** Many other types available.
Ex-Ministry OSCILLOSCOPE. CT436 Double beam DC 6MHZ **£95 ea.**
***TELEPHONES.** Post Office style 746. Black or two-tone grey **£6.50 ea.** Modern style 706. Black or two-tone grey **£4.50 ea.** P&P 75p each. Old black style **£1.50 ea.** P&P 75p.
TELEPHONE EXCHANGES. eg. 15-way automatic (exchange only) from **£95.**
MODERN FANS. 4 3/4 x 4 3/4 x 1 1/2". 240 Volts. Superbly quiet. 6 blades. **£4.50 ea.** P&P 75p.
PAPST Model 240V available at **£7.50 ea.** P&P 75p.
PHOTOMULTIPLIER Type 931A **£4 ea.** P&P 75p. Other types available.
***POTENTIOMETERS** — All **5p ea.** P&P extra. Metal bodied AB Linear, PCB Mount. Brand new. 10K, 100K ganged, 250K ganged, 100K ganged, concentric shafts.
***BEEHIVE TRIMMERS** 3/30pf. Brand New 10 off **£40p** P&P 15p; 100 off **£3.50,** P&P 75p. 500 off **£15,** P&P £1.25. 1,000 off **£25,** P&P £1.50.
LARGE RANGE OF ELECTROSTATIC VOLTMETERS. From 0-300V 2" **£3,** to 20KV Max. General guide 5KV 3 1/2" **£5.** Thereafter **1p per KV.** P&P 75p.
VARIACS 240V input 0-240V. output 8A **£18 ea.** 20A **£30 ea.** Carr. **£2.50.**
E.H.T. TRANSFORMERS 20KV 2KVA **£70 ea.** Many other EHT transformers and EHT Capacitors available.
DON'T FORGET YOUR MANUALS. S.A.E. with requirements.
TUBE Type DB7/36 — Replacement for Teleequipments S31 **£11 ea.** P&P **£1.50.**

PICK-A-PACK — 50 PENCE A POUND

FROM OUR "PICK-A-PACK" AREA WEIGH UP YOUR OWN COMPONENTS
NO RESTRICTIONS ON WHAT YOU TAKE

<p>SUPERB PROFESSIONAL VDU CASES, size 23" x 16" x 27" on stands. Hammer grey. BRAND NEW SCHLUMBERGER Surplus £35 each. Carriage £2.50</p>	<p>EX-DYNAMCO Oscilloscopes INVERTORS 30V Input 6KV Output. Size 2" x 4 1/2" x 1 1/2" Complete with circuit £10 each. P&P £1</p>	
<p>LINE PRINTERS — VARIOUS MODELS £100 each. Carriage £15 Size approx 4' 4" x 3' x 4' high</p>	<p>C.D.C. DISK DRIVES TWIN E.D.S. Single phase — air conditioning not essential. Guaranteed fine condition £240 each. Complete with copy of manual and 50 packs. Size approx. 2' x 2' 10" x 3' 6" high.</p>	<p>A LARGE QUANTITY OF MISCELLANEOUS TEST GEAR, CHASSIS, UNITS, etc., on view at LOW COST.</p>
<p>MINIATURE — OXLEY PATCH PANELS — BRAND NEW EX-DYNAMCO 10 x 10 complete with pins. £8 each. P&P 50p</p>		

SURPLUS — BRAND NEW — REPLACEMENT TUBES FOR DYNAMCO 7100 SERIES OSCILLOSCOPES TYPE BRIMAR D13-SIGH

Mesh P.D.A. Transistor Scan Wide Bandwidth 60MHZ + Rectangular 6 x 10cm — 1KV EHT X Sensitivity 15V/CM. Y Sensitivity 6V/CM Standard heaters. Length 13 1/4"

THIS IS A MUST AS A SPARE FOR THE DYNAMCO 7100 SCOPE OR IDEAL FOR THE HIGH QUALITY TRANSISTOR SCOPE BUILDER

At **£65 each.** Carriage **£2.50**

To Tube purchasers only. Numetal Shields at **£2.50**
ALSO AVAILABLE TUBE TYPE BRIMAR D10-210GH/32 Rectangular 7 x 5cm Mesh P.D.A. Short 9 1/4". 30MHZ + Sensitivity x 14V/CM. Y 10V/CM. BRAND NEW at **£70 each.** Carriage **£2.50**

DATA LOGGER by DYNAMCO





These are BRAND NEW — not finished — DATA LOGGERS BY DYNAMCO

They are completed but for the plug-in boards. The case with hinged lid is quite superb and extremely adaptable. It contains as well as the mother board an equally superb Power Supply with the following voltages +28V; +15V; +5V (2.5A) — this supply is crowbar protected; —5V; —14V; —20V; —24V; —48V and other supplies including auto 110V. This unit supplied in its original cardboard box complete with original manual and must be of serious interest to the professional constructor and anyone considering the construction of a micro processor system. Unit size 7 1/2" high x 19" wide x 23" deep

Price **£45 each.** Carriage **£2.50**

<p>PICK-A-PIECE — 50 PENCE EACH FROM OUR "PICK-A-PIECE" AREA</p>	<p>PICK-A-METER — £1 EACH A LARGE SELECTION OF BRAND NEW AND EX-EQ. METERS</p>
---	---

Minimum Mail Order **£2.** Excess postage refunded. **Unless stated — please add £2.75 carriage to all units**
VALUE ADDED TAX not included in prices — Goods marked with * 12 1/2% VAT, otherwise 8%
Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order
Open 9 a.m. to 5.30 p.m. Mon. to Sat.


7/9 ARTHUR ROAD, READING, BERKS (rear Tech. College, King's Road). Tel. Reading 582605

MICRO AMPLIFIER



Ex behind the ear hearing aids complete with volume control **£2.16.**

VEEDER-ROOT COUNTER



6 Digit 230-250v cycle operated, not resettable also needs perspex or similar panel over the wheels **£1.62.**

PP3/PP9 REPLACEMENT MAINS UNIT



Japanese made in plastic container, with leads size 2" x 1 1/2" x 1 1/2", this is ideal to power a calculator or radio, it has a full wave rectified and smoothed output of 9 volts suitable for a loading of up to 100mA **£2.53.**

DIGITAL DISPLAY UNIT (DIGIVISOR)



A precision made instrument which is basically a moving coil voltmeter. Instead of having a pointer, however, the scale is punched out with numerals, 0, 1, 2, 3, 4 and so on. When you apply a voltage for instance 8 volts — fig 8 comes in front of a lamp and is focused on to the front screen. This device which must have cost a small fortune to develop and make can also be used for a variety of other purposes. Voltage regulation for instance by making beam of light trigger a photocell, etc. **£5.40.**

MERCURY BATTERIES



Bank of 7 Mercury cells type 625 which are approx. 3/8" diameter by 3/8" thick in plastic tube giving a total of 10.7 volts. Being in a plastic tube it is very easy to break up the battery into separate cells and use these for radio control and similar equipment. Carton of 25 batteries **£1.60.**

LATCHING RELAY



by Guardian Electric, mains operated it is in fact two relays mounted on a metal base plate. The relays being mounted in such a way to ensure that when one closes the other opens and vice versa thus when closed relay A would remain locked until manually released or electrically released by energising relay B. Each relay has 2 sets of 10 amp changeover contacts. Should be ideal for burglar alarms and similar applications. **£2.11.**

24 HOUR MOTOR



beautifully made by Sangamo. This is 200-240v mains driven motor with gear box together in one housing, size approx. 1 1/4" dia by 1 1/4" deep. If you are contemplating making a 24 hour switch with a lot of on offs then this is obviously the motor. **Price £1.88.**

4 POLE MOTOR



Carefully balanced fitted with belt drive pulley for tape recorders, etc. Normal mains working, speed 1 250 rpm. **£2.12.**

HUMIDITY SWITCH



American made by Ranco, their type No J11. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive microswitch adjustable by a screw. Quite sensitive — breathing on it for instance will switch it on. Micro 3 amp at 250v AC. Overall size of the device approx. 3 3/4" long, 1" wide and 1 1/2" deep **65p.**

RECTANGULAR HOT PLATE



Aluminium panel with ridged top and angled underneath to strengthen it. This is approx. 10" x 4 1/2" of flat plate. Beneath please is 100w element and sensor switch which will maintain the surface of the plate just too hot to touch. With leads and tags. This is ideal if you are making up a food warmer or for an airing cupboard etc. **Price £1.03.**

EXTRACTOR FAN



Ex computers — made by Woods of Colchester ideal for fixing through panel — reasonably quiet running very powerful 2500 rpm. Choice of two sizes: 5" or 6 1/2" dia. **£4.43.**



ROTARY WAFER SWITCH

—wiper contacts 3 way 8 poles, 5 amp rating, break before make — 1/4" diameter 1" long spindle, slotted for knob screw, made by Plessey. **Price £1.08.**



PERSPEX ENCLOSED 12 VOLT RELAY

with 10 amp changeover contacts, size approx. 2" x 1" x 2 1/2" in case **£1.08.**

PAPST MOTORS

West German make, these fine motors are noted for their performance and reliability. Special features are the rotating heavy outer which acts as a flywheel to eliminate wow and flutter and switchable reversing. We have four types in stock, all 1350 revs., including starting capacitor.



- (1) Ref No. KLZ 20 50.4, 230 volts 50HZ **£6.30.**
- (2) Ref No. KLZ 32 50.4, 230 volts 50HZ **£7.28.**
- (3) Ref same as above, 115 volts 50HZ **£3.30.**
- (4) Ref same as above, 110 volts 60HZ **£3.30.**

HONEYWELL P.B. MICROSWITCH

1, 2 or 3 10 amp 250v change over microswitch thro panel mounting by cock nuts, 1" dia black knob 1 switch **40p**, 2 switch **55p**, 3 switch **70p.**



INSULATED TERMINALS



Well made with metal, panel insulators — screw down to trap wire or insert 4mm plug into top — **15p each**, following colours available

EDGE MOUNTING MOVING COIL METER

100VA fsd. Size 3" x 2" Sealed D/B made for G.P.O. new and unused **£3.60.**




50 VA MOVING COIL PANEL METER

Large 3 1/2" square flush mounting — mirrored scale for accurate reading scaled DB — beautiful instrument made for G.P.O. new and unused **£4.50.**

SPIT MOTOR WITH CARTER GEAR BOX

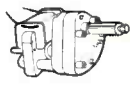Probably one of the best spit motors made. Originally intended to be used in very high priced cookers, however this can be put to plenty of other uses. For instance your garden barbecue or to drive a tumbler for stone polishing, in fact there are no instances to its uses. Normal mains operation. **£3.25** including POST & VAT



ELECTRO MAGNETIC MECHANISMS



4v-8v AC operated the electro mag easily removable from mechanism **50p each** — two types available.



TERMS

Cash with order — delivery same day as order received. Prices includes VAT and carriage unless stated but orders under £6 must add 50p to off-set packing etc. **BULK ENQUIRIES WELCOMED**

J. BULL (ELECTRICAL) LTD.

(Dept. WW)

103 TAMWORTH ROAD CROYDON CR9 1SG

IT'S FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived — often bargains which sell out before our advertisement can appear — it's an interesting list and it's free — just send S.A.E. Below are a few of the Bargains still available from previous lines.

Digital Thumbwheel Switch. Black face flush panel mounting, face size approx. 3 1/4" x 1 1/4". White digits 10 positions 0-9. These can be stacked edge-wise to any quantity. The right hand and left hand ends have projections for 6BA fixing to the panel. Price left-hand and right hand end switches £1.50 each + 12p. Intermediate switches £1.25 + 10p.

Mains Transformer upright mounting with top tagboard, primary 0.115, 210, 240, two secondaries, 15 volts 5mA, and 8.5 volt 1.25A. Note this transformer is ex-new equipment. Price £2.00 + 16p Post 30p + 2p.

Mains Transformer, primary 0.110, 127, 150, 180, 220. Secondaries (1) 3 15-0.3 15 (2) 2 5v, (3) 0-220v. Fitted primary screen. This is a 30w transformer, ex equipment £2.50 + 20p Post 40p + 3p.

Relay 6-12 volt. Single 2 amp changeover contacts, open miniature type, size approx. 1" cube P.C. mounting ex new equipment 30p + 2p.

Relay Miniature 6-12 volt plastic covered plug in type 4 changeover, gold plated contacts 52 ohm coil, size approx. 1 1/4" high, 1" wide, 3/8" thick, ex new equipment with base 75p + 5p.

Miniature Relay 12 volt plastic covered plug in type 200 ohm coil. Two changeover gold plated contacts ex new equipment with base 75p + 6p.

Three Digit Counter, resettable 12 volt coil, flush panel mounting, black with white digits, ex new equipment £1.75 + 14p.

Reed relay with double wound coil 12 volts one coil will close the reed switch, 12 volts on the other coil will open the contact or still further close it depending upon whether the current is opposing or assisting. Price £1.50 + 12p. Post 20p + 2p.

Push on Push off Panel Mounting Switch. 3 amps, 250 volts metal plunger similar to and mounted light toggle switch made by Arrow, 50p + 4p.

Push make Switch 250v 1 amp similar to and mounted like a toggle made by Arco Electronic. Price 35p + 3p.

Panel Mounting Neon Lamp. Compact type with bright chrome type mounting clip, these will flash from voltages of 100 upwards but need a series resistor of about 250k higher or lower depending upon how bright you want them. Price 30p + 2p, these are red but we also have another slightly larger in natural colour, same price.

Relay, Clare Elliott 670 ohm. Coil sealed in metal can size approx. 1 1/4" by 1/2" x 1/2", two pairs of changeover contacts. This type of relay is mounted by its own leads. £1.00 + 8p.

Desk Instrument Case with sloping front, overall size of sloping front is 4 1/2" wide and 5 1/2" long. Mounted on a heavy base for stability base size 4 1/2" x 4 1/2" with flex lock. The heavy base is easily removed if not required. The average depth below sloping panel 3" approx. Price £1.50 + 12p. Post 50p + 4p. Note the sloping front will be supplied with each of these cases but this already has quite a lot of holes in it, however it is a simple matter to cut and bend new aluminium front if you use this as a pattern.

Multicore flex lead, 25 coloured coded cores in PVC outer, length 20p + 2p. Post 50p + 4p.

Combined flex lead and cable bush. Self adjusts for most sizes of circular mains lead. This is a two part device held to the back panel by means of a screw, the tightening of which firmly locks the cable which prevents it being pulled to the detriment of the internal connections. Price 25p + 2p.

Valve selector, comprises a 9 pin valve holder and an insulated plug with a shorting link which can be made to short together any pair of the valve holder contacts. Price 30p + 2p.

This Month's Special Bargain Offer consists fluorescent chokes and if you take advantage of it you will be buying at approx. one half of the manufacturer's quantity prices. Three popular sizes, type (a) 2ft 20w size 4 1/2" x 1 1/4", price 50p + 4p, type (b) 4ft 40w or 1 metre 40w size 6 1/2" x 1 1/4", x 1 1/2" 70p + 6p. Type (c) 5ft 85w size 6 1/2" x 2 1/4" x 1 1/4", price 90p + 8p. These prices are cut so keen that we cannot give our normal quantity discounts but if you purchase a minimum of 100 — can be mixed over 3 types — then we will give a special 10% discount.

Riponda 6" Mains Battery TV's for spares, these are less tubes and less knobs and will have one or two other parts missing but in the main are complete and worth having if you have one of these televisions or if you do repairs to them. Price £3.50 + 44p Post £1.00 + 12 1/2p.

25 Way Plug & Socket by McMurdo. The socket is panel mounting and the plug has a metal shield and cable clamp. Ex unused equipment 60p + 4p. Carriage £2.50 + 20p.

12 Way Plug & Socket, ditto Price 50p + 4p a pair. Remember 7029. We are rapidly running out of this and if you have not put any into stock then this could well be your last chance. The price for 100 metre coil £9.50 + 76p. Carriage £2.50 + 20p.

Engine Revolution Counter. This is ex-Air Ministry item, beautifully made, a revolution counter, it is driven by a flexible shaft and having a permanent magnet field the voltage output would be dependent upon the speed. Of course it will also run as a low voltage D.C. motor and its speed will be dependent upon the applied voltage. This is dustproof and almost waterproof so it will still run in adverse conditions. One point however, is there are no brushes fitted to these motors, these are special and as yet we have not been able to find a supplier, so you will buy without brushes. The Air Ministry ref. number of the motor is 6A/7A2. We would like to hear from any customer who met this during his service career and who knows of a possible source of brushes. Price £2.00 + 16p. Post 40p + 4p.

Miniature Sealed Thermistor, German made, these are about the size of early power transistors, have 4" wire ends and are sealed, so suitable for immersion in many liquids. Operating temperature 90 C plus or minus 3%. We were not sure of the operating voltage and current but we tested one with 100w lamp off the mains and it worked perfectly ok. Price 50p + 4p.

Goose-neck as used on adjustable table lamps, microphone stands, etc. Normal brass 1/2" thread each end length 18" chrome plated. Price 75p + 6p. Post 30p + 2p.

Nical Battery Charger in neat plastic case size 4 3/4" x 3 3/4" x 2 3/4" approx with mains input lead and charging output lead terminated with din plug. This is a dual output charger but contains useful mains transformer which makes it easily adaptable for many voltage cells. If not wanted as a charger, could very easily be rebuilt as a power unit for receiver or other device. The plastic case has a neon indicator. Price £2.50 + 20p. Post 40p + 4p.

Panel Meter, 2 1/2" made for Air Ministry unused but storage soiled 30mA moving coil offered at a low price but these have loose glasses which will need reglazing. Price £1.50 + 12p. Post 20p + 2p.

Papst Motor, ref. KLZ 20 50.4-5400. This is normal mains working motor, capacitor run so easily reversible. May be a little storage soiled but these are unused and fully guaranteed by us. Price £5.00 + 40p Post 30p + 2p.

Garrard 4 Pole Motor, probably made for record player or tape recorder, this is 140v, 40-60 cycle. We do not know the Garrard ref. no. but the figure 12 is pressed on the bottom bearing cover. Price £2.00 + 25p. Post 30p + 4p.

Silmerstat by Sunvic for 2500 watts, Sunvic ref. 230707/10776. This is a larger than usual silmerstat, dimensions approx. 2 1/4" square by 2 1/2" deep. Price £1.50 + 12p. Post 20p + 2p.

Smiths Time and Set Switch, 15 amp normal mains operated device intended for use with cookers, etc. which could be set to be switched on up to 14 hours in advance and for and up to one period of 4 hours. A very neat glass fronted instrument with centre control knob, size approximately 4 1/2" x 3 1/2" x 2 1/2" deep. The Smiths ref. No. GS7400. One of these is useful for your heating on your heating an hour or so before you come home so you come home to a warm house. Price £2.50 + 20p. Post 30p + 3p.

10 Amp 12 Way Connector Block, black PVC 30p each. £24 for 100.

Fluorescent Choke, polyester filled compact size 5" x 1 1/4" x 1 1/4" for 4ft, 40w tube. We are selling these in minimum quantity of 100 at a time, price 60p each + VAT @ 8% carriage at cost.

FANTASTIC GOLDRING SAVINGS

GOLDRING G103 Belt Drive Turntable

Famous name turntable slashed to near half price. Complete with plinth, cover and leads. Accepts any standard cartridge (not included)

FULL 12 MONTH GUARANTEE

OUR PRICE £29.95

R.R.P. £54 (+p/p & Ins £2.25)



SAVE OVER £24

Build your own GOLDRING CK2 Belt Drive Turntable


Beautifully engineered unit from the famous Goldring company, comes complete with instructions and all necessary parts. Ready to incorporate into your design plinth and cover. The pleasure of assembling your own deck.

(Plinth, cover and cartridge not included). Usually sold for £54.95 with plinth and cover.

Call in or send cheque, P.O., M.O., Access, Barclaycard, Diners Club or American Express Number.

ONLY £16.95 (+ p.p & Ins. £1.50)

ALL PRICES INC. VAT

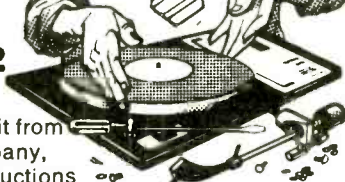

Sonic Sound Audio

248/250 TOTTENHAM COURT ROAD, LONDON W1. TEL: 01-637 1908

CIRCUIT SERVICES

BBC MATRIX H

We are offering a component kit comprising all resistors, capacitors, transistors, and diodes for this purpose built quadraphonic decoder. Price £20.00 including postage and packing. A pair of p.c.bs is available separately for £6.00 inclusive.

Other kits include the electrolytic capacitor tester (Wireless World, May 1977), and the sensitive metal detector (Wireless World, April 1977). Send s.a.e. for full list of parts and prices. **Mail order only to Circuit Services, 36 Hallowes Crescent, South Oxhey, Herts.**

Samson's (ELECTRONICS) LTD.

9 & 10 CHAPEL ST., LONDON, N.W.1
01-723 7851 01-262 5125
ADJACENT TO EDGWARE ROAD MET. LINE STATION

PLEASE ADD 8% TO ALL ORDERS INC. CARR.

CURRENT RANGE OF NEW L.T. TRANSFORMERS OPEN TYPE TAG CONNECTIONS ALL PRIMARIES 220-240V

Type	Sec Taps	Amps	Price	Carr
1	24-30-40-48-60v	12	£24.50	£2.00
2	24-30-40-48-60v	10	£22.31	£2.00
3	24-30-40-48-60v	8	£18.11	£1.75
4	24-30-40-48-60v	5	£12.47	£1.75
5	24-30-40-48-60v	3	£9.30	£1.00
6	24-30-40-48-60v	2	£6.60	£1.00
	6.8-10-12-16-18-20-24-36-40-48-60v			
CAN BE OBTAINED FROM THE ABOVE RANGE				
7	19-25-33-40-50v	10	£20.41	£2.00
8	19-25-33-40-50v	6	£14.62	£1.50
9	19-25-33-40-50v	3	£7.81	£1.25
10	19-25-33-40-50v	2	£6.10	£1.00
	5-7-8-10-13-15-17-20-25-30-40-50v			
OR 25-0-25V OR 20-0-20V CAN BE OBTAINED FROM THE ABOVE RANGE				
11	12-15-20-25-30v	10	£11.91	£1.75
12	12-15-20-25-30v	5	£7.93	£1.25
13	12-15-20-25-30v	2	£4.79	£1.00
	3-4-5-6-8-9-10-12-15-18-20-24-30v			
OR 12-0-12V OR 15-0-15V CAN BE OBTAINED FROM THE ABOVE RANGE				
14	12-24v	12v 60A 24v 30A	£22.90	£3.00
15	12-24v	12v 30A 24v 15A	£18.33	£2.00
16	12-24v	12v 20A 24v 10A	£12.55	£2.00
17	12-24v	12v 10A 24v 5A	£6.80	£1.00
18	12-24v	12v 4A 24v 2A	£3.74	£1.00

FULLY SHROUDED TYPE TERMINAL CONNECTIONS

19	2E-32v	4	£7.50	£1.00
20	14-16v	2	£4.50	£1.00
21	12-20-24v	10	£12.50	£1.25
22	12-20-24v	5	£7.50	£1.25
23	24-30-36v	5	£12.00	£1.50
24	24-30-36v	5	£9.95	£1.50
25	6-12v	10	£7.20	£1.25
26	8-0v	2	£4.35	£1.00

CENTRE TAPPED TRANSFORMERS

Fully shrouded terminal block connections. Screen. Pr. 220-240v sec. tapped 36-25-0-25-36v 5A **£13.50**, pp £1 30-25-0-25-30v 2A **£6.75**, pp £1 18-0-18v 2A **£5.25**, pp £1 Open frame types Pr. 220-240v, sec. 50-0-50v 1A **£5.95**, pp 75p 50-0-50v 2A **£8.95**, pp £1

HEAVY DUTY TYPES

Pr. 230-240v, sec. 12v 30A twice will give 12v 60A or 24v 30A **£23.00**, carr £2 Sec. 6-12v 20A **£10.95**, carr £1 75 Sec. 20v, 20A **£12.00**, carr £1 75

AUTO TRANSFORMERS FOR AMERICAN EQUIPMENT

240/110v 80-300 Watts, fitted with 2-3 pin sockets and 3 core mains lead. Send s.a.e. for price list. We have England's largest selection of American electrical accessories, 2-3 pin plugs recessed and surface type, 2-3 sockets, multi-way adaptors, 2-3 pin grounding adaptors. Cable type sockets. Extension cords 240v. Edison screw type light bulbs. Industrial plugs and sockets. Let us know your requirements

GARDNERS ISOLATION TRANSFORMERS

New fraction of maker's price. Open type top connections. Pr. 220-240v Sec. 240v 6amps **£22.50**, carr. £3. Open type cable lead connections. Pr. 200-220-240v Sec. 240v 700 watts **£10**, carr. £2

PARMEKO

Ex. equipment in perfect condition. Metal shrouded open table top connections. Pr. 200-250v in 5v steps. Sec. 240v 10amps **£35**, carr. £4. Pr. 200-250v in 10v steps. Sec. tapped 90-100-110-120v 7.5amps **£19.50**, carr. £3. Pr. 200-250v in 5v steps. Sec. 115v 13.5A **£39.50**, carr. £4

HEAVY DUTY AUTO TRANSFORMERS

For mains boosting ex. equipment input 200-260v in 10v steps, output 240v 6kVA. Enclosed in metal case **£40**, carr. £5. One only.

3 PHASE ISOLATION TRANSFORMERS BY FAMOUS MAKER

Input tapped 380-400-415-430 volts RMS. NOM. Line to line 3 phase 4 wire 50Hz output 415 volts. NOM 3 phase 4 wire at 215kVA. Regulation 2% secondary fully screened open type construction. Terminal board connections, size 16/18x7/8/1/2ins. Weight 90lbs. Brand new. Fraction of maker's price. **£29.50**, carr. £4

WOODEN 3000 WATT AUTO TRANSFORMERS

Ex. equipment, perfect condition. Tapped 105-115-125-135-200-215-230-245-260v. Open type terminal block connections **£22.50**, carr. £2. Can be supplied in metal case with two American 2/3 pin flush mounting sockets, 3 core 240v mains lead. Carrying handle **£37.50**, carr. £3

GE C L T. TRANSFORMERS ALL PRIMARIES 220-240V

G.P.D. spec. Sec. tapped 59-61-63-65-67-69v 10A **£10**, carr. £2. Sec. tapped 58-63-69-74v 3A **£4.50**, pp 75p. Both types terminal block connections

REDCLIFFE 'C' CORE TRANSFORMERS

New and boxed Pr. 220-240v Sec. 29.5 875 mVA twice conservatively rated **£3.00** p.p. 75p Pr. 220-240v, sec. 50v 375 mVA 50v 125 mVA 6.3v 4.5A 6.3v 3A **£6.00**, carr. £1.50 Pr. 200-240v sec. 11v 6v 3.5A **£2.00**, pp. 75p

REDCLIFFE 'C' CORE CHOKES

20H 180 mVA **£3.50**, pp. £1 25 0.7H 250 mVA **£1**, p.p. 50p 50H 25 mVA **£1**, p.p. 50p 20H 75 mVA **£1.50**, p.p. 50p

L.T. TRANSFORMERS

By famous makers. Fraction of maker's price. All primaries 220-240v open type. No. 1 Sec. 26v 10A. Top panel connections **£5.75**, pp £1 No. 2 Sec. 43v 3A. Wire end connections **£3.75**, pp 75p. No. 3 33v 5A and 18v 18v 1A. Wire connections **£3.75**, pp 75p. No. 4 30v 5.5A and 12v 2.2A **£5.50**, pp £1 No. 5 Sec. 14v 5A, 14v 2.5A, 12v 10A, 8v 10A, 24v 750mVA, separate windings **£10**, carr. £2 No. 6 26v 5A, 16v 4A, 25v 2A, separate windings **£8.50**, pp £1 Potted types. No. 7 Sec. tapped 24-30-32v 2A **£3**, pp 75p. No. 8 Sec. 2.0-2v 24A, high voltage insulation **£5.50**, carr. £1 No. 9 Sec. 6.6v 6A, 6.6v 6A, 5v 6A, separate windings. The following outputs can be obtained. 6.6v 6A, 6v 6A, 5v 6A, 13v 6A and 5v 6A, 6.6v 12A, 6v 9A, 11.6v 6A and 6.6v 6A, 18.2v 6A **£5.95**, carr. £1 No. 10 24-0-24v 470mVA and 4.5 1A and 150v 15mVA, separate windings **£2.50**, pp 75p No. 11 Sec. 4.2v 1A **£1.25**, pp 50p. No. 12 Sec. 50v 1A and 140v 195mVA and 6.3v at 1.25A **£3.50**, pp £1 No. 13 Sec. 6v 1A twice **£2**, pp 50p No. 14 Sec. 24v 1A, 24v 750mVA **£3**, pp 50p No. 15 Sec. 9v 2A and 9v 1A, open type **£2.50**, pp 50p. No. 15 Sec. 35v 5A, 200v 100mVA, 30v 100mVA, separate windings **£7.50**, carr. £1 50

'C' CORE TYPES ALL PRIMARIES 220-240V

No. 1 Sec. 18.0-18v 21A **£10**, carr. £2 No. 2 Sec. tapped 22-25-28v 5A and 16v 1A twice, 10v 1A twice, 26v 2.5A, 23v 1A, 6.3v 2A 145-0-145v 200mVA, separate windings **£6**, carr. £1 No. 3 Tapped 29-31-32v 15A and 23-24-26v 5A and 14-15-17v 5A **£12**, carr. £2 No. 4 Sec. tapped 27-28-30 39v 10A **£12**, carr. £2 No. 5 Sec. tapped 10 21v 5A and 1-3v 5A, the following outputs can be obtained. 1-3 10-11-13-21-22-24v **£4**, carr. £1 No. 6 Sec. tapped 1-3v 1A and 10-30v 1A **£2.50**, pp 75p No. 7 Sec. tapped 20 22v 1.5A **£2**, pp 75p No. 8 Pr. 50v only, sec. 100v 2.5A twice **£8.50**, carr. £1 50

H.T. TRANSFORMERS BY FAMOUS MAKERS

Fraction of original prices ALL PRIMARIES 220-240V

Potted types. No. 1 408-200-0-200-408v, 408v taps 165mVA, 200v taps 500mVA, £5 50, carr. £1 50 No. 2 Sec. 300-0-300v 200mVA, 6.3v 6.6A, 5v 3A **£4.75**, carr. £1 25 No. 3 350-0-350v 200mVA, 6.3v 6.6A 5v 3A **£4.95**, carr. £1 25 No. 4 300v 3mVA 1A twice 4v 1A, 4v 0.3A, 4kv DC wkg. **£3**, pp 75p No. 4 Sec. 630-0-630v 105mVA, 5v 4A, 5v 2A **£4.95**, carr. £1 25 No. 6 Sec. 400-0-400v 170mVA, 6.3v 6A, 6.3v 1.6A, 5v 3A **£4.50**, carr. £1 No. 7, 400-200-0-230-400v 120mVA, 6.3v 4A, 6.3v 3A, 5v 3A **£4.50**, carr. £1 No. 8 Sec. tapped 700-760v 50mVA, 6.3v 1.5A **£3.50**, pp 75p No. 9 Pr. 115v only, sec. 530-0-530v 330mVA, 6.5v 6A **£7.50**, carr. £1 50 No. 10 Sec. 65v 1A and 18 24v 0.5A **£3.75**, pp £1 No. 11 250-0-250v 60mVA, 2.8-0-2.8v 2A, 24v 3A, 6.3v 3A 'C' core type **£5.50**, pp £1

RELAYS

Keyswitch, Open type KMK1 230v AC 1 CO 65p, KMK3 230v AC, 3CO 85p; KM1 12v DC 1 CO 75p. Omron open types MK, 2 12v DC 24v AC 2 CO 75p. Plug in type Mk. 2P 12v DC 2 CO 85p. Schrack plug in type 1 pin 24v OC 3CO 95p. Miniature types. Siemens or similar: 700Ω 4CO 85p; 700Ω 3CO 65p; 521 4 CO 85p. RAPA open type: base mounting 220-240v AC, 1 make **50p**. American Miniature open type, single hole fixing, 6v OC 1CO 50p, pp all types 10p

AC WKG BLOCK CAPACITORS BY FAMOUS MANUFACTURERS

MFD	Volts	Price
0.25	1500vAC	50p
0.75	440vAC	50p
1	470vAC	60p
1.25	360vAC	65p
2	400vAC	75p
2.4	360vAC	75p
2.5	360vAC	75p
2.7 + 0.1	700vAC	£1.25
3	440vAC	£1.00
3.5	250vAC	£1.00
4	250vAC	£1.00
5	360vAC	£1.25
5	440vAC	£1.50
7.2	440vAC	£1.50
8.4	250vAC	£1.00
15	250vAC	£1.75

PP up to 2.5MFD 25p, 2.7 to 15MFD 50p + 8% on total.

OIL FILLED BLOCK CAPACITORS

TCC: 8mfd 800v OC wkg. **£1**, pp 35p, 1mfd 2000v DC wkg. **75p**, pp 35p, 1 mfd 1500v DC wkg. **60p**, pp 25p, 1 mfd 1000v DC wkg. **55p**, pp 25p, 1 mfd 600v DC wkg. **30p**, pp 15p, 2 mfd 200v DC wkg. Three for **50p**, pp 35p. Dubilier: 8 mfd 350v DC wkg. **50p**, pp 35p, 4mfd 1250v DC wkg. **£1**, pp 35p, 2mfd 750v DC wkg. **25p**, pp 25p, 2mfd 600v DC wkg. **40p**, pp 25p, 0.1 mfd 10kv DC wkg. 3kv RMS **£2**, pp 75p, 0.1 mfd 3000v OC wkg. **75p**, pp 25p. Hunts: 1 mfd 350v DC wkg. 2 mfd 200v OC wkg. either type, three for **50p**, pp 25p. American types 4+4+4+2+1 mfd 600v DC wkg. **£3**, pp 75p, 8+8+4+2mfd 650v DC wkg. **£3**, pp 75p, 6+4+3mfd 400v DC wkg. **£2**, pp 75p, 7mfd 600v DC wkg. **75p**, pp 35p, 6mfd 600v DC wkg. **60p**, pp 25p, 4mfd 600v DC wkg. **50p**, pp 25p. TMC Special Offer: 2mfd 100v DC wkg. Cartons of 12 **£1**, pp 50p, 50mfd 150v DC wkg. **£1**, pp 25p. AC Wkg Types: 15mfd 330v AC **£1.50**, 6mfd 300v AC **75p**, 4mfd 400v AC **75p**, 4mfd tubular 250v AC **60p**.

CLARE MERCURY WETTED RELAYS

300Ω 2 CO contacts size 1 1/2x1 1/2ins **£1**, inc. postage. Reed relays 2000Ω 2 CO **50p**, 800Ω 2M 35p, 600Ω 2M 35p inc. postage. Siemens miniature relay 700Ω 2 CO contacts metal cover with base **85p** inc. postage. Delco horn relays 12v enclosed type single hole fixing **75p** inc. postage

ELECTRO-TECH COMPONENTS LTD

315, 317, 364 EDGWARE ROAD, LONDON W2

TEL: 01-723 5667 & 01-402 5580

Shops and mail order dept (mail to 364) open 9 to 6 Mon. to Sat. inc.

Prices include VAT. Carr. / p. & p. quoted U.K. only

ACCESS & BARCLAY accepted. Minimum order £5 otherwise C.W.O. For credit on approved accounts invoicing costs necessitate minimum order of £20

TTL BULK USERS

Please note we have purchased a distributor's entire stock and can offer the following items in substantial quantities at half current 1000 up prices:

7416N	7441AN	7470	7495J	74151N
7417N	7443J	7476N	7495N	74153N
7420N	7445N	7480N	7410N	74155N
7423N	7445J	7482N	74105N	74155J
7423J	7446AN	7483	74107J	74156N
7430J	7446N	7485N	74107N	74180N
7437J	7448N	7485J	74126J	74180J
7437N	7453N	7491AN	74145J	74181N
7440N	7454N	7494J	74150N	74182N
7441AJ	7460N	7494N	74151J	74182J
				9601N

PHONE FOR QUOTATION NIXIE TUBES

ITT. GN4. Red. Standard numerals 0-9. Complete with ceramic base for PCB mounting. 1.08" dia. x 1.38" high plus 1/2" base depth inc. pins. Operating voltage 170V. DC min. Complete data and connections supplied. Brand new. £1.80. p. & p. 20p. 10 off £1.00 each. 100 or more 85p each. p. & p. 40p any quantity.

ROTARY STUD SWITCH

PLESSEY. 30 way, 2 bank. Single pole. Contacts 1 amp, 240V. AC/DC. 0.05D res. Break before make. Stop infinitely adjustable allowing for any desired arc of travel. Ideal for instrument and model switching. Size 2 1/2" dia. overall x 2 1/2" deep plus 1 1/4" x 1/2" dia. spindle. £2.25. p&p 20p. 8 off £1.95 each. p&p 40p.



UNI-SELECTOR

240V. AC or DC operation. Split 30-way double bank contacts. Overall size approx. 2 3/4" dia. x 2 1/2" deep. Brand new. Bargain at £4.50. p&p 65p.



TRANSFORMERS

DAVENSET AUTO
2KVA continuously rated. Tapped for any voltage from 5-260V in steps of 5v. With an isolated winding of 0.5-10v at 8 1/2 amps this transformer is an extremely useful buy. Push-on connections. Size 8 1/4" x 5 1/4" x 6 1/2". A really robust job. Bargain at £23.80. Carr. £3.00. 750VA continuously rated. Tapped as above with 0.5-10V. isolated winding of 5 amps. Same connections. Size 4 1/2" x 3 1/4" x 4 3/4". Also bargain at £12.50. Carr. £2.00.

GRESHAM
Pri. 10-0-200-220-240v. Sec. tapped 0.3 1/2-7-11-32-33-34-35 at 10 amps to give 24 useful voltages. £6.00 carr. £1.00


TORRIDAL
Pri. 15-0-210-240v. Sec. 140v at 35 m/a. 31v at 500 m/a c.t. 10v at 1.9 amps. Sec. Size 3 1/2" dia. x 1 1/2". £3.95 p. & p. 30p

MINIATURE
Pri. 240V Sec. 6v at 1/2 amp. Size 1 1/4" x 1 1/4" x 1 1/4". Ideal as power supply base for models, radios, cassettes, etc. £1.50 ea. p. & p. 20p. 6 off £1.00 ea. o. & o. 45p

GOODYEAR
1KVA auto transformer. 0-110-115-120-200-220-240V. Fully shrouded. Terminal block connections. Size 5 1/4" x 4 1/4" x 5 1/2". Plus block. cannot be bettered at £13.95. p. & p. £1.50.

ARROW SWITCH

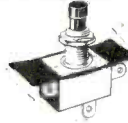Press-on switch. Single hole fixing. SP/ST. Size 1 1/4" x 1/4". Stud extends 1/2". Rated 1 amp at 240v. 2 1/2 amps at 125v. Price, for 5 (min. qty.) £1.78 p. & p. 30p. 10 or more 30p each p. & p. 40p.



REED SWITCHES

Glass encaps. N/O contacts. Glass length 1 1/4". dia. 1/4". Overall length 1 1/2". 10 off £1.00. p. & p. 25p. 100 off £8.00. p. & p. free. 1000 off £88.00. p. & p. free.

SYLVANIA SWITCH

Complete with magnet. Contacts N.C. 3amp. Vacuum sealed. 1 1/2" x 1/4" dia.



10 for £2.50
50 for £11.00
100 for £18.00
Plus 50p p. & p.
any quantity

MOTORS

RANCO 1/6 H.P. 1425 rpm, 240v, 50Hz. Split phase. 1/2" x 3" long shaft. Unused. Normally cradle mounted but offered without cradle, hence low price of £7.50 plus £1.50 carriage.



CITENCO F.H.P. reversible geared motor. 220/240v, 50 Hz. 1 Ph. cap start. cont. rating. 0.2 amps. Gearing 1/4:1. Final drive. 19 rpm torque. 14.5 Kg/cm. 5/16" dia. shaft. Size 6" x 3 1/2". dia. plus base. Brand new. Limited quantity. £14.50 p&p + 1.50




1/8 H.P. reversible geared motor. 220/240v, 50 Hz. 1 Ph. cap start. cont. rating. 0.2 amps. Gearing 1/4:1. Final drive. 19 rpm torque. 14.5 Kg/cm. 5/16" dia. shaft. Size 6" x 3 1/2". dia. plus cap and base. New. Robust. £23.95. carr. £3.00

ACADEX shaded pole motor. Open frame 230v, 50 Hz. Double ended 5/32" dia. spindle, each 1 1/4" long. Ideal for fans, motors, etc. Size 1 1/4" x 2 3/4" x 1 1/2" deep plus spindles. £1.80 p&p 45p.

CROUZET shaded pole motor. Open frame 115/230v, 50 Hz. 1425 rpm. Size 2 1/4" x 2 3/4" x 1 3/4" deep plus 3/4" long x 5/32" dia. spindle. £3.60 p&p 62p.

PAPT motors. Noted for advanced design and superb construction. Rotating decast outer body acts as flyweight and eliminates wobble and flutter. 50 Hz. capacitor start. MODEL HSZ 32 80/6/12. 220v. Dual speed tape deck motor. 500/1000 rpm. 12 mm. drive shaft. gives tape speeds of 9.53/19.05 cm/sec. (3 3/4/7 1/2 ins/sec) respectively. Size approx. 5 1/2" dia. x 3 1/2" plus 1 1/4" spindle. £18.50. p&p £1.10

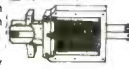SOLENOIDS 240V A.C.
MAGNETIC DEVICES LTD. No. 1) has 20lb pull for 50% duty. 1 1/2" travel, push or pull. Shackles both ends. Size 1 1/2" wide x 3 1/4" high x 4" long plus 3" arm travel. £6.78 plus p. & p. £1.00
(No. 2) has 2lb pull continuously rated 1/2" travel. Size 1 1/2" x 1 1/2" x 2 1/4" plus travel. £1.80. 30p p. & p.



PYE ETHER LTD. Thrust operated through spring loaded hinged lever giving a 1lb pull or push. Complete with mounting bracket and push-on connections. Size overall inc bracket 2 1/2" x 3 1/4" x 3 1/2" long. £2.25 P&P 45p

RELAYS

Octal base 2 C/O 6 amp contacts. Following ratings: 12V a.c. 48V d.c. 110 d.c. 230 a.c. all £1.25 each plus base 15p postage and packing 15p. 11-pin 3 C/O 6 amp contacts. following voltages 115 a.c. 48 d.c. 24 d.c. all at £1.50 each. base 15p plus 15p p. & p.



FANS

DUAL EXTRACTOR FAN. 240v, 50 Hz. Two thick stack shaded pole motors make this a highly efficient unit producing a powerful airflow. Mounted in heavy steel frame each has five element 6 1/2" blades. Size 22 1/2" x 14" x 5 1/2" deep. £8.85 carr. £2.75.



SINGLE FAN with motor similar to above. Very useful in home and workshop. Remember last summer. Keep cool this year. Only £3.95. p&p 65p.


MINIATURE LAMPS

Type	Size (Dia.)	Volt/Curr.	Type	Size (Dia.)	Volt/Curr.
A	3MM	5-6V 60 MA	D	3MM	2-5V 360 MA
B	4MM	4V 250 MA	E	4MM	5-6 60 MA
		5V 60 MA			6 3 200 MA
		12V 40 MA			14V 40 MA
		12V 100 MA			14V 75 MA
		28V 40 MA			28V 40 MA
		28V 40 MA			12V 160 MA
					14V 80 MA

Small telephone jack type 6 or 24V
Price Types A-F £4.00 for 25, 50 and upwards 13p each. Type G 45p each. p. & p. 20p per order.

SUPERBEND MAGNETIC CLUTCH

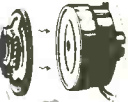Superb example of electro-mechanics. Main body in two sections, coil section fixed with main sleeve. Drive section rotating on outer perimeter. Uniting plate has 1/4" ID bearing concentric with main section and 1/8" tooth cog wheel. Extremely powerful transmission. 24V D/C. 240 m/a. £3.78 plus p. & p. 40p.



PCB EDGE CONNECTOR

CINCH. .15" pitch. 27 way but designed with adjustable fixing endplates enabling connector to be cut and used in any length desired. 50p p. & p. 15p. 10 off £4.00 p. & p. 30p.

MEM LIMIT SWITCH

Snap action 5 amps at 240/410 A.C. size base. 3 1/2" x 1 3/4" x 1 1/4" plus heavy duty roller plunger 1 1/2" ext. or 1" when compressed. Very robust for tireless operation. weather proof. Price £2.20 plus p. & p. 40p.

JABSCO (ITT) ROTARY PUMP

Self-priming. Works from electric drill or suitably powered motor for 3/4" drive shaft. 1/2" hose connections. Throughput 2/3 galls per min at 2400 rpm. Dozens of uses in home and workshop. Giveaway at £2.75 p&p 20p.



WW — 086 FOR FURTHER DETAILS

The SECOND-USER Computer Specialists

Mini-Computer Exchange

JUST ON THE MARKET—
SUPERB CRT/DA SYSTEM:
1774 32K Processor, 2 x 854 3meg Disk Drives, 2 x 608 7-track Magnetic Tape Units (NR2), 430 Card Read Punch (500/1000 cpm), 1742 Line Printer (300 lpm), 1713 ASR Teletype (10 cps), 5 x 211-2 CRT Displays, 1750 A/D Interface.
DEC PDP8M-ML 8K Processor — BRAND NEW
DEC PDP8I 8K Processor
Olivetti KC 7000
Philips Data 4000

PERIPHERALS

- DEC AF01 A/D Converter
- DEC DF32 Disk Drive & Control
- DEC DS32 Disk Expander Drive
- DEC RT02-B Alphanumeric Data Entry Terminal
- DEC TU55 DEC Tape Drive
- Computer Automation Dual Cassette Drive
- Cipher X-100 9-track 800 bpi tape deck
- Peripheral Equipment Corp. 7520 7-track deck
- Kennedy 7-track Incremental Tape Transport
- RDL 10000-series Incremental Tape Transport
- TALLY 425 60cps Panel-mounted P/T Reader
- ELLIOTT table-mounted photo-electric readers
- FACIT 4060 Heavy-duty rack-mounting P/T Punch
- FACIT 4001 High speed readers, table or rack-mounted

DEC MODULES

- BM792 Bootstrap Loader
- DC11AC/DC11DA Asynchronous I/F
- DK8EA Real Time Clock
- DR8EA Parallel Interface
- DR11B Direct Memory Access
- KDBE Data Break
- KE11A Extended Arithmetic
- KB8E PDP8E Processor Module Set
- KB8E Serial Interface
- KMBE Memory Extension Module
- KPBE Power Fail/Auto Restart

Many other modules in stock or on early call-off

OUR STOCKS ARE CONSTANTLY CHANGING — please phone for latest availabilities.

Add 8% VAT to all prices shown. Carriage extra details on request.

ELECTRONIC BROKERS

Printers and Terminals

Diablo Hi-Type 1 30cps Daisy-wheel Printer, complete with interface module for Nova processor — BRAND NEW!
CENTRONICS 102A Twin-head Printer
KSR33 and DD390-KSR Teletype Terminals
ASR33 and DD390-ASR Teletype Terminals
ASR35 Heavy-duty Teletype Terminals
IBM 735 Input/Output Writers
TEKTRONIX 611 Storage Display Unit
COSSOR DIDS 401-2A and 402-2A Visual Display Units
BALL Miralot TV Monitors, 9" tube, 12MHz bandwidth

Systems, Peripheral Equipment & Components for Data Processing Keyboards

LARGE STOCKS OF A WIDE RANGE OF KEYBOARDS ALWAYS AVAILABLE

KB6: 56-station ASCII-coded TTL-compatible 4-bank alphanumeric keyboard standard Teletype layout. 7-bit ASCII code (no parity) with ROM encoder chip. Two-key rollover and debounce supplied complete with circuit diagrams, pin connections and code chart.
Power Supply +5VDC +/-5% 150mA. -12VDC +/-10% 10mA. Output Logic Levels Data Bits 1 through 7.0V '0' 45V, 2.6V '1' 5.25V. Fan Out: One standard TTL load. Strobe: 2.6V '1' 5.25V. Fan Out: 10 standard TTL loads. Strobe signal delay 10 milliseconds nominal to allow data to stabilise.
Price £39.50 + £1 P&P + 8% VAT. Send £43.74.
DXS-CRT 96-station ASCII-coded TTL-compatible 4-bank alphanumeric keyboard. 8-bit code upper and lower case alpha output plus separate numeric pad. Delayed strobe and 2-key rollover. Mounted in attractive box overall dimensions 20 1/2" x 7 1/4" x 3 1/4". Price £65.00 + £3 carriage + 8% VAT. Send £73.44.

55SW-31 54-station BCD coded 4-bank alphanumeric keyboard. Hall-effect switches. Input +5VDC. negative logic and strobed output. two-key rollover. Set in attractive panel incorporating 5 indicator lamps and on/off switch. Dimensions 15 1/2" x 5 1/2" x 2 1/2". Price £39.50 + £2 P&P + 8% VAT. Send £44.82.

18-Key push-button calculator keyboard. Numerals 0-9, decimal point C, K, +, -, x, =. Mounted on PCB overall dimensions 5 x 4 1/4" x 1 1/2". Price £4.00 + 50p P&P + 8% VAT. Send £4.86.

MINIATURE MATRIX PROGRAMME BOARDS: Brand new X-Y Matrix boards, with 3mm grating. 3x10 positions (1 1/4" x 1"). £4.00 P&P 40p.

Callers welcome Monday to Friday 9 a.m. to 5 p.m.

WW — 100 FOR FURTHER DETAILS

ELECTRONIC BROKERS LIMITED (Computer Sales & Services Division)

49-53 Pancras Road, London NW1 2QB. Tel: 01-837 7781

SIGNAL SOURCES

ADVANCE
V H F Square wave Generator SG21 10 KHz-100MHz Max o/p 2V **£35**
H1 Audio Signal Generator. 15Hz-50KHz Sine and Square **£35.00**
E2 R.F. Signal Generator 10KHz-100MHz **£78.00**

H1E Audio Signal Generator. Sine & Square Wave 15Hz-50KHz. 200 V to 20V (Sine) Distortion 1% 1.4mV to 140V (Square). Brand new condition **£70.00**

GENERAL RADIO

Unit Oscillator 1209C. Freq. 250-920MHz Accuracy 1% Drift 0.2%. O/p in to 50ohms = 150mW supplied with Power Supply Type 1201-CQ **£145**

HEWLETT PACKARD

10515A Frequency Doubler Extends the useable frequency range of signal generators. Operating on input frequencies 0.5MHz to 500MHz it provides a doubled output in the range of 1MHz to 1GHz. The frequency response of this 50 ohm device is very flat ($\pm 2dB$ typically) over the entire frequency range and undesired harmonics are well suppressed. Brand 211A Square Wave Generator 1Hz-1MHz **£75.00**
F M / A M Signal Generator 202H F M A M C W & pulse coverage 54 to 216 MHz R F o/p 0.1 u V-0.2V 50ohms Impedance **£450**
Audio Signal Generator 206A 20Hz-20KHz $\pm 2\%$ accuracy Distortion $\pm 1\%$ **£90**
612A-U.H.F. Signal Generator 450-1230MHz 0.1uV-0.5V (50 ohms) A M internal & external. Pulse mod facilities SUPERB CONDITION **£1250.00**

MARCONI INSTRUMENTS

TF1060 U.H.F. Signal Generator 450-1250MHz. Sine wave and pulse a.m. **£350.00**
TF887 Signal Generator 15KHz-30MHz. O/p volts 0.4uV-4V **£185.00**



Signal Generator **TF887**. 15KHz-30MHz o/p 0.4uV-4V Int. & Ext. mod. Supplied with Terminating unit **£185**

TF2005R Two Tone Source. The instrument comprises two identical low-distortion a1 oscillators and a monitored attenuator unit, to form a compact test set for the measurement of inter-modulation distortion using the methods recommended by S.M.P.T.E. and C.T.F. Frequency range 20Hz to 20KHz in six bands (each oscillator can be adjusted and used independently). Harmonic distortion, less than 0.05% between 63Hz and 6KHz when using unbalanced output. Generally less than 0.1% under other conditions. Intermodulation Below -80dB with respect to the wanted signal. Amplitude Reference Level Up to +10dBm from each oscillator. Output attenuator 11dB in 0.1dB steps. Output impedance 600 Ω (unbalanced, or 600 Ω 150 Ω or 75 Ω balanced and centre-tapped) **£485.00**
S.H.F. Signal Generator 618C 2.8-7.6GHz $\pm 1\%$ 500 ohms **£500**
F.M./A.M. Signal Generator TF 995A/3S. Ministry type No. CT402 1.5MHz-220MHz R.F. o/p 2uV-200mV Internal & External Mod. Facilities. V good condition **£385**
F.M./A.M. Signal Generator TF995A/5 1.5-220MHz in 5 bands 0.1uV-200mV F.M. up to $\pm 120KHz$ from 50Hz-15KHz. A.M. up to 50% from 100Hz-10KHz o/p (1) 2uV-200mV (2) with terminating unit 1uV-100mV Int. mod. freqs 400Hz 1KHz & 1.5KHz. Distortion (1) on internal F.M. $\pm 25Hz$. (2) on internal A.M. 6% at 30% mod **£300 to £450**
A.M. Signal Generator TF801D/1 Freq range 10-470MHz R.F. output 0.1uV-1V Piston attenuator. 50ohms Impedance. Modulation Int. A.M. & d.f.H. A.M. 30Hz-20KHz Low spurious F.M. & d.f.H. V.S.W.R. 1.2 or less **£400-£800**
A.M. Signal Generator TF801D/1S Military version, 10-485MHz **£450-£800**
R.C. Oscillator TF1370A 10Hz-10MHz Square Wave up to 100KHz High Outputs up to 31.6V **£285**
Phase/A.M. Signal Generator TF 2003 0.4-12MHz **£150**
A.M. Signal Generator TF 801B/3S 12-485MHz 0.1uV-1V **£195**
R.C. Oscillator TF1101 Frequency range 20Hz-200KHz. Output Direct into 600 Ω 20V variable Attenuator 0.6dB in 10dB steps. Impedance 600 Ω Distortion Via 1KHz Filter less than 0.1%. Direct or via Attenuator. Less than 0.5% 50Hz-20KHz. Less than 1% 20Hz-200KHz **£120-£150**

Signal Generator TF144H/4 Late models in super condition **£500 to £650**
TF995B S AM/FM Signal Generator 200KHz-220MHz Narrow deviation model for mobile radio testing 3 mod. freqs. **£675.00**

MARCONI-SANDERS
Microwave Sweep Generator type 6600A c/w 6619 plug-in 1.7GHz-4.2GHz **£2900.00**

MUIRHEAD L.F. Decade Oscillator D880A 2-phase 0.01Hz-11.2KHz **£295**
Decade Oscillator D890D 1Hz-11.2KHz **£260**

Electronic Brokers Ltd. are one of the leading electronic instrumentation companies in the UK, providing a full range of services to Universities, Industry, Colleges and Governments both at home and overseas.

We have the largest stocks of secondhand test equipment in Europe as well as a selected range of new products. These are on display at our London showrooms where customers can examine the equipment of their choice and see it working.

Electronic Brokers Ltd. have fully equipped workshops on the premises to test and report on the majority of equipment we sell.

PHILIPS

PM 5167 Function Generator Sine, triangle, square positive pulse, negative pulse and ramp 9.1 and 1.9 0.001 Hz to 10MHz (sawtooth and pulse up to max 1MHz) Output 40V(P-P) Impedance 50 ohms Variable DC Offset External sweep Single shot set phase Hold function Overrange warning light Superb condition **£15.00**

PM5501 Colour bar generator. Extremely light and compact instrument for mobile maintenance. 5 different test patterns for colour and black/white TV installation and service. R.F. output signal switchable V.H.F. Band III and U.H.F. Band IV 1KHz tone for sound performance checks (same wave) **£135.00**
50MHz Pulse Generator PM5712 **£435.00**
Pulse Generator PM5775 **£800.00**
Pulse Generator PM5776 **£900.00**

SANDERS

CT478 Microwave Signal Generator 1.5GHz-4.5GHz **£285.00**

RHODE & SCHWARTZ

S.H.F. generator SMCB-BN 41042 1700-5000MHz **P.O.A.**

WANDEL & GOLTERMAN

U.H.F. Power Oscillator LMS-68 c/w plug in Oscillators
Type LO-4 4.41MHz
Type LO-40 40.108MHz
Type LO-170 170.330MHz
Type LO-610 610.960MHz

MULTIMETERS

AVO
Test Leads **£4.00**
Multimitor Mk 4 c/w carrying case & leads **£13.50**



Type 175A 50MHz. Bright, sharp trace, 6 x 10cm display. Plug-ins provide bandwidths to 50MHz. Vertical and time axis plug-ins for specific applications. Eight plug-ins provide maximum versatility. Easy to calibrate and maintain. Few adjustments, no distributed amplifiers or delay line adjustments. Positive syncing over entire bandwidth. Plug-in Units 1750A Dual Trace Vertical Amplifier 40MHz, 50 mV/cm. 1781B Sweep Delay Generator Sweep Selector provides (a) Main Sweep (b) Delaying Sweep, brightened segment of trace indicates time relationship between delaying sweep display and main sweep display. (c) Main Delayed Sweep (d) Mixed Sweep (e) Single Sweep of main sweep **£295**

POLAND

'Meratester' Multimeter 1.5 mv to 1.5kV full scale AC & DC 0.15uA to 1.5a full scale AC & DC Accuracy $\pm 1.5\%$ over wide range. Resistance & decibel measurement. Battery or AC supply operation. Input impedance 100Mohms (DC) 10 Mohms 60pF. 5 to 150mV ranges (AC) 100Mohms 20pF 500mV to 1.5kV (AC) NEW **£85**

BRIDGES

MARCONI INST.
TF936 Impedance Bridge **£125.00**
Universal Bridge TF1313A **£325**
L.C.R. Bridge TF 868B **£115.00**
TF1245 CCT Magn. Meter c/w Oscillator TF1246 **£685.00**


WAYNE KERR

Radio Freq. Bridge B601 **£95**
R.F. Admittance Bridge B701 **£85**
COMPONENT BRIDGE BS21 (CT 375) **£95**

Self-contained portable mains operated equipment designed to provide accurate measurements over an extremely wide range of resistance, capacitance, inductance and impedance values. Resistance 10 ranges from 1m ohm to 1000 M ohm. Capacitance 10 ranges from 50uF to 500pF. Inductance 10 ranges from 1uF to 500 KH. Capable of measuring components in situ **£105.00**

OSCILLOSCOPE

COSSOR

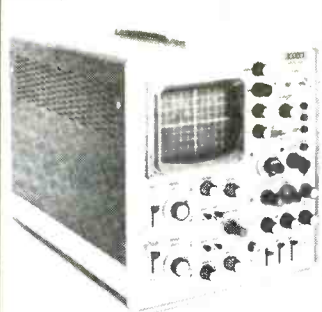

Dual Trace Scope 4000 50MHz 7nsec Rise Time 5mV/cm sensitivity. Calibrated sweep delay. Gated trigger. X-Y display 8 x 10cm display **£485**

DYNAMAC

Type 7200 15MHz Dual Channel Portable c/w Plug Ins 7201 & 7212. Solid State. 10mV/div to 5V/div. X10 on channel 1 permits 1mV/div to 12.5V/div. Calibrated Sweep Delay c/w batt pack **£310.00**

DC-30MHz Portable Oscilloscope 7100 c/w Plug-in Units 1X2 & 1Y2. Solid State. Dual Channel, Delayed Sweep. 10mV/div. sensitivity with X10 1mV/div. (10Hz-5MHz) **£315**

GREENPAR

Probe Kits GEB1600/1 - New **£25.00**
HEWLETT PACKARD 185B 1000 MHz Oscilloscope Sampling c/w Plug-in 188A or Plug-in 187C **£395.00**

PHILIPS

10MHz Dual Beam Oscilloscope PM3233 2mV sensitivity. True dual beam 8 x 10cm screen. Signal delay in both vertical channels. Triggering Auto. AC DC & TV **£520**
Transistor Curve Tracer PM 6507 **£525**

SOLARTRON

Portable Scope DC-6MHz Double Beam CT436 **£105**
Portable Scope CD 1400c-15MHz Plug ins available CX1441 1443 1448 1571 **£180**

TEKTRONIX

DC-15MHz Portable Oscilloscope 422 Dual Trace. Small size and lightweight 10mV/div to 20V/div. **£595**
DC-30MHz Oscilloscope 545A c/w CA & L Plug-ins **£445**

Sampling Scope 661 c/w plug ins **£450**
Scope Camera C-12 Superb cond. & complete **£190.00**
50MHz Model 546 c/w 1A1 plug-in **£635.00**

TV Waveform Monitor 525 Freq response Flat - within 1% between 60Hz & 5MHz. Low Pass - Passes star steps, eliminates H.F. High Pass - Passes H.F. eliminates star steps. IRE - meets IRE standards for level measurements. Sensitivity - Deflection factor of the vertical amplifier is 0.015V/cm. Vert. Atten - 1x, 2x, 5x. Keyed Clamp-type DC Restorer. Gain stability within 1% **£125**

Differential Unit 10A1 Used on 647 Series **£300**
585 c/w Type B2 Plug-in Dual Trace 80MHz. B-width Sweep Delay **£750**. Other plug-ins available 80 and B8


Transistor Curve Tracer 575 Displays curves of NPN & PNP transistors and dynamic characteristics of a wide range of semiconductor devices **P.O.A.**
Dual Beam Scope 551 2 vertical deflection systems. Accepts Amp Spect analyser. Sampling and special purpose Plug-ins DC-27MHz. Price dependent on plug-ins required **P.O.A.**

531A DC 15MHz Oscilloscope c/w K Plug-in. Single Trace 50mV/cm **£195.00**
531A 15MHz Oscilloscope c/w CA Plug-in. Dual Trace 50mV/cm **£210.00**
544 DC-50MHz Oscilloscope c/w CA Plug-in. Dual Trace 24MHz 50mV/cm **£375.00**
549 Storage Oscilloscope (Mainframe) **£610.00**

TELEQUIPMENT
D33R Oscilloscope min sensitivity 10mV/div DC-6MHz **£115.00**

WANDEL & GOLTERMANN
BLS 218 Storage Oscilloscope c/w Power Supply **£325.00**

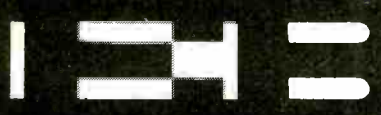PROBES (New)
X1 Part No 90 **£6.50**
X10 Part No 91 **£8.50**
X1 & X10 (switchable) Part No 95 **£10.50**



ELECTRONIC

49-53 Pancras Road
London NW1 2QB
Tel: 01-837 7781

ADD 8% VAT TO ALL PRICES

BROKERS LTD
equipment people

On these pages you will find just the briefest selection from the vast range which we hold in stock at any one time.

If you are seeking a specific item and it is not listed, it will pay you to ring us first — we believe we offer the best prices and the best service.

WORLD WIDE EXPORT

Enquiries and tenders welcome from any part of the world.
HOW TO REACH US

We are easy to reach, no matter where you live. Minutes away from Kings Cross or St. Pancras main-line stations, and a bus ride from Euston; only just over half an hour from Heathrow Airport.

49-53
 Pancras Rd
 London
 NW1 2QB
 Telephone:
 01-837 7781



Vacuum Tube Voltmeter 400H Freq Range 10Hz-4MHz Volts 10mV-300V FS (12 ranges) Accuracy $\pm 1\%$ (50Hz-500KHz) **£155 P.O.A.**

AC Voltmeter 400F & 400E **£155 P.O.A.**

Broad Band Sampling Voltmeter 3405A **£495.00 P.O.A.**

MARCONI
 Sensitive Valve Voltmeter TF 1100 100- μ V-300V AC Freq coverage 10Hz-10MHz Meter has dB scale facility **£85**

Valve Voltmeter TF 1041B General Spec 0-300V AC 0-1KV DC Resistance up to 500Mohms **£60/£85**

Electronic Voltmeter TF2604 **£225.00 P.O.A.**

Voltmeter No 3 CT 208 TF 95B AC 100mV-150V multiplier extends AC range to 1.5KV DC 50mV-100V Freq Range 20Hz-100MHz **£55**

Valve Voltmeter TF2600 **£175 P.O.A.**

PHILIPS
 H.F. Millivoltmeter GM 6014 Measuring Ranges 1mV-300mV in 6 ranges Accuracy at 30KHz at 3% of FSD = Amplitude Char 1KHz-30KHz flat within $\pm 5\%$ **£55**

DC Microvoltmeter GM6020 10- μ V-1KV current 10pA-10 μ A Accuracy 5% (FSD) 0-100- μ V 3% (FSD) AU other ranges Recorder o/p facility **£65**

TRANSMISSION TEST EQUIPMENT

AIRMEC/RACAL
 Wave Analyser 248A 5-300MHz **£250 to £300**

Wave Analyser 248 Freq range 5MHz-300MHz **£145.00 P.O.A.**

Modulation Meter 409 **£60/£85 P.O.A.**

Type 210 Modulation Meter (earlier version of 210A) **£85-£100 P.O.A.**

Type 210A Modulation Meter 2.5-300 MHz A.M. Range 0-100% F.M. Range 0 to = 100 KHz in 4 ranges **£185-£245 P.O.A.**

HEWLETT PACKARD
 Sweeping Local Oscillator 3595A Plug-in for use with 3590A Wave Analyser Freq range 20Hz to 620KHz **£650.00 P.O.A.**

MARCONI INSTRS.
 Distortion Factor Meter TF 142F Fundamental Freq Range 100Hz-8KHz Dist measuring ranges 0.5%-0.50% Measures all spurious components up to 30KHz **£60.00-£80.00 P.O.A.**

A.F. TRANSMISSION MEASURING SET Model TF2332 Frequency Range 20Hz to 20KHz Accuracy $\pm 0.2\%$ **£375.00 P.O.A.**

RADIOMETER
 Wave Analyser FRA 2 T3 Special version of FRA 2 with facilities for intermodulation measurements and selective measurements of frequency responses Freq range 30Hz to 16KHz Incremental freq 0Hz to 60Hz Selectivity 3 curves with following 1dB points $\pm 1.25\%$ - 12.5Hz - 63Hz and 80dB points - 40Hz - 130 Hz - 350 Hz - 150 Hz - 450 Hz

Voltage range 10V to 1KV Auxiliary Oscillator Range 0Hz to 1.6 KHz and 1.5 to 1.6KHz o/p - 10V (EMF) continuously variable Impedance 1 Kohms 16, F **£375.00 P.O.A.**

WANDEL & GOLTMERAN
 Level Transmitter TFPS 42 10 KHz-14MHz Generator 0 level 0.8mV -2.5V FSD Lowest adjustable 50 μ V Synchronous tuning of generator and level meter possible Output impedance 150 75 70 60 50 and ohms - 25KHz Fine Tuning range **£250.00 P.O.A.**

Level Meter TFM - 43 10KHz - 14MHz 3dB Bandwidth (800Hz and 4KHz) Selective measuring range 8V to 40 μ V (lowest readable 2 μ V) Switchable bandwidth -15KHz fine tuning High sensitivity Full specification for the above on request **£250.00 P.O.A.**

HEWLETT PACKARD
 Digital Recorder 560A **£110**

Digital Recorder 561B **£140**

Directional detector 7870 1 9-4 1Ghz **£90**

Directional detector 788C 3 7-8 3Ghz **£95**

UHF Attenuator 355C **£90**

HOUSTON
 XY Omnigraphic Recorder type 6520 **P.O.A.**

XY & XYY Omnigraphic Recorder type 6452 **P.O.A.**

MARCONI INSTRS.
 Attenuator TF 1073A-2S **£85**

Quantization Distortion Tester TF2343 **P.O.A.**

Probe Kit TM8120 1x1 for use with valve voltmeter TF2600 Brand new **£20**

A F Power Meter TFB93A 20 Hz-20KHz 1mW to 10 Watts FS Z = 2.5 ohms to 20Kohms in 48 Steps **£150.00 P.O.A.**

Out of Limits Indicator TF 2404 2M1 Checks readings from electronic counters and other digital instrs. Local and remote visual and electrical indicators suitable for use by unskilled personnel and with A.T.E. **P.O.A.**

Blank & Sync. Mixer TF 2908 **£90 P.O.A.**

RHODE & SCHWARTZ
 Polyscop Swob II **£1400**

Selektomat USWV **£835.00 P.O.A.**

Frequency Indicator FKN-BN 47051 **£475 P.O.A.**

TEKTRONIX
 Programmer 262 **P.O.A.**

Sweep Generator 3m2000 c/w plug-ins B-3M and S-6 and S4MM **P.O.A.**

WAYNE KERR
 Current Ratio Transformer T102C **P.O.A.**

VOLTMETERS

ADVANCE
 VM 77D AC Millivoltmeter **£50.00 P.O.A.**

GENERAL RADIO
 Electronic Voltmeter 1806A -AC DC & OHMS -2X Accuracy Wide freq. Range up to 1500 MHz **£200.00 P.O.A.**

HEWLETT PACKARD
 DC Vacuum Tube Voltmeter 412A 1mV-1000V 1% Accuracy Can also be used as Ohmmeter and Ammeter **£75 P.O.A.**

VTM 400D 1mV to 300V FSD 12 ranges 10Hz to 1MHz 2% accuracy Input Impedance 10Mohms **£85 P.O.A.**

VTM 400L Logarithmic vers on of 400D Reads RMS value of sine wave Log voltage scale 0.3 to 1 & 0 & 3 Linear dB scale Input Impedance 10Mohms **£90 P.O.A.**

MISCELLANEOUS

ADVANCE
 Frequency Counter TC16 **£110.00**

Recorder Calibrator HC20 **£15**

X-Y Plotter LR100 — Further details on request

Digital Panel Meter DPM302 (new) **£25.00**

Digital Panel Meter DPM301 (new) **£45.00**

AIRMEC
 Time Interval Meter 369 Mains operated transistorised unit Time Intervals 100ns to 30mscs \pm 0.5% up to 30mscs **£95.00 P.O.A.**

BECKMAN
 Transfer Oscillator 7580H DC-15GHz with counter 7.5MHz-15GHz without counter Sensitivity 100mV (R.M.S.) **SPECIAL OFFER £250 P.O.A.**

B & K
 Deviation Bridge 1504 **P.O.A.**

BIRD
 Coaxial Resistor 8053 10W RF coaxial load resistor **£20.00**

Wattmeter Terminate 6835 3 ranges 0.120/0.600/0.1200W 30-500MHz **£25.00**

Wattmeter Terminate 67 3 ranges 0.25 0-100 0-500W 30-500MHz **£25.00**

B.P.L.
 Component Comparator CZ457 5 **P.O.A.**

BRUEL & KJAER
 Automatic Vibration Exciter Control 1018 **£95.00**

FLUKE
 Industrial Counter Totaliser 1941A Freq Measurement 5Hz-40MHz 40mV sensitivity Totalise measurements to 999999 units Presettable display RPM measurement **£50.00**

Distortion Meter VZM 83 52/304/556 kHz This unit comprises a generator and receive portion and operates according to the intermodulation method. This distortion measuring set is mainly used to measure transmission distortions occurring on FM radio link systems **£190.00**

VZM2 Distortion measuring set for phase and amplitude mod. For Multichannel FM Radio Systems up to 12MHz base bands **£350**

TELEPHONE TEST EQUIPMENT

SIEMENS
 Level Meter 3D 332 0.3-1200KHz **£250**

Level Meter 3D 335 10KHz-17MHz **£300**

Level Oscillator 3W29 0.3-1200KHz **£250**

Level Oscillator 3W518 **£300**

OSCILLOSCOPES TEST EQUIPMENT

TEKTRONIX
 Time Mark Generator 184 **£250.00**

5msc Pulse Generator Model 2101 c/w loads & connections **P.O.A.**

Time Mark Generator 2901 **P.O.A.**

Pulse Generator Model 110 **£95**

DIGITAL VOLTMETERS AND MULTIMETERS

DYNAMCO
 D.V.M. DM 2022S 10- μ V-2KV Max reading 39999 Accuracy 0.02% Resolution 1 in 40 000 Input impedance 25KMohms **£265.00 P.O.A.**

Digital Voltmeter DM 2023 C/w DC Ranging unit 0.1 Scale 99999 0.001% FSD DC Accuracy 10- μ V-1KV DC **£450.00 P.O.A.**

D.V.M. DM 2004 **P.O.A.**

HEWLETT PACKARD
 OVM type 3430A 3 digit, 5 ranges 100mV to 100V FS Input resistance 10Mohms Overload protection **£145.00**

Digital Multimeter 34702A with Display 34740A. 4 digit display, 4 ranges both AC & DC plus 6 ranges of ohms AC function covers 45Hz to 100KHz. Ohms ranges are 100ohms to 10Mohms F.S. LED display, New condition. A much sought after device still in current production... **£400**

PHILIPS
 D.M.M. TYPE PM2423 3 1/2 digit, DC Volts 2V-1KV AC VOLTS 2V-350V R=200 ohms - 200 M ohms Accuracy 0.1% of reading. Automatic range switching for all functions. Automatic polarity indicator **£140.00**

D.M.M. TYPE PM2522 3 1/2 digit, DC Volts 0.2-1KV. AC Volts 0.2-600V AC/DC Current 0.2mA-2A R = 200 ohms - 20 M ohms Accuracy 0.1% - 0.1% of range DC Volts. Full circuit protection. LED display **£150.00 P.O.A.**

SIGN/ROGERS
 A.F. Voltmeter AM324 **£50.00**

SOLARTRON
 AC Converter LM1219 30mV-300V mean reading Freq range 10Hz-10KHz **P.O.A.**

D.C. Digital Voltmeter LM1420 2. 2.5-5V -1KV in 6 ranges 0.05% DC accuracy **£235.00 P.O.A.**

D.V.M. Type LM1420 2Ba DC true R.M.S. and mean AC sensing Accurate measurement irrespective of harmonic distortion accuracy $\pm 0.25\%$ Freq. 0.1Hz-20KHz **£325 P.O.A.**

D.V.M. Type LM 1440 2 10- μ V-2KV DC in 5 ranges Oven controlled zero-drift Accuracy -0.033% FSD -0.005% reading **P.O.A.**

D.V.M. LM 1480 3 Autoranging version of LM 1440 3 Max reading 39999 5- μ V-2KV DC Full spec on request **P.O.A.**

D.V.M. LM 1604 DC only 1- μ V sensitivity accuracy Max reading 19999 1- μ V-1KV Remote and Autoranging 110dB series mode reject on No common Mode error **P.O.A.**

D.M.M. 7050 (autoranging) **£245 P.O.A.**

REMEMBER

We also buy

We are interested in providing quotations for the purchase of good quality used and unused Test Equipment.

Shown on these pages are just a few samples of our huge stock. If the item you require is not shown please give us a ring.

01-837 7781

BROKERS LTD

Carriage and packing charge extra on all items unless otherwise stated

Please note: All instruments offered are secondhand and tested and guaranteed 12 months unless otherwise stated



SUPER SAVINGS FOR THE HOME CONSTRUCTOR

Goldring CK2 BELT DRIVE TURNTABLE CONSTRUCTION KIT

Complete with SAU2 arm, template and easy-to-follow instructions. Ready for operation in a short time.

A FEW OF THE MANY BIG FEATURES

- Wow Flutter 0.15% peak
- Rumble -60dB weighted
- Removeable headshell
- Viscouse damped cueing device
- Easily adjusted tracking force and bias setting
- Two speed, 16 pole synchronous motor
- Dimensions 37.8 x 28.3cms

Plinth, cover and cartridge available, P.O.A.
Call in or send a cheque, P.O., M.O., or Access, Barclaycard American Express or Diners Club number.

Lion House

227 Tottenham Court Road, London W.1. Tel 01-580 7383

BRAND NEW IN SEALED CARTONS
12 MONTHS GUARANTEE
OUTSTANDING VALUE
R.P.P. £31.50
OUR PRICE
£16.95
(+ £1.50 p/p & ins)

POCKET TTY



The GR Electronics Pocket TTY offers the keyboard facilities of a teletype - at a fraction of the cost.

- Outputs serial ASCII code to any Teletype-compatible device
- 20 mA loop or RS232 mode
- 36 keys giving full 64 character alphanumerics
- 9 digit LED display of characters entered
- All solid-state with optical coupling for reliability

Pocket TTY can be used for microprocessor programming, production data entry, warehousing, mobile data collection, training and education.

For further details contact: **G.R. ELECTRONICS LTD.**
80 Church Road, Newport NPT 7EH, Gwent, England.
Telephone: Newport (0633) 67426
Telex: 28604 Ref: 1796

WW-093 FOR FURTHER DETAILS

Appointments

BRUNEL UNIVERSITY DEPARTMENT OF EDUCATION

TECHNICIAN

required to supervise three others in a Visual Aids and Reprographics workshop and a Physical Sciences Laboratory. The successful applicant will be required to diagnose faults and, if appropriate, repair a wide range of electro-mechanical and electronic equipment. Applicants should be educated to H.N.C. level or equivalent, and a knowledge of photographic techniques is desirable, as is experience of simple TV production techniques.

Salary within the grade 6 scale £3328-£3964 plus £275 London Weighting Supplement. Four weeks annual leave (plus Easter and Christmas weeks). Good conditions of service, sports and social facilities etc.

Write for application form to Assistant Secretary (Establishment), Brunel University, Uxbridge, Middlesex UB8 3PH or telephone Uxbridge 37188 extension 49. Closing date: 8 July, 1977.

7302

The Media Department of the British Council has two vacancies for

Television Engineers

to operate and maintain their studios, situated in Tavistock Square, London

The studios are used to train personnel from countries overseas in broadcasting and closed circuit television techniques in support of developmental broadcasting and education. As well as for the regular training courses, the studios are used to produce videotapes, films and other audiovisual programmes.

Some of the training activity takes place in institutions situated overseas and there may be opportunities for the successful applicants to work and travel abroad.

An essential qualification is the City and Guilds Telecommunications Certificate or HNC or equivalent or broadcast engineering training. Candidates should also have practical experience in studio operations including vision control, lighting, sound and videotape. One of the posts includes responsibility for the supervision of a small team of operational and maintenance engineers; for this post experience of managing staff would be an advantage.

The salary scales, including London Weighting and pay supplements, range from around £4760 to around £5880. There is a non-contributory pension scheme.

For further details and an application form to be returned by 4 July telephone 01-499 8011 extension 3041 or write to Staff Recruitment Department, The British Council, 65 Davies Street, London W1Y 2AA, quoting reference G/5.

7309

CHELSEA COLLEGE
University of London

ELECTRONICS TECHNICIAN GRADE 2B

required for the construction and maintenance of equipment and apparatus and to assist in the running of Electronics and Physics Undergraduate Teaching Laboratories. Day release available for approved courses. Salary in range £2,769 to £3,112 per annum (inclusive). 37½-hour week. Further details and application form from:

Mr. M. E. Cane (2B.ET)
Chelsea College
Pulton Place, Fulham
London SW6 5PR

(7267)

CAPITAL APPTS.

FREE LISTS
101 Design/Development and Test Jobs.
Permanent and Contract
To £6,000

7317
637 5551 day; 350 0836 eve.

34, Percy St. London, W.1.

**FURTHER
APPOINTMENTS
CONTINUED ON
PAGE 122**

HART ELECTRONICS

The Only Firm for Quality Audio Kits

Are proud to offer the only DESIGNER APPROVED kit for the


J. L. Linsley-Hood High Quality Cassette Recorder



As these circuits are capable of such an excellent performance we feel that it is not sensible to sacrifice this potential by designing a kit down to a price. We have therefore spent a little more on professional hardware allowing us to design a very advanced modular system. This enables a more satisfactory electrical layout to be achieved, particularly around the very critical input areas of the replay preamps. These are totally stable with this layout and require no extra stabilising components. Many other advantages also come from this system which has separate record and replay amps for each channel plugging in to a master board with gold-plated sockets. The most obvious is the reduction of crosstalk and interaction which could cause trouble on a single plane board, with our modular system the layout is compact but there is no component crowding. Testing is very easy with separate identical modules and building with the aid of our component-by-component instructions is childishly simple, but the finished result is a unit designed not to normal domestic standards but to the best professional practice.

All printed circuits are of glassfibre material, fully drilled with a tinned finish for easy and reliable soldering. Component locations are printed on the reverse side of the board and are arranged so that all identification numbers are still visible after assembly.

- 71x Complete set of parts for Master Board, includes bias oscillator, relay, controls, etc. £9.83 + £1.23 VAT
- 72x Parts for Motor Speed and Solenoid Control for Lenco CRV deck. This is the proper board layout as given in the articles. £3.52 + 44p VAT
- 73x Complete set of parts for stereo Replay Amps. and VU Meter drive £8.12 + £1.02 VAT
- 74x Complete set for stereo Record Amps. £6.74 + 84p VAT
- 75x Complete set of parts for Stabilised Power Supply to circuit given in Article. This uses a special low hum field transformer with better characteristics than the commonly used toroid. £8.79 + £1.10 VAT
- 700M2 Individual High Quality VU Meters with excellent ballistics. £8.48 + £1.06 VAT Per Pair
- 700C/2 High Quality Custom built steel Case. Complete with Brushed aluminium front plate, mains switch, record microswitch, turned record level knob, plastic cabinet feet, all bolts, nuts and mounting hardware. All necessary holes are punched and all surfaces are electroplated. Complete step-by-step assembly instructions are included. The cover is finished in an attractive black crackle surface. £16.50 + £2.06 VAT

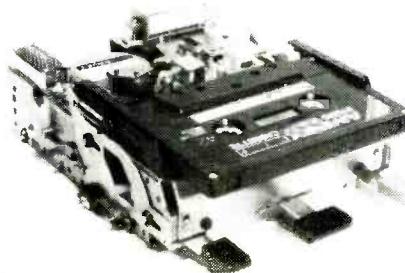

LENCO CRV CASSETTE MECHANISM

High Quality, robust cassette transport for Linsley-Hood recorder. Features fast forward, fast rewind, record, pause and full auto stop and cassette ejection facilities. Fitted with Record/play and erase heads and supplied complete with Data and extra cassette ejection spring for above horizontal use. Price £21.60 + £2.70 VAT

Total cost of all parts £83.58
Special offer for Complete Kits £81.50 + £10.19 VAT
Optional extra solid teak end cheeks, £3 pair + 38p VAT

Reprint of 3 Linsley-Hood Cassette Recorder articles, 45p post and VAT free.

MATRIX 'H' QUADRAPHONIC DECODER

Printed circuit boards and kits to our usual quality are being prepared for this design. Send for list.

We also supply complete kits to make a fully integrated 30 watt stereo amplifier using the Bailey Power Amplifier circuit and the Bailey/Burrows Pre-amplifier with the Quilter Tone control modification.

Printed circuits and components are available for the Stuart tape circuits. These articles described a high quality tape link circuit for use with a reel-to-reel deck. Reprints of the three articles are available from us price 40p Post Free (No VAT)

ALL PARTS ARE POST FREE

Please send 9 X 4 SAE for lists giving fuller details and Price breakdowns

Penylan Mill, Oswestry, Salop

Personal callers are always welcome, but please note we are closed all day Saturday

RELAYS—UNISELECTORS—SWITCHES

MINIATURE-PLUG-IN RELAYS (Siemens/Varley)

with perspex dust cover and base.
6-12-24 48v D.C. In Stock
2c/o 50p: 6 make 60p
4c/o 75p: P & P 10p

S.T.C. MINIATURE (P.C. Mounting)

with dust cover
2c/o (18/24v) 45p P.P. 10p
4c/o (24/36v) 50p P.P. 10p
6c/o (36/48v) 75p P.P. 10p

I.T.T. 240v A.C. Plug-In RELAYS

(with perspex cover) 10 amp contacts
3c/o 75p P.P. 10p

H.D. TIME SWITCHES (100 amp contacts) 1 on/off in 24 hrs. Excellent condition 240v-50 Hz £6.50 P.P. £1.00

UNISELECTORS 25 WAY

5 Bank Full Wipe 75 ohm £5.50 P.P. 50p
6 Bank Full Wipe 75 ohm £6.25 P.P. 50p
8 Bank Full Wipe 75 ohm £7.50 P.P. 50p
12 Bank Half Wipe 68 ohm £8.50 P.P. 60p
SMALL 12V UNISELECTORS 4 Bank 11 way £2.50 P.P. 50p

D.C. SOLENOIDS 24v (Cont. Rated)

10lb Pull .20 mm Stroke. Size 50 x 48 x 42 mm
75p P.P. 15p

TELEPHONE HANDSET with Press-to-Speak Switch.
£1.50 P.P. 40p

CITENCO GEARED MOTORS, 240v 50Hz. 19 r.p.m. torque 14.5 kg/cm. £6.75 (new) P.P. 50p

DECADE INDICATOR SWITCHES with plus & minus Push Buttons. 6 mm digits 75p each P.P. 10p

KEY SWITCHES '1000' TYPE

4c/o each way locking 60p P.P. 10p
6 make each way locking 60p P.P. 10p
Bank of 4. 4c/o each way. 1 biased £1.25 P.P. 15p

MAGNETIC COUNTERS

3 DIGIT RESET COUNTERS (12v D.C.) £1.50 (Ex Equip.) P.P. 20p
3 DIGIT RESET COUNTERS (240v 50 Hz) £1.75 (new) P.P. 25p
6 DIGIT RESET COUNTERS (24v D.C.) £4 (new) P.P. 25p
4 DIGIT NON-RESET (24v D.C.) £1 (New) P.P. 20p
5 DIGIT NON-RESET (24v D.C.) £1 (Ex Equip.) P.P. 20p
6 DIGIT NON-RESET (48v D.C.) £1.50 (New) P.P. 20p

MULTICORE CABLES

4 CORE RIBBON (RAINBOW) CABLE 4 x 10/2m.m forming 1/2in wide strip 10m—75p; 50m—£3; 100m—£6. P.P. 1p per metre

8 CORE RIBBON (RAINBOW) CABLE

8 x 14/76 Forming 1/2in wide strip
10m—£1.50—£6.50; 100m—£12.00 P.P. 1p per metre

5 CORE H.D. CABLE 5 x 70/76 P.V.C.

Black Outer P.V.C. O.D. 1/2in
10m—£2.50; 50m—£12; 100m—£22.50 P.P. 2p per metre

10 CORE CABLE 10 x 7/76 (10 colours) P.V.C. O.D. 7m.m.
10m—£2; 50m—£8.50; 100m—£16. P.P. 2p per metre

16 PAIR RIBBON CABLE 16 x 2 core P.V.C. double sheathed forming 55 m.m wide strip 10m—£3; 50m—£25; 100m—£40. P.P. 2p per metre

EQUIPMENT COOLING FANS (100 C.F.M.)
PAPST-LUFTER 120x120x38 m.m. 115v 50Hz £5.75 (New) P.P. 50p

PAPST 112x112x55 m.m. 220v 50 Hz £3.50 (Ex. Equip.) P.P. 50p

MUFFIN TYPE 120x120x38 m.m. £3 (Ex. Equip.) P.P. 50p

SMALL TRANSFORMERS 240/115v 40p each

WOODS EXTRACTOR 130x130x80 m.m. 240v. 50 Hz £3.50 (Ex. Equip.) P.P. 75p

PAPST (SQUIRREL CAGE) 9 Blade. Less Mounting. £3.50 (New) 240v 50Hz P.P. 50p

VARIOUS

AIR PRESSURE SWITCHES 0-10 lb variable switch contacts 15 amp change-over (a quality unit in turned plated brass) £1.50 P.P. 25p

E.H.T. MODULES. Input 190-260v 50 Hz. Output 13.7kV. PK @ 0.50 mA (150 x 95 x 70mm) £12. P.P. £1.

MYRIA MEGOHMMETER TYPE 35A. 20-200K MEG/ΩHMS 500v test. Excellent condition. £45, carr. £2.50

SYNCHRONOUS GEARED MOTORS (Smiths) 2 r.p.m. 3 r.p.m. 30 r.p.m. 20 r.p.m. 6 r.p.m. 2 r.p.m. all 240v £1.50 ea P.P. 25p

P.C. EDGE CONNECTORS

32 way (1 pitch) finished ends 45p P.P. 10p
56 way (1 pitch) cuttable 65p P.P. 10p
64 way (1 pitch) cuttable 75p P.P. 10p

Mounting Pillars for 56/64 way 15p pair
Gold Plated Contacts 15p extra

32 way (15 pitch) Double-Sided Gold Plate Contacts 50p P.P. 10p

H.D. ALARM BELLS (Ext./Int. use)

4 in Dome (Ext. Gong) 4 1/2/6v D.C. £2.50 P.P. £1.00
6 in Dome (Ext. Gong) 6/8v D.C. £2.75 P.P. £1.25
6 in Dome (Internal Gong) 12v D.C. £3.75 P.P. £1.25
10 in Dome (Int. Gong) 24/48v D.C. £5.00 P.P. £1.50

D.C. POWER SUPPLIES Input 240v A.C. TYPE 1 20v D.C. at 1 amp. Fully regulated 155 x 155 x 75 mm totally enclosed £5 P.P. 75p

PLEASE ADD 8% V.A.T.

J. B. PATTRICK
191/193 LONDON ROAD
ROMFORD, ESSEX RM7 9DJ
ROMFORD 44473

Appointments

Advertisements accepted up to 12 noon Monday, June 27, for the August issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £7.50 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £1.10 per line, minimum three lines.
BOX NUMBERS: 50p extra. (Replies should be addressed to the Box Number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU.)
PHONE: Eddie Farrell on 01-261 8508
Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

Radio Frequency Spectrum Engineering

An influential role £7265-£8435

These senior positions within the Directorate of Radio Technology, London, present Electrical Engineers with an outstanding opportunity to help shape future usage and considerable scope for exercising their individual initiative.

The Directorate provides the technical expertise and engineering support so necessary in forming and implementing management policy. It is concerned with all aspects of spectrum engineering — the forward planning, management and regulation of civil frequency bands; radio propagation over the whole frequency spectrum; specifications and equipment type approval for fixed and mobile services, including microwave links; the application of computer techniques to frequency management problems; the nationwide radio interference service; the provision of technical advice on radio services, licensing; and the operation of an international radio monitoring service. It is also very much involved in the technical preparations for the 1979 World Administrative Radio Conference.

The successful candidates will lead specialised teams responsible for key areas within the Directorate's activities. The work should appeal to those engineers who enjoy applying imagination and new ideas to problem solving.

For further information about the work, telephone Mr. R. A. Bedford on 01-275 3381.

Candidates must have a degree or equivalent qualification in electrical engineering and should be Chartered Engineers. In-depth knowledge and experience of spectrum engineering is essential together with a sound appreciation of allied disciplines. Candidates must also have managerial ability and be able to deploy and stimulate staff of different skills. Working knowledge of French an advantage.

Starting salary within the quoted range. Promotion prospects to £10,000 and above. Non-contributory pension scheme.

For an application form (to be returned by 8 July, 1977) write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). Please quote T/9536/2.

(7324)

HOME OFFICE

DESIGN TEST FIELD SERVICE

Immediate vacancies exist in most areas for engineers qualified to BSc/HNC/C&G with analogue, digital or R.F. experience.

Phone or write

APEX PERSONNEL
800 FULHAM ROAD
LONDON S.W. 6

01-731 4353

(7155)

ELECTRONICS ENGINEER

(Audio)

needed urgently by lively young West London Company.

Write/ring:

INTEGRATED MUSIC LIMITED
188 Blythe Road, London, W14
01-602 2302

(7288)

AVIONIC TECHNICIANS

required

Interesting and varied work on Navigation and Communication Equipment including VHF, VOR, ADF, HF, RADAR, TRANSPONDER / DME & CABIN ADDRESS SYSTEMS.

- ★ Salary from £3,750 to £4,100 according to experience, reasonable overtime opportunities could raise this to £5,000 if desired.
- ★ 5-day week.
- ★ 4 weeks' holiday per annum plus statutory holidays.

Contact: **ROBIN SHOPLAND**

AIR TRANSPORT (CHARTER) C.I.) LIMITED
7 WILLOW ROAD, COLNBROOK, SLOUGH, BERKS.
Telephone Colnbrook 2654

(7268)



CAPITAL APPOINTMENTS LTD.

FREE JOBS LIST
for
FIELD SERVICE ENGINEERS
BASIC SALARIES TO
£5,000 + CAR

7316

34 Percy Street, London, W1
01-637 5551

SUNNY SOUTH COAST

Expansion on the South Coast in the Electronics Industry now demands urgently the following personnel: **Electronic Engineers (R&D), Design Engineers, Software Programmers, Systems Engineers, Development Engineers, Sales Engineers, Trials Engineers, QA Engineers, Test Engineers, Production Engineers, design Draughtsmen, Inspectors, Buyers.**

All these positions offer excellent salaries and prospects and in most cases relocation expenses. Ring or write: C.B.S. Appointments - 224 Old Christchurch Road, Bournemouth, 292155 or Wimbourne 4891 evenings

(7319)

ELECTRONIC DESIGN/ DEVELOPMENT ENGINEERS

FERRANTI OFFERS YOU FREEDOM

..... freedom to create. Over the years leading design and development engineers have been attracted to Ferranti by our reputation for truly innovative engineering and together they have formed specialised teams involved on a variety of sophisticated projects related to the Tornado, Sea Harrier, Jaguar, Nimrod 2 and other front line aircraft.

We now require additional engineers to join these teams engaged on the creative work of designing and developing airborne radar, laser and inertial navigation systems and their associated test equipment.

Engineers are required in the following technical fields:-

Digital and analogue electronic circuitry design.

Design and application of small digital computers.

Microwave and laser techniques.

Advanced instrument design including gyroscopes of inertial quality.

Design of small mechanical structures and analysis of stress.

In addition to the above we have vacancies for production engineers with either electrical or mechanical backgrounds in these fields.

Applicants should have some design/development experience to offer in avionics and a desire to expand their experience to project leader level.

Edinburgh, with its outstanding facilities for education, housing, sport and entertainment, is one of the ideal cities in Europe in which to live, work and bring up a family. And to make moving here easier, we pay realistic relocation expenses. Salaries are negotiable and the Company operates a contributory pension and life assurance scheme.

Apply in writing, with full details of experience and qualifications to

Staff Appointments Officer,

Ferranti Limited,

Ferry Road,

EDINBURGH, EH5 2XS.

Please quote Ref. WW/5

FERRANTI

Electronics Engineer today?

You could be the Computer Engineer of tomorrow!

ICL, Europe's leading computer manufacturer, supplies systems to governments, universities, research, industry and commerce. ICL is renowned for its efficient customer service, and each of our customers relies on a team of Systems Engineers - which is where you come in.

We're building up our intake of Electronics Engineers who will undergo a thorough initial training over 18 weeks at our Training Centre in Letchworth, Hertfordshire - the largest of its kind in Europe, with accommodation provided. You will then work at one of three locations which you choose at interview, from the large number we have throughout the country. Within 18 months you will be a fully trained Systems Engineer with a career rich in opportunity

ahead of you, and you will have the satisfaction of using all your technical expertise, tact and personality as a representative of ICL.

You could be just the person we're looking for if you're 20-35 and have any one of the following qualifications plus two years' practical electronics experience:

- City & Guilds Full Electronics Certificate.
- HNC in Electronics.
- A Completed Electronics Apprenticeship.
- An HM Forces Electronics Training.

Why hesitate when one of the world's top technologies is there for the taking? Phone David Reeves on 01-788 7272 extension 4150 for an application form, or send the coupon.

To: David Reeves, ICL, 85/91 Upper Richmond Road, Putney, London SW15 2TE.

WW1389

I would like to find out more about becoming a Computer Engineer with ICL. Please send me details.

Name

Address

International Computers

think computers - think ICL

7299



ELECTRONIC CIRCUIT DESIGN PHGY 5182

Do you enjoy the challenge of using advanced technology to solve complex interdisciplinary problems. Are you thoroughly conversant with the use of discrete components, micro-circuit amplifiers, function generators, TTL and C.mos techniques? Can you design both analogue and digital circuits? We have one vacancy for a senior technician in a small team providing a comprehensive design, construction and maintenance service for teaching and research.

Candidates must have at least 9 years relevant experience including 2 years design work. HNC standard is required and the ability to supervise other staff is essential. Familiarity with medical electronics an advantage.

Salary on University Technical Scale Grade 6 £3315 x 7 - £3950. Letters of application stating age, qualifications, experience and the names of 2 referees to: Administrator, University of Oxford, Department of Physiology, Parks Road, Oxford OX1 3PT

Further details from Wilf Laycock, Supervisor, Electronics Group, Oxford 57451.

7310

APPOINTMENTS IN ELECTRONICS

Take your pick of the permanent posts in:

- MISSILES - MEDICAL COMPUTERS - COMMS
- MICROWAVE - MARINE HARDWARE - SOFTWARE

For expert advice and immediate action on career improvement, phone, or write to, Mike Gernat BSc

Technomark
Engineering and Technical Recruitment

11 Westbourne Grove
London W2 01-229 9239.

7098

UNIVERSITY OF STRATHCLYDE CENTRE FOR EDUCATIONAL PRACTICE (AUDIO VISUAL UNIT)

TELEVISION ENGINEER

Grade 3

required with experience in the maintenance of electronic equipment. The work includes the repair and operation of a wide range of audio visual equipment. The Engineer will also become a member of the studio crew as a Television Cameraman. Applicants should hold an O.N.C., O.N.D. or City and Guilds Certificate and have 3-5 years' relevant experience.

Salary Scale (including all supplements): £2455-£2788 per annum, dependent on experience and qualifications.

Applications in writing, QUOTING REFERENCE CEP. 13/WW, giving details of age, experience and qualifications, should be made to the Personnel Officer, University of Strathclyde, Royal College Building, 204 George Street, Glasgow G1 1XW.

7298

Hoggett Bowers

Executive Selection Consultants


Trade Magazine Editor

Hong Kong Attractive salary negotiable

Our client, a major South East Asia publishing group, requires an editor for a growing consumer electronics trade magazine. The successful candidate will initially assist the Group Managing Editor, who is currently editing this magazine, and will assume full editorial control as soon as he has gained sufficient knowledge of the trade in the region. He will then be expected to develop the magazine further and increase the coverage into new countries.

Applicants must have had at least five years experience in journalism with at least three in electronics, and will have gained some knowledge of the technical, as well as marketing aspects of the industry. Taxation in Hong Kong is very low and the package will include excellent fringe benefits.

H.W. FitzHugh, Ref: 20053/WW

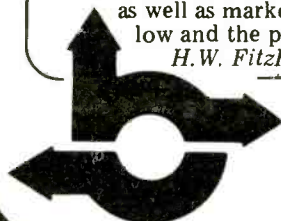

Male or female candidates should telephone in confidence for a Personal History Form to:
LONDON: 01-734 6852,
Sutherland House, 5/6 Argyll Street, W1E 6EZ.
Offices also in Birmingham, Glasgow, Leeds, Manchester, Newcastle and Sheffield.

7323

You listen to Radio? You watch Television? You're a qualified electronic engineer and yet you've never considered working in broadcasting?

Then perhaps you need to know a little more about some of the opportunities available with the BBC.

Studio Capital Projects

Engineering staff are based in central London, but will travel to various studio centres to assist in the design, installation and commissioning of radio and television studio equipment.

Transmitter Capital Projects

Again based in central London, engineers are required to travel to studios all over the U.K. to assist with the design and commissioning of radio and television transmitters and their associated aerial systems.

Candidates for both these departments should either possess a British university or polytechnic degree in electronic engineering or physics.

Television

Working in the Television Service, based in West London, engineers are involved in the maintenance and operation of the equipment used in the origination and distribution of television programmes.

Transmitters

Engineers are allocated to the major stations in various parts of the country and are respon-

sible for both the maintenance and operation of radio and television transmitter plant. For these positions a current driving licence would be an advantage.

BBC Receiving Station

This station, based at Caversham, Berkshire, requires engineers to operate and maintain the elaborate receiving terminal equipment to enable foreign broadcasts to be monitored.

For these three departments candidates should possess either a City and Guilds full Technological Certificate in Telecommunications (course No. 271) or an HNC in Electronic Engineering. Shift working will normally be involved, for which generous extra payments are made.

Candidates for all positions must have normal colour vision and hearing.

For further information and an application form, write stating which type of engineering you are interested in to the **Engineering Recruitment Officer, Broadcasting House, London**


W1A 1AA, quoting reference No. 77.E.4034/WW

and enclosing a self addressed foolscap envelope.

Closing date for completed application forms is 14 days after publication.



BBC

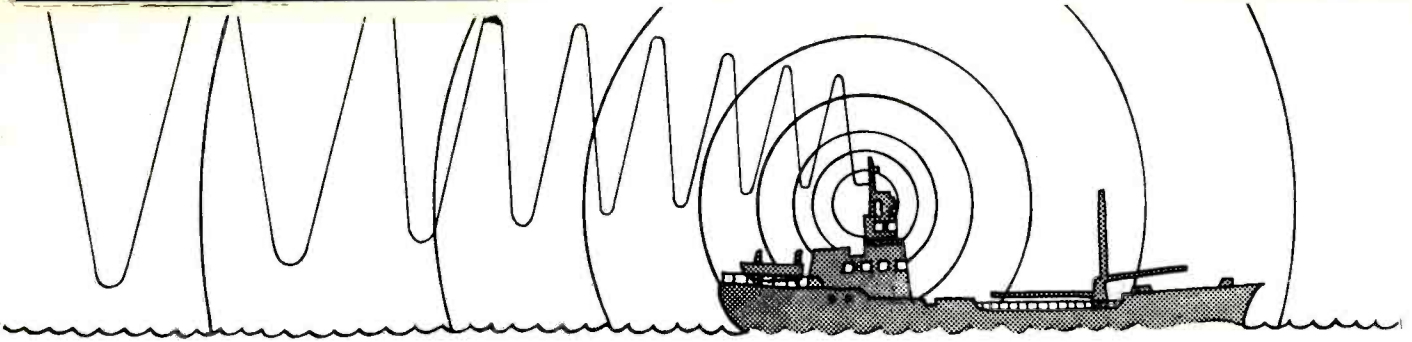

Radio Officers—now you can enjoy the comforts of home.

Working for the Post Office Maritime Services really makes sense. You still do the work that interests you, but with all the advantages of a shore-based job: more time to enjoy home life, job security and good money. To qualify, you need a United Kingdom Maritime Radiocommunication Operator's General Certificate or First Class Certificate of competence in Radiotelegraphy, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting salaries, at 25 or over, are £2905 rising to £3704 after three years service. Between 19 and 24, the starting salary varies from £2234 to £2627 according to age. In addition, a supplement of £312

p.a. is payable. You'll also receive an allowance for shift duties which at the maximum of the scale averages £900 a year and there are opportunities to earn overtime. There's a good pension scheme, sick pay benefits and prospects of promotion to senior management.

Right now we have a few vacancies at some of our coastal radio stations, so if you're 19 or over, preferably with sea-going experience, write to: ETE Maritime Radio Services Division (L690), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.

Post Office Telecommunications

RADIO TECHNICIANS

Government Communications Headquarters has vacancies for Radio Technicians. Applicants should be 19 or over.

Standards required call for a sound knowledge of the principles of electricity and radio, together with 2 years experience of using and maintaining radio and electronic test gear.

Duties cover highly skilled Telecommunications/electronic work, including the construction, installation, maintenance and testing of radio and radar telecommunications equipment and advanced computer an analytic machinery.

Qualifications: Candidates must hold either the City and Guilds Telecommunications Part I (Intermediate) Certificate or equivalent HM Forces qualification.

Salary scale from £2,230 at 19 to £2,905 at 25 (highest pay on entry), rising to £3,385 with opportunity for advancement to higher grades up to £3,780 with a few posts carrying still higher salaries. Pay supplement of £313.20 per annum.

Annual Leave allowance is 4 weeks rising to 6 weeks after 27 years' service.

Opportunities for service overseas.

Candidates must be UK residents.

Further particulars and Application forms available from

Recruitment Officer
Government Communications Headquarters
Oakley, Priors Road
CHELTENHAM, Glos GL52 5AJ
Tel. Cheltenham 21491 Ext. 2270
(STD 0242-21401)

(7219)

ilea

Learning Materials Service

Television Centre, Thackeray Road, SW8

Maintenance Engineer

The Television Centre of the ILEA Learning Materials Service, situated at Battersea, has a vacancy for a maintenance engineer with specialist knowledge of professional studio and film sound equipment. The Centre, which produces programmes for over one thousand educational establishments, is provided with television and film production facilities at broadcast level, which are shortly to be converted to colour.

The successful candidate will join the maintenance section (four in number) and, with other members, will be responsible for maintaining a very wide range of vision and sound equipment which includes helical scan VTR's and cassette machines. He or she will be expected to be the department's expert in sound with particular knowledge of professional mixing desks, tape recorders and 16mm magnetic film recorders and reproducers (some involving digital techniques) and must have a number of years experience in this work. An HNC, the final City and Guilds' certificate or a similar qualification in relevant subjects is desirable.

Salary within the scale £4,864-£5,191 (Studio Technician 3).

Application forms, returnable within 14 days of the publication of this advertisement, from the Education Officer, Estab 2A/2, Room 4A, Addington St. Annexe, County Hall, London SE1 7UY. Tel: 01-633 7456.

(7290)

Quick Quiz

Just a tick, that's all it will take you.

- | | Yes | No |
|---|--------------------------|--------------------------|
| 1. Can you fault find Electronic Circuits ? | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Do you know how to use an Oscilloscope ? | <input type="checkbox"/> | <input type="checkbox"/> |
| 3. Are you able to read circuit diagrams ? | <input type="checkbox"/> | <input type="checkbox"/> |
| 4. Can you use a Spectrum Analyser ? | <input type="checkbox"/> | <input type="checkbox"/> |
| 5. Do you understand the meaning of GHz ? | <input type="checkbox"/> | <input type="checkbox"/> |
| 6. Does V.S.W.R. mean anything to you ? | <input type="checkbox"/> | <input type="checkbox"/> |
| 7. Do you know how many "ohms" in a village ? | <input type="checkbox"/> | <input type="checkbox"/> |

If you score five or more "Yes" answers, then you could qualify for a really interesting career as a Test Technician with Marconi-Elliott Avionic Systems.

In our Mobile Radar Division at Borehamwood in Hertfordshire we're looking for men and women with a good basic electronics background to join teams working on the development, test and manufacture of a wide range of radar equipment and electronic surveillance and alarm systems.

It's challenging work and our Laboratories employ the most advanced techniques. Your experience, plus some training from us, will enable you to enjoy a satisfying future with a top company in the field of electronics development.

If you would like more details, get in touch now with G. Cock at Marconi-Elliott Avionic Systems Limited, Elstree Way, Borehamwood, Herts. Tel: 01-953 2030, Ext.3195.

MARCONI ELLIOTT AVIONICS

A GEC-Marconi Electronics Company

COMMUNICATIONS ENGINEER

Newcastle upon Tyne up to £4131

The Engineering Research Station at Killingworth is looking for a Communications Engineer to be involved in developing techniques which will increase the capacity of the Corporation's mobile radio channels. Work may be broadly split into two areas:

- (i) investigation of the performance and implementation restrictions of wide area-coverage schemes.
- (ii) investigations leading to more effective use of spectrum including problems associated with the transmission of digital information to mobile receivers.

A considerable involvement in discussions with user departments will be needed to ensure feasible integration of new techniques with existing systems.

Candidates should have a degree in Electronics, preferably with a specialisation towards communications.

Starting salary will be within an incremental scale rising from £2361 to £3819 plus a flat rate supplement of £312 p.a., with initial placing according to age, qualifications and experience.

Application forms may be obtained from the Manager/Management Services, British Gas Engineering Research Station Killingworth, Newcastle-upon-Tyne NE99 1LH quoting reference RD/539656/ERS (656) WW

BRITISH GAS



(7325)

TELEVISION ENGINEERS EXPORT OPERATIONS

Rediffusion Consumer Electronics is expanding its engineering team to give greater technical support to its customers with particular emphasis on export markets.

If you are a qualified television engineer with current experience in at least some of the following disciplines we should like to hear from you:

- ★ Design and development of colour TV receivers.
- ★ Safety engineering, radiation measurements and test house submissions.
- ★ Quality Assurance in a modern factory environment.
- ★ Customer service with particular emphasis on export markets.
- ★ Assessment of audio products from world wide sources.

The team is based at our engineering centre at Chessington, Surrey, but occasional visits to our factories in the North East of England and to our customers, home and abroad, will be required.

Salaries are attractive and assistance with relocation expenses will be offered if appropriate. If you feel you can make a real contribution towards the further success of our operation please write to:

Mr. H. Brearley
Head of Technical Services
REDIFFUSION CONSUMER ELECTRONICS LTD.
 Fullers Way South
 Chessington
 Surrey, KT9 1HJ
 or phone 01-397 5411



7301

TECHNICAL ASSISTANTS

Communications Department

Vacancies will exist for Technical Assistants in the Summer 1977 to work in the Communications Departments of the BBC based in Central London.

Technical Assistants will work under supervision on the maintenance and in some cases the operation of electronic equipment used in the distribution of radio and television programmes.

Duties

Technical Assistants will be concerned with the switching and routing of both television and radio programmes and in the provision and maintenance of all communication systems.

Training

Technical Assistants receive full-time training, which if successful should enable them to qualify internally as BBC Engineers in something over two years.

Qualifications

Applicants, who must be between the ages of 18 and 26 and have normal colour vision and hearing, should have had a good general education and be able to offer G.C.E. 'O' levels in English, Maths and Physics, or the equivalent, and have read up to 'A' level in Maths and Physics. Alternatively an ONC or Part I of the City & Guilds Telecommunications Technicians Course (No. 271) would be acceptable. In addition it is essential that they can demonstrate the ability to apply their knowledge of electricity and magnetism to related practical applications in the fields of communications, radio and television.

Salary

Depending upon experience the starting salary on appointment will be in the range £2514 to £2706 p.a. Additional payments will be made for those Technical Assistants who are required to work shift rotas or irregular hours. In addition a monthly pay supplement depending on total earnings of between £10.86 and £17.38 is payable under the current Incomes Policy.

For further details and application form please write to **The Engineering Recruitment Officer, BBC, Broadcasting House, London W1A 1AA** quoting reference number 77.E(R) 4036/WW and enclosing an addressed envelope at least 9" x 4". Closing date for completed applications is 14 days after publication.

BBC

7266

GRAMPIAN TELEVISION LIMITED

ENGINEERS/TECHNICIANS

The Independent Television Company for North and East Scotland seeks electronic engineers or technicians for duties at its Studio Centre in Aberdeen.

The successful candidates will be employed in the operation and maintenance of modern electronic broadcast equipment.

Experience in this field is desirable but candidates without this experience, having a sound technical training, will be considered.

Salary is in the range £2689 to £4887, dependent on experience, with the prospects of later promotion through competitive interview to more senior posts.

Applications, in writing, to:

Mrs. E. A. Gray
 Personnel Officer
 Grampian Television Limited
 Queen's Cross
 Aberdeen AB9 2XJ

(7328)



'SERVING THE OIL COUNTRY'

SALES ENGINEERS

If you are looking for a stimulating and demanding job with the prospect of regular overseas travel on a world wide basis, why not join Pye TVT, one of the world's leaders in the design and manufacture of broadcasting equipment?

Continuing expansion has led to the need within the Technical Sales Department for Sales Engineers in the following fields:

1. Video Tape Recording.
2. Video Mixing, Switching and Assignment, including Station Automation and Computer Editing Systems.
3. Colour Cameras and Telecine.

In each case the successful candidate will be required to discuss advanced and sophisticated equipment at a high engineering level and to assist the regional and area managers in the marketing of these products.

A degree or equivalent qualification is desirable, but several years experience in the relevant field is more important.

These are very responsible posts and salaries will reflect the importance we attach to these appointments. Relocation expenses to this pleasant part of East Anglia will be given in approved cases.

Please write or telephone: Dave Barnicoat, Pye TVT Limited, PO Box 41, Coldhams Lane, Cambridge CB1 3JU.

Telephone: Cambridge 45115

(7291)



A member of the Pye of Cambridge Group

Pye TVT Limited

The Broadcast Company of Philips

WIRELESS TECHNICIANS

There are vacancies at Home Office Wireless Depots throughout England and Wales for Wireless Technicians to assist with the installation and maintenance of VHF and UHF Systems etc.

Applicants must be able to drive a car and be in possession of a current United Kingdom driving Licence.

Salary

is £2010 (at 17), £2450 (at 21) and £2905 (at 25) rising to £3385, plus a 1976 pay supplement of £313.20 a year and a 1977 pay supplement of 5% of total earnings, subject to a minimum of £101.79 a year and a maximum of £208.80 a year.

A Secure Future

with a non-contributory pension scheme, good prospects of promotion and a generous leave allowance. There are opportunities for day release to gain higher qualifications.

Qualifications

Candidates, male or female, must hold a City and Guilds Intermediate Telecommunications Certificate or equivalent qualification and have had good experience in Telecommunications.

Interested?

Then write or telephone for further details and an application form to:- Mr C B Constable, Directorate of Telecommunications, Home Office, 60 Rochester Row, London SW1P 1JX. Telephone: 01-211 6420.

(7315)



Home Office

ELECTRONICS ENGINEERS

Are you a young flexible, electronics engineer preferably with HNC and some experience in design/development, able to analyse circuitry and modify existing equipment as well as creating original equipment?

Does the opportunity of joining a small Company in the forefront of scientific instrumentation where hard work and initiative are well rewarded appeal to you?

The job involves the on-site installation, commissioning and after-sales servicing of our range of complex instrumentation and requires a high degree of technical skill, initiative and responsibility.

In return we offer plenty of interest and travel (sometimes international) coupled with first-class working conditions. Salary is by negotiation and all travelling expenses are reimbursed.

Please apply in writing to:



R. F. LADBURY
BRUKER SPECTROSPIN LIMITED
 UNIT 3, 209 TORRINGTON AVENUE
 COVENTRY, CV4 9HN

7297

SITUATIONS VACANT

Botswana Telecomms Engineer

For varied engineering and administrative duties to ensure the efficient functioning of telex, telephone, telegraph, and broadcast services for the Botswana Ministry of Posts and Telecommunications.

Candidates, under 55, must be MIEE or MIERE, preferably with a degree. 15 years' experience in telecomms operations is required, including responsibility for maintenance of telex, radio relay and multiplex systems, automatic exchanges, subscribers' equipment and distribution networks. A knowledge of electronic exchange working, exchange signalling systems, and broadcast transmitters is desirable.

Starting salary is equivalent to £6145-£7680 pa and includes a substantial tax-free allowance paid under Britain's overseas aid programme. Basic salary attracts a 25% tax-free gratuity.

Benefits include free passages, generous paid leave, children's holiday visit passages and education allowances, subsidised housing, appointment grant and interest-free car loan.

For full details and application form write quoting MX/1202/wd to

Crown Agents

The Crown Agents for Oversea Governments and Administrations, Appointments Division,
4 Millbank, London SW1P 3JD

7296

RADIO ENGINEER/TECHNICIAN FOR THE CARIBBEAN

Needed to work as technical adviser to the Radio Schools in Haiti, a non-governmental literacy development programme. Responsibility for the training of local counterparts.

A British Volunteer Programme Post: volunteer terms of service include free accommodation, living and other allowances, return air travel, language and orientation courses.

CIIR

OVERSEAS
VOLUNTEERS

Write with details of curriculum vitae to
CIIR Overseas Volunteers, 1 Cambridge Terrace, London, NW1 4JL

7277

ARTICLES FOR SALE

MTV

Best choice for used TV

- Largest stock and selection of colour and mono TV in Britain.
- 1976 exports exceeded 250,000 sets.

Trade enquiries to:
Midland TV Trade Services,
Worcester Road, Kidderminster DY10 1HY,
England. Tel. Kidderminster 61907 or 67390.
Telex 337993 (7130)

MAGNETIC MICROPHONE SPEAKERS

4T Inserts, ideal for all sound speaking and listening applications. Very rugged. DC res. 20 ohms.
Size: 1 1/8" dia. 1/2" deep.
40p ea. + 10p P&P
6 for £2.20 + 20p P&P
12 for £4.50. P&P free.
S.A.E. for list. Many other items. Trade enquiries welcome.

B.B. SUPPLIES, 141 Shalford Street
Nr. CANTERBURY, Kent CT4 7QZ (6/92)

ITN

SENIOR ENGINEER VTR OPERATIONS

Independent Television News Ltd. has a vacancy for a Senior Engineer in the ITN Facilities Centre in Central London, able to operate and maintain a tape transfer area of, at present, 18 Helical Scan Video recorders.

Candidates should have several years' experience with such equipment, and experience of broadcast 2" quad recorders would be an advantage.

Salary £5712 per annum.
Contributory Pension Scheme and free Life Insurance.

Please telephone the Personnel Officer on 01-637 3144 for an application form, quoting reference 8312.

7294

ASSISTANT ELECTRONICS ENGINEER

required for a Research and Development company in West London.

A vacancy exists for a young engineer educated to HND standard to join a design and development section working on the control of vehicle engines. Experience in industry is desirable but not essential as the applicant would be at a junior level in the first instance.

Please apply, giving details of age, qualifications and experience to:

The Development Manager, SGRD Limited
Concord Road, LONDON W3 0SE

(7286)

ARTICLES FOR SALE

VHF Rx ass for use on 121.5Mc/s but can be moded to any freq 100/150Mc/s as 9 min. valves, O/P for phones, crystal controlled HC6/u type not supplied, new cond. with circ. £6.50. **ISOLATING TRANS** pria 230v sec 26v at 13 amp with c.t. fitted in case with ammeter new £17.80. I.F.F. **TRANSPONDER** for use in range 950/1100Mc/s with tunable Tx and Rx cavities. 60Mc/s I.F. strip, pulse modulator circs. 115 400C/s I/P, plus large number of misc parts with circ, note these are supplied less valves and ext store soiled otherwise complete £10.80. **INFRA RED TEST SETS** contain mains p.u. giving 24v. d.c. infra red source, ent unit giving 12Kv from 24v, meter, test jig cables, etc., all in neat case transistorised used to test image convertor tubes, good cond. £15. **BATTERIES**. Dryfit sealed lead acid two types 1.8 A/hr. size, 2 3/4x2x2" £5.40 and 2.6 A/hr size 5 1/4x1 1/2x2 1/4" £6.50, both new. **KEYBOARDS** for telephone 0 to 9 digits size 4x3" new £1.50. **PLUG & SK** min. 12-way req 3/4" fix hole new £2 per pair. C.R.T.s all new electrostatic CV2184 2 3/4" P7 £4.50. CV1746 6 1/2" P.1 ordf. tube £6. CV1534 11" P11 orange £10.80. **SELSYNS** mains power type 230V £25 per pair. **RADAR SCANNER** by Decca 24v drive X band with qty of w.g. £54. **TIMBERS** will measure up to 60 secs in 1/100ths of a sec 24v new £15. **TAPE RECORDER** airport type audio 10 track with rec and playback amps (no erase) for 230v 19" rack with handbook one only £108. **U.H.F. GROUND** Tx/Rx inst comprise Tx, Md & Rx covers 225/400Mc/s single channel, O/P 100 watts a.m. I/P 115v 50c/s units are for 19" rack mt, American surplus £173. The following for callers: Marconi h.f. spec analysers 3/30Mc/s £45. P.A. Amps 100watt valve type with c.u. etc. mains £27. P.A. speaker outdoor type 15" £8 ea. **TANNOY** 200 watt transis amps with control gear also high power p.a. speakers. **SCOPES**. Solartron CD643 DC to 15Mc/s large 5" single beam scopes £30. Prices inc. VAT and Carr. Goods ex. equip. unless stated new. Carr. applies mainland only.

A.H. SUPPLIES

122 Handworth Road, Sheffield S9 4AE. Phone 444278 (0742)

(7272)

ELECTRO-MECHANICAL METERS 4 digit, Magnetic meters, 48 volt. 75p inc. P&P. 42 St. Paul's Road, Bedford. (7281)

HEATHKIT SEMI CONDUCTOR TESTER. Latest model IT121. As new. Factory tested. £45. — Tele-radio 325 Fore St., London N9, 01-807 3719. (7278)

SITUATIONS VACANT

Interested in computers?

Lecture on Computer Servicing

International Computers

think computers—think ICL

We are looking for Lecturers to teach the practicalities of computer servicing. You will be based at our Engineering Training Centre in Letchworth, Herts – the largest of its kind in Europe. Here you will be given a comprehensive grounding in computer technology in general and ICL equipment in particular.

You will be thoroughly prepared to train engineers to the point where they will be capable of maintaining computers at the optimum operational specification.

Ideally, you will have an HNC or Forces' training in a technical subject. Any experience of digital electronics, computers or instructing on these subjects, while not essential, will be useful. Fluency in written and spoken French or German would be a distinct advantage but is not essential.

We'll start you as an Assistant Lecturer on a salary of not less than £3800 a year, subject to review in the near future. You'll be encouraged and expected to progress to the position of Senior Lecturer which carries a salary in excess of £5000.

Relocation expenses will be considered where appropriate.

For an application form, phone David Reeves on 01-788 7272 extension 4150, or write to him at ICL, 85/91 Upper Richmond Road, Putney, London SW15 2TE. *Please quote reference WW1398.*



Do us a service and put us to the test

Service and Test Engineers

As aircraft and electronics equipments become more sophisticated and our servicing programme expands, the need for experienced Service and Test Engineers increases.

At Stanmore, we are involved in the provision of spares and the repair, maintenance and overhaul of a variety of British and American airborne electronic equipment.

We need Engineers who can successfully maintain the high standards and efficiency required both in the aircraft and the workshop.

It's skilled work, calling for sound practical experience of radio and electronics theory, ranging from audio to microwave and including the use of advanced test equipment for fault diagnosis. Training in this field will be given to suitable, less experienced engineers.

The Company offers excellent salaries and benefits together with first-class working conditions in well-equipped workshops. This Unit is conveniently situated in pleasant surroundings within easy reach of the A1 and M1.

If the job sounds interesting and you'd like to put us to the test, write with details of experience to:
Mrs. E. Wagg,
Marconi-Elliott Avionic Systems Ltd.,
22-26 Dalston Gardens, Stanmore, Middlesex
HA7 1BZ. Tel: 01-204 3322.

MARCONI ELLIOTT AVIONICS

A GEC-Marconi Electronics Company

7300

MARINE ELECTRONIC ENGINEER/ TECHNICAL MANAGER

This fast expanding company seeks a qualified, experienced person capable of installing and servicing SSB, VHF, Auto Pilots, Radar, Instruments, Electrics, etc., and to take charge of all engineering aspects with a possibility of a Board appointment as Technical Director.

The successful applicant must live in, or very close to London. Salary negotiable.


Send full curriculum vitae to:

Telesonic Marine Limited
243 Euston Road, London, NW1
Tel: 01-387 7467/8

(7327)

V.H.F. SERVICE TECHNICIAN REQUIRED with full experience of Mobile Radio, mobile and base station equipment. Applicants will work in our modern and well equipped workshops in Croydon with occasional work in the field. Applicants should be responsible and fully experienced. Friendly and fast expanding company, salary commensurate with ability and experience with ample opportunity for overtime if required. — Telephone Jonathan Clark, London Car Telephones. 01-680 1010. (7293)

ARTICLES FOR SALE



Quartz Crystal Units
ACCURATE
RELIABLE

Private enquiries, send 1.3p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT
NEW MALDEN, SURREY 01-942 0334 & 2988

SITUATIONS VACANT

ELECTRICAL/ ELECTRONICS ENGINEERS

a consultancy/managerial/designer role

The Government Communications Headquarters has a constant demand for specialised complex equipment and systems designed by its own engineers, as well as readily available commercial equipment.

The successful candidates will undertake engineering project officer duties. These will include interpreting non-technical briefs; advising clients on the best method of approach; preparing specifications and designs; and managing projects right through to implementation.

Currently there are vacancies in the following fields: Radio Communication Systems across the range from VLF to microwaves and the millimetric bands; Line and Data Communication Systems including computer application; and Main Computer systems together with a wide range of peripherals.

Candidates must have a degree in electrical or electronic engineering or be academically qualified for corporate membership of the IEE or IERE, and have at least 5 years' recognised study, professional training and experience.

Starting salary between £3950 and £5240, depending on qualifications and experience. Promotion prospects. Non-contributory pension scheme.

For further details and an application form (to be returned by 11 July, 1977) write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). Please quote T(A) 85/1.

(7311)

GCHQ
Cheltenham

Engineer Programmers

For advanced test programming techniques

Engineer Programmers are needed by the Electronic Switching Products Division of S.T.C. The job is to prepare test programmes using a high level language and/or to derive test generation techniques to control the testing of digital printed circuit board assemblies on automatic test equipment.

If you have had experience in testing, fault finding, commissioning, or a similar field using modern electronic methods and devices, these positions may interest you. A formal qualification - degree, HNC or equivalent, in electronics is necessary.

We are situated on the outskirts of North London with all the amenities of a large established location. We are offering competitive benefits and there is a very real scope for advancement for the right men and women.

For further information please telephone or write to:

Mike Randal, *Electronic Products Switching Division, Personnel Dept, Standard Telephones and Cables Ltd, Oakleigh Road South, New Southgate, London, N11 1HB. 01-368 1200 Ext. 3066.*

Standard Telephones and Cables Limited

A British Company of ITT

7314

ARTICLES FOR SALE

EXCLUSIVE OFFER

WORLD-WIDE RANGE
NEVER BEFORE OFFERED

PHILCO HC-150 POINT-TO-POINT STRIP RADIO HF RECEIVERS 2/30 m/cs. Ten fully tuneable channels to 0.5 kcs with synthesiser. Single and diversity reception on ISB, DSB, SSB with 4 sub-bands to each channel. Full details and prices on application.

AUDIO AND INSTRUMENTATION-
TAPE RECORDER-REPRODUCERS

- * Plessey ID33 Digital Units, 7 track 1/2"
- * Plessey M5500 Digital Unit, 7 tracks 1/2"
- * Ampex FR-1100, 6 speeds, stereo 1/2"
- * Ampex FR600, 4 speeds, 7 tracks 1/2"
- * D.R.I. RM1, 4 speeds, 4 tracks 1/2"
- * EMI TR90 2 speeds, 1 track 1/2"
- * EMI BTR1, 1 speed, 1 track 1/2"
- * EMI R301G, 2 speeds, 2 tracks 1/4"
- * EMI RE321 1/2" 1 track
- * Ficord 1A 1/2", 1 track
- * Minicom CMP-100, 6 speeds, 7 tracks 1/4, 1/2, 1"
- * Leavers Rich DA-2P, 2 speeds, 2 tracks 1/4"
- * Leavers Rich Console 2 track 1/2", 2 speeds

Prices of above £70 to £500

Also Transport Decks only available

We have a large quantity of "bits and pieces" we cannot list - please send us your requirements, we can probably help - all enquiries answered.

All our aerial equipment is
professional MOD quality

- * Airmec 761 Frequency Standards £32.00
- * Gloster Digimasters £90.00
- * Davian Logic Testers £20.00
- * General Radio Stroboscopes £30.00
- * Data Efficiency Respooler, 240v £28.00
- * Airmec 201 Sig. Gen. 30 KC/30 MCS £70.00
- * Valradio Invertors 12V DC/240V AC 500W £42.00
- * Oscilloscopes Gen. purpose 3" £35.00
- * Solartron CD 711, 52 D/U Oscilloscopes £110.00
- * Airmec 702 Sig. Gen. 30/300KCS £35.00
- * R-216 Power Supply Units £15.00
- * 10ft Lightweight Mast sections, 8" sides £14.00
- * Oscilloscope Trolleys from £12.00
- * I.B.M. Video Display Units 4 col £48.00
- * 3AZP/2 C.R.T.s £18.00
- * Venner 5536 Counters £40.00
- * Autophon VHF Receivers 20/120mcs £140.00
- * Solartron CD 524 Oscilloscopes £90.00

HIGHEST QUALITY 19"
RACK MOUNTING CABINETS
& RACKS

FROM 5ft to 9ft HIGH

FROM £10 to £75

PLEASE SEND FOR STOCKLIST

Also Twin, Triple Consoles etc.

- * 100 amp Belling Lee Interference Filters £75.00
- * Marconi TF231 Distortion Meters £160.00
- * AVO VT Voltmeters CT-471A £75.00
- * Solartron Digital Voltmeters LM 1420/2 £120.00
- * Racal MA197 Pre-Selectors £65.00
- * Marconi TF-888 Receiver Testers £50.00
- * Collins 500 watt 2/18 mcs. Transmitters £1000.00
- * Collins KWT6 SSB 500w Transceivers £1250.00
- * Collins KWT6 200 m/w AM Transceivers £750.00
- * STC Rx5/25 mcs Receivers Diversity £140.00
- * Rack Mounting Operator Tables £10.00
- * Gaumont Kales 564 Flutter Meters £75.00
- * Hewlett Packard 618B Sig. Gen. 3.8/7.2 GHz £120.00
- * Rohn 95ft masts lattice 12" sides P.U.R.
- * 30ft Lattice Masts, 14" sides £55.00
- * 15ft Lattice Mast sections, 12" sides £35.00
- * 120ft Lattice Masts, 15" sides P.U.R.
- * 75/90ft Sky Towers, self-supporting £475.00
- * Heavy Aerial Rotators P.U.R.
- * Racal SA 504 Voltage converters £25.00
- * Elliot Recording M/A Meters £75.00
- * 75ft Aluminium Lattice Masts, 20" sides £400.00
- * Plessey peak distortion meters £35.00
- * Polaroid Microwave power meters £55.00
- * Rhode & Schwarz SBR sig gen. 1.6/2.4 gmc £470.00
- * Large Aerial Turning Units P.U.R.
- * 45 feet Uniradio 4 Co-ax 50 ohms £2.00
- * Baluns Professional Exterior 600/75 ohms £6.00
- * Addo 5/8 Track Tape Punches £48.00
- * Quality Weather Vanes 8 contacts (unused) £25.00
- * Racal MA-176 15 B. Modulators (new) £45.00
- * Inside Cabinet Shelf Sliders £3.00
- * DG7/5 C.R.T.s £3.00
- * Tally 5/8 Track Tape Readers 60 cps £48.00
- * Tally 5/8 Track Tape Readers with Spooling £65.00
- * Cav-kell FU 4 Band Pass Filter Testers £60.00
- * Racal RA-83 SSB Adaptors, new £70.00
- * Racal RA-237 L-W Converters, new £70.00
- * Racal RA-298 L.S.B. Transistorised Converters (new) £120.00
- * 400 Channel Pulse Height Spectrum Analysers £600.00

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

PLEASE ADD CARRIAGE AND
V.A.T.

P. HARRIS
ORGANFORD - DORSET

BH16 6BR

BOURNEMOUTH (0202) 765051

(33)

SITUATIONS VACANT

SYSTEMS TEST ENGINEERS

£3,500-£4,000

Several interesting opportunities are available for Test Engineers, qualified to O.N.C./H.N.C., degree standard, or ex-military personnel, to join our Test Engineering Department which is currently located in North London but will be moving to new premises in East Anglia/East Midlands later this year. Therefore, we would be interested in receiving applications from candidates who are either currently seeking a new appointment, or who may be interested in changing their jobs later in the year.

Suitable applicants will have had 1-5 years' practical experience of testing, modifying and repairing electronic systems. A knowledge of analogue and digital electronics is required and an understanding of computers would be an advantage. Full training will be given.

These positions offer progressive salaries with regular reviews and good employment benefits.

Please telephone or write for an application form quoting reference G/1013, to: -

Linda Geers, Personnel Officer,
CROSFIELD ELECTRONICS LIMITED,
 766 HOLLOWAY ROAD,
 LONDON N19 3JG, ENGLAND
 Telephone: 01-272 7766.

A member of the De La Rue Group of Companies.



7295

ARTICLES FOR SALE

PRECISION POLYCARBONATE CAPACITORS
 All High Stability - extremely Low Leakage

440V A.C. RANGE			63V D.C. RANGE		
Value (µF)	Dimensions (mm)	Price each	Value (µF)	Tol.	
0.1	27 12.7	68p	0.01 &	E1.28	75p 50p
0.15	27 12.7	80p	0.22	E1.32	77p 51p
0.22	33 16	86p	0.33	E1.32	77p 51p
0.25	33 16	92p	0.47	E1.32	77p 51p
0.33	33 16	99p	0.68	E1.44	84p 56p
0.47	33 19	E1.10	1.0	E1.56	91p 60p
0.5	33 19	E1.16	1.5	E1.74	E1.16 67p
0.68	50.8 19	E1.25	2.2	E1.98	E1.32 75p
1.0	50.8 19	E1.37	3.3	E2.40	E1.60 99p
1.5	50.8 25.4	E1.64	4.7	E2.82	E1.88 E1.23
2.0	50.8 25.4	E1.95	6.8	E3.48	E3.32 E1.47
			10	E4.98	E3.32 E2.01
			15	E7.14	E4.76 E2.88
			22	E9.66	E6.44 E3.90

TANTALUM BEAD CAPACITORS—Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8 µF at 15V/25V or 35V, 10.0 µF at 16V/20V or 25V, 22.0 µF at 6V/10V or 16V, 33.0 µF at 6V or 10V, 47.0 µF at 3V or 6V, 100.0 µF at 3V. All at 12p* each, 10 for E1.10*, 30 for E3*, 100 for E9*.

TRANSISTORS I.C.'s

BC107/8/9	9p	*BC212/212L	12p	2K3955	50p
*BC114	12p	*BC213/213L	11p	OC71/2	12p
*BC147/_/9	10p	*BC214/214L	11p	*N6555 Timer	61p
*BC153	16p	*8E194/5	12p	*T41 Agm OR	32p
BC154/7/8/9	12p	BFY50/1/2	20p	ZM414	E1.15
*BC182/182L	11p	AF178	40p	SN76013ND	E1.50
BC183/183L	11p	AF239	38p	SN76023ND	E1.50
*BC184/184L	12p	*ZK3702/4	11p	T8A81DAS	E1.42*

POPULAR DIODES—IN914 6p, 8 for 45p, 18 for 90p, IN916 8p, 6 for 45p, 14 for 90p, 1S44 5p, 11 for 50p, 24 for E1.00, IN4148 5p, 6 for 27p, 12 for 48p, IN4001 5p, 002 6p, 003 6p, 004 7p, 005 7p, 006 8p, 007 8p.

LOW PRICE ZENER DIODES—400mW Tol. -5% at 5mA. 3V, 3V3, 3V6, 4V7, 5V1, 5V6, 6V2, 6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. All at 7p each, 5 for 33p, 10 for 65p, 50 for E3.12. SPECIAL OFFER: 100 Zeners (may be mixed) for E6.00.

RESISTORS—High stability, low noise carbon film 5% 1/4W at 40°C. C. 1/4W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. All at 1p* each, 8p* for 10 of any one value, 70p* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2Ω (730 resistors) E5*

SILICON PLASTIC RECTIFIERS—1.5 amp. wire-ended 0027: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p)

BRIDGE RECTIFIERS—2% amp. 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: All at 5p* each: 50, 100, 220, 470, 680 ohm; 1K, 2K, 4K, 7.5K, 10K, 15K, 22K, 47K, 47K, 100K, 220K, 580K, 1M, 2M, 5M.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with * which are 12%.

Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept P5)
 The Old School, Edinstown, Wern, Shropshire
 Tel: Whixall 464/465 (STD 094 872)
 [Proprs. Minicost Trading Ltd.]

CASSETTE HEADS. 4 track head: this head which is used in audio/visual equipment can also be fitted for the recording/replay of Quadrophonic material: 3-head system; fitting these 3 heads to existing cassette decks will allow off-tape monitoring during recording: Cassette mechanism; top loading, with stereo heads and piano-key controls: C90 cassette tapes available in small quantities at bulk prices. For data send large SEA, Box No. 7139. (7139)

PHOTO ETCH LIMITED

9 LOWER QUEEN STREET
 PENZANCE, CORNWALL
 TR18 4DF

Prototype or long run - we will supply your printed circuit requirements. Also facilities for Design, Assembly and Test

Prompt and efficient service assured

CONTACT: David Webster
 PENZANCE (0738) 4478

56

ARTICLES FOR SALE

SOWTER TRANSFORMERS

FOR SOUND RECORDING AND REPRODUCING EQUIPMENT


We are suppliers to many well-known companies, studios and broadcasting authorities and were established in 1941. Early deliveries. Competitive prices. Large or small quantities. Let us quote. SOWTER TYPE 3678

A recent release
MULTITAP MICROPHONE TRANSFORMER
 Primary windings for 600 ohm, 200 ohm and 60 ohm with Secondary loadings from 2K ohm to 10 K ohm. Frequency response plus/minus 1/2dB 20 Hz to 25 KHz. Contained in well finished Mumental box 33mm diameter by 22mm high, with colour coded and leads. low distortion DELIVERY (small quantities) EX-STOCK. HIGHLY COMPETITIVE PRICE. FULL DETAILS ON REQUEST.

E. A. SOWTER LTD.
 Transformer Manufacturers and Designers
 7 Dedham Place, Fore Street
 Ipswich IP4 1JP. Tel. 0473 52794 7269

QUARTZ CRYSTAL UNITS from

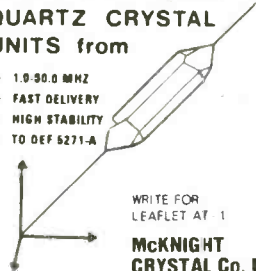- 1.0-30.0 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 5271-A



WRITE FOR LEAFLET AT 1

McKNIGHT CRYSTAL Co. Ltd.

HARDLEY INDUSTRIAL ESTATE, HYTHE, SOUTHAMPTON SO4 6ZY

TEL HYTHE 848961
 STD CODE 0703

(6044)

SILICON SOLAR CELLS and modules can provide a useful alternative to transformer power supplies. Adequate energy for low power instruments and entertainment equipment can be obtained from nickel-cadmium batteries charge - maintained by silicon cells. We have in stock two types of cell: - 35mW, 5V - £5.95, 250mW, 5V - £9.55. Prices include VAT and postage. Data is supplied free with the units or separately at 20p. Booklet 'Solar Cells' 75p - Edencombe Ltd, 16 Princes Avenue, Kingsbury, London NW9. (7271)

WE INVITE ENQUIRIES from anywhere in the world. We have in stock several million carbon resistors (th 1, 1/2, and 1 watt, 1/2 million wire wound resistors 5 and 10 watt - 1 million capacitors - 1 million electrolytic condensers - 1/2 million transistors and diodes, thousands of potentiometers, and hosts of other components. Write phone or call at our warehouse - Broadfields and Mayco Disposals Ltd, 21 Lodge Lane, North Finchley, London, N.12. 01-445 0749, 445 2713. (5907)

18 watts of power at 240 v straight to the bit

MINIATURE SOLDERING IRON

Probably the smallest 18 watt soldering iron to comply with Consumer Protection Regulations BS No. 3456 2.14. New method of bit-securing (pat. pend.) Built-in suspension hook. All parts very easily replaced. Insulation tested at 1500 v. ac at max. temp.

S&R BREWSTER
 86-88 UNION ST., PLYMOUTH
 Telephone 0752-65011
 Manufacturers and Distributors

7292


VALVES RADIO - T.V.-Industrial-Transmitting. We dispatch valves to all parts of the world by return of post, air or sea mail, 2,700 types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00. Closed Wednesday 1.00. We wish to purchase all types of new and boxed valves. Cox Radio (Sussex) Ltd, Dept WW, The Parade, East Wittering, Sussex PO20 SBN, West Wittering 2023 (STD Code 024366). (5392)

T.V. TUBE REBUILDING - FAIRCREST ENGINEERING LTD. offer a comprehensive range of equipment for processing all types of picture tubes. Standard or custom built units for established or new businesses. Full training courses. Individually tailored & backed by 27 years' experience in tube making. FAIRCREST ENGINEERING LTD. Willis Road, Croydon CR0 2XX. Tel: 01 689 8741. (7305)

SITUATIONS VACANT

Marconi Instruments

ELECTRONIC TECHNICIANS

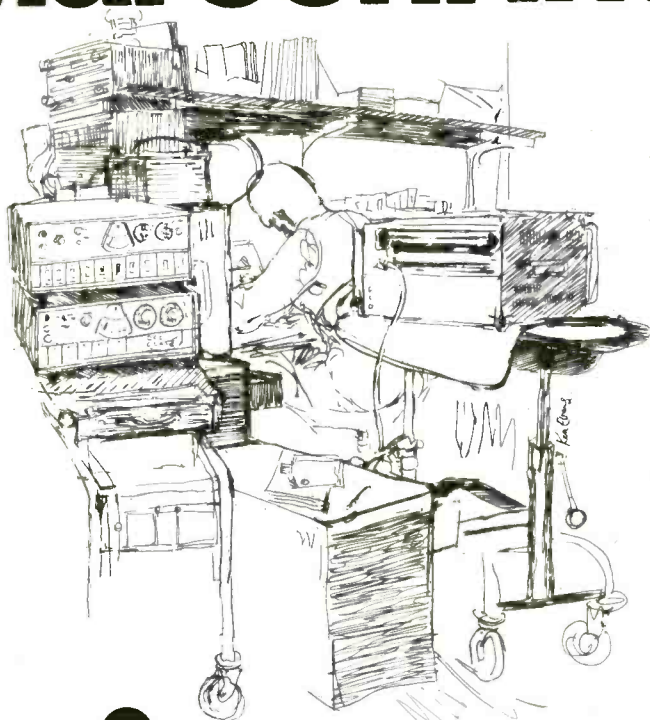

Opportunities for the experienced and sometimes inexperienced in St. Albans and Luton. Work situations range from fault finding on PCB's and components, to batch product testing of equipment that utilise very advanced techniques including microprocessors and the repair/calibration of all manner and types of test instruments.

Attractive salaries and, where appropriate, relocation are offered for the right candidates. Further information may be obtained in confidence from John Proddger

Marconi Instruments Limited,
Longacres, St. Albans, Herts. tel St. Albans, 59292



A GEC-MARCONI ELECTRONICS COMPANY

7236

mi

ARTICLES FOR SALE

ENAMELLED COPPER WIRE

s.w.g.	1 lb reel	1/2 lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All the above prices are inclusive of postage and packing in UK

COPPER SUPPLIES

102 Parrawood Road, Withington, Manchester 20
Telephone 061-445 8753 (100)

TELEPHONE ANSWERING Machines for Sale. New £120. Answers and Records. Plus 2-way Conversations and Dictation. Free Accessories and guaranteed 1 year. Callsaver. — C.R.V. Electronics Ltd. 01-249 0416, 01-580 1800. 30 Goodge Street, London W1. (7096)

60KHz MSF Rugby Receiver. BCD TIME OF DAY OUTPUT. High performance, phase locked loop radio receiver. 5V operation with 1 second LED indication. Kit complete with tuned ferrite rod aerial £14.08 (including postage and VAT). Assembled circuit and cased-up version also available. Send for details Toolex, Sherborne (4359), Dorset. (21)

300,000 MULLARD C280 & C281 for sale, values from 01uf to above 1uf 250/400 v/w, price per mixed pack, 100/£1.50, 500/£6.00. P&P (export 50p). Electronic Mailorder Ltd, Ramsbottom, Bury, Lancs. (7172)

FOR DISPOSAL AT CLEARANCE PRICES. Up to 15 miles of 10-way cable. Overall diameter 8 millimetres approx. SAE for sample. Eddystone receiver 500-1000 MHz. £50 + VAT, as seen. Jennings vacuum capacitors. Variable 8 to 35mm fd nominal 35.K.V. £6 + VAT ea. including p&p. Fixed 25mm fd 30 K.V. £4 + VAT ea. Some larger ones for callers only. G.W.M. RADIO LTD, 40/42 Portland Road, Worthing, Sussex. Tel. 34897. (7313)

FOR SALE

10.7 MHz CRYSTAL FILTERS.
ITT024DE/923L 12 1/2 KHz channel spacing. £6.00 ea.
ITT024DC 12 1/2 KHz channel spacing. £6.00 each. STC455/LQU/901A 50 KHz channel spacing. £2.50, all new and unused.
Plastic semi-airspaced trimmers 10mm dia. 2-25pf. £5.00 per 100. £33.00 per 1,000.
ITT Miniature Nixie Tubes type 5853S 170v 1/2" characters with left and right hand decimal points. 10 for £4.75; £32.00 per 100. £250.00 per 1,000.
ITT GN9A std size nixie tubes, no decimal point, same price as above.
1" VIDICON SCAN COILS transistor type to suit std 1" vidicon tube, with picture centring magnets and tube clamp no gen., new, £6.25
1/4 WATT CARBON FILM RESISTORS pre-formed vertical mounting. We have a large quantity of these at £3.50 per 1,000. Send for list or phone for values in stock (only supplied in 1,000 of one type).
EIRE 1000pf 500v disc ceramic capacitors. 7mm dia., £11.00 per 1,000.
ALL ITEMS ex-stock prices include VAT & POST; manufacturing quantities available on most items. — A.J.H. ELECTRONICS, 59 Waverley Road, Rugby, Warks. Phone 76473 (0788). Callers by appointment only.

10.7MHz WOBBLATOR KIT: 111mm x 57mm p.c.b.; R's; C's; i.c.; transistors; pots; skts. You supply case, battery, etc. Features sawtooth generator. Can be altered to other (lower) frequencies. £12.96 inc. VAT (8 per cent rate) and post and packing. Dovedale Electronics Limited, Post Office Box 47, Derby, DE1 2BE, Derby (0332) 40717. (7282)

LINSLEY-HOOD AMPLIFIERS constructed and repaired. Brand new, guaranteed, spares by return. BDY 56 £1.85. BD529 55p. BD530 55p. 2N5457 35p. 2N5459 45p. BF258 35p. BFR39 25p. BFR79 25p. Interference suppression kit, with instructions £1.35. Inclusive prices. P&P 15p. SAE for list. I. G. Bowman (Dept WW), 59 Fowey Avenue, Torquay, S. Devon. (7287)

ELECTRONIC INSTRUMENTATION. If you are interested in the buying or selling of good quality used Electronic Test Instruments, ring Reading 51074, Martin Associates and converse with our Sheila Hatch who will deal promptly with your enquiry. (6578)

ANTIQUE COLLECTOR'S ITEM, 30 years old, HMV IS INS television tube. Offers to McBain, 52 Hawne Lane, Halesowen, West Midlands. Tel. 021 550 2827. (7312)

SEMICONDUCTORS International Dictionary in seven languages English - French - German - Italian, Portuguese-Russian-Spanish. 2 volumes, originally published in 1971 at £15, now offered at £3 post free by Weatherhead's Bookshop, 58 Kingsbury, Aylesbury, Bucks. Tel. 0296 23153. (7330)

TEKTRONIX 4 1/2 DMM DM501, universal counter DC503, function generator FG501, dual power supply PS503, dual trace scope, portable 326 vgc £550 ono. — Tel. Welwyn Garden City 32271. (7331)

PROFESSIONAL TV TUBE REBUILDING PLANT designed and manufactured with 20 years' experience of tube rebuilding. Also all associated supplies including Electron guns. Regular training courses. Western-Whybrow Engineering, WECO Works, Penzance, TR20 9QT (073676) 2265. (6542)

BURGLAR ALARM EQUIPMENT — Safes — Trade supplies — Astro alarms. — 25 Stockton Road, Sunderland, Tyne & Wear. Tel. 77825. Free lists. SAE. (7274)

WIRELESS WORLD NOVEMBER 1939 TO SEPTEMBER 1947 COMPLETE. Offers. — Hayes, 159 Beechwood Drive, Glasgow, G11 7DX. Telephone 041-334 4369. (7275)

THE TTL DATA BOOK FOR DESIGN ENGINEERS

By Texas Instruments

PRICE: £5.50

RADIO, TV & AUDIO TECHNICAL REFERENCE BOOK by S. W. Amos. Price £24.70.
MICROPROCESSOR / MICROPROGRAMMING HANDBOOK by B. Ward. Price £4.00.

WORLD RADIO TV HANDBOOK. J. M. Frost. Price £5.50.

BUILD YOUR OWN WORKING ROBOT by D. L. Heiserman. Price £3.70.

THE RADIO AMATEUR'S HANDBOOK 1977 by A.R.R.L. Price £6.60.

THE MEMORY & MICROPROCESSOR DATA BOOK FOR DESIGN ENGINEERS by Texas. Price £3.40.

TOWERS' INTERNATIONAL TRANSISTOR SELECTOR by T. D. Towers 1977. Price £5.00.

SOUND RECORDING PRACTICE by Borowick, J. Price £16.60.

* Prices include postage *

THE MODERN BOOK CO.
SPECIALISTS IN SCIENTIFIC & TECHNICAL BOOKS
19-21 PRAED STREET
LONDON W2 1NP
Phone 723 4185
Closed Sat. 1 p.m.

ARTICLES FOR SALE

COLOUR, UHF AND TV SPARES NEW COMBINED COLOUR BAR GENERATOR PLUS CROSS HATCH KIT (MK4) UHF Aerial input type. Also gives R-Y, B-Y, Luminance combinations, Grey scale etc. Push button controls, Battery operated, £35, Case £1.80, battery holders 78p, p/p 85p.

CROSS HATCH KIT, UHF aerial input type, also gives peak white and black levels, battery operated, £11, p/p 45p. Add-on Grey Scale kit £2.90 p/p 30p. Add-on Colour Bar kit (Mk3) £25, cases £1.40, p/p 85p.

CEEFAX parts shortly available, details on request
 "Wireless World" TV Tuner and FM Tuner Projects by D. C. Read. Kits of parts available. CRT Reactivator kit for colour and mono, £18*, pp £1. Signal Strength Meter kit £18*, p/p 85p. 625 TV IF Unit, for Hi-Fi amps or tape recording £6.80 p/p 65p. Decca Colour TV Thyristor Power Supply Unit, incl. H.T., L.T., etc. Incl. circuits £3.80 p/p 95p. Bush CTV 25 Power Supply Unit incl. H.T., L.T., etc. £3.20 p/p £1.20. Bush CTV 25 Convergence panel plus yoke, blue lateral £3.60 p/p 80p. Philips single stand convergence units complete, incl. 16 controls, £3.75 p/p 75p. Colour Scan Coils, Mullard or Plessey £6 p/p 90p. Mullard AT1023/05 Convergence Yoke £2.50 p/p 75p. Mullard or Plessey Blue Laterals 75p p/p 30p. BRC 3000 type scan coils £2 p/p 80p. Bush CTV 25 Scan Coils £2.50 p/p 80p. Delay Lines: DL20 £3.50. DL40 £1.50. DL1E, DL1 85p p/p 40p. Lum. delay lines 50p p/p 30p. Bush/Murphy CTV 25 3/174 EHT quadrupler £8.50 p/p 85p. G8 Tripler £6, BRC 3000 £6.60 pp 75p others available. Philips G8 Panels, part complete, surplus/salvaged: Decoder £2.50. T. Base £1 p/p 70p. CRT Base 75p p/p 30p. GEC 2040 Decoder panel for spares £3.50 p/p 70p. VARICAP TUNERS: UHF: ELC 1043 £4.20, ELC 1043/05 £5, VHF: ELC 1042 £4.90, Philips VHF £3.80. Salvaged UHF & VHF Varicaps £1.50 p/p 35p. SPECIAL OFFER: RBM 6 psn. Varicap control unit £1 p/p 35p. UHF Tuners transd. incl. slow motion drive £3.80. 4 Psn. and 6 Psn. push button ransd. £4.20 p/p 85p. Helical pots 100K, 4 for £1.20, p/p 20p. Thorn 850 dual stand time base panels 50p. Philips 625 IF panel incl. cct. 50p, p/p 75p. VHF Turret tuners AT 7650 for KB Featherlight Philips 19TG170. GEC 2010, etc. £2.50. Fireball tuners. Ferguson, HMV, Marconi 80p p/p all tuners 75p. Mullard Mono scan coils for Philips, Stella, Pye, Ekco. Ferranti, Invicta £2 p/p 75p. Large selection LOPTS FOPTS available for most popular makes MANOR SUPPLIES, 172 West End Lane, London, N.W.6. Shop premises. Callers welcome. Thousands of additional items available not normally advertised. (Nos. 28, 159 buses or West Hampstead Bakerloo Line and British Rail). Mail Order: 64 Golders Manor Drive, London, N.W.11. Tel.: 01-794 8751. V.A.T. Please ADD 24% TO ALL PRICES (EXCEPT WHERE MARKED * V.A.T. 8%). (60)

BOOKS

TV REPAIRS SIMPLIFIED. Full repair instructions any British TV for £4.50. Circuit Diagram on request; details unique books, e.g. Every mono British TV circ. diag./layout £9.50. Also colour. Aus + WW, 76 Church Street, Larkhall, Lanarks. 7217

"VINTAGE CRYSTAL SETS, 1922-1927". Just published by Wireless World, contains 128 pages. Chapters on the first days of broadcasting. The Crystal Set, Vintage Wireless Trademarks. Also catalogue sections listing and describing crystal sets together with their original prices in £:s:d. A book for the collector or those interested in nostalgia. Available from main bookshops or direct from us. Please send £2.80 inclusive to IPC Business Press Ltd., Room 11, Dorset don W1.

ARTICLES WANTED

★ **MINICOMPUTERS**
 ★ **PERIPHERALS**
 ★ **INSTRUMENTATION**

For fastest, best CASH offer, phone

COMPUTER APPRECIATION
 Godstone (088 384) 3221

Wanted: Test Equipment, RF power transistors, and components of VHF/UHF type. Immediate cash available

Wanted: Philips E10-12 scope tube. Modular Electronics 95 High Street, Selsey Chichester, Sussex PO20 0QL Tel. 024-361 2916 7321

★ **MINICOMPUTERS**
 ★ **PERIPHERALS**
 ★ **INSTRUMENTATION**

For fastest, best CASH offer, phone:

CHILTMEAD LTD.
 Reading (0734) 586419

WANTED, all types of communication receivers and test equipment. Details to R. T. & I. Electronics Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (63)

SURPLUS COMPONENTS Equipment and Computer panels wanted for cash. Ring Southampton 772501. (16)

WE BUY new valves, transistors and clean new components, large or small quantities, all details, quotations by return. — Walton's, 55 Worcester St., Wolverhampton. (62)

BUSINESS OPPORTUNITIES

FINANCE FOR ELECTRONICS

£10 - £100,000 available to young Engineers with bright ideas for a business venture.

Write in confidence to
 Box No. WW7270

CONTRACTOR/INSTRUMENT Maker required to produce 1,000 unipivot Pick-up arms monthly. Box No. (7198)

PLANT FOR SALE

HEATSKIL INFRARED CONVEYOR OVEN SM114 380/415 volts 3PH Netral Secomak soft air blower SM S1131. Gas-fired Barlow Whitney stoving oven type G.D. 300/763 VAF Kresslink silk screen printing machine, type G2, FABR 2042. Gyrex roller coater model 530c — SN 10163. — Teleng Ltd., Arisdale Ave., South Oclenden, Essex. (7280)

ARTICLES FOR SALE

RECHARGEABLE BATTERIES. 'AA' pence (HP7) £1.26; Sub 'C' £1.29; 'C' (HP11) £2.38; 'D' (HP2) £2.92; PP3 £4.98. Matching chargers £5.91 each except PP3 charger £4.99. Charging holders for 2, 3, 4, 5 or 6 pence cells 35p; 'C' & 'D' size holders, 4 cell only 50p. Prices include VAT. Add 10% post, package and insurance orders under £20. 5% over £20. SAE for full details plus 50p for 'Nickel Cadmium Power' booklet. Mail orders to SANDWELL PLANT LTD., 1 Denholm Road, Sutton Coldfield, West Midlands. Tel. 021 354 9764 Callers to T.L.C., 32 Craven Street, Charing Cross, London, W.C.2. (7306)

WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC.

SPOT CASH

CHILTMEAD LTD.

7, 9, 11 Arthur Road Reading, Berks. Tel. (0734) 582 605

WANTED: TEST AND COMMUNICATION EQUIPMENT



single items or quantities, also RF plugs, sockets and connectors.

Call or phone.

170 Goldhawj Road, London, W.12 01-743 0899 (7006)

WILL BUY ANYTHING, any quantity if price is right ring Stan Willetts, West Bromwich, 021 553 0186. (6815)

5pf APROX SINGLE TURN TRIMMERS, large stock required. Electronic Mailorder Limited, Ramsbottom, Bury, Lancs. Tel. (070 682) 3036. (7279)

WANTED OSCILLOSCOPES TEST EQUIPMENT, cheap electronic kits, Hobby Computers Eng. E. Acticles S-42431 Angered/Sweden Skolpacet 31. (7276)

ALL SURPLUS or used equipment wanted. Radio telephones — complete systems purchased. Ships equipment and small boat radio's — components, partly assembled chassis etc. etc. Established 20 years. For prompt attention contact Mr Grout at Worthing 34897. GWM Radio Limited 40/42 Portland Road, Worthing, Sussex. (7307)

SERVICE

EURO CIRCUITS

Printed Circuit Boards — Master layouts — Photography — Legend printing — Roller tinning — Gold plating — Flexible films — Conventional fibre glass — No order too large or too small — Fast turnaround on prototypes. All or part service available NOW

EURO CIRCUITS TD.

Highfield House West Kingsdown Nr. Sevenoaks, Kent. WK2344

LABELS, NAMEPLATES, FASCIAE on aluminium or plastic. Speedy delivery G.S.M. Graphic Arts Ltd., 1-5 Rectory Lane, Guisborough (02873-4443), Yorks, U.K. (13)

AGENTS WANTED

TECHNICAL BREAKTHROUGH in sound radiation by small English Company has resulted in an increasing range of unique prestige products for Hi Fi Studio and Sound Reinforcement applications. We are now seeking home and overseas agents to handle these on an exclusive basis - E. J. Jordan Ltd., 'Stoneyway' Bovingdon Green, Marlow, Bucks. England SL7 2JH. (7329)

FOR

CLASSIFIED ADVERTISING RING
EDDIE FARRELL
 ON
01-261 8508

EQUIPMENT WANTED

BROADFIELDS AND MAYCO DISPOSALS

21 Lodge Lane, N. Finchley London, N12 8JG Telephone: 01-445 2713

01-445 0749

01-958 7624

WE ARE INTERESTED IN PURCHASING ALL KINDS OF RADIO, T.V. AND ELECTRONIC COMPONENTS AND EQUIPMENT IN BULK QUANTITIES. WE PAY PROMPT CASH AND CLEAR MATERIAL BY RETURN. (46)

CAPACITY AVAILABLE

ELECTRONIC ASSEMBLY AND WIRING CAPACITY AVAILABLE

M.O.D. approved

J.N. Electronic Supplies
 Osiers Road, London, SW18 Tel. 01-874 6162 (7284)

SMALL BATCH PRODUCTION wiring, assembly to sample or drawings. Specialists in printed circuit assembly. Rock Electronics, 41 Silver Street, Stansted, Essex. Tel. Stansted (0279) 33018/814006. (19)

AIRTRONICS LTD. for coil winding Large or small production runs. Bobbin — Layer — Wave — Bifilar — Miniature Toroids, Airtronics Limited, Gardner Industrial Estate, Kent House Lane, Beckenham, Kent BR3 1UG. Tel. 01-659 1147. (7158)

PRINTED CIRCUITS Ultra fast turnaround, very competitive prices. Also Prototype, Artwork, Photography. Tel. Redhill 68850. (7283)

PRINTED CIRCUITS. Ultra fast turnaround. Very competitive prices paper or glass. Punched or drilled. Single or double sided. Also prototypes, artwork, photography. Phone Redhill 68850. (7304)

PRINTED CIRCUIT BOARDS — Quick deliveries, competitive prices, quotations on request, roller tinnings, drilling, etc. speciality small batches, larger quantities available. Jamieson Automatics Ltd 1-5 Westgate, Bridlington, N. Humberside, for the attention of Mr. J. Harrison. Tel. (0262) 74738/77877. (18)

PRINTED CIRCUIT ASSEMBLY to sample/drawings. Fast professional work at lowest prices. Glenronics (Chesham), 34 Glenister Road, Chesham, Bucks. Tel. 6005. (7308)

COURSES

RADIO and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ. (25)

RECEIVERS AND AMPLIFIERS

HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc. in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11. Ley 4986. (65)

SIGNAL Generators, Oscilloscopes, Output Meters, Wave Voltmeters, Frequency Meters, Multi-range Meters, etc., etc. in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (64)

I.C.E. MULTIMETERS

TWICE the information in **HALF** the size

The I.C.E. range of multimeters provides an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.

All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc., and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write of phone for list, or for details of direct mail-order service.

Supertester 680R (illustrated)


20k Ω /V, \pm 1% fsd on d.c.
4k Ω /V, \pm 2% fsd on a.c.
80 Ranges — 10 Functions
140 x 105 x 55mm
£25.25 + VAT
(For Mail Order add 80p P&P)

Supertester 680G

20k Ω /V, \pm 2% fsd on d.c.
4k Ω /V, \pm 2% fsd on a.c.
48 Ranges — 10 Functions
109 x 113 x 37mm
£19.95 + VAT
(For Mail Order add 80p P&P)

Microtest 80

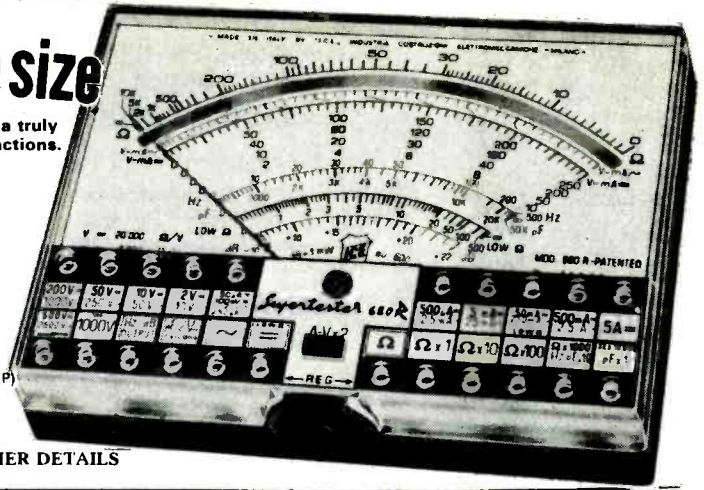20k Ω /V, \pm 2% fsd on d.c.
4k Ω /V, \pm 2% fsd on a.c.
40 Ranges — 8 Functions
Complete with case — only 93 x 95 x 23mm
£14.95 + VAT
(For Mail Order add 80p P&P)



Electronic Brokers Ltd.
49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781

WW-090 FOR FURTHER DETAILS

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 122-135

	PAGE		PAGE		PAGE
Acoustical Mfg. Co. Ltd.	5	Gardners Transformers	6	Q. Max Electronics Ltd.	18
AEL Crystals Ltd.	28	G.R. Electronics	120	Radio Components Specialists	101
Amateur Components	100	Greenwood Electronics Ltd.	13	Ralfe, P. F.	90
Ambit International	31	Hall Electric	69	Ramp Electronics	111
Antex	87	Hampton Video Systems Ltd.	29	R.C.S. Electronics	18
Aspen Electronics Ltd.	29	Harmsworth Townley & Co. Ltd.	18	R.S.T. Valves Ltd.	96
Astra-Pak	96	Harris Electronics (London) Ltd.	12, 16	RTVC	91
Audix Ltd.	112	Harris, P.	132	Sabtronic (U.K.) Ltd.	23
Avo Ltd.	6, 26, 77	Hart Electronics	121	Samsons (Electronics) Ltd.	116
Barr & Stroud Ltd.	14	Heyco Co. Ltd.	30	Scopex Instruments Ltd.	112
Barrie Electronics Ltd.	105	Hi-Fidelity Designs	93	Semicon Indexes Ltd.	32
Bentley Acoustic Corp. Ltd.	114	Icon Designs	21	Service Trading Co.	97
Beyer Dynamics (G.B.) Ltd.	8	ILP Electronics Ltd.	33	Servo & Electronic Sales Ltd.	103
Bi-Pak Semiconductors Ltd.	94, 95	IMO Precision Controls Ltd.	17	Shure Electronics Ltd.	11, 13, 15
Billboard Publications	102	Industrial Tape Applications	102	Sinclair Instruments Ltd.	78
Boss Industrial Mouldings Ltd.	11	Integrex Ltd.	106, 107	Sintel	104
Bradley G. & E. Ltd.	cover iii	Interface Quartz Devices Ltd.	31	SME Ltd.	70
Bull, J.	115	IIT Instrument Services	34	Sonic Sound Audio	116
Butterworth	loose insert	Leeson Instruments Ltd.	16	Sowter, E. A.	133
Cambridge Learning	10	Leeds Exhibition	31	Special Products Ltd.	12
Catronics	104	Leavers-Rich Equipment Ltd.	24	Storno Ltd.	27
CEC Corporation	24	Levell Electronics Ltd.	3	Strumech Engineering Ltd.	10
Chiltmead Ltd.	113	Light Soldering Developments Ltd.	11	Suggden, J. E. & Co. Ltd.	22
Circuit Designs	89	Lion House	120	Sullivan, H. W. Ltd.	12, 20
Cliffpalm Ltd.	30	London Instrument Repairs	31	Surrey Electronics Ltd.	109
Colomar (Electronics) Ltd.	103	Lynx (Electronics) London Ltd.	108	Swanley Electronics Ltd.	90
Commercial T/Travel	110	McKnight Crystals	133	Swift of Wilmslow	92
Compoc Electronics	105	MacInnes Laboratories Ltd.	8	Technomatic Ltd.	111
Crimson Elektrik	28	Maplin Electronic Supplies	9	Teleprinter Equipment Ltd.	32
Crofton Electronics Ltd.	22	Marconi Instruments Ltd.	Cover ii	Teleradio Hi Fi	109
Circuit Services	116	Marshall, A. & Sons (London) Ltd.	88	Tempus	92
Dema Electronics International	109	Maughan, Thos. & Assoc. Ltd.	105	Trampus Electronics	90
Doram Electronics	27, 105	MCP Electronics	15	Trident Audio Developments Ltd.	22
Dow Corning	4	Modern Book, The	134	Valradio Ltd.	27
Eagle International	24	Multicore Solders Ltd.	Cover iv	Vintage Crystal Sets	108
ECS (RCA)	7	Nombrex (1969) Ltd.	26	West Hyde Developments Ltd.	92
Eddystone Radio Ltd.	19	OMB Electronics	27	West London Supplies	111
Electronic Brokers Ltd.	114, 117, 118, 119, 136	Patrick, J. B.	121	Whiteley Electrical Radio Co. Ltd.	16
Electronics Weekly	26	PBRA Ltd.	109	Wilmot Breeden Electronics Ltd.	2
Electro-Tech Components Ltd.	117	Phonosonics	28	Wilmslow Audio	32
E.S.P.	30	Powertran Electronics	98, 99	Z. & I. Aero Services Ltd.	20, 26, 100
Fairchild Semiconductor Ltd.	28	Precision Petite Ltd.	30	Zettler (UK) Division	29
Farnell Instruments Ltd.	Readers Card				
Fluke International Corp.	25				
Future Film Developments	22				
Fylde Electronic Labs. Ltd.	29				

OVERSEAS ADVERTISEMENT AGENTS:

France: M. D. Soubeyran, Compagnie Francaise D Editions, Division Internationale, 40 Rue du Colisee, Paris 8e Telephone: 225-77-50 — Telex: 280274

Hungary: Mrs. Edit Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget Telephone: 225 008 — Telex: Budapest 22-4525 INTFOIRE

Italy: Sig. C. Epis, Etas-Kompass, S.p.a. — Servizio Estero, Via Mantegna 6, 20154 Milan Telephone: 347051 — Telex: 37342 Kompass


Japan: Mr. Inatsuki, Trade Media — IBPA (Japan), B212 Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106 Telephone: (03) 585-0581

United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 — Telephone: (212) 689 5961 — Telex: 421710 Mr. Jack Farley Jr., The Farley Co., Suite 1584, 35 East Wacker Drive, Chicago, Illinois 60601 — Telephone: (312) 63074 Mr. Richard Sands, Scott, Marshall, Sands & Latta Inc, 5th Floor, 85 Post Street, San Francisco, California 94104 — Telephone: (415) 421 7950 — Telegrams: Dascotcco, San Francisco Mr. William Marshall, Scott, Marshall, Sands & Latta Inc, 1830 West Eighth Street, Los Angeles, California 90057 — Telephone: (213) 382 6346 — Telegrams: Dascotcco, Los Angeles

Mr. Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 — Telephone: (216) 621 1919 Mr. Ray Rickles, Ray Rickles & Co., P.O. Box 2008, Miami Beach, Florida 33140 — Telephone: (305) 532 7301 Mr. Jim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305 Telephone: (404) 237 7432 Mike Loughlin, IPC Business Press, 15055 Memorial, Ste 119, Houston, Texas 77079 — Telephone: (713) 783 8673

Canada: Mr. Colin H. MacCulloch, International Advertising Consultants Ltd, 915 Carlton Tower, 2 Carlton Street, Toronto 2 — Telephone: (416) 364 2269

*Also subscription agents

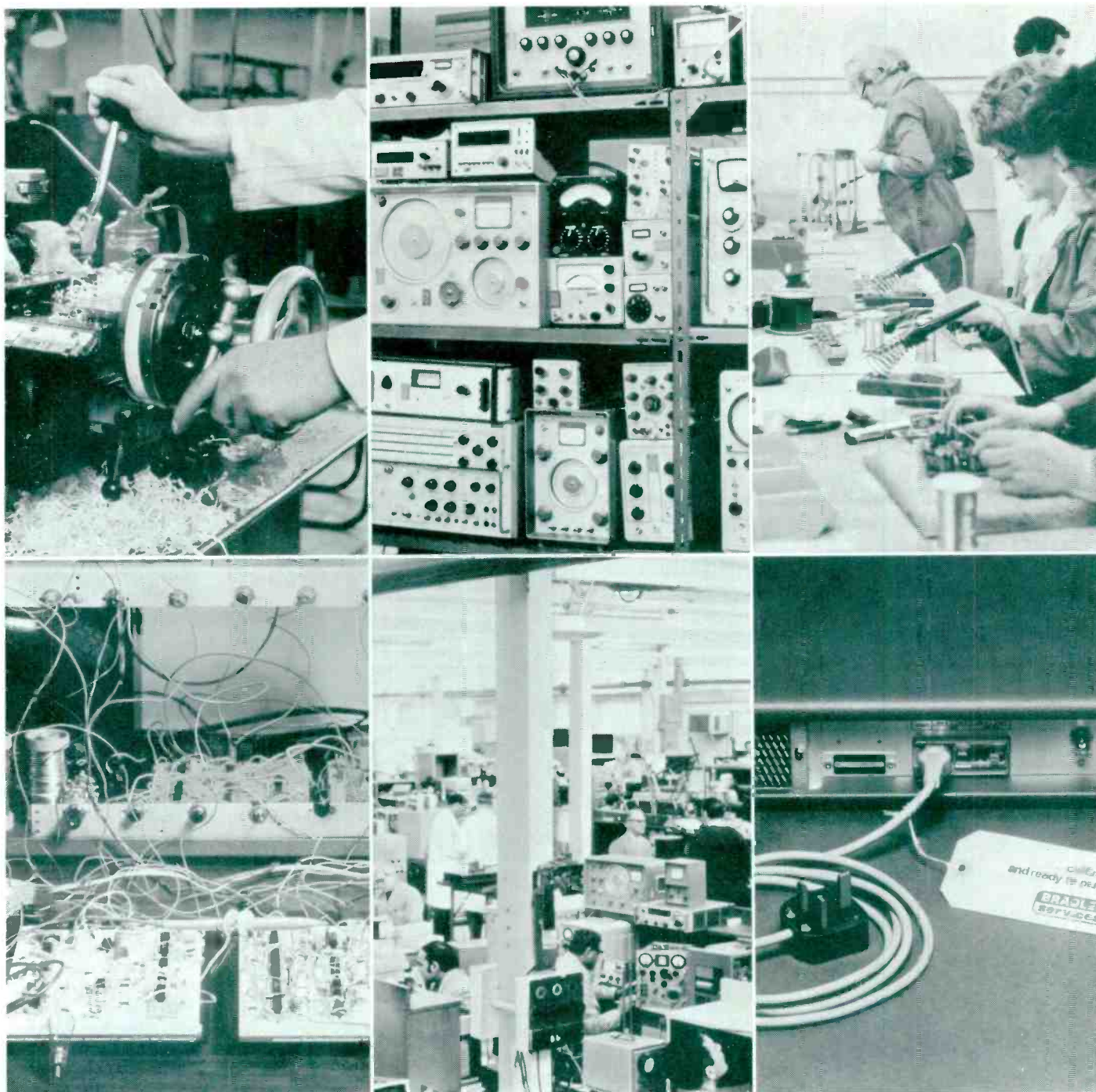

Even if we didn't make it, we'll make it work.

Bradley Services have the expertise and manufacturing capability necessary to make the most sophisticated electronic systems and electro-mechanical devices. However, equally important are the facilities we have for repair and calibration. We can handle virtually any type of instrument within the frequency range DC to 36 GHz – irrespective of manufacturer.

We also have a Post Design Services Group which provides every type of

after-sales engineering support, from the provision of technical literature to the upgrading of complete systems.

These facilities all approved to MOD Def. Stan. 05-21, have been developed over more than 20 years and during that time we've handled practically every type of instrument in use. So, if you've got a problem with some equipment, the chances are that, even if we didn't make it, we can still make it work.

Bradley Electronics

G & E Bradley Limited
Electral House, Neasden Lane
London NW10 1RR
Telephone: 01-450 7811
Telex: 25583



Even if tin prices stabilised, a change from 60/40 alloy to Savbit Solder could save you £100/tonne, ensure a better job...


The reason is that Multicore Savbit not only solves the problem of fine copper wires and thin foils deteriorating during soldering, but also contains less tin than 60/40 alloy. **We make both so we are just offering to alleviate your rising metals costs.**

During normal soldering, a dissolving action causes the wire to weaken and embrittle – often to break during subsequent field use.

Savbit, however, is a rosin based, 5-core wire solder comparable in joint quality to standard high performance alloys, but capable of dramatically inhibiting the copper dissolving action.

As this diagram shows*, compared with a 60/40 alloy, Savbit can reduce the dissolution of copper by as much as 100 times. Yet wetting rate, flow, conductivity and capillary force are almost identical – with creep strength and shear strength actually increased.

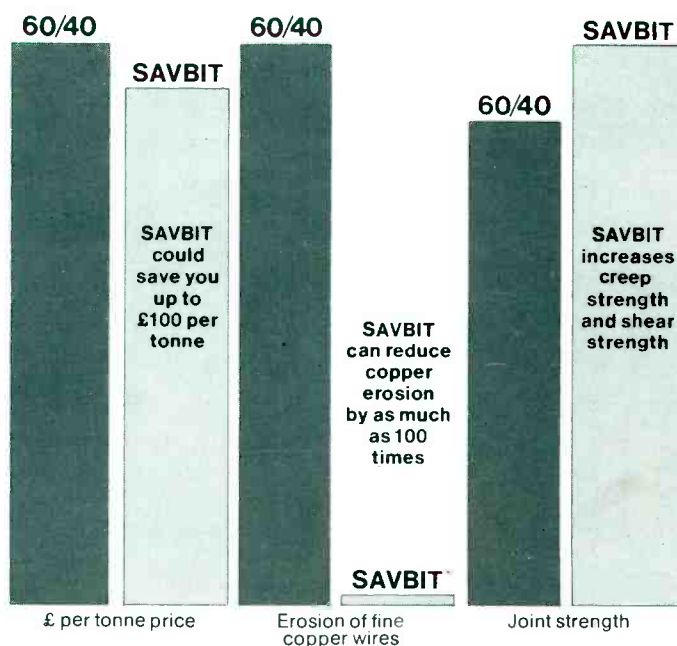*(Indicative of product advantages only; not to scale)




...and more



Cracked iron-plated bit, after 40,000 simulated operations using 60/40 Solder.

Some people think Savbit alloy is only usable with plain copper soldering iron bits, but this isn't true.

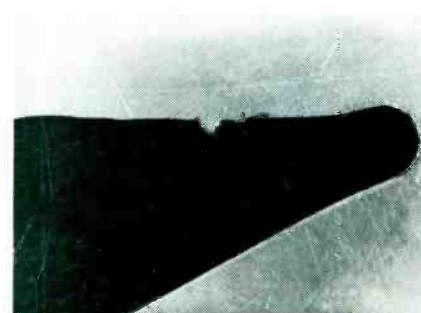As these photographs illustrate dramatically, Savbit also saves significantly on the cost of iron-plated soldering iron bits, which have a copper core. This is exposed through cracks in the plating.



Cracked iron-plated bit, after 40,000 simulated operations using SAVBIT Solder.

Add this advantage to the increased reliability and joint quality Savbit offers, and you'll understand why more and more 60/40 users are making the change – and profiting. The Ministry of Defence have given a special new Approval No. DTD 900/4535A for Savbit alloy with ERSIN 362 flux to be used in lieu of Solders to B.S. 219 and B.S. 441.

ERSIN
Multicore

For full information on Savbit or any other Multicore products, please write on your company's letterhead direct to:

Multicore Solders Limited,

Maylands Avenue, Hemel Hempstead, Herts. HP2 7EP
Telephone: Hemel Hempstead 3636. Telex: 82363